

wireless world

APRIL 1982 70p

Stage lighting system

**30W Dmosfet
audio amplifier**

**Receivers for
optical fibre
communication**

Australia A\$ 2.40
Belgium BFR. 74.00
Canada C\$ 3.25
Denmark DKR. 28.25
Germany DM. 6.50
Greece DRA. 160.00
Holland DFL. 8.00
Italy L 3100
Norway NKR. 24.00
Singapore M\$ 5.50
Spain PTS 240.00
Switzerland FR. 6.50
U.S.A. \$ 3.75

THROUGH-LINE POWER METER

leads by a head



For colour brochure contact:

FARNELL INSTRUMENTS LIMITED
WETHERBY LS22 4DH
TELEPHONE (0937) 61961
TELEX 557294 FARIST G

- Single detector head covers wide frequency and power band
- 25MHz to 1GHz ■ 20mW to 100W and VSWR from 1 to 3
- Head can be used 1.5m from meter (e.g. inside closed car boot)
- Fully portable – works from internal battery or vehicle battery
- Mains adaptor/charger and rechargeable battery available
- Manufactured, tested and inspected to Min. Def. Std. 0524.



wireless world


ELECTRONICS

TELEVISION

RADIO

AUDIO

APRIL 1982 Vol 88 No 1555

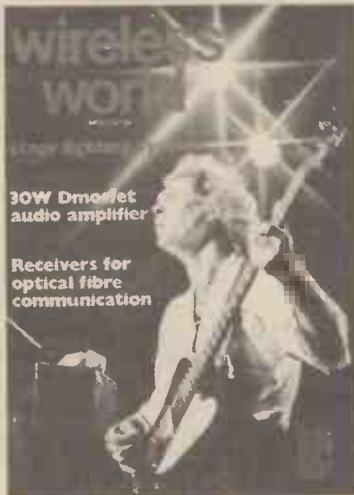

30W Dmefet
audio amplifier

Receivers for
optical fibre
communication

Front cover picture illustrates the article on microprocessor stage lighting systems, starting this month.

NEXT MONTH

Digital filters – a new series giving theory, design techniques and microprocessor implementation.

Program exchange by telephone – design of software systems for loading source-code programs into memory.

Orchestral sound, halls and timbre – or 'Why does it sound so beautiful?' Denis Vaughan examines the Kingsway Hall and puts forward a theory to account for its excellence.

Current issue price 70p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.6p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3500. Advertising 01-661 3130.

Telegrams/Telex: 892084 BISPRS G.

Subscription rates: 1 year £12 UK and £15 outside UK.

Student rates: 1 year £8 UK and £10 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3500.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA: \$39 surface mail, \$98.30 airmail.

US subscriptions from IPC B.P. Subscriptions Office, 205 E.42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1982 ISSN 0043 6062

35 ENGINEERING – OR DOMINOES?

36 MICROPROCESSOR – CONTROLLED LIGHTING SYSTEM

by J. D. H. White and N. M. Allinson

41 555-TYPE INTEGRATED CIRCUITS

by J. L. Linsley Hood

44 DIGITAL, MULTI-TRACK TAPE RECORDER

by A. J. Ewins

48 WORLD OF AMATEUR RADIO

49 EPROM PROGRAMMER

by H. S. Lynes

53 NEWS OF THE MONTH

56 SIMPLE POWER AMPLIFIER

by P. Wilson

59 LETTERS TO THE EDITOR

62 RECEIVERS FOR OPTICAL-FIBRE COMMUNICATION

by I. Garrett

66 HEATING-FUEL SAVER

by D. Ryder

68 CIRCUIT IDEAS

70 DESIGNING WITH MICROPROCESSORS

by D. Zissos and G. Stone

75 ELECTRONIC ORGAN WITH PIPE-ORGAN SOUND

by J. H. Asbery

77 DISC DRIVES

by J. R. Watkinson

81 16-CHANNEL DATA ACQUISITION

by P. Hickey

85 SYMMETRICAL-OUTPUT DIVIDERS

by G. Girolami and P. Bamberger

87 ASC11 KEYBOARD TESTER

by Waleed Habib Abdulla

89 NEW PRODUCTS

EP4000 EPROM EMULATOR PROGRAMMER

- ★ Programs 2704/2708/2716(3)/2508/2758 2516/2716/2532/2732
- ★ Emulates same devices with a single keypress
- ★ 300ns access time in emulation mode
- ★ Editing facilities — data entry, match, display, shift, move, clear, define, block program, etc.
- ★ Input/output as standard — RS232 (ASC11-hex), 20mA, printer, cassette & DMA
- ★ Video output for memory map display
- ★ Expandable with 2764 adaptor & Bipolar Prom modules
- ★ Fully buffered cold ZIF socket
- ★ Price £545 + VAT + £12 delivery




P4000 PRODUCTION PROGRAMMER

- ★ Program 1-8 devices simultaneously
- ★ Programs same devices as EP4000
- ★ No personality cards needed
- ★ Simple operation
- ★ Blank check & verify functions
- ★ Powered down master & copy sockets
- ★ Individual socket LED indicators
- ★ Mode indicators for blank check, program verify, and socket power down
- ★ Price £545 + VAT + £12 delivery



MODEL 14 EPROM ERASERS

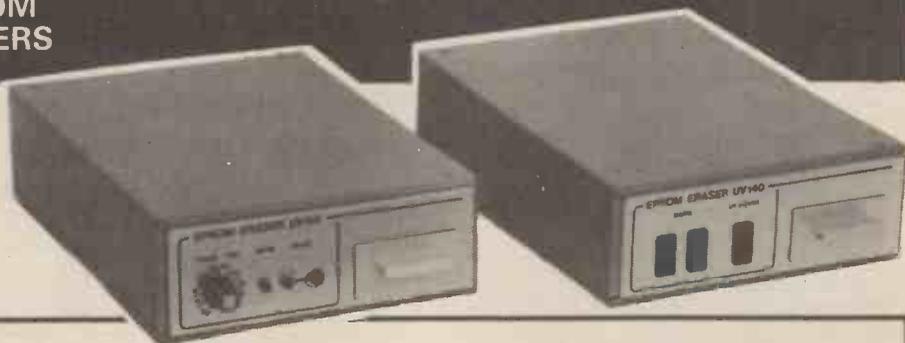- ★ 14 EPROM capacity
- ★ Safety interlocked
- ★ Convenient tray loading of devices
- ★ UV141 (with timer) £78 + VAT
- ★ UV140 £61.50 + VAT



To cope with increased demand

WE HAVE MOVED

GP Industrial Electronics Ltd.

Unit E, Huxley Close
Newnham Industrial Estate
Plymouth PL7 4JN

Tel: Plymouth (0752) 332961

Electronic Brokers

Second User Test Equipment.

Makes engineers smile without making accountants cry.

Electronic Brokers are Europe's leading Second User Equipment Company. We carry large stocks of the very latest test equipment which is refurbished in our own service laboratories and calibrated to meet the

manufacturer's sales specifications. When you buy used equipment from Electronic Brokers, it can be yours in just days. No waiting for manufacturers lengthy production schedules. All equipment is fully guaranteed.

ANALOGUE VOLTMETERS

AVO	
EA113 Electronic Multimeter	£115.00
Bruel and Kjaer	
2409 TRUE RMS Average and Peak 2Hz-200KHz	£250.00
Hewlett Packard	
3400A True RMS 1mV-300V 10Hz-10MHz	£600.00
Marconi	
TF2603 RF Millivoltmeter 300µV Sensitivity, 50KHz-1.5GHz	£255.00
TF2604 Electronic Voltmeter AC 20Hz-1.5GHz 300mV-1KV DC 10mV-1KV, 0.2µ-500mΩ	£350.00

ANALYSERS

Dymar	
1785 AM/FM Modulation meter 30-480MHz	£295.00
Hewlett Packard	
331A Distortion analysers, 5Hz-600KHz to 0.1% voltmeter 300µV-300 volts at 2%	£350.00
332A Distortion Meter 5Hz-600KHz	£495.00
333A Distortion Meter with Auto null	£675.00
8407A/8412A Network Analyser	£1950.00
8555A Plug in, 10MHz-18GHz	£5000.00
Racal	
9009 Automatic AM/FM modulation meter 30-150MHz manual tuning 8-1500MHz	£395.00
Sound Technology	
1700A measures distortion down to 0.002%, AC voltage 30µV-300V, S/N Ratio 100dB Dynamic range, power into 8Ω, 0.001% distortion Oscillator	£950.00
Marconi	
TF2303 AM/FM Modulation meter AM to 225MHz FM to 520MHz	£475.00
TF2370 Spectrum Analyser, 30Hz-110MHz, 0.1dB and 5Hz resolution	£6500.00
TK2374 Zero loss probe for TF2370	£375.00
Tektronix	
R491 Spectrum Analyser 10MHz-40GHz	£3500.00
7603 Main Frame with 7L13 plug in 1KHz-1.8GHz, 30Hz-3MHz resolution, -128dBm sensitivity	£9850.00

BRIDGES

Boonton	
63H Inductance Bridge, 0-110mH, Bridge frequency 5-500KHz	£1250.00
Marconi	
TF1245A + TF1246 'O' meter	£1100.00
TM4520 Set of Inductors	£350.00
Rohde & Schwarz	
LRT (BN6100) Inductance Meter, 1pH-100µH, 2-2.285KHz	£395.00
Wayne Kerr	
SR26B Source and Detector	£875.00

BRIDGES

Boonton	
63H Inductance Bridge, 0-110mH, Bridge frequency 5-500KHz	£1250.00
Marconi	
TF1245A + TF1246 'O' meter	£1100.00
TM4520 Set of Inductors	£350.00
Rohde & Schwarz	
LRT (BN6100) Inductance Meter, 1pH-100µH, 2-2.285KHz	£395.00
Wayne Kerr	
SR26B Source and Detector	£875.00

BRIDGES

Boonton	
63H Inductance Bridge, 0-110mH, Bridge frequency 5-500KHz	£1250.00
Marconi	
TF1245A + TF1246 'O' meter	£1100.00
TM4520 Set of Inductors	£350.00
Rohde & Schwarz	
LRT (BN6100) Inductance Meter, 1pH-100µH, 2-2.285KHz	£395.00
Wayne Kerr	
SR26B Source and Detector	£875.00

BRIDGES

Boonton	
63H Inductance Bridge, 0-110mH, Bridge frequency 5-500KHz	£1250.00
Marconi	
TF1245A + TF1246 'O' meter	£1100.00
TM4520 Set of Inductors	£350.00
Rohde & Schwarz	
LRT (BN6100) Inductance Meter, 1pH-100µH, 2-2.285KHz	£395.00
Wayne Kerr	
SR26B Source and Detector	£875.00

1920A with Option 13 9 Digit 1GHz	£750.00
1925A Multifunction, EMI Proof 9 Digit 125MHz	£625.00
1953A Counter Timer Opt 04, 07, 14, 15, 0-1.25GHz with prescalers, I.E.E.E. interface	£975.00

Hewlett Packard	
5340A 8 Digit 10Hz-18GHz	£3750.00
Marconi	
TF2430 unused condition, 7 digit 10Hz-80MHz 25MV Sensitivity	£175.00
TF2432 10Hz-560MHz 10mV sensitivity	£325.00

DVM's AND DMM's

Fluke	
8022A 3½ digit hand held	£65.00
Solartron	
7055 Microprocessor DMM, Scale Length 20,000, AC/DC volts, resistance, 1µV resolution	£600.00
7065 Microprocessor DMM, Scale length 1,400,000, AC/DC volts, resistance	£695.00

OSCILLOSCOPES

Marconi	
TF2213/1 + TK2214 X-Y Display and memory	£550.00



Philips	
PM3212 25MHz Dual Trace Portable	£475.00
SE Labs	
SM121 6 Channel Monitor, 12" crt, internal sweep	£395.00
Tektronix	
465 Dual Trace Portable Oscilloscope, DC - 100MHz, 5mV-5V/div, Full delayed sweep	£1395.00
465 with DM40	£1450.00
475 Dual Trace 200MHz Portable	£2000.00
7603 100MHz Mainframe with 7A18N and 7B53N	£3000.00
7704A 250MHz Mainframe c/w 7A22 Diff. Amplifier, 7A26 Dual Channel, 7B80 Timebase and 7B85 Delaying Timebase	£4610.00
SI Sampling Head, As New	£450.00
7D14 Digital Counter plug-in 525MHz	£850.00

Telequipment	
D66A 25MHz Dual Trace	£350.00
RECORDERS	
Watenabe	
MC641 6 Channel 250mm Chart Recorder	£1495.00
Yokogawa	
3047 2 Channel 2 cm/HR - 60cm/MIN	£435.00

Yokogawa	
3047 2 Channel 2 cm/HR - 60cm/MIN	£435.00
SIGNAL SOURCES	
Hewlett Packard	
4204A Decade LF Oscillator 10Hz-1MHz, 1mV-10V into 600Ω	£695.00
606B AM Signal Generator 50KHz-65MHz AM 0-95%	£850.00
608F 10-455MHz AM/PCM Modulation 0.1µV-1V output	£600.00
616B 1.8-4.2GHz int or ext PCM/FM 0.1µV-0.224V	£1000.00
616B UHF Signal Generator 1.8 to 4.2GHz, Int pulse Mod.	£1000.00

Philips	
PM5715 Pulse Generator 1Hz-50MHz	£675.00
PM6456 Stereo Generator	£250.00
Radiometer	
SMG1 Stereo Generator	£375.00

Siemens	
D2040 Selective Level Analyser and Voltmeter, 10Hz-60KHz	£1200.00
D2072 + W2072 Level Meter and Oscillator, 50KHz-100MHz	£2200.00
W2006 + D2006 Carrier Level Test Set, 10KHz-17MHz, -100 to +10dB	£1650.00
W2007 + D2007 Carrier Level Test Set, 6KHz-18.6MHz, -120 to +20dB	£1800.00
Wandel and Goltermann	
PF-1 Digital Error Rate Measuring Set, Consisting of PFM-1 Digital Error Rate Meter and PFG-1 Peltier Generator	£2490.00
SPM-6 and PS-6 Level Measuring Set, 6KHz-18.6MHz, -110dB to +20dB, Mains / battery operation	£2150.00

651B Test Oscillator, 10Hz-10MHz	
0.1mV-3, 16V	£415.00
3200B 10-500MHz Signal Source	£475.00
3320A Frequency Synthesizer 0.01Hz-13MHz	£995.00
8690A/B699B RF Sweeper System, 0.1-4GHz in 2 ranges, Max O/P 10mW to 2GHz and 6mW to 4 GHz	£2300.00
Marconi	
TF144H/4 AM Signal Generator 10KHz-72MHz 2µV-2V	£750.00
TF2002B AM/FM 10KHz-88MHz	£1200.00
TF2170B Synchronizer for TF2002B	£450.00
TF995B/2 AM/FM 200KHz-200MHz	£695.00
TF2005R 2 Tone Signal Source, 20Hz-20KHz, 0-111dB in 0.1dB steps	£295.00
TF2008 AM/FM 10KHz-510MHz built in sweeper, Output 0.2µV-200mV	£3500.00
6070 Signal Source 400-1200MHz	£695.00

PCM-1 PCM Test Set, PDA-64 PCM Signalling Analyser, PSM-4 Level Measuring Set Scanner, PDG-1 Digital Signal Generator, PDA-1 PCM Digital Signal Analyser	P.O.A.
---	---------------

MISCELLANEOUS	
Dymar	
2085 AF Power meter 30Hz-30KHz 10µW-50W input imp 1.2-1000Ω	£250.00
Fluke	
3010A Logictester, Self Contained, Portable, Full Spec. on Request	£8500.00
Hewlett Packard	
355E 12dB Programmable Attenuator unused	£90.00
4329A High Resistance meter 500KΩ-2 x 10 ¹⁰ Ω test voltages 10-1000V	£500.00
8405A Vector Voltmeter 1-1000MHz	£2000.00
8403A Modulator Fitted With 8732B PIN MODULATOR	£1500.00
8412A Phase Magnitude CRT display for network analyser	£1500.00
8482H Power Sensor 100KHz-4.2GHz, AS NEW	£250.00
8745A S Parameter Test Set, Fitted with 11604A Universal Arms 0.1-2GHz	£2750.00
5930BA HP-IB Timing Generator	£300.00
Marconi	
TF2162 M.F. Attenuator, 0-111dB	£135.00
TF21635 UHF Attenuator 0-142dB 50Ω impedance DC-1GHz	£250.00
TF2331 AF Distortion Meter 20Hz-20KHz	£395.00
TF2500 AF Power Meter, 7 ranges 100µ watts to 25 watts	£275.00
TF2807A PCM Multiplex tester	£1500.00
TF2950/5 mobile Radio Test Set AM/FM	£1550.00
TM8339 AC/DC mixer for use with TF2702	£250.00
Philips	
PM5519 Colour TV Pattern Generator AS NEW	£650.00
PM9380 Camera and Accessories (as new)	£200.00
Rohde and Schwarz	
MSC Stereo Coder, 30Hz-15KHz	£500.00
Tektronix	
141A PAL Test Signal Generator	£1750.00
1481C PAL TV Waveform Monitor	£2375.00
191 Constant Amplitude Sig. Gen. 350KHz-100MHz 5mV-5.5V	£350.00
TM504 mainframe with SG503 + PG506 + DMS01 + TG501	£3500.00



Philips	
PM5715 Pulse Generator 1Hz-50MHz	£675.00
PM6456 Stereo Generator	£250.00
Radiometer	
SMG1 Stereo Generator	£375.00

TRANSMISSION MEASURING EQUIPMENT

Siemens	
D2040 Selective Level Analyser and Voltmeter, 10Hz-60KHz	£1200.00
D2072 + W2072 Level Meter and Oscillator, 50KHz-100MHz	£2200.00
W2006 + D2006 Carrier Level Test Set, 10KHz-17MHz, -100 to +10dB	£1650.00
W2007 + D2007 Carrier Level Test Set, 6KHz-18.6MHz, -120 to +20dB	£1800.00
Wandel and Goltermann	
PF-1 Digital Error Rate Measuring Set, Consisting of PFM-1 Digital Error Rate Meter and PFG-1 Peltier Generator	£2490.00
SPM-6 and PS-6 Level Measuring Set, 6KHz-18.6MHz, -110dB to +20dB, Mains / battery operation	£2150.00

Please note: Prices shown do not include VAT or carriage.




Electronic Brokers Limited
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G



AMCRON INDUSTRIAL MUSCLE

- ★ POWER RESPONSE DC — 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.)
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS.
- ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

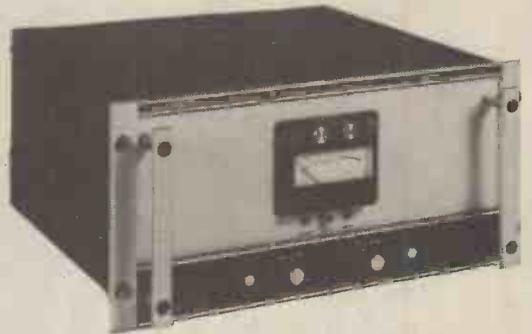

Model — M600

For full details on all Amcron Products write or phone Chris Flack

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

Analogue Associates

PROFESSIONAL INDUSTRIAL ELECTRONICS

WW - 020 FOR FURTHER DETAILS

Happy Memories

Part Type	1 off	25-99	100 up
4116 200ns	.95	.85	.65
4116 250ns	.90	.80	.60
2114 200ns Low power	1.20	1.10	.95
2114 450ns Low power	1.10	1.00	.85
4118 250ns	3.25	2.95	2.65
6116 150ns CMOS	4.95	4.45	3.65
2708 450ns	1.95	1.85	1.65
2716 450ns 5 volt	2.25	2.15	1.95
2716 450ns three rail	6.40	6.00	4.95
2732 450ns Intel type	4.25	3.95	3.35
2532 450ns Texas type	4.25	3.95	3.35

Z80A-CPU £4.75 Z80A-P10 £4.25 Z80A-CTC £4.25

Low profile IC sockets: Pins 8 14 16 18 20 22 24 28 40
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:
5 inch SSSD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00
8 inch SSSD £19.25 8 inch SSDD £23.65 8 inch DSDD £25.50

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or telephone for list.

Please add 30p post & packing to orders under £15 and VAT to total
Access & Barclaycard welcome
24-hr. service on (054 422) 618

Government & Educational orders welcome, £15 minimum
Trade accounts operated: Telephone or write for details
Prices are still tending to drop
Telephone for a quote before you buy

Happy Memories (WW)
Gladestry, Kington
Herefordshire HR5 3NY
Telephone:
(054 422) 618 or 628

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

**AUDIO FREQUENCY
TRANSFORMERS OF EVERY TYPE
YOU NAME IT! WE MAKE IT!
OUR RANGE INCLUDES**

Microphone transformers (all types), Microphone Splitter/Combiner transformers. Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, 'Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.

We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E.E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.

E. A. Sowter Ltd.

Manufacturers and Designers


E. A. SOWTER LTD. (Established 1941): Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
P.O. Box 36, Ipswich, IP1 2EL, England
Phone: 0473 5 2794 and 0473 219390
Telex 987703G Sowter

WW - 015 FOR FURTHER DETAILS


We supply FLUKE for Industry

Hilomast Ltd

**HILOMAST
SYSTEMS**

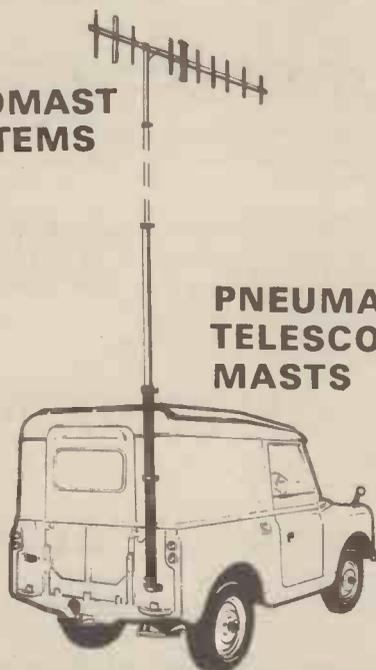

**PNEUMATIC
TELESCOPIC
MASTS**

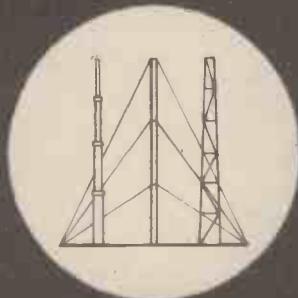

HILOMAST LIMITED

THE STREET HEYBRIDGE — MALDON
ESSEX CM9 7NB ENGLAND
Tel. MALDON (0621) 56480
TELEX NO. 995855

WW — 058 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1982

* NOW WITH A 2 YEAR WARRANTY

*** Fluke 8022B**

3½ Digit hand held LCD, DMM, AC/DC volts, DC/AC current, resistance, diode test, 0.25% basic DC accuracy, Overload protection. Vinyl carrying case C90 £8.00 **£85.00**

*** Fluke 8021B.**

Same spec as 8022B with additional audio tone for continuity. Vinyl case C90 £8.00 **£95.00**

*** Fluke 8020B**

3½ digit 0.1% basic DC accuracy, DC/AC volts, DC/AC current, resistance, diode test and conductance. Continuity beeper. Vinyl case C90 £8.00 **£125.00**

*** Fluke 8024B**

3½ digit, 0.1% basic DC accuracy, DC/AC volts, DC/AC current, resistance, Diode test, conductance, logic + continuity detect + temperature. Peak hold on voltage and current functions, continuity beeper. Vinyl case C90 £8.00 **£155.00**

FLUKE 8050A

4½ Digit LCD DMM with true RMS on AC volts and current DC volts 200mV-1KV, 10µV resolution AC volts, 200mV-750V, 10µV resolution, DC/AC current 200µA-2A, 0.01µA resolution resistance 200Ω-20MΩ, 0.01Ω resolution. Also reads dB direct referenced to 16 stored impedances. Conductance ranges 2mS and 200nS. **£255** mains model **£285** mains battery.

FLUKE 8012A

3½ Digit LCD DMM with true RMS on AC volts and current, DC volts 200mV-1KV, 100µV resolution, AC volts 200mV-750V, 100µV resolution, DC/AC current 200µA-2A, 0.1µA resolution, Resistance 200Ω-20MΩ, 0.1Ω resolution Low resistance 2Ω and 20Ω, 1mΩ resolution Conductance ranges 2mS-20µS-200nS **£229.00** mains model **£259.00** mains battery.

FLUKE 8010A

3½ Digit LCD DMM Same spec as 8012A plus a 10Amp AC/DC current range, but not low resistance range. **£175.00** mains model **£203.00** mains battery.

ACCESSORIES

A81-230 Battery eliminator	£14.00
C90 Carry case for hand held	£10.00
801-600 Amp clamp	£68.00
80J-10 Current shunt 10A	£22.00
80K-40 H.V. probe 40kV	£56.00
80K-6 H.V. probe 6kV	£40.00
80T-150 Temperature probe	£72.00
80T-H Touch hold probe	£36.00
83RF R.F. probe 100MHz	£40.00
85RF R.F. probe 500MHz	£69.00
Y8102 Thermocouple probe	£41.00
Y8103 Bead thermocouple	£18.00
Y8104 K type thermocouple termination	£8.00
Y8133 Deluxe test leads	£13.00

The above prices do not include carriage or VAT (15%).


**EXPRESS
DELIVERY
SERVICE**

Simply Phone or
Telex your order for
Immediate dispatch.

Electronic Brokers Ltd
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G
WW — 201 FOR FURTHER DETAILS

Electronic Brokers

METER PROBLEMS?

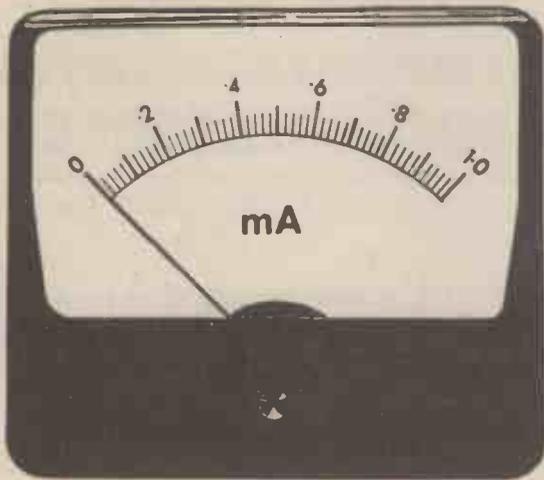

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)
138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937
Telex: 892301 HARTRO G

WW - 013 FOR FURTHER DETAILS

TELEMET ABI64 COUNTER TIMER

a professional, portable low cost unit



- 3 frequency ranges DC to 180MHz with 1 Sec gate including phase locked loop 1Hz-1KHz providing 0.01Hz resolution within 10 seconds.
- Period/Time ranges to 1 μ Sec, 1mSec and 1 Sec resolution.
- Manual and logic gating on the time and event ranges.
- 13mm 8 digit display with leading zero suppression.
- Internal charger and NiCad batteries.

Price £195.00 plus VAT (carriage Inc!) from

Telemet

Unit S17, Europa House,
Fraser Road, Erith,
Kent DA8 1QL.
Tel. (03224) 39677.

WW - 046 FOR FURTHER DETAILS

We supply HAMEG for Industry



HM 307 OSCILLOSCOPE

Single trace. DC to 10MHz. Rise time 35ns. 5mV/cm to 20V/cm. Timebase 0.5 μ S-0.2S. Built in component tester. LPS technique provides stable and reliable triggering up to 30MHz £138.00



HM 203 PORTABLE OSCILLOSCOPE

Dual Trace. DC to 20MHz 8 x 10cm display. Rise time 17.5ns. Sensitivity 5mV/cm-20V/cm. Timebase 0.5 μ S-0.2S. x 5 magnifier. X-Y operation. Auto or variable trigger. Channel 1. Channel 2. line and external. Coupling AC, or TV low pass filter. Weighs only 6Kg. Size (mm.) H. 145, W. 285, D. 380 £220.00



HM 412-5

Dual Trace. DC to 20MHz 8 x 10cm display with internal graticule. Rise time 17.5ns. Variable input 2mV-20V/cm. Add and invert modes. Timebase 0.5 μ S-0.2S with sweep delay 100ns-1S x 5 expansion. X-Y operation Z modulation. Trigger CH1, CH2, CH1/2. Line or EXT. £350.00



HM 705

Dual Trace DC-70MHz 8 x 10cm display with internal graticule. Rise time 5ns. Variable input 2mV-20V. Add and invert modes. 95ns Signal Delay Line. Timebase 50ns-1S/cm with Sweep delay 100ns-1S x 10 expansion. XY operation. Z modulation. Trigger CH1, CH2, CH1/2 line or EXT. £580.00

The above prices do not include carriage or VAT (15%).

Simple Phone or Telex your order for immediate dispatch.

Electronic Brokers Ltd
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

WW - 202 FOR FURTHER DETAILS



Electronic Brokers

AP'82



April 15th & 16th
9am to 6pm
April 17th
9am to 5pm

The exhibition for every radio amateur




AP'82 is a specialist exhibition of one of the fastest growing areas of communications today. Organised by The Radio Society of Great Britain, the UK's national amateur radio society, this exhibition brings together every aspect of amateur radio in what has been called "Europe's largest tent," Alexandra Pavilion. Exhibitors include leading UK manufacturers and importers, affiliated societies for the specialist operator, displays of the latest microwave techniques and a comprehensive selection of publications.

If you too are interested in the future of amateur radio, a visit to the RSGB stand is a must, where staff and volunteers will be available to give information on the wide range of services offered by the society.

If you're a newcomer or an ardent radio amateur AP'82 is an exhibition not to miss.

For RSGB membership details, send a post-card to address shown below.

How to get there

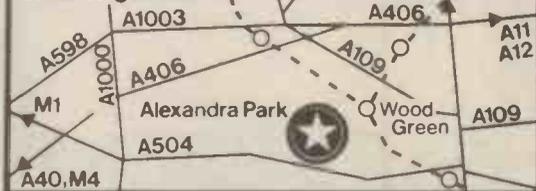

Public Transport. Alexandra Palace is easily reached by road and has free car and coach parking. Bus services 29, 41, 102, 123, 134, 212, 221, and 244 are within easy walking distance, and service W3 connects with the Underground at Wood Green (Piccadilly Line) and Finsbury Park (Piccadilly and Victoria Lines).

By Car. A.P. is near Muswell Hill or Wood Green, off the North Circular Road.

Talk-in: GB2AP. FM S22 or SU8 (initial calls).
SSB 144.28MHz (listening watch).

Discover the world of

• AMATEUR RADIO •

with RSGB

Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE.

An entire range of low-cost high-performance instruments



sabtronics

'Making Performance Affordable'

*2010A 3½-Digit L.E.D. Bench DMM	*5020A 1Hz-200KHz Function Generator
*2015A 3½-Digit L.C.D. Bench DMM	*8110A 100MHz 8-Digit Frequency Meter
2020 3½-Digit L.E.D. Bench DMM with Microcomputer Interface	*8610A 600MHz 8-Digit Frequency Meter
*2033 3½-Digit L.C.D. Hand DMM	*8610B 600MHz 9-Digit Frequency Meter
*2035A 3½-Digit L.C.D. Hand DMM	8000B 1GHz 9-Digit Frequency Meter
*2037A 3½-Digit L.C.D. Hand DMM with Temp.	8700 10MHz Universal Frequency Counter/Timer
LP-10 10MHz Logic Probe	PSC-65 600MHz Prescaler
	9005 5MHz Single Trace Oscilloscope

* Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from:

BLACK STAR LTD.,
9a Crown Street, St. Ives,
Cambs. PE17 4EB
Tel: (0480) 62440. Telex 32339



WW - 047 FOR FURTHER DETAILS

RADIOCODE CLOCKS

are powerful and comprehensive instruments which receive, decode and analyse time-coded standard frequency transmissions to provide accurate, secure and completely automatic time/calendar or synchronisation systems.



Applications

- Automatic master clock and slave controller.
- Synchronisation of separate equipment and events.
- Programmable energy management system.
- Computer clock/calendar with battery backup.
- Data logging and time recording.
- Process and equipment control.
- Broadcasting, Astronomy, Navigation.
- Satellite tracking.

If you have a time or synchronisation problem, write or phone for further details of our portable and new microcomputer-controlled Radiocode Clocks.

Circuit Services, 6 Elmbridge Drive
Ruislip, Middlesex. Ruislip 76962

WW - 008 FOR FURTHER DETAILS



Just **50p** will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

★ Lowest prices — Largest stocks ★

★ Expert staff — Sound advice ★

★ Choose your DIY HiFi Speakers in the comfort ★ of our listening lounge.

(Customer operated demonstration facilities)

★ Ample parking ★

★ Access Visa American Express accepted ★



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



WW - 050 FOR FURTHER DETAILS

ONLY £48.50 Post free, inc VAT



LOW COST EPROM ERASURE

- HOLDS UP TO SIX EPROMS
- SAFETY INTERLOCKED TRAY
- FAST ERASE TIME
- QUALITY STEEL CASE
- MONEY-BACK GUARANTEE

Send cheque or official order for prompt delivery. Telephone orders will be despatched C.O.D. at no extra charge.

Also available in London from: Technomatic Ltd. Transam and in Aberdeen from: Granite Chip.

NORTHERN ELECTRONICS

51 Arundel Street, Mossley, Lancashire Tel: Mossley (04575) 4119

WW - 034 FOR FURTHER DETAILS

NOW!
FROM SESCOM

ORDER YOUR FAVOURITE AUDIO ACCESSORIES BY MAIL

SEND FOR YOUR FREE COPY OF OUR 1982 CATALOG



48 PAGES
8 1/2" x 11"

OVER 250 ITEMS

INCLUDING DIRECT BOXES, MIC-SPLITTERS, SIGNAL PROCESSING, AUDIO MODULES, TRANSFORMERS & MANY OTHER ACCESSORIES

WITH TECHNICAL DATA & USE DIAGRAMS

We Ship the fastest & most convenient way for you! Most Shipments From Stock



SESCOM, INC.
RETAIL SALES DIVISION
1111 Las Vegas Blvd. North
Las Vegas, NV 89101-1197 U.S.A.

(702)384-0893
(800)834-3487
TWX (610)397-8996

WW - 006 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1982

Electronic Brokers

DEC SALE

a selection from our huge stocks



MASSBUS

11/70 512KB MOS, RWM05 Disk, LA120 Console.....**£57,000.00**
TVU77 Master Tape deck c/w formatter and control.....**£15,500.00**

UNIBUS

11/04 10 1/2'32KB MOS.....**£3,825.00**
11/34A 256KB, KY11, DL11.....**£8,500.00**
11/40 64KW, KT11D.....**£4,250.00**
11/45 96KW CPU.....**£7,450.00**
LP11 M7258 Printer Interface.....**£325.00**
PC11A Reader Punch and Ct1.....**£1,250.00**
RK06 Disk Drive [NEW].....**£2,500.00**
RK611 RK06 and Ct1.....**£4,250.00**
RL01 Disk Drive.....**£895.00**
RL11 RL01 and Ct1.....**£1,745.00**
RL02 Disk Drive.....**£2,500.00**
RL211 RL02 and Ct1.....**£3,250.00**
RX11 Dual Floppy and Ct1 [NEW].....**£895.00**
RX211 Dual Floppy and Ct1 [NEW].....**£1,450.00**
TU10 Tape Deck.....**£2,250.00**
TM11 TU10 and Ct1.....**£3,750.00**
TS11AB Tape Deck.....**£5,850.00**

Q-BUS

11/03-LJ 5 1/4'32KB CPU [NEW].....**£1,500.00**
BA11-MF 3 1/2' Expander Box.....**£825.00**
DZV11A 4-Line MUX.....**£350.00**
LPV11 M8027 Printer Interface.....**£325.00**
RKV11 Controller for RK05 Disk [NEW].....**£395.00**
RXV11 Dual Floppy and Ct1 [NEW].....**£995.00**

OMNIBUS

PDP8A-205 CPU, 32KW MOS [NEW].....**£1,750.00**
RX8E Dual RX01 Floppy and Ct1 [NEW].....**£895.00**
RX28 Dual RX02 Floppy and Ct1 [NEW].....**£1,450.00**
BE8A Omnibus expander.....**£395.00**
DKC8-AA Option module [NEW].....**£295.00**
DP8EB Communications Adaptor.....**£395.00**
KE8E Extended Arithmetic.....**£895.00**
KL8E Asynchronous Interface.....**£175.00**
LP8 M8342 Printer Interface.....**£225.00**



VDU & PRINTER OFFERS

HAZELTINE H2000 VDU

27 x 74 Display, 64 ASCII, RS232, full half duplex and full editing XY cursor addressing and batch mode, green phosphor CRT, detachable keyboard.

SPECIAL QUANTITY DISCOUNT OFFER

1-2 **£289.00** 5-9 **£255.00**
3-4 **£275.00** 10+ **£250.00**

Also a few remaining H1000 12 x 80 display RS232, 110/300 or 300/1200 baud £199.00



AJ832 DAISY WHEEL PRINTER / PLOTTER

Scoop purchase of Anderson-Jacobson AJ832 Daisy Wheel Printers complete with full keyboard integral stand and RS232 interface

Utilising the famous GUME Printer Mechanism
1-4 **£995.00**
5-9 **£950.00**
10+ **£895.00**



LINE PRINTERS

DEC LP11-VD 300 1pm Drum Printer upper/lower case, including control module.....**£2,750.00**
DEC LP04 900 1pm upper/lower case drum printer BRAND NEW SURPLUS, including control module.....**£5,750.00**
DATA PRODUCTS B600 band printer including control module.....**£3,750.00**

DEC LA36/LA38 and LA180 MATRIX PRINTERS

LA36 30cps keyboard printer with integral stand, 132 column tractor-feed, upper/lower case ASCII LA36 with 20mA interface **£450.00**
LA36 with RS232 interface **£495.00**
LA35 - Receive only version of LA36 - AMAZING VALUE!
LA35 with 20mA interface **£250.00**

LA35 with RS232 interface **£275.00**
LA180 high-speed output printer with 180 cps printing, 132 column tractor-feed, upper/lower case ASCII. Integral stand [NEW]
LA180 printer standard parallel [Centronics type] interface... **£495.00**
LA180-ED with optional RS232 or 20mA interface **£670.00**

AJ212 ACOUSTIC COUPLERS

Special Purchase of Anderson-Jacobson Acoustic Couplers suitable for use with RS232 or 20mA devices, full or half duplex, at speeds up to 300 baud. Attractive wooden case..... **£125.00**

VT50 AND VT52 DECScope VDUS

VT50 DECScope, 12 x 80 upper case ASCII, 9 switch-selectable baud rates 75-9600 baud, 20mA or RS232 interface..... **£250.00**
VT52 DECScope, 24 x 80 upper/lower case ASCII, 9 switch-selectable baud rates 75-9600 baud, 20mA or RS232 interface..... **£525.00**
All items reconditioned unless otherwise stated

ADD 15% VAT TO ALL PRICES
Carriage and Packing extra

Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex 298694



Electronic Brokers

CMOS

4000	0.11
4001	0.11
4002	0.12
4007	0.13
4008	0.50
4008AE	0.80
4009	0.25
4010	0.30
4011AE	0.24
4011	0.11
4013	0.25
4015	0.50
4016	0.22
4017	0.40
4019	0.38
4020	0.55
4021	0.55
4022	0.55
4023	0.15
4024	0.33
4025	0.15
4026	1.05
4027	0.28
4028	0.50
4029	0.55
4030	0.35
4035	0.67
4040	0.50
4042	0.50
4043	0.50
4043AE	0.93
4044	0.60
4046	0.60
4047	0.58
4049	0.24
4050	0.24
4051	0.55
4052	0.55
4053	0.55
4054	1.30
4055	1.30
4056	1.30
4059	5.75
4060	0.75
4063	1.15
4066	0.30
4067	4.30
4068	0.15
4069AE	0.14
4070	0.16
4071	0.16
4072	0.16
4073	0.16
4075	0.16
4076	0.55

4077	0.18
4078	0.18
4081	0.12
4082	0.18
4093	0.30
4099	0.80
4175	0.80
4150	0.60
4503	0.50
4506	0.70
4507	0.37
4508	1.50
40161	1.05
4510	0.55
4511	0.45
4512	0.55
4514	1.25
4515	1.25
4516	0.60
4518	0.35
4520	0.80
4521	1.30
4522	0.89
4527	0.80
4528	0.85
4529	0.70
4531	0.85
4532	0.80
4534	4.00
4536	2.50
4538	0.85
4539	0.80
4543	0.80
4549	3.50
4553	2.70
4554	3.20
4555	0.35
4556	0.40
4557	2.30
4558	0.80
4559	3.50
4560	2.50
4561	1.00
4562	2.50
4566	1.20
4568	1.45
4569	1.70
4572	0.23
4580	3.25
4581	1.40
4582	0.70
4583	0.80
4584	0.27
4585	0.45
4702	4.50
4703	4.48
4704	4.24

4705	4.24
4706	4.50
4720	4.00
4723	0.95
4724	0.95
4725	2.24
40014	0.54
40085	0.99
40098	0.54
40106	0.69
40160	1.05
40161	1.05
40162	1.05
40163	1.05
40174	1.05
40175	1.05
40192	1.08
40193	1.08
40194	1.08
40500	1.08

TTL N


7400N	0.10
7401N	0.10
7402N	0.20
7403N	0.11
7404N	0.12
7405N	0.12
7406N	0.22
7407N	0.22
7408N	0.15
7409N	0.15
7410N	0.12
7411N	0.18
7412N	0.19
7413N	0.27
7414N	0.51
7415N	0.27
7416N	0.27
7417N	0.27
7418N	0.27
7419N	0.27
7420N	0.13
7421N	0.28
7422N	0.34
7423N	0.22
7425N	0.22
7426N	0.22
7427N	0.22
7430N	0.12
7432N	0.23
7437N	0.22
7438N	0.22
7440N	0.14
7441N	0.54
7442N	0.42
7443N	0.62
7444N	0.62
7445N	0.62
7446N	0.62

7447N	0.62
7448N	0.56
7450	0.14
7451N	0.14
7453N	0.14
7454N	0.14
7460N	0.14
7470N	0.28
7472N	0.27
7473N	0.28
7474N	0.28
7475N	0.35
7476N	0.30
7480N	0.26
7481N	0.20
7482N	0.75
7485N	0.75
7486N	0.24
7489N	1.05
7490N	0.30
7491N	0.55
7492N	0.35
7493N	0.35
7494N	0.70
7495N	0.60
7496N	0.45
7497N	1.40
74100	1.10
74104	0.62
74105	0.62
74107	0.26
74109N	0.35
74110N	0.54
74111N	0.68</

hi! reliability hi! service hi! performance hi! competitive hi!

Low cost excellence


with a 2 YEAR guarantee

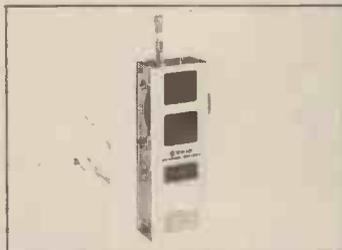

**DM 801
DIP METER**
£55

DM 801 DIP Meter — 700 KHz to 250 MHz in 7 bands — Inductive and Capacitive coupling with an 'RF Searcher' — high sensitivity — absorption Frequency Meter — Xtal tester — Marker generator — CW and AM monitor.
FC 754A Digital Frequency Counter — 6 digit — 10 Hz to 250 MHz
FC 756 — 10 Hz to 500 MHz.
DF 760 — Combined 7 digit Frequency Counter and 3½ digit DMM.

**AG 202A
SINE-SQUARE
OSCILLATOR**
£68

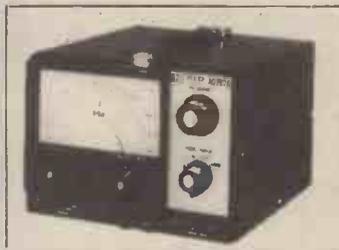

AG202A 200KHz R.C. Oscillator — 20Hz to 200KHz in 4 ranges — Sine and Squarewave — Flat O/P to 10V r.m.s. from 600 ohms — < 0.5% distortion — > 60dB of variable O/P atten — Ext. Sync. — Large easy to read single dial with smooth precise tuning control —
AG203 Low Distortion Oscillator — < 0.1% distortion — 10Hz to 1MHz in 5 ranges.




**SG 402
30 MHz A.M.
SIG. GEN.**
£59

SG402 A.M. Signal Generator — 100KHz to 30MHz in 6 bands — 100mV of O/P with variable attenuator — Int. and Ex. A.M. — Solid State — Lightweight and portable — Large clear easy to read frequency dial.

**CO 1303D
5 MHz
OSCILLOSCOPE**
£108



CO1303D, DC to 5MHz Oscilloscope — 10mV/div sensitivity with variable atten. — Int. variable sweep frequency in 4 ranges from 10Hz to 100KHz — Int. and Ext. sync. — Direct deflection terminals can monitor R.F. up to 450MHz. CO1303G as above, plus 1:8 to 54MHz monitor freq. range from 1 to 500W direct coupling — Two Tone gen. 1KHz and 1.575KHz — ideal for SSB, A.M. C.W. etc.

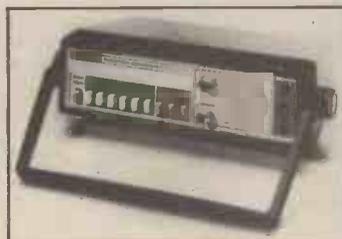

**FG 270
FUNCTION GEN.**
£139

FG270, Function Generator — 0.1Hz to 1MHz in 6 ranges — sine, square and triangle — 20V p-p open circuit output — < 1% distortion — D.C. offset — TTL O/P — Ext. VCO for sweep tests. FG271 as above plus 0.02Hz to 2MHz in 7 ranges — Int. sweep — Pulse, Tone Burst and A.M.

**DL 705
3½ DIGIT
DMM**
£92



DL 705 3½ Digit LED DMM — 2V FS 1000V FS (DC and AC) — 20A FS to 200 mA FS (DC) — 2 ohms FS to 20 M ohms FS — Accuracy 0.5% of reading — Compact, reliable and easy to use.
DL706 3½ Digit Auto Ranging and Zero — 0.1% of reading — 100µV resolution — AC Amps.
DL 720 4½ Digit — 0.03% of reading.

Plus many other Trio Products such as high sensitivity electronic voltmeters, Wow and Flutter meters, DIP meters and of course the main range of Trio scopes up to 100MHz — JUST ASK FOR THE CATALOGUE



TRIO®


House of Instruments Ltd.,
Clifton Chambers,
62, High Street,
Saffron Walden,
Essex CB10 1EE.
Telephone: (0799) 24922
Telex: 81653.

hi!
House of Instruments Ltd.

performance hi! competitive hi! reliability hi!

reliability hi! service hi! performance hi! competitive hi! service hi!

Testing... Testing... Testing...

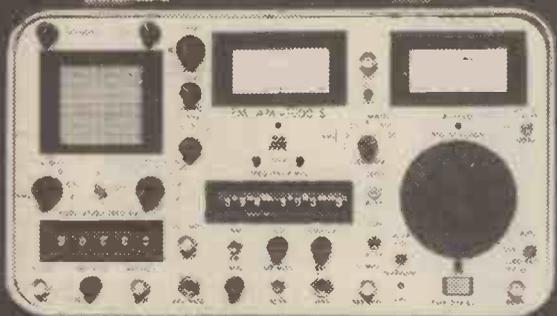

anywhere!

FM/AM 1000s with Spectrum Analyser — we call it the SUPER — S

A portable communications service monitor from IFR, light enough to carry anywhere and good enough for most two-way radio system tests.

The FM/AM 1000s can do the work of a spectrum analyser, oscilloscope, tone generator, deviation meter, modulation meter, signal generator, wattmeter, voltmeter, frequency error meter — and up to five service engineers who could be doing something else!

A PRACTICAL TOP UP! MM-100 MULTI-METER

Simply replaces the protective lid of the FM/AM 1000s. It includes a modified probe, PB-114, and a built in speaker unit with independent volume control for audible response to signal measurement. This practical 'top up' will perform the following functions.

Sinad: Measurements for 1 kHz tone (± 20 Hz)


Distortion: To 30%

DC Volts: Up to 300 volts and up to 800 volts when the X10 probe is used

AC Volts: 600 VRMS maximum for frequencies between 25 Hz and 25 kHz

Ohms: Using the modified probe, part number PB-114, Ohms can be measured on scales X1 to X10 K

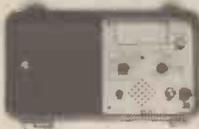% AM Measured on the RF signal applied to the FM/AM-1000 unit



OPTIONAL ACCESSORIES

A choice of R.F. power attenuators and protective carrying cases.

For further information contact Mike Taylor




**Fieldtech
Heathrow**

Fieldtech
Heathrow Ltd.
Huntavia House
420 Bath Road
West Drayton
Middlesex UB7 0LL
Tel: 01-897 6446
Telex: 23734
FLDTEC G

IFR precision simulators

WW - 021 FOR FURTHER DETAILS

50+ CASES FOR SPECIALISTS referred by JENSEN

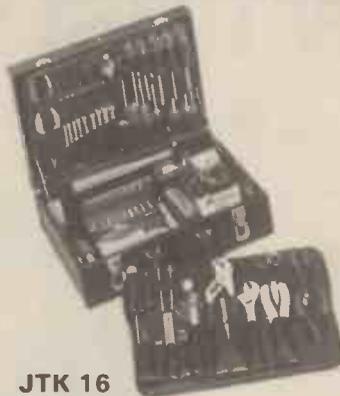

JTK 16

Designed for the professional electronic technician requiring a complete set of tools in a compact package

50 professional tools. VOM Test meter optional.
Also available with metric tools (JTK 16mm).

See these cases together with more than 20 other complete specialist tool kits and a complete range of over 30 empty cases in the Jensen catalogue available on request from:



JTK 17

Available in 12 different case modifications. Specially suited for maintenance of electronic equipment, communications, radar, computers and office machines. 57 top quality tools. VOM Test Meter optional. Deluxe attache case of hardwood construction, llama grain covering and solid brass fittings. Metric conversion kit available.

Special Products Distributors Limited
81 Piccadilly, London W1V 0HL

Tel. 01-629 9556 Cables: Speciproduct, London, W.1

WW - 059 FOR FURTHER DETAILS

The new CES micropad



The microphone for mobile radio, with *DTMF* signalling and optional *ANI*, brings greater system flexibility to your telecom network.

**Interface
Quartz
Devices
Limited**

For further information contact the sole agents

IQD

29 Market Street
Crewkerne
Somerset TA18 7JU

Crewkerne (0460) 74433
Telex 46283 inface g

WW - 014 FOR FURTHER DETAILS

The WERSI Concept

Build your own electronic organ with the WERSI system

WERSI presents their new generation of electronic organs and accessories to you, the do-it-yourselfer. All the tools you need are illustrated left. The electronics involved is very revolutionary, making it very easy to understand. Every non-specialist who can read is able to do it. Building a WERSI organ from a kit can save you more than half the cost of a similarly equipped ready-made instrument and that means with WERSI and your own initiative and involvement you can afford a sophisticated electronic organ.

Do you have to be a virtuoso or a music lover to benefit from building a WERSI organ? No . . . this would mean failure to recognize the sense of the hobby. Even after your project is completed you will be able to discover new excitement from the world of music.

Whether you play haunting blues, stomping disco, liturgical hymns or classic renditions the new generation of WERSI organs will make your life more enjoyable.


Want to know more? Just fill in the coupon below, enclosing £1.00, and we'll send you the big, full colour catalogue. It will answer all your questions.



AURA SOUNDS LTD are the first company to successfully market WERSI organs and kits in the U.K. We have three modern show-rooms where we pride ourselves you will receive a friendly welcome. Why not pop in and see the WERSI range for yourself — we can always arrange a free demonstration. We also offer a free technical telephone support service which is second to none.

Alternatively, fill in the coupon below for the full colour catalogue. For immediate action telephone 01-668 9733 24 hour answering service quoting Access/Barclaycard Number.

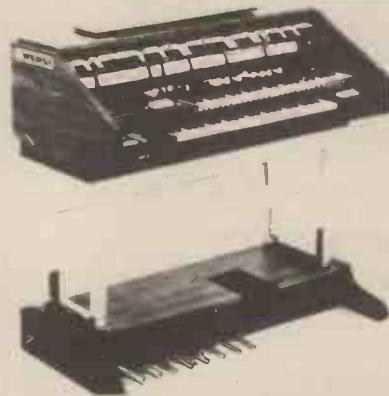AURA SOUNDS LTD.
14-15 Royal Oak Centre, Brighton Road, Purley, Surrey.
Tel: 01-668 9733
17 Upper Charter Arcade, Barnsley, Yorkshire.
Tel: (0226) 5248
1729 Coventry Road, Sheldon, Birmingham. Tel: 021-707 8244



Please send me the full colour WERSI Catalogue. I enclose cheque/P.O. for £1.

NAME _____

ADDRESS _____

Send to Aura Sounds Ltd., 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.

WW - 060 FOR FURTHER DETAILS

The Arc single-board computer with BASIC



- o Z8671 MICRO PROCESSOR WITH ON-CHIP BASIC INTERPRETER
- o REAL TIME CLOCK/CALENDAR WITH ON-BOARD BATTERY BACKUP
- o RS232 INTERFACE WITH 8 BAUD RATES 110-19200
- o 4K BYTES OF RAM-PLUS DEMONSTRATION PROGRAMS IN 2K EPROM
-CAN BE EXPANDED ON BOARD TO 20K BYTES OF RAM/EPROM
- o CHOICE OF TWO BUS SYSTEMS -64WAY EURO CARD -50 WAY RIBBON CABLE
- o 19 UNCOMMITTED I/O LINES

This microcomputer represents a breakthrough in single-board computer performance. Its BASIC interpreter, real-time clock and calendar, large memory capacity, serial and parallel I/O, timers, interrupt and expansion capabilities make it the most cost-effective solution for control problems.

Using Zilog's Z8 BASIC/DEBUG interactive BASIC, programs can be entered into RAM and tested with a vdu or other RS232 terminal, then transferred to EPROM. The computer includes 4K bytes of RAM, with provision for another 4K bytes on board. Some or all of this RAM may be replaced with EPROM for stand-alone applications, and a sample EPROM with demonstration and utility programs is included.

An exciting feature of the ARC is its real-time clock and calendar. This greatly extends its usefulness in the fields of real-time control, monitoring, timing and security systems.

ALSO AVAILABLE

POWER SUPPLY MODULE
Outputs 5v 30v (nom)
12v -12v

EPROM PROGRAMMER
WITH 1200 BAUD
CASSETTE INTERFACE.
Programs may be stored on
cassette and transferred to
2K or 4K EPROMS for
stand-alone controller appli-
cations.

FUTURE PRODUCTS

Opto isolated relay board
a/d and d/a converters
speech synthesiser.

PRICES

ARC1 computer	£135.00
EPROM programmer	£58.00
Power supply	£32.00


Please specify bus connection (euro card or ribbon cable).
Prices include carriage in U.K., but exclude VAT.

Arcom

CONTROL SYSTEMS LTD.

Head Office: 37 Grahame Close, Blewbury, Oxon. OX11 9QE Tel Blewbury(0235) 850544

WW - 074 FOR FURTHER DETAILS

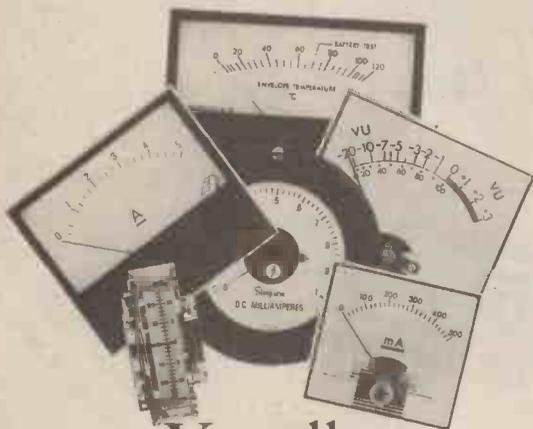

You tell us
we'll deliver!

We have the UK manufacturing facilities, experience and skills to give you the panel meter you want. With all aspects of panel meter construction under our control it means you can specify and get the sensitivity, movement ballistics and scale you want. It all adds up to greater flexibility and a wider choice. You want them quickly? - of course! Low quantities or large quantities present no problems. Next time why not give us a call - ask for Colin Williams, tell him what you want - you could be surprised at what he may have to tell you!



Bach-Simpson

Bach-Simpson (U.K.) Limited,
Trenant Estate, Wadebridge, Cornwall, PL27 6HD.
Telephone: (020881) 2031 Telex: 45451

WW - 025 FOR FURTHER DETAILS

SOUND INVESTMENT



QUALITY REEL TO REEL & CASSETTE TAPE HEADS

FITTING A NEW TAPE HEAD CAN TRANSFORM THE PERFORMANCE OF YOUR TAPE RECORDER.
OUR FULL CATALOGUE (PRICE 50p) ALSO INCLUDES TAPE TRANSPORTS, DISC DRIVES,
PRE-AMPLIFIERS AND ACCESSORIES

POPULAR UNIVERSAL CASSETTE HEADS TO EIAJ STANDARDS

C21RPS18 MONO R/P	£4.62	Hole Centres 17mm Apart, 12mm From Head Face
B24-02 STEREO R/P	£7.66	C42RPH20 STEREO R/P SENDUST FOR
B24-07 STEREO R/P FOR OOLBY	£9.05	CHROME/METAL TAPES . . . £10.67
SYSTEMS	£9.05	C42RPH04 STEREO R/P GLASS FERRITE
C21ES18 MONO/STEREO ERASE	£2.13	THE ULTIMATE LONG LIFE,
HEAD	£2.13	HIGH PERFORMANCE HEAD £13.34

POST AND PACKING 40p EX STOCK DELIVERIES, ALL PRICES INCLUDE V.A.T.

The Monolith Electronics Co. Ltd.,
5/7 Church Street, Crewkerne,
Somerset TA18 7HR
Tel: 0460 74321.
Telex: 46306 MONLTH G.

MONOLITH

electronic products

WW - 039 FOR FURTHER DETAILS

TV TUBE REBUILDING

Faircrest Engineering Ltd. manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers' requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

4 Union Road, Croydon, CR0 2XX
01-684 1422/01-684 0246

WW - 033 FOR FURTHER DETAILS


HANDSOME!

First there was the 130. A handheld D.M.M. which still sets the standards our competitors strive to match.

Next came the 131. The introduction of the 135 saw 4½ digits on a handheld D.M.M. for the very first time.

And that same commitment to innovation has resulted in the latest additions to the range. The Keithley 128 D.M.M. with audio-tone and 870 Digital Thermometer with centigrade and fahrenheit readout.

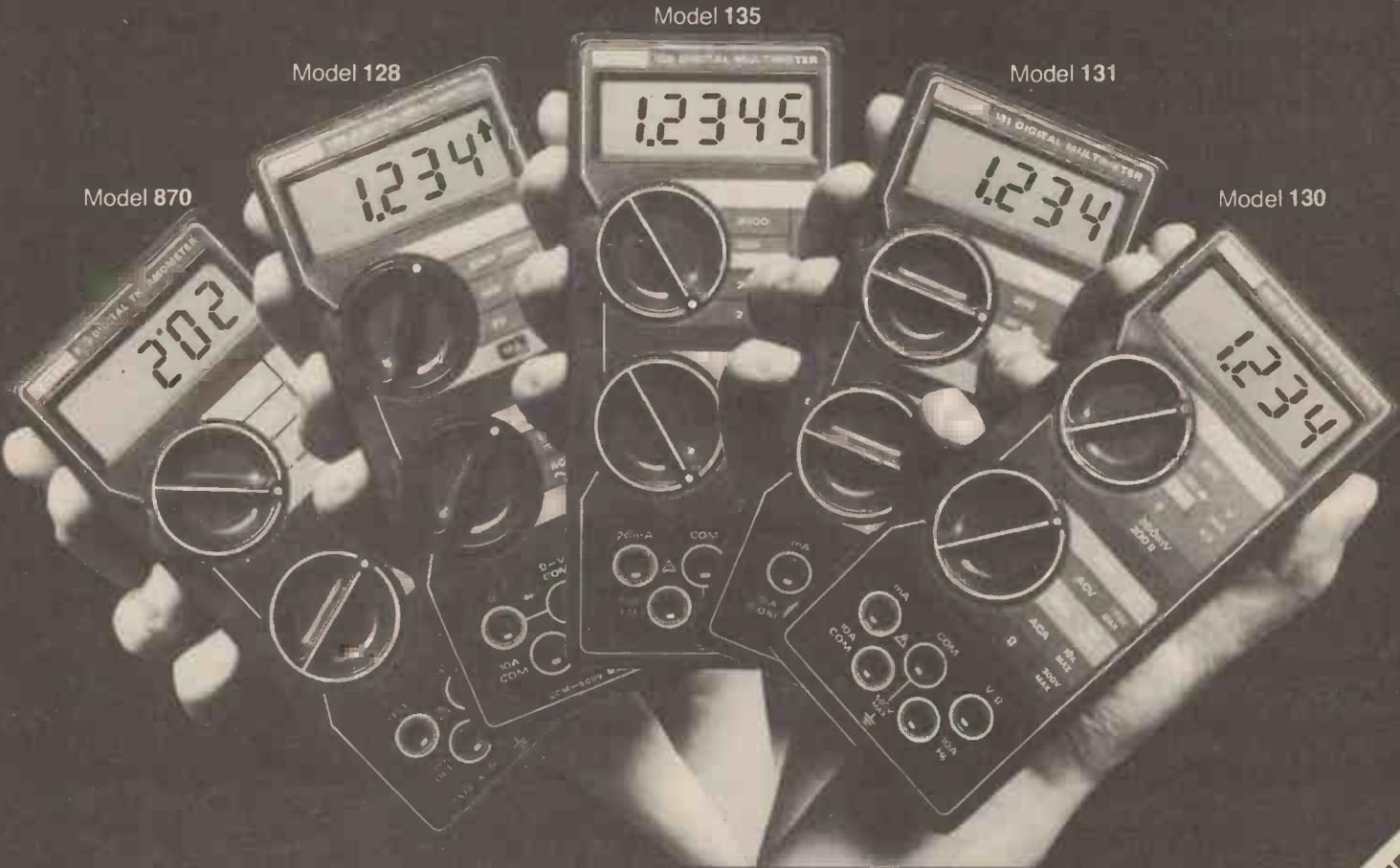The result is an unrivalled selection of handheld measuring devices. Each specification carefully matched to a given need. With performance that looks pretty good on paper. And even better in the field!



Model 870 ● 0.025% accuracy ● Centigrade and fahrenheit readout ● Measures up to 1370°C

● 0.1° resolution up to 200°C

Model 128 ● Audio-tone with adjustable threshold ● 25 ranges: 5 functions ● 10 amp span

Model 135 ● 0.05% accuracy ● Full overload protection ● ACU bandwidth to 20 KHz

Model 131 ● 0.25% accuracy ● 25 ranges: 5 functions ● 10 amp span

Model 130 ● 25 ranges: 5 functions ● 10 amp span ● 0.5% accuracy

All models are guaranteed accurate for one year. And built to the high standards of quality expected of the Keithley name.

For more information simply fill in the coupon.

And learn about a range which will serve you . . . handsomely!

KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

Also available from
I.T.T. Instrument Services, Tel. Harlow 29522

WW - 031 FOR FURTHER DETAILS

I would like to know more about your Handheld Units.
Please send me details on D.M.M.'s 870 Thermometer

Name _____ Position _____
Company _____
Address _____
Telephone _____

TEST INSTRUMENTS

SABTRONICS

NEW 2033 HANDHELD DMM
Housed in a tough ABS case with bench stand. Mains or Battery operated. Large 3 1/2 digit LCD display.

BASIC SPECIFICATION

DC Volts	100µV-1000V
AC Volts	100µV-1000V
DC Amps	10µA-2A
AC Amps	10µA-2A
Ohms	1Ω-20MΩ

Only £36.75

P&P £1



2035A Handheld DMM	Assm. £62	Kit £49
Similar Basic spec. as 2033 except able to measure down to 0.1µA AC/DC and 0.1Ω and with greater accuracy		
2015A Bench DMM	£83	£73
Similar Basic spec. as above except able to measure up to 10A AC/DC, with more facilities.		

P&P £1

FREQUENCY METERS: 8 digit LED

8110A 20Hz-100MHz	Assm. £67	Kit £56
8610A 20Hz-600MHz	£82	£68



8610A

FREQUENCY METERS: 9 digit LED

8610B 10Hz-600MHz	£99	£84
8000B 10Hz-1000MHz	£155	-

P&P £1

TOUCH AND HOLD PROBE:


for use with SABTRONICS Multimeters. Enables you to hold a signal on display.
THP 20 £13

I.C.E. Multitester

Specification

Volts DC	100mV-2000V
Volts AC	2V-2500V
Amps DC	50µA-10A
Amps AC	250µA-5A
Ohms	0.1Ω-100MΩ
Frequency	0-5000Hz
Capacity	0-20,000µF

Size with case
13.7cm x 10.4cm x 5.4cm

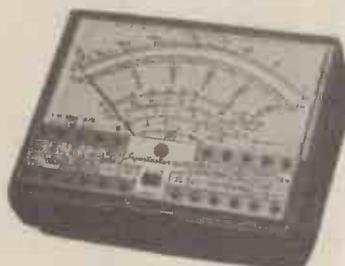

Only £32

P&P £1

SAFGAN British-made Scopes

- ★ DUAL TRACE
- ★ 5mV/Div sensitivity
- ★ XY facility
- ★ Z modulation
- ★ Calibration output
- ★ Portable/lightweight

DT410	10MHz	£179.00
DT415	15MHz	£185.00
DT420	20MHz	£198.00
X1-REF-X10 probe		£11.50

P&P £2



DAROM SUPPLIES

4 Sandy Lane
Stockton Heath
WARRINGTON
Cheshire WA4 2AY
Tel. 0925 64764

Add 15% VAT on ALL prices
All prices correct at 2-2-82 E&OE
ACCESS or BARCLAYCARD Welcome
Callers welcome Mon.-Fri., 9 a.m.-5.30 p.m.

Catalogue FREE

WW 044 - FOR FURTHER DETAILS



YC1000L

JOIN THE MICRO REVOLUTION WITH THE YC1000L DATA LOGGER

This new laboratory grade instrument features microprocessor control for increased versatility. Its many functions include - a frequency counter (0.02ppm accuracy), a precision AC/DC voltmeter, a thermal sensor and a programmable timer. The test results may be read direct from the digital display or recorded on the integral logger.

Price £725+VAT

PMR HIGHBAND

"COMPACT SMC1015L1"



The SMC1015L1 "compact" VHF highband transceiver is currently available ex-stock at realistic prices. Why pay more? We are satisfied that our standard of construction matches that of the leading names. Write for details:



South Midlands Communications Ltd.
Osborne Road, Totton
Southampton SO4 4DN, England.
Tel: Totton (0703) 867333
Telex 477351 SMCOMM G

WW - 052 FOR FURTHER DETAILS

MICRO TIMES

19 Mill St., Bideford, North Devon
EX39 2JR, England (WWM)
Telephone Bideford (023 72) 79798

ORDERING INFORMATION
Please add 50p P&P plus 15% VAT to all orders.
EXPORT ORDERS
Add 15% P&P
VAT not applicable



ACCESS/BARCLAYCARD WELCOME
Schools, Univ., Official Orders welcome.
All items brand new, full spec.

EPROMS	
2708 450ns	£2.30
2716 5v 450ns	£2.45
2732 Intel type	£6.00

NEW ELECTRONIC DRUM KIT	
6 programmable rhythms, 5 instruments: Snare, hi-hat, tom-tom, cymbal, bass drum. Optional stereo output	£23.95

CMOS AND 74LS SERIES AVAILABLE AT COMPETITIVE PRICES ON REQUEST	
---	--

MEMORIES	
2114 450ns	£1.20
2114 300ns	£1.20
TC5514P 450ns	£3.50
4 K C m o s R A M (1K x 4)	
4116 200ns	£1.20
4116 150ns	£1.35
5101	£3.00
HM6116-3 (16K, 150ns)	£8.00

KITS FOR BEGINNERS	
Wheel of Fortune	£5.00
Ultronic Fly Repeller	£4.50
Light Activated Switch	£3.75
ANTEX SOLDERING IRONS	
Model CX 17W	£4.80
KR SK1 15W	£8.50
Incl. Base, stand, solder	
KIT SK3 17W	£6.50
KR SK4 25W	£8.50
MLX Repair Kit	£5.30
Spare Bits, each	60p

Intersil ICL7660 Volt. Converter	£2.00
----------------------------------	-------

AY-3-8910 C11 SOUND COMPUTER CHIP Special Price	£8.95
---	-------

ELECTROWARE DISTRIBUTORS Tools, kits, boards, etc. Catalogue available. Please send 30p P&P	
---	--

COMBO CHIP (280)	
MK3886 2 1/2 meg.	£19.50
Data £1 (26p S.A.E. please)	
CPU's	
6502	£4.95
6504	£8.20
6802	£5.70
6809	£15.00
8080A	£3.50
8085A	£5.00
Z80	£4.00
Z80A	£4.80

TILs	
TIL32	45p
TIL209 red	10p
TIL232 green	18p
TIL212 yellow	16p
TIL216 red	18p
TIL218 red	20p
TIL220 red	12p
TIL224 yellow	18p
TIL311	£5.25
TIL 312-3	£1.00
TIL321-A	£1.15
TIL 330A	£1.15

6809 SINGLE BOARD COMPUTER KIT	
IEEE S-100 STANDARD Complete Kit plus 15% VAT I1 P&P	£175
Bare Board	
Uses 6809, 6850, 6821, AD5MON (2716) DATA AVAILABLE ON S.A.E. please	£48

S-100 KLUGE CARD SIMPLIFY YOUR PROJECTS WITH A PROTOTYPE BREADBOARD WITH EXTRAS! Bare Board & Manual £33 Delivery: 2 weeks	
--	--

SUPPORT DEVICES	
6520	£3.10
6522	£5.00
6532	£7.70
6810	£1.35
6821	£1.70
6845	£10.00
6850	£1.75
6852	£2.45
8212	£1.30
8216	£1.70
8228	£3.80
8255	£2.95
Z80 CTC	£4.00
Z80 PIO	£4.00
Z80ACTC	£4.00
Z80APIO	£4.50
Z80 DMA	£11.50
Z80ADMA	£14.00
Z80 S10/0	£13.50
Z80AS10/0	£14.50
Z80 S10/1	£14.50
Z80AS10/1	£14.50
Z80S10/2	£13.95
Z80AS10/2	£14.50

LOW PROFILE DIL SOCKETS	
8 pin	8p
14 pin	11p
16 pin	12p
18 pin	15p
22 pin	22p
24 pin	24p
28 pin	26p
40 pin	29p

FLOPPY DISC CONTROLLERS	
FD1771	£19.50
FD1791-2	£32.00
WD1691D	£14.50
WD2143-01	£5.00
SPECIAL Complete package includes FD1791-2 + W D 1 6 9 1 D + WD2143-01 £50 Set data available £3 (26p S.A.E. please)	

S-100 PROM BLASTER PROGRAMS MOST FAMILIES OF EPROMS! BARE BOARD PROMWRITER KJT	
Incl. all parts, sockets and Promwriter Del. 2 weeks.	£49
Promwriter	£40
KJT	£175



VERO PRODUCTS VEROBLOC S100 Prototyping Boards: Microboard pattern 06-2175L	
Sq. ad. Universal Patt. Prototyping Board for Apple II 2020	£17.95
Other Vero Products available on request.	£3.15

VOLTAGE REGULATORS	
100mA 78L05 5v	29p
78L12 12v	29p
7805 5v 500mA	
7812 12v 50p	79M12 12v 60p
7905 5v 55p	79M05 5v 60p
7912 12v 55p	723 31p

WW - 022 FOR FURTHER DETAILS

Data recording and analysis:

meet the time shrinker!

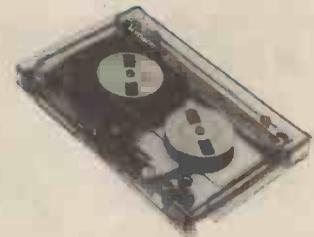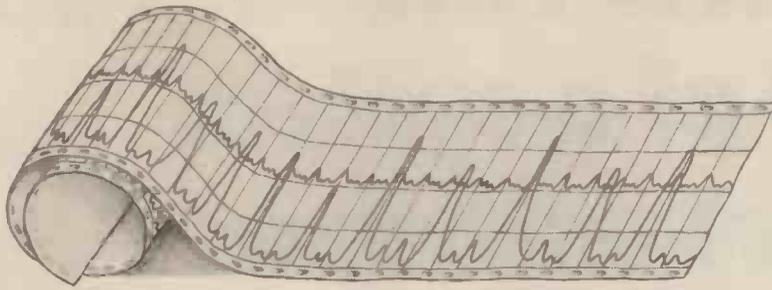

If you need to record and analyse data from multiple inputs, consider the advantages of using the Microdata M1600L data logger.

Magnetic tape cartridge Because it records on a standard 1/4 inch magnetic tape cartridge in ECMA/ANSI format, the output can be replayed at high speed into a computer, calculator or other data processing equipment. Alternatively, the internal replay facility of the data logger can be used. *No other data logger has this capability.*

Individual conditioning cards Individual, plug-in signal conditioning cards are used—one for each of the 20 input channels (expandable up to 100). As a result, each customer receives a bespoke instrument ready to handle mixed

analogue and digital inputs from most transducers. Cards are available at low cost to condition virtually every type of electrical signal, to reconfigure the instrument for different projects. *No other data logger offers these facilities.*

Exceptional versatility The M1600L is available either as a mains powered, free-standing, laboratory instrument or in the portable weatherproof form operating from its internal batteries. For more permanent installation in existing systems, it can be supplied in chassis form for mounting in a 19 inch rack. *No other data logger displays this versatility.*

The M1600L is now widely adopted for projects in energy, transportation, agricultural and environmental research. If you would like further details, please

write, telephone, or return this advertisement clipped to your letterheading.

MICRODATA LIMITED, MONITOR HOUSE,
STATION ROAD, RADLETT, HERTS. WD7 8JX.
ENGLAND. Telephone: RADLETT (09276) 3333.
Telex: 924937.



MICRODATA leaders in the field

WW - 055 FOR FURTHER DETAILS

JOIN THE PROFESSIONALS...

If you are looking for amplification, take advantage of the same superb quality Crimson modules that the BBC, IBA, KEF and numerous recording studios have been using for years! Our expertise in this field of electronic design is internationally renowned, our reputation is based on quality, reliability and value for money and when it comes to technology, our modules feature possibly some of the world's most advanced audio circuitry yet devised. The Crimson range of audio amplifier modules is available to industry and public alike and is backed by full technical data, free technical advisory service, fast delivery and a full range of complimentary components available such as toroidal power supplies and heatsinks, etc.

SPECIFICATIONS

Type	O/P 8 ohms*	O/P 4 ohms	PSU	H/sinks	Slew limit	S/N	Sensitivity	THD (typ)	FR (-3dB)	Size
CE 608	38	—	CPS 80	H550	30VuS	110dB	775mV	0.0035%	1.5Hz—50KHz	80—120—25
CE1004	44	70	CPS150	H550/100	30VuS	110dB	775mV	0.0035%	1.5Hz—50KHz	80—120—25
CE1008	65	—	CPS150	H550/100	30VuS	110dB	775mV	0.0035%	1.5Hz—50KHz	80—120—25
CE1704	85	121	CPS250	HS100/150/FM1	30VuS	110dB	775mV	0.0035%	1.5Hz—50KHz	80—120—25
CE1708	125	—	CPS250	HS100/150/FM1	30VuS	110dB	775mV	0.0035%	1.5Hz—50KHz	80—120—25
CE3004	170	250	CPS250	HS150/FM2	30VuS	110dB	775mV	0.008 %	1.5Hz—50KHz	161—102—35
CPR1X	output	775mV	REG1	—	3VuS	70dB	2.8mV	0.008 %	10Hz—50KHz	138—80—35
MC1X	output	2mV	REG1	—	3VuS	65dB	70/150uV	0.008 %	10Hz—50KHz	80—120—35
XO2/3	output	775-2500mV	REG1	—	9VuS	90dB	775mV	0.01 %	Preset	150—50—20

* Power output is quoted in WRMS and is given for two modules off the same power supply. Higher powers can be obtained if using our dual power supplies or one module per PSU or if using a stabilised power supply.

Crimson modular audio amplifiers feature
 * low values of transient and steadystate distortions
 * envelope distortion (below 500 Hz) less than 0.05%
 * on board electronic protection
 * PCB pin and edge connector termination
 * full range of complimentary components available i.e. PSUs, heatsinks, etc.

NEW: We now have a completely new Hi-Fi Kit package to offer:
CK 1010 contains pre-amp circuitry, all metalwork, connectors, wire, etc., to make a complete pre-amplifier.

CK 1040 contains power amp modules, all metalwork, dual power supply, connectors, heatsinks, wire, etc., to make a complete 40 w/channel power amplifier.

CS 1100 as CK 1040 but at 100 w/channel
 Unlike other module manufacturers CRIMSON have a major share of the esoteric, specialist Hi-Fi market. Unlike many manufacturers we acknowledge the massive audible differences that small component/circuit changes can produce. However our amplifiers are technically outstanding and have been subjectively 'tuned' to a stunning level of crisp and detailed reproduction.

PRICES

Power amp modules

CE 608	£21.00
CE1004	£24.50
CE1008	£27.50
CE1704	£35.00
CE1708	£35.00
CE3004	£49.00

Power supply modules

CPS80	£26.24
CPS80D	£31.77
CPS150	£29.74
CPS150D	£36.40
CPS250	£36.83
CPS250D	£45.34

Heatsinks

H5 50	£1.84
HS100	£2.99
HS 50	£4.20
FM1	£36.95
FM2	£41.52

All prices include VAT. Please add £1.10 for orders up to £20.00, £2.50 up to £50 and £2.65 £50 and over. To allow for post and packing (UK only).

Export—No problem. Please write for quotation or quote your Visa/Master-Card number.

Pre amp modules

CPR1X	£36.00
MC1X	£32.00
REG1	£ 9.30
TR6	£ 3.30

Active crossovers

XO2	£ 3.30
XO3	£ 3.30
MU1	£ 3.30

COMPLETE KITS

PRE-AMP CK1010	£90.00
POWER AMP CK1040	£119.00
POWER AMP CK1100	£149.00
(MOVING COIL ADD-ON)	£25.00



Please send more details of all CRIMSON ELEKTRIK amplifier modules

Name _____
 Address _____
 Ref. _____
 WWW/4

Crimson Elektrik

9 Claymill Road, Leicester LE4 7JJ · Tel 0533 761920 · Telex 34964 Chamco G Crimlek

Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



New BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

Kit: £49.⁹⁵

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.




Built: £69.⁹⁵

Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

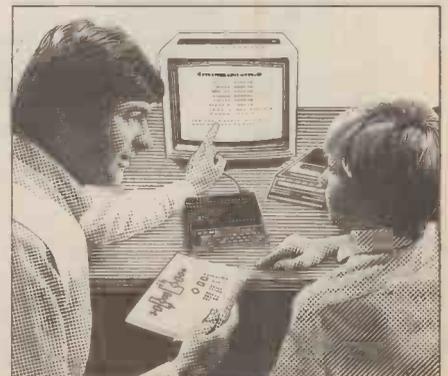Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



ter-



Available now - the ZX Printer for only £49.⁹⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha-numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software - the Business & Household management systems for example.

How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call

01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.

Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £ _____

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ _____

*Please charge to my Access/Barclaycard/Trustcard account no. _____

*Please delete/complete as applicable. _____

Please print.

Name: Mr/Mrs/Miss _____

Address: _____

FREEPOST - no stamp needed. Offer applies to UK only.

WRW 04

sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: (0276) 66104 & 21282.

WW - 012 FOR FURTHER DETAILS

**FAST
ERECTING**

CLARK MASTS

25
years in this
specialist
field


Here is the expertise you can depend on

When you choose a mast from the comprehensive Clark range you are assured of a high standard of engineering and operational reliability.

Why compromise?

Extended heights 4 metres-30 metres, capable of lifting headload 1 kg-200 kg. Sectional or telescopic air operated for field or vehicle mounting. Write or phone us for details today.

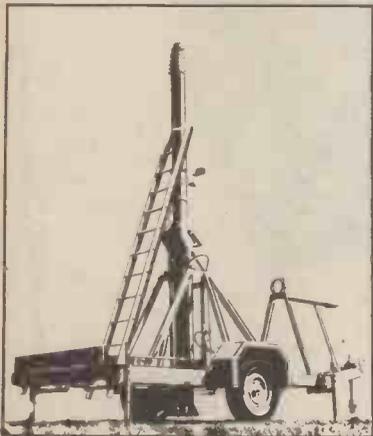63/70 Trailer-mounted Mast - The ideal 21 metre mobile communication HQ Mast, capable of supporting a headload of 40 kg at its maximum height of 70 ft.



CLARK MASTS LTD, Binstead, Isle of Wight, PO33 3PA, England, Telephone (0983) 63691. Telex 86686.


WW - 017 FOR FURTHER DETAILS

SAFGAN DT-400 Series BRITISH MAKE DUAL TRACE 'SCOPES

**NEW
20MHz**

LOW COST

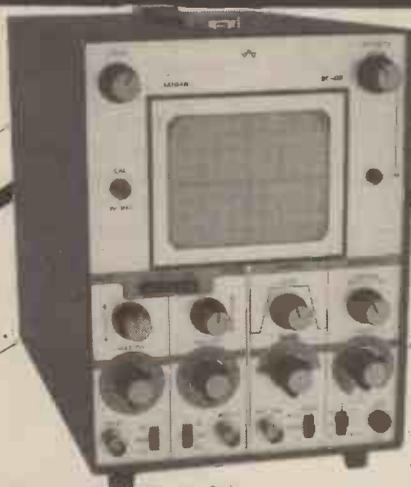DT-410 £179*
DT-415 £189*
DT-420 £199*
* Ex V.A.T.



**RELIABLE
WITH
18 months
GUARANTEE**

DT-410, 10 MHz DT-415 15MHz DT-420 20MHz

- ★ CH1, CH2: 5mv/div - 20v/div.
- ★ Time Base: 1 sec/div - 100ns/div.
- ★ XY Facility: Matched XY inputs.
- ★ Trigger: Level control, ± Slope selection.
- ★ Auto, Normal, TV Triggering.
- ★ External Trigger
- ★ Z-Modulation.
- ★ CAL output 1v 1kHz.
- ★ Graticule blue ruled 8x10 div. (4in. CRT)
- ★ Size: H215mm, W165mm, D280mm.
- ★ Weight: 4kg.

PROBE (XI-REF-X10) £11.50

SAFGAN ELECTRONICS LTD.

OMEGA ROAD, WOKING, SURREY TEL. WOKING (04862) 69560
Carriage: England & Wales £7.50 + V.A.T.; Scotland £10.50 + V.A.T.






London Stockist: Audio Electronics - Tel: 01-724 3564
North-West Stockist: Darom Supplies, Warrington, Ches. - Tel: Warrington 64754
Avon Stockist: L. F. Hanney, Bath - Tel: Bath 24811
Cardiff Stockist: Steve's Electronics Supply Co., Cardiff - Tel: (0222) 41905
Chesterfield Stockist: Kays Electronics, Chesterfield - Tel: (0246) 31896
Newcastle Stockist: Aitken Bros. & Co., Newcastle - Tel: 0632 26728
Birmingham Stockist: P.A.T.H. Electronic Services - Tel: 021-327 2339
Derby Stockist: RTS, Derby - Tel: (0332) 41235

WW - 040 FOR FURTHER DETAILS



LOW PROFILE KEYBOARD SWITCHES

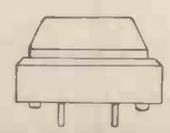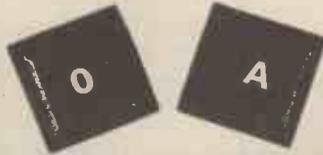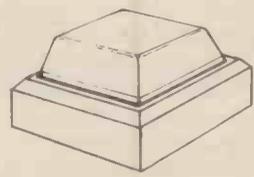

GOLD PLATED, FIVE MILLION OPERATIONS

- CMOS TTL TRANSISTORS LEDs
- RESISTORS DIODES SWITCHES
- POTENTIOMETERS CONNECTORS MULTIMETERS

Full details on all these items and more in our
NEW TRADE CATALOGUE, OUT NOW!!

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex. SS0 7JX
Tel: Southend (0702) 32338

WW - 053 FOR FURTHER DETAILS

The Thinking Cap



Now you can measure, sort and check capacitance in less time, with more accuracy.

The new 3001 Digital Capacitance Meter is yet another superb instrument from G.S.C. Designed specifically for professional laboratories, test and production benches, it offers outstanding accuracy with features and accessories to match. All in a well designed, rugged unit for only £165*.

As usual, we continued where everyone else left off. Behind the 3½-digit LED display is a unique Dual Threshold circuit that gives an accuracy of 0.1% of the reading (0.5% in the two highest ranges). Other features include nine overlapping ranges, up to 0.1999 F, with down to 1pF resolution, automatic over and under-range indications, and the 3001 isn't fooled by dielectric absorption. Once the range is selected, measurement is speedy — less than half a second!

Our back panel has more facilities too. An easy interface for remote display, sorting and control accessories, and, to eliminate battery problems an AC mains input.

A great deal of thought has been put into the accessories which include a production test fixture, a Limits Unit, a variety of test cables, and an extremely comprehensive manual covering not only measurement on capacitors but also applications to testing other types of components and even cables.

The 3001 Digital Capacitance Meter. The only one worth thinking about.

* price excluding P&P and 15% VAT.

Tomorrow's tools for today's problems

GLOBAL SPECIALTIES CORPORATION



G.S.C.(UK) Limited,


Dept. 7FF, Unit 1, Shire Hill Industrial Estate
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682 Telex: 817477

G.S.C. (UK) Limited, Dept. 7FF, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.			
Model 3001	Digital Capacitance Meter	Unit price inc. P&P 15% VAT £193.20	Qty Reqd <input type="checkbox"/>
Name _____		Address _____	
I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/			
American Express card no. _____		exp date _____	
FOR IMMEDIATE ACTION — The G.S.C. 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately.			for FREE 21 catalogue tick box <input type="checkbox"/>

WW - 061 FOR FURTHER DETAILS

**When your
Two Way Radio
supplier is
acting like
a monkey,
the complete
Zycomm range
will put him in
the background**

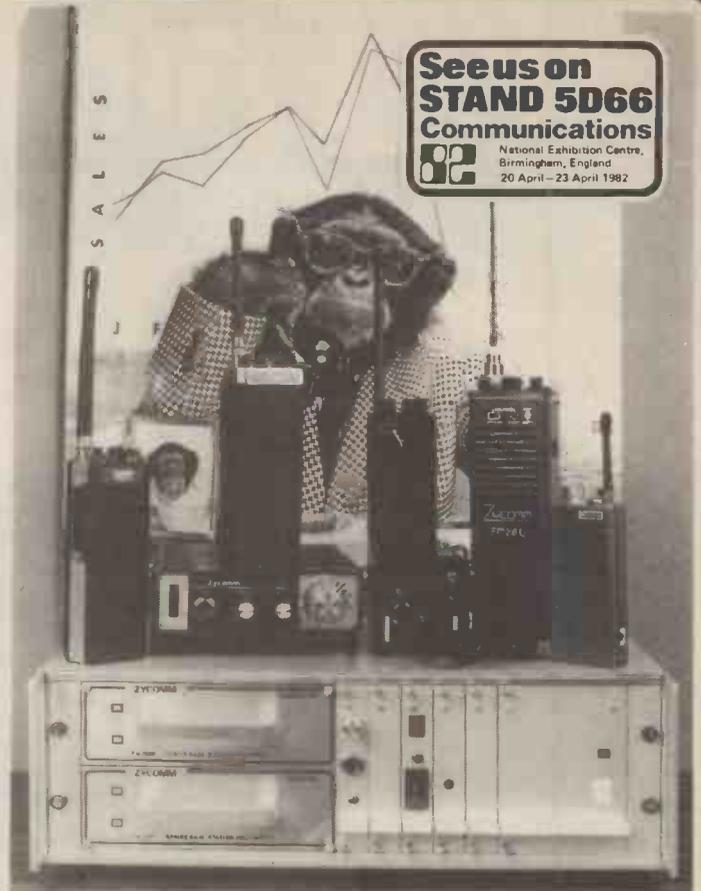ZYCOMM ELECTRONICS LIMITED
47/51 Pentrich Road, Ripley, Derby DE5 3DS
Tel: Ripley (0773) 44281 Telex: 377477



**See us on
STAND 5D66
Communications**
National Exhibition Centre,
Birmingham, England
20 April - 23 April 1982

Agencies available throughout the UK and the World

WW - 078 FOR FURTHER DETAILS

IRVINE BUSINESS
SYSTEMS LTD

IBS

NEW PRODUCTS

I.B.S. now manufacture Industrial quality S100 products in Scotland.
I.B.S. 1903 and 1906. S100 19" Sub Rack System.
These racks were designed originally to the exacting specification of the Electricity Generating Board for use on nuclear power stations.
1903 is a 3U high card cage and 8-amp power supply and will take 6 S100 cards.
1906 is a 6U high card cage and 16-amp power supply and will take 12 S100 cards.
★ IEC mains connector, filter, fuse and tap change switch on rear panel.
★ Key operated ON/OFF/RESET for maximum security.
★ Heavy duty painted front panel.
★ Carrying handles.
★ Supplied assembled complete with Power supply, IEEE (696) motherboard, card guides, and cooling fans.

I.B.S. 1903 £299.00
I.B.S. 1906 £399.00
6-slot Card cage, card guides, mother board and fan £119.00
12-slot Card cage, card guides, mother board and fans £249.00

I.B.S. 64K CMOS Static RAM/PROM Board for S100.
This is a superior quality Ram/Prom board for the industrial user, the board will accept either H6116-3 (2K x 8) Ram chips or 2716 EProm in any combination.

- ★ S100 IEEE (696) Compatible.
- ★ 24 Bit Addressing.
- ★ Can be used with any CPU.
- ★ Prom/Ram selectable on 2K boundary.
- ★ Prom/Ram can be disabled to suit popular memory mapped devices.
- ★ Low power.
- ★ Will run at 6Mhz with standard Rams.
- ★ Wait state generation for Proms.
- ★ Phantomable.

PRICES:

BARE BOARD Assembled/ tested £65.00	16K	32K	48K	56K	64K
	£179.00	£239.00	£299.00	£329.00	£359.00

Educational and industrial discounts available.

SOFTWARE SALE (whilst stocks last).

Microsoft Basic 80	WAS £175	NOW £149.00
Microsoft Basic Compiler	WAS £180	NOW £159.00

Introductory offer

MicroPro CALC STAR	WAS £175	NOW £149.00
--------------------	----------	-------------------

- ★ Visit our stand at the Thames Valley Business Show, on 23/24/25th March '82
- ★ Stand H50/51
- ★ The Fulcrum Centre
- ★ Slough

The above prices exclude VAT at 15%

IRVINE BUSINESS SYSTEMS LTD.


 P.O. BOX 5
10 NORTH VENNEL
BOURTREEHILL
IRVINE
AYRSHIRE KA11 1NE

TEL. 0294 218888
Telex 777582
Mark: attn. IBS



NEW Quality Bench Power Unit Kit

Fully punched, two colour steel case

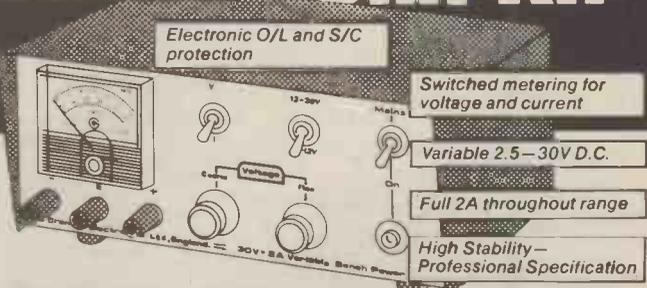

Build yourself this professional specification bench power unit. You will have a development tool as good as units sold to research laboratories and industry at more than twice the price.

The Kit comes complete with pre-punched, painted and silk-screened steel case, full assembly and setting-up instructions and every item necessary to complete the unit as shown.

£35.00
+ £3.35 post and packing
+ £5.75 V.A.T. Also available fully built up and tested at £59 + £3.35 post and packing + £9.35 V.A.T.

Allow 14 days delivery
Send cheque or Postal Order to:

 **GRENSON ELECTRONICS LIMITED**
High March Rd, Daventry, Northants,
NN11 4HQ. Telephone: 03272 5521

WW - 071 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1982

AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT
INDUSTRIAL-EDUCATIONAL

LONDON'S TEST EQUIPMENT CENTRES

CALL IN AND SEE FOR YOURSELF
OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY



**GROTECH 3035
10 MHz Scope
Plus Component
Tester**

5" - 130mm Flat Face
Tube DC - 10 MHz
5mV/DIV 220/240V AC Trig. to 20 MHz

SAVE £21 PLUS

As advertised by us at £189.75 inc. VAT
NOW £168.50 Inc. VAT
(UK c/p £3.50) Exclusive to Audio Electronics


**PROFESSIONAL 100 K OHM/VOLT
MULTIMETER**

30 ranges 15A AC/DC
1.5 KV, 200 meg ohms.
Features mirror scale,
polarity reverse, electronic
overload protection, taut band
suspension.

As advertised by us at £67.50
+ case i.e. £84.00

NOW £49 Inc. VAT
(UK c/p £1.50) with leather case
Exclusive to Audio Electronics

SAVE £35

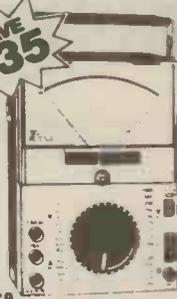

LCD LOW COST MULTIMETERS

DD601 3 1/2 digit LCD 26 range push button 2A
AC/DC 20 meg ohm Basic 0.5% £37.95
HC703 0.1% version of above £54.00
DM6011A/18mm 3 1/2 digit LCD 15 range push
button plus Hfe Tester 10A DC (No AC A) £43.50
18mm 3 1/2 digit LCD 30 range Rotary switch plus
Hfe Tester 10A AC/DC £69.95

Callers will always find a range of low cost test
equipment, accessories, tools, irons and
boards in stock, also special offers for certain
equipment which will vary from time to time.

Price correct at time of preparation E&OE
All prices include VAT

CHOOSE FROM UK'S LARGEST RANGE

STOP PRESS Few only 6110 23 range 10A AC/DC, range
hold, continuity buzzer plus much more Rotary Switch
£59.95



SABTRONICS EQUIPMENT NEW LOW PRICES!!


New reliable range of DMM's and
frequency computers with those
extra facilities and competitive
prices. All battery operated
(supplied). Except 5020A mains.
Optional mains eliminators available.
8 DIGIT COUNTERS 0.1 HZ to 10 HZ Res.
10mV sensitivity to 100 MHz
(UK c/p £1.00)
8110A 20 HZ-100 MHz in 2 ranges
£77.00
8610A 20 HZ-600 MHz in 3 ranges
£94.00
9 DIGIT COUNTERS 30mV sensitivity
to 1GHz. Resolution 0.1 HZ-10 HZ
8610B 10 HZ-600 MHz in 3 ranges
£113.85
8000B 10 HZ-1GHz in 3 ranges
£178.00
2015A LCD version of above £95.00
(c.p 2035/37A 6Sp: All others £1.00)

FUNCTION GENERATOR (UK c/p £1.00)
with mains adaptor
5020A 1 HZ-200 KHZ Sine/Square/
Triangle/TTC Freq. sweep. Low
distortion £90.00
DIGITAL MULTIMETERS Two LCD
hand held - one with temperature
range. Also LCD and LED Bench
models. 0.1% basic accuracy.
2035A 3 1/2 digit LCD hand 2A AC/DC
20Meg ohm ETC £71.00
2037A As 2035A with -50°C to
+150°C Temp. range 0.1°C
resolution £77.00
2010A 3 1/2 Digit LED. Auto decimal &
minus. 10A AC/DC. 20Meg ohm etc.
£81.50
THP 20 Touch and Hold optional
probe for DMM's £14.95




HAMEG OSCILLOSCOPES

Range of top quality scopes for Amateur and
Professional (UK c/p 307" £3.00, other £4.00)
307 Single trace 10 MHz, 5mV: 0.5 micro sec. Plus built in
component tester 6 x 7cm display
(Optional carry case £18.40) £158.70
203 Dual 20 MHz: Trig to 30 MHz 5mV: 0.5 micro sec.
8 x 10cm display (replace model 312) £253.00
412-5 Dual 20 MHz delayed sweep: trig to 40 MHz: 5mV
0.1 micro sec 8 x 10cm display. £402.50
705 Dual 70 MHz. Delayed sweep: Single sweep: Delay
line: Trig to 70 MHz: 2mV: 0.1 micro sec. 8 x 10cm display
£667.00
Options 203/412/705 Viewing hood £6.90
Component tester 203, 412, 705 £29.95!
Carry case (state model) £21.85
Optional Probes (All models) X1 £7.95: X10 £9.45
X1-X10 £10.50: X100 £16.95
HZ65 Add on component tester - Any Scope £29.95

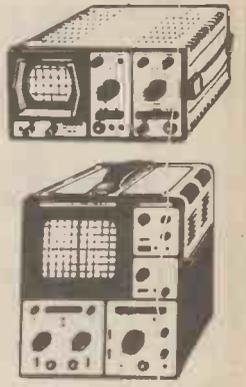

RF AND AUDIO SIGNAL GENERATORS Mains operated
(UK c/p £1.00) Audio 20 HZ-200 KHZ 4 band. Sine/Square o/p

TE220 Distortion max 1% £69.95
LAG26 Distortion 0.5-1% leader £73.70
LAG120A 5 range 10 HZ-1 MHz. Size/sq. 0.05-0.8% DIS £146.00
LAG125 Low distortion version of LAG120A 0.02% £273.00
AG202A Distortion 0.5-1% Trio £8.20
AG203 10HZ-1 MHz 5 band max distortion 0.1% Trio £126.50
RF All feature Int/Ext. MOD. Variable output £59.95
TE200 100 KHZ-100 MHz 6 band (300 MHz harmonics) £63.25
LS616 100 KHZ-100 MHz 6 band (300 MHz harmonics) Leader £68.00
SG402 100 KHZ-30 MHz 6 band professional trio

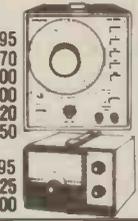

**VARIABLE AND FIXED
POWER SUPPLIES**
(UK c/p £1.00 any model).

SPECIAL PURCHASE
1205 13.8v 5 to 7 amp £12.95
*PP241 0/12-12-24V 0/1 amp £35.00
*PP243 0/12-12/24V 0/3 amp £59.95
*RP154 5-15V 0/3 amp £49.95
*meter display



**THURLBY DIGITAL
MULTIMETER MODEL 1503**



4 1/2 Digit. 0.05% 7 Function LCD
30 ranges: 1200V DC, 750V AC, 10A AC/DC, 132 Meg
ohm. Also includes frequency measurement to 4
MHz and 4 KHz output.
Made to exacting standards in the UK.
Price is with batteries, test leads and mains
adaptor.
(optional carry case £20.45) £171.00
UK c/p £1.00

**AMATEUR/CB
TESTING** - Full lists send SAE

KDM6 1.5 to 250 MHz 6 range
DIP meter £47.95
HM20 20K/VOLT multirange
multimeter. Plus SWR/Power
meter 150 MHz £28.95
RC1000 0/10/100/1000 watts
SWR etc. 150 MHz max. £52.50
MJ666A 10 ch. Pocket 2 metre
scanner £69.00
MJ666M Marine band version
£69.00
UH74 SWR 0/10w Power.
0/50/144/430 MHz tester. £21.00
FC100M 12V 100 MHz Freq.
Counter £89.95




**SPECIAL CB ACCESSORY
PURCHASES (Post 55p)**

CB20 SWR/Power twin meter to
30 MHz, 1Kw £11.95
175 SWR/Field strength/aerial
matcher single meter £11.95
171 Twin meter SWR/Field
strength 0/10/100w
Power 144 MHz £11.95
1205G 13.8v 5 to 7 amp
regulated power supply
(post £1.00) £12.95

Just a selection of a huge range
in stock - send for latest lists
including professional ranges.

**PROFESSIONAL
MULTIMETERS**

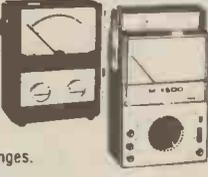(UK c/p £1.50)
All featuring AC/DC
Volts/Current & Ohms ranges.
M1500 43 range 20K/Volt: AC/DC 10A £67.50
M1200 30 range 100K/Volt: AC/DC 15A 200 Meg ohm. £49.00
K1400 26 range large scale 20K/Volt: 10A AC/DC,
20 Meg ohm: 5KV AC/DC £95.00
K200 39 range 10 Meg ohm input. 25 HZ-1 MHz £105.00
OPTIONS Cases: M 1500 & 1200 £16.50: K 1400 £19.00
Temperature Probe for K1400 £16.00



**DIRECT READ
HV PROBE (UK c/p 65p)**

0/40KV: 20K Volt £18.40




SAFGAN PORTABLE OSCILLOSCOPES

Range of low cost Dual Trace Scopes mains operated. Made in UK to
exacting standards. Available as 10 MHz, 15 MHz or 20 MHz. All feature
5mV sensitivity, 0.5 micro sec. 6.4 x 8cm display (UK c/p £2.50)
DT410 Dual 10 MHz £205.85
DT415 Dual 15 MHz £217.35
DT420 Dual 20 MHz £228.85



MADE IN UK

OPTIONAL SCOPE PROBES - SEE HAMEG ABOVE

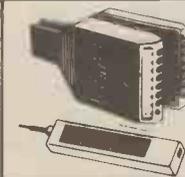

**LOGIC PROBES/MONITORS/PULSERS circuit
powered (UK c/p 60p)**

LP1 DTL/TTL/CMOS. 10 MHz: Pulse: Memory £35.50
LP2 DTL/TTL/CMOS. 1.5 MHz: Pulse: £19.95
LP3 DTL/TTL/CMOS. 50 MHz: Pulse: Memory £25.95
LM1 Logic monitor for 8 to 16 pin IC's £33.00
DP1 Digital pulser. Single or 100pps. £58.50
LDP078 50 MHz: 10Meg ohm: Logic Probe, with case £56.90

AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564
ALSO AT HENRY'S RADIO, 404/406 EDGWARE ROAD, LONDON W2

WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post
with CHEQUES/
ACCESS/VISA
or Telephone
your order
Allow up to 10 days
for delivery

FREE
CATALOGUE
Send large SAE
(20p UK)
Schools, Companies,
etc. free on request.

ALL PRICES INCLUDE VAT

Alley Electronics 762/763 * Alusett UK 827/828 * Amphol 322/323 * Amplicon Electronics 498 * Analog
 * BICC General Cables 772 * BICC-Vero Electronics 460-464/467/468 * B & R Relays 351 * Bahco Tools 228
 Circuits 764/765 * Britimpex 705 * British Central Electrical 575 * British Sonceboz Co 719 * British Standards
 dge Electronic Industries 650-655/662-664 * Capital Electronic Developments 742 * Capital (U-E) 500 * Ceidis 470
 Conductive Products 590 * Contraves Industrial Products 443 * CorinTech 774 * Corning 531 * Coutant Electronics
 Datacapture 834/835 * Data International 218 * Daturr 201/202 * S Davall & Sons 657 * Dean Electronics 665/666
 d Electronic Components 824/825 * Eaton 481 * Electrautom 136 * Electromatic 138 * Electrothermal
 Exacta Circuits 344/345 * FR Electronics 745 * Farnell Electronic Components 210 * Farnell Instruments 521

is now at The Barbican,
 Tuesday to Thursday, April 20 to 22.
 10 a.m. 'till 6 p.m. except Thurs.
 (When 5.00 p.m.)

1 Use this form if you're going to use our coaches...

They depart from the towns listed at 9 a.m.-ish. And they leave the Barbican between 5 and 6 p.m.

Please tick the appropriate boxes, return the form enclosing your cheque/P.O. made out to The All-Electronics/ECIF Show, and we'll send you full information (including the departure points, their nearby car parking facilities, luncheon alternatives, and so on).

If, by any chance, fewer than 30 people wish to journey from the town of your choice on the day of your choice, you'll get your money back a.s.a.p.

The cost includes the postage for a catalogue, a free season ticket. And we'll enclose a receipt.

"I require (insert quantity)

packages and enclose cheque/P.O.

for: £ _____

Name (please use clear capital letters)

Address _____

PRICES QUOTED ARE RETURN FARES

		Tues 20/4	Wed 21/4	Thur 22/4
AYLESBURY	£7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
BASILDON	£4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
BASINGSTOKE	£8.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
BEDFORD	£6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
BIRMINGHAM	£10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
BRENTWOOD	£4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
BRIGHTON	£4.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
BURY ST. ED.	£6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
CAMBRIDGE	£6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
CHELMSFORD	£4.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
COLCHESTER	£5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
COVENTRY	£9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
CRAWLEY	£4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
DARTFORD	£4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
DOVER	£5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
FARNBOR'GH	£6.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
GUILDFORD	£5.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
HARLOW	£4.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
HASTINGS	£4.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
HEMEL HEMP.	£5.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
HIGH WYCOMBE	£4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
IPSWICH	£5.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
KETTERING	£9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
KING'S LYNN	£10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
LEATHERHEAD	£5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
LEICESTER	£10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
LINCOLN	£9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
LOUGHBOR'GH	£11	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
LUTON	£5.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
MAIDENHEAD	£5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>



		Tues 20/4	Wed 21/4	Thur 22/4
MAIDSTONE	£4.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
MILTON KEYNES	£8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
NORTHAMPTON	£7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
NORWICH	£10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
NOTTINGHAM	£12	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
OXFORD	£4.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
PETERBR'GH	£8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
READING	£5.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
RUGBY	£8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
SLOUGH	£5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
SOUTHAMPTON	£10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
ST. ALBANS	£5.50	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
STEVENAGE	£7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
SWINDON	£6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
THETFORD	£8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
TUN' WELLS	£4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
WELWYN G.C.	£5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
WARWICK	£10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
WATFORD	£5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Post to 'The Show,' 34/36 High Street, Saffron Walden, Essex. 4776P

NOW POST YOUR FORM TO 'THE SHOW,' 34-36 HIGH STREET, SAFFRON WALDEN, ESSEX, CB10 1EP. ENQUIRIES: 0799 27137.

For the Barbican

Liverpool Street - and a seven-minute walk. Or take the Metropolitan or Circle Line tube from any of the rail termini to 'The Barbican' and it's a 1-minute walk! Your free ticket gives you all the details. Buses: 4, 277, 279 to Barbican underground station. 21, 43, 76 and 141 to Moorgate. Red Arrow 502 from Waterloo to London Wall.



2 Making your own way? Use this

Please attach a 20p stamp by its corner to cover postage and packing costs for your free season ticket to 'The Show.' Plus a 120-pp catalogue with full details of the event. And comprehensive details of the activities (seminars, receptions, etc.)

(please use clear capital letters)

PLEASE AFFIX STAMP BY ITS CORNER

Name _____

Address _____

4776P

3 If you're just going to turn up...

Well, admission is £1 without a ticket. We're open between 10 a.m. and 6 p.m. on Tuesday and Wednesday. But between 10 a.m. and 5 p.m. on Thursday. (This - and other - information goes with the ticket, so do ask for one now!)

PLUS AC Automation Components 760 * Ajax 565 * Ambar Components 412 & 413 * Cathodeon Crystals 650-655, 662-664 * Celab 373 * Cox 292 * Egan 650-655, 662-664 * Electronics & Power 420 * GMT Electronic Systems 118 * Gentech International 607 & 608 * Healey Meters 311 * I & J Products 221 * ITT Cannon 812 & 813 * ITT Semiconductors 829 * Lumberg UK 173 * MIT Engineering 103 * New Electronics 219 * Newmarket Microsystems 650-655, 662-664 * Ormed Ltd 160 * Plier International 246 * Precision Circuits 819 * Pye Borders & Pye Connectors 650-655, 662-664 * Raytheon Semiconductors 493 * Sellmark Electronic Systems 221 * Thurlby Electronics 100 * Vareloc 650-655, 662-664.

Organised from:
 34/36 High Street,
 Saffron Walden, Essex CB10 1EP.
 Telephone: (0799) 22612. Telex: 81653.



Component Systems 441/442 * Hypertek Connectors 474/475 * IC Master 424 * I & J Products 221 * ITT Components Group 800-803/ (UK) 306/308 * Intime Electronics 203 * Ivo Counters 206 * Jackson Brothers 775 * Joseph Electronics 795 * KCP 798 * Kelvin Impex * Lawtronics 113 * Lee Green Precision Industries 703/704 * Lemo (UK) 131/132 * Light Soldering Developments 822 * Linstead * MTL Microtesting 609/611 * McMurdo Instrument Co 721/723 * Mann Components 205 * Marconi Electronic Devices 571-573 * Marconi & John Minister Instruments 579/580 * Molex Electronics 410/411 * Mostek UK 768 * Mullard 613/620-623 * NSF 164 * National Microprocessor & Electronics Centre 315 * Nicon Electronics 491 * Pickering Electronics 659 * Plessey Circuits 701/702 * Plessey Connectors, Plessey Semiconductors, Plessey Wound * Print Services Bv 307/309 * Protech-BPL 499 * Protrotron 24' 380 * Pulsetek 586 * Pye Electro-Devices 667/668 * Pye Unicam 457/458 * Quadrant Meter Co 116 * Rainford Metals 529 * Rank Electronic Tubes 726 * Rectifier Modules International 348 * Redpoint 304 * Rendar 612 * E G & G Reticon 730 * Rifa AB 374/375 * Rittal 603-604 * Sealectro 341/342 * Selectronix 743 * Seltek Instruments 554/555 * Semelab 746/761 * Semicoms 744 * Semiconductor Specialists 223 * Semtech 821 * Sfe 525 * Spectronics Microsystems 576 * Sprague Electric 373 * Stealite Group 804/805 * Stocko (Metal Works) 818 * Stotron 98/99 * Suflex 776/777 * Superflexit-1

NEW

QUALITY OSCILLOSCOPES, THE RANGE FOR EUROPE!

HM307.4 £138

Y: Bandwidth DC-10MHz (-3dB) - Sensitivity 5mV-20V/cm ($\pm 5\%$)
 X: Timebase 0.2s-0.5 μ s/cm ($\pm 5\%$) - Triggering 2Hz-30MHz (3mm) - Built in component tester - Calibrator - Screen 6 x 7 - 1kV.

HM203 £220

Y: Bandwidth DC-20MHz (-3dB) - Sensitivity 5mV-20V/cm ($\pm 3\%$) - Dual trace
 X: Timebase 0.2s-40ns/cm incl. x5 Magn. - Trigger 3Hz-30MHz (4mm) - X-Y operation - Calibrator - Screen 8 x 10cm - 2kV.

HM412 £350

Bandwidth DC-20MHz (-3dB) Sensitivity 2mV/cm - 20V/cm ($\pm 3\%$) Timebase 40ns/cm Triggering DC - 40MHz (5mm) Algebraic Add., Sweep Delay, x5 Mag., Overscan Ind., Var. Holdoff, Single Sweep.

HM705 £580

Bandwidth DC-70MHz (-3dB) Sensitivity 2mV/cm - 20V/cm ($\pm 3\%$) Timebase 5ns/cm - 2.5s/cm - Triggering DC - 100MHz (5mm), Algebraic Add., Sweep Delay, x10 Mag. | Alt. Trigger, Trig. After Delay, CRT 14kV.

For free data sheets of the full range contact:

HAMEG

England
HAMEG, LTD.
 74-78 Collingdon Street
 Luton, LU1 1RX
 Tel: (0582) 413174/Telex: 825484


France:
HAMEG S.A.R.L.
 5-9, Avenue de la République
 94800 Villejuif,
 Tél: 678.09.98/Telex: 270705

West Germany:
HAMEG GmbH
 6 Frankfurt am Main 71,
 Ketsterbacher Str. 15-19
 Tel: 0611/676017/Telex: 0413885

Spain
HAMEG IBERICA S.A.
 Villaroel 172-174
 Barcelona-36
 Tel: 230.15.97

United States:
HAMEG, INC.
 88-90 Harbor Rd.
 Port Washington, N.Y. 11050
 Phone: 516-883-3837/516-883-6428
 TWX: 510 223 0889


Prices U.K. List Ex. VAT

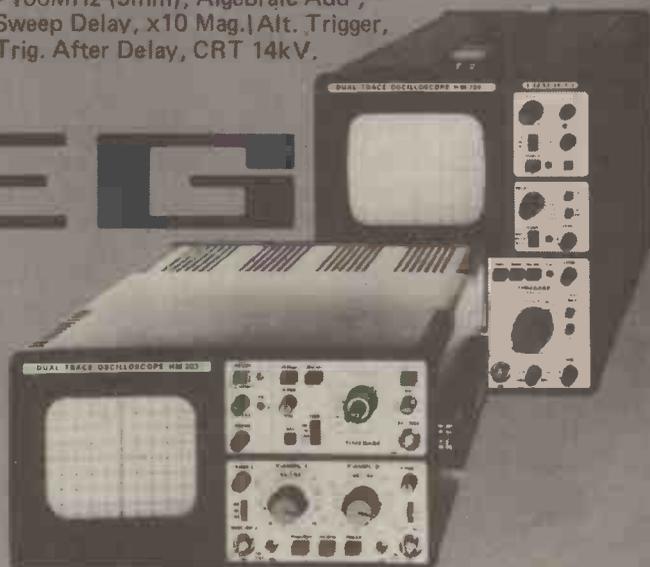

WW - 067 FOR FURTHER DETAILS

fagor

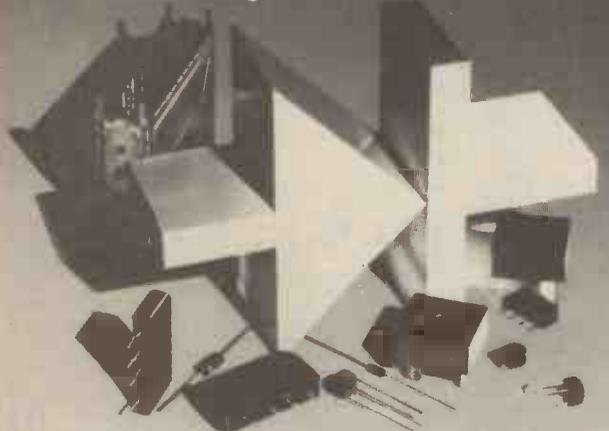Diodes-High Speed Diodes-Zener Diodes
 Rectifier Bridges-UHF VHF Tuners



Rectifier Diodes
 1A Series IN 4000
 3A Series IN 5400 and BY 251

High Speed Diodes
 1A Series BA 150 and 1P 640
 2A Series BY 290
 3A Series BY 390

Switching Diodes
 0.1A Series BA 243 - BA 243A

Zener Diodes
 500mW Series ZPD (2V7 - 51V)
 500mW Series BZK55C (5V1 - 62V)
 1.3W Series BZX 85C (5V1 - 62V)
 1.5W Series BZY97C (7V5 - 200V)

Rectifier Bridges
 0.8A Series C800, C800A
 1A Series C1000, C1000A
 1.5A Series C1500R
 1.5A Series C1500/1000
 2A Series C2000/1500
 3.7A Series C3700/2200
 5A Series C5000/3000
 10A Series FB1000, FB1000L
 25A Series FB2500

UHF/VHF Tuners
 *CCTR Standard
 *French System
 *RTMA System
 *Other Standards on Request

UK DISTRIBUTORS

Fieldtech Heathrow Limited
 Huntville House, 420, Bath Road,
 Longford, Middlesex, UB7 0LL, England.
 Telephone: 01 897 6446
 Telex: 23734 FLDTEC G

Fieldtech Heathrow

WW - 048 FOR FURTHER DETAILS

STABILIZER 4

APRS Stand 35
 June 23-25th




The Stabilizer is a high quality frequency shifter for howl reduction on speech and music. It offers variable shifts either up or down between 1 and 10 Hertz so allowing choice of the optimum shift for the particular acoustics and sound sources involved in each installation. Rack and box versions.

+5 Hz FIXED SHIFT CIRCUIT BOARDS as WW July 1973 article but improved noise level, lower distortion, adjustment-free oscillator and IC sockets; Mark 4. Small enough to be built inside the cabinets of many amplifiers. Complete kit and board £40. Board built and aligned £58. Including psu and mains transformer.

DESIGNER APPROVED. C.W.O. less 5% + VAT 15%.
 Stereo Disc Amplifier 2 & 3 * 10 Outlet Distribution Amplifier * PPM2 & PPM3 Drive Circuits and Ernest Turner Movements * Illuminated PPM Boxes * Peak Deviation Meter * Programme & Deviation Chart Recorders * Moving Coil Pre-amplifier * Broadcast Monitor Receiver 150kHz-30MHz.

SURREY ELECTRONICS, The Forge, Lucks Green, Cranleigh, Surrey GU6 7BG
 Telephone 04866 5997

UNIVERSAL BENCH POWER SUPPLY

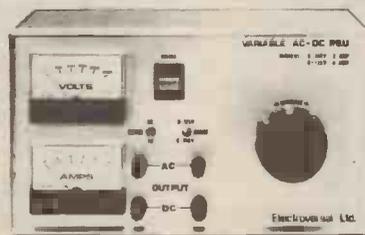

2 ranges:

0-125v @ 4amps

0-250v @ 2amps

AC or DC

Continuously variable.

£198.00

Exc. carriage and VAT.

Output is fused and mains isolated.

Electrovernal Ltd. 32 Portland Road, Luton, Bedfordshire LU4 8AX
 Telephone: Luton (0582) 54309

WW - 045 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1982

Carston

Used test equipment, calibrated to Manufacturer's original specification.

ACOUSTIC & VIBRATION

BRUEL & KJAER	
1621 Tunable Band Pass Filter	550
2113 Audio Frequency Spectrometer	1400
2203 Sound Level Meter	450
2215 Sound Level Meter inc. Oct. Filter	1050
2218 Sound Level Meter inc. Leq.	1475
2305B Level Recorder inc. 50 dB pot.	1350
2625 Vibration pick-up amplifier	350
2808 Power Supply/Mains Adapter	90
2972 Tape Signal Gate	200
4230 Sound Level Calibrator	95
4423 Noise Dosimeter	350
4424 Noise Dosimeter	375
CASTLE ACOUSTICS	
CS181 Sound Level Meter & Calibrator	295
C. E. L.	
112 Environmental Noise Analyser	300
144 Environmental Noise Analyser	500
DAWE	
419C Audio White Noise Generator	190
1461CV Vibration Analyser	350
1463B 1/2 Octave Filter	200
1465 Octave Band Filter	150
KISTLER	
504A Charge Amplifier	200
WAYNE KERR	
B731B Vibration Meter inc. probe	270

BRIDGES & V and I STANDARDS

ADVANCE	
T1 Q Meter 100 KHz-100 MHz	160
CINTEL	
2773 Inductance Bridge	160
HEWLETT PACKARD	
4261A Digital Automatic LCR Bridge	975
4342 QLC Meter 22 KHz-70 MHz	1600
MARCONI	
TF868A Universal LCR Bridge	250
MUIRHEAD	
D30A DC Bridge 0.15%	180
PHILIPS	
PM6302 RCL Bridge — direct reading	395
WAYNE KERR	
B224 RCL Bridge 0.1%	500
B521 LCR Bridge	115
B801/CU681/Q801/SR268 VHF Admittance Bridge with source and detector transistor adapter & D.C. Control Unit for transistor measurements	750

COMMS & CABLE TEST EQUIPMENT

DYMAR	
BC282 Battery charger for 883 Radio Telephone	80
883 Radio Telephone — VHF band — hand held	245
HEWLETT PACKARD	
3556A Psophometer 20 Hz-20 KHz	250
MARCONI	
TF2809 Data Line Analyser	600
NORTHEAST ELECTRONICS	
TT537B Psophometer/VU Meter	200
SEIMENS	
U2033 Psophometer	475

Carston Electronics Ltd
01-267 5311

Shirley House, 27 Camden Road, London NW1 9NR. Telex: 23920.

Prices from £

S.T.C.

74184B Selective Level Measuring Set	600
74216A Noise Generator	300
74261A Psophometer	300
74262B White Noise Generator & Receiver	2000
74307C Level Measuring Set	175
74834C Distortion Measuring Set	500
96016 Selective Null Detector	200
GTA-2 Quantization Distortion Tester	800
GTA4B Pattern Generator	900

TEKTRONIX

1502 TDR Cable Tester CRT + Recorder	2950
--------------------------------------	------

COMPUTER EQUIPMENT CENTRONICS

702 matrix printer	500
--------------------	-----

TEKTRONIX

4610-1 Hard copy printer for 4010 series computer display terminals	1800
---	------

Prices from £

DIGITAL TESTING EQUIPMENT

HEWLETT PACKARD	
1600A Logic Analyser 16 ch 20 MHz	1400
1600S Logic Analyser 32 ch 20 MHz	2250
1602A Logic Analyser 16 ch 10 MHz	900
1607 Logic Analyser 16 ch 20 MHz	950
TEKTRONIX	
832 Datacom Tester R5232/V24	1150
833 As 832 plus BERT/BLERT feature	1300
7DOIF/DFI Logic Analyser/Formatter 16 ch 50 MHz P/in	2650
7603/7DOIF/DFI As above with display mainframe	3600

MAINS TEST EQUIPMENT

COLE	
T1007 Volt/Freq/Spike Monitor Rec O/P	110
DATALAB	
DL019 Mains Interface for DL905	300

Prices from £

PM 6455 Stereo FM Generator
PM 6456 Stereo FM Generator
RESEARCH INSTRUMENTS
Micro manipulator — 4 Probes moveable in all planes. Adjustable test table — Watson Barnett optics. Complete system mounted in perspex enclosure

ROHDE & SCHWARZ
BN252 Transistor Y Parameter Test Set
S. T. C.

74600J Attenuator 0-9 dB 50Ω in 1 dB steps
74616A Attenuator 0-100 dB 600Ω in 0.1 dB steps

TEKTRONIX
521PAL Vectorscope
528 TV Waveform Monitor
575 Semiconductor Curve Tracer
1485C TV Waveform Monitor PAL/NTSC

YELLOW SPRINGS
YS157 Water Pollution Measurement System

NETWORK ANALYSERS/ PHASEMETERS

GENERAL RADIO
1710/11/12/14 0.4-500 MHz 115 dB range
HEWLETT PACKARD
8405A Vector Voltmeter 1-1000 MHz
8414A Polar Display for 8410 N.W.A.
8745A S Parameter Test Set 0.1-2 GHz
11570A Accessory Kit for 8405A
11600A Transistor Test Fixtures TO18/TO-72
11602A Transistor Test Fixtures TO5/TO-12
11604A Universal extension arm for 8745A
11605A Flexible arm for 8743A

OSCILLOSCOPES & ACCESSORIES

CROTECH
(New CROTECH Oscilloscopes)
3030 15 MHz 1 Trace 5mV built-in component tester
3033 15 MHz 1 Trace 5mV battery operation
3034 15 MHz 2 Trace 5mV battery operation
3035 10 MHz 1 Trace 5mV built-in component tester
3131 15 MHz 2 Trace 5mV built-in component tester
3337 30 MHz 2 Trace 5mV wth signal delay
GOULD ADVANCE
OS1000B 20 MHz 5mV 2 Trace
OS3000A 40 MHz 5mV 2 Trace 2T base
HEWLETT PACKARD
182C 100 MHz Mainframe
182T 100 MHz Mainframe with digital normaliser interface
1804A 50 MHz 20mV 4 Trace Plug-in
1825A Dual Timebase Plug-in
1805A 100 MHz 5mV 2 Trace Plug-in

PHILIPS
PM3207 15 MHz 5mV 2 Trace TV trig
PM3211 15 MHz 2mV 2 Trace TV trig
PM3212 25 MHz 2mV 2 Trace TV trig
PM3233 10 MHz 2mV 2Ch fixed delay Dual Beam
PM3244 50 MHz 5mV 4 Trace 2T base
PM3260 120 MHz 5mV 2 Trace 2T base
PM3262 100 MHz 5mV 2 Trace 2T base Tr View

TEKTRONIX
465 100 MHz 5mV 2 Trace 2T base
465B 100 MHz 5mV 2 Trace 2TB, Inc Probes
475 200 MHz 2mV 2 Trace 2T base
475A 250 MHz 2mV 2 Trace 2T base
485 350 MHz 5mV 2 Trace 2T base
5B42 2 T/base plug-in 50 MHz Trig for 5000 series Mainframe
DD501 Digital Events Delay — P/in for TM500 series
661/4S3/5T1A 1 GHz Sampling scope
7A12 105 MHz 5mV 2 Trace Plug-in
7A18 75 MHz 5mV 2 Trace Plug-in
7A19 500 MHz 10mV 1 Trace Plug-in
7A22 1 MHz 10μV Differential Plug-in
7A24 350 MHz 5mV 2 Trace Plug-in
7A26 200 MHz 5mV 2 Trace Plug-in
7B53A 2 Timebase Plug-in 100 MHz Trig
7B80 Single Timebase 400 MHz Trig
7B85 Timebase with delay 400 MHz Trig
7403N 75 MHz 3 slot M/Frame
7603 100 MHz CRT r/out 3 slot M/Frame
7704A 200 MHz CRT r/out 4 slot M/Frame
P6013A X1000 12KV Probe

TELEQUIPMENT

D63/V1/V1 15 MHz 2 Trace 1mV

SPECIAL OFFER

PHILIPS PM2454B £180

A.C. Analogue millivoltmeter.
Frequency range 10 Hz – 12 MHz.
12 ranges 1 mV-300 V F.S.D.
Voltage and dB scale provided.
D.C. output proportional to meter reading.

COUNTERS & TIMERS

FLUKE	
1910A-1 125 MHz 7 digit Cntr. AC/Batt	300
1912 520 MHz 7 digit Counter	375
1912A01 As 1912A but inc. re-charging batteries	430
1920A 520 MHz 9 digit Counter inc. Brst. mode	575
1920A14 1250 MHz otherwise as 1920A	750
HEWLETT PACKARD	
5243L 20 MHz 8 Digit Counter	150
5245L 50 MHz 8 Digit Counter	200
5300A/5304A 10 MHz 6 Digit Counter Timer	250
5300A/5305B 1300 MHz 6 Digit Counter	425
5345 500 MHz 11 Digit Counter Timer	2000
MARCONI	
TF 2432 560 MHz 8 digit Counter	350
RACAL-DANA	
371 18 GHz 11 digit Counter with Source Locking facility	4950
8110 50 MHz 8 Digit Counter Timer	320
9024 600 MHz 7 1/2 digit Counter	220
9025 1 GHz 8 digit Counter	450
9520 10 MHz 4 Digit	95
9905 200 MHz 8 digit Counter Timer	360
SYSTRON DONNER	
6053 3 GHz 9 digit Counter BCD O/P	790
5103B Strip Printer for 6053/6054	375
TEKTRONIX	
DC501 7 Digit 100 MHz Counter — TM500 Plug-in	180

DRANETZ

606 3ch Volts Av/Spike/Time/Printer	2950
616 2ch AC 1ch DC Volts/Av/Spike/Time/Printer	3300

GAY

LDM AC/DC/Spike/Time inc. Printer	1250
-----------------------------------	------

MISCELLANEOUS

A.I. INDUSTRIES
TCS General Purpose Gas Leak Detector — intrinsically safe

290

BRADLEY
192 Oscilloscope Calibrator

825

COMARK
1601BLS Thermom 10ch 87 + 1000°C type K

50

N.B. Thermocouples not included

CROWCON
71P Inflammable Gas Detector/Alarm

125

DATALAB
DL905 Digital Transient Recorder/Display

1050

FLANN
16/11 Rotary Vane Attenuator WG16

250

HEWLETT PACKARD
342A Noise Figure Meter

500

X382A Rotary Vane Attenuator WG16

175

MULTIMETRICS
AF120 Dual H/Pass L7 Pass active filter 20 Hz – 2 MHz

800

PHILIPS
PM 5501 Colour TV Pattern Generator

199

Check before you test

Before you decide on a test instrument, check the Avo range. Chances are you'll find precisely what you want. And because it carries our name, you can be sure it will perform with consistent accuracy and reliability. Even if a problem does occur, our new streamlined service department will ensure that it won't be a problem for long. So before you test, check with your usual Avo Appointed Distributor, or contact us for a copy of our Shortform Catalogue.



THORN EMI Instruments Limited,
Archcliffe Road, Dover, Kent CT17 9EN
Telephone: 0304 202620. Telex: 96283

A THORN EMI company

The test of ability

WW - 076 FOR FURTHER DETAILS

ELECTROVALUE



CATALOGUE 82

Send 70p for your copy now - 64 pages (A4).

More than 6000 stock items from nuts and bolts to complete computer systems.

With it we include a Reclaim Voucher value 70p for spending towards orders value £10 or more.

FROM CATALOGUE 82, PAGE 22



I.L.P. TOROIDAL TRANSFORMERS
With secondary O/P voltage of 9 + 9, 12 + 12, 15 + 15, 18 + 18, 25 + 25, 30 + 30, 110, 220, 240. STATE REQUIRED VALUE WHEN ORDERING.
50VA - £7.36; 80VA - £7.82; 120VA - £8.92
(Prices include rigid mounting kit and V.A.T.)

UK CWO orders over £5.75 sent POST FREE

WE CARRY FULL I.L.P. 240V TOROIDAL RANGE AS ADVERTISED

DISCOUNTS
5% on C.W.O. orders £23 and upwards
10% on C.W.O. orders £57.50 or more

ELECTROVALUE LTD. Dept WW4, 28 St Judes Road, Englefield Green, Egham, Surrey TW20 0HB
Phone Egham 33603 (STD 0784, London 87). Telex 264475.
Northern Branch: 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

CLEF ELECTRONIC MUSIC

PIANOS



SPECIALISTS SINCE 1972 DOMESTIC OR STAGE SIX OR 7 1/4 OCTAVES KITS OR MANUFACTURED

The most advanced form of touch-sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

Component Kits include Keyboard.

Full Kits further contain: Cabinets, Harness, Power Amp and Speaker.

DOMESTIC PRICES

	£	SIX	7 1/4
Comp	217	244	
Full	363.00	399.00	
MFD	595	675	



BAND-BOX
An Electronic Backing TRIO. Drums, Bass & Chord Instrument. User Programmable for 50-100 scores, using microprocessor.

MASTER RHYTHM
User Programmable DRUM MACHINE. Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation.



£79 KIT £119 BUILT

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr. & Ins. and we operate Telephone BARCLAY-CARD/ACCESS. Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED
Dept. W, 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 005 FOR FURTHER DETAILS

P.&R. COMPUTER SHOP

IBM GOLFBALL PRINTER 3982, £70

EPSON MX-80 80.GPs 3982 IBM I/O PRINTERS DOT MATRIX PRINTER WITH SPECIAL INTERFACES. VDUs, ASCII KEYBOARDS, ASR, KSR, TELETYPES, PAPERTAPE READERS, PAPERTAPE PUNCHES, SCOPES, TYPEWRITERS, FANS 4" 5" 6". POWER SUPPLIES, STORE CORES, TEST EQUIPMENT AND MISCELLANEOUS COMPUTER EQUIPMENT. OPEN: MONDAY TO FRIDAY 9 a.m.-5 p.m., SATURDAY TILL 1 p.m.

COME AND LOOK AROUND
SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, ESSEX.
PHONE MALDON (0621) 57440

WW - 029 FOR FURTHER DETAILS

The Professional Choice



AMCRON 

Since the introduction of the DC300 in 1967, AMCRON amplifiers have been used worldwide — wherever there has been a need for a rugged and reliable amplifier. Their reputation amongst professional users, throughout industry, has made the name of AMCRON synonymous with power amplification. For power you can depend on - choose AMCRON, the professional choice.

For further details contact the UK Industrial distributor:

G.A.S.

G.A.S. ELECTRONICS

16, ST. ALFEGE PASSAGE, LONDON SE10

TELEPHONE: 01-853 5295

TELEX: 923393 LASER G


WW - 024 FOR FURTHER DETAILS

Spoilt for choice

14D-10
2mV/cm at 10MHz

14D-15
15MHz
Active TV sync.

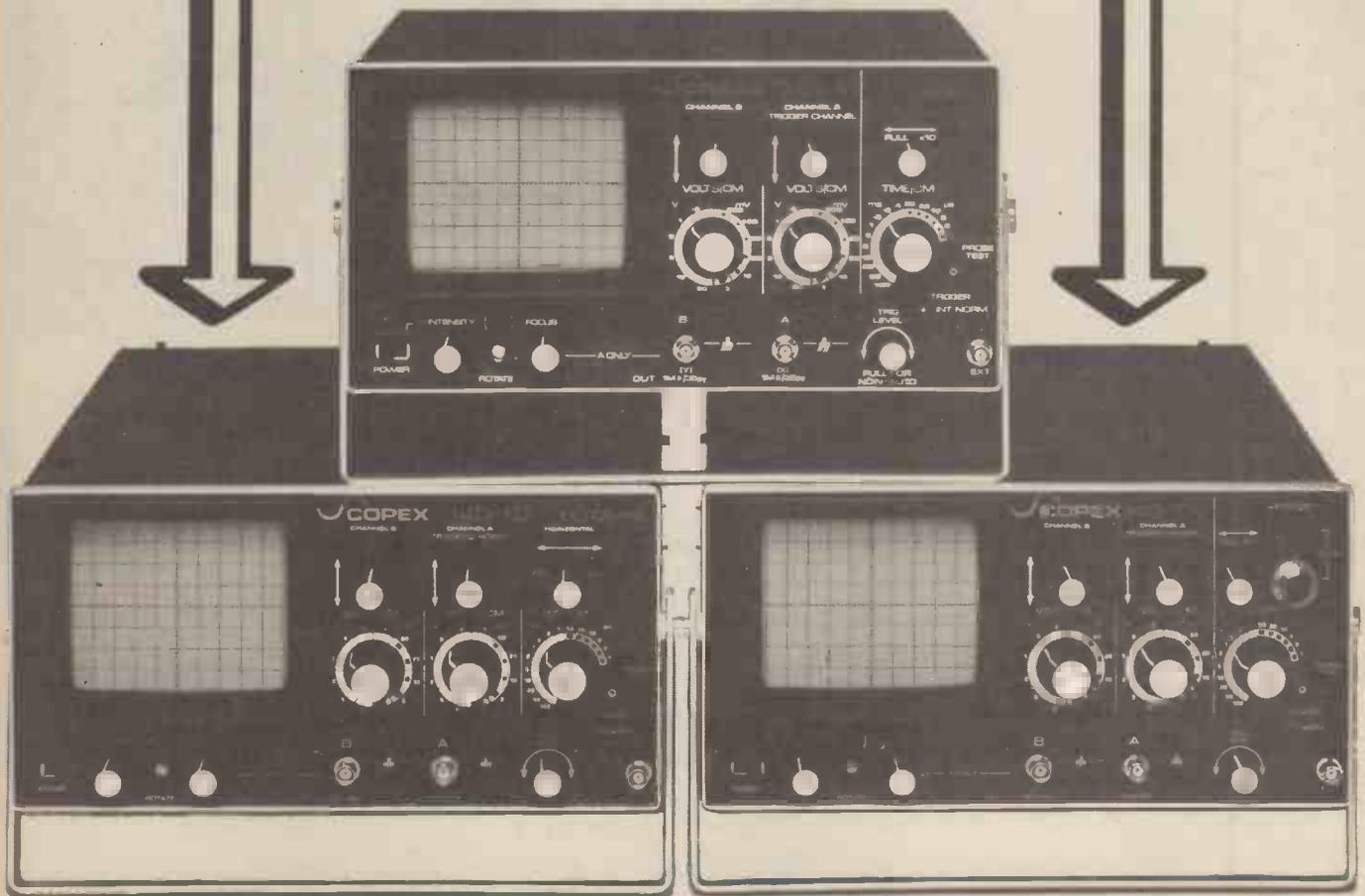14D-10V
Line selector
Active TV sync.
2mV/cm at 10MHz



Scopex Instruments now offer you an unrivalled choice of oscilloscopes at under £300.

The straightforward and successful 14D10 with a sensitivity of 2mV/cm at 10MHz on both channels at £240 + VAT. The new 14D15 15MHz dual trace 5mV/cm with active TV sync separator at £250 + VAT and the sophisticated 14D10V 10MHz dual trace 2mV/cm active TV sync. separator and line selector at £290 + VAT. All these above prices include two probes, mains plug and carriage U.K. mainland. 10cm X 8cm display, add and invert facility, probe compensation, pushbutton x-y and trace rotate are all standard features of this 14D range.

You the customer decide the extras you need to fulfil your specific requirement.

An Independent British Company

Credit Cards and Orders
contact our Sales department at:

SCOPEX
Pixmore House
Pixmore Avenue, Letchworth,
Herts SG6 1HZ Tel: (04626) 72771.

Please send me full details of the 14D range.

Name _____

Company _____

Address _____

Tel: _____

LOW COST VOLTMETERS



LEVELL
PORTABLE INSTRUMENTS

LEVELL A.C. MICROVOLTMETERS AND BROADBAND VOLTMETERS are part of our comprehensive range of test and measuring instruments.

These voltmeters give accurate readings over a wide range of frequencies. They are housed in robust steel cases and are powered by long life batteries. Mains power units and leather carrying cases are available as optional extras.

A.C. MICROVOLTMETERS

VOLTAGE & dB RANGES

15 μ V, 50 μ V, 150 μ V . . . 500V fsd
Acc. $\pm 1\%$ $\pm 1\%$ fsd $\pm 1\mu$ V at 1kHz,
-100, -90 . . . +50dB.
Scale -20dB/+6dB ref. 1mW/600 Ω .

type
TM3A

£130

RESPONSE

± 3 dB from 1Hz to 3MHz,
 ± 0.3 dB from 4Hz to 1MHz above
500 μ V.
TM3B filter switch; LF cut 10Hz.
HF cut 100KHz, 10KHz or 350Hz.

type
TM3B

£145

INPUT IMPEDANCE

Above 50mV: 10M Ω <20pF.
On 50 μ V to 50mV: >5M Ω <50pF.

BROADBAND VOLTMETERS

H.F. VOLTAGE & dB RANGES

1mV, 3mV, 10mV . . . 3V fsd.
Acc. $\pm 4\%$ $\pm 1\%$ fsd at 30MHz,
-50, -40 . . . +20dB.
Scale -10dB/+3dB ref. 1mW/50 Ω

type
TM6A

£199

H.F. RESPONSE

± 3 dB from 300kHz to 400MHz.
 ± 0.7 dB from 1 MHz to 50MHz.

type
TM6B

£215

L.F. RANGES

As TM3

LEVELL ELECTRONICS LTD.

Moxon Street, Barnet, Herts. Tel. 01-449 5028/440 8686

+P&P and VAT

WW - 023 FOR FURTHER DETAILS

Strongboxes

High voltage, heavy current, delicate instruments or sensitive switching systems. Whatever you need to protect, there's a Sarel enclosure to make sure it stays put, stays protected.

Fumes, fire, water, solvents, dust, impact or unauthorised hands. Whatever you want to keep out, there's a Sarel enclosure to make sure it stays out.

When you want to keep valuable components and vital connections working—come what may—you need more than just a pretty box. You need the total protection and security of a Sarel enclosure.

Steel, plastic, GRP; small

enclosures, giant monobloc enclosures, control desks, fittings and accessories. You'll find exactly what you're looking for in the new Sarel catalogue. You'll find the price, and the address of a nearby stockist. Getting Sarel enclosures—and peace of mind—is easy, when you know how. Getting your copy of the Sarel catalogue is easy, too.

All you have to do is complete and post the coupon below. We'll mail your catalogue by return, without obligation.

Send the coupon today!



Think big - think Sarel
Sarel Electric Limited
Cosgrove Way, Luton, Beds. Tel: Luton 20122

Send me my free copy of the new Sarel Electric Catalogue, soon!

Name _____

Position _____

Company _____

Address _____

Telephone _____

Sarel Electric Limited, Cosgrove Way, Luton, Beds.

WW4



WW - 056 FOR FURTHER DETAILS



**What brings home the world's best broadcasting system
at the touch of a button?**

Simple.

The QUAD FM4

Simply write or phone for more information to
The Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs. PE18 7DB. Telephone: (0480) 52561.

QUAD 
for the closest approach
to the original sound

WW - 018 FOR FURTHER DETAILS

Editor:

PHILIP DARRINGTON

Technical Editor:GEOFF SHORTER, B.Sc.
01-661 3500 X3590**Communications Editor:**MARTIN ECCLES
01-661 3500 X3589**News Editor:**DAVID SCOBIE
01-661 3500 X3587**Design Editor:**

ALAN KERR

Drawing Office Manager:

ROGER GOODMAN

Technical Illustrator:

BETTY PALMER

Advertisement Manager:BOB NIBBS, A.C.I.I.
01-661 3130DAVID DISLEY
01-661 3500 X3593BARBARA MILLER
01-661 3500 X3592**Northern Sales**HARRY AIKEN
061-872 8861**Midland Sales**BASIL MCGOWAN
021-356 4838**Classified Manager:**BRIAN DURRANT
01-661 3106OPHELIA SMITH
01-661 3033**Production:**BRIAN BANNISTER
(Make-up and copy)
01-661 3500 X3561

Engineering — or dominoes?

During the 1940s, at a grammar school in the north of England, the most wonderful things on display in the glass case outside the science laboratories were a cloud of glass-fibre wool and some coal with a fossil leaf in it. The glass was impossible because everyone knew that glass was hard and brittle and yet here was this soft (though scratchy) stuff made from it, and the coal was just so unimaginably old — older, even, than the physics master who had, some said, discovered fire. Simple things, goodness knows, but worth a couple of lessons in the physics class.

In those days, there was little talk of wireless in the classroom, let alone 'electronics'; classes were taken up with interminable experiments on the latent heat of vaporization and the laborious plotting of magnetic fields. Then, one day, a visiting teacher told the class of his wartime work on radar, speaking of microwaves, 'metallic insulators' and times measured in microseconds. This was a great deal more wonderful than the glass wool and bits of coal and led to rather a lot of daydreaming for some of the class.

Science teaching has advanced greatly in the ensuing 35 years. Microcomputers are becoming commonplace and labs are stocked with oscilloscopes, signal generators and all the other impedimenta of the electronic '80s. Pupils handle circuitry switching at 3ns or oscillators working at several gigahertz or truly compendious i.cs with remarkable nonchalance, if the youngsters seen on television programmes or in the news as competition winners are anything to go by.

It is, it goes almost without saying, necessary for the modern pupil to have the use of advanced, modern equipment. It is right that programming microprocessors should have taken the place of connecting components, in school, as in the world of

work. A micro, given the correct data and program, will do exactly what is expected of it very efficiently, as can be verified by a glance at the storage oscilloscope or logic display, but where is the striving? And, without the striving, where is the learning? Is there a danger of producing a great number of people who call themselves electronic engineers but whose knowledge of electronics stops short at an ability to program and an awareness of the cheapest supplier of interfaces?

The only answer to all these weedy, half-baked questions is that undoubtedly that is exactly what engineers will be like, and quite soon, too: there is no reason why they should be any different. It has been said for years that the microprocessor is a component, to be used as any other component. There can be little advantage to a user in knowing the precise details of the internal working of a micro — it can be regarded as a machine which will do its job when asked. It is not necessary to know the finer points of oscilloscope design to use one to its fullest extent: neither is it absolutely necessary to know more than the capabilities and characteristics of a micro, or any other i.c., to obtain the maximum performance from it. And when the remaining parts of circuits are also integrated, there will be no pressing need to understand the use of power transistors, or passive components, either, unless one has to design the i.cs. 'Systems engineering' will be supreme.

This is not, of course, to say that all engineers will be satisfied without a detailed knowledge of exactly what happens inside the i.cs. Perhaps these people will be the originators — the ones who, because they know more of the internal operation, will be able to apply i.cs with a greater imagination. But do not decry the simple user of modules: he will know all he needs to know.

MICROPROCESSOR-CONTROLLED LIGHTING SYSTEM

Stage and theatre lighting control is a complex task – yet a task easily handled by a microprocessor. As even the simplest of microprocessors can be programmed to provide and accept data for controlling a lighting system, these articles concentrate on using an existing microprocessor board to process and store complex lighting patterns set by conventional faders, and cover interfacing from digital data, to human input, to light dimmers. Software for the 8085A processor used in the prototype will be discussed in the third and final article.

by John D. H. White and Nigel M. Allinson

This system is designed to simplify the control of complex lighting patterns as used in theatres and studios or at pop concerts. The prototype described in these articles made use of a commercially available 8085A processor board to control up to 256 lighting channels with 8-bit accuracy phase control. Here, we discuss the system's hardware and its ability to linearize the relationship between lamp brightness and fader position.

Background

Before the introduction of high-power semiconductors the brightness of lamps in lighting systems was controlled by variable resistors or inductors. The cost and size of such inefficient power-control methods meant that systems were kept small and were usually difficult to operate. With high-power thyristors, it was possible to construct very compact dimmers which could be controlled remotely. Initially, this improved power control was used to copy the previous systems; however, the compact nature of the dimmers meant that much larger lighting systems could now be built and controlled. At present, "portable" lighting systems with 80 separate output channels are in common use for pop-group concerts and even larger systems are employed in tv studios and theatres.

All lighting-control systems may be split into two separate sections – the power-control section (the dimmers) and the control desk, which is used to control the dimmers. These are usually remote from each other, being connected by multi-core cable. Although the size of lighting systems has increased over the years, the control facilities available have remained rudimentary. A small number of digitally controlled desks are commercially available, though these are expensive and tend to be used in large, fixed installations.

The most common type of circuit used in an analogue control desk is outlined in Fig. 1. Each row of channel faders (presets) is voltage driven by a master fader (master preset). Outputs from each preset for a given channel are then gated together through diodes; thus the final

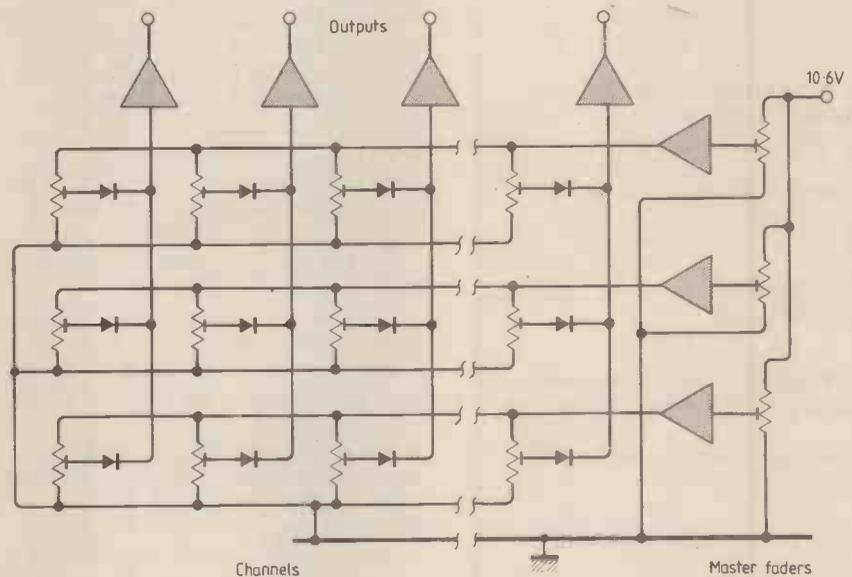


Fig. 1. This type of matrix is often used in analogue lighting-control desks. In this way, lighting patterns stored at preset fader positions can be recalled using the master faders.

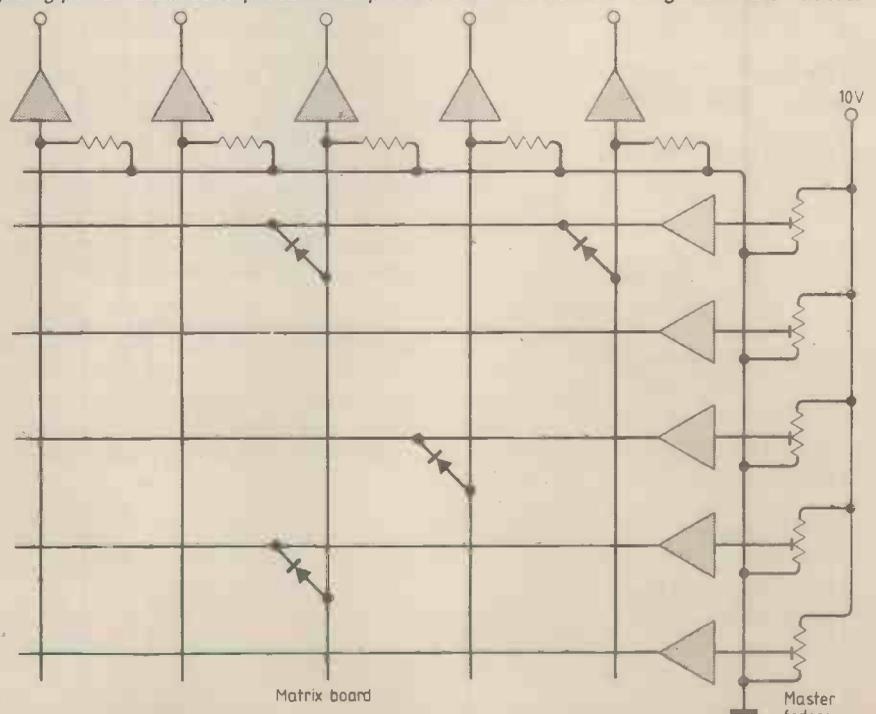


Fig. 2. Using this type of matrix, with plug-in diodes, a great number of lighting patterns can be stored cheaply but the ability to vary lamp brightness continuously is lost.

output from the control desk is the largest preset voltage for each channel. In this way, each master preset can be used to recall a stored lighting pattern (i.e. stored in a row of presets). Because of the cost of faders, the number of master presets is usually fairly small. For pop-group concerts and certain stage applications, the ability to control continuously the brightness of each light is forfeited to allow the storage of a greater number of lighting patterns. The patterns are created and stored by positioning pins, containing diodes, in interchangeable matrix boards, as indicated in Fig. 2.

As the dimmers will use different mains phases (total power requirements may exceed 500kW for a large system), a standard interface format between the control desk and dimmers is necessary. A direct voltage of 0-10V has become the convention in most lighting systems, 0V corresponding to the lamps being off, and 10V to full brightness. Figure 3 shows the schematic lay-out of a typical dimmer module. The d.c. control voltage is compared with a ramp synchronized with the line frequency, hence phase-control of the load is possible.

Before considering the output hardware, one other question that needs answering; how many control bits are required to give apparently stepless light output variations? For a very wide range of lighting conditions, it was found that seven bits were sufficient for "stepless" light control. Since the microprocessor is an 8-bit device and most of the integrated circuits used to construct the system are 4-bit devices, it was decided to use 8-bit codes throughout. This also provides some immunity to the effects of truncation errors in the output code from software calculations.

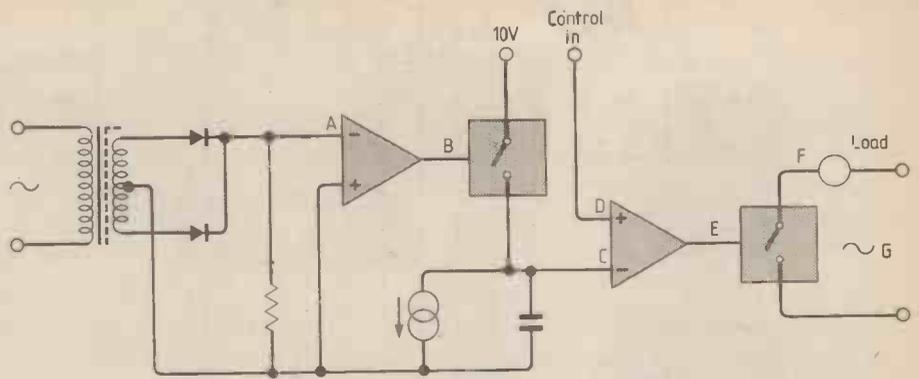


Fig. 3. Outline of a typical circuit. A d.c. control voltage is compared with a ramp synchronized with the line frequency, making phase control at the load possible.

Circuit description

Because of the large number of output channels each dimmer unit must be kept simple and economical. Also, since one may wish to increase the number of output channels in the future, a modular design is advantageous. The overall output-control layout is shown in Fig. 5. Each dimmer module is enabled so as to accept data from the microprocessor data bus by a 2-bit code derived from the 8 low-order bits of the address bus. Hence up to 256 dimmer modules can be given a unique address. Conventional output ports could have been used to enable data transfer to each dimmer module. However, the 8085A processor instruction set contains only one output-port instruction (OUT port) and this can only be used in a direct-addressing mode, i.e., the second byte of the instruction must contain the port address. The restriction of direct addressing makes this method unsuitable for use in a lighting-control desk because of the large number of outputs required. The solution is to employ mapped-memory output, which uses a section of "memory locations" for

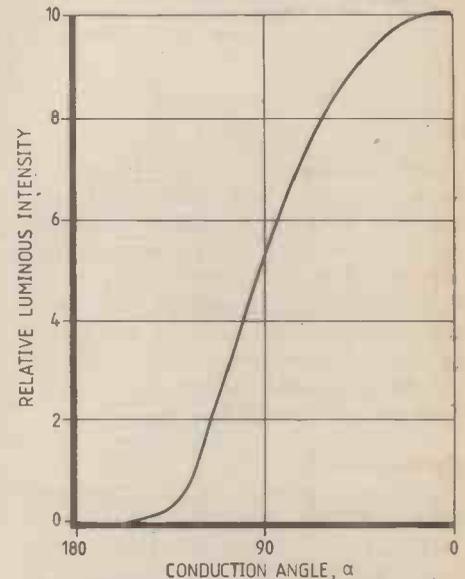


Fig. 4. Measured luminous intensity, as a function of conduction angle, for a 1000W lamp (see text).

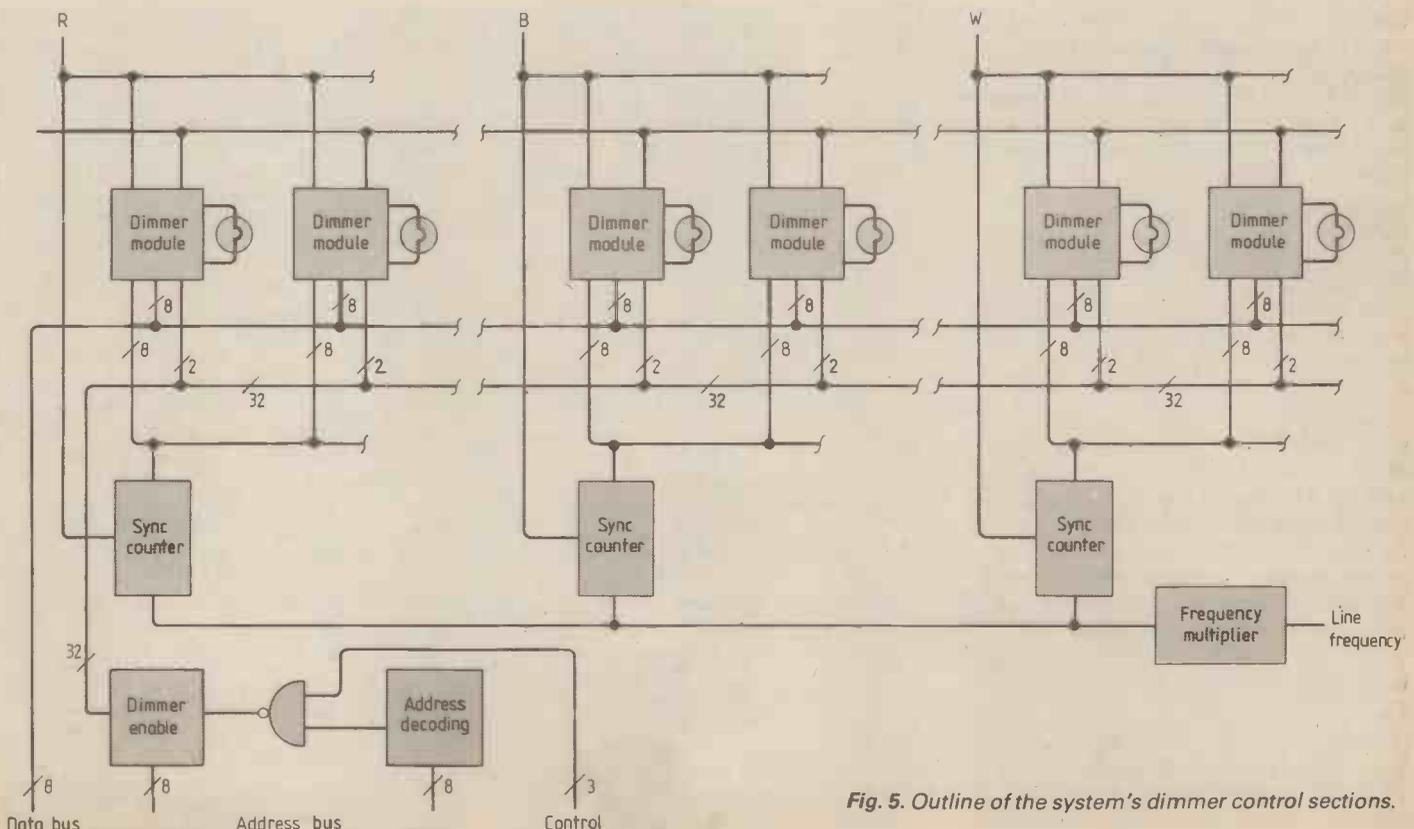


Fig. 5. Outline of the system's dimmer control sections.

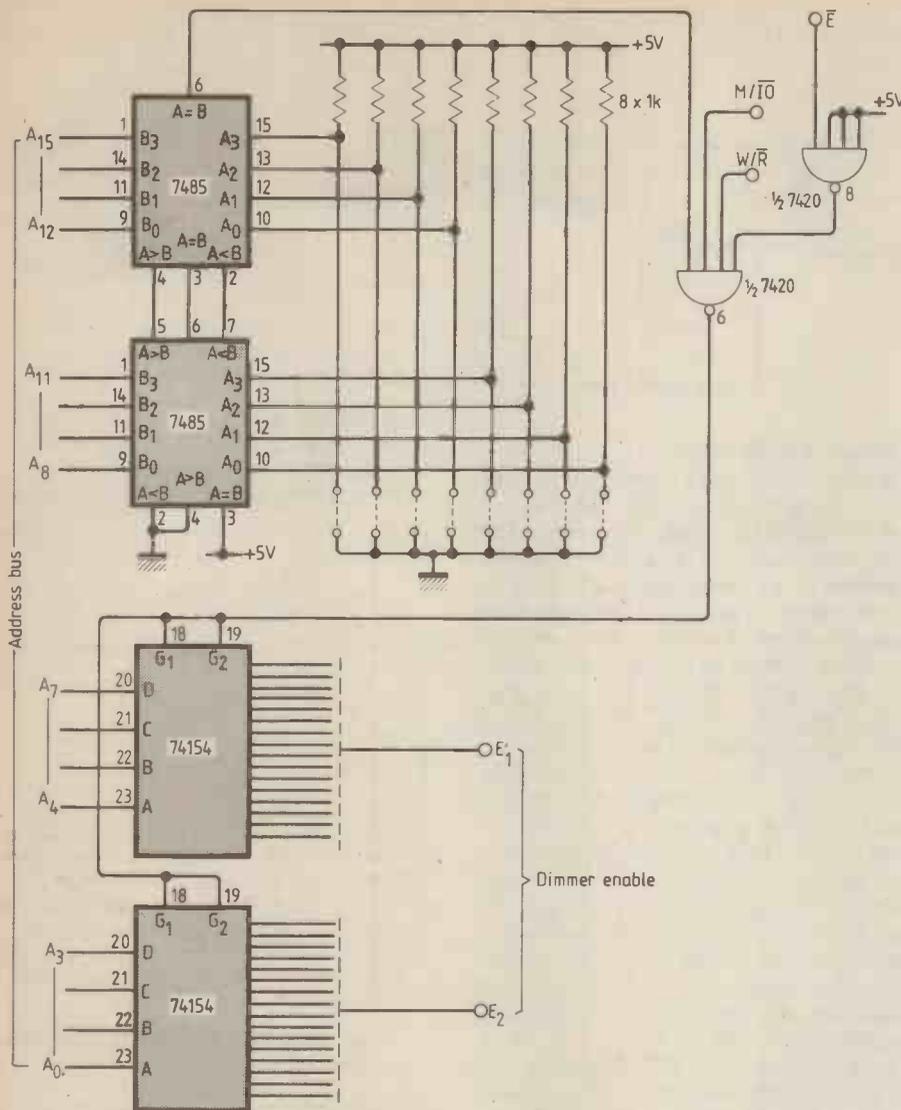


Fig. 6. Address decoding and dimmer enable module.

output. This arrangement allows any instructions which write to memory to be used as output instructions, giving considerable advantages in the software as indirect addressing is permitted. A small amount of extra hardware is, however, required to decode the address lines to enable the outputs.

The digital equivalent to the linear-voltage ramp in an analogue dimmer is an 8-bit binary code counting from 0 to 255 in each line half-cycle. The 8-bit synchronous counter is clocked by 51.2 kHz signal derived by multiplying the line frequency. The counter is reset every line half-cycle by a zero-crossing detector.

Each dimmer module compares the latched 8-bit code from the control desk to the 8-bit code from the counter. When the counter output is greater than the control-desk code, a 51.2 kHz signal is applied to gate the thyristors, hence accurate phase control of the lamps is possible.

The complete lighting system will contain one address-decoding and dimmer-enable module, one frequency-multiplier module, three counter and reset modules (one for each phase used), and one dimmer module per output channel.

Address decoding and dimmer enable module

The eight high-order bits of the address bus are compared with a bit pattern set by 8 wire-links to determine the location of the 256 output addresses in the memory map. Two cascaded 7485 4-bit magnitude comparators, see Fig. 6, generate a high-level signal when both inputs are equal. This signal, the M/I0 and W/R control signals and the system enable signal, E, enter a NAND gate to give a signal which is high when valid output

Subjective brightness control

For full-wave control using a triac or inverse-parallel connection of two thyristors, the r.m.s. output voltage, V_o , is;

$$V_o = V_s \left(\frac{\pi - \alpha + \frac{1}{2} \sin 2\alpha}{\pi} \right)^{1/2}$$

where V_s is the r.m.s. supply voltage and α is the conduction angle. This, of course, assumes a purely resistive load. Tungsten lamps have associated with them some inductance and a thermal inertia, which affects their transient behaviour. The perceived brightness of a controlled light source is a complex function of the voltage, and hence the position of the fader on the control desk. A number of factors contribute to this function:

- The resistance of the lamp filament increases over a range of about 20:1 for its entire operating range.
- As the temperature increases, the spectral distribution of the radiant energy changes, approximately in accordance with Planck's distribution law. With increasing temperature, the peak of the radiant energy moves towards shorter wavelengths (i.e. the light is "whiter"). A tungsten-filament lamp may be considered as a near-perfect universal radiator.*

- Due to the above, the fraction of the total radiant energy visible also changes. Mathematically, the visible output is the convolution of the modified Planck's distribution function and the standard luminosity curve of the human eye.

All these factors can be approximated, with reasonable accuracy, by the simple expression:

$$\text{luminous intensity, } I = kV_s^c$$

where k and c are constants for a particular type of tungsten lamp. The type of lamp (maximum voltage, wattage, etc.) has a slight effect on c . Most references consider c to lie between 3.2 and 3.5. Our experience suggests a slightly lower value for a wide range of lamp types. The measured luminous intensity as a function of conduction angle for a 1000W PAR64 lamp is given in Fig. 4. This general curve holds for all forms of tungsten lamp, and is used to linearize the relationship between lamp brightness and fader position in this system. It is worth noting here, that measured photometric brightness, L , of a surface (its luminance) is not generally the same as its subjective brightness, B . Subjective brightness is determined in part by the luminance of an object, and in part

by the conditions of observation such as the state of adaptation of the eye and the luminance of surrounding areas. The relationship between luminance and subjective brightness is still an area of active psychophysical research. Engineers are often satisfied with approximate relationships, and, from accumulated experimental evidence, a simple though approximate relationship is:

$$B = aL^\gamma$$

where γ is $1/3$ or $1/2$, for dark or bright surroundings respectively. γ -correction is most commonly encountered in the design of tv displays. However, our experimental work with slowly increasing the brightness of lamps suggested that the best subjective linear increases in subjective brightness was obtained by ignoring γ -correction and simply using the relationship for luminous intensity. The inverse of the above function (i.e., the first two equations combined) is calculated for each discrete step in the dimmer control code.

*This term is used in preference to black body because a very hot object or surface radiator will radiate visibly; "universal" applies to both absorption and emission.
- Ed.

data is present on the data bus. The 8085A processor system employed in the prototype design was a Quarndon Electronics Ltd. QMS 85 8085 development system, which produces an overall system-enable strobe. \bar{E} will be low whenever the WR, RD or INTA of the 8085A is low. For "write" cycles, the data bus is stable while \bar{E} is active.

The valid-data signal is used to strobe the G1 and G2 inputs of two 74154 4-to-16-line demultiplexers connected to the eight low-order bits of the address bus. Two dimmer enable signals, E1 and E2, from the 32 outputs of the demultiplexers, give 256 unique addresses for the dimmer modules.

Frequency multiplier module

A 51.2kHz clock signal for the 8-bit counters, shown in Fig. 7, is obtained by multiplying the line frequency by 1024. The phase-locked loop (NE565) has a feedback divider chain consisting of five 7474 dual D-type flip-flops. The capture range is set at ± 2 Hz. The t.t.l. input signal to the phase comparator is at half-wave rectified mains frequency. Although t.t.l. compatible, the square-wave output of the v.c.o. will only provide a current of about 1mA, so the output is buffered to drive the counter and divider chain.

Synchronous counter and reset module

This circuit, shown in Fig. 8, generates a 8-bit binary code which counts from 0 to 255 in half a line period. The 51.2 kHz signal from the frequency multiplier is used to clock two cascaded 74161A 4-bit counters. The CLEAR inputs of these counters are used to reset them at the zero-crossing points of the mains. The full-wave rectified a.c. is applied to the voltage comparator (741). The output of the op-amp is inverted and converted to t.t.l. levels by the following common-emitter stage.

Dimmer module

The 8-bit code from the control desk, through the data bus, is stored in two 7475, 4-bit bistable latches, Fig. 9. These latches are enabled, i.e., data on the data bus is transferred to their Q outputs, when the dimmer module is addressed by its own 2-bit dimmer enable signal, E1 and E2. Data stored in the latches is compared to the output of the counter by two cascaded 7485s. When the count from the counter is greater than the latch data, the 51.2 kHz signal is gated to the thyristors through some buffer stage and pulse transformer. Some interference and transient protection is provided by the inductor and capacitor.

System performance

Some advantages of feeding data to a large number of channels have already been mentioned. Also, since the access time for each dimmer is less than the 410ns (the maximum data-bus access time permitted by the processor), no processor WAIT states are involved in transmitting data. This, of course, maximizes the data transference for updating the dimmers and


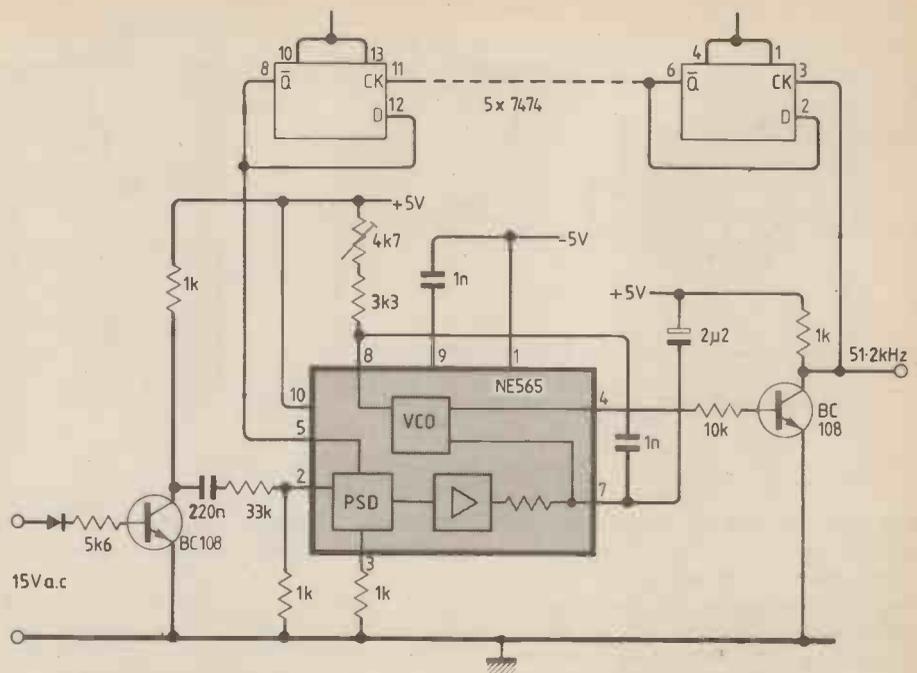


Fig. 7. This circuit is used to multiply the line frequency by 1024 to provide a 51.2kHz clock signal for the 8-bit counters.

Fig. 9. A dimmer module. The 8-bit code from the control desk is stored in two 4-bit bistable latches, and passes to the outputs when the enable signal, derived from E1 and E2, is given. When the counter input to the comparators is greater than the latch output data, the 51.2kHz signal is passed to the thyristors through a buffer stage and transformer.

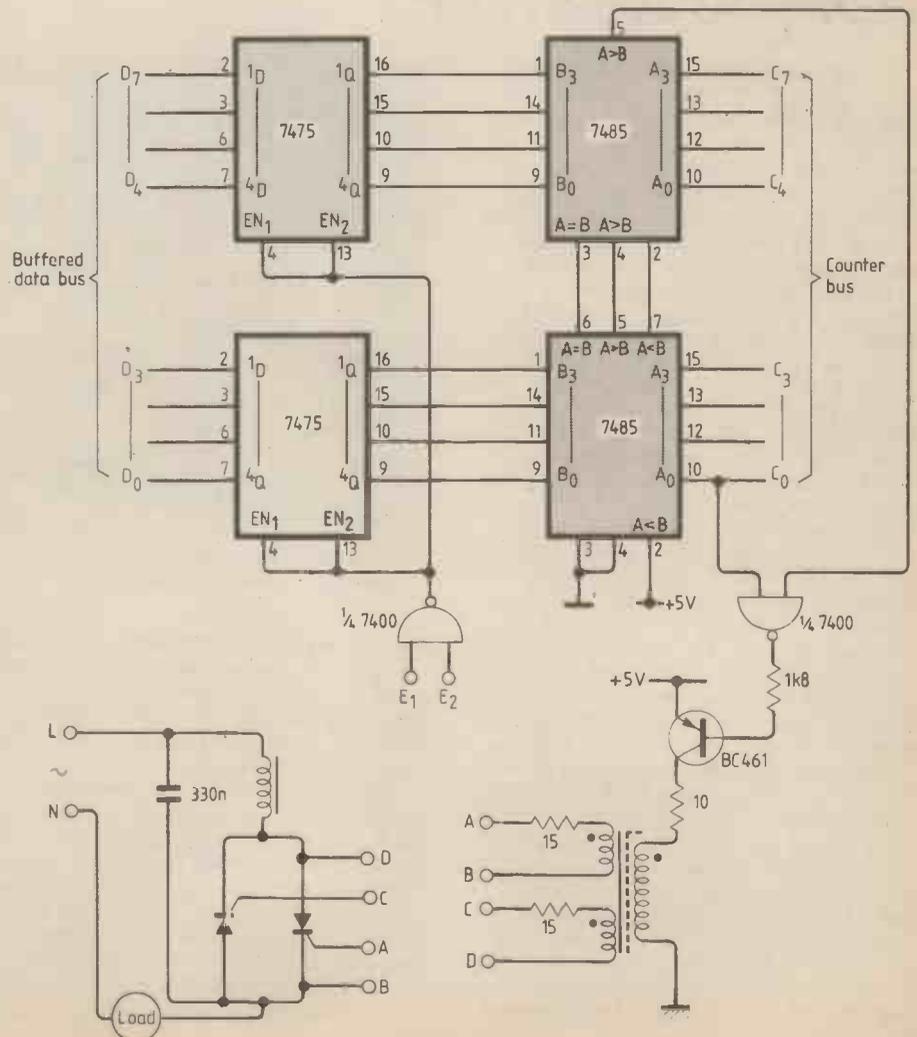

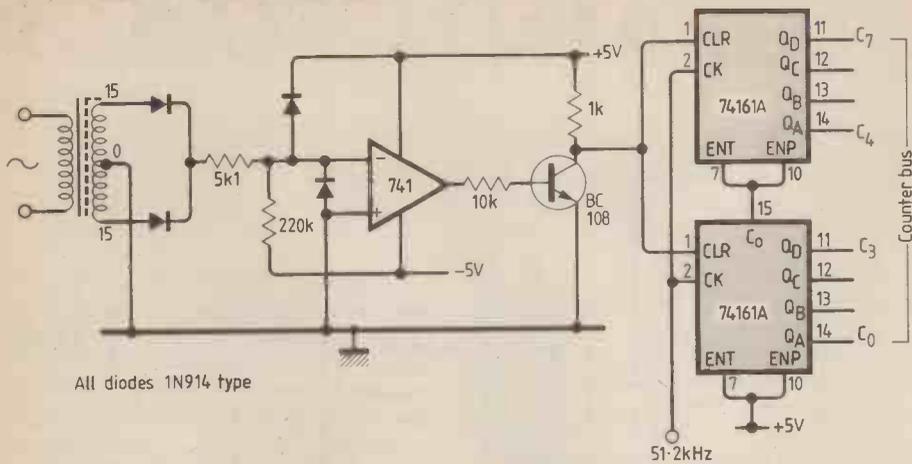


Fig. 8. Synchronous counter and reset module. An 8-bit binary code counting from 0 to 255 in a half-line period is generated.

helps to produce a highly interactive lighting system.

The effect of linearizing the luminous output of the lamps with the position of the faders is indicated in Fig. 10. The output code FF corresponds to the lamp being off, and the code 00 corresponds to full brightness. The slight delay at the start is due both to truncation errors in forming the inverse function mentioned earlier and to slight measurement difficulties. It could be removed by incorporating a suitable offset in the output coding, but from an operating point of view there are quite

distinct advantages in having a definite "lamps off" position on the faders. In the system, the 256 values of this inverse function are held in a "look-up table" in the operating software. For a non-microprocessor system, there is no reason why these values could not be contained in a p.r.o.m.

The complete operating system not only provides routines for inputting and outputting data, but also various methods for processing the stored lighting patterns. In the next article, the control desk will be discussed.

To be continued

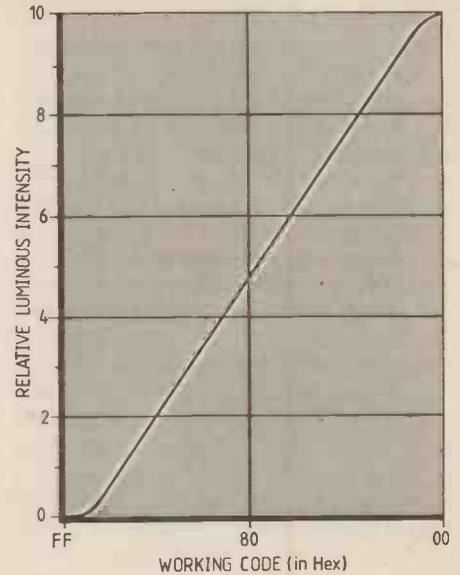


Fig. 10. The effect of linearizing the luminous outputs of the lamps in relation to the fader position.

Fibre optics at ITT

Joining optical fibres, especially in the field, is very difficult. ITT have developed a fibre optic splicing kit, the OFSK-10. Primarily intended for the joining of 50/125µm telecommunications grade fibres and other fibres of an all-silica construction, the kit uses an electric arc to fuse together the two ends. A V-groove jig has been developed to locate the ends accurately so that very high quality splices can be achieved.

Testing fibres in the field can also be a problem; it is very unlikely that the engineer has access to both ends of a cable but needs some method of locating a fault in a cable which can be up to 15km long, between repeaters. An answer has been provided by ITT in the OFR-3, an optical fibre reflectometer. If a short pulse of high intensity light is launched into an optical fibre, a small proportion of the light is reflected back towards the source from every point in the fibre. The reflections are 'backscatter' caused by imperfections in the molecular structure of the silica. The power of the reflected light, measured at the source end, decays exponentially with time, and by inference, with distance of the pulse into the fibre. The OFR-3 uses a laser to launch a pulse into the fibre and can measure and record the response from the reflections. Joins along the cable can cause extra reflections causing a peak in the response. Faults in the cable will cause drops in the response. The OFR-3 can display that response on an oscilloscope which includes an alpha-numeric display of all the relevant parameters. With the use of a cursor any part of the response can be looked at in more detail and the oscillogram with all the data display can be printed out for permanent record. The 'scope and printer are incorporated into the equipment which all fits into a portable case. All the controls and the laser are incorporated in the lid. The laser fits



The OFR-3 can trace faults in an optical fibre to within six metres over a length of 15000m.

behind a locked hatch and cannot be switched on unless connected to a cable. Any fault can be traced to within six metres resolution over a distance of 15km. ITT are already working on the OFR-4 which will be able to inspect a cable of even greater length - up to 100km.

ITT are particularly proud of two new applications for fibre optics. There is a plan to link the British and French electricity grids. One hour's difference between the clocks in the two countries means that peaks occur at different times and an extra boost can be provided across the channel. To avoid the need for frequency matching, the link will be d.c. G.E.C. are building the U.K. end of the link. Rectification will be by stacked thyristors each of which will work

at a different potential and will therefore have to be isolated from the other in the stack. To avoid using a number of isolating transformers, the switching pulses will be carried to the thyristor gates by fibre optic cables. A special cable has been developed to withstand voltage potentials of up to 5kV/cm. In parallel with the development of the cable has been the design of an l.e.d. edge connector array for providing the individual pulse firing signals for each thyristor. The link is to be commissioned in 1985/86.

Another new application is a cable television link which is to be given a trial by British Telecom to 18 houses in Milton Keynes. The trial will use optical transmission based on p.f.m. (pulsed frequency modulation) in which the tv signal frequency modulates a square wave carrier which then drives an l.e.d. source. All the transmitter and receiver modules including the modulators and demodulators have been supplied by ITT Leeds.

BT are already running a cable tv service in Milton Keynes. For the trial, the programmes are down-converted into baseband and separated into individual channels (0 to 6 MHz PAL, video with sound). In addition a channel is formed consisting of the f.m. radio programmes on carriers in the range 0 to 7MHz. Each channel is fed to its own transmitter and a ten-fibre cable carries the channels to a distribution point. The cable used for the 3.5km primary link contains fibre of better than 4dB/km loss and 400MHz-km bandwidth-distance product. From the distribution point the secondary link of between 50 and 200m goes to each customer. Signal information and channel selection are transmitted back from the customer's end to a microprocessor control which provides the channel switching and can monitor information about transmission on both primary and secondary links. In the home the signal is received optically, demodulated to baseband and then up-converted to u.h.f. so that it can be fed into the aerial socket of an ordinary tv.

555-TYPE INTEGRATED CIRCUITS

The 555 group of i.c.s is one of the most popular ever made, with an enormous variety of applications in oscillators and timers. John Linsley Hood explains its internal design and method of operation

by J. L. Linsley Hood

If the 1950s were the decade in which linear electronic circuits, previously implemented using thermionic valves as their active components, were progressively taken over by transistors, then the '60s were the decade in which such circuits, built up from an assembly of discrete components and transistors, were increasingly constructed using one or two simple packages of purpose-built circuitry, containing all the necessary active and passive components in a single lump. The term 'integrated circuit' was coined at this time to describe this packaged assembly of components.

While it was the enormous progress in the field of digital computers; which convinced the i.c. manufacturers of the enormous benefits of scale, it was the consumer market which provided the chance of profitable manufacture away from the computer field.

The realization that there was a large potential market set the design departments of many of the larger semiconductor manufacturers exploring the possibilities for useful functional packages. Clearly, an i.c. functional block which could be used with a relay and a timing capacitor to provide time delays or timing cycles, as, for example, in a washing machine or a darkroom enlarger timer, would have a lot of uses, and several such i.c.s were evolved at the end of the 1960s. Of these, by far the most successful was the Signetics 555. A number of manufacturers have copied it in identical form — in the process of what is known as 'second sourcing' — and produced in dual (556), quadruple (558) and c.m.o.s. (ICM7555) versions, along with sundry improved devices having the same pin configurations, such as the LM555C.

With the possible exception of the ubiquitous i.c. operational amplifier, few integrated circuits have had such an appeal

to the hobby electronics constructor, with several complete books of circuits having been published showing possible applications for this device. Yet, in spite of this, to most of its users, its method of operation remains needlessly obscure, and many attempted applications founder on inadvertent incompatibilities between the internal and external circuitry.

Circuit description

The 555 is fundamentally intended to give an output voltage waveform, as a 'one-shot' or in a repetitive manner, at a low enough output impedance to operate a reasonably sensitive relay. To simplify calculations for the timing RC chain — in which the time constant RC, in seconds, is the time taken for a capacitor C to charge through resistor R to 63.2% of the applied voltage — the internal voltage switching levels are chosen so that the external timing capacitor charges through about this voltage differential. A simplified block diagram showing the internal arrangement is given in Fig. 1.

In this, the heart of the circuit is a bistable 'flip-flop' with an external overriding reset input R. The two normal inputs are the threshold and the trigger connections, both of which are fed in through relatively high-impedance buffer amplifiers, connected, respectively, to reference voltages of $\frac{2}{3}V_{cc}$ and $\frac{1}{3}V_{cc}$, derived from the 15k resistor chain. Two buffered outputs from the flip-flop are provided through amplifiers A₁ and A₂, the first of which is a normal 'totem pole' output arrangement, as typically used in t.t.l. logic, to give a fairly low output impedance, and good current-sourcing characteristics. The second output, from A₂, is derived simply from a single transistor 'open collector' stage.

The way in which the 555 would normally be connected to operate as a 'one-shot' timer driving a relay, is shown in Fig. 2(a). In this the threshold input and the discharge (open-collector amplifier) output are joined together, and taken to the junction of timing resistor R and timing capacitor C; the timing cycle is initiated by

Fig. 2. 555 as a one-shot relay timer, with manual start and reset.


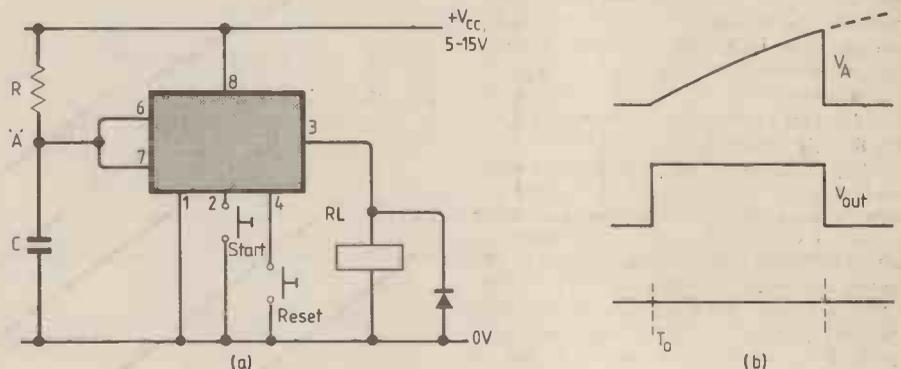


Fig. 1. Operations inside the 555.

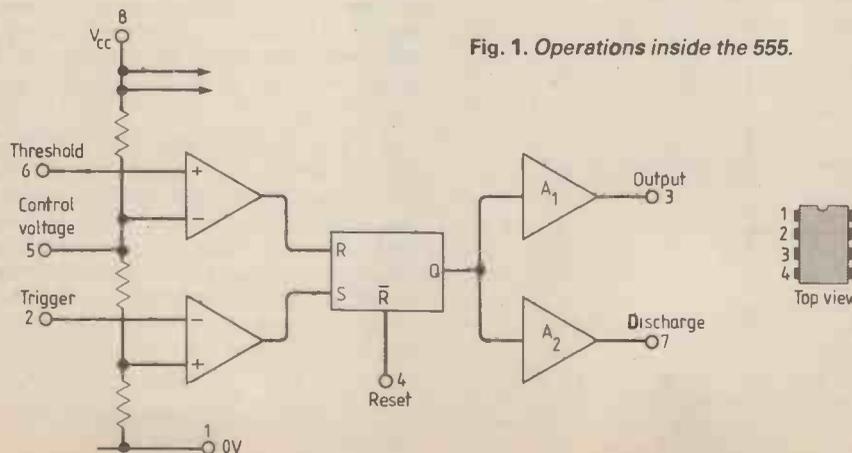

a momentary operation of a push-switch connected to the trigger input. This sets the Q output from the bistable, and both of the non-inverted outputs from A₁ and A₂, to a high state. In the case of A₁, this will energize the relay RL₁, and in the case of A₂, the result will be that its output becomes an open circuit, so that the timing capacitor C is free to charge up towards the +V_{cc} line.

Once the Threshold input level has reached $\frac{2}{3}V_{cc}$, the 'reset' input to the bistable, R in Fig. 1, is taken high, when it reverts to its initial state, with A₁ output 'low' — so that the relay is de-energized — and A₂ at a low impedance. This holds the

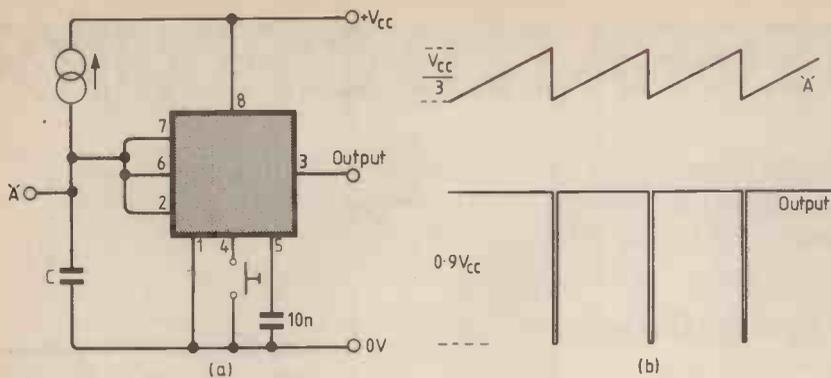


Fig. 3. Connexion for a free-running oscillator, with a frequency determined by the constant-current source and the value of C.

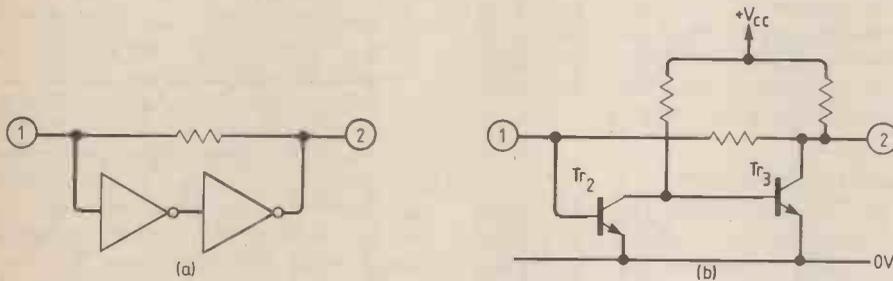


Fig. 4. Flip-flop block of Fig. 1 in logical form at (a) and in its practical arrangement at (b).

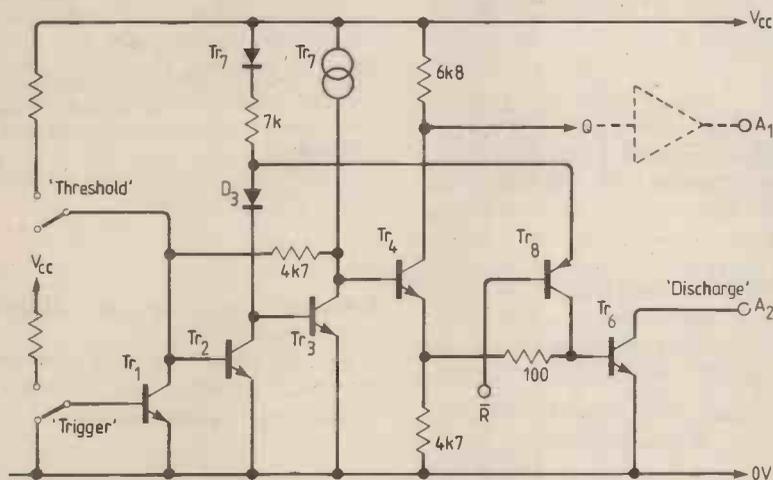


Fig. 5. Flip-flop (Tr_2 and Tr_3) shown in relation to threshold, trigger and output circuitry.

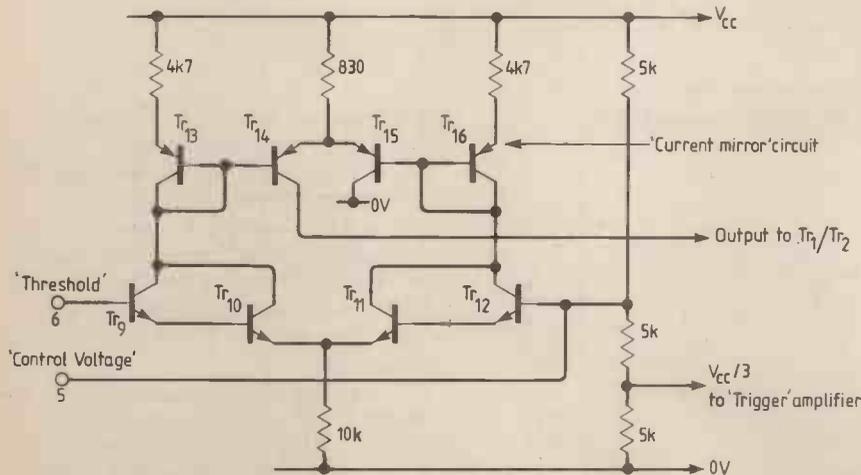


Fig. 6. Input amplifier for threshold voltage.

timing capacitor discharged and at a potential close to the 0 volt line level, ready for a further timing cycle to be initiated, by an input at a level less than $\frac{1}{3}V_{cc}$ being applied to the Trigger. The output waveforms are shown in Fig. 2(b).

Since the Trigger input is also taken to the bistable through a impedance buffer amplifier, it is practicable to connect this to the timing circuit as well, without imposing too much of a static load. This will convert the circuit into a 'free-running' sawtooth generator, with an output of $\frac{1}{3}V_{cc}$, as shown in Figs 3(a) and 3(b). Moreover, if the timing resistor R is replaced by an appropriate constant-current source, the output at point A will be a highly linear waveform, suitable for use in a time-base generator, and with a sync. input available at the override reset R of the bistable.

The bistable flip-flop is itself a very simple arrangement, shown schematically in Fig. 4(a) and in its practical form in Fig. 4(b). In this circuit, if the input (1) is taken high, even momentarily, the output will also go high and remain at that state. Similarly, if the input is taken low, the output will also follow, and remain. The fact that the transistor circuit of Tr_2 and Tr_3 can be made to behave like this depends on the characteristic that a transistor turned hard on will have a collector-emitter voltage drop of only some 0.1 to 0.4 volts, depending on construction and I_b and I_c , whereas the minimum voltage necessary at the base, for conduction, will be at least 0.5 volts in a silicon device.

The way in which this circuit is organized, with respect to its output circuitry, and its threshold, trigger, and reset inputs, is shown in Fig. 5. Because the transistor Tr_8 , in the reset circuit, acts as a switch directly connected between the positive end of D_3 and the discharge circuit open-collector amplifier, this will cause Tr_3 to be turned off, with Tr_4 and Tr_6 turned on. This will reset both A_1 and A_2 outputs to the low level.

While this input, being connected later in the circuit than the trigger input, will over-ride the trigger signal, if the trigger input is held low, the circuit will revert to the operating condition, with A_1 high and A_2 open circuit, as soon as the reset signal is removed.

The two input amplifiers used in the threshold and trigger circuits, are of similar form, as shown in Figs 6 and 7, using Darlington connected, four-transistor, long-tailed pairs. However, it should be borne in mind, as explained in the first article of this series on the 741, that the integrated circuit manufacturing process does not normally allow the construction of p-n-p transistors, within the i.c., which have a very high current gain, except in the circumstance that their collectors are directly connected to the substrate, (which is normally the 0V line). Since the input p-n-p transistors of the trigger circuit do not meet this condition, they must be of the 'lateral' type, which gives an inferior input impedance to this amplifier to that of the n-p-n input devices

p.s.d., whose other input is that from the tachogenerator pulse shaper. When the phase-locked loop of the speed-control system is in lock, the frequency from the tachogenerator pulse shaper is exactly that of the v.c.o., but it leads it in phase by about 90°. Consequently, the D input to the D-type flip-flop is at the logic 1 level when the Ck input goes positive, putting a logic 1 on the Q output of the flip-flop, lighting the l.e.d. and giving a visual 'in-lock' indication. With logic 0 on the \bar{Q} output, the audible indicator is silent. In the event of a loss of lock the l.e.d. will flash and the audible indicator will warble at a frequency dependent upon the rate of slippage between the two frequencies.

The output from the p.s.d. is passed to the motor drive circuit of Fig. 48(a) or (b). It is filtered by a lead-lag low-pass filter, consisting of the 100k input resistor to the 351 op-amp and the 39k plus 5µF capacitor (11µF in Fig. 48(b)) feedback loop. The low-frequency gain of the inverting op-amp is limited to unity by the 100k feedback resistor. The resulting out-

put from the op-amp drives the motor via the emitter-follower circuit using a Darlington power transistor, TIP121. The 10k resistor and base-collector feedback capacitor of 1nF provide some necessary high-frequency cut-off to the emitter-follower stage. The values of the filter components were found by trial and error to produce a stable and trouble-free p.l.l. servo system under all conditions of Play, Rewind and Fast Forward operation of the deck.


The direct offset voltage produced at the output of the op-amp by the potential divider circuit on the non-inverting input is essential to the self-starting action of the servo system. The 20k resistor should be adjusted such that the p.l.l. finds lock in one or two seconds after pressing the Play, Rewind or Fast Forward keys. If the voltage on the non-inverting input is too low, the p.l.l. will not find a 'lock', the

motor speed remaining too low; if it is too high, the loop will find and lose its 'lock', the motor speed ending up too high. When a satisfactory setting for the 20k resistor has been found it will be observed that the tachogenerator waveform leads the v.c.o. output by a little more than the ideal 90°. This phase difference will change a little under varying load conditions but should not vary so much as to lose lock.

The tachogenerator pulse shaper circuit shown in Fig. 48(a) is that for the motor with the built-in tachogenerator, while that in Fig. 48(b) is for the motor with the mechanically coupled magnetic disc and Hall-effect sensor. Because the output from the speed sensing circuit of Fig. 48(b) is exactly double that of Fig. 48(a), the output from the pulse shaper is divided by 2.

C.m.o.s. circuits of Fig. 47 and the pulse shapers of Figs. 48(a) and (b) are powered from a 15V supply, which is provided by a 15V, 100mA regulator powered by the cassette recorder's 20V stabilized supply line. The 20V supply powering the

Fig. 48. Motor drive circuit and tachopulse shaper. Version for motor Type R14-7430, 03Y8D is at (a), while that used for motor Type MMX-6H2LSB is shown at (b).

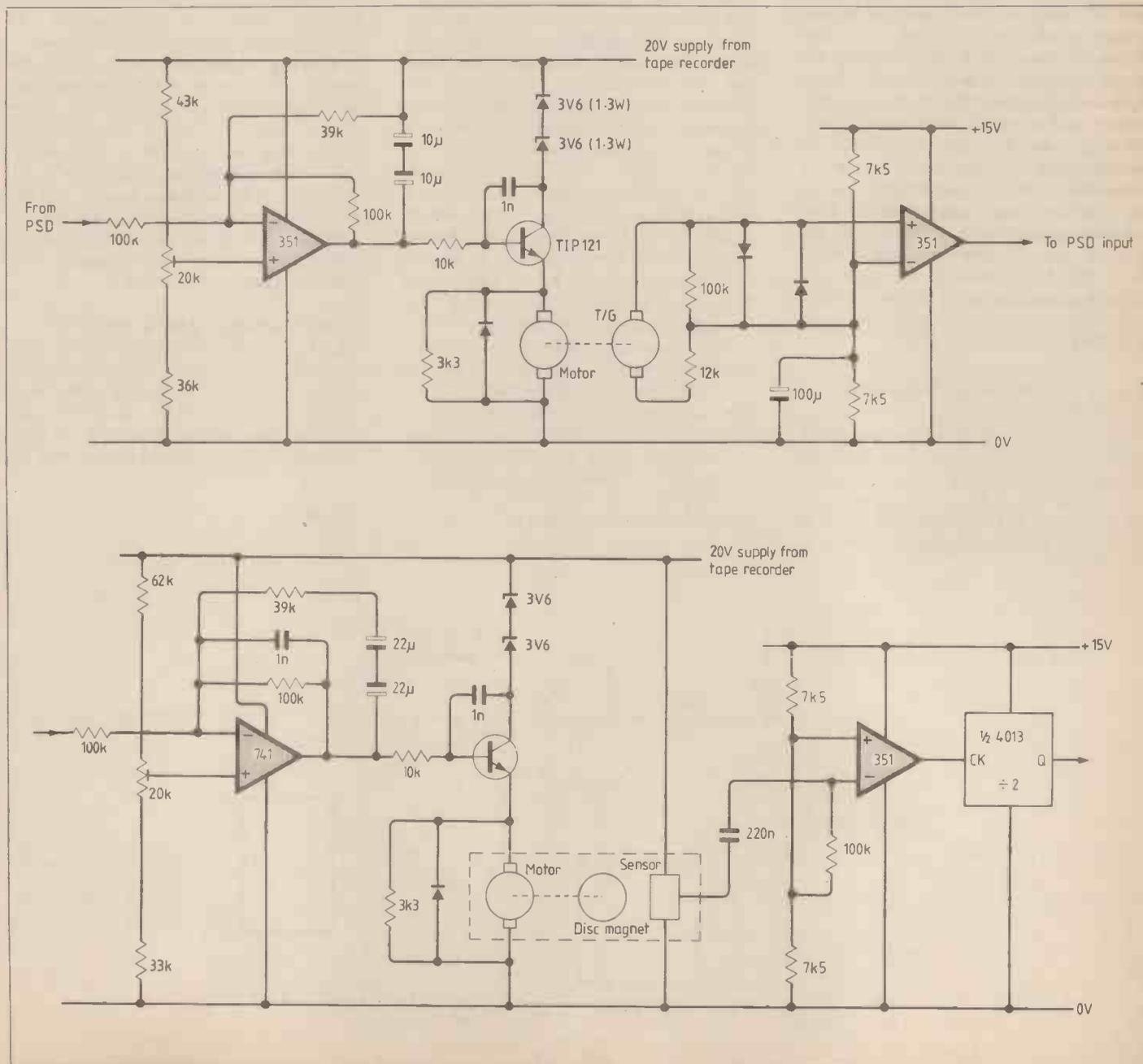

motor drive circuit is that normally supplied to the positive lead of the motor, switched by the various keys of the cassette deck.

Motor modifications

Both types of motor may be removed from their outer casings by careful removal of the back-plate. For motor type R14-7430, 03Y8D, the built-in electronics should be completely removed. The tachogenerator output is identified by two yellow leads, whilst the motor contacts are two terminal posts to which the internal p.c.b. is soldered. The two yellow leads should be extended, and two wires, red and black, should be soldered to the two terminal posts of the motor, making certain which is the positive and negative terminal. Reversal of these two motor connections will result in the motor running backwards, but no damage will be done.

With the back off the motor type MMX-6H2LSB, the frequency output of the Hall-effect sensor should be identified before any modifications are carried out. This is done by running the motor from a nominal 12V source and using an oscilloscope to identify the frequency output pin of the i.c. Having done this, remove the power transistor of the built-electronics: this automatically breaks the internal servo loop. A low-value resistor from the positive supply line to the positive pin of the motor drive should then be removed, and a link made from the negative pin of the motor drive to the negative supply line. Connections then need to be made to the positive supply line of the built-in electronics, the positive pin of the motor drive, the negative supply line of the built-in electronics and the frequency output pin of the Hall-effect i.c.

Use of the reference frequency circuitry

When operated with the rest of the digital electronics of the recorder, the reference frequency for the speed control circuit is supplied by the 'reference frequency circuitry', shown in block form in Fig. 11 of part 2. During the recording process, the

reference frequency is the TC frequency of 22,755.5Hz divided by 50, i.e. 455.1Hz. When this source is connected to the external frequency input of the motor speed control circuit, the internal v.c.o. source is automatically 'knocked-out'. The 4017 counter of Fig. 47 is continually reset by the presence of the external frequency source with the result that CO remains at the logic 1 level and the 5 output at logic 0. The external frequency source thus passes through Nands 2 and 4 to the input of the p.s.d., the output of Nand 3 being permanently maintained at logic 1.

On playback, the reference frequency presented to the speed control circuit is that from a v.c.o. whose output frequency is dependent upon the average voltage at its input, which is the filtered output of a p.s.d. comparing the crystal-controlled TC with the recovered TC from the recorded data of one track of the tape-recorder. Thus, on playback, the speed control of the tape is maintained by a p.l.l. servo system within another p.l.l. Some readers may think this a very curious system and wonder why the output from the p.s.d. comparing the crystal and recovered tape-clocks is not simply connected to the motor driver circuit. The answer to this is that the dynamics of the record and playback servo loops are totally different. On record, the tachogenerator is directly coupled to the motor, but on playback the recovered tape clock is mechanically coupled to the motor through the capstan and belt drive. It is not impossible to achieve a p.l.l. by the more obvious method, but it is very unstable and easily disturbed, losing lock, by any vibration of the deck. The solution used here is very much more satisfactory, offering as it does a very convenient method of switching from one reference frequency (on record) to another (on playback). by having a very much lower natural frequency for the p.l.l. of the reference frequency generator than for that of the motor speed control circuit, the instability produced by the belt drive mechanism is removed and there is no instability produced by one p.l.l. upon the other.

Power supplies

The Hart version of the Linsley-Hood cassette recorder is mains-powered but can very conveniently be made to operate from a 24 volt d.c. source. Because there was a requirements for the recorder to be operable independently of a mains supply it was decided that it, too, should be capable of operating from 24 volts d.c. As a result, the power supply of Fig. 49 was designed and constructed. Since a very large number of c.m.o.s. i.c.s are used in the digital circuitry it was decided that they were worth protecting from any over-voltage spikes. Consequently the 'crowbar' circuit was added: in the event of an over-voltage spike, the thyristor is triggered, causing the fuse in the positive supply rail to the 7815 regulator to blow. An over-voltage of approximately 16 volts is needed to trigger the 'crowbar' circuit.


A switching inverter circuit, shown in Fig. 50, is used to generate the negative rail voltage. The heart of the circuit is the 78S40 switching inverter. Using the values indicated, the output voltage from the switching inverter circuit across the 47µF capacitor should be approximately -18 volts, at a load current of about 120 mA.

This type of switching inverter does not operate very well under varying load conditions, so a shunt regulator is used to drop the -18 volts to -15 volts. Approximately 100mA is drawn from the -15 volt rail by the various analogue and digital i.c.s in the circuitry: there is thus no need for the 2N3053 transistor to be fitted with a heatsink. The 2N2905 transistor of the switching regulator also dissipates little power and needs no heatsink.

Modifications to tape-recorder

The Miller-coded data recorded onto tape is effectively a series of square-shaped pulses, ranging in frequency from about 5.5kHz to 11kHz, which should be modified, or distorted by the recorder as little as possible. The transient response of the

Fig. 49. Power supplies.

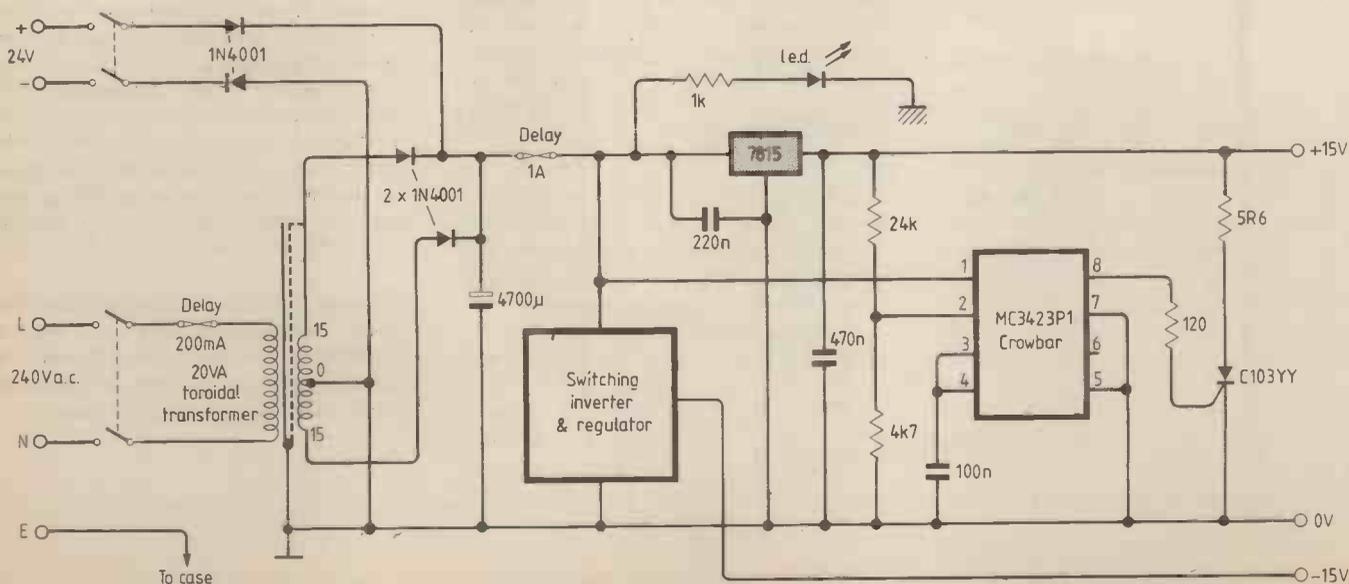

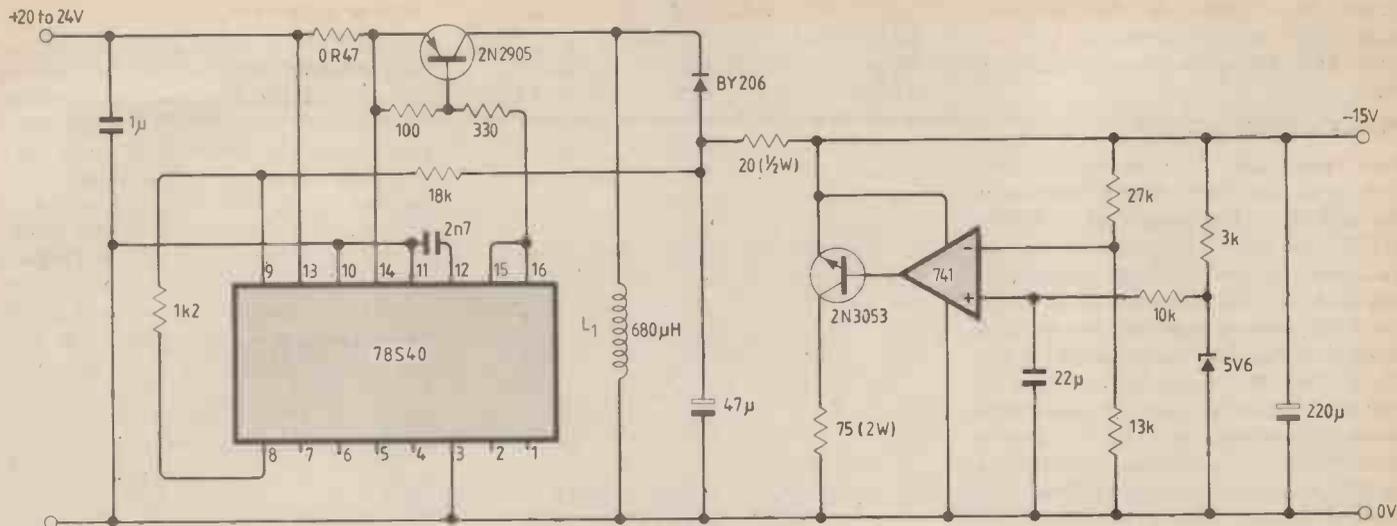


Fig. 50. Circuit diagram of switching inverter and regulator block seen in Fig. 49.

tape-recorder is more important, in its present use, than a flat frequency response.

To obtain the desired record/replay characteristics, the signal level, bias level and equalization must be adjusted. Firstly, the frequency response of any tape-recorder is the wider, the lower the signal level recorded. In normal use, the level of the signal to be recorded is a compromise between frequency response, distortion and signal-to-noise ratio: too high a level results in distortion and too low a level results in a poor signal-to-noise ratio. Signal-to-noise ratio is not a problem in the present use of the tape-recorder since the Miller-coded data is recorded at a constant signal level with no amplitude variation. The recording level can thus be reduced, improving the quality of the signal in terms of frequency response and distortion, provided, of course, it is not reduced to a level where noise imposes itself on the signal.

The level of the high-frequency bias can have a considerable effect upon the recorder's frequency response; high levels of bias producing an attenuation to the high frequency signals but some reduction in distortion.

Finally, adjustment of the equalization characteristic has a great effect upon the amount of high-frequency pre-emphasis and modifies considerably the transient response of the recorder.

In addition to all the possible adjustments mentioned, it must not be forgotten that the quality of the tape used is of prime importance. The author formed a considerable liking for Maxell UDXL II cassette tapes, both C60s and C90s. It is a CrO-type tape, requiring a high bias level and a 70µs equalization characteristic and has all the usual advantages of good frequency response, etc. The cassettes are also very sound mechanically. This is not the only suitable tape available — other tapes may perform just as well — but the tape recorder should be set-up using this tape. Having satisfactorily adjusted the tape-recorder to operate with the digital electronics, other brands of tape may be tried to determine their suitability.

When I began recording the Miller-encoded data on to tape to discover how well

the recorder performed, a problem occurred with the transport mechanism that was not immediately appreciated. The replayed signal, having passed through the peak detector and Miller decoder, was found to contain errors in the data stream which were initially thought to be due to the recorder's limited frequency response. Consequently, I experimented at length with the various adjustments mentioned earlier. Subsequently, the main reason for the errors in the replayed and decoded data was found to be due to jerkiness in the take-up spool of the tape-recorder, which was caused by incorrect operation of the slipping-clutch mechanism driving the take-up spool. The slipping-clutch was not, in fact, slipping, but the brass bush on the end of the slipping-clutch spindle, in contact with the rubber-tyred pulley of the take-up spool mechanism, was slipping jerkily. The problem was effectively cured by taking the slipping-clutch mechanism apart and 'weakening' its compression spring. The author is pleased to be able to say that a second tape-recorder, bought from Hart electronics at a later date, has a cassette deck with a modified slipping-clutch mechanism that gave no such problems. However, as a result of this fault, the author discovered a number of adjustments that should be made to the recorder to improve its record/replay characteristic of the Miller waveform.

- The 0dB recording level of 2.25 volts r.m.s. at the output of the recording amplifier should be reduced by about 4dB to 1.42 volts r.m.s., which corresponds, on playback, to an output from the replay amplifier of about 250 mV r.m.s., i.e. 4dB down on the original 400mV level. The 'VU' meter circuit sensitivity should be adjusted accordingly for a 0dB reading when the output from the recording amplifier is 1.42 volts r.m.s.

- The amount of high-frequency pre-

emphasis should be reduced to a minimum by adjustment of V_{r2} to maximum resistance on the recording amplifier board.

- The bias oscillator frequency should be raised from about 55kHz to nearer 80kHz by replacing the capacitor, C_{23} (10nF), of the bias oscillator circuit with one of 6.8nF and by changing R_{50} from 150 ohms to about 200 ohms.

- The 70µs record/playback equalization characteristic should be used and a slight improvement may be obtained by changing the value of C_6 , on the replay board, from 27nF to 18nF.

- The bias level should be high with the 47k variable resistor adjusted for the highest level possible. This should result in a bias voltage, as measured at the junction of the 47k variable resistor, and the 220pF capacitor C_{20} (L or R), of about 10V r.m.s.

The actual bias level does not appear to be very critical, but a high level produces a steadier signal, on replay, with less amplitude flutter. As the recorded signal has no low-frequency content below 5.5kHz the erasing effect of a high bias is of little consequence and the reduced distortion probably beneficial.

With all the above adjustments carried out, and the cassette deck operating in a mechanically satisfactory manner, little or no errors should be observed in the resulting replayed decoded data. Those errors that do occur should be due only to imperfections in the tape.

This concludes the series of articles. Strip-board layouts prepared by Mr Ewins are available in photocopy form: please write, including a large, stamped and addressed envelope, if you would like copies. □

AMATEUR RADIO

50MHz stays good

In the February WoAR I suggested rather prematurely that "fewer transatlantic signals have been heard on 50MHz this winter although some 28/50MHz cross-band working has proved possible". J. R. R. Baker, GW3MHW, near Aberystwyth, Dyfed, a devoted 50MHz enthusiast, feels my comment does less than justice to what, in his view, has proved to be an even more fascinating period than two years ago at the peak of Sunspot Cycle 21. Then, he admits, there were outstandingly strong 50MHz signals that enabled a number of British amateurs to work all ten American "call areas". Altogether some 150 British amateurs and more than 20 other Western European stations participated in the transatlantic cross-band working. A few European stations, including about a dozen in Holland, were permitted to transmit on 50MHz.

Good results were also achieved during the 1980-1 season, with rather more Central American and Caribbean signals. No high hopes were held for the 1981-2 season, yet GM3MHW considers it has proved as good, in its way, as the two previous years: a few openings in late October, daily openings throughout November (except November 7), almost daily in December, and occasional openings in January 1982. On January 27, GW3MHW made his 449th cross-band contact for the season, compared with about 400 in each of the two preceding years, including many Caribbean and South American stations. Ken Ellis, G5KW contacted 48 of the American States. Several British amateurs made 70/50MHz contacts with Canadian VE1ASJ.

These results, two years after the peak of Cycle 21, are being regarded as so encouraging that it is proposed to publish a regular newsletter for 50MHz enthusiasts (from G4JCC or G4JLH for modest payment to cover postages and stationery).

The GaAs mosfet

The current availability of lower cost gallium arsenide f.e.t. devices, including dual-gate mosfets at around £5 or less, means that receivers with noise figures of under 1dB and with good dynamic range can now be achieved by amateurs on 144 and 432MHz. Devices include the 3SK97 and 3SK98 developed in Japan for use in television receiver tuners but it is believed that comparable devices will soon become available from European firms. For example, D. J. Robinson, G4FRE, has measured 0.9dB noise figure with 18dB gain (circuit, not total system figures) at 430MHz. On 144MHz the French amateur F6CER has described a receiver front-end comprising a 3SK97 r.f. amplifier,

MD151 doubly-balanced diode mixer and P8000 impedance-converting grounded-gate amplifier, followed immediately by a 9MHz crystal filter. These GaAs mosfets are roughly one-quarter or less of the cost of most high-performance s.h.f. gasfets.

Further advances in the field of super low-noise GaAs mosfets have been reported recently by Hughes Aircraft who, with laboratory devices, have achieved a noise figure of 1.3dB with 10.3dB gain at 12GHz. The GaAs mosfet seem destined to play an increasingly important role at frequencies from about 100MHz upwards.

From all quarters

Following the example of the British teletext services, the Dutch Teletekst service by NOS now includes a page of information for the transmitting amateur.

When last November an incendiary set fire to a key telephone exchange in the Lyons area of France, some 50,000 telephone and telex lines, including trunk lines, were put out of action, local radio amateurs provided a special emergency communications service, handling urgent calls filtered through the police to ensure that all calls were of a non-commercial nature. They used h.f. bands and the FZ8VHF repeater.

Kathy Marsh, VK5NKM, the only amateur in Coober Pedy, an opal-mining town in central South Australia, operates from an unusual "dug-out" home some 20-feet underground. Such buried homes fashioned from former mines are popular in the township since they avoid the high summer surface temperatures (almost 50°C) yet remain comfortably warm in winter. Australia has some 15,000 licensed amateurs in a population of about 15 million people.

Shortly after Australian amateur Ray Naughton, VK3ATN, had climbed to the 45ft level of his 110-foot mast to make everything secure during a gale, a 100mph gust collapsed the tower. He escaped with some broken bones and a stay in hospital.

The Reseau des Emetteurs Francais has warned its members that some French c.b. associations are making demands on amateur frequencies in the 28, 144 and 432MHz bands. The society recommends that amateurs should show that they are making full use of these bands.

IARU Region 1 reports that the Irish Radio Transmitters Society will be 50 years old in June but can trace its beginnings to the Dublin Wireless Club founded in June 1913. First president of IRTS was Colonel J. M. C. Dennis, E12B (formerly DNX) who is widely believed to have been the owner of the world's first non-professional experimental wireless station, established in 1898. During World War II,

those Irish amateurs who were not enlisted in the Forces, offered their services as listening stations.

Awards knocked

Bill Verrall, VK5WV, writing in *Amateur Radio*, has strongly attacked many aspects of the emphasis on DXCC and other "award collecting" by amateur radio operators. He feels that country-chasing has led to such abuses as: "dx nets" claiming exclusive occupancy of spot frequencies; an increasing amount of deliberate jamming and interference; use of illegally high power; split-frequency operation by "rare" stations that spreads interference over many channels; blatant soliciting for "dx-pedition" funds and extraction of payment for QSL cards; and the use of QSL cards bearing political or "religious" messages. He also condemns the recognition of uninhabitable rocks and reefs as "countries" and the risks that this involves for those who set up stations at locations which may at times be entirely covered by the sea; "bootleg" QSL cards that may be entirely fake, or sent or sold to stations with which no contact has been made; and the widespread use of a standard RS(T) report of 59(9).

P. A. Wolfenden, VK3KAU, Federal president of the Wireless Institute of Australia, has pointed out that despite the growth in the number of training courses by clubs and educational bodies, newcomers still need more practical assistance from active and competent amateurs of experience: "the newcomer has to learn the ways of amateur radio, the procedures and the standards, and the various gentleman's agreements about such matters as band plans, correct repeater operating, etc . . . only a few clubs provide practical 'hands-on' experience".

In brief

Gerald Stancey, G3MCK identifies the "Early French Resistance suitcase set" in Toulon museum ("Clandestine Radio - the early years" February issue) as an early SOE equipment Type A, Mk II and draws attention to a book published in France "Armement Clandestin" by Pierre Lorain, F2WL which includes details and circuit diagrams of a number of British and German suitcase sets. The photograph by the way was taken by Dick Rollema, PAoSE . . . The 1982 RSGB VHF Convention is at Sandown Park, Esher, on March 20 . . . The Northern Amateur Radio Societies Exhibition is at Belle Vue Leisure Park, Manchester, on April 4 . . . Plymouth Radio Club has its third annual rally at Tamar Secondary School, Paradise Road, Millbridge, on May 30 . . .

PAT HAWKER, G3VA

E.P.R.O.M. PROGRAMMER

Most commercially available e.p.r.o.m. programmers are expensive as they include software and other facilities to enable them to be used on their own. The cost of a programmer can be significantly reduced if it is designed for use with an existing microprocessor system, as will be shown in these articles. The design presented is for 2708, 2716 and 2532 e.p.r.o.m.s, but with small modifications other devices may be programmed.

by H. S. Lynes


Sooner or later, probably all serious microcomputer system users in the hobbyist field will consider incorporating a program in e.p.r.o.m. (erasable programmable read-only memory). Unfortunately, commercial e.p.r.o.m. programmers are expensive and include facilities not essential for the enthusiast, who usually only wants to program the occasional device.

Commercial programmers fall into two main categories: those in the first category are expensive, have built-in data/address display and use 'personality' cards for programming different e.p.r.o.m. types. Units in the second category are very expensive. They have all the facilities of programmers in the first category but also include built-in v.d.u., tape interface, printer port, etc. All these programmers use comprehensive software and have large random-access memories to enable e.p.r.o.m.s to be copied or modified at will. But if an existing microprocessor system is used to control an e.p.r.o.m. programmer, these facilities are unnecessary.


If therefore explored the possibility of adding e.p.r.o.m. programming hardware to an existing system. The first problem

Port C connections	PC7	PC6	PC5	PC4	PC3	PC2	PC1	PC0	Hex
2708									
Function	logic	n.c.	26V	12V	n.c.	n.c.	address		
I.c. pin numbers			18	20			22	23	
Read	0	-	0	0	-	-	x	x	00
Write									
pulse off	0	-	0	1	-	-	x	x	10
pulse on	0	-	1	1	-	-	x	x	30
2716									
Function	logic	*	25V	n.c.	*	address			
I.c. pin numbers		20	21		18	19	22	23	
Read	0	0	0	-	0	x	x	x	00
Write									
pulse off	0	1	1	-	0	x	x	x	60
pulse on	0	1	1	-	1	x	x	x	68
2532									
Function	logic	*	25V	n.c.	address				
I.c. pin numbers		20	21		18	19	22	23	
Read	0	0	0	-	x	x	x	x	00
Write									
pulse off	0	1	1	-	x	x	x	x	60
pulse on	0	0	1	-	x	x	x	x	20

Notes: The hex. value is the code, or 'pin-profile', used for port C, ignoring the address. When programming 2716 and 2532 e.p.r.o.s, pin 21 is held high during the read cycle. Functions marked with an asterisk indicate that the port is used as a logic, i.e., the port is tied directly to the e.p.r.o.m. pin. Where x is given, both logic levels are used for addressing. PC7 is used to detect the high-impedance state after reset.

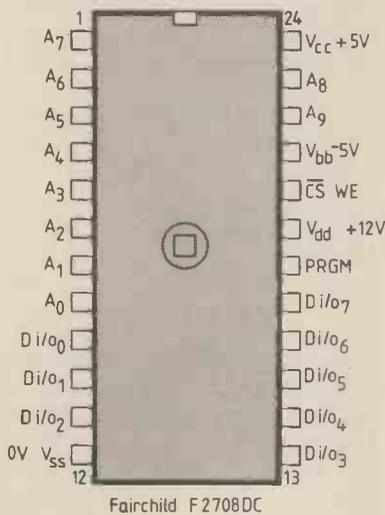


	Pin numbers			
Mode	18	19	20	21
READ	0V	+12V	0V	-5V
WRITE	26V*	+12V	+12V	-5V

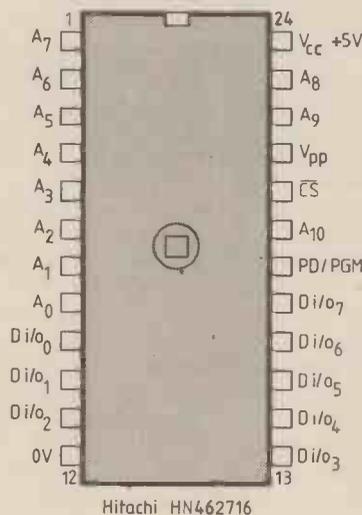

	Pin numbers			
Mode	18	19	20	21
READ	0V	x	0V	+5V
WRITE	+5V*	x	+5V	+25V

Pin 19 is used for the address


* pulsed

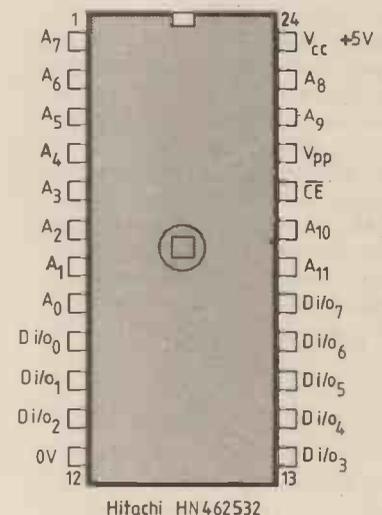

	Pin numbers			
Mode	18	19	20	21
READ	x	x	0V	+5V
WRITE	x	x	+5V*	0V* +25V

Pins 18, 19 are used for the address
Pin 20 is LOW during during WRITE, with 25 volts applied to pin 21.

Fig. 1. The three e.p.r.o.m.s for which the programmer was designed with tables showing control and programming logic requirements.

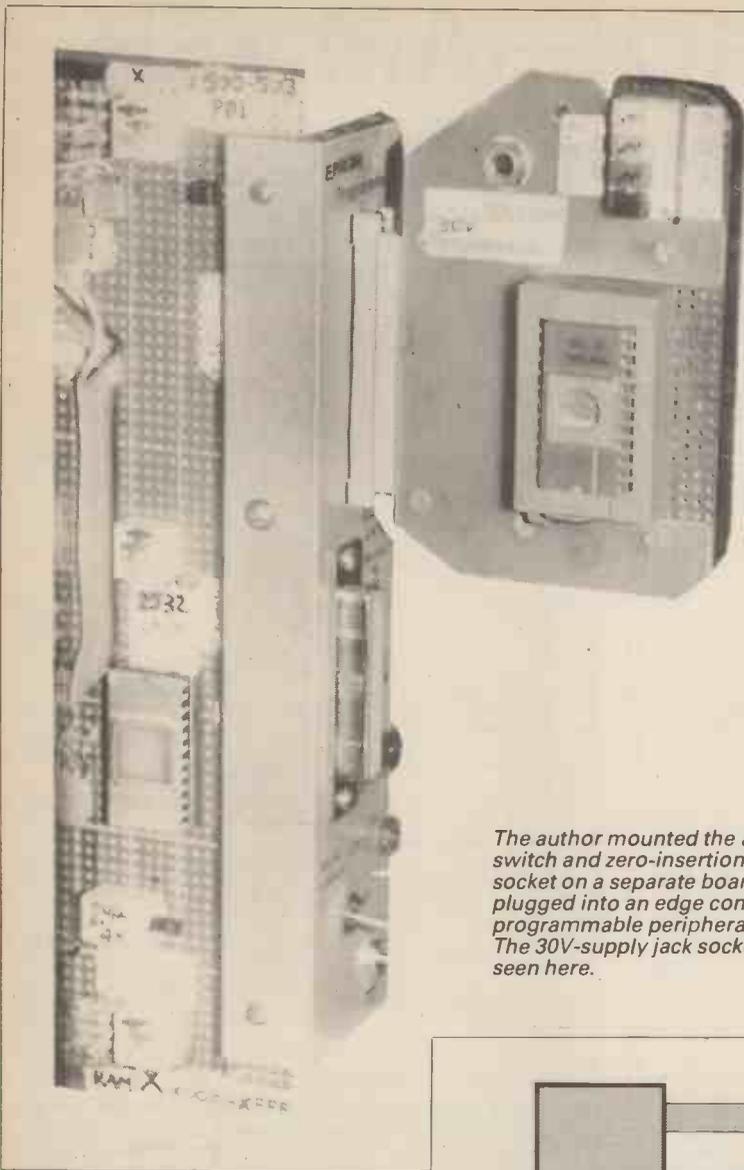

The author mounted the address d.i.l. switch and zero-insertion-force e.p.r.o.m. socket on a separate board which can be plugged into an edge connector on the programmable peripheral interface unit. The 30V-supply jack socket can also be seen here.

Table 1: Wiring from the 8255 p.p.i. and supplies to the e.p.r.o.m. programming board. Lines with prefix PA are for addressing and lines with prefix PB are for data. Prefix PC denotes lines used for both address and data.

E.p.r.o.m. socket pin numbers	Supply and p.p.i. lines
1	PA7
2	PA6
3	PA5
4	PA4
5	PA3
6	PA2
7	PA1
8	PA0
9	PB0
10	PB1
11	PB2
12	0V
	0V
13	PB3
14	PB4
15	PB5
16	PB6
17	PB7
18	PC5
19	+12V
20	for 2708s PC4
21	-5V
22	PC1
23	PC0
24	+5V
(18)	PC3
(19)	for 2716/2532s PC2
	+30V
	PC7
(20)	PC6
(21)	PC5
	PC4
	Reset
	R/W
	+5V
	02
	02
	spare

encountered was that programming requirements for different types of e.p.r.o.m. can vary considerably. Also, there is no standardization in pin configurations. So, taking into account the popularity, price and availability of various e.p.r.o.ms, it was decided that the programmer should be designed for 2708 and 2716 (5V supply) e.p.r.o.m. types. As the 2532 looked promising at that time it was also included. The latter device is similar to the 2716 both in pin assignments and programming requirements, although its inclusion meant that an additional address line would be needed. Design objectives were thus as follows:

E.p.r.o.m. type	Organization	Requirements
2708 (3-rail)	1024 × 8	500µs programming pulse, sequential programming
2716 (5V)	2048 × 8	50ms t.t.l. programming pulse, bit-selectable programming
2532	4096 × 8	50ms t.t.l. programming pulse, bit-selectable programming

For the 2708, I used data published by Intel, which covers the subject of e.p.r.o.ms at length. This data was used to

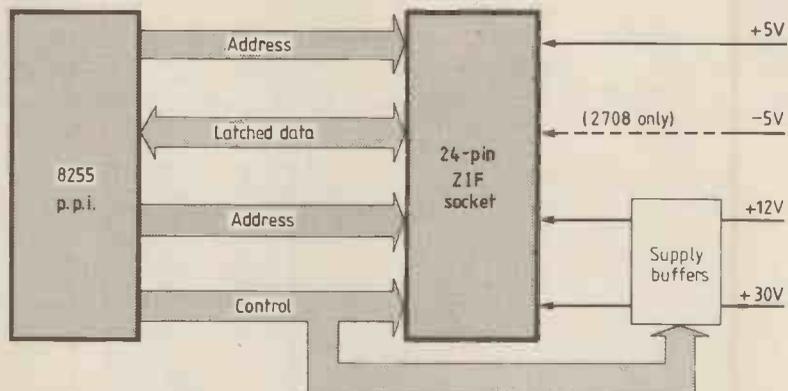


Fig. 2. Simplified block diagram of the programmer.

define the programming pulse rise-and-fall time limits of 0.5µs-2µs. For the 2716, Mostek data was used (which agrees with Fairchild and Hitachi data), and for the 2532, Hitachi data. The latter manufacturer's data was easiest to understand*. Pin configurations and level requirements are given in Fig. 1.

Although these three devices are at present the most popular, readers designing new systems using e.p.r.o.ms might want to omit the 2708 programming facility, since one 2716 can be obtained for less than the price of two 2708's. Furthermore, the 2708 must be programmed in small

* This could be a useful tip for aspiring technical writers - Ed.

stages sequentially - a process often called 'spray-coat' programming. This is inconvenient when developing using 1K × 8 devices but if 2 or 4K devices are used, the method is intolerable. Fortunately, later devices may be programmed bit-by-bit as required. Inclusion of the 2532 programming facility is now justified, since it can be obtained for less than the price of two 2716's. The reasons for not including the 1702 among the chosen e.p.r.o.ms are that in my view, programming of it requires twisted logic, it is relatively expensive and it cannot be used with the software for the chosen devices in read mode.

The programmer was designed for use with a 6800 microprocessor system but is based on an 8255 programmable periph-

pheral interface (Intel or National Semiconductor). Some extra logic is required to drive the 8255 control pins but this p.p.i. provides three 8-bit ports and programming is relatively simple. If the 6821 had been chosen, two i.cs would have been required and programming would, in my view, have been more difficult: there is no reason why support devices should not be chosen for their ability to fulfil objectives.

The 8255 is used in mode 0 (see manufacturer's data for further information) with the 8-bit ports A and C as outputs and port B as either input or output depending on the control word stored in one of the device's four memory locations. By changing port B from output to input it is possible to check that data entered into the e.p.r.o.m. has been correctly received. This function corresponds to the verify function of expensive programmers.

Since e.p.r.o.m. bits are all at logic 1 when the memory is empty, it would be possible to check the amount of memory available in partly full 2716/2532 devices. Unfortunately, the 6800 uses instruction FF to store the index register so confusion could result if the end of the existing program used FF as an instruction or address.

It is advisable to finish programs with three 00's to avoid the risk of placing a new program over the top of an existing one.

Fig. 4. Address decoding for the 8255 and one other device (see text).

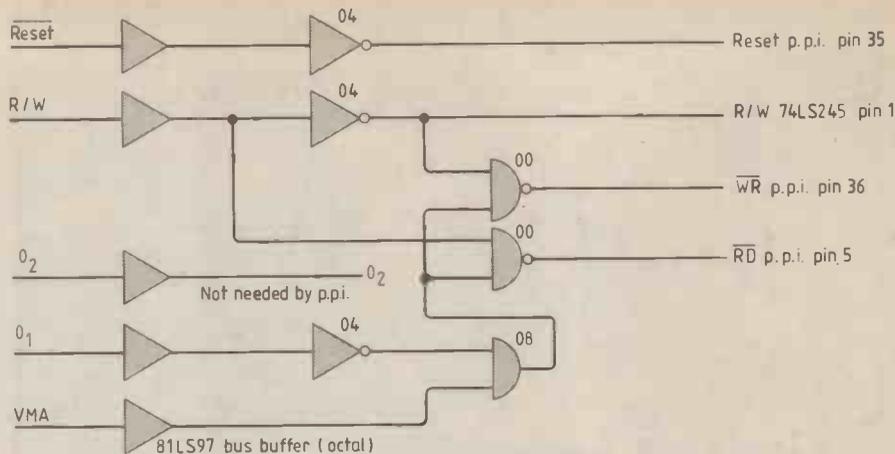
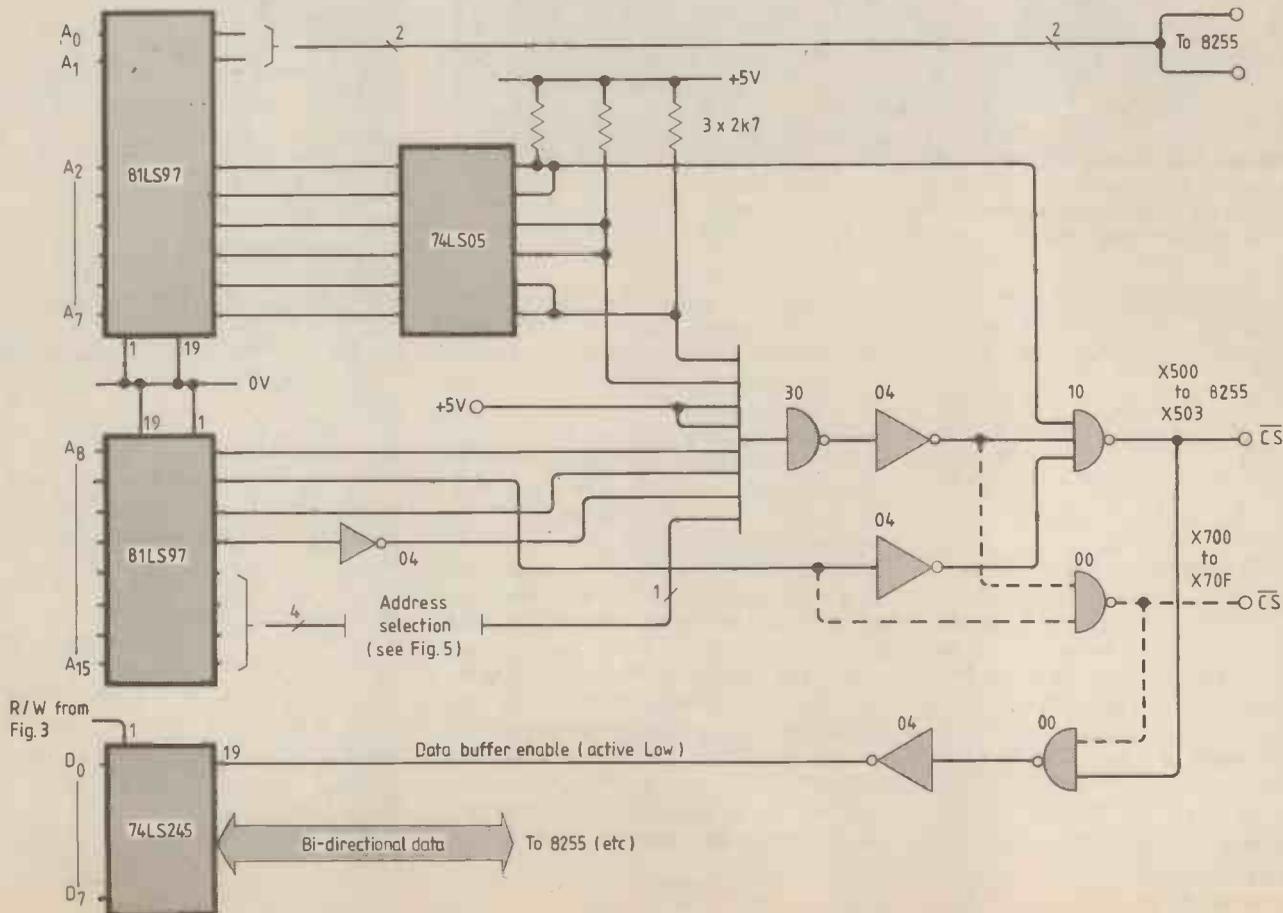


Fig. 3. Logic for converting outputs from a 6800 processor for use with an 8255 p.p.i. If an 8080 processor is used to control the programmer, this conversion is not required.


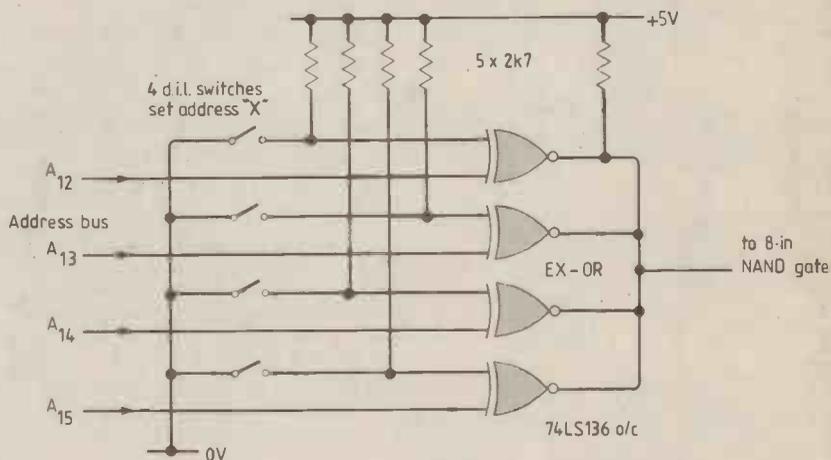


Fig. 5. Circuit for selecting the most significant digit of the p.p.i. address (see Fig. 4).

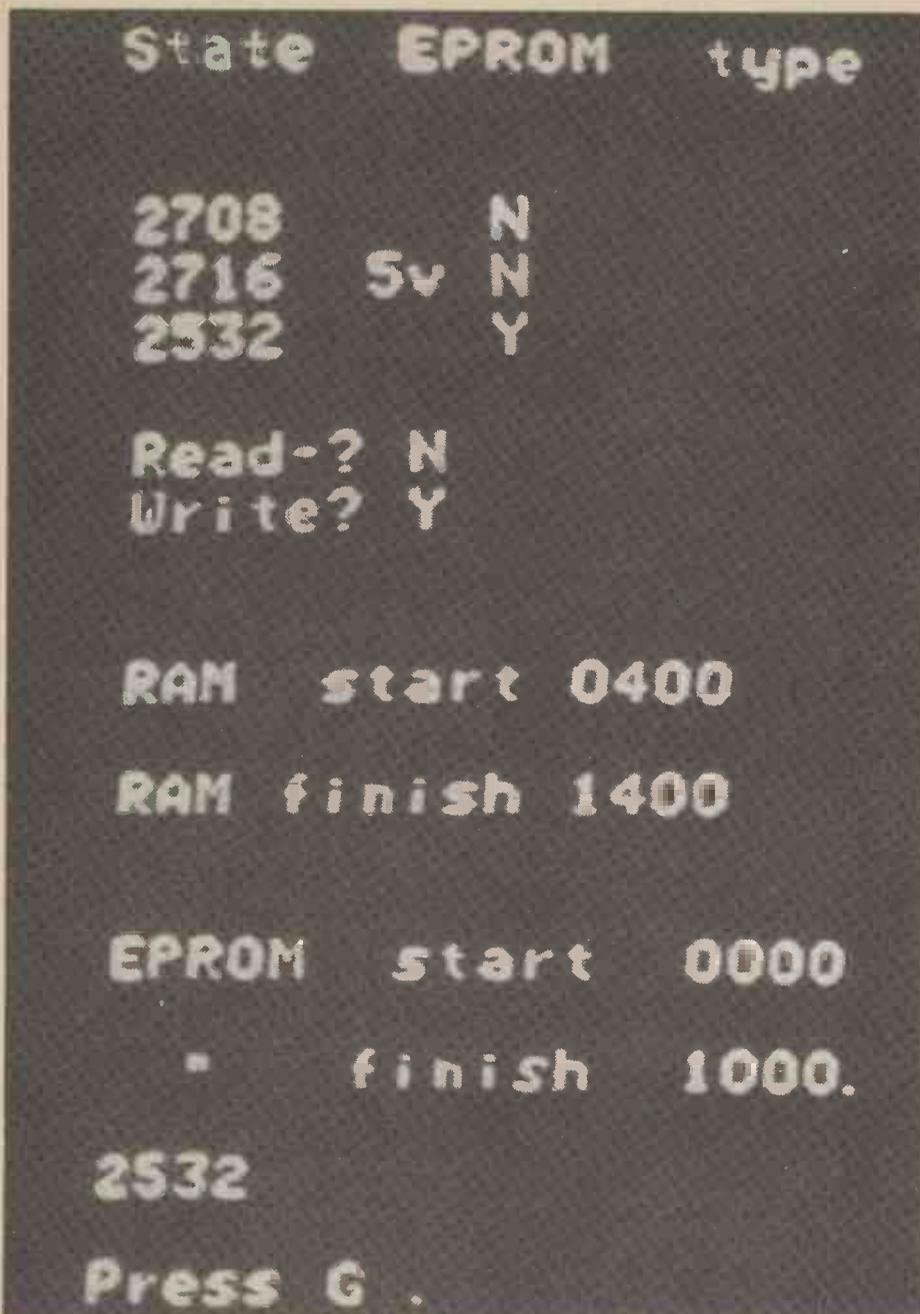

This photo is an example of the author's display and illustrates the type of prompting that may be used. Because of the differences between microprocessor systems, a full software listing is not given, but a 'scratch-pad' and software outline will be included in the next article.

Also, a careful note of the current program state of each e.p.r.o.m. should be made. Colour coding the i.cs makes it easy to log their history.

Figure 2 is a block diagram of the programmer, and logic conversion for driving the 8255s RD and WR lines from the 6800 is shown in Fig. 3. If an 8080 processor is used to control the programmer, this conversion is not required.

The 8255 address, see Fig. 4, requires four consecutive locations. In my system the address is fully decoded, but the four most significant address lines can be altered using a d.i.l. switch as shown in Fig. 5. The four locations are from X500 to X503, where X may be from 0 to F depending on the d.i.l. switch setting. Being able to change the address is useful if the 8255 is to be used as a general purpose port, as opposed to being dedicated to e.p.r.o.m. programming.

Table 1 shows lines from the p.p.i. to

the board on which the programming socket, switching between 2708 and 2716/2532 functions, and a voltage regulator were mounted. In the table, pins 18 to 21 of the programming socket are shown connected for programming the 2708. In practice, pins 18 to 21 are connected to a 4-pole, 2-way d.i.l. switch so that they may be taken to PC3, PC2, PC6 and PC5 respectively when 2716/2532 e.p.r.o.ms are to be programmed. PC5 is a 25V signal and PC4 a 12V signal, the conditioning circuits of which will be shown later. PC7 is used to check logic but it could be used to detect changes on pins 18 to 21, or even omitted to reduce the number of lines from the p.p.i. circuit to the programming board. 37 lines were used, as shown in the table but by omitting unwanted lines, combining the 0V rail and bringing in the 30V supply separately, the total may be reduced to 30. □

To be continued

IN OUR NEXT ISSUE

Digital filter design

Accuracy, versatility and a rapidly declining cost will ensure that digital filters take over from their analogue counterparts. A new series gives their theory, design techniques and microprocessor implementation.

Program exchange by telephone

There is a growing need to facilitate the easy exchange of programs and data from one person to another. Philip Barker discusses program distribution and the design and implementation of software systems capable of loading source code programs into memory.

Orchestral sound, halls and timbre

Taking the Kingsway Hall as a model, Denis Vaughan investigates the effect of concert hall shapes and sizes, and the working of the filtering of the outer ear on timbre and perceived directionality.

**On sale
April 21**

Polytechnical computer

The opening of the new computer centre at Coventry Lancaster Polytechnic was accompanied by a civic reception and a protest demonstration by some of the students. The centre has been constructed to house two Harris computers which provide impressive processing power with storage capabilities for a high volume of batchwork and can service some 100 terminals distributed over the Polytechnic campus.

The centre incorporates a Harris 800 computer system which has 2 megabytes of memory, with four 300-megabyte disc drives and one 80-megabyte disc drive, a line printer, card reader, a 9-track magnetic tape unit and a CIL plotter.

Also housed in the same building is a Harris H500 computer, a separate system with one megabyte of memory and one 300-megabyte disc drive with a line printer, a card reader, a magnetic tape unit and a paper-tape reader/punch.

Elsewhere on the campus is a Harris H100 for the polytechnic's Electrical and Electronic Engineering department. Eventually it is planned to connect all three computers together by synchronous links into one processor network.

The system is the biggest Harris system outside the United States and is claimed to be



The Computer Centre at Lanchester Polytechnic, Coventry, specially built to house the computer facilities, including the two Harris Computers and some special terminals.

the largest available to any further educational establishment in the UK.

The student protest was very civil and was not about student grants, despite the presence

of the Parliamentary Under-secretary of State, Department of Education and Science, Mr William Waldegrave; it was about the delay in getting the computer actually working, their work was being delayed by the lack of terminal time as only a few were actually running. Harris assured us that these were teething problems and that they were flying a team of specialists from their factory in Florida to assist in the initialisation of the system.

Timex to sell Sinclair in the U.S.A.

You may know that the Sinclair ZX81 Microcomputer is manufactured under a sub-contracting agreement by the Timex Corporation in their Dundee factory. The current production rate is about 30,000 units each month, which some clever mathematician has

worked out to be one unit every ten seconds. Timex seem to be impressed by the sales and have come to an agreement with Sinclair Research, whereby they can sell a Sinclair/Timex computer in North America. Sinclair are at present selling in the U.S. by mail order at a rate of

15 thousand a month; Timex have about 170,000 retail outlets in North America, and could sell at a phenomenal rate.

The agreement is for Sinclair to provide the technical expertise and for Timex to manufacture a computer which will include their own brand name. The name is not to be more prominent than the Sinclair marque which will remain on the equipment.

Timex will pay Sinclair a 5% royalty on all hardware that is related to the Sinclair microcomputer, even if it is not originated by Sinclair. They will also pay a 5% royalty on any Sinclair originated software. And they will even pay 2½% on software from any other source as long as it is intended for use on the Sinclair equipment. There will be a cross-licensing agreement for any hardware that Timex may develop themselves.

Clive Sinclair says that he has been looking for a large marketing outlet for his products for some time. He intends to keep Sinclair Research as a compact research and development team, concentrating on improvements to existing products and development of new ones. The date for the probable launch of the Microvision flat tv is given as the last quarter of 1982. It has already been announced that the tv is being incorporated into a desk-top terminal for ICL, and there may be some clue as to the likely format of the next-generation ZX computer in that. Sinclair's research into electric vehicles is continuing.



The Sinclair ZX81 which is to be manufactured, and marketed in North America, by Timex. The ZX81 is shown together with the add-on 16K RAM pack and the ZX Printer.



Having produced new versions of their pre- and power-amplifiers and their electrostatic loudspeakers, Quad have come up with an f.m. tuner, the Quad FM4. It has been styled to match the Quad 44 pre-amplifier with which it is shown. It incorporates a microprocessor which can recall the preset stations from memory and also controls inter-station muting and a.f.c. Manual tuning is used to program the seven preset stations and occasionally to tune in to a station not already programmed. A bar graph displays signal strength and centre tuning. The preset buttons and the tuning knob are the only controls: the microprocessor takes care of everything else.

Teletext, a new campaign

One way to mass market viewdata is believed to be the growth of private viewdata systems which are compatible with Prestel; used by companies for in-house systems. Another way is the development of a more attractive Prestel package for the consumer.

It was decided at the conference that Prestel could be made more attractive to the consumer by:

- working towards a consumer package, providing an overall viewdata service which would include transactional applications, i.e. the ability to order goods by pressing the appropriate buttons;
- including entertainment and communications as well as 'straight' information;
- examining the tariff structure;
- working towards a reduction in the cost of viewdata receivers;
- improving the quality and attractiveness of the information provided;
- promoting new applications of business viewdata;
- working towards the acceptance of viewdata as the principle means of communication between business and industry.

Further analysis of the view expressed at the conference will lead to the publication of another 'action document'. October has been selected as National Teletext Month as was October last year, this will be used for an intensive campaign to promote teletext.

1982 is Information Technology Year, and as part of the Government's commitment to IT, the Department of Industry is promoting further awareness of Teletext and Viewdata.

According to a survey published in Prestel (page 19191), 65% of the population now know what Ceefax is; for Oracle it's 55%, teletext, 50% Prestel 30% and viewdata 15%. There are still 20% who have no knowledge of any of these. Television viewers with facilities to receive teletext numbered over 300,000 at the end of 1981.

This is a result, claims the DoI, of the promo-

tion campaign launched at a 'Commitment Conference' in January 1981, which brought together the manufacturers of the equipment with the information providers, with television rental and retail traders, software suppliers, trade associations and with representatives from British Telecom, the DoI and the NEDO. One of the chief aims of the campaign was to familiarize consumers with the process of obtaining information from the tv screen. It is believed that such familiarization could lead to more recognition for Prestel, BT's telephone viewdata system.

In February of this year, another Commitment Conference was held in London to plan a further campaign for 1982. Once again the accent would be on promoting teletext to the general public and Prestel to the business community.

Free specifications and standards

London Information have started a free consultancy service to help engineers identify and acquire the specs and standards or other documentation they may need for their projects. Enquiries are already running at hundreds of 'phone calls a week. The documents are not confined to the electronics industry and London Information have told us that they have recently supplied copies of quarantine regulations for Australian wallabies and building regulations for a middle east sports complex. They provided an electronics firm with the relevant US Mil specs and this resulted in a big export order to the US.

London Information claim to be able to get any available document from anywhere in the world. If they cannot supply the information then they will put companies in contact with a source that can. Further details can be obtained from: London Information (Rowse Muir) Ltd, Index House, Ascot, Berks SL5 7EU. Telephone: 0990 23377.

Arthur C. Clarke honoured

The science writer, Arthur C. Clarke has been chosen to receive the eighth Marconi Fellowship Award by the Marconi Fellowship council.

The \$35,000 award is given annually in recognition of scientific achievement for the benefit of humanity in the field of communications science and technology.

Clarke predicted the geosynchronous communications satellite as early as 1945 in the *Wireless World* article "Extra-terrestrial relays: can rocket stations give world-wide radio coverage?". We issued a reprint of the article with our October 1981 issue. In it, he addressed very specifically the technical issues involved in such satellites, which have since become such a significant part of the earth's communications.

Clarke's other innovations include the use of satellite platforms for observing the earth in a quantitative manner, the concept of the manoeuvrable solar sail for low-acceleration interplanetary flight, and the concept of the 'space elevator' for reaching orbital altitudes using materials of very high strength/weight ratio which are likely to be developed soon.

Recently, Arthur C. Clarke has been strongly supporting proposals for the use of satellites for communicating with remote communities. Many such systems have been installed in villages in Alaska and Canada.

As far as the general public is concerned, Clarke is best known for his science fiction writings, especially for his collaboration with Stanley Kubrick on *2001: A Space Odyssey*. Rumour has it that they are to work together again on another s.f. film.

Mr Clarke is now the Chancellor of the University of Moratuwa in Sri Lanka.

● The Marconi International Fellowship was founded in 1974 by Gioia Marconi Braga, daughter of the Italian inventor, Guglielmo Marconi. It is sponsored by companies and institutions from ten different countries.

Licence sensation

There is a belief that the Home Office has made another "snafu" and will be forced to rescind part of a new schedule which appears to contain a host of technical errors and misreading of the International Radio Regulations. A four-page Home Office announcement appeared in the London Gazette on February 12 addressed to "all holders of Amateur (Sound) Licence A and Amateur (Sound) Licence B" setting out a new schedule of frequencies, classes of emission and power limitations "as from January 1, 1982." These are regarded as "unacceptable" by the R.S.G.B. which immediately called for urgent discussions with the Home Office. The new schedule, as printed, not only introduces the new international symbols and defines power in terms of output to the aerial in dBW, But also removes 10kHz from the British 1.8MHz band, restricts 3.5MHz transmission to the very low power of 9dBW (carrier power), compared with 20dBW for other h.f. bands, and also introduces an entirely new form of power restriction (30dBW maximum equivalent isotropically radiated power) for all bands above 1.2GHz. There are also many other apparent technical anomalies that are inexplicable in any rational technical terms.

A Home Office spokesman has told us that it was all a terrible mistake based upon a series of mis-prints. It must be pointed out however that publication in the London Gazette makes it a legal announcement.



The Husky 144 by DVW Microelectronics is a sturdy, waterproof microcomputer for data entry in the field

Computers in the field

The computer industry at the moment seems obsessed with 'the man in the field', the roving executive, salesman, engineer or even the journalist. The theory is that these peripatetic representatives can feed in the latest information, deal, sales figures or stories down the line to their parent companies.

One approach to this is illustrated by the new portable terminal by Digital Equipment Corp. The Correspondant is a hard copy printer terminal about the shape and size of an electric typewriter. It can handle plain paper and can have tractor feed as an additional option. It offers 132-column printing with a range of typefaces and because it is bit-map addressable it offers high resolution graphics (132 x 72 dots per inch) and can be used in conjunction with Digital's visual display terminals. What makes it portable is the 'universal' power input which will accept any a.c. mains supply of any voltage or frequency. It may be fitted with an acoustic coupler to communicate with the base computer. Digital are eager to point out however that it is also highly suitable as a fixed printer terminal with an RS232 interface.

The Digital Correspondant is a terminal and must be connected, by whatever means, to a computer to be of any use. An alternative approach is the portable computer. This has the advantage of being able to collect data 'in the

field' and one example, the Husky 144, made by DVW Electronics, has been designed with a tough case and a flat, touch-sensitive keyboard. It can be used literally in the field, out of doors. It has a liquid crystal display of up to 128 characters in four lines. It is battery powered and thus can include an internal memory which does not lose its data and real-time calendar and clock so that entries can be 'tagged' with collection time automatically. The Husky 144 is provided with 144K-bytes of memory and has 'user-friendly' software. A key marked 'Help' may be pressed at any time during operation and a part of the internal 'manual' is displayed on the screen giving information on what to do next.

To communicate with the outside world the Husky 144 can use an RS232 interface for direct communication with a host computer or a printer. It can use an acoustic coupler for telephone contact. It can also be used as its own base station and may be plugged into an optional disk drive for storage and retrieval of files. With a disk drive it can also be operated under CP/M which gives it access to a large library of commercial programs.

Correspondant - Digital's plain paper portable terminal designed 'for executives on the move'

Xenix and the supermicro

Xenix is the name of a computer operating system for use on 16-bit microcomputers. It has been developed by Microsoft and is an implementation of Unix, a software system originally developed by Bell Laboratories for use on DEC minicomputers, first on the PDP-7 and later on the PDP-11. Xenix is the 16-bit operating system which seems likely to become a standard, much as CP/M has become for the 8-bit processor. One advantage it has is that there are comparatively few codes which are specific to a particular processor; so it can be fairly easily implemented on many 16-bit processors.

All this is by way of introduction to the Bleasdale 600 Xenix computer which uses the Zilog Z8001 16-bit microprocessor. The Z8001 runs at 4Mhz and can address up to 8 megabytes of memory through a 23-bit address bus. The Bleasdale computer is a general-purpose applications for professional system designers and engineers and may be used in simulation, process control, image processing, instrumentation, scientific workstations. It may also be used for office automation equipment, communications networks, banking/financial systems etc. The first customers are the Monotype Corporation, who will use the computer for typesetting, and Precision Software, a financial information services company.

The 600 computer is of modular design, constructed from a range of plug-in p.c.bs which offer a wide range of different configurations. The boards are interconnected using the Multibus system with 24 address lines for up to 16 megabytes of memory.

The computer is manufactured at Bleasdale's factory in Lutterworth, Leicester, and is to be marketed through a network of distributors



throughout Europe. The majority of the computers are likely to be sold to O.E.M.s. A version of the computer based on the Motorola M68000 processor is being produced and this will also operate on Xenix.

Eddie Bleasdale the managing director of Bleasdale Computer Systems believes that Xenix will be very popular in scientific and educational applications because of the widespread use of Unix in DEC computers. As Bleasdale are in the forefront of users of Xenix, he intends that his company will maintain that position and become a leading centre of expertise in Xenix/Unix.

● Zilog have given their official blessing to CP/M and Unix have warned that manufacturers should be wary of 'lookalike' systems. Traditionally a new computer system engendered a

new operating system which became 'machine-dependent'. So if a computer system was selected the operation system went with it and the user became stuck with it. If, however, the operating system were selected first then a number of manufacturers could offer computers which operated the system. CP/M and Unix are suitable candidates but some systems are being marketed as 'Unix-like', for example, but do not have the universal application or constant development of the original. One has a feeling that the warning may not be entirely altruistic; CP/M and Unix both operate on Zilog equipment.

SIMPLE POWER AMPLIFIER

Complementary Hexfet devices offer improved performance over the equivalent bipolar output stage and allow simplified drive circuitry. This design delivers 60 watts into a four-ohm load, 32 watts into an eight-ohm load, from a simple $\pm 30V$ supply.

by Peter Wilson

International Rectifier Co

The split power supply rails of this design give good rejection of supply voltage ripple allowing both a simple supply circuit to be used and the load to be directly coupled. The output devices operate in the source follower mode, which offers a two-fold advantage: the possibility of oscillation in the output stage is reduced as voltage gain is less than unity, and signal feedback through the heatsink is eliminated as the drain terminal, which is electrically connected to the tab on the TO-220 package, is at a direct voltage.

Symmetrical output is achieved by providing a "boot-strapped" drive to the gate of the n-channel device from the output. The use of the bootstrap circuit, C_4 , R_8 , R_9 , also allows the driver transistor to operate at near constant current, which improves the linearity of the driver stage. The diode clamps the bootstrap circuit, restricting the positive voltage at the gate of Tr_5 to $+V_{DD}$ to maintain symmetry under overload conditions.

Transistor Tr_3 and resistors 11, 12 & 13 provide gate-source offset voltage for the output device with R_{12} variable to adjust quiescent current for variation in threshold voltage. A degree of temperature compensation is built into the circuit as both the emitter-base voltage of Tr_3 and the combined threshold voltages of the f.e.t.s have a temperature coefficient of $-0.3\%/deg C$.

The class A driver transistor operating at a nominal bias current of 5mA set by R_8 , R_9 is driven by the p-n-p differential input pair biased at 2mA by R_3 . Components R_7 , C_2 set the closed-loop gain of the amplifier R_6/R_7 and provide low-frequency gain boosting. Additional components R_{15} , C_7 connected between the output and ground suppress the high-frequency response of the output stage, allowing the h.f. performance of the amplifier to be determined by the input circuit. Component R_1 , R_2 , C_1 at the input of the amplifier define the input impedance and suppress noise.

To achieve 60 watts into a four-ohm load, the current in the load is 3.9A r.m.s. or 5.5A peak. To sustain this source current, the n-channel Hexfet, IRF533, requires a gate-source voltage of 5V.

As peak load voltage is 22V, gate bias voltage to achieve peak power in the positive sense is $V_{pk} + V_{gs} = 27V$. A similar calculation for the negative peak, using the p-channel device IRF9533, shows that a negative gate bias supply of $-28V$ is required. Consequently, a $\pm 30V$ supply is adequate for a 60 watt output, provided that the supply voltage does not fall below $\pm 28V$ when loaded: a source impedance

of one ohm or better. When the supply voltage impedance is high, use a higher voltage supply together with complementary Hexfets of a higher voltage rating — IRF532/IRF9532.

When an eight-ohm load is used, 32 watts output power can be achieved from a $\pm 30V$ supply with source impedance better than two ohms.

The curves drawn in Fig 1 show the power consumption of the amplifier, output power and power dissipated in the f.e.t.s as a function of r.m.s. output current with $\pm 30V$ supplies and four and eight-ohm loads. It can be deduced that the maximum power dissipated in the devices is 56 watts and 28 watts with four and eight ohm loads respectively. Limiting the case temperature to $90^\circ C$ and making an allowance for the thermal impedance of insulating washers, heatsink requirements are $0.5^\circ C/watt$ with a four ohm load and $1.67^\circ C/W$ with eight ohm load. Smaller heatsinks may be tolerated if the amplifier is not operated continuously at rated output power.


Open-loop gain measured with gate and source connections to the f.e.t.s broken is 30 dB, $-3dB$ points occurring at 15Hz and 60kHz, Fig. 2. Closed-loop curves are shown for amplifier gains of 100 (R_7 470 Ω) and 20 (R_7 2.2k). In both cases the curves remain flat to within $\pm 1dB$ between 15Hz

and 100 kHz with an eight ohm load. The slow rate of the amplifier, measured with a 2V pk-pk square wave input is 13V/ μs positive-going and 16V/ μs negative-going. The discrepancy could be balanced out by addition of a series gate resistor for Tr_6 .

Reduction of the closed-loop gain from 100 to 20 produces a significant improvement in distortion figure, Fig 3. Considering the simplicity, performance is quite acceptable. The output stage quiescent current was adjusted to 100mA and can influence the distortion measurement significantly if allowed to fall below 50mA.

The dependence of the quiescent current in the output stage and of the output offset voltage on power supply voltage are illustrated in the Table. Current is set by first adjusting the potentiometer R_{12} for minimum offset voltage — turned fully anticlockwise if the p.c.b. layout shown is used — and apply the power supply voltage, the positive supply passing through an ammeter with 1A f.s.d. It is then adjusted until the meter reading is 100mA with a $\pm 30V$ supply. Remove the meter from the circuit before applying an input signal to the amplifier.

When assembling the printed circuit board, mount the passive components first, ensuring the correct polarity of electrolytic capacitors. Then solder in bipolar transistors, checking for correct pin identification. Finally mount the f.e.t.s, avoiding static discharge by shorting the pins together to ground and using a grounded soldering iron. Check the assembled board for correct component place-

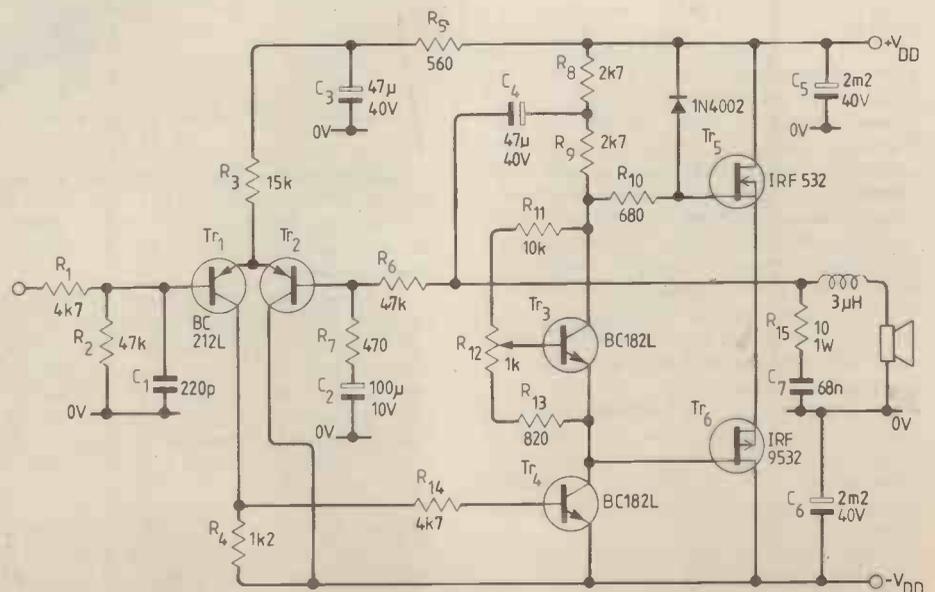

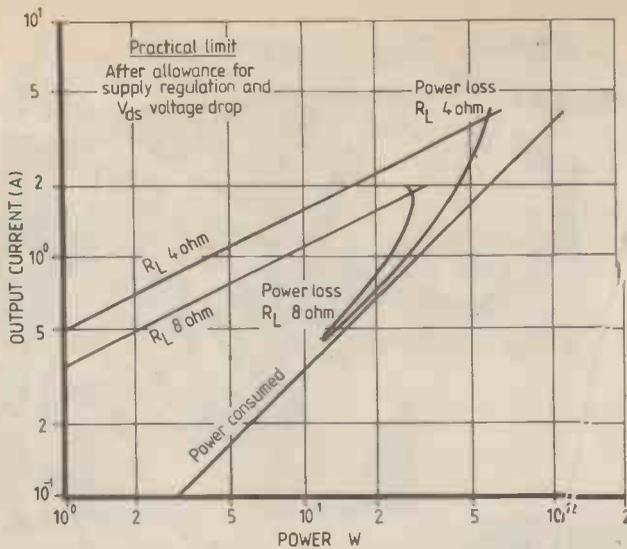


Fig. 1. Power curves of the amplifier with four and eight ohm loads and $\pm 30V$ power supplies.

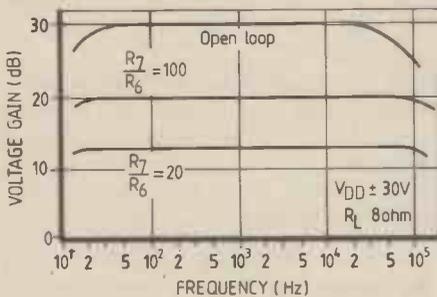


Fig. 2. Frequency/amplitude curves for open-loop, 20 and 100x gain connections.

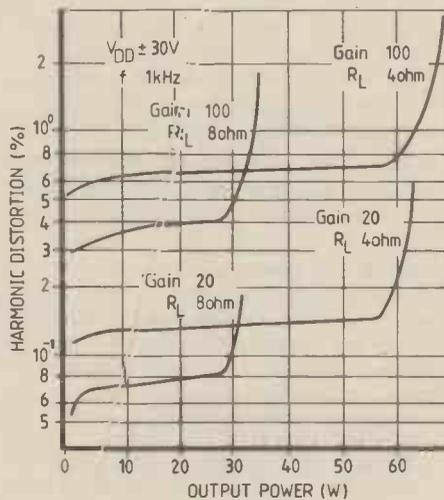


Fig. 3. Distortion curves for gains of 100 and 20 with loads of four and eight ohms.

Variation in output offset voltage and quiescent current with supply voltage.

Supply voltage (V)	Output offset (mV)	Quiescent current (mA)
35	-40	135
30	-20	100
25	+4	75
20	+30	54

effects of common-mode ground current. Similarly use a common output node, the load, feedback resistor and h.f. suppression components being taken from a common point on the board.

- Keep the length of connecting lead to the gate terminals of Hexfets to an absolute minimum to avoid oscillation of the power output stage. Series gate resistor R_{10} suppresses oscillation, but too high a value limits slew rate. Series resistor R_{14} suppresses amplifier oscillation caused by capacitive coupling to the base of Tr_4 .

- Phase shift in the amplifier when driving a reactive load can lead to high-frequency instability. With a capacitive load, the addition of a small air-cored choke - $3\mu H$ with an 8Ω , $2\mu F$ load - restores stability. The final value of the choke is defined by experiment.

With the current set, remove the ammeter from the positive supply and apply a signal to the amplifier input. Signal level required for full rated output is 150-160mV for a gain of 100, and 770 to 800mV for a gain of 20. Clipping of the output waveform when operating at rated power indicates poor supply regulation and is remedied by reducing the input signal amplitude and derating the amplifier. Alternatively use a lower-impedance supply. Amplitude response of the amplifier can be checked over the frequency


ment. Check the copper side of the board for solder bridges between tracks, and remove them. Check for dry solder joints visually and electrically using a resistance meter and rework if necessary.


Now apply power to the amplifier with heat dissipators fitted. Adjust potentiometer R_{12} for minimum offset (fully anticlockwise on the p.c.b. layout) connect an ammeter in series with the positive supply and adjust R_{12} for a reading between 50 and 100mA.

If a loudspeaker load is connected in circuit, protect it from d.c. overload with a fuse.) With the quiescent current set, confirm the output offset voltage is zero ± 100 mV. Excessive and erratic variation in quiescent current as R_{12} is adjusted indicates circuit oscillation or faulty wiring. Oscillation can only be satisfactorily identified and suppressed using an oscilloscope. Also, supply decoupling capacitors should be mounted close to the amplifier output stage and load ground point.

Additional circuit components have been added to ensure high-frequency stability of the complete amplifier. Placement and values depend to some extent on the printed-circuit board layout. Observe the following points when designing the printed circuit board.

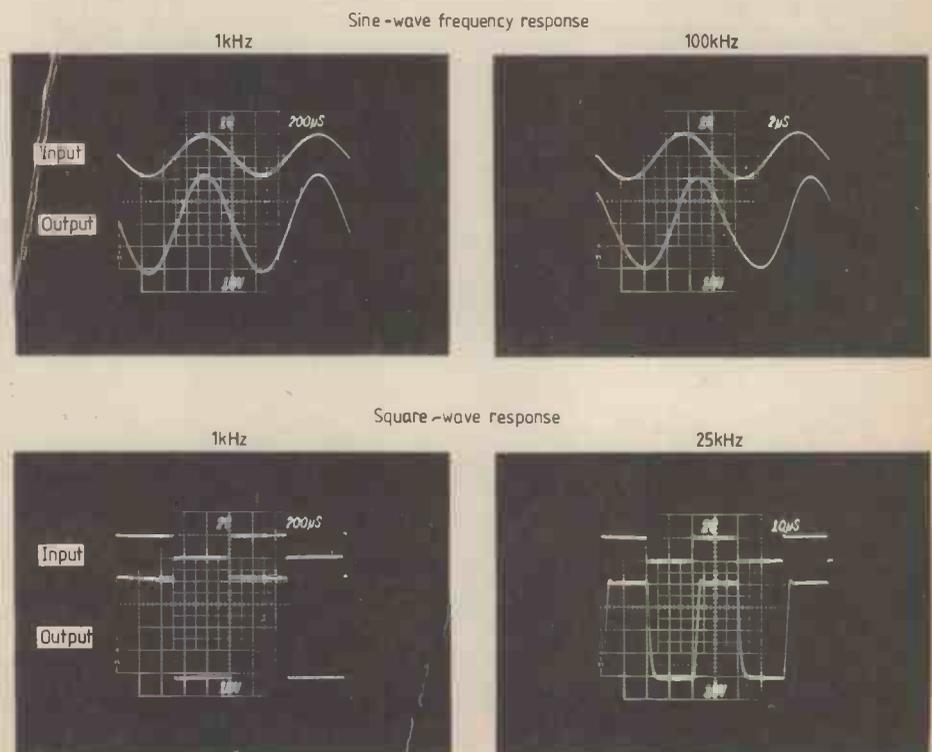- Adopt a common ground principle, i.e. take power supply decoupling capacitors, load and input stage bias components to ground in close proximity, eliminating the



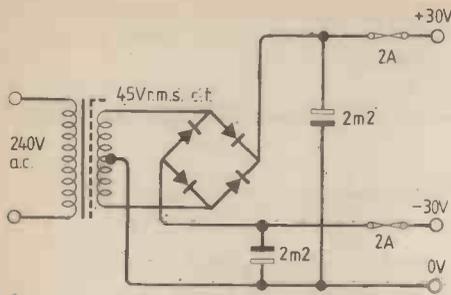

Decoupling capacitors reduce the supply frequency ripple to 5.5V pk-pk at full load. Off load, the supply voltage should not rise significantly above $\pm 35V$.

range 15Hz - 100 kHz with the aid of an audio test set or signal generator and oscilloscope. Distortion of the output waveform at high frequency indicates a reactive load: adjust the output choke to restore the waveform. Tailor h.f. frequency response with a compensation capacitor in parallel with R₆. The l.f. response is controlled by R₇, C₂.

Supply-frequency breakthrough is most discernible in a high-gain circuit. Minimize pick-up at the high-impedance input by a screened cable, grounded at the signal source. Supply-frequency ripple injected through the supply to the input stage of the amplifier can be detected across capacitor C₃. This is normally atte-



A glass-fibre printed circuit board for the heating-fuel saver will be available for £4.50 inclusive of VAT and UK postage from M. R. Sagin, Nancairas Mill, The Level, Constantine, Falmouth, Cornwall.

nuated by the common-mode rejection of Tr₁ and Tr₂ before being amplified but if this is the source of breakthrough, adjust

the values of C₃, R₅ to suppress the signal amplitude.

If the output stage is destroyed either through short-circuit load or h.f. oscillation, replace both Hexfet devices; it is unlikely other circuit components will have been affected. Repeat set-up procedure with the new devices in circuit. □

R.f. radiation hazards

Last year we published a news item¹ briefly pointing out the controversy surrounding the r.f. radiation-exposure safety limits accepted by most western countries. In America, the ANSI and ACGIH (American Conference of Governmental Industrial Hygienists) have both suggested new frequency-dependent standards based on the same work and both assuming 0.4W/kg as a safe maximum absorbed energy rate, and it is expected that the Americans will revise their existing 10mW/cm² maximum safe level in the near future.

Although we in the UK originally based our maximum safe level (10mW/cm²) on that decided in the US some 20 years ago, whether or not we will again follow suit is not clear. According to Mr S. Allen of the NRPB, one possible point of contention is that the two proposed standards mentioned above are based on results from far-field radiation tests. It is

accepted that measurements in the near field, and hence assessment of potential health hazards, are more complex than in the far field. Taking into account near-field effects when determining maximum safe-level standards would nevertheless be sensible.

An article recently published in Radio Communication² gives a good account of r.f. radiation hazard, as far as the radio amateur is concerned. The authors state that reports of "non-thermal" effects of r.f. radiation, mostly emanating from Eastern Europe, should be "regarded with suspicion", and go on to say, "there is no evidence that r.f. radiation produces long-

term damage of the kind associated with ionizing radiation, i.e., cancer or genetic damage." Not a hint is given that the authors feel the accepted maximum level might be too high.

But not everyone is happy with the situation. Mr Herbert Goldwag, for one, summarizes the opposing point of view in an article called 'Microwave hazards' published in the IEEE Spectrum³. □



References

- 1 Small wavelengths - large doubts, *Wireless World*, October 1981, p42.
- 2 R.f. hazards and the radio amateur, Blackwell, R. P. and White, I. F., *Radio Communication*, February 1982, p136.
- 3 Microwave hazards, *IEEE Spectrum*, May 1979, p66.

Further reading

Reference Data for Radio Engineers, Howards W. Sams and Co., Inc., p27-46.
Handbook for Radio Engineering Managers by J. F. Ross, Butterworths, pp372-387.
Radio hazards in the m.f./h.f. band, Rogers, S. J. and King, S. R., *Non-Ionizing Radiation*, vol. 1, No. 4, pp178-189.

ABSORPTION IN MUSCLE

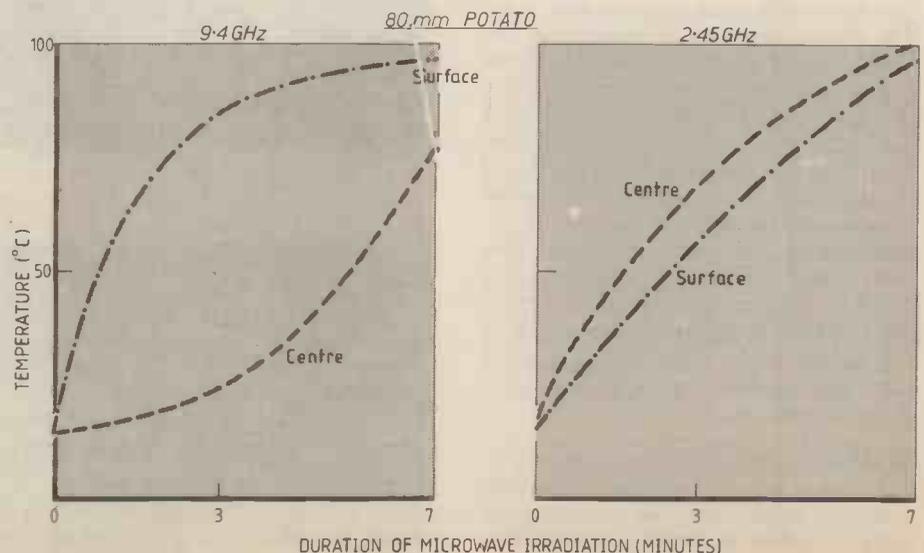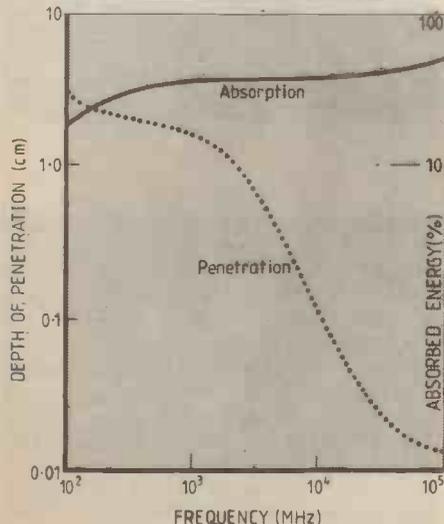

LETTERS

SITUATION NORMAL...

In your February issue, Pat Hawker mentions "SNAFU" as a coinage of War II. I think he and your readers may be interested to know its pre-war origin.

During the said war it was my pleasure to work for a time with two clever and humorous American Western Electric telephone engineers, and they told me that their pre-war jobs had been to go to telephone exchanges where there was trouble and rectify it. Upon arrival at the site an engineer would make a brief estimate of how serious was the trouble, establish a telephone link to his headquarters and send back a code word. His home base would therefore know he had arrived where the problems were, have a rough idea of how long it would take to clear them and have a telephone number where he could be contacted if need be. There were three code words: SNAFU - "Situation normal, all fouled up" (or words to that effect); TARFU - "Things are really fouled up"; and FUBAR - "Fouled up beyond any repair". The latter would be sent if, for instance, a telephone exchange had been seriously damaged by fire or flood, while SNAFU would be used for a situation where cables or machinery had been damaged but where repairs or replacement would be relatively straightforward.

SNAFU became widely used in many situations during the war, but strangely the other code words were rarely used or were unknown. It would be a pity if this bit of folk lore was lost.

C. H. Banthorpe
Northwood
Middlesex


WOODPECKER

As a radio amateur, I have often been annoyed by the Russian "woodpecker" pulse transmissions which have plagued the h.f. bands for many years¹. There has been no official explanation of the purpose of these transmissions, and various theories have been expounded in the media, ranging from spy communications to death rays. However, as a result of accidentally coming across some of these signals on a laboratory spectrum analyser, and storing the waveforms on a transient recorder, I think I can shed a bit more light on their structure and purpose.

Figure 1 is based on a printout of a typical pulse, plotted as logarithmic amplitude versus time. The overall duration of the pulse is 3.1ms. The interesting feature is the presence of "glitches" in the top of the pulse, the pattern of which remains the same from pulse to pulse, and they occur at intervals which are multiples of 100 μ s. This led me to suppose that the glitches formed a binary sequence of length 31 bits.

I also guessed that the glitches arose from phase reversals in the transmitted signal, the finite width of the glitches resulting from the effect of the finite bandwidth of the transmitter and/or spectrum analyser. Thus, arbitrarily assigning a zero to the first data bit, the original modulation pattern could be reconstructed, with 0 representing 0 degrees and 1 representing 180 degrees. This gave the pattern 0000011100100010101111011010011.

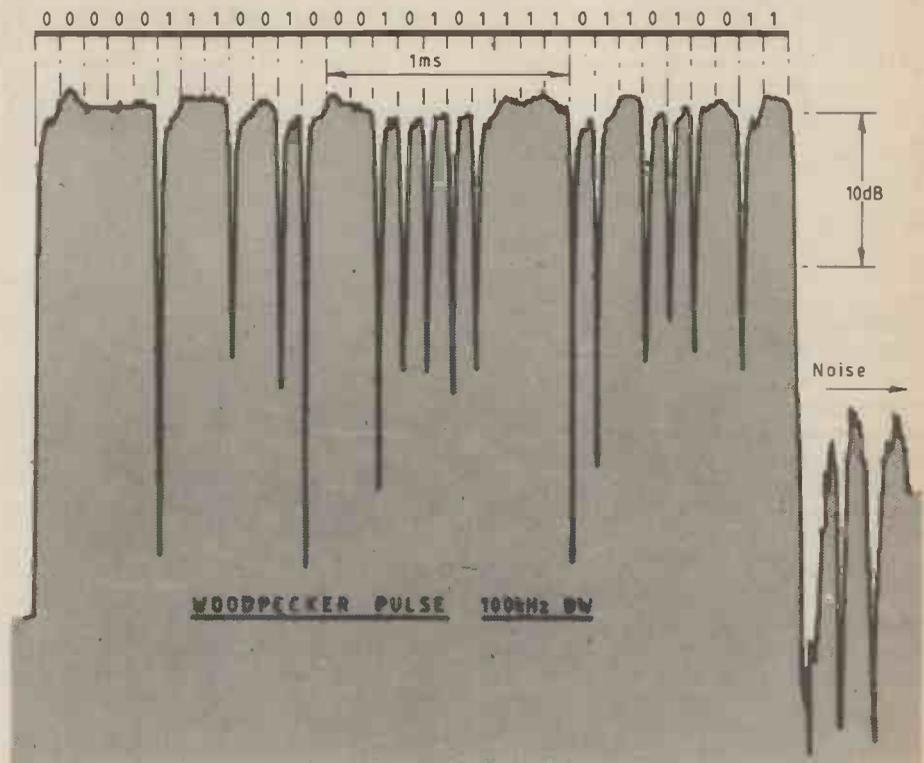This sequence turns out to be a maximum-length, pseudo-random binary sequence², which can be generated by a 5-bit shift register with feedback formed from the parity function of the contents of stages 3 and 5. I subsequently



observed other pulse transmissions with different sequences of the same length, and was able to match these to p.r.b. codes from shift registers with feedback from stages 2,5 2,3,4,5 and 1,2,3,5. Four different codes, implying four different transmitters, agreeing with observations previously reported¹.

The interesting point about this use of p.r.b. codes arises from the shape of their autocorrelation function. If such a sequence is compared bit-for-bit, with a shifted version of itself, at all possible shifts, then, apart from the position where all 31 bits match, at all other shifts no more than 1 bit matches between the two sequences. Thus, if a woodpecker pulse is fed through a 3.1 ms delay line with 31 equally spaced taps, and the outputs of the taps are vectorially combined with appropriate inversions, so that the inversion pattern itself is the same sequence as the transmitted phase-inversion sequence, then the combined output will be a single pulse of 100 μ s duration, 31 times the amplitude of the input signal, with virtually no sidelobes.

The conclusion from all this, it seems to me, is that the woodpecker must be simply a pulse compression radar system, with a resolution of 100 μ s (10 miles), but the sensitivity 31 times that of a 100 μ s radar of the same power. Not only does the p.r.b. sequence cancel out shifted versions of itself in order to achieve its performance, but it has a high immunity to other codes in the same family, thus reducing cross-interference between separately sited radars on the same frequency. The use of four different sites presumably enables the target to be pinpointed in three dimensions in spite of the poor directivity of h.f. antennas and the variabilities of the ionosphere which is used to extend the range beyond the horizon.

Although this information leads to the possibility of jamming these signals, or at least puzzling the distant radar operator, whether we

shall ever be rid of these wretched signals is another matter altogether.

J. P. Martinez G3PLX
Gosport

References

1. Mystery Soviet over-the-horizon tests. *Wireless World*, February 1977 p.53.
2. Pseudo-random binary sequence generators. F. Butler, *Wireless World*, February 1975 p. 87.

POOR DEAL FOR AMATEUR RADIO

I wish to congratulate you for publishing a letter (February 1980) criticising the RSGB: at last someone has dared to make public the feelings of many RSGB members. I myself have written to the RSGB on several occasions but I have never been privileged with an acknowledgement, not to mention an explanation of their actions.

Whilst the RSGB has been trying desperately to prevent the introduction of c.b. (I, like many, see through their claims of neutrality), radio amateurs have ended up with a very raw deal. Firstly, we have lost 200 kHz of 70 MHz; secondly, only one of the h.f. bands has been introduced; thirdly, despite the introduction of c.b. on 27 MHz (with no Morse), B licencees still need Morse for 70 MHz to 28 MHz. Whilst pip/kay tones are not to everyone's taste, they are used freely on c.b. but are severely restricted on the amateur bands. Selcal type signals are not permitted on the amateur bands whilst they are on c.b. I must add at this point that I am totally pro-c.b. and I am not some jealous, sour-grapes radio amateur.

Furthermore, whilst expending its energy on anti-c.b. propaganda, the RSGB have totally ignored the decline of amateur radio. Little mention is even made in *Rad-Com* of the illegal operation on London repeaters. Why does the

LETTERS

RSGB not close them down or, better still, persuade the Home Office to catch the offenders. The RAE is now a joke. Amateur radio is meant as a technical hobby; the new RAE has virtually eliminated any serious technical requirements. How many radio amateurs repair, let alone build, their own equipment?

As radio amateurs, we have virtually sold our birth right and the RSGB has stood by and let it happen.

B. Reay
Woolwich
London SE18

WALK-ABOUT TELEPHONES

The Post Office and its successor British Telecom have in the past been accused of being slow to meet the demand for telephone instruments other than those of the standard type, but this has now been to a large extent corrected by the availability of types ranging from the elegant baroque to the frivolous Mickey Mouse.

One facility which does not appear in the lists is the hand-held device which allows the user to make and receive calls while at the same time to be free to roam about his house and garden. Radio linkage is one way of making this possible and is the means employed in certain instruments which are obtainable by the general public from suppliers other than Telecom.

This may be because of the possibility of the radio signals involved being received by someone who is not a member of the subscriber's household.

It is unlikely that the prospective user of one of these devices will have been warned that his future conversations may be overheard and even if the point is made he may shrug off the matter and say that he does not mind. A more important factor is that even if the user is indifferent to being overheard this may not apply to those with whom he is in communication and who may have objections to what they are saying being broadcast.

It may be argued that the threat to one's privacy is pretty small since suitably equipped listeners may be thin on the ground in the immediate neighbourhood. However, a single eavesdropper of less than good intent could be at least an embarrassing nuisance or there could be legal implications in a situation where a stranger might seek to profit as a result of information received.

Finally, there may very well be a real need for this type of telephone facility but there are pitfalls in the use of unauthorized equipment. One assumes that a Telecom-approved system awaits the provision of suitable safeguards and defences against illicit tapping of the telephone network.

G. Dann
Chipstead
Surrey


NANOCOMP E.P.R.O.M. PROGRAMMER

I have been experimenting recently with a photographic flash tube and am concerned about inductive flashes and their erosion of the button in Fig. 1. on page 30 of the January 1982 *Wireless World*.

I think that problem could be reduced by having a low-voltage, high-current winding on the choke core in addition to the 4H. This would make the choke a transformer as well. A suggested outline for a circuit accompanies this

letter and a description follows.

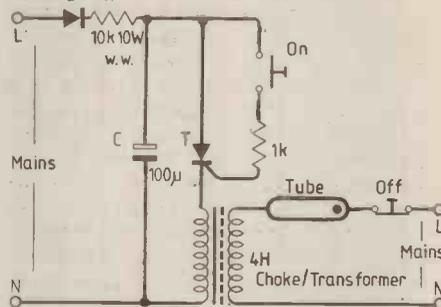On the left the main voltage is rectified by D and charges C through R to mains peak voltage. Mains is also applied permanently to the tube and 4H winding in series but, since the tube has not struck, no current flows: the tube is open-circuit.



When the On button is pressed, C discharges via the low-voltage winding, inducing an inductive voltage of, say, 2kV in series with the mains across the open-circuit tube. But as soon as the 2kV causes the tube to strike, it is anticipated that mains current will flow through the tube, using the 4H winding now as the choke. When the Off button is pressed, the tube should go off. In the event of a thyristor short-circuit or capacitor short-circuit the 10kΩ resistor would get warm and only consume a few watts. Normally, when off, only capacitor leakage current should be taken. The operation would depend on a real difference between striking voltage and maintaining voltage in the tube.

J. R. D. Powell
Harlow
Essex

DATA STORAGE

I would like to comment on two articles in the February 1982 issue: "Data recording on audio cassette" and "Economical Z80 development system". To start with, I would like to introduce myself as the designer of SOFTY, which appears in the latter article, and the inventor of TRANSWIFT, a software modem used in SOFTY to store data on cassette tape. The point that I will try to illustrate is that there are more ways of killing a cat than choking it with cream.

Data storage using audio tape is like a serial transmission in a medium of limited bandwidth (forget that the data stays in the medium for an indefinite time). The low-frequency limitations are the bigger nuisance — so why not use a system which has no low-frequency components? If the data recording is for a microsystem why not do it with software? If you are willing to ignore convention you can use a simplified recording and playback circuit.

Most microsystems have a bit of i/o going spare, either on the microprocessor itself or via an 8255 or similar. You could use a separate port for input and for output. You could add some sort of signal conditioning — but it isn't necessary. This circuit will store data using the cheapest cassette recorder at well over 3000 baud-equivalent.

Transmit a zero by putting the port high for a jiffy, then low for the same jiffy. A 1 is transmitted by using bigger jiffies. All binary transmissions are 0s and 1s strung together and the low-frequency components have vanished. You can put this transmission through a capacitor, for instance, without degrading it. You can also store it on tape and get it back unchanged. Recovering the succession of 0s and 1s is a matter of measuring the intervals between zero

crossings. The resistors suspend the port at the transition point. You might recover the data in one of two ways: either you take a positive transition as a starting point, delay for a step interval and then input the bit, or you measure the time between similar transitions and decide whether it represents 1 or 0.

Examination of this transmission shows two important properties: turning it upside down makes no difference to reception, and clock-speed errors don't accumulate — each bit contains a clock, 10% or more difference in speed won't baffle it.

A TRANSWIFT transmission doesn't use start, stop or parity bits. The speed of the transmission is more likely to be restricted by the processor's agility in handling the data than by the bandwidth of the recording system. It is up to the processor to make an intelligent decision about whether it has a valid transmission or not, and where that transmission starts. If the input is to an interrupt this process can be automatic.


SOFTY2 uses 500μs and 1000μs as the transmission times for a 0 and a 1. To show that a transmission is coming, and to get over the bounce period of the recorder's automatic gain control, a leader of 20 bytes of 'AA' bytes are sent. (AA in hex. is 10101010). Then a hex '69' (which is 01101001), and the data, with no extra bits of any kind.

Recovery uses a routine which samples forward from each positive transition by 750μs and shifts the sample bit into a register. The word in the register is then compared with '55' and 'AA' and either are accepted as valid leaders. A leader counter with a starting value of perhaps 40 is decremented for each valid leader byte, but restored to starting value if an invalid leader is received. When the counter reaches zero the program starts looking for the '69'. The '69' is there for alignment — so that you can chop the succession of bits into bytes in the right places.

To establish the best form of error checking it is necessary to anticipate how the recorder will mess up the data. The usual system of adding a parity bit to each word fails because lateral displacement is common. All error checking systems use redundancy — they transmit extra information to catch errors. SOFTY uses a single byte appended to the transmission which is formed by exclusive-ORing all the data bytes with AA. (I used AA because it happens to be the leader and in the right register at the right time). The reception routine exORs the transmission and shows you the result — if it isn't AA then you have errors. I call this parallel parity.

In case you're wondering how much programming space this takes: A Z80 device (MENTA), designed later, uses 147 bytes for the cassette interface. SOFTY uses about 300.

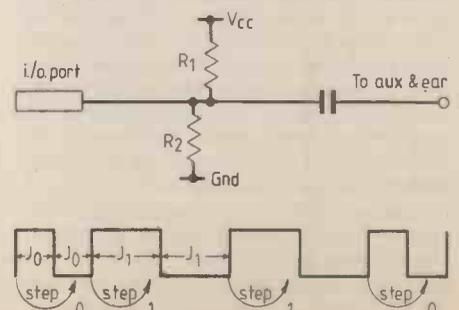The article "Economical Z80 development system" supports my claim that the combination of any assembler and a SOFTY makes a powerful design tool. However the process of linking a Nascom to SOFTY described is un-



necessary. Leaving aside the fact that SOFTY2 already has a parallel interface with normal handshake, plus serial routines for 110, 300, 600, 1200 and 2400 bauds, all of which ignore all ASCII characters except 0 to 9 and A to F — by far the simplest solution is to write a TRANSWIFT routine for the assembler's processor to dump the code into SOFTY using the cassette jack-socket. This reduces the hardware to a piece of wire and a jack-plug. In fact, I use a similar system from my Sharp MZ80K. The port used is the Sharp's keyboard l.e.d. — mainly because the connector is provided on the p.c.b.

TRANSWIFT is the simplest and most economical method of implementing a serial data transmission system, and is especially useful if the bandwidth of the medium is limited.

B. Savage
Dataman Designs
Dorchester

THE DEATH OF ELECTRIC CURRENT

Ivor Catt's latest letter suggests that some progress has been achieved in an uphill struggle, for he seems to acknowledge that we are discussing models of reality and not reality itself. However, there is some way still to go, for he seems to regard models as "true" or otherwise. Models can be bad or good or better in relation to their accord with observation, but never true or false. So it is fatuous to assert that a model shows that electric current does not exist.

Certainly, there is much to be said for keeping models simple, but I think that other correspondents have shown that the "insurmountable difficulties" introduced by ρ and f exist only in Mr Catt's mind. Further, simple models are not always best: albedo measurements had shown the shortcomings of the green-cheese model of the moon, long before Armstrong arrived to test the flavour!

I was interested by Mr Davidson's achievements with discharging capacitors, but I suspect that those of us not fortunate enough to have a capability for time-domain reflectometry will continue to use the exponential model. This model does have a shortcoming in that it suggests that the discharge current continues for an infinite time, whereas observation shows that it does not. Of course, if we use an electric current model we can account for this by supposing that the discharge current becomes submerged in the noise, currents generated by random motion of the electrons within the conductors. Presumably there is a means of describing the effect using an e.m. wave model?

R. T. Lamb
College of Engineering Studies
British Telecom

DANGERS OF LOW-FREQUENCY SOUND

I have just read the letter of S. Frost of Edinburgh, who replies to my earlier letter concerning my invention and operation of a hi-fi speaker system whose response is flat down to four Hz, suggesting that I should be careful. He quotes from the paperback "Supernature" by Dr Lyall Watson and suggests that my speaker could be harmful to certain people, due to its infrasound output.

I know that infrasound of very high intensity can give temporary effects which might be termed uncomfortable or disquieting by some people. However, the subject of infrasound in

general is now much better understood that it was in 1974 (the date quoted by Mr Frost which applies to the above publication) and it is now known that even prolonged exposures to infrasound of even very high intensities up to that experienced, say, in a rapidly moving railway carriage with the window open (which I believe in the order of 135-138dB?) do not cause lasting deleterious effects. My speakers at present have a maximum output on transients of around 15-20dB less than this, or around the level of v.l.f. caused in a house by a very strong wind blowing outside. There is no risk of permanent harm arising from their use as hi-fi speakers. Infrasound produced by helicopter blades, pneumatic drills, heavy trucks, etc. (from the driver's seat) can be louder than this and are still not harmful. It takes sound loud enough to physically shake one out of one's seat before even temporary damage is caused (note sound pressures, not structure-borne vibrations). Levels such as those of a full sized fog horn (marine, shore-based) at 3ft are at the danger area.

G. Holliman
Watford
Herts

MICROCHIPS AND MEGADEATHS

Further to Mr P. C. Smethurst's letter in the December issue, may I suggest that the only way in which the technical society will become a reality is by a major evolutionary development of the human species.

The nearest approach the average homo-erectus makes to the technical society is to buy a digital wrist watch with alarm and graphic display, kidding himself that he will be able to tell the time with it. Such mistakes are inevitable with our present learning process.

Until our DNA reorganizes itself a little so that accumulated knowledge (only the facts, of course) can be passed directly to offspring, our ability will depend on Mr Smethurst's learning period of 15-20 years. Few people will reach his 'unusual' standard and buy watches with hands.
R. G. Brown
Watnall
Notts

Tim Bierman (October Letters) and Roy C. Whitehead (January Letters) are wrong to imagine that refusal to fighting wars will avert their occurrence. Modern technological warfare, involving nuclear and space-based weapons, does not depend upon the recruitment of willing and gullible warriors. A small, minority elite now possesses the power to destroy the earth and, if competition over markets, trade routes and natural resources necessitates it, will sacrifice millions of human lives to the god of profit. If the threat of war is to be removed, political action must be taken to transfer power away from the possessing minority into the hands of the democratically organized world community. If the weapons are used, there will be no hiding places for conscientious objectors; the time for objecting is now.

Instead of listing names of *Wireless World* readers who would refuse to fight in the event of a future war, may I suggest that a better course would be to list the names of readers who have taken the step of extending their scientific interest in technology into a scientific analysis of society?

Steve Coleman
Clapham
London SW4

THE NEW ELECTRONICS

The article by Hugh Jaques in your January edition prompts me to add my own comments on the subject of "The new electronics".

It is all very well to decry falling standards, but I find the tone of that article rather counter-productive. The standard in Germany, if we wish to draw comparisons, is far lower — yet the number of "Diplomingenieur" (dipl — Ing) and Doctors of Science is far greater. Previous *Wireless World* editorials have covered the question of status — and one gets the clear impression that British engineers are developing an inferiority complex with regard to the Germans.

Yet, years ago, I attended a conference in Frankfurt when Cosmos and l.c.ds were introduced. The meeting began with German engineers pounding the table Kruschev-style; everyone was quite unruly. When I pointed out that l.c.ds, with a quoted life-expectancy of fifty thousand hours, could not complete for longevity with l.e.ds (up to one million hours), everyone was on his feet screaming "l.c.ds no good." The meeting broke up in chaos and I never did find out if one could prolong the life of l.c.ds by interposing ceramic capacitors in the leads to block the d.c. components of the signal, which causes electrolysis of the liquid crystals.

Dipl-Ing colleagues were forever asking me such questions as "What is the difference between a p-n-p and an n-p-n transistor", and a doctor of physics never answered any question without his "schlaue Buch" (clever book) which was his real brains.

No — the Germans are dishing out high-level qualifications in every branch of science almost like the free-gifts with chewing-gum. Yet the television programme "Bilder aus der Wissenschaft" (pictures from science) complained that Germany was not winning any Nobel Prizes.

To improve standards one must set an example through excellent work — rather than trying to catch people out. Indeed, there is nothing very wrong in a newly-qualified engineer being a little "green". The real education is the work itself, and if the British withhold their qualifications whilst the Germans mass-produce them, Britain will not be well represented at future international congresses, will lose presence in the world and cease to sell goods.

It would appear that Mr Jaques was not so "word-perfect" as he claims. In his Fig. 2, the gain is only $-R_2/R_1$ if the source — impedance at point X is zero, which is what one would infer from the "gain between X and Z", because any generator impedance would be added to R_1 . Secondly, the input-impedance at Y is $R_2/(1+A)$ only if the source — impedance at X is infinite. Otherwise R_1 and the source impedance form a series-string in parallel with $R_2/(1+A)$. What source impedance does Mr Jaques have in mind?

Perhaps you can see how destructive such a style of cross-examination can be. We all make mistakes which are not mistakes at all unless we want them to be. "What is the input impedance at Y with X open-circuit" would have been a better question, which would have saved Mr Jaques face. But I am just picking him up on words — as he was doing.

In the final analysis, engineers are paid for engineering — not for passing tests. Given the chance, many will succeed and many will fail. Be over selective and all will fail.

C. Wehner
London, W2

RECEIVERS FOR OPTICAL FIBRE COMMUNICATION

During the next few years optical fibre systems will be used increasingly for long-distance telecommunications with emphasis on achieving greater bandwidth and greater spans between repeaters. In this rapidly developing subject it is essential to be aware not only of the latest published results but also of the underlying principles to fully appreciate the potential of optical communication. With this in mind, Dr Garrett reviews both the best reported performance in detectors and receivers and the areas where there is still room for improvement.

Optical fibre communication systems are beginning to be used extensively for data links and for long-haul systems. The first "generation" of systems operates in the near infrared - a wavelength of about $0.85\mu\text{m}$ - where light sources may be made from gallium arsenide and detectors from silicon. At slightly longer wavelengths, 1.3 to $1.6\mu\text{m}$, glass fibre is a better transmission medium, having enormous bandwidth and extremely low attenuation - 0.5dB/km or even lower. Fibre systems are being used to carry telephone traffic at 140 Mbit/s over unrepeated spans of 10 to 12 km in the UK. Within the next few years it will be possible to operate at ten times that rate over at least five times that distance. As the market for fibre grows and the cost comes down, it will become economic to use fibre systems at lower data-rates as well, and also to transmit video either for entertainment or for teleconferencing.

The three basic functions of an optical receiver are to convert the signal from an optical to an electrical form, to amplify the signal, and to regenerate the transmitted message. The first of these is performed by an optical detector. Amplification is not specific to optical systems except for the special design of the front-end of the receiver, which is inseparable from the detector in determining the sensitivity. Estimation and regeneration of the message involves dealing with the noise and various system impairments; only the

by I. Garrett

more basic ideas are covered; for more depth refer to the bibliography. In these functions, an optical receiver seems similar to a radio receiver. However, current optical receivers are quite different in the way in which they perform. Heterodyne detection, universal in radio practice because of its excellent sensitivity and rejection of adjacent channels, is at present impractical in optical receivers. It requires a local oscillator which matches the arriving signal in frequency, phase, and polarization. Today's semiconductor lasers have spectral line-widths of 25MHz to 1000GHz , and current fibres do not preserve a predictable polarization at the output end. Although the possible advantages of increased sensitivity and use of frequency and phase-shift keying have stimulated research into overcoming these and other problems, today's systems use incoherent (direct) detection, in which only the variations in optical power are sensed.

Unity-gain detectors

The device which converts the optical signal to an electrical form must be efficient at the operating wavelength and must respond at a speed appropriate to the message data rate or frequency band. One may also require a linear response, operation at ambient temperature from a convenient voltage supply, and a preference for a small, light, cheap and reliable device. Semiconductor photodiodes fit all these requirements remarkably well, and there is little interest in other types of detector for optical telecommunication, at least in normal terrestrial environments. Photoconductive detectors have inferior noise performance except when the incident optical power level is high; pyro-electric detectors can only be made fast at the expense of sensitivity, and photomultipliers offer no advantage in sensitivity when, as is normally the case in fibre optic systems, the optical power level on zero bits is not zero. Phototransistors are convenient devices for low-speed data links, but are

generally not sufficiently fast and sensitive for telecommunication.

A photodiode is a reverse-biased p-n junction formed in a semiconductor material. Photons are absorbed in the semiconductor and create electron-hole pairs. These carriers can be separated by an electric field, such as exists in the depletion region of a p-n junction, and then give rise to a current in the external circuit. To convert light efficiently, the semiconductor material must have a high absorption coefficient at the wavelength of the light so that different materials are appropriate for different wavelength ranges.

The speed of response is governed by the time taken for the photogenerated electrons and holes to reach the terminals of the device, and by the RC time constant of the measuring circuit, which may be affected or even dominated by the junction capacitance. Photo-generated carriers travel across the device to the terminals from the points at which they are generated by diffusion and by drift in any internal field. The rate of diffusion is generally so slow that except in very thin layers most carriers are lost by recombination and do not contribute to the photocurrent. The device is made fast and efficient by ensuring that the incident photons are absorbed in the high-field depletion region of the junction.

Figure 1 illustrates a photodiode structure used in practice. It is a silicon device designed for the wavelength range 0.8 to $0.9\mu\text{m}$, and has a thick depletion region 30 to $100\mu\text{m}$ thick formed in low-doped material. The absorption coefficient of silicon in this wavelength range is 950 to 350cm^{-1} , so that several tens of microns of material are needed for almost complete absorption. Very little of the incident radiation is absorbed in the undepleted n^+ layer at the surface, which is only about $1\mu\text{m}$ thick. The device is designed so that the field required to deplete it fully is well below the breakdown field strength, but sufficiently high to accelerate the carriers to their scattering-limited velocity (around 10^7cm s^{-1} in many semi-conductors at room temperature) resulting in a response time of about 10 ps per micron of depletion region. Depletion region doping is very low so that fast response is obtained with a moderate applied voltage. Such a device is known as a p-i-n photodiode, the i-region

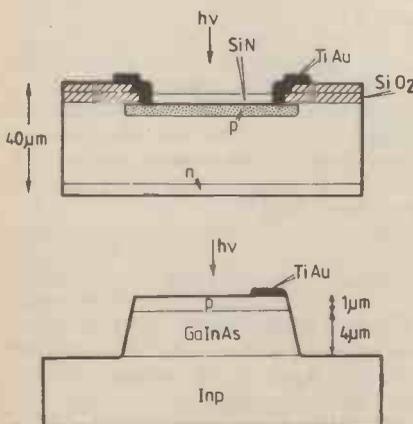


Fig. 1. Silicon p-i-n photodiode is suitable for wavelengths from 0.8 to $1\mu\text{m}$ (top), while InGaAs/InP p-i-n diode covers wavelengths from 1 to $1.6\mu\text{m}$ (bottom).

Ian Garrett, MA, Ph.D, MIEE, is with British Telecommunications Research Laboratories, Martlesham Heath, Ipswich.

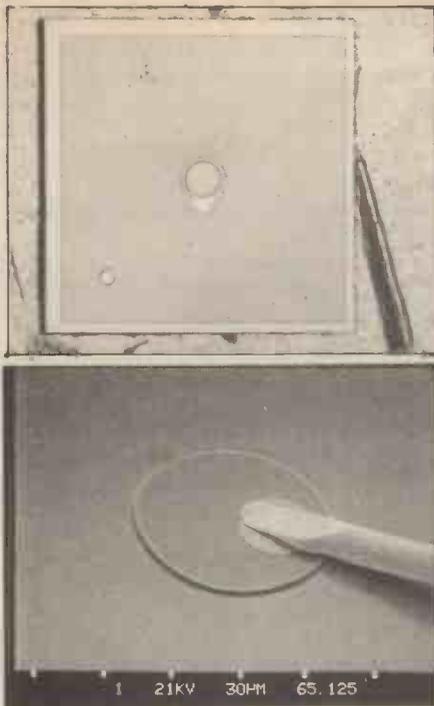


Fig. 2. Silicon p-i-n diode chip, top, is 1mm square with circle 100 μ m diameter and bonding pad beside it. Chip capacitance is below 0.1 pF, and reverse bias leakage current is around 50 pA at -10 V bias. Quantum efficiency at 0.85 μ m wavelength, corresponding to gallium arsenide injection lasers, is 0.95. Active area of InGaAs/InP photodiode isolated by mesa etching is 100 μ m in diameter in scanned electron micrograph (bottom). A small bonding pad is formed on the top surface as the device was intended for front illumination. Capacitance is 0.3 pF and reverse bias leakage current below 10 nA at -10V bias. Quantum efficiency is only about 0.4 because many carriers recombine in the undepleted surface layer but this can be overcome by illuminating through the substrate; anti-reflective coatings also increase efficiency.

being nearly intrinsic. The wide depletion layer reduces the junction capacitance too. The device illustrated is 100 μ m in diameter and has a capacitance of less than 0.1 pF.

At wavelengths beyond 1 μ m, silicon becomes increasingly transparent and a different material is required for photodiodes intended for communication systems. An obvious choice is germanium which has a bandgap of 0.66 eV and so should be sensitive out to 1.8 μ m or so, well beyond the optimum transmission wavelengths of 1.3 and 1.55 μ m. The small bandgap of germanium is something of a disadvantage: coupled with the high density of states in the conduction band it means that the reverse bias dark current is large, which degrades the performance of an optical receiver. The other possible materials are the so-called group III-V compounds, binary compounds of elements from groups IIIb and Vb such as gallium arsenide and indium phosphide. To detect light at 1.55 μ m, a material with a bandgap near 0.8 eV is needed. None of the binary III-V compounds has such a bandgap, but many of the III-V compounds form extensive solid solutions with each other, and the mixed

compounds have properties intermediate between those of the binaries. So it looks as if there ought to be a wide choice of materials. In practice the choice is limited by the techniques available for preparing these materials in sufficiently pure and perfect form. The most usual materials for detectors in this range are the ternary compound (Ga,In)As and the quaternary (Ga,In)(As,P). In either material, the bandgap can be adjusted over a wide range by selecting a suitable composition. Reverse-bias dark current is smaller than in germanium by one or two orders of magnitude typically because of the much smaller density of states in the conduction band. Recently, the II-VI compounds such as (Cd,Hg)Te have also been studied for use as fast photodiodes in communication systems.

The second device illustrated has an absorbing layer of InGaAs deposited on an InP substrate, with the p-n junction formed by diffusing a dopant such as zinc into the absorbing layer. This device is designed for the wavelength range 1 to 1.6 μ m, in which the InGaAs layer has a high absorption coefficient, around 10^4 cm^{-1} , so only a thin absorbing layer is needed, about 3 to 10 μ m. This makes the response fast, but an important fraction of the incident radiation is absorbed in the undepleted p⁺ region at the surface even if it is only 1 μ m thick. Many of the carrier pairs formed in this region are lost by surface recombination or by recombination within this layer, so that the efficiency is reduced considerably. It is not easy to control the thickness of this layer much below 1 μ m, but the problem can be surmounted by arranging for the light to be incident through the back of the device, i.e. through the InP substrate, which is transparent at wavelengths beyond 0.95 μ m.

The quantum efficiency of a photodiode is the number of carrier pairs formed on average for each incident photon. It is less than unity in practical devices for three main reasons: some of the incident light is reflected; some carrier pairs are formed in undepleted material and so do not contribute to the photocurrent at high frequencies; and some carrier pairs recombine before reaching the terminals of the device. To improve the quantum efficiency, the surface of the device is often

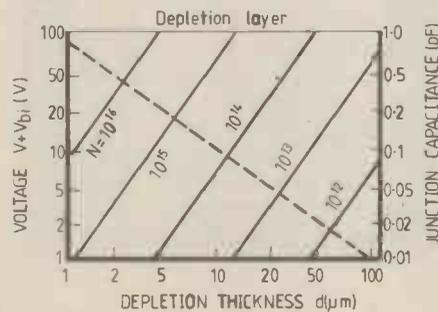


Fig. 3. Depletion voltage and junction capacitance as functions of the depletion layer thickness for a 100 μ m diameter diode, taking the relative dielectric constant to be 10, typical of many semiconductors.

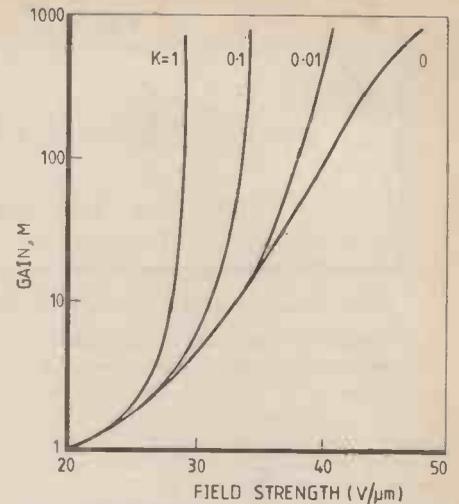


Fig. 4. Avalanche gain as a function of field strength - the breakdown characteristic. Parameter k is the ratio of ionization rates for electrons and holes.

given an anti-reflecting dielectric coating like the blooming of a camera lens; the surface reflection coefficient may be reduced from around 30% to almost zero. If the light has to pass through undepleted material, as in the lower diagram, this is kept as thin as possible or made of a semiconductor which is transparent at the wavelength of interest. Recombination of carriers within the depletion region is generally minimized by reducing deep-level impurities and crystal defects as far as possible.

The depletion layer thickness d is determined by the applied voltage V and the doping level N_b :

$$V + V_{bi} = qN_b d^2 / 2\epsilon\epsilon_0$$

where q is the electron charge and ϵ is the relative dielectric constant, typically 10 to 15. Junction capacitance is

$$C_d = A\epsilon\epsilon_0/d$$

where A is the area of the junction. These relationships are plotted in Fig. 3, assuming a device diameter of 100 μ m. Doping levels of 10^{12} to 10^{13} cm^{-3} are available in silicon, so that a few tens of microns can be depleted at 5 to 10 volts. In the mixed III-V compounds levels of 10^{15} cm^{-3} are the best normally available, so that 15 to 20 volts are required to deplete a few microns. Junction capacitance is typically 0.1 to 0.5 pF for a high-speed device so that the capacitance of a packaged device is usually dominated by the package.

The reverse-bias leakage current (dark current) of a photodiode is important because the shot noise on this current can be the dominant receiver noise in some situations. The dark current is caused by current leakage over the surface of the device as well as through the depletion region (bulk leakage). Surface leakage is minimised by careful processing and by coating the device with a passivating layer: methods vary from one material to another. Bulk leakage is due to diffusion of minority carriers from the undepleted

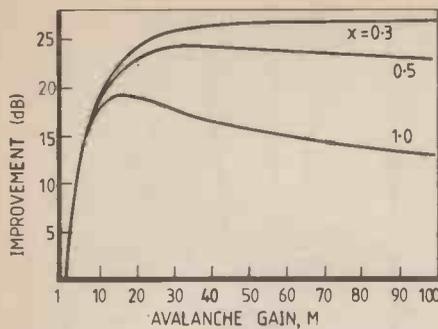


Fig. 5. Signal-to-noise ratio is improved as a result of avalanche gain. Parameter x is the exponent in the empirical expression for the excess noise factor $F = M^x$. Value of 0.3 to 0.5 relates to silicon reach-through diodes while germanium and III-V a.p.ds have a value close to 1.

regions and by generation and recombination of carrier pairs in the depletion region. The diffusion term usually dominates in materials with a large intrinsic carrier concentration, such as germanium. The generation-recombination term is the most important in silicon and in most III-V compounds of interest.

Detection in the presence of noise

The most important parameter of any receiver is its sensitivity, and there are several factors which prevent arbitrarily weak signals from being handled. The signal will have suffered various impairments during transmission, because of the dispersion and attenuation of the fibre. In addition to being distorted, the signal leaving the optical receiver has wideband random fluctuations produced by the components of the amplifier. Lastly, even with an infinite fibre bandwidth and a noiseless amplifier, the optical signal itself is statistical because of the quantum nature of light. Radio waves are also quantized, of course, but the quantum energy $h\nu$ is much less than the thermal energy kT of electrons in the amplifier components so that quantum effects do not show up at radio frequencies. At room temperature kT/h is about 6000 GHz, well above the highest frequencies used in radio transmission, and well below the frequency corresponding to a wavelength of $1 \mu\text{m}$, which is 300 THz. Photons arrive at the detector at random instants with a Poisson probability distribution so that the variance in arrival rate is equal to the mean. If the expected number of photons in some time interval is m , then the probability that the number detected will be n is

$$p(n) = \text{Pos}[n, m] = \frac{m^n e^{-m}}{n!}$$

Consider a binary digital system in which one needs to decide whether or not a pulse was received during each bit period. The number of detected photons n is counted for each bit period, and if that number exceeds some threshold number d a one-pulse is recorded, otherwise a zero is recorded. Errors occur if n is less than d when a one-pulse was transmitted. It is easy to see that fewest errors are made

when the threshold d is set between 0 and 1 photons. The error probability is then $P_e = e^{-m}$, and one cannot have zero error probability with finite m . For $P_e = 10^{-5}$, $m = 11.5$ and for $P_e = 10^{-9}$, $m = 20.7$.

In an analogue system, we are interested in the signal-to-noise ratio (snr) at the receiver output with a post-detection bandwidth B which smooths fluctuations over an integration time $t = 1/2B$. If the mean photon arrival rate is r , then the number m which arrives, on average, during the time t is $m = r/2B$. At the output of the receiver, the signal power is proportional to m^2 , while the noise power is proportional to the variance of m , which is just m . Thus signal-to-noise ratio is

$$m^2/m = r/2B$$

For example, a 50dB signal-to-noise ratio and a 1MHz bandwidth requires, average, 2×10^{11} photon/s or 40 nW at a wavelength of $1 \mu\text{m}$.

That is the best performance one could expect, even with a perfect detector and a noiseless amplifier, limited only by the quantum fluctuations in the incoming optical signal. In real life, amplifiers are not noiseless because electrons in the conductors move with randomized velocities with energy $\sim kT$, and the amplifier has to have non-zero input conductance. Using conventional components, an amplifier with input

capacitance of 10pF and a bandwidth of 10MHz would need to have an input resistance of about 10kohm or less loading the photodiode. The mean square thermal noise voltage in a bandwidth B due to a resistance R is $\langle V^2 \rangle = 4kTRB = 8.3 \times 10^{-10} V^2$ at room temperature for an R of 5 kohm and B 10 MHz. The signal voltage generated across R due to m photons at a wavelength of $1 \mu\text{m}$ detected in time t is $V_s = mqR/t = 1.6 \times 10^{-8} m$ volts. The signal-to-noise ratio is

$$(1.6 \times 10^{-8} m)^2 / 8.3 \times 10^{-10} = 3 \times 10^{-7} m^2$$

so that in a digital system of 22 dB ratio, m is about 20,000 photons in a bit period t (taken as $1/2B$ here). This is 1000 times or 30dB greater than the quantum noise limit, which justifies ignoring quantum noise in this calculation. As 30dB can be translated into perhaps 100 km of extra fibre at $1.55 \mu\text{m}$ — by no means a small benefit — one would like to improve this situation. There are four ways of increasing the receiver sensitivity to consider. Reducing amplifier noise is one way, obviously — discussed see later — another way is discussed in the next section, and in the last section of this article two other ways are considered: optical amplifiers and coherent detection.

Avalanche photodiodes

An electron or hole accelerated by an electric field may gain sufficient energy so that when it is scattered by the lattice a lattice atom is ionized, creating an electron-hole pair. The newly created carriers can then cause impact ionization and so lead to an avalanche process with current gain.

If only one type of carrier were capable of causing impact ionization the avalanche process would advance across the high field region, the number of carriers increasing exponentially with distance but remaining finite: avalanche breakdown would be impossible. In real materials, however, both carrier types can cause impact ionization, usually with different efficiencies, providing a regenerative or positive feedback mechanism which can lead to a (theoretically) unbounded number of carriers in the breakdown. The avalanche current gain M is plotted as a function of electric field in Fig. 4; k is the ratio of ionization rates for electron and holes. The gradient of all the curves in Fig. 4 becomes infinite for some finite field, except for $k = 0$. The implication is as follows: to get useful current gain from the diode it must be biased close to breakdown — very close if k is near to unity. But any variation in field due to the diode not being perfectly uniform or the supply voltage being imperfectly regulated causes a change in the current gain, and this change can be large if k is near unity. The current gain becomes variable and also noisy. In silicon k can be as low as 0.01, and silicon diodes can be operated at gains of a few hundred or even thousands in some cases. In germanium and many III-V compounds, k is 0.3 — 1 and it is hard to fabricate and control a device for a gain

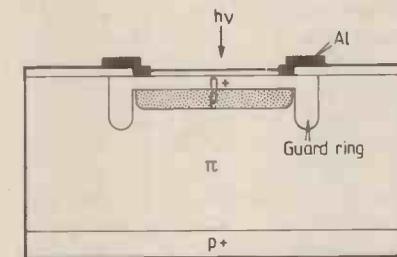


Fig. 6. Silicon reach-through avalanche photodiode is made by diffusion and implantation of dopants into a low-doped silicon substrate. Guard ring lowers electric field at the perimeter of the junction, preventing premature breakdown. Commercial silicon reach-through avalanche photodiode in a TO-18 can is the RCA 3090ZE.

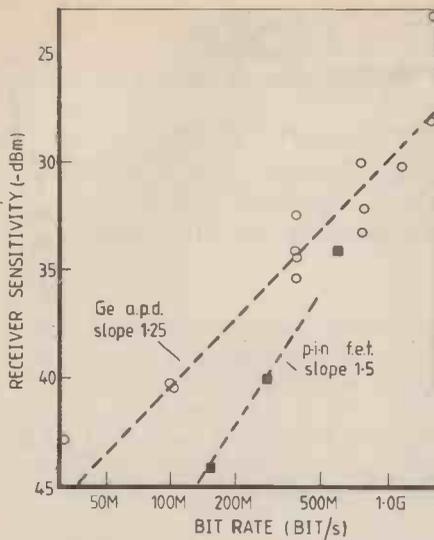


Fig. 7. Some published results on receiver sensitivity in experimental optical fibre transmission systems. Circles represent germanium diodes, and the slope of approximately 1.25 is expected for an excess noise factor exponent x close to unity. Filled squares are for p-i-n-f-e-t receivers discussed in part 2.

above 10 to 15. There are also noise problems associated with a value of k close to unity.

How is this current gain used to improve the sensitivity of an optical receiver? Current gain arising from avalanche gain increases the signal voltage across the amplifier input and so improves the signal-to-noise ratio as the amplifier noise is unaffected. However, the current gain also increases the quantum noise by the same amount as the signal, so that one cannot get beyond the quantum noise limit. In practice one cannot even get near to it because of extra noise introduced by the random impact ionization process. Consider a steady optical power P incident on the detector. The resulting multiplied photocurrent is $\langle i_p \rangle = 2P\eta qM/h\nu$. The mean square shot noise current on the photocurrent in a bandwidth B is $2q \langle i_p \rangle BM^x$, where M^x is the excess noise factor from the avalanche gain process ($0 < x < 1$). The mean square thermal noise current is $4kTB/R$. So the output power signal-to-noise ratio is

$$\frac{(2P\eta qM/h\nu)^2}{2P\eta q^2 RM^{2+x}/h\nu + 4kTB/R}$$

With $M = 1$ the thermal noise term dominates. As M is increased from unity the signal power increases as M^2 , but so long as the thermal noise term dominates the total noise power is little affected and the signal-to-noise ratio increases. When M is large, thermal noise is insignificant and the signal-to-noise ratio decreases with increasing M as M^x . There is an optimum avalanche gain:

$$M^{2+x} = (4kT/R)(h\nu/xP\eta q^2)$$

so that

$$\frac{\text{Shot noise}}{\text{Thermal noise power}} = \frac{2}{x}$$

The empirical parameter x is related to k , the ratio of ionization rates for holes and electrons. Both depend on the material, and also on the electric field strength and direction. In silicon, k is about 0.02 and x is 0.3 typically. In germanium, k is between 0.7 and 1 and x is close to 1. In III-V alloys, k ranges from 0.2 to 1 and x is 0.7 to 1. The equation is plotted in Fig. 5 with different values of x . If x is small, as with a silicon diode, the optimum gain is large and the maximum in signal-to-noise ratio is broad. The diode can, in fact, be used to vary the gain of the receiver and so provide a.g.c. When x is near unity, less improvement is possible, the optimum gain is lower and the maximum much sharper. Such diodes may be difficult to control for optimum performance.

The theory of the avalanche process and the statistics of excess avalanche noise are important in the study of optical receivers, but they are beyond the scope of this article — consult the papers by McIntyre and co-workers in the bibliography for further details (part 2).

To make an avalanche photodiode in silicon with a fast response a simple p-n junction will not do because most photons will be absorbed in undepleted material where the field is negligible. It is necessary to use the "reach-through" structure shown in Fig. 6 in which the depletion region consists of a high-doped, high field-gain region followed by a lower field, low-doped absorbing region. The problem is to ensure that the absorbing region is fully depleted well before the gain region breaks down, and this demands great control over the fabrication of the device. Nevertheless, good commercial silicon reach-through diodes have been on the market for several years.

Most system work at longer wavelengths has been carried out using germanium avalanche photodiodes. Germanium seems an obvious material, as the photodiodes can be made sensitive out to 1.6 μm and beyond by reducing the thickness of undepleted material near the surface. Germanium is not ideal because the ratio of ionization coefficients k is close to unity (i.e. $x = 1$) so that the excess noise factor is high. More importantly, the reverse bias leakage current density is high because the high intrinsic carrier concentration results in a large diffusion contribution to the leakage current. The unmultiplied leakage current density is typically $3 \times 10^{-4} \text{A cm}^{-2}$ at room temperature, sufficient to cause a

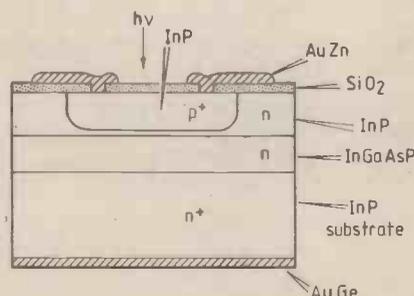


Fig. 8. Group III-V heterostructure a.p.d. has the high-field (gain) region within the large band-gap InP layer.

system penalty of a few decibels at a data-rate of a few hundred Mbit/s. The leakage current depends on temperature and at 50°C is about an order of magnitude greater than at 20°C, resulting in a large system penalty and reducing the optimum gain to about 3 to 5 as the dominant noise source may be multiplied bulk leakage. At room temperature, receiver sensitivities of -34 dBm at 400Mbaud and -30 dBm at 800 Mbaud have been reported using germanium photodiodes. These figures would be several dB worse at 50°C. Published receiver sensitivities at 1.3 and 1.55 μm are shown in Fig. 7 for the available range of bitrates, and it can be seen that the bit-rate dependence is approximately the 5/4 power, as one would expect from an a.p.d. with an x -factor near unity. Also shown are the results for p-i-n receivers with a 3/2 power dependence, as discussed in part 2 of this article.

In pursuit of the excellent performance achieved with silicon a.p.d.s considerable effort has been expended in research on diodes made in III-V compounds. To date no system results have been reported although there is much published material on the devices themselves. As with semiconductor lasers for wavelengths beyond 1 μm . The main work has been carried out on the GaInAsP/InP system, and until recently avalanche gains in the region 10 to 20 were typical, limited probably by non-uniformity of the material of the high-field region leading to micro-plasma breakdown. More recently, a structure with the high-field region in InP has been described as shown in Fig. 8, and gains of up to several thousand reported. A different reverse-bias leakage current mechanism becomes important in the high-field region of III-V diodes: tunnelling of electrons from the valence band to the conduction band. This leakage is very sensitive to field and to band-gap. The implication is that the dark current can be reduced to an acceptable level only by keeping the high field region to low-doped, large band-gap material such as InP. The excess avalanche noise properties of the device then depend on this material. □

Correction

Phase-shifting oscillator, By Roger Roosens.

A number of misprints crept into this article published in the February issue, for which we must apologise. Many of the mathematical formulae were affected and we would be happy to provide interested readers with a corrected copy if they send us a stamped-addressed envelope.

The author has asked us to point out that this distortion was measured using fixed 1% resistors for the tuning elements. Such figures could not be achieved with a two-gang potentiometer.

A numerical analysis of the thermistor distortion was made with a computer and the results were compatible with calculated ones. The only significant distortion generated in the n.t.c. is third harmonic.

The measured distortion figures show that the second-harmonic distortion of the circuit increases at low frequencies. This is due to second-order effects in the i.c.s due to temperature variation with the oscillator signal. This distortion sets the performance limit of the circuit at low frequencies.

HEATING-FUEL SAVER

Over the season some saving can be made in heating fuel bills by switching on later when the weather is less cold. This feature is usually incorporated in large systems but the unit described, which may be built at low cost, is intended for domestic use. There is an outdoor temperature sensor which is not essential but may be used to monitor the heating system.

by David Ryder, Ph.D.

The outdoor sensor is a thermistor, of which the resistance (R_t) must be known, or measured, at three relevant temperatures, for example 0°, 10°, and 20°C, which is connected in series with a fixed resistance R_s , across a stabilised voltage. By appropriate choice of R_s (see appendix), the relationship of the mid-point voltage (V_t to temperature can be quite well linearised, as shown in the table. The timing circuit uses a slowly-rising voltage V_p , and a comparator to close the switching relay when V_p reaches V_t . The ramp voltage V_p is generated digitally using a data-a converter in the prototype the popular Ferranti ZN425E, clocked at v.l.f. to give for example a delay of one hour per 10°C.

The power supply section shown in Fig 2 is suitable for a standard 24V d.c. octal-based relay, of which the coil resistance is typically 470 ohms. If a different voltage is used, R_d should be adjusted to give 8-12V input to the regulator.

Counting-up

In Fig. 3, the 425 internal counter is brought into use by tying pin 2 high. The internal resistance ladder is connected to the internal reference source (V_{ref}) by joining pins 15 and 16, and the analogue output V_p at pin 14 is then given by:

$$V_p = V_{ref} \times N / 256$$

where N is the count reached. The counter has eight stages, and the maximum count is (1 + 2 + 4 + 8 + 16 + 32 + 64 + 128) or 255. The nominal reference is 2.56V, giving 10mV per count, but its exact value is unimportant, since the thermistor R_t is also supplied from V_{ref} , and:

$$V_t = V_{ref} \times R_s / (R_s + R_t)$$

Thus the count required to make V_p exceed V_t , and so turn on the relay via comparator IC_{2a} is given by:

$$N = \text{nearest whole number above}$$

$$\left(256 \frac{V_t}{V_{ref}} = 256 \frac{R_s}{R_s + R_t} \right)$$

The table shows N values for various temperatures, relating to RS code 151-237 thermistor, which is a close-tolerance device ($\pm 0.2^\circ\text{C}$). Resistance R_s should be made up to within 1% from metal-film

resistors. Other thermistors can be used by measuring them and calculating the appropriate R_s (see appendix). Setting-up is easier if test-resistances are made up to substitute for the thermistor at say 0°, 10°, and 20°C, and in the prototype these were built in using a four-way switch.

Circuit operation

The 425 is clocked, pin 4, from a conventional 555 oscillator divided by a c.m.o.s. 4040B. The division ratio to 4040 pin 1 is 4096, and to pin 3, 64, the latter output being used via Tr₃ to flash an l.e.d., and via S₁ to give fast clocking of the 425 for test purposes. From the table the number of counts between 0°C and 20°C is 59, and if this is to occupy 59 minutes, one count per min, the 555 period must be 60/4096 \approx 0.0146 sec, or 14.6 ms. Vr₁ gives a range of about 1 to 3 hours per 20°C.

The comparator IC_{2a} has an open-collector output, which is pulled up by the 1k resistor, and the relay is switched via Tr₂. The positive feedback from the output C to the non-inverting input is needed to latch the comparator, since V_t may subsequently rise above V_p , but diode D₄ avoids loading on the input, and so on the 425

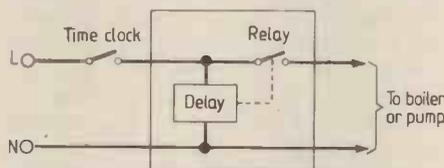


Fig. 1. In-line connection of delay unit between time-clock and load.

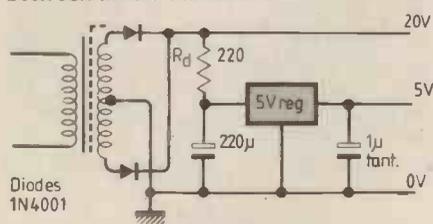


Fig. 2. Power-supply section. The regulator may be 100 mA or 1 A type.

Linearisation of RS code 151-237 thermistor, using calibration points 0°, 10°, and 20°C, resistor R_s , 15,485 ohms. Thermistor tolerance is ignored.

°C	-5	0	5	10	15	20	25
$R_t \Omega$	42,295	32,650	25,377	19,900	15,701	12,490	10,000
V_t / V_{ref}	0.2680	0.3217	0.3790	0.4376	0.4965	0.5535	0.6076
Error °C	+0.4	nil	-0.1	nil	+0.1	nil	-0.3
N (counts)	69	83	98	113	128	142	156

output, during the count-up, when C is low. The 'Set' button allows the relay to be closed without waiting for the time delay.

The 'Reset' button resets the 425 counter, pin 3, resets the comparator via D₅, and resets the 4040 via the p-n-p inverter Tr₁. At switch-on, the same function is performed by the 10µF capacitor, which delays the rise of point B. The 4040 (alone) is also reset via D₆ when C eventually goes high, stopping the count at this point, and causing the l.e.d. to glow continuously.

The op.amp section of IC₂ is used to drive a milliammeter from V_t to indicate outdoor temperature, and almost any f.s.d. can be used up to say 5mA. In the prototype an existing 0-100 scale was used for degrees Fahrenheit, and the biasing shown, R_b and R_f , gives a reading of approx 32 at 0°C, which can be trimmed by the mechanical zero adjustment. The resistance of R_m was made up to give a swing of 36 divisions between 0°C and 20°C (32°F and 68°F). The meter may of course be remotely mounted, perhaps alongside your barometer.

Checks

The eight counter outputs of the 425 are available at pins 5-7 and 9-13, and in that order have weights 1, 2, 4 . . . 128. A count of 83 for example, or 64 + 16 + 2 + 1, corresponds to pins 12, 10, 6, 5 high (and the rest low), and this allows the counting to be checked using the test resistances, and the 'fast' setting of S₁. An error of one count is not important. The 555 timing can be checked by a frequency meter, or from the l.e.d., which flashes 64 times per 'normal' 425 count.

Variations

The basic circuit still has a long delay in cold weather, for example 69 counts at -5°C, and though this can be compensated by advancing the time-clock, it is more elegant to suppress it by jumping, clocking the 425 directly from the oscillator, point F, until an appropriate count is reached. Figure 4 shows two possible circuits, 4(b) being that used in the prototype. The logic shown may be realised in various ways, but diodes and transistors are cheap, and easy to lay out on Veroboard.

If it is required to use the thermometer when the time-clock is off, the delay unit must be continuously-powered, and reset may then be modified to Fig. 5, in which the time-clock signal is detected by a transistor-type optoisolator. Reverse voltage is limited by D₇. Resistor R_r should pass 5-10mA rms, and may be replaced by a capacitor, say 0.1µF, provided it is a type suitable for continuous mains working. The intermittent output allows the 1µF capaci-

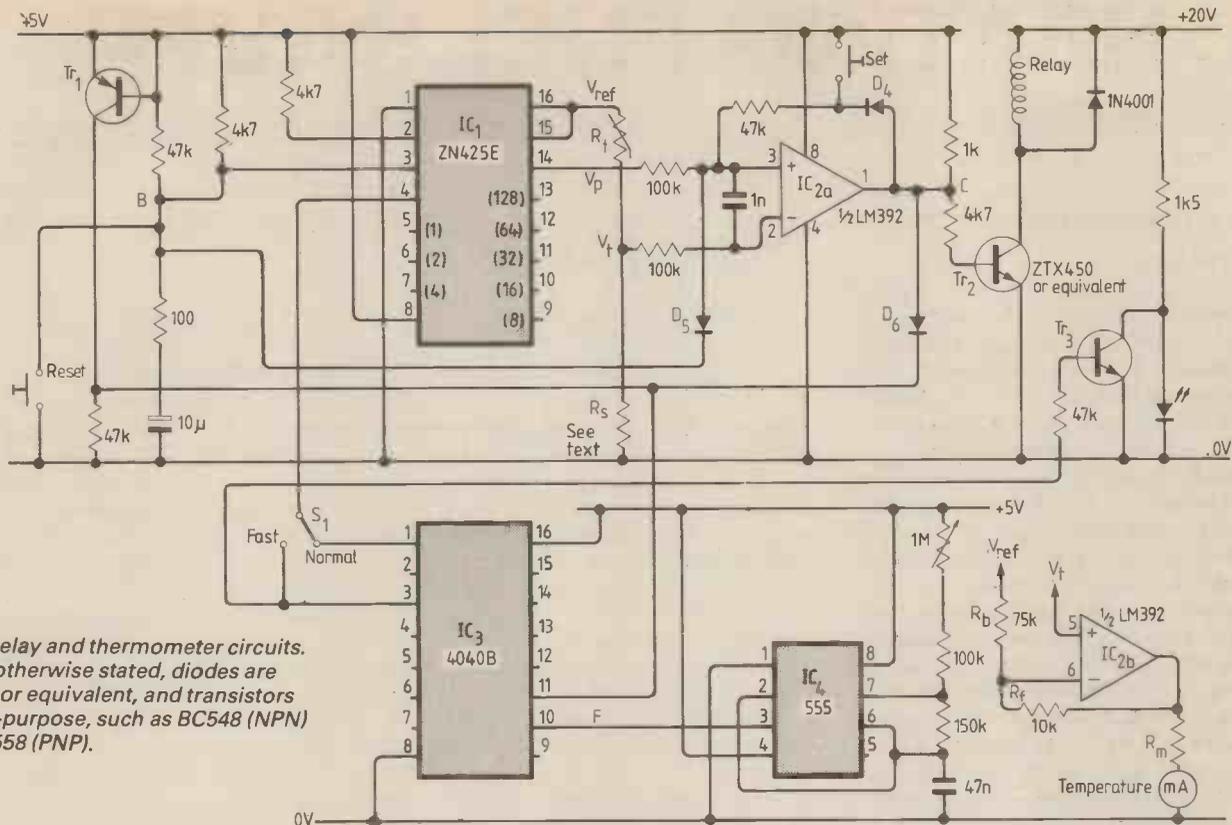


Fig. 3. Delay and thermometer circuits. Unless otherwise stated, diodes are 1N4148 or equivalent, and transistors general-purpose, such as BC548 (NPN) and BC558 (PNP).

tor to provide initial reset even if the delay unit is powered up with the time-clock on.

Since the 425 count stops at switch-on, it stores the switch-on temperature, which may be read out later in the day by switching IC2_b input to V_p (425 pin 14) rather than V_t. However it is necessary at the same time to break the normal pin 14 connection, because the feedback with C high raises V_p above its actual switch-on value.

Thermistor mounting

The RS device is a small bead, about 1.5mm dia. For the prototype, a 1.6mm hole was drilled nearly through a 12mm cube of aluminium, then enlarged part-way to a push-fit for a 4mm tube about 10cm long, which in turn fits through a 4mm hole drilled in the frame of a north-facing window. The thermistor leads were extended by 7/02 wires, and the assembly pushed down the tube, so that the thermistor bead entered fully into the 1.6mm hole. A blob of heat-conductive grease was used to improve thermal contact, and the block and tube were painted dull black. Thin twisted wire was used for connection. If a long run is needed, it would be advisable to decouple V_t to ground via 10µF to suppress any hum pick-up.

Appendix

The usual thermistor formula is $R_t = A \exp(B/T)$, where T is absolute temperature in degrees Kelvin ($C + 273$), and A (ohms) and B (K) are nominally constant. B is often around 3,000, and A is a small fraction of an ohm. Values can be deduced from measurement at any two temperatures, but since they are only approximately constant, calculations are best restricted to interpolation only.

The method of calculating R_s does not

however depend on A and B , but merely makes three calibration points lie on a straight line. The arithmetic is simplest if the calibration temperatures are equally spaced, $T_3 - T_2 = T_2 - T_1$. Suppose the value of R_t at T_1 is R_1 , at T_2 $a.R_1$, and at T_3 $b.R_1$. Then R_s is given by:

$$R_s = R_1 \times \frac{a - 2b + a \cdot b}{1 - 2a + b}$$

As the table shows, the linearity between calibration points is good, and it is acceptable over a larger range. It may be noted that, from Thévenin's theorem, the same value of R_s applies in a circuit using a constant current through R_s and R_t in parallel. Maximum thermistor power occurs when $R_t = R_s$, and for Fig. 3 is $1.28^2/15,485$, about 0.1 mW, which for the device used, in free air, would produce about 0.1°C self-heating. When using lower-resistance thermistors, the possibility of self-heating error should be borne in mind.

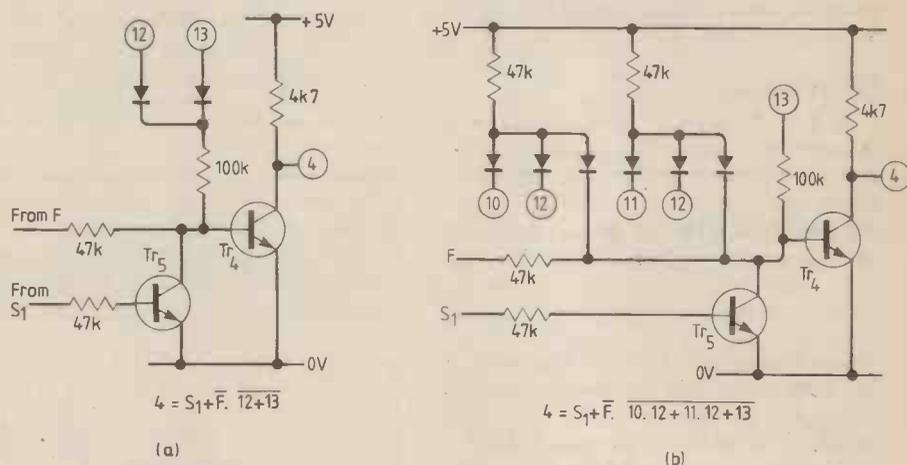


Fig. 4. Count-jumping; 4(a), jump to 64; 4(b), jump to 80. Numbers in circles are 425 pins, and the circuits replace the direct connection of S₁ to pin 4.

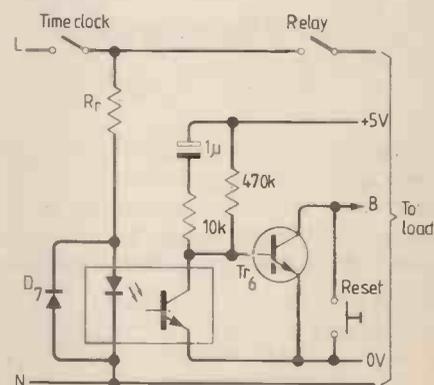


Fig. 5. Opto-isolator reset, for use when delay unit is independently powered. With this circuit omit components 100R, 10µF from Fig. 3.


CIRCUIT IDEAS

Low-power grid blanking

Electron-beam blanking at the first grid can involve much higher voltages than cathode blanking but is sometimes desirable. This circuit was designed for digitally-controlled grid blanking of a camera tube used for quantitative light measurements. The grid voltage (equal to V_-) can be accurately controlled during the active picture line and transitions to and from the blanking potential are short, at 40ns and 300ns respectively, with no ringing when a Schottky t.t.l. input is used.

Because grid-leakage current is extremely low, the high voltages required can be achieved by switching the connections of a charged capacitor. When the input-logic signal goes low, Tr_2 is turned off and Tr_1 and Tr_3 turned on so that the voltage over capacitor C, V_C , is the difference between the rail voltages, $V_+ - V_-$. The output to g1 is held at the negative rail, which controls the beam current.

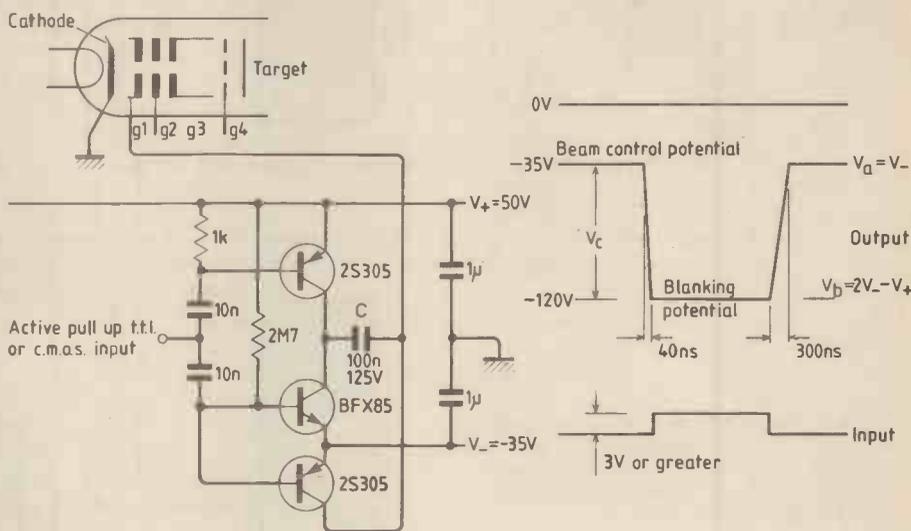When the input goes high, Tr_1 and Tr_3 are turned off and Tr_2 turned on, so that the more positive side of C is taken to V_- and the negative side consequently to the



blanking potential, $V_- - V_C$ which is also $2V_- - V_+$. The droop in blanking potential caused by leakage through Tr_3 is negligible in normal use. There is no droop in the beam-control voltage as Tr_3 remains sufficiently conductive throughout the ac-

tive line. The g1 lead **must** be kept well away from the target connection to avoid interference.

D. J. Thomas
MRC
Cambridge



Telephone-line interface

Conventional telephone-interface circuits use relays and/or transformers for loop detection and speech coupling. In this circuit, a 5V positive-voltage regulator is used to feed a constant current to the telephone line. The line current is set by R_1 and the regulator output provides a logic signal that will 'follow' dialling pulses from the telephone.

As this circuit provides unbalanced transmission to the telephone, it is only suitable for internal (intercom type) exchanges. A ring circuit could be provided by a third wire to the telephone. Acknowledgement to the Director of Research* for permission to publish this information.

F. T. Lyne

*British Telecom Research Labs
Ipswich

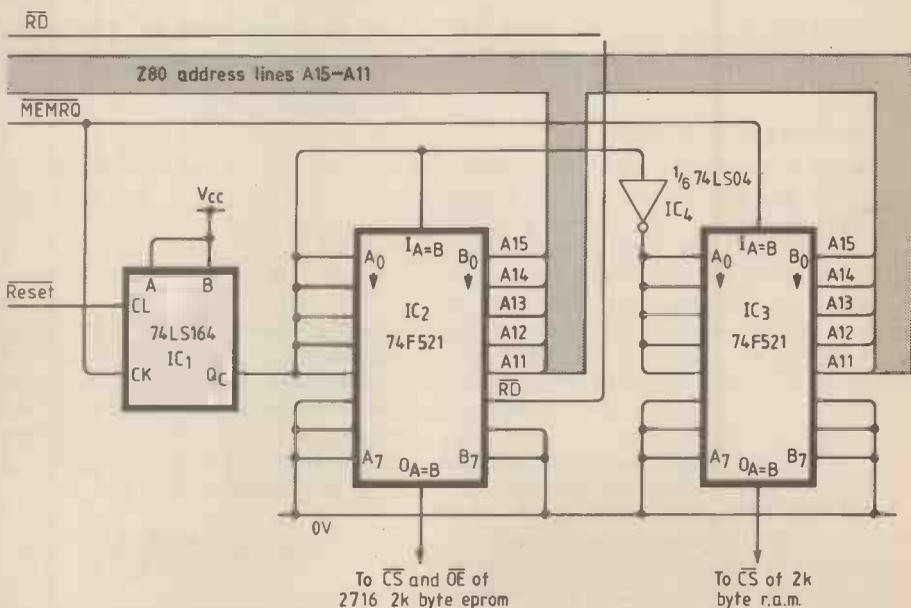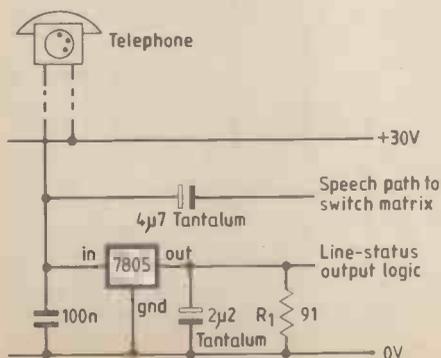

Z80 memory mapping

R.a.m. area for interrupt restart vectors and e.p.r.o.m. write protection are provided by this automatic memory map and switch for a Z80 microprocessor system. On power-up, or after a reset, a 2K-byte e.p.r.o.m. (2716) occupies addresses 0000 to 07FF and a 2K-byte r.a.m. is address mapped to F800-FFFF. After a reset, the Z80 will perform an op-code fetch from location 0000. The e.p.r.o.m. will be selected after \overline{MREQ} is activated. The instruction at locations 0000 to 0002 is JP F803

and the circuit will automatically switch r.a.m. and e.p.r.o.m. locations after the third memory access. The next op-code fetch will occur at location F803, causing execution to continue from the next contiguous location in e.p.r.o.m. Locations 0000 to 07FF are now occupied by the 2K r.a.m. so it is possible to initialize and modify the interrupt restart vectors, hence providing a greater degree of flexibility.

C. Jay
Fairchild Camera and Instrument Ltd
Bristol

Testing p.r.b.s. generators

Readers experimenting with p.r.b.s. generators may find this circuit useful for evaluating possible feedback configurations. Driven by an external clock at any speed up to a few hundred kHz, it gates clock-pulses to an external counter for exactly the duration of one complete sequence, maximal or otherwise, so that the final counts shows the number of steps in the sequence. The generator is preset so that the count begins almost immediately.

The shift-register shown has n effective stages and is negative-edge triggered (e.g. 4006's); for a positive-edge triggered shift-register the inverted clock-signal is used.

When the system is at rest, both flip-flops are in the reset state and no clock-pulses appear at the output. Point A is low,

so the auxiliary counter is held at zero and the input to the shift-register is held high. After a maximum of n clock-cycles all the stages of the shift-register will be in the high state, and the system ready to start.

The start button sets the start flip-flop on the next negative-going transition of the incoming clock-signal; contact-bounce has no effect. Point A goes high. This allows the generator to run normally, with its output (from stage n of the shift-register) controlling the auxiliary counter. When the generator output is high, the counter advances one count on each positive-going transition of the incoming clock-signal; when the generator output is low the counter is held at zero.


Once per complete sequence the generator output remains high for n consecutive clock-cycles; the counter then reaches the count of n causing point B to go high until

the counter is reset (nominally a half clock-cycle later).

Because all stages of the shift-register were initially preset to the high state, the first signal at B occurs during the n 'th clock-cycle from the start. This signal sets the gate flip-flop. This in turn allows clock-pulses to appear at the output, and also resets the start flip-flop while maintaining point A high so that the system continues to run. These conditions continue until the next signal appears at B exactly one sequence later, and resets the gate flip-flop; then the clock-pulses cease to appear at the output, point A goes low, the generator ceases to run, and, after a maximum of n clock-cycles, the system is back in the ready state.

Pressing the reset button will return the system to the ready state at any time.

E. L. Jones
Bucknell
Shropshire

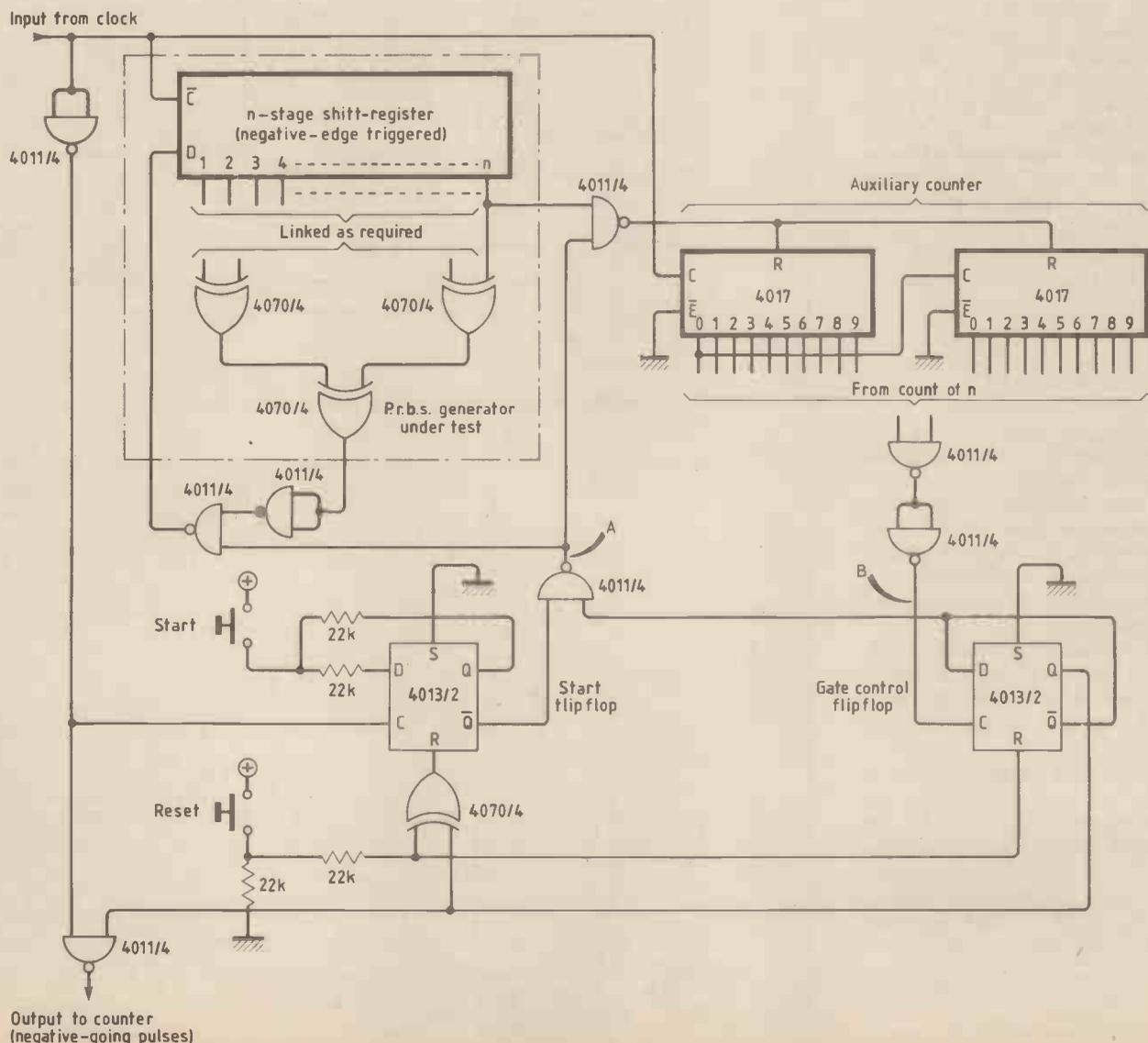

DESIGNING WITH MICROPROCESSORS 13

Clear-cut step-by-step procedures for the design and implementation of d.m.a. interfaces are described. Specifically, it is proved that in the case of action/status peripherals the interface reduces to two wires.

The block diagram of a d.m.a. system is shown in Fig. 1. The function and operation of the address decoder, the d.m.a. controller and the cycle-steal logic has been explained in the previous article (February, 1982). Briefly what happens is this. The programmer sends to the d.m.a. controller (by means of i/o instructions) three items of information specifying (i) the starting memory address, (ii) the size of the block, and (iii) the direction of transfer, followed by the 'go' command. On receipt of the 'go' command, the d.m.a. controller activates the peripheral interface by pulling enable signal E in Fig. 1 high ($E := 1$). When activated, the interface monitors the status signals of the peripheral, and requests a cycle steal when the peripheral is ready. When the microprocessor responds, the interface and the d.m.a. controller generate the appropriate command signals needed by the peripheral and the memory chip for the transfer of one item of information (usually a byte) between them. At the end of each cycle steal, the memory address is incremented/decremented, and the word count is decremented ($n := n - 1$). This process continues until the word count reduces to zero ($n = 0$), at which time the interface is disabled and the end-of-transfer signal, ϵ , is generated.

D.m.a. interfaces

The function of d.m.a. interfaces is to request the microprocessor to go on hold when the main memory is to be accessed, and to generate the appropriate signals needed by the peripheral when the memory becomes accessible. In the case of cycle-steal systems, as we have already seen, the hold request is generated each time the memory is to be accessed, and removed after a memory cycle is granted.

The block diagram of a suitable d.m.a. interface, assuming logic signals throughout, is shown in the shaded section of Fig. 2. It operates in the following manner.

When logic block 1 recognizes that the peripheral is ready to be accessed, it sets flip-flop 3 by pulsing its clock terminal. Its output is Anded with the enable signal E to produce the cycle request signal c. (Assume $\bar{e} = 1$). When the requested memory cycle is granted, line h is pulled high and a pulse is generated on line k. Signal h being

by D. Zissos* assisted by Glen Stone*

high, and $E = 1$, activates logic block 2, which responds by generating the appropriate command signals needed by the peripheral for accepting or receiving an item of information. Similarly, pulse k activates the d.m.a. controller, which ini-

tiates either a memory read or a memory write cycle. At the end of the memory cycle the microprocessor resumes normal activity, until the peripheral becomes ready, which causes logic block 1 to pulse the clock terminal of FF3. This pulls the cycle-steal line c high and sometime later a link between memory and logic block 1 is established for a memory cycle. The process repeats itself until the last item has

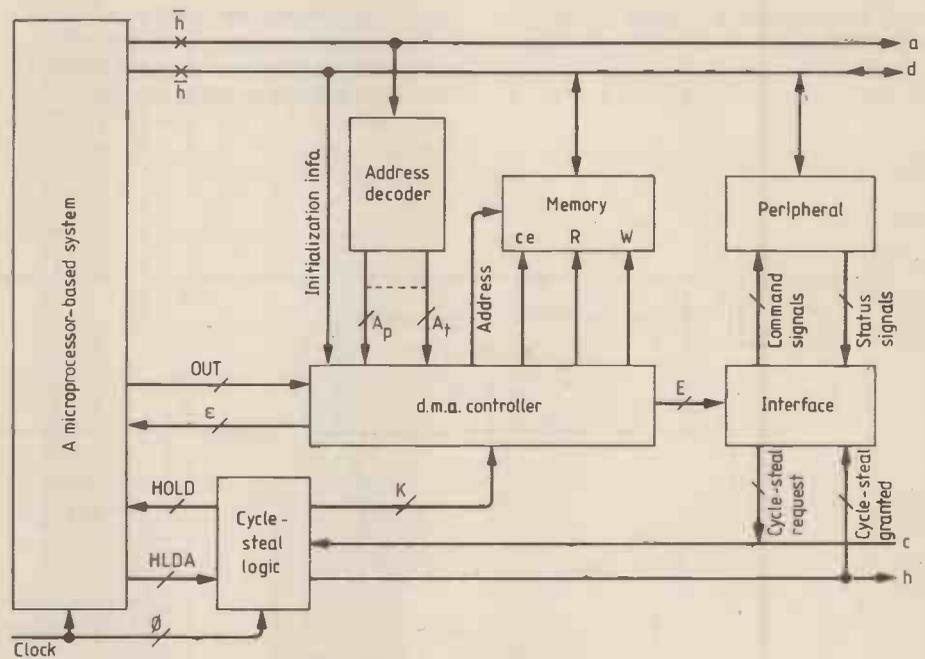


Fig. 1. Block diagram of a d.m.a. system using cycle stealing.

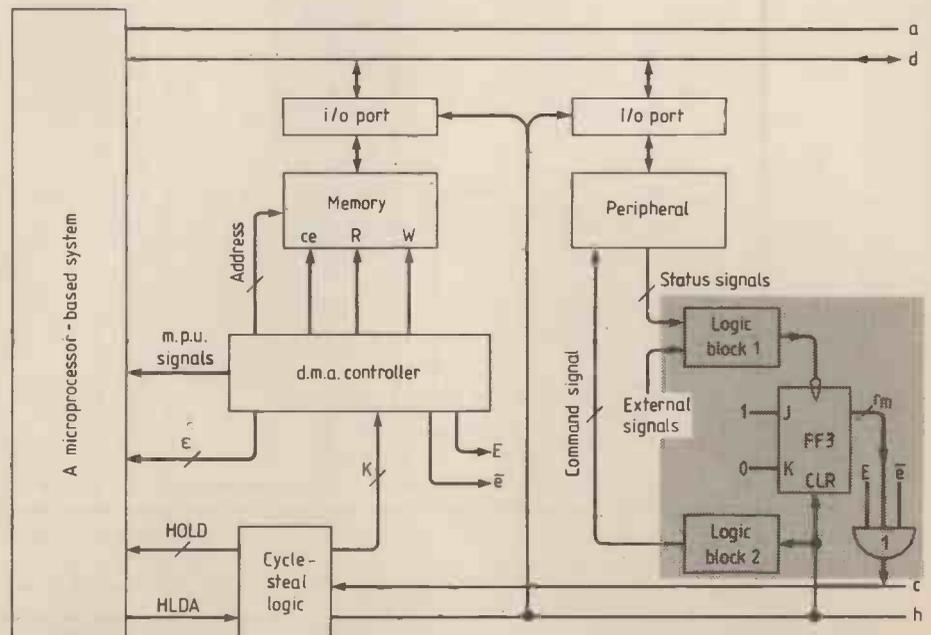


Fig. 2. Block diagram of peripheral interfaces in d.m.a. systems (shaded section).

* Department of Computer Science, University of Calgary, Canada

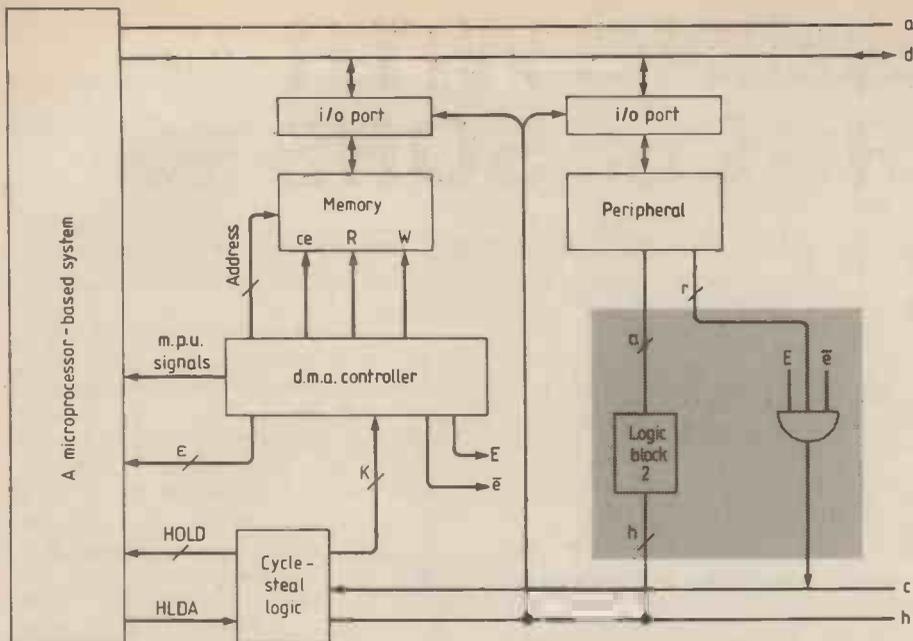



Fig. 3. D.m.a. interface for action/status peripherals.

been transferred between the peripheral and memory. At this time the d.m.a. controller generates end-of-transfer signal, ϵ , to inform the system that the requested block transfer has been completed. The system responds by turning signal E off; this disables the interface.

The two-wire interface

In the case of action/status devices and no external signals, signal r_n is generated directly by the peripheral, thus eliminating the need for logic block 1 and FF3 in Fig. 2. This reduces the peripheral interface to logic block 2, as shown in Fig. 3.

Fig. 5. Circuit implementation of d.m.a. systems.

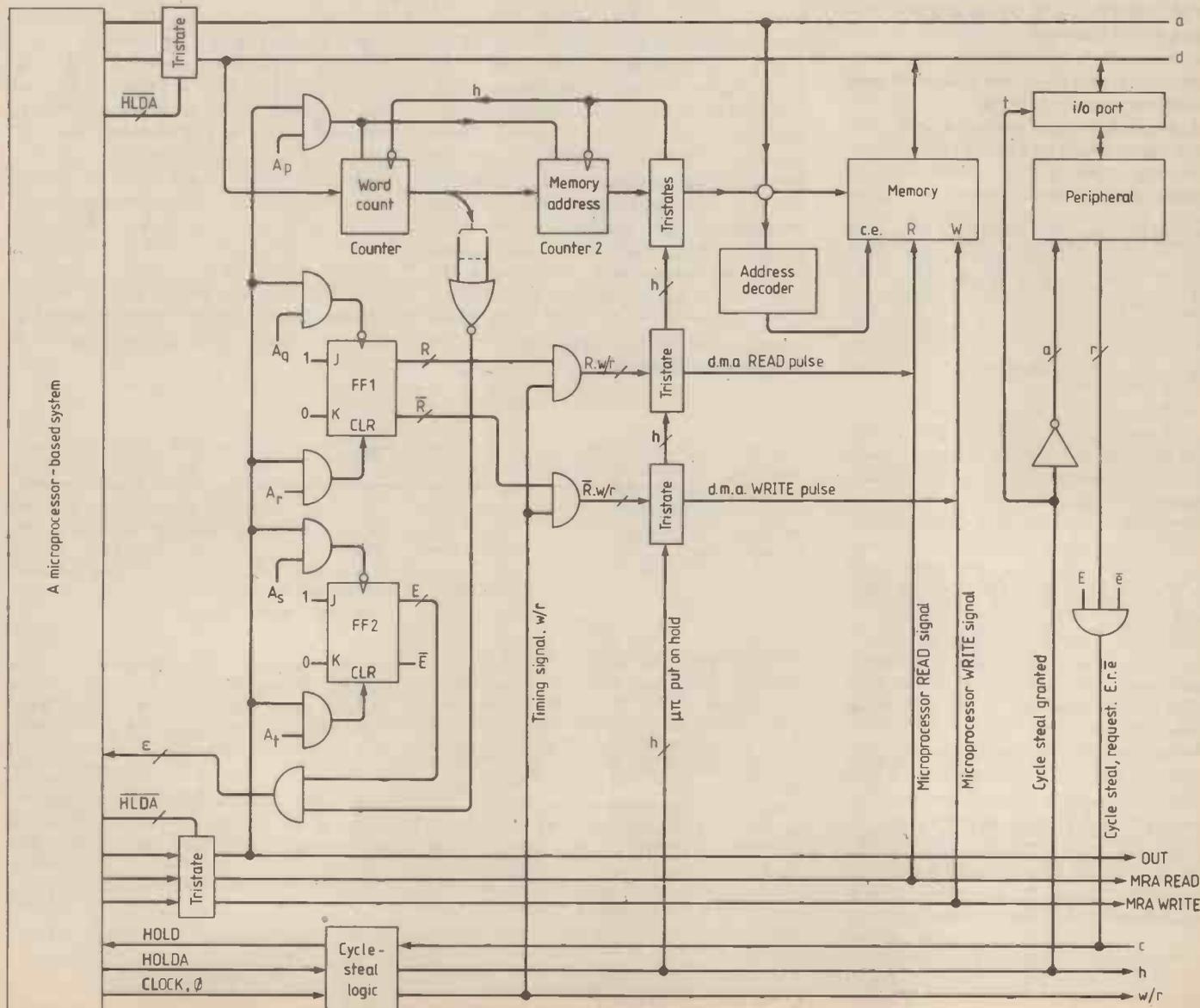

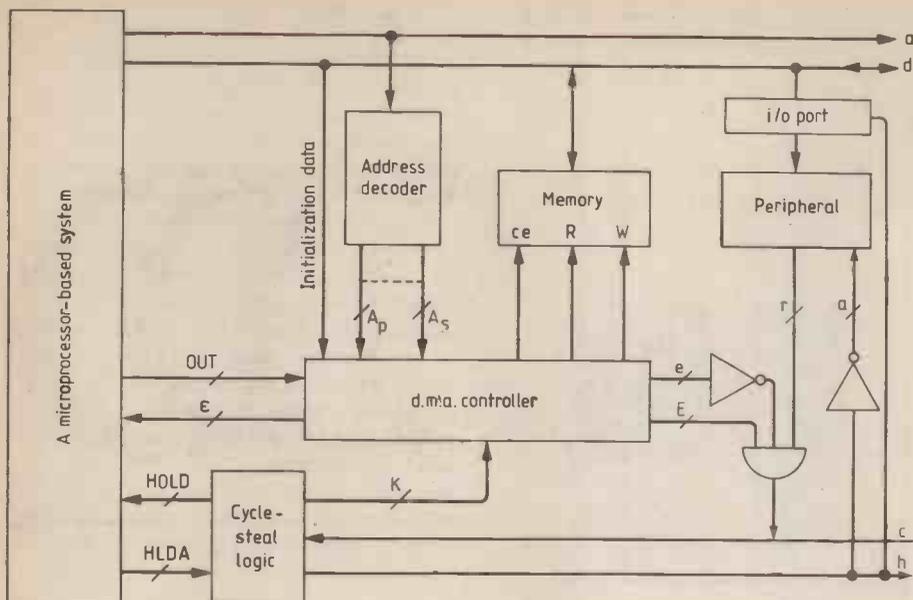


Fig. 4. The two-wire interface.

Now, to avoid possible problems resulting from peripherals being activated while data transfers take place, a peripheral will be activated when a cycle steal is terminated; that is, when the value of h changes from 1 to 0. Since action/status peripherals are activated by pulling their action terminal high, it follows that

$$a = \bar{h}$$

That is, logic block 2 reduces to a single inverter, as shown in Fig. 4.

The detailed circuit implementation of a d.m.a. system is shown in Fig. 5.

D.m.a. software

Because in d.m.a. systems transfers of data between a peripheral and the main memory take place autonomously, software is needed only to send initializing information to the d.m.a. controller in Fig. 1, and to clear the end-of-transfer signal, ϵ , if it is implemented as an in-

terrupt flag. The initializing information, as we have already explained, consists of the following items

- the starting address,
- the block length,
- the direction of transfer, and
- the 'go' command.

It is transferred into the d.m.a. controller in the following manner. The programmer loads the accumulator with the initial memory address and executes an Out instruction with address A_p . This pulses the load terminal of the two counters, which transfers the accumulator contents (the initial memory address) into counter 1. At the same time, because the two counters are connected in cascade, the contents of counter 1 are pushed into counter 2. The programmer then transfers into the accumulator the block length and executes the same Out instruction. This causes the memory address in counter 1 to be pushed into counter 2, and the value of the block length (held in the accumulator) to be loaded into counter 1.

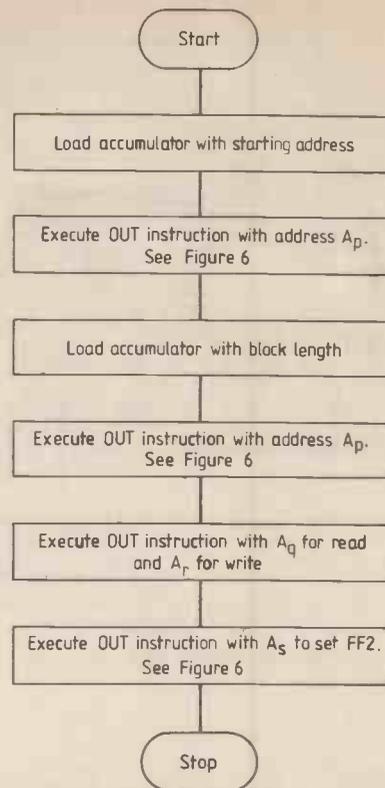


Fig. 6. D.m.a. software.

Next the programmer executes another Out instruction with A_q if the block of data is to be read from memory, and with address A_r if the data is to be written into the memory. In the first instance FF1 is set, and in the second is reset. The 'go' command consists also of executing an Out instruction with address A_s . Execution of this instruction sets FF2, turning signal E on which initiates the block transfer. For ease of reference the d.m.a. software is flowcharted in Fig. 6.

In our case acknowledging the end-of-transfer flag (ϵ) consists of resetting FF2, that is of executing an out instruction with address A_r . □

LITERATURE RECEIVED

SE labs have issued a new shortform catalogue on the company's range of instrumentation tape recorders. There are a large number of recorders for laboratory or field use with a variety of numbers of track and recording speeds up to the SE9000, a 42 track digital recorder. Data Recording Division, SE Labs (EM) Ltd, Spur Road, Feltham, Middlesex TW14 0TD.

WW401

The Micro Focus Newsletter has been produced to keep readers up to date with the latest COBOL computer language products and developments. COBOL is in increasing use in microcomputers and Micro Focus have announced a COBOL II which may be used on both mainframes and micros. The Newsletter is available free from Micro Focus, 58 Acacia Road, London NW8.

WW402

The 1981/82 Colorado Video short form catalog describes a series of specialised video instruments designed for slow scan tv telecommunications, computer/video input and output, measurement and analysis. The UK agents are Anaspec Ltd, Pearl House, Bartholomew Street, Newbury, Berks RG14 5LL.

WW403

RS Catalogue. The latest edition of the catalogue from RS Components Ltd has 344 pages and includes a newsheet called Rapid Scan, which is running a competition to find out who is RS's longest standing customer. Anyone who can find an old catalogue, delivery note or invoice from RS (or Radiospares as they were then) could win a magnum of champagne. The catalogue lists as additions to its contents over 75 items including data transmission cables, splashproof connectors, a bubble etch tank for p.c.b.s, a front panel with keyboard and the p.c.bs for a programmable timer, many new displays, a wide selection of tools and accessories and additions to the engineers bookshelf. Details from RS Components Ltd, PO Box 427, 13-17 Epworth Street, London EC2P 2HA.

WW404

Racks. The full range of Series 80 instrument racks from Imhof-Bedco Standard Products Ltd, Ashley Works, Ashley Road, Uxbridge, Middlesex, is detailed in a catalogue available from the company. The range includes the new S80/600 racks which meet the latest IEC297 specification. Detailed with the racks is a range of standard accessories such as tops, doors, mobile bases, etc.

WW405

A wide range of TMK testmeters including digital multimeters, clamp ammeters and industrial thermometers, is detailed in literature from Harris Electronics (London), 138 Gray's Inn Road, London WC1X 8AX.


WW406

The French company Radiall offer a short catalogue of microwave components, including transitions, couplers, attenuators, relays and isolators. Write to Microwave Components, Lts, Invincible Road, Farnborough, Hants.

WW407

A forty-page catalogue of panel meters, multimeters and test equipment is available from Bach-Simpson, who are at Trenant Estate, Wadebridge, Cornwall PL27 6HD.

WW408

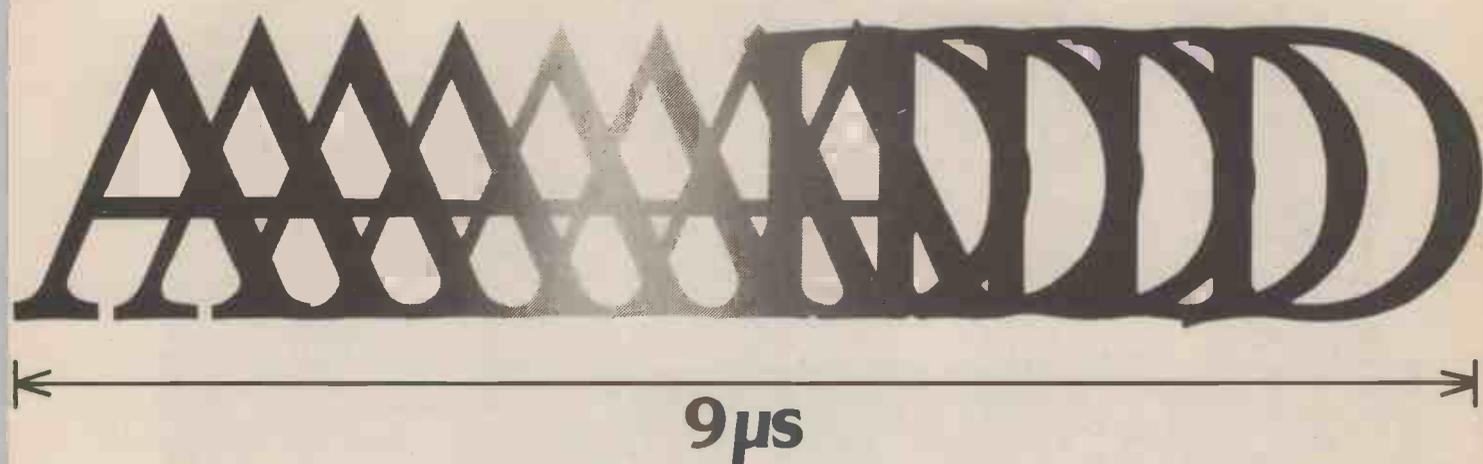

A to D in 9 μ seconds. And that's only the start.

The fact that the new Ferranti ZN447, ZN448 and ZN449 A to D converters are probably the fastest microprocessor compatible converters on the market is only one reason for choosing them.

They offer a better cost/performance ratio than others.

They have bus compatible, three-state outputs and control inputs for easy microprocessor interfacing.

They come complete with on-chip clock and precision bandgap reference, needing only passive external components to operate with unipolar or bipolar input voltages.

You get a wide choice of error specification and operating temperature ranges.

And simple operation.

Send for data or contact,

Ferranti Electronics Limited,
Fields New Road, Chadderton, Oldham OL9 8NP
Tel: 061-624 0515 Telex: 668038




FERRANTI

Semiconductors

WW - 037 FOR FURTHER DETAILS

Distributors: Celdis, Reading, Tel: 0734 585171 • Comway Electronics, Bracknell, Tel: 0344 24765 • Intel Electronics, Henlow, Tel: 0462 812505
ITT Electronic Services, Harlow, Tel: 0279 26777 • Semicomps, Keighley, Tel: 0535 65191 • Semicomps, Kelso, Tel: 0573 24366
Swift-Sasco, Crawley, Tel: 0293 28700 • Swift-Sasco, Rochdale, Tel: 0706 47411

test instruments
for every need

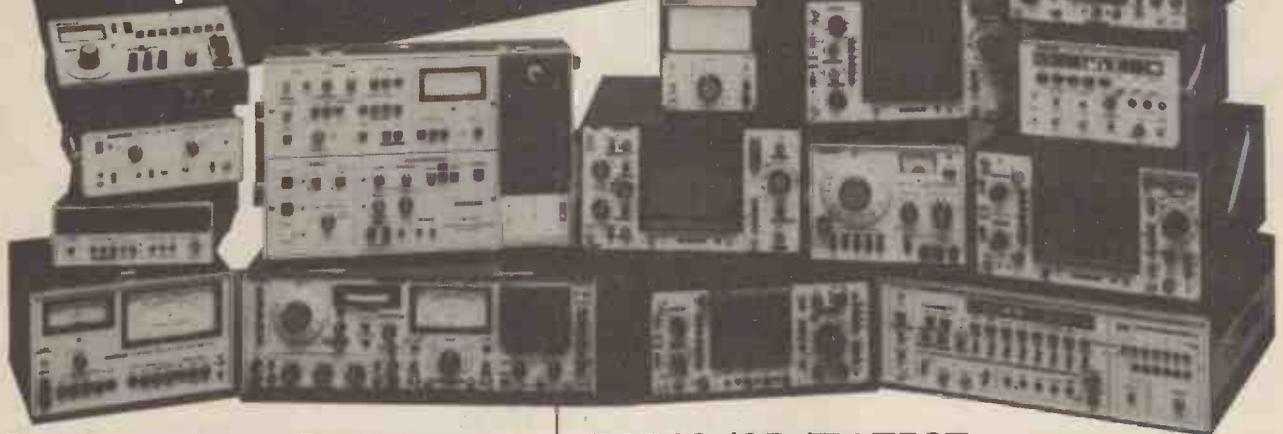

The full range of Leader Test Equipment, the first choice of engineers around the world, is now available in the U.K.

Leader products, with a long history of high reliability, back by a 1-year warranty, are engineered and built to the most rigid standards, and incorporate the latest technology. A complete technical and service facility is provided in the U.K. by Thandar Electronic Ltd

OSCILLOSCOPES

4-50MHz Oscilloscopes with more performance and reliability for less cost. The Leader range of oscilloscopes includes 14 models, single and dual trace, for bench or field use. All models offer comprehensive triggering controls, TTL compatible Z-AXIS modulation and convenient colour-keyed front panel layout. Probes are included with each model.



**LBO508A
OSCILLOSCOPE**

With 20MHz bandwidth and 10mV input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications

- *5" Dual trace
- *DC-20 MHz bandwidth (vert amp)
- *10mV Sensitivity
- *Sweep mode: chop - ALT, CH1, CH2, X-Y
- *Synchronisation: Auto, Norm, TV, Int., Ext., +, -
- *Timebase Sweep Speeds: 0.5µs/cm - 200 ms/cm
- *X5 Magnification (max speed 100ns/cm)

LBO 310A	4 MHz	20 mV Single Trace	3"	
LBO 301	8 MHz	10 mV Single Trace	3"	
LBO 308A	20 MHz	2mV Dual Trace	3.5"	Mains/Battery
LBO 510A	4 MHz	20 mV Single Trace	5"	
LBO 512A	10 MHz	10 mV Single Trace	5"	
LBO 513	10 MHz	5 mV/1 mV Single Trace	5"	
LBO 514	10 MHz	5 mV/1 mV Dual Trace	5"	
LBO 552A	10 MHz	20 mV Dual Trace	5"	Stereo Scope
LBO 506A	15 MHz	10 mV Dual Trace	5"	
LBO 507A	20 MHz	10 mV Single Trace	5"	
NEW				
LBO 515B	30 MHz	5 mV Dual Trace	4.5"	Sweep Delay
LBO 520A	35 MHz	5 mV Dual Trace	5.5"	
NEW				
LBO 517	50 MHz	5 mV/1 mV Quad Trace	6"	Sweep Delay

From £102 + VAT

Thandar Electronics Ltd. reserve the right to alter prices and specifications on Leader equipment without prior notice.

RADIO/CB/TV TEST

CRT Testers · Pattern Generators · Signal Generators
Antenna Impedance Meters · RF Power Meters ·
C.B. Signal Generators · Stereo Signal Generators ·
Dip Meters · SWR/Wattmeters

LSG16 SIGNAL GENERATORS

A compact R.F. generator ideally suited to checking alignment of AM/FM and T.V. receivers.

- *Frequency Range 100 KHz - 100 MHz
- *Frequency accuracy ± 1.5%
- *Crystal Oscillator 1-15 MHz
- *Modulation Internal 1kHz for A.M.
- *Output Voltage 0.1Vrms or higher to 100 MHz £55 + VAT



GENERAL TEST

Function Generators · Transistor Checkers · LCR Bridges
Power supplies · Millivoltmeters · Curve Tracers · Home
Appliance Testers

LHM 80A H.V. METERED PROBE

- *Input Impedance 20K Ω per volt
- *Range 40K Volts
- *Accuracy ± 3% Full Scale £16 + VAT

LDP 076 LOGIC PROBE

- Fast servicing and analysis of digital circuits
- *Input Impedance > 10M Ω
- *Frequency Range DC to 50 MHz
- *Minimum Pulse Width 10nsec £49.50 + VAT

NEW



AUDIO TEST

Audio Generators · Frequency Response Recorders
Audio Systems Analyzers · Wow & Flutter Meters
Speaker Analyzers · Audio Testers · Distortion
Meters · Attenuators

LFR5600A FREQUENCY RESPONSE RECORDER

Designed to graphically record wow and flutter, drift, voltage, temperature and frequency response of Audio equipment.

- *Frequency Range 20 Hz - 30 KHz
- *Variable chart speed
- *Voltage range 0.1V, 10V
- *Sweep Oscillator *Pilot Signal *Cartridge pen
- *Metered, swept frequency input/output voltage £1450 + VAT

NEW



LEADER



For full technical details together with price list please contact.

thandar

ELECTRONICS LTD
ELECTRONIC TEST & MEASUREMENT
London Road, St. Ives,
Huntingdon, Cambs PE17 4HJ.
Tel: St. Ives (0480) 64646 Telex 32250

ELECTRONIC ORGAN WITH PIPE ORGAN SOUND

Observation of the waveforms emitted from a pipe organ show that many of them are triangular or closely related in shape. This design uses triangle-wave generators in a simplified organ system to reproduce them, and offers more accurate sound than those organs using sine, pulse, saw-tooth or square wave generators.

The signals from the waveform generators can be fed by way of an appropriate stop, directly to the output amplifier without any filter. This simplifies the design and the use of high-level signals reduces noise problems.

If a triangle wave is rectified, an open diapason sound is produced. Full-wave rectification produces a triangle wave of twice the frequency which can be used as a 'four-foot flute' stop.

To reduce the cost and complexity of the organ, a multiphonic system¹ has been used which required only six generators, however many alternatives are possible.

An on/off detector to drive the attack/delay modulators has been developed which provides an improved performance.

by **J. H. Asbery**,
Ph.D., M.I.E.R.E.

The detector can also be used with other synthesizer circuits to eliminate one pole of the switching system. An ultrasonic signal is superimposed on the d.c. voltage of the resistor chain of the keyboard. When a key is pressed, this signal appears at the input of IC₂ which switches on the modulators at a steady rate and switches them off at a steady rate when the key is released. Collector resistors R₅₄ and R₅₈ of Tr₃ and Tr₄ can be common to all generators and

should be positioned close to the amplifier to avoid pick-up from the common earth wiring.


To produce an 'eight-foot diapason' signal it is not necessary to rectify the original triangle wave. By resistively mixing the original wave with one at half the amplitude of the full-wave rectified signal, the required tone is formed (at R₅₆, R₅₇).

Switching transistor Tr₂ is used in the reverse mode to reduce the voltage drop and improve the v.c.o. linearity.

The capacitor across the volume control (R₆₃) compensates for a loss of sensitivity at low frequencies.

The complete organ is powered by a single +15V supply. The choice of a power amplifier has been left to the constructor.

Complete circuit showing one generator.

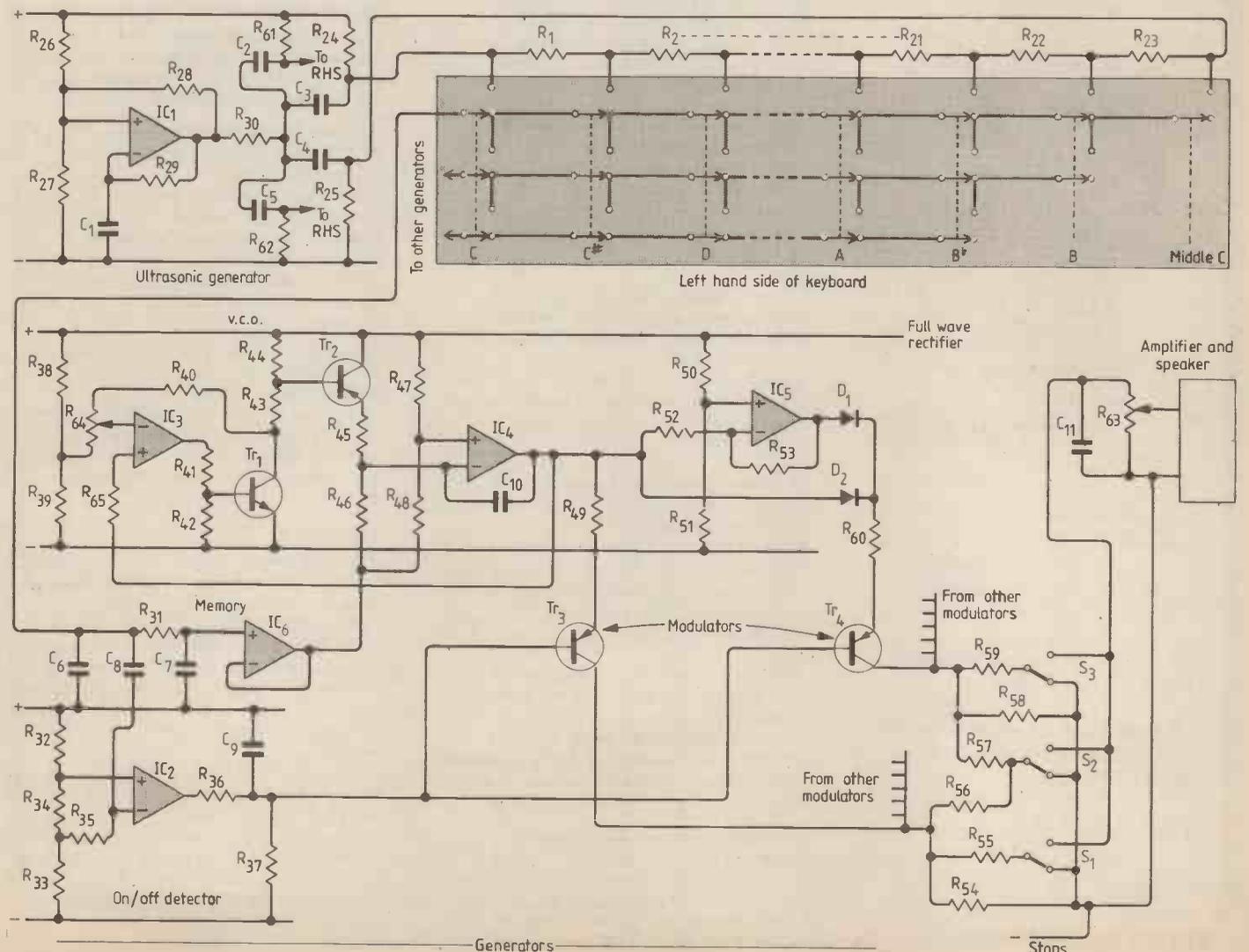

Components

Resistors

1 to 23 a set of music scale resistors from 10 Ω upwards

24	165 1%
25	162 1%
26, 27, 28	33k
29, 30, 31	10k
32, 33	33k
34	68
35, 36	100k
37	220k
38	20k 5%
39, 40	20k 5%
41	10k
42	1k
43	1.2k 5%
44	470
45	11.5k
46	23k 1%
47	20k 5%
48	20k 5%
49	47k
50	15k
51	15k
52	15k
53	15k
54	10k
55, 56	100k
57	220k
58	10k
59	100k
60	33k
61	165 1%
62	162 1%
63	10k
64	3k preset (tuning)
65	10k

Capacitors

1	2.2n
2, 3, 4, 5	0.1 μ
6	220 μ
7	0.18 μ
8	15n
9	0.47 μ
10R	0.025 μ (right-hand generators)
10L	0.1 μ (left-hand generators)
	(Both 2½% polystyrene)
11	0.1 μ

IC ₁ , IC ₂ , IC ₃	709
IC ₄ , IC ₅ , IC ₆	741
Tr ₁	BC149 or similar
Tr ₂ , Tr ₃ , Tr ₄	BC307 or similar
D ₁ , D ₂	1N4148
S ₁	(8ft flute)
S ₂	(8ft open diapason)
S ₃	(4ft flute)

Component kits are available from the author at 87 Oakington Manor Drive, Wembley, Middlesex.

Reference

1. Asbery, J. H. Multiphonic Organ, *Wireless World*, June 1973, p.303.

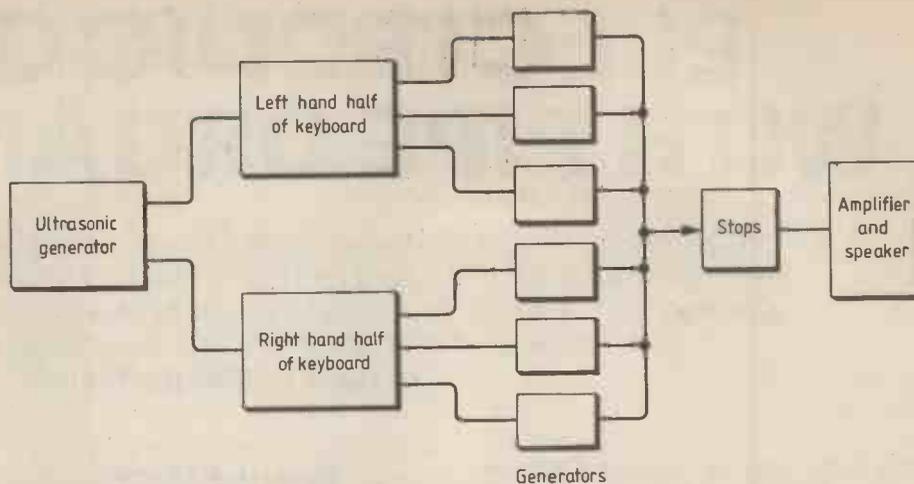


Fig. 1. Multiphonic organ system based on six triangle-wave generators.

BOOKS

COMPUTING

Practical Trouble-shooting Techniques for Microprocessor Systems, by J. W. Coffron. 246 pages, hardback. Prentice-Hall, £13.95.
Fault-finding techniques for the hardware of 8-bit systems using 8080, 8085, Z80 and 6800 microprocessors. Final chapter devoted to TRS-80 microcomputer.

The S-100 and other Micro Buses, by E. C. Poe and J. C. Goodwin, 206 pages, paperback. Prentice-Hall, £6.95.
 The S-100 and 20 other buses, as applied to most of the popular microcomputers. Includes a description of methods of converting signals on other buses to S-100 signals. Provides pin designations of various bus systems.

Microprocessor and Microcomputer Technology, by Noel M. Morris. 255 pages, hardback/paperback. Macmillan £15.00/£5.95.
 An introduction to the use of logic devices and microcomputers, starting from very simple description and progressing to programming and application.

Learn Computer Programming with the Commodore VIC, by L. R. Carter and E. Huzan. 100 pages, paperback. Hodder and Stoughton, £1.95.
 A short course in the use of Basic on the VIC microcomputer. A number of applications and programs are given, and there are problems (with answers).

Microelectronics and Microcomputers, by L. R. Carter and E. Huzan. 232 pages, paperback. Hodder and Stoughton, £1.95.
 Rather more general than the previous book, this is intended as an introduction to computing for the business or scientific user, and for those working on industrial control and measurement.

The 68000: Principles and Programming, by L. J. Scanlon. 238 pages, paperback. Prentice Hall, £10.45.
 A full description of the 68000 16-bit microprocessor, its capabilities and operation. Many programs are used as illustration in the text.

Microprocessors and Microcomputers, Hardware and Software, by R. J. Tocci and L. P. Laskowski, 404 pages, hardback. Prentice-Hall, £15.70.
 Micros introduced in a practical manner. First section is on basics of logic and number

systems; second section deals with computer architecture; last part is on programming in machine code and assembly language.

PROPAGATION

Adaptive Array Principles, by J. E. Hudson. 253 pages, hardback. Peter Peregrinus, £13.00.
 The design of adaptive aerial arrays, which automatically present nulls in their polar diagrams to sources of noise. Such aerials are used in radar, sonar, communications and radio monitoring.

Wave Propagation Theory, by J. R. Wait. 348 pages, paperback. Pergamon Press, £22.50.
 Primarily on electromagnetic wave propagation in, on or about the earth, but methods described can also be applied to acoustic waveguides.

Aperture Antennas and Diffraction Theory, by E. V. Jull. 173 pages, hardback. Peter Peregrinus, £27.00.
 The analysis of radiating apertures, using two complementary techniques. One is the Fourier relation between aperture field and far-field pattern, giving results for the forward radiation. Second method is based on diffraction at the aperture edge, and can be used for rear and side radiation.

Microstrip Antenna Theory and Design, by J. R. James, P. S. Hall and C. Wood. 290 pages, hardback. Peter Peregrinus, £31.00.
 Design and fabrication of flat plate, 'printed' microwave aerials, with a resumé of recent advances and a chapter on trends and possible developments in the future. An appendix compares microstrip materials.

VIDEO

Video Handbook, by R. V. Van Wezel, edited by G. J. King. 403 pages, hardback. Newnes Technical Books, £19.90.
 Television, video recording on tape and disc, audio and tv production, measurements and descriptions of some typical commercial equipment. Written for the video amateur and technician, using a practical approach. Includes information on building a monochrome tv camera.

Home Video Yearbook 1982. 323 pages, paperback. Link House, £7.50.
 In three parts. Firstly, hardware concerned with television reception and video recording, prices and suppliers; secondly short descriptions of commercially available video tapes; thirdly, lists of addresses of manufacturers and tape suppliers.

DISC DRIVES

Read/write head assemblies involve aerodynamic, mechanical and electro-mechanical techniques and are the most critical aspect of disc-drive design. But an equally important aspect of the system is how serial data is stored and recalled on a magnetic medium moving at high speed using a single low-mass head. These subjects form this chapter.

by J. R. Watkinson

As previously stated, hard discs have a thin coating of magnetizable material and rotate at high speeds. Readers familiar with other magnetic recording systems will realize that ideally, the read/write head will be forced against, or at least touch, the recording medium. But because of the speed at which the disc rotates and the fragility of the medium, a gap is essential. Therefore, the head is designed to float, or 'fly', on the layer of air rotating with the disc. Consequently, the head is of low mass, so the gap between head and disc can be kept constant over the whole surface of the disc and a small degree of warping can be compensated for. Figure 1 outlines the read/write head's structure.

The magnetic head is carried by the slipper and consists of a permeable core with a coil wound round it. A paramagnetic barrier on the head core forces the flux out of the head onto the medium. Reluctance of the magnetic circuit depends mainly on the air gap between the head and the disc so the write flux is a function of the flying height. The air gap limits the recording wavelength to about ten times that of the flying height.

Slippers. Current 'state-of-the-art' slippers fly at less than 20 micro-inches (0.5 micron) above the disc. It is obvious that the lower the flying height, the more efficient reading and writing becomes, but what isn't perhaps so obvious is that the major design problem is making the slipper fly low enough. Lift rises rapidly as the separation reduces so to get the head closer to the disc, some of the lift has to be dumped. Early slippers had two small bleed holes, as shown in Fig. 2(a) to dump lift. These slippers had a flying height of around 100 micro-inches. Figure 2(b) shows a second generation slipper, with a large longitudinal bleed groove, designed for flying heights of about 50 micro-inches. The third example, Fig. 2(c), is designed for use below 20 micro-inches and has substantial bleed grooves and vestigial working surfaces. Although the surface of this slipper appears flat to the naked eye, it is actually formed to a high degree of accuracy in a compound curve.

Suspension. The slipper is mounted at the end of a rigid cantilever sprung toward the medium. The force with which the head is pushed toward the disc by the spring is equal to the lift at the flying height for which the head is designed. Because of the spring, the head may rise and fall over small warps in the disc; it would be virtually impossible to manufacture discs flat enough to allow this feature to be

dispensed with. As the slipper negotiates a warp it will pitch and roll, in addition to rising and falling, but it must be prevented from yawing. Downthrust is applied to the slipper at its aerodynamic centre by a spherical thrust button and the required degrees of freedom are provided by a flexural gimbal.

The mass of the head/cantilever and the spring compliance have a natural reso-

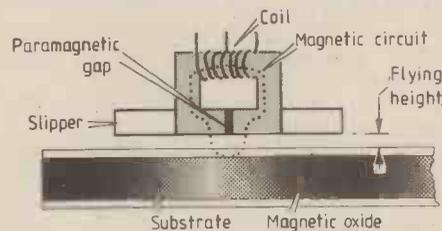


Fig. 1. An outline of the read/write head in relation to the disc. The slipper carries the head and is aerodynamically designed so that it flies on the air rotating with the disc.

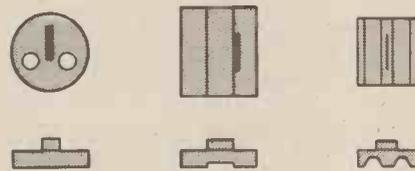


Fig. 2. Three generations of slipper design. The first generation, shown at (a), had two bleed holes to reduce lift and flew at around 100 micro-inches above the disc. A subsequent design, (b), had a longitudinal bleed groove and flew at around 50 micro-inches. This was superseded by the current head, (c), with substantial bleed grooves for flying heights of less than 20 micro-inches. The head shown in (c) has a compound curve on its working surface which aids aerodynamics but is invisible to the naked eye.

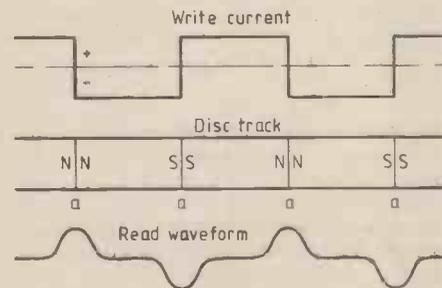


Fig. 3. In digital recording the polarity of the medium, either N-S or S-N, is controlled by the direction of the write current. Flux reversal, at points marked a, are referred to as transitions and determine the read waveform.

nance which must be set away from expected warp frequencies. Some cantilevers are fitted with synthetic-rubber dampers to control unwanted resonances.

Other essentials of the cantilever are the head separating ramp, which lifts the head clear of the disc as the positioner retracts, and some receptacle for an adjusting tool to align all of the heads to the same distance from the spindle at a given cylinder.

Handling and setting head assemblies requires care and skill; in some cases skin acid from a fingerprint is sufficient to etch the slipper surface and destroy its aerodynamic contour.

Encoding techniques

With the exception of some non-interchangeable disc drives, only one head is active at any one time. A production tolerance exists between the actual lateral position of the head gap and the ideal, and this dimension may be several wavelengths at the densities used. As a result it is not generally possible to use parallel encoding in disc drives. This constraint largely defines the encoding techniques used.

As in all modern digital recording, the medium has only two states of magnetization, N-S and S-N. Devices have been made using the unmagnetized state, but these must be considered obsolete. The write process consists of supplying sufficient current to almost saturate the medium first in one direction, then the other. No erase process is necessary, as writing to saturation will erase a previous recording. Some heads do, however, have erase poles, the use of which will be detailed.

The output voltage from a read head is proportional to the rate of change of flux, hence an output pulse will only be obtained at the point where the write current changes direction, i.e. at a transition. Figure 3 shows that the pulses alternate in polarity. The pulse amplitude is a function of the cylinder address, as the relative speed of the outer cylinders is higher.

Data to be written enters the write circuitry as serial binary with a separate clock. Encoding consists of merging these two signals into one channel in such a way that they can be subsequently separated. Perhaps the simplest form of encoding is to reverse the write current every time the data is a binary one. It can be seen from Fig. 4(a) that this approach is of no use in a single channel, as when successive zeros occur, it is not possible to reconstitute the clock.

An earlier head assembly. Two bleed holes in the slipper reduce lift caused by air rotating with the disc.

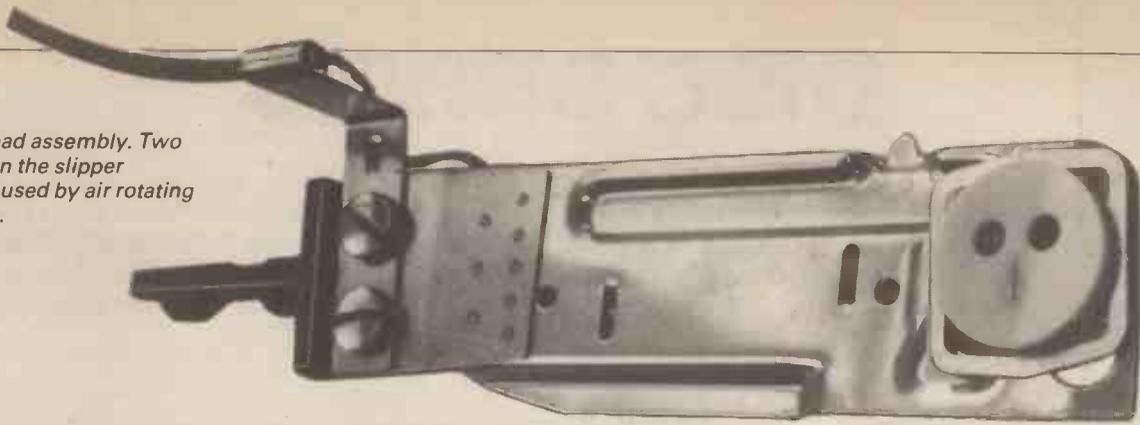


Figure 4 also introduces the concept of the 'bit cell', i.e. the time taken to record one bit. In a simple encoding system, there must be at least one transition per bit cell to carry the clock. Figure 4(b) shows a popular encoding technique, where each bit cell begins with a clock transition, and may or may not contain a further transition, depending on whether the data bit is a one or a zero. As the presence of the second transition doubles the recording frequency, the technique is known variously as f.m. or double-frequency recording. Data separation can be very simple, provided the signal-to-noise ratio is adequately high. The signal-to-noise ratio is determined not only by intrinsic medium noise and the electromagnetic environment, but also by the accuracy of the positioner. Consider the example in Fig. 5(a). Originally, data is written along path A, but positioner inaccuracy means that new data is being written along path B. Subsequently a read may take place along path C, where it will be seen that the read signal is degraded by the previous recording. The solution to this problem is to incorporate two erase gaps in the head, which erase a small area either side of the new data after writing. In Fig. 5(b) it can be seen that this process protects the data with a margin of unidirectionally magnetized oxide. The process is called 'tunnel erase' or 'side trim', and is generally employed on drives with relatively simple positioners. Such devices usually have low recording densities and accordingly a generous flying height, giving them the advantage that they can be used reliably in environments that would normally be considered unsuitable.

F.m. is easy to decode, but it is also fairly extravagant with transitions. Any encoding method in which the number of transitions per data bit can be reduced has to be an improvement, because for a given flying height, and hence a given minimum wavelength, a greater data density is possible.

In the next generation of read electronics, it is possible to relax constraints on the clock information through phase-locked-loop techniques. With this approach, it is acceptable for a bit cell to contain either clock information or data but both are not necessary. The read clock comes from a p.l.o. which continues in the absence of a transition at clock time, and which corrects its own frequency by continuously comparing its own phase with that of data

or clock transitions. In Fig. 4(c) it can be seen that the write current is reversed at the bit-cell centre for a one, and that the problem of successive zeros is handled by reversing the write current at the bit-cell boundary. It is interesting to compare the number of transitions required with the example of Fig. 4(b). On reading the data,

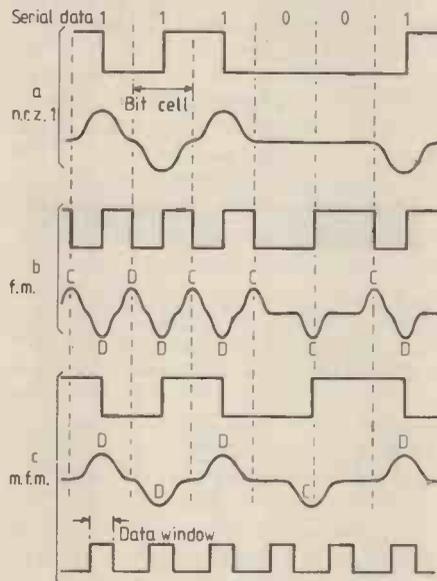


Fig. 4. Three data-recording methods compared. At (a), n.r.z.1 (modified non-return-to-zero) information is of little use on single-track recording apparatus as clock information cannot be carried. In 'f.m.' recording, (b), a clock transition is always present at the bit-cell boundary. The presence of a data '1' causes an extra transition at the bit-cell centre. In m.f.m. recording, shown at (c), a data '1' causes a transition at the bit-cell centre but the only other transitions are at the bit-cell boundaries between successive zeros. Both types of transition are used to synchronize a p.l.i. which opens a 'data window' at the bit-cell centre through which only data '1' pulses are read.

the p.l.o. can be used to open a 'time window' at the centre of the bit cell, so that only transitions corresponding to a binary one can pass through. Obviously, the system only works if the p.l.i. is synchronized, so a series of zeros, or preamble, is used before each block to allow the loop to lock. A unique synchronizing pattern delineates where actual data begins. This phase-locked data-recovery technique is used with modified-frequency modulation encoding (or Miller encoding) and allows the arrival time of read pulses to be predicted, and therefore noise pulses to be rejected. This means that a smaller s-to-n ratio can be tolerated than with f.m. encoding, allowing tunnel erase to be dispensed with. In any case, drives employing the m.f.m. technique are likely to have more accurate positioners.

Where f.m. requires signal-to-noise ratio, m.f.m. requires minimum phase errors, if the phase-locked data recovery is not to be upset. In Fig. 6, a head is depicted reading closely packed transitions. Owing to the airgap between the head and the medium, pulses generated tend to run into one another such that the waveform peak positions do not correspond to the actual position of the transitions. The phenomenon is referred to as peak-shift distortion, and is overcome by introducing opposing timing changes during the write process. This technique, precompensa-

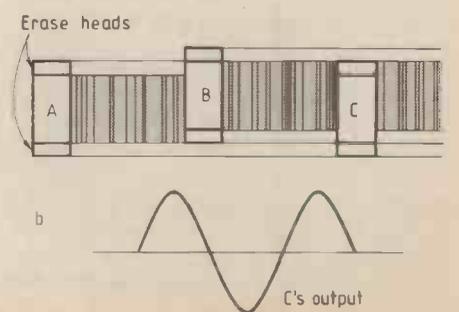
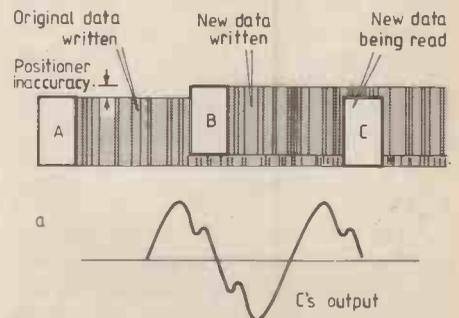


Fig. 5. In (a), track B has been written over track A, but through wide tolerances on the positioner repeatability, some of the original data remains at the edge of path B. If the new data is read while the head travels the same path it did when the original data was written, remaining original data will be read together with the new data, hence the signal-to-noise ratio will be degraded. At (b), the problem is solved by including two erase heads, one at either side of the write head, so that wherever data is written, any original data at either side of the track will be erased.

tion, artificially advances transitions subject to delay on reading, and delays advanced transitions by taking a running sample of (usually) four data bits, and decoding the patterns to generate different clock times in a tapped delay line. M.f.m. requires a running sample, so the two processes are sometimes combined in one circuit.

Recently, a different approach to high density recording has been developed. Central to this approach is that transitions are not permitted at successive active edges of the write clock. Figure 7(a) shows that the four combinations of any two data bits may be expressed as three-bit codes which do not contain successive 'ones'. There are, however, four combinations of adjacent pairs of bits to violate the rule, Fig. 7(b). In these cases, the six bits are substituted by alternative bit patterns which must follow certain conditions; firstly, that the substitution contains no adjacent ones, secondly that the substitution ends in a zero so that no subsequent data can violate the rule, and thirdly the position of the ones is chosen to generate transitions at sequential integer multiples of the write-clock period. Fig. 7(c) shows that the highest recorded density results from a data stream of 0011's, and that this requires only six transitions for eight data bits. At maximum density, m.f.m. requires one transition per bit, so the relative efficiency is 8/6 or 33% greater. Fig. 7(c) also shows that much of the time the recorded density is below the maximum, and that seven even steps exist in the periods between any two transitions. This evenness allows effective phase-locked noise rejection to be employed, as the arrival time of readback pulses can be accurately predicted. In addition, precompensation is only required when changing to and from the highest density, as at all lower densities the transitions are far enough apart to make peak-shift distortion insignificant. This recording technique is known as 2/3 (pronounced "two three") for obvious reasons. It is difficult to imagine a method

which would achieve a significant improvement in efficiency over it. Encoding is performed by a p.r.o.m. which takes in a running sample of data in the same way as m.f.m. Similarly, reading requires phase-locked circuitry, with a further p.r.o.m. containing the reverse truth table to the encoding p.r.o.m.

Circuits

The same head is used for both reading and writing, and as stated, usually only one head is active at one time. The circuits involved in reading, writing and head selection come together at the read/write matrix where the flexible head cables plug in. It can be seen from Fig. 8 that the centre-tapped heads are isolated by connecting the centre tap to a negative voltage, which reverse-biases the matrix diodes. The centre tap of the selected head is made positive. When reading, a small current flows through both halves of the head coil, as the diodes are forward biased. Opposing currents in the head cancel, but read signals resulting from flux transitions on the disc can pass through the forward-biased diodes to become differential waveforms on the matrix bus. During a write, the current from the write generator passes alternately through the two halves of the head coil. Further isolation is necessary to prevent write-current voltages destroying the read amplifier inputs.

Write-current programming. The flying height changes as a function of relative velocity which is governed by the track radius. It is possible to program the write current from the current cylinder-address register such that the write flux remains essentially constant, despite changes in flying height. The number of write-current steps is usually between two and eight across the working surface of the disc, although some drives dispense with write current programming altogether. In Fig. 9, the write current is generated by holding the base of a transistor at a temperature-compensated reference voltage, and by selecting different emitter resistors

with transistor switches. As the current source is usually at about -40V, the switches are fed from the drive logic through level shifters. The write current is directed through the head by a pair of transistors in series with the current generator, which are driven in a complementary fashion by a bistable. The purpose of write

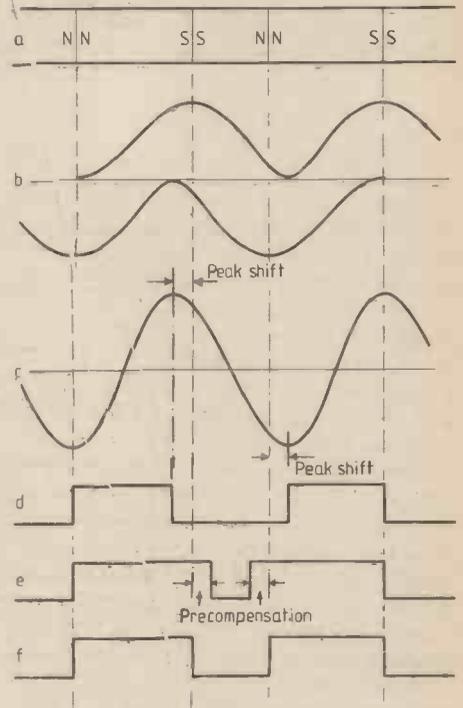


Fig. 6. Timing diagram showing peak distortion and precompensation. (a) shows the flux pattern of an ideal m.f.m. data track, and (b) shows individual read pulses from each transition, which are spread out because the head is not in contact with the medium. Peaks of the closely packed transitions are moved apart as shown in the summation of the waveforms of (b) at (c). Phase errors in the binary signal from the peak detector are shown at (d). To compensate for these errors, the write waveform is as shown in (e) and the adjusted peak detector output is shown in (f).

A modern head assembly. This type of head is designed to fly at around 50 micro-inches above the disc.

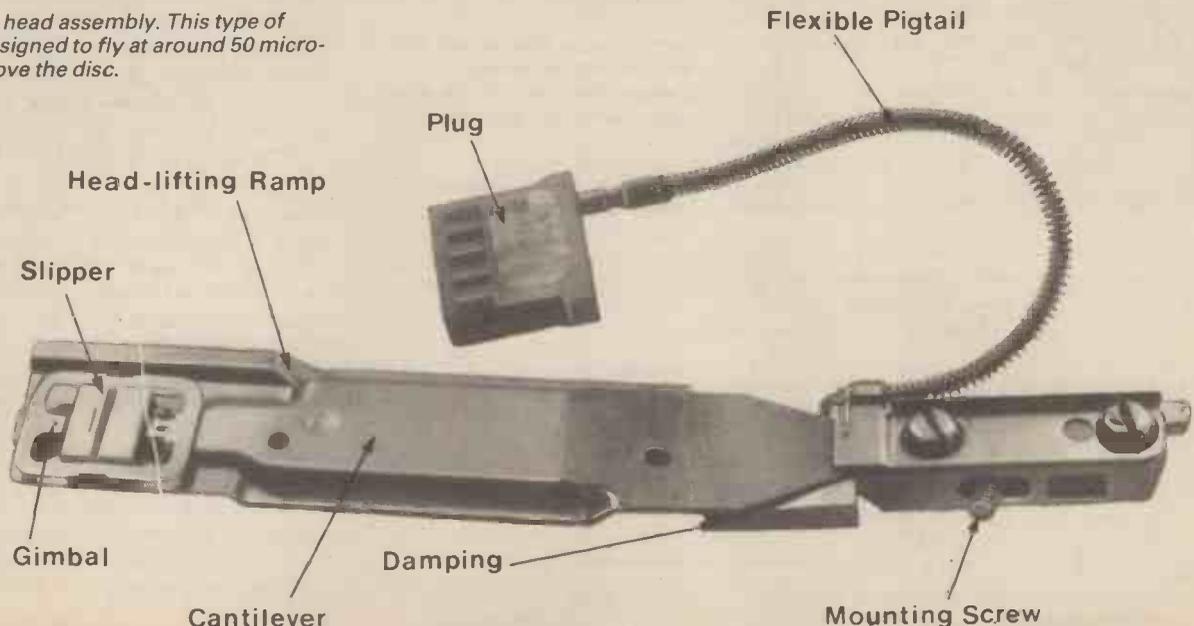


Fig. 7 (a). Two bits can be expressed as three code bits without successive transitions. In (b), adjacent pairs can break the encoding rule and in these cases, substitutions are made. Write current waveforms for seven different data streams using 2/3 encoding are shown at (c). The time steps between transitions are uniform, allowing phase-locked data recovery in the presence of noise. A maximum of six transitions are required for eight data bits; when compared with m.f.m. encoding, this gives a saving of 33%.

(a)

Data	Code
00	101
01	100
10	001
11	010

(b)

Data	Illegal code	Substitution
0000	101101	101000
0001	101100	100000
1000	001101	001000
1001	001100	010000

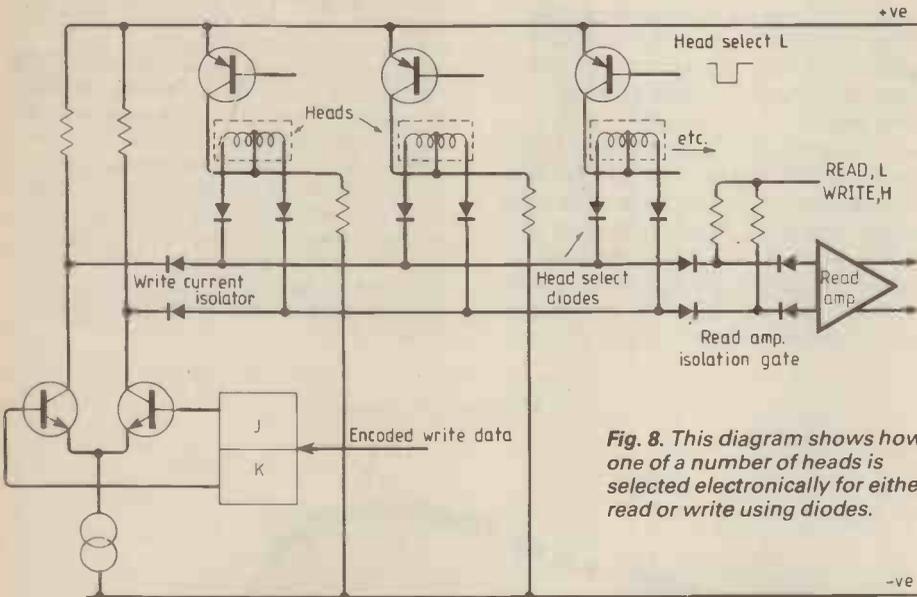
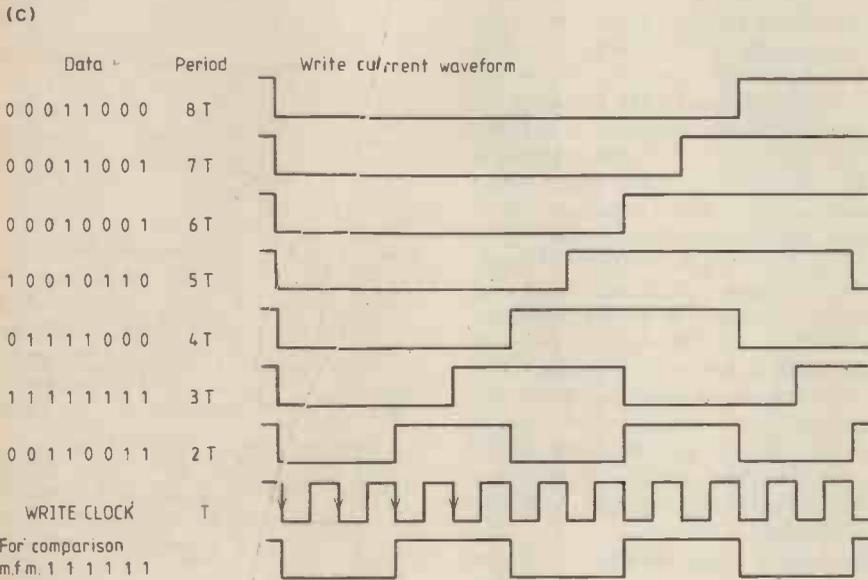


Fig. 8. This diagram shows how one of a number of heads is selected electronically for either read or write using diodes.

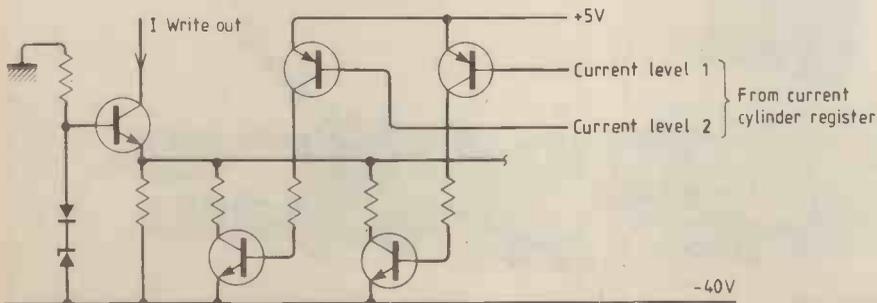


Fig. 9. A programmable write-current generator. Write current is generated by holding the base of a transistor at a temperature-compensated reference voltage, and by selecting different emitter resistors using transistor switches.

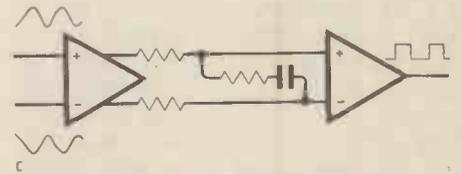
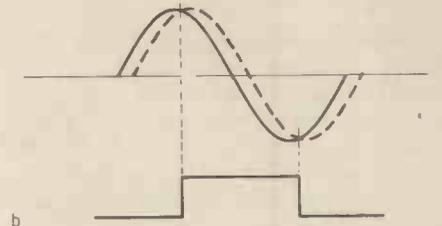
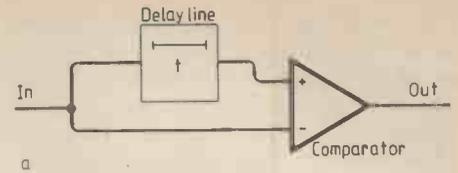


Fig. 10 (a). A simplified delay-line peak detector, and associated waveforms (b). A differential phase-lead peak detector is shown at (c).

encoding is to decide at what time to clock the bistable so that a transition is written by the current reversal.

Reading. When not actually writing, the write-current generator is turned off and the write-isolation diodes are reverse biased. The read isolation gate is enabled, allowing the differential read signal into the read linear amplifier. This amplifier raises the amplitude of the read signal to a constant level suitable for data recovery, and filters out unwanted signals. To this end the linear amplifier often contains both bandpass filters and an a.g.c. loop. In some cases, the linear amplifier's input and the a.g.c. capacitor are shorted during the address mark to stabilize the gain in the shortest possible time after entering a block. The address mark is a short section of the track preceding a data block and contains no transitions. A.g.c. squelch is released as the block is entered, and the linear-amplifier gain reduces from maximum using the fast attack slope of the forward-biased signal rectifier.

The constant-amplitude read signal now passes to the peak detector, as the position of the signal peaks corresponds to the position of the transitions on the disc. In Fig. 10(a) an analogue waveform is compared with a delayed version of itself. The comparator changes state at the signal peak. A differential version of this type of peak detector is shown in Fig. 10(c). The principle holds equally well if one signal is phase advanced, and thus the delay is sometimes substituted by the RC network shown.

The detected signal is fed to an appropriate data separator, which splits the signal into data and clock information to pass to the deserializer, which recreates data words.

To be continued

16-CHANNEL DATA ACQUISITION SYSTEM

A 4½-digit, 16-channel data acquisition system (d.a.s.) is described which functions as a talker-listener on the IEEE-488 bus (GPIB). It uses a 4½/5½-digit a-to-d subsystem, AD7555, with $\pm 1.9999V$ full scale, as an easy interface with the Fairchild 96LS488 GPIB circuit.

Figure 1 shows a block diagram of the GPIB 16-channel data acquisition system. The 96LS488 connects directly to the IEEE bus and controls all the other sections. (For clarity, a number of the control signals have been omitted.) A set of eight transceivers determines the flow of information (talking or listening) and the 'listen decode' circuitry sends the appropriate address to the 16-channel multiplexer. On selection of a channel, a start conversion signal is sent to the AD7555 a-to-d converter.

When conversion is complete, a service request is transmitted to the 96LS488, which in turn interrupts the IEEE bus: the bus can then interrogate the device for status or data information. Status information includes the last channel selected and the conversion status, while data information consists of a 4½-digit b.c.d.-encoded representation of the analogue voltage.

The IEEE bus in brief

A full description and specification of the GPIB system is published in the IEEE document "IEEE Standard Interface for Programmable Instrumentation", IEE Std 488(1978), which should be referred to for a fuller explanation.

GPIB communication lines consist of eight data lines, three hand-shake lines, five control lines and eight ground lines, as shown in Fig. 2 (the IEEE connector). Data lines (D1-D8) contain the bidirectional data or information and are true low signals.

Handshakes. NRFD, DAV and NDAC are the three bidirectional handshake signals. DAV (Data Valid) is pulled low by a talker when the data has been placed on the bus, which tells the listener that the data is valid. NRFD (Not ready for data) is brought high (or released) by each instrument on the bus: when all the instruments have released it, it acts as an indication to the talker that a data transfer can begin. NDAC (Not Data accepted) is controlled by the device receiving the data, a low indicating that the data has not been captured and a high that this has been done. A simplified data transfer sequence is shown in Fig. 3.

A timing sequence starts when the listener brings NRFD high (1), saying it is ready to receive the data. The talker places the data on the bus (2), allows it to settle and brings DAV low (3), telling the listener that the data is valid. The listener brings NRFD low (4), indicating that it is not ready for another data transfer until

by Pat Hickey

this transfer is completed. When the data has been processed, the listener brings NDAC high (5), saying that it has received the data. The listener responds by taking DAV high (6) (data is no longer valid) and removing the data from the bus (7). The listener brings NDAC low (8), acknowledging this, and NRFD high (9), indicating that it is ready for the next data byte. The timing of this sequence is not discussed here, since the 96LS488 IEEE-interface circuit takes complete control of the procedure.

Control. The five control lines are ATN, IFC, REN, SRQ, and EOI. The ATN (Attention) is asserted only by the controller and, when low, indicates that information on the line is address or control information: it is high when data is being transferred. The IFC (Interface Clear) line is asserted low by the controller to reset all GPIB devices.

REN (Remote Enable) allows local (i.e. front panel) control of devices if it is allowed to become high. When low it ensures that the controller is in command. SRQ (Service Request) is forced low by a talker/listener when it wishes to indicate to

the controller that it needs service. EOI (End or Identify) can be pulled low by a talker to signify the last byte in a multi-byte transfer.

All the aforementioned signals are taken care of by the 96LS488.


96LS488 GPIB circuit

Figure 4 shows a block diagram for the 96LS488, and the following description should be referred both to that and Fig. 7 (full circuit diagram). CP is a 10MHz clock which controls all internal timing, and can be generated using a 150Ω resistor and 150pF capacitor connected to an internal Schmitt trigger.

TXST (Transmit Status) and TXRDY (Transmit Ready) signals are used in transferring data from the AD7555 a-to-d converter to the 96LS488, as shown in Fig. 5. When the d.a.s. is requested to transfer information to the IEEE bus controller, the 96LS488 checks that TXRDY is high (meaning a byte is waiting). If it is high, the 96LS488 will read the data and bring TXST high (1), indicating that it has the information. TXRDY is then brought low (2), acknowledging this fact and TXST is brought low (3) again. When the next byte is ready (4), the AD7555 brings TXRDY high (5) and the sequence is repeated.

RXST (Receive Status) and RXRDY

Analog Devices, Limerick, Ireland

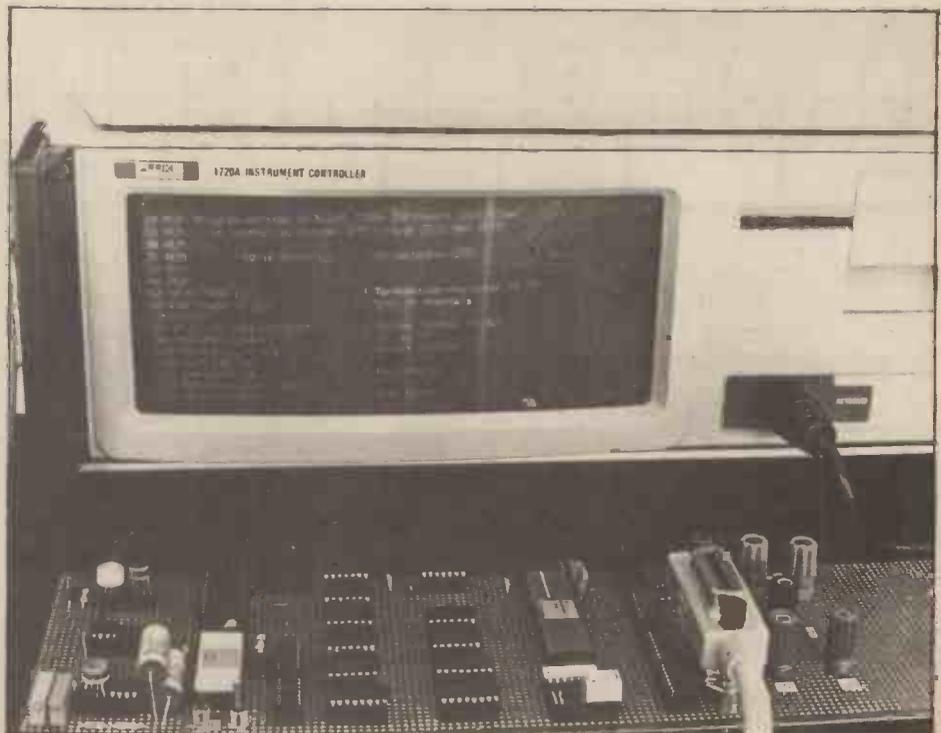

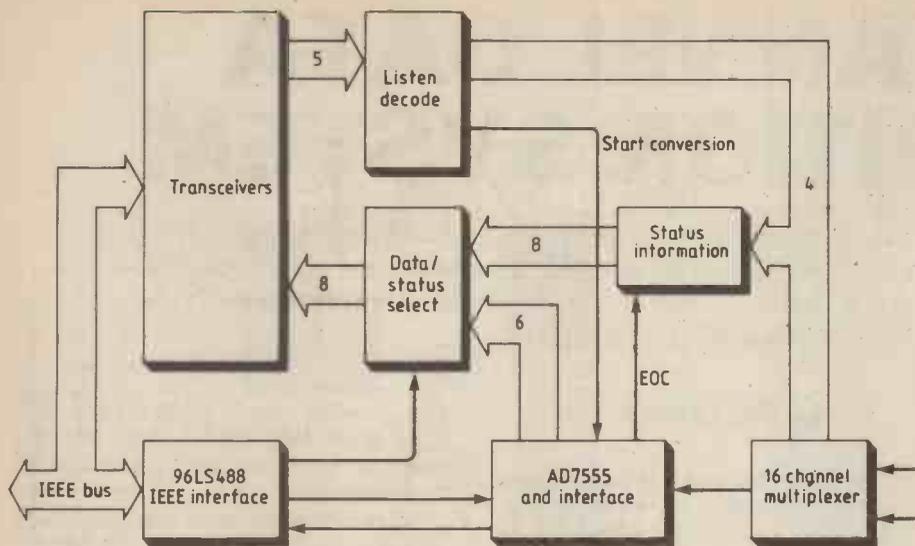


Fig. 1. Block diagram of complete system. 96LS488 interfaces and controls rest of unit.

(Receive Ready) are used as seen in Fig. 6 for transferring data from the 96LS488 to the 16-channel d.a.s. When valid data has been placed on the bus (1), RXST is taken high (2), indicating that the data is valid. When the data has been accepted, RXRDY is taken low (3), indicating that the data has been accepted, RXST is taken low (4), acknowledging this fact, and the data becomes non-valid (5). RXRDY is brought high (5), signalling that it is ready for the next byte of information. In Fig. 7, RXST is inverted and connected to RXRDY, in which case data is transferred at a data rate determined by the bus handshake.

The Drive Bus Output (DRB) signal is low when data is being transferred from the AD7555 a-to-d converter to the IEEE bus, and high when information is being

Fig. 4. Functional block diagram of 96LS488.

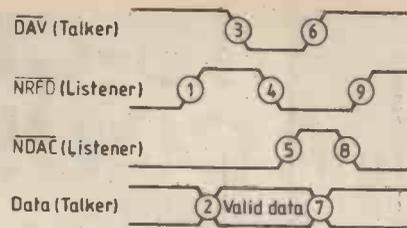
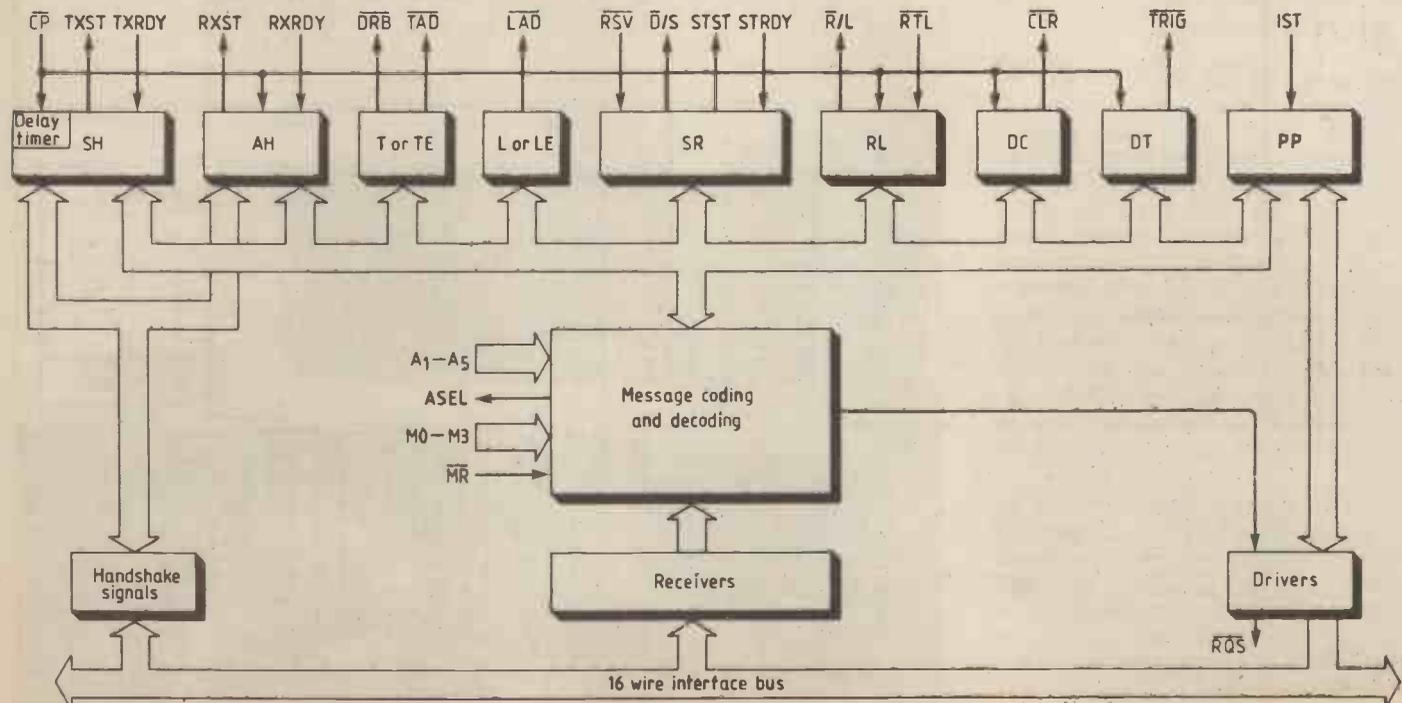


Fig. 3. Simplified data transfer sequence.

interrupt. This occurs when a conversion is completed.

D/S (Data/Status) is held low when data is being transferred to the IEEE bus, or high if status information is being transferred during a serial poll. In this application, it is used to select either data or status information via a data selector (2x74C157).

The STST (Status Status) and STRDY (Status Ready) signals operate similar to the TXST and TXRDY signals when sending status information during a serial poll. STRDY can be formed from an inversion of STST.

RTL (Return to Local Input) is tied high in this application, since the device is operating only in remote control.

CLR issues a negative pulse when the device receives a Device Clear command. This will reset all functions within the device.

TRIG (Trigger output) issues a negative pulse when the device receives a DT (Device Trigger) command. It is not used in this application. The IST (Instrument Status Input) is used in parallel poll enable.

For more information on the above signals see the Fairchild 96LS488 data sheet.

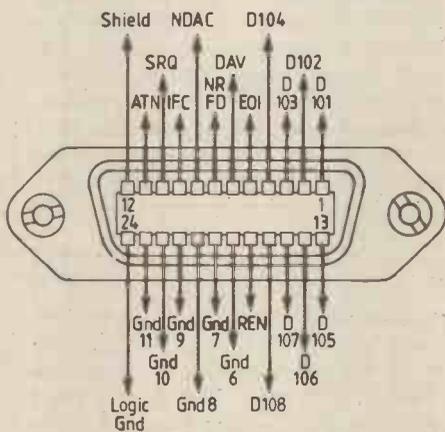


Fig. 2. GPIB communication lines shown in relevant positions on IEEE connector.

sent to the data acquisition system. In Fig. 6, the signal is used to enable (or disable) a set of transceivers.

TAD (Talk-Addressed) and LAD (Listen-Addressed) are active low when the device is addressed to talk or listen.

RSV (Request Service) is brought low by the AD7555 to initiate a service request

Data acquisition system

Figure 7 shows the complete circuit diagram of the data acquisition system. A brief review of each i.c. should help to understand its operation before the more complex timing of the system is discussed.

Circuits IC_{1,2} are quad interface

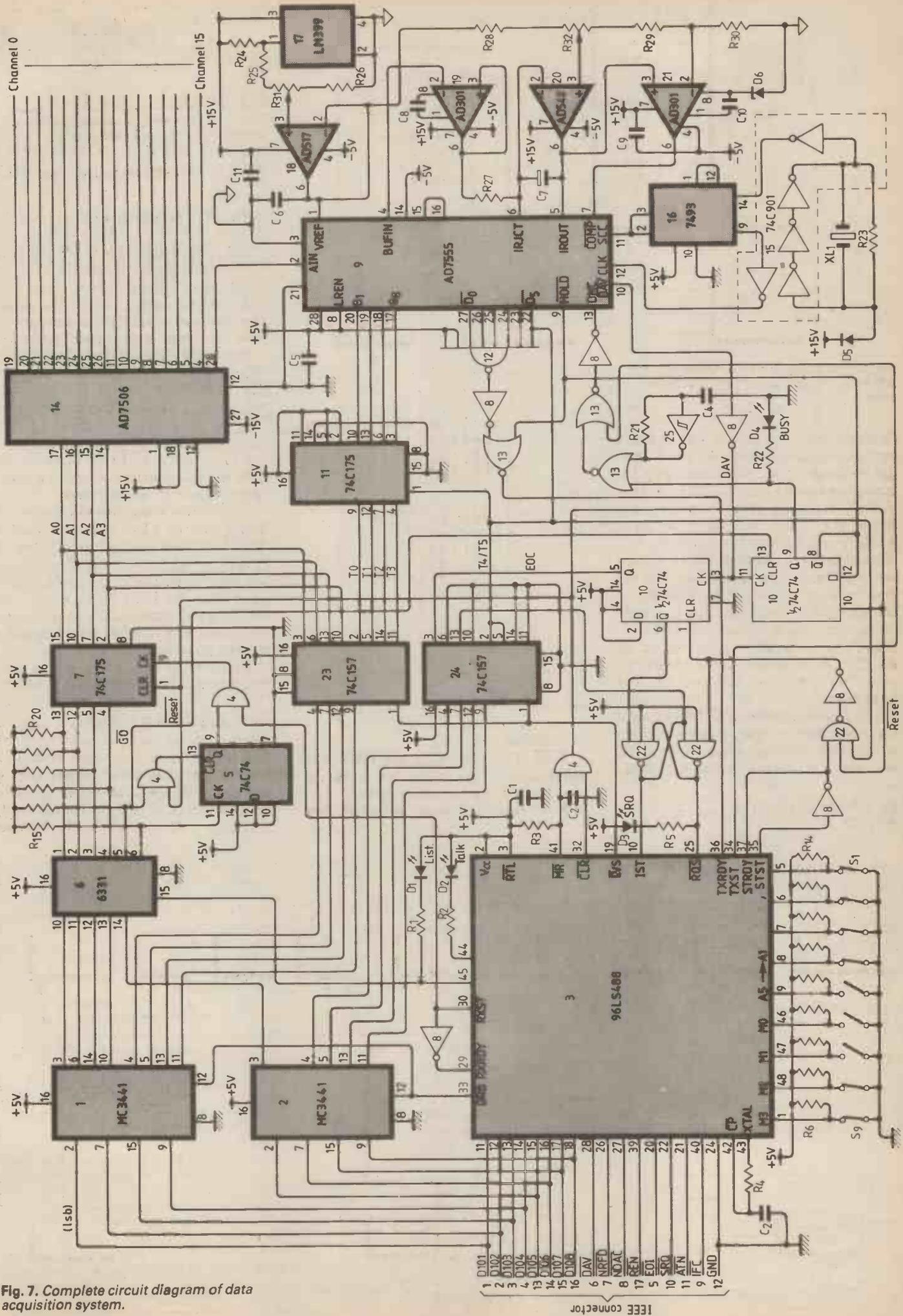


Fig. 7. Complete circuit diagram of data acquisition system.

IEEE connector

Table 1. Contents of IC₆ r.o.m. for decoding ASCII information to binary.

R.o.m. inputs (addresses)					R.o.m. outputs (data)						
A 4	A 3	A 2	A 1	A 0	06	05	04	03	02	01	
0	0	0	0	0	1	1	1	1	1	1	
0	0	0	0	1	"A"	1	1	1	0	1	0
0	0	0	1	0	"B"	1	1	1	0	1	0
0	0	0	1	1	"C"	1	1	1	1	0	0
0	0	1	0	0	"D"	1	1	1	1	0	1
0	0	1	0	1	"E"	1	1	1	1	1	0
0	0	1	1	0	"F"	1	1	1	1	1	1
0	0	1	1	1		1	1	1	1	1	1
0	1	0	0	0		1	1	1	1	1	1
0	1	0	0	1		1	1	1	1	1	1
0	1	0	1	0	"*"	0	1	1	1	1	1
0	1	0	1	1		1	1	1	1	1	1
0	1	1	0	0		1	1	1	1	1	1
0	1	1	0	1	CR	1	0	1	1	1	1
0	1	1	1	0		1	1	1	1	1	1
0	1	1	1	1		1	1	1	1	1	1
1	0	0	0	0	"0"	1	1	0	0	0	0
1	0	0	0	1	"1"	1	1	0	0	0	1
1	0	0	1	0	"2"	1	1	0	0	1	0
1	0	0	1	1	"3"	1	1	0	0	1	1
1	0	1	0	0	"4"	1	1	0	1	0	0
1	0	1	0	1	"5"	1	1	0	1	0	1
1	0	1	1	0	"6"	1	1	0	1	1	0
1	0	1	1	1	"7"	1	1	0	1	1	1
1	1	0	0	0	"8"	1	1	1	0	0	0
1	1	0	0	1	"9"	1	1	1	0	0	1
1	1	0	1	0		1	1	1	1	1	1
1	1	0	1	1		1	1	1	1	1	1
1	1	1	0	0		1	1	1	1	1	1
1	1	1	0	1		1	1	1	1	1	1
1	1	1	1	0		1	1	1	1	1	1
1	1	1	1	1		1	1	1	1	1	1

transceivers (MC3441) and are designed to meet the IEEE standard 488-1975. The data direction is controlled by the DRB output of the 96LS488 (IC₃): When it is low, data is transferred to the bus, and transferred from the bus when DRB is high. Switches S₁-S₅ are used to select the address of the device. As an example:- For an address of 16, S₅ is open, while S₄, S₃, S₂ and S₁ are closed. (Address is 10000 = 16). Switches S₆-S₉ are used to select the operating mode of the 96LS488 (the Fairchild data sheet gives more information on this). For a talker/listener on low speed, M₀ and M₁ are high, and M₂ and M₃ are low (ie, S₆ and S₇ are open, while S₈ and S₉ are closed).

Since all information is transmitted in parallel ASCII code, it is necessary to decode this to binary. The 6331 (IC₆) is a 32x8 bit r.o.m. which is used for this purpose, whose contents are outlined in Table 1. The address latch, IC₇ (74C175), holds the address of the selected channel, its output being connected to the input of IC₁₄ (AD7506), a 16 channel multiplexer,

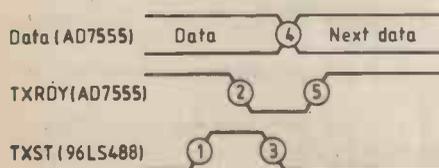


Fig. 5. Simplified talking sequence.

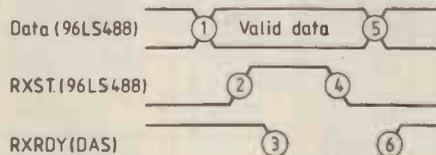


Fig. 6. Simplified listening sequence.

which in turn selects the appropriate analogue signal to the a-to-d converter subsystem (AD7555) IC₉. On completion of a conversion, the b.c.d. data is held in internal latches, and can be accessed by control of the DMC pin. The IEEE transmit handshake signals are used to access this information during a readback cycle. A data selector IC₁₁ (756157) send 4½ digits and a carriage return to the 96LS488: When D₅ is high, b.c.d. data from the a-to-d converter is selected, and when D₅ is low a CR code is selected.

The hex. c.m.o.s.-t.t.l. inverter (IC₁₅) generates the 4.096 MHz clock with the crystal, whilst IC₁₆ (7493), a 4-bit binary counter, divides this by four, producing a 1.024 MHz clock for the AD7555.

The two multiplexer/selectors (IC_{23,24}) are used to transfer either data or status information to the 96LS488. When D/S is low, data information is selected (T₀-T₅), and when high the status byte is sent.

The concluding article will continue this circuit description and include a program for scanning 16 channels. □

EVENTS

23/24/25th March

Electro-optics/Laser International '82 UK, at Metropole Convention Centre, Brighton. Details from: Cahners Exposition Group, Cavridy House, Ladymead, Guildford, Surrey GU1 1BZ.

25th March

Computational Techniques in Image Processing, at Queen Elizabeth College, London. Details from: The Meetings Officer, The Institute of Physics, 47 Belgrave Square, London, SW1X 8QX.

30th March/1st April

ETM '82 and Sensors & Systems '82 (Electronic testing and measurement) at Wythenshawe Forum, Manchester. Details from: Trident International Exhibitions Ltd, 21 Plymouth Road, Tavistock, Devon PL9 8AU.

30th March/1st April

CAD '82, (Computer-aided design conference and exhibition) at Brighton Metropole, Sussex. Details from: IPC Exhibitions Ltd, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ.

4th-7th April

National Association of Broadcasters, Exhibition, at Las Vegas, Nevada USA.

6th April

Current Research in Magnetism, at the Institute of Physics, London. Details from: The Meetings Officer, The Institute of Physics, 47 Belgrave Square, London SW1X 8QX.

12th-15th April

Electrostatics Conference, at St Catherine's College, Oxford. Details from: The Meetings Organiser, Institute of Physics.

13th-16th April

Basic Electronics for Teachers, at University of Salford. Details from: The Administrative Assistance (Short Courses) Room 110, Registrar's Department, University of Salford, Salford M5 4WT.

20th April

Satellite Development in Broadcasting: M. W. Harman, at Room SG27, University of Aston, Gosta Green, Birmingham at 6.30pm. Details from: The IETTE, 2 Savoy Hill, London WC2R 0BS.

20th-22nd April

International Conference on Video and Data Recording (I.E.R.E.) University of Southampton, Southampton. Details from: Conference Registrar, IERE, 99 Gower Street, London WC1E 6AZ.

20th-22nd April

All Electronics Show, at the Barbican Exhibition Centre, London.

20th-23rd April

Communications '82, IEE Conference and Exhibition at the National Exhibition Centre, Birmingham. Details from: IEE Conference Department, Savoy Hill, London WC2R 0BL.

22nd April

Microprocessor in Building Services: M. W. Harman, at University of Strathclyde, Glasgow at 6.30pm. Details from: IEETE, 2 Savoy Hill, London WC2R 0BS.

23rd-25th April

The Computer Fair, at Earls Court. (Sponsored by *Practical Computing and Your Computer*) Details from: Exhibition Manager, IPC Exhibitions Ltd, Surrey House, 1 Throwley Way, Sutton, Surrey.

28th April

Propulsion Research - Impact on Fuel/Emergency Conservation, at Hawthorns Hotel, Woodland Road, Bristol at 7.30pm. Details from: IEETE, 2 Savoy Hill, London WC2R 0BS.

SYMMETRICAL-OUTPUT DIVIDERS

(Expanding on February's article, the author first shows how further hexadecades may be added to the previously described binary-programmable counter. A basic b.c.d.-programmable counter follows and to conclude, details of how to add further decades. These circuits are designed to accept and provide equal mark-to-space ratio digital signals, and are programmable in integer steps. As frequency-dependent components are not used, the speed of each circuit is only limited by the speeds of the logic devices used.

For dividing in the range $16 \leq N \leq 256$, whether or not N is a prime number is important. If N is not prime then $N = N_1 N_2$ and the divider can be made using two programmable divide-by-1-to-16 circuits described in the previous article. These may be connected either asynchronously or synchronously, the latter method being the fastest. To divide synchronously it is necessary to enable the 74C163 inputs as shown in Fig. 9. To divide asynchronously, the output of the divide-by- N_1 circuit has to be connected to the input of the

by Gerard Girolami and Philippe Bamberger

divide-by- N_2 circuit. The latter solution is not much simpler than connecting the dividers synchronously so the sacrifice in speed is usually unwarranted.

On the other hand, if N is prime, this solution no longer applies and it is necessary to design a programmable divide-by-1-to-256 counter using a slightly different approach. The procedure is identical to

that used for the 1-to-16 programmable counter except that the relationships in equations (1), (2) and (3) given in the previous article must be changed to force the counter to 'oscillate' around the transition between counts 127 and 128. The new equations are:

$$L + D = 255 = 2^8 - 1 \quad (4)$$

$$D - I/2 = 127 \text{ if } I \text{ is even} \quad (5)$$

and

$$D - (I + 1)/2 = 127 \text{ if } I \text{ is odd.} \quad (6)$$

These relationships can again be implemented using two binary adders as shown in Fig. 10.

As shown previously, it is possible to find the logic relationships between input and load data as follows,

$$L_0 = I_0 \oplus I_1$$

$$L_1 = (I_0 + I_1) \oplus I_2$$

and so forth up to

$$L_6 = (I_0 + I_1 + I_2 + I_3 + I_4 + I_5 + I_6) \oplus I_7$$

$$L_7 = 0$$

$$D = \bar{L}$$

B.c.d. programmable counters

If division ratios from one to nine are required, the previously described binary-programmable circuit may be used. If, however, a similar circuit is designed using a decade counter, and the maximum divisor range of one to ten is required, the counter will have to 'oscillate' at the 4-5 transition, rather than at the 7-8 transition as was the case with the binary-programmable circuit. This means that as Q_D is used as the output, the signal obtained will not be square. In fact, if the dividing ratio is from 1 to 6, there will be no output at all. It is easy to get round this problem by producing a logic 0 for states zero to four and logic 1 for the remainder, but this creates new problems;

- more circuits are required
- even with a synchronous counter, it is difficult to avoid spikes on the output, so the clock will have to latch the output signal
- the maximum operating frequency is lowered.

So, for division ratios from one to nine, it is more practical to use a binary-counter circuit. But the decade counter can be used to advantage if division ratios up to 100, or

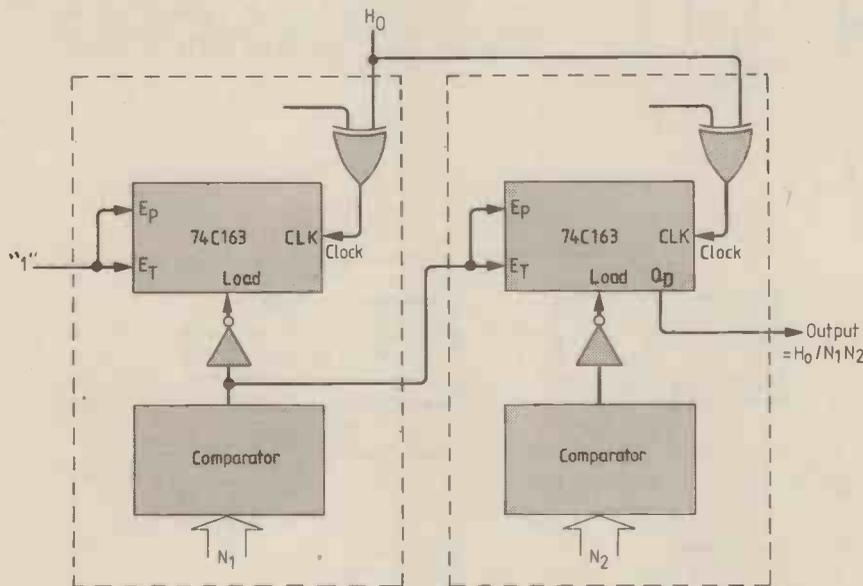


Fig. 9. Synchronous cascading of programmable divide-by-1-to-16 circuits. H_0 is the input and $N_1 N_2$ is the divisor, N . This method only applies where N is not prime.

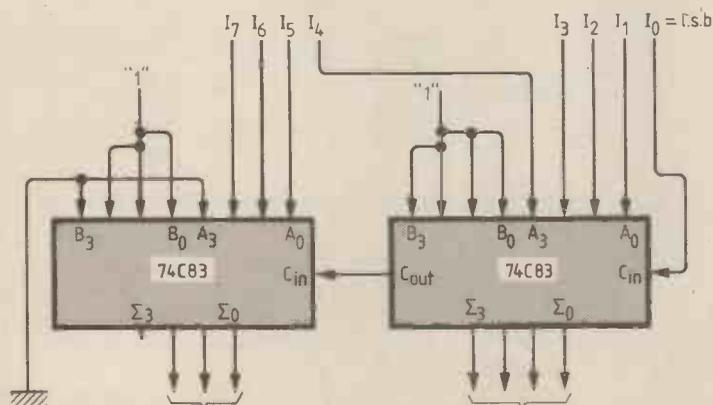


Fig. 10. Connecting binary adders for a programmable 1-to-256 divider, applying equations (5) and (6). Σ_3 of the most significant decade is not used.

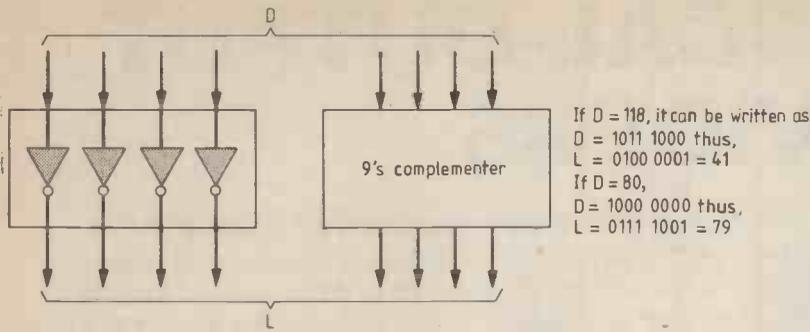


Fig. 12. Two b.c.d adders connected to give an output of $I/2$ when the divisor (I) is even, or $(I + 2)/2$ when the divisor is odd. The b.c.d. input value is shifted one position toward the least significant bit and a correction made through the adders when the l.s.b. of each decade is logic 1. In the original circuit, MC14560 natural b.c.d. adders were used.

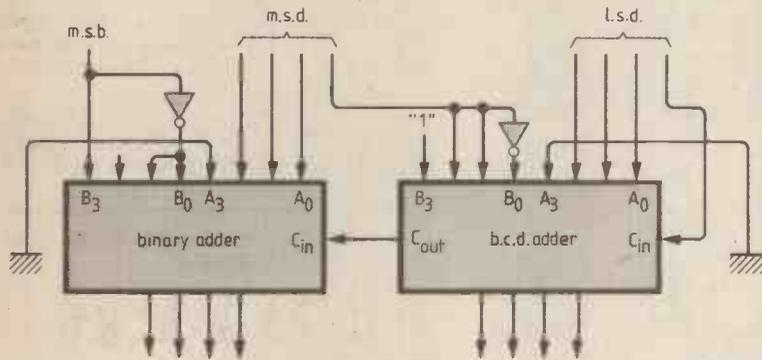
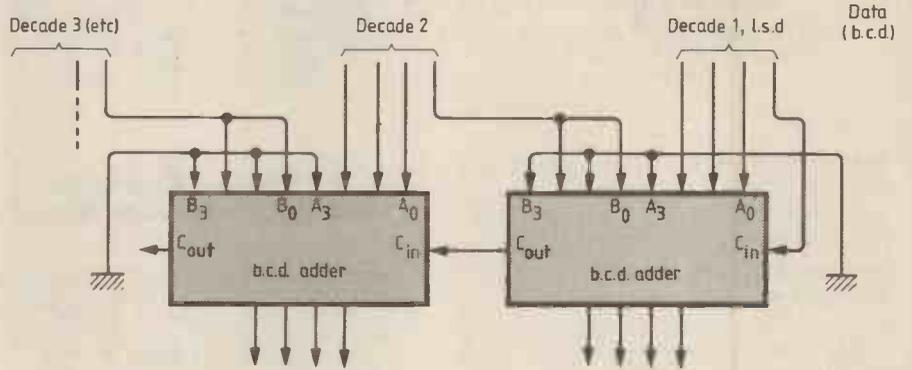


Fig. 14. Sections shown in Figs 11 and 13 combined with comparator and division circuits to form the b.c.d. input programmable divider for ratios $1 \leq I \leq 100$. Divisors up to 160 may be used with this circuit and further decades may be added.

even greater, are required. The following describes such dividers for ratios $1 \leq I \leq 100$, and further expansion.

For ratios $1 \leq I \leq 100$, two dividers are connected synchronously and are made to 'oscillate' around a given transition (at p to $p+1$). It should be obvious from the previous paragraph that a binary counter will still have to be used for the most-significant decade (m.s.d.).

If the output obtained is to be square, and one is to be free to choose a division ratio from 1 to 100, it is necessary to use the transition between counts 79 and 80 (or 799 and 800 if three decades are used) as the starting point.

Table 4 gives values for the following relationships;

$$L + D = 159 \quad (7)$$


$$D - I/2 = 79 \text{ if } I \text{ is even} \quad (8)$$

$$D - (I + 1)/2 = 79 \text{ if } I \text{ is odd} \quad (9)$$

To apply the value 159, a 9's complementer must be used in the least-significant decade, and four inverters for the next decade, Fig. 11. In the original circuit an

Fig. 11. Inverters and 9's complementers are used to apply equation (7) when cascading b.c.d.-input programmable dividers. Each additional decade will require the use of another 9's complementer.

Fig. 13. The two adders, as shown, perform a similar function to those shown in Fig. 12, but by replacing the most significant decade i.c. by a binary type, the maximum possible division ratio is raised to 160 and the m.s.b. may be used to change the input function.

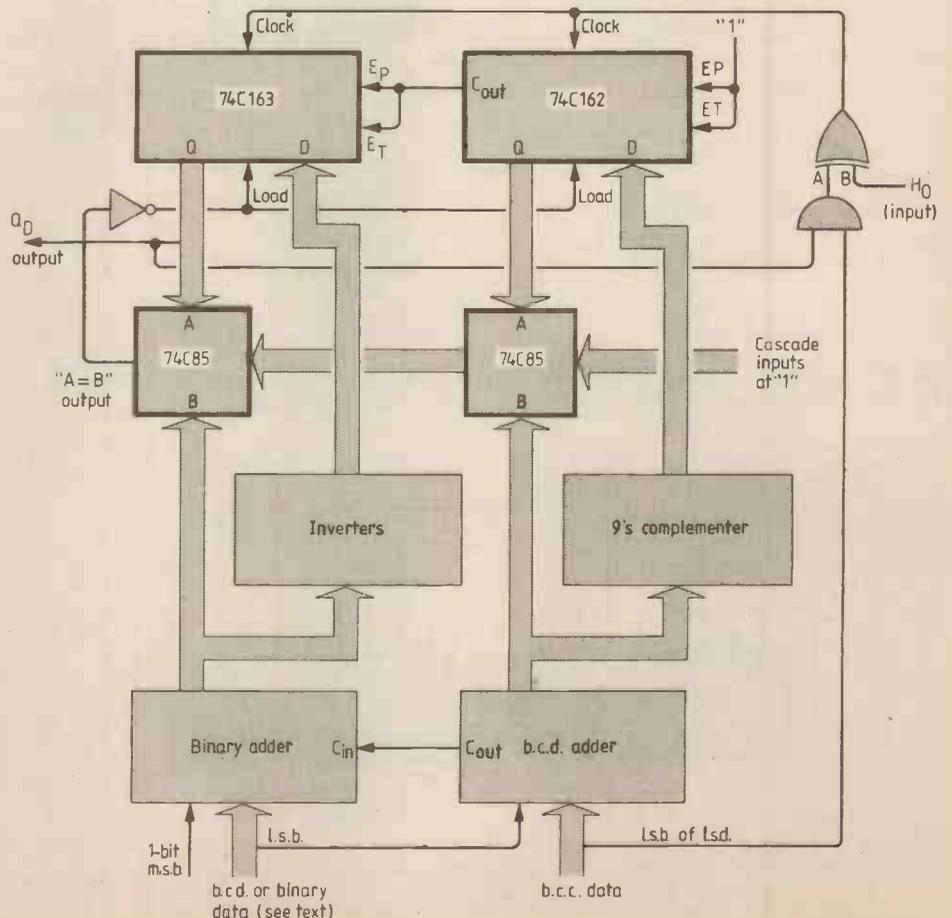

MC14561 9's complementer was used. To implement relationships (8) and (9), $I/2$ or $(I + 1)/2$ must be in b.c.d., see Fig. 12. The b.c.d. value is shifted one position to the least significant bit, and a correction is made through the b.c.d. adders when the l.s.b. of each decade is 1.

This method works well, but it is possible to make more use of the MC14560 adders because their design is such that arithmetical operations like $14 + P$ ($0 \leq P \leq 5$), which are not supposed to be valid in b.c.d., are possible and provide the correct result. Consequently, relationships (8) and (9) can be applied using a binary adder (for the m.s.d.), and a b.c.d. adder, as shown in Fig. 13. This circuit may be expanded to suit the desired number of decades. Figure 14 shows the complete circuit, which consists of the previously mentioned sections with two comparators and the dividers added. As can be seen in Fig. 14, the b.c.d.-input divider differs from the binary-input divider mainly through the inclusion of a b.c.d. adder for processing program-input data and the 9's complementer for the counter-load data.

Two other interesting features are inherent in the circuit;

- if the data m.s.b. is held high, the maximum programmable ratio is 199, whereas the maximum-possible division

Table 4: Divisor, load and detect (I, L and D) values for the b.c.d. programmable counter. This table is not given in full as it is obvious how omitted values are derived from the values given.

Divisor	Load	Detect
1	79	80
2	79	80
3	78	81
4	78	81
11	74	85
12	74	85
19	70	89
20	70	89
39	60	99
40	60	99
79	40	119
80	40	119
99	30	129
100	30	129

ratio is 160. Consequently, if a number higher than 160 is programmed, the actual ratio will be $N - 160$. For example if $N = 173$, the division ratio will be 13.

- if the data m.s.b. is held low, it is possible to use the full potential of the most significant digit, i.e., the input may be programmed to give ratios from 1 to 15. This means that the total division range will be from 1 to 160, the ratio 160 occurring when the value of the two input decades is zero.

If three decades are required, the fol-

lowing additional components are needed;

- a decade counter between the binary and b.c.d. counter (take care with the carry and enable-output connections)

- a comparator
- a 9's complementer
- a b.c.d. adder for input data (B inputs of this adder are connected as those of the l.s.d. adder).

C.m.o.s. i.c.s were originally used for the design and worked well up to 1MHz, depending on the division ratio. Changing the counters, comparators and gates to 74LS series i.c.s will bring the maximum usable frequency up to around 10MHz.

Bibliography

C. F. Chen, Design of a divide-by-N asynchronous odd number counter with 50/50 duty cycle. *IEEE Proceedings*, September 1974, pp.1278-1279.

J. L. Huertas, Square-wave frequency divider provides symmetrical output for odd divisors. *Electronic Design*, 21 September 1975, p100.

P. Bamberger, G. Girolami, Méthodes simples pour la division de fréquence symétrique. *Electronique et applications industrielles*, No 258, 15 October 1978, pp.59-61.

A. M. Madni and R. R. Orton, Cross-coupled one shots divide by odd numbers and give a symmetrical output. *Electronic Design*, 25 October 1979, p.114.


L. E. Getgen, Divide symmetrical clock pulses by odd numbers, get a symmetrical output. *Electronic Design*, 1 March 1980, p.110. □

ASCII KEYBOARD TESTER

A time-saving method for detecting faulty keys or data lines. Traditionally keyboards have been tested by using a voltmeter or an oscilloscope in conjunction with a table of ASCII codes. This takes a long time and can be prone to error. The tester described here can detect faults quickly and easily.

by Waleed Habib Abdulla

Fig. 1. The keyboard tester in outline.

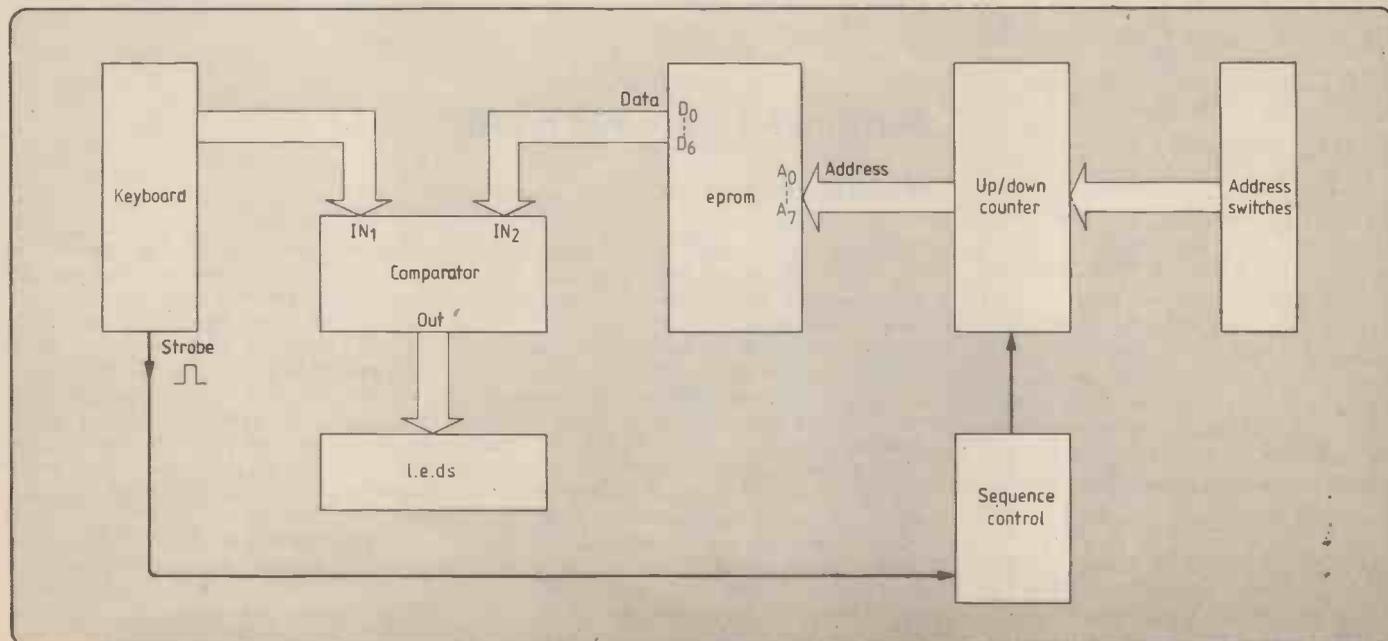

NEW PRODUCTS

WAVEFORM RECORDER

Digital waveform recorders are a new venture for Hewlett Packard but with their past experience in test and measuring instruments they have been able to jump in at the deep end. The HP5180 is a so called 'universal' waveform recorder, that is, it can be used on its own or under the control of a computer. A 10-bit a.-to-d. converter providing sampling rates up to 20MHz, and a 16K-by-10-bit memory that can be divided into a maximum of 32 segments form part of the system. Digital triggering is used so trigger times before or after the event, and trigger voltages, may be set and read accurately. One of the functions of two adjustable cursors is to pin-point a section of a waveform for vertical and/or horizontal zoom; these cursors may also be used to set trigger points. The front panel is, of course, designed ergonomically but nevertheless holds some 50 push buttons and one multi-purpose knob. With this in mind, up to four front-panel settings may be stored and recalled at will. All the front panel controls, and data i/o, are accessible through the HP-interface bus and 16-bit parallel d.m.a. (direct memory access) at transfer rates of up to 1M-word/s is possible. Hewlett-Packard Ltd, 308-314 Kings Road, Reading, Berks RG1 4ES. WW301



ranges has a resolution of 10fA and the maximum possible current reading is 2mA. Less than 200 μ V is present over the terminals on all current ranges. Resistances up to 200G Ω may be measured, also in nine ranges and resolution on the lowest range is 1 Ω . Three other ranges are used for charge measurements down to around 10fC on the lowest range and up to 20nC on the highest. Outputs are provided for a chart recorder and for guarding when making voltage and current measurements. A rechargeable lead-acid battery is included. Keithley Instruments Ltd, 1 Boulton Road, Reading, Berks RG2 0NL. WW302

TOOLS

This company has a wide range of tools and has recently introduced two kits, in wallets with zips, for



routine servicing. The more elaborate of these contains 25 tools, including a miniature soldering iron, de-solder braid, solder, pliers, cutters, tweezers, a knife, an i.c. extraction tool, scissors, a wire stripper and a range of screwdrivers and adjusting tools. Seven tools are contained in the smaller kit, pliers, side-cutters, tweezers and four screwdrivers. The former, the 'computer-service wallet, sells at £39.50 including v.a.t. and postage, and the latter, the 'micro wallet'; at £13.50, also inclusive. Toolmail Ltd, Parkwood Industrial Estate, Sutton Road, Maidstone, Kent ME15 9LZ. WW303


BEAD THERMISTORS

Often, thermal and voltage/current overloads in transformers, chokes, motors, generators, etc., are sensed by means of a p.t.c. thermistor. For this application, the response speed of a protection circuit is mainly de-

termined by the size of the thermistor and the thickness of its protective coating. Compstock have a range of general-purpose bead thermistors which all have a nominal resistance of 1k Ω at one of 13 temperatures from 80°C to 180°C, and each can be obtained as a bare pellet, resin dipped, sleeved or both resin dipped and sleeved. For all 13 reference temperatures, -5°C reduces the resistance to 550 Ω and +5°C increases the resistance to 1.3k Ω . Compstock Electronics Ltd, Compstock House, London Road, Stanford-le-Hope, Essex SS17 0JU. WW304

VOICE FILTERS

Active voice-frequency filters for use in telecommunications are available from Barr and Stroud as small p.c.b.-mounting modules. There are currently four modules, the EF117, 118, 118A and 119, all with elliptic-type transfer functions providing a minimum attenuation rate of 40dB. The 117 is a band-pass filter for the range 300Hz to 3.4kHz; attenuation variation between 350Hz and 3.0kHz is less than ± 0.5 dB. Both versions of the

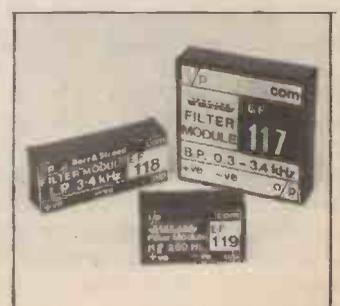

ELECTROMETER

Voltage, current, resistance and charge functions are included on Keithley's model 614 electrometer. On the three measuring ranges for up to 20V direct, the 4 1/2-digit meter's input impedance is 5 $\times 10^{13}$ Ω and 20pF; resolution on the lowest range is 10 μ V. The most sensitive of nine direct-current



NEW PRODUCTS

118 are low-pass filters, the first with a cut-off frequency of 3.4kHz and the second (suffix A) with a cut-off frequency of 1.8kHz. Using the latter version, the upper part of the voice-frequency channel is left free to carry data. Lastly is the 119 high-pass filter with a cut-off frequency of 300Hz and an upper limit of 50kHz. Supply rails between $\pm 5V$ and $\pm 18V$ are required for these modules. Barr and Stroud, Melrose House, 4-6 Savile Row, London W1X 1AF.
WW305

ANTENNAE FOR MOBILE RADIO

A Swedish company, Allgon Antenn AB, has produced two antennae, one for the aeronautical and land-mobile distress frequencies of 121.5 and 243MHz, and the other an omnidirectional broadband type for transmit and receive in the range 225 to 400MHz. The first, called simply type 4104 (shown in




photo) operates on both distress frequencies simultaneously and can be used in base stations, on mobile-radio units and ships, or on helicopters and aircraft travelling at less than 200mile/h. The second, type 477, is a base-station antenna covering the 225 to 400MHz frequency range without tuning. In the middle of this range, the antenna's gain is 6dB. The maximum average transmitting power is 1.5kW. Allgon Antenn AB, Box 500, S-184 00 Åkersberga, Sweden.
WW306

MODULAR ORGAN KIT

A "budget-priced" electronic organ with features only previously available on more expensive instruments is claimed for the Wersi Comet. Imported non-exclusively to the UK from Germany by Aura Sounds Ltd, 17 Upper Charter Avenue, Barnsley, Yorks.
WW307



WW307

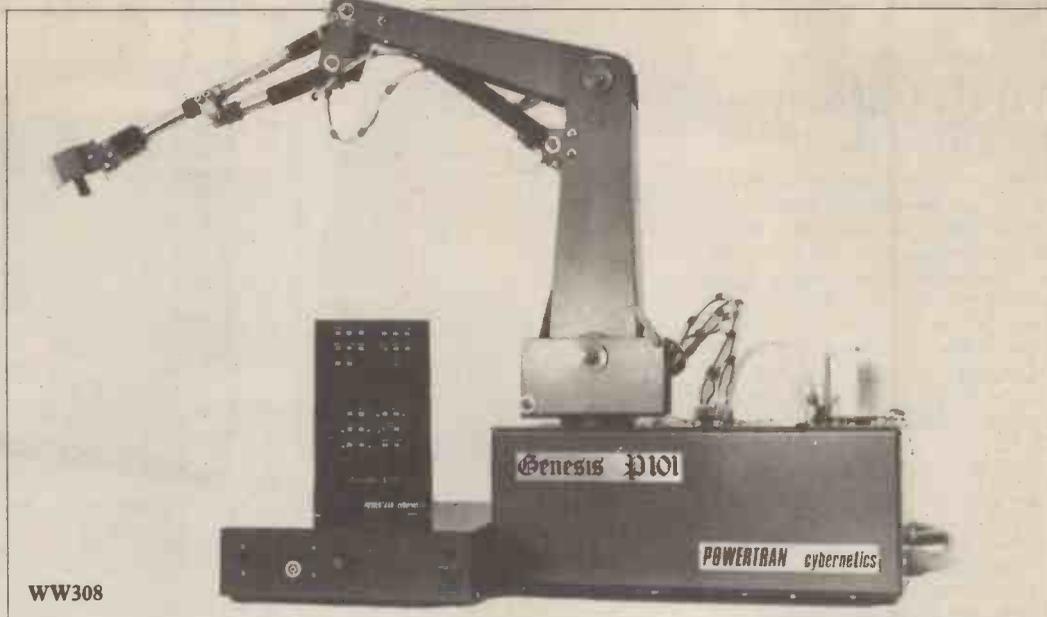

WW308

able and spinet versions, it can be bought in stages, the basic organ comprising four packs totalling £1293. Further packs include auto-accompaniment, registration memory/piano, and string/guitar facilities, bringing price to about £1900 against a factory built price of £3,600. Satellite keyboards – up to four can be connected with sections of the organ assigned to them – cost £138 in kit form. The makers claim numerous "realistic" and interesting tonal colours including synthesizer effects and guitar voices as well as the more traditional drawbar and orchestral sounds. How far the claim to realism is justified is obviously open to question, especially with auto accompaniment, but it seems much the best at simulating pipe organs. In addition to features now common to electronic organs and synthesizers that rely on voltage-controlled filters and amplifiers, this microprocessor design also has a program memory for 20 registrations; and a key memory can play background chords after notes are released. A digital transposer can pitch the organ in any key so that tuning is not required. Aura Sounds Ltd, 17 Upper Charter Avenue, Barnsley, Yorks.
WW307

GENERAL PURPOSE ROBOTS

Hydraulically driven robot arms that can be controlled either manually or by computer are manufactured by Powertran Cybernetics for industrial, educational or home use. Complete systems range in price from around £600 to £800. Each unit has its own 6802-microprocessor control and hydraulic system, and is capable of handling several pounds. One of these units, the M101, has either four or five axes of arm movement and can be fitted with wheels capable of carrying over 50kg. Communication with a computer is through an optional RS232 interface. Powertran Cybernetics, Portway Industrial Estate, Andover, Hants SP10 3NN.
WW308

CABLE SIMULATOR

Cable transmission characteristics are important in digital communication systems, especially where p.c.m. regenerators are concerned. To reduce the amount of floor space often required for testing such designs, Wandel and-Goltermann have introduced the PKN-1 for simulating cables with conductors between 0.6 and 1.4mm diameter. Cable attenuation is displayed on a digital readout and adjusted by means of two push buttons in steps of 1dB at a frequency of 1MHz. Both balanced and co-axial inputs and outputs are provided and a version of the PKN-1 with a 772kHz reference frequency can be supplied. A portable 200Hz to 620kHz level meter for measurements on voice channels in

local and remote networks has also been recently introduced by the same company. This meter has an analogue dB readout, a digital frequency display and a built-in generator. Wandel & Goltermann GmbH & Co., Postbox 45, Mühleweg 5, D-7412 Eningen, F. R. Germany.
WW309

Professional readers are invited to request further details on items featured here by entering the appropriate WW reference number(s) on the mauve reply-paid card.

CW AND RTTY TERMINAL

A communication terminal for encoding/decoding Morse or Baudot is manufactured by Polemark Ltd with inbuilt display, keyboard and real-time clock. The Microdot is a portable unit, microprocessor controlled, and has a 2Kbyte r.a.m. and 4K r.o.m., part of which contains some frequently used abbreviations and test-text which may be called using single key commands. Both modulator and demodulator are incorporated for c.w., f.s.k. and a.f.s.k. (audio-frequency shift keying). On receive, speed tracking is automatic; three fixed speeds may be set when transmitting and both transmit and receive speeds are displayed on the screen. Receive and transmit may be carried out simultaneously. The terminal's input may be connected directly to the output of a receiver or tape recorder, and the output directly to a transmitter. Self test is carried out by connecting the output to the input and supply requirements are 13.8V, direct at 2.4A. A price of £395 including v.a.t. and carriage is quoted. Polemark Ltd, 148-150 High Street, Barkway, Royston, Herts SG8 8EG.
WW310

First time on Earth.



**SHARP
MZ80B**

Sharp bring you the MZ80B.

A machine that offers you functions previously only associated with more powerful, more expensive computers; that gives you versatility to handle a huge range of software and hardware applications in scientific, business and personal use.

The MZ80B opens up a new world of graphic display potential, more flexible data storage and retrieval, and ease of operation.

Here is the computer from the future. Available today.

Stunning Graphic Display.

Seeing is believing. The large-screen, high-focus, green-face display incorporated in the MZ80B gives you high-resolution graphics of 320 x 200 dots.

An additional graphic RAM can be added which allows another 320 x 200 dot resolution pattern to be displayed.

This dual high-resolution graphic ability is especially useful for simulating and displaying a dynamic picture. It can display 40 characters x 25 lines or 80 characters x 25 lines via software switching.

In addition there are facilities for full, on-screen editing, reverse video, partial scrolling and a full range of graphic symbols.

Character and Graphic Printer.

This fast, quiet printer will reproduce your graphic displays and, of course, print-out upper and lower case letters and symbols. A tractor/friction feed version is also available.

Data Storage/retrieval.

The MZ80B has a remarkable memory. 64K of RAM. And that constitutes all the memory area, giving flexible storage of any computer language and its software. The cassette deck is electromagnetically-controlled, with a data transfer speed of 1800 bits/sec combined with a unique

programme search facility to make data storage and retrieval super-fast.



A typewriter-style keyboard incorporates characters and symbols plus a numeric key-pad and ten user-definable keys for fast and simple operation.

BASIC is, of course, provided with Z-80 Assembler Packages, PASCAL and a BASIC compiler.

Floppy Disk Drive.

A twin Floppy Disk Drive unit can be added which will give you 560 bytes of storage on double-sided, double-density disks.



Comprehensive Documentation.

Each MZ80B comes complete with a full set of documentation including an owners' manual giving full circuit diagrams, a monitor reference manual and programming manuals.

Interfaces

RS-232C and IEEE Interfaces are available from January 1982 allowing the MZ80B to communicate with scientific instruments and other peripherals.

CP/M*2.2

CP/M* is also available making a wide range of packages immediately available including wordprocessing, financial modelling, data base management to mention but a few. CP/M* also increases the disk capacity to 680K.

(CP/M* is a Trade Mark of Digital Research Ltd.)

SHARP

First, and foremost

SHARP ELECTRONICS (UK) LTD., COMPUTER DIVISION,
SHARP HOUSE, THORP RD., NEWTON HEATH,
MANCHESTER M10 9BE. TELEPHONE: 061-205 2333.

Why on Earth don't you find out more?



Please send me full information on the Sharp MZ80B computer.

Name

Address

Tel:

To: Sharp Electronics (UK) Ltd., Computer Division,
Sharp House, Thorp Road, Newton Heath,
Manchester M10 9BE. Telephone 061-205 2333.

(WW4/82)

WW - 011 FOR FURTHER DETAILS

Item No.	Description	Price
238	TEKTRONIX PORTABLE OSCILLOSCOPE type 422. Dual Trace.....	£360
239	TEKTRONIX STORAGE MONITOR type 613.....	£955
240	TEXAS SILENT 700 PRINTER Model KSR733-300 baud.....	£275
241	MARCONI UNIVERSAL BRIDGE type TF7200.....	£195
242	CALCOMP DRUM PLOTTER Model 564.....	£265
243	MARCONI AM/FM SIGNAL GENERATOR TF995A/3/S (CT402) 1.5-220MHZ.....	£245
244	MARCONI AC MILLIVOLTMETER TF2600 10HZ-5MHZ; 1mV-300V.....	£385
245	MOSELEY WAVEFORM TRANSLATER type 101.....	£380
246	MARCONI HETERODYNE FREQUENCY METER TF1067/1 5 to 1000MHZ.....	£355
218	R&S CAPACITANCE METER BN5201.....	£35
219	S.E. LABS OSCILLOSCOPE type SM11B Dual Trace Solid State DC-20MHZ.....	£245
220	RADAR DISH AERIAL 17" Wavguide size 0.5x1 1/4" complete with couplers.....	£55
221	EX-MINISTRY MASTS. Approx. 27ft. Heavy duty with guys etc.....	£25
222	PHILIPS VIDE COLOUR TEST GENERATOR type PM5522.....	£225
223	As above but NO CASE.....	£185
192	BELUX POWER UNIT type CMT3001. +/- 0-1000Volts in 3 ranges.....	£40
193	PHILIPS AUTOMATIC ELECTRONIC VOLT OHM METER type PM2405.....	£20
194	KAY ELECTRIC VARI-SWEEP Model 400 15-470MHZ.....	£30
195	TAYLOR VALVE VOLT METER type 112A.....	£15
196	ROGERS DISTORTION FACTOR METER OM344A 100HZ-10KHZ 0.01%.....	£75
198	STP MULTITEMP type 6610CA.....	£45
187	PYE PH METER Model 79.....	£80
188	FENLOW L.F. SPECTRUM ANALYSER 0.3c/s-1Kc/s. CW CHART RECORDER.....	£35
197	PLESSEY TELEGRAPH SIGNAL GENERATOR TSG10 with TOMS type 70. Speed 50-75-100 (2 units).....	£30
198	As above but SPEED 45.5-50-75.....	£100
199	HEWLETT PACKARD DIGITAL VOLTMETER type 3430A.....	£75
200	HEWLETT PACKARD WAVE ANALYSER Model 302A (No case).....	£150
167	KNIGHTS SWEEP/MARKER GENERATOR & RF GENERATOR (2 units).....	£75
168	PRESTON DIGITAL MULTIMETER X-Mod 723.....	£25
169	R&S LIMIT BRIDGE K2S BN500.....	£45
170	MARCONI VARIABLE ATTENUATOR TF1073A/2S (CT421).....	£25
171	SOLARTRON/SCHLUMBERGER JM1861 Programmable Pseudo Random Signal Generator.....	£120
172	WAYNE KERR VHF ADMITTANCE BRIDGE B801.....	£100
173	WAYNE KERR BRIDGE DETECTOR R181.....	£75
174	LABGEAR COLOURMATOR 625 Pattern Generator CM6004-PG.....	£30
175	GAUMONT-KALEE FLUTTER METER type 1740.....	£40
176	R&S SELEKTOMAT USVW BN5212/2.....	£80
177	BRITISH PHYSICAL LABORATORIES MEGOHMMETER RM 160/3.....	£35
153	R&S RESONANCE FREQUENCY METER 30-500MHZ WAM BN4312/2.....	£50
154	ADVANCE SIGNAL GENERATOR type E2 100KHZ-100M.....	£45
155	VIDEO CIRCUITS TUBE TESTER V32.....	£45
156	HEWLETT PACKARD OSCILLOSCOPE 182A with 1808A and 1825A 75MHZ Dual Trace Delayed Sweep.....	£395
159	MARCONI UNIVERSAL BRIDGE TF1313 1/4.....	£200
160	ADVANCE DIGITAL MULTIMETER DMM2.....	£50
161	TAYLOR AM-FM SIGNAL GENERATOR Model 62A MK2.....	£35
151	WAYNE KERR BRIDGE type B211.....	£25
152	BELL 110A GAUSSMETER with V32.....	£50
153	MARCONI SIGNAL GENERATOR TF8012/S 10-485 MHZ.....	£85
154	AVO VALVE TESTER CT160.....	£20
155	ADVANCE AUDIO SIGNAL GENERATOR type J1A.....	£30
84	ADVANCE UHF SIGNAL GENERATOR S689 370-1040 MHZ.....	£150
85	HEWLETT PACKARD DC POWER SUPPLY type 6448B. 0-500Volts 0-1.5Amps.....	£395
86	GRUNDIG UNIVERSAL UHF CONVERTER type V52.....	£25
87	DECADE CAPACITOR 1413 with ANALOG LIMIT COMPARATOR 1782 and IMPEDANCE COMPARATOR 1654 by GENERAL RADIO.....	£175
88	TEKTRONIX VECTORSCOPE type 526.....	£175

Item No.	Description	Price
89	BELL & HOWELL TV CAMERA with SHIBAN FUJINON TV ZOOM LENS FIZ-8 1.1.8f-20-100mm.....	£125
90	RACAL 600MHZ DECADE DIVIDER type 9010.....	£50
91	RACAL UHF FREQUENCY METER type 9839. 10-560MHZ.....	£275
71	WAYNE KERR COMPONENT BRIDGE type B521.....	£50
72	B & K LEVEL RECORDER type 2304.....	£40
73	RHOODE & SCHWARZ UHF TEST RECEIVER BN1523 280-340MHZ.....	£35
74	R & S FREQUENCY METER VHF-UHF. 30-300MHZ type WID BN442.....	£50
75	R & S ATTENUATOR type DPR BN1804/50.....	£25
76	HEWLETT PACKARD WIDE RANGE OSCILLATOR type 200CD.....	£50
77	HEWLETT PACKARD AUDIO OSCILLATOR type 200J.....	£50
78	FERRIS GRAPH RECORDER TEST SET type R152.....	£275
51	BEMEX CROSSHATCHDOT GENERATOR UHF/VHF.....	£25
52	MARCONI AF Output Meter type TF893.....	£20
53	RHOODE & SCHWARZ NOISE GENERATOR SKTU BN4151/2/60 3-1000MHZ.....	£100
54	TAYLOR RF SIGNAL GENERATOR type 68A/M MK2.....	£75
55	ADVANCE Q METER type T2 100KHZ-100MHZ.....	£30
56	ADVANCE PULSE GENERATOR type PG5002D.....	£25
57	ARMCO MILLIVOLTMETER type 301.....	£20
58	TAYLOR VALVE TESTER type 45D.....	£80
59	B & K LEVEL RECORDER type 2305, 50dB Potentiometer, Brand new with acces.....	£395
90	B & K LEVEL RECORDER type 2305.....	£325
81	MARCONI AM SIGNAL GENERATOR type TF801D/8S 10-485MHZ.....	£125
82	MARCONI UHF SIGNAL GENERATOR type TF1060.....	£125
83	AVO TRANSISTOR ANALYSER type TA.....	£30
64	ADVANCE STABILISED POWER UNIT type PP1 0-600V; 300MA.....	£25
65	PYE SCALAMP 40KV RMS Max ELECTROSTATIC VOLTMETER.....	£90
66	PYE SCALAMP 20KV RMS Max ELECTROSTATIC VOLTMETER.....	£85
4	TEKTRONIX 561A with 3A1 & 3B3 Plug-ins. Dual Trace Oscilloscope.....	£280
5	EQUIPMENT OSCILLOSCOPE type D61A. Dual Trace 10MHZ.....	£700
6	SCOPEX OSCILLOSCOPE type 4D10. Dual Trace 10MHZ.....	£160
7	B & K ACCELEROMETER PREAMPLIFIER type 282.....	£20
8	B & K DEVIATION BRIDGE type 1503.....	£85
9	B & K MICROPHONE AMPLIFIER type 2602.....	£75
10	B & K MICROPHONE AMPLIFIER type 2605.....	£40
11	B & K BEAT FREQUENCY OSCILLATOR type 1013.....	£165
12	B & K BEAT FREQUENCY OSCILLATOR type 1018.....	£50
13	B & K AUDIO FREQUENCY SPECTROMETER type 2112.....	£295
14	B & K FREQUENCY RESPONSE TRACER type 4707.....	£125
15	HEWLETT PACKARD LCR BRIDGE type 4261A.....	£850
16	HEWLETT PACKARD QLC METER type 4342A.....	£1350
17	AUTO TRANSFORMER 1.4kVA Pn Volts 90/240 Sec. 115.....	£18
18	POLARAD FIELD STRENGTH METER type FIM-B2 with RF Tuning Unit FIM-X2 7360-10,000MHZ.....	£150
20	POLARAD MICROWAVE SIGNAL GENERATOR Model MSG-1 950-2400MHZ.....	£250
21	POLARAD MICROWAVE SIGNAL GENERATOR Model MSG-2 2150-4600MHZ.....	£250
23	TEKTRONIX CURVE TRACER type 575.....	£150
24	KROHN-HITE BANQ PASS FILTER Model 330A.....	£35
25	KROHN-HITE REJECTION FILTER Model 350A.....	£35
26	POLARAD In SITU UNIVERSAL BRIDGE type TF2701. Battery Operated.....	£35
27	BRANDENBURGH HIGH VOLTAGE GENERATOR type MR50.....	£75
28	PHILIPS FM STEREO GENERATOR type PM6456. Separate L & R Signals Corner Freq. 100MHZ +/- 1%. RF 0/P 3mV pk-pk.....	£150
34	MARCONI WIDE RANGE OSCILLATOR TF1370. 10HZ-10MHZ.....	£75
35	RACAL H.F. SELECTIVE ANALYSER type 9056.....	£325
36	RANK ADBENA E.I.T. METER 0-30KV.....	£35
37	MARCONI (SANDERS) MICROWAVE POWER METER type 6598 with probe.....	£225

PLEASE CHECK AVAILABILITY BEFORE ORDERING
COMPONENT LIST AVAILABLE S.A.E. OR PHONE

TELETYPE PRINTERS ASR 33 - ASC11 Keyboard with 8 bit paper tape punch & reader £75 KSR33 (No punch or reader) £50 PDP8 In 6R RACK CABINET £100
AVO SIGNAL GENERATOR No. 2 AM/FM AM 0.45-225MHZ FM 20-100MHZ £75 each
IKEGAMI MONITOR 20" Black & White Solid state. Video in. int. ext. Sync. £75 each
SINE & SQUARE WAVE AUDIO GENERATOR TYPE TE-22, 20HZ-200KHZ. Portable, as new ONLY £35 each. P&P £4
MULTIMETER Russian Type 4324 AC/DC volts; AC/DC current; ohms, etc. Brand new, boxed. £12.50 each. P&P £2.50
GENERAL PURPOSE OSCILLOSCOPE TECH TYPE T02 Single beam. Size approx. 6x7x9 1/2 in. Weight 7lbs. Ideal for the beginner or school user. ONLY £35 each. P&P £4.
TEKTRONIX PLUG-INS TYPE D Single Trace High Gain DC Differential..... £20 TYPE E Single Trace Low Level AC Differential..... £20 TYPE G Single Trace Wide Band DC Differential..... £25 TYPE L Single Trace 30MHZ High Gain..... £25 TYPE M 4 Trace DC-20MHZ..... £125 TYPE O Operational Amplifier..... £95 TYPE Q Transducer & Strain Gauge..... £75 TYPE R Transistor Rise Time..... £75 TYPE TU-2 Testing..... £25 TYPE W Differential Comparator..... £125 TYPE Z Differential Comparator..... £75 TYPE 1A5 DC-50 MHZ Differential..... £75 TYPE 1S1 Sampling..... £175

BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. All units £6 carriage. Plus V.A.T. on total

CHILTMHEAD LTD

NORWOOD ROAD, READING

TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")

THE W.W. DISK OFFER

We have obtained a limited stock of European single sided mini floppy drives so please get orders in soon

Circle the enquiry number for data
Total U.K. price including VAT at 15% and carriage, CWO

ONLY £155 EACH INCLUSIVE
(Drive £132, P and P £2.78, VAT £20.22)

Please make cheques and P.O.s payable to
W.W. Disk Offer and send to:

W.W. DISK OFFER
49 Milford Hill
Batford
Herts

Please call **0582-429122** to check on availability before ordering

Allow 21 days for delivery. This offer applies to U.K. only and is subject to availability. For non U.K. orders send SAE for quotation

Also a few double sided 8" drives of the same manufacture. Check for availability, c.w.o. price: £395 + £5 carriage + VAT giving a total of c.w.o. price of £460 each

WW - 088 FOR FURTHER DETAILS

Catronics GREAT SPRING SALE

Everything covered by our
THREE STAR GUARANTEE

TELETEXT Kits, Components & Ready-Built

Ready built decoder (based on W.W. design) built by Datafax. This decoder (with power supply) is housed in a Teak Veneered plywood case measuring 22"x8 1/2"x3 1/4" and uses thumbwheel switches to select the pages. It includes conceal/reveal and colour background facilities.

CTT1715 - Sale Price only £95 + VAT = £109.25

'WIRELESS WORLD' TELETEXT DECODER KIT SALE OFFER SAVES 30% on our normal price

Catronics main kits contain all the printed circuit boards and components necessary to build the complete decoder.

A reprint of the series of articles is available at £1.95 + large 21p SAE (included free in complete kit).

Prices are for the Version with TEXAS X887 INCLUDING VAT.



Set of PCBs..... £16.30 + 50p P&P
Components Kit incl. PCBs..... £87.70 + £1.50 P&P
Cabinet..... £12.90 + £1.00 P&P

Also PLATED THROUGH hole PCB at additional cost of £17.00

New Facilities "Board 3" Kit..... £23.10 + 50p P&P
Ultrasonic Remote Control..... £54.65 + 50p P&P

FULL FAULT-FINDING AND REPAIR SERVICE AVAILABLE
COMPONENTS ALSO AVAILABLE SEPARATELY.
SAE for price list.

Pay by Barclaycard, Trustcard, VisaCard, Access, EuroCard, Master Charge, etc. Cash, Cheque, H.P., or Catronics Creditcharge Card

CB

We carry a full range of CB rigs & accessories.
Walkie-Talkies from £24.50. Mobiles from £64.95. Ask for details.

Catronics LTD.

COMMUNICATIONS HOUSE
(Dept. 224) 20 WALLINGTON SQUARE
WALLINGTON, SURREY SM6 8RG

Tel. 01-669 6700 (9am to 5.30pm, Sat. 12.45pm) / Closed lunch 12.45-1.45

WW - 027 FOR FURTHER DETAILS

LANGREX SUPPLIES LTD

Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

RST Tel: 01-677 2424 Telex: 946708 RST

SEMICONDUCTORS																					
AA119	0.12	AS215	1.38	BC172	0.13	BD131	0.51	BF257	0.31	GEX541	5.75	OAZ207	1.73	OC205	3.16	ZTX504	0.24	2N1671	1.73	2N3819	0.35
AA190	0.20	AS216	1.27	BC173	0.13	BD132	0.55	BF258	0.31	GJ3M	1.73	OC16	2.88	OC206	3.16	ZTX531	0.28	2N1893	0.37	2N3820	0.45
AA230	0.48	AS217	1.15	BC177	0.32	BD137	0.46	BF337	0.38	GM0378A	2.02	OC20	2.88	OC207	2.88	ZTX550	0.29	2N2147	4.60	2N3823	0.69
AA231	0.17	AS220	2.64	BC178	0.16	BD138	0.55	BF338	0.41	KS100A	0.52	OC22	2.88	ORP71	2.30	IN914	0.06	2N2148	4.31	2N3866	1.15
AA235	0.17	AS221	2.88	BC179	0.32	BD139	0.55	BF339	0.41	MJE370	0.84	OC24	3.45	R2008B	2.30	IN4001	0.07	2N2218	0.37	2N3904	0.20
AA237	0.17	AU113	2.88	BC182	0.13	BD140	0.58	BFS21	4.60	MJE371	0.82	OC25	1.15	R2009	2.59	IN4002	0.07	2N2220	0.23	2N3906	0.20
AC107	0.63	AU110	3.45	BC183	0.13	BD141	2.30	BFS61	0.23	MJE521	0.84	OC28	2.30	R2010B	2.30	IN4003	0.07	2N2221	0.23	2N4058	0.23
AC125	0.29	AU110	2.88	BC184	0.13	BD141	1.38	BFS98	0.23	MJE2955	1.50	OC29	2.30	TIC44	0.31	IN4004	0.08	2N2222	0.23	2N4059	0.23
AC126	0.29	BA145	0.15	BC212	0.13	BD182	1.36	BFW10	1.12	MJE3055	1.27	OC35	1.73	TIC226D	1.38	IN4005	0.10	2N2223	4.89	2N4060	0.18
AC127	0.29	BA148	0.17	BC213	0.13	BD237	0.62	BFW11	1.10	MPE105	0.40	OC36	1.73	TIP29A	0.49	IN4006	0.14	2N2368	0.29	2N4061	0.18
AC128	0.35	BA154	0.12	BC214	0.13	BD238	0.62	BFX84	0.31	MPE103	0.40	OC37	1.15	TIP42A	0.48	IN4007	0.14	2N2369A	0.29	2N4062	0.18
AC141	0.32	BA155	0.13	BC237	0.13	BDX10	1.05	BFX85	0.35	MPE104	0.40	OC42	1.04	TIP31A	0.38	IN4009	0.08	2N2646	0.58	2N4126	0.18
AC142	0.32	BA156	0.12	BC238	0.13	BDX32	2.30	BFX87	0.35	MPE105	0.40	OC43	1.73	TIP32A	0.41	IN5400	0.15	2N2904	0.37	2N4286	0.17
AC142K	0.40	BAW62	0.06	BC301	0.38	BDY20	1.73	BFX88	0.35	MPSA06	0.30	OC44	0.98	TIP33A	0.62	IN5401	0.15	2N2905	0.37	2N4288	0.21
AC176	0.35	BAX13	0.07	BC303	0.39	BDY60	3.16	BFY50	0.29	MPSA56	0.32	OC45	0.75	TIP34A	0.77	IS44	0.05	2N2906	0.24	2N4289	0.21
AC187	0.32	BC107	0.18	BC308	0.13	BF115	0.40	BFY51	0.29	MPSU01	0.61	OC71	1.65	TIP41A	0.51	IS920	0.09	2N2907	0.24	2N4547	0.37
AC188	0.32	BC108	0.18	BC327	0.14	BF152	0.18	BFY52	0.29	MPSU06	0.75	OC72	1.15	TIP42A	0.48	IS921	0.10	2N2924	0.29	2N4548	0.37
AC189	0.32	BC109	0.18	BC328	0.14	BF153	0.18	BFY53	0.29	MPSU07	0.75	OC73	1.15	TIP2955	0.81	IS921	0.10	2N2925	0.25	2N4549	0.37
AC191	1.50	BC115	0.17	BC329	0.14	BF154	0.18	BFY54	0.29	MPSU08	0.75	OC74	0.81	TIP3055	0.64	IS922	0.11	2N2926	0.17	25017	11.50
AC192	1.27	BC114	0.17	BC338	0.14	BF159	0.20	BFY19	1.09	NES55	0.52	OC75	0.75	IS43	0.49	IS923	0.11	2N2927	0.17	25019	13.80
AC193	1.27	BC115	0.21	BC339	0.14	BF160	0.20	BFY20	1.09	NKT401	4.03	OC76	1.15	IS44	0.49	IS924	0.11	2N2928	0.17	25020	13.80
AC194	1.27	BC116	0.21	BC340	0.14	BF161	0.28	BFY21	1.09	NKT402	2.88	OC77	1.15	IS45	0.49	IS925	0.11	2N2929	0.17	25021	13.80
AC195	1.27	BC117	0.22	BC341	0.14	BF162	0.28	BFY22	1.09	NKT403	2.88	OC78	1.15	IS46	0.49	IS926	0.11	2N2930	0.17	25022	13.80
AC196	1.27	BC118	0.22	BC342	0.14	BF163	0.28	BFY23	1.09	NKT404	2.88	OC79	1.15	IS47	0.49	IS927	0.11	2N2931	0.17	25023	13.80
AC197	1.27	BC119	0.22	BC343	0.14	BF164	0.28	BFY24	1.09	NKT405	2.88	OC80	1.15	IS48	0.49	IS928	0.11	2N2932	0.17	25024	13.80
AC198	1.27	BC120	0.22	BC344	0.14	BF165	0.28	BFY25	1.09	NKT406	2.88	OC81	1.15	IS49	0.49	IS929	0.11	2N2933	0.17	25025	13.80
AC199	1.27	BC121	0.22	BC345	0.14	BF166	0.28	BFY26	1.09	NKT407	2.88	OC82	1.15	IS50	0.49	IS930	0.11	2N2934	0.17	25026	13.80
AC200	1.27	BC122	0.22	BC346	0.14	BF167	0.28	BFY27	1.09	NKT408	2.88	OC83	1.15	IS51	0.49	IS931	0.11	2N2935	0.17	25027	13.80
AC201	1.27	BC123	0.22	BC347	0.14	BF168	0.28	BFY28	1.09	NKT409	2.88	OC84	1.15	IS52	0.49	IS932	0.11	2N2936	0.17	25028	13.80
AC202	1.27	BC124	0.22	BC348	0.14	BF169	0.28	BFY29	1.09	NKT410	2.88	OC85	1.15	IS53	0.49	IS933	0.11	2N2937	0.17	25029	13.80
AC203	1.27	BC125	0.22	BC349	0.14	BF170	0.28	BFY30	1.09	NKT411	2.88	OC86	1.15	IS54	0.49	IS934	0.11	2N2938	0.17	25030	13.80
AC204	1.27	BC126	0.22	BC350	0.14	BF171	0.28	BFY31	1.09	NKT412	2.88	OC87	1.15	IS55	0.49	IS935	0.11	2N2939	0.17	25031	13.80
AC205	1.27	BC127	0.22	BC351	0.14	BF172	0.28	BFY32	1.09	NKT413	2.88	OC88	1.15	IS56	0.49	IS936	0.11	2N2940	0.17	25032	13.80
AC206	1.27	BC128	0.22	BC352	0.14	BF173	0.28	BFY33	1.09	NKT414	2.88	OC89	1.15	IS57	0.49	IS937	0.11	2N2941	0.17	25033	13.80
AC207	1.27	BC129	0.22	BC353	0.14	BF174	0.28	BFY34	1.09	NKT415	2.88	OC90	1.15	IS58	0.49	IS938	0.11	2N2942	0.17	25034	13.80
AC208	1.27	BC130	0.22	BC354	0.14	BF175	0.28	BFY35	1.09	NKT416	2.88	OC91	1.15	IS59	0.49	IS939	0.11	2N2943	0.17	25035	13.80
AC209	1.27	BC131	0.22	BC355	0.14	BF176	0.28	BFY36	1.09	NKT417	2.88	OC92	1.15	IS60	0.49	IS940	0.11	2N2944	0.17	25036	13.80
AC210	1.27	BC132	0.22	BC356	0.14	BF177	0.28	BFY37	1.09	NKT418	2.88	OC93	1.15	IS61	0.49	IS941	0.11	2N2945	0.17	25037	13.80
AC211	1.27	BC133	0.22	BC357	0.14	BF178	0.28	BFY38	1.09	NKT419	2.88	OC94	1.15	IS62	0.49	IS942	0.11	2N2946	0.17	25038	13.80
AC212	1.27	BC134	0.22	BC358	0.14	BF179	0.28	BFY39	1.09	NKT420	2.88	OC95	1.15	IS63	0.49	IS943	0.11	2N2947	0.17	25039	13.80
AC213	1.27	BC135	0.22	BC359	0.14	BF180	0.28	BFY40	1.09	NKT421	2.88	OC96	1.15	IS64	0.49	IS944	0.11	2N2948	0.17	25040	13.80
AC214	1.27	BC136	0.22	BC360	0.14	BF181	0.28	BFY41	1.09	NKT422	2.88	OC97	1.15	IS65	0.49	IS945	0.11	2N2949	0.17	25041	13.80
AC215	1.27	BC137	0.22	BC361	0.14	BF182	0.28	BFY42	1.09	NKT423	2.88	OC98	1.15	IS66	0.49	IS946	0.11	2N2950	0.17	25042	13.80
AC216	1.27	BC138	0.22	BC362	0.14	BF183	0.28	BFY43	1.09	NKT424	2.88	OC99	1.15	IS67	0.49	IS947	0.11	2N2951	0.17	25043	13.80
AC217	1.27	BC139	0.22	BC363	0.14	BF184	0.28	BFY44	1.09	NKT425	2.88	OC100	1.15	IS68	0.49	IS948	0.11	2N2952	0.17	25044	13.80
AC218	1.27	BC140	0.22	BC364	0.14	BF185	0.28	BFY45	1.09	NKT426	2.88	OC101	1.15	IS69	0.49	IS949	0.11	2N2953	0.17	25045	13.80
AC219	1.27	BC141	0.22	BC365	0.14	BF186	0.28	BFY46	1.09	NKT427	2.88	OC102	1.15	IS70	0.49	IS950	0.11	2N2954	0.17	25046	13.80
AC220	1.27	BC142	0.22	BC366	0.14	BF187	0.28	BFY47	1.09	NKT428	2.88	OC103	1.15	IS71	0.49	IS951	0.11	2N2955	0.17	25047	13.80
AC221	1.27	BC143	0.22	BC367	0.14	BF188	0.28	BFY48	1.09	NKT429	2.88	OC104	1.15	IS72	0.49	IS952	0.11	2N2956	0.17	25048	13.80
AC222	1.27	BC144	0.22	BC368	0.14	BF189	0.28	BFY49	1.09	NKT430	2.88	OC105	1.15	IS73	0.49	IS953	0.11	2N2957	0.17	25049	13.80
AC223	1.27	BC145	0.22	BC369	0.14	BF190	0.28	BFY50	1.09	NKT431	2.88	OC106	1.15	IS74	0.49	IS954	0.11	2N2958	0.17	25050	13.80
AC224	1.27	BC146	0.22	BC370	0.14	BF191	0.28	BFY51	1.09	NKT432	2.88	OC107	1.15	IS75	0.49	IS955	0.11	2N2959	0.17	25051	13.80
AC225	1.27	BC147	0.22	BC371	0.14	BF192	0.28	BFY52	1.09	NKT433	2.88	OC108	1.15	IS76	0.49	IS956	0.11	2N2960	0.17	25052	13.80
AC226	1.27	BC148	0.22	BC372	0.14	BF193	0.28	BFY53	1.09	NKT434	2.88	OC109	1.15	IS77	0.49	IS957	0.11	2N2961	0.17	25053	13.80
AC227	1.27	BC149	0.22	BC373	0.14	BF194	0.28	BFY54	1.09	NKT435	2.88	OC110	1.15	IS78	0.49	IS958	0.11	2N2962	0.17	25054	13.80
AC228	1.27	BC150	0.22	BC374	0.14	BF195	0.28	BFY55	1.09	NKT436	2.88	OC111	1.15	IS79	0.49	IS959	0.11	2N2963	0.17	25055	13.80
AC229	1.27	BC151	0.22	BC375	0.14	BF196	0.28	BFY56	1.09	NKT437	2.88	OC112	1.15	IS80	0.49	IS960	0.11	2N2964	0.17	25056	13.80
AC230	1.27	BC152	0.22	BC376	0.14	BF197	0.28	BFY57	1.09	NKT438	2.88	OC113	1.15	IS81	0.49	IS961	0.11	2N2965	0.17	25057	13.80
AC231	1.27	BC153	0.22	BC377	0.14	BF198	0.28	BFY58	1.09	NKT439	2.88										

Samson's

(ELECTRONICS) LTD.

9 & 10 CHAPEL STREET, LONDON, NW1

01-723 7851

01-262 5125

ADJACENT TO EDGWARE ROAD MET. LINE STATION

PLEASE ADD 15% TO ALL ORDERS INC. CARR.
CURRENT RANGE OF NEW L.T. TRANSFORMERS
OPEN TYPE TAG CONNECTIONS
ALL PRIMARIES 220-240V

Type	Sec. Taps	Amps	Price	Carr.
1	24-30-40-48-60v	12	£36.50	£2.00
2	24-30-40-48-60v	10	£31.50	£2.00
3	24-30-40-48-60v	8	£27.50	£1.75
4	24-30-40-48-60v	5	£16.75	£1.75
5	24-30-40-48-60v	3	£11.50	£1.25
6	24-30-40-48-60v	2	£7.50	£1.25

6-8-10-12-16-18-20-24-36-40-48-60V
CAN BE OBTAINED FROM THE ABOVE RANGE

7	19-25-33-40-50V	10	£27.50	£2.00
8	19-25-33-40-50V	6	£19.50	£1.75
9	19-25-33-40-50V	3	£9.25	£1.25
10	19-25-33-40-50V	2	£7.75	£1.25

5-7-8-10-13-15-17-20-25-30-40-50V
OR 25-0-25V OR 20-0-20V CAN BE
OBTAINED FROM THE ABOVE RANGE

11	12-15-20-25-30V	10	£18.50	£1.75
12	12-15-20-25-30V	5	£10.50	£1.50
13	12-15-20-25-30V	2	£8.25	£1.25

3-4-5-6-8-9-10-12-15-18-20-24-30V
OR 12-0-12V OR 15-0-15V CAN BE
OBTAINED FROM THE ABOVE RANGE

14	12-24v	12v 60A, 24v 30A	£39.50	£3.50
15	12-24v	12v 30A, 24v 15A	£19.50	£2.00
16	12-24v	12v 20A, 24v 10A	£15.25	£2.00
17	12-24v	12v 10A, 24v 5A	£8.75	£1.50
18	12-24v	12v 4A, 24v 2A	£4.25	£1.25

HEAVY DUTY OP TRANSFORMERS

Type OT28EL 100 watts, 3.75Ω, 7.5Ω, 15Ω, 1.75K CT, 4 EL34 2x25 m/a dc max. £15.50, P&P £1.25. Type OT29EL 50 watts, 3.75Ω, 15Ω, 3.5K CT, rated 2x125 m/a dc max £8.95, P&P £1.

AUTO STEPDOWN TRANSFORMERS FOR AMERICAN EQUIPMENT

240/110 Volts. 80-2250 watts. Regular stock line. Types 80-1500 watts are fully shrouded. Fitted with American two or three pin socket outlets and 3 core 240V mains lead. Types 1750 and 2250 watts are steel cased with two American socket outlets. Neon indicator, three core mains lead and carrying handle. Send SAE for price list and further details. American sockets, plugs, adaptors also available.

SPECIAL OFFER. HINCHLEY MAINS ISOLATION TRANSFORMERS

Prim 240V. Sec 240V 250 watts. Open frame type. Tag connections. Fused input. £10, p.p. £2, V.A.T. £1.80. Parmeko pri tapped 115-220-240V. Sec 240V 6 amps. Fully shrouded top panel connections. Sec can be wired to give 120-0-120V. £25, carr. £5, V.A.T. £4.50.

HEAVY DUTY ISOLATION TRANSFORMERS

240-240V ex-computer equipment. Large selection available 10-15 amps. Fraction of maker price. Telephone for further details.

SPECIAL OFFER HEAVY DUTY TRANSFORMERS

Pri 240V sec 50V 15 Amps. Twice will give 100V CT or 50V 30A. Open frame type. Terminal block primary. Sec heavy wire leads. Frame size 8 1/2 x 7 x 5 inches. Screen winding between pri and sec. Brand new, fraction of list price, £32, carr £5, V.A.T. £5.95.

HEAVY DUTY LT CORE TRANSFORMERS

Pri 110-220-240V Secs 14V, 3V, 1 1/2V, 1V. Separate windings. All at 40 Amps. 14-15-15 1/2-17-18-18 1/2-19-19 1/2V can be obtained. £25, carr £4, V.A.T. £4.35.

IMPORTANT NEWS!!

We would like to announce the opening of our new branch at 21-23 BELL ST., NW1. It will, of course, stock our fantastic range of products that have made us famous over the past 25 years, PLUS!! many new ranges, i.e. computer and electronic components, test equipment, panel meters, multimeters, semiconductors, ICs and a large selection of plugs and sockets.

WHY NOT PAY US A VISIT - IT COULD SAVE YOU POUNDS!!

SPECIAL OFFER. HIGH POWER AMPLIFIER TRANSFORMERS

Pri tapped 120-240V sec tapped 34-29-0-29-34V 6amps and 46V 1A. Open frame type. Tag connection. Size 5 x 4 1/2 x 4 ins. £9 inc. postage and V.A.T.

POTTED HT CHOKES

45H 280 M/A £3.95, P&P £1.75, V.A.T. 70p. 10H 180 M/A £3.95, P&P £1.75, V.A.T. 70p. 10H 120 M/A £3, P&P £1, V.A.T. 60p. 5H 180 M/A £3, P&P £1, V.A.T. 60p. 15H 300 M/A £5, P&P £2, V.A.T. £1.05. 100H 10 M/A £1.75, P&P £1, V.A.T. 40p. 50H 25 M/A £2, P&P £1, V.A.T. 45p. 10H 75 M/A £2, P&P £1, V.A.T. 45p. Open types top panel connections 5H 350 M/A £3.50, P&P £2, V.A.T. 82p. 1H 1 amp £2.95, P&P £2, V.A.T. 90p. 25H 60 M/A £1.75, P&P £1, V.A.T. 40p. 15H 75 M/A £2, P&P £1, V.A.T. 45p. Gardners enclosed type 180H 24 M/A £4, P&P £2, V.A.T. 90p. 30H 120 M/A £4, P&P £2, V.A.T. 90p.

LT CHOKES

'C' core 8 M/H 15A £5.75, P&P £2, V.A.T. £1.32. 4.8 M/H 10A open frame type £3.95, P&P £1.50, V.A.T. 81p. Potted types 100 M/H 2A £4.50, P&P £1.50, V.A.T. 90p. 130 M/H 1.15A £2.50, P&P £1, V.A.T. 52p. 2 M/H 12A x 2, 2 M/H 24A or 4 M/H 12A £4.50, P&P £1.50, V.A.T. 30p. Open type 20 M/H 3A open type £1.95, P&P 75p, V.A.T. 40p. 'C' core 10 M/H 25A £10, Carr £3, V.A.T. £1.95. 'C' core 200 M/H 8A size 9 x 8 x 7 in. £20, Carr £5, V.A.T. £3.75.

INDUSTRIAL AUTOMATIC 24 VOLT 20 AMP BATTERY CHARGERS

AC input 240V 50Hz. DC output 24V 20A. Built in steel case size 15 x 12 x 9 1/2 ins. Complete with battery leads £65 + V.A.T. Callers only.

HIGH-GRADE TRICKLE CHARGERS

Input 240v AC. Output 12v DC 2 Amps. With mains lead, red and black battery leads with attached clips. Completely fused. Housed in wall mounting, steel case size 6 x 4 3/4 x 4in. £4.50, P&P £1.50 plus VAT. Total £6.90.

HEAVY DUTY LT TRANSFORMERS BY FAMOUS MAKERS

Pri 220-240V sec 70-0-70V 10A C core type top panel connections £20, carr £4, V.A.T. £3.60. Pri 115-220-240V sec 22.8V 10.5A and 10V 14A open frame tag panel connections £10, P&P £2, V.A.T. £1.80. Pri 220-240V secs 40V 8A, 38V 4A, 20V 4A, 30V 2.6A, 26V 2.6A 28V 2.5A, 51V 200 M/A £15, carr £3. Pri 110-220-240V secs 14V 5A, 14V 2 1/2A, 12V 10A, 8V 10A, 24V 1A. Separate windings £10, carr £3, V.A.T. £1.95.

ISOLATION TRANSFORMERS

Pri tapped 220-240V sec 240V 500 watts. Open frame type, top panel connections. Ex-equipment, but in perfect condition, £15, carr £3, V.A.T. £2.70.

BERCO VARIABLE TRANSFORMERS

Type 42A panel mounting, input 240V, output 0-270V 2A with control knob. Ex-equipment, but in perfect condition, £10, P&P £2.50, V.A.T. £1.88.

DC WKG BLOCK CAPACITORS

8 MFD 1000V OC WKG £3, P&P £1, V.A.T. 60p. 8 MFD 350V DC WKG £1.25, P&P 50p, V.A.T. 26p. 5 MFD 350V DC WKG £1, P&P 50p, V.A.T. 22p. 4 MFD 500V DC WKG £1, P&P 50p, V.A.T. 22p. 2 MFD 600V WKG 60p, P&P 20p, V.A.T. 12p. 1 MFD 1000V DC WKG 60p, P&P 20p, V.A.T. 12p. 1 MFD 600V DC WKG 5 for £1.50, P&P 50p, V.A.T. 30p. 0.25 MFD 500V DC WKG 6 for £1.25, P&P 50p, V.A.T. 16p. 0.1 MFD 1500V DC WKG 5 for £1.25, P&P 50p, V.A.T. 16p. 2 MFD 100V DC WKG ten for £1.50, P&P 75p, V.A.T. 33p. Tubular metallised paper caps 20 MFD 350V DC WKG with clip £3, P&P 50p, V.A.T. 52p.

LOW CURRENT LT TRANSFORMERS

Open frame clamped type, split bobbin. All primaries 240V No. 1 sec tapped 12-15-20-24-30V 750 M/A £4. No. 2 sec 9-0-9V 1A and 6.3V 200 M/A £2.50. No. 3 15-0-15V 600 M/A and 6.3V 200 M/A. No. 4 sec 12-0-12V 750 M/A and 6.3V 200 M/A £4. No. 5 sec 13V 1/2A £1.50. No. 6 sec 8V 1/2A 6.3V 600 M/A, 6.3V 300 M/A, 50V 40 M/A £2.50. No. 7 sec 17V 1/2A (DC) £1.75. No. 8 sec 16.5V 1/2A x 2 £1.75. No. 9 sec 18V 2A £4. No. 10 sec 24V 2A £4.50. No. 11 sec 15V 2A £3.50. All prices include postage and V.A.T.

SPECIAL OFFER LT TRANSFORMERS

Computer grade Pri 115-230V sec 27V 10A 9V 3A, 15V 0.5A, 15V 0.5A, 175V 100 M/A. Separate windings, open frame type, top panel connections. £3.95, postage £2.40, V.A.T. 34p.

LATEST PURCHASE. COMPUTER GRADE T TRANSFORMERS. All Primaries 240V. No. 1 sec. 26V 6A £8.50, carriage £1.50.

No. 2 sec. tapped 26-31-36V, 11.2A £12, P&P £2.
No. 3 sec. 36V 6A £8.50, P&P £1.50.
No. 4 sec. 43V 3A £4.75, P&P £1.50.
No. 5 sec. 24V 2A £2.75, P&P £1.25.
No. 6 sec. 27.5-0-27.5V 1.2A and 7-0-7V 0.75A £3.50, P&P £1.25.
No. 7 17V 1A £2 P&P 75p.
No. 8 13V 3A and 15V 1A £3.50, P&P £1.25.
No. 9 18V 2A £2.50, P&P £1.

PLEASE ADD V.A.T.

WW - 070 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS

Now available with
3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC

OUTPUT 2: 0-70v, 10A AC

OUTPUT 3: 0-250v, 4A AC

ALL
Continuously
Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW - 049 FOR FURTHER DETAILS

FOTOLAK

POSITIVE LIGHT SENSITIVE AEROSOL LACQUER

Enables YOU to produce perfect printed circuits in minutes!
Method Spray cleaned board with lacquer. When dry, place positive master of required circuit on now sensitized surface. Expose to daylight, develop and etch. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

FOTOLAK	£2.25	Pre-coated 1/16 Fibre-glass board	£1.50
Developer	35p	204mm x 114mm	£3.00
Ferric Chloride	55p	204mm x 228mm	£6.00
		408mm x 228mm	£9.00
		467mm x 305mm	

Plain Copper-clad Fibre-glass.	Single-sided	Double-sided
(Approx. 1.00mm thick ft. sq.)	£2.00	£1.75
Clear Acetate Sheet for making master, 260mm x 260mm	£2.00	15p

Postage and packing 60p per order. VAT 15% on total

G. F. MILLWARD ELECTRONIC COMPONENTS LIMITED

P.O. Box 19, Praa Sands, Penzance, Cornwall TR20 9TF

Telephone GERM0E (073-676) 2329

TRADE ENQUIRIES INVITED

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV Tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology. Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Seal-offs, and all other associated items for TV Tube Production. A Full Technical Back-up and Advisory Service is available to all customers World-wide.

Please request our current catalogues and Data Information.

GRIFTRONIC
EMISSION LTD
2 SWAN STREET
ALCESTER
WARWICKSHIRE B49 5DP
ENGLAND.

Telephone: (0789) 764852/764100 Telex: 312354 Grifem G

WW - 030 FOR FURTHER DETAILS

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER £20

Plays 12", 10" or 7" records, Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13 1/2 x 11 1/4 in. 3 speeds. Above motor board 3 1/2 in. Below motor board 2 1/2 in. Post £2 Board £1 extra



HEAVY METAL PLINTHS Post £2

Cut out for most BSR or Garrard decks. Silver grey finish, black trim. Size 16x13 3/4 in. **£4**

DECCA TEAK VENEERED PLINTH. Post £1.50 Superior finish with space and panel for small amplifier. Board is cut for B.S.R. 18 1/2 in. x 14 1/4 in. x 4 in. Black/silver fascia trim. Also with brackets cut out for Garrard only £3. Plastic cover £6 **£5**

TINTED PLASTIC COVERS Post £2

17 7/8 x 13 1/2 x 3 1/4 in.	£6	18 1/4 x 12 1/2 x 3 in.	£6
17 1/4 x 9 3/8 x 3 1/2 in.	£3	14 3/8 x 12 1/2 x 2 7/8 in.	£5
13 3/4 x 12 x 2 1/4 in.	£5	16 5/8 x 13 x 4 in.	£6
15 1/4 x 13 1/2 x 4 in.	£6	14 1/2 x 13 1/8 x 2 9/16 in.	£5
17 1/4 x 12 7/8 x 3 1/2 in.	£6	17 1/4 x 13 3/4 x 4 1/8 in.	£5

Callers Only (not suitable for post)

21 1/2 x 14 1/4 x 2 1/2 in.	£6	21 x 13 7/8 x 4 1/2 in.	£6
23 3/4 x 14 x 3 1/4 in.	£6	30 3/4 x 13 3/8 x 3 1/4 in.	£6

BSR SINGLE PLAYER DECKS

BSR P232 BELT DRIVE QUALITY DECK Manual or automatic play. Precision ultra slim arm. Cueing device. Bargain price With stereo ceramic cartridge **£24** Post £2



BSR P204 SPECIAL SINGLE PLAYER ideal for portable two-speed Hi-Fi system with ADC QLM30 stereo magnetic cartridge and cueing device. **£24** Post £2 BSR ready cut mounting board. Only £1 extra.

GARRARD 6-200 SINGLE PLAYER DECK Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. Cueing Device. **£22** Post £2 Ready cut mounting board £1 extra.

BATTERY ELIMINATOR MAINS TO 9 VOLT D.C. Stabilised output, 9 volt 400 mA. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5 x 3 1/4 x 2 1/2 in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models, £4.50. Post 65p.

DE LUXE SWITCHED MODEL STABILISED. £7.50. Post £1. 3-6-7 1/2-9 volt 400mA DC max. Universal output plug and lead. Pilot light, mains switch, polarity switch.

DRILL SPEED CONTROLLER-LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains, £3. Post 65p.

DE LUXE MODEL READY-BUILT 800 watts. Front plate fits standard box, £5. Post 65p.

EMI 1 1/2" x 8 in. LOUSPEAKERS Model 450, 10 watts R.M.S. with moving coil tweeter and two-way crossover; 3 ohm or 8 ohm. £9.50 post £1.50. "Final Clearance". SUITABLE BOOKSHELF CABINET £6.50.



RELAYS. 12V DC £1.25. 6V DC 95p. 18V £1.25. BLANK ALUMINIUM CHASSIS. 6x4-£1.45; 8x6-£1.80; 10x7-£2.30; 12x8-£2.60; 14x9-£3; 16x6-£2.90; 16x10-£3.20. All 2 1/2 in. deep. 18 swg ANGLE ALI. 6x3 1/4 x 3 1/4 in. 18 swg. 25p.

ALUMINIUM PANELS. 18swg. 6x4-45p; 8x6-75p; 14x3-75p; 10x7-95p; 12x8-£1.10; 12x5-75p; 16x6-£1.10; 14x9-£1.45; 12x12-£1.50; 16x10-£1.75. PLASTIC AND ALI BOXES IN STOCK. MANY SIZES

ALUMINIUM BOXES. 4x4x1 1/2 £1. 4x2 1/2 x 2 £1. 3x2x1 £1. 6x4x2 £1.60. 7x5x3 £2.40. 8x6x3 £2.50. 10x7x3 £3. 12x5x3 £2.75. 12x8x3 £3.60. All with lids.

BRIDGE RECTIFIER 200V 1P 2A £1. 4A £1.50. 8A £2.50. TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p. RESISTORS. 10Ω to 10M. 1/4W, 1/2W, 1W, 1P: 2W 10p. HIGH STABILITY. 1/2W 2% 10 ohms to 1 meg. 8p.

Ditto 5%. Preferred values, 10 ohms to 10 meg. 3p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 20p PICK-UP CARTRIDGES SONATONE 9TA £2.50. 9TAC £3.80 BSR Stereo Ceramic SC7 Medium Output £2. SC12 £3.

PHILIPS PLUG-IN HEAD. Stereo Ceramic. AU1020 (G306-GP310-GP233-AG3306-AG3310) £2. LOCKTITE SEALING KIT DECCA 118. Complete £1. ANTEX SOLDERING IRON 240V 15W. 3mm bit £4.75.

JACK PLUGS Mono Plastic 20p; Metal 30p. JACK PLUGS Stereo Plastic 30p; Metal 35p. JACK SOCKETS Mono Open 20p; Closed 25p. JACK SOCKETS Stereo Open 25p; Closed 30p.

FREE SOCKETS - Cable end 30p. Metal 45p. 2.5mm and 3.5mm JACK SOCKETS 20p. Plugs 20p. DIN TYPE CONNECTORS Sockets 3-pin, 5-pin 10p. Free Sockets 3-pin, 5-pin 25p. Plugs 3-pin 20p; 5-pin 25p; Speaker plugs 20p; Sockets 15p.

PHONO PLUGS AND SOCKETS aa. 15p. Free Socket for cable end 20p. Screened Phono Plugs 25p. U.H.F. COAXIAL CABLE SUPER LOW LOSS, 25p vd. COAX PLUGS 30p. COAX SOCKETS 20p. NEON PANEL INDICATORS 250V 30p.

POTENTIOMETERS Carbon Track 5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5K. SP 45p.

MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument. Impedance + Capacity - 2000 o.p.v. Battery included. 11 instant ranges measure: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0-100mA. Continuity and resistance to 1 meg ohms in two ranges. **£6.50** Post 65p

De Luxe Range Doubler Model, 50,000 o.p.v. £18.50. 7 x 5 x 2 in. Post £1

NEW PANEL METERS £4.50

50µa 100µa, 500µa, 1ma, 5ma, 50ma, 100ma, 500ma, 1 amp, 2 amp 25 volt, 50 volt, VU Meter. 2 1/4 x 2 x 1 1/4 in. Post 65p



RCS SOUND TO LIGHT CONTROL KIT

Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. Suitable for home or disco. Easy to build. Full instructions supplied. Post 95p Cabinet £4.50 extra. Operates from 200MV to 100W. 200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights, Edson Screw. 6 for £4, or 12 for £7.50. Post 65p. Suitable panel mounting holders 85p.

RCS "MINOR" 10 watt AMPLIFIER KIT £14.

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Specification 10W per channel; size 9 1/2 x 3 x 2 in. SAE details. Full instructions supplied. 240V AC mains powered. Post £1.

RCS STEREO PRE-AMP KIT.

All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board Can be ganged to make multi-way stereo mixers **£2.95** Post 65p

MAINS TRANSFORMERS

250-0-250V 70ma, 6.5V, 2A	£4.50
250-0-250V 80ma, 6.3V, 3.5A, 6.3V 1A	£5.00
350-0-350V 250ma, 6.3V 6A CT	£12.00
300-0-300V 120ma, 2.6V, 3V 2A C.T., 5V 2A	£12.00
220V 45ma, 6.3V 2A	£2.50

AUTO 115V to 240V 150W £9. 250W £10. 400W £11. 500W £12. £2.

GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available		
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V		£6.00
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£6.00
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£10.50
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£12.50
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£16.00
5-8-10-16V. 1/2 amp.	£2.50	80p
6V. 1/2 amp.	£2.00	£1
6-0-6V. 1/2 amp.	£3.50	£1
9V. 250ma.	£1.50	80p
9V. 3 amp	£2.50	£1
9-0-9V. 50ma	£1.50	80p
10-0-10V. 2 amps	£3.00	£1
10-30-40V. 2 amps	£3.50	£1
12V. 100ma	£1.50	80p
12V. 750 ma	£2.00	80p
12V 3 amps	£3.50	£1
12-0-12V. 2 amps	£3.50	£1
15-0-15V. 2 amp	£3.75	£1
20-0-20V 1 amp	£3.50	£1
20-40-60V 1 amp	£4.00	£2
25-0-25V 2 amps	£4.50	£1
28V 1 amp Twice	£5.00	£2
30V 1/2 amp	£3.50	£1
30V 5 amp and	£4.50	£2
17-0-17 2a	£4.00	£2
35V 2 amps	£4.00	£1

CHARGER TRANS	Post	RECTIFIERS	Post
6-12 volt 3a	£4.00+£2	6-12 volt 2a	£1.10+80p
6-12 volt 4a	£6.50+£2	6-12 volt 4a	£2.00+80p

OPUS COMPACT SPEAKERS £22 pair Post £2

TEAK VENEERED CABINET 11 x 8 1/2 x 7 in, 15 watts 50 to 14,000 cps. 4 ohm or 8 ohm

OPUS TWO 15 x 10 1/2 x 7 3/4 in 25 watt 2-way system £39 pair. Post £3.

LOW VOLTAGE ELECTROLYTICS 10p

1 mf, 2 mf, 4 mf, 8 mf, 10 mf, 16 mf, 25 mf, 30 mf, 50 mf, 100 mf, 250 mf. All 15 volts. 22 mf/6V/10v; 25 mf/6V/10v; 47 mf/10v; 50 mf/6v; 68 mf/6v/10v/16v/25v; 100 mf/10v; 150 mf/6v/10v; 200 mf/10v/16v; 220 mf/4v/10v/16v; 330 mf/4v/10v; 500 mf/6v; 680 mf/6v/10v/16v; 1000 mf/2.5v/4v/10v; 1500 mf/6v/10v/16v; 2200 mf/6v/10v; 3300 mf/6v; 4700 mf/4v. 500mF 12V 15p; 25V 20p; 50V 30p; 1200mF 76V 80p. 1000mF 12V 20p; 25V 35p; 50V 50p; 100V 70p. 2000mF 6V 25p; 25V 42p; 40V 60p; 2000mF 100V £1.20. 2200mF 63V 90p; 2500mF 50V 70p; 3000mF 50V 65p. 4500mF 64V £2. 4700mF 63V £1.20. 2700mF/76V £1.

HIGH VOLTAGE ELECTROLYTICS

8/450V 45p 8+8/450V 75p 32+32+16/350V 90p 8/800V £1.20 8+16/450V 75p 100+100/275V 65p 16/350V 45p 20+20/450V 75p 150+200/275V 70p 32/500V 75p 32+32/350V 50p 220/450V 95p 32/350V 50p 32+32/500V £1.80 32+32+32/325V 75p 50/500V £1.20 50+50/300V 50p 50+50+50/350V 95p

CAPACITORS Various 10p to 100,000pF 5p

PAPER 350V-0.1 7p; 0.5 20p; 1mF 150V 20p; 2mF 150V 20p; 500V-0.001 to 0.05 12p; 0.1 15p; 0.25 25p; 0.47 35p.

VALVE OUTPUT Transformers (small) 90p.

TRIMMERS 10pF, 30pF, 50pF, 5p. 100pF, 150pF, 15p.

MICROSWITCH SINGLE POLE CHANGEOVER 30p.

SUB-MIN MICRO SWITCH, 30p. Single pole changeover.

TWIN GANG, 120pF 50p; 500 + 200 pF £1.

GEARED TWIN GANGS 25pF 95p. 365pF £1.

GEARED 365+365+25+25pF £1.

TRANSISTOR TWIN GANG. Japanese Replacement 50p.

HEATING ELEMENTS, WAFER THIN

Size 11 x 9 x 1/8 in. Operating voltage 240V, 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, Propagation, etc. Must be clamped between two sheets of metal ceramic, etc. ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

NEW baker Star sound

high power full range quality loudspeakers produced to give exceptional reproduction. Ideal for Hi-Fi, music P.A. or discotheques. These loudspeakers are recommended where high power handling is required with quality results. The high flux ceramic magnet ensures clear response.



MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£14	£2
DELUXE MK II	12	8	15	HI-FI	£14	£2
SUPERB	12	8-16	30	HI-FI	£24	£2
AUDITORIUM	12	8-16	45	HI-FI	£22	£2
AUDITORIUM	15	8-16	80	HI-FI	£34	£2
GROUP 45	12	4-8-16	45	PA	£14	£2
GROUP 75	12	4-8-16	75	PA	£18	£2



BAKER 150 WATT MIXER/POWER AMPLIFIER £89 Post £2 SLAVE VERSION £75

For Organs, Discotheque, Vocal, Public Address. Three loudspeaker outputs for 4, 8 or 16 ohms. Four high gain inputs, each 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. 150 watts into 8 ohms R.M.S. Music Power. Distortion less than 1%. Slave output 500 M.V. 25K.ohm. Frequency Response 25 Hz - 20kHz ± 3dB. Integral Hi-Fi preamp separate Bass & Treble. Compact - 16" x 8" x 5 1/2". Lightweight - 14lb: Master volume control. Made in England. 12 months' guarantee. 200/250V A.C. mains or 120V to order. All transistor and solid state devices. 100 Volt Line £15 extra.

New Stereo Slave Model 150 + 150 watt £125. Post £4. BAKERS NEW PA150 MICROPHONE PA AMPLIFIER £129. Post £3 & channel 8 inputs, dual impedance, 50K-600 ohm 4 channel mixing, volume, treble, bass. Presence controls, Master volume control, echo/send/return socket. Slave input + output sockets.

BAKER 50 WATT AMPLIFIER £69 Post £2

Ideal for PA systems, Discos and Groups. Two inputs, Mixer, Volume Controls, Master Bass, Treble Gain.



RCS offers MOBILE PA AMPLIFIERS. Outputs 4-18-16 ohms 20-watt RMS 12V DC, AC 240V, 3 inputs. 50K £46 (PP £2). 40-watt RMS 12V DC, AC 240V, 4 inputs. 50K 100V Line £75 (PP £2). Mic 1; Mic 2; Phono; aux. outputs 4 or 8 or 16 and 100V line 60-watt RMS, Mobile 24 volt DC & 240-volt AC mains. inputs 50K. 3 mics + 1 music. Outputs 4-8-16 ohm + 100 volts line £95

FAMOUS LOUSPEAKERS "SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
SEAS	TWEETER	4in	50	8	£3.50	£1
GOODMANS	TWEETER	3 1/2 in	25	8	£4.00	£1
AUDAX	TWEETER	4in	30	8	£6.50	£1
SEAS	MID-RANGE	4in	50	8	£7.50	£1
SEAS	MID-RANGE	5in	80	8	£12.00	£1
SEAS	MID-RANGE	4 1/2 in	100	8	£12.50	£1
GOODMANS	HIFAX	7 1/2 x 4 1/4	100	4/8/16	£22	£2
AUDAX	WOOFER	8in	40	8	£14.00	£2
GOODMANS	WOOFER	8in	25	4/8	£6.50	£1
GOODMANS	HB	8in	60	8	£12.50	£1
CELESTION	DISCO/P.A.	10in	20	8/16	£11.50	£2
CELESTION	DISCO/P.A.	10in	60	8/16	£21.50	£2
RIGONDA	GENERAL	10in	15	8	£5.50	£2
AUDAX	WOOFER	10in	50	8	£16.00	£2
GOODMANS	PP12	12in	75	8/15	£24.50	£2
GOODMANS	GR12	12in	90	8/15	£27.50	£2
GOODMANS	HPD	12in	120	8/15	£27.50	£2
EMI	HI-FI	13x8 10	3/8	£9.50	£1	

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

B.A.F. LOUSPEAKER CABINET WADDING 18in wide 35p ft.

CASSETTE MONO REPLAY. Complete working £12.50

CASSETTE MOTOR. 8 volt £1

CASSETTE MECHANISM. 6 or 12V Stereo Heads £5

CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm £1.90. 3-way 950 cps/3000 cps. 20 watt rating. £2.20. 3 way 60 watt £6.

LOUDSPEAKER BARGAINS

3 ohm, 5in, 7 x 4in, £2.50; 6 1/2 in, 8 x 5in, £3; 8in, £3.50.

8 ohm, 2 1/2 in, 3in, £2; 5in, £2.50; 6 1/2 in, £3; 8in, £4.50; 12in, £6.

15 ohm, 3 1/2 in, 5 x 3in, 6 x 4in, £2.50.

2 1/2 ohm, 3in, £2; 5 x 3in, 7 x 4

VIDEOTEX SYSTEMS '82 CONFERENCE

Cunard International Hotel
Hammersmith, London W6

May 5, 6, 7, 1982

This important two day conference will cover in depth, both technical and marketing aspects of videotex technology.

Presentations will be made by experts, drawn from the industry's leading equipment manufacturers, system operators and users.

Subjects include: Day One — The politics · Gateway · Direct transfer · Hardware and Software compatibility · International networks. Day Two — Marketing the product · Economics · Umbrella services · The Canadian experience · Private systems · The next ten

Speakers include: John Wakeham, MP,

John Durham, Alan Haines, David Gilbert, Ken Knight, Ted Sedman, J Döring, Murray Cook, Tony Book, Jenny Clayton, Tim Chapman, Colin Tipping, Geoff Hutt, Andrew Lighting, Anthony Harris, James Smith, John Marsh, Chris Singer, Mike Aston and Malcolm Smith.

Conference organised on behalf of AVIP The Association of Viewdata Information Providers Limited.

Run in parallel with
VIDEOTEX SYSTEMS '82 EXHIBITION
Cunard International Hotel May 5-7

Full details from: Sue Bonnell,
IPC Conferences Ltd, Surrey House,
Throwley Way, Sutton, Surrey SM1 4QQ.
Tel: 643 8040 Ext. 4889 and 4891

Please send details about Videotex Systems '82 conference/exhibition to:

Name _____
Company _____
Address _____
Tel: _____

BARCLAYCARD

VISA

Master Charge

PM COMPONENTS LTD VALVE & COMPONENTS SPECIALISTS

INTEGRATED CIRCUITS

AN124 2.50	PLLO2A 6.75	SN76660N 0.80	TBA530Q 1.10	TDA1170 1.95
AN214Q 2.50	SAA1020 8.95	SN76666N 0.70	TBA540 1.25	TDA1170S 1.95
AN240P 2.80	SAA1021 7.50	SW153 2.74	TBA540Q 1.35	TDA1190 2.15
AN612 3.25	SAA1024 4.50	TA7061AP 3.15	TBA550 1.45	TDA1270Q 3.95
AN7150 2.95	SAA1025 7.25	TA7073AP 1.80	TBA550Q 1.45	TDA1327 1.70
BA521 3.35	SAA5000A 3.05	TA7108P 1.00	TBA560C 1.45	TDA1352B 1.43
BRC1330 0.78	SAA5010 6.35	TA7120P 1.85	TBA570 1.00	TDA1412 0.85
BTTE22 2.10	SAS5605 1.60	TA7172P 1.85	TBA641A12 2.50	TDA2020 2.45
ET1016 1.75	SAS570S 1.60	TA7176AP 2.50	TBA641B11 3.00	TDA2030 2.80
HA1151P 2.50	SAS580 2.85	TA7203 2.95	TBA641-B11 3.00	TDA2140 3.75
HA1366W 2.95	SAS590 2.85	TA7204P 2.15	TBA651 1.75	TDA2522 1.95
LA3350 2.50	SAS660 1.85	TA7205AP 1.95	TBA673 2.45	TDA2524 1.95
LA4031P 2.70	SAS670 1.85	TA7222AP 1.80	TBA700Q 1.80	TDA2530 1.54
LA4032P 2.50	SL490 1.95	TA7310P 1.80	TBA720A 2.45	TDA2532 1.95
LA4400 4.15	SL501B 4.35	TA7313 2.95	TBA720AQ 2.45	TDA2540 2.15
LC7120 3.50	SL917B 6.25	TAA310A 2.15	TBA750 1.85	TDA2541 2.15
LC7130 3.50	SL918A 6.00	TAA320A 2.00	TBA800 0.89	TDA2560 2.15
LC7131 5.50	SL1310 1.80	TAA370A 2.50	TBA810AS 1.35	TDA2581 1.15
LC7137 5.50	SL1327 1.10	TAA470 3.50	TBA810S 1.35	TDA2590 2.95
M51613L 2.30	SL1327Q 1.10	TAA550 0.25	TBA820 2.45	TDA2591 2.95
M51615L 2.95	SL1431 1.37	TAA570 1.80	TBA890 2.45	TDA2593 2.95
MB3712 2.00	SL3046 0.95	TAA621AX1 3.00	TBA920 1.65	TDA2600 2.95
MC1307P 1.00	SL76544 2.05	TAA630S 3.15	TBA920Q 1.65	TDA2611A 1.95
MC1327 0.95	SN16848N 1.00	TAA661B 1.20	TBA950/ZX 2.35	TDA2640 2.60
MC1330P 0.78	SN16861AN 1.00	TAA700 1.70	TBA990 1.49	TDA2650 2.15
MC1348P 1.20	SN7603N 1.65	TBA120A 0.70	TBA990Q 1.49	TDA2653 2.15
MC1349P 1.20	SN7603N 1.65	TBA120AS 0.70	TBA100 1.30	TDA2658 2.15
MC1351P 1.50	SN7603N 1.65	TBA120B 0.70	TCA270 1.10	TDA2690 1.35
MC1352P 1.00	SN7603N 1.65	TBA120S 0.70	TCA270S 1.10	TDA3950 2.50
MC1357 2.35	SN76110N 0.89	TBA120SB 0.70	TCA270SQ 1.10	TDA9503 3.95
MC1495 3.00	SN76115N 1.25	TBA120SO 0.70	TCA640 2.50	UPC1185H 3.95
MC14011BCP	SN76131N 1.30	TBA120T 0.70	TCA650 2.50	UPC3568H3 2.95
	SN76260N 1.55	TBA120U 1.00	TCA800 2.15	UPC3575C2 2.95
ML231B 1.75	SN76227N 1.05	TBA395 1.50	TCA830S 1.40	UPC1001H 2.50
ML232B 1.75	SN76532N 1.40	TBA396 0.75	TCA940 1.85	UPC1025H 2.50
ML237B 1.95	SN76533N 1.30	TBA440N 2.55	TCEP100 1.95	UPC1156H 2.95
ML238B 4.20	SN76544N 1.30	TBA480Q 1.25	TDA440 2.20	UPC1182H 2.95
ML239B 4.20	SN76650N 1.05	TBA510 1.65	TDA1002 1.25	UPC1350C 2.95
ML320 4.12	SN76670N 1.00	TBA510Q 1.65	TDA1004A 1.10	UPC1420H 1.95
ML322 2.28	SN76620N 0.95	TBA520 1.10	TDA1006A 2.50	ZTK33B 0.37
ML328 1.65	SN76650N 0.95	TBA520Q 1.10	TDA1010 2.15	555 0.35
MSM5807 6.75	SN76651N 1.50	TBA530 1.10	TDA1054 0.90	741 0.35

SEMICONDUCTORS

AC126 0.22	BC158 0.09	BD139 0.32	BF336 0.34	R2323 0.66
AC127 0.20	BC159 0.09	BD140 0.30	BF337 0.29	R2540 2.48
AC128 0.20	BC160 0.28	BD159 0.65	BF338 0.32	RCA1633A 0.90
AC128K 0.32	BC161 0.28	BD166 0.46	BF355 0.37	RCAP1635 0.80
AC141K 0.34	BC170B 0.10	BD179 0.72	BF362 0.38	TP29 0.40
AC142K 0.30	BC171 0.08	BD182 0.70	BF363 0.31	TIP29C 0.42
AC176 0.22	BC171B 0.10	BD201 0.80	BF371 0.30	TIP47 0.43
AC176K 0.31	BC172B 0.10	BD202 0.65	BF384 0.19	TIP31C 0.42
AC187 0.25	BC173B 0.10	BD203 0.78	BF457 0.23	TIP32C 0.42
AC187K 0.28	BC174 0.09	BD204 0.70	BF458 0.23	TIP33B 0.75
AC188 0.22	BC182 0.09	BD222 0.46	BF459 0.23	TP41C 0.45
AC188K 0.37	BC182LB 0.10	BD223 0.48	BF595 0.26	TIP42C 0.47
AD142 0.90	BC183 0.12	BD225 0.48	BF597 0.25	TIP47 0.65
AD143 0.82	BC183L 0.09	BD233 0.35	BF639 0.23	TIP120 0.60
AD149 0.70	BC184LB 0.09	BD234 0.35	BF641 0.28	TIP122 0.79
AD161 0.39	BC204 0.18	BD236 0.45	BF742 0.28	TIP161 2.95
AD161/2 0.30	BC208B 0.13	BD237 0.30	BF792 0.85	TIP255 0.84
AF124 0.32	BC212 0.09	BD238 0.33	BFX29 0.30	TIP3055 0.66
AF125 0.32	BC212L 0.09	BD410 0.55	BFX84 0.26	TIS91 0.20
AF126 0.32	BC213 0.09	BD437 0.50	BFX86 0.30	2N2219 0.28
AF127 0.32	BC213L 0.09	BD517 0.60	BFX88 0.25	2N2905 0.48
AF139 0.42	BC227 0.09	BD520 0.65	BFY50 0.21	2N3054 0.59
AF150 0.42	BC251a 0.12	BDX32 1.50	BFY51 0.21	2N3055 0.52
AF239 0.42	BC252A 0.15	BF115 0.35	BFY52 0.25	2N3702 0.12
AU106 0.06	BC258A 0.39	BF178 0.26	BFY90 0.27	2N3703 0.12
AU107 1.75	BC300 0.30	BF179 0.34	BR100 0.19	2N3704 0.12
AU110 2.00	BC301 0.30	BF180 0.29	BR101 0.30	2N3705 0.12
AU113 1.48	BC303 0.26	BF182 0.29	BRC4443 0.85	2N3706 0.12
BC107 0.10	BC307 0.09	BF183 0.29	BT106 1.00	2N3708 0.12
BC107A 0.10	BC327 0.10	BF184 0.28	BT108 1.22	2N5294 0.38
BC107B 0.10	BC337 0.10	BF185 0.28	BU116 1.20	2N5296 0.48
BC108 0.10	BC338 0.09	BF191 0.11	BU108 1.69	2N5298 0.52
BC108A 0.10	BC347 0.20	BF192 0.11	BU124 1.00	2N5496 0.66
BC108B 0.10	BC347B 0.10	BF193 0.11	BU126 1.22	2SC496 0.80
BC109 0.10	BC348 0.10	BF194 0.11	BU204 1.55	2SC1096 0.80
BC109B 0.10	BC348A 0.08	BF195 0.11	BU208A 1.52	2SC1097 0.80
BC114 0.11	BC350 0.07	BF196 0.11	BU208B/02 1.89	2SC1173 1.15
BC116A 0.12	BC355 0.07	BF197 0.11	BU326A 1.42	2SC1306 1.25
BC119 0.24	BC357B 0.07	BF198 0.10	BU407 1.24	2SC1307 1.85
BC125 0.12	BC358 0.07	BF199 0.10	BUJ500 1.75	2SC1449 0.80
BC140 0.31	BD115 0.30	BF200 0.30	MJ100 1.99	2SC1678 1.25
BC141 0.25	BD116 0.52	BF201 0.30	MJE340 0.40	2SC1945 2.10
BC142 0.21	BD131 0.32	BF256 0.28	MJE520 0.48	2SC1953 0.95
BC143 0.24	BD132 0.35	BF257 0.28	MRF450A 11.50	2SC1957 0.80
BC143A 0.09	BD133 0.40	BF258 0.25	MRF453 13.50	2SC1969 1.95
BC148A 0.09	BD135 0.30	BF259 0.25	MRF477 10.00	2SC2028 1.15
BC148B 0.09	BD136 0.30	BF260 0.25	MRF478 10.00	2SC2030 1.60
BC149 0.09	BD137 0.26	BF261 0.26	R2008B 1.70	2SC2078 1.45
BC157 0.10	BD138 0.30	BF273 0.13	R2010B 1.70	2SC2091 0.85
			R2322 0.58	2SC2314 0.80
				3N211 1.50

DIODES

AA119 0.08	BY126 0.10	BYX36-150R 0.20	IN4001 0.04	IN5405 0.13
BA102 0.17	BY127 0.11	BYX38-600R 0.60	IN4002 0.04	IN5406 0.13
BA115 0.13	BY133 0.15	BYX55-600 0.30	IN4003 0.04	IN5407 0.18
BA145 0.16	BY176 1.20	BYX71-600 0.60	IN4004 0.05	IN5408 0.16
BA148 0.17	BY179 0.63	OA47 0.09	IN4005 0.05	ITT44 0.04
BA154 0.06	BY208-800 0.33	OA90 0.05	IN4006 0.05	ITT827 0.49
BA155 0.13	BY210-800 0.33	OA91 0.06	IN4007 0.06	ITT921 0.08
BA156 0.15	BY223 0.90	OA95 0.06	IN4148 0.02	ITT923 0.15
BAX13 0.64	BY298-400 0.22	OA202 0.10	IN4448 0.10	ITT2002 0.11
BB105B 0.30	BY299-800 0.22	IN60 0.06	IN5401 0.12	
	YX10 0.20	IN914 0.04	IN5402 0.12	
			IN5403 0.12	
			IN5404 0.12	

WIREWOUND RESISTORS

4 Watt	PREFERRED VALUES	
	4R7-1K6	0.13
	2K2-6K8	0.16
	10K	0.22
7 Watt	R47-4K7	0.14
	5K6-12K	0.15
	15K-22K	0.18
11 Watt	1R-10K	0.18
	15K	0.21
17 Watt	1R-10K	0.24
	15K-22K	0.25

BASES ETC.

B7G 0.15
B7G Skirted 0.30
B8G 0.70
B9A 0.20
B9A Skirted 0.30
B10B 0.18
B13B 0.50
8 Pin DIL 0.10
14 Pin DIL 0.12
14 Pin DIL/Q 0.30
16 Pin DIL 0.15
OCTAL 0.35
CANS 0.27

ZENER DIODES

BZX61 0.15
6V2 7V5 8V2 9V1 10V 11V 12V 13V 15V 16V 18V 20V 22V 24V 27V 30V 33V 36V 39V 47V
BZY88 0.07
2V7 3V 3V3 3V6 3V9 4V3 4V7 5V1 5V6 6V2 6V8 7V5 8V2 9V1 10V 11V 12V 13V 15V 18V 24V 27V
THERMISTORS
VA1040 0.23
VA1056S 0.23
VA1104 0.70
VA8650 0.45
BATTERIES
7V Power Mike batteries
TR175 £1.40 ea other prices on request

PHONE
0474 813225
3 LINES

P.M. COMPONENTS LTD

SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
965966
WEST ST G



A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 14.50	E180F 5.25	EL81 2.75	KTW63 1.50	PL82 0.80	TB2.300 45.00	Z66 1.00	6/30L2 0.70	6F14 1.00	10P14 2.50	57 0.85
A1998 11.50	E186F 8.50	EL82 0.58	KTZ41 2.00	PL83 0.52	TD1-100 29.00	Z77 1.20	6A/203K 9.00	6F15 1.00	10LD11 1.00	6063 2.00
A2087 11.50	E235L 11.00	EL84 0.66	KTZ63 1.25	PL84 0.65	TD3-10F 18.00	Z300T 5.00	6A6 1.50	6F17 1.00	10LD12 0.85	6096 2.85
A2134 14.50	E238L 8.00	EL85 3.85	KY50 0.68	PL88 1.00	TD3-12 4.00	Z303C 9.00	6A8G 1.50	6F18 1.50	10Y 6.00	75B1 1.50
A2293 7.20	E280F 19.50	EL86 0.80	KY80 0.90	PL95 1.00	TP25 1.50	Z502C 12.00	6A87 0.80	6F19 0.48	11E2 16.50	75C1 1.20
A2426 22.50	E283CC 8.25	EL90 0.82	L63 1.00	PL302 1.00	TT11 1.50	Z504S 13.50	6A88 0.86	6F21 2.50	11E3 55.00	80 1.50
A2521 19.00	E810F 12.50	EL91 6.00	L77 0.60	PL345 12.50	TT21 19.50	Z749 0.48	6A92 1.00	6F22 0.48	12A4 2.50	83A1 7.00
A2599 37.50	E2134 12.00	EL95 0.70	L2319 0.85	PL500 1.12	TY2-12 14.75	Z759 16.00	6AFA4 1.20	6F23 2.48	12A6 0.80	84 0.85
A2900 19.00	EA50 1.00	EL96 6.00	L2329 0.65	PL504 1.20	TY2-12SA 45.00	Z800U 4.00	6AG7 1.20	6F24 1.25	12AD6 0.80	85A1 5.40
AC/HL/DD 3.00	EAF76 2.00	EL360 9.00	L2339 0.65	PL508 1.75	TY3-250 45.00	Z801U 4.00	6AH6 1.00	6F25 1.25	12AE6 0.85	85A2 2.00
AC/THI 2.515	EAA91 0.80	EL504 1.40	L2359 0.40	PL509 3.15	TY3-250 45.00	Z803U 13.50	6AU7 1.20	6F26 1.00	12AG8 1.50	89 1.20
AC/PEN 3.50	EAA901S 1.50	EL519 4.50	L2372A 135.00	PL519 3.15	TYF50 60.00	Z803U 13.50	6A85 2.00	6F28 1.25	12AH7GT 0.85	90AV 10.00
AC/SP3 4.50	EABC80 0.56	EL821 10.00	M537A 160.00	PL820 3.00	TY4-500A 60.00	Z7014 9.00	6AK6 2.00	6F29 19.00	12AH8 5.50	90C1 2.10
ACP 3.00	EAC91 0.90	EL822 10.00	M8079 6.00	PL806 2.95	TY7-6000A 315.00	ZA101 5.00	6AL5 0.52	6F30 1.00	12AL5 1.00	90CG 10.85
ACVP1 3.50	EAF42 1.40	EL222 2.50	M8083 3.25	PL820 3.00	TY8-600W 315.00	ZA1000 9.00	6AM6 3.00	6F31 1.00	12AT6 0.59	91AG 10.00
ACVP2 1.50	EAF801 1.40	EM1 4.00	M8091 7.50	PL806 2.95	TY8-600W 315.00	ZA1002 1.48	6AM5 6.00	6F32 1.00	12AT7 2.55	92AG 10.00
AH201 4.00	EB94 1.50	EM4 9.00	M8096 3.00	PL806 2.95	TY8-600W 315.00	ZC1040 8.00	6AM6 3.00	6F33 1.00	12AT7WA 2.50	92AV 10.00
AH221 39.00	EB41 2.30	EM34 11.00	M8137 5.00	PL806 2.95	TY8-600W 315.00	ZM1001 5.00	6AM6 3.00	6F34 1.00	12AU6 0.80	9507 3.00
AH238 31.50	EB91 0.52	EM80 0.70	M8137 5.00	PL806 2.95	TY8-600W 315.00	ZM1002 4.00	6AM6 3.00	6F35 1.00	12AV6 0.90	150C4 1.50
AP4 1.50	EB2C1 1.50	EM81 0.70	M8162 3.85	PL806 2.95	TY8-600W 315.00	ZM1021 8.00	6A05 0.82	6F36 1.00	12AX4GT 1.00	150CV 25.00
APV4 1.50	EB3C3 2.00	EM84 0.70	M8162 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F37 1.00	12AX7 0.60	155UG 15.00
AR 0.70	EB4C1 0.85	EM85 0.85	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F38 1.00	12AX7WA 2.50	18B5T 1.50
ARF12 0.70	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F39 1.00	12AY7 4.00	257A 6.00
ARF34 1.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F40 1.00	12AZ7A 1.50	325 5.00
ARF35 1.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F41 1.00	12BA6 0.75	408A 4.00
ARF37 1.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F42 1.00	12BA6 0.75	431U 2.00
AV3 1.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F43 1.00	12BA6 0.75	708A 5.00
AU13 1.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F44 1.00	12BA6 0.75	715A 6.00
AX224 12.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F45 1.00	12BA6 0.75	801A 15.50
AZ31 1.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F46 1.00	12BA6 0.75	803A 16.00
B2A 6.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F47 1.00	12BA6 0.75	807 1.50
B36 1.85	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F48 1.00	12BA6 0.75	808 3.00
B36 1.85	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F49 1.00	12BA6 0.75	811A 9.00
B45 0.69	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F50 1.00	12BA6 0.75	813 18.50
B89 0.75	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F51 1.00	12BA6 0.75	833A 115.00
B719 1.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F52 1.00	12BA6 0.75	836 7.00
B729 1.20	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F53 1.00	12BA6 0.75	845 8.00
BL63 1.20	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F54 1.00	12BA6 0.75	866A 3.00
BT58 43.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F55 1.00	12BA6 0.75	868 5.00
BT17A 95.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F56 1.00	12BA6 0.75	885 2.00
BT19 32.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F57 1.00	12BA6 0.75	954 0.50
BT79 12.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F58 1.00	12BA6 0.75	958A 0.90
CA 7.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F59 1.00	12BA6 0.75	1027 7.00
CA3A 10.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F60 1.00	12BA6 0.75	1029A 0.80
C143 18.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F61 1.00	12BA6 0.75	1027 7.00
C180 18.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F62 1.00	12BA6 0.75	1029A 0.80
C1108 30.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F63 1.00	12BA6 0.75	1027 7.00
C1111 15.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F64 1.00	12BA6 0.75	1027 7.00
C1112 52.15	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F65 1.00	12BA6 0.75	1027 7.00
C1134 15.50	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F66 1.00	12BA6 0.75	1027 7.00
CCB1 2.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F67 1.00	12BA6 0.75	1027 7.00
CCA 2.80	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F68 1.00	12BA6 0.75	1027 7.00
CL30 1.05	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F69 1.00	12BA6 0.75	1027 7.00
CMG25 9.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F70 1.00	12BA6 0.75	1027 7.00
CMG29 1.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F71 1.00	12BA6 0.75	1027 7.00
CMV25 10.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F72 1.00	12BA6 0.75	1027 7.00
CV Nos prices on request	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F73 1.00	12BA6 0.75	1027 7.00
D3a 35.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F74 1.00	12BA6 0.75	1027 7.00
D63 0.60	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F75 1.00	12BA6 0.75	1027 7.00
DA107 6.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F76 1.00	12BA6 0.75	1027 7.00
DAC32 1.20	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F77 1.00	12BA6 0.75	1027 7.00
DAF91 0.45	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F78 1.00	12BA6 0.75	1027 7.00
DAF96 0.85	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F79 1.00	12BA6 0.75	1027 7.00
DC70 1.75	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F80 1.00	12BA6 0.75	1027 7.00
DC90 1.20	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F81 1.00	12BA6 0.75	1027 7.00
DCX4-1000 35.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F82 1.00	12BA6 0.75	1027 7.00
DD620 1.20	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F83 1.00	12BA6 0.75	1027 7.00
DR3 1.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F84 1.00	12BA6 0.75	1027 7.00
DDT 3.00	EB37 1.10	EM86 0.70	M8190 3.85	PL806 2.95	TY8-600W 315.00	ZM1023 6.00	6A05 0.82	6F85 1.00	12BA6 0.75	1027 7


RETAIL SALES
AND DEMONSTRATIONS

404 EDGWARE RD. LONDON, W2 1ED TEL: 01-402 6822

TANGERINE • TANGERINE • TANGERINE • TANGERINE • TANGERINE

MICROTAN 65

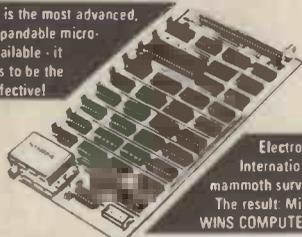MICROTAN 65 is the most advanced, powerful, expandable micro-computer available - it also happens to be the most cost effective!



Electronic Today International held a mammoth survey of kits. The result: Microtan 65 WINS COMPUTER CLASS!

MICROTAN 65 CONTENTS

High quality, plated thru hole printed circuit board, solder resist and silk screened component identification 6502 microprocessor 1K monitor TANBUG Now with V Bug 1K RAM for user programme, stack and display memory VDU alphanumeric display of 16 rows by 32 characters MICROTAN 65 system file binder 136 page, bound, users hardware / software manual with constructional details and sample programmes Logic and discrete components to fully expand MICROTAN 65

KIT FORM £69.00 + V.A.T.

MICROTAN 65 assembled and tested.

Specification as above, but assembled and fully bench tested by ourselves

£79.00 + £11.85 V.A.T., total £90.85

TANBUG V2.3 Kit **£21.85** incl.

POWER SUPPLIES

Input 240V AC, Output 5 Volts at 3 Amps Regulated. Will power both MICROTAN and TANEX fully expanded. Built on the same size printed circuit board as MICROTAN etc Available as a fully built and tested unit

£23.00 + V.A.T. £3.45, total £26.45

X MPSZ +5V 6A, +12V, -5 and -12V switch mode system PSU

£69.13 + V.A.T

71 KEY ASCII KEYBOARD £56.34 + V.A.T

NO EXTRAS NEEDED

Uses gold crosspoint keys Includes numeric keypad and ribbon cable

Available as fully assembled and tested

SUPER METAL CABINET IN TANGERINE / BLACK

£20.00 + V.A.T. £3.00, total £23.00



NEW PRODUCTS (all V.A.T. incl.)

SYSTEM MOTHERBOARD (4 CONNECTOR)	£44.25
SYSTEM MOTHERBOARD (12 CONNECTOR)	£72.55
EXTRA EDGE CONNECTIONS	£3.50
SYSTEM RACK FRONT PANEL	£15.64
SERIAL I/O BOARD MIN. (2 PORTS)	£86.70

**SEND FOR
FREE BROCHURE**

FULL MANUALS: MICROTAN,
TANEX, BASIC, X BUG
All £5 each

TANRAM

AVAILABLE NOW TANRAM - 40K Bytes on one board! Single board of bulk memory offering 7K Static RAM (2114), and 32K Dynamic RAM (4116) Onboard refresh is totally transparent to CPU operation and is unaffected by normal DMA's TANRAM fully expands the available address space of the 6502 microprocessor MICROTAN, TANEX and TANRAM together provide 16K RAM, 48K RAM and 1K I/O - that's a lot of memory and a lot of I/O! Built and tested TANRAM ASSEMBLED



40K RAM CARD with 16K DYNAMIC RAM £76 + V.A.T

CONTENTS High quality plated thru hole printed circuit board, solder resist and silk screened component identification Full complement of I.C sockets for maximum expansion 64 way DIN edge connector 1K RAM (2114) Data bus buffering TANRAM users manual.

EXTRA RAM:

1K STATIC (2114) £2.95 each 16K DYNAMIC (4116) £1.50 each

MEMORIES EXPAND YOUR SYSTEM WITH OUR TANGERINE APPROVED CHIPS

Discounts 10% for 4, 15% for 8, 20% for 16	
2102 1K x 1 Static RAM 80p	IM 6402 UART £4.50
2708 £3.50	2114 1K x 4 Static RAM £2.95
2716 £6.50	4118 1K x 8 Static RAM £7.50
MK 4116 16K x 1 Dynamic RAM	
£1.50	All Including VAT

MONITORS (PROFESSIONAL)

RECONDITIONED AND NEW - FROM £35.00 to **£129.95**

CENTRONICS Ideal for Tangerine PRINTERS

SHEIKOSHA £199 + VAT

Model 730 **£350 + V.A.T**

Model 737 **£395 + V.A.T**



NEW MICROTANTEL

POST OFFICE APPROVED

PRESTEL - VIEWDATA

• FULL COLOUR GRAPHICS • MICROTAN OWNERS CAN COMMUNICATE WITH EACH OTHER • CAN STORE PRESTEL • CAN BE USED AS AN EDITING TERMINAL • CAN BE INTERFACED WITH PET, APPLE AND NASCOM

Just connect to the aerial socket of any colour or black and white domestic T.V. receiver and to your Post Office installed jack socket and you are into the exciting world of PRESTEL. Via simple push button use you are able to view 170,000 pages of up to the minute information on many services, order goods from companies - all this without leaving your armchair!



£170
+ V.A.T

TANEX £43.00

Minimum
Config Kit

+ V.A.T £6.45, total £49.45

CONTENTS

High quality plated thru hole printed circuit board, solder resist and silk screened component identification I.C sockets for maximum expansion 64 Way DIN edge connector 1K RAM, cassette interface, 16 parallel I/O lines, a TTL serial I/O port, two 16 bit counter timers, data bus buffering, memory mapping, logic and discrete components for maximum expansion TANEX users manual

TANEX (Minimum configuration) Assembled

£53.00 + V.A.T £7.95, total £60.95



TANEX EXPANSION

Expanded TANEX offers 7K RAM, locations for 4K EPROM (2716).

locations for 10K extended

MICROSOFT BASIC, 32 parallel I/O

lines, two TTL serial I/O ports, a

third serial I/O port with

RS232/20mA loop, full modem

control and 16 programmable baud

rates, four 16 bit counter timers,

cassette interface, data bus

buffering, and memory mapping

EXPANDED TANEX KIT (Excludes ROM, XBUG and BASIC)

£89.70 + V.A.T £13.46, total £103.16

EXPANDED TANEX ASSEMBLED

£99.70 + V.A.T £14.96, total £114.66

OPTIONS TO FULLY EXPANDED TANEX

10K Extended MICROSOFT BASIC in EPROM (with manual)

£49.00 + V.A.T £7.35, total £56.35

Extra RAM 1K (2 x 2114) **£5.20 + V.A.T 78p, total £5.98**

SERIAL I/O KIT **£10.26 + V.A.T £1.60, total £11.80**

6522 VIA **£8.00 + V.A.T £1.20, total £9.20**

XBUG **£17.35 + V.A.T £2.60, total £19.95**

± 12v KIT **£9.20** incl.

ADD-ON KEYPAD

A compact 12 button keypad suitable for use with keyboard to extend its functions plus four extra keys. Supplied brand new with with data. A 3 x 4 non-encoded single mode keyboard in sloped format



LIST PRICE
£22.00
OUR PRICE
£7.95
- V.A.T

PROFESSIONAL ASCII KEYBOARDS

Ideal for

Tangerine

£29.95 - V.A.T

• 52 key 7 bit ASCII coded

• Positive strobe +5V-12V

• Full ASCII characters

• Parallel output with strobe

• Power light on control

• Chip by General Instrument

(G1) TTL output



- Superbly made
- Size 13 x 5.5 x 1.5 ins.
- Black keys with white ledgens
- Escape shift return & reset keys
- Control repeat & bell
- Complete with DATA

TANGERINE • TANGERINE • TANGERINE

FULLY GUARANTEED - BUY WITH CONFIDENCE
BRITISH DESIGN & MANUFACTURE AND ON DEMONSTRATION
IN OUR COMPUTER DEPT.

All orders pre-paid and official advertised here to be forwarded DIRECTLY to
COMPUTER DEPT., 11/12 PADDINGTON GREEN, LONDON W2

HYDRAULIC DRIVE

USING SELF-CONTAINED HYDRAULIC POWER PACK

FEEDBACK

CLOSED LOOP CONTROL SYSTEM

ROBOTS FROM POWERTRAN

MICROPROCESSOR CONTROLLED

USING DEDICATED SYSTEM OR EXTERNAL COMPUTER VIA ON-BOARD RS232C INTERFACE
UP TO SIX PROGRAMMABLE AXES
READY-BUILT OR KITS FROM £355

CURRENTLY BEING PUBLISHED IN

PRACTICAL ELECTRONICS

For further details please contact:
POWERTRAN CYBERNETICS
PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3MM
Tel. Andover (0264) 64455



Digital Accuracy, Effortless Convenience:



Calorimetric
MODULOAD® System
from 1kW to 50kW
RF Power

Terminate and measure RF Power
up to 50,000 watts from AM and FM

through VHF and UHF frequencies in 1/8", 3/8" or 6/8" coax lines.
Three models cover 1-10kW, 1-25kW and 1-50kW ranges with calorimetric accuracy of ± 2 1/2% of Indication (above 5kW).

Self-cooled MODULOAD Termination assures low SWR in 50-ohm lines, can be permanently mounted — or wheeled in place on dolly.


To measure power, push a button, wait briefly to stabilize, zero the display and apply RF!

Can be used to calibrate or check other meters. Detailed specs in CalMOD Bulletin. Ask for it

Who else but
BIRD

Aspen Electronics Limited
YOUR EXCLUSIVE U.K. REPRESENTATIVE

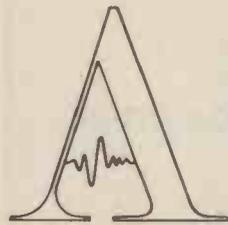2/3 Kildare Close, Eastcote,
Ruislip, Middlesex HA4 9UR
Telephone: 01-868 1188
Telex: 8812727
FAX: 01-866 6596



WW - 075 FOR FURTHER DETAILS

ILP TOROIDALS UNBEATABLE VALUE FOR MONEY!

New production capacity at Canterbury has increased our range, decreased our prices, improved our special customer design service. Choose from toroidal transformers in a range of 98 types.

Order using
the FREEPOST
coupon below.

Trade enquiries are welcome.

Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. GUARANTEED 5 YEARS.

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE inc VAT	PRICE ex VAT
30 VA 70 x 30mm 0.45 Kg Regulation 18%	1X010	6+6	2.50	£5.28 P/P	£4.40 +0.870 P/P
	1X011	9+9	1.66		
	1X012	12+12	1.25		
	1X013	15+15	1.00		
	1X014	18+18	0.83		
	1X015	22+22	0.68		
	1X016	25+25	0.60		
50 VA 80 x 35mm 0.9 Kg Regulation 13%	2X010	6+6	4.16	£5.83 P/P	£4.93 +£1.10 P/P
	2X011	9+9	2.77		
	2X012	12+12	2.08		
	2X013	15+15	1.66		
	2X014	18+18	1.38		
	2X015	22+22	1.13		
	2X016	25+25	1.00		
80 VA 90 x 30mm 1 Kg Regulation 12%	3X010	6+6	6.64	£6.51 P/P	£5.47 +£1.43 P/P
	3X011	9+9	4.44		
	3X012	12+12	3.33		
	3X013	15+15	2.66		
	3X014	18+18	2.22		
	3X015	22+22	1.81		
	3X016	25+25	1.60		
120 VA 90 x 40mm 1.2 Kg Regulation 11%	4X010	6+6	10.00	£7.55 P/P	£6.38 +£1.43 P/P
	4X011	9+9	6.66		
	4X012	12+12	5.00		
	4X013	15+15	4.00		
	4X014	18+18	3.33		
	4X015	22+22	2.72		
	4X016	25+25	2.40		
160 VA 110 x 40mm 1.8 Kg Regulation 8%	5X011	9+9	8.89	£9.92 P/P	£8.44 +£1.43 P/P
	5X012	12+12	6.66		
	5X013	15+15	5.33		
	5X014	18+18	4.44		
	5X015	22+22	3.63		
	5X016	25+25	3.20		
	5X017	30+30	2.66		
225 VA 110 x 45mm 2.2 Kg Regulation 7%	6X010	6+6	16.66		
	6X011	9+9	11.11		
	6X012	12+12	8.33		
	6X013	15+15	6.67		
	6X014	18+18	5.56		
	6X015	22+22	4.55		
	6X016	25+25	4.00		
300 VA 110 x 50mm 2.6 Kg Regulation 6%	7X010	6+6	26.66		
	7X011	9+9	17.78		
	7X012	12+12	13.33		
	7X013	15+15	10.67		
	7X014	18+18	8.89		
	7X015	22+22	7.27		
	7X016	25+25	6.40		
500 VA 140 x 60mm 4 Kg Regulation 4%	8X010	6+6	40.00		
	8X011	9+9	26.66		
	8X012	12+12	20.00		
	8X013	15+15	16.00		
	8X014	18+18	13.33		
	8X015	22+22	11.11		
	8X016	25+25	10.00		
625 VA 140 x 75mm 5 Kg Regulation 4%	9X010	6+6	62.50		
	9X011	9+9	41.66		
	9X012	12+12	31.25		
	9X013	15+15	25.00		
	9X014	18+18	20.83		
	9X015	22+22	17.19		
	9X016	25+25	15.62		

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE inc VAT	PRICE ex VAT
225 VA 110 x 45mm 2.2 Kg Regulation 7%	6X017	30+30	3.75		
	6X018	35+35	3.21		
	6X025	45+45	2.50		
	6X033	50+50	2.25		
	6X028	110	2.04		
	6X029	220	1.02		
	6X030	240	0.93		
300 VA 110 x 50mm 2.6 Kg Regulation 6%	7X017	30+30	3.75		
	7X018	35+35	4.28		
	7X026	40+40	3.75		
	7X025	45+45	3.33		
	7X033	50+50	3.00		
	7X028	110	2.72		
	7X029	220	1.36		
500 VA 140 x 60mm 4 Kg Regulation 4%	8X017	30+30	8.33		
	8X018	35+35	7.14		
	8X026	40+40	6.25		
	8X025	45+45	5.55		
	8X033	50+50	5.00		
	8X042	55+55	4.54		
	8X028	110	5.4		
625 VA 140 x 75mm 5 Kg Regulation 4%	9X017	30+30	10.41		
	9X018	35+35	8.92		
	9X026	40+40	7.81		
	9X025	45+45	6.94		
	9X033	50+50	6.25		
	9X042	55+55	5.68		
	9X028	110	5.68		

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovalve, Mapin, Marshalls, Technomatic and Watford Electronics.

Please send me the following

ILP modules

Total purchase price

I enclose Cheque

Postal Orders

Int. Money Order

Please debit my Access/Barclaycard No. _____


Name _____

Address _____

Signature _____

WW 1/4

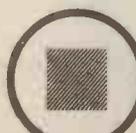Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone (0227) 54778 Technical (0227) 64723; Telex 965780.



ILP
TRANSFORMERS

(a division of
ILP Electronics Ltd)

STAY AHEAD. STAY WITH US

PRINTED CIRCUITS

FOR WIRELESS WORLD PROJECTS

Stripline r.t. power amp—Sept. 1975—1 d.s.	£5.00
Audio compressor/limiter—Dec. 1975—1 s.s. (stereo)	£4.25
F.m. tuner (advanced)—April 1976—1 s.s.	£5.00
Cassette recorder—May 1976—1 s.s.	£5.00
Audio compander—July 1976—1 s.s.	£4.25
Time code clock—August 1976—2 s.s. 3 d.s.	£15.00
Date, alarm, b.s.t. switch—June 1977—2 d.s. 1 s.s.	£9.50
Audio preamplifier—November 1976—2 s.s.	£8.50
Additional circuits—October 1977—1 s.s.	£4.00
Stereo coder—April 1977—1 d.s. 2 s.s.	£8.50
Morse keyboard and memory—January 1977—2 d.s. (logic board 10 1/4 in. x 5 in.) (keyboard and matrix 13 in. x 10 in.)	£14.00
Low distortion disc amplifier (stereo)—September 1977—1 s.s.	£2.00
Low distortion audio oscillator—September 1977—1 s.s.	£3.50
Synthesized f.m. transceiver—November 1977—2 d.s. 1 s.s.	£12.00
Morsemaker—June 1978—1 d.s.	£4.50
Metal detector—July 1978—1 d.s.	£3.75
Oscilloscope waveform store—October 1978—4 d.s.	£18.00
Regulator for car alternator—August 1978—1 s.s.	£2.00
Wideband noise reducer—November 1978—1 d.s.	£5.00
Versatile noise generator—January 1979—1 s.s.	£5.00
200MHz frequency meter—January 1979—1 d.s.	£7.00
High performance preamplifier—February 1979—1 s.s.	£5.50
Distortion meter and oscillator—July 1979—2 s.s.	£5.50
Moving coil preamplifier—August 1979—1 s.s.	£3.50
Multi-mode transceiver—October 1979—10 d.s.	£35.00
Amplification system—Oct. 1979—3 preamp 1 poweramp	£4.20 each
Digital capacitance meter—April 1980—2 s.s.	£7.50
Colour graphics system—April 1980—1 d.s.	£18.50
Audio spectrum analyser—May 1980—3 s.s.	£10.50
Multi-section equalizer—June 1980—2 s.s.	£8.00
Floating-bridge power amp—Oct. 1980—1 s.s. (12V or 40V)	£4.00
Nanocomp—Jan. 1981—1 d.s. 1 s.s.	£9.00
Logic probe—Feb. 1981—2 d.s.	£6.00
Modular frequency counters—March 1981—8 s.s.	£20.00
Opto-electronic contact breaker (Delco)—April 1981—2 s.s.	£4.00

Boards are glassfibre, roller-tinned and drilled. Prices include V.A.T. and U.K. postage.
Airmail add 20%, Europe add 10%, Insurance 10%.
Remittance with order to:
M. R. SAGIN, 23 KEYES ROAD, LONDON, N.W.2

WW - 009 FOR FURTHER DETAILS

WW - 079 FOR FURTHER DETAILS

VALVES			Minimum Order £1	VALVES VAT IS INCLUDED							
A1065	1.40	EL509	3.95	QV03-12	4.20	6AM5	0.70	12AT6	0.70	6067	2.30
AZ293	8.80	EL802	1.70	SC1/400	4.50	6AM6	1.50	12AT7	0.65	6080	5.30
A2900	9.20	EL821	8.20	SC1/600	4.50	6AN8A	2.50	12AU7	0.60	6146	4.95
AR8	0.75	EL822	9.95	SP61	1.80	6A04	3.40	12AV6	0.95	6146B	5.20
ARF3	0.70	EM80	0.85	TT21	17.50	6A05	1.00	12AX7	0.65	6360	2.85
AT74	0.80	EM87	1.30	U25	1.15	6A05W	1.90	12BA6	0.90	6550	6.80
B12H	3.90	EY51	0.95	U26	1.15	6AS6	1.15	12BE6	1.25	6870	14.00
CY31	1.40	EY81	0.65	U27	1.15	6AT6	0.90	12BH7	1.65	8552	8.20
DAF96	0.70	EY96/87	0.60	U191	0.85	6AU6	0.60	12C8	0.65	7199	2.85
DET22	26.95	EY88	0.65	U281	0.70	6AV6	0.85	12E1	18.95	38P1	11.00
DF96	0.70	EZ80	0.70	U301	0.65	6AX4GT	1.30	12J5GT	0.55	5FP7	18.00
DH76	0.75	EZ81	0.70	U600	11.50	6AX5GT	1.30	12K7GT	0.70	4EP1	32.00
DL32	0.60	GM4	5.90	U801	0.90	6BA6	0.55	12K8GT	0.60	88L	14.00
DY86/87	0.65	GY501	1.30	UBCA1	1.20	6BE6	1.60	12Q7GT	0.60	88L	14.00
DY802	0.70	GZ32	1.05	UABC80	0.75	6BG6G	0.60	12SC7	0.65	CV1526	16.00
E55L	14.90	GZ33	4.20	UAF42	1.20	6BJ6	1.30	12SH7	0.65	DG7-32	34.80
E88CC	1.60	GZ34	2.75	UBF80	0.70	6BQ7A	0.85	12SJ7	0.70	DG7-36	36.00
E88CC/01	3.10	GZ37	3.95	UBF89	0.70	6BR7	4.80	12S07	1.45	DPM9-11	38.40
E92CC	1.20	KT66	6.30	UBL21	1.75	6BW6	6.20	12SQ7GT	0.85	D13-33GM	
E180CC	0.80	9.20*	UCC84	0.85	6BW7	0.90	12Y4	0.70			
E190F	6.30	KT88	8.95	UCC85	0.70	6C4	0.50	13D3	0.70	*spec Q	41.80
E182CC	4.95	13.80*	UCC80	1.30	6C6	0.55	13D5	0.90			
EA76	2.25	MH4	2.50	UCH42	1.65	6CH6	8.20	13D6	0.80	PLUMBICON	
EABC80	0.80	ML6	2.50	UCH81	0.75	6CL6	2.75	14S7	1.15	P800 3LF	
EB91	0.60	MX10/01	21.50	UCL82	0.95	6CX8	3.80	19A05	0.85	4CX 1000A	
EC33	1.15	N78	9.90	UF41	1.35	6CY5	1.15	19G3	11.50	P800 IB	
ECB90	0.90	OA2	0.70	UF80	0.95	6D6	0.70	19G6	8.50	XQ1020R	
EBF80	0.60	OB2	0.80	UF85	0.95	6F6	1.60	19H5	39.55	XQ1020B	
EBF80	0.60	PABC80	0.60	UL84	0.95	6F6GB	1.10	20D1	0.80		
EBF89	0.80	PC85	0.75	UM80	0.90	6F7	2.80	20F2	0.85	SPECIAL V	
EC52	0.65	PC96	0.95	UM84	0.70	6F8G	0.85	20E1	1.30	4CX 5000A	
EC31	4.40	PC88	0.95	UY82	0.70	6F12	1.50	20P1	0.65	BM 25L	
EC92	0.85	PC97	1.50	UY85	0.85	6F14	1.15	20P3	0.75	BM 153	
EC81	0.65	PC900	1.15	VR105/30	1.25	6F15	1.30	20P4	1.25	DM 25LB	
EC82	0.60	PC884	0.50	VR150/30	1.35	6F17	1.15	20P5	1.35	DM 25LB	
EC83	0.65	PC889	0.85	X66	0.95	6F23	0.75	25L6GT	0.95	YL 1420	
EC84	0.60	PC189	1.05	X61M	1.70	6F24	1.75	25Z4G	0.75	YL 1430	
EC85	0.60	PCF80	0.90	XRI-6400A	0.63	6F33	10.50	30C15	0.50	YL 1440	
EC86	1.70	PCF82	0.70	82.90	6FH8	4.20	30C17	0.50	GXU6		
EC88	0.80	PCF84	0.75	Z759	19.00	6GA8	1.95	30C18	2.45	CV1597	
ECC189	0.95	PCF86	1.50	Z749	0.75	6GH8A	0.95	30F5	1.15	CV2116	
ECC804	0.90	PCF87	0.50	Z800U	3.45	6H6	1.60	30FL2	1.40	BR 189	
ECF80	0.85	PCF200	1.60	Z801U	3.75	6J4	1.35	30FL12	1.25	BR 179	
ECF82	0.85	PC201	1.65	Z803U	16.00	6J4WA	0.85	30FL14	2.15	CV6131	
ECF801	1.05	PCF800	0.50	Z900T	2.45	6J5	2.30	30L15	1.10	GMU 2	
ECH34	2.25	PCF801	1.75	1A3	0.85	6J5GT	0.90	30L17	1.10	TY4-500	
ECH35	1.70	PCF802	0.85	1L4	0.50	6J6	0.65	30P12	1.15	BK485/5552A	
	2.10*	PCF805	2.45	1R5	0.60	6J6W	0.90	30PL13	1.25	MIL 5948/1754	
ECH42	1.20	PCF806	1.20	1S4	0.45	6J6CC	2.95	30PL14	2.45		
ECH81	0.70	PCF808	2.75	1S5	0.45	6J6CC	2.95	35L6GT	1.40	IC	
ECH84	0.80	PCH200	1.35	1T4	0.45	6K7	0.80	35W4	0.80	SN5402N	0.28
ECL80	0.70	PC181	0.75	1U4	0.80	6L6M	2.80	35Z4GT	0.80	SN5410F	0.32
ECL82	0.75	PC182	0.95	1X2B	1.40	6L6G	2.50	50C5	1.15	SN5470F	0.48
ECL83	1.40	PC184	0.90	2D21	1.10	6L6GC	3.15	50C6D6G	1.35	SN54196J	1.20
ECL85	0.80	PC186	1.05	1.85*	6L6GT	1.25	7581	1.25	SN7407N	0.29	
ECL86	0.90	PC1805/85	1.25	2K25	18.95	6L7G	0.65	75C1	1.25	SN7408N	0.18
EF37A	2.15	PF500/510	3.30	24.50*	6L18	0.70	76	0.95	SN7445P	0.85	
EF39	1.25	PF200	1.10	2X2	1.15	6L06	2.95	78	0.95	SN74453P	1.10
EF80	0.65	2.80*	3A4	0.70	6LD20	0.70	80	1.70	SN7453N	0.18	
EF83	1.75	PL36	1.25	3AT2	2.40	6KG6A	2.70	85A2	1.40	SN74L73N	0.38
EF85	0.60	PL81	0.85	3D6	0.50	6O7G	1.30	2.85*	SN7474N	0.30	
EF86	0.75	PL82	0.70	3D22	23.00	6O7	1.00	807	1.25	SN7485N	0.95
EF89	1.05	PL83	0.50	3E29	19.00	6SG7	1.10		1.90*	SN74L85N	1.10
EF91	1.50	PL84	0.95	3S4	0.60	6S7J	1.05	813	19.32	SN7491AN	0.32
EF92	2.90	PL504	1.45	4B32	18.25	6SK7	0.95	68.50*	SN74123N	0.42	
EF95	0.65	PL508	1.95	5B/254M	16.90	6SL7GT	0.85	829B	14.00	DM74123N	0.38
EF96	0.60	PL509	2.90	5B/255M	14.50	6SN7GT	0.80	832A	8.90	SN15836N	0.26
EF183	0.80	PL519	3.20	5B/258M	12.50	6SR7	1.10	866A	3.90	cX4	0.95
EF184	0.90	PL522	3.20	5B/252	29.90	6S07	0.65	866E	6.25	SN76013N	1.80
EF12	0.75	PY33	0.70	5R4GY	1.80	6V6G	1.50	931A	13.80	SN76003N	1.60
EFL200	1.85	PY80	0.70	5U4G	0.75	6V6GT	0.95	954	0.60	SN76033N	1.35
EH90	0.85	PY81/800	0.85	5V4G	0.75	6X4	0.95	955	1.20	MC6800P	5.80
EL32	1.10	PY82	0.65	5Y3GT	0.95	6X4WA	1.20	956	0.60	MC68800P	1.50
EL34	1.80	PY83	0.80	5Z3	1.50	6X5GT	0.65	957	1.05		6.40
	2.90*	PY88	0.85	5Z4G	0.75	6Y6G	0.90	1625	1.80	MC14511BA	2.20
EL37	4.40	PY900	1.70	5Z4GT	1.05	6Z4	0.70	1629	1.85		
EL81	2.45	PY809	6.45	6/30L2	0.90	7B7	1.75	2051	2.90	B1702AL	3.30
EL82	0.70	PY801	0.80	6AB7	0.70	8BN8	2.95	5763	4.20	MM6300-LJ	3.80
EL84	0.80	QV03/10	2.85	6AC7	1.15	9D2	0.70	5842	7.50		
EL86	0.95	QV03/20A	6AG5	0.60	9D6	2.90	5881	3.40		MCM6810AP	
EL90	1.00		6AH6	1.15	10C2	0.85	5833	6.90			3.40
EL91	4.20	QV03-25A	6AK5	0.05	10F18	0.70	6057	2.20	6340-1J	3.60	
EL95	0.80		6AK8	0.60	10P13	1.50	6060	1.95	MC945-50	0.28	
EL94	1.70	QV06/40A	6AL5	0.60	11E2	19.50	6064	2.30	MC936-50	0.22	
EL803	5.90		6AL5W	0.85	12A6	0.70	6065	3.20			

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc. retail 749 3934, trade and export 743 0899.
"D10" CABLE FIELD TELEPHONES
Geiger Muller Tubes GM4, MX12/01 and others.

TEST SET FT2 FOR TESTING Transceivers A40, A41, A42 and CPRC26.
HARNES "A" & "B" CONTROL UNITS "A" "B" "J1" "J2" Microphones No 5, 6, 7 connectors, frames, carrier sets, etc.
DRUM CABLE continuous connection YC 00433.

Signal Generators MARCONI TF 144H/4S; TF144H/6S 10 kHz-72MHz.
Prices on application

COLOMOR (ELECTRONICS LTD.)
170 Goldhawk Rd., London W.12

FIELD TELEPHONES TYPE "J".
Tropical, In metal cases.
10-line MAGNETO SWITCH-BOARD. Can work with every type of magneto telephones.

PRICES MAY VARY

POSTAGE: £1-£3 45p; £3-£5 55p; £5-£10 60p; £10-£15 80p; £15-£20 100p.

Tel. 01-743 0899 or 01-749 3934
Open Monday to Friday
9 a.m.-5.30 p.m.

RF POWER VMOS LOW-NOISE GASFET

- TYPE 9051 VMOS LINEAR POWER AMPLIFIER. 10W. RF output. Frequency as specified in the range 1-250 MHz. £65
- TYPE 9054 VMOS LINEAR POWER AMPLIFIER. 20W. RF output. £85
- TYPE 9053 VMOS LINEAR POWER AMPLIFIER. 8W. RF output. Frequency as specified in the range 250-600 MHz. £85
- TYPE 9045 VMOS WIDEBAND LINEAR POWER AMPLIFIER. 30 KHz.-20 MHz. Without tuning. 4W RF output. £39.50
- TYPE 9050 VMOS WIDEBAND LINEAR POWER AMPLIFIER. 20-200 MHz. Without tuning. 4W RF output. £39.50
- TYPE 9052 VMOS HIGH DYNAMIC RANGE AMPLIFIER. Output 1W + 30 dBm. N.F. 2.5 dB. Gain 20 dB. Frequency as specified in the range 1-250 MHz. £49.50
- TYPE 9049 VMOS HIGH DYNAMIC RANGE AMPLIFIER. Output 1W + 30 dBm. N.F. 1.0 dB. Gain 60 dB. Adjustable -40 dB. Frequency as specified in the range 1-250 MHz. £59.50
- TYPE 9000 GASFET STRIPLINE PREAMPLIFIER. 250-500 MHz. N.F. 0.5 dB. Gain 25 dB. Masthead/local use. £49.50
- TYPE 9001 GASFET STRIPLINE PREAMPLIFIER. 450-900 MHz. N.F. 0.6 dB. Gain 20 dB. Masthead/local use. £49.50
- TYPE 9015 UHF TELEVISION PREAMPLIFIER. N.F. 2.8 dB. Gain 16 dB. Channel 'A' 21-34, 'B' 39-51, 'CD' 49-68. £14.50
- TYPE 9025 RF PREAMPLIFIER. Aligned to your specified frequency in the range 1-250 MHz. N.F. 1.0 dB. Gain 40 dB. £29.50
- TYPE 9030 WIDEBAND RF PREAMPLIFIER. 10 KHz.-100 MHz. Without tuning. N.F. 3.0 dB. Gain 40 dB. Increases sensitivity of instruments by 100 times. £29.50
- TYPE 8032 PHASE LOCKED SIGNAL SOURCE. 1-1000 MHz. £54.50
- TYPE 8026 FREQUENCY CONVERTER. Input in the range 100-1500 MHz. Output in the range 1-1500 MHz. £164.50
- TYPE 9075 FREQUENCY COUNTER. 150 MHz. £74.50
- TYPE 9060 FREQUENCY DIVIDER BY 10. 600 MHz. £19.50
- TYPE 9055 FREQUENCY DIVIDER BY 10. 1200 MHz. £49.50

POST AND PACKING £1.50 PER UNIT
PLEASE ADD VAT 15% ON TOTAL

RESEARCH COMMUNICATIONS LIMITED

43/4 COURT STREET, FAVERSHAM, KENT ME13 7AL
TEL. 010 33 45 96 36 39

WW-073 FOR FURTHER DETAILS

FINAL RADIO AND ELECTRONICS EXHIBITION AT BELLE VUE

by the NORTHERN RADIO SOCIETY ASSOCIATION

LANCASTER HALL
BELLE VUE, MANCHESTER


on SUNDAY, 4th APRIL, 1982. Doors open at 11 a.m.
The North's Premier Amateur Radio and Electronics Event

Features: Inter-club quiz; grand raffle; construction contest; amateur computer stands; RSCB book stall; Radio Society stands and Trophy Home Office and Raynet stands

Belle Vue has ample car parks
FM talk-in on GB3NRS and G8NRS/A on 145MHz Chs22 R2 R6 and on 433MHz Chs SU8-RB4 RB14

ADMISSION 60p BY RAFFLE TICKET AND EXHIBITION PLAN
Enter at rear of Belle Vue, opposite main car park off Hyde Road A57

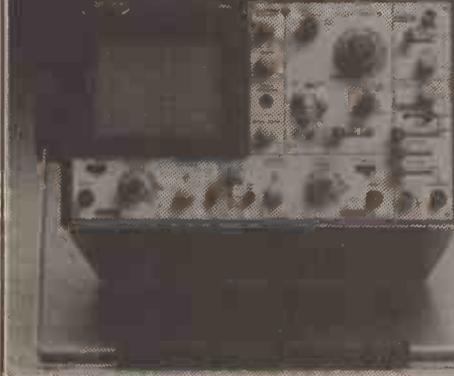Immediate Availability! Exceptional Value! Hitachi V-550B high performance 50MHz Oscilloscope



The Hitachi V-550B combines a host of professional features with unrivalled quality, reliability and cost-effectiveness.

Features include full dynamic-range bandwidth to over 50MHz, dual timebases with B trigger and calibrated multiplier, variable hold-off, 1mV/cm sensitivity, 5nsec/cm sweep, trigger view and an internal graticule C.R.T. At around £700 it offers the best value available.

Equally important, the whole Hitachi range including the V-550 is available from stock now!

The range covers bandwidths from 15MHz to 100MHz and includes battery mini-portables. All models carry a two year warranty and are supplied with probes. Prices start at around £230 ex VAT.

For full colour brochures giving detailed specifications and prices ring (0480)

Reltech Instruments Coach Mews, St. Ives, Cambs. PE17 4BN 63570.

WW - 063 FOR FURTHER DETAILS

TRANSFORMERS CONTINUOUS RATINGS

MAINS ISOLATORS (screened)
Pri 0-120; 0-100-120V (120, 220, 240V) Sec 60
55-0-55 60 twice to give 55, 60, 110, 115, 120,
125, 175, 180, 220, 225, 230, 235, 240V.

Ref. VA (Watts)	£	P&P
07★	20	4.84
149	60	7.37
150	100	8.38
151	200	12.28
152	250	14.61
153	350	18.07
154	500	22.52
155	750	32.03
156	1000	40.92
157	1500	56.52
158	2000	67.99
159	3000	95.33
161	6000	203.65

★115 or 240v sec only. State volts required.
Pri 0-220-240V.

12 or 24-VOLT RANGE
Separate 12V windings Pri 220-240V

Ref.	12v Amps	24v	£	P&P
111	0.5	0.25	2.42	.95
213	1.0	0.5	2.90	1.00
71	2.0	1.0	3.86	1.00
18	4.0	2.0	4.46	1.20
85	5.0	2.5	6.16	1.20
70	6.0	3.0	6.99	1.20
108	8.0	4.0	8.16	1.44
72	10.0	5.0	8.93	1.60
116	12.0	6.0	9.89	1.60
17	16.0	8.0	11.79	1.72
115	20.0	10.0	15.87	1.84
187	30.0	15.0	19.72	2.04
226	60.0	30.0	40.41	OA

30 VOLT RANGE (Split Sec)
Sec. Volts available 3, 4, 5, 6, 8, 9, 10, 12,
15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V

Ref.	Amps		£	P&P
	30v	15v		
112	0.5	1	2.90	1.00
79	1	2	3.93	1.00
3	2	4	6.35	1.20
20	3	6	7.39	1.20
21	4	8	8.79	1.60
51	5	10	10.86	1.60
117	6	12	12.29	1.72
88	8	16	16.45	1.96
89	10	20	18.98	1.84
90	12	24	21.09	OA
91	15	30	24.18	OA
92	20	40	32.40	OA

50 VOLT RANGE
Sec. Volts available 5, 7, 8, 10, 13, 15, 17, 20,
25, 30, 33, 40 or 20V-0-20V or 25V-0-25V

Ref.	Amps		£	P&P
	50v	25v		
102	5	1	3.75	1.20
103	1	2	4.57	1.20
104	2	4	7.88	1.44
105	3	6	9.42	1.60
106	4	8	12.82	1.72
107	6	12	16.37	1.84
118	8	16	22.29	2.20
119	10	20	27.48	OA
109	12	24	32.89	OA

60 VOLT RANGE
Pri 220-240V (Split Sec)
Voltages available 6, 8, 10, 12, 16,
18, 20, 24, 30, 36, 40, 48, 60V, or
24V-0-24V or 30V-0-30V

Ref.	Amps		£	P&P
	60v	30v		
124	5	1	4.27	1.20
126	1	2	6.50	1.20
127	2	4	8.36	1.60
125	3	6	12.10	1.72
123	4	8	13.77	1.96
40	5	10	17.42	1.84
120	6	12	19.87	2.04
121	8	16	27.92	OA
122	10	20	32.51	OA
189	12	24	37.47	OA

SCREENED MINIATURES Pri 240V

Ref.	mA	Sec Volts	£	P&P
238	200	3-0-3	2.83	.50
212	1A, 1A	0-6, 0-6	3.14	1.00
13	100	9-0-9	2.35	.50
235	330, 330	0-9, 0-9	2.19	.60
207	500, 500	0-8-9, 0-8-9	3.05	.95
208	1A, 1A	0-8-9, 0-8-9	3.88	1.20
236	200, 200	0-15, 0-15	2.19	.60
239	50MA	12-0-12	2.88	.50
214	300, 300	0-20, 0-20	3.08	1.00
221	700 (DC)	20-12-0-12-20	3.75	1.00
206	1A, 1A	0-15-20, 0-15-20	5.09	1.20
203	500, 500	0-15-27, 0-15-27	4.39	1.20
204	1A, 1A	0-15-27, 0-15-27	6.64	1.20

AUTO TRANSFORMERS
Voltages available 105, 115, 190, 200, 210, 220,
230, 240. For step up or step down.

Ref. VA (Watts)	TAPS	£	P&P
113*	15 0-10-115-210-240V	2.77	1.00
64	80 0-10-115-210-240V	4.41	1.20
4	150 0-10-115-200-220-240V	5.89	1.20
67	500 0-10-115-200-220-240V	12.09	1.84
84	1000 0-10-115-200-220-240V	20.64	2.20
93	1500 0-10-115-200-220-240V	25.61	OA
95	2000 0-10-115-200-220-240V	38.31	OA
73	3000 0-10-115-200-220-240V	65.13	OA
80s	4000 0-10-115-200-220-240V	84.55	OA
57s	5000 0-10-115-200-220-240V	98.45	OA

CONSTANT VOLTAGE TRANSFORMERS
For 'clean' mains to computers, peripherals.

250VA	500VA	1kVA	£	p&p	VAT
			95.00		
			127.00		
			147.00		

SPECIALIST TRANSFORMER WINDING SERVICE

TOROIDALS NOW AVAILABLE

Send stamp for list

PLEASE ADD 15% VAT AFTER P&P
Overseas post extra

OTHER PRODUCTS

AVO TEST METERS
8 Mk. 5 Latest Model £122.10
71 (Electronics & TV Service) £45.80
73 TV Service £63.90
MMS Minor £40.50
DA211 LCD Digital £58.50
DA212 LCD Digital £81.90
DA116 LCD Digital £121.70
Megger 70143 500v £97.20
Megger Battery BM7 £66.30
Avo Cases and Accessories P&P £1.32 + VAT 15%

MAINS BATTERY ELIMINATORS
No wiring, ready to plug into 13A socket. 6, 9,
12V DC 300mA £5.10 + VAT

ANTEX SOLDERING IRONS 15W. CCN240 or C£4.50
Safety stand £1.75 25W X25 £4.80
12V 25W car soldering kit £5.30
P&P 50p + VAT

PANEL METERS £6.70 ea + 76p P/P + VAT
43 x 43mm or 82 x 78mm V.U. Indicator
50µA, 500µA, 1mA, 30V d.c. £1.95+30p P&P+VAT
Educational Meter 10A8 30V £4.50+VAT

Precision De-Solder Pumps - Spring loaded quick action button release for one hand working. Large £5.86 P&P 35p+VAT. Small £5.17 P&P 30p+VAT. Replacement tips: Small 65p+VAT. Large 86p+VAT.

ANTEX SOLDERING IRONS 15W CCN240 or C £4.50
25W X25 £4.80, 12V 25W car solder kit £5.30. Safety stand £1.75. P&P 55p + VAT

METAL OXIDE RESISTORS £1/100
Special Offer TR4 5% Electrofil (100s only). Use in place of e.film. 47Ω - 75Ω - 180Ω - 360Ω - 390Ω - 430Ω - 470Ω - 510Ω - 560Ω - 820Ω - 1K - 1K2 - 1K3 - 1K6 - 1K8 - 2K - 2K4 - 3K - 16K - 20K - 22K - 24K - 27K - 47K - 82K - 100K - 110K - 120K - 130K - 180K - 220K - 270K - 300K. P&P 30p + VAT

BRIDGE RECTIFIERS

200v	2A	45p
400v	2A	55p
100v	25A+	£2.10
100v	50A	£2.60
200v	4A	65p
400v	4A	85p
400v	6A	£1.40
500v	12A	£2.85

P&P 20p. VAT 15%

Send 20p for catalogue.
Prices correct at 20/3/81

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

WW - 069 FOR FURTHER DETAILS

YOU CAN'T BEAT ILP BIPOLAR POWER AMPS FOR POWER AND PRICE

Get maximum power at minimum price, yet still with hi-fi specifications and a wide choice of outputs. ILP Bipolar power amps, now with or without heatsinks are unbeatable value for domestic hi-fi — but for disco, guitar amplifiers and PA choose the new range of heavy duty power amps, again with or without heatsinks, with protection against permanent short circuit, added safety for the disco or group user. Connection in all cases is simple — via 5 pins.



Every item has a 5 year no quibble guarantee and includes full connection data. So send your order FREEPOST today!

Load impedance, all models, 4 ohm — infinity. Input impedance, all models 100K ohm. Input sensitivity, all models, 500 mV. Frequency response, all models 15Hz-50KHz-3db.

BIPOLAR Standard, with heatsinks

Model No.	Output power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4.1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex. VAT
HY 30	15w/4-8Ω	0.015%	<0.006%	±18±20	76×68×40	240	£8.28	£7.29
HY 60	30w/4-8Ω	0.015%	<0.006%	±25±30	76×68×40	240	£9.58	£8.33
HY 120	60w/4-8Ω	0.01%	<0.006%	±35±40	120×78×40	410	£20.10	£17.48
HY 200	120w/4-8Ω	0.01%	<0.006%	±45±50	120×78×50	515	£24.39	£21.21
HY 400	240w/4Ω	0.01%	<0.006%	±45±50	120×78×100	1025	£36.60	£31.83

BIPOLAR Standard, without heatsinks

HY 120P	60w/4-8Ω	0.01%	<0.006%	±35±40	120×26×40	215	£17.83	£15.50
HY 200P	120w/4-8Ω	0.01%	<0.006%	±45±50	120×26×40	215	£21.23	£18.46
HY 400P	240w/4Ω	0.01%	<0.006%	±45±50	120×26×70	375	£32.58	£28.33

Protection: Load line, momentary short circuit (typically 10 sec). Slew rate 15V/µs Rise time: 5µs. S/N ratio 100db. Frequency response (-3dB): 15Hz-50KHz. Input sensitivity 500mV r.m.s. Input impedance 100KΩ. Damping factor (8Ω/100Hz)>400.

HEAVY DUTY with heatsinks

Model No.	Output power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4.1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex. VAT
HD 120	60w/4-8Ω	0.01%	<0.006%	±35±40	120×78×50	515	£25.85	£22.48
HD 200	120w/4-8Ω	0.01%	<0.006%	±45±50	120×78×60	620	£31.49	£27.38
HD 400	240w/4Ω	0.01%	<0.006%	±45±50	120×78×100	1025	£44.42	£38.63

HEAVY DUTY without heatsinks

HD 120P	60w/4-8Ω	0.01%	<0.006%	±35±40	120×26×50	265	£22.82	£19.84
HD 200P	120w/4-8Ω	0.01%	<0.006%	±45±50	120×26×50	265	£27.17	£23.63
HD 400P	240w/4Ω	0.01%	<0.006%	±45±50	120×26×70	375	£39.42	£34.28



Protection: Load line, PERMANENT SHORT CIRCUIT (ideal for disco/group use should evidence of short circuit not be immediately apparent). The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs as for standard types.

How to order Freepost: Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules

Total purchase price

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

WW 2/4

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 54778 Technical (0227) 64723; Telex 965780.

ILP ELECTRONICS LTD
STAY AHEAD. STAY WITH US

WW - 080 FOR FURTHER DETAILS

RHODE & SCHWARZ

Selective UHF V/Meter. Bands 4 & 5. USVF
Selectomat Voltmeter USWV £450.
UHF Sig. Gen. type SDR 0.3-1GHz
UHF Signal Generator SCH £175.
XUD Decade Synthesizer & Exciter.
POLYSKOPS SWOB I and II.
Modulator/Demodulator BN17950/2.

MARCONI

TF995B/2 AM/FM Signal Generator.
TF2500 Audio power meter
TF1101 RC oscillators £65.
6551 SAUNDERS. 1400-1700MHz. FM.
TF1066B/1. 10-470MHz. AM/FM.
TF1152A/1. Power meter. 25W. 500MHz
£50.
TF1370A RC Oscillator £135.
TF791D Carrier Deviation Meter.

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.

★ VIDEO EQUIPMENT SALE ★ CONTENTS OF COMPLETE MONOCHROME STUDIO

MARCONI Video/Audio mixing desks.
Monochrome Video cameras complete with on-board monitors.
Video monitors types CONRAC II (9" tube) PROWEST 13".
To be sold in first-class working condition.
Offers invited for complete lot.

SEALED LEAD ACID BATTERIES

Gould GELYTE type PB660. 6V. 6AH. Measures 3 3/4 x 2 3/4 x 2 3/4 inches. Excellent condition. £4.90. (75p post).

20-WAY JACK SOCKET STRIPS. 3 pole type £2.50 each (+ 25p p.p.). Type 316 three-pole plugs for above—20p ea. (p.p. free).

P. F. RALFE ELECTRONICS


10 CHAPEL STREET, LONDON, NW1
TEL: 01-723 8753.



RANK KALEE 1742 Wow & Flutter Meter.
AIRMEC 314A Voltmeter. 300mV (FSD)-300V.
AIRMEC Wave Analysers types 853 & 248A.
DERRITRON 1KW Power Amplifier with control equipment for vibration testing, etc.
TELEONIC type 1204 0-500MHz sweep generator £150
TELEONIC type 121 Display scopes £90
TELEONIC type 101 Display scopes £75
WAYNE KERR AF signal generator S121 model £85
RADIOMETER Distortion Meter BKF6 £125.

SPECIAL PURCHASE OF TEKTRONIX 454 PORTABLE OSCILLOSCOPES

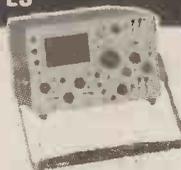Tektronix 454 DC-150MHz dual-beam oscilloscopes in stock now. 5mV/cm Y-amplifier (1mV cascaded). 2.4ns risetime. Calibrated sweep delay. We can offer these units in first-class operational condition complete with three months' guarantee, for a once only price of £850. Full specification sheet upon request.



★ OSCILLOSCOPES ★ TEKTRONIX 500 SERIES SCOPES AT BARGAIN PRICES:

All in good working order. Available to callers only
TYPE 543B with 'CA' plug-in 25MHz DB SOLD OUT
TYPE 545B with 'CA' plug-in 25MHz DB SOLD OUT
TYPE 585A with '82' unit. 80MHz. Few left-£250. Reduced to £200.

PLEASE NOTE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES.

DC POWER SUPPLIES

★APT 10459/8, 12-14V @ 5 Amps £25 (£2 p.p.)
★APT 10459/8, 24V @ 5 Amps £25 (£2 p.p.)
★We can supply the above power supply at any fixed voltage between 5V and 36V at 5A £25.
★Mullard Dual supplies. Brand new with handbook. Pos & Neg 12V at 1A and 0.4A respectively. Dimensions 9x4x5ins. £10 + (£1 p.p.)
★FARNELL Current limited. Dimensions 7x5x4ins. Following types available: 13-17 Volts @ 2A £15. 27-32 Volts @ 1A 5V £15. 5V @ 3A £15. (pp £1.50).

SPECIAL PURCHASE

LAMBDA POWER SUPPLIES

Excellent LXS Series DC power units at less than a tenth of new price. The snag? — they're all 110V AC input. Prices as follows:
5V at 24A. LXS D5 0V R. £25. (List £350). Carriage .each
5V at 14A. LXS CC 5 0V. £20. (£25B). £2.50 extra
24V at 3.1A. LXS C 24. £15. (£223).
Special note: The 5V power supplies may be operated (both primary from 230V) and DC output to give a maximum output voltage of 12.5DC when connected in series. Deduct 10% from price for two off or more, i.e., 12V DC at 24A for £45 + Tax! Very cheap!

VARIABLE VOLTAGE BENCH SUPPLIES

Variable voltage DC power supplies for workshop use. Constant voltage, variable 0-30V output at 1A. Cased, free standing, volt-metered output. Short circuit proof. Size 4 x 5 x 7". Only £30—each (pp £1.50).

COMMUNICATIONS TEST EQUIPMENT

★ MARCONI TF1066B/1. AM/FM Signal Generator. 10-470MHz. 0.2uV-200mV output. FM Deviations up to ±100KHz from 30Hz-15KHz £550
★ MARCONI TF995A/5 AM/FM Signal generator. Narrow deviation model 995 covering 1.5-220MHz £450
★ MARCONI TF1064B/5 FM signal generator covering in three ranges 68-108, 118-185 and 450-470MHz. Modulation FM fixed deviations of 3.5 and 10KHz. AM fixed 30% £225
★ MARCONI TF791D FM Deviation meter £185

ROTRON INSTRUMENT COOLING FANS

Supplied in excellent condition, fully tested:
115V. 4.5 x 4.5 x 1.5" £4.50. 230V
£5. 115V. 3 x 3 x 1.5" £4 + postage ea. 35p.

100V DC ELECTROLYTIC CAPACITORS


Sprague 'Powerlytic' type 36D. 10,000uF. 100V. Brand new at surplus price! Only £4 ea. PP 50p.

GRAPHICS & GRAPHICS GRAPHICS

What's going on in Computer Aided Design—and how will it develop? Ever wondered about the maths behind interactive 3-D graphics? Want to know about the graphics capabilities of the powerful Hewlett Packard HP-83?

Our April issue examines three aspects of graphics in computing. We review Grandstand, a game for gamblers with a Pet computer; show how microprocessor control has come to the farm ...

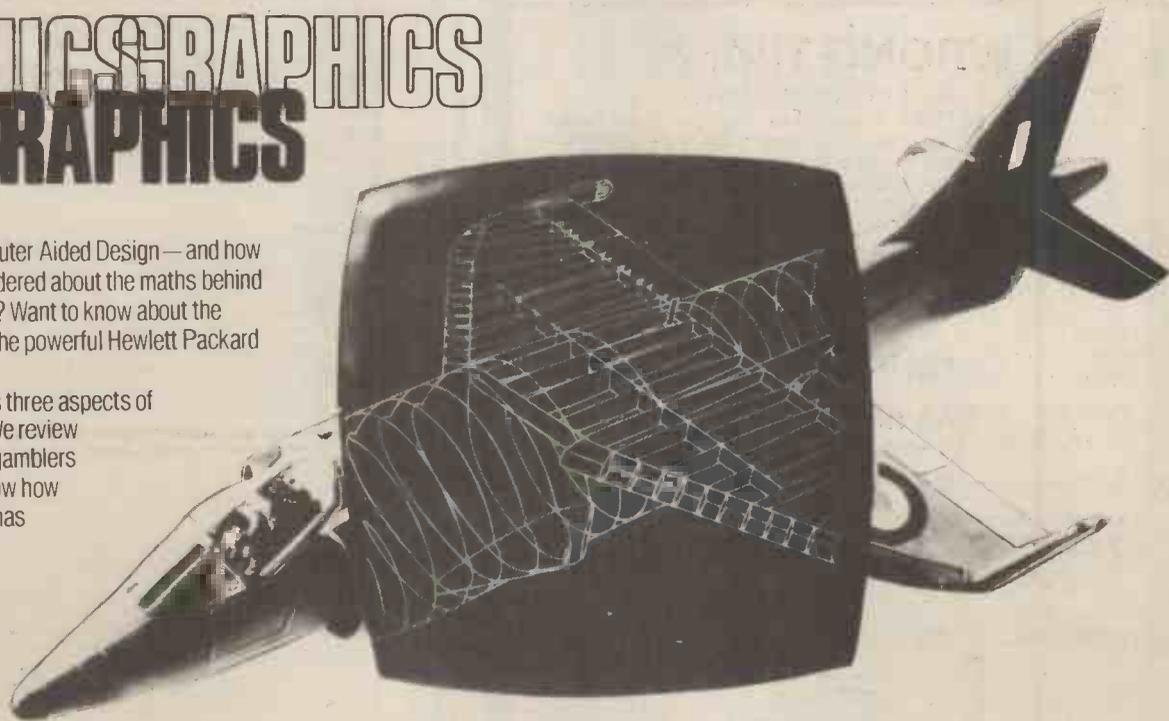That's just a sample of Practical Computing, together with advice for users of Pet, Apple, Tandy and Sinclair ZX 80/81 computers. Buy Britain's leading personal computer magazine.



APRIL ISSUE OUT NOW. 80p AT YOUR NEWSAGENT'S—BUT HURRY.

Practical Computing

CHILTERN ELECTRONICS

B.C.M. Box 8085, LONDON, WC1N 3XX
BRAND NEW SURPLUS DISK DRIVES

Due to bulk purchase of bankrupt stock, we are able to offer these Floppy and Hard Disk drives at a fraction of their usual cost. Both are brand new in original boxes dated 1979/80. They are both manufactured by the famous Data Recording Equipment Co. who are known worldwide for their high engineering standards.

★ DRI SERIES 32 5-MEGABYTE CARTRIDGE DRIVE

Successor to the famous Series 30, these are similar in design but double the density on the same type of cartridge. It will either operate as a single 5.6 Megabyte drive or emulate two 2.5 MByte drives, and can be daisy chained on to all similar drives such as RK05, Pertec, Wangco, etc.

Manufacturer's list price is over £3,000. Our price £420!

Controllers available for S-100 Bus Systems for £400, complete with all documentation and software. This gives you a beautiful hard disk system for less than the cost of many floppies. Controllers also available for PDP11 and LSI-11.

★ DRI SERIES 7200 FLOPPY DISK DRIVES

These are new 8-inch double-sided single or double density units, giving up to 1.6 Megabytes unformatted capacity on a single disk. Interface is the same as Shugart, die cast alloy construction, top quality.

Our price only £250 or two for £450!

OTHER COMPUTER BARGAINS

MINIATURE 5 VOLT 20-AMP POWER MODULES

These beautiful little pocket-sized power supplies weigh less than 4lbs, and yet deliver a massive 22 amps at 4 to 6 volts with 0.1% regulation and full overvolts and overcurrent protection. Standard 230v mains input.

Usually these units cost over £250 each — manufactured by Farnell/Gould.

Our price £34.50 brand new, INCLUDING VAT AND POSTAGE

PERTEC 9-Track Magtapes. (Model 6840)

For callers only we have some of these beautiful tape drives available for only £130 each. Originally these cost over £2,500 each — and they are only a few years old. They are sold without guarantee and need a good clean-up, but we have spares available cheaply and they are very easy to interface to a micro.

ASCII 84 Key Professional Keyboards in case..... £30

Video Monitors, 9 inch with PSU..... £27

Video Monitors, Ball Inc. 14 inch..... £40

Video Monitors, 14 inch green screen in case..... £99

Proto cards: Over 350 TTL ICs and sockets — none are soldered, and 5V 3A Regulated PSU for £25 or £30 inc. VAT/Postage.

Please add 15% VAT and carriage to above.

We stock wide range of DEC Systems from PDP8E to PDP11/70 and have lots of one-off bargains. Why not visit our office near High Wycombe sometime.

Please telephone Nigel Dunn on 0494 714483 any time

WW-065 FOR FURTHER DETAILS

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, can expand to Years, Months, Weekdays and Milliseconds, also parallel BCD output for computer or alarm, etc., receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, GET the RIGHT TIME £62.80.

V.L.F.? EXPLORE with a 10-150KHz Receiver, £16.50.


60KHz RUGBY RECEIVER, as in MSF Clock, serial data output for computer, etc., decoding details, £17.90.

Each fun-to-build kit (ready made to order) includes all parts; printed circuit, case, postage, etc., instructions, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (WD) Old School Lane, Milton, Cambridge. Tel: 860150

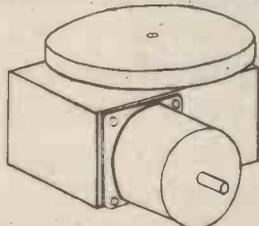STEPPING MOTOR ROTARY TABLE MICRO-PROCESSOR CONTROLLED



Stepping motor driven rotary table machined from cast aluminium parts, table diameter 130mm, gear ratio 120:1, motor 200 steps per revolution, 24,000 motor pulses per table revolution, max. speed in start/stop mode 10 degrees per second. Easily stackable to produce a pan and tilt mechanism, £192 each. Motor drive pcb type 440 to interface to microprocessor port, £32 each. Other machines made to order. Complete 8085 based computer systems with software available.

F.H. PRECISION ENGINEERS

24 Belvoir Avenue, Trentham, Stoke-on-Trent ST4 8SY
Tel. 0782-643278 (AnsaPhone)


WHY AN ILP MOSFET POWER AMP?

Because ILP MOSFET power amps give you ultra-fi performance without costing big money. Performance you thought you couldn't afford at a price you know you can.

All ILP modules are compatible with each other — you'll find many more in other ILP ads in this magazine. Choose ILP MOSFET power amps when you need the fastest possible slew rate, low distortion at high frequencies, better thermal stability. MOSFET power amps work with complex loads without difficulty and without crossover distortion. Connection is simple — via 5 pins. With other ILP modules you can create almost any audio system, whatever your age or experience.

ILP MOSFET power amps are now available with integral heatsink (no extra heatsink required), or ready for mounting on to your own heatsink or chassis. Full dissipation detail on data sheet, available on request. Each carries a 5 year no quibble guarantee and comes with full connection data.

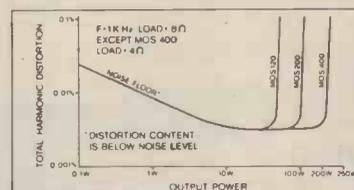Send your order FREEPOST today on the coupon at the foot of this ad.



Load impedance, all models, 4 ohm — infinity
Input impedance, all models 100k ohm
Input sensitivity, all models, 500 mV
Frequency response, all models 15Hz-50kHz-3db

MOSFET Ultra-Fi, with heatsinks

Model No.	Output power Watts rms	T.H.D. Typ at 1kHz	DISTORTION I.M.D. 50Hz/7kHz 4.1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex. VAT
MOS 120	60w/4-8Ω	<0.005%	<0.006%	±45±50	120×78×40	420	£29.76	£25.88
MOS 200	120w/4-8Ω	<0.005%	<0.006%	±55±60	120×78×80	850	£38.48	£33.46
MOS 400	240w/4Ω	<0.005%	<0.006%	±55±60	120×78×100	1025	£52.20	£45.39

MOSFET Ultra-Fi without heatsinks

Model No.	Output power Watts rms	T.H.D. Typ at 1kHz	DISTORTION I.M.D. 50Hz/7kHz 4.1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex. VAT
MOS 120P	60w/4-8Ω	<0.005%	<0.006%	±45±50	120×26×40	215	£26.82	£23.32
MOS 200P	120w/4-8Ω	<0.005%	<0.006%	±55±60	120×26×80	420	£32.81	£28.53
MOS 400P	240w/4Ω	<0.005%	<0.006%	±55±60	120×26×100	525	£44.75	£38.91

Protection:

Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice).

Ultra-fi specifications:

Slew rate 20V/μs. Rise time 3μs. S/N ratio 100db. Frequency response (−3dB) 15Hz-100kHz. Input sensitivity 500mVrms. Input impedance 100k. Damping factor (8Ω/100Hz) > 400.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILPElectronics Ltd. cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following
ILP modules _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access / Barclaycard No. _____

Name _____

Address _____

Signature _____ WW3/4

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Rooper Close, Canterbury CT2 7EP, Kent, England.
Telephone (0227) 54778 Technical (0227) 64723; Telex 965780.

ILP
ELECTRONICS LTD
STAY AHEAD. STAY WITH US

WW-081 FOR FURTHER DETAILS

HART KIT

LINSLEY HOOD CASSETTE RECORDER 2



Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 910 vertical front mechanism and circuit modifications to increase dynamic range. Board layouts have been altered and improved but retain the outstandingly successful mother-and-daughter arrangement used on our Linsley-Hood Cassette Recorder 1.

This latest version has the following extra features: Ultra low wow-and-flutter of .09% - easily meets DIN Hi-Fi spec. Deck controls latch in rewind modes and do not have to be held. Full Auto-stop on all modes. Tape counter with memory rewind. Oil damped cassette door. Latching record button for level setting. Dual concentric input level controls. Phone output. Microphone input facility if required. Record Interlock prevents rerecording on valued cassettes. Frequency generating feedback servo drive motor with built-in speed control for thermal stability. All these desirable and useful features added to the excellent design of the Linsley-Hood circuits and the quality of the components used makes this new kit comparable with built-up units of much higher cost than the modest. £94.90 + V.A.T. we ask for the complete kit.

LINSLEY-HOOD CASSETTE RECORDER 1



We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High-quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust Lenco mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily-built and tested layout. All these features added to the high-quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our latest HS 16 Sendus Alloy super head, available separately at £8.20 but included free with the complete kit at £75 plus VAT.

Reprints of the 3 original articles describing this design 45p. No VAT.
Reprint of the subsequent postscript article 30p. No VAT.

PRACTICAL WIRELESS 'WINTON' TUNER

Brilliant new Ted Rule designed Tuner with everything! Gives you fantastic stereo f/m reception with pilot cancelling decoder i.e., fluorescent display, digital frequency readout along with clock and timer functions. In addition to f.m. covers l.w., m.w., s.w. and even TV sound. Further details are in our lists; send for your copy.


Part Cost of Post, Packing and Insurance
Order up to £10-50p
Orders £10 to £49-£1
Over £50-£1.50

P&P Export Orders-Postage or shipping at cost plus
£2 Documentation and Handling

Please send 9 x 4 S.A.E. or telephone for lists giving fuller details and price breakdowns.

Instant easy ordering, telephone your requirements and credit card number to us on
Oswestry (0691) 2894

LINSLEY-HOOD 300 SERIES AMPLIFIERS

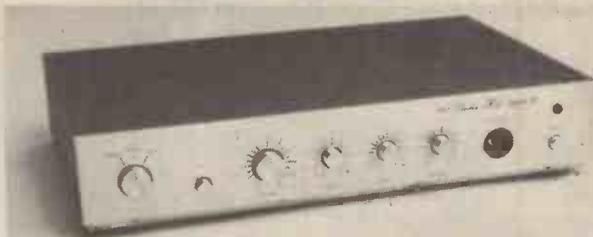

These latest designs from the drawing board of John Linsley-Hood, engineered to the very highest standard, represent the very best that is available on the kit market today. The delicacy and transparency of the tone quality enable these amplifiers to outperform, on a side-by-side comparison, the bulk of amplifiers in the commercial market-place and even exceed the high standard set by his earlier 75-watt design.

Three versions are offered, a 30-watt with Darlington output transistors, and a 35- and 45-watt, both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2.

As with all Hart kits the constructors interests have been looked after in a unique way by reducing the conventional (and boring) wiring almost to the point of extinction.

Any of these kits represents a most cost-effective route to the very highest sound quality with the extra bonus of the enjoyment of building a sophisticated piece of equipment.

30-watt Darlington amplifier, fully integrated with tone controls and magnetic pick-up facility. Total cost of all parts is £81.12. Special offer price for complete kits £72.

35-watt Mosfet amplifier. Total cost of parts £98.41. Special offer for complete kits, £87.40.

45-watt Mosfet amplifier. Total cost of parts £104.95. Special offer price for complete kits £94.80.

Reprints of original Articles from Hi-Fi News 50p. Post free. No VAT.
Reprints of MOSFET article 25p. No V.A.T. Post free.

FEED YOUR MICRO BYTES WITH OUR SOLENOID CONTROLLED CASSETTE DECK



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £2.70 plus V.A.T. and 50p postage.

CASSETTE HEADS

HS16 SENDUST ALLOY SUPER HEAD, Stereo R/P. Longer life than Permalloy. Higher output than Ferrite. Fantastic frequency response. Complete with data.....	£8.20
HC20 Stereo Permalloy R/P head for replacement uses in car players, etc.....	£4.25
HM90 Stereo R/P head for METAL tape. Complete with data.....	£7.20
HS61 Special Erase Head for METAL tape.....	£4.90
HS24 Standard Ferrite Erase Head.....	£1.50
4-Track R/P Head, Standard Mounting.....	£7.40
R484 2/2 (Double Mono) R/P Head, Std. Mtg.....	£4.90
ME151 2/2 Ferrite Erase, Large Mtg.....	£4.25
CCE/8M 2/2 Erase, Std. Mtg.....	£7.90

All prices plus VAT

HART KIT

HART ELECTRONIC KITS LTD
OSWESTRY
SHROPSHIRE
phone (0691) 2894
Telex 35661
Hartel G

AMATEUR RADIO HANDBOOK 1982

by A.R.R.L. £8.50

30-hour Basic by Prigmore	£6.50
UCSD Pascal Handbook by Clark	£13.00
Electronic Equipment Reliability by Cluley	£7.50
Micros in Amateur Radio by Kasser	£8.00
How to Design, Build Remote Control Devices by Stearne	£10.00
Modern Communication Switching Systems by Hobbs	£8.00
Art of Electronics by Horowitz	£14.50

★ PRICES INCLUDE POSTAGE AND PACKING ★

THE MODERN BOOK CO.

Specialist in Scientific and Technical Books

15/21 Praed Street, London, W2 1NP
PHONE: 01-402 9176 : Closed SATURDAY 1 p.m.

Please allow 14 days for reply or delivery

WW - 062 FOR FURTHER DETAILS

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner


Telephone 445 2713/0749

(9461)

WW - 066 FOR FURTHER DETAILS

£100 COMPUTER

CASIO FX-702P POCKET COMPUTER

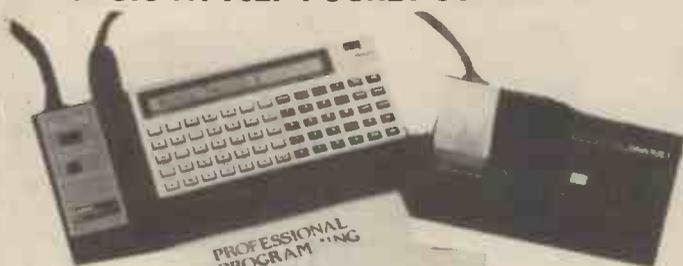

ONLY
£99.95

Plus FREE MiCROL Professional Programming Pack (RRP £9.95)
Or we will beat any lower advertised price by 5%
Eat your hearts out, H-P, Sharp and Texas!

The Casio FX-702P features: The biggest program storage capacity (up to 1,680 steps) the biggest data storage capacity (up to 226 memories), the widest range of math, science and statistics functions (55 in all, including Regression and Correlation), the most powerful English-like BASIC program-writing language and the fastest operation, for results without waiting! Subroutines; 10 levels, FOR:NEXT looping; 8 levels. Comprehensive edit, debug and trace modes. 240 hours battery life. 17x165x82mm.

FA-2 Cassette Adaptor £19.95; FP-10 Printer £44.95; NP-4M Rechargeable Battery Pack £6.90; AD-4150 Mains Adaptor £5.

SYSTEM PRICES - Save up to £40 on RRP

Pack A: FX-702P+MiCROL Professional Programming Pack **£99.95**
Pack B: FX-702P+FA-2 cassette interface+PPP+PROCOS **£139.95**
Pack C: FX-702P+FP-10 Printer+FA-2+PPP+PROCOS **£179.95**

MiCROL PROCOS for PROFESSIONAL USERS

Now you can create powerful, reliable programs in just minutes, even if you have never programmed a computer before!

MiCROL PROCOS is an advanced integrated operating system that cuts programming time by 80-90% in most applications areas, saving many hours of valuable time. PROCOS A and PROCOS B are supplied together on a ready-to-run cassette, with a fully detailed User Manual offering features to suit every application. PROCOS A is ideal for complex multivariable calculations, while PROCOS B provides many of the features of a 'Visicalc' type modelling system - answers 'what if' questions and analyses trends. Both systems feature easy-to-use commands and support FP-10 print options. Brochure on request.

MiCROL PROCOS (A+B) Price **£24.95**

SENSATION

of the Japanese Music Fair

CASIOTONE 701 COMPUTERISED ORGAN

Fully Programmable, 5 Octave, Polyphonic Keyboard

"THE instrument of 1982 . . . probably the best instructive keyboard I have come across. But it is also a top line musical instrument capable of satisfying even the most proficient musician." Keyboards & Music Player.



CT-701 (RRP £555) **ONLY £495**

Program the 345 melody steps and the 201 chord steps (max.) with music specially scored in bar code and read by a light pen, or enter your own chords and melody via the keyboard, with full editing and repeat facilities. 3-way replay; Automatic; One Key Play; Melody Guide (lights above the keyboard indicate the next note to play). Split keyboard; 20 superb instrument voices; 16 rhythm accompaniments; fingered or auto chords with walking bass and arpeggio; fill-in and effect buttons. 37 1/4 x 13 1/8 x 5 inches. Weight: 12.5kg (27.6lbs).

CT-601. As 701 but without programming functions **£395**

CATALOGUE of latest CASIO calculators, watches and keyboards available on request. 15 1/2p stamp appreciated.

PRICE includes VAT, P&P. Delivery normally by return of post
Send your Company Order, cheque, postal order or phone your Access, Visa or Barclaycard number to the UK's leading CASIO Specialists:

Dept. WW
38 Burleigh Street, Cambridge.
CB1 1DG. Tel: 0223 312866

TEMPUS

WW - 086 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1982

LOTS OF NEW ILP ENCAPSULATED PRE-AMPS- COMPATIBLE WITH ALL ILP MODULES

Suddenly, instead of two ILP encapsulated pre-amps, there are eight - everything from the simple mono pre-amp (HY6), through mixing mono pre-amps (HY12 and HY69), to a dual stereo pre-amp (HY71). Plus a new guitar pre-amp (HY73).

Each gives the very best reproduction from your equipment that your money can buy, and all are protected against short circuit and wrong polarity.

All ILP modules are compatible with each other - combine them to create almost any audio system. Every item carries a 5 year no quibble guarantee and includes full connection data.

So send your order today - the Freepost coupon needs no stamp.



PRE-AMPS

Model No.	Module	What it does	Current required	Price inc. VAT	Price ex. VAT
HY 6	Mono pre-amp	Provides inputs for mic/mag. cartridge/tuner/tape/auxiliary, with volume/bass/treble controls.	10 mA	£7.41	£6.44
HY 9	Stereo pre-amp	Two channels. mag. cartridge, mic + volume control.	10 mA	£7.71	£6.70
HY 12	Mono pre-amp	Mixes two signals into one, with bass/mid-range/treble controls.	10 mA	£7.71	£6.70
HY 66	Stereo pre-amp	Two channels, with inputs for mic/mag. cartridge/tape/tuner/auxiliary, with volume/bass/treble/balance.	20 mA	£14.02	£12.19
HY 69	Mono pre-amp	Two input channels: mag. cartridge mic, with mixing and volume/treble/bass controls.	20 mA	£12.02	£10.45
HY 71	Dual stereo pre-amp	Provides four channels for mag. cartridge/mic with volume control.	20 mA	£12.36	£10.75
HY 73	Guitar pre-amp	Provides for two guitars (bass + lead) and mic with separate volume/bass/treble and mixing.	20 mA	£14.09	£12.25
HY 75	Stereo pre-amp	Two channels, each mixing two signals into one with bass/mid-range/treble controls.	20 mA	£12.36	£10.75



For easy mounting we recommend: B 6 mounting board for modules HY6-HY13 £0.90 inc. VAT. (0.78 ex. VAT.) B 66 mounting board for modules HY66-HY77 £1.12 inc. VAT. (0.99 ex. VAT.) All modules are encapsulated and include clip-on edge connectors. All operate from +15V minimum to +30V maximum, needing dropper resistors for higher voltages. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered.

C. O. D. - add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following
ILP modules _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____ WW/44

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone (0227) 54778 Technical (0227) 64723; Telex 965780.



ELECTRONICS LTD

STAY AHEAD. STAY WITH US


WW - 082 FOR FURTHER DETAILS

CX80 COLOUR MATRIX PRINTER

New low price
£795 + V.A.T.

At last a low-cost Colour Matrix Printer for Text, Graphics, Histograms, Colour VDU Dumps, etc.

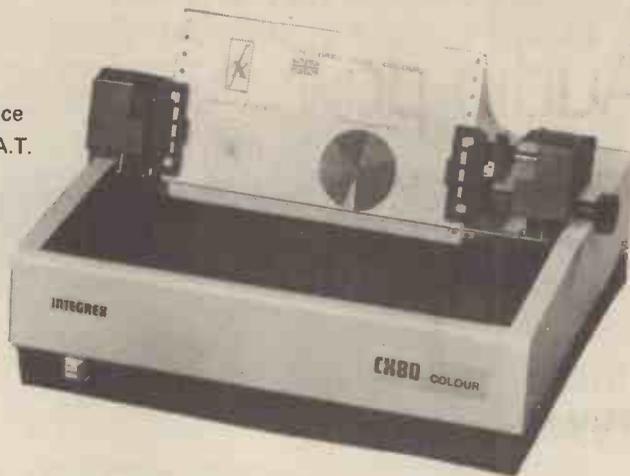Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.



Compatible with most microprocessors, prints in 7 colours – sophisticated internal programme makes the CX80 easy to use.

Dot Addressable + 15 user programmable characters, 96 ASCII and 64 graphics characters in rom. Centronics interface with RS232 and IEEE488 options. Apple II interface gives dot for dot colour dump. New viewdata interface prints out two pages side by side in full colour. See Prestel 200650.

The CX80 is a product of our own design and development laboratories. It represents a British breakthrough in colour printer technology. Colour brochure on request. OEM pricing available.

INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432. Telex: 377106



Metal cased 9" PM101

CROFTON MONITOR


10 MHZ Bandwidth
P4 Standard

Also available
with P31

Price on application

Plastic cased 12"

NEW-PRINCE MONITOR

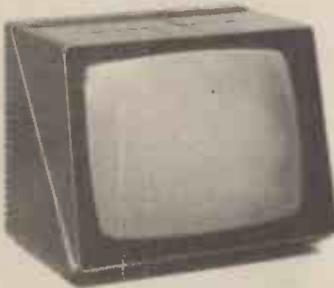

High resolution
24 MHZ Bandwidth

P31 (green) Standard
P4 high resolution
standard

Price on application

DEALER OEM enquiries welcome
CROFTON ELECTRONICS LTD
35 Grosvenor Road, Twickenham, Middx TW1 4AD
01-891 1923/1513. Telex: 295093

POWER SUPPLIES

HIGH QUALITY COMBINATION SWITCH MODE AND STATIC POWER SUPPLIES

Model No.		Price
AV81	5V 8s.....	£28
AV82D	12V 5A + 1A disc drive supply.....	£29
AV83	+5V 8A + 12V 800mA -12 50mA. -5V 10mA. + 25V 30mA.....	£33
AV84	+5V 8A. + 12V 50mA. +25V 30mA.....	£33
AV86	Transformer/Rectifier and Mounting Plate, Fuses.....	£18

Prices inc. VAT

Please add £1.20 p.&p. to order. All units are supplied on a satisfaction or money back basis and carry a full guarantee.


Send cheque/P.O. to:

AVALON ELECTRONICS
Ship Lane, Farnborough, Hants
Tel. 0252 511098
Trade and other enquiries welcome

WW - 072 FOR FURTHER DETAILS

ANY MAKE-UP
OR COPY
QUERIES CONTACT
BRIAN BANNISTER
01-661 3500
extension 3561

Audio power meter

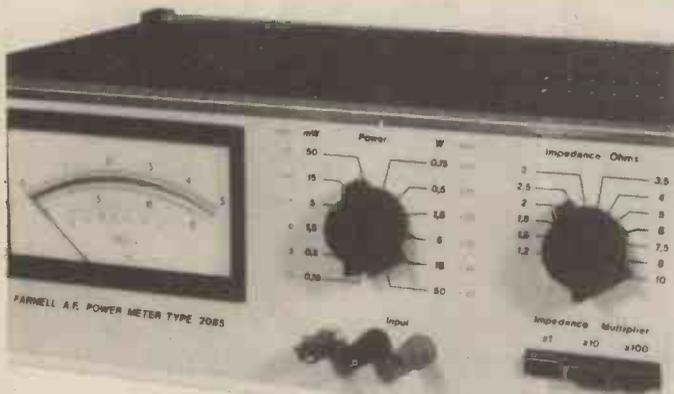

Wide range:

- * 30Hz to 30k Hz * 10 μ W to 50W
- * 1-2 to 1000 Ω * mains/battery
- * decibel scale - 18dBm to + 47dBm



FARNELL INSTRUMENTS LIMITED
SANDBECK WAY · WETHERBY
WEST YORKSHIRE LS22 4DH
TELEPHONE (0937) 61961

WW - 077 FOR FURTHER DETAILS

SUPERSEM

PLYMOUTH 0752 21256

MEMORIES AT UNFORGETTABLE PRICES

	1-24	25-99	100+	1,000+
4116 P-3 200ns.....	.90	.85	.80	.75
2114 LP 450ns.....	.90	.87	.85	.80
2708k 450ns.....	2.70	2.50	2.30	2.25
2716k 450ns.....	2.45	2.30	2.10	2.00
2732k 450ns.....	3.85	3.65	3.60	3.25
8981 P-45 Cmos.....	2.25	2.15	2.05	1.85
8725 S 200ns.....	7.05	6.55	6.05	5.55
K4164 200ns.....	5.00	4.75	4.50	4.25
8039 8-bit.....	3.05	2.90	2.75	2.45
8080AP CPU.....	2.15	2.05	1.95	1.75
8085A CPU.....	2.80	2.65	2.50	2.20
8155P + Timer.....	3.10	2.95	2.80	2.50
8156P + Timer.....	3.45	3.25	3.05	2.65
8212P i/o Port.....	1.10	1.05	1.00	.85
8216 Bus Driver.....	1.05	1.00	.95	.85
8224P Clock Gen.....	1.30	1.20	1.15	1.05
8226P Bus + B/Drives.....	.92	.87	.82	.75
8228P System Cont.....	2.25	2.15	2.05	1.85
8243P i/o Exp.....	2.00	1.95	1.90	1.80
8251AP Prog. Int./Face.....	2.60	2.50	2.40	2.30
8253P Prog. Int./Time.....	3.60	3.40	3.20	2.85
8255AP Perip./Inter.....	2.25	2.15	2.05	1.85
8257P DMA Cont.....	3.75	3.65	3.35	3.00
8259 Inter Cont.....	3.60	3.40	3.20	2.85
8279P Key Disp.....	4.60	4.50	4.00	3.50
4044 P-3 300ns.....	1.90	1.80	1.70	1.55

Please add V.A.T. to all orders

FAST DELIVERY : TOP QUALITY

Phone 0752 21256

SUPERSEM

Export enquiries welcome

3rd Floor
 Britannic House
 Drake Circus
 Plymouth PL4 8AQ

WW - 085 FOR FURTHER DETAILS

MIXERS, FADERS, VU METER DRIVERS AND MORE - ALL NEW FROM ILP!

Just some of the 28 new amazingly compact modules from ILP Electronics, Britain's leader in electronics modules — you'll find more new products in the amps and pre-amps advertisements.

All ILP modules are compatible with each other — you can combine them to create almost any audio system. Together they form the most exciting and versatile modular assembly system for constructors of all ages and experience.

Every item from ILP carries a 5 year no quibble guarantee and includes full connection data. So send your order on the Freepost coupon below today!

MIXERS

Model No.	Module	What it does	Current required	Price inc. VAT	Price ex. VAT
HY 7	Mono mixer	Mixes eight signals into one.	10 mA	£5.92	£5.15
HY 8	Stereo mixer	Two channels, each mixing five signals into one.	10 mA	£7.19	£6.25
HY 11	Mono mixer	Mixes five signals into one — with base/treble controls.	10 mA	£8.11	£7.50
HY 68	Stereo mixer	Two channels, each mixing ten signals into one.	20 mA	£9.14	£7.95
HY 74	Stereo mixer	Two channels, each mixing five signals into one — with treble and bass controls.	20 mA	£13.17	£11.45

AND OTHER EXCITING NEW MODULES

Model No.	Module	What it does	Current required	Price inc. VAT	Price ex. VAT
HY 13	Mono VU meter	Programmable gain/LED overload driver.	10 mA	£6.84	£5.95
HY 67*	Stereo headphone driver	Will drive stereo headphones in the 4 ohm-2K ohm range.	80 mA	£14.20	£12.35
HY 72	Voice operated stereo fader	Provides depth/delay effects.	20 mA	£15.07	£13.10
HY 73	Guitar pre-amp	Handles two guitars (bass and lead) and mic with separate volume/bass/treble and mix.	20 mA	£14.09	£12.25
HY 76	Stereo switch matrix	Provides two channels, each switching one of four signals into one.	20 mA	To be announced	
HY 77	Stereo VU meter driver	Programmable gain/LED overload driver.	20 mA	£10.64	£9.25

For easy mounting we recommend:

B 6 mounting board for modules HY6 -HY13 £0.90 inc. VAT (0.78 ex. VAT.)

B 66 mounting board for modules HY66-HY77 £1.12 inc. VAT (0.99 ex. VAT.)

*All modules are encapsulated and include clip-on edge connectors. All operate from \pm 5V minimum to \pm 30V maximum, needing dropper resistors for higher voltages. HY67 can be used only with the PSU 30 power supply unit. Modules HY6 to HY13 measure 45 \times 20 \times 40mm. HY66 to HY77 measure 90 \times 20 \times 40mm.

FP 480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by ILP for use with any two power amplifiers of the same type to double the power output obtained and will function with any ILP power supply. In totally sealed case, size 45 \times 50 \times 20mm with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8 Ω . Contributory distortion less than 0.005%. Price: £5.51 inc. VAT. (Ex. VAT £4.79.)

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd.; cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules.....

Total purchase price.....

I enclose Cheque Postal Orders Int. Money Order


Please debit my Access/Barclaycard No.....

Name.....

Address.....

Signature..... WWS/4

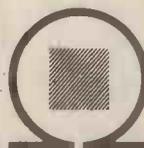Post to: ILP Electronics Ltd, Freepost 2 Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
 Telephone (0227) 54778 Technical (0227) 64723 Telex 965780



ELECTRONICS LTD

STAY AHEAD. STAY WITH US

WW - 083 FOR FURTHER DETAILS

Practical Computing and Your Computer present...

THE Computer Fair

*Personal computers
Home computing
Small business systems*


April 23-25, 1982
Earls Court,
London

Friday & Saturday: 10am – 6pm
Sunday: 10am – 5pm

Admission £2.00 adults
£1.00 children under 16.

At The Computer Fair you can see and compare an enormous range of personal and home computers. Find out what they can do and which one would suit you best. Talk to the experts and discover for yourself how much – or how little – you need to spend. Choose from an amazing abundance of software programs and packages, cassette units, VDU terminals and scores of computer games.

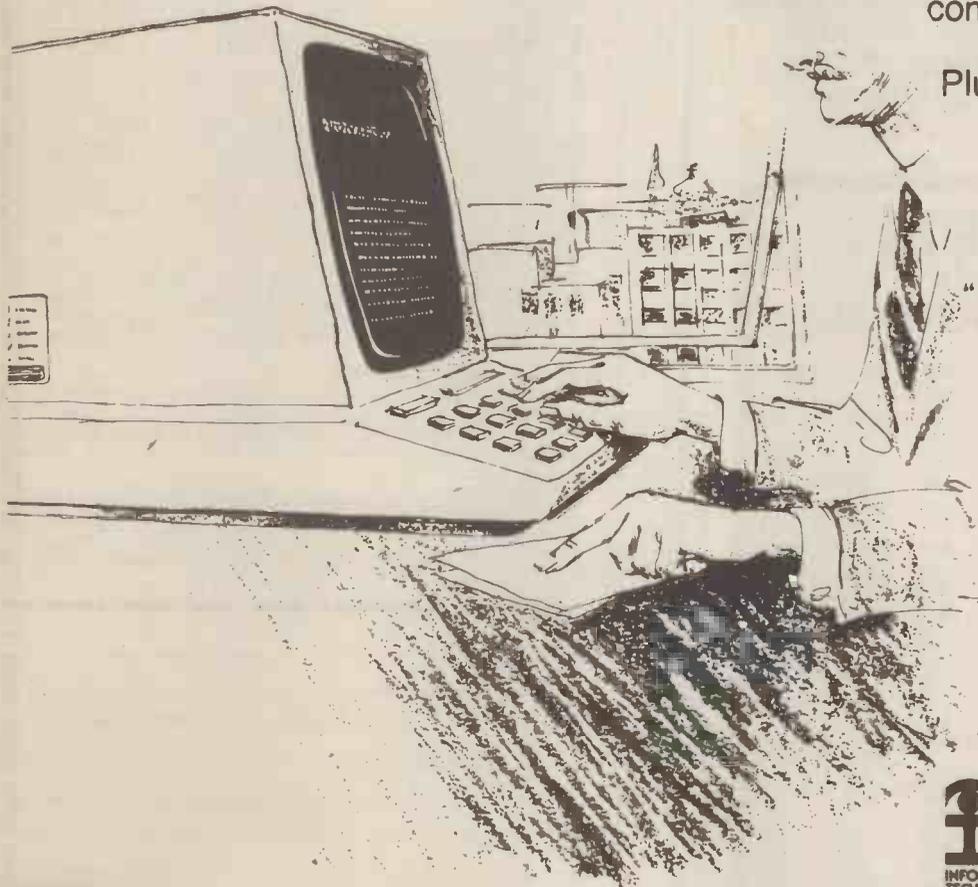Swap your views and know-how with hundreds of other home computer enthusiasts – and find out a whole lot more from computer professionals.



Plus – The Micro Mouse Contest.

Come and watch the incredible ingenuity of computer controlled "mice" and how they find their way (or not!) to the centre of a maze. The knockout heats and the Euromicro British Final can all be seen at The Computer Fair!

Bring the whole family – don't miss this opportunity of bringing computers into your everyday life.



Bringing computers to everyday life

RF POWER TRANSISTORS—EX-STOCK

TYPE	£	TYPE	£	TYPE	£	TYPE	£
2N3137	1.88	2N4933	7.80	BLX13C	15.05	BLY53A	7.33
2N3375	5.27	2N5070	10.09	BLX14	25.70	BLY53AP	7.33
2N3553	1.09	2N5071	12.10	BLX65	1.67	BLY55	9.40
2N3632	6.03	2N5090	8.44	BLX66	4.91	BLY83	7.45
2N3733	6.13	2N5102	9.44	BLX67	5.41	BLY84	7.25
2N3866	0.92	2N5590	7.85	BLX68	7.29	BLY85	6.02
2N3924	1.66	2N5591	10.21	BLX69X	21.15	BLY87A	6.43
2N4040	9.29	2N5641	4.68	BLX91A	8.84	BLY87C	6.43
2N4041	10.97	2N5642	8.11	BLX92A	13.06	BLY88A	8.66
2N4127	9.18	2N5643	12.44	BLX93A	19.19	BLY89C	9.10
2N4128	11.03	2N5913	2.34	BLX94A	35.79	BLY89A	12.65
2N4129	12.08	2N6080	5.94	BLX95	44.59	BLY69C	11.90
2N4427	1.15	2N6081	9.87	BLX98	84.95	BLY91A	6.95
2N4429	9.89	2N6082	10.17	BLY33	1.87	BLY91C	6.90
2N4430	11.30	2N6083	11.08	BLY34	1.07	BLY92A	9.25
2N4431	12.50	2N6084	12.27	BLY35	7.50	BLY92C	9.06
2N4932	5.50			BLY36	6.60	BLY93A	13.40
						BLY93C	11.40

COMMUNICATION TUBES—EX-STOCK

TYPE	£	TYPE	£
4-65A	35.10	6155/QY3-125	47.30
4-125A	42.90	6155/QY3-125(AEL)	
4-250A	50.70		22.40
4-400A	58.20	6156/QY4-250	45.30
4-1000A	331.00	6883B	4.30
4CX250B	38.00	7527/QY4-400	42.00
4CX350A	55.00	7854/YL1060	53.80
4CX1500A	498.00	8042	16.50
4CX1500B	319.00	A2426	19.25
4X150A	36.00	QQV03-10	5.60
4X500A	175.00	QQV03-10(AEL)	2.54
5B254M	23.40	QQV03-20A	39.00
5B255M	23.40	QQV03(AEL)	17.20
6F33(AEL)	15.62	QQV06-40A	43.60
12E1	16.94	QQV06-40(AEL)	11.70
13E1	141.00	QQV07-50	68.00
5763	3.25	QV08-100	125.00
6080	5.40	QY5-3000A	234.00
6146A	3.80	TBL2-300	286.00
6146B	4.07	TT21	19.76
		TT22	19.76

SEND NOW FOR PRICE LISTS SHOWING QUANTITY DISCOUNTS

AEL

EXPORT SPECIALIST

SEND FOR DETAILS TO,
AERO ELECTRONICS (AEL) LTD.
GATWICK HOUSE
HORLEY, SURREY, ENGLAND
TEL. (02934) 5353
TELEX 871116 (AERO G)
CABLES AERO G TELEX HORLEY

WW - 026 FOR FURTHER DETAILS

TEMPERATURE MEASUREMENT

6-way thermocouple temperature to voltage conversion unit. Output 1mV/°C suitable for connecting to DMM. Range -30 to 400°C.

TEMPMATE I PRICE £49.50 (+ 50p carriage + VAT)

MAPLE INSTRUMENTS

C/O VISTRA INSTRUMENTATION LTD. Phone 093-67 4223
465/7 CREWE ROAD, SANDBACH, CHESHIRE CW11 0QT

WW - 089 FOR FURTHER DETAILS

64K EPROM PROGRAMMER

- ★ Copy/Program/Verify 2758/2716/2732/2732A/2532/2764/2564/68764 + 128K and 256K EPROMS.
- ★ Program up to 8 EPROMS simultaneously from internal RAM or master socket.
- ★ Stand-alone or remote operation.
- ★ Download code directly via RS232 interface.
- ★ Price £560 + £9 Delivery.

Available through:

Sunrise Software Ltd.
Ropamida House, Launton Road, Bicester, Oxon
(08692) 45187

WW - 057 FOR FURTHER DETAILS

ILP POWER SUPPLIES— MOST WITH ILP TOROIDAL TRANSFORMERS

Space-saving, efficient ILP power supplies are designed to give you flexibility in planning audio assemblies. Nine of the eleven models have toroidal transformers manufactured on new cost-efficient high technology machines in our own factory. So we keep the quality up, and the price down.

ILP power supplies are compatible with all other ILP modules — combine them to produce almost any audio system. All carry the ILP 5 year no quibble guarantee and include full connection data.

So send your order on the Freepost coupon below today!



POWER SUPPLY UNITS

Model No.	For use with	Price inc. VAT	Price ex. VAT
PSU 30	±15V combinations of HY6/66 series to a maximum of 100 mA or one HY67.	£5.18	£4.50
	The following will also drive the HY6/66 series except HY67 which requires the PSU 30.		
PSU 36	1 or 2 HY 30.	£9.32	£8.10
PSU 50	1 or 2 HY 60.	£12.58	£10.94
PSU 60	1 x HY 120/HY 120P/HD 120/HD 120P.	£15.00	£13.04
PSU 65	1 x MOS 120/1 x MOS 120P	£15.32	£13.32
PSU 70	1 or 2 HY 120/HY 120P/HD 120/HD 120P.	£18.31	£15.92
PSU 75	1 or 2 MOS 120/MOS 120P	£18.63	£16.20
PSU 90	1 x HY 200/HY 200P/HD 200/HD 200P.	£18.63	£16.20
PSU 95	1 x MOS 200/MOS 200P.	£18.77	£16.32
PSU 180	2 x HY 200/HY 200P/HD 200/HD 200P or 1 x HY 400/1 x HY 400P/HD 400/HD 400P.	£24.54	£21.34
PSU 185	1 or 2 MOS 200/MOS 200P/1 x MOS 400 1 x MOS 400P.	£24.68	£21.46

All models incorporate ILP toroidal transformers except PSU 30 and PSU 36 which include our own laminated transformers.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these modules, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered. C. O. D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order


Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____ WW6/4

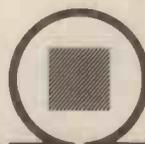Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone (0227) 54778 Technical (0227) 64723 Telex 965780



ILP ELECTRONICS LTD

STAY AHEAD. STAY WITH US

WW - 084 FOR FURTHER DETAILS



TEXAS INSTRUMENTS TECHNICAL PUBLICATIONS

FROM BA ELECTRONICS LIMITED

SEMICONDUCTOR DATA BOOKS	PRICE EACH
MOS MEMORY	£5.67
BIPOLAR MEMORY	£2.72
OPTO ELECTRONICS	£5.72
OPTO ELECTRONICS THEORY AND PRACTICE	£7.72
LINEAR CONTROL CIRCUITS	£5.72
VOLTAGE REGULATORS	£6.22
BIPOLAR MICROCOMPUTER COMPONENTS	£6.22
INTERFACE CIRCUITS	£8.72
T.T.L.	£10.22
9900 FAMILY DATA BOOK	£11.72
SOFTWARE DEVELOPMENT HANDBOOK	£14.62
MICROSYSTEMS DESIGNERS HANDBOOK	£5.22
"UNDERSTANDING" SERIES	
SOLID STATE ELECTRONICS	£5.67
DIGITAL ELECTRONICS	£5.67
MICROPROCESSORS	£5.67
COMMUNICATIONS SYSTEMS	£5.67
CALCULATOR MATH	£5.67
COMPUTER SCIENCE	£5.67
OPTRONICS	£5.67
BASIC ELECTRICITY SERIES	
BASIC A.C. CIRCUITS	£10.22
BASIC ELECTRICITY AND D.C. CIRCUITS	£11.47
POCKET GUIDES	
VOLUME ONE - TTL	£5.22
VOLUME TWO - LINEAR AND INTERFACE	£4.22

HOW TO ORDER
Books are available by direct mail. Send your order together with a cheque (payable to BA Electronics Ltd.) for the appropriate amount to:
BA ELECTRONICS LIMITED
MILLBROOK ROAD
STOVER TRADING ESTATE
YATE, NR. BRISTOL BS17 5NX
Please note prices include packaging and postal charges

WW - 091 FOR FURTHER DETAILS

reprints

If you are interested in a particular article / special Feature or advertisement published in this issue of
WIRELESS WORLD
why not take advantage of our reprint service.
Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)
For further details contact
Michael Rogers, IPC Electrical-Electronic Press Ltd. Phone 01-661 3036 or simply complete and return the form below.

To **Michael Rogers, Reprints Department**
Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS

I am interested in copies of the article / advertisement headed featured in **WIRELESS WORLD** on page(s) in the issue dated

Please send me full details of your reprint service by return of post.

Name

Company

Address

Tel. No.

TECHNOMATIC TECHNOMATIC TECHNOMATIC

★ SPECIAL OFFER ★

See our prices on opposite page for updated list for popular RAMS, ROMS & CPUs.



UNIVERSAL INTERFACE FOR PETS

Self-contained all-purpose interface unit for new or old PETs providing a range of parallel input/output ports, 16-bit timers, ultrafast multi-channel Analogue to Digital Converters, Digital to Analogue Converters and Programmable Sound Generators. Internal Motherboard System allows easy upgrading. Built-in PSU.
£149 + £2.50 P&P
SEND FOR DETAILS



ATOM

Basic 8K + 2K

Kit £120 Built £135
Fully Expanded 12K + 12K £185
(P&P £2.50/Unit)

F.P. ROM £20 1K RAM (2 x 2114L) £2
Full range of Hardware and Software available.
Send for the Atom List



BBC Microcomputer Memories, Expansion Sockets and Connectors now available.

TELETEXT DECODER

(As described in Elektor Oct./Nov./Dec., '81)
Kit for complete decoding board and keyboard £85 + £1 P&P
Reprint of articles £1.25

SOFTY II



An Ideal software development tool. A program can be developed, debugged and verified and then can either be committed to an EPROM or the program can be used in any host computer by plugging the SOFTY into its EPROM socket.
See the review in Sept. '81 PE for the various facilities provided on SOFTY.
SOFTY complete with PSU, ROMULATOR & TV leads
£169 + £2 P&P



MENTA

New Z80 Development System. Plugs into TV and cassette recorder. 40-key direct ASSEMBLER/EDITOR, 24 bits of I/O. Ideal for study, microcontrol and robotics. Power supply and TV lead incl.
£115 + £1.50 P&P

UV ERASERS

UV1B £42 Up to 6 EPROMS	UV140 £61.50 Up to 14 EPROMS	UV141 £78 As UV140 but with timer
-------------------------------	------------------------------------	---

All above ERASERS fitted with the safety interlocks to avoid accidental exposure to UV rays.
Remember, UV rays are very dangerous to human eyes and skin.

TECHNOMATIC TECHNOMATIC TECHNOMATIC



TITAN TRANSFORMERS AND COMPONENTS
 DEPT. WW, CENTRAL HALL CHAMBERS
 DUNCOMBE STREET, GRIMSBY
 SOUTH HUMBERSIDE DN32 7EG
 Mail order. Prices include 15% V.A.T.
 Send for our catalogue

12/24V RANGE PRI 220/240V				30/60V RANGE PRI 120/220/240V				CASED AUTOTRANSFORMERS			
SEC: 00000000 00000000				SEC: 00000000 00000000				240V LEAD IN: 115V 2PIN SOCKET OUT			
TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P
242	0.3	1.70	0.50	124	1	3.30	1.57	56W	20	6.60	0.94
213	10.50	2.65	0.94	126	2	6.36	1.57	64W	80	8.43	1.57
71	2	2.77	1.20	127	4	7.86	1.90	4W	150	10.86	1.90
18	4	3.98	1.57	125	6	11.78	2.10	69W	250	13.17	2.10
68	3	3.46	1.57	123	8	14.72	2.40	67W	500	20.46	2.40
85	5	6.06	1.57	40	10	17.10	2.40	84W	1000	30.24	2.50
70	6	6.67	1.57	120	12	19.44	2.55	95W	2000	54.83	5.50
108	8	8.03	1.57	121	16	27.70	2.90	73W	3000	78.67	7.00
116	12	9.31	2.10	122	20	32.05	4.50				
17	16	11.46	2.25	189	24	37.02	5.50				
115	20	13.69	2.25								
187	30	19.23	2.55								
232	40	27.61	5.00								
226	60	35.35	4.50								


15/30V RANGE PRI 220/240V				48/96V RANGE PRI 120/220/240V				LINE ADJUSTMENT AUTOTRANSFORMERS			
SEC: 00000000 00000000				SEC: 00000000 00000000				0 200 210 220 230 240 250			
TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P
112	1	0.50	2.84	430	1	0.5	4.69	415C	50	2.31	0.94
79	2	1.0	3.29	431	2	1	7.84	416C	100	3.46	0.94
3	4	2	6.18	432	4	2	12.94	417C	200	4.00	1.20
20	6	3	7.19	433	6	3	14.62	418E	350	6.26	1.57
21	8	4	8.52	434	8	4	20.04	419F	500	6.74	1.90
51	10	5	10.57	435	10	5	28.75	420E	750	8.33	2.10
117	12	6	11.94	436	12	6	36.16	421F	1000	11.64	2.25
88	16	8	16.14	437	16	8	39.47				
89	20	10	18.54								
90	24	12	20.57								
91	30	15	23.63								
92	40	20	33.21								

25/50V RANGE PRI 120/220/240V				AUTOTRANSFORMERS 240/220-115V				MANS ISOLATORS (SAFETY SCREEN)			
SEC: 00000000 00000000				SEC: 00000000 00000000				PRI 120/220/240V SEC 600V 00000000 00000000			
TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P	TYPE	VA	PRICE	P/P
102	1	0.50	3.29	25	65	3.90	1.20	149F	60	8.40	1.90
103	2	1.0	4.09	64	80	4.82	1.20	150F	100	9.71	1.90
104	4	2	7.65	4	150	6.21	1.57	151F	200	13.84	2.25
105	6	3	9.09	69	250	7.54	1.57	152F	250	16.69	2.40
106	8	4	12.24	53	350	9.73	2.10	153F	350	20.77	2.80
107	12	6	16.15	67	500	11.70	2.40	154F	500	26.03	2.90
118	16	8	22.46	83	750	13.51	2.25	155F	750	36.75	5.50
119	20	10	27.05	84	1000	18.31	2.55	156F	1000	47.42	6.50
109	24	12	32.44	95	2KVA	34.36	5.50				
				73	3	64.74	5.50				
				57	5	97.85	7.00				
				101	10	179.05	10.50				

WW - 093 FOR FURTHER DETAILS

AN EPROM COPIER

from £49.90

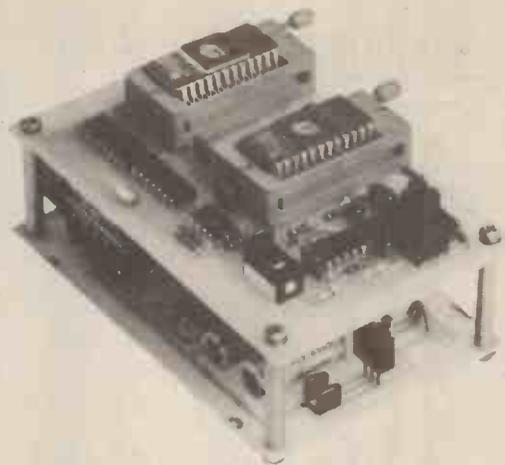

Yes, the new Delph EPROM copier will copy 2516, single rail 2716, and 2532 EPROMs. No computer required. Just insert the ROMs and press the button. Programming is finished when the LED goes out. 2K-4K select switch on board.

Price List

- EC1 Copier (standard d.i.l. sockets) £49.90
- EC2 Copier (zero insertion force sockets) £56.00
- PS2 Power supply board (fits underneath) £18.50
- EC3 Copier (EC2 assembled with PS2 in case) £79.95
- RE4 Plug-in 4K ROM Emulator £56.00

Plus £2.50 carriage and insurance plus VAT at 15%.

Delph Electronics Ltd.
 4 Deeping Road,
 Baston, Peterborough.

Tel: (07786) 535.

WW - 092 FOR FURTHER DETAILS

ATTENTION ZX81 Owners!

The April issue of Your Computer is full of good things:

- How to write your own adventure game for the ZX81
- Review of the growing range of ZX81 boards and control ports
- How to adapt the ZX81 to use Atari joysticks

Also in this issue:

- Expanding your VIC20. Tim Hartnell looks at peripherals and add-ons
- BBC graphics. A further look at the colour and graphics facilities of the BBC micro.

All this, PLUS our regular features and pages of program listings and games for YOUR micro.

Why not place a regular order to avoid disappointment?
 Or take out a subscription by completing the coupon.

To: Marketing Department, Room 316,
 IPC Electrical Electronic Press,
 Quadrant House, The Quadrant,
 Sutton, Surrey SM2 5AS

Please send me 12 issues of Your Computer
 I enclose cheque/PO for £8 UK/£14 Overseas,
 payable to IPC Business Press Ltd

Name

Address

WW09

At all leading newsagents.
 Price 60p.

C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG. Telephone: 01-747 1555
Telex 291429 01-994 6275

9.30 a.m.-6 p.m.
MON.-SAT.
CONTINUOUS

STABILISED POWER SUPPLIES

FARNELL A15: 210/240V 1P. Dual Op. 12-17v per rail at 100mA. Remote sensing, current limit protection. (164x130x38mm), with manual. £12.

FARNELL 7/3SC: 120/240V 1P. Adjustable current limit. Remote sensing. (188x96x93mm.) Two versions available: 15V at 2A or 30V at 1A. £15 ea.

COUTANT OA2: Op. amp, psu, 120/240V 1P. Dual Op. 12-15v at 100mA. (138x80x45mm.) £12 ea. or 2 for £22.

BRANDENBURG Photomultiplier PSU. 19in. rack mounting. Metered, current limit protection.

374 300V-1KV at 5mA 376 660V-1K6V at 10mA
375 500V-1K5V at 6mA. All models £40.

PIONEER MAGNETICS POWER SUPPLIES . . . 5V 150 amp, output input 115 vac. (Switchmode) Price £120 each.

Various other makes of power supplies in stock. Please send for lists. S.A.E. please.

D TO A CONVERTERS

15MHz, 8 BIT

By Micro Consultants Ltd. 50Ω cable drive op. Linearity 0.25%, max. 0.125% typ. Settling time: 2V step 70nS typ. 2MV step 50nS colour television transmission standard. Diff. gain 0.5% diff. phase shift 0.5° types rad 802 and MC2208/8. Unused. Ex-maker's pack.

SPECIAL OFFER PRICE: £20

NEW IN STOCK

A range of high quality transformers SPECIALLY WOUND for us. By buying direct we can offer these superb SPLIT PRIMARY & SECONDARY transformers at highly competitive prices.

6VA	0-12, 0-12		0-12V, 0-12V	3.80
	0-15, 0-15	2.20	0-15V, 0-15V	
12VA	0-4V5, 0-4V5		0-20V, 0-20V	
	0-6V, 0-6V		0-6V, 0-6V	
	0-9V, 0-9V		0-9V, 0-9V	
	0-12V, 0-12V	2.99	0-12V, 0-12V	4.75
	0-15V, 0-15V		0-15V, 0-15V	
	0-20V, 0-20V		0-20V, 0-20V	
20VA	0-4V5, 0-4V5		0-30V, 0-30V	
	0-6V, 0-6V		0-40V, 0-40V	8.90
	0-9V, 0-9V			

CASED AUTO TRANSFORMERS

240V Cable input. American outlet socket.

Rating	Price	750VA	£23.50
300VA	£13.00	1000VA	£27.00
500VA	£18.00	1500VA	£36.00

Other Transformers

1.2VA. 6-0-6, 9-0-9, 12-0-12	all 1.14	12VA	
1.5VA		0-12, 0-12	2.96p
12V	80p	18VA	
15V	1.00p	9-0-9	2.64p
2.4VA		24VA	
12-0-12	1.48p	12-0-12	3.36p
24V(pcb)	1.00p	12V	4.84p
4VA		30VA	
5-0-5	1.25	15-0-15	3.62p
6VA		36VA	
24V	1.50	9-0-9	4.70p
		50VA	
		0-2-4-6-8-10	6.00p

VERO PRODUCTS

Veroboard 0.1 Copper		Apple proto boards	4.00p
2 1/2x3 3/4	70p	Vero boxes - 2 tone grey/white plastic boxes	
2 1/2x5	80p	4x2x1	1.99p
3 3/4x3 3/4	80p	4x2x1 1/2	2.22p
3 3/4x5	90p	4 1/2x2 1/2x1 1/2	2.51p
2 1/2x17	2.40p	7 1/2x4 1/4x2 1/2	3.75p
3 3/4x17	3.15p	7x4 1/2x2 1/4 (alinfrent)	3.51p
4.7x17	4.20p	Vero ABS Black Plastic Boxes	
0.1 plain		4 1/2x3 1/4x1 1/2	78p
2 1/2x3 3/4	50p	7x4 1/2x2 1/4	1.42p
3 3/4x5	75p	Veropins 45p/100. Stand off 45p/100. Track cutters £1.18p.	
V-Q Board	1.30p		
DIP Board (113x156mm)	3.26p		
RS DIP Board (100x160mm)	3.00p		

4 MILLION I.T.T. ELECTROLYTICS NEW AND BOXED NOW IN STOCK

EN 1212 AXIAL EN 1235 RADIAL

The whole range available at unbeatable prices. Send for list.

5 million Disc Ceramics in stock. Ceramic plate. Multi-layer ceramic. Low voltage discs. Monolithics. Ceramics. High voltage discs. Subminiature plate, epoxy cased. Send for lists or please phone for details.

MULLARD: Series 106 Computer grade electrolytics 10,000µF at 16V. Brand new and boxed 39p ea.
SPRAGUE: Series 36D Computer grade electrolytics 3,300 at 40V. Brand new and boxed 35p ea.
SIEMENS: Procond Radial Polyester Film Capacitors. 10µF at 63V. Brand new Only 40p
Quantity available

VIDEO GAME BOARD

FIELD GOAL VIDEO GAME, BY TAITO. A top quality board complete with 6800 CPU system with 2716 eeproms with circuit diagram, plus all connections for either colour or black and white monitors (TV sets). Price £20 + VAT £3. P/P £2.55.

POWER SUPPLY KIT TO SUIT + circuit diagram. Price £15 + VAT £2.25. P/P £3.45.

2 x 22-WAY GOLDPLATED DOUBLE-SIDED 0.156" EDGE CONNECTORS to suit videoboards. Price £1.60 pair + VAT 24p. P/P included.

THE COMPLETE KIT £46 INCLUSIVE. Full details on application.

WE PURCHASE

Surplus component stocks, redundant materials, obsolete computers, for cash.

We also collect - distance no object. Just call:

C. T. Electronics (Acton) Ltd.


267 & 270 Acton Lane, London W4 5DG

Telephone 01-747 1555; 01-994 6275

Telex 291429

This advertisement is mainly of our excess stockholding. We also have excellent stocks of semiconductors, hardware, cables, etc., etc. For further details send for our lists and retail price catalogue, phone or visit our shop. All prices are exclusive of VAT (and P&P). Minimum Mail Order £5 + P&P + VAT. Government departments, schools, colleges, trade and export welcome.


Aaron from M.I.T.(Eng.) your best buy!

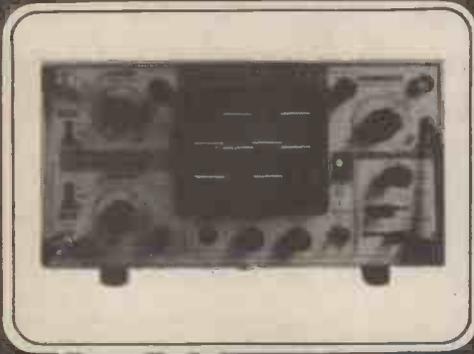

BS-310
BATTERY/MAINS PORTABLE
OSCILLOSCOPE

- 15MHz Bandwidth.
- Dual Channel with 95mm Internal Graticule CRT.
- Sensitivity - 2mV/Div. to 10V/Div.
- Sweep Time - 0.5µSec/Div. to 0.5 Sec/Div.
- X-Y Operation Facility.

£313.00

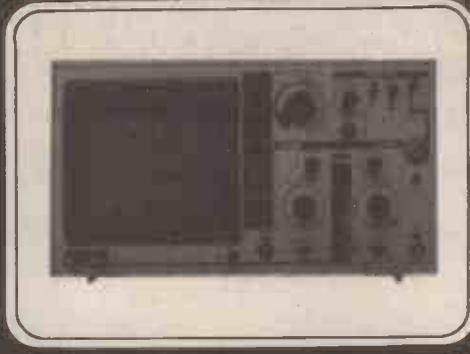

BS-601
20 MHz DUAL TRACE OSCILLOSCOPE

- Sensitivity - 5mV/Div. to 20V/Div.
- Sweep Time - 0.2µSec/Div. to 0.5 Sec/Div.
- "Z" Axis Intensity Modulation.
- 6" Internal Graticule CRT.
- Component Test Facility.

£245.00



MM-100
HAND HELD MULTIMETER

- 3½ Digit, ½" LCD Display.
- D.C. Volts - 200 mV to 600V.
- A.C. Volts - 200V and 1,000V.
- D.C. Current - 200µA to 200mA.
- Resistance - 200Ω to 2MΩ

£47.00

Micro Image Technology
(Engineering)Ltd

M.I.T. (Engineering) Ltd.

Greenhill Industrial Estate, Riddings, Derby DE55 4DA, England.
Telephone: Leabrooks (0773) 604411 10 Lines Telex: 377008G

WW - 087 FOR FURTHER DETAILS

BLINDED by SCROGGIE'S



Unravel the mysteries of radio and electronics with a copy of Foundations of Wireless and Electronics by M.G. Scroggie. 250,000 enthusiasts and students have already used this remarkable book to master the elementary principles of electronics. In fact, many of today's radio and electronic engineers were weaned on Scroggie.

The book is written clearly and concisely in Mr. Scroggie's well-known and often humorous style. He assumes no previous technical knowledge and only uses mathematics where essential.

Order your copy now —

Postage and packing is £1.10 each copy in the UK, £1.30 overseas (surface mail).

only
£5.25
+ p. & p.

Please send me _____ copy/copies of Foundations of Wireless and Electronics by M.G. Scroggie at £5.25 per copy plus postage and packing as above.

I enclose my cheque/postal order for £ _____ made payable to IPC Business Press Ltd.

Name _____

Address _____

Return to: **General Sales Manager, IPC Electrical-Electronic Press Ltd.,**
Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS England.

Registered Office:
Quadrant House,
The Quadrant, Sutton,
Surrey SM2 5AS

ELECTRONIC BROKERS

SPRING CLEARANCE SALE

INCREDIBLE BARGAIN OFFERS. FIRST COME FIRST SERVED.

HEWLETT PACKARD

9830A PROGRAMMABLE CALCULATOR with 8K memory extended I/O ROM, string variables ROM, 1 serial interface and 3 parallel interfaces. **£750.00**

MONITORS

BALL MIRATEL TTL150 15" green phosphor CRT (NEW) **£65.00**
 BALL MIRATEL TVX90 9" white phosphor CRT (NEW) **£40.00**
 BALL MIRATEL 9" Monitor installed in plastic case with space for keyboard (used, tested) **£55.00**
 All above include power supplies and require separate vertical, horizontal and sync input.

PRINTERS

DATA DYNAMICS KSR390 (refurbished) **£225.00**
 ELECTROSENSITIVE (Aluminised) Paper rolls 300' x 8 1/2" (NEW) **£2.50**
 IBM 735 I/O WRITER (as seen) **£99.00**
 SCOPE DATA SERIES 200 Electrostatic RO Printer, RS232, 120 cps (AS SEEN) **£99.00**
 SEIKOSHA GP80 PRINTER (NEW) **£175.00**
 SEIKOSHA INTERFACES & ACCESSORIES (NEW)
 Apple Interface **£47.50**
 IEEE (Pet) Interface **£47.50**
 RS232 Interface **£47.50**

TRS80 Interface (for expanded version) **£15.00**
 TTL Interface **£20.00**
 Friction Feed Adaptor **£18.50**
 TELETYPE 33 PRINTER MECHANISM (refurbished) **£75.00**
 TEXAS 725 PORTABLE (Spares only) **£125.00**
 TEXAS 733 KSR (as seen) **£225.00**

KEYBOARDS

CLARE-PENDAR KB3 (tested) **£25.00**
 EDGE CONNECTOR KB15P (NEW) **£1.50**
 GEORGE RISK 56-STATION KEYBOARD in steel enclosure incl. power supply (NEW) **£55.00**
 NUMERIC KEYPAD KB710 (NEW) **£5.00**
 TMS 5000 ENCODER (as used in KB6) (NEW) **£8.50**
 CLARE REED KEYSWITCHES - Brand new surplus (per 100) **£5.00**
 (Offers invited for lot - approx 16,000)

MISCELLANEOUS

CALCOMP 12" DRUM PLOTTER model 565 (As Seen) **£250.00**
 FACIT 4060 P/T PUNCH C/W 5106 Control Unit (As Seen) **£375.00**
 HOUSTON DP3-1/5 FLAT BED PLOTTER (incomplete as seen) **£325.00**
 NOVAMETRIC MICROSYSTEM EVK300 (As Seen) **£110.00**
 RACAL MODEM model 26 (As Seen) **£199.00**

SHUGART SA450 Double-sided mini-floppy (NEW) **£250.00**

TEST EQUIPMENT

AVO 7 Refurbished **£60.00**
 ADVANCE Switching Power Supply MG5-20AN (115V) **£30.00**
 BOONTON 280AP VHF Q meter **£50.00**
 BRUEL & KJAER 2105 Freq meter **£225.00**
 COSSOR 4000 Oscilloscope 50MHz **£200.00**
 COSSOR 4100 Oscilloscope 75MHz **£400.00**
 GENRAD Sound Level meter 1981 **£200.00**
 GENRAD Sound Level meter 1983 **£75.00**
 HEWLETT PACKARD 741B AC/DC Diff Voltmeter **£300.00**
 HEWLETT PACKARD 1402A Scope Plug in **£25.00**
 HEWLETT PACKARD 1404A Scope Plug in **£50.00**
 HEWLETT PACKARD 1416A Scope Plug in **£25.00**
 HEWLETT PACKARD 34702A + 34740A 4 1/2 digit DMM **£125.00**
 WAYNE KERR Testomatic TM30 **£125.00**
 OSCILLOSCOPE CRT D13-57G/26 Brand New Surplus **£17.50**
 TEKTRONIX CRTS 500 Series Brand New Boxed **P.O.A**

All items are sold in 'AS IS' condition
 All prices subject to carriage (unless collected) and VAT.

Cash with order only

Inspection is invited at our address Mon/Fri 9-1, 2-5

Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex 298694

WW - 204 FOR FURTHER DETAILS

MARKETING Ltd.



VITAVOX
 HIGH QUALITY LOUDSPEAKERS

D.S.N. Marketing is a newly established subsidiary company, part of a group of companies centred around one of the U.K. market leaders in electro-acoustic equipment, established for over 50 years. We make use of the extensive research facilities on our premises, which include a large anechoic chamber and B & K measuring equipment, to ensure the highest quality of our products.

Our System 191 has won 'State of the Art' awards in the discerning world of Japanese audiophiles.

Our music loudspeakers endure and excel in the nomadic extremes of a rock band on tour.

Our robust B60 and B80 microphones meet the tough intrinsically safe requirements of the offshore oil industry.

Our blast-proof, water-tight loudspeakers meet the stringent needs of the Armed Services.

We are approved to DEF. STAN 05-21.

'Hi-Fi', high power, high seas, high ambient noise - whatever the demand - Vitavox have something to offer.

For further details on the entire Vitavox range of cone loudspeakers, pressure drivers, horns, dividing networks and complete speaker systems, please complete this coupon.

- Please send further details of:
- VITAVOX loudspeaker equipment
 - BULLET loudspeaker components
 - D & R mixing consoles
 - HELIOS mirror balls

NAME

ADDRESS

D.S.N. MARKETING LTD, Westmorland Road, London NW9 9RJ
 Telephone: 01-204 7246. Telex: 895 4243.
 Trade, Wholesale, O.E.M. & Export enquiries welcome.



VISA

WW 4/82

WW - 043 FOR FURTHER DETAILS



COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30

BULK BUY SPECIALS

RAM SCOOP

4116 200 NS 8 for £12.95
4164 200 NS £8.50 each
2102-650 NS 8 for £5.50
INC VAT

25 WAY "D" CONNECTORS

	50+	100+
25p	1.70	1.10
25s	1.90	1.20
ALL + VAT		

WIRE WRAP SKTS.

24 Pin Vero 28p
14 Pin Gold 22p
16 Pin Gold 24p
100 PCS Min Ord.

C10
DATA CASSETTES
10 for £5.75
Inc. VAT

RF CONNECTORS

50Ω BNC PLG 50p
75Ω BNC PLG 50p
PL259 PLG 40p
SO239 SKT 35p
100 PCS MIN ORD.

TELETYPE ASR33 I/O TERMINALS




From £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232C serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT

KSR33 With 20ma loop interface £125.00 + VAT.
Sound proof enclosure £25.00 + VAT

"OLIVETTI TE300" PRINTER/TERMINALS

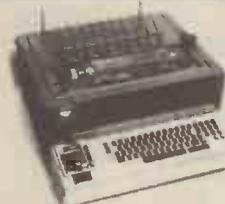

A complete I/O terminal with integral 8 hole paper tape punch and reader, full ASCII keyboard, 120 column printer, and control unit. The printer is capable of 150 baud with a serial TTL or balanced input/output sold in good overall condition but untested. Complete with circuit unguaranteed. Connect direct to your micro at ONLY £99.00 + £11.50 carr + vat.

MPU EXPERIMENTORS +5v+12v-12v+24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!!! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 160mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:
+5v @ 2 amps DC +12v @ 800 ma DC
-12v @ 800 ma DC +24v @ 350 ma DC
and if that's not enough a fully floating 5v output @ 50 ma DC which may be sensed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 240v mains input. They are ex GPO and may have minor scratches on the front panels, they are sold untested but in good internal condition. £16.50 each + £2.50 p+p complete with circuit and component list. Transformer guaranteed. HURRY WHILE STOCKS LAST!!

HIGH SPEED DATA MODEMS

A superb piece of engineering made by SE Labs Ltd. to a "no cost spared" spec for the GPO, the Modem 12 is a synchronous Modem for use on DATEL 2412 services, or other data links. Many features include switchable V26 modulation, 2400 baud full duplex 600/1200 standby, auto answer, 4 wire or 2 wire operation. Self test, LED status indication, CMOS technology, modular construction, original cost over £700 each. Believed brand new, supplied complete with PSU etc.
£185.00 + £9.50 carriage + VAT.
*Perme 'on may be required for connection to PD lines

DISTEL ©

"Dial our Database!"
Get information on 1000's of stock items and order via your computer. 300 baud on 01-689 6800
18.30 to 0900 6 days a week and all day Sundays. IT'S FREE!

DIABLO S30 DISK DRIVES

Another shipment allows us to offer you even greater savings on this superb 2.5 MB (formatted) hard disk drive. Two types are available both fully refurbished and electronically identical, the only difference is the convenience of changing the disk packs.

S30 front loader, pack change via front door £550 + vat

S30 fixed, pack change via removal of top cover £295 + vat

+ & - 15v PSU for 2 drives £125 + vat

Carrage & insurance on drives £15.00 + vat fully DEC RK05, NOVA, TEXAS compatible further info on controllers etc on request.

MAINS FILTERS

Professional type mains filters as used by "Main Frame Manufacturers" ideal for curing those unerving hang ups and data glitches. fit one now and cure your problems! Suppression Devices SDS A10 5 amp £6.95
Corcom Inc F1900 30 amp £13.95 + pp £1.00

DC SYSTEM SUPPLY

Professional fully cased fan cooled system supply. Standard 240 V ac input with the following DC outputs 5V @ 11 amps +15-17v @ amps -15-17v @ 8amps and +24v @ 4 amps. All outputs are fully crowbar protected and the 5 volt output is fully regulated. Sold tested and in a new or little used condition complete with circuit £55.00 + carr £8.50 + vat DIM 15.5" x 9" x 6"

NATIONAL MA1012 LED CLOCK MODULE

- ★ 12 HOUR
- ★ ALARM
- ★ 50/60 HZ



The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 11" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am, pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only Suitable transformer £1.75. £5.25

ELECTRONIC COMPONENTS & EQUIPMENT

66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kts £ 4.75 + pp £1.25 5kts £ 6.75 + pp £1.80
10kts £11.75 + pp £2.25 20kts £19.99 + pp £4.75

THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER

A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities which all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232/V24 serial interface - 7 xtal controlled baud rates up to 9600 ★ 194 characters per line ★ Parallel interface ★ Handshakes on serial and parallel ports ★ 4 Type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in 2708 eproms easily reconfigured for custom fonts etc.

All this and more, not refurbished but BRAND NEW At Only £525 +VAT

OPTIONAL EXTRAS * lowercase option £25.00 * 16k buffer £30.00 * Second tractor for simultaneous dual forms £85.00 * Floor stand £45.00 * specialist carriage £19.00 All items plus VAT data sheet on request.

8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today, the only difference being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring, IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc compatible. Supplied BRAND NEW with user manual and 90 day warranty.

7100 single sided £225.00 + 9.50 carr + vat
7200 double sided £295.00 + 9.50 carr + vat
full technical manual £20.00 alone £9.00 with drive, refund of difference on purchase of drive. Data sheet on request.
SPECIAL new, KODE PSU, drives 2 DRE drives £39.99 + carr + vat
8" single sided, single or double density diskettes £1.80 each £1.50 for 10 inc. lib case + vat.

COOLING FAN SPECIAL

Keep your equipment cool and reliable with our range of professional fans.
ETRI 99XU01 Miniature equipment fan 240v ac working DIM 92 x 92 x 25 mm BRAND NEW complete with finger guard. Makers price £16 our price £10.25
BUHLER 69.11 22 micro miniature 8-16 vDC reversing fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC serv. motor, almost silent running ideal portable equipment. Life in excess of 10,000 hours. BRAND NEW manufacturers price £32.00 our price £13.95
MUFFIN/CENTRAL cooling fans, tested ex equipment 240v £6.50, 115v £5.50 + p+p £1.90
KOOL TRONICS Powerful snail type blower gives massive air movement with centrifugal rotor DIM as a cube 8" x 8" x 6" air aperture 2.5" x 2.5" with flange fixing. BRAND NEW 110v 50 Hz ac working ONLY £9.95 + £1.90 p+p.



Dept. W.W., 64-66 Mellort Rd., Thornton Heath. MAIL ORDER
Croydon, Surrey. Tel: 01-689 7702 or 01-689 6800 INFORMATION

Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00 Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Boni Fida account orders minimum £20.00. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.

SOFTY 1 & 2 EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMs or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT.
Softy 2 for 2716/2732 £169 + VAT
Write of phone for more details.

9" VIDEO MONITORS

Ex-equipment 9" Motorola Video Monitors 75Ω composite input, tested but unguaranteed. £39.99 + £7.50 carriage + VAT. Complete with circuit.

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s, triacs, diodes, bridge rect., etc. etc. All devices guaranteed brand new full spec. with manufacturer's markings, fully guaranteed. 50p bag £2.95 100p bag £5.15 TTL 74 Series.

A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed at I.C.'s full spec. 100+ £6.90 200+ £12.30 300+ £19.50

RCA FULLY CASED ASCII CODED KEYBOARDS

IDEAL - TANGERINE, OHIO ETC.

Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc. £43.95
VP611 Same as VP601 with numeric pad. £54.95
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. £64.26
VP616 Same as VP606, with numeric pad, Plug and cable for VP601, VP611 £2.25 £84.34
Plug for VP606, VP616 £2.10

Post, Packing and Insurance. £1.95
ORDER NOW OR SEND FOR DETAILS.

5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply. Supplied complete with circuit at only £10.95 + £1.75pp. Believed working but untested, unguaranteed.

Appointments

Advertisements accepted up to 12 noon Monday, 5th April, for May issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £13.50 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £2.50 per line, minimum 5 lines. (Prepayable.)
BOX NUMBERS: £1.50 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.)
PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to IPC Business Press Ltd.



ECM

ALWAYS AHEAD WITH THE BEST!

£5,000-£15,000

COMMUNICATIONS: VHF - UHF - MICROWAVE - TROPO - SATCOM

COMPUTERS: MINI - MICRO - ATE - PROCESS CONTROL - SIMULATION: Hardware & Software

DATA COMMS: MODEM - MUX - TELEGRAPHY - MESSAGE SWITCH - PACKET SWITCH

Where does your skill and interest lie - Design? Test? Service? Software? Consultancy? or perhaps Research?

- * Our clients are drawn from all sectors of industry;
- * There are opportunities for Managers, Project Managers, Engineers and Technicians.
- * Most UK locations and some Overseas.
- * Make your first call count - Contact **MIKE GERNAT** on 076 384 676/7 (usually until 8 p.m.)

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED

148-150 High St., Barkway, Royston, Herts SG8 8EG.

(1471)

**BBC TRANSMITTER DEPARTMENT
MOTSPUR PARK, SURREY**

ENGINEER, VACUUM DEVICES

£8,950-£10,924 p.a.
(according to qualifications and experience)

We require an Electronic Engineer, with C.Eng./degree/HNC qualification, plus a minimum of three years' post-qualification experience in the design, manufacture or application of vacuum devices used in broadcast transmission.

Specific areas of involvement and responsibility include the application, acquisition, testing and distribution throughout the BBC of all types of vacuum devices and in particular the valves and klystrons, etc., used at transmitting stations, computerised stock control and in staff management.

Relocation expenses will be considered and benefits include 5 weeks' annual holiday. Men and women are equally eligible to apply.

Requests for application forms to **The Engineering Recruitment Officer, BBC, Broadcasting House, London W1A 1AA**, quoting reference **82.E.1140/WW** and enclosing an addressed envelope at least 9" x 4".

BBC

(1544)



CAPITAL
APPOINTMENTS LTD.

**CAPITAL HOUSE
29-30 WINDMILL
STREET
LONDON W1P 1HG
TEL: 01-637 5551**

THE UK's No. 1 ELECTRONICS AGENCY

Design, Development and Test to £14,000
Ask for Brian Cornwell

SALES to £15,000 plus car
Ask for Maurice Wayne

FIELD SERVICE to £12,000 plus car
Ask for Paul Wallis

We have vacancies in ALL AREAS of the U.K.

Ask for a Free Jobs List

Telephone: 01-637 5551 (3 lines)

(291)

Sound Attenuators Limited require an

Electronics Engineer

to work on the active control of sound in ducts. We require a graduate in electronics with at least two years' practical experience and an interest in acoustics. The project involves the implementation of basic research already undertaken at the University of Essex. The successful candidate must demonstrate self-reliance, practical ability and a keen interest in seeing the project through to a successful conclusion.

Write in the first instance, enclosing a full c.v. to:

**Mr. A. T. Fry
Sound Attenuators Ltd.
Eastgates, Colchester, Essex
Tel: 0206 866911**

(1566)

Systems Design Team

Satellite Communications Ground Terminals

Marconi Space and Defence Systems are Europe's acknowledged leaders in the development of advanced systems for aerospace and satellite communications.

To meet the growing interest in satellite communications we are strengthening the specialist teams working on sophisticated satellite ground terminals - offering total involvement from initial design and development through to implementation.

We need ambitious and enthusiastic men and women with several years' post-graduate experience in the design, development or operation of ground terminals or in other communications systems drawing on similar RF techniques. A knowledge of military satellite communications would be a distinct advantage.

SYSTEMS MANAGER

Aged 30+ must be able to combine high level technical expertise with the man-management skills necessary to weld a group of systems professionals into a closely knit team. At least 4 years' experience in a similar role is essential.

SENIOR SYSTEMS ENGINEERS

Applicants should be in their late 20's to early 30's and have had relevant in-depth experience.

SYSTEMS ENGINEERING

We have a number of openings for graduates in their mid-20's with an Honours degree in Engineering, Physics or Mathematics and 1-2 years' post-graduate experience.

These are key career positions carrying salaries that fully reflect their importance, as well as an attractive range of benefits, including relocation assistance where necessary.

To discuss any of these posts with one of our senior specialists or project managers, telephone Bill Seton, Ext. 18, or Liz Kahn, Ext. 22, on (01) 954 2311 or write to them at Marconi Space and Defence Systems Ltd., The Grove, Warren Lane, Stanmore, Middlesex, HA7 4LY.

Marconi
Space & Defence Systems



1546

CAMBRIDGE HEALTH DISTRICT
(TEACHING)
PHYSICS DEPT.
ADDENBROOKE'S HOSPITAL
HILLS ROAD, CAMBRIDGE

Medical Physics Technician Grade II (£6,668-£8,316 p.a.)

An electronics technician is required to provide maintenance and support services to the CT Head Scanner at Addenbrooke's Hospital and to electro-medical equipment in the thoracic surgical unit, Papworth Hospital. Applicants should hold an appropriate HNC or equivalent qualification and have several years' experience in the field of electronics. (Mini-computer experience advantageous).

For further details contact
Mr P. E. Ward,
Principal Physics Technician
Addenbrooke's Hospital
Hills Road, Cambridge CB2 2QQ
Tel: (0223) 245151 ext. 471

Application form and job description from the Personnel Dept. Ext. 7350.

INSTITUTE OF PSYCHIATRY AUDIO-VISUAL TECHNICIAN

A vacancy exists for an Audio-Visual Technician at this postgraduate medical school and associated teaching hospital. Applicants should be experienced in maintenance of television equipment and preferably hold relevant technical qualifications: eg City & Guilds Course 222 or 224.

Salary according to experience and qualifications on Whitley Council Medical Laboratory Scientific Officer scale currently £4,958 p.a. to £6,993 p.a. plus London Weighting £932 p.a.

For application form with job description please write to the Assistant Secretary, Institute of Psychiatry, De Crespigny Park, Denmark Hill, London SE5 8AF or telephone 703 5411 Ext 214 quoting reference MJC/WV.

(1547)

LEADING LONDON ADVERTISING AGENCY Requires

YOUNG ENGINEER

to take charge of all in-house audio and video equipment including Rank Cintel, Sony 1" and studio cameras. Applicants should send details of experience to Box 1552, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. (1552)

HIGH-LEVEL VACANCIES FOR HIGH-FLYING ENGINEERS!

GRADUATE SENIOR SYSTEMS ENGINEER to take charge of design and development of microwave frequency synthesizers, navigation transponders and other sub-systems. Must have strong technical background, have experience, and be over 30. Salary at least £10,000. Bedfordshire.

TECHNICAL SUPPORT ENGINEER. OCR systems. Large peripheral experience essential including CDC/Pertec/Data Products range. National and international travel. To £9,500. S.W. London.

SENIOR DIGITAL DESIGNER. Applied research in radar signal processing. Experience high speed real-time HW/SW. Knowledge of bitslice processors, array multipliers useful. To £11,000. South Coast.

SENIOR ENGINEER to establish feasibility of LSI or VLSI chip sets for signature verification products and carry through the design up to production, whilst also assisting in design of discrete version. Salary up to £10,000. Surrey.
Please telephone or send c.v. to:

Charles Airey Associates

13/16 Jacob's Well Mews, George Street, London W1H 5PD
Tel. 01-486 9250

"PROBABLY THE BEST KNOWN SUPPLIER OF ELECTRONIC ENGINEERS IN THE COUNTRY" Financial Times (1357)

THE THOMSON FOUNDATION TELEVISION COLLEGE

An

ENGINEERING LECTURER

and an

ASSISTANT ENGINEERING LECTURER

are required at the College to join a team of staff training engineers from developing countries, in Television and Radio. The successful candidates will have had a minimum of 5 years' or 3 years' experience respectively and broadcasting technology, and will hold an appropriate degree, HND or equivalent.

Salaries: Lecturer - £9,251 by 5 increments to £11,504;
Asst. Lecturer - £7,284 x 5 to £9,052.

The posts are pensionable, based at Glasgow where the residential training is conducted, but involve also short assignments abroad each year for in-country training.

Please write or phone for application form to Principal, Thomson Foundation TV College, Kirkhill House, Newton Mearns, Glasgow G77 5RH (041-639 1021).

(1545)

Electronics – up to £7,500

Have you an Electronics Qualification? Could you apply it to Scientific Instruments?



then this could be just the job you're looking for. It offers variety and real opportunity to apply both skill and design initiative to the solution of a whole range of technical problems of a one-off nature.

We are:

- * a leading pharmaceutical company with world-wide interests.

You will:

- * help to design, modify and where necessary repair advanced scientific instruments and computers in the Physical Chemistry Department.

Probably in your 20's, male or female, you should ideally have:

- * formal training up to HNC or equivalent
- * an interest in scientific measurement techniques
- * sound practical experience of electronics.

We offer:

- * a competitive salary dependent upon experience and ability
- * day release opportunities for further study
- * Flextime working
- * very modern facilities in a newly opened building.

Interested? For an application form please ring our automatic telephone answering service on 01-650 6541, giving your name, address and quoting reference no. WRL/176.

Alternatively write to A. G. Murdoch, Personnel Officer, The Wellcome Research Laboratories, Langley Court, Beckenham, Kent BR3 3BS.



Wellcome

(1543)



THEATRE PROJECTS

Theatre Projects Special Projects Group is a manufacturing company specialising in audio and lighting control equipment for the broadcast, film and theatre industries. We are currently seeking the following additional staff to provide a firm foundation for expansion.

PRODUCTION MANAGER

Must be capable of planning and controlling all aspects of a mixed batch production/custom manufacturing environments often working to tight schedules. Will be required to plan and set up own manufacturing facility when we shortly move to new premises. The applicant should have 2-3 years in a related area of responsibility and be educated to HNC or degree standard. He/She will be part of the core of management of this part of the company.

PROJECT ENGINEER — BROADCAST AUDIO SYSTEMS

The candidate must have prior engineering design experience and a broad understanding of the design/manufacturing environment. He/She will be required to oversee projects from concept/quotation through to installation. Specialist skills in either circuit or mechanical design are required along with familiarity of the broadcast environment. Both posts command a salary from £7,500, which is negotiable according to the skills and experience of the applicants.

Theatre Projects, 11 Marshalsea Road, London SE1. Tel: 01-403 3838

(1562)

REPORTER/STAFF WRITER MIDDLE EAST ELECTRONICS

An enthusiastic journalist, ideally with technical qualifications (Degree or HND) and experience, to work on Middle East Electronics.

This magazine, which is going monthly in May, is read by senior electronic engineers in the Middle East and the Editor is looking for a responsible number two to develop the journal's potential.

Writing and subbing skills essential plus knowledge of the industry and, preferably, experience of developing countries and their technology problems. Computer science background an advantage.

Our UK office is located in Morden, Surrey, but we offer opportunities for travel. Salary £7,613 p.a. (subject to NUJ consultation).

For an application, please write to, or telephone Ray Ashmore, Editor, Middle East Electronics, Crown House, London Road, Morden, Surrey. Tel: 01-543 3051.

Salary and conditions is accordance with the IPC/NUJ agreement.

We are an equal opportunity employer.

IPC BUSINESS PRESS
THE LARGEST COMPLEX OF BUSINESS
AND SPECIALIST PUBLICATIONS IN THE WORLD.

(1563)

Research & Development Engineers

YOUR OPPORTUNITY TO ADVANCE BROADCAST TELEVISION TECHNOLOGY

Tremendous growth and success has resulted in career opportunities at Sony Broadcast Ltd., a company established four years ago to specialise in the high technology field of broadcast television equipment. The Advanced Developments group is part of an international R&D team committed to pioneering new technology. Applications are invited from experienced engineers capable of contributing to one or more of the following activities:

- Digital Video Systems
- Digital Audio Systems
- Audio/Video Digital Recording
- Mathematical Modelling
- Computer Control Systems
- Microprocessor Applications
- Analogue Video Development

The successful candidates will join one of the following sections:-

Research & Development

Established as a world leader pioneering digital recording, we are currently extending our range of activities. The R/D team is responsible for studying the development and application of digital video and audio processing techniques. In addition increasing support is required from theoretical studies and computer simulation.

Special Design Projects

Increasing use is being made of computer and microprocessor based equipment for signal routing and control in studio centres. Hardware/Software engineers are required for the development of automated broadcasting and remote control systems. This can include "one off" developments designed to customer requirements.

Appointments will be made at all levels and applicants should have an honours degree or equivalent qualification. Attractive salaries are offered together with first class conditions of employment and relocation assistance will be given where appropriate.

If you are interested contact:-

Mike Jones,
Senior Personnel Officer



Sony Broadcast Ltd.

City Wall House
Basing View, Basingstoke
Hampshire RG21 2LA
United Kingdom
Telephone (0256) 55 0 11
(1540)

An Electronics Engineer

Is needed to make original contributions within a lively internationally collaborative space sciences programme. The post will be concerned initially with a magnetospheric sounding satellite and will include some travel to Germany and the U.S.A.

Applicants, holding a degree or equivalent chartered institution status, should be able to offer two or three years of proven practical design experience, preferably with VHF/UHF systems, digital and analogue circuits or micro processor application.

The appointment, at Professional and Technical Officer Grade II level, attracts a starting salary between £6,557 and £7,520, with increments to £8,697.

Some assistance with the expenses incurred in house sales/purchase may be available.

The Laboratory, situated 18 miles south of Oxford, offers excellent working conditions. Benefits include an extensive bus system, generous holidays and sickness leave and a non-contributory superannuation scheme.

Apply by phone or letter to Lorna Bird, Ext. 510, quoting VNO 17.
Closing date: 8th April 1982.

Science and Engineering Research Council
Rutherford Appleton Laboratory
Chilton, Didcot, OXON, OX11 0QX. Telephone Abingdon 21900.

(1548)

£25,000?

S/W QUALITY ENGINEERS

with PDP 11/34 and RSX experience to work on Software to 0521 standards. To £10,000 - Hants.

SERVICE ENGINEER

To carry out field maintenance on Business Computer Systems. To £10,000 + car - London.

PROJECT MANAGER

To control the development of Industrial Process Control Systems. To £11,500 - Bucks.

DEVELOPMENT ENGINEER

to work on Static Inverter Systems. To £12,000 - London S/W.

R.F. DESIGN ENGINEER

to lead the development of a new Low Power Transmitter. To £10,000 - Yorks.

DESIGN ENGINEERS

with R.F. Micro Wave, Analogue, Digital or Software experience to work on new Instrumentation Systems. To £11,000 - Herts.

CLIVEDEN CONSULTANTS

87 St. Leonard's Road
Windsor, Berks.
Windsor (07535) 57818/58022
24-hour service (1119)

CLIVEDEN

CHARING CROSS HOSPITAL MEDICAL SCHOOL (University of London) MEDICAL PHYSICS TECHNICIAN

An enthusiastic person is required in the Department of Anaesthesia in Charing Cross Hospital Medical School.

Work involves a full range of physiological measurements on patients in the operating theatres and Intensive Care Unit, and maintenance of equipment.

Assistance will also be required in the development of instrumentation for measurements and techniques in the cardiovascular, respiratory and electro-physiological fields.

The successful candidate should be qualified in at least one of these fields and show an interest and willingness to learn about the others.

An aptitude for meeting the many demands that working in a small team places on the individual will also be sought.

Salary will be within the range of £4,958-£6,993 per annum plus £859 London Weighting Allowance, according to qualifications and experience.

Applications on forms obtainable from The Secretary, Charing Cross Hospital Medical School, The Reynolds Building, St. Dunstan's Road, London W6 8RP (tel: 01-748 2040 ext 2067) within three weeks of the appearance of this advertisement.

(1533)

DIGITAL EXPERIENCE? FIELD SUPPORT R & D AND SALES VACANCIES IN COMPUTERS NC, COMMS., MEDICAL VIDEO, ETC.

For free registration ring
0453 883264
01-290 0267

LOGEX

ELECTRONICS RECRUITMENT SERVICE
LOGEX HOUSE, BURLEIGH, STROUD
GLOUCESTERSHIRE GL5 2PW
TEL 0453 883264, 01-290 0267 (321)

Electronics Engineers

Glaxo have the following opportunities at their Research Central Services Unit at Greenford, which is involved in the design and maintenance of electronic equipment needed for experimental work:

ELECTRONICS DESIGN ENGINEER

£6705 pa to £9475 pa

to carry out design work on a wide range of laboratory equipment employing analogue, digital and microprocessor techniques. Candidates, aged 25+, should be qualified to degree level or equivalent with several years general design experience.

SERVICE TECHNICAL OFFICER/ENGINEER

£5874 pa to £9210 pa

to be responsible for general servicing work. Candidates, qualified to Higher National Certificate or City & Guilds Full Technical standard should have several years experience of analogue and digital equipment, preferably in a laboratory environment.

Starting salaries will be between the figures quoted which include London Allowance and will reflect qualifications and experience.

In addition the Company operates a bonus scheme and non-contributory pension scheme. Assistance with relocation expenses will be available in appropriate cases.

Please write or telephone for an application form to: Miss E. M. Butler, Personnel Department, Glaxo Group Research Limited, Greenford Road, Greenford, Middlesex UB6 0HE. Tel: 01-422 3434, ext. 2707 quoting reference number ZH/418.

Glaxo Group Research Ltd.

(1641)

GWENT HEALTH AUTHORITY

ELECTRONIC AND BIO-MEDICAL EQUIPMENT MAINTENANCE TECHNICIAN GRADE II

This is an established post offering wide scope and opportunity in the development of electronic and bio-medical services. The successful candidate will be responsible to the Area Engineer for the testing and maintenance of a variety of electronic and bio-medical equipment throughout the area, and will also be responsible for the development of policy regarding maintenance contracts.

The technician will be based at a purpose-built workshop at Allt-Yr-Yn Hospital, Newport, and will be responsible for an establishment of two junior grade technicians, but authority has been given for the further development of this service.

Applicants should be in possession of ONC/HNC (or equivalent qualifications) in Electrical/Electronic Engineering, and should have wide experience of Health Service electronic equipment and safety aspects involved. In addition to these requirements, the applicant should be capable of preparing reports and be able to develop and operate a planned preventive maintenance scheme.

Hours: Normally 38 per week.

Salary: £6,668-£8,316

Application form and job description are available from:

The Area Personnel Department
Mamhilad, Pontypool, Gwent

Closing date: 31.3.82

(1559)

TRAINEE BROADCAST ENGINEERS

ITN needs more engineers to support its expanding programme of news coverage – expansion which is expected to continue through the 80s with the development of the Channel Four news service.

We have a number of vacancies for Engineering Trainees, vacancies which could give you the opportunity to start a career in Broadcasting Television Engineering with ITV.

First, we need you to have a firm interest in pursuing a career in the technical branch of broadcasting.

Then you should have completed, or expect this year to complete, theoretical training in Electronic Engineering with a bias towards Television or Audio applications. Qualifications most suitable are T.E.C. Higher Technical Diploma, T.E.C. Higher Technical Certificate or the HND/HNC equivalent.

Initially, you would be involved in a 9-12 month familiarisation period by a rotational attachment to our four maintenance areas and the Projects Department.

After successful training you would be employed on the maintenance or operation of a wide range of broadcast equipment in our Central London Studios near Oxford Circus, from which the ITN national news programmes are networked.

Successful applicants will join ITN in early September, 1982. Starting salaries would lie within the range of £5,120 (at 18) rising to £6,472 at age 20.

If you have the qualifications and the drive to work with us in a busy, lively environment then call us on 01-637 8644 ext 275 or write to

The Manager, Technical Training
ITN House
48 Wells Street
London W1P 4DE

for an application form quoting reference 476099

(1532)

Appointments

Electronics R&D

£8,589

Join us in the forefront
of technology

Senior Engineer – Broadcast Video Equipment

**A challenging role in high technology
Quality Assurance**

Due to significant continued expansion, an excellent opportunity has arisen at the international headquarters of Sony Broadcast, a world leader in professional broadcast television equipment. The Company has an expanding range of high technology products which includes video cameras, VTRs, editing control systems, digital time base correctors and monitors.

An experienced engineer is required to join the Quality Assurance team and assume responsibility for the throughput of cameras and other products. Activities will include close liaison with other engineering departments and will necessitate working to stringent specifications. A knowledge of current camera measurement practices would be advantageous.

Age 25+ applicants should be educated to at least HNC Electronics and have several years engineering experience. The position would suit a self starter who also has the ability to lead and motivate a small team. Prospects for career development are considerable.

We offer a first class working environment in our new prestigious engineering complex, together with an attractive salary and excellent conditions of employment, which include Company pension/life assurance schemes, private medical cover and staff restaurant.

If you are interested please write, giving details of experience and present salary, to Mike Jones, Senior Personnel Officer.

SONY
Broadcast



Sony Broadcast Ltd.
City Wall House
Basing View, Basingstoke
Hampshire RG21 2LA
United Kingdom
Telephone (0256) 55 0 11
1529

HF-VHF-UHF and Microwave

**A challenging and full career in
Government Service**

Candidates, normally aged under 30, should have a good honours degree or equivalent in a relevant subject, but any candidates about to graduate may be considered.

Appointments as Higher Scientific Officer (£6,530-£8,589) or Scientific Officer (£5,176-£6,964) according to qualifications and experience. Promotion prospects.

Please apply for an application form to the Recruitment Officer (Dept WW 4.82), H M Government Communications Centre, Hanslope Park, Milton Keynes MK19 7BH.

1425

Communications Proposals Engineer to £10,500

Join the UK's leading Communications System House specialising in oil field locations.

Palmer EAE require a Proposals Engineer with a broad experience of Multi-Channel Microwave links, P.A. and entertainments systems, standby power supplies, SOLAS and telephone plant.

Applicants should be educated to HNC/DEGREE standard and be familiar with recognised international standards, i.e., C.C.I.R., C.C.I.T.T., etc. Duties will include preparing technical proposals, procurement specifications and procedures relating to installation/commissioning.

This post is based in Great Yarmouth and occasional overseas travel will be required. Excellent terms and conditions are offered including pension scheme, BUPA, relocation expenses, etc.

There are also a number of vacancies for suitably qualified COMMUNICATIONS ENGINEERS and TECHNICIANS to work both in the UK and overseas.

For further information regarding these opportunities on an application form for the post of Communication Proposals Engineer, please telephone:

Mike Futter on Great Yarmouth (0493) 58541

Palmer EAE Limited, Offshore House, Gt. Yarmouth, Norfolk

PALMER EAE

(1560)

TECHNICAL/SERVICE MANAGER

Due to the expansion of our business we are urgently seeking a person capable of setting up and running a pager service department, of maintaining transmitters and of evaluating and commissioning both paper and mobile systems. This is an exciting position in an established company and will appeal to the person who has technical experience and wishes to become involved also in the commercial side of a company with expansion plans for the future. A high salary, car and other benefits are available for the right person.

Send CV to: **P. Sinnot, Managing Director
Pageboy Services (UK) Ltd., Westley House
Trinity Avenue, Bush Hill Park, Enfield
EN1 1HP. Tel. 01-367 4545**

(1516)

CAPE WARWICK LTD.

require

Electronics, Control & Instrumentation Engineers

As an expanding independent testing laboratory we require suitably qualified/experienced engineers to design, arrange, manufacture, commission and maintain test equipments.

Send c.v. or telephone for application forms to:

Mrs. E. Archer
Cape Warwick Ltd.
Cape Road, Warwick
Warks CV34 5DL
Tel: Warwick (0926) 496421
(A Thomas Tillings Company)

(1535)

UNIVERSITY COLLEGE CARDIFF
FACULTY OF SCIENCE

ASSISTANT EXPERIMENTAL OFFICER

Applications are invited for the post of Assistant Experimental Officer in the faculty of science electronics workshop. Duties will include the design, development and maintenance of electronic equipment, particularly microprocessors for both research and teaching.

Applicants should have a degree in electronics or related subject or an equivalent qualification. Experience in microprocessor interfacing techniques and electronic instrument design would be an advantage.

Salary scale O.R. 18 £5,285-£8,925

Applications to the Vice Principal (Administration) and Registrar, University College Cardiff, P.O. Box 78, Cardiff, from whom further particulars may be obtained.

Closing date 2nd April. Ref. No. 2348a.
(1556)

APPOINTMENTS IN ELECTRONICS

to £15,000

MICROPROCESSORS
COMPUTERS - MEDICAL
DATA COMMS - RADIO

Design, test, field and support engineers - for immediate action on salary and career advancement, please contact

Technomark
Engineering and Technical Recruitment

11, Westbourne Grove
London W2. 01-229 9239 (9257)

HARROW COLLEGE OF HIGHER EDUCATION. Audio-visual Aids Technician. Salary to maximum of £6,009 p.a. To supervise the closed-circuit television studio in the Educational Resources Centre and to assist with other audio-visual services. Ability to provide first-line maintenance of video equipment essential. Applications are invited from men or women. Application form obtainable from the Administration Office, returnable by 15 April, Harrow College of Higher Education, Northwick Park, Harrow, Middlesex HA1 3TP. Telephone 01-864 5422, extn 232.
(1554)

R & D OPPORTUNITIES. Senior level vacancies for Communications Hardware and Software Engineers, based in West Sussex. Competitive salaries offered. Please ring David Bird at Rediffusion Radio Systems on 01-874 7281.
(1162)

Microwave Specialists

Communications Satellite Payload Equipment

Marconi Space and Defence Systems, Europe's acknowledged No 1 in the development of advanced satellite systems, are seeking the following specialists to play key roles in new communications satellite projects at their Stanmore location. We would like to hear from suitably qualified and experienced men or women who want the chance to work in a high technology environment that offers total involvement and lots of excitement.

MICROWAVE EQUIPMENT MANAGERS

Will be responsible for an Equipment forming part of the Communication Payload programme. This will involve original design, manufacture and test of breadboards; engineering; qualification and flight model hardware; and will entail liaison with European prime contractors on all aspects of the programme. The programmes are usually of an international nature, requiring high technology designs, coupled with demanding timescales.

MICROWAVE DEVELOPMENT ENGINEERS

Will report to the Equipment Manager and will be responsible for development work on the payload equipments. Tasks will include the design of microwave circuits with the emphasis being on lightweight, high reliability designs including extensive use of MIC technology

Applicants for both positions should hold a degree or equivalent qualification and have had at least 2 years' relevant experience.

Salaries will be negotiable and accompanied by an excellent range of benefits.

To find out more details, write or telephone Bill Seton, Personnel Manager with brief details of your career to date.

Marconi Space and Defence Systems, The Grove, Warren Lane, Stanmore, Middx. HA7 4LY. Tel: 01-954 2311 Extn. 18

Marconi

Space & Defence Systems



1558

ELECTRONICS DEVELOPMENT AND SERVICING:
CANCER HOSPITAL AND RESEARCH INSTITUTE

An

ELECTRONICS TECHNICIAN

is required to join an established group working on development and maintenance of medical and cancer research equipment. The job will entail a fair degree of responsibility and calls for someone able and willing to work as a member of a team. Interest and ability in computing and/or r.f. work would be an advantage. The work will be located at our Institute/Hospital site at Sutton, Surrey, which is well provided with staff amenities. Salary on either Research Officer (£5,600-£7,336 p.a.) or Technician (£4,958-£6,993 p.a.) scale plus London Allowance of £557 p.a. Starting point will depend on qualifications and experience, and opportunities for later promotion to higher scales. Candidates should hold City & Guilds Final Certificate, HNC, BSc or an equivalent qualification in electronics or telecommunications. Further information may be obtained from Mr. John Phelps (01-643 8901).

Applications in duplicate with the names and addresses of two referees should be sent to the Secretary, Institute of Cancer Research, 34 Sumner Place, London SW7 3NU, quoting ref. 301/B/14.
(1549)

WILTSHIRE COUNTY COUNCIL Department of Architectural Services

Appointment of

CHIEF SERVICES ENGINEER

(Salary £11,220-£12,408)

Applications are invited for this post, the duties of which concern the design and provision of electrical and mechanical services for building projects and for the associated maintenance and energy conservation work in buildings throughout the county.

The successful candidate should be a Member of the Chartered Institution of Building Services with sound experience of Mechanical Services and should also be a Member of the Institution of Electrical Engineers.

Application forms and full details may be obtained from the County Architect, County Hall, Trowbridge (Tel. 3641 ext. 2115) quoting reference AR.82.35 and should be returned to him by 19th March, 1982.

(1526)

Appointments

Develop your potential in our future



Founded in 1936, Marconi Instruments today employs some 2,000 people in the design, development, production and marketing of its advanced communications test equipment and A.T.E.

To meet the challenges of tomorrow's markets, we need more electronics designers and technicians. And to turn new ideas into fully operational equipment we need production and service personnel as well.

If you would like to develop your potential in the exciting future of Europe's leading test equipment specialist, complete the coupon and send it to us at the address below:-

marconi instruments

Return this coupon to John Prodger, Marconi Instruments Limited, Freepost, St. Albans, Hertfordshire, AL4 0BR. Telephone: St. Albans 59292
A GEC-Marconi Electronics Company

Name _____	Age _____			
Address _____				

Telephone Work / Home (if convenient) _____				
Years of experience	<input type="checkbox"/> 0-1	<input type="checkbox"/> 1-3	<input type="checkbox"/> 3-6	<input type="checkbox"/> Over 6
Present salary	<input type="checkbox"/> £4000-5000	<input type="checkbox"/> 5000-6000	<input type="checkbox"/> 6000-7000	<input type="checkbox"/> Over 7000
Qualifications	<input type="checkbox"/> None	<input type="checkbox"/> C&G	<input type="checkbox"/> HNC	<input type="checkbox"/> Degree
Present Job _____	(1234)			

Technicians in Communications

GCHQ We are the Government Communications Headquarters, based at Cheltenham. Our interest is R & D in all types of modern radio communications - HF to satellite - and their security.

THE JOB All aspects of technician support to an unparalleled range of communications equipment, much of it at the forefront of current technology.

LOCATION Sites at Cheltenham in the very attractive Cotswolds and elsewhere in the UK; opportunities for service abroad.

PAY Competitive rates, reviewed regularly. Relevant experience may count towards increased starting pay. Promotion prospects.

TRAINING We encourage you to acquire new skills and experience.

QUALIFICATIONS You should have a TEC Certificate in Telecommunications, or acceptable equivalent, plus practical experience.

HOW TO APPLY For full details on this and information on our special scheme for those lacking practical experience, write now to

Recruitment Office
GCHQ, Oakley, Priors Road, Cheltenham
Glos. GL52 5AJ
or ring
0242 21491
ext 2269

(1530)

ELECTRONICS RESEARCH AT THE UNIVERSITY OF ESSEX

Graduates who have (or final year students who expect to obtain) a first or upper second class honours degree are invited to apply for research leading to a higher degree (M.Sc., M.Phil. or Ph.D) in the following areas:

Acoustic Noise and Vibration Cancellation (adaptive microprocessor-controlled systems); **Audio Engineering** (amplifier design, digital signal processing, stereo); **Circuit Design Studies** (circuit theory, sensitivity effects, CAD, filter realisations); **Digital Transmission for Telecommunications** (filters, line codes); **Interactive Systems** (handwriting analysis, computer graphics, personal databases), **Microcomputer Systems** (embedded microcomputer applications, microprogramming, architectures); **Microwave and Millimetre Wave Propagation** (scattering from precipitation particles, space frame radomes); **Optical Communications** (detectors, noise processes, signal design, switching); **Picture Coding and Processing** (data reduction, adaptive filtering and coding, feature extraction); **Satellite Communication Systems** (business systems, protocols, data and video services, intermodulation studies); **Telecommunication Switching Systems and Software** (computer control, software production, teletex and viewdata); **Visual Displays and Television Engineering** (computer graphic input systems, stereo and colour displays).

Further information and application form available from: Dr. J. K. Fidler, Chairman, Department of Electrical Engineering Science (Ref. Jan/2), University of Essex, Wivenhoe Park, Colchester CO4 3SQ.

(1542)

SITUATIONS VACANT

Electronic Engineers - What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £4000 to £12000 p.a.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you. All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

TJB ELECTROTECHNICAL
PERSONNEL SERVICES,
12 Mount Ephraim,
Tunbridge Wells,
Kent. TN4 8AS.

Tel: 0892 39388



Please send me a TJB Appointments Registration form:

Name

Address

(861)

BROADCAST FIELD SERVICE ENGINEERS

MIDDLE EAST

To join highly professional team based in Reading, Berkshire, responsible for installation and service of television studio equipment at customer sites throughout the Middle East.

Key requirements are:

- ★ Degree/HNC in Electronics or equivalent qualification demonstrating a sound theoretical knowledge.
- ★ Three years' experience in Broadcast Television servicing VTRs, Cameras, Vision Mixers, etc.
- ★ Ability to work on own initiative while travelling away from base.

Successful applicants will receive product training, excellent basic salary with generous overseas allowance as appropriate.

AMPEX

Please contact Maureen Brake on: Reading (0734) 85200, Ampex Great Britain Limited, Acre Road, Reading, Berks.

(1555)

Southampton
THE
UNIVERSITY

INSTITUTE OF SOUND AND
VIBRATION RESEARCH
VOICE COMMUNICATIONS SYSTEMS

SALARY TO £12,500

Electronic and Electroacoustic Engineers are required to join a small team working on innovative R & D projects for industry.

Work includes speech processing, noise cancellation systems and microprocessor-controlled adaptive filters. Duties may involve equipment development, production of prototypes, testing and field trials.

Further details from D. A. S. Copland, The University, Southampton SO9 5NH to whom applications (in duplicate) should be sent quoting reference No. 320/A/WW. 1557

ARTICLES FOR SALE

AIRMEC 248A Wave Analyser.....	£75
PARAMETRON 477 Spectrum Analyser.....	£650
H-P 85518 Spectrum Analyser.....	£2500
R & S FNA Audio Spectrograph.....	£70
B & K 3316 Audio Spectrometer & Level Recorder.....	£950
Attenuators H-P, Marconi, Philco, from.....	£30
Bridges Marconi, Wayne Kerr, from.....	£175
Counter/Timers H-P, Marconi, Racal from.....	£130
RACAL 409 Modulation Meter.....	£250
RADIOMETER BKF.8, Distortion Meter.....	£120
TEKTRONIX 130 L & C Meter.....	£75
TELEQUIPMENT D.43 Dual Beam Oscilloscope.....	£125
TELEQUIPMENT S54 Single Beam Oscilloscope.....	£80
<i>Ideal for Christmas Present</i>	
TEKTRONIX 564 Storage Oscilloscope.....	£350
MARCONI 2950/5 Mobile Test Set.....	£1950
ADVANCE HIE Oscillator.....	£75
MARCONI TF 144/4 A.M. Signal Generator.....	£350
MARCONI TF 1099 Sweep Generator.....	£100
PROSSER A100/A340 Wave Form Generator.....	£500
TEKTRONIX 109 Pulse Generator.....	£300
MARCONI TF 1101 R-C Oscillators.....	£75
MARCONI TF 8010/8 Signal Generator.....	£95
TELESEC 2 Pen Flat Bed Recorder.....	£275
RIKIDENKI B.34.3 Pen Recorder.....	£350
RANK 12084/2 Insulation & Pulsed Flash Tester.....	£50
BARNET Dead Weight Tester c/w Weights.....	£500
L.C.I. Ultrasonic Cleaner.....	£2750 o.n.o.

Send S.A.E. for list to:

MARTIN ASSOCIATES

'PARTHIA', BECKHAMPTON
NEAR MARLBOROUGH, WILTS.
TEL: AVEBURY (067-23) 219

(1384)

**ELECTRONIC AND
COMPUTER SERVICES**
Tel. 04862 67918

HARD DISC BARGAINS

- ★ Diablo series 30 25 megabyte exchangeable disc drive. Industry standard. Easily interfaced to most micros, etc. Complete with power supply unit..... £300
 - ★ Teletype ASR 33..... £60
 - ★ Deckwriter LA36..... £300
 - ★ Fast papertape punch..... £25
- All prices inclusive VAT - Carriage extra. (1557)

FOR SALE

2 Pye Cambridge radio telephone mobile transceiver: Low band AM boot and dash mounted. Forms of tender which should be returned by 5th April, 1982, are available from the Divisional Manager, Sussex River and Water Division, Southern Water Authority, Falmer, Brighton BH1 9PY. Tel: (0273) 606766. (1551)

PRINTED CIRCUITS. Make your own simply, cheaply and quickly. Golden Fotolak Light Sensitive Laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibreglass Board approx. 1mm thick £1.75 sq. ft. Post/Packing 60p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall. (714)
£15,000 PLUS VAT buys 100 TV rentals releasing £10,000 p.a. gross income. Scope for expansion. South Bristol area. Box No. 1527 (1527)

ARTICLES FOR SALE

WORLD RADIO TV HANDBOOK 1982, write for details. "Broadcasts to Europe," quarterly frequency guide, £1.30, full year £4.50. Trade/club enquiries welcome. Pointsea, 25 Westgate, North Berwick, East Lothian. (1534)

TRANSFORMERS, line adjustment type, 2.5 KVA, tapped at 0V, 200V, 220V, 230V, 240V £8 each. Also mains transient suppressors, 11 amp, boxed, 4in x 4in x 3in £5 each. Both plus VAT and postage. Electroversal Ltd, Luton 54309. (1524)

EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment low cost, used and new. Also for CRT reginning metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

SITUATIONS VACANT

SYSTEMS ENGINEER

£NEG. + BUPA + 4 WEEKS + CAR

To assist the Sales Manager with design and specification of television systems, particularly pulse and routing systems. The position will involve interface with both customers and factory with overall responsibility for smooth flow of large projects. The successful candidate will probably be a broadcast technician or have gained experience in the systems division of a major manufacturer.

SALES ENGINEER

£NEG. + BUPA + 4 WEEKS + CAR

To assist the Sales Manager in selling to the major TV Network in the U.K. and possibly assisting our European distributors. The successful candidate will be experienced in selling broadcasting equipment and will know the structure of the U.K. and European Networks.

Apply to:

J. Prigmore, Sales Manager
Seltech International Limited,
 Rose Industrial Estate,
 Cores End Road,
 Bourne End, Bucks. SL8 5AT
 Tel. Bourne End (062 85) 29131 (1566)



TELECOMMUNICATIONS ENGINEER — £10,000 p.a.

A vacancy exists in the Communication Department of the company for an Engineer of HNC/City & Guilds standard. Responsibilities would mainly lie in the installation and maintenance fields of the company's Financial/Commodities Retrieval Service, necessitating involvement with in-house computers and client located terminals.

Apply in the first instance to:

Miss J. T. Cowell
 The Associated Press
 83-86 Farringdon Street
 LONDON EC4A 4BR (1564)

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALE & BULK BUYERS ONLY

Large quantities of Radio, T.V. and Electronic Components.
RESISTORS CARBON & C/F 1/8, 1/4, 1/2, 1. 1 Watt from 1 ohm to 10 meg.
RESISTORS WIREWOUND. 1 1/2, 2, 3, 5, 10, 14, 25 Watt.
CAPACITORS. Silver mica, Polystyrene, Polyester, Disc Ceramics, Metalamite, C280, etc.
 Convergence Pots, Slider Pots, Electrolytic condensers, Can Types, Axial, Radial, etc.
 Transformers, chokes, hopts, tuners, speakers, cables, screened wires, connecting wires, screws, nuts, transistors, ICs, Diodes, etc., etc.
 All at Knockout prices. Come and pay us a visit. Telephone 445 2713, 445 0749.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho Corner! (9461)

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, any quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO
 86 Bishopsgate Street
 Leeds LS1 4BB
 0532-35649

PRE-PACKED screws, nuts, washers, solder tags, studding. Send for price list. A1 Sales (WW), PO Box 402, London SW6 6LU. (1253)

BRIDGES, Waveform/transistor analysers, Calibrators. Standards, Millivoltmeters, Oscilloscopes. Recorders. Signal Generators. 040-376236. (8250)


TELEQUIPMENT D54 dual beam 10MHz oscilloscope, vgc, £150 ono. Large quantity of WW from 1954 to 1979 for sale. Ipswich 210903. (1536)

ARTICLES FOR SALE

QUARTZ CRYSTALS

- HIGH STABILITY GOLD ELECTRODES
- COLD WELD UNITS
- GUARANTEED 7-DAY SERVICE AVAILABLE
- ANY FREQUENCY 1MHz-70MHz

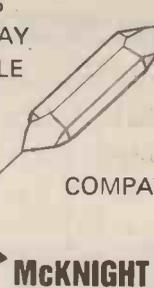ALSO
 200KHZ-70MHZ
 CLOCK CRYSTAL
 OSCILLATORS TTL
 COMPATIBLE DIP PACKAGE



HYTHER (0703) 848961
 TELEX: 47506 - CRYSTL G

McKNIGHT CRYSTAL CO. LTD.
 HARDLEY INDUSTRIAL ESTATE
 HYTE, SOUTHAMPTON. SD4 6ZY (1407)

IONISER KIT (MAINS OPERATED)

This negative ion generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions. £12.50
 A suitable case including front panel, neon switch, etc. £6.50

HOURS:
 Monday to Friday 9 am-5 pm. Price includes post & VAT
 Saturday 9 am-4.30 pm. Barclay/Access Welcome

Wide range of Japanese integrated circuits and transistors stocked

T. POWELL
 Advance Works, P.E., 44 Wallace Road, London N1 1PQ
 Tel. 01-226 1489 Please allow 14 days for delivery

LARGE PURCHASE OF RACAL EQUIPMENT

COMMUNICATIONS RECEIVERS

500kc/s-30mc/s 1mhz wide. RA17L - £175. RA117E - £225. A few sets available as new at £75 extra. All receivers are air tested and calibrated in our workshop, supplied with full manual, dust cover, in fair used condition. New black metal louvered cases for above sets £25 each. RA98D - ISB - SSB - £75. RA218 SSB - ISB and fine tune for RA117 - £50. TRANSMITTER DRIVE UNIT MA79. 1.5mc/s-30mc/s - SSB - ISB - DSB - FSM - CW - £150. AEON L TUNING UNIT and protection unit MA197B - £25 to £50. DECADE FREQUENCY GENERATOR MA50B solid state synthesiser for MA79 or RA117 - RA217 - RA1217 - £350 to £200. MA250 - 1.8mc/s to 31.6mc/s - £150 (New). MA259G - precision frequency standard - 5mc/s lmc/s1 100khz - £100 to £250. RA70 & PV78 - frequency shift converter - £50. UNIVERSITY UNIT MA168 - new and boxed, contains product detector for SSB & BFO - £25. L.F. CONVERTOR RA137 - £50 to £75. Most above supplied with full manuals. RACAL SPARES, new & boxed - RA17L Chassis - £20 - I.F. Strip - £15 - Calibrator - £8. RACAL MA152 - Standing wave ratio indicator, FX 2mc/s-25mc/s. Power up to 1000watts - 50ohms - Auto trip switch - Transistor mains 100-250AC, new & boxed - £40. RACAL COUNTER 836 (9036) 32mc/s TTL circuit design - tested with manual, £50 to £75. RACAL 9010 FREQUENCY DIVIDER for above, extends range to 50mc/s 10mV sensitivity - £50 tested. OSCILLOSCOPES COSSOR CDU150 - 35mc/s - Twin Beam - Solid State - £175 with manual. AIRNEC Racal Display Oscilloscope 383 - £100. TEKTRONIX OSCILLOSCOPES - 845A - £70 - 681 - £85. PLUG-IN UNITS B-D-E-G-H-K all £15 - £20 - F - £25 - N-R-Z - £50 - 1A1 - £120 - 1A2 - £80 - 1A4 - £100. EXTEL TRANSEL MATRIX PRINTERS 5 level baudot code, accepts speeds up to 300 bauds, supplied set to 50 and 75 bauds switched, tested with manual. £165. MOTOROLA frequency standard 1011 - 1mc/s - 100kc/s - £250. TF801D/BS - 10mc/s to 485mc/s - £100. H.P. WAVE ANALYSER 302A - £30. TRACOR VLF Tracking receiver Model 599 - £200. Latest Government release - MARCONI SIG GEN TF995A2 - AM & FM 1.5mc/s-22mc/s covered in 5 bands - crystal check facilities, supplied in A1 condition, tested circuit and instructions - £100. TEKTRONIX OSCILLOSCOPE 647 and 647A Solid State - 50mc/s and 100mc/s bandwidth - £250 and £350. Tested, circuit and instructions. AERIAL MASTS - we have three masts approx. 130ft. high, complete with all fittings. Base - Insulators, etc. Mast steel tube 8" all parts galvanised, supplied brand new, all items boxed - £1000 - or each complete mast - £400.

All items are bought direct from H.M. Government, being surplus equipment. Price is ex-works. SAE for all enquiries. Phone for appointment for demonstration of any item. John's Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. (0274) 684007. (848)

SURPLUS ITEMS: LP1186 £3.25. LP1175 £1.15. MS4A Ferranti Photo Trans. 50p. Electrolytics 2200 mfd. 63v 75p, 2500 mfd. Mullard £1. 4-pole 2-way push switches 50p. P.&P. 40p. Transformers 170-0-170v 30ma, 6.3v, 1.75a £1.15 (P.&P. £1). Linsley Hood 75-watt amp. Kit £65. (P.&P. £3). - TELERADIO, 325 Fore Street, London N9 0PE.

INVERTERS

High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.



COMPUTER POWER SYSTEMS
Interport Mains-Store Ltd.
 POB 51, London W11 3BZ
 Tel: 01-727 7042 or 0225 310916 (9101)

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT - never gains or loses. SELF-SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output for computer or alarm, etc. STOPCLOCK, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, RIGHT TIME, £62.90. 60KHZ RUGBY RECEIVER, as in MSF Clock, audio and serial data outputs, decoding details, £17.90. Each fun-to-build kit includes all parts, printed circuit, case, postage, etc. money back assurance so GET yours NOW.

CAMBRIDGE KITS
 45 (WD) Old School Lane
 Milton, Cambridge (1538)

COMPUTER APPRECIATION

86 High Street, Bletchingley, Redhill, Surrey RH1 4PA. Tel: Godstone (0883) 843221

PDP 11/23 SYSTEM COMPRISING KDF11-AA processor with KEF11-AA floating point option and MMU; MSV11-DD 64K byte memory; MXV11-A multitrack card with dual serial interfaces. 32K byte memory, real time clock and MXV11-A2 bootstrap ROM; XYLOGICS disc controller, BA11-MF box and PSU with 8 slots; one fixed and one removable DIABLO Series 30 2.5 megabyte disc drives. All processor cards were purchased new by ourselves Sept., '81. Disc psu, all cabling and BA11-MF all unused prior to assembly Sept., '81. Price includes 2 cartridges and RT11 £3,900
 PDP 11/23 with LSI/11 processor, MSV11-DD 64K byte memory, DLV11-J quad serial interface, DICOLL Model AMD 6200 dual double density floppy disc drives. All contained in compact portable case £2,250
 DTC MICROFILE MICROCOMPUTER. Compact 8080 based system with 56K bytes, dual serial interfaces and programmable front panel display. Machines are available with one PERSCI dual drive (currently \$1700 each). Software includes operating system, powerful BASIC, assembler and letter writer. NEW £685
 VENTEK Model 1100 MICROCOMPUTER with 16K byte memory incorporating 12 line x 80 ch. VDU, twin 8" floppy disc drives, QUME Model 545 daisy wheel printer, communications interface and disc operating system £950
 TEKTRONIX Model 4006/1 high resolution graphics display terminal. Compact storage tube based terminal with 800 x 1024 addressable points in graph mode or 35 lines x 74 ch. in alpha mode. RS232 interface up to 4800 Baud. Current (Jan., '81) new price £2,490 £850
 IBM Model 1053 GOLFBALL PRINTER. Compact 15 cps high-reliability mechanical printer in fully refurbished condition. Exactly equivalent to 735 less keyboard. Can be driven from PIA (or similar) with addition of PSU and solenoid driver (a details available soon). Accepts standard office golfballs £95
 DIABLO Model 1620 HyTerm TERMINAL. Daisy wheel terminal/typewriter. 110, 300 and 1200 Baud, RS232 interface. In ex-demo, condition £850
 FACIT 4070 PAPER TAPE PUNCH. for 5-hole or 8-hole operation. Complete with feed and take up spools, chad box and perspex cover. Parallel interface. New cost in excess of £1,200 £175

MOSELY ANALOGUE X-Y PLOTTER. A4 size. Without pens £75
 AMF VENNEN WIDE RANGE OSCILLATOR. Sine and square wave to 1 MHz. Battery powered. AS NEW £50
 TEKTRONIX Model 463 DUAL BEAM PORTABLE OSCILLOSCOPE. 75 MHz version of 465. Almost as new £750
 LASER ASSOCIATES Nd GLASS LASER. 1.06 micron wavelength. 1-2 J per pulse. A single pulse from this laser burns a hole through a steel rule. Complete with colling system and output monitor. FULLY OPERATIONAL £660
 HOUSTON INSTRUMENTS Model EDP-1 high resolution digital plotter using fan-fold paper. With Model ETC-5A intelligent microprocessor-based controller with character generation, etc. and interfacing to a serial (V24) line. Software to drive this plotter from PDP 11 machines is available from DECUS. Current list price in excess of £3,500 £740
 FACIT Model 4001 1000 cps capacitative paper tape reader £150
 TREND Model HSR 500 optical paper tape reader £175
 EMS SYNTHESIZER Model SYNTHI A complete with AKS keyboard and OK2 keyboard. Current (Jan., '81) new price £1,921 £350
 EIKO 18mm sound projector with Q-H lamp £50
 MULTIDYNE synthesized communications receiver complete with FSK demodulator and EXTEL Model AF baudot coded printer £350

Please note:
 ★ VAT and carriage extra all items
 ★ Visitors welcome, but by appointment please
 ★ We are keen to bid competitively for all good used equipment

INDEX TO ADVERTISERS APRIL

Appointments Vacant Advertisements appear on pages 117-127

PAGE	PAGE	PAGE
Acoustical Mfg. Co. Ltd. 34	Faircrest Engineering 14	PM Components 96, 97
Aero Electronics (AEL) Ltd. 109	Farnell Instruments cover ii, Reader Card, 107	Powertran Cybernetics 98
All Electronic Show 24, 25	Ferranti Electronics Ltd 73	Practical Computing 102
Ambit International 10	F. H. Precision Engineering 103	P & R Computer Shop 30
Analogue Associates 4	Fieldtech Heathrow 12, 26	
Anglia Components 6	Foundations of Wireless 114	
Antex (Electronics) Ltd. cover iii		
Arcom Control Systems 14	Gas Electronics 31	Radio Components Specialities 95
Aspen Electronics Ltd. 99	Global Specialities Corp. 21	Radio Society of Great Britain 8
Audio Electronics 23	GP Industrial Electronics Ltd. 2	Ralfe, P. F., Electronics 102
Aura Sounds Ltd. 13	Grenson Electronics 22	Reltech Instruments 100
Avalon Electronics 106	Griftronic Emission 94	Reprints 110
Avo Ltd 30		Research Communication 100
		RST Valves 93
Bach-Simpson (UK) Ltd. 14	Hameg 26	
B.A. Electronics 110	Happy Memories 4	Safgan Electronics Ltd 20
Barrie Electronics Ltd. 101	Harris Electronics 7	Sagin, M. R. 99
Black Star Ltd. 8	Harrison Brothers, Electronic Distributors 20	Samsons (Electronics) Ltd 94
Broadfields and Mayco Disposals 104	Hart Electronic Kits Ltd 104	Sarel Electric Ltd. 33
	Henry's Radio 98	Scopex Instruments 32
Cambridge Kits 103	Hilomast Ltd. 5	Sescom Inc. 9
Carston Electronics Ltd 28, 29	House of Grolier Loose insert	Sharp Electronics (UK) Ltd. 91
Catronics Ltd 92	House of Instruments 11	Sinclair Research Ltd. 18, 19
Chiltern Electronics 103		South Midlands Communication Ltd. 16
Chiltmead Ltd. 92	ILP Electronics 101, 103, 105, 107, 109	Sower, E. A. Ltd. 4
Circuit Services 8	ILP Transformers 99	Special Products (Distributors) Ltd. 12
Clark Masts Ltd. 20	Interface Quartz Devices 12	S & R Amplification 109
Clef Products (Electronics) Ltd. 30	Intergrex 106	Sunrise Software 109
Colomor Electronics Ltd 100	Irvine Business Systems 22	Supersem 107
Communique 6		Surrey Electronics 26
Computer Appreciation 128	Keithley Instruments Ltd. 15	
Computer Fair 108	Kelsey Acoustics Ltd. 6	Technomatic Ltd. 110, 111
Crimson Elektrik 17		Tektronix UK Ltd. cover iv
Crofton Electronics Ltd 10, 106	Langrex Supplies Ltd. 93	Telemet (Alpha Bridge) Ltd. 7
CT Electronics (Acton) Ltd. 113	Levell Electronics 33	Tempus 105
		Thandor Electronic Ltd. 74
Dataman Designs 6	Maple Instruments 109	Titan Transformers & Components 112
Darom Supplies 16	Microdata 17	
Delph Electronics 112	Micro Times 16	Valradio 94
Disk Offer 92	Midwich Computer Co. Ltd. 27	Videotex 82 96
Display Electronics 116	Millward, G. F., Electronic Components Ltd. 94	
DSN Marketing 115	M.I.T. (Engineering) Ltd. 114	Wilmslow Audio 9
	Modern Book Co, The 104	
Electronic Brokers Ltd. 3, 5, 7, 9, 115	Monolith Electronics Co. Ltd., The 14	Your Computer 116
Electrovalue Ltd. 30		Zycomm Electronics Ltd. 22
Electroversal Ltd. 26	Northern Amateur Radio Soc. 100	
	Northern Electronics 9	

OVERSEAS ADVERTISEMENT

AGENTS:
 France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Mrs Edit Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget.
 Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
 Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106.
 Telephone: (03) 585 0581.


United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080, Telex: 238327.

Mr Jack Farley Jr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.

Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1919.
 Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
 Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.
 Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.

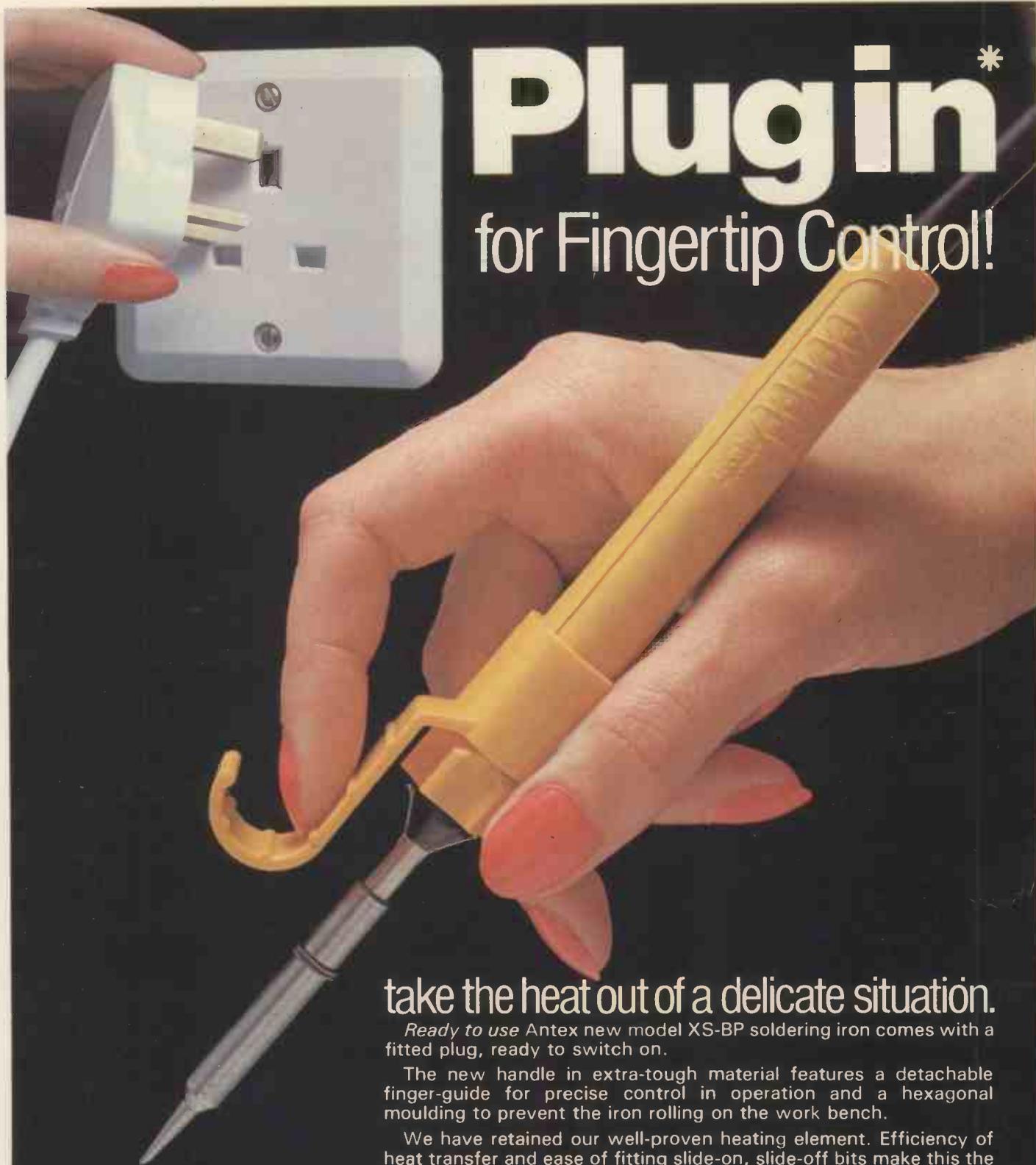Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
 * Also subscription agents.



Plugin*

for Fingertip Control!

take the heat out of a delicate situation.

Ready to use Antex new model XS-BP soldering iron comes with a fitted plug, ready to switch on.

The new handle in extra-tough material features a detachable finger-guide for precise control in operation and a hexagonal moulding to prevent the iron rolling on the work bench.

We have retained our well-proven heating element. Efficiency of heat transfer and ease of fitting slide-on, slide-off bits make this the professional's choice of soldering instrument. The iron is also available for 115, 50, 24 or 12 volt.

* fitted with the NEW safety plug.



RSP Model XS-BP (25 Watts £5.30 + VAT)
Model CS-BP (17 Watts £5.30 + VAT)

Send now!

ANTEX (ELECTRONICS) LIMITED

MAYFLOWER HOUSE, ARMADA WAY, PLYMOUTH, DEVON TELEPHONE 0752 667377 · TELEX 45296

Please send the ANTEX New Range full colour brochure to: NAME _____

ADDRESS _____

WW-002 FOR FURTHER DETAILS

WW4

TEK MULTI-PURPOSE
OSCILLOSCOPES

SO ADVANCED
THEY COST YOU LESS

The Tektronix 2200 Series. Simply great.



Tektronix traditions of excellence in designing and manufacturing oscilloscopes are recognised all over the world. But rather than rest on past laurels, we have veered dramatically from the well established design paths we ourselves have laid down.

With the 2213 priced at £670* and the 2215 at £850*, these 60 MHz dual trace oscilloscopes are an entirely new form of instrument.

Their most remarkable characteristic is the way in which major design advances have provided full-range capabilities at prices significantly below what you would expect to pay. How has this been accomplished? To begin with, we have reduced the number of mechanical parts by more than half. This not only saves manufacturing time, it lowers costs and improves reliability.

Board construction has been greatly simplified and the number of boards reduced. Board connectors have also been reduced substantially and cabling cut by an amazing 90%.

The 2213 and 2215 have a high efficiency regulated power supply which does away with the need for a heavy power transformer. There are no line-voltage adjustments. Just plug the instrument into a power socket supplying anything from 90 to 250 volts, 48-62 HZ, switch on and you are ready to measure. Power saving circuitry has eliminated the cooling fan, resulting in further economies in size and weight.

These scopes have it all. Dual trace. Delayed sweep for fast, accurate timing measurements. Single time base in the 2213, dual time bases in the 2215. An advanced triggering

system, automatic focus and intensity. Beam finder - and much more.

Interested? Then why not telephone your nearest Tektronix office or circle the enquiry number for further information.

Performance Specifications

Bandwidth

Two channels, DC-60 MHz to 20 mV/div, 50 MHz to 2 mV/div.

Light Weight

6.1 kg (13½ lbs). 6.8 kg (15.0 lbs) with cover and pouch.

Sweep Speeds

Sweeps from 0.5s to 0.05 μ s (to 5 ns/div with $\times 10$ magnification).

Sensitivity

Scale factors from 100 V/div (10 \times probe) to 2 mV/div (1 \times probe). Accurate to $\pm 3\%$. AC or DC coupling.

Also available from Electroplan.

* Prices subject to change without notice.

Tektronix UK Limited
PO Box 69, Harpenden, Herts. AL5 4UP
Tel: Harpenden 63141 Telex: 25559

Regional Telephone Numbers: Maidenhead
0628 73211, Manchester 061 428 0799,
Livingston 32766, Dublin 850685/850796

Tektronix
COMMITTED TO EXCELLENCE