

wireless world

MARCH 1983 80p

Australia A\$ 2.70
Canada C\$ 3.25
Denmark DKR. 33.25
Germany DM. 7.00
Greece DRA. 190.00
Holland DFL. 8.50
Italy L 3700
New Zealand NZ\$ 3.00
Norway NKR. 26.00
Singapore M\$ 5.50
Spain PTS 275.00
Switzerland FR. 7.00
U.S.A. \$ 3.75



Home alarm system
120W audio amplifier



Autoranging frequency meter
Spread-spectrum communications

upgrade to an ORIC-1



**16 colours
professional
keyboard
full graphics
real sound**

- Superb styling
- Choice of 16K, 32K or 48K RAM
- Ergonomic keyboard with 57 moving keys
- 28 rows x 40 characters high resolution
- Teletext/viewdata compatible graphics
- 6 octaves of real sound plus Hi-Fi output
- Centronics printer interface and cassette port
- Comprehensive user manual

FOR HOME, EDUCATION, BUSINESS & ENTHUSIASTS.

OPTIONAL MODEM OFFERS COMPUTER PHONE LINK FOR: ELECTRONIC MAIL ● TELESOFTWARE ● PRESTEL
COMING SOON, TO COMPLETE YOUR SYSTEM: ORIC MICRO-DRIVE DISCS & SPEED PRINTER

ORIC is no toy! Its professional keyboard, Basic language and extensive specification, will do all you expected of your home computer, plus a whole lot more. For home, educational, business and games use.

If you're buying for the first time beware! Only ORIC computers offer full colour capability for under £100 and the most powerful and comprehensive micros in their price brackets.

So whether you're just starting out, or upgrading existing equipment, make the professional decision and choose ORIC. Send for our comprehensive brochure NOW, or better still, order your ORIC today. Delivery is around 28 days with a money back guarantee if you're not delighted.

Clip the coupon below, or call our telesales number ASCOT (0990) 27641

FROM
£ 99⁹⁵
incl VAT

**Disk Drive & Printer
available soon.**

WW-001 FOR FURTHER DETAILS

The Real Computer System

ORIC PRODUCTS INTERNATIONAL LTD

Coworth Park Mansion, Coworth Park, London Road,
Sunninghill, Ascot, Berks SL5 7SE

Prices	ORIC-1 16K RAM	£ 99.95	
Include	ORIC-1 32K RAM	£139.95	
VAT	ORIC-1 48K RAM	£169.95	
	ORIC Communications Modem	£ 79.95	
	Postage and Packing	£ 5.95	
	TOTAL	£	

Please charge my Access, Barclaycard
Amex, Diners Club account no.

*Please delete/complete
as applicable.
*I enclose a cheque/
P.O. payable to:
ORIC PRODUCTS
INTERNATIONAL
LIMITED
for £

Name

Address

If you require a brochure please tick

WW

©Copyright ORIC PRODUCTS INTERNATIONAL 1982


BROADCASTING
ELECTRONICS
AUDIO

wireless world

COMMUNICATIONS
COMPUTING
VIDEO

MARCH 1983

VOL 89 NO 1566

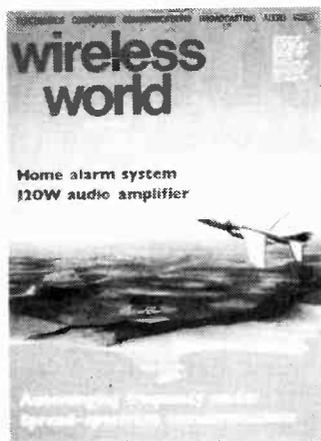

Computer-generated image by
Sogitec of Boulogne.

NEXT MONTH

Constructional article on a Viewdata display module, which is used with a home computer and modern to show Prestel and teletext on a colour tv. Printed board layout is presented.

Digital tape timer shows length of tape, in hours, minutes and seconds, remaining on an open-reel machine to within 1 part in 1000. Uses tape-driven optical sensors.

Amateur satellite tracker continuously adjusts aerial to track one of four amateur and weather satellites under the control of a PET microcomputer.

Single-chip microcontrollers using eprom for program storage allow development on an eprom emulator. The circuit shown enables this to be done.

Current issue price 80p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.23, back issues (if available) £1.80, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS Tel: 01-661 8668.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3614. Advertising 01-661 3130. See leader page.

Telax: 892084 BISPRS G.

Subscription rates: 1 year £14 UK and £17 outside UK.

Student rates: 1 year £9.35 UK and £11.70 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3248.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone: 0444 59188. Please notify a change of address.

USA: \$44 surface mail, \$98.30 airmail. US subscriptions from IPC B.P., Subscriptions Office, 205 E.42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd class postage paid at New York.

© IPC Business Press Ltd. 1983 ISSN 0043 6062.

27 DESIGN FOR LIVING

28 DOMESTIC ALARM SYSTEM

by P. E. Bruin

31 HIGH-IMPEDANCE ELECTRONICS

by R. D. Purves

33 ASSEMBLY LANGUAGE PROGRAMMING

by R. Coates

36 AUTORANGING FREQUENCY METER

by F. P. Caracausi

39 TWO-METRE TRANSCEIVER

by T. D. Forrester

43 WAVES IN SPACE

by I. Catt

44 LIMITATIONS OF INDETERMINACY

by W. A. Scott Murray

47 ULTRA-HIGH DENSITY DATA RECORDING

by J. R. Watkinson

51 LETTERS TO THE EDITOR

Amateurs and cable Stereo width control

57 NEWS OF THE MONTH

Cable tv Recordable laser disc Fibre research funds

61 CIRCUIT IDEAS

Joystick control Mini-floppy tester Discrete op-amp audio

64 SOME PRACTICAL PROBLEMS OF AERIALS AT SEA

by J. J. Wiseman

67 COMMUNICATIONS

69 HIGH-POWER AMPLIFIER USING MOSFETS

by E. Borbely

76 SPREAD-SPECTRUM COMMUNICATION SYSTEM


by N. Mahmood

81 NEW PRODUCTS



AMCRON INDUSTRIAL MUSCLE

- ★ POWER RESPONSE DC - 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.)
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS.
- ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

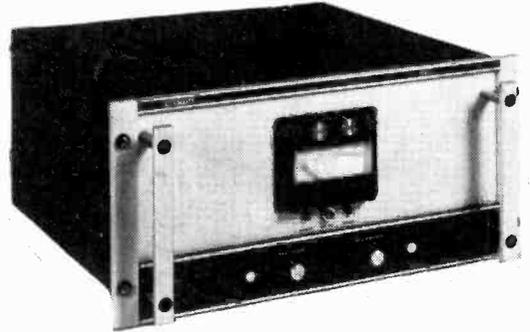

Model - M600

For full details on all Amcron Products write or phone Chris Flack

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

Analogue Associates

PROFESSIONAL INDUSTRIAL ELECTRONICS

WW - 018 FOR FURTHER DETAILS

REGD. TRADE MARK



TEONEX ELECTRONIC VALVES AND SEMICONDUCTORS

SERVING THE WORLD FOR 30 YEARS

We specialise in the supply of
Industrial Valves of British, European and USA manufacture,
and semiconductors from the Philips Group.
Many types, including obsolete and obsolescent types,
always available from stock.

For further details, contact Mrs. Janet Lowy.

T.O. SUPPLIES (EXPORT) LTD., 2A Westbourne Grove Mews, London W11 2RY.
Telephone: (01) 727 3421 Telex: 262256 Answerback TOSPLY G

WW - 061 FOR FURTHER DETAILS

THE SOURCE... of all good used test equipment

Electronic Brokers are Europe's leading Second User Equipment Company. We carry large stocks of the very latest test equipment which is refurbished in our own service laboratories and calibrated to meet the manufacturer's sales specifications. When you buy used equipment from Electronic Brokers, it can be yours in just days. No waiting for manufacturers lengthy production schedules. All equipment is fully guaranteed.

ANALYSERS

- Dranetz**
606-3 Line Disturbance Monitor £2500.00
- Hewlett Packard**
141T/8552B/8554B 100KHz-1250MHz £6500
141T/8552B/8555A 10MHz-18GHz £9750.00
332A Distortion Meter 5Hz-600KHz £495.00
- 3582A Spectrum Analyser £6350.00
0.02Hz-25.5KHz
5420A Digital Signal Analyser c/w Digital Filter 54470B, A/D Converter 54410A £21,000.00
- 8407A/8412A Network Analyser £1950.00
8444A Tracking Gen. For use with 8554B £2100.00
- Marconi**
TF2331A Distortion 20Hz - 20KHz to Less than 0.05% £875.00
- Solartron**
1172 TFA £4000.00
- Tektronix**
AA501 opt 01 Distortion 10Hz - 100KHz to Less than 0.0025% £1450.00
DF1 Display Formatter For 7001 £750.00
DF2 Display Formatter with 1EEEE/GPIB/ASCII £1000.00
30B Portable 8 Channel 20MHz Data Analyser £1950.00
491 Spectrum Analyser 10MHz-40GHz £7000.00
492 [opt 01, 2, 3] Spectrum Analyser 50KHz-220GHz £14000.00
492P [opt 01, 2, 3] Programmable Version of 492 £20000.00
7LS Spectrum Analyser with opt 25 [Tracking Gen] and L3 [50Ω input] 20Hz - 5MHz £7500.00
7L12 Spectrum Analyser 100KHz-1.8GHz £6000.00
7L13 Spectrum Analyser 1KHz-1.8GHz £7600.00
7L14 Spectrum Analyser 10KHz-1.8GHz £9450.00
7L18 Spectrum Analyser 1.5GHz-60GHz £9850.00
- TR502 Tracking Generator [for 7L12, 13 & 14] £3200.00
TR503 Tracking Generator [for 492/496 series] £3250.00
5L4N Spectrum Analyser 20Hz-100KHz £2350.00
7DD1 16 Channel 100MHz Sample Rate £2450.00
7D02 opt 01 Logic Analyser £3200.00

BRIDGES

- Marconi**
TF1313A 0.1% LCR Bridge £775.00
TF2700 1% LCR Bridge £345.00
TM4520 Set of Inductors £350.00
- Wayne Kerr**
B642 LCR 0.1% £795.00
SR 268 Source & Detector £875.00

DVM'S AND DMM'S

- Datron**
1059 Bench DMM 5 1/2 digit DC and True RMS AV volts and current + resistance £700.00
- Solartron**
7055 Microprocessor DMM. Scale Length 20,000 AC/DC volts, resistance 1μV resolution £495.00

WW - 200 FOR FURTHER DETAILS

WIRELESS WORLD MARCH 1983

OSCILLOSCOPES

- Hewlett Packard**
1809A 100MHz 4 Channel Plug In £2000.00
1821A Timebase Plug In £1000.00
- Philips**
PM3232 Dual Beam 10MHz £495.00
PM 3234 True Dual Beam Storage Oscilloscope 10MHz New CRT. £1500.00
- Tektronix**
213 Miniscope/DMM Battery 1MHz £975.00
305 Portable battery scope/DMM, D.T. 5MHz £975.00
475 Dual Trace 200MHz Portable £2200.00
T922-01 15MHz DT Scope Diff. input £515.00
200C Trolley for 400 Series £120.00
2336 Dual Trace 100MHz Portable £1450.00
- 7313 100MHz Storage Mainframe £2225.00
7603 100MHz Mainframe £1450.00
5223 Digital Storage 10MHz £2000.00
5440 50MHz Mainframe £1000.00
5441 50MHz Variable Persistence Storage Mainframe £1600.00
7104 1GHz Scope Mainframe £11,500.00
7704A Scope DC-200MHz Mainframe £1950.00
- 7613 Storage Scope Mainframe DC-100MHz £2600.00
7633 Multimode Storage Scope Mainframe DC - 100MHz £4500.00
7834 Storage Scope Mainframe DC 400MHz £7000.00
7844 Dual Beam 400MHz Mainframe £7750.00
- 7854 Waveform Processing Scope DC-400MHz £8250.00
7904 opt 02, 03 500MHz £5350.00
S1 Sampling Head As New £450.00
P6015 HV Probe £295.00

- Tequipment**
DM63 Storage Oscilloscope Fitted with 2 x V4 Plug-ins to give 4 Trace 15MHz £1350.00
D1016A Dual Trace 20MHz 'As New' £350.00

TEKTRONIX PLUG INS

- 5A13N Diff. Comparator DC - 2MHz £675.00
5A18N Dual Trace DC - 2MHz £375.00
5A48 Dual Trace Amp DC-50MHz £400.00
5B12N Dual Sweep Time Base £500.00
5B25N Digital Time Base £500.00
5B42 Delay Timebase £600.00
7A11 DC - 250MHz with built in FET probe £1450.00
7A13 Diff. Comparator Amp DC-105MHz £1500.00
7A16A Single Trace Amp. CC-225MHz £425.00
7A18 Dual Trace Amp. DC-75MHz £450.00
7A19 opt 04 DC - 600MHz with variable delay £1450.00
7A22 Diff. Amp. DC-1MHz 10μV/Div £525.00
7A29 Dual Trace Amp. DC-1GHz £1250.00
7B10 Delayed Time Base for 7104 £1250.00
7B15 Delaying Time Base for 7104 £1400.00
7B53A Dual Timebase For use in 7600 series £650.00

- 7B85 Delaying Time Base for 700 Series £900.00
1809A Dual Timebase For use in 7900 series £1500.00
7D14 Digital Counter: 525MHz £850.00
7M11 Dual 50Ω Delay Line £575.00
7S14 Dual Trace Delayed Sweep Sampler DC-1GHz £3250.00
S1 Sampling Head [unused] £450.00

SIGNAL SOURCES

- Hewlett Packard**
616B 1.8-4.2GHz int or ext PCM/FM 0.1μV-0.224V £1000.00
651B Test Oscillator: 10Hz-10MHz 0.1mV-3.16V £415.00
3320A Frequency Synthesizer: 0.01Hz-13MHz £995.00
- Marconi**
TF2120 0.0008Hz-100KHz Waveform Generator £900.00
TF2008 AM/FM 10KHz-510MHz built in sweeper Output 0.2μV-200mV £3500.00
TF2016A + TF2173 Synchroniser AM/FM 10KHz-102MHz £2000.00
TF2169 Pulse Modulator for use with TF2015 or TF2016 £200.00

- Philips**
PM6456 Stereo Generator £250.00
- Racal**
9081 AM, FM, Phase and Pulse Synthesized 5-520MHz £2200.00

- Radiometer**
SMG1 Stereo Generator £375.00

TEKTRONIX TM500 SERIES

- AF501 Bandpass Filter/Amplifier £400.00
AM501 Op Amp Gain 10,000 £300.00
AM502 Diff. Amp Gain 1 - 100K £500.00
DM502A True RMS S 3 1/2 digit DMM £250.00
DC503A 125MHz Counter £450.00
DC505A 225MHz Counter £600.00
DC508A 10Hz - 1.3GHz 9 Digit DMM £900.00
DD501 Digital Delay £495.00
FG501 Function Generator 0.001Hz-1MHz £375.00
FG501A Function Generator 0.002Hz-2MHz £425.00
FG502 Function Generator 0.1Hz-11MHz £425.00
FG503 Function Generator 1Hz-3MHz £275.00
FG504 Function Generator 0.001Hz-40MHz £1250.00
PG505 Pulse Generator 1Hz-100KHz £450.00

- PG508 Pulse Generator 5Hz-50MHz £1100.00
SC502 15MHz Dual Trace Scope £1000.00
SC504 80MHz Dual Trace Scope £1250.00
SG503 Sinewave Generator 250KHz-250MHz £950.00
SG504 Sinewave Generator 245MHz-1050MHz £1650.00
TG501 Timemark Generator £950.00
TM513 Mainframe (5 wide) £350.00

TEKTRONIX TV TEST EQUIPMENT

- 141A PAL Test Signal Generator £1750.00
148 PAL Insertion Test Generator £4000.00
1481C PAL Waveform Monitor £2500.00
1485C PAL/NTSC Dual Standard Waveform Monitor £2950.00
651HR 12 PAL Colour Monitor [Mint] £3250.00
655HR-1 TV Colour Picture Monitor [NTSC + PAL + RGB] £3800.00
656HR PAL/SECAM Monitor £3900.00
1411R TV Generator Various Systems available POA

MISCELLANEOUS

- Bruel & Kjaer**
2203 Sound Level Meter £975.00
- Ferrograph**
RTS1 Test Set £295.00
- Fluke**
883 AC/DC Differential £615.00
845 AB Null Detector £610.00
3010A Logic Tester Self Contained Portable Full Spec on Request £8500.00
- Hewlett Packard**
5340A Counter 10Hz-18GHz 8 Digit £3750.00
8403A Modulator Fitted With B732B PIN MODULATOR £1500.00
8482H Power Sensor 100KHz-4.2GHz AS NEW £250.00
8745A S Parameter Test Set. Fitted with 11604A Universal Arms 0.1-2GHz £2750.00
59308A HP-IB Timing Generator £300.00
- Marconi**
TF2162 M.F. Attenuator 0.111dB £165.00
- Schaffner**
NSG 509 5KV Insulation Tester £785.00
- Tektronix**
106 Square Wave Generator 1ns risetime 10Hz-1MHz without accessories £175.00
284 Pulse Generator 70pS risetime £950.00
832 Data Comms Tester £925.00
833 Data Comms Tester £1350.00
2901 Time-Mark Generator £195.00

Please note: Prices shown do not include VAT or carriage.



Electronic Brokers Limited
61/65 Kings Cross Road
LONDON WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

When the power fails or falters Galatrek lets you carry on.



Prices From £350

Uninterruptible Power Supplies -

UPS CVT Reliability 125va to 50kva, 50 or 60hz.

■ **STANDBY POWER.** Invaluable for winding down a computer programme on mains failure and wherever continuous power is essential.

■ **STABILISATION.** $\pm 3\%$ Vital to combat mains voltage fluctuations and ensure the operation of equipment at peak efficiency. **Frequency** stabilised $\pm 0.1\%$ 47 to 65Hz.

■ **TRANSIENT ATTENUATION.** Provides suppression of mains born interference (spikes). Model above £795

Line Conditioners from £150 and Voltfilt from £114

For more information, cut the coupon.

Galatrek International, FREEPOST, Scotland Street, Llanrwst, nr. Llandudno, Gwynedd LL26 0AL, BRITAIN, Tel No: 0492-640311/641298, Telex: 617114 A/B Galahu. Made and Designed in Britain by Galatrek.



Please send me full details of your range of voltage stabilisers, filters, cutouts, generators and CVT's

Please send me full details of UPS

Please send me a requirement check sheet

Consultation with Galatrek Engineer

Name

Position

Company

Address


TelNo Telex

Trade OEM (please tick where appropriate) (WW/3/83)

WW - 060 FOR FURTHER DETAILS

HBED

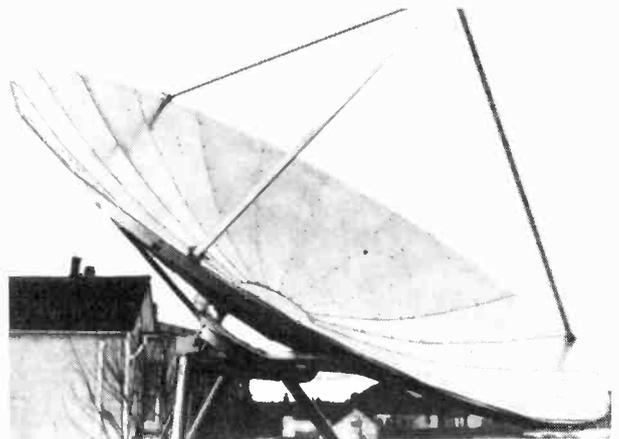6FT. PARABOLIC DISHES FROM ONLY £85 PLUS V.A.T.



6ft. dia. dishes, feed horns and electronics for use in 4GHz satellite reception. GaAs Fet transistors, SMA connectors, P.T.F.E., etc. available. Please send s.a.e. for full details and data sheets.

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX
Tel. Southend (0702) 332338

WW - 027 FOR FURTHER DETAILS

PRINTED CIRCUITS FOR WIRELESS WORLD PROJECTS

Audio compressor/limiter—Dec. 1975—1 s s (stereo)	£4.25
Cassette recorder—May 1976—1 s s.	£5.00
Audio compander—July 1976—1 s s.	£4.25
Audio preamplifier—November 1976—2 s s.	£8.50
Additional circuits—October 1977—1 s s	£4.00
Stereo coder—April 1977—1 d s 2 s s	£8.50
Low distortion disc amplifier (stereo)—September 1977—1 s s.	£2.00
Low distortion audio oscillator—September 1977—1 s s	£3.50
Synthesized f.m. transceiver—November 1977—2 d.s. 1 s s.	£12.00
Morsemaker—June 1978—1 d s	£4.50
Metal detector—July 1978—1 d s	£3.75
Oscilloscope waveform store—October 1978—4 d s	£18.00
Regulator for car alternator—August 1978—1 s s.	£2.00
Wideband noise reducer—November 1978—1 d s	£5.00
Versatile noise generator—January 1979—1 s s	£5.00
200MHz frequency meter—January 1979—1 d s	£7.00
High performance preamplifier—February 1979—1 s s	£5.50
Distortion meter and oscillator—July 1979—2 s s	£5.50
Moving coil preamplifier—August 1979—1 s s	£3.50
Multi-mode transceiver—October 1979—10 d s	£35.00
Amplification system—Oct 1979—3 preamp 1 poweramp	£4.20 each
Digital capacitance meter—April 1980—2 s s	£7.50
Colour graphics system—April 1980—1 d s	£18.50
Audio spectrum analyser—May 1980—3 s s	£10.50
Multi-section equalizer—June 1980—2 s s	£8.00
Floating-bridge power amp—Oct 1980—1 s s (12V or 40V)	£4.00
Nanocomp 6802 or 6809—Jan., July, 1981—1 d.s. 1 s.s.	£9.00
Cassette interface—July, 1981—1 s.s.	£1.50
Eprom programmer—Jan., 1982—1 d.s.	£4.50
Logic probe—Feb., 1981—2 d.s.	£6.00
Modular frequency counters—March, 1981—8 s.s.	£20.00
Opto electronic contact breaker (Delco)—April, 1981—2 s.s.	£4.00
CB synthesiser—Sept.—1 d.s.	£6.00
Electronic ignition—March, 1982—1 s.s.	£4.00

Boards and glassfibre roller-tinned and drilled. Prices include VAT and UK postage. Airmail add 30%, Europe add 10%. Insurance 10%. Remittance with order to:

M. R. SAGIN, NANCARRAS MILL, THE LEVEL CONSTANTINE, FALMOUTH, CORNWALL

WW - 029 FOR FURTHER DETAILS

SCOOP PURCHASE OF TEKTRONIX GRAPHICS EQUIPMENT

**HUGE SAVINGS FROM NEW PRICES
ONLY SLIGHTLY USED — COVERED BY FULL WARRANTY**

GRAPHICS TERMINALS • COLOUR GRAPHICS DESKTOP COMPUTERS • PLOTTERS • MONITORS

4006-1 HIGH RESOLUTION GRAPHICS DISPLAY TERMINAL

Alphanumeric Mode: 35 x 74 characters
(63 ASCII character set)
Graphics Matrix: 1024X x 1024Y
Baud Rate: 75 thru 4800 Interface: Standard RS232
£1525



4010-1 HIGH RESOLUTION GRAPHICS DISPLAY TERMINAL

Alphanumeric Mode: 35 x 74 characters
(63 ASCII character set)
Graphics Matrix: 1024X x 1024Y
Baud Rate: 110 thru 9600 Interface: Standard RS232
Thumbwheel crosshair cursor Integral Stand
£2750



4014-1 and 4015-1 HIGH RESOLUTION BIG (19") SCREEN GRAPHICS DISPLAY TERMINALS

Alphanumeric Mode: up to 133 x 64 characters
(94 ASCII character set or 188 ASCII + APL on model 4015)
Graphics Mode: 4096X x 4096Y
(includes enhanced graphics option)
Interface Standard RS232
Thumbwheel crosshair cursor Integral Stand

4014-1 **£6950** 4015-1 **£7250** 4016-1 25" Screen model **£8950**



4027 COLOUR GRAPHICS TERMINAL

Providing 8 displayable colours from a palette of 64 colours, and 120 user defined patterns
Interface: Standard RS232 Baud rates: up to 9600
£5250



4051 DESKTOP COMPUTER PROVIDING

High resolution Graphics and Alphanumerics,
32KB Memory, Integral Cartridge Tape Drive
£2250




4952 OPT. 2 JOYSTICK

(for 4050 series) sensitive cursor-control
with .1% accuracy and XY zero feature
£275

4662 INTELLIGENT DIGITAL PLOTTER

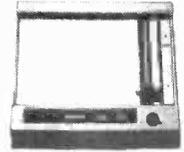Microprocessor Controlled high speed plotting up
to 1.0" x 15" with built-in joystick control.
IEEE general purpose interface
£1800



4663 INTELLIGENT DIGITAL PLOTTER


Microprocessor Controlled high speed plotting up
to 1.7" x 22" with built-in joystick control.
Standard RS232 Interface.
Baud rates 110-9600
£4000



HIGH RESOLUTION DISPLAY MONITORS

606 DISPLAY MONITOR

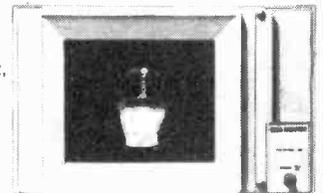5" CRT, 5ml Spot size, XY amplifier DC to 3MHz,
2-axis amplifier DC to 10MHz
£650




606A DISPLAY MONITOR

as above **£875**

606B DISPLAY MONITOR

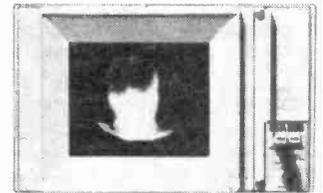5" CRT, 3ml Spot size, XY amplifier DC to 3MHz,
2-axis amplifier DC to 5MHz
£950



607A VARIABLE PERSISTENCE DISPLAY MONITOR

5" CRT, Storage view time 3 mins plus,
XY amplifier DC to 3MHz, 2-axis DC to 5MHz
£875

611 STORAGE DISPLAY MONITOR

11" CRT, Storage view time 15 mins plus, XY amplifier, Programmable
Erase, write-thru, non-store and view functions
£1450

DEC SALE a selection from our huge stocks All items reconditioned unless otherwise stated

DEC SYSTEMS

PDP11/23 SYSTEM
11/23 CPU, 128KB MOS, Dual RLO2
& Control, DLV11J 4-line Interface,
Cabinet, VT100 Console, NEW
£10,975

PDP11/24 SYSTEM
11/24 CPU, 256KB MOS, Dual RLO2
& Control, Cabinet, VT100 Console,
NEW
£15,750

PDP11/34 SYSTEM
11/34 CPU, 256KB MOS, Dual
RK07 & Control, Cabinet, LA36
Console
£13,725

PDP11/70 SYSTEM
11/70 CPU 1MB CORE Dual Data
System Cabinet, RMO3 & Control,
LA120 Console
£38,500

WS78 WORD PROCESSOR
WT78 Word Terminal and Processor
RX01 Dual Floppy Disk Drive Diablo
Letter Quality Printer. Complete with
cabinets and full documentation
£2950

DEC CONTROLLERS

RH11 (NEW) **£3,000**
RK11D (NEW) **£895**
RK711 **£1,750**
RKV11 **£525**
RX211 **£195**
TMB11 (NEW) **£1,250**

DEC 11/70 MEMORY

MJ11BY Memory box including
Controller and 64KW Core
(excluding cables)
£2250
MJ11BM 32KW Core Stack
£600

DEC PRINTERS AND TERMINALS

LA36 DECwriter II 20mA **£295**
LA36 DECwriter II RS232 **£325**
LA180-PD DECprinter I
(NEW) **£495**
VT50 DECscope 20mA **£199**
VT50 DECscope RS232 **£225**
VT105 Graphics Terminal **£950**

NEW HAZELTINE VDUS

Hazeltine 1420 **£350**
Hazeltine 1510 **£550**
Hazeltine 1520 **£625**

VT100-PLUS


SPECIAL PURCHASE BRAND NEW SURPLUS

DEC PDT11/130 PROGRAMMABLE DATA TERMINAL COMPRISING:

- ★ VT100 with Advanced Video Option & Printer Port
- ★ Integral LSI Processor with 32K RAM
- ★ Integral dual TU58 mini cartridge

Fantastic value whether for use
as VT100 only or as full PDT

£995 including
comprehensive manual

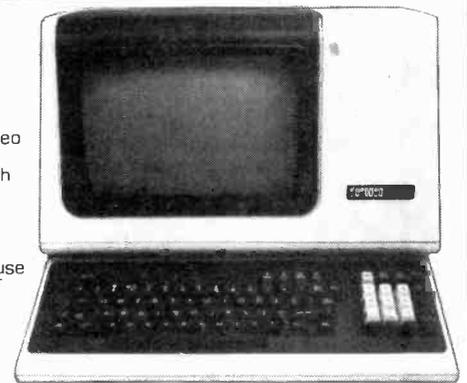


New Winter '82/83 Catalogue now out. Send for your FREE copy now.
ADD 15% VAT TO ALL PRICES Carriage and Packing extra

**Electronic Brokers Ltd., 61/65 Kings Cross Road
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**




GET BIG POWER

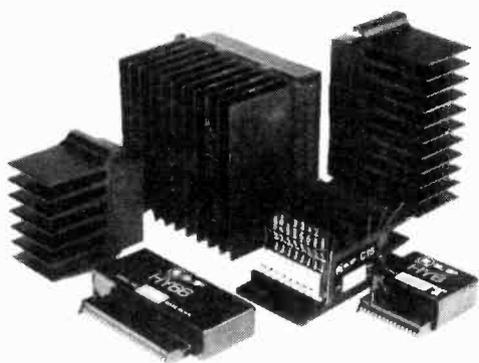

Modular Amplifiers the third generation

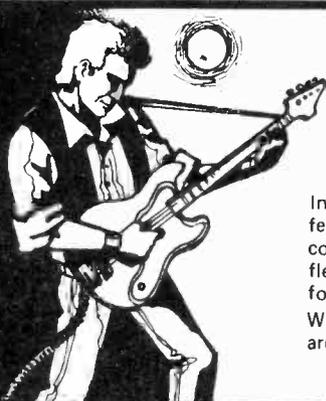Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
HY240	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY64	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15V/ μ s. Rise time: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass/Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules, if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93	PSU 52X	2 x HY124	£17.07
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83	PSU 53X	2 x MOS128	£17.86
PSU 42X	1 x HY128	£15.90	PSU 54X	1 x HY248	£17.86
PSU 43X	1 x MOS128	£16.70	PSU 55X	1 x MOS248	£19.52
PSU 51X	2 x HY128, 1 x HY244	£17.07	PSU 71X	2 x HY244	£21.75

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	120	£11.47
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£31.86
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20V/ μ s. Rise time: 3 μ s. S/N ratio: 100db.

Frequency response (-3dB) 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz.

S/N ratio (DIN AUDIO) 80dB. Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248 1 x MOS368	£24.20

WITH A LOT OF HELP FROM





PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

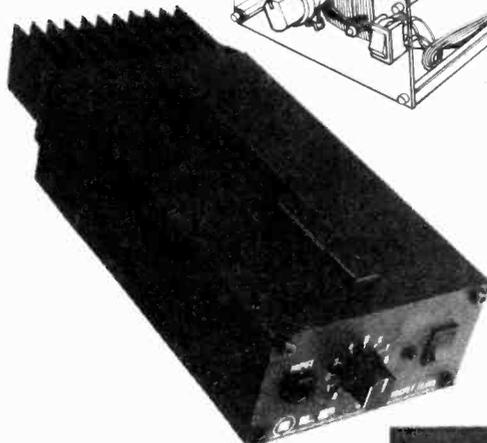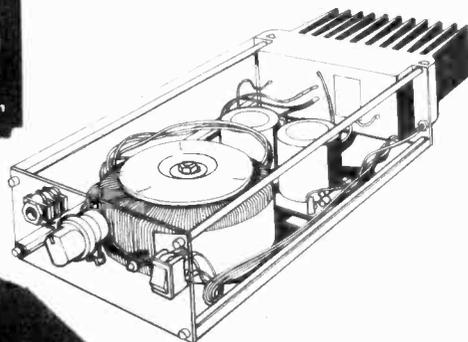Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.

UNICASES

HiFi Separates					Price inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4 Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4 Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.96
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.

TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd, if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED



Post to: ILP Electronics Ltd., Freepost, 5 Graham Bell House, Roper Close, Canterbury, CT2 7EP, Kent, England. Telephone: (0227) 54778. Technical: (0227) 64723. Telex: 965780.

Please send me the following _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____


Signature _____

Middle East Wire & Wireless Ltd.

TILEMAN HOUSE, 131 UPPER RICHMOND ROAD, PUTNEY, LONDON SW15. TEL: 785 6422, TELEX: 261768 MEWIRE G.

*FULL RANGE OF VHF/UHF RADIOTELEPHONES
BASE/MOBILE/HAND-HELD AND MARINE RADIOTELEPHONES*

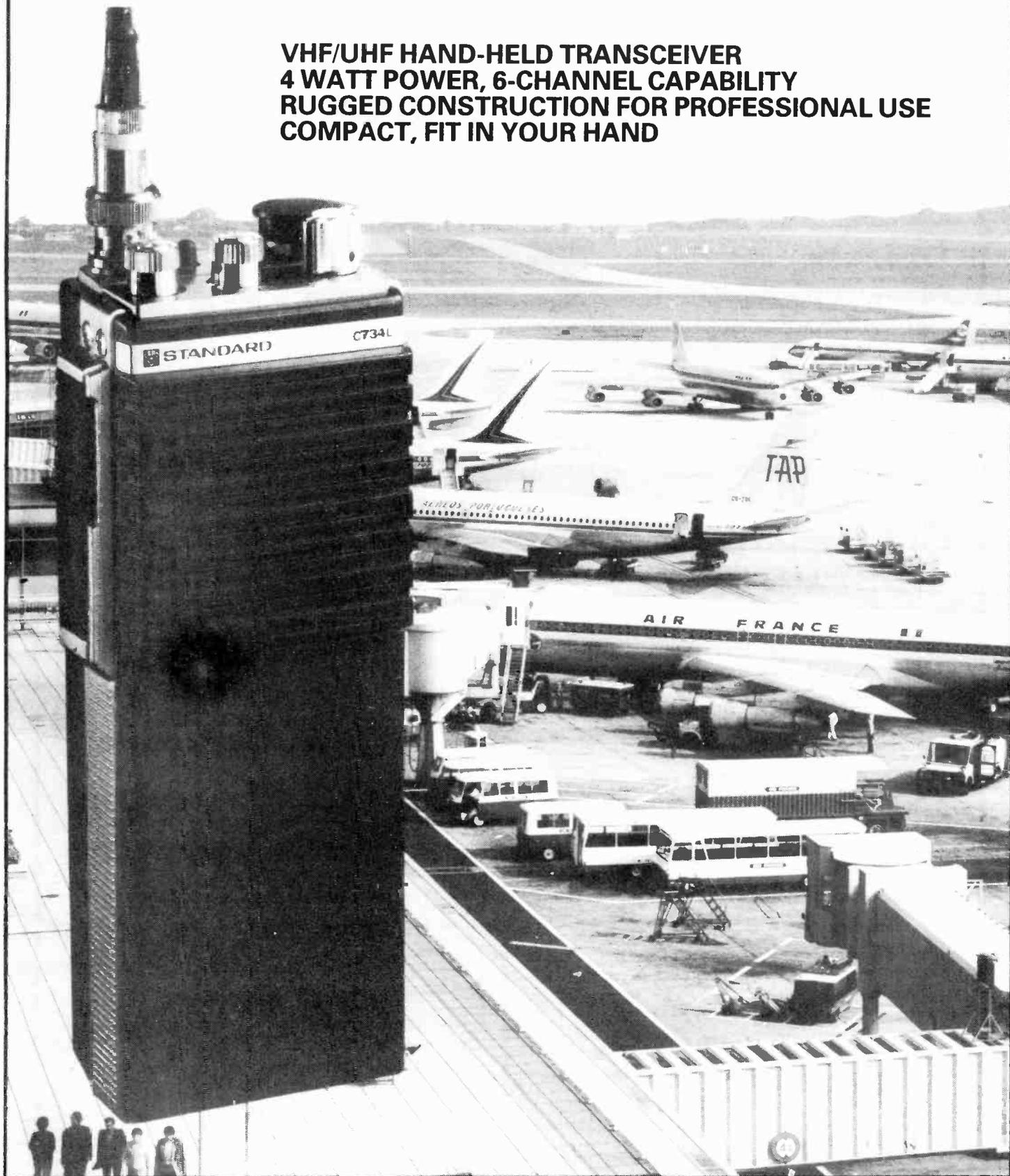**VHF/UHF HAND-HELD TRANSCEIVER
4 WATT POWER, 6-CHANNEL CAPABILITY
RUGGED CONSTRUCTION FOR PROFESSIONAL USE
COMPACT, FIT IN YOUR HAND**



WW - 066 FOR FURTHER DETAILS



RSGB National Amateur Radio Convention

National Exhibition Centre, Birmingham

Saturday 5th March 10am to 6pm, Sunday 6th March 10am to 5pm

FEATURING



Introduction to Amateur Radio for Beginners.



Lectures on Propagation, VHF and Microwaves.



Annual RSGB HF Convention.



Forum for VHF and Repeater Enthusiasts.



Major Exhibition of Amateur Equipment & Components.

**Entrance Fee £2
Car Parking Free**



Organised by RSGB Exhibition Rally Committee

Do you know anybody who can build a Digital Pulser for only £18.00? *




The answer is yes — its YOU!

With GSC's new DPK-1 kit, you can build a sophisticated portable test instrument for stimulus/response testing. It automatically delivers just the right signal for whichever logic family you're using — and it's equally suited to single pulses or pulse trains at a frequency of 100 per second. The fully featured DPK-1 kit includes all components, leads, circuit board and case — and is supplied complete with detailed assembly instructions and an operating manual.

Get rid of your digital hang-ups; send off for a DPK-1 straight away.

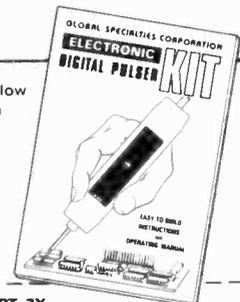Easy to follow
Instruction
Manual
with every
Kit



GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) LIMITED
UNIT 1, SHIRE HILL INDUSTRIAL ESTATE
SAFFRON WALDEN, ESSEX CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

GLOBAL SPECIALTIES CORPORATION (UK) LIMITED, DEPT. 7X
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

DIGITAL PULSER KIT DPK-1	£22.42 (inc. P & P & 15% VAT)	Quantity Reqd.	For FREE catalogue tick box <input type="checkbox"/>
-----------------------------	----------------------------------	-------------------	--

Name _____ Address _____

I enclose PO/Cheque for £ _____ or debit my

Barclaycard/Access/American Express. No. _____ exp date _____

WW - 011 FOR FURTHER DETAILS

SWITCHES TOGGLE 2A 250V SPST 33p DPDT 44p SUB-MIN TOGGLE SPST on/off 54p SPDT c/over 60p SPDT centre off 85p SPDT biased both ways 105p DPDT 6 ways 75p DPDT centre off 88p DPDT biased both ways 145p DPDT 3 positions on/one/on 185p 3-pole/2 way 205p SLIDE 250V DPDT 1A 14p DPDT 1A c/off 14p DPDT 1/2A 13p PUSHBUTTON 6A with 10mm Button SPDT latching 99p DPDT latching 145p SPDT moment 99p DPDT moment 145p Mini Non Locking Push to Make 15p Push to Break 25p ETI PROJECTS 24 We stock most of the parts  IDC Female Header Socket Jumper Leads 24" 40p 20 pin 26 pin 34 pin 40 pin Single ended 160p 200p 260p 300p Double ended 290p 370p 480p 525p	DIL SWITCHES (SPST) 4-way 70p; 6-way 85p; 8-way 90p; 10-way 145p. (SPDT) 4-way 190p. ROTARY SWITCHES (Adjustable Stop type) 1 pole/2 to 12 way; 2p/2 to 6 way; 3 pole/2 to 4 way; 4p/2 to 3 way 45p ROTARY: Mains DP 250V 4 Amp on/off 58p ROTARY: (Make-a-switch) Make a multi-way switch. Shafting assembly has adjustable stop. Accommodates up to 4 wafers. (max 6 pole/12 way - DP switch) Mechanism only 90p WAFERS: (make before break) to fit the above switch mechanism 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6p/2 way 65p Mains DP 4A Switch to fit Spacers 4p. Screen 6p ROCKER: 5A/250V SPST 28p ROCKER: 10A/250V SPDT 38p ROCKER: 10A/250V DPDT c/off 96p ROCKER: 10A/250V DPST with neon 85p THUMBWHEEL: Mini front mounting Decade Switch Module 220p B.C. Switch Module 275p Mounting Cheeks (per pair) 75p	VEROBOARD 0.1in 2 1/2 3/4" clad plain 80p 2 1/2 3/4" 91p 3/4 5" 105p 87p 3/4 17" 360p 232p 4 3/4 17" 470p 50p Pkt of 100 pins 50p Spot face cutter 135p Pin insertion tool 175p VERO WIRING PEN + Spool 340p Spare Spool 75p Combs 6p FERRIC CHLORIDE 1 lb bag Anhydrous 195p 5 lb bag P&P 475p	VQ Board DIP Board 350p Vero Strip 95p PROTO DECS Veroblock 405p S-Dec 350p Eurobreadboard 520p Bimboard 1 575p Superstrip SS2 1350p DALO ETCH RESIST PEN Plus Spare Tip 27p ULTRASONIC TRANSDUCER 40kHz 325 pr	IC CONNECTORS PCB Plugs Female Female with latch Pins Hdr. Card Pins Angle Plug Edge Conn. 10 way 90p 95p 85p 120p 16 way 130p 150p 110p 120p 20 way 145p 160p 125p 195p 26 way 175p 200p 150p 240p 34 way 205p 236p 169p 320p 40 way 225p 250p 190p 340p 50 way 235p 270p 200p 395p 60 way 230p 230p 495p EURO CONNECTORS Female Socket Male Plug Strt. Angle 3Strt. Angle Pins Pins Pins DIN41617 170p - - 175p DIN41612 275p 320p 220p 285p 2x32 A+B DIN41612 295p 340p 240p 300p 2x32 A+C D1N 4 16 1 2 360p 360p 360p 360p DIL PLUG (Header) IDC 14 pin 40p 99p 16 pin 49p 105p 24 pin 89p 178p 40 pin 250p 255p RIBBON CABLE price per foot 10 way 12p 22p 16 way 18p 32p 20 way 25p 40p 24 way 35p 50p 34 way 48p 60p 40 way 55p 75p 50 way 65p 90p 64 way 85p 110p ZIF DIL SOCKETS 24 pin 575p 28 pin 820p 40 pin 975p	PANEL METERS FSD 80x46x35mm 0.50uA 0.100uA 0.500uA 1.0mA 0.5mA 0.10mA 0.50mA 0.100mA 0.500mA 0.1A 0.2A 0.50V AC 0.300V AC "VU" 425p each RELAYS Miniature enclosed PCB mount SINGLE POLE Changeover RL6-91 205u Coil; 12V DC, 10V5 to 19.5V. 10A at 30V DC or 250V AC 185p DOUBLE POLE Changeover. 6A 30V DC or 250V AC RL6-100 53u Coil, 6V DC (5V4 to 9V9) 190p RL6-111 205u Coil, 12V DC (10V7 to 19V5) 195p RL6-114 740u Coil, 24V DC (22V to 37V) 200p AMPHENOL PLUGS IEEE 24 way Centronics Parallel 36 way solder 550p Centronics Parallel 36 way IDC 530p Centronic Parallel 36 way IDC 495p BUZZERS: miniature, solid-state 6V, 9V & 12V PIEZO TRANSDUCERS 70p PB2720 55p LOUDSPEAKERS Miniature 0.3W 8u 2in, 3 1/4in, 2 1/2in, 3in 2 1/2in 40u, 64u or 80u 90p ASTEC UHF MODULATORS Standard 6MHz 280p Wideband 8MHz 480p 'WEMON' New Version WATFORD'S Ultimate Monitor IC A 4K Monitor chip specially designed to produce the best from your Super board Series I & II. Enhanced Super board & UK101. As reviewed by Dr A. Berk in Practical Electronics, June 1981. Only £10
--	--	---	---	---	--

TRANSFORMERS: 3-0-3V; 6-0-6V; 9-0-9V; 12-0-12V; 15-0-15V @ 100mA 95p pcb mounting Miniature Split Bobbin 3VA: 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p 6VA: 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A 270p Standard Split Bobbin type 8VA: 2x6V 0.5A; 2x9V 0.4A; 2x12V 0.3A; 2x15V 0.25A 220p 12VA: 2x4.5V-1.3A; 2x6V-1A; 2x9V 0.6A; 2x12V 0.5A; 2x15V 0.4A; 2x20V 0.3A 290p 24VA: 2x6V-1.5A; 2x9V-1.2A; 2x12V-1.2A; 2x15V-0.9A; 2x20V-0.6A 330p (60p p&p) 50VA: 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x20V-0.8A 465p (60p p&p) Specially wound for Multirail Computer PSU's 50VA; Outputs: +5V/5A; +12V; +25V; -5V; -12V/1A 575p (60p p&p) 100VA; 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and over our normal postal charge).	VOLTAGE REGULATORS 1A T0220 Plastic casing 95p 5V 7805 40p 7905 45p 12V 7812 40p 7908 60p 15V 7815 40p 7912 45p 18V 7818 40p 7915 45p 24V 7824 40p 7918 45p 24V 7824 40p 7924 45p 100mA T092 Plastic package 5V +ve 30p -ve 78L05 60p 6V 78L06 30p 78L06 30p 8V 78L08 30p 78L12 60p 12V 78L12 30p 79L12 60p 15V 78L15 30p 79L15 60p SOLDERCON PINS Ideal for making SIL or DIL sockets 100pins 75p 500pins 350p ALUM BOXES 3x2x1" 85p 4x2x2 1/2" 85p 4x4x2 105p 4x4x2 1/2" 120p 5x4x1 1/2" 99p 5x4x2 1/2" 120p 5x2x4 1/2" 99p 6x4x2 120p 6x4x3 150p 7x5x3 210p 8x6x3 210p 8 1/2 H G + 5 V 1 10x4x3 240p +25V/5A 599p 79HG +2.25V 12x5x3 240p 24V5A 24x8x3 295p	D CONNECTORS: Miniature 9 way 15 way 25 way 37 way MALE Solder lugs 80p 105p 180p 250p Angle pins 150p 210p 250p 385p PCB pins 120p 130p 195p 295p FEMALE Solder lugs 105p 160p 200p 335p Angle pins 185p 215p 290p 440p PCB pins 150p 180p 240p 385p COVERS 90p 85p 90p 100p IDC 25 way D Plug 385p Skt. 450p 25 way 'D' CONNECTOR Jumper Lead Cable Assembly 495p 18" long, Single end, Male 495p 18" long, Single end, Female 525p 36" long, Double ended, M/M 1025p 36" long, Double ended, F/F 1050p 36" long, Double ended, M/F 995p ★ SPECIAL OFFER ★ 2532 285p 6116 375p 2764 550p 6522 280p
---	--	---

CMOS 4000 10 4075 50 4001 10 4078 15 4002 12 4081 13 4006 50 4082 13 4007 14 4085 50 4008 32 4086 80 4009 24 4087 125 4010 24 4093 20 4011 10 4094 70 4012 18 4095 95 4013 20 4096 70 4014 46 4097 770 4015 40 4098 75 4016 20 4099 110 4017 32 4100 95 4018 45 4101 99 4019 25 4102 99 4020 42 4103 99 4021 40 4104 99 4022 40 4105 105 4023 13 4104 105 4024 32 4408 790 4025 13 4408 790 4026 80 4410 725 4027 20 4411 675 4028 39 4412 775 4029 45 4415 480 4030 15 4419 280 4031 125 4420 770 4032 80 4435 850 4033 125 4440 999 4034 140 4450 350 4035 45 4451 350 4036 275 4460 350 4037 115 4500 675 4038 110 4501 28 4039 250 4502 60 4040 40 4503 40 4041 40 4504 75 4042 40 4505 185 4043 40 4506 305 4044 40 4507 35 4045 105 4508 130 4046 46 4510 46 4047 40 4511 45 4048 40 4512 50 4049 25 4513 199 4050 25 4514 115 4051 45 4515 115 4052 60 4516 55 4053 50 4517 275 4054 85 4518 40 4055 85 4519 30 4056 85 4520 50 4057 1915 4521 90 4058 435 4522 125 4060 45 4526 70 4061 1195 4527 70 4062 995 4528 70 4063 85 4529 150 4066 24 4530 90 4067 245 4531 130 4068 14 4532 70 4069 16 4534 40 4070 13 4536 275 4071 13 4538 80 4072 13 4539 90 4073 15 4541 140	OPTO ELECTRONICS LEDs with Clips TIL209 Red 10 TIL211 Green 14 TIL212 Yellow 14 TIL220 2" Red 12 2" Green, Yellow or Amber 14 0.2" Bicolour Red/Green 65 Green/Yellow 78 0.2" Tricolour Red/Green/Yellow 85 Hi-Brightness Red 85 Flashing Red 0.2" Red 55 Square LEDs, Red, Green, Yellow 30 Rectangular Stackable LEDs: Red, Green or Yellow 18 Triangular LEDs Red 18 Green or Yellow 22 LD271 Infra Red 46 SFH205 Detector 118 LM317KP 58 TIL32 Infra Red 60 TIL32 Detector 60 TIL38 45 TIL100 80 BARGRAPH Red 10 seg-ments 225 ISOLATORS IL74 55 ILD74 99 ILQ74 185 TIL111/2/4 90 TIL117 125 #N33 Photo 60 Darlington 135 7 Segment Displays TIL307 675 TIL312 3" CA 105 TIL313 3" CA 105 TIL321 5" CA 115 TIL322 5" CC 115 DL704 3" CC 99 FL707 3" CA 99 FN0357 Red 120 FND930 70 3" Green CA 115 6" Green CA 215 3"±1 Red CA 150 3"±1 Green CA 150 DVM 176 1885 LCD 3 1/2 Digits 495 LCD 4 Digits 530 LCD 6 Digits 625 NEONS Rectangular, nut fixing Red, Amber, Green 30 3" Green CA 150 6" Green CA 215 1" Red CA 150 REFLECTIVE Optical 105 Switch type TIL139 170 SLOTTED Optical Switch similar to RS Combs 186
---	--

COMPUTER CORNER ● MX80FT/3 EPSON PRINTER. 10" & Friction feed, 9 x 9 matrix, 80 column, Speed 80CPS. Bidirectional, Centronics Interface standard. Baud-rate 110-9600 (RS232), Hi-Res. Bit image graphics. Subscript & Superscript, Italics & Underlining facility plus 500 sheets of paper FREE £324 (+£7 carr.) ● MX100 EPSON Printer, 136 Column, 15" carriage, plus all the features of MX80FT/3. Plus FREE 500 sheets of paper. Only £425 (+ carr.) ● SOFTY II. An intelligent Eprom Programmer and Emulator. Accepts a 24 pin 5V Eprom. Has Memory Map TV Display, RS232 and Centronics I/P & O/P. Copies, Emulates and programs. RS 232 and centronics routines standard. PSU included. £169 ● TEX EPROM ERASER. Erases up to 32 ICs in 15-30 minutes £33 ● TEX EPROM ERASER with a safety switch £35 ● TEX EPROM ERASER plus our Solid State ELECTRONIC TIMER £44 ● ELECTRONIC TIMER. Solid state, 15-30min. Connects directly to above Erasers. Protects your expensive Chips from overcooking. Our timer pays for itself in no time £15 ● SPARE 'UV' Lamp bulb £8 ● POWER SUPPLY. Regulated with Overload protection. Variable output, 5V to 15V at 4A. Professionally finished. £38 ● MULTIRAIL POWER SUPPLY KIT. Especially designed for Micros. Tested output: +5V/5A; +12V; +25V; -12V of 1A £37 ● C12 COMPUTER GRADE CASSETTES in library cases £40p ● 8 1/2" and 9 1/2" Fan Fold paper (1000 sheets) £7 (£1.50 carr.) ● SEIKOSHA GP100A 10" Tractor Feed, 80 Column. 30CPS, Normal and Double Width Char. Dot Res Graphics £175 (£7 carr) ● SEIKOSHA GP250X. 10", 50 CPS, Normal and Double width and height Char. RS232 and Centronic Infr. standard £240 (£7 carr) ● Printer Cable for our printers and BBC £12 FLOPPY DISC DRIVES ● TEAC FD50A - Uncased, S/S, 40 track, 5 1/4", 100K £125 ● TEAC FD50A - Cased S/S, 40 track, 5 1/4", no PSU £150 ● TEAC FD50A - Cased with PSU, S/S, 40T, 5 1/4" £180 ● TEAC FD50A - Twin Cased, PSU, S/S, 5 1/4", 200K £350 ● TEAC FD50E - Twin Cased, PSU, D/S, 80 track, 400K £475 ● Drive CABLES for BBC Micro. Single £8; Double £12 N.B. All above drives are BBC Micro compatible ● SIEMENS FDD 100-5 Drive. Cased with PSU. Has track zero micro switch and motor control. PCB with read, write and control electronics. Connecting cable incl. Especially made for APPLE II Micro £215 ● APPLE II Interface Card for above £42 ● 10 VERBATIM Diskettes 5 1/4", S.S.D.D. £20 ● 10 VERBATIM Diskettes 5 1/4", D.S.D.D. £30 ● 10 VERBATIM Diskettes 8", S.S.D.D. £28 N.B. Carriage is extra on all disc drives.	NEC PC8023BE-C PRINTER Europe's most popular printer 100CPS bi-directional, Logic seeking, 80 column, 7 x 9 Dot matrix head, true descenders on lower case, Superscript & Subscript & Underlining facility. Proportional spacing, Forward & reverse line feed, Tractor or friction feed, Hi-res & block graphics. Auto underlining. Plus FREE 500 sheets of Paper. Price: Only £320 + £7 carr.
--	--

MONITORS ● MICROVITEC 1431. 14" Colour Monitor. RGB input (as used in BBC prog.) £250 ● ZENITH 12" Green Monitor, Hi-Res. £80 ● AVT 9" Green, Anti-glare filter, 12MHz £95 ● AVT 9" B&W, Anti-glare filter, 12MHz £89 ● AVT 9" Amber, Anti-glare filter, 12MHz £98 Carriage on all Monitors is £7 (Securicor)	WE - ROM for ACORN ATOM A highly sophisticated Acorn Utility ROM. Plugs straight into floating point Atom's Utility socket. Gives many unique BASIC Extensions: Hi-speed Tape Interface, 2 Key rollover Keyboard, Full disassembler, Memory dump modify, Machine code breakpoints; Basic error trapping; READ, DATA & RESTORE; Full BASIC Keyboard scanner (BBC like); Find line and delete; Auto line numbering; Plus: Chain, Cursor movement, Loop aborting; Easily extendible further. Manual supplied. Only £9.95
--	--

Xtec

TAC

The best route for data communications

New, low-cost Terminal Access Controller (TAC) can solve both immediate and future data communications needs. Versatile, software-controlled data switchboard caters for multiple service requirements and growing user needs without disrupting or replacing existing services and equipment.

TAC SERIES 3 for micro-networking
TAC SERIES 4 for the higher volume user

Whether you need 16 or 256 communications channels Xtec can provide full data communications capability, with intelligent switching, protocol conversion, multiplexing and coupling as required.



For further information contact
Xtec Limited, High Street, Hartley Wintney
Basingstoke, Hampshire RG27 8PB
Tel: Hartley Wintney 4222/4233/4344 Telex: 849286 CAVAC


WW - 024 FOR FURTHER DETAILS

THE UNIQUE:-

'ATLAS' ROBOTIC SYSTEM



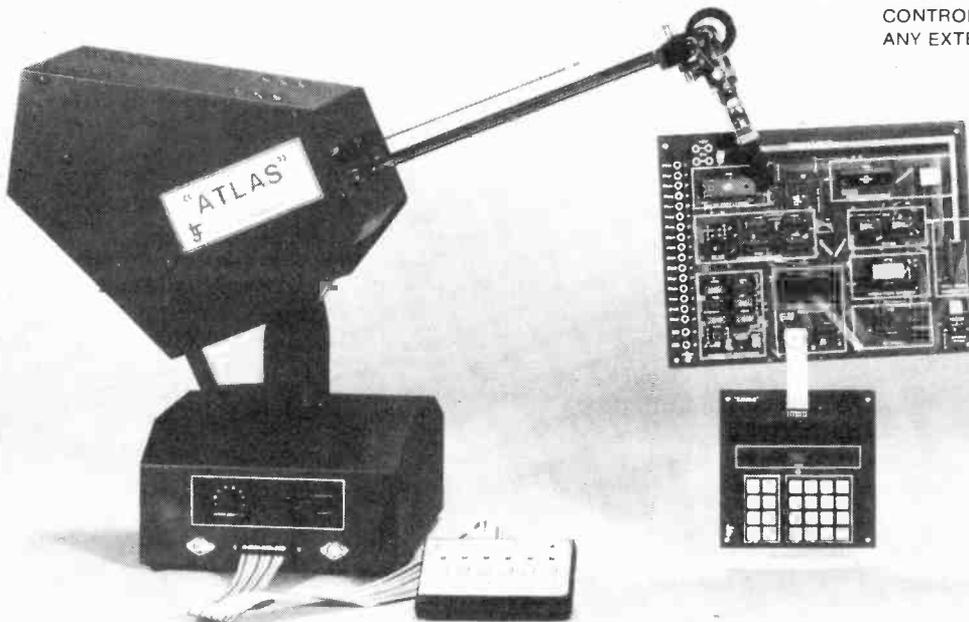- INTELLIGENT/BUILT-IN MICROCOMPUTER
- SIX OPERATING FUNCTIONS, STEPPER MOTOR DRIVEN
- HIGH PRECISION REPEATABILITY OF OPERATION SEQUENCE
- LIGHT INDUSTRIAL QUALITY
- EASY GENERATION OF OPERATION SEQUENCES FROM THE REMOTE CONTROL PAD SUPPLIED, OR FROM ANY EXTERNAL COMPUTER



THE SUPERB 'ATLAS' ROBOT REPRESENTS JUST ONE ITEM FROM OUR EVER-EXPANDING RANGE OF MICROPROCESSOR TEACHING SYSTEMS.

SEND FOR DETAILS TODAY, FROM THE FASTEST GROWING SUPPLIER OF MODERN EDUCATIONAL MICROELECTRONICS

L.J. ELECTRONICS LTD.

FRANCIS WAY, BOWTHORPE IND ESTATE, NORWICH, NR5 9JA TEL: 0603 - 748001/2 TELEX: 975504

WW - 020 FOR FURTHER DETAILS

RADIOCODE CLOCKS

are powerful and comprehensive instruments which receive, decode and analyse time-coded standard frequency transmissions to provide accurate, secure and completely automatic time/calendar or synchronisation systems.



Applications


- Automatic master clock and slave controller.
- Synchronisation of separate equipment and events.
- Programmable energy management system.
- Computer clock/calendar with battery backup.
- Data logging and time recording.
- Process and equipment control.
- Broadcasting, Astronomy, Navigation.
- Satellite tracking.

If you have a time or synchronisation problem, write or phone for further details of our portable and new microcomputer-controlled Radiocode Clocks.

Circuit Services, 6 Elmbridge Drive
Ruislip, Middlesex. Ruislip 76962

WW - 031 FOR FURTHER DETAILS

METER PROBLEMS?

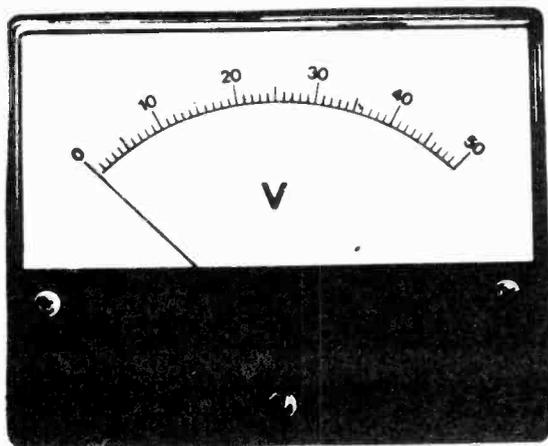


137 Standard Ranges in a variety of sizes and stylings available for 10-14 days' delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)
138 GRAY'S INN ROAD, W.C.1 Phone: 01-837 7937
Telex: 892301 HARTO G

WW - 039 FOR FURTHER DETAILS

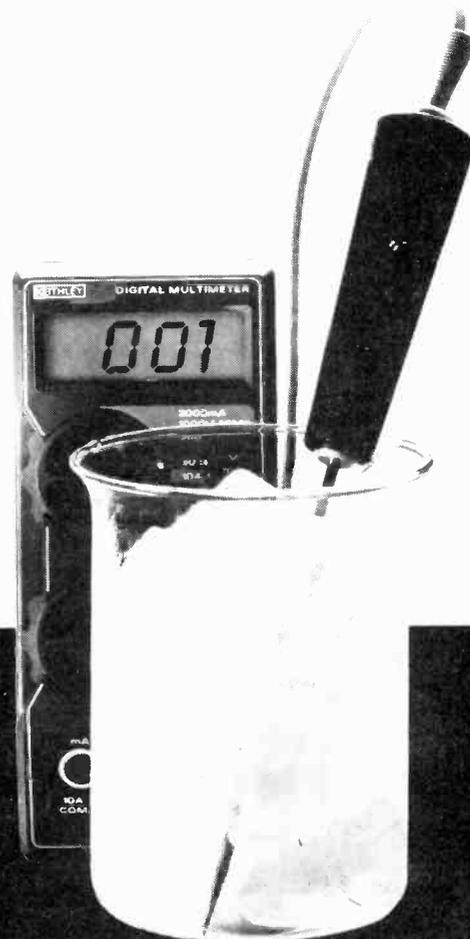

IS YOUR TRMS DMM RUNNING A TEMPERATURE?

The answer is almost certainly no, unless you've got your hands on a brand new Keithley 132C.*

The latest addition to a trend-setting range of handheld units from Keithley Instruments, the 132C is a 3½ digit meter with TRMS, TEMP and 0.25% DCV accuracy.

Key features include

- AC and DC amps from 1 µA resolution to 2 amps full scale
- Ohms from 100mΩ resolution to 20MΩ
- DC Volts (±0.25% reading + 1 digit)
- TRMS AC Volts from 45 - 500Hz range (±1% reading + 9 digits)
- Temperature Range: -20°C to +150°C (±3% + 1 digit), 150°C to 1370°C (±3% of reading), Type K non-linearized, 1°C resolution

For more information get in touch now. You'll find it pretty hot stuff!

*Model 132F available for those requiring fahrenheit scales

KEITHLEY Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telex 847047

0734 861287

WW - 037 FOR FURTHER DETAILS



HF COMMUNICATIONS RECEIVERS

FOR

POINT TO POINT/TRANSPORTABLE

AND

MARINE SYSTEMS

DESIGNED AND MANUFACTURED TO HIGHEST INTERNATIONAL SPECS

Fully Synthesised
 10Hz or 100Hz steps
 Continuously Tuned 50KHz to 30MHz
 Modes LSB/USB/CW/AM/FSK
 Stability ± 1 part in $10^{7/0}C$
 Tuning Keypad/Spin/Decade
 Power Supplies
 110V/240V AC and 24V DC

WE ANNOUNCE NEW MODELS

- (a) SR 520 To meet new C.E.P.T. Spec for Ships Main Receiver.
 - (b) SR 522 with Preselector for Point to Point/Transportable.
 - (c) SR 530 As (a) above but MICROPROCESSOR/KEYPAD controlled, 200 channel memory, Scanning.
 - (d) SR 532 As (c) above but for Point to Point/Transportable.
- OPTIONS. Full Remote Control by VHF Radio or Telephone Line, Dual Diversity, FSK Demodulator and 600 ohm Line Amplifiers.

SEND FOR TECHNICAL BROCHURES TO:


VIGILANT COMMUNICATIONS LTD, UNIT 5, PONTIAC WORKS, FERNBANK ROAD, ASCOT, BERKS, ENGLAND

TELEPHONE: (0344) 885656

TELEX: 849769 VIGCOM G

WW - 036 FOR FURTHER DETAILS

Quartz Crystals

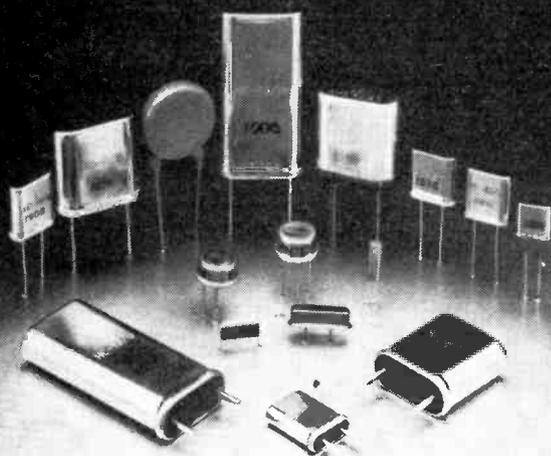

Stocks of standard items exceed a quarter of a million. Individual units to the tightest specification made to order.

This technology is available now from

**Interface
 Quartz
 Devices
 Limited**



29 Market Street
 Crewkerne
 Somerset TA18 7JU
 Crewkerne (0460) 74433
 Telex 46283 inface g

WW - 035 FOR FURTHER DETAILS

CLEF ELECTRONIC MUSIC

PIANOS



**SPECIALISTS SINCE 1972
 DOMESTIC OR STAGE
 SIX OR 7 1/4 OCTAVES
 KITS OR MANUFACTURED**

The most advanced form of touch-sensitive action simulating piano key inertia by patented technique

Four mixable voices for serious tone variation plus electronic chorus and flanger effects

DOMESTIC PRICES

£	SIX	7 1/4
Comp	234	266
Full	398	442
MFD	620	696

Component Kits include Keyboard.

Full Kits further contain: Cabinets, Harness, Power Amp and Speaker.

BAND-BOX

An Electronic Backing TRIO Drums, Bass & Chord Instrument. User Programmable for 50-100 scores, using microprocessor.



£79 KIT £119 BUILT

Kit £314
 Mfd £439
VOCAL & INSTRUMENTAL SOLOISTS

**MASTER RHYTHM
 DRUM MACHINE.**
 Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation.

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carriage & Ins. and we operate Telephone BARCLAY-CARD/ACCESS. Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED
 Dept. W, 44a Bramhall Lane South
 Bramhall, Stockport, Cheshire SK7 1AH
 061-439 3297

WW - 048 FOR FURTHER DETAILS

RECHARGEABLE BATTERIES

PRIVATE & TRADE ENQUIRIES WELCOME

Full range available to replace 1.5 volt dry cells and 9 volt PP type batteries, SAE for lists and prices. £1.45 for booklet, "Nickel Cadmium Power," plus catalogue.

★ New sealed lead range now available ★

Write or call at:

SANDWELL PLANT LTD.
 2 Union Drive, Boldmere
 Sutton Coldfield, West Midlands, 021-354 9764
 After Hours 0977 616913

WW - 033 FOR FURTHER DETAILS

CALL IN AND SEE FOR YOURSELF


AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)

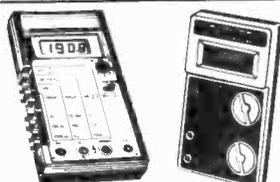

HAND HELD
 KD25C 13 range 0.2A DC 2 meg ohm £24.95
 KD30C 26 range 1A AC/DC 20 meg ohm £34.95
 KD55C 28 range 10A AC/DC 20 meg ohm £39.95
 6010A 22 range 10A AC/DC 20 meg ohm £34.40
 7030A As 6010 but 0.1% basic £41.30
 189M 16 range 10A DC 2 meg plus Hfe tester £39.95
 189M 30 range 10A AC/DC 20 meg plus Hfe tester £69.95

BENCH MODELS (3 1/2 digit unless stated)
 TM353 27 range LCD 2A AC/DC £86.25
 TM355 29 range LCD 10A AC/DC £86.25
 TM351 29 range LCD 10A AC/DC £113.85
 2001 28 range LCD 10A AC/DC plus 5 range Cap Meter with case £108.00
 TM451 4 1/2 digit LCD every facility [0.02%] £171.00
 1503a 4 1/2 digit LCD every facility [0.05%] £171.00
 1503M 0.03% basic version of above £189.00
 *Optional carry case £2.95 *With free carry case
 *Additional carry case £6.84

HAND HELD AUTO RANGE
 DM2350 21 range 10A AC/DC 20 meg ohm (Miniature) £49.95
 HD30 16 range 0.2A AC/DC 2 meg ohm £41.95
 HD30/B As above plus cont buzzer £44.50
 HD31 22 range 10A AC/DC 2 meg ohms plus cont buzzer £58.95

EDUCATIONAL DISCOUNTS AVAILABLE FOR ALL STOCKS - PLEASE ENQUIRE

FREQUENCY COUNTERS

PFM200A 200 MHz hand held pocket 8 digit LED £67.50
 8110A 8 digit LED bench 2 ranges 100 MHz £77.00
 8610B 9 digit LED bench 2 ranges 600 MHz £113.85
 8000B 9 digit LED 3 ranges 1 GHz £178.00
 TF040 8 digit LCD 40 MHz £126.50
 TF200 8 digit LCD 200 MHz £166.75
 *Optional carry case £6.84
 Prescalers - Extended range of most counters
 TP600 600 MHz £43.00
 TP1000 1 GHz £74.00

SIGNAL GENERATORS (220/240v AC)

FUNCTION: All sine/square/triangle/TTL etc
 TG100 1 Hz 100 KHz £90.00
 TG102 0.2 Hz 2 MHz £166.75

PULSE
 TG105 Various facilities 5 Hz - 5 MHz £97.75

AUDIO: Multiband Sine/Square
 AG22 10 Hz to 1 MHz £86.00
 AG20A 20 Hz to 200 KHz £78.00

RF
 SG402 100 KHz to 30 MHz £59.95
 LSG17 100 KHz to 150 MHz £71.00

ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100m with carry case £63.00

MULTIMETERS (UK C/P 65p)

Y7206 20K/V 19 range pocket meter SPECIAL PRICE £7.95
C7081 50K/V 21 ranges Range doubler 10A DC SPECIAL PRICE £15.95
ETC5000/5001 21 ranges 50K/V Range doubler 10A DC £16.50
TMK500 23 ranges 30K/V 12A DC plus cont buzzer £23.95
NH56R 20K/V 22 range pocket £10.95
EUI102 14 range 2K/V pocket £5.95
830A 26 range 30K/V 10A AC/DC over protection, etc £23.95
360TR 23 range 100K/V Large scale 10A AC/DC plus Hfe £36.95
AT1020 18 range 20K/V Deluxe plus Hfe tester £17.50
ST303TR 21 range 20K/V plus Hfe tester £16.95

AUDIO • RF • FUNCTION • PULSE OSCILLOSCOPES



Full specification any model on request. SAE by post.
'HM Series HAMEG: SC THANDAR: 'CS Series TRIO: '3 Series CROTECH

SINGLE TRACE
 3030 15 MHz 5mv 95mm tube plus component tester C/P £3.00 £172.50
 SC110A *Miniature 10 MHz battery portable Post free £171.00
 HM103 15 MHz 2mv 6 x 7 display plus component tester C/P £3.00 £177.00
 *Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50

DUAL TRACE (UK C/P £4.00)
 NM203/4 Dual 20 MHz plus component tester £276.00
 CS1566A Dual 20 MHz All facilities £299.00
 NM204 Dual 20 MHz plus component tester sweep delay £419.75

OPTIONAL PROBE KITS
 X1 £7.95 X10 £9.45
 X1 X10 £10.50 X100 £16.95

VARIABLE POWER SUPPLIES

PP241 0/12/24V 0/1A £35.00
 PP243 3 amp version £59.95 (UK C/P £1.00)

DIGITAL THERMOMETER

TM301 LCD 50°C to +750 with thermocouple £68.43

AC CLAMP METER

ST300 0/300A 0/600 VAC 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

LOGIC PROBS

LP10 10 MHz £28.50
 LDP76 50 MHz £56.90

STOCKISTS FOR TRIO: HAMEG: CROTECH: SAEFAN: SCOPES. MOST MODELS IN STOCK.

HIGH VOLTAGE METER

Direct reading 0/40 KV 20K/Volt (UK C/P 65p) £18.40

DIGITAL CAPACITANCE

0.1 pF to 2000 mfd LCD 8 ranges DM6013 £57.95 (Carry case £2.95)

TRANSISTOR TESTER

Direct reading PNP-NPN, etc. TG1 (UK C/P 65p) £21.95

AUDIO ELECTRONICS Cubelite Limited
 301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564
 ALSO AT HENRY'S RADIO.
 404/406 EDGWARE ROAD, LONDON W2

MIDWICH COMPUTER COMPANY LIMITED

FAST EX-STOCK DELIVERY OF MICROCOMPUTER COMPONENTS AT UNBEATABLE PRICES

SPECIAL OFFERS	MEMORIES	2716 450ns	4116 200ns	6116 150ns
280ACPU 3.45	2114 Low Power 0.80	3 Rail 5.95	4118 150ns 3.38	6116 LP3 3.33
2732 45 2.99	2716 450ns 2.79	2732 350ns 4.40	4164 200ns T1 4.65	6116 LP3 5.75
2532 45 2.99	2708 450ns 2.10	2732 450ns 2.99	4164 200ns NEC 4.95	
4164 20(T1) 3.99	2716 450ns (+5V) 2.10	2564 450ns 8.99	4516/4816 100ns 2.25	
UPD7002 4.35	2716 350ns (+5V) 3.59	2764 450ns 9.99	5516 250ns 0.38	
DP8304 4.50		4116 150ns 0.85		

MIDWICH NOW APPOINTED OFFICIAL ACORN BBC MICRO DEALER

MEMORY UPGRADE FOR SPECTRUM

★ Increases Memory to 48K
 ★ Just Plugs in
 ★ Suitable for Later Blue Keyboard Machines only
 Ex-stock 20.95

Device	Price	Device	Price	Device	Price
ZN Ref 062 6 17V 1.80	4512 0.49	251 0.29			
ZN Ref 100 1 96V 2.56	4514 1.14	253 0.30			
	4515 1.14	257 0.34			
	4516 0.58	258 0.35			
	4518 0.39	259 0.57			
	4519 0.28	261 1.95			
	4520 0.49	266 0.19			
	4521 1.09	273 0.59			
	4522 1.24	279 0.59			
	4526 0.83	283 0.39			
	4527 0.64	290 0.57			
	4528 0.69	293 0.40			
	4532 0.69	365 0.29			
	4541 0.89	366 0.29			
	4543 0.79	367 0.39			
	4553 0.64	368 0.39			
	4555 0.50	373 0.54			
	4556 0.50	374 0.64			
	4585 0.78	377 0.69			
		378 0.45			
		379 0.65			
		386 0.34			
		390 0.49			
		393 0.41			
		629 1.21			

BBC Microcomputer Upgrades

*Memory Upgrade (BBC2) 18.00
 *Printer & User I/O kit (BBC2) 7.80
 *F Disc interface inc. D05 (BBC3) 70.00
 *Analogue input kit (BBC4) 6.70
 *Serial I/O & RGB kit (BBC5) 7.25
 *Expansion bus & tube kit (BBC6) 5.95
 *Printer cable inc Amphenol plug (not assembled) (BBC2) 13.00
 *User port connector & cable (BBC2) 2.00
 *Analogue input plug & cover (BBC4) 2.25
 *5 pin DIN plug for serial kit (BBC1) 1.00
 *6 pin DIN plug for RGB int (BBC109) 0.60
 *7 pin DIN plug for cassette (BBC141) 0.60
 *Connector for bus & cable (BBC6) 3.50
 *Single disc drive (100K) (BBC31) 230.43
 *Industry Standard EPROMS 350.00
 *Games Paddles (per pair) (BBC45) 11.30
 *Prices on these items are likely to change, please contact sales office before ordering. As some items are on extended delivery from Acorn please check availability before ordering items marked **

NEW EPROM PROGRAMMER FOR BBC MICROCOMPUTER

★ Programs 2516 2716 2532 2732
 Industry Standard EPROMS
 ★ No external power supply required
 ★ Plugs straight into expansion socket
 ★ Easy to use ★ Includes all Software required
 EPROM Programmer (Kit) 49.95
 EPROM PROGRAMMER (Assembled) 57.95

NEW JOYSTICKS AND CONTROLLER FOR ZX81 AND SPECTRUM

★ Controls 1 or 2 Joysticks
 ★ Fire Button Facility (1 or 2)
 ★ Easy to use
 ★ Plugs straight into Expansion Slot
 ★ Edge Connector provided for RAM Pack Discs etc

Joystick Controller (kit) 14.95 ea
 Joystick Controller (assem) 19.95 ea
 Joysticks 6.95 ea
 (All kits supplied with full assembly instructions)

Device	Price	Device	Price
280 FAMILY		8T26A	1.20
280CPU 2.95		8T28A	1.20
280ACPU 3.45		8T95	1.35
280CCT 2.64		8T97A	1.35
280ACTC 2.95		8T98	1.45
280ADART 5.70			
280ADMA 11.95			
280PU 6.75			
280API 2.95			
280ASIO 0 11.99			
280ASIO-1 11.99			
280ASIO-2 11.99			
280ASIO-3 11.99			
280ASIO-100 11.99			

CMOS 4000 'B' SERIES

4001 0.10
 4002 0.12
 4003 0.65
 4007 0.15
 4008 0.90
 4009 0.34
 4010 0.39
 4011 0.11
 4012 0.15
 4013 0.24
 4014 0.49
 4015 0.49
 4016 0.19
 4017 0.37
 4018 0.67
 4019 0.41
 4020 0.49
 4021 0.69
 4022 0.65
 4023 0.15
 4024 0.31
 4025 0.18
 4026 1.29
 4027 0.23
 4028 0.40
 4029 1.69
 4030 1.64
 4031 1.90
 4032 0.94
 4033 0.49
 4034 0.77
 4035 0.44
 4036 0.89
 4037 0.84
 4038 0.51
 4039 0.58
 4040 0.15
 4041 0.18
 4042

EP4000 EPROM EMULATOR PROGRAMMER



The microprocessor controlled EP4000 will emulate and program all the popular EPROMs including the 2704, 2708, 2716(3), 2508, 2758, 2516, 2716, 2532 and 2732 devices. Personality cards and hardware changes are not required as the machine configures itself for the different devices. Other devices such as bipolar PROMs and 2764 and 2564 EPROMs are programmed with external modules.

The editing and emulation facilities, video output and serial/parallel input/output provided as standard make the EP4000 very flexible to allow its use in three main modes:

- As a stand alone unit for editing and duplicating EPROMs.

Items pictured are: ● EP4000 Emulator Programmer - £545 + £12 delivery; ● BSC buffered simulator cable - £39; ● MESA 4 multi EPROM simulator cable - £98; ● 2732A Programming adaptor - £39; ● 2764 Programming adaptor - £64; ● 2564 Programming adaptor - £64; ●

- As a slave programmer used in conjunction with a software development system or microcomputer.
- As a real time EPROM emulator for program debugging and development (standard access time of the emulator is 300ns).

Data can be loaded into the 4k x 8 static RAM from a pre-programmed EPROM, the keypad, the serial or parallel ports and an audio cassette. Keypad editing allows for data entry, shift, move, delete, store, match and scroll, and a 1k x 8 RAM allows temporary block storage. A video output for memory map display, as well as the built-in 8 digit hex display allows full use of the editing facilities to be made.

BP4 (TEXAS) Bipolar PROM Programming module - £190

Also available (not shown): ● VM10 Video monitor - £99; ● UV141 EPROM Eraser with timer - £78; ● GP100A 80 column Printer - £225; ● PI100 interface for EP4000 to GP100A - £65.

VAT should be added to all prices

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

P8000 — THE PRODUCTION PROGRAMMER THAT HANDLES ALL NMOS EPROMS



**NEW
PRODUCT**

- Checks, Programs, Compares up to 8 devices simultaneously
- Handles all NMOS EPROMS up to projected 128K designs with no personality modules or characterisers — See list
- Easy to use, menu driven operation for blankcheck, program, verify, illegal bit check, checksum, self-test
- Constant display of device type, mode and fault codings
- Individual socket LED indicators for EPROM status
- Comprehensive EPROM integrity checks — Illegal bit check, data and address shorts, constant power line monitoring
- Full safeguard protection on all sockets
- Automatic machine self-test routine
- Powered down sockets
- Cost effective price — £695 + VAT
- Available from stock

2704
2708
2716(3)
2508
2758A
2758B
2516
2716
48016
2532
2732
2732A
68732-0
68732-1
68766
68764
2764
2564
MK2764

Write or phone for more details

DISTRIBUTORS REQUIRED



EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.


Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW — 015 FOR FURTHER DETAILS

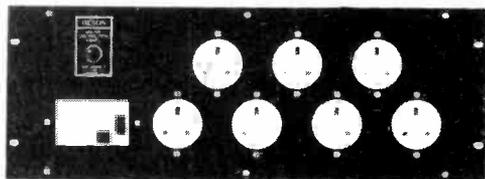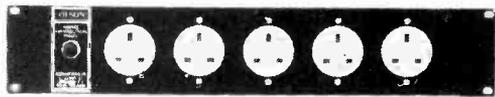

**V
E
R
T
I
C
A
L**

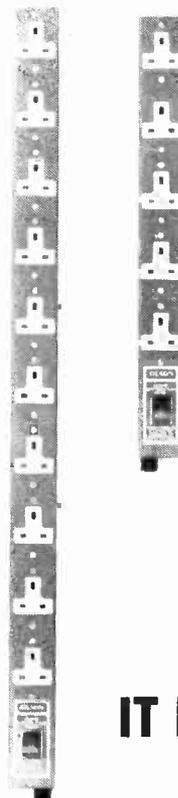

**WHEN
IT COMES
TO POWER
FOR RACKS
IT MUST BE OLSON**

HORIZONTAL OR


**VERTICAL RANGE FROM 3-10 SOCKETS
ALL EX-STOCK!
SPECIALS TO ORDER**

OLSON ELECTRONICS LIMITED


**5-7 LONG STREET LONDON E2 8HJ
TEL: 01-739 2343 TELEX 296797**

WW - 032 FOR FURTHER DETAILS

NEW receivers from Eddystone

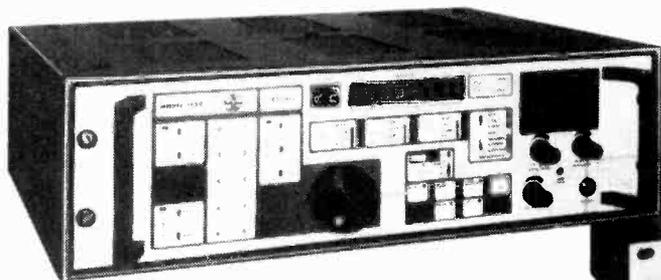

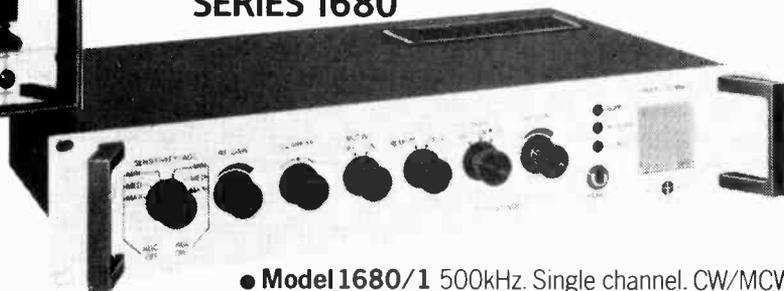**LOW-COST SINGLE AND
MULTI-CHANNEL RECEIVERS
SERIES 1680**



**HIGH STABILITY HF/MF
SYNTHESISED RECEIVER
MODEL 1650**

- 10kHz to 30MHz, tunable within 3Hz.
- Storage for 100 channels, interrogated/changed without interruption.
- Rack-mounted/table-mounted version available.

- **Model 1680/1** 500kHz. Single channel. CW/MCW.
- **Model 1680/2** 400kHz-535kHz. Seven channels. CW/MCW. Variable BFO and FSK.
- **Model 1680/3** (illustrated) 1.6MHz-30MHz. Single channel. AM/USB. Optional LSB/CW. Variable BFO and FSK.
- **Model 1680/4** 1.6MHz-30MHz. Dual channel. AM/USB. Optional LSB/CW. Variable BFO and FSK.
- Remote control facilities (all models).

PLEASE ASK FOR DETAILS

Eddystone Radio Limited

Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England
Telephone : 021-475 2231 Telex : 337081

A GEC-Marconi Electronics Company



WW - 056 FOR FURTHER DETAILS

ambit INTERNATIONAL

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST.

ALWAYS USE STOCK CODE WHEN ORDERING PLEASE.

4000 CMOS				7ALSXX				7AHCXX				LINEAR ICs			
Type	Stock No.	Price		Type	Stock No.	Price		Type	Stock No.	Price		Type	Stock No.	Price	
4000UR	22 04000	0.11		7ALS245	31 74245	1.00		7AHC00	30 07400	0.50		LM100	61 00010	3.00	
4001	22 04001	0.11		7ALS251	31 74251	0.30		7AHC02	30 07402	0.50		MF10	61 00011	5.00	
4002	22 04002	0.12		7ALS253	31 74253	0.30		7AHC04	30 07404	0.50		L140	61 00149	1.00	
4007	22 04007	0.13		7ALS257	31 74257	0.30		7AHC10	30 07410	0.50		UA823	61 00237	1.20	
4008	22 04008	0.50		7ALS258	31 74258	0.30		7AHC12	30 07412	0.50		U2478	61 00247	1.20	
4008B	22 04009	0.25		7ALS260	31 74260	0.20		7AHC13	30 07413	0.50		U2578	61 00257	1.20	
4011	22 04011	0.11		7ALS266	31 74266	0.20		7AHC16	30 07416	0.50		U2678	61 00267	1.20	
4011B	22 04011	0.11		7ALS273	31 74273	0.70		7AHC17	30 07417	0.50		LM301AH	61 03010	0.87	
4012	22 04012	0.14		7ALS275	31 74275	0.35		7AHC18	30 07418	0.50		LM301AN	61 03011	0.27	
4013	22 04013	0.25		7ALS283	31 74283	0.40		7AHC19	30 07419	0.50		LM308H	61 03080	0.70	
4015	22 04015	0.50		7ALS290	31 74290	0.40		7AHC20	30 07420	0.50		LM308CN	61 03081	0.85	
4016	22 04016	0.22		7ALS293	31 74293	0.40		7AHC22	30 07422	0.50		LM324	61 03240	0.45	
4017	22 04017	0.40		7ALS296	31 74296	0.54		7AHC24	30 07424	2.00		LM324B	61 03250	0.50	
4020	22 04020	0.55		7ALS300	31 74300	0.40		7AHC27	30 07427	1.00		LF347	61 00347	1.00	
4021	22 04021	0.55		7ALS303	31 74303	0.40		7AHC28	30 07428	0.80		LM348	61 03480	0.80	
4022	22 04022	0.55		7ALS308	31 74308	0.30		7AHC29	30 07429	0.80		LF351	61 03510	0.40	
4023	22 04023	0.15		7ALS313	31 74313	0.72		7AHC30	30 07430	0.80		LF353	61 03530	0.78	
4024	22 04024	0.33		7ALS317	31 74317	0.72		7AHC32	30 07432	1.30		LM380N	61 00380	1.00	
4025	22 04025	0.15		7ALS324	31 74324	0.30		7AHC33	30 07433	0.80		ZNA423	61 04230	1.00	
4027	22 04027	0.26		7ALS327	31 74327	0.80		7AHC34	30 07434	0.74		ZNA426B	61 04260	3.00	
4028	22 04028	0.50		7ALS337	31 74337	0.80		7AHC35	30 07435	0.80		ZNA4276H	61 04270	0.28	
4029	22 04029	0.55		7ALS338	31 74338	0.44		7AHC36	30 07436	0.44		ZNA4281H	61 04280	4.78	
4035	22 04035	0.87		7ALS339	31 74339	0.88		7AHC37	30 07437	0.74		ZNA4290	61 04290	2.10	
4040	22 04040	0.88		7ALS340	31 74340	0.88		7AHC38	30 07438	0.74		ZNA432C10	61 04320	28.00	
4042	22 04042	0.50		7ALS342	31 74342	0.88		7AHC39	30 07439	0.51		ZNA433C10	61 04330	22.50	
4043	22 04043	0.80		7ALS343	31 74343	0.40		7AHC40	30 07440	0.40		ZNA440	61 04400	0.80	
4044	22 04044	0.88		7ALS345	31 74345	0.44		7AHC41	30 07441	0.88		ZNA450E	61 04500	7.00	
4045	22 04045	0.22		7ALS348	31 74348	0.88		7AHC42	30 07442	1.33		NE542	61 05420	1.20	
4049B	22 04049	0.24		7ALS350	31 74350	2.48		7AHC43	30 07443	2.48		NE544	61 05440	1.80	
4050	22 04050	0.24		7ALS351	31 74351	1.15		7AHC44	30 07444	1.00		NE555N	61 05550	0.20	
4051	22 04051	0.55		7ALS352	31 74352	0.40		7AHC45	30 07445	0.50					
4052	22 04052	0.55		7ALS353	31 74353	0.30		7AHC46	30 07446	0.74					
4053	22 04053	0.55		7ALS354	31 74354	0.30		7AHC47	30 07447	0.74					
4056	22 04056	0.30		7ALS355	31 74355	0.30		7AHC48	30 07448	0.74					
4068	22 04068	0.18		7ALS356	31 74356	0.30		7AHC49	30 07449	0.74					
4069B	22 04069	0.14		7ALS357	31 74357	0.14		7AHC50	30 07450	0.74					
4070	22 04070	0.18		7ALS358	31 74358	0.18		7AHC51	30 07451	0.74					
4071	22 04071	0.18		7ALS359	31 74359	0.14		7AHC52	30 07452	0.74					
4072	22 04072	0.16		7ALS360	31 74360	0.14		7AHC53	30 07453	0.74					
4073	22 04073	0.18		7ALS361	31 74361	0.14		7AHC54	30 07454	0.74					
4075	22 04075	0.18		7ALS362	31 74362	0.14		7AHC55	30 07455	0.74					
4076	22 04076	0.55		7ALS363	31 74363	0.14		7AHC56	30 07456	0.74					
4077	22 04077	0.18		7ALS364	31 74364	0.14		7AHC57	30 07457	0.74					
4078	22 04078	0.18		7ALS365	31 74365	0.14		7AHC58	30 07458	0.74					
4081	22 04081	0.18		7ALS366	31 74366	0.14		7AHC59	30 07459	0.74					
4082	22 04082	0.18		7ALS367	31 74367	0.14		7AHC60	30 07460	0.74					
4083	22 04083	0.30		7ALS368	31 74368	0.14		7AHC61	30 07461	0.74					
4089	22 04089	0.80		7ALS369	31 74369	0.14		7AHC62	30 07462	0.74					
4175	22 04175	0.18		7ALS370	31 74370	0.14		7AHC63	30 07463	0.74					
4502	22 04502	0.80		7ALS371	31 74371	0.21		7AHC64	30 07464	0.74					
4503	22 04503	0.50		7ALS372	31 74372	0.21		7AHC65	30 07465	0.74					
4506	22 04506	0.70		7ALS373	31 74373	0.21		7AHC66	30 07466	0.74					
4507	22 04507	0.37		7ALS374	31 74374	0.21		7AHC67	30 07467	0.74					
4508	22 04508	0.70		7ALS375	31 74375	0.21		7AHC68	30 07468	0.74					
4510	22 04510	0.55		7ALS376	31 74376	0.21		7AHC69	30 07469	0.74					
4511	22 04511	0.45		7ALS377	31 74377	0.21		7AHC70	30 07470	0.74					
4512	22 04512	0.55		7ALS378	31 74378	0.21		7AHC71	30 07471	0.74					
4514	22 04514	1.25		7ALS379	31 74379	0.21		7AHC72	30 07472	0.74					
4515	22 04515	1.21		7ALS380	31 74380	0.21		7AHC73	30 07473	0.74					
4516	22 04516	0.80		7ALS381	31 74381	0.21		7AHC74	30 07474	0.74					
4518	22 04518	0.35		7ALS382	31 74382	0.21		7AHC75	30 07475	0.74					
4520	22 04520	0.80		7ALS383	31 74383	0.21		7AHC76	30 07476	0.74					
4521	22 04521	1.30		7ALS384	31 74384	0.21		7AHC77	30 07477	0.74					
4522	22 04522	0.80		7ALS385	31 74385	0.21		7AHC78	30 07478	0.74					
4526	22 04526	0.80		7ALS386	31 74386	0.21		7AHC79	30 07479	0.74					
4527	22 04527	0.80		7ALS387	31 74387	0.21		7AHC80	30 07480	0.74					
4528	22 04528	0.85		7ALS388	31 74388	0.21		7AHC81	30 07481	0.74					
4529	22 04529	0.70		7ALS389	31 74389	0.21		7AHC82	30 07482	0.74					
4531	22 04531	0.85		7ALS390	31 74390	0.21		7AHC83	30 07483	0.74					
4532	22 04532	0.80		7ALS391	31 74391	0.21		7AHC84	30 07484	0.74					
4534	22 04534	4.00		7ALS392	31 74392	0.21		7AHC85	30 07485	0.74					
4536	22 04536	2.50		7ALS393	31 74393	0.21		7AHC86	30 07486	0.74					
4538	22 04538	0.85		7ALS394	31 74394	0.21		7AHC87	30 07487	0.74					
4539	22 04539	0.80		7ALS395	31 74395	0.21		7AHC88	30 07488	0.74					
4543	22 04543	0.80		7ALS396	31 74396	0.21		7AHC89	30 07489	0.74					
4549	22 04549	3.50		7ALS397	31 74397	0.21		7AHC90	30 07490	0.74					
4553	22 04553	2.70		7ALS398	31 74398	0.21		7AHC91	30 07491	0.74					
4554	22 04554	1.20		7ALS399	31 74399	0.21		7AHC92	30 07492	0.74					
4555	2														

MARCONI SIGNAL GENERATORS

TF2002A/S (illustrated) 10kHz-72MHz. AM/FM. £750
 TF2002. As above but AM only. £450

MARCONI TF1066B/1. AM/FM Generator. 10-470MHz. 0.2uV-200mV output. FM Deviation up to ±100kHz. £550

MARCONI TF995A/5. AM/FM Generator. Narrow deviation model 995 covering 1.5-220MHz. £450

MARCONI TF1064B/5. AM/FM Signal generator covering in three ranges 68-108, 118-185 and 450-470MHz. FM fixed deviations of 3.5 & 10kHz. AM fixed 30%. £225

'DOLBY' NOISE WEIGHTING FILTERS

Cat. No. 98A. Noise weighting filters for CCIR/ARM signal-to-noise ratio measurements. As new units. £40 each (+£1 p&p).

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.

'VARIACS' - SPECIAL PURCHASE

We now have a stock of used but excellent condition, fully tested, variable (0-260V) transformers at the following ratings.

BERCO (enclosed) 2A.....	£12.50 + £1.50 pp
BERCO (non-enclosed) 8A.....	£25.00 + £2.50 pp
BERCO (non-enclosed) 10A.....	£28.00 + £2.50 pp
ZENITH (enclosed) 8A.....	£28.00 + £2.50 pp

Also available, small quantity of Heavy Duty and 3 Phase Variacs. P.O.A.

AUDIO WATTMETERS

Switchable 1W & 10W FSD. Internal 3.5 & 8 Ohm load impedances. Housed in grey enamelled case 6x6x3". Large easy to read 3" sq. meter. Scope output provision. £19 (+£1).

HEATHKIT Model AW-11J. Internal load switchable 3, 8, 15 & 600 Ohm. Meter scaled 0-50W (+dB scale). 5 Ranges, from 5mW-50W FSD. Mains powered. £25 (+£1).


MARCONI TF893A. 1mW-10W Full scale in 5 ranges. Impedances 2.5-20K Ohm in 48 steps. Direct calibration in Watts and dBm. £85 (+£2).

GPO JACK SOCKET STRIPS. 20-WAY Type 320 (3-pole) £2.50 ea. Type 520 (3-pole with switching contacts) £4 ea. Please include 35p each for postage on these. GPO type 316 jack plugs for above 20p ea. (10+ post free). Plus VAT please. Also recent stock of new, mint condition 720 Type, £6 each.

PHILIPS RF SIGNAL GENERATOR

As new condition Philips PM 5326. AM/FM RF Signal generator covering 0.1-125MHz. Integral 5 digit Frequency display. Mod AM & FM + Sweep facilities. 1 only available.

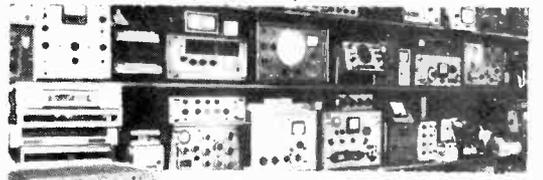P. F. RALFE ELECTRONICS
 10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753



OSCILLOSCOPES

TEKTRONIX 465. 100MHz at 5mV/div. Dual-beam, sweep-delay portable scope in first-class order. £1,250

TEKTRONIX 454. 150MHz. £750

TEKTRONIX 565. Twin time-base with two 2A63 Y-amplifiers (DC-300kHz. 1mV/div).

TRIO CS1577A. 35MHz Dual-beam £375. Brand new (LP) £475

DYNAMCO D7200. DC-15MHz dual-beam sweep-delay, mains or battery operated, portable. £250

TEKTRONIX 500 Series in stock with 'CA' Dual-beam plug-in units, e.g. 543B £125, 545A. £150

COSSOR CDU150. 35MHz dual-beam & sweep delay. £250

ADVANCE VM77D Millivoltmeters. 15Hz-4.5MHz. 1mV Full scale -300V AC £55

WOELKE ME104C. Wow & Flutter Meter £95

AVO Type 1 LCR Component Bridge.

WAYNE KERR AF Signal Generator Type S121 £75

AIRMEC Wave Analysers Models 853 and 248A.

CENTRONICS P1 Printer, one only. AND Type 663 Printer.

ROHDE & SCHWARZ SDR Signal Generator. 300MHz-1GHz.

HEWLETT PACKARD 608C Signal Generator. 10-480MHz AM.

MARCONI Component Bridge Model TF2700. (LC&R).

OKIDATA CORP Series 3300 Hard-Disc Drives.

TALLY Model 220 Line Printers.

BELL & HOWELL MICROFICHE VIEWERS

Type SR5. Screen size 9x5". Recent small quantity now avail. £55

DISC CARTRIDGES

BASF 12-Segment Single Hard Disc Cartridges. Brand new surplus stock.

MUIRHEAD FACSIMILE UNITS

MUFAX 'COURIER' facsimile receiver type K441-CN and transmitters K400 AMCH in stock in excellent condition.

SWEEPERS

TELEONIC Sweep generator system type 2003. Fitted with Marker, attenuator, Detector plug-in units and Generator covering 800-1500MHz. £325

PLEASE NOTE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months' guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES.

DC POWER SUPPLIES

- APT.10459/8. Stabilised Regulated supplies. New stock arrival hence LOWER PRICES. Available in preset output voltages between 6 and 30V DC (state requirements) ±4V approx. Three sizes available, 5A, 7½A & 10A. Prices £20, £25 & £30 respectively (plus postage £2, £2.50 and £4).
- Mullard Dual supplies. Pos/Neg 12V @ 1A & 0.4A. Dimensions 9x4x5". £10 ea. (+£1 p&p).
- Farnell Current limited. 13-17V DC @ 2A. £15. 27-32V DC @ 1A. £15 (+£1 p&p).
- Lambda LXS Series supplied 110V AC Input. 5V @ 14A. £20 (+£2.50 p&p). Various other voltages available from stock in small quantity.
- Contant 5/6V @ 5A. Small size (7x5x3"). £20 (+£1).
- Variable 0-30V @ 1A. Volt-metered. £30.
- Farnell 5V Switching. 60A. £85.

RF SIGNAL GENERATORS

ADVANCE Type E2. 100kHz-100MHz. Internal AM & Audio O/P. 1uV-100mV output. Price each £50 inc. VAT.

TAYLOR Type 68A/M. 100kHz-240MHz. Internal Modulation. £60 inc. VAT.

All of these units are in full working condition and carry our usual 90-Day Warranty. In both cases please add £2 each for carriage.

MILLI-VOLT MEASUREMENT, ANALOGUE

MARCONI TF2600. Twelve ranges 1mV-300V FSD. Wide-band to 10MHz.

MARCONI TF2603. Frequency range 50kHz-1.5GHz. High Sensitivity from 300uV.

MARCONI TF2604. Electronic Multi-meter. AC/DC 300mV Full scale to 300V (1kV DC). Resistance ranged. AC Frequency range 20Hz-1500MHz.

BRUEL & KJOER

Model 2006 Heterodyne Voltmeter. AM/FM/Voltage measurements to 240MHz.

CLAUDE LYONS 240V AC REGULATORS

Small quantity available of constant voltage mains regulators. Continuous current rating 5A. Model no. CVR-1200. Input 204-252V. Output adjustable 200-254V AC ± 0.3%. 45-65Hz. Condition as new. (Dims - 11"x7"x6"). Weight 20Kgs). Price £95 ea. + Carriage £5.

ROTRON INSTRUMENT COOLING FANS

- Supplied in excellent condition, fully tested.
- 115V, 4.5x4.5x1.5" £4.50, 230V £5. 115V. 3x3x1.5" £4 + postage ea. 35p.
- Also brand new 230V at £6 ea.

meet the **metrics**

A great variety of tools and sets to help you turn most any Metric fastener or adjusting screw you're likely to encounter... hex socket set screws and cap screws, hex nuts, hex head cap screws, and whatever.


All tools precision made for exact fit. Bright nickel chrome nutdriver shafts and protective black oxide finished hex socket screwdriver blades. Plastic (UL) handles shaped for perfect grip and balance.

FIXED HANDLE NUTDRIVERS



COMPACT SETS

No. 99-PS-41-MM (7 Metric hex socket blades, extension and handle)

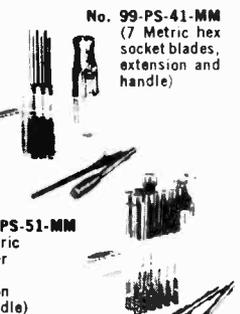

No. 99-PS-51-MM (10 Metric nutdriver shanks, extension and handle)



Replacement Blades and Shanks separately available for 99 Series Sets
 Full catalogue available on request

XCELITE

Cables Speciproduct London W1

Distributed by SPECIAL PRODUCTS DISTRIBUTORS LTD
 81 Piccadilly London W1V 0HL

Tel 01-629 9556

WW - 040 FOR FURTHER DETAILS

PICOTUTOR & ANALOGUE INTERFACE

ASSEMBLY LANGUAGE TRAINER

The ideal way to learn machine language and become acquainted with the new "single chip" control oriented microprocessors. 1.8K of EPROM, 20 I/O lines, 112 bytes of RAM and a timer all in a single 28-pin IC. As featured in this, and subsequent issues of WW.

COMPLETE KIT £39.87
 PCB, Programmed 68705 and all parts

ANALOGUE INTERFACE £9.39
 PCB and all components

PCB only £4.35
 Prog. 68705 £21.98
 Data £1.95

MAIL ORDER ONLY ALL PRICES INCLUDE VAT ADD 45p POSTAGE

PCB only £1.73
 16-way Jumper Lead £2.35

MAGENTA ELECTRONICS LIMITED (W15)
 135 Hunter Street, Burton-on-Trent, Staffs. DE14 2ST, 02-83-85435

WW - 059 FOR FURTHER DETAILS


RADFORD

Audio Measuring Instruments, Audio Amplifiers, Loudspeakers and Loudspeaker Components for the professional and enthusiast

RADFORD AUDIO LTD.
 10 BEACH ROAD
 WESTON-S-MARE, AVON BS23 2AU
 TEL. 0934 416033

WW - 026 FOR FURTHER DETAILS

An Approved Professional Source.

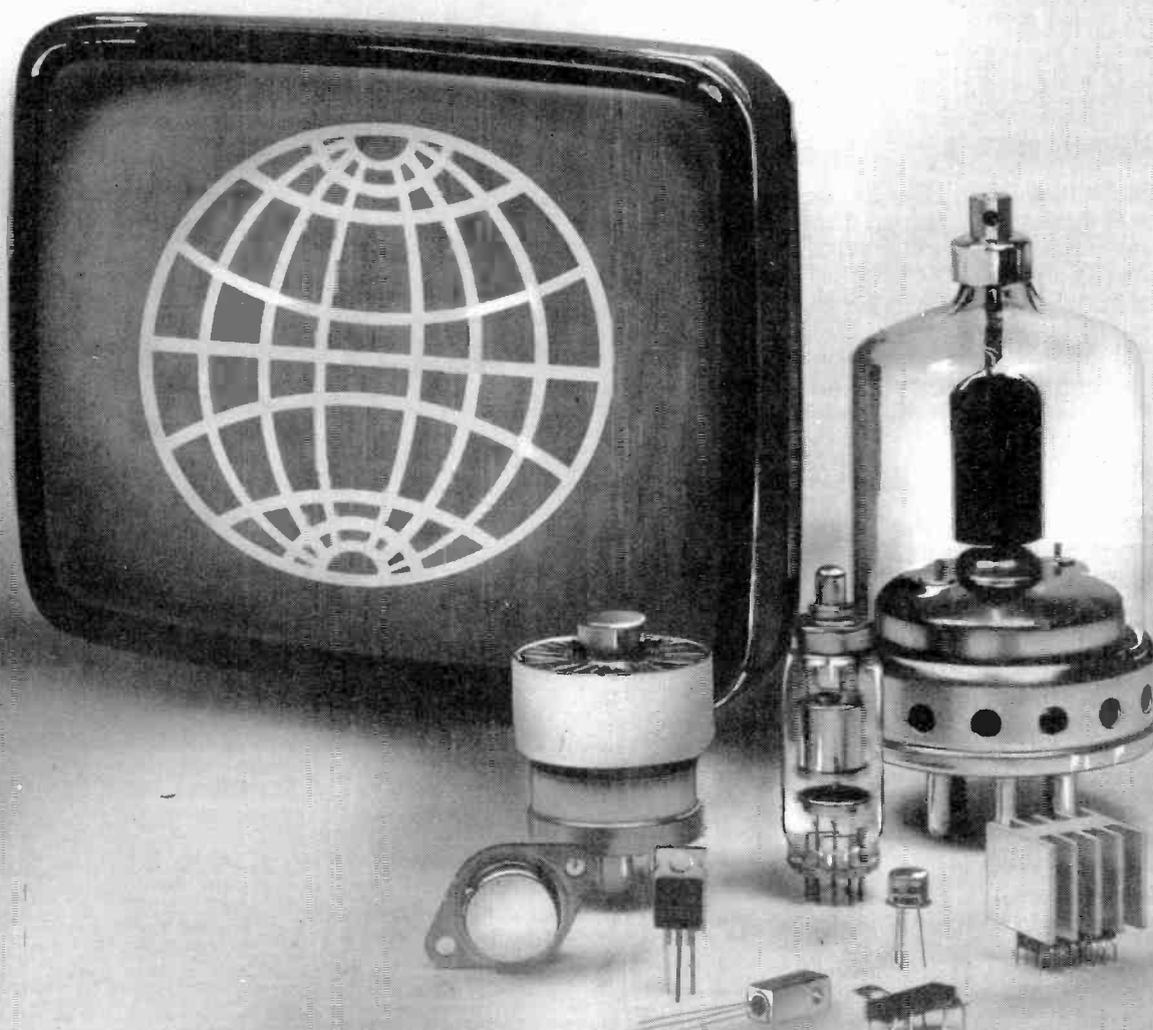

We supply Power Valves, CRT's, Microwave Tubes, Semiconductors and Indicators for use in Electronic Warfare, Radio and Satellite Communication, Radar and Industrial Heating Systems.

As an MOD Contractor with an in-house microfiche based sourcing service covering current and out of production NATO, CV and Commercial Part Numbered devices we could be Your Approved Professional Source.



Hall Electric Ltd., Electron House, Cray Avenue, St Mary Cray, Orpington, Kent BR5 3PH, England.
Telephone: Orpington (0689) 27099, Telex: 396141.

WW - 008 FOR FURTHER DETAILS

THE ALL-ELECTRONICS SHOW OTHER EXHIBITION


Three events. For free!

First, the Show of shows.

You may visit 450 All-Electronics/ECIF stands at the Barbican in air-conditioned, carpeted comfort free of charge – if you use the coupon on the right.

You may also have the 120-page 'Morgan-Grampian' guide to both the industry and the event absolutely free as well (if you kindly allow us 26p for postage and packing).

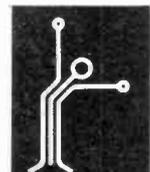Now the ticket will also gain you free entry to our two sister events:



'Circuit Technology' at the Kensington Exhibition Centre; and 'Fibre Optics' in the adjacent-to-the-Barbican Porter Tun Room.

There has never, ever, been such an opportunity to glean the facts and figures from Component and Instrument manufacturers and, as an innovation in '83, the PCB and Fibre Optics industries.



A refreshing scope of options that can be yours as fast as you can spell Heineken!

And for a fiver...?

In conjunction with 'Electronics Times' we proudly present 'The Business of High Technology.'

Four of the world's most honoured specialists revealing industry trends in an action-packed, three-hour session.

(Come in the morning, or the afternoon; our programme is duplicated.)

We're catering for no fewer than 2,500 people at each session; and, of course, you can see the exhibition as well – either before or after.

The setting is the most prestigious in Britain: The Barbican's Concert Hall, of which Her Majesty the Queen said: "It must have claim to be one of the modern wonders of the world."

Sit in luxury – and hear from Wilf Corrigan, Founder and President, LSI Logic: "Semi-Custom Circuits"; Pasquale Pistorio, Chief Executive Officer, SGS: "The European Semiconductor Industry"; John Alvey, Senior Technical Director, British Telecom: "Fifth Generation British Computers"; Derek Roberts, Director of Research, GEC: "Key Technology, the User's View." The overall title: The future of electronics and the business of high technology.

All for only a five pound note! (Order form alongside.)



Go and see...

Top: Fibre Optics (so far); Middle C.T.; Bottom A.E.S. It's a 50-yard walk from the Barbican's Hall to the Porter Tun Room. And we've there-and-back buses on the hour, every hour, betwixt Kensington and the Barbican for those interested in Circuit Technology and the A.E.S.

Amphenol; Amplicon; Belling & Lee; BICC General Cables; Cossor Electronics; Dynacast International; Ealing Beck; Eurotec Optical Fibres; Fibre Optiques Industries; GEC Optical Fibres; Hellerman Deutsch; Honeywell Control Systems; ITT Cannon; STC Components; Lambda Photonics; Laser Lines; London Universities; McMichael; MPC Electronics; Metiles Griot; Norban Electro Optics; Optical Fibres; Oriol Scientific; Pilkington PE; Pirelli General; Plessey Optoelectronics; Production Techniques; Rofin; Sira; Standard Telephones & Cables; Sulmer Electronics; Systems Production; TBL Fibres; Thomson-CSF Components & Material; Vickers Instruments; Walmore Electronics; York Technology;

Alpha Metals; Arnold Electronics; Argos Electronics; AEG Telefunken (UK); Anda Circuits; BPA (Technology & Management); G Bopp & Co; Boby Tempest & Associates; Bush Beach Engineering; Coates Special Products; Chemlec Solutions; Circuit Foto Products; Cirquip R&D; Cochran & Johnson; Ciba-Geigy Plastics & Additives Co; Computational Digital Data Electronics; DPC Electronics; Dek Printing Machines; Degussa; Dorrivier; Du Pont De Nemours International SA; Du Pont UK; Dymet Alloys; EGM Solders; Exacta Circuits; Electrochemicals; Engelhard Industries; Electrovert; Excellon; Finlay Microvision Co; Ferranti Computer Systems; Fischer Instrumentation (GB); Frys Metals; G&H Electrographics; GTS Flexible Materials; GSPK (Circuits); Gemini Electronic Developments; Hunter Equipment; Sales; Instagraphic Products; International Tin Research Inst; Imasa; ITT/Cannon Electric (GB); Kam Circuits; Lamco; Litton Precision Products Int. Inc.; Lesar-Ronal (UK); M&T Chemicals; MEPD; MacDermid GB; Multicore Solders; Manchester Circuits; McGregor Industries; Muirhead Vetric Components; Marconi; Norplex UK Div UOP; Nevin Electric (Holdings); New England Laminates; Oxy Metal Industries (Sel-Rex) Division; Packman Research; Prestwick Circuits; Photopolymer Systems; Photoprinting Products; Planer Products; Protokote; Robertsons Chemicals; Rexham UK; Seletrons; Shipley Chemicals; Systems Efficiency; Serflico UK; Scientific & Electronic Enterprises; S.B.E.E.L.; Sarat Process Photography; Thiokol Chemicals; Vero Advanced Products; Vision Engineering; Veratronic; VM Circuit Equipment; W. Canning Materials; Welwyn Printed Circuit Services;

AB Electronic Products Group; AEG Telefunken (UK); AMF Potter and Brumfield; AMI Microsystems; AVX; Able Systems; Adcola Products; Allen Bradley Electronics; Alma Components (ESV); Alusett UK; Ambar Components; Amplicon Electronics; Analog Devices; Anders Electrical; Anglia Components; Aerial Pressings; Aries Electronics (Europe); Armon Electronics; Arrow Hart (Europe); Ashburton Resistance Co.; Ashcroft Electronics; Assman Electronics; Astralux Dynamics; Augat; BFI Electronics; BICC General Cables; BICC Vero Electronics; Bach Simpson (UK); B and R Electrical Products; Bahco Record Tools; FWO Bauch; Belclere; Bell & Howell; Black Star; Boxer Marketing; Brandenburg; Briticent International; Britimpex; British Standards Institution; Broyce Marvid; AFBulgin & Co.; CGS Resistance Co.; CRP Electronics; Calex Electronics; Cambion Electronic Products;

Cambridge Electronic Ind.; Campbell Collins; Capital Electronic Developments; Celab; Centronic; Cherry Electrical Products; Ciba-Geigy Plastics Division; Citec; CP Clare Electronics; Coden Engineering; Collett Terminals; Compstock Electronics; Conductive Products; Contraves Industrial Products; Cooper Tools; Corintech; Corning (Electrosl Division); Coutant Electronics; Cox; Critchley Brothers; Custom Cases; DAT Engineering Co.; DAU (UK); Dage Eurosem; Danavox (Great Britain); Danbridge UK; Datacapture; Data International Incorporated; Datac; Daturr; S Davali & Sons; Dean Electronics; Diamond H Controls; Digitran UK; Drake Transformers; Dubilier Components; Duracell UK; Duralith Corporation; ERG Components; ETRI Fans; East Grinstead Elec.; Electronic Components Ind. Fed.; Electronics Weekly; Electronum; Electronic Components; Electroplan; Electrothermal Engineering; Enclosure Technology; English Electric Valve Co.; G English Electronics; Exacta Circuits; FR Electronics; Farnell Electronic Components; Farnell Instruments; Farnell International Instruments; Felco; Ferranti Electronics; Fieldtech; Heathrow; Hlar Electronic Systems; GE Electronics (London); General Instrument Microelectronics; Genrad; Gentech International; Gitech; Gould Power Supplies UK; Graphic Electronics; Greendale Electronics; Greenpar Connectors; Gresham Lion; Groatmoor; Hakuto International UK; Hamlin Electronics Europe; H and T Components; H B Electronics; Harris Systems; Harrow Scientific; Harting Elektronik; Harwin Engineers SA; Hawke Electronics; Hayden Laboratories; Healey Meters; Hesto (Henkels Stock); Highland Electronics; Hinchley Engineering Co.; Hitachi Denshi (UK); Hitachi Electronic Components (UK); Hivolt Capacitors; Holden and Fisher; Holsworthy Electronic (Sales); Honeywell Control Systems; House of Instruments; Howells Radio; Hunting Hivolt; Hybrid Systems; Hypertac; I and J Products; IC Master; ICC Information Group; IDD Crystal Electronics; ITT Cannon; STC Components Group; ITT Semiconductor; ITT Switches (UK); Imhof Bedco Stand Products; Industrial Science; Imo; Intelec; The Institution of Elec. Eng.; Intel Electronics Group; International Rectifier Co. (GB); Intersi Datal (UK); Intime Electronics; Irlandus Circuits; Iskra; Ivo Counters; Jackson Brothers; Kelvin Impex; Kemo; Klippon Electronics; Lambda Electronics; FC Lane Electronics; Lawtronics; Leonische Drahtwerke AC Nürnberg; Lee Green Precision Inds.; Lemo UK; Light Soldering Developments; Littex; Littelfuse (GB); Londe; Longs; Lyons Instruments; 3M United Kingdom; Microstesting; The McMurdo Instrument Co.; Marconi Instruments; Metway Electrical Industries; Micro Circuit Engineering; John Minster Instruments; Mitsubishi Electric (UK); Melex Electronics; Mostek (UK); Mounted Electronic Components Int.; Mullard; Murata Erie Electronics; NF Electronics; NSF; National Panasonic (UK); Neom (UK); Newport Components; Nietronix; OK Machine & Tool (UK); Optima Enclosures; Oxley Developments; PSP Electronics; Papst Motors; Parmeko; Pelco (Electronics); Pickering Electronics; Plessey Circuits; Plessey Connectors; Plessey Hybrids; Plessey Semiconductors; Portescap (UK); Powerline Electronics; Powertron; Preciconact; Precision Metal Depositors; Precision Circuits; Precision Components & Equipment; Precision Instruments; Preformations (Magnets); Pressac; Print Service BV; Protech BPL; Prototron 24; Pulsetek; Pye Unicam; Quadrant Meter Company; Quiller Components; RF Components; RS Components; Raca; Dana Instruments; Radatron; Radialtron Components; The Radio Resistor Company; Radio & Electronics World (AMB); Radiotron (UK); Ramford Metals; Raytheon Semi-Conductor; REMO Components Group; Redpoint; E.G. & G. Reticon; RIFA AB; Richo International; Rittal; Roadrunner Electronic Products; Rockwell; Salford Electronic Instruments; Sealectro; Settek Instruments; Schroff UK; Semelab; Semiconductor Specialists (UK); Semtech; Stemic; Siemens; Sifam; Siliconix; Souriau (UK); Spectrol Reliance; Sprague Electric (UK); Star Systems (RHB); Steatite Insulations; Stocko (Metal Works); Stotron; Sulfex; Superflex-I-core; Suvicon; Swissnico; Symec Electronics; Synchro Services; TRW Carr; Tam Systems; Technation; Techni Measure; Tekelec Components; Teknis; Teledyne

8-20, 1983. THE ALL-ELECTRONICS/ECIF SHOW. THE BARBICAN. APRIL 19-21, 1983. FIBRE OPTICS '83. THE PORTER TUN ROOM. APRIL 19-21, 1983. THE ALL-ELECTRONICS/ECIF SHOW. THE BARBICAN. APRIL 19-21, 1983. FIBRE OPTICS '83. THE PORTER TUN ROOM.

SHOW REFRESHES THE PARTS S CANNOT REACH.



Philbrick; Tele-Haase Stevergerate GmbH; Telonic Berkeley (UK); Tempatron; Tencco Distribution; Thandar Electronics; Thame Components; Thomson - CSF; Thorn Brimar; Today Electronics; Townsend Coates; Transradio; Trident Engineering; Ultra Electronic Components; United Electronics; VSI Electronics (UK); VTM (UK); Vako Electronics; Variohm Components; Varta; Vishay Resistor Products (UK); Vitramon; 'W' Electronics; WKR; Wallis Electronics; Welwyn Electric; Weir Electronics; Wescorp Europe; Wessex Advanced Switching Prods.; West Hyde Developments; Widney Dorlec; Willsher & Quick; Winslow International.

The stand numbers for all three events are given in the Morgan-Grampian catalogue. And so are details of all the conference programmes at all three events.

We're working like Trojans for the industry as a whole – and not just YOU.

This is no ordinary exhibition week.

All the key industry influences will be attending our seminars and conferences.

All the folks with vacancies (or with CV's!) will be parading the aisles.

All... well, in simple terms, 'The Show' is the recognised annual occasion when everyone gets together to swap news, views, trends and friends. Freely.

The Tobie Awards

The pre-eminence of 'The Show' is augmented by its 'TOBIE' awards – to be presented, this year, at the Electronics Shows' Ball at the Dorchester.

Last year's winners were:

NEW PRODUCT OF THE YEAR

Ferranti FAB-2

Ferranti Electronics Ltd.

RESEARCH ACHIEVEMENT OF THE YEAR

Laser Gyro Inertial Navigation System

EXPORTER OF THE YEAR

Sinclair Research Ltd.

ELECTRONIC APPLICATION OF THE YEAR

Songuard Burglar Alarm

Eurolec Group Ltd.

PERSONALITY OF THE YEAR

Robb Wilmot - ICL

DISTRIBUTOR OF THE YEAR

Memec Ltd.

And this year? Watch E.T.'s space!

And remember, only The All-Electronics/ECIF Show can do all this...

How to get to the Barbican/Kensington Exhibition Centre/Porter Tun Room.

The Barbican: Tube to Barbican Station. 400 yards straight ahead from the exit. And you're there.

Kensington: Tube to Kensington High Street. Walk through shopping arcade. Turn right, and right again. In 100 yards you've made it.

Porter Tun Room: Leave 'The Show'. Turn left into Beech Street. And it's 50 yards on the right past the cross roads.

Remember – on the hour, every hour, there are buses from Kensington to the Barbican. Full details on your ticket and in the catalogue; both free. How refreshing!

(No-one under 16 admitted. Admission without ticket £1.)

To: Pat Rusted, 34-36 High Street, Saffron Walden, Essex CB10 1EP. Tel: 0799 22612. Telex: 81653.

Please send me a free season ticket to The All-Electronics/ECIF Show, Circuit Technology, and Fibre Optics.

Please send me a free 'Morgan-Grampian' catalogue for all three shows, for which I enclose postage stamps for p & p (26p please).

Please send me details of the various seminars and conferences running during 'the week'.

Name: _____

Company: _____

Address: _____

40010 A

**FILL IN THIS TODAY
TO GET FREE TICKETS,
FREE TRAVEL...
FREE EVERYTHING.**

Please attach 26p in stamps lightly by their corner to this coupon.



34-36 High Street, Saffron Walden, Essex
CB10 1EP. Telephone: 0799 22612
Telex: 81653



SPECIFICALLY DESIGNED FOR THE

Z80

BASED SYSTEM
4, 6 OR 8 MHz

This **MACHINE CYCLE LOGIC STATE ANALYSER** gives a logic state map of 37 active pins of the CPU to a depth of 2048 (or 4096*) machine cycles leading up to a preset conditional break. Passive, timed by the target system clock, the analyser samples the address, data and control buses simultaneously with the CPU and stores them with an elapsed M cycle and clock count. Specific machine cycles may be excluded to increase the apparent memory depth. Up to FFF delay on start/end acquisition condition true.

*Available with 2K or 4K memory depth and 4, 6 or 8 MHz speeds.

FULL SPECIFICATION AND DETAILS

SEYKER

LIMITED

First Floor, 18A Bridge Street, Godalming, GU7 1HY. Telephone 048 68 20924


- A HIGH PERFORMANCE, LOW COST, POWERFUL 'IN CIRCUIT' TOOL TO DEBUG THE MOST RANDOM FAULT OR SIMPLY STUDY PROGRAM FLOW.
- OSCILLOSCOPE TRIGGER AT END, START OR DELAYED ON START. DELAY IN MACHINE OR CLOCK CYCLES.
- 19" RACK MOUNTABLE.
- SELECTABLE AUTOMATIC CHANGEOVER TO DMA ON BUSAK ACTIVE.
- BOTH START AND END ACQUISITION CONDITIONS SELECTABLE FROM STATE OF ADDRESS AND DATA BUS TO STATE OF SINGLE DATA BIT.
- END ACQUISITION ALSO INCLUDES A START TO END LOGICAL COMPARISON (AND, NAND, OR, NOR, XOR, NXOR) INDEPENDENTLY SELECTABLE ON EACH DATA BIT.
- 12" DISPLAY MONITOR.
- PRINTER OUTPUT FOR A HARD COPY COMPARE TO YOUR LISTING.
- ALL PRICES EXCLUDE VAT CARRIAGE AND PACKING £12.

MODEL 10280 A
2K MEMORY DEPTH
TO 4MHz CLOCK
£747
EX. VAT

WW - 021 FOR FURTHER DETAILS

Hitachi Oscilloscopes

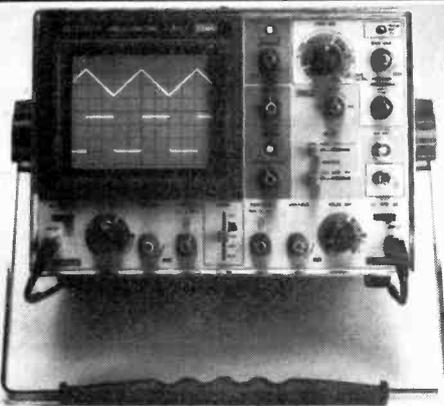performance, reliability, exceptional value and immediate delivery!



Hitachi Oscilloscopes provide the quality and performance that you'd expect from such a famous name, in a newly-extended range that represents the best value for money available anywhere.

V-152F 15MHz Dual Trace	V-353F 35MHz Sweep Delay
V-202F 20MHz Dual Trace (illustrated)	V-650F 60MHz Dual Timebase, Trigger View
V-203F 20MHz Sweep Delay	V-1050F 100MHz Quad Trace, Dual Timebase
V-302F 30MHz Dual Trace	V-209 20MHz Dual Trace, Mini-Portable
V-352F 35MHz Dual Trace	V-509 50MHz Dual Timebase, Mini-Portable
	V-134 10MHz Tube Storage Oscilloscope

Prices start from under £250 (ex. V.A.T.) including 2 high-quality probes and a 2-year warranty. We hold the range in stock for immediate delivery.

For colour brochure giving detailed specifications and prices ring (0480) 63570. Reltech Instruments, 46 High Street, Solihull, W. Midlands, B91 3TB

WW - 057 FOR FURTHER DETAILS

RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS

- Ideal for the experimenter
- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH
- 0-5 R
British design & manufacture
Tested and fully guaranteed. Ex-stock delivery.
As supplied to Fire Services/Civil Defence

FREE RECHARGE SERVICE AFTER PURCHASE

£6.95

Add. VAT, Post & Packing

COMPLETE WITH DATA

Official Orders welcome

Henry's

01-723 1008/9

CALLERS: 404 EDGWARE ROAD, LONDON W2 1ED
Mail Orders/Export Enquiries to: 11-12 Paddington Green, London W2



INSTANT PRINTED CIRCUITS!!

Make your own - to professional standards - within minutes using either "Fotolak" Light-sensitive Aerosol Lacquer or Pre-coated board. No Darkroom or Ultra-violet source needed!

Fotolak aerosol	£2.50 (30p)	Developer	£0.30 (15p)
Ferric Chloride	£0.60 (45p)	Acetate Sheet	£0.15 (15p)
Copper-clad Fibre-glass Boards:		Single-sided	£2 ft. sq. (45p)
		Double-sided	£2.25 ft. sq. (60p)

Pre-coated Fibre-glass Board:					
8"x4 1/2".....	£1.75 (25p)	16"x9".....	£7 (60p)	24"x18".....	£18 (£1.70)
8"x9".....	£3.50 (45p)	24"x12".....	£13 (£1.20)	Eurocard	£1.25 (25p)

Double-sided Board (all sizes) add 20%
Postage individual items in brackets. Maximum charge £2 per order

12V FLUORESCENT LIGHTING! FANTASTIC BARGAIN!

21" 13-watt Batten Type (complete with tube)	£6 (£1.20)
Kit Form:	£5 (£1.20). Inverter Transformers only: £1 (30p)


WHITE HOUSE ELECTRONICS PRAA SANDS, PENZANCE TR20 9TF
Telephone: Gernoe (073-676) 2329

RF LINEAR POWER AMPLIFIERS




TYPE 9045
VMOS WIDEBAND LINEAR POWER AMPLIFIERS
 4 watts and 20 watts max. RF output. Without tuning. Power gain 10 dB

TYPE 9045 10 KHz.-100 MHz. 4 watts£49.50+£2 p&p
 TYPE 9050 20 MHz.-200 MHz. 4 watts£49.50+£2 p&p
 TYPE 9066 10 KHz.-100 MHz. 20 watts£120.00+£4 p&p
 TYPE 9064 As above with integral mains power supply unit.....£180+£8 p&p
 TYPE 9067 20.MHz.-200 MHz. 20 watts.....£120+£4 p&p
 TYPE 9065 As above with integral mains power supply unit.....£180+£8 p&p

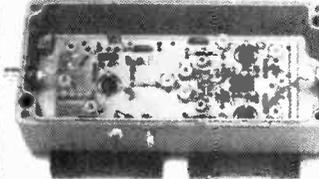

TYPE 9058
TELEVISION LINEAR POWER AMPLIFIERS
 Bands IV or V.
 Channel group 'A' 21-34, 'B' 39-51, or 'CD' 48-68

TYPE 9052 10 mW. input, 500 mW. output. Adjustable gain.....£120+£4 p&p
 TYPE 9058 50 mW. input, 2 watts output.....£120+£4 p&p
 TYPE 9059 500 mW. input, 5 watts output.....£150+£4 p&p

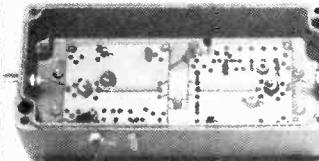

TYPE 9054
VMOS LINEAR POWER AMPLIFIERS
 Tuned to your specified frequency in the range 1-250 MHz.


TYPE 9054 200 mW. 2 watts input, 20 watts output. Gain adjustable 10-20 dB£120+£4 p&p
 TYPE 9060 As above with integral mains power supply unit.....£180+£8 p&p
 TYPE 9057 1 watt-8 watts input, 80 watts output. Gain adjustable 10-20 dB. With integral mains power supply unit.....£210+£8 p&p
 TYPE 9082 FM TRANSMITTER. 88-108 MHz. 50 watts RF output£180+£4 p&p
 TYPE 9083 As above with integral mains power supply unit.....£230+£8 p&p

LOW NOISE GASFET PREAMPLIFIERS




TYPE 9008 in 9010
TWO STAGE GASFET STRIPLINE PREAMPLIFIERS
 Television bands IV or V.
 Channel group 'A' 21-34, 'B' 39-51, or 'CD' 48-68

TYPE 9008 Two stage Gasfet preamplifier. N.F. 0.7 dB. Gain 25 dB£65+£1.50 p&p
 TYPE 9002 Two stage Gasfet preamplifier. N.F. 0.7 dB. Gain 10-35 dB. variable. High Q filter.....£85+£1.50 p&p
 TYPE 9009 UHF two stage Gasfet preamplifier. N.F. 0.6 dB. Gain 25 dB. Aligned to your specified frequency in the range 250-500 MHz.....£65+£1.50 p&p
 TYPE 9004 UHF TWO STAGE Gasfet preamplifier. N.F. 0.6 dB. Gain 10-35 dB. variable. Aligned to your specified frequency in the range 250-500 MHz. High Q filter.....£85+£1.50 p&p
 TYPE 9011 Gasfet preamplifier mains power supply unit.....£15+£1.50 p&p
 TYPE 9010 Masthead Weatherproof unit.....£4.50+£1.50 p&p

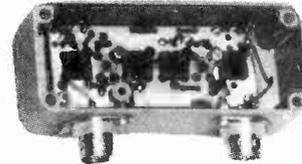

TYPE 9026
GASFET/MOSFET RF PREAMPLIFIERS
 Aligned to your specified frequency in the range 1-250 MHz.
 Masthead/local use

TYPE 9026 N.F. 1.0 dB. Gain 10-40 dB. variable.....£39.50+£1.50 p&p
 TYPE 9026 FM. As above. Band II 88-108 MHz.....£39.50+£1.50 p&p
 TYPE 9006 Gasfet. N.F. 0.6 dB. Gain 10-40 dB. variable.....£65.00+£1.50 p&p
 TYPE 9035 Mains power supply unit for above.....£19.50+£2.50 p&p

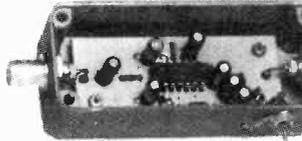

TYPE 9031
WIDEBAND RF PREAMPLIFIER
 1 KHz-100 MHz without tuning

TYPE 9031 N.F. 3.0 dB Gain 40 dB£39.50+£1.50 p&p
 TYPE 9056 1500 MHz PRESCALER. Divides 100-1500 Mhz by 10.....£59.50+£1.50 p&p
 TYPE 8033 PHASE LOCKED SIGNAL SOURCE using low frequency reference crystal. Specify output in the range 1-600 MHz. Output 10 mW. + 10 dBm£64.50+£1.50 p&p

RESEARCH COMMUNICATIONS LTD.

UNIT 3, DANE JOHN WORKS, GORDON ROAD, CANTERBURY, KENT CT1 3PP
 TELEPHONE: CANTERBURY (0227) 56489

PLEASE ADD 15% V.A.T.
 ON TOTAL

WW-050 FOR FURTHER DETAILS

CX80 COLOUR MATRIX PRINTER

New low price
£795 + V.A.T.

At last a low-cost Colour Matrix Printer for Text, Graphics, Histograms, Colour VDU Dumps, etc.

Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.



Compatible with most microprocessors, prints in 7 colours – sophisticated internal programme makes the CX80 easy to use.

Dot Addressable + 15 user programmable characters, 96 ASCII and 64 graphics characters in rom. Centronics interface with RS232 and IEEE488 options. Apple II interface gives dot for dot colour dump. New viewdata interface prints out two pages side by side in full colour. See Prestel 200650.

The CX80 is a product of our own design and development laboratories. It represents a British breakthrough in colour printer technology. Colour brochure on request. OEM pricing available.


INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley
 Burton-on-Trent, Staffs DE11 9PT
 Burton-on-Trent (0283) 215432. Telex: 377106

LEADER

instruments set the pace

TV & FM Test

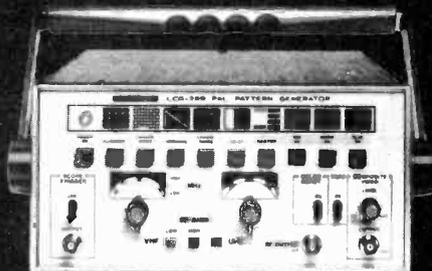

- Colour Bar Pattern Generators
- Sweep and Marker Generator
- CRT Tester
- Field Level Checker
- Signal Level Meter
- High Voltage Metered Probe
- Signal Generators

Audio Test




- Generators
- Attenuators
- System Analyser
- Audio Tester
- Distortion Meter
- Equaliser Amp
- Wow and Flutter Meter
- Frequency Response Recorders
- Millivoltmeters
- Log Amplifier
- Speaker Analyser

WW - 064 FOR FURTHER
DETAILS

When you select an instrument from the Leader range, you get more than just sound engineering. That's guaranteed - by rigorous quality assurance at manufacture, and a one year warranty. A broad range that covers most areas of test, measurement and calibration, with advanced features and high specification as standard. Prices that are lower than you'd expect are the bonus. Probes, covers, hoods and pouches are all available to enhance the application potential and ensure that Leader instruments set the pace for others to follow.

 **thandar**
ELECTRONICS LIMITED

Oscilloscopes

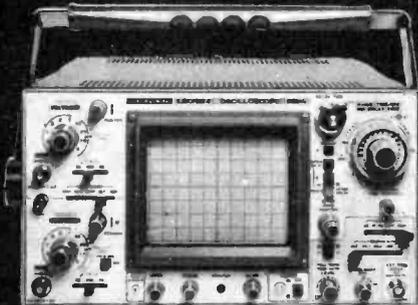

- 4 to 50MHz
- Single, Dual and Quad trace
- Delayed sweep
- Wide bandwidth
- High sensitivity
- High accuracy
- Battery operated

General Test

- LCR Bridge
- Semiconductor Curve Tracer
- Transistor Testers
- Logic Probe



Power Supplies

- Laboratory bench type
- 5 models
- 500mA to 5A
- Overload Protected

Thandar Electronics Ltd,
London Road, St. Ives,
Huntingdon,
Cambridgeshire
PE17 4HJ England.
Tel: (0480) 64646.
Telex: 32250.

TH02

Editor:

PHILIP DARRINGTON
01-661 3128

Deputy Editor:

GEOFFREY SHORTER, B.Sc.
01-661 8639

Technical Editor:

MARTIN ECCLES
01-661 8638

News Editor:

DAVID SCOBIE
01-661 8632

Drawing Office Manager:

ROGER GOODMAN
01-661 8690

Technical Illustrator:

BETTY PALMER

Advertisement Manager:

BOB NIBBS, A.C.I.I.
01-661 3130

BARBARA MILLER

01-661 8640

Northern Sales:

HARRY AIKEN
061-872 8861

Midland Sales:

BASIL MCGOWAN
021-356 4838

Classified Manager:

BRIAN DURRANT
01-661 3106

IAN FAUX

01-661 3033

Production:

BRIAN BANNISTER
(Make-up and copy)
01-661 8648

Publishing Director

DAVID MONTGOMERY
01-661 3241

Design for living

Military needs are a powerful stimulus to invention. Large companies fall over themselves to tender for the latest 'defence' requirement for a communications system or missile guidance, and many rely on military procurement for their existence. No expense is too high and the concept of deterrence, which implies that none of the equipment will ever be used for its designed purpose is, apparently, irrelevant.

Domestic equipment is the other major sink for materials and inventive talent. The pace of development in passive home entertainment shows no sign of slackening, even though the performance of, for example, audio systems is at the stage where it takes a collection of instruments to measure the difference between the original and the reproduction. Video recorders are a latter-day "opium of the people".

All this is not to say that the design effort expended on offensive or brain-paralysing electronics is wasted: very little ingenuity is ever a total loss, since engineering is engineering, in whatever walk of life it is applied, and 'spin-off' is always a benefit.

It seems to us that the truly gigantic body of knowledge in electronics should be applied in an immediately useful, peaceful and thrifty manner to enrich human life. Since most of us in the developed countries already enjoy an existence which is far above the tolerable, it makes sense to assist those whose lives are made more difficult than they need be through physical handicap.

With this in mind, our publishers announce this month a design competition, very open in its aims, to stimulate invention of aids to the handicapped. Anyone can enter — individuals or organizations — but perhaps the most rewarding form of entry would be by a small group, with the implied teamwork behind it. Such a

competition offers two challenges: firstly, to decide what is needed, to stick to the decision when the going becomes difficult and not to change horses; and secondly, to carry out the design work itself — perhaps the easier of the two.

The constraints to be applied, both in selection of goal and its realisation, are few, and are practical. For example, it serves no purpose to design a brilliant device to enable the deaf to hear if no-one can afford to buy it: similarly, a blind pedestrian will not thank the designer of his 'hazard detector' if it breaks down every time he goes out, leaving him exposed in the middle of the High Street race-track.

It must be feasible to manufacture the equipment, and it must be usable by the type of person for whom it is intended: aids have been produced in the past for which a commercial pilot's licence would have been a distinct advantage.

Maintenance — replacement of batteries, mechanical attention and the renewal of components such as tungsten bulbs should be kept to a minimum and, above all, the device must be safe: to be savaged by a deranged robot would not contribute greatly to one's peace of mind.

The rules stipulate that designs should be electronics-based, for the obvious reason that our readers are electronic engineers: this does not mean that designs for equipment which would be better without electronics will be welcomed — a sense of proportion is necessary. And solutions which are simply software written for existing hardware are not acceptable: this is an engineering competition, for which engineering design skills are needed.

Schools, university departments, company design teams and individuals are all eligible to enter: the prizes are worthwhile and the highest reward of all is that of having assisted someone to live a more active life.

Domestic alarm system

A low-cost unit which possesses a number of features designed to cause the maximum confusion and frustration for a house-breaker

Of the many low-cost domestic alarm systems on the market today, most combine their arm, disarm and other circuitry in a single box, sometimes including a built-in intruder sensor and a noisemaker. Although convenient to use and install, such devices can be self-defeating: if spotted by an intruder, they may be quickly disabled or destroyed. This relatively economical project is designed to be less vulnerable. A remote arm/disarm facility and remote sensors allow its main unit to be safely hidden and locked away. Once the system fires, clocked logic sequentially sets off three individually placed noisemakers to distract and confuse the intruder. These later shut down to save neighbours' nerves, but an outdoor lamp flashes for an additional 20 minutes to persuade them that a true break-in has occurred. The lamp also helps police localize the endangered premises. Finally, the system rests and awaits a new trigger. An external storage battery provides the relatively high current consumed by the noisemakers and the lamp, and

By Paul E. Bruin

supplies over-all circuit power in case mains power fails.

Main unit

Figure 1 shows the system's main circuit, controlled via input terminals DISARM and FIRE. The FIRE input goes low only when a normally closed alarm loop, routed through perimeter sensor switches to V^+ , is broken. If DISARM is made high, the output of IC_2 goes low, forcing the \bar{Q} output of master latch IC_{3b} and IC_{3c} high. This clears or resets all subsequent circuitry and prevents further circuit operation. The DISARM high level is 9 V. Should external tampering short-circuit DISARM to V^+ (13.8 V), Tr_8 , acting as a



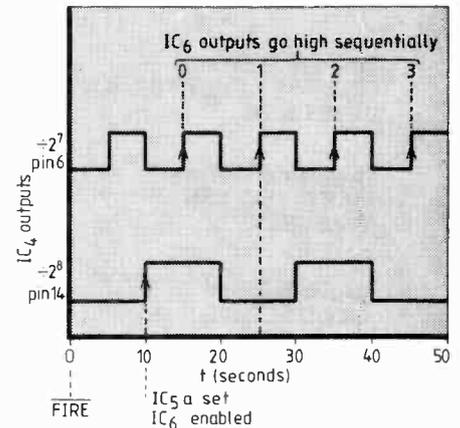


Fig. 2. Counter IC_4 timing diagram, showing 20s delay after FIRE input.

Fig. 3. Remote-control unit.

Fig. 1. Main control circuit diagram — inputs are DISARM and FIRE.

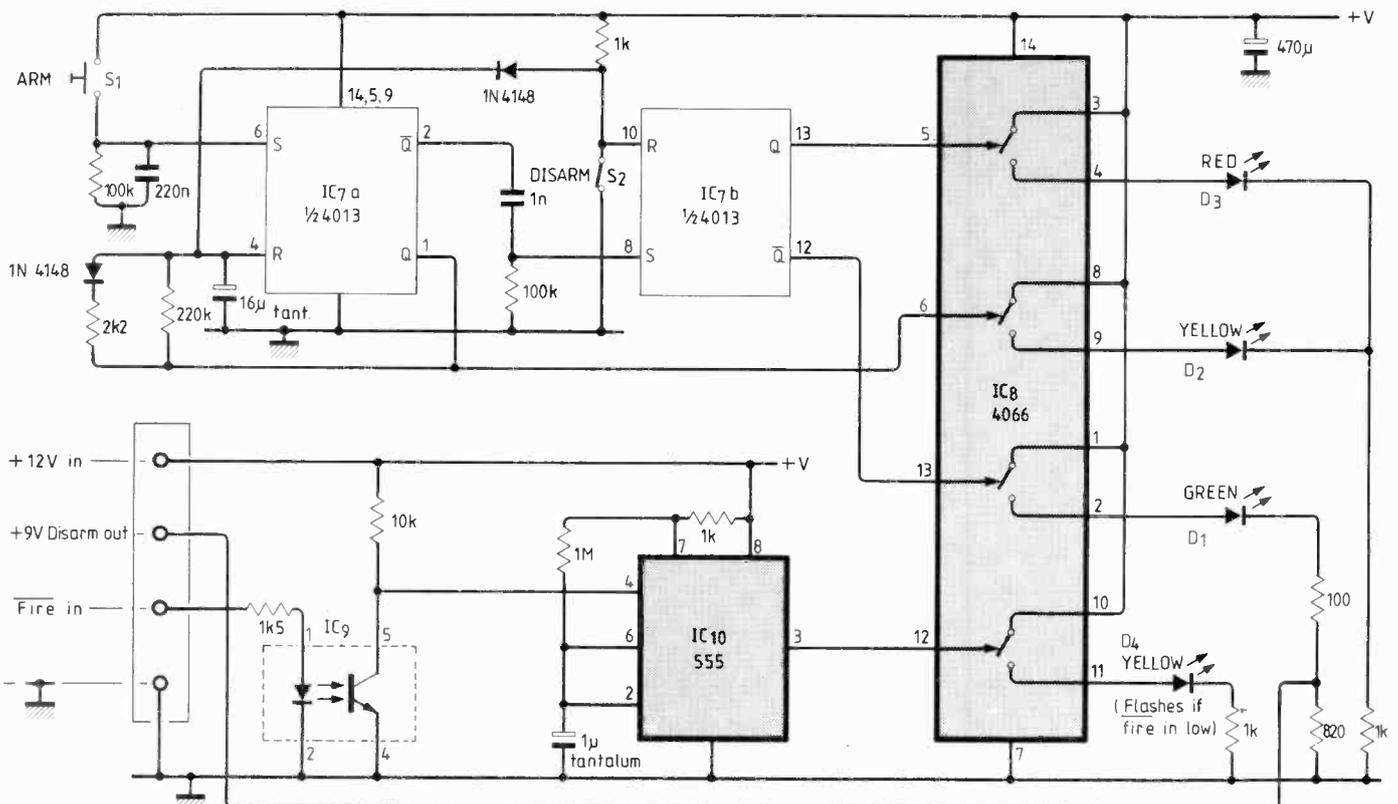

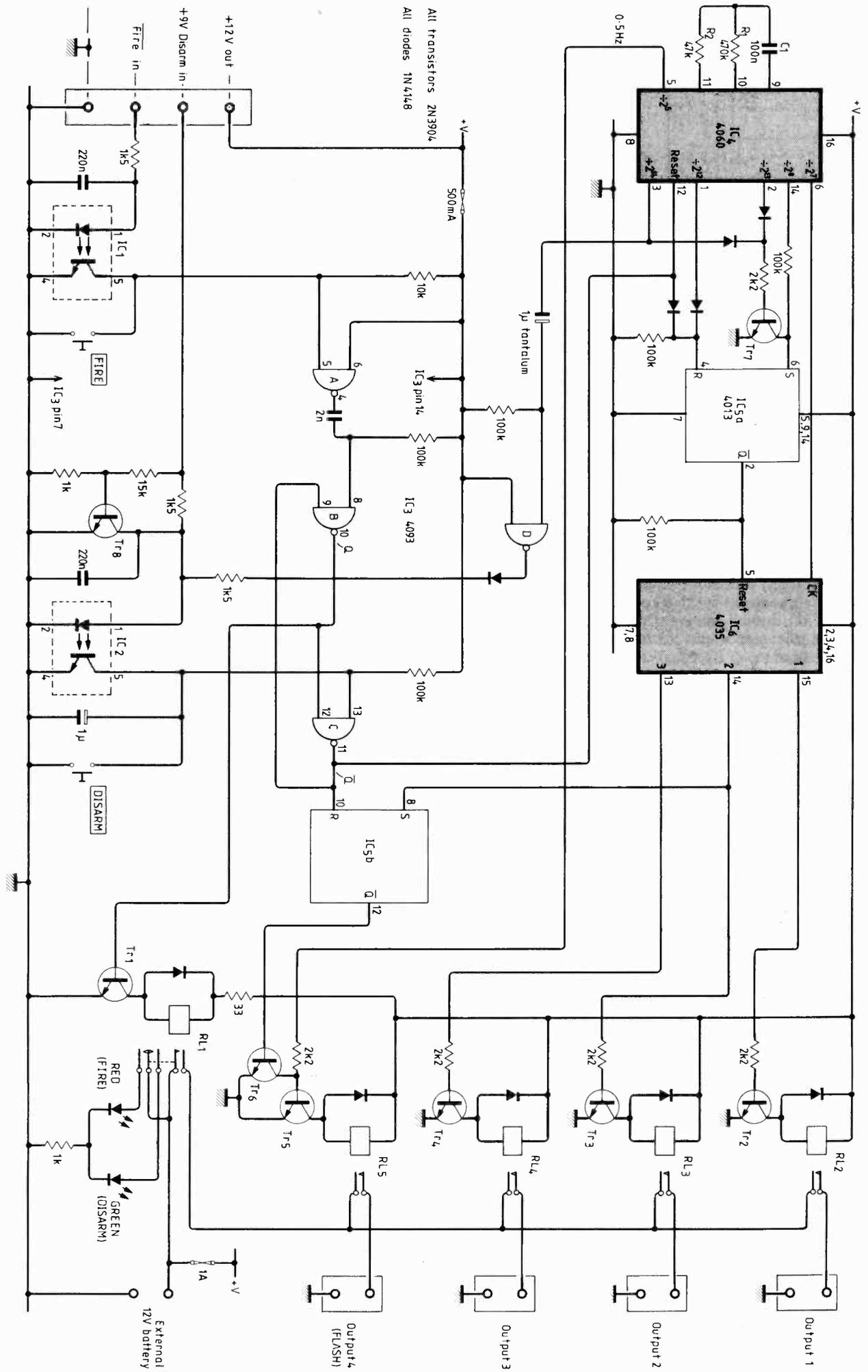

All transistors 2N3904
All diodes 1N4148

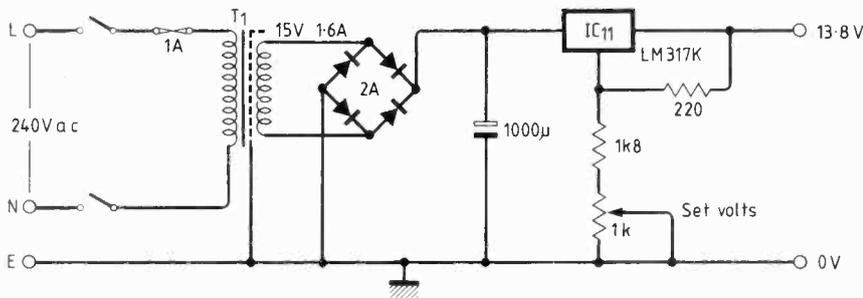


Fig. 4. Power supply, which also charges external battery.

level detector, inhibits false disarming by clamping the IC₁ input to ground.

If DISARM goes low, all remains passive until the alarm loop is broken. Then, IC₁ output goes high, producing a fast, negative-going voltage at pin 4 of Schmitt trigger IC_{3a} as it inverts the change. This edge triggers the master latch, bringing its Q output low and further enabling the system. Safety relay RL₁, is activated by driver transistor Tr₁, providing current for the other relay contacts while switching on a red led to indicate the FIRE condition. The system can be placed in the FIRE or DISARM states manually by depressing S₁ or S₂ respectively.

Ripple counter IC₄ is the system clock. It divides its internal oscillator frequency (set at 12Hz by R₁ and C₁) by 2ⁿ, where n can be one of several integer values depending on the output pin selected. Thus, the 2⁸ output pin of IC₄ completes a timing cycle $\tau = (2^8 \times 1/12)$ about 20 seconds after the clock is enabled by a FIRE input. For the first half of this period, the 2⁸ output stays low; it then sets latch IC_{5a} at its 10-second positive-going transition. This enables IC₆, a parallel-output shift register, which serially loads a 'one' every time a 10-second signal clocks it from the 2⁷ output of IC₄. In this way, the IC₆ outputs, which drive transistors Tr₂, Tr₃ and Tr₄ to close noisemaker relays RL₂, RL₃ and RL₄ go high

sequentially from 25 seconds after FIRE occurs, at 10-second intervals (as in Fig. 2). They stay high until the shift register is later cleared. As IC₆ pin 14 clocks high, latch IC_{5b} is set, removing drive from Tr₆. This allows Tr₅ to be turned on and off with a 0.5Hz signal, derived from the clock, and can flash an exterior warning lamp through relay RL₅. Approximately three minutes after the FIRE input goes low, IC₄ pin 1 goes high, shutting off the noisemakers. Transistor Tr₇ prevents IC₅ from re-starting them during repetitive clock progressions before final system reset. Some 20 minutes later, IC_{3d} triggers on the falling edge of the clock's slowest output count, resetting the master latch and IC_{5b}. The external lamp stops flashing, and the system's timing cycle is complete.

Control unit

The heart of the remote control unit in Fig. 3 is latch IC_{7b}, whose Q output determines the state of the DISARM line routed to the main control unit. When the latch's Q output is high, analogue switch IC_{8a} is closed, illuminating green led D₁ to indicate the system is disarmed. The 100Ω and 820Ω resistors form a voltage divider which sources the 9 V DISARM signal when the green led is on.

Pushing S₃ brings monostable IC_{7a} Q output high, lighting yellow led D₂ - an intermediate condition. About 20 seconds later, the monostable times out, positive-edge setting the latch and lighting red led D₃. Now the system is armed, for with IC_{7b} Q low, the DISARM signal is also low and the main control unit is free to respond to a break in its perimeter d.c. alarm loop. Optoisolator IC₉ monitors that loop. If there is a break, its output goes high, enabling IC₁₀ to flash led D₄. This warns the user against activated sensors (e.g., forgotten open doors, windows, etc.) before he sets the alarm. To disarm the system, S₄ must be briefly opened. This is a normally closed reed switch, hidden either inside the control unit itself or elsewhere, and is activated by brushing a magnet nearby.

Power supply

The power supply combines a full-wave rectifier bridge, a smoothing capacitor and an LM317K adjustable regulator to provide a d.c. source from its a.c. line-power transformer. The power supply output voltage, which is also used to

Mr Bruin was born in Amsterdam, Holland, was raised in Lebanon and attended British and American schools there. After graduating from the American University of Beirut with a B.Sc. in 1976, he found work with CBS News as a television sound recordist covering the Lebanese civil war. The job later took him to Africa for 18 months, travelling around the continent with a cameraman and correspondent. By 1978, photographic film had given way to fully electronic video news coverage, and he was moved to Europe to give technical support to news operations and set up a video maintenance facility in London. As a field engineer, Mr Bruin now travels abroad to install and operate television systems at remote news events, and supervise electronic maintenance.

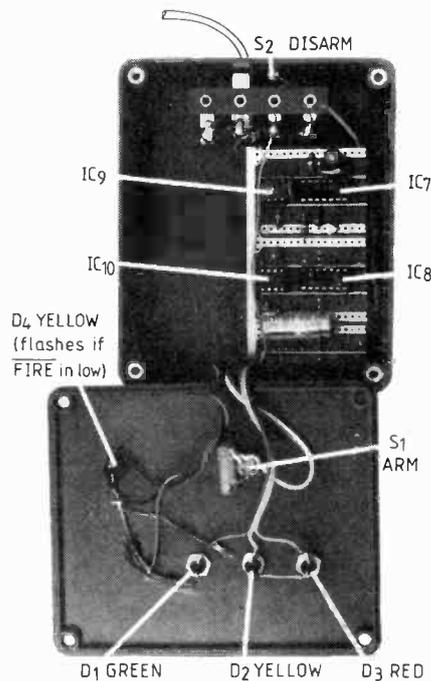


Fig. 6. Remote unit in its metal box.

charge the external battery, is set by the 1k potentiometer.

Construction

The prototype's main circuit board (that is, Fig. 1) was built on 10 × 15 cm Veroboard in a metal case. The power supply regulator, IC₁₁, should be mounted separately on a heat sink that will dissipate 15 W comfortably.

Normal c.m.o.s. handling precautions should be observed, and i.c. sockets should be used so that the integrated circuits can be inserted after soldering is complete.

Wiring is not critical, but the lead to C₂ should be kept as short as possible, and the wires carrying high current via the relays to the noisemaker and lamp outputs should be as thick and short as practical to reduce IR losses.

On the rear of the main unit, insulated binding posts or 'speaker type' spring-action terminals can be used to connect the output loads and the external battery. A four-terminal barrier strip allows

continued on page 35

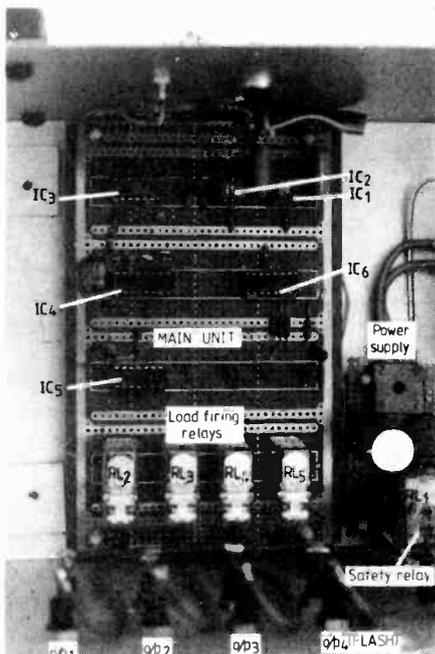


Fig. 5. Main unit construction, on Veroboard. IC₁ and IC₂ are opto-isolators.

High-impedance electronics

A discussion of voltage-follower circuitry for measurements from high-impedance sources. A subsequent article will describe the precise generation and measurement of currents in the nanoampère range

A common experimental procedure in neurophysiology and biophysics is the recording of voltage signals from single nerve or muscle cells¹. The most accurate measurements are usually made via a fine-tipped hollow glass tube (micropipette) filled with concentrated salt solution and inserted into the interior of the cell (Fig. 1). To minimize damage to the cell's membrane, the diameter of the micropipette at its tip is only 0.05 – 0.5 μm and the resistance of the tapered column of salt solution is therefore high, typically 5 – 50 $\text{M}\Omega$ or more. The biological signals of interest are 0.1 – 100 mV in amplitude, occupying a bandwidth extending from zero to perhaps 5 or 10 kHz.

The principal tasks of the electronics are to offer an input resistance at least two orders of magnitude greater than the equivalent source resistance, and to generate a bias current sufficiently small not to disturb the impaled cell or produce a significant offset potential. Some nerve cells may be excited by currents less than 1 nA and so the bias current needs to be below 10 pA. Other aspects of performance that may be important in certain applications include bandwidth, noise, drift, gain accuracy and dynamic range. Voltage gain *per se* is not usually a consideration since it can be provided without difficulty once the signal is made available at low impedance.

These design constraints were formerly met, not very conveniently, by the use of electrometer valves such as the Mullard ME1400 (actually a "domestic" pentode with top grid-cap, selected for small grid current) connected in pairs as differential cathode followers, and run with reduced anode voltage and heater current. When fets were introduced, attempts were made to use them because of their small size and easily met power-supply needs. However, the rather large temperature coefficient of V_{GS} (about 2 mV/°C) posed problems, subsequently solved by the appearance of monolithic dual fets. In the circuit of Fig. 2 both fets operate at the same drain current (I_{DSS} of Tr_2). Since the fets are

matched and at the same temperature, $V_{GS1} = V_{GS2} = 0$. The output buffer prevents loading and disturbance of the match of drain currents.

by R. D. Purves, Ph.D.

In recent years, fet operational amplifiers with extremely good specifications have become widely available. The RCA CA3130 and its internally compensated version the CA3160 are priced at less than £1 and offer an input resistance of more than 1 T Ω with a typical bias current of 5 pA at room temperature. The CA3140 has only slightly worse specifications and allows operation from ± 15 V supplies, whereas the CA3160 is restricted by its c.m.o.s. output stage to a total supply of 16 V and gets very hot indeed if inadvertently connected to ± 15 V. The LF356 is another low-cost device with good noise performance. More expensive devices include the Teledyne-Philbrick 1425 and 1439, and the Burr-Brown 3523, the last-named giving – at a price – spectacularly low noise.

Bootstrapping

Bootstrapping (Fig. 3) provides a simple means of increasing apparent impedances (or equivalently of reducing apparent admittances). The principle is that when a signal voltage is applied simultaneously to the two ends of a resistor or capacitor, no signal current flows. In Fig. 3(b), if the gain of the feedback amplifier is A , the apparent value of the admittance element is $Y(1 - A)$. Since for a voltage follower $A \approx 1.0$, the unwanted admittance can be reduced to virtual non-existence.

The input admittance of an operational voltage follower, whatever its internal construction may be, is chiefly an admittance to the power supply terminals, because the other relevant terminals (output and

inverting input) already have the unity-gain signal impressed on them. Bootstrapping the supply lines is readily accomplished by circuits like that of Fig 4. Readers unacquainted with the concept may feel uneasy about bootstrapping an entire

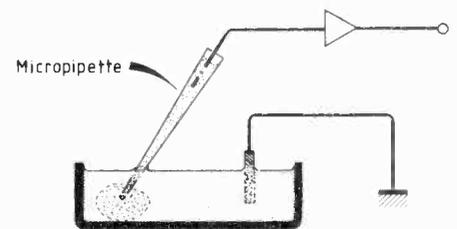


Fig. 1. Intracellular recording of potentials from a nerve or muscle cell. The tip of the micropipette is inserted through the cell's membrane. A reference potential is established by an earthed electrode contacting the extracellular electrolyte.

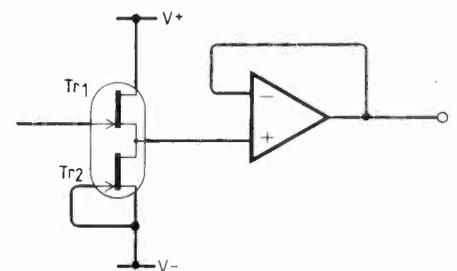


Fig. 2. Voltage follower using matched junction fets as input stage.

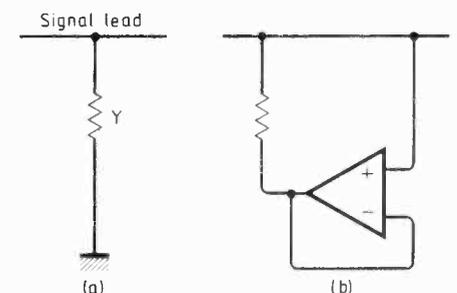


Fig. 3. The bootstrap. (a) An unwanted admittance Y shunts the signal lead. (b) The earthy end of Y is driven by the signal at unity gain. Y is still physically present, but no signal current flows through it.

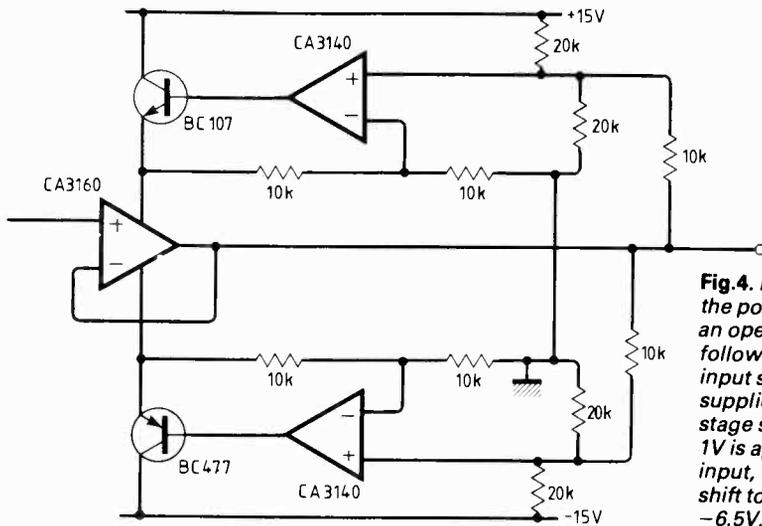


Fig. 4. Bootstrapping the power supplies to an operational voltage follower. With no input signal, the supplies to the input stage sit at $\pm 7.5\text{V}$. If 1V is applied to the input, the supplies shift to $+8.5\text{V}$ and -6.5V .

amplifier (surely one only bootstraps passive components?), but the circuit does work as advertised. Indeed, some operational amplifiers have *internal* bootstrapping of the input stage. If the signal gain from input to supply leads in Fig. 4 is adjusted to be very close to unity, improvements of several orders of magnitude in the input impedance can be obtained. Even ordinary bipolar amplifiers such as the 741 can be given an effective input resistance of many G Ω .

The bootstrapped configuration, unfortunately, does not lead to similar improvements in the bias current. The 741 with its 80 nA bias remains grossly unsuitable for signal sources of high resistance. Some fet devices have bias currents in the sub-picoamp range (Analog Devices AD41, AD42 and AD515, and Teledyne-Philbrick 1035), but for the ultimate in low bias current, parametric (varactor bridge) amplifiers can be used. The Teledyne-Philbrick 1702 and Analog Devices AD322 feature bias currents of 2 fA and 10 fA respectively. Parametric operational amplifiers have extremely limited bandwidths, but signals from ultra-high-resistance sources rarely have rise times of less than a few tens or hundreds of milliseconds.

The physical design of the input circuit needs careful treatment if source resistances in excess of 100 M Ω are contemplated. To mount one of these high quality amplifiers on an ordinary printed circuit board is to destroy its performance utterly. The pin connexions of the T05 and 8-pin d.i.l. packages are not ideal, since V^- is adjacent to the non-inverting input. A fingerprint or other contaminant at this position can easily increase the leakage current to the nanoamp range. The more exotic amplifiers are sometimes packaged in a physically large form giving better isolation to the input. The most reliable insulator for high-impedance work is air; the input lead should pass directly to the amplifier's input terminal, any intervening mechanical connexions being made on p.t.f.e. stand-off insulators. After construction, the input stage should be degreased with fluorocarbon solvent and rinsed several times in deionised distilled water before careful drying.

Response speed

The principal enemy of response speed is the total shunt capacitance at the input which, together with the source resistance, forms a low-pass filter. The input capacitance of the amplifier by itself is typically 4 pF; when combined with a source resistance of 50 M Ω this contribution alone gives a rise time of $2.2RC=440\mu\text{s}$, considerably too slow for some neurophysiological applications. Fortunately the bootstrap technique of Fig. 4 reduces the amplifier's input capacitance to an effective low frequency value of a fraction of a picofarad².

The stray capacitance of the connecting lead depends on physical layout and is minimized by construction of the input circuitry as a small probe placed as close to the source as possible. Alternatively, the input lead can be screened and the core-to-screen capacitance bootstrapped from the voltage follower's output. This approach tends to degrade noise performance since the necessarily large capacitance from core to screen couples noise at the output back into the input.

The remaining capacitance is that of the signal source itself. The neutralizing or "negative capacitance" arrangement of Fig. 5 is commonly used to overcome this last limitation on response speed. A textbook account of this circuit would describe it as a negative immittance converter, in which the shunt value of C_f as seen from the input is $C_f(1-A)$, where A is the signal gain at point Y. If $A > 1$, the effective value of C_f is negative. More concretely, we can analyse the circuit by recognising that whenever the input signal (and hence the potential at point X) is changing, some current is shunted to earth via C. In the absence of the feedback circuit this current must be drawn from the input and causes an ohmic potential drop across R. Under these conditions the potential at X cannot be a faithful replica of the input. The purpose of the feedback components is to supply most of the "error" current through C_f , so that it does not have to be drawn from the input.

Ideally A would be adjusted to the value $(1+C/C_f)$ so that the negative effective value of C_f exactly cancels the positive value of C. In practice, perfect neutralization is prevented by phase shift in the

amplifiers. The rise time with optimum neutralization is roughly the geometric mean of the amplifier's rise time and the original (unneutralized) input circuit's rise time (see appendix). The feedback amplifier should be compensated for fastest response at the gain used, not for stability at unity gain. A 357 operational amplifier is shown in Fig. 5; this is a version of the 356 internally compensated for a gain of 5.

There is an advantage both for low noise and short rise time if the total capacitance seen by the input lead is made as small as possible. In an ingenious design by Thomas³ the feedback capacitor is not present at all, negative capacitance being applied via the amplifier's own input capacitance. The supply lines to the follower are driven by the signal, as in Fig. 4, but with a gain adjustable from 1 to 3.2. Thomas illustrates step responses with rise times less than 10 μs from a 10 M Ω source.

Appendix

Rise time of capacitance neutralized input stage

In Fig. 5 the high-frequency behaviour of the voltage follower may be represented by a single pole with time constant τ (typically 0.04-0.15 μs); its transfer function E_{out}/E_x is therefore $1/(1+s\tau)$. For simplicity the feedback amplifier will be assumed infinitely fast. Kirchoff's current law applied to the input (point x) gives:

$$C \frac{dE_x}{dt} = \frac{E_{\text{in}} - E_x}{R} + C_f \frac{d(AE_{\text{out}} - E_x)}{dt}$$

In the Laplace transform domain the output signal following an input step of magnitude E is found, after some rearrangement, to be

$$\bar{E}_{\text{out}} = \frac{E}{s\{s^2\tau R(C+C_f) + s(RC + \tau + RC_f[1-A]) + 1\}}$$

where s is the transform variable and \bar{E}_x has been eliminated by the relation \bar{E}_x

continued on page 66

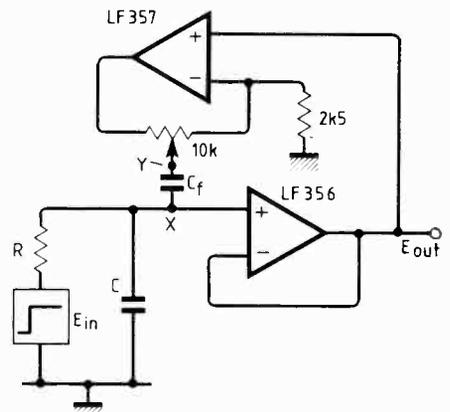


Fig. 5. Capacitance-neutralized voltage follower. R and C are the series resistance and shunt capacitance of the signal source. Signal gain at point Y is adjustable from 1 to 5. The follower stage, here shown as a 356 operational amplifier, is often constructed with bootstrapped supplies as in Fig. 4.

Assembly language programming

The main hurdle to overcome with assembly language programming is getting started, and the object of this series is to guide beginners to the subject through the fundamentals to a stage where you are able to continue with the processor of your own choice.

Many people are becoming acquainted today with programming microcomputers, usually in a high-level language such as Basic. High-level languages provide an easy means of programming and take all the hard work out of data processing and "number crunching" tasks. However, not all programming of microprocessors is done at a high level.

In many applications, programming at a low level, or assembly language, is preferred for several reasons. High-level languages have the disadvantages that they use a great deal of memory for program storage compared with programming in the processor's native code, are slow in operation and are usually not well suited to control applications.

For high-volume production applications, the higher initial costs of program development in assembler will be more than offset by the lower memory costs per unit. For smaller applications there is a simple rule-of-thumb guide for the best approach; if the task is mainly maths or data processing, use a high-level language; if it is mainly process control, use assembler.

Architecture

When programming a computer in a high-level language, the architecture of the particular central processing unit, or microprocessor, in use is not a matter of great interest to the programmer, but when programming in Assembler it is essential to fully understand the workings of the processor in use.

Figure 1 shows the programming models of the various microprocessors which will be referred to in this series. These models consist of a list of the registers in the central processing element available. The various registers have different and specialized functions, but generally speaking, registers are stores of bits of information which the c.p.u. can use or manipulate.

Data can be passed in both directions between the registers and memory or peripheral devices along the data bus in groups of eight bits (the processors discussed are eight-bit devices). In the registers the data can be manipulated by arithmetic and logic functions, the functions performed de-

pending on the instructions given to the c.p.u. by the program.

Five registers

Accumulator. Let's have a look first at the five registers available on the 6805. The first is the accumulator, an eight-bit register with the individual bits numbered 0 to 7. This is designed to hold the data for manipulation. All the processors have at least one accumulator.

Operations that can be performed on the data in the accumulator include adding a binary number to the contents of the accumulator, the result replacing the first number in the accumulator; subtracting a

binary instruction code it contains on the data bus, to be read by the c.p.u. and acted on. The program counter is then automatically incremented to point at the next instruction, which is fetched from the memory when the current instruction has been completed.

The 11bit program counter means that there are 2^{11} possible binary combinations it can provide, so that it can address 2048 different memory locations. In fact, there are 1796 locations in the program memory (eprom) of the 68705 used in the Picotutor; the rest contain ram and i/o ports and a few are unused. The other processors have a 16bit program counter.

Stack pointer. This is also an 11bit register, but bits 5 to 10 are permanently fixed at a certain binary value and only bits 0 to 4 can be altered. Only one instruction allows the user to alter this register, and that sets bits 0 to 4 to a logical 1. The stack pointer then just happens to contain an 11bit address which corresponds to the address of the last location of ram in the 6805.

But what is the stack pointer for? Though the c.p.u. fetches instructions in numerical sequence from the program memory, life isn't always that simple. Sometimes it is necessary to jump to somewhere else in memory to execute a collection of instructions there. It is common to have a particular sequence of instructions which may occur several times in a program, and rather than repeat them, it saves memory space if it is inserted once, and when required, the numerical sequence of instructions is broken and control jumps to this separate section, or subroutine, and returns back to the main program when finished.

This is exactly the same as the GOSUB function in Basic. When a program encounters a 'jump to subroutine' instruction it has to provide some means of recording where it has to return to after executing it. A device called stack, an area of ram is used for this and the 'jump to subroutine' instruction causes the address of the next instruction in the sequence (obtained by advancing the program counter) to be placed in that ram.

The stack pointer indicates the next free space available on the stack. The return


by R. F. Coates

number from it; shifting the bits by one, either left or right. Shifting is useful when multiplying. Only the 6809 has a specific instruction for multiplying two numbers together, and so with the others it's down to basics if you wish to multiply, by shifting and adding. How this is done is described later in the series.


Index register. The index register (X) is generally used as an index or pointer to data. For instance, there is an instruction to enable the accumulator to be loaded with data from a specified location in memory. It is also possible to do this without specifying the address of the memory, but specifying that the address is contained in the index register, or 'pointed' to it by the index, having been previously loaded with the address.

Program counter. The program counter is also used as a pointer, not to data, but to the program in memory.


Microprocessors operate by fetching and executing instructions stored in memory as sequential binary codes. The program counter itself contains an 11bit binary number which gives the address of the next instruction to be executed. The c.p.u. places this 11bit binary number onto the address bus, which selects the memory location containing the next instruction. The memory then places the eight-bit bi-

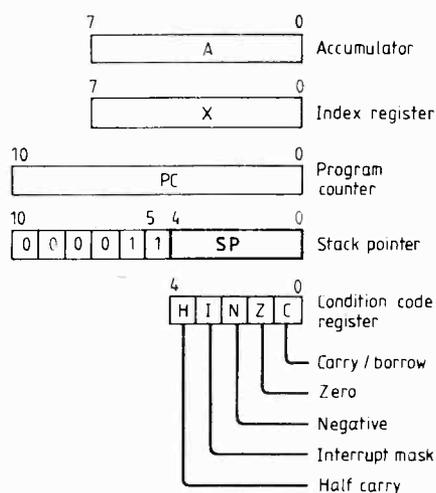


(a)

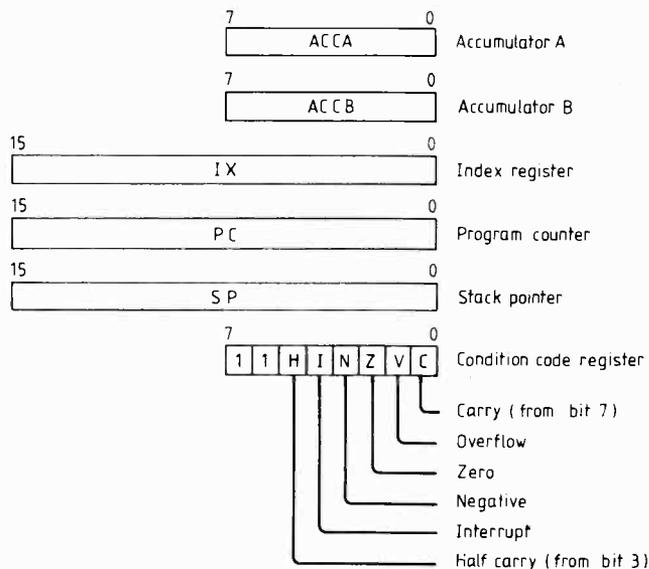

(b)

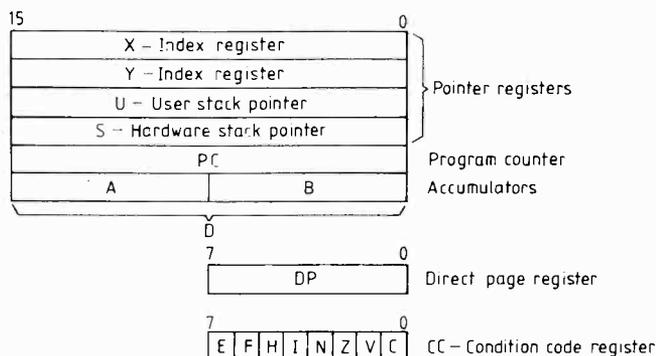

(c)

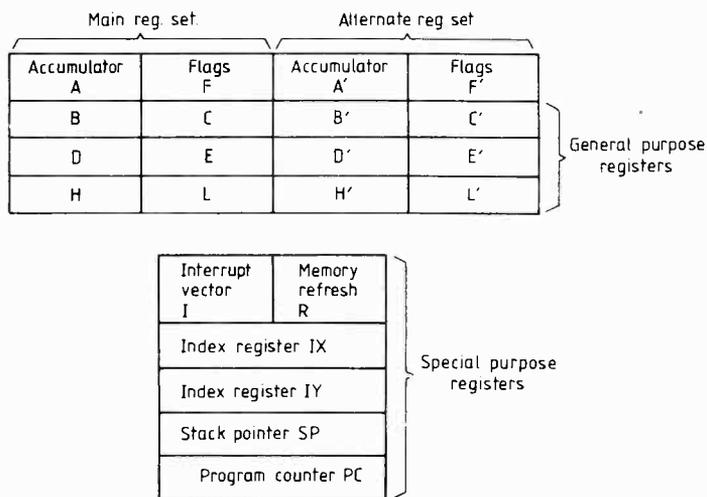

(d)

Fig. 1. Programming models for four microprocessors, (a) for the 6805, (b) for the 6809, (c) for the 6809 and (d) for the Z80. Blocks represent registers with different functions used for storing data directly manipulated by the processor.

Picotutor calibration

Resistor R_1 on the analogue interface board should be reduced to 8.2k if calibration cannot be achieved. Some of the first kits from Magenta have a 12k Ω resistor in this position so a replacement will almost certainly be needed. Display type numbers omitted from the main Picotutor parts list are either NSA1588A (8-digit, 0.14in) or NSA1198 (9-digit, 0.1in); both are National Semiconductor devices.

address is pushed onto the stack, and the pointer automatically moves down one.

Each ram location though is only eight bits wide and the program counter contains 11bits, so two ram locations are required. Bits 0 to 7 are pushed to the stack first, and SP decremented. The remaining three bits, 8 to 10, are now pushed on leaving five bits in that ram location unused. SP is decremented again, and now points to the next free stack location, in case our subroutine happens to call another subroutine itself. This is nesting.

At the end of the subroutine, a 'return from subroutine' instruction is executed which causes the return address to be pulled from the stack, incrementing the SP as it does so. The return-address is now forced into the program counter, and execution continues from that point.

With all the other processors, the stack pointer is a 16bit register and can be pointed anywhere in memory for greater flexibility. Also, other registers may be pushed onto the stack to temporarily save them.

Condition code register. The condition code register (flag register on the Z80) is a collection of individual bits or flags which are used to indicate certain conditions that prevail following execution of the last instruction. There are five flags in the 6805 condition code register. The H and I flags are discussed later.

The N bit indicates if the result of the last operation was negative, the Z bit if the result was zero, and the C bit if a carry was generated, say from adding two eight-bit numbers which save a nine-bit result. These flags can then be used by instructions following the one that set them to

make decisions as to how to proceed. Their use will be clearer when we come to the programming examples.

Other registers. Finally a word on some of the other registers available on the other processors. The 6809 has two index registers X and Y and a second stack pointer, U, can also function as another index register if required. A "direct page" register on the 6809 will be explained when we come to addressing modes.

Besides the registers already mentioned the Z80 has a number of general-purpose registers not available on the Motorola processors. These can be used for manipulating data within the c.p.u. Transferring data from memory to c.p.u. takes a considerable amount of time and having a number of general-purpose registers within the c.p.u. can speed up the operation, particularly in 'number-crunching' applications. However, there are situations in real-time applications where multiple c.p.u. registers can actually slow things down. This has led to processors such as the Texas 9900 which implements all required registers in ram rather than in the processor. Consequently there are argu-

ments for and against multiple general-purpose registers and Motorola chose a compromise of essential registers on the c.p.u. and the ability to implement registers in ram, which offers greater flexibility and is not possible with the Z80.

Probably the most important factor for the beginner is the fact that the fewer the registers the easier it is to learn to program, and this was a major factor in using the 6805 as our basis.

The numbering system almost universally used in microprocessor programming is hexadecimal notation, and in counting to the base 16, the characters A to F represent the decimal values from 10 to 15 in hexadecimal.

A group of four binary digits gives a possible 2^4 or 16 combinations, and these could be represented by one of the 16 hexadecimal characters shown in the following table

Binary value	Hex character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	B
1100	C
1101	D
1110	E
1111	F

If we take a binary number and divide it up into groups of four digits each group can be assigned its hexadecimal equivalent, which reduces the number of characters required by four. The 16bit value
1011010000001111
becomes B40F, which is much easier to write and remember.

To avoid confusion when working with hex numbers a suffix or prefix is normally added to a hex number to distinguish it from decimal. Motorola use the prefix '\$' whilst Zilog use the suffix 'H' for this purpose. In these articles the '\$' prefix will denote a hex number where necessary.

So much for the boring fundamentals of assembly language programming; next we shall be looking at some of the instructions of the 6805 and trying out some simple programs and the equivalents for the other processors.



To be continued

continued from page 30

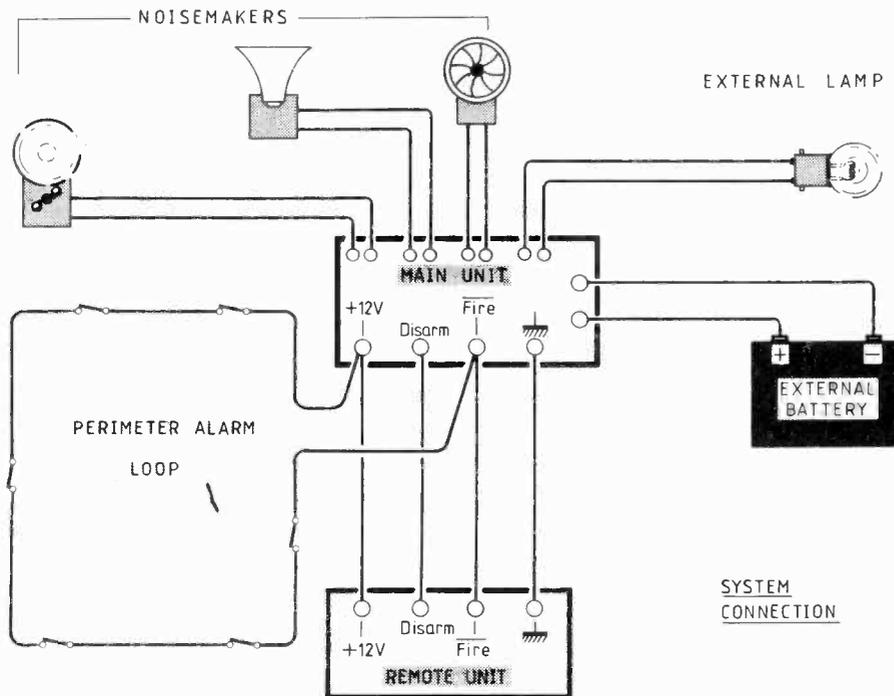


Fig. 7. Connexion of units to form complete system.

connection of the DISARM, FIRE, +12V and ground lines to the remote control unit.

The remote circuit can also be wired on veroboard. Leads to C_x should be kept short. The board can be fitted inside a small plastic box. Holes drilled in the back (or a strip of Velcro stuck to it) will allow wall mounting.

Peripherals

All perimeter alarm loop switches must be of the 'normally closed' variety (these open when triggered). They can be anything from simple magnetic reed or pressure mat

switches to the output contacts of a motion detector or light beam device. All switches must be wired in series.

Any 12 volt d.c. bells, horns or sirens with a current drain of less than 2A can be used with this project, and a wide selection are readily available. An accessory red, 12V rear light for a caravan or trailer makes a good external lamp for the alarm, and can be bolted to an outside pipe, railing or wall. Wires running to these loads should be at least 16A. w.g., or 1mm in copper core diameter, and each run *must* be fused at the control unit end with a 2A fuse. Automotive in-line fuse holders are convenient and cheap for this purpose.

For the external battery, an ordinary lead/acid car or motorcycle type is recommended. It should be placed in a reasonably ventilated location, to prevent small amounts of gas released during charging from collecting to become a possible explosion hazard.



Autorangeing frequency meter

This meter measures frequencies in four ranges up to 10MHz (9,999kHz) with automatic switching between the ranges. It displays the four most significant digits.

The meter consists of four principal parts: input, timing, scaling and counter/display sections. Each is described separately but it must be noted that they are not necessarily separate modules, for example IC₁₀ and IC₁₁ are shared between the timing and scaling sections.

Counting and display

The main counter, Fig. 1, is built around a 74C926 i.c. which has four binary-coded decimal counters with multiplexed outputs to common-cathode led seven-segment displays. The counter module receives the

by F. P. Caracausi

signal to be counted through MCP. A positive signal (see note) on the MCP line, labelled 'store', will latch the counter value into the internal output latches and this value is displayed permanently as the display select input to the 74C926 is held low. The counter is cleared by a positive pulse on the MCL line and the 'carry out'

signal is used to indicate an overflow, occurring whenever the count advances from 9999 to 0000. This negative-going transition is switched back to positive between 5999 and 6000. The underflow signal at MUF is a 1kHz (multiplexer frequency) pulse train which occurs as long as the most significant digit is zero; when the m.s.d. is not zero, there is no output.

Scaling

The signal to be measured is fed to three cascaded decimal dividers, IC_{6,7,8} (Figure


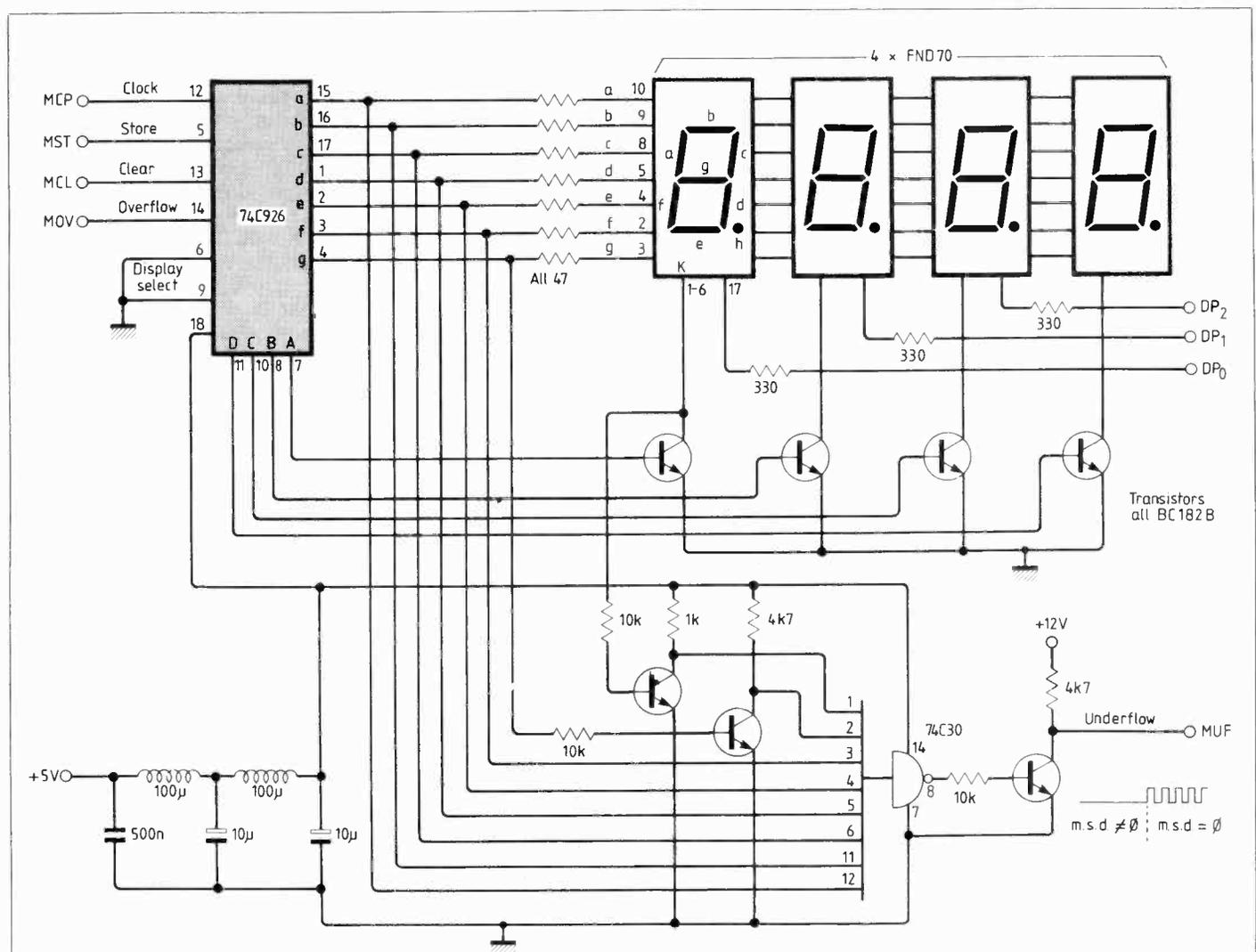


Fig. 1. The counter and display module built around a 74C926 i.c.

Fig 2. The scaling circuit automatically selects the range to be displayed.

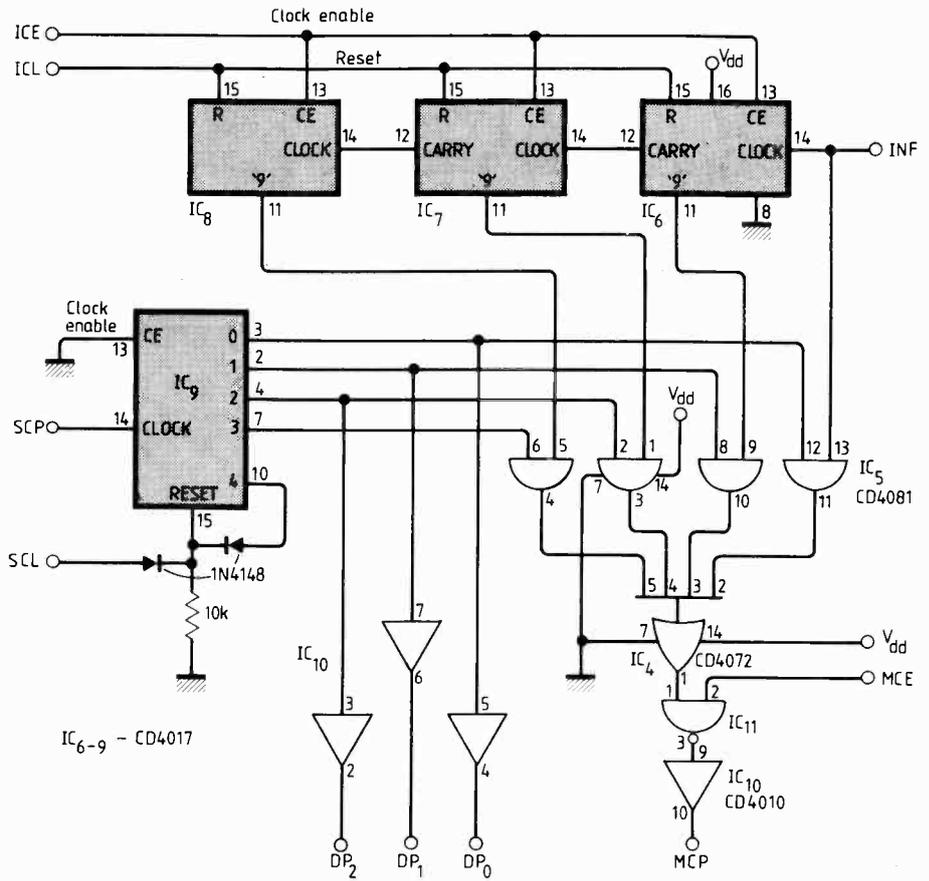

Dr Francesco Paolo Caracausi studied physics at Palermo University. He has published several articles in electronics magazines. He works at the Cassa Centrale di Risparmio as a senior programmer for systems and data processing.



2). Depending on the value of the scale counter IC₉, the input frequency is divided by 1, 10, 100 or 1000. Provided that the MCE line is 'high', the signal is fed to the counter section through MCP, while the appropriate decimal point signal is sent through DP₀, 1 or 2. The displayed number is read as kHz.

Counter IC₉ is advanced by a positive clock pulse, SCP, and is cleared whenever it reaches a count of four or when the SCL signal is high. SCL and SCP both come from the counter module where SCP is generated when there is an overflow signal from the counter and SCL is derived from the underflow signal.

The counters IC_{6,7,8} are enabled by a low signal on ICE and cleared by ICL going high. ICE and ICL are generated in the timing circuit when overflow or underflow signals occur.

Timing

The decimal counters IC₁ and IC₂ (figure 3), fed with a 50Hz pulse train, give a positive signal once a second. On the signal, MCE goes high which enables counter IC₃, disables IC_{2,6,7,8}, and stops the clock going to the main counter (signals MCE and MCP on the scaling circuit). MCE goes low if an overflow occurs on the main counter (MOV is low) and this makes Q on

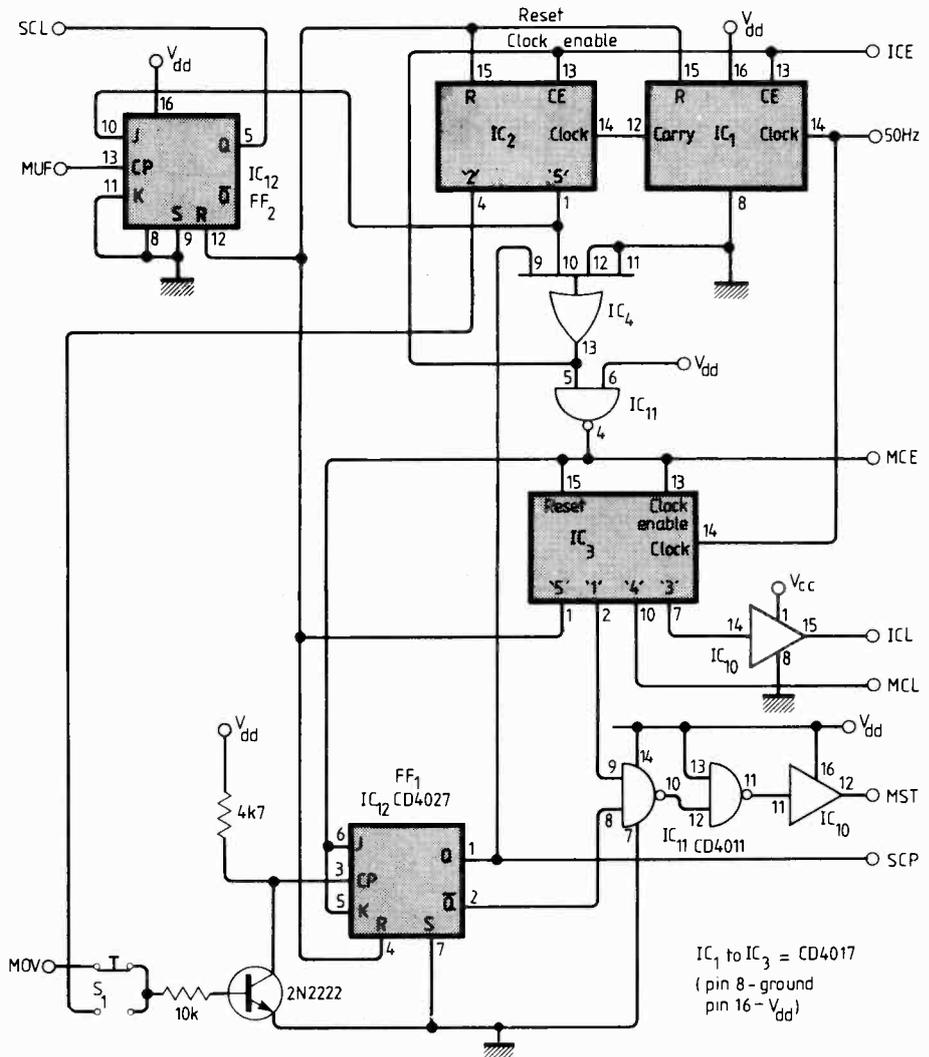


Fig 3. The timing module generates control signals for the scaling and counting circuits.

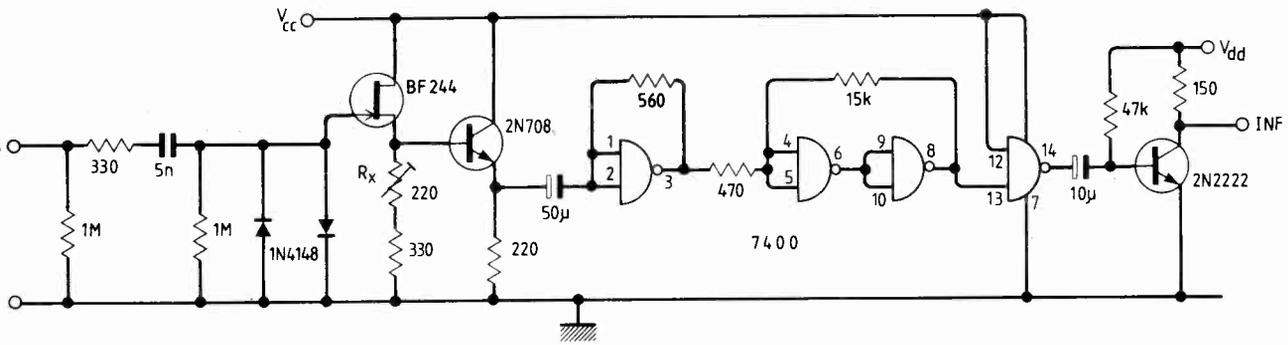


Fig. 4. Input module.

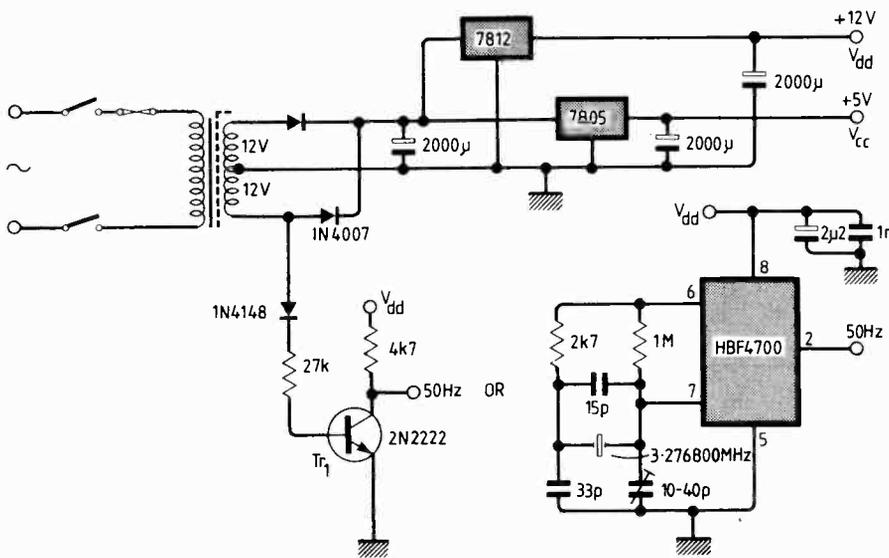


Fig. 5. Power supply. Two versions of a 50Hz clock generator are given, one derived from the mains frequency, the other gives quartz crystal precision.

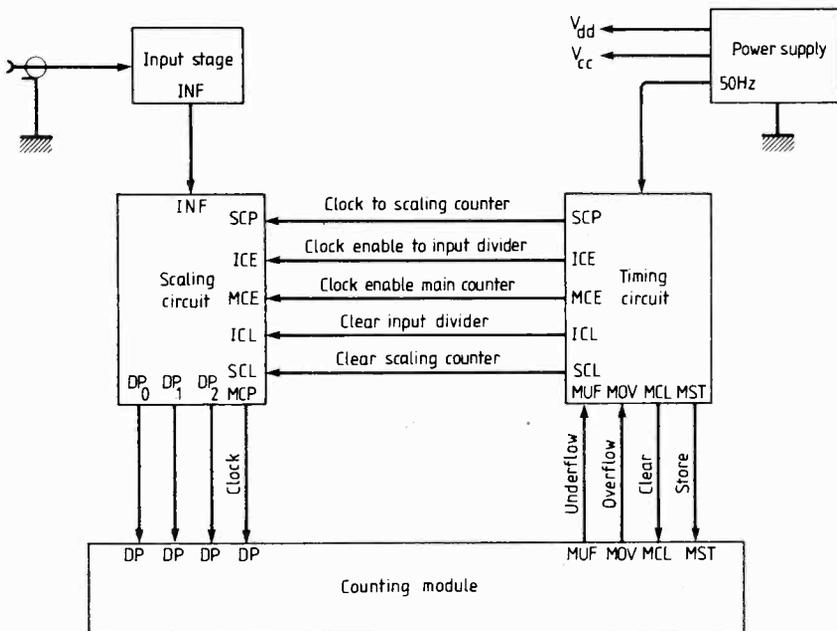


Fig. 6. Interconnections between the sections.

FF₁ go high and advances counter IC₉ by one to change the range. As IC₃ is enabled, it can generate the store signal, MST, and the clear signal, MCL. At the same time, through ICL, IC_{6,7,8}, both flip-flops and IC_{1,2} are all reset and the next count period starts.

In an underflow condition FF₂ is set at the end of the count period as J on FF₂ is connected to output 5 of IC₂ which only goes high on a count of 50. When FF₂ is set, IC₉ is cleared through SCL and the next count starts at the lowest range (X.XXXkHz). An overflow condition may be simulated by pushing S₁. This may be necessary if the main counter locks, which can happen because the 74C926 can operate at frequencies up to 3 or 4MHz.

Input circuit

Figure 4 represents a classical circuit which requires no comment. R_x is set to give the best results.

Power supply and 50Hz generator

The power supply is a standard circuit to give V_{dd} (12V) and V_{cc} (5V). In Figure 5 there are two circuits for clock generators for the timing circuit. The first derives a signal from clipping the a.c. input, theoretically 50Hz. The second is built around an HBF4700 to give 50Hz with quartz precision.

Note. According to the 74C926 data sheet: "A low signal on the latch enable input will latch the number in the counters into the internal output latch". I found that it needed a high signal but if some versions of the i.c. work as described, it would be necessary to invert the signal by disconnecting the link between pin 11 of IC₁₀ and pin 11 of IC₁₁ and then connecting pin 11 of IC₁₀ to pin 10 of IC₁₁ (Figures 2 and 3).


Bibliography

- A. Fantini, Note sui frequenzimetri digitali. *CQ Elettronica*, July, 1974.
- F. P. Caracausi, Frequenzimetro digitale automatico. *CQ Elettronica*, Sept. 1976
- F. Bonadio, 50Hz con lo HBF4700A, *CQ Elettronica*, April, 1980.


Two-metre transceiver

Coordination and frequency indication are functions carried out by these two modules of Forrester's multi-mode transceiver. At the heart of module 8 – the processor/interface board – is a 6805 microprocessor with built-in p.i.a. This section interprets front-panel settings and controls mode, frequency, and memory operations while module 9 converts port signals into an l.e.d. readout.

Module eight uses a c.m.o.s. MC146805 microprocessor (Motorola) which was chosen from the many now available for several reasons. Most modern processors have built-in ram and clock-generator circuits but the 6805 also has its own peripheral-interface adapter, or p.i.a., which provides a means of getting data in and out of the processor. This factor, combined with the device's low power consumption of 20mW and its potential for single-stepping through a program to aid debugging make it ideal for this application. Memory in the form of a 2716 eprom and five other i.cs

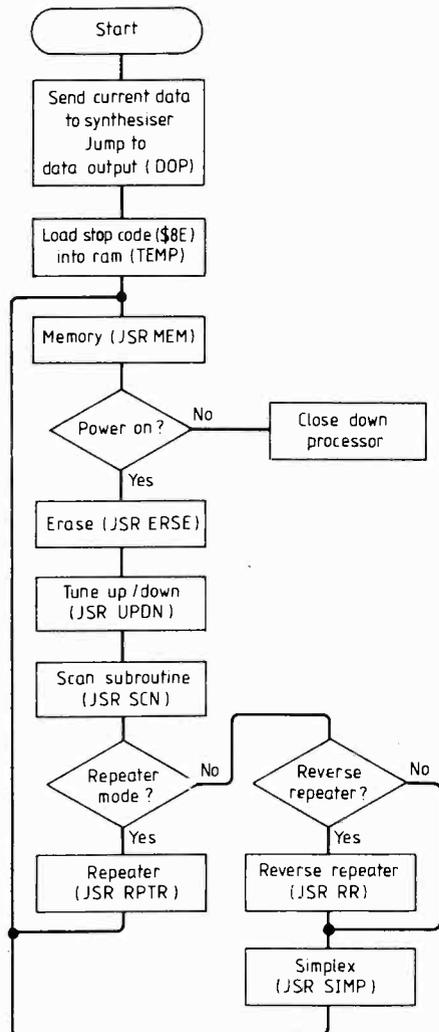

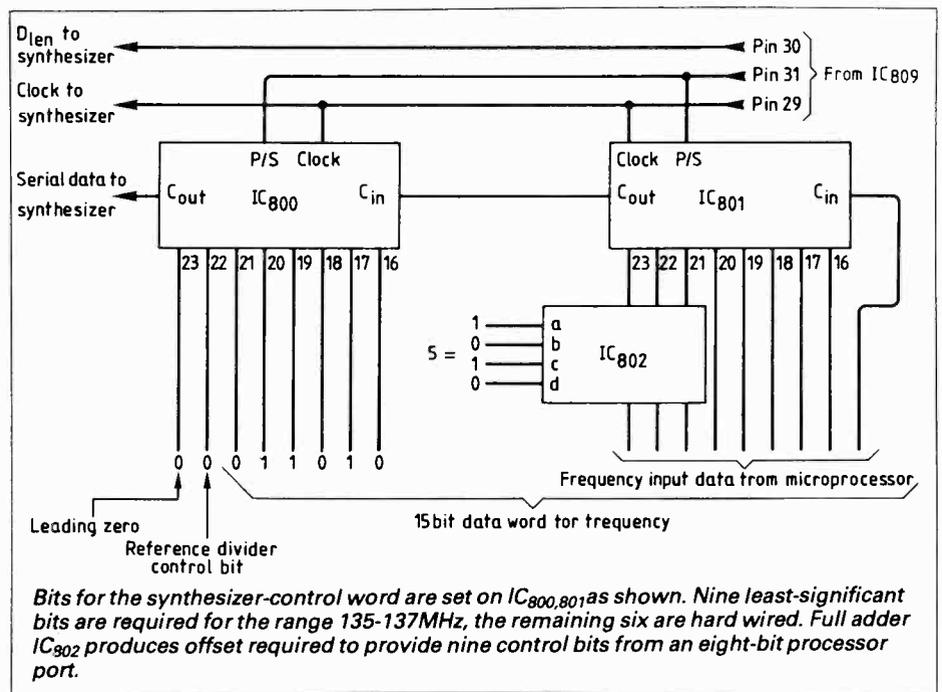Transceiver software breaks down into these main routines. Mnemonics shown are used in the assembly-language program.



are all that is required to interface the microprocessor to the transceiver, as the circuit diagram shows.

First described is the operation of the microprocessor as this will lead to a better understanding of the hardware around it and how the software functions. In the software, a master-control program calls various subroutines depending on control settings and these subroutines may call further subroutines; at times there may be eight levels of subroutine in use.


Before the microprocessor can act, it has to contain data relating to the front-panel control settings and it acquires this information by setting one of its p.i.a. B-port lines high. Pin 36 of the processor is one line used for this purpose. This line, called controls enable, is connected to the common of switches for mode, scan, memory, memory write and skip control. These switches are sensed by p.i.a. A-port lines through diodes when pin 36 is high; any switch closed while the controls enable line is high shows a logic 1 on its A-port line. This port is examined by the software and a decision made as to which subroutine is to be called for the mode concerned.

Port A of the 6805 p.i.a. is also used for


sensing the channel-switch condition. When memory mode is entered the channel-enable line at pin 35 of the 6805 goes high and the channel switch is represented on the A port through diodes. Interaction between channels is prevented by these diodes.

In this situation, port A is bidirectional and each device driven by the processor through it is selected independently by control lines from port B. For example, when frequency is to be displayed, display latches are enabled by taking the enable-display line low. The five l.e.d. drivers are selected sequentially by lines PA₄₋₆ and presented with four-bit words representing their digit value on lines PA₀₋₄. Likewise for transmitting data to the synthesizer the 4034 shift registers are enabled and the appropriate data loaded then clocked out sequentially.

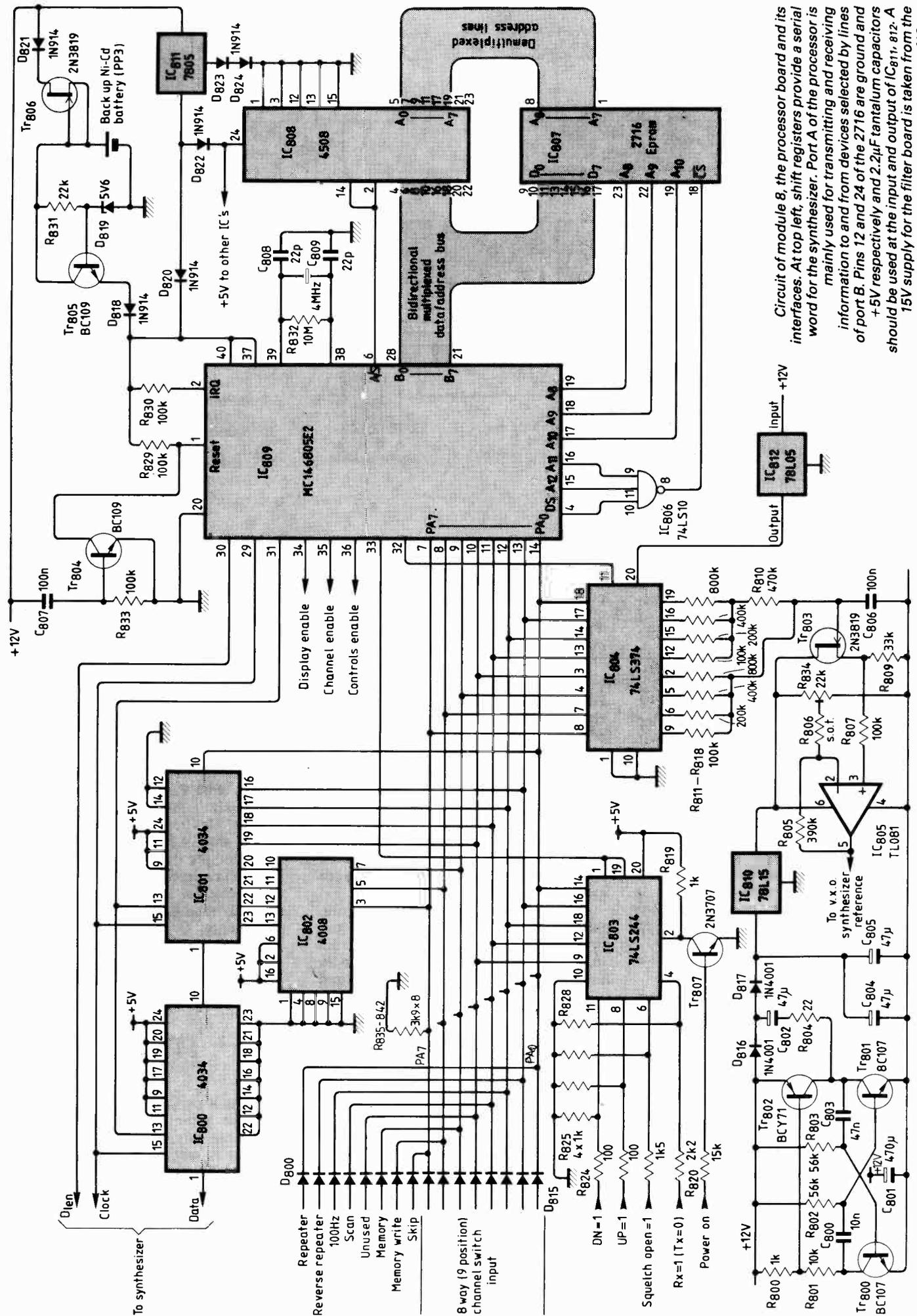Appropriate control bits for the synthesizer are set on IC_{800,801} as shown in the diagram. As mentioned in the description of the synthesizer control logic in module 5 (see January 1983 issue), only the nine least significant bits are required to change to cover 135 to 137MHz, so the other six bits of frequency-data word are hard wired



Circuit of module 8, the processor board and its interfaces. At top left, shift registers provide a serial word for the synthesizer. Port A of the processor is mainly used for transmitting and receiving information to and from devices selected by lines of port B. Pins 12 and 24 of the 2716 are ground and +5V respectively and 2.2µF tantalum capacitors should be used at the input and output of IC 811. A 15V supply for the filter board is taken from the output of IC 810.

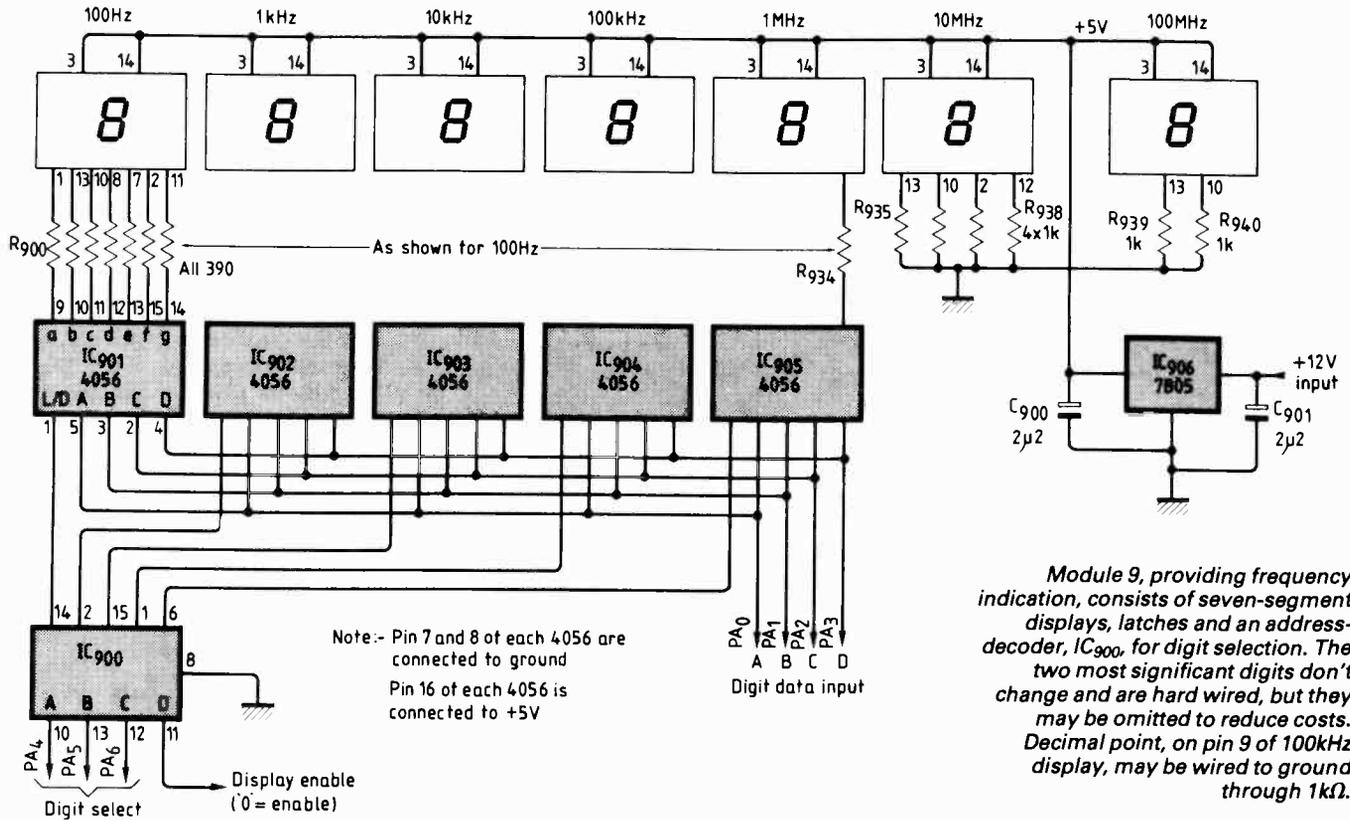

Module 9, providing frequency indication, consists of seven-segment displays, latches and an address-decoder, IC900, for digit selection. The two most significant digits don't change and are hard wired, but they may be omitted to reduce costs. Decimal point, on pin 9 of 100kHz display, may be wired to ground through 1kΩ.

converter and the d.c. level at C₈₀₆ is buffered and modified by Tr₈₀₃ and IC₈₀₅ respectively. A starting frequency of 135.0000MHz is set using R₈₃₄ and the synthesizer-reference pulling range is set by R₈₀₆, which is nominally 200 kilohm. To ensure a stable supply voltage, IC₈₀₄ has its own 5V supply. Transistors 800-802 and IC₈₁₀ form a d.c.-to-d.c. converter supplying a stabilized 15V rail for IC₈₀₅; this rail is also used to power IC₅₀₃ of module 5.

Five status signals are switched onto the A port through IC₈₀₃ by the enable line from pin 33 of IC₈₀₉. These active-high status signals are

- up button pressed
- down button pressed
- squelch open
- receive/transmit
- power on.

The first four indications act straightforwardly on the microprocessor but the fifth, power on, it a little more involved. When the transceiver is turned off, Tr₈₀₇ conducts momentarily using charge stored in the set's capacitors and pulls pin 2 of IC₈₀₃ low, forcing the processor to revert to its low-power standby mode. Resistor 820 is wired to the off contact of the mode switch, the common of which normally distributes a 12V supply to the appropriate modules.

In standby mode, the processor ram contents are held intact by an NiCd battery through D₈₁₈. A 2N3819 fet, Tr₈₀₈, forms a constant-current charger for the back up battery while Tr₈₀₅ and D₈₁₉ regulate the voltage. Under normal conditions, IC₈₀₉ is powered from IC₈₁₁ through D_{820,818} to allow charging of the battery. Diode 820

isolates the battery supply from logic power lines when the transceiver is turned off. When the transceiver is switched on, Tr₈₀₄ is momentarily turned on through C₈₀₇, causing the microprocessor to reset.

As the processor's data and address buses are multiplexed, a latch, IC₈₀₈, is required to separate the two. This latch is controlled by the address strobe line, pin 6 of IC₈₀₉. Demultiplexed addresses are then fed to IC₈₀₇, a 2716 eeprom; this memory is enabled when its chip-select input is low, and this only occurs when address lines A11 and A12 combined with the data strobe line in NAND gate IC₈₀₆ go high. Prospective builders of this transceiver should not be deterred by the need for eeprom-based software as these devices are available ready programmed from me.

Channel switch, skip, memory-write, memory, scan, 100Hz-step, repeater and reverse repeater controls are all connected to the p.i.a. A port through 1N914 diodes forming OR gates. Sixteen diodes are used

in all, including a spare one for future expansion. Eight 3.9kΩ pull-down resistors, R₈₃₅₋₈₄₂, are connected to A-port lines PA₀₋₇. IC₈₁₂ should be mounted on the metal enclosure to keep it cool.

The only adjustments needed on this board are to R₈₀₆ and R₈₃₄. Initially, R₈₀₆ should be set at around 200kΩ with the transceiver set to 144MHz and R₈₃₄ adjusted so that the synthesizer produces exactly 135MHz. Now the frequency is changed to 144.0099MHz, i.e. 9.9kHz higher, and R₈₀₆ adjusted so that the synthesizer frequency increases by 9.9kHz. This process should be repeated.

This module is mounted directly to the chassis of the transceiver without screening. R.f. radiation is emitted by devices in this circuit but screening and filtering on the other modules is sufficient to prevent interference. On the current transceiver, the interrupt-request input (IRQ) is not used but I plan to incorporate an infra-red remote control unit using this line.

Frequency display – module 9

Microprocessor control makes driving of the frequency display relatively easy. Seven-segment l.e.d.s were used for the display in preference to l.c.d.s because they were cheaper, but by now the situation may have changed. Display latching is used to ensure that the maximum brightness is obtained for viewing in sunlight; many transceivers using strobed displays suffer from lack of brightness.

Display-drive data are taken from the processor p.i.a. A port, the digit being represented by PA₀₋₃ and the digit address represented on lines PA₄₋₆. Digit-address

decoding is performed by IC₉₀₀ which enables the appropriate latch. The display latches can only be enabled if the D input of IC₉₀₀ is taken low by the processor. Resistors 900-934 limit the display current for the active digits and R₉₃₄₋₉₄₀ hold the two most significant digits permanently at 14. Here, the five-volt regulator, IC₉₀₆ is mounted to the chassis to keep it cool.

Programmed eeproms at £8 and software listing at £1.50 including UK postage and vat are available from T. Forrester, 125 Seven Way, Bletchley, Bucks.

Waves in space

In an open circuit, only an electric field is detectable. Is this because there is no magnetic field present?

Prior to Maxwell, a great deal of theory had been developed around electric and magnetic fields. This theory included Kirchhoff's Laws, the Biot-Savart Law and Ampère's Rule. Electrical circuits were generally steady state, or at worst slowly varying, and the problem of whether electrical and magnetic effects traversed distance instantaneously or took time to propagate did not arise.

Because fields were steady or slowly varying, experiments were generally limited to the study of closed circuits of conductors (and resistors). However, capacitors (electrolytics) were also used, and these created an anomaly in a theoretical structure which included Ampère's circuital law ($\oint \mathbf{H} d\mathbf{l} = i$) and Kirchhoff's second law ($\sum \mathbf{i} = 0$). When the switches were closed, electric current flowed in the loop and (following Ampère's circuital law, also called Ampère's Rule,) magnetic flux appeared in the space around the wires.

Ampère's Rule says that if we describe a closed loop, the line integral of the magnetic field strength along the edge of the loop is related to the electric current through any surface bounded by the loop.

The capacitor created an anomaly, because a closed loop could be described where i had more than one value, depending on whether the surface (S_1) cut the conductor or S_2 passed between the plates of the capacitor. Consequently the absurd situation arose that $\oint \mathbf{H} d\mathbf{l}$ had to have two values at the same time.

Maxwell 'cut the Gordian Knot' by asserting that the rate of change of electric field between the capacitor plates behaved just like a real current i . So Ampère's rule became

$$\oint \mathbf{H} d\mathbf{l} = i + \int \frac{d\mathbf{D}}{dt} \cdot d\mathbf{s}$$

It is important to remember that the *premise* which preceded the problem of the capacitor was that electric currents and fields were steady or slowly varying. It was accepted that, at the moment the switches closed, the current i appeared at all points in the circuit. The time for the effect of the switch closure to travel across the distance from switches to capacitor was zero.


The current-like field $d\mathbf{D}/dt$ between the capacitor plates led Maxwell to conjecture that there could be electromagnetic 'waves in space'. It was already known that a changing magnetic field produced electric current (Faraday's Law $\mathbf{v} = d\phi/dt$) and that electric current produced a magnetic field (Biot-Savart Law $\mathbf{H} = i d\mathbf{l} \sin \theta / 4\pi r^2$.) The changing electric field $d\mathbf{D}/dt$ seemed to be an electric current in space. With both changing magnetic fields and changing electric

by Ivor Catt


currents in space, we seemed to have the possibility of wire-less propagation of electromagnetic signals using a crabwise progression of cause and effect; electric current \rightarrow magnetic field \rightarrow electric current

The error in this whole business occurred right at the start. Let us assume that the conductors linking battery to capacitor are one light year long. When the switches are closed, it is obvious that current will not immediately flow in the capacitor. A wave front must travel from switches to capacitor, and behind that front will be electric field and magnetic field - we have a transmission line. Also, should the distance between the two conductors or their shape change, some of the wave front will continue to the right and some will reflect to the left, carrying back the message about the change.

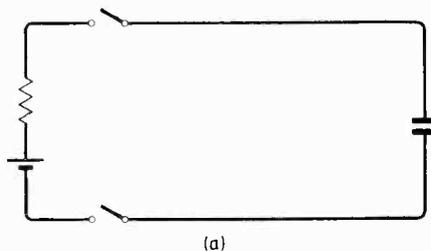The front end of the capacitor is merely one such change in the cross section of the transmission line. The far (open circuit) end of the capacitor is another such change.



(a)

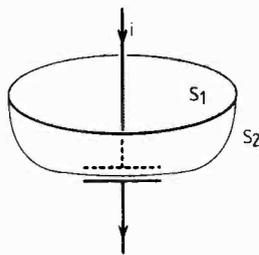

(b)

Fig 1. The elemental closed loop (a), in which the capacitor creates the difficulty that the current must have two values, depending on whether the surface (b) cuts the conductor or bisects the capacitor.

The problem Maxwell should have been concerned about was how the electromagnetic field developed between the wires when the switches were closed, not what happened in a capacitor. The transmission line problem (AB) precedes the capacitor problem (CD), and the capacitor problem would be solved automatically with the solution of the transmission line problem.

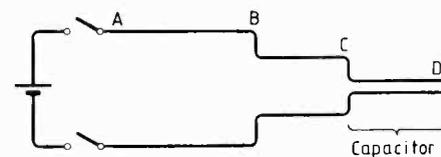


Fig 2. A changing separation between conductors reflects energy. The capacitor is simply another change.

Before the switches are closed, we can measure a voltage and electric field but find no trace of a magnetic field. When the switches are closed, an electric current starts off down the wires and a magnetic field begins to appear between the wires. The conclusion that the voltage (or pressure) causes the electric current which in turn causes the magnetic field is compelling, and it is not surprising that this mistaken view has lasted for a century. It is then a short step to say that the changing magnetic field in its turn (by Faraday's Law) generates an electric field and thence a (displacement) current, and the sequence can start again.

But was there *really* no magnetic field before the switches were closed?

Let us consider a steady charged capacitor. Does it have no magnetic field, only an electric field? In order to understand the situation in the battery and wires up to the switches before they are closed, it is useful to study the reed-relay pulse generator.

The reed relay pulse generator was a means of generating a fast pulse using rather primitive methods. A one metre section of 50 ohm coax. AB was charged up to a steady 10 volts (say) via a one megohm resistor, and then suddenly discharged into a long piece of coax. BC by the closure of two switches.

A five volt pulse two metres wide was found to travel off to the right at the speed of light for the dielectric on closure of the switches, leaving the section AB completely discharged.

(The practical device lacked the second, lower switch at B, which is added in the diagram below to simplify the argument.)

The curious point is that the width of the pulse travelling off down BC is twice as much as the time delay for a signal between A and B. Also, the voltage is half of

continued on page 66

- 1 Theories and miracles
- 2 Electromagnetic analogy
- 3 Impact of the photon
- 5 Quantization and quantization
- 6 Waves of improbability
- ▶ 7 Limitation of indeterminacy
- 8 Haziness and its applications
- 9 State of physics today

The limitation of indeterminacy

Knowing the difference between physics and metaphysics, likewise between "matter-waves" and probability theory, one can begin to understand where modern physics went wrong. Two well-known Copenhagen doctrines can then be taken apart: in consequence the law of causation can be restored to its rightful, paramount place in natural philosophy.

I have drawn attention to the two principal confusions of thought which were allowed, or perhaps even encouraged, to enter physical science during the decade 1925 to 1935 and which have caused untold philosophical chaos ever since. These were: the indiscriminate juxtaposition or equation of physical entities, such as electrons and mechanical momentum, together with metaphysical entities such as probability and knowledge; and the failure to reject the wave theory of matter when it had been disproved (on both experimental and logical grounds), and to distinguish between its concepts and those of the legitimate statistical quantum mechanics. Even the popular name for the last-mentioned, "wave-mechanics", which derives from its conceptual origin under Schrödinger but is no longer relevant, contributes to the perpetuation of the muddle; a first-rate example of confusion is to be found in the frequently-used expression "probability waves".

Lest it should be thought that these confusions have been innocuous in their effects I will instance a famous statement by a member of the Copenhagen School which provides a vignette of both of them. The date of presentation was 1933, the place Chicago, the reporter Alfred Landé, and the speaker on this occasion Werner Heisenberg. He was referring to the partial reflection of light by a half-silvered mirror, in a thought-experiment that we have already considered in the contexts of quantization and determinacy. His words were as follows:

"There is, then, a definite probability of finding the photon either in the one or the other part of the divided ψ -wave packet. Now, if an experiment finds the photon in the reflected part, say, then the probability of finding it in the other part immediately becomes zero. The

experiment at the position of the reflected part thus exerts a kind of action, a 'reduction of the wave packet', at the distant point occupied by the transmitted part. And one sees that this action is propagated with a velocity greater than that of light".

Feeling the draught, perhaps, he then went on to say,

"... This 'action' can never be used for the transmission of signals".

by W. A. Scott Murray,
B.Sc., Ph.D.

By all accounts Heisenberg made this statement with a completely straight face and believed in what he was saying. It is manifestly nonsense, but for that very reason it may be difficult to make a rational reply to it. The argument that light waves are electromagnetic waves which carry energy and therefore cannot collapse faster than the velocity of light is not quite sufficient because Heisenberg has dodged it by referring to " ψ -waves". He is, however, proposing that *something* associated with the photon must collapse in this way; as Professor Frisch said in a passage that I quoted earlier,

"... It would seem that something does travel along both paths in the interferometer even when only one photon is admitted; but what is it?"

Clearly we are right at the centre of the duality paradox.

The understanding that we have been able to build up of the dualistic machinations of Copenhagen will now stand us in very good stead for dealing with Professor Heisenberg's curious proposal. The ψ -

waves that he is playing with are not real waves but metaphysical waves. They do not have to comply with the laws of physics. Like Castles in Spain, he can give them any properties he wishes. If those properties should make his equally metaphysical ψ -function provide a reasonably accurate statistical analogue of how real photons behave, that is all to the good, but his ψ -waves need not otherwise relate to the physical world and indeed for reasons that we have discussed it is clear that they must remain always "unobservable". They are subjective, mathematical abstractions. The photon, on the other hand, is a physical entity which is indivisible and which travels strictly at the speed of light. It goes one way or the other at the mirror surface, but not both; there is no question of a transmitted part of the photon collapsing when a reflected part is detected. The photon's existence is objectively real. So where is the paradox?

The rationale for Heisenberg's statement is that the intensity of his ψ -waves represents *the precision of his knowledge* of the past, present, and future location of this particular photon. (You will note that both "precision" and "knowledge" are metaphysical quantities, appropriately described by ψ -waves). When his knowledge becomes sure – 100% certain because he has detected the photon – the probability that it may be elsewhere instantly becomes zero, as he says. This has nothing to do with the photon, but only with his knowledge; it would be quite wrong to assume, as the Copenhagen School assumed and declared as doctrine on the basis of extensions of this argument and others, that the observer's knowledge or even the observer himself had any influence on the physical, mechanical

process of detecting the photon. Indeed, neither the photon nor the rest of the apparatus cares two pence whether an observer is present or not. We now see that the metaphysical doctrine of the relevance of the observer was just another Copenhagen fallacy.

Before leaving this topic let me mention a point which was first picked up by Sir Karl Popper, who has tended to specialise in this sort of thing. Even his ψ -wave packet does not in fact collapse as Heisenberg says it does. The distribution of ψ -wave intensity as a probability density – the probability of finding a photon here or there – does not change when any one photon is detected. It is to be identified as a prediction, the probability of detecting “any” photon as estimated before the event; for after the event the probability of a contrary result is a meaningless concept. And however many times you may have tossed a coin, the probability of obtaining heads or tails on the next toss remains always the same, 50/50 . . .

Thus Heisenberg’s celebrated puzzle of the “reduction of a wave-packet” turns out not to have been a puzzle after all. It was a man-made nonsense consisting of one false concept and two logical errors held together by two major confusions concerning, respectively, the mixing of matter-waves with probability theory and the mixing of metaphysics with physics. It was also unnecessary. We can see how it came about, but as physicists we have no cause to be proud of it.



I am going to conclude my exposition by analysing one more example of twentieth-century mysticism in the same way. The great Principle of Indeterminacy was enunciated by Heisenberg in 1927, and its profound philosophical message has dominated human thinking ever since. Like so many concepts of modern physics it is partly true. My purpose now is to examine the limits of its applicability and truth.

In its legitimate form the Principle of Indeterminacy (or Uncertainty) has to do with making measurements. For a host of reasons, all of which in the end boil down to the desire to make predictions in order to better manage our surroundings, we are interested in the positions and motions of things. We measure the position and motion of an oncoming motor-car by eye when we are deciding whether or not to cross the road; for more precise measurements we make use of various instruments such as rulers, gauges and gratitudes. In the ultimate of fineness of measurement our measuring instrument may consist of one photon or one electron which we aim carefully toward the target object whose location we wish to know; the electron or photon will be reflected (or bounce) on contact, and its reflection will tell us where the object was. Microphysical Nature being granular or “quantized”, this represents the most delicate measurement that we can ever hope to make.

It was Heisenberg who pointed out, correctly, that this process doesn’t provide a measurement of where the object is, but of where it *was* at the instant of making the

measurement. The measuring process itself must disturb the object being measured, to an extent that depends on how massive the object is. Projecting one photon of visible light at an elephant, for example, wouldn’t shift the elephant very far, but if that same photon were to hit an isolated electron it would set it in motion at a speed of several hundred miles per second. (This is the Compton effect discussed earlier). If you were to use a less massive photon – that is to say, conventionally, a quantum of light of lower “frequency” or longer “wavelength” – you wouldn’t disturb the target electron so much but you wouldn’t get such a precisely-defined reflection from it either. You can’t have it both ways.

Heisenberg condensed these ideas into what was to become one of the most famous Principles of physics. (For those who don’t mind equations, I am referring now to $\Delta p \cdot \Delta x \approx h$). Stated in words, it says that there is a natural limit to the accuracy (Δ) with which physical quantities can be *measured*. The position and momentum of any particle as measured are in a sense complementary. We can in principle devise an experiment to measure either position (x) or momentum (p) as accurately as we wish, but if we try to measure both simultaneously we come up against this natural limit. We cannot measure, and therefore cannot know, both the location and the subsequent velocity of an individual electron with greater accuracy than is indicated by Heisenberg’s formula. No evidence has yet been found to suggest that his formula when interpreted in this way is not always and exactly true.

Now it must follow as the night the day that *if* we cannot measure the position and velocity of an electron precisely at the beginning of an experiment or during it, *then* we cannot predict with precision where that electron will be at the end of the experiment. The Principle of the indeterminacy of measurement must therefore lead directly to a corollary Principle of the limitation of prediction. This realisation came as an unwelcome shock to the physics of the 1930s and also, when news of it leaked out, to philosophy in general; for physical science had come to extol its ability to make precise predictions above all other virtues, while human vanity was unwilling to accept that there was anything that human technology ultimately could not do. Faced with this crisis of confidence it was perhaps inevitable that certain spirits should cast about in the hope of finding an escape clause.

We shall examine the defensive antics and flights of fancy of those folk in the next article, but before doing so it will be well to establish how far the *experimentally-verified* aspects of the indeterminacy principle can carry us. Suppose that a fundamental particle (an electron, say) is initially at point A at time zero and travelling at velocity v . According to our best possible measurements we know only that it is within, say, one micrometre of A at that instant and travelling subsequently at a velocity within, say, 100 metres per second of v . From this knowledge we can predict that the electron will in due course pass

within one centimetre of a second point, B. The quantum mechanics as a mathematical tool will perform that prediction for us beautifully – there is nothing mystical about it or its calculations, which rely on the conservation laws. But we should note that it is not the position of the electron which is uncertain; it is *we* who are uncertain about its position. The electron itself travels from point A (exactly) to point B (exactly) along a track AB which is precisely determined. It is *our knowledge* of that track, not the track itself, that is imprecise; and it is *the imprecision of our knowledge*, not the physical body itself, that is transferred from the vicinity of point A to the vicinity of point B by the so-called “operators” – metaphysical operators – of the statistical quantum mechanics.

Now what I have just said constitutes a new interpretation of the function of the quantum mechanics or “wave mechanics”, and it is controversial. It is also very dangerously heretical, because anyone who accepts it must eventually refute the Copenhagen dogma. I should therefore amplify it a little. Even Heisenberg, under pressure, admitted that his indeterminacy principle did not apply to retrospective measurements. By observing the same electron on two occasions very far apart in time and space, we can determine where that electron was at the time of the first measurement and how fast it was then moving, and we can in principle determine *both* those quantities after the event *to any accuracy we please*. I believe that to be the most important single point I have to make in all these discourses; for Heisenberg, hedging hard, claimed vehemently that such retrospective determinations, although valid, were irrelevant to science

Catastrophic misconceptions

A fine example of the effect on physics of man-made confusions is afforded by Heisenberg’s famous proposal of the “reduction of a wave-packet”. On the basis of physical arguments already generated it is possible to refute this proposal on three counts and to resolve it as a paradox. Similar treatment may be extended to the great Principle of Indeterminacy. It is readily argued that as applied to current measurements and forward predictions the Principle is almost certainly true. However, it is not true in the case of retrospective determinations, and it follows that, contrary to the generally-accepted Copenhagen doctrine, the behaviour of every microphysical entity is determinate and complies with the conservation laws. This is equivalent to the statement that the law of causality is obeyed universally in inanimate Nature, not only statistically but by individual micro-objects. Such a view is philosophically consistent with the laws of conservation. It is likely that the opposing (Copenhagen) doctrine, now widely held, arose from the 1930s confusion of inanimate physics, always determinate, with animate metaphysics, not necessarily determinate or rational.

(which he declared should be concerned only with prediction), whereas you and I will discern instead that they are highly relevant. We will recognise that our ability to calculate precisely the earlier position and momentum of an electron on the basis of later knowledge constitutes philosophical proof that the electron's behaviour during the interval was determinate. During that particular but arbitrary interval it must have obeyed the law of causality: and if then, always. The reason why this new argument is especially important, although one might have thought it obvious, is that the most celebrated doctrine of Copenhagen physics categorically asserts the opposite – that microphysical particles do *not* obey the causality law as individuals, but only “on average”, in a statistical manner.

Thus the vital limitation or restriction which I now suggest must attach to the great Principle of Indeterminacy is that it may deal legitimately with the indeterminacy of measurement and prediction but may not, *repeat not*, express or imply any mystical indeterminacy of Nature. Despite general belief and conventional doctrine there is not, and never has been, any experimental evidence in support of the established idea that its operations are not bearings” and that its operations are not precisely determined. How that gross error came to be made will be reviewed in the next article, together with some examples of its catastrophic effects; in the meantime

I shall ask the printer to set this statement out by itself, so that there can be no mistake about what I am saying:—

The law of causality is obeyed throughout inanimate nature

I cannot prove that statement. No scientific law can be proved, but its strength lies in the fact that no record exists of its ever having been broken. Specious Copenhagen “quantum” arguments notwithstanding, I can only re-assert that there is no experimental evidence against causality. Evidence in its favour surrounds us at every turn, because the law is itself a paraphrase of the great conservation laws of energy and momentum whose universal applicability is generally accepted. Therefore one cannot in logic acknowledge conservation while at the same time denying causality; that is what was so very odd about the 1930s doctrine that nature is indeterminate.

Almost certainly the confusion arose out of the failure to distinguish between physics and metaphysics, the science of the mind. There is plenty of evidence that *decisions* (made by living creatures)* are not always necessarily rational. That fact alone is sufficient to prevent a “Laplacian being” – or anyone else – from making an ultimately precise prediction of the future of the universe. Free will does, indirectly, modify the course of events, as human beings are fully aware; determinism applies only to inanimate, physical

interactions. There is room in God's world for both vitalists and mechanists! But here for our sins we must stick with inanimate nature.

I said earlier, in connection with the reflection of photons by the half-silvered mirror, that the word determinate is not synonymous with “predictable by mankind”, and went on to say that the arrogant assumption that it was had led to much philosophical trouble in physics. It has also been exported, and caused much trouble elsewhere. It was the basis of the twentieth-century denial of causality, in which the whole of philosophy followed the physicists' misguided lead.

If I were to give you three guesses as to where that assumption came from I'm sure you would be right first time – and not by guessing. It came from the already-disproved but still unrejected wave theory of matter. Let us next explore how. 

* Automatic electronic computers do not make decisions. They are inanimate machines, physical structures driven by energy, which obey a set of instructions or program in a strictly causal, pre-determined way. A program, however, is a metaphysical structure – an expression of a human programmer's will. It is not a tape or a disc, but the information which is stored on tape or disc (it is equally valid in typescript or in the form of a flow diagram). It consumes no energy itself, and it can influence physical events only when it is able to control the operation of a physical computer as intermediary. The analogy with mind and brain is self-evident.

LITERATURE RECEIVED

PCB assembly can be made easier using a Royonic semi-automatic assembly table, according to a brochure describing the system. Components are presented to the assembler in order from a dispenser and their position is indicated by a light spot projected on to the p.c.b. which can draw an outline round the position of an integrated circuit or flash to indicate that polarity needs to be checked for a diode or an electrolytic capacitor. The machine may be programmed by using a joystick or a touch-sensitive pad and the program stored on a floppy disc. Fast assembly of boards with fewer faults is claimed for the system. The brochure is available from W. J. Stickland (Electronics) Ltd, 60 Tower Hill, Chipperfield, Kings Langley, Herts WD4 9LH. WW 400

Recent additions to the Online Conferences 1983 catalogue of conference proceedings. Viewdata 82, Videotex, Local Area Networks and distributed office systems and the Computer Graphics 1982 conferences. Online act as distributors for other publishers including QED Information Sciences and list their publications on data processing and information

management. Online Publications Ltd, Argyle House, Northwood Hills, Middlesex HA6 ITS. WW 401

Tools, cases, breadboards, circuit boards and p.c.b. etching patterns are included in the *Hobby Herald*, a catalogue for the “hobby engineer”, presented in a newspaper format by BICC-Vero Electronics, Parr, St Helens, Merseyside. WW 402

Specifications, standards and technical documents from the world over are available through a service described in a brochure from London Information (Rowse Muir) Ltd, Index House, Ascot, Berks SL5 7EU. WW 403

Line conditioners to protect computers and other digital systems against noise and voltage variations on a.c. power lines are featured in a leaflet. It includes a selection guide to range of units in the GT series, with detailed information on the electrical parameters which affect the choice of unit. Gould Electronic power conversion Division, Rhosymedre, Wrexham, Clwyd, LL14 4YR. WW 404

Two volumes and over 1,500 pages describe data acquisition products of Analog Devices. The Data Acquisition Databook includes 500 standard products and includes both data sheets and tutorial sections. Products include converters, op amps, conditioners, computing circuits, power supplies, panel instruments,

systems and subsystems for measurement and control, and component test systems. Key specifications and applications are given for all the products and a price list is included. Analog Devices Ltd, Central Avenue, East Molesey, Surrey KT8 0SN. WW 405

A glossary of filter terminology and design examples with information on the use of filters in duplexers and multiplexers are included in the Lark Engineering catalogue. Product information includes performance characteristics of bandpass, band reject, tuneable, high and lowpass filters and switchable filter banks. The company uses c.a.d. to produce filters to specified requirements in the frequency range from 12Hz to 18GHz. March Microwave Ltd, 112 South Street, Braintree, Essex. WW 406

Measurement of the suppression characteristics of passive radio interference filters and suppression components is subject to a new Standard, BS6299. The standard specifies methods for measuring insertion loss of passive r.f. filters which may consist of single elements, singly or in combination and either lumped or distributed types. Methods include those for laboratory testing or on a production line tests using fixed impedance terminations. The standard costs £19.50 from BSI sales department, 101 Pentonville Road, London N1 9ND. WW 407

Ultra high density data recording

Since the disc-drive series was written a great deal of significance has happened in the field – the next few years will see progress that will make 10^7 bit per square inch seem pedestrian.

The first disc drives appeared around 1956, when computers were exotic vacuum tube monsters, and these early drives offered densities of about 2000 bit/in². Currently available machines offer around 10^7 bit/in² – a staggering increase in such a short time, but the next few years will see progress that will make these figures seem very pedestrian. Current research is concentrated in three areas, the medium, thin-film heads and vertical recording.

The great majority of today's discs are coated with the gamma form of ferric oxide, the familiar brown material. If tracks are to be made narrower to pack more of them on to a surface, there will be a pro-rata reduction in signal output, and

by J. R. Watkinson, M.Sc.

it is necessary to adopt a medium which has greater magnetization to maintain s/n ratio at a level which gives acceptable data error rates. Cobalt has been found to have this desirable property. Given the greater magnetization of cobalt, the coating can be made thinner as well as the tracks narrower. With conventional longitudinal recording, the smaller the cross-section of the recorded magnets (track width × coating thickness) the shorter they can be

John Watkinson is now with Sony Broadcast Ltd

before self-demagnetization makes them unreadable.

Although thin cobalt coatings are more sensitive to substrate irregularities, this has not been the main reason for the slowness of the industry to adopt the medium. The main cause is that the process required to make cobalt-coated discs is totally different from that required for conventional oxide coating. Oxide is applied in the form of a slurry, which then dries out; cobalt cannot be applied by this old technique and requires either ion bombardment or spluttering. As the industry cannot tolerate instantaneous obsolescence of current media plant, the move to the metal-coated discs will be gradual.

Conventional heads are made of ferrite with a glass gap. The performance limits set by this form of construction have now been reached; losses in ferrite mean that it cannot follow more than about 10^7 transitions per second. Width of the recorded track is determined by the thickness of the magnetic circuit in the head and the brittle nature of ferrite sets a limit of about 1000 tracks per inch, beyond which the head would lack durability.

A solution to the problem is the thin-film head. Unlike a conventional head, which is assembled from a variety of components, the new thin-film head is fabricated by plating in the same way as thin-film microcircuits. The magnetic circuit is a nickel-iron alloy, permalloy, plated onto a silicon substrate along with a single-plane copper coil in the form of a spiral. The permalloy can be plated to write a track of any desirable width, because it is evenly supported by the silicon substrate which then subsequently becomes the aerodynamic head slider, as shown in Fig. 1.

This arrangement has a number of advantages. Firstly, permalloy has a frequency response an order of magnitude better than ferrite. Secondly, the thin-film construction and the characteristics of permalloy cause a very sharp fall in flux density away from the gap along the longitudinal axis. The final magnetization of the medium is determined by the trailing edge of the head field. This effect restricts ferrite heads to about 10,000 transitions per inch, whereas the thin film head can give a 50% improvement on

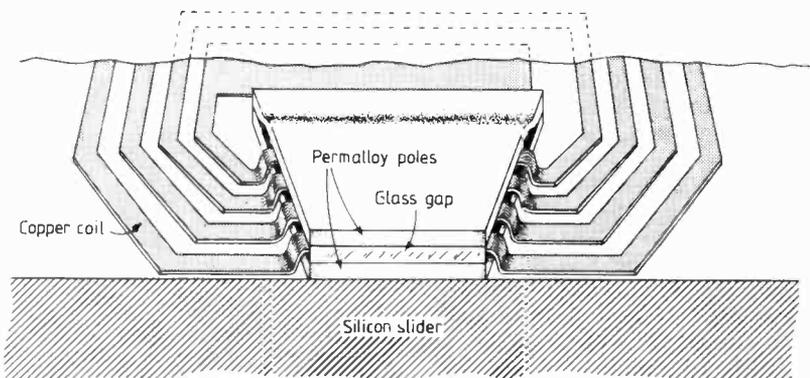


Fig. 1. Thin-film head made using microcircuit technology on a silicon substrate which becomes the slider.

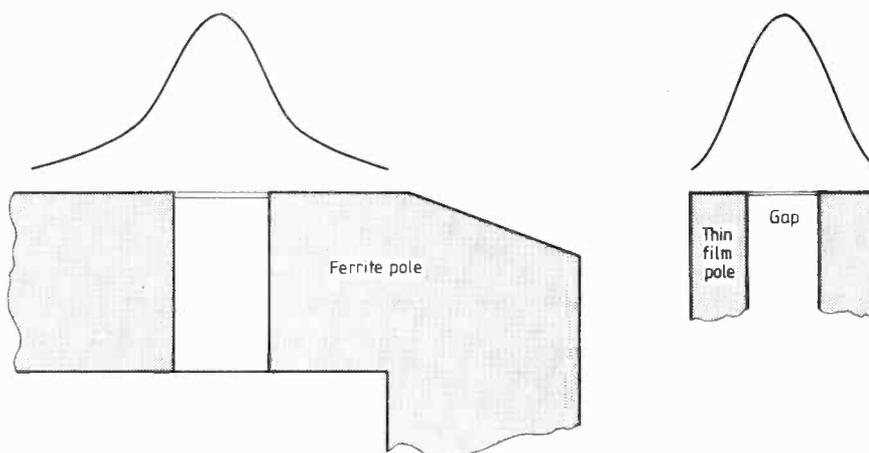


Fig. 2. Comparison of fields of ferrite (left) and thin-film heads (right). Curves show longitudinal field strength at typical working distance from poles. Sharper curve of thin-film head allows shorter wavelength recording.

oxide media, and may give as much as 25,000 transitions per inch with metal media, Fig. 2.

Very short magnetic domains tend to demagnetize themselves. The effect is governed by the ratio of the length to the width; the longer and thinner a magnet, the less likely it is for the opposing poles to neutralize each other. As Fig. 3 shows, it is an unfortunate fact of life in longitudinal recording that the higher the density, the shorter the domains.

Now vertical recording organizes the domains at right angles to the substrate such that the higher the density, the narrower the domains. Domain length is now controlled by the coating thickness. Claims have been made that 10^5 bits per inch will soon be available in production equipment, with ultimate density perhaps an order of magnitude greater. The problem is one of designing a compatible head and medium; chromium cobalt is sputtered onto a substrate.

The head must consist of a pole at right angles to the disc which throws the field into, rather than along, the medium. As the trailing edge of the field determines the final state of the medium, the pole used for writing only could have a relatively large dimension along the track, but a head used for reading would need a very small pole indeed. The minute signals induced at such high densities might require an amplifier to be integrated into the slider. Thin film technology might enable the magnetic circuit and the amplifier to be fabricated in one process.

Optical recording

Optical recording is as old as talking pictures, when recording was by modulating the width or density of a track alongside the picture frames, which could be read with a lamp and a photocell. Such techniques were studied in the 1940s when the first digital computer emerged. These optical storage projects were quietly forgotten when the first magnetic drums and subsequently discs started to show their paces. Film needed to be processed before it could be read back, whereas magnetic storage offered immediate read back. But optical recording never died, and the invention of the laser with the consequent study of its applications gave it new potential.

The essence of modern optical storage is that laser light is used to melt or otherwise affect the medium in such a way that the changing reflecting power of the surface can be used in the read process. There are a number of different approaches to the basic principle, but the optical assembly required is similar in construction in all of them, Fig. 4. There are two lasers, the write laser being the more powerful; a half-silvered mirror allows light from either into the system. For reading, the low power read laser is activated. Unlike magnetic reading, where the read head acts as a generator, optical reading requires an external source of energy that is modulated by the medium, permitting large signals to be generated.

The most interesting aspect of the read

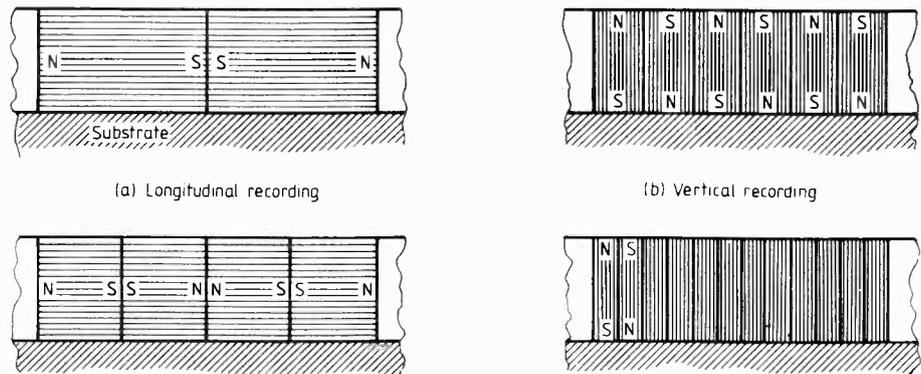


Fig. 3. With conventional longitudinal recording, an increase in density reduces the aspect ratio of the media domains (a) aggravating self-demagnetization. With vertical recording increased density actually improves the situation (b).

process is the separation of incident and reflected light. The polarizing beam splitter acts as a plain block for light polarized in one direction, but as a prism for light polarized at right angles. The quarter-wave plate rotates the plane of polarization by 45° .

It consists of a crystal whose refractive index is anisotropic; the principle is similar to that used in structural analysis, where models of engineering components made in clear acrylic are placed under stress and studied with polarized light. Rotation of the plane of polarization is a function of the wavelength, so the monochromatic output of the laser is essential. Light from the laser travels once through the quarter-wave plate on its way to the medium, and once again following reflection from it. Reflected light entering the beam splitter is thus polarized at right angles to the incident light, and the splitter acts as a prism, reflecting the light onto the read sensor assembly.

For writing, the output of the write laser passes straight through the system, and is focused on the medium. What takes place on the medium can be one of several mechanisms shown in Fig. 5. In the ablative process, the laser beam is focused on a thin metal film supported on a substrate. This melts right through the film, and surface tension causes a hole to appear before the metal re-freezes. The most common material proposed for this is tellurium because it offers high density, but it suffers from a number of drawbacks. It is difficult to deposit permanently onto a substrate, and is subject to deterioration caused by oxidation and humidity.

In a different technique the laser beam passes through a very thin film into a plastics substrate where the intense heat causes decomposition to gas, forming a blister in the metal film. Although these

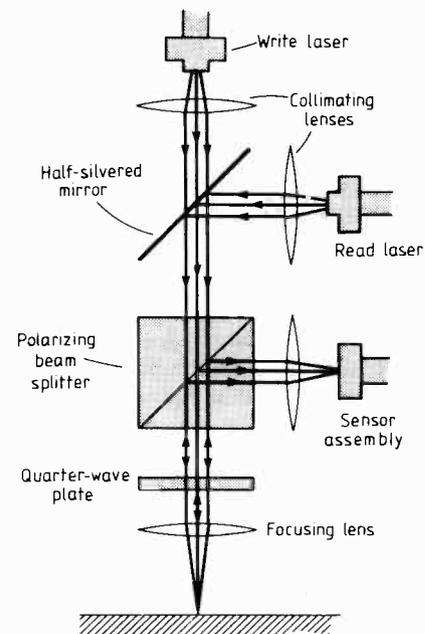


Fig. 4. Components of an optical read/write head, see text for details.

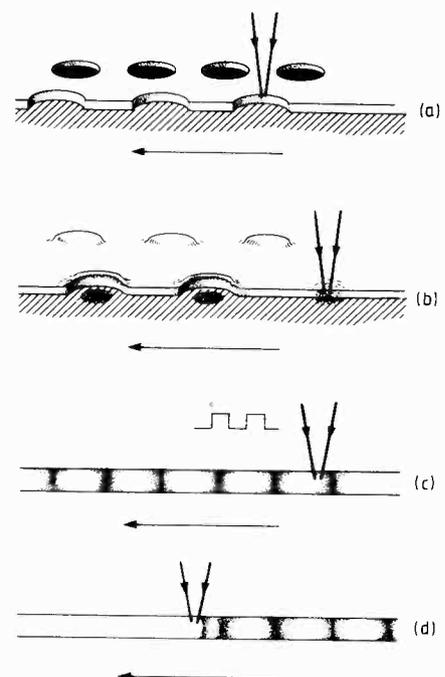


Fig. 5. Three optical writing techniques. In the ablative technique (a) the laser melts holes in a tellurium film. At (b) laser beam decomposes plastics substrate, causing gas pressure which raises thin coating film in a blister. In (c), a possible erasable recording, surface ripples are left where the medium has been partly melted. In the erase process a steady beam melts the track continuously; surface tension smooths out the tracks.

two new techniques permit reading and writing, the last-mentioned process is once and for all. There is no parallel with the ability of the magnetic head to erase and re-write.

Eraseable optical storage exists at the laboratory stage, but it remains to be seen whether it will be marketed. The essentials of the process are to melt part way through the medium only, to prevent evaporation and the formation of holes. A steady erase beam could melt the entire surface of a track, allowing surface tension to smooth out the surface, but it is not inconceivable that a beam switching between two levels might erase and write at the same time. Inherent in the process is a very small displacement of the medium, so that erasure is possible. This will inevitably cause the read-back signals to be small — another problem to be overcome.

An optical disc drive requires many of the same components as a magnetic drive; spindle drive, read/write encoding logic, and some form of positioner are common to both. However, magnetic heads need to fly close to the medium to read short-wavelength signals, and they are designed to follow disc warps. As light can be focused, the optical head can be a short distance from the medium. This eliminates the possibility of head crashes caused by contamination, but it also prevents the head following warps and an active focus system is necessary.

This is commonly provided by using the principle of astigmatism. If a cylindrical lens is interposed between the prism and the sensor, the image of the round read-laser spot on the sensor will only be circular at the point of correct focus. Fig. 6 shows that the shape of the image becomes an ellipse on leaving the focal plane, with the angle of the major axis being determined by the direction of movement. If the image falls on a four-quadrant sensor, the four outputs can be summed and differenced to produce a focus error signal, used to drive an actuator on the focus lens.

For high-density magnetic recording, the track-following signals come from the disc itself (part 5) and this remains true for optical discs. Whereas in a magnetic drive the positioner and head have to move precisely to follow the track, the laser head performs fine tracking by steering the beam and the positioner is only used for coarse positioning. Fig. 7 shows the two major approaches to fine tracking. Where only a single platter is used fine tracking can be done by shifting the lens laterally, Fig. 7(a), which must be fast enough to follow disc run out; a moving coil actuator is one solution. At Fig. 7(b), fine tracking is done by rotating a mirror to reduce the height of the assembly. (The assembly can scan two surfaces by turning the mirror 90°.) In both cases focus is by moving a lens along the axis of the beam. In case (a) it can be the same lens as the tracking lens, in which case it will need to be driven in two axes. Control signals for fine tracking are derived from disc patterns and are, in the broadest sense, optical analogues of magnetic servo-head techniques.

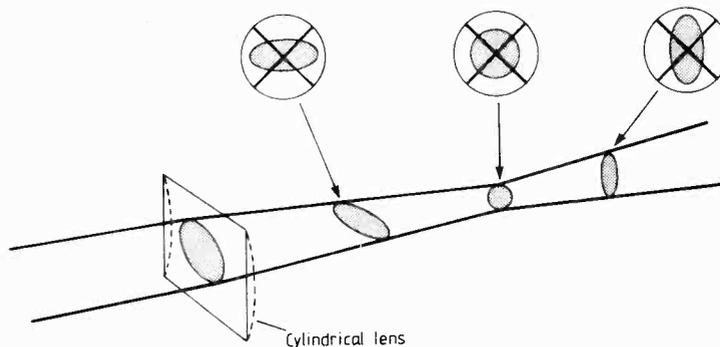
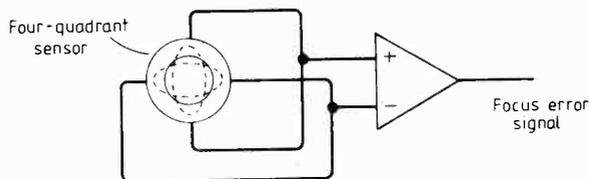


Fig. 6. Use of a cylindrical lens prevents a point focus and results in an elliptical image, circular at one point only. Horizontal ellipse causes more light to fall on left and right sensor quadrants, vertical ellipse favours upper and lower quadrants, and a differential amplifier provides focus error signal. Four quadrants are summed for read signal output.

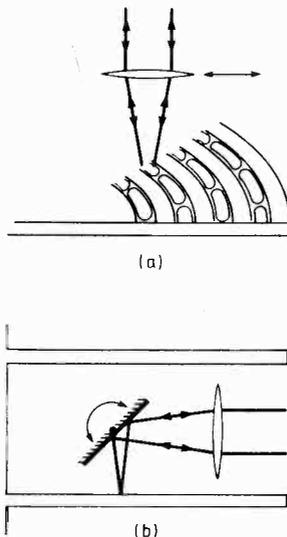


Fig. 7. Where space is no problem, fine track-following can be done by lateral lens shift (a). More compact arrangement uses a rocking mirror as shown at (b).

A simple arrangement is shown in Fig. 8 — here a diffraction grating creates two side beams which follow different paths through the system to fall on different sensors. Modulation of the side beams changes differentially with tracking error, allowing the generation of a feedback signal. A disadvantage of this method is that a space has to be left between tracks that is slightly greater than the track width, which wastes space on the medium. A more complex approach is shown in Fig. 9.

A great drawback of magnetic recording from the point of view of duplication is that every copy has to be individually recorded. One of the reasons why vinyl discs have survived the coming of the compact cassette is that they can be duplicated by stamping. Both video and audio optical discs are now available where the read mechanism is by laser, as

described. In the case of video discs, the length of the holes or pits in the disc is modulated directly by the programme waveform, whereas in audio discs, the sound waveform is digitized and encoded using similar techniques to those on the latest magnetic discs. None of these laser players can record — they are intended solely for playing recorded discs.

The optical discs are duplicated by electroplating a master to form a die. The master can be made by writing on photoresist with a low-power laser and developing to leave areas of hardened resist in relief, or by direct writing with a high-power laser. The resulting dies are used to stamp plastic discs which then receive a thick electroplated metal coat and a transparent protective layer. The medium is thus sandwiched between plastics and is very resistant to damage.

Magnetic and optical recording compared

It is too early to be able to write definitively on this subject as so much research remains to be done. Proponents of optical recording claim that magnetic discs are further along their learning curve than optical ones, and that future research in the field will follow the law of diminishing returns. The fact that the magnetic head has to be very close to the medium is also held to be a drawback, as great cleanliness is required.

Proponents of magnetic recording claim that combinations of metal media, thin-film heads and vertical recording will enable them to match the densities claimed for optical recording. It has been suggested that diffraction may set a limit to the density of optical discs from which magnetic discs will not suffer. Criticism can also be directed at the high raw error rates of current optical devices, and the inability to erase in most of them.

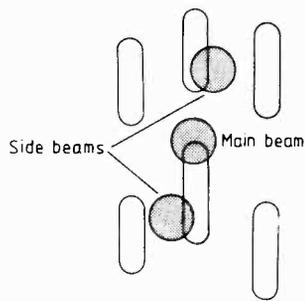


Fig. 8. Simple tracking system uses two auxiliary beams each side of the reading beam. Track misalignment causes the two side beam signals to change in amplitude differentially.


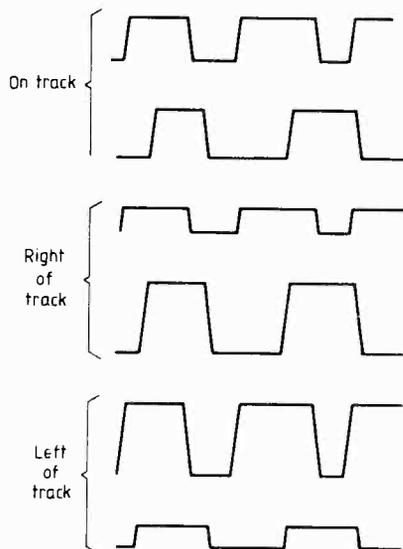


Fig. 9. A possible embedded servo technique for optical discs uses one beam for track following. Two beams spaced at $\frac{1}{2}$ track apart could generate two-phase signal to count track crossings. In the three examples shown, notice the effect of position error on the second part of the pulse waveform. (Compare with article on servo surface drives, August 1982 issue.)

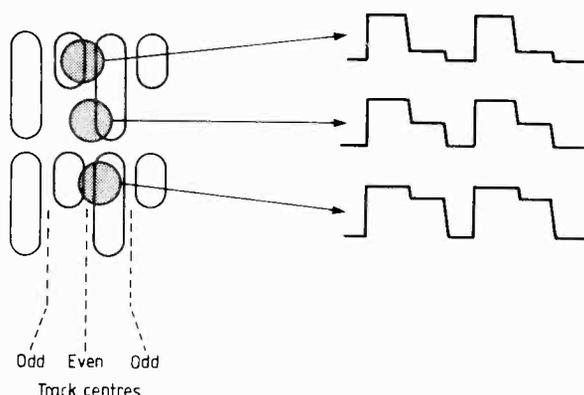

The truth lies somewhere between the extremes of this clamour. In my view, the optical and magnetic data discs are complementary rather than competitive. In large-scale data processing, there will be no significant departure from the well-proven combination of multiprogramming processor and swapping disc, as the emerging magnetic technologies will produce hard-disc drives offering low cost per bit and retaining the ability to erase. For backup and archival purposes, the write-once characteristic of optical discs is not a problem, and their resistance to contamination makes them ideal where the medium is to be removed from the drive. This may well have an impact on magnetic tape storage.

Possibly the greatest potential for optical discs lies not in the existing data processing fields, but in new applications for which their characteristics are better suited. These include electronic filing cabinets, where images of documents are stored as disc data. In these applications, non-eraseability is an asset rather than a drawback.

One far reaching consequence of the latest generation of computer equipment is its impact on maintenance philosophy. Most of the current units incorporate microdiagnostic hardware and firmware in such a way that in the event of a hardware malfunction a code is displayed that

specifies the faulty assembly to be replaced. It is no longer necessary to know how these units work in order to repair them. In normal disc drive operation, microprocessors eliminate the need to make manual adjustments. In some current disc drives, the critical access time adjustment is performed automatically every "power-up". Hard-disc technology eliminated head alignment problems for non-exchangeable drives, but now a combination of embedded servo drives and intelligent controller eliminates head alignment in exchangeable pack drives, and in fact enhances compatibility between drives.

This is, of course, good news for the computer user, as reliability will be increased and repair costs will be reduced in line with falling hardware cost. What is also implied is that the requirement for engineers who have both the mechanical and electronic skills necessary to repair hardware of the last generation has simply gone away, along with the requirement to provide in-depth training. A process of de-skilling is well under way in computer maintenance. The next generation of computer technicians is already being recruited from television and domestic appliance repairers — a sobering thought when it is remembered that the first stored-program computer ran as recently as 1949.

WW

Next month

Viewdata display module, linked to a home computer, allows a colour tv to receive and display Prestel and teletext. Full design and construction information, including a printed-board design, is presented.

Digital tape timer is a replacement for the mechanical counter used in tape recorders. Accuracy is around one part per thousand on a 10½ in. reel. The tape itself drives optical sensors, which also ensure that the reading is maintained in both forward and reverse directions.

Amateur satellite tracking system, controlled by a Pet micro, will continuously adjust aerial altitude and azimuth to track Oscar 7, Oscar 8, Tiros-N or NOAA-6 by means of rotators.

Single-chip microcontrollers with program in eeprom are now available cheaply. Program development can therefore be carried out using an eeprom emulator; this article describes a circuit to enable this to be done.

On sale March 16

LETTERS

AMATEURS AND CABLE

As Pat Hawkey (G3VA) has mentioned on more than one occasion the question of cable tv being installed for tv links and its possible interference to the amateur bands between 5MHz and above is looming.

With the ratification of the R.F.I. Bill S.929 last September it would appear that 'we' as the amateur population are dragging our feet somewhat.

Hopefully, as I ask you to publish these few words, someone somewhere, both in industry and the amateur world, here in the UK at least, will take note and realise that if cable tv is to progress without (?) problems then parties must get together quickly. It not only affects the amateur and industry at large but in some cases the short-wave and domestic listener/viewer.

Bearing in mind the radio amateurs throughout the world form a substantial part of this balance of payments of varying countries and after all not every firm depends on MoD contracts.


The naive idea that amateurs do not count according to some professional engineers must be looked at in the light of future and past developments in both radio and tv. In short, what works in theory doesn't always work in practice so consequently the need for liaison between interested parties, notably the RSGB on the one hand and industry and the Home office on the other. The RSGB and others are aware of this problem regarding cable tv and it should not be allowed to drift. I thank you in anticipation of publication as the subject does affect all radio amateurs and listeners alike.

J.A. Holmes
London E4

CONSTRUCTING AN ELLIPSE

I required a simple method that would give a visual picture of the specified ellipse; the distance between its foci, F_1 and F_2 ; and the area of the ellipse.

Imagine the ellipse's auxiliary circle, shown dotted, (see diagram), to rotate about diameter $X-X$. It would project an infinity of ellipses each having a common major axis, with corresponding minor axes diminishing to 0, as it resolves into a straight line on $X-X$. The relative foci, F_1 , F_2 ; diverge from the centre, finally reaching the extremities of the major axis $X-X$. The sine of the angle of inclination a to project a specified ellipse = minor axis/major axis = angle a , and, if this angle is projected on to the auxiliary circle, passing through its centre, similar to a side projection to itself, $A-B$, then

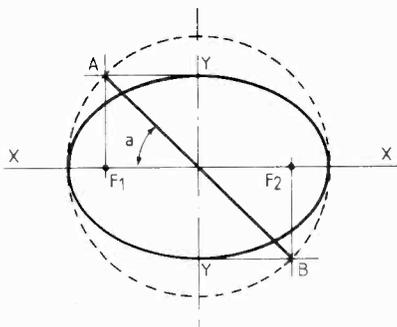

perpendiculars are erected from A and B to meet $X-X$, these points will meet it at F_1 and F_2 , their accurate distance apart = major axis $\times \cos "a"$. To find the area of the ellipse I multiply the area of the auxiliary circle by $\sin a$.

L.G. Miller
Lydney
Glos.

THE NEW BUREAUCRACY

When Dr Catt produced the first of his series of articles attacking me and my colleagues, I tended to dismiss them as the ravings of a confused mind, even when they were printed as leading articles in a journal which I respect. Could this outpouring be from the same office which produced "Microchips and megadeaths," I wondered? Now, after the third attack, it is time to speak.

Like Dr Catt, I have worked for computer manufacturers and computer users for the past twenty years, but in software. Like him, I have been confounded by bureaucratic interference and bloody-mindedness, but the strength of his feeling is truly amazing. What a pity he turns his feeling against his colleagues.

In short, it is facile in the extreme to argue that programmers, whose job it is to convert a statement of requirements to a working system on a given set of hardware, can be blamed for the adoption, retention or, indeed for any influential action at all when it comes to computer hardware. We use what is available, that is all.

To those of us in the real world - implementing working systems - the idea of us "infiltrating and subverting" the process of hardware design, while attractive, is unreal. None of us likes the von Neumann architecture - we spend our lives trying to circumvent it. Indeed, when I showed his article on Wafer-Scale Integration to some of my colleagues, there was universal interest. As an aside, our Systems Manager would like to find these systems programmers who are politically adept, for they would be rare beasts indeed.

It seems that we have given offence because we have neither science nor technology. I must confess that is some months since I integrated my last expression (compound interest calculation, as it happens), and I agreed that university courses are of little relevance to the practising programmer. But my craft is not to blame for that, and the universal requirement for experience is a good illustration that the industry is being condemned by the action of a few. My Oxford dictionary, incidentally, relates the word "technology" to grammar and a study of the techniques of art, or the arts. Our use of the expression "Software Engineering" was devised as a tribute to our hardware colleagues, and a good pointer to the way we had to go. It is churlish to refute such a tribute because, we have not yet completed the journey.

Finally, if Dr Catt has difficulty in finding software people to design and develop his software (should he concede that he needs it), then he need look no further. I am a consultant with a background similar to his, with experience in the fields he requires. My only qualms in volunteering to work with him is that, although I understand him, will he understand me?

D. W. Scott
Nettlestead Green
Kent

NO SUCH THING AS A MAGNETIC FIELD

I have always been pleased and surprised by *Wireless World's* editorial policy which seems to take a far wider view of the world than the purely technical, electronic one.

Over the years we have frequently seen letters, articles and editorials which enrich the subject matter of *Wireless World* on such topics as relativity, fundamental electronic philosophy and the morality of contributing to warfare. A very healthy and refreshing state of affairs.

May I be permitted to make a small contribution. When learning about electricity at school, it suddenly struck me rather forcibly that there can be no such thing as a magnetic field. Some readers will no doubt find this assertion very curious as we measure, use and describe magnetic fields mathematically. We can even feel them if we take hold of a couple of magnets, and by using rather specialised techniques we can make them visible.

The simple fact about the magnetic field however, is that it has no separate existence; all the techniques for measurement or detection of the magnetic field have common features and none can demonstrate or identify the separate existence of the thing we call a magnetic field.

When, for example, we "detect" a "magnetic field" between wires in which a current flows, the only factor we can be reasonably certain of is that we are bringing into proximity moving electric charges. There is no proof of a "field" and nothing to be dignified by a special name "magnetic". We simply have a force between moving electrons.

When we bring two magnets together, the force between them is not due to any invisible etherial field, but is due to the proximity of moving electric charges, the electrons confined to orbits (or orbitals of the Schrödinger wave equation). All the force effects between magnetic (ferro, para or diamagnetic) materials can be explained in terms of moving electrons.

What other "proofs" or "measurements" of "magnetic fields" exist? The Hall effect springs to mind. Here again, we are simply looking at a force between moving electrons, which is either allowed to set up a transverse potential gradient, or a small transverse current in a conducting medium when another medium containing moving electrons is brought nearby. Once again, all we have is a force between moving sets of electrons.

These common features are found in any test or experiment concerning the "magnetic field", whether we consider electron beam deflection in a c.r.t., electro-magnetic induction, compass needles or whatever.

The history of science is littered with examples of concepts which at best summarize the truth, and at worst hinder the understanding of the true state of affairs, and as Bertrand Russell said, once people believe a thing really must be so, it takes a tremendous weight of evidence to change their minds. Examples are "phlogiston", a gas once supposed by chemists to be given out during any combustion, "caloric", the fluid responsible for heat, and the ether, once supposed essential to the transmission of electromagnetic waves. The trouble with the foregoing concepts is a natural tendency to believe that if a special name exists for a concept we know all about it. In fact we know next to nothing about this force between moving electrons, just its size and existence are known.

How it arises and why are a mystery which the mere name "magnetism" does nothing to explain.

It would be rather perverse to attempt to tear down a cornerstone of electromagnetic beliefs without attempting to make some progress. Perhaps it would be useful to clarify the situation by discarding all the terms containing the "magnetic" root and use the following.

Electrokinetic force – the force between moving electrons (formerly known as magnetism).

Electrostatic force – as before, the force between stationary charges.

We could manage very nicely with just these two. It would be useful to dispense with the antiquated term "field" (does it originate somewhere in our agrarian past?) and write all the equations in terms of forces instead of invoking this roundabout complication.

It is to be hoped that by clarifying the situation in these ways, more would call into question the fundamental nature of the forces between electrons at rest and in movement and some real progress could be made.

I hope there may be something of originality and controversy in this, I have not seen such ideas expressed in your columns before (equally, I have not read every issue of *Wireless World*). If you would like to publish any of this letter I would be very pleased and grateful. In the meantime, I shall continue to look forward to the "questioning" letters and articles I have come to expect as a part of your excellent publication.

A. R. Churchley
SARA Krd
Warrington

ELECTROMAGNETIC DOPPLER

I have been unable to find the answer to what is superficially a straightforward question. What is the mechanism by which Doppler shift is produced in the case of electromagnetic waves?

In acoustics, when two observers in relative motion observe the same sound wave they measure different frequencies due to the simple fact that the wave is passing each at a different relative velocity. If V_{R1} and V_{R2} represent the velocities of observers 1 and 2 relative to the wave then

$$\frac{f_1 \lambda}{V_{R1}} = \frac{f_2 \lambda}{V_{R2}} \quad (1)$$

$$\text{or } f_1/f_2 = V_{R1}/V_{R2} = (V - V_1)/(V - V_2) \quad (2)$$

Equation (2) is the derivation of the more familiar form of the equation where the relative velocity of wave and observer is expressed in terms of the velocity of propagation in the medium V , and the velocity of the observers relative to the medium v_1 and v_2 .

The e.m. Doppler shift equation (3) can be verified experimentally to a high degree of accuracy.

$$\frac{f_o}{f_s} = \frac{C - V}{C} \quad (3)$$

Now if, as I have seen stated, "similar principles apply" one can deduce two things: that

the velocity of light relative to the observer is $c-v$ which is in direct opposition to the postulate of relativity which insists that the velocity of light is always c independent of relative motion between source and observer; that the velocity of light is constant relative to the source which would provide an adequate explanation of the null result of the Michelson Morley experiment and would support the corpuscular/photon model of light, photons being "shot" out of matter at constant "muzzle" velocity.

A further piece of evidence supporting (2) is that of star aberration. In 1729 Bradley showed that the apparent direction of a star is actually the vector sum of the velocity of the light from the star and that of the earth.

It would seem that there is at least some evidence to support the view that the velocity of light is constant with respect to the source and that this would resolve the dilemma presented to physics by the Michelson Morley experiment. As physics has not accepted this path one can logically assume that there must be overwhelming evidence to the contrary which supports the postulate that the velocity of light is always constant independent of the velocity of the source. I have looked in vain for such evidence, most books seem to manage without any: the only evidence which I have found is de Sitters observation of double stars. If the whole of modern physics is based only on that I think we should all be worried.

The standard technique seems to be to ignore Doppler and aberration, to fudge the evidence in respect of the postulate and dive straight into the mathematics of relativity. From this appear the relativistic Doppler shift equation and aberration equation. Thus having shown that both are embraced by relativity one never has to ask the questions I have raised. Now the relativistic Doppler equation may be written.

$$\frac{f_o}{f_s} = \left(\frac{C - V}{C} \right) \left(\frac{1}{\sqrt{1 - V^2/C^2}} \right)$$

The second term is time dilation which for modest values of v is equal to unity. My question is what is the physical mechanism which produces the first term which appears to be the ratio of two velocities. If the velocity of the wave is the same to both observers there is effectively only one other possible variable and that is time (note distance can be defined as the distance travelled by a light beam in unit time) so that if the first term is not due to a difference in velocity of the wave it must be due to a time difference or time dilation. Both observers observe the same wave. They both observe that it is travelling at the same velocity yet they disagree as to its frequency because their clocks are ticking at a different rate. But whose clock is ticking faster than whose. It depends on which observer is sourcing the beam of light. If both send a beam to the other simultaneously then we get the mathematical absurdity

$$T_A > T_B \text{ and } T_A < T_B$$

This type of "paradox" has been mentioned in *WW* before, but surely either the result must be rejected because it doesn't conform to the laws of mathematics, or the laws of mathematics are wrong, in which case the derivation of the result must be rejected as being based on faulty

mathematical laws.

I would welcome any suggestions as to where I am going wrong.

I have followed Dr Murray's articles with interest but he has lost me on one point. If, as he suggests, light waves are periodic variations in photon density then presumably destructive interference occurs when the peaks in density of one wave 'fill in' the troughs of the other so that the variation in density is zero but the actual density is the combined average density of the two waves. Surely this could be easily checked experimentally as the photo-electric current produced by a dark fringe of an interference pattern should be the same as that of a light fringe. I cannot see either how his model can explain polarization.

Appendix

Double stars

For those unfamiliar with this piece of evidence the idea is that if the velocity of light were constant with respect to the source, then the light from a star in a binary system which is travelling towards us would tend to overtake that from the star going away from us with the result that their observed orbits would seem irregular. De Sitter observed double stars and no orbital irregularity. I have yet to find out when or where these observations took place, the magnitude of the expected irregularity, de Sitter's measurement accuracy, and why he didn't get a Nobel prize for this obviously vital work.


J Kennahugh
Callington
Cornwall

STEREO WIDTH CONTROL

In the article 'Modular preamplifier' Mr J. L. Linsley Hood describes a circuit to blend or separate 2 stereo channels (*WW* Jan, 83 page 47/48, Figs. 20, 21). Although there can be no doubt that these circuits can work satisfactorily, with some minor modifications a combined separate blend circuit is possible – see Fig. 1. As you can see, by adding four extra resistors, just a one-section potentiometer is required, and width control can be turned completely back to mono.

I like to use this opportunity to warn experimenters, who for some reason use bipolar op-amps of the 741 type for audio purposes, that a negative d.c. bias at the output of such op-amps (e.g. a 3k9 resistor from output to minus supply) can reduce crossover distortion at higher frequencies remarkably.

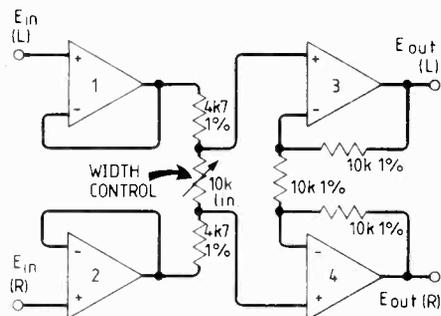P. C. W. Demmer
Amsterdam-O.dorp
Netherlands



ELECTRONIC IGNITION

Users of the electronic ignition published in the March 1982 edition may be interested in an important secondary use for the change-over switch recommended in the article for all electronic systems, in the event of failure.

It is a well-known effect that the contact breaker tends to get dirtier soon with electronic ignition, an effect which is made worse if the distributor capacitor is removed. This results in misfiring and eventual stoppage. However a few minutes running with the change-over switch in the conventional mode every now and then will prevent an accumulation of dirt, which is presumably burnt off by the arcing and sparking that is a normal feature of conventional ignition.

Contamination of the contact breaker can be surprisingly difficult to diagnose unless you know of its effects, and can lead to time wasted in a search for component failure in the electronic ignition.

Rod Cooper
Lichfield
Staffs

FAILURE OF DISTRESS SIGNALS AT SEA

I would like to make a few comments on the letters from Mr Hans P. Faye-Thilesen (*WW* February, 1983).

Whatever the losses in the insulators and wires of an aerial caused by dielectric and induction heating, these are (for a particular frequency) constant and predictable losses, which, as for any electrical machine, are taken into account in any calculation of efficiency, and which *ought* to very much increase with frequency. Losses due to inductive heating of parts of a ship's superstructure, caused by poor siting of aeriels, are probably worse, but not readily measurable.

Some of the "top loaded unipole" aeriels mentioned by Mr Faye-Thilesen are only 10 per cent efficient at 500kHz, according to their manufacturers' data. Even this we are grateful for (and it isn't very good), *when* it is available, but it is not the theoretical aerial efficiency under ideal theoretical conditions that people at sea have been criticizing; it is the total collapse of any efficiency *at all* in bad weather conditions, and there is no denying that it is related to two main factors, namely aerial capacity and insulator leakage. This is experimentally demonstrable by the instant improvement in performance obtainable by parallel connecting several aeriels and washing, shielding and/or reducing numbers of insulators. I could speculate that dielectric heating of water droplets in moist air contributes to the problem, but then it *ought* to be evident at h.f. as well as 500kHz, and it is not. We have no problems with these aeriels at h.f.

For information about the performance of low-powered 500kHz life-boat transmitters, I would refer readers to my letter in *WW* June, 1981, in which I quoted from actual experience. I have, as a matter of routine, regularly tested life-boat radio equipment on board ship. With a 5W transmitter on 500kHz, and 30 feet of wire, six feet above the deck, 40 feet above the water, it is not very difficult to obtain a good signal report from a coast station 25 miles away in daylight hours. I would not agree that this equipment is "useless". I don't know how to keep 60 feet of wire supported from a kite or

balloon in a storm either, but I still wish to have the kite or balloon available for possible use in the calm that follows the storm.

I certainly support Mr Faye-Thilesen's contention that only 500kHz is reliable for DF purposes and that 2182kHz is *absolutely useless*. This was borne out a few years ago in the loss of the German ship Munchen. DF bearings taken on a 2182kHz EPIRB beacon later proved to be wildly inaccurate. No trace of either ship or crew was ever found.

Finally, SOLAS means Safety Of Life At Sea.
John Wiseman
London, E3

THE RIGHT FORMULA

Referring to R. G. Young's letter in the November issue, when Max Bohr was discussing the existence and reality of purely theoretical (abstract) entities, the conclusion reached was that their existence and reality were both unnecessary attributes. From this conclusion one may safely say that materiality diminished to its ultimate stops at Newtonian physics and the molecule. Anything smaller such as concepts of atoms, electrons and nuclear particles reside only in the mind and are devolutions of the physicists' credo and not science. The theories evolved from such conceptual devolutions comprise metaphysics. It is for this reason that 1.1×10^{-14} grams increased mass (1.1×10^{14} was a slip of the pen as was the use of 'velocity' rather than 'motion' in the definition of mass) does not exist.

If there ever was a 'big bang' start to the universe then there must be an absolute still from which the increases in mass may be measured. Einstein denies this absolute still point, hence some absurdities result from his theory, which only partially accounts for phenomena. Hence perhaps one may say that 1.1×10^{-14} grams is a mathematical figment of the imagination and also that it is neither real nor existent.

The mathematics used in science must follow the same laws as the physical phenomena being investigated so that it may be regarded as valid. It is, for example, mathematics which rules that light must be a wave or a particulate phenomenon but not both. It is the physical phenomenon of light which rules that it is both a wave and a particle and therefore scientists ought to get used to thinking this way and cast out some of the imprinted ideas of their earlier days of what exists, what is real, and what can or cannot happen, if they wish to advance in knowledge rather than speculation.

O. Balean
Chatham
Kent

SEEING RED

I have had recently to up-date my rented colour television receiver because of problems as regards replacement spares for the old one which was still performing satisfactorily.

I was immensely impressed with the technological progress which has been made not only as regards the facilities provided but the way in which they can be controlled. No longer does it feel as if I am operating an oil circuit-breaker when I change channels and I am given access to a vast amount of information by courtesy of Teletext. I am moreover given remote control of

all this by the choice of something like 30 different commands over an infra-red link.

Being so impressed, I was perhaps somewhat slow in giving a critical eye to the receiver's main purpose, namely to produce a picture of at least as good quality as that available from the old receiver.

What I found was, that while the pictures were sharp and bright, the colour rendering was not what I might have expected.

It is in the red part of the colour range where I feel most dissatisfaction because what I am shown is a red which is more of an orange hue though some might refer to it as flame colour.

Some well-known objects have a particular colour association and errors in colour rendition in such instances, can be quite disturbing. Grass can be more or less green and sky can vary in its blueness but the colour of a London omnibus and that of a guardsman's uniform is well-remembered in the mind's eye and it is here that errors will be immediately apparent.

Switching to Teletext on the new receiver showed that red was the same hue as obtained in the tv picture and this would seem to show that the modern "red" phosphor has a characteristic rather different from the primary red phosphors of a few years ago. Manufacturers may have seen fit to do this in order to give increased brightness when viewing under conditions of high ambient lighting but if this is the case, a regrettable error is being built in to the modern receiver.

For instance, where a floral display is involved, the inability to portray a pure or primary red could result in flowers being seen with hues quite inappropriate to their species.

Finally, I can admire my receiver as a product of high technology and it produces some very pretty pictures but in the circumstances I have described, I find them unsatisfactory if only because I am no longer allowed to see red.

Gwilym Dann
Chipstead
Surrey

DESIGNING WITH MICROPROCESSORS

It is unfortunate that several errors appear in the 8080 PRINT program in the article by Zissos and Valan (December 1980 issue).

The MVI instruction at location 1003 does not set the zero flag, so a zero length block will not be trapped.

The JNZ instruction at location 1005 should be a JZ.

The JMP instruction at location 1013 jumps to the wrong place, causing an endless loop.

A possible revised program, in Assembler format, appears below:

```
ORG 1000H ; program start
                ; address
LXI H,2040H ; address of first byte
                ; to be printed
MVI A,n ; A=length of block
MOV C,A ; C=length of block
ORA A ; set flags
L3: JZ L1 ; jump to L1 if
                ; count=0
L2: IN 60H ;
RLC ;
JC L2 ; loop if printer not
                ; ready
MOV A,M ; next byte to be
                ; printed
```

LETTERS

OUT 61H ; print
 INX H ; point to next byte
 ; to be printed
 DCR C ; decrement count
 JMP L3

L1: HLT
 Neil Roberts
 Leasco Software Limited
 Maidenhead
 Berkshire

NON-BINARY LOGIC CIRCUITS

I was saddened to see the article by C. W. Ross in the December 1982 issue, page 68. The idea of something other than straight binary surfaces every few years, and then sinks out of sight. The reality is that in around 1960 there was an historic shift from the supremacy of analogue to the supremacy of digital. The full power of binary has been missed during the last 20 years due to the worldwide fixation on the expensive, fully parallel binary. This is very limiting, and makes more plausible the partial resurgence of analogue in the form of Ross's ideas, ternary logic, majority logic, etc., etc.

In 1964 at Motorola (see "A high-speed integrated circuit scratchpad memory," Fall Joint Computer Conference, November 1966), my team delivered a system in which logic pulses 4ns wide (2ns rise time, 2ns flat, 2ns fall time) were used as a matter of course. At that time, an eight-bit byte could be delivered as a routine matter in serial form down one single wire (plus 0V return) in 32ns, a 16-bit word in 64ns. Today, 20 years later, we could probably go 10 times faster if we tried, delivering a 16-bit word in serial form down one wire (plus 0V return) in 6.4ns. (In fact, for all the ballyhoo about increasing speed, we have not tried at all to increase speed during the last 20 years!)

Serial working would reduce the cost and increase the reliability of present-day microprocessors and rams, drastically reducing the number of legs on the chip, the number of interconnecting leads, and the chip d.i.p. size. It would also drastically reduce the cost of standard buses. [In 1964, signals starting on one board, transferring to a mother board, and then transferring back to another daughter board, retained their fast (2ns) rise and fall times.]

Fixation on fully parallel working shows how this crazy industry can ignore the strongest financial imperatives. This is because of the extreme youth of the people in the industry. They learn about what should be temporary phases in the industry and assume that it was always thus and will always be thus. In fact, serial working was the norm until around 1960. Today, you are not allowed to design serial working into a digital system. (This includes a ban on serial memory.) How this fixation can hold out against the present alleged trend of computer linking up with a fully serial industry, telecom, I do not understand. It proves the strength of a fixation, how it can stand firm against all odds, including strong financial pressures.

Fully parallel working, with its concomitant complex failure (breakdown) modes, has spawned the growth of the very complex, expensive logic analyser industry, and massively forced up the complexity and rate per hour of system repair. By contrast, a serial system can be analysed using a normal oscilloscope. The bits lay themselves out along the trace, and failures are easy to find because they are catastrophic — the whole word disappears.

Ivor Catt
 St Alans
 Herts

MODERN PHYSICS

Congratulations to Wireless World for providing publication for Dr Murray's series. To find such an open-minded and intelligent discussion in a respected journal is today exceedingly rare.

Modern thinkers have become so entrapped in preconceived notions that their power of detached observation has almost entirely disappeared. To illustrate, it has never been explained *why* an electron should orbit the nucleus of an atom. Surely, if an electron and a proton experience a mutual attraction they should simply move together and unite; there is nothing to suggest that any sort of rotational motion is either necessary or possible. The fact of the matter, and one that is becoming increasingly obvious to many thoughtful persons, is that Nature does not consist of the attraction or repulsion of *two* opposing principles, but is formed by the interplay of *three* mutually interdependent principles.

Neither the electric, nor the magnetic, nor the gravitational forces exist in reality; they are merely concepts used to explain observed phenomena. An electron possesses the single property of ever-increasing motion; a proton possesses the tendency to absolute stillness; the third principle that seeks to unite the other two is as yet un-named, but determines the phenomena which our theories clumsily attempt to explain. And this view is not without historic precedent.

Although it is reassuring to assume that men of antiquity were less intelligent than we are today, this assumption is not supported by investigation. The Bhagavad Gita, an ancient text, states that Nature is formed from three 'Gunas' or principles, referred to as inertia, motion, and harmony; even Christianity insists that God is a trinity. When scientists learn to interpret their observations as being the interplay of three principles and not two, they will not only have re-established a teaching that is thousands of years old, but will be well on the way to a truly scientific understanding of the Universe, instead of a merely mechanistic one. Einstein's famous equation, $E=mc^2$, is a relationship between three concepts; mass, space, and time, and simply states that the tendency to infinite motion reaches an upper limit established by the balance between the principles. It does *not* state, as so many suppose, that "Nothing can travel faster than light". If it be re-written in the form $c^2=E/m$, then it is obvious that the limiting velocity relationship between three concepts; mass, space, and time, and simply states that the tendency to infinite motion reaches an upper limit established by the balance between the principles. It does *not* state, as so many suppose, that "Nothing can travel faster than light". If it be re-written in the form $c^2=E/m$, then it is obvious that the limiting velocity is determined by the ratio between 'energy' and 'matter', and that where this ratio is low, as in a piece of glass, the limiting velocity is lower than the 'speed of light', and where the ratio is high, as in interstellar space, the limiting velocity is higher.

I hope that this letter, the first I have been encouraged to write to any journal, serves to stimulate vital discussion on ideas that are very much in need of a thorough research and restatement.

P. Craig
 Wellington
 New Zealand

ICE Analogue Handheld Multimeters

Microtest 80
 Sensitivity DC 20K Ω /V
 AC 4K Ω /V
 Accuracy 2% fsd
 DC volts 100mV — 1000V
 AC volts 1.5V — 1000V
 DC amps 50 μ A — 5A
 AC amps 250 μ A — 2.5A
 Ohms 1 Ω — 5M Ω
 dB +6 — +62dB
 Capacitance 25 μ F — 25,000 μ F
£16.60



Supertester 680G — 48 ranges
 (Additional functions to previous product)
 AC volts to 2500V.
 Ohms 0.1 Ω — 100M Ω . dB from -10 to +70dB.
 Frequency up to 5KHz.
£24.50

Supertester 680R — 80 ranges
 (Additional functions to previous product)
 DC volts to 2000V. DC current to 10A. AC current to 5A. dB from -24 to +70dB.
 Accuracy DC 1% fsd
 AC 2% fsd.
£32.00

Full Supporting accessories available.

Our distribution division now supplies Electronic Test and Measuring Instruments from Philips, Fluke, Hameg and ICE. Electronic Brokers Ltd, a company with many years excellent service to the industry, offer full technical support and demonstration facilities on the premises. All orders are despatched promptly from stock. Contact us for further information.
 (24 hour telephone answering service).

KE Handheld and Bench/Portable DMM's

- 8022B** — Handheld DMM capabilities:-
 Digit Resolution
 Bandwidth True RMS
 100KHz
 Continuity (audible & visual)
 Bm, Relative dB
 Frequency to 200KHz
 Relative Reference
 Autoranging Megohms
 Conductance
 Diode Test
 Self Diagnostics
 Basic DC accuracy 0.04%
£275.00



Full Product range:-

- 8022B 3½ digit handheld DMM £95.00
- 8021B 3½ digit handheld DMM, with audio continuity £105.00
- 8020B 3½ digit handheld DMM, with conductance ranges £135.00
- 8024B 3½ digit handheld DMM, with enhanced functions £165.00
- 8010A 3½ digit bench/portable, 10A range (mains pwr) £185.00
- 8010A-01 Rechargeable Ni-Cd battery £215.00
- 8012A 3½ digit bench/portable, low ohm version (mains pwr) £245.00
- 8012A-01 Rechargeable Ni-Cd battery option £270.00
- 8050A 4½ digit bench/portable DMM (mains pwr) £275.00
- 8050A-01 Rechargeable Ni-Cd battery option £305.00
- 8060A 4½ digit handheld multi-function DMM £275.00
- 8062A 4½ digit handheld DMM £210.00

Full Supporting accessories available

Philips Electronic Test & Measuring Equipment

PM 3217 Oscilloscope



£880.00

Full Product range:-

- PM2517X DMM — portable 4 digit, autoranging £149
- PM2521 DMC — bench/portable 4½ digit, autoranging £358
- PM3207 Oscilloscope, 15MHz, 5mV/div., dual trace with TV triggering £358
- PM3215 Oscilloscope, 50MHz, 2mV/div. General purpose £675
- PM3217 Oscilloscope, 50MHz, 2mV/div., as PM3215 plus delayed time base £880
- PM3219 Oscilloscope, 50MHz, 2mV/div., dual trace, storage, delayed sweep, alternate time base £2225
- PM3254 Oscilloscope, 75MHz, 2mV/div., dual trace — ruggedized portable £990
- PM3256 Oscilloscope — as PM3254, plus delayed sweep and alternate time base £1075
- PM5107 Function Generator — sine, square, wave, low distortion 10Hz — 100KHz. £275
- PM5131 Function Generator — sine, square, triangle, TTL output 0.1Hz — 2MHz £349
- PM5132 Function Generator — as PM5131, plus pos. and neg. pulses, adjustable duty cycle £525
- PM5501 Pattern Generator — 5 different PAL patterns for colour and black/white TV £285
- PM55191 Pattern Generator — 20 combination PAL patterns, electronic tuning £725
- PM5705 Pulse Generator, 0.1Hz — 10MHz, 10nS, general purpose £425
- PM5712 Pulse Generator, 1Hz — 50MHz, 4nS, extensive facilities £725
- PM6667/01 Automatic Counter, 7 digit, 10Hz — 120MHz, high resolution £248
- PM6668/01 Automatic Counter, 7 digit, 10Hz — 1GHz, high resolution £375
- PM6668/02 Higher stability version of above £496

HAMEG Oscilloscopes

- HM 705 — Oscilloscope**
 DC to 70MHz
 Dual Trace
 Sensitivity 2mV — 20V/cm
 Timebase 5nS — 2.5S/cm
 (x 10 expansion + variable)
 Add and invert mode
 X — Y display
 Trigger — CH1, CH2, alt 1 & 2,
 line or external
 Sweep Delay 100nS — 0.1S
 Z Modulation
£580.00



Full Product range:-

- HM103 Single trace 10MHz 2mV/cm component tester £154.00
- HM203-3 Dual trace 20MHz 5mV/cm £220.00
- HM203-4 2mV/cm algebraic add With long persistence CRT £240.00
- HM203-4N Dual trace 20MHz 2mV/cm sweep delay component tester £265.00
- HM204 With long persistence CRT £365.00
- HM204-N Dual trace 20MHz 2mV/cm sweep delay component tester £390.00
- HM705-N With long persistence CRT £580.00
- HM705 With long persistence CRT £620.00

Supporting accessories available

All prices exclude VAT and delivery

Distributed by Electronic Brokers



Electronic Brokers Limited 61/65 Kings Cross Road
 London WC1X 9LN Tel: 01-833 1166 Telex 298694 Elebro G

WWW - 201 FOR FURTHER DETAILS

NOW in Birmingham – the centre of Industrial Britain . . .

THE Midland Computer Fair

Personal computers
Home computing
Small business systems

Bingley Hall, Birmingham.
April 28-30, 1983

Sponsored by **Practical Computing** and **YOUR COMPUTER**

This exhibition is the ideal showcase for companies who need to demonstrate their products to the fast expanding market for home and personal computers, small business systems and associated software. When you consider that the markets for personal computers are regional and that Birmingham has a developing computer awareness with a great deal of computer expertise in the area, you'll appreciate the need for The Midland Computer Fair. The public has already demonstrated its appreciation of The Computer Fair in London by sheer volume of numbers. We know the success will continue in Birmingham.

Personal computers are part of everyday life.

Make Sure Your Computer Products And Services Are Seen At The Midland Computer Fair.

For the full story contact the Exhibitions Manager,
The Midland Computer Fair, IPC Exhibitions Ltd,
Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ.



Please contact me with further information about exhibiting at
The Midland Computer Fair.

Name _____

Position in Company _____

Company _____

Address _____ Tel _____

THE
**Midland
Computer
Fair**

Seeing the light?

Around 30 000 homes in a San Francisco suburb are to be wired with a 50:50 coaxial/optical cable tv network costing only 3% more than an entirely coaxial system by Commco Cable TV of Texas who have recently formed an Anglo-American partnership. Using both aerial and underground cable routes, this \$10m switched star system has optical fibre trunk-to-house links carrying only one signal at a time so tv-converter costs are possibly 10 times lower than they would be with a tree and branch network and switching circuits, being outside the home are said to be cheaper to maintain. Labour-intensive hole digging is avoided as the optical-fibre cables are thin enough to pass through existing ducts.

Commco's partnership with Cable and Wireless and Charterhouse Group plc, called Cable TV Construction, will start its life in the Birmingham area involved with planning and consultancy contracts. As the name implies, the company also plans to install networks in the future.

A second recent Anglo-American partnership, Cabletime, plans to offer a cheap cable tv system in the UK by the end of the year. Their system, a star network combining typically 85% optical-fibre cable with 15% coaxial, is based on one designed in America mainly for use with blocks of flats, each with their own distribution unit. But David Mann, managing director of Cabletime, emphasises "the system that we plan to offer in the UK is not the same as its US counterpart. Modifications make the switching units and cable more suitable for outdoor use and we are upgrading the system to comply with PAL requirements, probable UK standards on the number of channels for each home, and satellite broadcast interfaces. The network's final form will depend on the requirements yet to be decided upon. All our equipment is to be made in the UK." One arm of the company, Cabletime Installations, will manufacture robots for laying cables in sewers. Times Fiber Communications of America who formed Cabletime together with Britain's UEI group provided the system for Commco's San Francisco installation.

"If cable tv is to start soon, a system such as ours is the answer - if a wholly wideband optical-fibre system has to be used, Britain will have to wait another 10 years," adds Mr Mann. Many network-cost estimates for the UK are high, since they are based on prices for communications systems using high-grade optical-fibre cables carrying fast signals over long distances. A star-switched system such as the one proposed by Cabletime would be far cheaper than one using only optical

fibres and meet requirements so far outlined by the government for an initial 20-year licence (tree and branch systems will probably receive 12-year licences). The government is likely to insist that cables be laid in ducts, paving the way for future improvements.

In January, an agreement providing for the formation of a joint venture company in the UK - Plessey Scientific-Atlanta Ltd - was announced by Plessey's chief executive, Sir John Clark. The new company is to "exploit developing business opportunities for satellite and cable communications in Western Europe". In Sir John's words, "With the joint resources of our two companies, we shall be addressing the European satellite communications market which is set to take off with the launch of the ECS1 satellite during 1983. Furthermore, it is clear that many govern-

ments in Europe, including in particular our own, are seeking to provide as rapidly as possible a national wide-band network financed from the public's appetite for tv entertainment." A second agreement between the two companies gives Scientific Atlanta Inc. access to Plessey's v.l.s.i., microwave device and optical-fibre technologies.

Scientific Atlanta of Georgia in the US opened up a catalogue service called Cablemart in November of 1982 that illustrates the type of business that cable tv has become in America. "Cablemart promises 24-hour order processing of hundreds of cable tv products listed in its catalogue . . . customers can call in orders using a toll-free telephone number . . . to hasten delivery, in-stock items will be shipped within 24 hours," reads the description.

Among other companies involved with cable tv are GEC, who are to manufacture hardware; Racal, who have combined with Oak Industries of America to make both equipment and programmes (see News, October 1982), and Thorn, who have set

Wideband cable systems

Terms of reference used by the DoI technical working group chaired by Dr E. N. Eden to provide draft British Standards for wideband cable systems read as follows:

"To consider the specifications necessary for the design and operation of wideband cable systems, in particular as respects the needs for cable systems

- to be compatible with appropriate technical and service features of the networks operated by BT and Mercury
- to have the capacity to provide interactive services
- to comply with the requirements for the prevention of electro-magnetic interference laid down by the UK, the EC and the international specifications of the International Special Committee on Radio Interference (CIS PR)
- to have some reserve capacity for which standards will be specified in the future (the level of spurious signals for other services that may appear should be specified)

and for existing tv receivers used for uhf reception to be capable of being linked to the system (the properties of receivers with other interface ports and of receivers equipped to take adaptors for the reception of transmissions from satellites of direct broadcasting will also need to be taken into account).

In considering these specifications the working group should take into account all the various types of services, including switched interactive services, that it can envisage as being provided in due course by wideband cable systems, with the exception of voice telephony, and where appropriate British Standards do not exist it is asked to draft

them. These standards should encompass the principal alternative configurations and technologies and the working group may therefore find it necessary to produce alternative standards for particular services.

The principal services that the Department can anticipate as being among the potential capability of wideband cable systems are

- downstream video channels, where the Department wishes the working group to look towards 30 channels each with its associated sound and teletext data signals (a proportion of these should be capable of handling the features included in the standards for direct broadcasting by satellite, where appropriate with any necessary transcoding)
- audio channels
- at least one return video channel, with an associated sound capability, which may be used for a range of services
- two-way data channels, some of which should have a signalling rate of 80kbit/s.

In the case of the latter two services the Department would wish the working group to produce standards that allow for a number of subscribers to have simultaneous access to those two-way services including viewphone.

The working group is asked to produce drafts of the appropriate standards on or about 1 March 1983 in such a form, using the guidance of BS0:1981 wherever possible, that the British Standards Institution may issue them for public consultation. An interim progress report should be submitted by 1 October, 1982."

up a new company called Thorn EMI Cable Television Services to coordinate their various interests in c.tv. These interests include receiver and decoder design, the preparation of programme material and studio equipment. Operating experience from Radio Rentals Cable Television, who are currently managing services in Swindon and Medway, will also be used by CTS.

BT and its unions are opposed to the fast turnover, low-bandwidth approach and would rather that the UK embarked on a long-term project to provide a high-bandwidth national network with the potential to supply demands well into the future. There is a chance that independent and incompatible services could be dotted about the country if a free-for-all is allowed. BT has the experience and resources to lay such a network but their role in cable tv is not yet clear.

Whether cheap hybrid systems may be applied in the UK hangs on requirements yet to be decided. A pending government White Paper discussing legislation to ena-

ble cable tv authorities to be set up, franchises, etc., in response to the Hunt report and results of the Eden inquiry due early in March are important factors. The Eden inquiry, which will be presented to BSI, will include draft technical specifications for the type of service to be provided (see Wideband cable systems).

An attractive system is only the first hurdle – given the organ, providers must offer a viable service. UK trials have shown that American material can be very expensive and feature-film channels could run into difficulties as under 150 English-language films are produced each year (excluding Indian films). Redifusion's Starview film-channel service (see News, November 1981) covers a potential 56 000 viewers in five towns but according to recent figures only 9 000 of these have subscribed. In Hull, 22% of the potential audience use Starview whereas in Reading, only 6% have taken the service (these figures represent the highest and lowest percentages for the five towns).

UK robot plant expands

A UK company is to develop a new robot and supply western Europe with its parent company's existing range as a result of a jointly funded £10m investment plan. Creating more than 250 jobs, Kenneth Baker, Minister for Information Technology, said that the project "clearly gives the lie to any belief that robots simply take away jobs". The company concerned, Unimation Ltd, and its US parent are to provide £6.5m towards the investment and financial support from the British Technology Group and the DoI yet to be finalised is expected to provide the remainder.

Announcing the plans, Mr Baker said: "The Unimation project is a major step forward in the government's policy of encouraging the establishment of Britain as a major robot supplier . . . the adoption of robots and other advanced manufacturing

technology is not only vital to maintain our competitiveness in world markets and hence safeguard existing jobs, it can create new ones as well." Unimation's European base in Telford currently employs around 120 people.

Part of the investment will be used to set up a systems engineering division to tailor robots for use in applications other than assembly tasks in the automotive industry which are currently their mainstay.

● Thorn EMI are to manufacture a range of large-screen colour tv sets for JVC at their Enfield and Gosport plants but as the sets are constructed by robots, new jobs are not likely to be created by the planned deal in the near future. Five Thorn sets from 20 to 26in will extend JVC's colour tv range to ten sizes, starting at 6in. Production is expected to start in mid-1983.

Charity buys school micros

A comprehensive school with 1 500 pupils has been given a £16 000 microcomputer grant as a result of a report submitted to a local charity. The report, written by the school's computer development advisory committee, recommended a computer classroom with at least one computer between two pupils. Parents and teachers of the school formed the committee which includes members from Lanchester Polytechnic and Warwick University.

As a result of the committee's concerted efforts and the Edwards Kenilworth School Charity's awareness of the problems facing pupils and teachers, the school now has 27 computers. This is the first donation of its kind made by the charity, which covers all schools in the area.

The grant has funded a 14-unit Nascom computer network, but the school also has 380Z, BBC and ZX80 computers. When asked why such a variety of machines were bought, computer studies teacher Bill Nash replied, "To give the pupils a truer picture of the world of microcomputers." Between one and three pupils in each class have their own microcomputer.


Mr Nash said that during the school's evaluation of computers for use in the network, Acorn Computers were not very helpful. He added that contrary to claims made for them, some of the computers looked at didn't have a true networking facility. Lucas Logic, manufacturers of the Nascom, are based in the area.

"To be fully equipped," concludes Mr Nash, "we need another 15 computers to construct a computer-aided learning laboratory" – and they have been lucky.

More money for fibre development

Under a joint opto-electronic research scheme set up by the DoI and Science and Engineering Research Council, £15m will be available to support collaborative research projects between industry and universities. Project work will be shared equally between the partners, companies receiving up to 50% grants from the DoI and universities receiving up to 100% SERC awards. The joint opto-electronics research scheme is expected to run for five years.

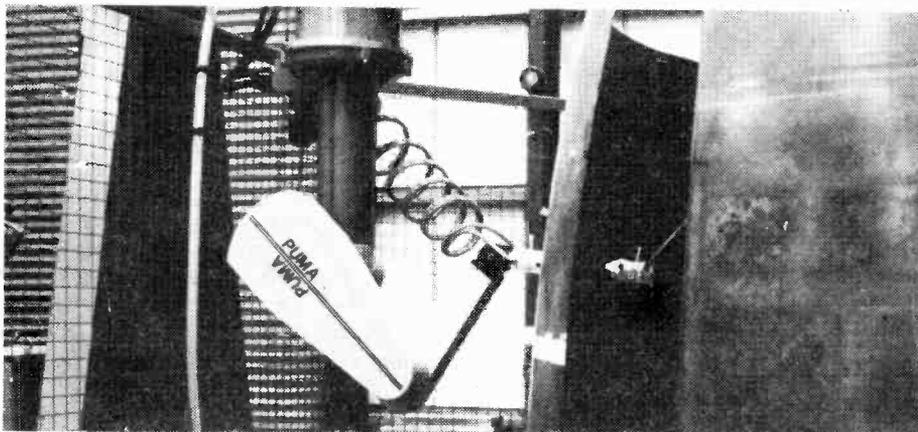The DoI also announce a £15m boost to the £25m set aside in 1981 under the fibre-optic scheme, £20m of which has already been used for grants covering up to a third of the costs involved in designing, developing and launching new fibre-optic products, including equipment and new building expenses.



A Puma robot manipulating transmitting and receiving probes for ultrasonic inspection of carbon-fibre aircraft components.

Satellite to observe Halley

European Space Agency and British Aerospace have designed a £34m contract for the Giotto spacecraft, Europe's first deep space probe, which is to intercept Halley's comet eight months after its launch scheduled for July 1985. Russian and Japanese satellites will also observe Halley but

Giotto will carry the most advanced instrumentation and pass closest to the comet. Instruments will investigate the chemical composition of the comet's coma region, take colour photographs of the nucleus and measure magnetic fields.

Mac overseas


On January 24-25, tv pictures with multi-channel sound were sent via OTS to Stockholm in the first demonstration outside the UK of the IBA's Mac system for satellite-tv broadcasting. C-Mac's ability to provide eight sound channels will be of particular interest in Scandinavia due to the number of different languages spoken in countries likely to be covered by a Nordic direct-broadcast satellite service.

Apart from its acceptance by the BBC, Mac has had another recent boost in that it is to be used by a third US company. This latest patent-licensing agreement with the United States Satellite Broadcasting Corporation is the first to be concluded since the Part report.

Optical fibres sink

Britain's first undersea optical-fibre cable carrying telephone calls 25km across the Solent linking Portsmouth and Ryde is to be installed by 1985. BT say that the 140Mbit/s cable, supplied by STC, costs £600 000 and will carry "a variety of information technology services" as well as speech.

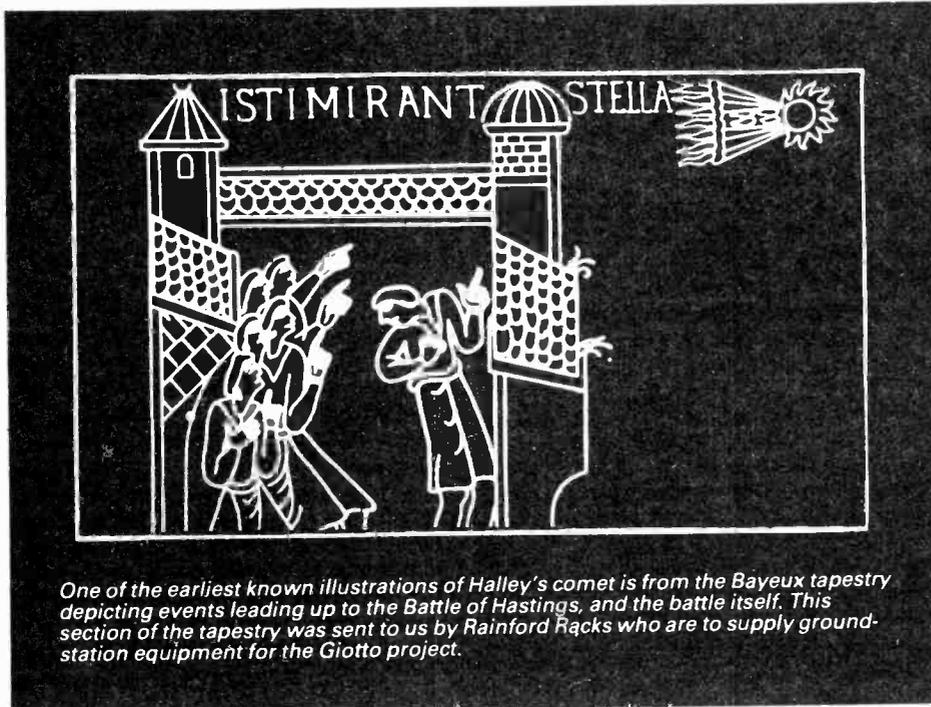Negotiations between telecommunications authorities in the UK, Holland, Germany and Belgium for a European optical-fibre link are underway. An agreement is expected this year.



One of the earliest known illustrations of Halley's comet is from the Bayeux tapestry depicting events leading up to the Battle of Hastings, and the battle itself. This section of the tapestry was sent to us by Rainford Racks who are to supply ground-station equipment for the Giotto project.

15Gbit recordable laser disc


Laser discs that can be used to record both analogue and digital signals at high densities have been developed by Sony. Densities of 15×10^9 bits per side on a 300mm-

diameter disc are claimed for the prototype system and although this achievement represents a significant step towards the optical equivalent of magnetic media, the

last hurdle — that of disc erasure — is yet to be crossed. But because of its high recording density Sony's disc is likely to be attractive, especially in archiving applications.

Each disc surface has two layers evaporated onto it. When recording, a modulated laser beam of less than 7mW changes 'bits' of the upper recording surface from an amorphous to a crystalline state. Areas heated to 170° by the beam have three times the reflectivity of the untouched amorphous areas, and information on the disc represented by the reflectivity of crystalline and amorphous areas is read in the same way as a conventional optical video disc. The recording layer is a film of antimony-selenide.

A second layer of bismuth-telluride underneath the recording layer provides a reflective surface behind crystalline areas to increase the difference between reflective and non-reflective areas, but more important it absorbs heat from the laser during recording to increase the definition of transitions between amorphous and crystalline areas. This means that the lengths of reflective and non-reflective areas can be accurately defined, facilitating analogue recording.

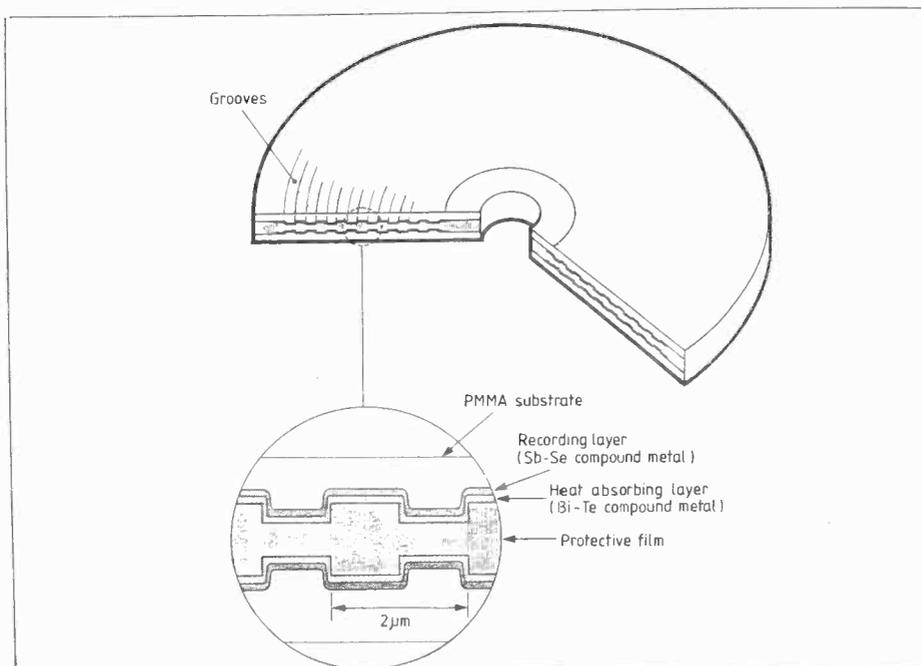


Mastering metals for mothers


A licensing agreement to manufacture records using a metal mastering process has been signed by EMI Music, holding company for EMI's international record interests. The new process eliminates several steps in the record-making chain, allowing a record master to be cut directly into copper thus producing a positive-image "mother". Direct metal-mastered records, which will carry a DMM logo, cost no more than normal pressings but can be made in about two hours as opposed to about a day with conventional discs. Audibly, the new discs claim to virtually eliminate surface clicks and pops, increase signal-to-noise ratio by up to 10dB, allow up to 15% more playing time per side, and eliminate the pre and post-echo associated with lacquer springback.

There are well-known difficulties with traditional nitro-cellulose lacquer blanks. Though it is ideal for cutting it is an unstable material in that it changes with both climatic conditions and time. It is also adversely affected by stylus heat and by burnishing facets, both of which are important for good groove-wall structure. There are problems of groove tearing, horn formation and of plastic deformation in the lacquer material, which results in the well-known phenomenon of springback of the engraved groove (both time and temperature dependant). Then there are severe demands placed on the next step — nickel pre-plating onto a silver conductive coating. It must be extremely thin, its metallurgical structure fine-grained, and it must not contain impurities. The cleaning process should not attack the lacquer surface and the activation or sensitizing process must produce even deposition of silver atoms.

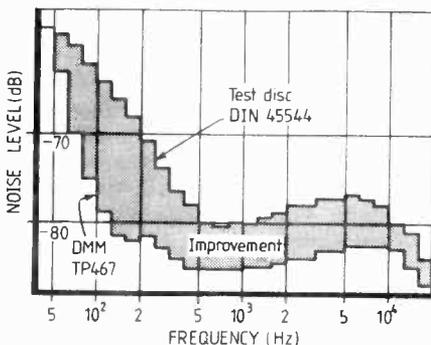According to its developers, Teldec in Berlin, the new process eliminates all three problems by circumventing those steps.



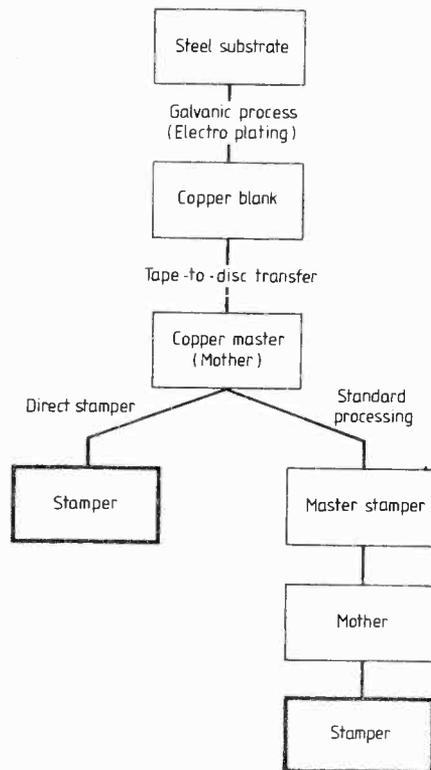Teldec curves show that new direct metal mastering audibly reduces background noise (measured by third-octave filter). Reference level measurement corresponded to a recorded velocity of 10cm/s for one groove wall. Curve A shows the background noise of rumble test record DIN 45544, and B shows the same measurement with the DMM record TP467.



In contrast to lacquer masters, numerous matrices can be produced from a direct metal master, permitting easy correction of defects which may appear in the plating steps en route to the stamper. Process gives a significant time economy in the plating process, especially when making a stamper directly.

First proposed over 90 years ago and recently revived by RCA for capacitance video discs (see page 39, September 1981), the direct cutting into metal means that the cutting lathe produces the mother (metal positive) for the plating process. But the demands on the video disc manufacturing process were small by comparison, as indeed are the groove dimensions: depth is 1µm and width 2µm (not 2mm as misprinted in that article), with a modulation depth of only tens of nanometres.

But the electrolytically-produced copper coating is not readily applicable to conventional records. As the cross-section of the groove is 100 times larger than that cut from videodiscs its ductility and elasticity must be right; the copper coating needs an amorphous rather than the crystalline structure of pure electrolytic copper. Equipment for producing the copper blank developed in conjunction with Euro-pafilm of Sweden deposits the copper onto the 0.8mm-thick stainless steel substrate, and may be immediately used when cut as the mother in the plating process.

This metal cutting blank provides a higher resistance to the cutting stylus than does the traditional lacquer blank. To reduce cutting resistance three measures

have been applied. Unusually, the diamond cutting stylus has no burnishing facets. This means that the innermost turns of the groove show no amplitude losses, even when cutting at the highest frequencies. Secondly, the face angle of the diamond stylus is greater than 90°. The sum of the face and stylus angles is chosen so that for the maximum groove excursion there still remains sufficient space between the groove walls and the back of the stylus. And thirdly, the cutting stylus is excited at an ultrasonic frequency whose amplitude increases with increasing groove depth, where cutting resistance is greater. This results in an extremely smooth groove wall and keeps the mechanical loading of the cutterhead — a Neumann SX80CM — and the resulting electrical power demand within reason.

Experience up till now has shown that the stampers from the new masters are "entirely free" of ticks and pops and the surface noise is diminished more than 10 dB, against a mother made from lacquer blank. For carefully pressed records, this can extend all the way to the final product. Background noise of the final disc shows fewer impulse-type disturbances compared to traditionally produced l.p.s, and Teldec say unwanted high frequency components are significantly reduced.

The elimination of lacquer springback eliminates pre and post-groove echo. It is therefore possible to reduce the groove-to-groove spacing and to fully utilize pitch control methods. With the Neumann VMS80 tape-to-disc transfer system the result is 10 to 15% more playing time per record side. Elimination of groove deformation during or after the cutting process has provided A/B comparisons between discs cut in lacquer and the new masters which show improved transient behaviour, and Teldec say that instruments rich in upper harmonics and sibilant voices are particularly free of coloration.

Initial manufacturing experience has confirmed Teldec's original assumption — that manufacturing reliability will be much higher than through the use of traditional technology. After conversion to the new process the number of recuts necessitated either in the cutting or plating process were reduced "drastically."

But despite this, and significant savings in the plating process particularly for short-run classical recordings, the price of DMM records will not be lower, though an EMI spokesman did concede that some increases may be circumvented. According to the BPI, manufacturing costs are but a small fraction of the selling price of records, typically 38 pence in £4.39, and the new process will only bring about small savings in that fraction. EMI say they will introduce the process in its Köln pressing plant in about six months time, and in its other main plants by early 1984. Until then EMI's initial releases will be pressed by Teldec in Germany.

CIRCUIT IDEAS

Floppy-disc drive tester

All major functions on a standard 5¼in mini-floppy disc drive are tested by this circuit without the aid of a computer. Using the box with an alignment disc allows the read/write head to be accurately aligned with the disc. As the connections on the drives shown are standard, logic signals and power come out on two plugs. There are four inputs to the box from the drive,

- write protect (WP)
- track 0 (TR00)
- index, signal showing each revolution of drive
- read data, data output from disc.

Inputs simply light LEDs through CMOS buffers to show conditions of the various signals. Outputs from the test unit to the drive are almost all switch closures,

- drive selects, DS₁, DS₂ and DS₃, set up code to select drive unit
- motor, switches on drive motor
- direction, selects step in or step out of read/write head
- step, pulse that steps head in or out

(depending upon condition of direction signal)

- write gate, low for write enable, high for read enable
- write data, does not write any useful data to the drive but produces a digital pulse train used for tracing through disc circuitry.

S. J. Evans
Cradley Heath
West Midlands


Low-cost 3-digit common-cathode d.v.m.

The three-digit common-anode d.v.m. based on CA3162E & CA3161E integrated circuits from RCA is well known; the CA3162E is a multiplexed a-d converter, and the CA3161E is a simple b.c.d.-to-seven-segment common-anode display decoder/driver, with integral segment-current limiters. For a d.v.m. with common-cathode display (like most of pocket cal-


culator led displays), you can't use the CA3161E; it must be substituted by another display decoder/driver i.c. The MC14511B is a CMOS b.c.d.-to-seven-segment common-cathode display decoder/driver, but without segment-current limiters that must be added externally. A 10kΩ pull-up resistor must be added to each 14511 b.c.d. input to operate correctly with the CA3162E.

The switch selects the sample rate. In the 4Hz position (pin 6 to ground) a sample is taken every 0.25 second; in the 96Hz position (pin 6 to +5 V) a sample is taken every 0.01 second (approximately); and in the hold position (pin 6 to +2.5 V) the display is frozen.

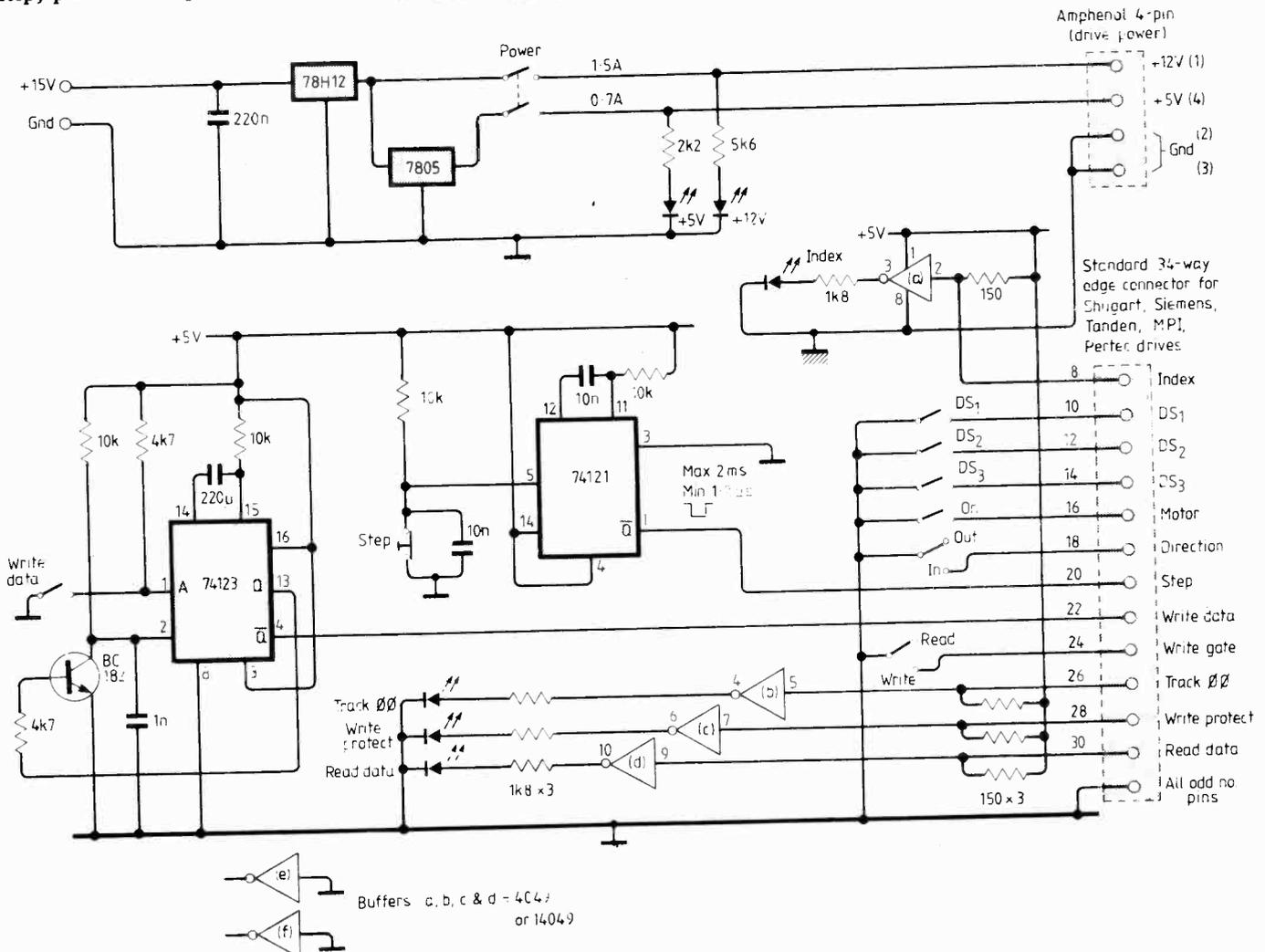Calibration should be as follows. Firstly, connect the input to ground. The 47kΩ preset potentiometer is then adjusted so that the display reads 000. Now, an accurate known voltage of, for example, 800 mV is connected to the input, after which the 10kΩ preset potentiometer is adjusted to give the correct display of 800. The range is -99 to +999 mV. However, the



CIRCUIT IDEAS

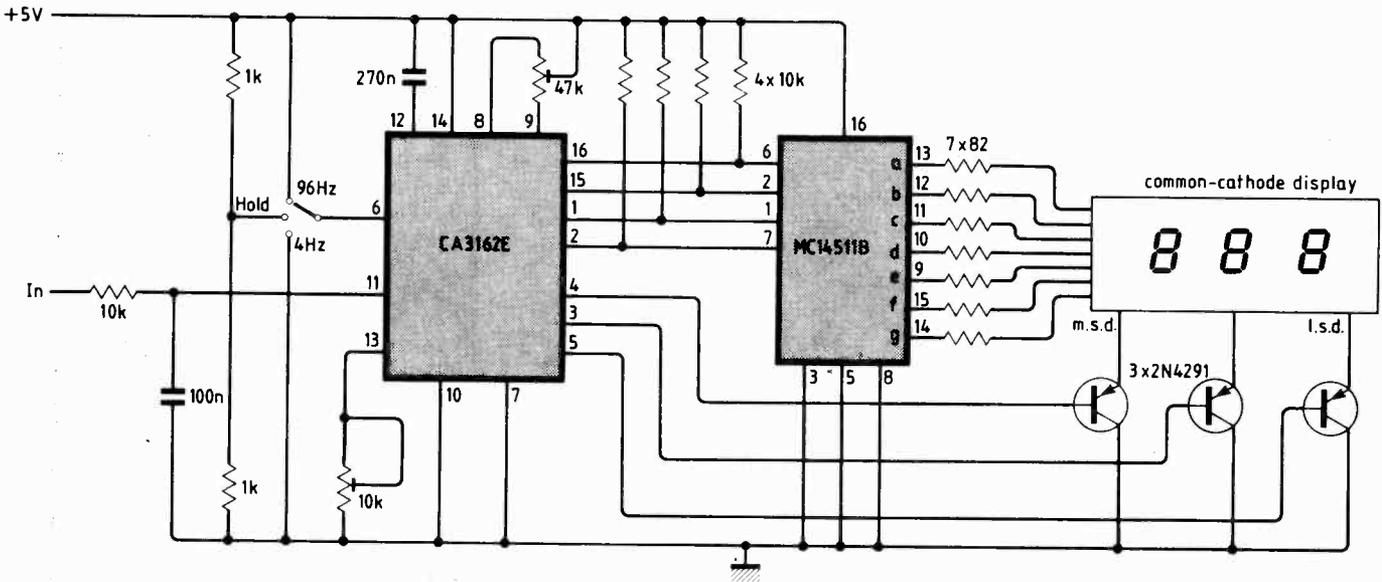

MC14511B is not able to display the “-” (minus) and the “E” (overload) characters. With negative input signals the most significant digit will be blanked, and with overrange input signals all digits will be blanked.

Francisco J. Herrero
Soria
Spain

voltage at either of the op-amps causes an abrupt step at zero crossover, just where it matters most for many digital audio applications, and maintaining 14-bit linearity requires offsets below $100\mu\text{V}$. A more satisfactory way of obtaining bipolar operation is to use the 7134U and offset the output by $-\frac{1}{2}V_{\text{ref}}$. Normally this would require a second op-amp in the signal path, but the internal resistor values turn out to be exactly $2R$. Used with an op-amp as shown they provide an offset current which accurately matches the internal feedback resistor in value and temperature coefficient. Offset voltages on either op-amp now result in only d.c. shift, with no effect on linearity.

P. J. Skirrow
Lindos Electronics
Woodbridge
Suffolk

Improving the 7134 d-to-a for audio use



The Intersil 7134 14-bit d-to-a converter is designed for a unipolar, $+10\text{V}$, or bipolar, $\pm 10\text{V}$, output range depending on whether the m.s.b. of its R-2R ladder is fed from V_{ref} directly or through an inverter. It provides two resistors for use with an external inverter and the 7134B is programmed to correct for any error in the resistor ratio. Unfortunately an offset


Darlington difficulty

The Darlington transistor configuration has proved its worth in many designs but budding engineers can be caught out by overlooking one of its basic parameters – no matter how hard the first transistor of the pair is driven, V_{CEsat} will never be less than 0.7V ($V_{\text{CEsat1}} + V_{\text{BE2}}$), important when the Darlington is used to turn off transistors in logic circuits or as a power switch.

Extra power consumed by the device because of the voltage drop is also often overlooked. For example, a 600mW device would be working close to its maximum dissipation rating with a collector current of only 800mA . Both problems are overcome by using separate transistors.

D. Gray
Todley
Hants

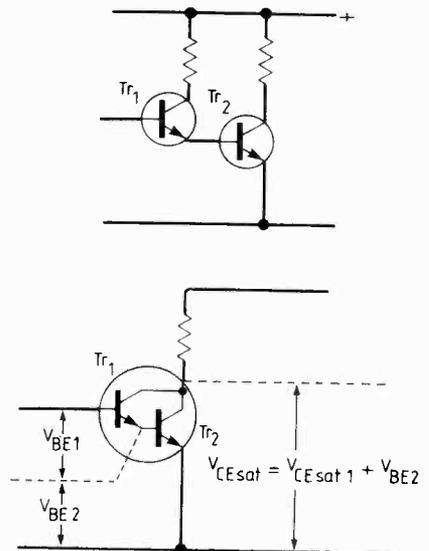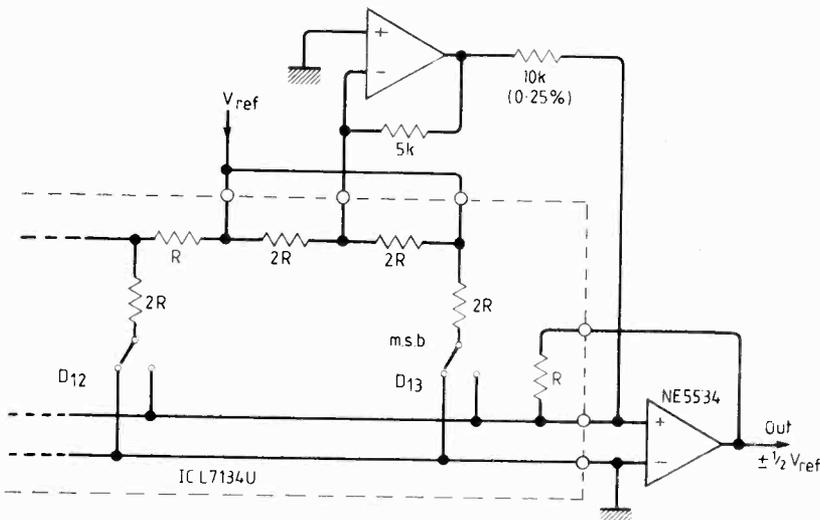

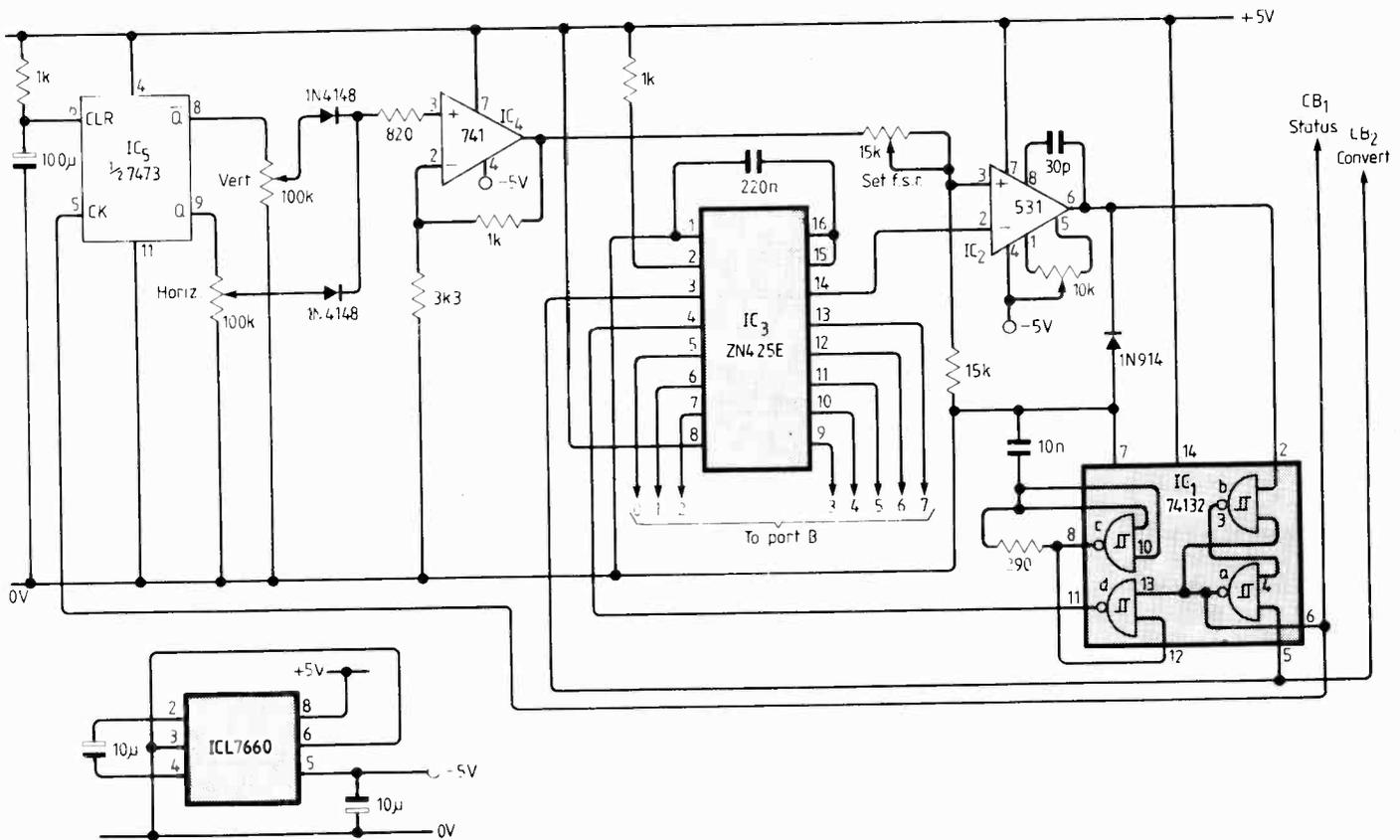

Joystick interface

Conventional joysticks use either two expensive a-to-d converters with three-state outputs and good resolution in microseconds or include cheaper, slower converters with limited resolution. This interface offers the best of both designs with 500μs conversion time: if speed is important, a ZN427E a-to-d converter may be used. The circuit shown uses port B of a 6522 v.i.a. with CB₁ and CB₂ acting as input and output lines respectively. But any p.i.a. or v.i.a. with more than nine inputs and one output may be used.

On power up the clear input of IC₅ is held low for around 100ms to give Q=0 and Q̄=1 so there is no potential drop across the horizontal-axis potentiometer and the non-inverting input of IC₄ represents the vertical potentiometer position. Diodes connected in series with the potentiometer wipers block the ground path.

To start conversion, CB₂ is pulsed to 0V. The falling edge of this pulse sets the counter of IC₃ to zero and sets the status line (CB₁) and the output of IC₂ high while the rising edge starts the clock, IC₁, which runs at around 200kHz. When the output of IC₃ exceeds the output of 1.3-gain buffer, IC₄, the output of IC₂ returns to zero and through gating by IC_{1a,b,d}, clock pulses to IC₃ are inhibited and the status line returns to zero. The digital output of IC₃ now represents the vertical-potentiometer position.

When the clock input of IC₅ receives a falling edge from the status line, the i.c. outputs change to Q=1 and Q̄=0. Now,

triggering the a-to-d will result in conversion of the horizontal-axis potentiometer representation at the output of IC₄ to digital form and IC₅ reverting to its original state. Thus the same routine used twice gives x and y coordinates of the joystick.

The Atom-Basic list shown reads and displays the control settings but machine code will probably be required in practice. For other computers, v.i.a. base address B800 will need changing. Query operator, ?, achieves peek or poke depending on its context. Program actions are

Line	Action
5	set B port as 8 input lines
10-40	control loop
150	set and reset converter (B80C is PCR controlling CB ₂ through bit 5; set=224, reset=192)
160	loop until CB ₁ is low (B80D is interrupt flag register; bit 4 indicates negative transition on CB ₁ ; other bits are zero and bit 4 set to zero when B port is read.
170	return to control loop

If the microcomputer only has a positive supply, the 7660 circuit may be added to provide -5V for IC_{2,4}.

D. C. Grindrod
Sutton Coldfield
West Midlands

```

5 ?#B802=0
10 DO
20 GOS.150;X=?#B800;
   GOS.150;X=?#B800
30 PRINT X,Y

```

```



40 UNTIL 0
150 ?#B80C=192; ?#B80C=224
160 DO; UNTIL ?#B80D>0
170 RETURN

```

Simple clock doubler

I have used this frequency doubler on numerous occasions to generate high rate clock pulses around spare gates/inverters left on circuits.

D. J. Greenland
Bar Hill
Cambridge

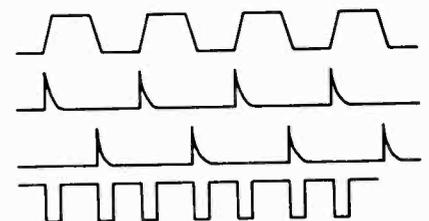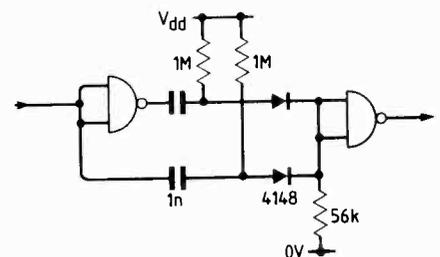

Some problems of aerials at sea

Many marine radio installations are far from competently carried out. More photographic evidence is presented

In the September 1982 issue of *WW I* discussed the merits of a variety of merchant ship transmitting aerials from a theoretical point of view. In this article, I propose to show some of the problems which have been experienced with a fairly typical aerial installation and the transmitters which it serves, adding a word, wherever possible, on what might be done to bring about improvement. Most of the equipment depicted dates from the late 1960s –

by J. J. Wiseman

early 1970s, but this is what hundreds of ships at sea still depend on. There is no reason to believe that more recently manufactured installations, with all their ics and digital readouts, work any better.

The two aerials in question are shown in Fig 1. The 'main' aerial is a popular mast or cage type, widely used on ships of many nationalities. Height from base to tip of the whip is 16.2 metres; height from base to top of the cage is 10.5 metres; and nominal capacity is 400 pF. The central support is a hollow, tapered, tube of glass fibre, which deteriorates with age, especially out-of-doors, the surface becoming crazed as water seeps in. The other aerial (reserve) is a rather short piece wire of the "It'll be all right if it ends in a whip" school. Its capacity I estimate as less than 100 pF, and its usefulness as 'emergency' aerial as doubtful – it is *far too short* and the two aerials

are so close together that any catastrophe befalling one of them is likely to damage the other as well. Note how both these aerials are raked, indicative of ship-builders' obsession with style over function. Figures 2 and 3 show the feedthrough arrangements for mast and wire aerials respectively.

First problem:

The main transmitter, (Fig 4), delivers 400 watts on 500 kHz and 6 other frequencies in the band 410/512 kHz. It has ample tank-circuit loading/tuning adjustment and can put 10A up the mast aerial, still delivering 2 to 5A in wet and humid weather. Radiated power under these conditions may be down to 50 watts, still quite useful and not unusual. However, in hot dry climates, less than half maximum power can be realised due to severe arcing to ground in the aerial switching unit, in Fig 5. This indicates insufficient aerial capacity: if that cannot be increased, then it is still possible to distribute tank-circuit inductance between transmitter and aerial by means of loading coils in the aerial,

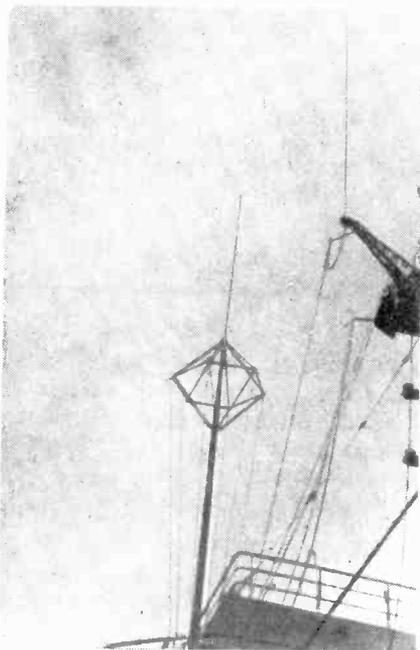


Fig. 1. Popular mast or cage aerial.

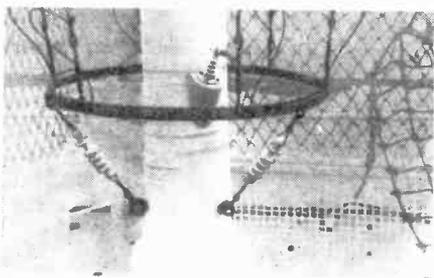


Fig. 2. The base of the fibre-glass supporting pole of the mast aerial is also the feed-through insulator. The ring at the bottom is a rain-cone.



Fig. 3. Feed through insulator of emergency aerial.

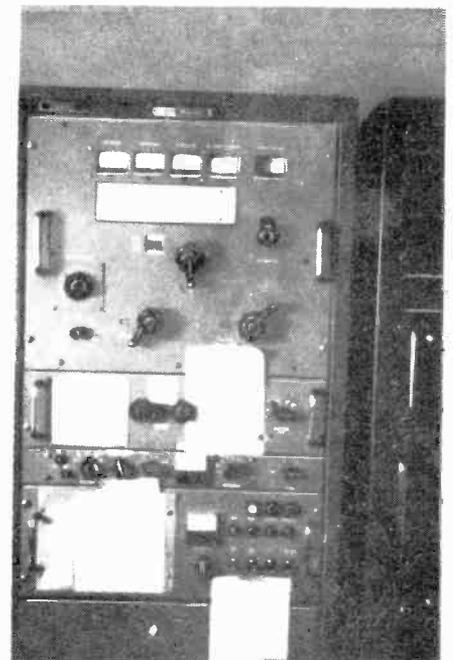


Fig. 4. The main transmitter.

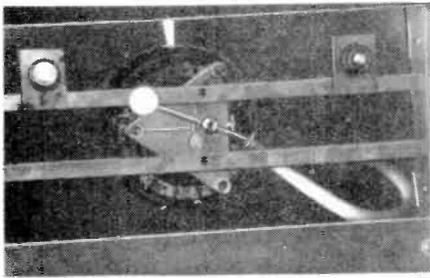


Fig. 5. Arcing from frame to switch interconnecting wire, top centre. The round objects, left and right hand sides, are neon bulbs.

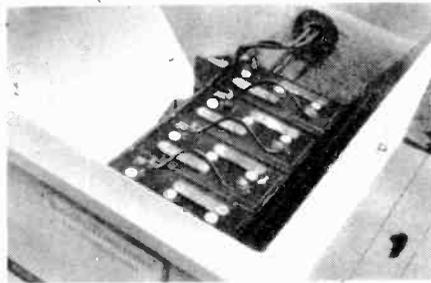


Fig. 8. The emergency radio batteries.

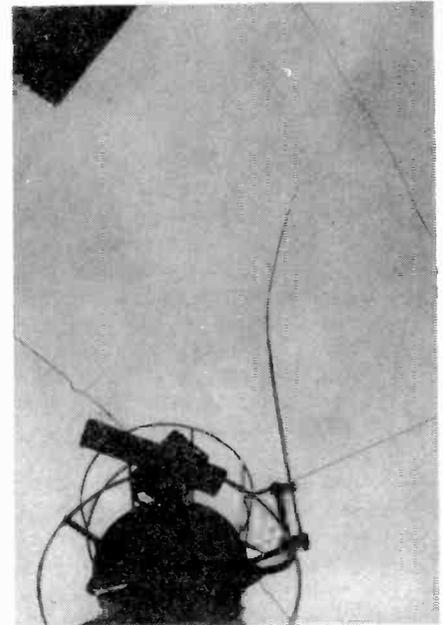


Fig. 12. British Flag, B. 1974. Short receiving whip, long co-ax., no impedance matching transformer.

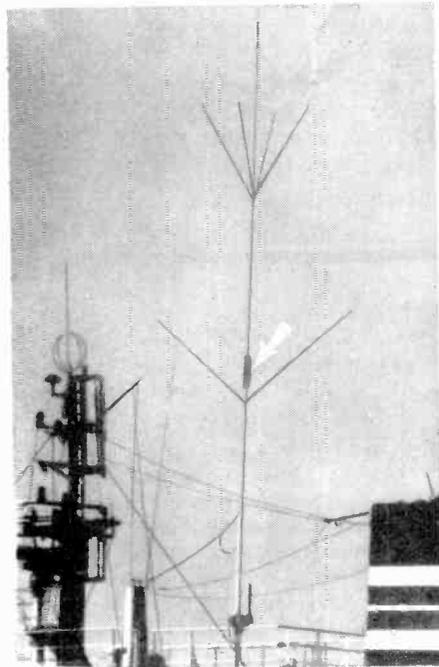


Fig. 6. German mast aerial with loading coil.



Fig. 9. (1) P.a. valve (2) Coupling adjustment (3) Neon tuning indicator.

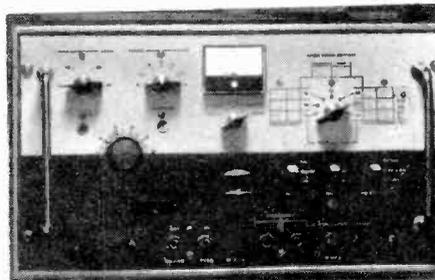


Fig. 10. Emergency transmitter with much better facilities.

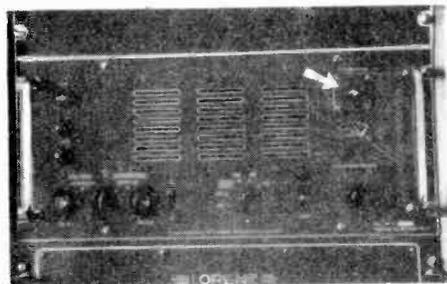


Fig. 7. 70 Watt emergency transmitter.

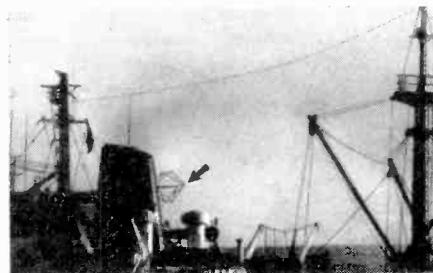


Fig. 11. British Flag, 6925 g.r.t, Built 1974. Photographed in Gulf of Aqaba, October 1982. Mast aerial struck by lightning.

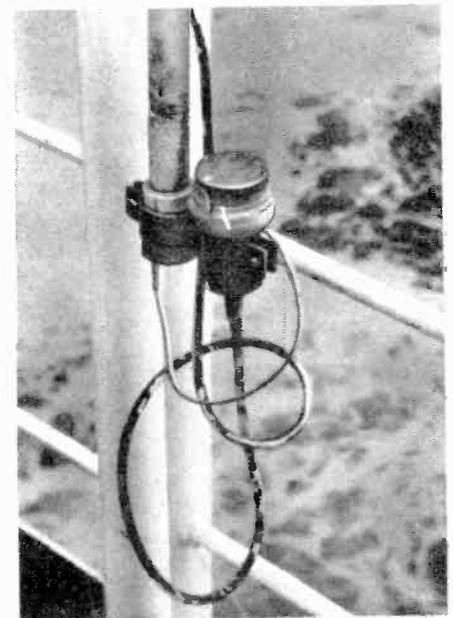


Fig. 13. Matching transformer on receiving whip greatly improves 500 kHz reception.

shown in Fig 6. (Some old ships actually had large loading coils built into the rack — never seen these days.) The same transmitter delivers up to 1400 watts h.f., but no arcing problems occur; aerial capacity is always very large by the requirements of h.f. tuned circuits, or the aerial is operating in other modes, near 0.25 wavelength or multiples thereof. This is exclusively a 500 kHz problem — power radiated is critically dependent on the weather. Is it an aerial or a barometer?

Second problem

The reserve or 'emergency' transmitter in Fig. 7 delivers a nominal 70 watts, at 500 kHz and six other frequencies in the band 410/512 kHz only. It is powered, via a

rotary converter, from the bank of batteries giving 24V, 180A seen in Fig. 8, and is all one has to depend on if the main transmitter or the power mains fail. It lacks: external coupling adjustment; overload trip; power reduction switch; metering of any kind; external h.t. fuse. The panel has a meter-shaped hole cut in it (arrowed), but this is occupied by a neon bulb capacitively coupled to the tank coil by means of a piece of stiff wire close to the coil. This is the only tuning indicator provided. Internal adjustment of coupling is available (Fig. 9). The 70 watts is squeezed out of a very small valve seen at the bottom l.h. corner of the photograph. If the weather is even slightly humid, the neon bulb fails to light. Then the only means of

tuning available is to listen for an increase of signal strength in the receiver. Since only a vague and shallow dip is obtained, and there is no overload trip or power reduction, the anode of the very small valve glows red-hot, threatening self destruction. When the ship is pitching, listing, sinking, or on fire, that is not a good time to be pulling the transmitter out of the rack, screw-driver in hand, fiddling with the internal coupling, which in any case proves quite inadequate when the Q of the tank circuit is at the mercy of the vagaries of the weather.

This equipment has been Post Office approved in its country of origin, and surveyed and passed, year after year. This being 'Holy Writ', it is useless to com-

plain, because, "It passed survey". To those who claim that you can 'burn off' moisture on aerial insulators by holding the key down, I would point out that: there has to be enough energy available to vaporise a lot of water, and there isn't; if the key is held down, the p.a. valve will melt! (just as well the p.a. isn't transistorized!); the dielectric properties of humid air seem to play a part. No output or dip whatsoever can be obtained with the "reserve" aerial connected during wet or humid weather.

A far better emergency transmitter is shown in Fig 10. It has: ample tank tuning/coupling adjustment; metering of five functions, including aerial current and p.a. cathode current; overload trip; four very robust valves in parallel in the p.a. stage, the drive and power supply being all transistorized; power reduction switch; numbered controls, which, in conjunction with the instruction card enable the transmitter to be put into operation by

unskilled personnel in an emergency, and automatically to key an alarm signal and distress call. But still, a too-short, low-capacity, high-leakage aerial and severe weather, *even this* has been known to fail. The aerial is all important. An h.f. capability for emergency transmitters would be very useful.

Third problem

This is the ultimate problem. The mast aerial of this British ship has been struck by lightning, and it is laying on deck with its whip tip burned right off. A traditional long wire aerial has had to be rigged. The aerial switching unit was also destroyed. Benjamin Franklin would not have been surprised.

Fourth problem

This concerns receiving aerials. The whip aerial (Fig. 12) is quite short and is

mounted next to the radar scanner, where it is likely to pick up noise from the modulator pulses and scanner motor commutator. It has a very long run of coax. and no impedance matching is attempted, so that signals at 500 kHz are very much attenuated. (There is a naive belief in shipyards that coax. is a magical electrical 'water pipe'.) If the aerial is mounted near the bow to isolate it from the transmitting aerials, then a short receiving whip may have an unmatched coax. run exceeding 100 metres. Inefficient transmitting aerials *plus* inefficient receiving aerials makes for poor communication at 500 kHz. Figure 3 shows a simple matching transformer on a 500 kHz Auto-Alarm receiving whip. Broad-band transformers are available, but seldom seen.

A more professional approach to design of ships' radio installations will be needed if the unique properties of 500 kHz as a marine distress frequency are to be realised fully.



continued from page 32

$= (1 + \tau t) \bar{E}_{out}$. In use, the gain A is adjusted to give the fastest response without overshoot, i.e. the circuit is critically damped. Hence the denominator of the above expression can be factored to give a squared term:

$$\bar{E}_{out} = \frac{E}{s(\alpha s + 1)^2}$$

where $\alpha = \tau R(C + C_f)$. The inverse

transform from standard tables is

$$E_{out} = E \{ 1 - (1 + t/\alpha) \exp(-t/\alpha) \}$$

The rise time of this function is governed by the value of α (it can be found graphically to be approximately 3.4α). The rise time of the original input circuit is $2.2RC$. Comparison of the two values shows that for the greatest improvement by neutralization C_f should not be unduly large, and the amplifier time constant τ should be as small as possible.



References

1. Purves, R. D. *Microelectrode Methods for Intracellular Recording and Ionophoresis*. Academic Press, London, 1981.
2. Kootsey, J. M. and Johnson, E. A. Buffer amplifier with femtofarad input capacity using operational amplifiers. *IEEE Trans. Bio-Med. Eng.*, vol. BME-20, pp. 387-389, 1973.
3. Thomas, M. V. Microelectrode amplifier with improved method of input-capacitance neutralisation. *Med. & Biol. Eng. & Comput.*, vol. 15, pp. 450-454, 1977.

continued from page 43

what one would expect.

It appears that after the switch was closed, some electromagnetic energy must have started off to the *left*, away from the now closed switch; bounced off the open circuit at A, and then returned all the way back to the switch B and beyond.

This paradox, that when the switches are closed, electromagnetic energy promptly rushes *away* from the path suddenly made available, is understandable if one postulates that a steady charged capacitor AB is not steady at all; it contains electromagnetic energy, half of it travelling to the right at the speed of light, and the other half travelling to the left at the speed of light.

Now it becomes obvious that when the switches are closed, the rightwards travelling electromagnetic energy will exit down BC first, immediately followed by the leftwards travelling electromagnetic energy after it has bounced off the open circuit at A. Even before the switches were closed, every segment of electric field had coexisting with it a segment of magnetic field at right angles, and both were travelling together at the speed of light.

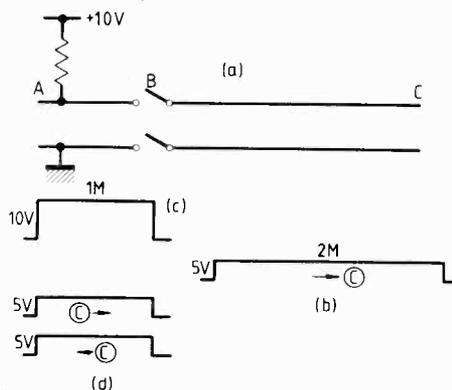


Fig 3. Pulse generator (a). Changing AB to 10V and closing switches produces 5V pulse twice as long as AB (c) and (d), caused by left and right travelling pulses following down line BC.

What is true of a 'steady' charged capacitor or coax. cable is also true of a pair of wires connected to the battery. Before closure of the switches, electromagnetic (not electric) energy was oscillating to and fro between battery and switches. Since the same amount travelled in both directions, the magnetic fields being equal and oppo-

site cancelled, and only an electric field could be detected. 'Waves in space' existed between these two wires long before the switches were closed and before the capacitor came into the picture.



The author

In 1953, at the age of 17, Ivor Catt won a State Scholarship in mathematics. In 1959 he gained a B.A. in engineering at Trinity College, Cambridge. He is married with four children ranging in age from 22 down to 1.

Ivor Catt's 25 year career has been mostly in R&D in industry but partly in teaching. His field of experience is centred on computer hardware design, for instance at Ferranti (now I.C.L.) Manchester, and on microelectronics, for instance at Motorola, Phoenix, Arizona.

Catt's second field of research, which resulted from his experience spanning both microelectronics and computer hardware, led to his patented inventions in Wafer Scale Integration and computer architecture, described in the July 1981 *Wireless World*.

COMMUNICATIONS

A.m. stereo standards

The difficulties of obtaining international or European agreement on broadcast transmission standards are well-known, but they begin to pale into insignificance beside the dog-fight in the USA over which system to use for a.m. stereo broadcasting on the medium-wave band. Following several years of technical investigations and field trials, the FCC decided early in 1982 that the choice between six competing systems — Motorola "C-QUAM"; Magnavox AM-PM; Harris V-CPM; the Kahn/Hazeltine independent-sideband system; the Belar a.m.-f.m. system; and the Fisher DPC system — would have to be left to "the market place." This process is made infinitely more difficult by American anti-trust legislation which makes it impossible for any organization, or group of broadcasters or manufacturers to take responsibility for agreeing with others to adopt a particular system. Even in a city having half-a-dozen a.m. broadcast stations, each is expected to make up its own mind regardless of what the others intend to do. Since the systems are, at least to a considerable degree, non-compatible, this would create a situation where a listener might receive stereo from only one station.

The FCC technical assessment of the four systems, issued on March 18, 1982, generally appeared to favour the Harris system, particularly in view of the future use of synchronous-detector technology, stating: "Of the five proposed systems, the Harris is the only one which can make full use of this technology . . . and has the potential to evolve into an even better system."

Nevertheless in the FCC evaluation, the Magnavox system scored 76 points; Harris 72; Motorola 71; Kahn 65; and Belar 58, taking into account monophonic compatibility, interference characteristics, coverage, transmitter stereo performance and receiver stereo performance.

Since March 1982 there has been virtually a stalemate, with most broadcasters waiting for others to see which way the wind will blow. However, in December 1982 the Delco Electronics division of General Motors announced that it was recommending for GM cars the Motorola system. This system amplitude modulates two r.f. carriers that are separated in phase by 90°, but uses non-linear hard limiting to achieve a better degree of compatibility.

The Delco recommendation, because of the firm's prominence in the car radio industry, is seen as a major boost for the Motorola system. It followed bench and field tests carried at station WIRE, India-

napolis, on three of the four still contending systems: Motorola, Harris and Magnavox. Leonard Kahn, originator of the i.s.b. system, declined to participate. At NAB1982 he made it clear that he would be prepared to challenge in the courts any possible breach of the anti-trust legislation. It remains to be seen whether other radio manufacturers and broadcasters will jump on the Motorola bandwagon or whether the struggle between linear and non-linear systems will continue.

A "market place" choice may seem a good idea in theory. The buyer pays his money and takes his choice. But in a matter as complex as a stereo transmission system, where consumers are not even interested in such questions as coverage and interference, provided that they can hear the stations they want to hear with some sort of stereo effect, this is surely a curious way of choosing a system that may have to last the American public for many years to come.

Places at risk

Communications and broadcasting installations have always been regarded as places at risk in the event of civil disobedience, revolutionary coups and the like. The first news of such happenings often emerges when a takeover brings strange new voices to the microphones. World War I was started by an assassination in Sarajevo but the first shots in World War 2 were fired when the Germans, using concentration camp prisoners dressed in Polish uniforms, staged a mock coup on one of their own radio stations close to the Polish frontier.

A story which is virtually unknown in the UK comes from a book published some years ago to mark 50 years of Japanese broadcasting, produced by the "History Compilation Room" of NHK's Radio and TV Culture Research Institute. In the period immediately following the Japanese surrender in August 1945 there were several attacks on broadcasting stations. For instance, on the morning of August 24, a group of former Japanese soldiers, under the cover of a severe rainstorm, attacked the Kawaguchi site of the main Tokyo transmitting station "trying to force the station officials to broadcast a message urging continuation of the war" (which had cost over three million Japanese lives). They interrupted the regular programmes for nine hours.

Two days later, a group of 40 former soldiers and what the book calls "rightists" attacked the Matsue station in western Japan but "they also failed in trying to rouse

support for a continuation of the war." It could thus be argued, I suppose, that World War 2 both started and ended with attacks on radio stations!

Centralized broadcast and telecommunications facilities are still clearly recognized as being at risk — as witness the closing for so many years of what was planned as a major London tourist attraction: the public observation galleries of the Post Office Tower.

Radiation hazards

The possible effects of a different type of hazard occurred to me last year when I made the ritual trip to the very top of the Empire State Building in New York. Looking out of the glass windows one seemed very close to some of the many broadcasting aerials that adorn the building. I began to wonder just what levels a field strength meter might have revealed, particularly when compared to the guidelines in the new American "ANSI C95.1-1982 American National Standard Safety Levels with respect to human exposure to radio frequency electromagnetic fields." This recognises that it is prudent to restrict exposure, on frequencies between 30 and 300MHz, to power densities of less than 1mW/cm² rather than the older limit of 10mW/cm² (the current British figure). ANSI now recognises that non-ionizing radiation at some frequencies is potentially more hazardous than at others. Below 3MHz the guide limit increases to 100mW/cm² and above 1500MHz to 5mW/cm²; between 300 and 1500MHz it is $f/300$ and between 300 and 1500MHz $f/300$ where f is in MHz. The ANSI standard, however, admits some important exclusions to these figures: for example for hand-held, mobile and marine transmitters which can produce strong localized fields but tend to result in lower overall body absorption the guide figures do not apply below 1 GHz for transmitters with less than 7 watts r.f. output. The ANSI standard is quite a complex document but clearly deserves careful study in the U.K.

Consumers and EMC

A few years ago the susceptibility of so much consumer electronics equipment in homes and cars to strong out-of-band r.f. fields was of concern mainly to the 30,000 or so UK radio amateurs. Today there are not only the 350,000-plus CB transmitters to take into account but also the many consumer digital-type systems and electronic devices such as semiconductor

lamp dimmers that can affect television, radio and audio. In addition many high-gain audio systems, including tape recorders and record reproducers, are vulnerable to the sync pulses of strong television signals. Home Office statistics normally cover only complaints of interference to the off-air reception of local television and radio broadcasts, today only part of the problem.

In North America leakage into and out of wideband cable tv systems is proving a difficult problem and represents an argument in favour of fibre-optics systems which should be far less susceptible to r.f.i. and not give rise to outward leakage problems.

In the UK a more immediate problem is the added susceptibility of domestic tv where a video cassette tape recorder is in use. This vulnerability extends to off-air reception where the signals pass through the wideband v.h.f./u.h.f. amplifiers in the recorders. These amplifiers often exhibit gain from about 12 MHz up to 900 MHz and can be overloaded by a strong signal anywhere in this range. For the UK market, the v.h.f. capability of the recorder amplifiers is unnecessary, and it would reduce susceptibility to local transmitter interference if u.h.f.-only recorders were marketed in the UK.

A further problem, affecting primarily amateurs using the 3.5 MHz band, is the high-gain head amplifier with a frequency range extending up to about 5 MHz. In some recorders this is comparatively well screened, but this is not always the case; the general use of plastics enclosures for recorders does not help.

A problem common in the USA that has not yet arisen in the UK is that of interference to the receivers used for opening garage doors by radio control. Apparently it is by no means unusual to see a succession of garage doors swing open when a mobile transmitter passes by. Yet in many cases the manufacturers of the radio control equipment are well aware that the problem can often be solved by fitting just one or two r.f. bypass capacitors at suitable points.

It can be argued that the Home Office accepts that susceptibility of consumer equipment to out-of-band signals cannot be blamed on the transmitter. Nevertheless, it was precisely this susceptibility that led the Home Office to restrict legal c.b. to the f.m. mode. For both radio amateurs and c.b. operators there are the difficult social problems that arise with neighbours. It is near impossible to convince somebody who has just spent £450 on a video recorder that the interference is due to its

deficiencies! The owner always blames the transmitter.

Two California cable tv operators were recently ordered to stop using their 151.25 MHz channels in wideband cable systems because leaking signals interfered with Department of Forestry firefighting communications. The FCC Field Office told cable operators to ensure their systems comply with FCC rules, and added that even if a system complies fully with the rules but still causes harmful interference, it is up to cable operator to remedy the problem.

AMATEUR RADIO

Natural energy

For portable and transportable two-way radio, the power source remains the key factor. Even for the popular 144MHz hand-held transceivers the most frequent complaint is that power consumption is such that it gives rise to too-short battery life, even though this may be rechargeable. Many units incorporate a "high/low" power-output switch and, particularly when used with repeaters, the low-power mode often provides adequate range. Power consumption, however, is not helped by some of the recent digital techniques that provide additional operator convenience but shorten battery life.

The use of solar generators is thus of increasing interest although currently not economically viable in many cases. However a relatively powerful solar generator using 20 solar modules each with an array of photovoltaic silicon solar cells and used in conjunction with a 500Ah lead-acid battery has been used at the Jet Propulsion Laboratory in California to power a combined h.f. and v.h.f. "emergency" station based on standard amateur-radio transceivers. In sunlight the solar generator provides about 200 watts of electrical power to charge the battery. This is capable of keeping the equipment running with a low transmit/receive duty cycle for several days. However such installations are costly and not readily transportable so that their application to amateur radio is

likely to be limited: possibly in future the development of large area amorphous silicon solar cells may widen the scope.

Pedal-to-talk

A man-wife team of British amateurs – J. R. G. Corbett, G3TWS and Mrs M. G. Corbett, G8TWS – have recently assembled a pedal-powered generator for use in Zaire to power an h.f. network linking Mission hospitals – bicycle minus a front wheel and with a generator driven by the back wheel held in a cradle. Pedal generators of a similar type have been widely used in the past and can deliver well over 100 watts of power when an energetic cyclist is available – considerably more than can be readily obtained with a hand generator.

An energetic American college professor, Elliot Kleinman, WA4YDK, in a variation on this theme, has recently accomplished the feat of working all 50 American states while operating "bicycle mobile" and is reported to be well on his way to making it 100 different countries. In his case, however, the power source is a 9Ah motorcycle battery which powers a compact h.f. Atlas transceiver for rather over an hour per charge, although liable to die suddenly as it finally discharges. His aerial is a 66-in whip. He uses the 21MHz band.

Not surprisingly, in view of the unstable nature of his loaded vehicle, he reports that the reaction of the people on the streets varies from interested to dumb-founded.

In brief

The Norwegian N.R.R.L. society has awarded its 1982 Golden Key Award to Noel B. Eaton, VE3CJ, former president of IARU. He becomes only the third non-Norwegian amateur to receive this award . . . Father Maksymilian Kolbe, SP3RN, who gave his life to save that of a fellow concentration-camp prisoner in World War 2, has been canonized. In 1938 he set up an amateur station to communicate with missionary stations worldwide . . . A new Russian amateur radio satellite, ISKRA-3 was launched by hand from the Salyut spacecraft during November . . . The RSGB national amateur radio convention at the National Exhibition Centre on March 5 and 6 is to include both lectures and convention features as well as a large trade exhibition . . . The Society's VHF Convention is at Sandown Park Racecourse, Esher, Surrey, on March 26.

– PAT HAWKER, G3VA

High power high quality amplifier using mosfets

Though power mosfets are superior to bipolars because of wide frequency response, high switching speed and absence of secondary breakdown, input capacitance can cause non-linearity problems at high frequencies if you don't have enough drive current. This is especially important when paralleling mosfets for higher output power.

The amplification of very low level signals delivered by a pickup to the high power level needed to drive inefficient loudspeakers presents unique problems which have attracted the attention of many engineers, as witnessed by the many articles in WW. Some of these are closely related to the devices used: bipolar transistors. The relatively new power devices in m.o.s. technology, power mosfets, are capable of solving most of these problems.

Audio power amplifiers using bipolar devices tend to be overload protection. The first one is needed because of the positive temperature coefficient of the collector current versus base-emitter voltage. With increasing power dissipation we get an increasing junction temperature, which increases with the collector current and therefore power dissipation. Eventually, this will lead to thermal runaway, causing destruction of the device. To avoid it a sophisticated circuit is needed to sense the temperature on the output devices and regulate the quiescent current through them accordingly.

Bipolar power transistors are also well known for current concentration under high current conditions. This causes local

by Erno Borbely
Dipl. Eng., M.I.E.E.E.

hot-spots which can eventually lead to secondary breakdown. This is especially dangerous at combinations of high voltage and high current. Consequently bipolar power amplifiers use sophisticated volt-amp limiting to get the maximum from the devices without damaging them.

The Hitachi 2SK134/2SJ49 power mosfets used in this design do not have such problems. Their most important advantage is the negative temperature coefficient of the drain current versus gate-source voltage. As Fig. 1 shows, the drain current is decreasing with increasing temperature above approximately 100mA. This means that thermal runaway cannot occur and complicated temperature-tracking circuits are therefore not required.

Another advantage is the uniform current distribution across the whole silicon

die, which does not deteriorate in the high current, high voltage area. The result is that there are no hot spots and no second breakdown. Sophisticated V-A limiters are

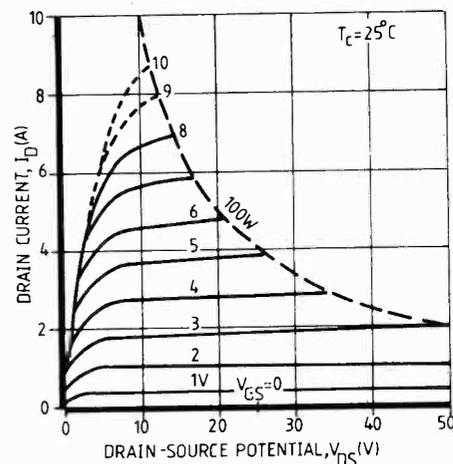


Fig. 3. Typical I_D - V_{DS} curves for 2SK134 show that maximum drain current is limited to seven amps.

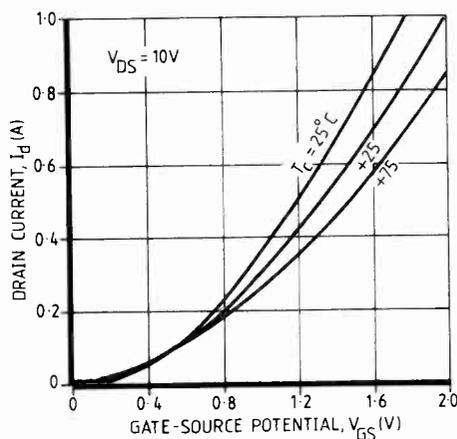


Fig. 1. Negative temperature coefficient of the drain current above 100mA prevents thermal runaway with Hitachi 2SK134/2SJ48 type mosfets and avoids use of temperature-tracking circuits.

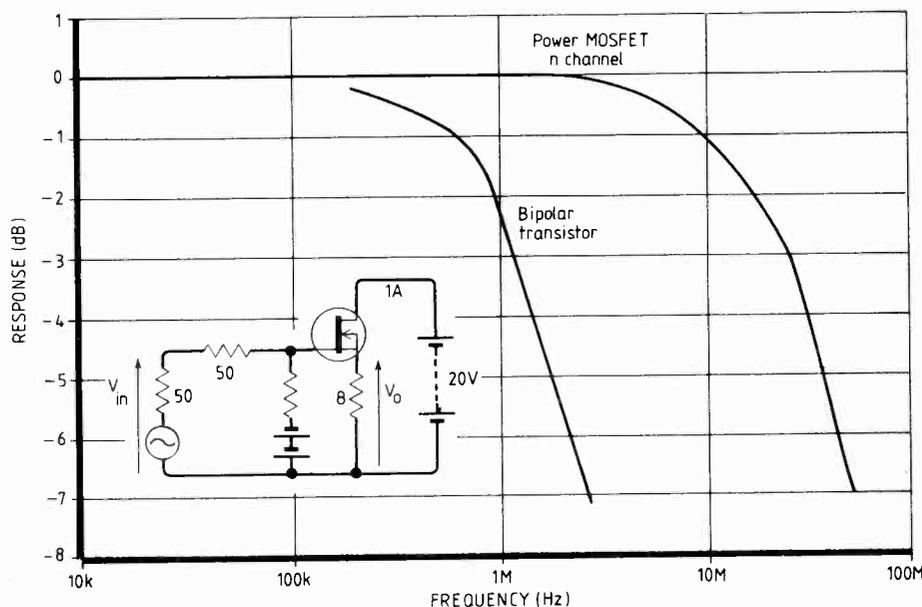


Fig. 2. This n-channel mos source follower has ten times the bandwidth of an emitter follower.

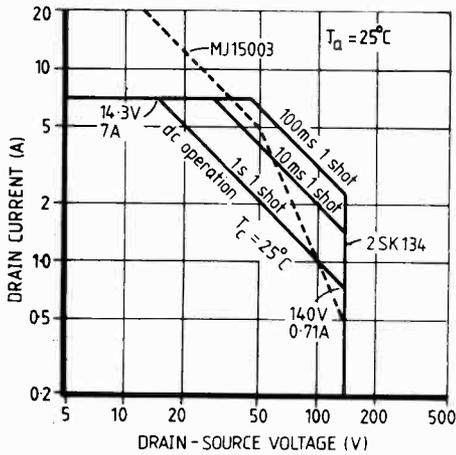


Fig. 4. Compared to a giant bipolar transistor, the mosfet has limited current capability at low voltages, but outperforms the bipolar at combinations of high current and high voltage.

therefore not required for protection. In fact most amplifiers do not need any protection at all.

There are several more advantages with mosfets that are important in audio applications. One is that they are majority carrier devices. Because the charge carriers are controlled by electric fields and not by injection of minority carriers in the active region, there is no stored charge in the gate region. The result is wide frequency response and fast switching, even when coming out of clipping.


Like bipolar transistors, mosfets are usually used in the follower configuration in audio amplifiers. Fig. 2 shows the frequency response of an n-channel mosfet in source-follower configuration. For comparison, the response of an emitter follower is also shown: bandwidth of the source follower is ten times wider than that of a bipolar device.

Another important advantage is their high input impedance. Together with the uniform current distribution, this allows paralleling of mosfets without undue problems. However the spread in the gate-source turn-on voltage has to be considered when doing this, as we will see later. Although the statement "high impedance" is correct at very low frequencies, it is by no means applicable for the whole audio frequency range. The input looks like a pure capacitor with a value of about 1nF. This can cause non-linearities at high frequencies if you don't have enough drive current available. The input capacitance therefore becomes the most important factor in selecting the driver circuit.

Disadvantages of power mosfets

Although having a number of advantages compared to bipolars, mosfets are by no means ideal. The most important disadvantage with the 2SK134/2SJ49s is the high on-resistance. Worst-case calculations show that it can go up to 1.7ohm; a current of 5 amps through the device gives a voltage drop of 8.5 volt across it. Clearly this would increase power dissipation and decrease efficiency. Power supply design

Fig. 5. Many top-quality amplifiers have used a fully balanced, complementary, dual-differential topology, known for very low static distortion at low levels and for good power supply ripple rejection, but it's difficult to get good linearity at high levels, because the second-stage transistors are working with extreme V_{CE} -excursions, causing large gain variations.

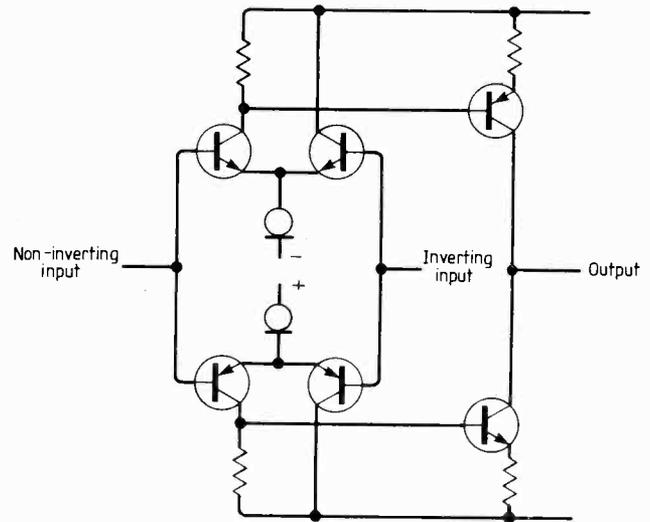

has to be based on this worst-case on-resistance. Typical on-resistance is around one ohm, so there is some margin built-in if we calculate with the worst-case value. Other manufacturers are offering devices with much lower on-resistance but they are limited in other parameters such as breakdown voltage and/or in offering complementary devices. A wider selection of mosfets is expected to be available on the market in the next few years.

When looking at the I_D - V_{ds} characteristics of the Hitachi mosfets, Fig. 3, notice that the curve is not shown at higher drain currents than about 7A - the maximum rated drain current. Compared to some of the bipolar transistors rated at 20-30A this might look meagre. But taking into consideration the device's complete freedom from secondary breakdown, one can usually use more of the available current capability of the mosfets than of the bipolars. Fig. 4 shows the safe operating areas for the Hitachi 2SK134 and, for comparison, of a representative bipolar power device, the MJ15003, being a 20A device and superior at low voltages. At high voltages the mosfet is equal to, or in one area it is even better than, the bipolar device.

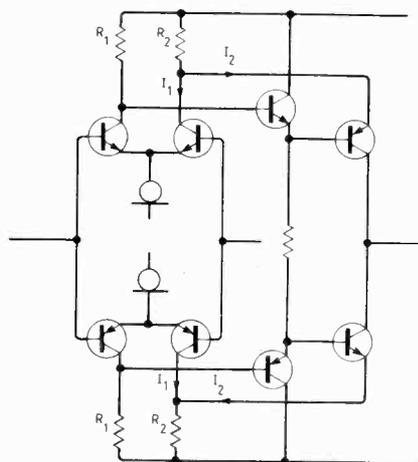


Fig. 6. This offers very good linearity and easy control of the second stage current, I_2 .

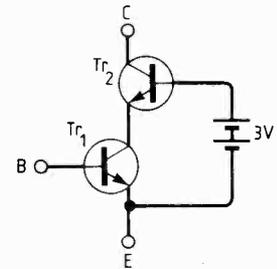


Fig. 7. The cascode configuration is one of the best for large signal handling capability.

The maximum output power one can get with power mosfets is limited only by the thermal capability of the die/package combination. A 2SK134/2SJ49 pair can easily deliver 60W into 8Ω and more than 75W into 4Ω. Two pairs in parallel make a 120W/8Ω or a 150W/4Ω amplifier, as in this design.

Driver design


The most important considerations when selecting the topology for the driver circuit are

- linearity
- open-loop bandwidth
- drive capability.


Although there are some three-stage driver circuits in commercial amplifiers of Japanese origin, most European and American designers prefer the two-stage design which can achieve both good linearity and wide bandwidth.

The differential input is universally accepted as the input stage. The second stage, which has to supply all of the drive to the output stage, is either a common-emitter stage with a current source as a load, or a differential amplifier using a current mirror for differential to single-ended conversion.

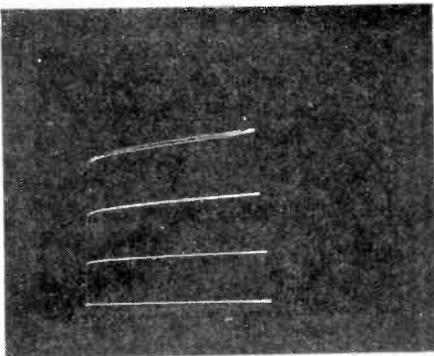Many top-quality amplifiers have been using a fully-balanced complementary dual-differential topology in recent years, known for very low static distortion at low levels and for good power supply ripple rejection, Fig. 5.



(a)

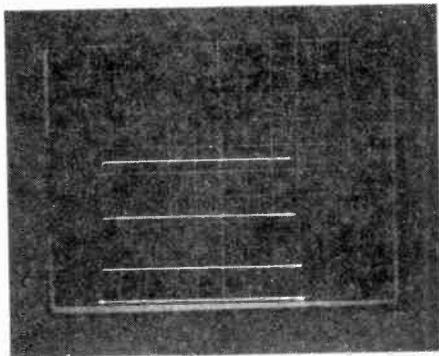

(b)

Fig. 8(a) shows the I_C - V_{CE} characteristics of a typical high-voltage transistor, the MJE340. Although limited in terms of voltage and current, the curves clearly indicate gain variations with changing collector-emitter voltage. (b) shows the characteristics of cascode circuit where Tr_2 is a MJE340, and Tr_1 is MPSA55. The composite characteristics of this circuit are extremely linear, approaching that of an ideal transistor. Voltage variations across the transistors do not cause significant gain variations, consequently these can handle large voltage swings with very little distortion.

It is more difficult to get good linearity at high levels because the second-stage transistors are working with extreme V_{ce} excursions, causing large gain variations. There are a number of ways to improve large-signal handling capability; I have found the circuit shown in Fig. 6 excellent in this respect. This fully symmetrical circuit also allows easy control of the current in the second stage; it is fixed by the ratio of the two collector resistors in the input stages:

$$R_1/R_2 = (I_2 + I_1)/I_1$$

I have found that this current transformation from first stage to second stage works well up to a ratio of about 30 and, with the particular transistors used, up to a second stage current of 30mA. This current was used to drive a pair of 2SK134/2SJ49s in a 60W amplifier with good linearity and slew rate. However, if we want to drive two pairs of devices to increase the output power to over 100W, this current is not sufficient any more (see calculations below). To be able to use higher current in the second stage with

good linearity, I redesigned it using a cascode configuration.

Fig. 7 shows the basic cascode connection of two transistors. Used alone, a high-voltage transistor such as the MJE340 clearly suffers from gain variations with changing collector-emitter voltage; see the I_C - V_{ce} characteristics in Fig. 8(a). The composite characteristics of a cascode circuit (MPSA55, MJE340) are extremely linear, approaching that of an ideal transistor, Fig. 8(b). Voltage variations across the transistors do not cause significant gain variations, consequently these can handle large voltage swings with very little distortion.

An additional advantage of the cascode circuit is its wide bandwidth. It was established many years ago¹ that we need an open-loop frequency response up to 20kHz to avoid transient overload inside the feed-

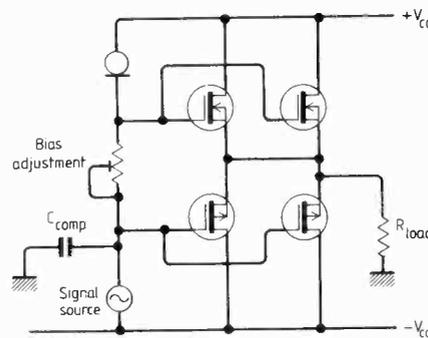


Fig. 9. Paralleling mosfets is easy, thanks to the high-input impedance and the uniform current distribution across the die.

back loop. Using the cascode configuration in the second stage, we can easily satisfy this requirement.

As the collector-base voltage of Tr_1 is held constant in this circuit there is minimum charging of its collector-base capacitance, effectively eliminating the influence of this capacitor on the frequency response. Transistor Tr_2 is operating in common-base mode, which is inherently a wideband configuration. Together, they offer a very linear operation over a wide frequency range. A slight disadvantage is the increased voltage loss across the two devices. This is not a problem in our application because the voltage loss across the output devices due to the on-resistance will dominate. Alternatively the driver circuit could be supplied from a higher voltage.

Finally, look at the drive requirements. Fig. 9 shows the output stage, consisting of two pairs of n and p-channel devices operating in source-follower mode. The input capacitance of the p-channel fets is around 900pF, the n-channel around 500pF. Used in the source-follower mode, the input capacitance is reduced by the local feedback. As the transconductance of the devices is fairly low ($g_m = 0.7$ to $1.4S$), this reduction is moderate. Calculations based on the published figures in the Hitachi data sheets show that we will end up with 100 to 200 pF input capacitance for each of the devices using an 8Ω load.

The input of the output stage is normally used as the main roll-off point for the amplifier. Because input capacitance varies with operating conditions, it is necessary to add a real capacitor here (C_{comp} in Fig. 9), to come up with the total value needed to stabilize the amplifier. Assuming C_{comp} 400pF, and 150pF each

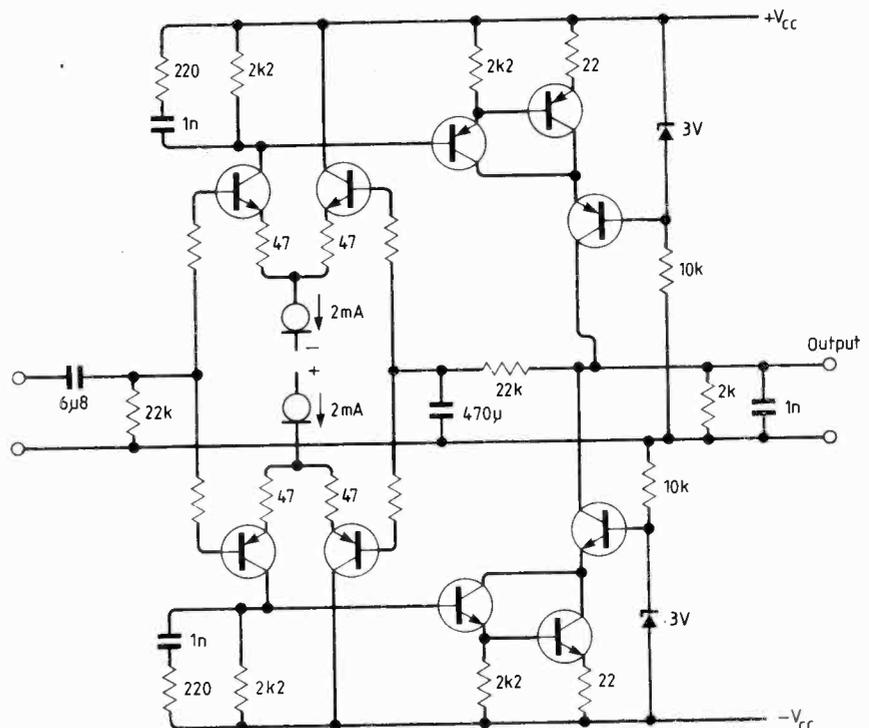


Fig. 10. Driver circuit chosen is as it was for open-loop measurements: gain without the load was too high: the $2k\Omega$ load reduced it to about 66dB. In parallel with 1nF the distortion was 0.1%, both at 1 and 10kHz. Response was down 1dB at 20kHz, 2dB at 30kHz.

for the mosfets, the total load capacitance seen by the driver circuit is around 1nF.

To avoid non-linearities caused by this input capacitance, we have to have enough current available in the driver stage to charge and discharge it under all conditions. I was especially interested in very low distortion across the whole audio band with a reasonably high internal slew rate as a secondary requirement. This was to be higher than the slew rate of any signal capable of entering the amplifier, through the low-pass filter used at the input. Using the well-known formula for the slew rate

$$dV/dt=i/C$$

calculate the necessary current to charge and discharge the input capacitance at the rate required. For a slew rate of 100V/ μ s, and assuming an input capacitance of 1nF, 100mA is needed in the driver stage.

The final driver circuit selected consists of a balanced complementary differential input stage and complementary cascode second stage, Fig. 10. The differential input stages are working with 2mA each (1mA per transistor) while the second stage, for reasons of linearity and power dissipation, ended up with approximately 50mA.

Open-loop distortion for the whole amplifier is approximately 0.5% measured at 1kHz and 100W into 8 Ω . If all of the feedback (40dB in this case) reduced the distortion effectively, we would end up having 0.005% in the final amplifier. This is more than adequate for any high quality amplifier. However, the 2k Ω resistor is shunting too much of the available current away from the load capacitor (corresponding to the input capacitor of the output stage), resulting in a little higher distortion at high frequencies than I was looking for. To avoid this, I removed the 2k Ω load and replaced it with 10k Ω (actually 2 \times 22k, see final circuit). This increased the open-loop gain and the feedback, and the final amplifier shows very low distortion across the whole audio range.

It has been said that due to the low g_m of the mosfets, special circuit configurations like the composite source-follower or extremely high open-loop gain in the driver stage are necessary to get an acceptable linearity². It is my experience that the only precaution necessary is to have enough current available to charge and discharge the mosfet input capacitances. The design described shows that very good linearity can be achieved with a moderate amount of feedback (30 and 40dB, respectively) and normal source-follower configuration.

Circuit discussion

In the complete circuit diagram, p.73, the blocking capacitor C_1 together with R_1 - R_2 and the output impedance of the preamplifier determines one of the low-frequency roll-offs of the amplifier. Assuming that the impedance feeding the amplifier is low, the -3dB point will be about 1Hz. The non-polar capacitor C_1 , should be polypropylene, polycarbonate or, if these are not available, a polyester capacitor. Worst case, a non-polar electrolytic or two non-

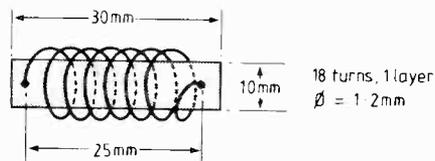


Fig. 11. A suitable output coil can be made on a plastics spacer with parallel resistor to dampen ringing caused by capacitive load.

mal electrolytics connected to form a non-polar capacitor can also be used. The layout gives a number of possibilities as far as type and size of the capacitor(s) are concerned.

Components R_1 and C_2 form a low-pass network to prevent high frequency signals with slew rates higher than the internal slew rate of the amplifier from reaching the input. As the output impedance of the preamplifier forms part of this filter, the value of C_2 should be adjusted for the particular system it is used in. Assuming that the output impedance is very low, the values shown give a -3dB point of over 200kHz, so C_1 should be changed to 1 to 1.2nF, bringing the -3dB point down to about 60kHz. The value shown can be used with preamplifiers with output impedance up to about 10k Ω . C_2 should be a polystyrene or polypropylene capacitor. The d.c. path for the input transistors goes through R_2 which for minimum d.c. offset at the output of the amplifier should be equal to R_{22} .

For minimum d.c. offset we also need high-gain transistors in the input stages but it is difficult to find them with high breakdown voltage. The best compromise I have found is the BC546B and BC556B complementary pair; h_{FE} is specified as 180-450 at 2mA collector current and breakdown voltage 65V. A better choice as far as breakdown voltage is concerned is the MPS8099 and MPS8599 pair (80V) which gives the possibility of higher supply voltages; h_{FE} is 100-300 at 1mA, but does not create any problems with the relatively low-impedance d.c. path used.

The current sources, which supply 2mA to the differential stages, require a stable voltage reference. This is normally obtained from low-voltage zener diodes or a string of small-signal silicon diodes. 1N4148 can be used in this circuit: they show a good repeatability and are very inexpensive. Operating the 1N4148s at around 1mA, the voltage drop is very close to 0.6V: two in series with 2mA through them give an acceptable performance (R_{11} , $R_{13}=22k$, R_{10} , $R_{12}=300\Omega$).

A zener diode solution, shown on p73, needs zener diodes operated at a higher current than the 1N4148s, hence the change of R_{11} , R_{13} to 10k Ω . Although not shown in the schematic, a good temperature compensation can be achieved by connecting a silicon diode in series with the 4.7V zener, which follows the V_{BE} variations of the current-source transistor. This is recommended when operating the amplifier at very high ambient temperatures.

The proposed layout accepts all three solutions: two silicon diodes in series, a

single zener diode or a zener diode and a silicon diode in series.

The 3V reference for the cascode circuit (formed from Tr_7 , Tr_8 & Tr_9 as the p-n-p part, and Tr_{11} , Tr_{12} and Tr_{13} as the n-p-n part) is derived from a string of 1N4148s. This might seem extravagant, but the only alternative, a 3V zener diode, required a much higher operating current. Operating at 5mA, the average forward drop is 0.64V, five of them in series supply 3.2V for the cascode circuit.

Transistor 10 and associated circuitry is for bias adjustment. Hitachi recommend a regular potentiometer for this but as the relatively high current in the second stage is 50mA I didn't find it satisfactory to pass all of this through the wiper of a small trimpot. Instead, I use a normal bias adjustment circuit (V_{BE} -multiplier) found in practically all bipolar amplifiers. The difference is that this circuit is not supposed to have any temperature compensation: Tr_{10} should therefore not be mounted on or near the output heatsink.


When switching the amplifier on the first time, the potentiometer should be set to its anti-clockwise position. While monitoring the current through the whole amplifier (for example by removing one of the fuses and connecting an ammeter across its terminals), the quiescent current should be adjusted to 260mA (100mA in each of the output devices, plus driver). This ensures an optimum operation from the point of view of temperature stability, and low-level distortion.

The mosfets are guaranteed for a minimum gate-source breakdown of $\pm 14V$. The devices have built-in protection diodes, so it should not be necessary to use external protection unless the amplifier is overloaded at very high frequencies. For testing I usually drive the amplifier to maximum output in the frequency range 30 to 50kHz with an 8 Ω load and then connect a large capacitor (around 4 μ F) across the output. The amplifier should work either normally if current handling capability permits or should automatically limit the output.

I have seen the Hitachi devices act a number of ways, depending on the circuit configuration. They might latch, conducting a very high current; they might break up, delivering a very distorted wave form; or they might go into oscillation. Although none of these conditions ever produced a destruction, the devices should not operate under such conditions for an extended period of time. Diodes D_{13} - D_{16} serve that purpose; no matter what current is demanded from the output stage, the diodes prevent the driver stage from delivering more than $\pm 10.6V$ peak gate-to-source voltage. This protects the output from out-of-audioband overstress and just about any sort of abuse is tolerated, until we reach the thermal limitation of the die/package combination.

There are three more blocks of components on the p.c.-board. One is the feedback network, in which d.c.-feedback is applied through R_{22} ; for minimum offset this is equal to R_2 and a.c.-feedback, given by R_{23} and R_{21} , isolated from the d.c.

P.C. BOARD

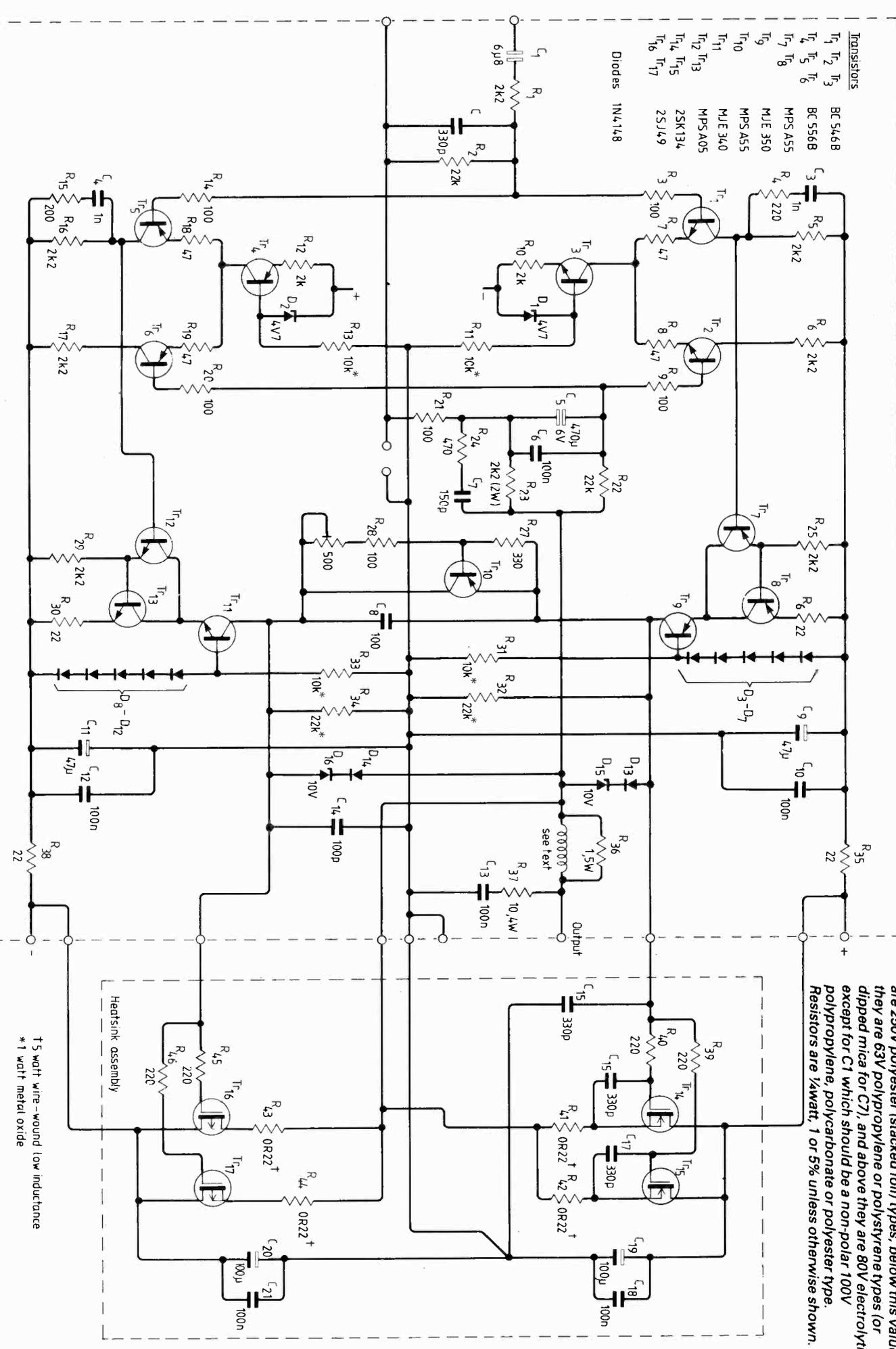

Transistors

T ₁	T ₂	T ₃	BC 546B
T ₄	T ₅	T ₆	BC 556B
T ₇	T ₈		MPS A55
T ₉			MJE 350
T ₁₀			MPS A55
T ₁₁			MJE 340
T ₁₂	T ₁₃		MPS A05
T ₁₄	T ₁₅		2SK134
T ₁₆	T ₁₇		2SJ49

Diodes 1N4148

Capacitors are of three main types - those marked 100nF are 250V polyester (stacked foil) types, below this value they are 63V polypropylene or polystyrene types (or dipped mica for C1), and above they are 80V electrolytics, polypropylene, polycarbonate or polyester type. Resistors are 1/4watt, 1 or 5% unless otherwise shown.

T5 watt wire-wound low inductance
* 1 watt metal oxide

feedback by C_5 and C_6 . The d.c. gain is unity, and a.c. gain is approximately

$$(R_{23} || R_{22} + R_{21}) / R_{21}$$

which is close to 20 times or 26dB. Capacitor 5 is a non-polar electrolytic and since electrolytics have an increasing impedance at higher frequencies, I connected a $0.1\mu\text{F}$ capacitor in parallel with it.

Components C_7 and R_{24} provide lead compensation and optimize square-wave response; C_7 should be polystyrene, polypropylene or a dipped-mica type.

The next block is the output network, consisting of L in parallel with R_{36} , and the RC network R_{37} - C_{13} . To prevent short circuit of the output with capacitive load and high frequencies, an inductance is in series with the output. This has an increasing impedance with frequency, thus preventing the short circuit. This can cause sustained ringing with a capacitive load, so we dampen the inductance with R_{36} . A suitable coil is shown in Fig. 11 (I used a plastics spacer as a coil former).

Components R_{37} - C_{13} terminate the amplifier resistively at very high frequencies, necessary because loudspeakers represent a very high or uncontrolled impedance at h.f., causing oscillation that can destroy tweeters.

Finally, there are RC networks in each of the supply connections. Although the amplifier has a good inherent ripple rejection, additional filtering is an advantage from the point of view of isolating the two channels. This is especially important at high frequencies, hence the paralleling of the electrolytic with a $0.1\mu\text{F}$ polyester capacitor.

Heatsink assembly

The rest of the components are mounted directly with the output devices on the heatsink assembly.

The power mosfets are high speed devices, and require special mounting and

wiring precautions. The first one is a proper decoupling of the power supply connections directly at the device packages. Again, a combination of electrolytic and polyester capacitors is used for this. The second one is the usual source follower problem of parasitic oscillation with capacitive load: a resistor in series with the gates to prevent this. Resistors R_{39} , R_{40} , R_{45} and R_{46} should be wired directly to the gate pins of the devices.

The uniform current distribution across the die means hot-spots cannot occur and together with the fact that they have a high input impedance enables operation in parallel mode without too much trouble. However, some precautions have to be taken because of the V_{GS} spread. We want to operate them at a quiescent current of 100mA. Unfortunately, the V_{GS} voltage necessary to turn on the mosfet to this drain current varies from device to device.

Ideally, the devices should be matched to within $\pm 10\text{mA}$ at 100mA drain current. But unfortunately, this requires a large number of devices to select from and can only be done in large-scale production. Happily, devices coming from the same production batch (bought at the same time from a distributor and marked with the same date code), seem to be close enough to work satisfactorily in the amplifier. Resistors R_{41} , R_{42} , R_{43} and R_{44} are also helping in equalizing the current at the same time, as they help linearize the characteristics of the mosfets. These resistors should be non-inductive types.

Although the n and p-channel devices are said to be complementary, some parameters are different. One is input capacitance, specified as 900pF for the p-channel and 500pF for the n-channel ones. This difference can influence rise and fall times in the amplifier, make square-wave response a symmetrical, and made stabilizing more difficult.

As we usually do not know the exact value of the input capacitances, we can

Measurements on practical amplifier

Gain	26dB
Input impedance	24k Ω
Output power	120W into 8 Ω 150W into 4 Ω
Harmonic distortion	0.002% at 120W into 8 Ω 0.0065% at 120W into 8 Ω
Slew rate	60V/ μs without input filter
Rise time	1.2 μs without input filter 2 μs with input filter


only make an approximate balancing of these by adding extra capacitance to the n-channel devices, the optimum value found by experiment. Capacitors C_{16} and C_{17} , should be polystyrene or dipped mica, and soldered directly to the gate-source pins of the n-channel fets.



Capacitor C_{15} , together with C_{14} on the p.c. board, make up the compensation shown in Fig. 9. The reason for dividing it into two is to accommodate a wide variety of wiring schemes. A minimum value of around 100pF is needed on the board, the rest does a better job when connected directly at the input of the mosfets. Make them polystyrene types, polypropylene or dipped-mica.

Although not intended primarily for plug-in systems, the p.c. board is made in a standard-size Eurocard format (100x160mm), including a 31pin connector. For simplicity, the input is available at the other end of the board. This makes the layout very straightforward; except for the ground path, the layout follows the circuit diagram very closely. There are two jumpers on the board, both indicated on the component layout.


Thermal resistance should be around 0.5deg C/W per channel, which allows the amplifier to operate at a very high average output power continuously. A 150mm piece of a standard SK47 extrusion, with a T or L-bracket to mount the mosfets on, works fine. If the possibility for continuous operation with very low impedance loads exists (less than four ohms), it is a

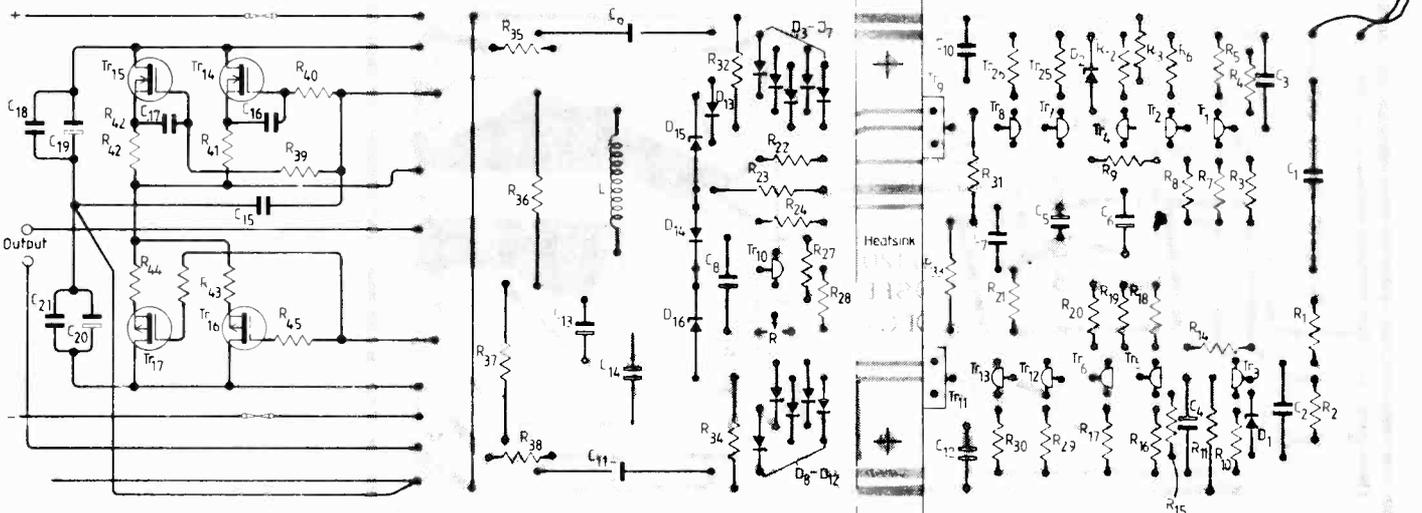Transistors 9 & 11 need heat dissipators - either a standard extrusion (SK09) or an L-bracket can be used.



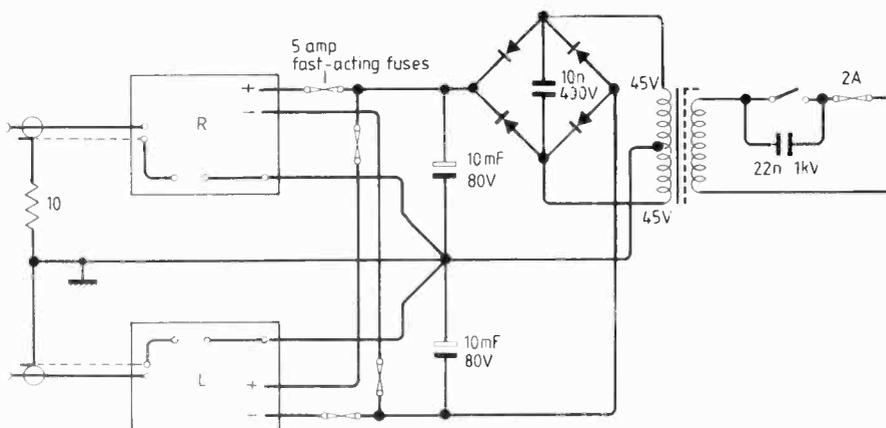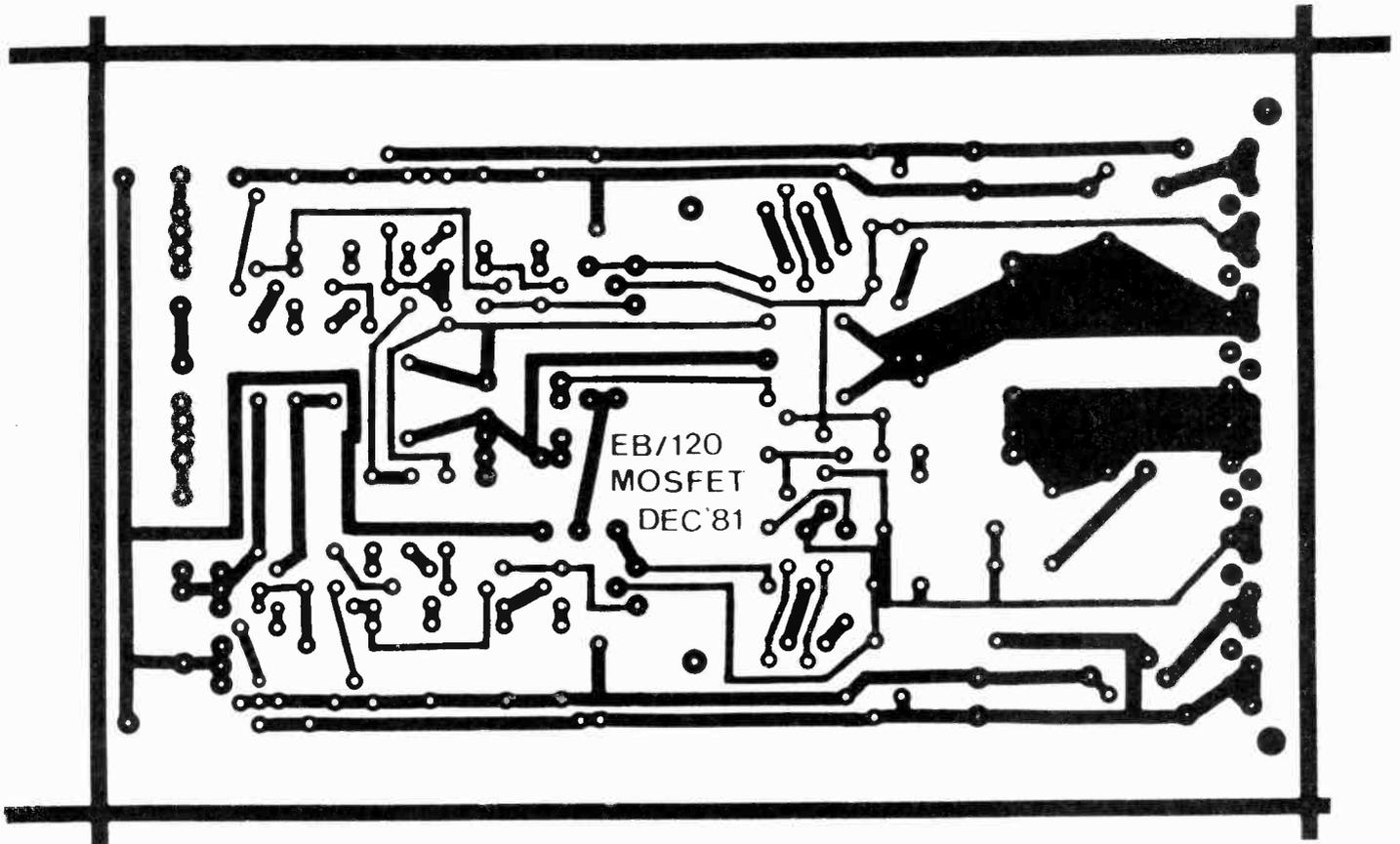

The grounding scheme is flexible in that output ground and input ground are not connected together on the board. This makes it very simple to adopt a number of wiring schemes: a proposed wiring diagram for a stereo amplifier using a common power supply is shown. Using the boards with separate supplies, output and input ground can be connected together, which gives the best signal/hum ratio in a system.

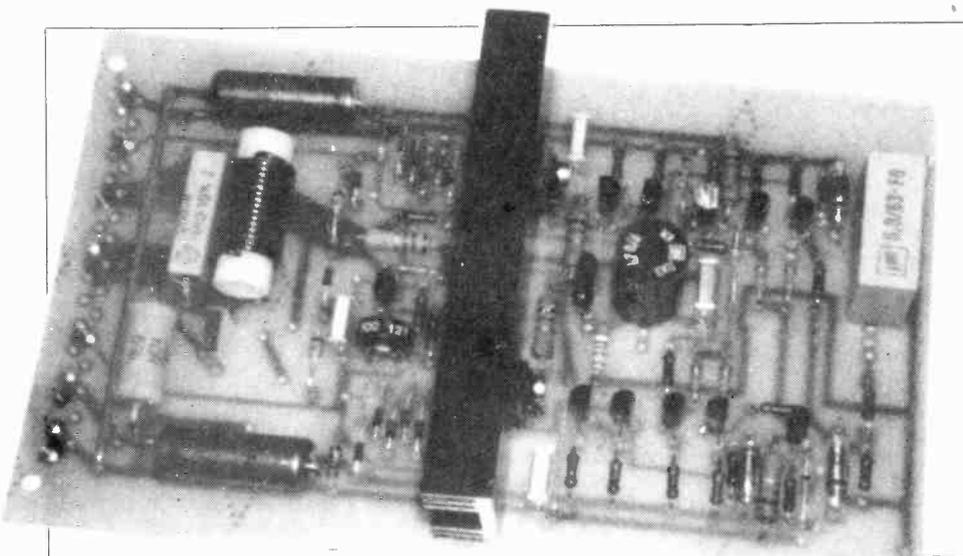

The author

In 1973, Erno Borbely joined Motorola in Geneva as a senior applications engineer, responsible for audio and radio. He worked mostly on low-noise circuit design and on power amplifier circuits, and some of the ideas formulated there later found their way into the products of the David Hafler Co., which he joined in 1978 and where he designed the DH-200 mosfet power amplifier.

He'd previously got a degree in electronic engineering from the Technical University of Norway in 1961 and for seven years worked for the Norwegian Broadcasting Corporation designing professional audio equipment. In 1969 he moved to the U.S. to work for David Hafler at Dynaco.

He now works in Furstenfeldbruck as National Semiconductors european training manager.

good idea to put thermal breakers on the heatsinks with a cut-out temperature of about 75°C.

Plus and minus 57V supplies are needed for 120W into an eight ohm load. Assuming a 10% transformer regulation, the no-load voltage should be $\pm 63V$. This translates into a transformer with a $2 \times 45V$ secondary, and rated at 500VA, toroidal for minimum hum. The filter capacitors must be at least 10mF each, rated at 80V. The bridge has a rating of 30A with a surge rating of 300A. 

References

1. D. G. Daugherty & R. A. Greiner. Some design objectives for audio power amplifiers. *IEEE Trans.* vol. AU-14, no.1, March 1966.
2. J. Linsley Hood. 80-100 watt mosfet audio amplifier. *Wireless World*, June 1982. 

Spread spectrum communication system for civil use

Considering the present congestion in civilian communication bands more efficient use by exploiting the multiplexing capabilities of spread spectrum systems should be welcomed. High complexity – not a problem for space and military systems – can be avoided by reducing the number of electrodes in the surface wave devices.

The h.f. band is one of the most congested parts of the spectrum, and also suffers from multipath and flat fading. Spread spectrum systems would be particularly useful in this field. The spread-spectrum technique is a modulation method in which the bandwidth used is much greater than that required by the message. To be classified as spread spectrum, the modulated signal bandwidth is at least 10 to 100 times the information rate, and the information itself should not be a factor in setting the modulated signal bandwidth. The result is very low signal-to-noise ratio which makes reception of the signal complicated. This is the major problem to be encountered. Various methods of synchronization and demodulation have been suggested and tested without really solving the problems of high synchronization delay and the difficulties of maintaining synchronization.

Considering its potential advantages and the wide coverage of h.f. the research being carried out in this field is very limited, and deserves more investigation. Though spread-spectrum has its own characteristic problems, it offers the kind of promise which could revolutionize communication technology, by offering channel multiplexing for more efficient use of the spectrum; antijam capability; low detectability by an unwanted receiver; accurate ranging; and inherent multipath rejection.

Antijam capability can be proved directly from Shannon's equation of channel capacity $C = W \log_2(1 + S/N)$, where W is bandwidth and S/N is signal-to-noise ratio

$$C = W \log_e(1 + S/N) \log_2 e.$$

When $s/n \ll 1$, that is for low signal-to-noise ratio as is always the case with spread-spectrum,

$$\log_e(1 + S/N) = S/N - (S/N)^2/2 + (S/N)^3/3 \dots \approx S/N, \text{ and } C = 1.45W(S/N).$$

As the bandwidth is increased more jamming power N will be required to effectively jam the signal.

Multiplexing capability. Each channel user has a unique pseudo-random sequence code assigned which has very low cross-correlation with pseudo-random sequence codes assigned to others using the same channel. Receivers are designed to use a local code generated to produce an

find a sufficient number of orthogonal codes of the same length. There is no rule available for predicting the mutual cross-correlation performance of sets of pseudo-random sequences. One rule of thumb that can be used in the choice of sets of sequences is to examine the factors of the length of the sequence. Sequence lengths that have small factors are almost certain to exhibit large values of cross-correlation between some pairs of the possible sequences. Sequence lengths that do not have small factors are relatively free from high values of cross-correlation.

The importance of orthogonality between codes in the same channel is made clear by the following example. Suppose $f_1(t), f_2(t), \dots, f_n(t)$ are the several spreading sequences used by different users of the channel. Each user is using the different signals $s_1(t), s_2(t) \dots s_n(t)$ to modulate their respective data. The modulation is done by multiplying the signal with the spreading sequence e.g. $s(t) * f(t)$. When these are sent over a channel the resulting overall channel signal is

by Noman Mahmood M.Sc.

identical pseudo-random binary code as transmitted by a particular user to correlate the received sequence. When properly synchronized the result is an autocorrelation of the particular code as the output of the correlator. Interference produced by other user's codes is spread out by the action of the multiplier in the correlator.

The problem of the multiplexing is to

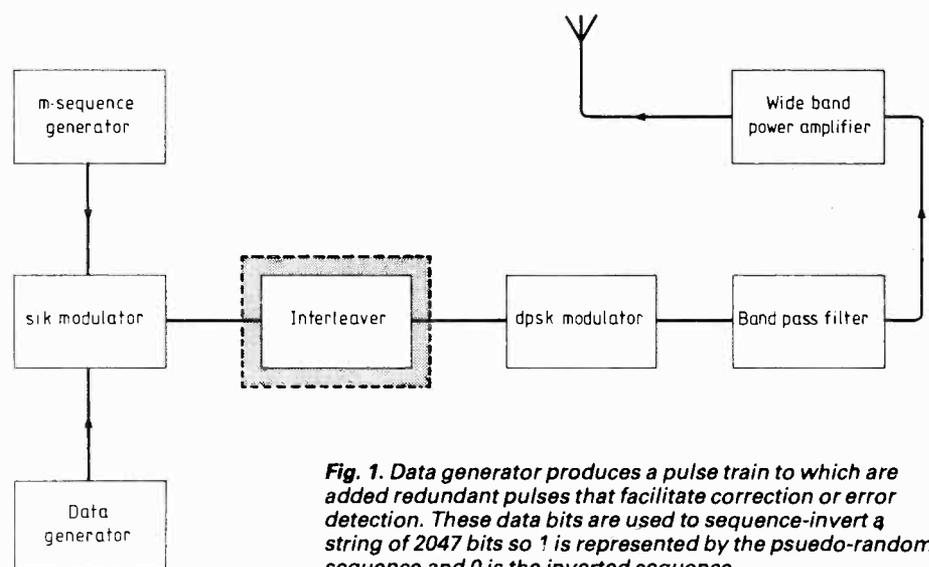


Fig. 1. Data generator produces a pulse train to which are added redundant pulses that facilitate correction or error detection. These data bits are used to sequence-invert a string of 2047 bits so 1 is represented by the pseudo-random sequence and 0 is the inverted sequence.

Properties of pseudo-random sequence

In any spread-spectrum system, the base-band signal is spread over the channel with the help of a pseudo-random sequence, even though the actual system may differ according to what method is used. A pseudo-random (pn) sequence is chosen because of its excellent two-valued autocorrelation function which aids in correlation detection, its noise-like properties, as well as certain other characteristics.

- Any cyclic shift of a pseudo-random sequence is also a pseudo-random sequence.
- Any sequence may be generated by a maximal sequence (m-sequence) generator polynomial, provided the polynomial is irreducible and prime. The polynomial can be represented by

$$C(x) = \sum_{i=0}^{n-1} b_i x^i, \text{ where } b_i = 0, 1.$$

- If a sequence is generated by a polynomial of degree n and a window of width n is slid along a sequence, each of the $2^n - 1$ non-zero binary n -tuples is seen exactly once.
- Any sequence contains 2^{m-1} ones and 2^{m-1} zeros, that is the number of ones and zeros differ by one in a sequence.
- The modulo-2 sum of two sequences is another sequence.
- The modulo-2 sum of a sequence and a cyclic shift of itself is another sequence.
- The autocorrelation function of a sequence of length $2^n - 1$ is given by $P(0) = 1$, $P(1) = -1/n$ for $1 \leq i \leq 2^n - 2$, where n is an integer and $P(1)$ is normalized autocorrelation. The normalized cross-correlation of two such sequences is measured by $(A-D)/(A+D)$, where A is the number of agreements between bits, and D is the number of disagreements between bits. If we modulo-2 add two sequences the number of zeros would be the bits that agree and the number of ones are the bits that disagree. The distance between two codes is defined by the total number of bits that disagree. If p is the number of bits that agree and d is the distance between two sequences, then it is possible to find an expression for the normalized correlation in terms of distance between the codes as follows. From the last expression, normalized correlation is thus $(p-d)/(p+d)$. If the total number of bits in a sequence is N then the normalized correlation is

$$((N-d)-d)/N = (N-2d)/N = 1 - 2d/N,$$

where d the distance between codes. The distance between two codes always remains the same and constant even after cyclic shift.

$s_1(t)f_1(t) + s_2(t)f_2(t) + \dots + s_n(t)f_n(t)$. If a receiver is to retrieve $s_1(t)$ the signal would be multiplied by $f_1(t)$ giving an output

$$s_1(t)f_1^2(t) + s_2(t)f_2(t)f_1(t) + \dots + s_n(t)f_n(t)f_1(t).$$

If $f_i(t)$ are chosen so that they are orthogonal, then

$$f_i^2(t) = 1 \text{ for } i=j, f_i(t)f_j(t)f_k(t) = 0 \text{ for } i \neq j$$

so that $s(t)$ will be the output of the coherent detector. Hence each receiver can retrieve its particular signal with the knowledge of the particular transmitter signature or pn sequence.

Low detectability. The processing gain in a spread spectrum is defined as the ratio of the r.f. spread bandwidth W_{rf} to the mes-

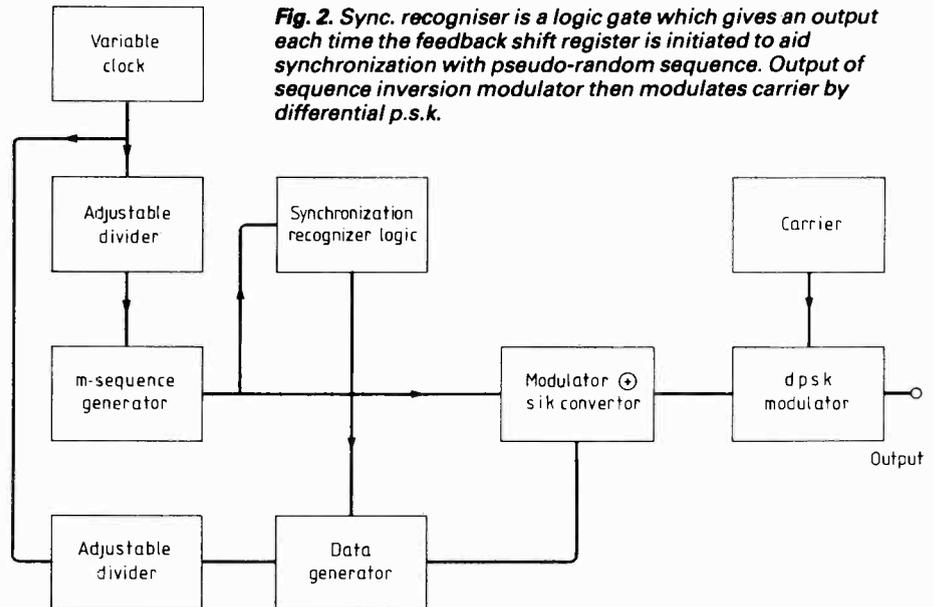


Fig. 2. Sync. recogniser is a logic gate which gives an output each time the feedback shift register is initiated to aid synchronization with pseudo-random sequence. Output of sequence inversion modulator then modulates carrier by differential p.s.k.

sage bandwidth W_b or $PG = W_{rf}/W_b$. Expressed as a time bandwidth product substituting $T_b = 1/W_b$ gives $PG = T_b W_{rf}$. If $(S/N)_b$ is the bandwidth needed by a conventional receiver then the signal-to-noise ratio that a spread-spectrum system can operate on is $(S/N)_{rf} = 1/PG * (S/N)_b$ on account of the processing gain. So the detectability is reduced by $1/PG$, which is enormous.

Multipath rejection comes about due to the method of detection used and the autocorrelation property of the sequence. The pn sequence has only two values for its autocorrelation in different phase shifts of the sequence. Now a delayed version of the pn sequence reaching the correlator would be out of phase with the locally generated pn sequences used in the correlator. This would not be detected as the output would remain low due to the low autocorrelation.

Engineering details

The h.f. band is one of the most congested of all; it also suffers from the multipath effect and flat fading. Spread spectrum systems would be particularly useful here.

An h.f. radio link is a time-varying channel in which the attenuation and delay characteristic vary with time. This is called frequency-selective fading, and can be a serious source of error. The main cause of additive noise is atmospheric noise caused by lightning discharges, occupying a frequency from v.l.f. to around 30MHz at the input to the radio receiver.

Fading rates for both flat and frequency selective fading are normally in the range of 4 to 15 fades per minute. The flat fading may vary from 0 to 70dB, so a.m. is not suitable. Suppressed-carrier a.m. when binary coded is equivalent to p.m. Both f.m. and p.m. may be used at h.f. satisfactorily, with p.m. requiring less bandwidth than f.m. To overcome the phase ambiguity inherent in a p.m. system, data is differentially encoded before phase shift keying is used, which is actually binary p.m. A phase ambiguity occurs in the receiver as absolute phase reference is not available.

This is called differential phase shift keying and uses 180° phase shift of the carrier to represent a 1 and zero phase shift for 0.

A problem that is faced in any kind of modulation scheme is pattern noise. This is due to the fluctuating sidebands caused by the data modulation and becomes especially important when extracting the carrier from the signal. The fluctuating amplitude of the sidebands is attenuated by the carrier filter but the remaining phase fluctuations are irremovable. It exists even if the incoming signal is perfectly free of noise.

A major drawback with multi-user spread spectrum systems is their proneness to self-jamming. If all the received signal amplitudes are approximately the same at all user locations, then the correlation processing gain of the receiver is sufficient to clearly detect each signal separately. In practice however the distances between various users in a multi-user system vary widely and correspondingly the signal strengths vary widely, resulting in jamming of the weaker ones. This situation is commonly referred to as the "near and far problem".

The problem can be reduced by the use of a modulation format that includes a modest amount of signal spreading with signal encoding, while the remainder of the spectrum spreading is accomplished by rapid frequency hopping of the signal in a predetermined sequence over the total band of interest.

Transmitters

The most popular type of spread spectrum system is the direct sequence system where a pseudo-random sequence is used to spread data. Other methods are frequency hopping, time hopping, or a hybrid between these two. In frequency hopping a sequence switches a frequency synthesizer to hop to different frequencies it switches onto.

The method studied here is the use of direct sequence spreading using sequence inversion-keying modulation at baseband,

with differential phase-shift keying for transmission. The sequence inversion keying of the pseudo-random sequence by the data is achieved by modulo-2 addition of the data with the sequence at a rate $1/T$, where T is the stretch of one sequence. Sequence inversion keying gives optimum protection against inter-symbol interference and bit error because the detection of half of the sequence provides the decision on the data received. The d.p.s.k.-modulated signal is then passed through a band-pass filter to conserve power, and amplified before radiation in the electromagnetic field.

A "data generator" produces a train of pulses carrying the information, to which are added a fixed number of redundant pulses to facilitate the correlation or detection of errors by the receiver. These data bits are used to sequence-invert a string of 2047 bits, so the 1 is represented by the pseudo-random sequence and 0 is the inverted sequence.

The m-sequence generator is a well-known technique. For a feedback shift register of N bits the sequence produced is of length $2^N - 1$. The taps of an eleven-bit feedback shift register was modulo-2 added in a feedback loop to produce the 2047 pseudo-random sequence. The polynomials that would generate the sequence of this length are

$$\begin{aligned}
 &1+x^4+x^{11}. \\
 &1+x^2+x^5+x^8+x^{11} \\
 &1+x^2+x^3+x^7+x^{11} \\
 &1+x+x^4+x^9+x^{11} \\
 &1+x^9+x^{11}
 \end{aligned}$$

The last polynomial offers least complexity in hardware terms.

The sync recognizer in Fig. 2 is a logic gate which gives a pulse each time the initial state of the feedback shift register is reached. The data are synchronized with the pseudo-random sequence with the help of these pulses. The output of the sync modulator is then used to modulate a carrier by differential phase-shift keying. The clock pulses for all these sequential logic circuits are derived from a stable crystal clock by passing the output through a Schmitt trigger and then dividing down to the required frequencies. The output of the d.p.s.k. modulator is applied to a band-pass filter to restrict power requirements for transmission as well as spill-over into adjacent channels.

Other methods of encoding using pseudo-random sequences include modulating a long sequence with a shorter one to enable use of a short surface-wave matched filter, use of a recirculation loop or charge-coupled devices to reduce synchronization time at the receiver, and the use of a shorter section of the sequence that is a multiple of the number of bits in the f.s.r. used to generate the sequence along with a recirculation loop to enhance the output.

Receivers

The most complicated part of a spread spectrum communication system is the receiver.

It has to perform under the difficult conditions of

- very low signal-to-noise ratio, as low as 30dB
- time uncertainty of receiver sequence-complicated synchronization circuits required
- maintaining synchronization after it is achieved is difficult so code-tracking circuits are required.


So the design of carrier extraction, clock recovery and demodulation must be such that it can operate at the very low signal-to-noise ratio that is available. The block diagram in Fig. 3 gives a simplified version of the receiver. The operation of each box on the signal input is described below, headed by the labels in the diagram.

Band-pass filter following the down-converter has a bandwidth centred at W_{if} and just wide enough to let the data components pass through. This slices off the unnecessary interference and allows the i.f. amplifier to operate efficiently.

Demodulator. In search of a d.p.s.k. demodulator which can operate under low signal-to-noise ratio, two sorts of demodulators are favourable - Costa's loop and the squaring loop. They have similar performance, but Costa's loop has some implementation advantage even though tuning is a little more difficult as the two arms (Fig. 4) have to be accurately balanced for satisfactory performance. Once acquired a signal should be introduced to hold the input to the voltage-controlled oscillator steady.

Surface wave filter and recirculation loop. The main purpose of using a surface matched filter and recirculation loop is to

Fig. 3. Design of carrier extraction, clock recovery and demodulation must allow operation of very low s/n route. See text for box descriptions.

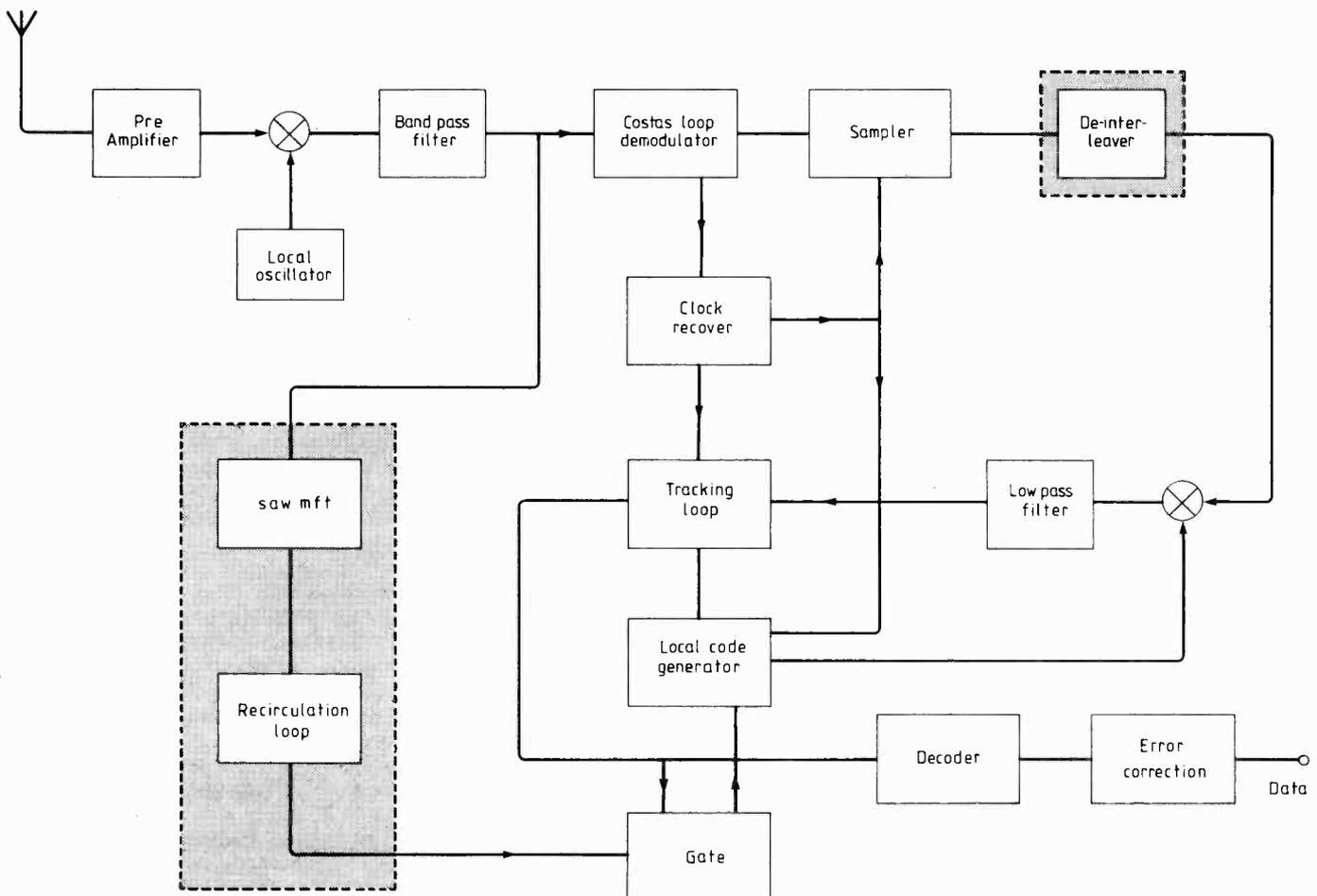

achieve code synchronization so that the local code generator can be synchronized with the received code. As soon as code synchronization is obtained, the tracking loop is switched on and decoding by correlation begins. Further description of acoustic surface-wave matched filters is given later.

A tracking loop is needed to stay in lock with the signal. There are two main methods: a tau-dithering loop, and a delay lock loop; the first time-shares a signal correlator, whereas the other uses two separate correlators. They have been found to have almost similar performances: assuming ideal bandpass arm filter the tau-dither loop requires approximately 1dB more S/N than the delay-locked loop, for equal r.m.s. tracking jitters. In a delay-lock loop two local reference signals are generated differing only by a time delay and may be extracted by tapping two adjacent bits in the feedback shift register generating the local sequence. This is used to correlate with the incoming signal. The correlation between output of each correlator is a triangular function two bits wide. Once the system is synchronized and tracked the rest of the operation uses more-or-less conventional circuits.

The received signal is digitally correlated with a locally generated signal and the output filtered. If more than half of the received bits are in error then it is considered to represent the inverted sequence and if they are correct it is a true sequence. The composite correlation function for a delay-lock loop has a double-peaked triangular shape before summing in which one half of the double triangle is inverted so that the composite correlation has a linear region centred around the point half way between the two correlation maxima. When the summed output is filtered and used to control the receiver's voltage controlled oscillator, the receiver's code will track the incoming code at a point half way between the maximum and minimum of the composite correlator output (Fig. 5). A serious consequence of spectrum spreading is the complexity of the signal processing required to extract the useful information.

With a direct sequence method, the longer the sequence used to spread the data energy, the greater is the security of the system as it resembles noise more closely. But this increases the synchronization problem enormously; with a conventional digital correlator it would take from seconds to half an hour before synchronization is achieved.

Other methods, such as the use of a combination of shorter sequences to form a long one called Gold's code, can be used. The system would then have to look for one of these short codes which would shorten the sync time to some extent; it would also be easy for intruders to synchronize their systems too.

One possible way out is to use a long code, then a matched filter to match a section of the long code. A matched filter requires an accurately synchronized clock to clock the bits in. A small Doppler shift may result in part of the signal being

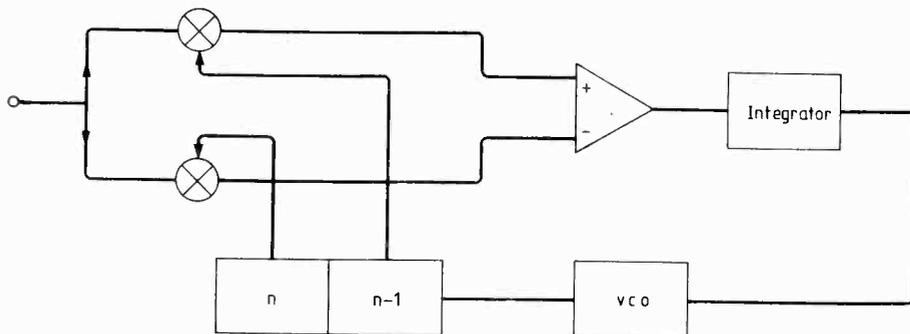


Fig. 4. A d.p.s.k. demodulator that can operate under low s/n ratio is the Costas loop, which requires accurate balancing of the two arms. Loop filter is similar to that used in phase-locked loops.

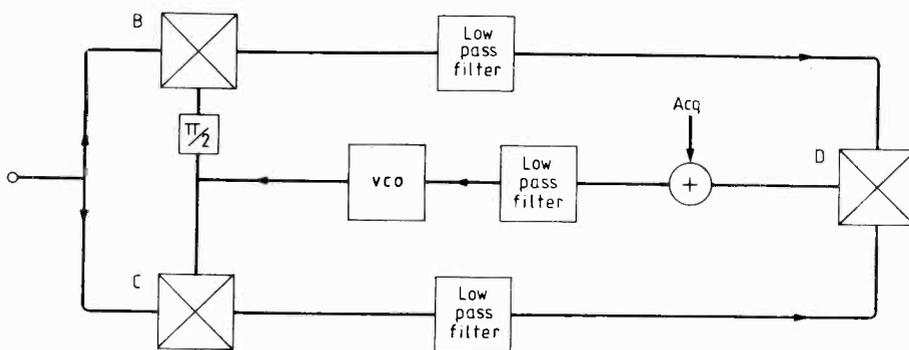


Fig. 5. Received signal is digitally correlated with local signal and filtered. If more than half of the bits are in error it is taken to represent the inverted sequence, and if correct it is a true sequence. The composite correlation function for a delay-lock loop has a double-peaked triangular shape before summing in which one half of the double triangle is inverted so that the composite correlation has a linear region centred around the point half way between the two correlation maxima. When the summed output is filtered and used to control the receiver's voltage controlled oscillator, the receiver's code will track the incoming code at a point half way between the maximum and minimum of the composite correlator output.

matched at one shift and the remainder at the next shift, so that instead of one high peak one obtains two smaller peaks. To avoid this difficulty the shift register may have $2N$ stages and be clocked at a rate of twice the frequency of the encoder. The match in this case will not be spoiled for fractional Doppler shift in frequency as large as $D = \pm 1/4N$, where $D = 2v/C$.

Acoustic surface wave matched filters have the potential to revolutionise spread spectrum systems. They can be used for analogue matched filters which require no clocking. But the problem is that the longer the code to be matched the greater the cost of fabrication.

Comparison between surface wave and charge transfer filters.

	Surface wave	Charge transfer
Centre frequency	10M to 1GHz	20MHz max
Insertion loss	6dB min	nil
Storage time	depends on length	1s
Length limited by Signal bandwidth	losses	c.t. eff. (<2)
	50kHz to 0.4f.	< 1/2 clock

Another sort of long-transversal-type matched filtering may be possible with the help of charge-transfer devices. The principle advantages of c.t.d. transversal filters are tunability and flexibility in spectral characteristic. Filter length is limited by tap-weight inaccuracy and weighting-coefficient error poses a severe limitation on many applications.

If the sequence is of length 2047 bits then the surface-wave matched filter must have pre-programmed or programmable 2047 electrodes plus the launcher electrodes. This increases the fabrication problems, though when used this would give excellent two-valued autocorrelation. So a study was made to reduce the number of electrodes in the matched filter.

In a sequence of length $2^m - 1$ bits any section of m bits will appear only once. Called the "window effect", this property is true because the polynomial is primitive, which also implies that if n is an integral number then any consecutive length of mn bits would occur only once. With the help of a computer program, a sequence of length 2047 was generated. Out of these 2047 bits generated by an 11 bit shift register for the length $N = 2^m - 1$, a set of 11 bits were picked up at random. This set was then slid along the sequence of 2047 bits

and the normalized correlation function at all positions calculated. This was tabulated along with the number of times certain values occurred

$$\frac{\text{agreements} - \text{disagreements}}{\text{total number of bits}}$$

Sliding correlation for m=11 bits with 2¹¹-1=2047 in sequence.

Normalized correlation of random 11 bit window	Number of times value occurs
1.00	1
0.81	10
0.63	55
0.45	165
0.27	330
0.09	461
-1.00	1
-0.81	10
-0.63	54
-0.45	160
-0.27	329
-0.09	460

The correlation values are pretty well balanced due to the random characteristic of the occurrence of 0s and 1s. If an eleven-bit matched filter correlates the 2047 bit sequence, the outputs would appear proportional to the correlation values. As the maximum value of 1.00 occurs only once (the autocorrelation function of the 11 bits) and if this can be detected in the output it would drastically reduce the synchronization delay, at much reduced hardware complexity. Unfortunately the next lower value is 0.81, and this occurs ten times in the sequence and would give high sidelobes. In the case of high Gaussian noise it would result in many false alarms.

A second study was made with a randomly picked window of length nm where n=2 i.e. of length 22 bits. The table shows the highest correlation achieved:

Normalized correlation of random 22 bit window	Number of times value occurs
1.00	1
0.72	1
0.63	2
0.54	8
0.45	31

So this tends to give slightly improved sidelobe-to-signal characteristic, as expected.

A third program attempted to reduce the sidelobes. This picks up two 11 bits adjacent to each other. If R1 is the value of the correlation of the first 11 bits with the section of the main sequence and R2 for the next 11 bits, then R=R1*R2 is the output of the simulated correlator. This gave some interesting results. The sidelobes were drastically reduced. Also the number of occurrences of the sidelobes or high correlation is much reduced. So most of the time the output remains pretty low, as tabulated below:

Normalized correlation of random 11 bit window	Number of times value occurs
1.00	1
0.52	2
0.40	2
0.37	2
Remainder ≤ 0.28.	

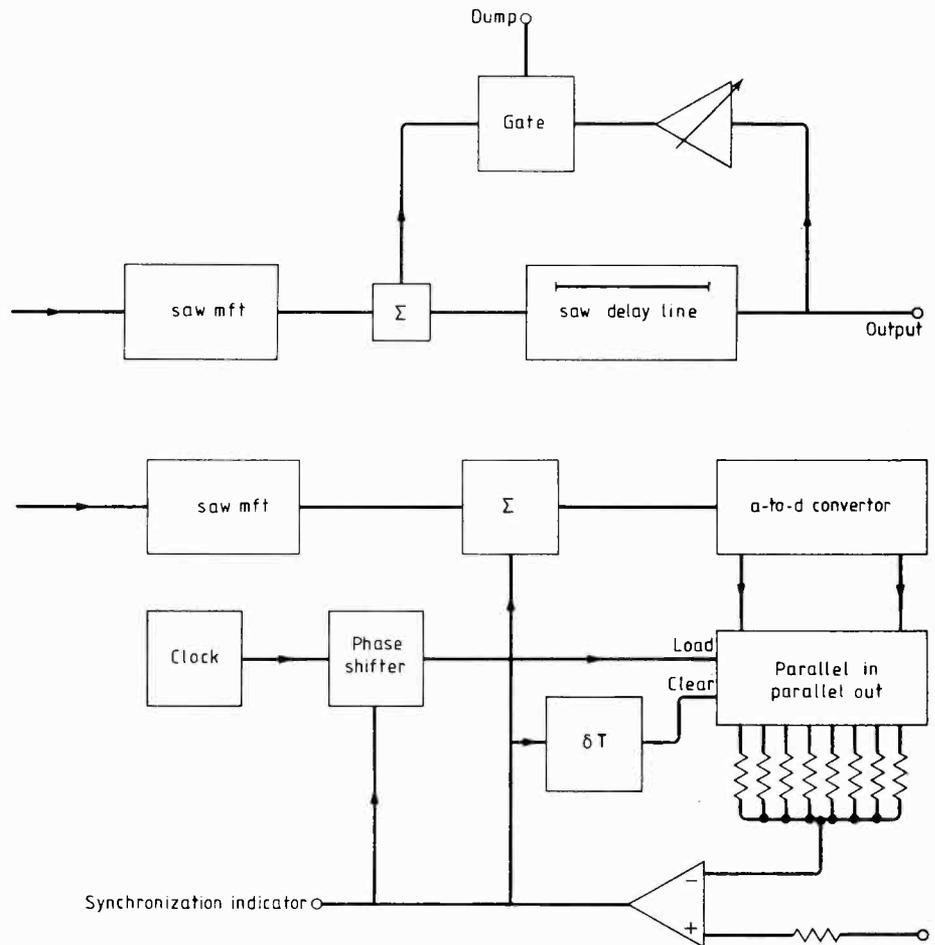


Fig. 6. Recirculation loop enhances otherwise noisy output. As data rate is fixed, section of the sequence appears after a fixed time T. The first output is delayed by T so that it reaches the input of the summer at the same time as the next output of the filter arrives. The output of the summer would go on increasing until a threshold is reached, when the gate would open and sync achieved. A t.t.l. version of the recirculation loop is shown at bottom.



After obtaining an M.Sc. in electronics from the University of Kent at Canterbury, Norman Mahmood worked at the same place as an Experimental Officer for three years. He is presently working as Development Engineer with Chalwest Ltd, subsidiary of the Ladbroke Group, dealing with microprocessor control systems.

It may therefore be possible to reduce the number of electrodes required in a surface ware device by using two 11-bit matched filters and multiplying the outputs, thus drastically cutting down on the cost of having a long matched filter. In practice the effect of noise would reduce performance of such a device. The output may be amplified using a conventional amplifier, but this would also amplify the noise and sidelobes.

A method using a recirculation loop as in Fig. 6 may be used to enhance the output. As the data rate is fixed our section of the sequence appears after a fixed time T. The first output is delayed by T so that it reaches the input of the summer at the same time as the next output of the filter arrives. The output of the summer would go on increasing until a threshold is reached, when the gate would open and sync would be achieved. False sync cannot occur as it will have to be caused by random errors which do not always occur at the same time. A t.t.l. version of the recirculation loop also shown.



NEW PRODUCTS

MEASURING WOW AND FLUTTER

For use in the servicing and testing of recording and sound studio equipment, the Bang & Olufsen wow-and-flutter meter has been improved by the inclusion of a high-stability, crystal-controlled 3.15kHz oscillator for very accurate measurements. Wow from 0.2 to 10Hz, flutter from 10 to 300Hz or wow and flutter combined can be measured linearly or weighted to an accuracy of 0.003%. Drift in speed may be measured from 0.03% to 20% relative to the oscillator frequency.


The WM 1A meter includes a frequency spectrum analyser which can determine which wow or flutter frequencies are dominant and thus help to point to any faulty rotating component, be it idler, belt drive, motor or bearings, etc. The meter costs £682 from David Bisset Ltd, 52 Luton Lane, Redbourn, Herts AL3 7PY.

WW301

SOLID-STATE RELAYS

The Sigma range of relays are capable of switching 10A a.c. loads and remaind unharmed by surges of up to 60A. The design guarantees leakage to be less than 1mA and meets standard requirements for isolation when used in 120 or 240V line applications. The relay is mounted on a heat-sink base which is isolated and has TO-3 spacing for mounting on external heat sink or chassis. Input control voltages range from 3 to 24V with a drive current of 6mA. This, combined with zero-crossing switching eliminates interference and enables the relays to be operated by microprocessor or t.t.l. logic circuits. Zero-crossing switching makes the relays useful in filament lighting applications, providing them with high-speed starting. Unimatic Engineers Ltd, 122 Granville Road, London NW2 2LN.


WW302

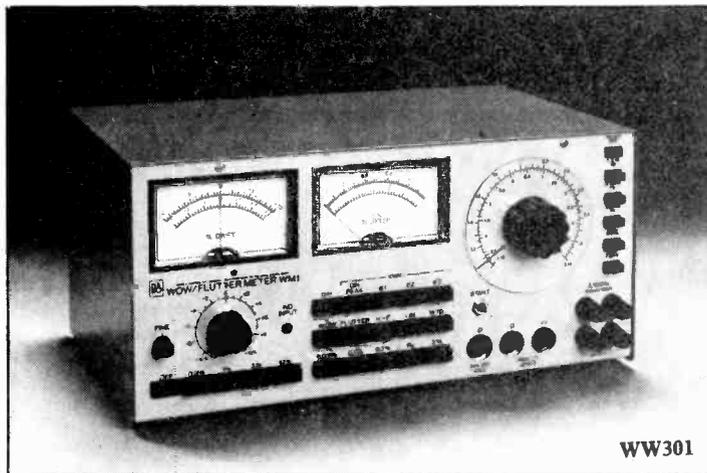

WW301

UNISEX CONNECTORS

It is no longer necessary to specify male or female when the Jaguar power connectors are used. The manufacturers describe them as hermaphrodite and the contacts are the same for both halves of a connected pair. Wires do not need to be stripped of insulation, as the

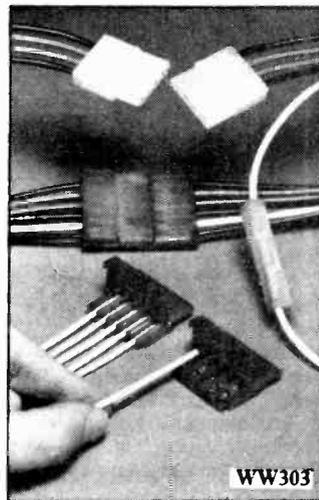

WW303

contacts pierce the insulation when the wires are installed. Various wire gauges may be used in the same connector which is rated at 12A. Various colours are available to indicate which pairs are connected. Different connectors can accommodate one to six wires and various colours are available to identify which pairs are connected. The nylon connectors slide together and are provided with a keyway to hold them. Methode International Inc, PO Box 98, Berkhamsted, Herts HP4 2AT.


WW303

MINI LASER TUBES

Intended for use in compact alignment and aiming systems the CWR LTRG is a miniature HeNe laser tube with an output power of greater than 1mW t.e.m. It gives a 0.64mm diameter output beam with divergence of 1.27mrad. It requires 1150V at 3.5mA to operate and a suitable battery power supply is available. Because of its sturdy construction, the tube may be used in conditions where it may be subject to extreme shock. Laser Lines Ltd, 19 West Bar, Banbury, Oxon OX16 9SA.

WW304

WW304

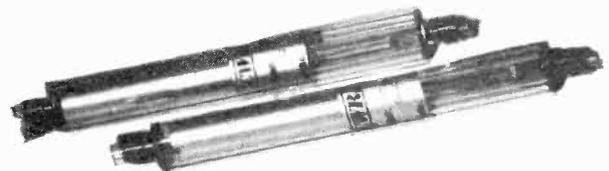

COMPUTING METER

Based around a 6502 microprocessor, the Thurlby DM 1905a is a 5½-digit bench multimeter with extensive calculating and data-storage facilities. There is 8K of rom which is used to control the a-to-d converter, the display and keyboard, and all the calculating functions.

A full range of measuring functions is available: direct voltage from 1µV to 1,100V; alternating voltage from 10µV to 750V; resistance from 1mΩ to 21MΩ; d.c. from 1nA to 5A and a.c. from 10nA to 5A. Accuracy over a year is 0.015%.

Twenty keys are built in to give

access to the computing functions, which include linear scaling with offset, percentage deviation, limits comparison, offset zero, dB and general logarithmic calculations. Automatic data logging is available and up to 100 readings can be stored in memory at programmed intervals. The meter can keep a running average and the highest and lowest of a set of readings. Priced at £298 (+ v.a.t.), Thurlby claim that the meter is in the same bracket as many general purpose d.m.ms that don't have the computing facility. Thurlby Electronics Ltd, Coach Mews, St Ives, Huntingdon, Cambs PE17 4BN.

WW305




WW305

EEPROM CHANGES A WORD AT A TIME

Designed as a replacement for circuit board d.i.p. switches, as may be used in computer terminals, present calibration references in instruments, and intelligent control applications, the ER5901 is a 1k-bit word-alterable electronically erasable prom. It operates at 5V in all modes and has an automatic erase/write cycle, data and address latches are on the chip. Access time is less than 250ns and the minimum data retention capability (how long it remembers) is 10 years. General Instruments Microelectronics Ltd, Times House, Ruislip, Middlesex HA4 8LE.


WW306

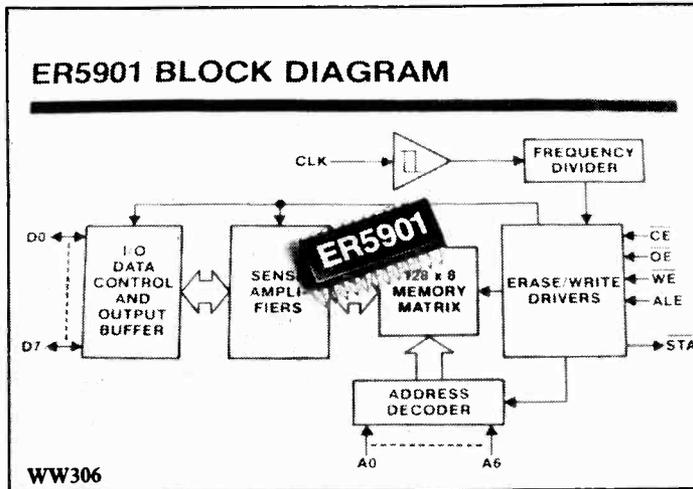

WW306

AREA METER

A standard c.c.t.v. camera can be used to measure the area of an object or any image that can be seen in high contrast. The Delta-T area meter displays the area in view, a cumulative total of the areas measured and the number of measurements. Objects moving past the camera can be automatically measured and counted. The readings can be transferred by a digital interface to

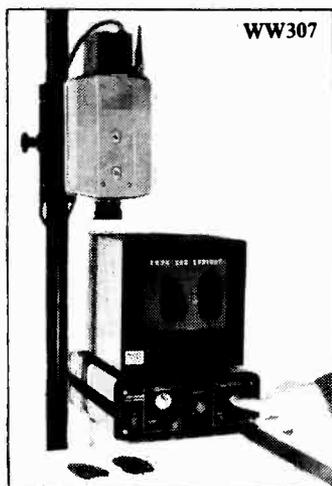

WW307

an alarm system for use with process control.

Applications for the meter include industrial control, the measurement of photographs, for example X-rays, the counting and sizing of many things including fish (!), the lengths of roots, studies of diseased leaves, etc.

For those with tv equipment the meter costs £440. It is available as a complete system including tv camera and monitor, camera stand

and light box for £990. Prices exclude v.a.t. and freight. The company that manufactures the meter is a workers' co-operative wholly owned and controlled by its nine members. It has expanded in 12 years from its one founder member. Delta-T Devices Ltd, 128 Low Road, Burwell, Cambridge CB5 0EJ.

WW307

TV SOUND RECEIVER

Assuming that a large number of viewers also have hi-fi equipment, Kingsbrook Marketing have designed and developed a tv sound tuner to take full advantage of the transmitted sound by feeding sound to the hi-fi amplifier with a re-modulated r.f. signal to the tv. They claim to use a very high quality tuner which includes a surface acoustic-wave filter. There are six preset channels, of which one may be used for a video recorder. The audio frequency response is 30Hz to 12kHz \pm 1dB with a total harmonic distortion less than 1%. The tuner incorporates the National Semiconductor dynamic noise reduction (DNR) integrated circuit, and also Viosound, a method of spreading the output between two speakers to give a spacious sound quality.

The r.f. output to the tv set is at a fixed frequency (channel 36) so channel switching is transferred to the new tuner. This eliminates the sound distortion of the picture in high signal areas. Its full title is the VT1000 Tele Video Tuner and is available from a number of audio dealers at £99.50. Kingsbrook Marketing Co Ltd, 29 Heathfield, Stacey Bushes, Milton Keynes MK12 6HR.

WW308


VIDEO COLOUR BALANCE METER

In our item on the Invotron Meter (January) it was stated that the meter is used *with* an oscilloscope. In fact it is designed to be used *instead* of a 'scope and, being hand-held, is useful where it is not convenient to use an oscilloscope to check the illumination level for tv studios or outside locations. Invotron, of Dublin, have informed us that the meter is now available in the UK through Shipping Services Ltd, 9/15 Grundy Street, Liverpool L5 9YH.

WW309

MAINS FILTER FOR MICROCOMPUTERS

Spikes and holes in the power supply can cause havoc in a microcomputer. Programs or data can be lost or corrupted. A solution is provided in a mains filter from Power International; fitting into an enlarged 13A plug it is called 'The Plug'. It provides mains voltage, up

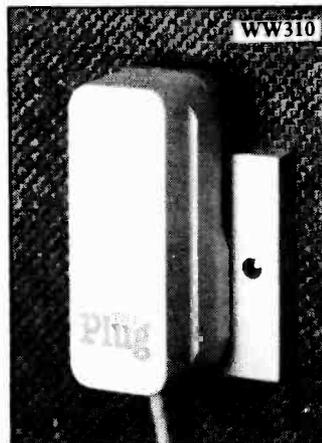

WW310

to 4A current and as well as transient suppression it also protects against radio-frequency interference. The Plug may be used on any portable electronic equipment which may need such protection. It costs £15.50 inclusive from Power International Ltd, 2A Isambard Brunel Road, Portsmouth, Hants PO1 2DU.

WW310

HYBRID ASSEMBLIES

A prototyping service of hybrid circuits using leadless passive components and semiconductors directly mounted on to printed wiring boards, is offered by AB Microelectronics. The process has been developed to provide low power circuitry where miniaturization is essential at low cost. This is possible because of the mechanized assembly methods used.

The degree of miniaturization is comparable to that of thick-film circuits, though the temperature range is restricted to 0 to 85°C for the FR4 circuits. Polyimide circuits have a greater range. The packages have leads at 0.1 in. pitch for both single and dual in-line styles. AB Microelectronics, Dinas, Rhondda, Mid Glamorgan.

WW311

C.R.T. POWER

A power supply specifically for use with high-definition cathode-ray tubes has been developed by Wallis Electronics. The three outputs are for the main anode (10 to 12kV at 25 μ A beam current), the focus anode (2.4 to 4kV at 250 μ A) and the third anode (300 to 600V). The focus voltage can be switched to 200V in 100 μ s to correct for defocusing at the edge of the c.r.t. The unit is intended for c.r.t.s with fibre-optic face plates which are used in phototypesetting, computer microfilm storage and other precision applications. It has high stability against changes in supply voltage and is guaranteed a drift of better than 500p.p.m. over eight hours. Wallis Electronics Ltd, Decoy Road, Worthing, Sussex BN14 8ND.

WW312

If you would like more information on any of the items featured here, enter the appropriate WW reference number(s) on the mauve reply-paid card.

The magazine with a different approach to micro's.



Electronics and Computing Monthly looks at a computer as the beginning of something interesting rather than an end in itself.

We thought that using a micro to drive something other than a TV screen could open up fascinating possibilities.

A few simple circuits, used as building blocks, can stretch your computer, your imagination and your fun, a long way.

If you understand the basics of digital electronics, you'll appreciate the fun you can

have by linking logic circuits to your micro.

If you don't, then read our new series which starts this month and explains digital electronic circuits from basics. Also this month, we show you how to build an infrared remote controller for your micro.

That's what Electronics and Computing is all about – giving you ideas for new

applications, and giving you the software to expand your micro. Project by project we show you how to add another dimension to your computer.

For example, in this month's issue we explain dialogue programming using the PILOT system – what it is and how it works.

And inside is enough information to build your own hi-res graphics computer.

All you need is a hot soldering iron and a cool 75p.

WHERE ELECTRONICS AND COMPUTING INTERFACE.

**At your newsagent
from Feb 12th**

DISC DRIVE DISCOUNTS

FD200 5 1/4" S/S D/D only **£99.95** formatted 175K Byte.
 FD514 8" S/S D/D only **£149** formatted 600K Byte.
 FD650 8" D/S D/D only **£199** Formatted 1.2 Megabyte.
 Manufactured by Pertec Corporation. Factory fresh - 90-day warranty. Shugart compatible.

NEW

TEAC DISC DRIVES

TEAC 55E Mini S/S 80-track formatted single density 200K, double density 400K Only **£179**
 TEAC 55F Mini D/S 80-track formatted single density 400K, double density 800K Only **£229**

- ★ Ideal for use with BBC Micro
- ★ Full warranty
- ★ Low power consumption
- ★ Slimline - latest technology

To order: Add carriage at the following rates: Monitor £10, other goods £7 and 15% VAT to total, and send your order to:



OPUS SUPPLIES, 10 BECKENHAM GROVE, SHORTLANDS, KENT
Tel: 01-464 5040 or 01-464 1598



★ 22 INCH RGB COLOUR MONITOR ONLY £99.95 ★

We have available a limited quantity of VMC 22 Colour Monitors with free isolating transformers. The Monitor has a 22" Mullard 110°C CRT and for shipping purposes the CRT and scan coil assembly are separate from the chassis. The lugs of the CRT allow it to be mounted in a standard 22" colour TV cabinet or a unit of your own design. The unit is assembled by plugging the wires from the chassis to the tube and soldering the power connector, input connector and isolating transformers. A comprehensive instruction sheet and circuit diagrams are included.

NEW

COMPUTER FURNITURE

For home use - houses your micro/monitor/cassette player/drives, etc. Send for details. Computer furniture - for the office. 10 Models available.

DEALER ENQUIRIES INVITED

LOOK

A DAISY WHEEL PRINTER ONLY £499

TEC Starwriter FP - 1500-25. 25 CPS, Friction Feed - Serial Interface.

WW - 067 FOR FURTHER DETAILS

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

AUDIO FREQUENCY TRANSFORMERS OF EVERY TYPE YOU NAME IT! WE MAKE IT! OUR RANGE INCLUDES

Microphone transformers (all types), Microphone Splitter/Combiner transformers. Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.

We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas agents in the COMMONWEALTH, E.E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post questionnaires by return.

E. A. Sowter Ltd.

Manufacturers and Designers

E. A. SOWTER LTD. (Established 1941) : Reg. No. England 303990
 The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
 P.O. Box 36, Ipswich, IP1 2EL, England
 Phone: 0473 52794 and 0473 219390
 Telex 987703G Sowter

WW - 038 FOR FURTHER DETAILS

- | | | | |
|----------|----|---|------|
| Item No. | 1 | TELEQUIPMENT OSCILLOSCOPE type D83. Dual Trace 50 MHz. Delay Sweep | £550 |
| | 2 | TEKTRONIX OSCILLOSCOPE type T335A Dual Trace 35MHz Delay Sweep AS NEW | £550 |
| | 3 | TELEQUIPMENT OSCILLOSCOPE type D67A. Dual Trace 25MHz Delay Sweep | £385 |
| | 4 | TELEQUIPMENT OSCILLOSCOPE type D65. Dual Trace 15MHz | £225 |
| | 5 | TELEQUIPMENT OSCILLOSCOPE type D61A. Dual Trace 10MHz | £180 |
| | 6 | TEKTRONIX OSCILLOSCOPE type 547 with 1A1. Dual Trace 50MHz. Dual TB | £250 |
| | 7 | TEKTRONIX STORAGE OSCILLOSCOPE type 5645 | £275 |
| | 8 | BRUEL & KJØER Audio Frequency Spectrometer type 2112 with 6&K 2205 Level Recorder | £275 |
| | 9 | 6 & K AUDIO Frequency Spectrometer type 2112 | £275 |
| | 10 | 6 & K LEVEL RECORDER type 2205 with 50dB Potentiometer | £150 |
| | 11 | 6 & K BAND PASS FILTER SET type 1612 | £75 |
| | 12 | 6 & K RANDOM NOISE GENERATOR type 1402 | £75 |
| | 13 | 6 & K EXTENSION FILTER SET type 1620 | £40 |
| | 14 | 6 & K ELECTRONIC VOLTMETER type 2409 2Hz-200KHz | £75 |
| | 15 | 6 & K AUTOMATIC VIBRATION EXCITER CONTROL type 1018 | £40 |
| | 16 | 6 & K AUTOMATIC VIBRATION EXCITER CONTROL type 1019 | £40 |
| | 17 | MARCONI FM/AM SIGNAL GENERATOR TF995A/2M 1.5-220MHz AM/FM Mod. | £180 |
| | 18 | MARCONI CIRCUIT MAGNIFICATION METER TF1245 with TF1246 OSCILLATOR 40Hz-50MHz | £250 |
| | 19 | MARCONI 1/4% UNIVERSAL BRIDGE TF1313 | £195 |
| | 20 | MARCONI UNIVERSAL BRIDGE type TF868B | £35 |
| | 21 | MARCONI UNIVERSAL BRIDGES type TF868, TF868-1, TF868A | £30 |
| | 22 | MARCONI VACUUM TUBE VOLTMETER type TF1041B | £20 |
| | 23 | MARCONI VHF ALIGNMENT OSCILLOSCOPE type TF104 | £20 |
| | 24 | DECCA PAL COLOUR BAR GENERATOR type EP85A | £150 |
| | 25 | DECCA KORTING COLOUR TV SERVICE GENERATOR type 82515 | £140 |
| | 26 | FERRUGRAPH RECORDER TEST SET type RT52 | £225 |
| | 27 | LABGEAR PAL COLOUR BAR GENERATOR type CM6037/DB | £75 |
| | 28 | LABGEAR COLOURMATCH 625 PATTERN GENERATOR type CM6004-PG | £25 |
| | 29 | VIDEO CIRCUITS TUBE TESTER type V33 | £30 |
| | 30 | RANK U.H.F. SIGNAL STRENGTH METER | £20 |
| | 31 | RANK E.H.T. METER 0-30KV DC | £20 |
| | 32 | METRIX WOBULATOR type 210 | £25 |
| | 33 | PHILIPS WOBULATOR type GM2877S | £50 |
| | 34 | ADVANCE RF SIGNAL GENERATOR type 62 150KHz-220MHz CW/Mod | £20 |

- | | | | |
|----------|----|--|-----|
| Item No. | 35 | ADVANCE RF SIGNAL GENERATOR type SG62B 150KHz-220MHz CW/Mod | £50 |
| | 36 | ADVANCE WIDE RANGE LF OSCILLATOR type SG67A 1Hz-1MHz | £50 |
| | 37 | ADVANCE AUDIO SIGNAL GENERATOR type H1 15Hz-50KHz Sine/Square | £25 |
| | 38 | ADVANCE LF OSCILLATOR type H1E 15Hz-50KHz Sine/Square | £45 |
| | 39 | ADVANCE RF SIGNAL GENERATOR type E2 100KHz-100MHz CW/Mod | £40 |
| | 40 | PYE SCALAMP ELECTROSTATIC VOLTMETER 0-10KV | £10 |
| | 41 | ERNST TURNER 6" ELECTROSTATIC VOLTMETER Model 32 0-2.5KV | £12 |
| | 42 | ERNST TURNER 6" ELECTROSTATIC VOLTMETER Model 32 0-10KV | £14 |
| | 43 | ERNST TURNER 6" ELECTROSTATIC VOLTMETER Model 32 0-10KV | £16 |
| | 44 | ERNST TURNER 6" ELECTROSTATIC VOLTMETER Model 32 0-20KV | £20 |
| | 45 | ADVANCE DIGITAL MULTIMETER type DMM2 | £25 |
| | 46 | SOLARTRON DIGITAL MULTIMETER type LM1240 | £25 |
| | 47 | TMK MULTIMETER Model 700. 20kohm per Volt. Ranges to 10 Amps & 5KV | £18 |
| | 48 | AVO MULTIMETER Model 72 Compact | £12 |
| | 49 | LINSTEAD LF SIGNAL GENERATOR type G2 100KHz-100KHz Sine/Square. Compact | £30 |
| | 50 | SOLARTRON DIGITAL VOLTMETER type LM1420.2 | £20 |
| | 51 | ROBAND TRANSISTORISED SUPPLY Type T104 0-300.30V 1A DC Metered | £30 |
| | 52 | RACAL DIGITAL FREQUENCY METER type SA520 | £10 |
| | 53 | TEKTRONIX TIME MARK GENERATOR type 180A | £50 |
| | 54 | AVO TRANSISTOR TESTER type TT169 with leads As new (P&P £2) | £20 |
| | 55 | ESP AUTOMATIC CAPACITANCE BRIDGE Model 300A. 1pf-2000mf. Auto ranging 0.5% accuracy (P&P £4) | £40 |
| | 56 | WAYNE KERR UNIVERSAL BRIDGE type 8221 | £70 |
| | 57 | TAYLOR VALVE TESTER Model 45D2 | £35 |
| | 58 | ROBAND TRANSISTORISED SUPPLY type T106 0-100V 1A DC. Metered | £30 |
| | 59 | RANK FLUETTER METER type 1740 | £20 |
| | 60 | PYE SCALAMP ELECTROSTATIC VOLTMETER 0-40KV | £35 |
| | 61 | HEATHKIT CAPACITOR CHECKER Model IT-28 (Resistance range) (P&P £4) | £20 |
| | 62 | ENGLISH ELECTRIC ELECTRONIC INSULATION TESTER IOKV DC | £25 |
| | 63 | CAMBRIDGE PORTABLE POT no 1-361098 (P&P £4) | £20 |
| | 64 | RHODE & SCHWARZ MICROVOLTMETER UVM BN1201 0.1mV to 10 Volts | £25 |
| | 65 | R & S UNBALANCED STANDARD ATTENUATOR DPR BN18042/50 0-100dB 50 ohms | £25 |
| | 66 | AUTO TRANSFORMER 1000VA. BRAND NEW | £15 |
| | 67 | VARIAC 8 Amp. 0-270 Volts. Cased | £25 |

STOCKISTS OF NEW SCOPEX & SAFGAN OSCILLOSCOPES. Also MANY OTHER ITEMS OF TEST EQUIPMENT & COMPONENTS in Stock. For FURTHER DETAILS CONTACT DWAYNE STEWART



STEWART OF READING
 110 WYKEHAM ROAD, READING, BERKS RG6 1PL
 Tel: 0734 68041



Callers welcome 9am-5.30pm Monday to Saturday inclusive

WW - 043 FOR FURTHER DETAILS

LANGREX SUPPLIES LTD

Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

RST

Tel: 01-677 2424 Telex: 946708

RST

SEMICONDUCTORS

AA19	0.10	AS215	1.20	BC172	0.11	BD131	0.44	BF257	0.27	GEX541	5.00	OA2207	1.50	OC205	2.75	ZTX504	0.21	2N1671	5.00	2N3819	0.30
AA19	0.10	AS216	1.10	BC175	0.11	BD132	0.48	BF258	0.27	GJ3M	1.50	OC16	2.50	OC206	2.75	ZTX531	0.24	2N1893	0.32	2N3820	0.39
AA30	0.15	AS217	1.00	BC177	0.28	BD136	0.40	BF336	0.34	GM0378A	1.75	OC20	2.50	OC207	2.50	ZTX550	0.25	2N2147	4.00	2N3823	0.60
AA30	0.17	AS218	1.00	BC178	0.28	BD138	0.48	BF338	0.36	KJ100A	0.45	OC22	2.50	OC21	2.00	IN914	0.05	2N2148	3.75	2N3866	1.00
AA31	0.15	AS219	2.50	BC179	0.28	BD139	0.48	BF521	4.00	MJE370	0.70	OC23	4.00	OC22	3.00	IN916	0.09	2N2218	0.32	2N3904	0.17
AA31	0.15	AS220	2.50	BC180	0.11	BD140	0.50	BF522	4.00	MJE520	0.47	OC24	3.00	OC23	2.00	IN916	0.09	2N2218	0.32	2N3906	0.17
AC107	0.55	AU110	3.00	BC183	0.11	BD144	2.00	BF561	0.20	MJE521	0.73	OC28	2.00	OC24	3.00	R2008B	2.00	IN4001	0.06	2N2219	0.32
AC125	0.25	AU110	3.00	BC184	0.11	BD181	1.20	BF598	0.20	MJE295	1.30	OC29	2.00	OC25	1.00	R2009	2.25	IN4002	0.06	2N2220	0.20
AC126	0.25	BA145	0.13	BC212	0.11	BD182	0.25	BF599	0.20	MJE305	1.10	OC35	1.50	OC26	1.50	R2010B	2.00	IN4003	0.06	2N2221	0.20
AC127	0.25	BA148	0.15	BC213	0.11	BD2137	0.54	BFW10	0.97	MJE305	1.10	OC35	1.50	OC27	2.00	T1C44	0.27	IN4004	0.07	2N2222	0.20
AC128	0.30	BA154	0.10	BC214	0.11	BD238	0.54	BFX84	0.30	MJE305	1.10	OC35	1.50	OC28	2.00	T1C226D	1.20	IN4005	0.07	2N2223	0.20
AC141	0.28	BA155	0.11	BC237	0.11	BDX10	0.91	BFX85	0.30	MJE305	1.10	OC35	1.50	OC29	2.00	T1L209	0.16	IN4006	0.11	2N2368	0.25
AC141K	0.35	BA156	0.11	BC238	0.11	BDX12	2.00	BFX87	0.30	MJE305	1.10	OC35	1.50	OC30	2.00	T1P29A	0.43	IN4007	0.12	2N2369A	0.25
AC142	0.35	BAW62	0.05	BC301	0.33	BD170	1.50	BFX88	0.30	MJE305	1.10	OC35	1.50	OC31	0.90	T1P29A	0.43	IN4008	0.07	2N2484	0.25
AC142K	0.35	BAX13	0.06	BC303	0.34	BD170	1.50	BFX89	0.30	MJE305	1.10	OC35	1.50	OC32	0.90	T1P31A	0.33	IN4148	0.04	2N2486	0.16
AC176	0.30	BAX16	0.06	BC307	0.11	BF151	0.35	BFY51	0.25	MPSA56	0.28	OC44	0.85	OC43	1.50	T1P32A	0.36	IN5400	0.13	2N2904	0.32
AC187	0.28	BC107	0.16	BC308	0.11	BF152	0.16	BFY52	0.25	MPSU06	0.65	OC72	1.00	OC44	0.85	T1P33A	0.54	IN5401	0.13	2N2905	0.32
AC188	0.28	BC108	0.16	BC327	0.12	BF153	0.16	BFY54	0.30	MPSU06	0.65	OC72	1.00	OC45	0.65	T1P34A	0.67	IN5402	0.13	2N2906	0.21
AC189	0.28	BC109	0.16	BC328	0.12	BF154	0.17	BFY90	0.95	NEK55	0.45	OC74	0.70	OC46	0.65	T1P41A	0.44	IN5921	0.08	2N2907	0.21
AC191	1.10	BC113	0.15	BC338	0.12	BF159	0.17	BSX19	0.27	NKT401	3.50	OC75	0.65	OC47	0.55	T1P42A	0.42	IN5921	0.09	2N2924	0.26
AC192	1.10	BC115	0.18	BCY30	1.25	BF167	0.24	BSX21	0.29	NKT403	2.50	OC76	1.00	OC48	0.65	T1P43A	0.54	IN5921	0.09	2N2925	0.22
AC193	1.10	BC116	0.19	BCY31	1.50	BF173	0.30	BT106	1.20	OA7	0.60	OC81	0.65	OC49	0.65	T1P44A	0.44	IN5921	0.09	2N2926	0.15
AC194	1.10	BC117	0.23	BCY32	1.50	BF177	0.35	BTY79/400R	2.00	OA7	0.60	OC81Z	1.20	OC50	0.65	T1P45A	0.44	IN5921	0.09	2N2927	0.15
AD149	0.15	BC118	0.18	BCY33	1.10	BF178	0.35	BU205	1.30	OA7	0.60	OC82	1.00	OC51	0.65	T1P46A	0.44	IN5921	0.09	2N2928	0.15
AD161	0.35	BC125	0.18	BCY34	3.40	BF179	0.35	BU206	1.30	OA7	0.60	OC82	1.00	OC52	0.65	T1P47A	0.44	IN5921	0.09	2N2929	0.15
AD162	0.35	BC126	0.18	BCY39	3.40	BF180	0.35	BU207	1.30	OA7	0.60	OC83	0.80	OC53	0.65	T1P48A	0.44	IN5921	0.09	2N2930	0.15
AF106	0.35	BC135	0.15	BCY40	2.80	BF181	0.28	BU208	2.00	OA7	0.60	OC84	0.80	OC54	0.65	T1P49A	0.44	IN5921	0.09	2N2931	0.15
AF114	0.75	BC136	0.19	BCY42	0.30	BF182	0.30	BU209	2.00	OA7	0.60	OC85	0.80	OC55	0.65	T1P50A	0.44	IN5921	0.09	2N2932	0.15
AF115	0.75	BC137	0.19	BCY43	0.30	BF183	0.28	BU210	2.00	OA7	0.60	OC86	0.80	OC56	0.65	T1P51A	0.44	IN5921	0.09	2N2933	0.15
AF116	0.75	BC147	0.12	BCY58	0.19	BF184	0.28	BU211	2.00	OA7	0.60	OC87	0.80	OC57	0.65	T1P52A	0.44	IN5921	0.09	2N2934	0.15
AF117	0.75	BC148	0.12	BCY70	0.17	BF185	0.30	BU212	2.00	OA7	0.60	OC88	0.80	OC58	0.65	T1P53A	0.44	IN5921	0.09	2N2935	0.15
AF119	0.33	BC149	0.13	BCY71	0.18	BF186	0.28	BU213	2.00	OA7	0.60	OC89	0.80	OC59	0.65	T1P54A	0.44	IN5921	0.09	2N2936	0.15
AF186	1.00	BC157	0.13	BCY72	0.17	BF195	0.12	BU214	2.00	OA7	0.60	OC90	0.80	OC60	0.65	T1P55A	0.44	IN5921	0.09	2N2937	0.15
AF239	0.39	BC158	0.13	BCY71	1.75	BF196	0.13	BU215	2.00	OA7	0.60	OC91	0.80	OC61	0.65	T1P56A	0.44	IN5921	0.09	2N2938	0.15
AFZ11	4.00	BC159	0.13	BD115	0.42	BF197	0.14	CRS140	0.60	OA210	1.50	OC92	1.00	OC62	0.65	T1P57A	0.44	IN5921	0.09	2N2939	0.15
AFZ12	4.00	BC167	0.11	BD121	1.70	BF200	0.40	CRS340	0.75	OA220	1.50	OC93	1.00	OC63	0.65	T1P58A	0.44	IN5921	0.09	2N2940	0.15
AS226	4.40	BC170	0.11	BD123	0.25	CRS360	0.90	CRS630	0.90	OA220	1.50	OC94	1.00	OC64	0.65	T1P59A	0.44	IN5921	0.09	2N2941	0.15
AS227	0.90	BC171	0.11	BD124	2.00	CRS660	3.00	GEX66	3.00	OA220	1.50	OC95	1.00	OC65	0.65	T1P60A	0.44	IN5921	0.09	2N2942	0.15

VALVES

A1834	9.00	E180C	10.50	EF86	1.75	GU51	20.00	PC86	2.50	QY4-250	73.15	UF85	1.75	4C35	78.00	6CW4	8.00	12BA6	2.50	5670	4.50
A2087	13.50	E182CC	13.25	EP91	2.95	GXU2	30.00	PC87	2.50	QY4-400	76.80	UF89	2.00	4CX250B	40.00	6D2	1.50	12BE6	2.50	5675	28.00
A2134	17.50	E186F	11.50	EP92	6.37	GXU3	25.00	PC97	1.75	QY5-3000A	15.00	UL84	1.75	4X150A	73.00	6DK6	3.00	12BH7	1.50	5687	6.00
A2293	16.00	E188CC	8.25	EP93	1.50	GXU4	44.50	PC90	1.75	QZ06-20	32.70	UM80	2.00	4X150D	56.00	6G06B	4.75	12BY7	3.00	5696	4.50
A2426	11.50	E203C	12.00	EP94	2.50	GXU5	20.00	PC88	1.50	R10	6.00	UY41	2.25	5B254M	35.00	6EA8	3.00	12E	20.00	5718	7.50
A2521	22.50	E283CC	12.00	EP95	5.99	GZ32	3.40	PC85	2.00	R17	3.00	UY85	2.25	5B255M	35.00	6EB8	2.50	12E11TT	170.00	5725	5.50
A2900	22.50	E288CC	17.50	EP98	2.00	GZ33	4.75	PC89	1.75	R19	9.24	VL5631	15.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5726	11.37
A3343	45.00	EA52	32.25	EP183	2.00	GZ37	4.75	PC80	1.50	R20	2.50	VL5631	15.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5727	7.05
AZ31	2.75	EA76	2.50	EP184	2.00	GZ37	4.75	PC80B	1.60	RG3-250	32.48	VG1	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5728	2.50
AZ41	2.60	EACB80	1.25	EP185	2.00	KT61	5.00	PC80C	1.60	RG3-250A	32.48	VG2	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5729	2.50
BK448	114.90	EAF85	1.75	EP186	2.00	KT66	8.00	PC80D	1.60	RG3-250A	32.48	VG3	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5730	4.50
BK484	155.35	EAF42	2.50	EK90	1.75	KT88	11.00	PC80E	1.60	RG3-250A	32.48	VG4	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5731	4.50
BS90	58.00	EAF801	2.00	EK91	1.50	KTW61	2.50	PC80F	1.50	RG3-250A	32.48	VG5	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5732	4.50
BS452	60.00	EB41	4.00	EL32	2.50	KTW62	2.50	PC80G	1.50	RG3-250A	32.48	VG6	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5733	4.50
BS510	60.00	EB91	1.50	EL33	4.00	KTW63	2.50	PC80H	1.50	RG3-250A	32.48	VG7	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5734	4.50
BTS	58.95	EL34M1	3.00	M8079	12.34	KT66	8.00	PC80I	1.50	RG3-250A	32.48	VG8	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5735	4.50
BT17	151.00	EB83	2.50	EL34M2	3.00	M8080	9.82	PC80J	1.50	RG3-250A	32.48	VG9	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5736	4.50
BT19	44.05	EB81	1.50	EL41	2.80	M8081	9.82	PC80K	1.50	RG3-250A	32.48	VG10	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5737	4.50
BT29	349.15	EB90	1.25	EL42	2.50	M8082	9.69	PC80L	1.50	RG3-250A	32.48	VG11	45.00	5B255M	35.00	6E6W	2.25	12E11A	35.00	5738	4.50
BT69	354.80	EBF80	1.50	EL81	5.25	M8083</															

Backplane bus standards

a special issue of

Microprocessors and Microsystems

Guest Editor: Paul Borrill (University College, London)

This special issue contains six full-length articles on the major backplane buses, detailing their specifications, modifications, special features and the technical and political problems of agreeing their standard format.

STD bus by the proposer of STD on Eurocard, Tim Elsmore

S100 bus by the S100 MSC chairman, Mark Garetz


Multibus by the Multibus MSC chairman, Rich Boberg

VERSAbus and VMEbus by Motorola bus development manager, Rich deBock

Eurobus by UK Ministry of Defence executive, John Hill

Futurebus (P896) by the P896 MSC secretary, Paul Borrill

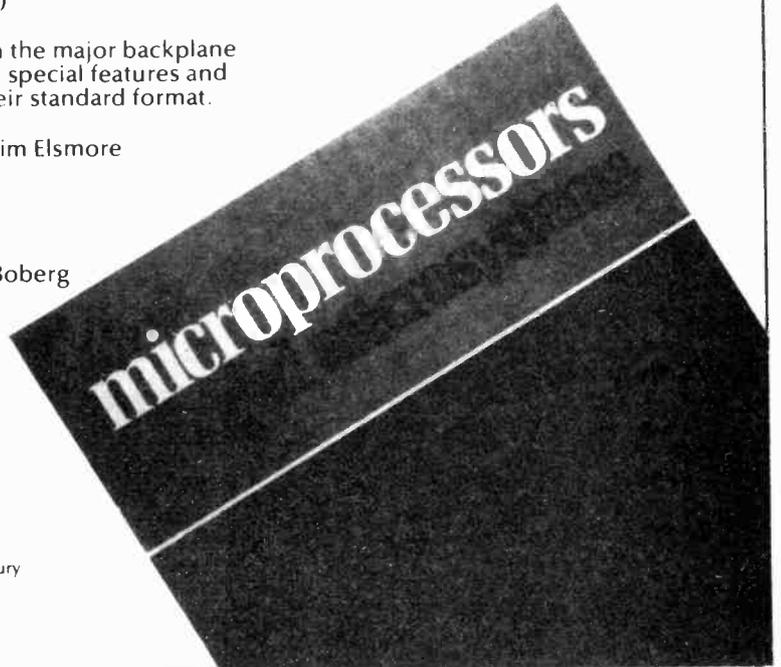For further details contact:
 Danny Green, Butterworth Scientific Limited - Journals Division, Westbury House, Bury Street, Guildford, Surrey GU2 5BH, UK
 Telephone: 0483 31261 Telex: 859556 SCITEC G



EASIBINDERS

Quick, neat and easy!



It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold six issues and is attractively bound and blocked with the WIRELESS WORLD logo.

Price U.K. £4.30 including postage, packing and V.A.T.

Overseas orders add 25p per binder

Nat. Giro No. 5157552.

Please allow 3/4 weeks for fulfilment of order.

Payment by ACCESS/BARCLAYCARD/VISA. Send coupon below detailing credit card no. and signature.

Why not place your order now? Send the completed coupon below with remittance payable to:

Easibind Ltd., 42 Hoxton Square
 London N1 6NS

Order Form WIRELESS WORLD

I enclose P.O./cheque value..... for.....binders
 Years required.....

BLOCK LETTERS PLEASE

Name

Address.....

Date..... Registration No. 307469



STEREO MICROPHONE AMPLIFIER



- 50 or 200 Ohm balanced microphones to balanced lines
- Variety of low frequency characteristics for improving the clarity of recordings
- Inputs filtered against radio interference
- Complete boxed unit or double mumetal screened amplifier module alone

Surrey Electronics Ltd., The Forge, Lucks Green, Cranleigh, Surrey
 GU6 7BG England. Tel: 0483 275997

ScheTronics Limited

We offer the following services

- ★ Repair and calibration of precision electronic test equipment
- ★ Prototype wiring of P.C.Bs
- ★ Technical drawing facilities
- ★ Second user test equipment for sale

Unit 10, Dunstall Estate
 Crabtree Manorway
 Belvedere, Kent DA17 6AW
 Telephone: 01-311 9657

WW - 065 FOR FURTHER DETAILS

ICOM HOME OFFICE APPROVED RADIO

The ICM-12, synthesized, marine hand-portable radio

FEATURES:

- 12 channels – 6 and 16 fitted as standard.
- No waiting for crystals, can be diode programmed between 156-164MHz.
- Automatic semi-duplex for private and link calls.
- Slide-on nicad pack recharges from mains or 12V.
- Lots of options, speaker mics, alternative battery packs, 12V leads, and desk chargers.
- Complete with nicad battery pack, mains charger, belt clip, earphone, rubber antenna.

● **PRICE £219 + VAT. Free carriage.**

Trade enquiries very welcome – Ask for Phil Hadler

LAND MOBILE BUSINESS BAND RADIO

VHF and UHF base, mobiles and hand portables. Built in Sel-call and CTCSS; very compact indeed. Synthesized - Diode - Programmed.

Dealers! Forget your crystal problems! Very competitive prices.

Dealer outlets required. Ask for Chris Lambert.

Thanet Electronics

143 Reculver Road, Herne Bay, Kent
Tel: 02273 63859. Telex 965179

WW - 030 FOR FURTHER DETAILS

TEST EQUIPMENT

Tequipment D83 50MHz Dual Trace	£465
Tequipment D61A 10MHz Dual Trace	£155
Tequipment S54A 10MHz Single Trace	£95
Tek. 549 50MHz Storage Mainframe	£225
Tek. 564 10MHz Storage, complete	£225
Tek. CA Plug-in	£25
Tek. M Plug-in 4-Channel 20MHz	£85
PDP 8/F Computer	£220
Tek. 611 Storage Monitor	£595
Philips Computer	£150
H.P. 608C Sig. Gen	£95
Tek. 565, complete	£295
Tek. 1A2, 1A6 Plug-ins	£60
Marconi TF2600 VVM	£65
Tek. 661 Sampling Scope + 4F1 and 5T3PI	£175
Racal Dana 9415 9-digit 100MHz Counter with manuals, IEEE interfaced, immaculate condition	£650
Tek. 647A 100MHz Scope	£375
Hitachi 15MHz Dual Trace	£165
Hitachi 35MHz Dual Trace	£295
H.P. 5300/5302 50MHz Counter	£250
H.P. 140A + 1415A TDR System	£300
J. J. Lloyd PL51 X-Y Plotter	£350
Marconi TF1313 LCR Bridge	£195
G.R. 20cm Adjustable Airlines	£60
Tek. 1A1 Plug-in	£60
Philips Gas Chromatography System	P.O.A.
Computerised Digitiser System	P.O.A.
Tally Printer	£220
Teletypes	£70
Polyskop II	£250
R. & S. SMAF Generator AM/FM	£200
Scopex 4D10 10MHz Scopes	£150
Radiometer SG1 Stereo Generator	£195
Tequipment D67 25MHz Scopes	£275
Brookdeal Ortholoc Vector Voltmeter and Lock-in Amplifier with plug-ins	£495

Carriage additional : All prices exc. V.A.T.

TIMEBASE

94 ALFRISTON GARDENS
SHOLING, SOUTHAMPTON SO2 8FU
TEL: 431323 (0703)

Callers welcome

Access, Barclaycard : Telephone your order

WW - 069 FOR FURTHER DETAILS

TOROIDALS



The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

- ★ 294 TYPES TO CHOOSE FROM!
- ★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
- ★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
30 VA 70x30mm 0.45Kg Regulation 16%	1x010	6+6	2.50	£5.12 +p/p £1.04 +VAT £0.92 TOTAL £7.08
	1x011	9+9	1.66	
	1x012	12+12	1.25	
	1x013	15+15	1.00	
	1x014	18+18	0.83	
	1x015	22+22	0.68	
	1x016	25+25	0.60	
50 VA 80x35mm 0.9 Kg Regulation 13%	2x010	6+6	4.16	£5.70 +p/p £1.30 +VAT £1.05 TOTAL £8.05
2x011	9+9	2.77		
2x012	12+12	2.08		
2x013	15+15	1.66		
2x014	18+18	1.38		
2x015	22+22	1.13		
2x016	25+25	1.00		
80 VA 90x30mm 1 Kg Regulation 12%	3x010	6+6	6.54	£6.08 +p/p £1.67 +VAT £1.16 TOTAL £8.91
3x011	9+9	4.44		
3x012	12+12	3.33		
3x013	15+15	2.66		
3x014	18+18	2.22		
3x015	22+22	1.81		
3x016	25+25	1.60		
120 VA 90x40mm 1.2 Kg Regulation 11%	4x010	6+6	10.00	£6.90 +p/p £1.67 +VAT £1.29 TOTAL £9.86
4x011	9+9	6.66		
4x012	12+12	5.00		
4x013	15+15	4.00		
4x014	18+18	3.33		
4x015	22+22	2.72		
4x016	25+25	2.40		
160 VA 110x40mm 1.8 Kg Regulation 8%	5x010	6+6	8.89	£7.91 +p/p £1.67 +VAT £1.44 TOTAL £11.02
5x011	9+9	6.56		
5x012	12+12	5.33		
5x013	15+15	4.44		
5x014	18+18	3.63		
5x015	22+22	3.20		
5x016	25+25	2.66		

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
225 VA 110x45mm 2.2 Kg Regulation 7%	6x012	12+12	9.38	£9.20 +p/p £2.00 +VAT £1.68 TOTAL £12.88
	6x013	15+15	7.50	
	6x014	18+18	6.25	
	6x015	22+22	5.11	
	6x016	25+25	4.50	
	6x017	30+30	3.75	
	6x018	35+35	3.21	
300 VA 110x50mm 2.6 Kg Regulation 6%	6x026	40+40	2.81	£10.17 +p/p £2.00 +VAT £1.83 TOTAL £14.00
	6x025	45+45	2.50	
	6x033	50+50	2.25	
	6x028	110	2.04	
	6x029	220	1.02	
	6x030	240	0.93	
	7x013	15+15	10.00	
500 VA 140x60mm 4 Kg Regulation 4%	7x014	18+18	8.33	£13.53 +p/p £2.35 +VAT £2.38 TOTAL £18.26
	7x015	22+22	6.82	
	7x016	25+25	6.00	
	7x017	30+30	5.00	
	7x018	35+35	4.28	
	7x026	40+40	3.75	
	7x025	45+45	3.33	
625 VA 140x75mm 5 Kg Regulation 4%	7x033	50+50	3.00	£16.13 +p/p £2.50 +VAT £2.79 TOTAL £21.42
	7x028	110	2.72	
	7x029	220	1.36	
	7x030	240	1.25	
	8x016	25+25	10.00	
	8x017	30+30	8.33	
	8x018	35+35	7.14	
8x026	40+40	6.25		
	8x025	45+45	5.55	
	8x033	50+50	5.00	
	8x042	55+55	4.54	
	8x028	110	4.54	
	8x029	220	2.27	
	8x030	240	2.08	

IMPORTANT: Regulation - All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovalue, Maplin and Technomatic.

Please send _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd., Freepost 5, Graham Bell House, Roper Close
Canterbury CT2 7EP, Kent, England
Telephone Sales (0227) 54778; Technical (0227) 64723. Telex 965780.




WW - 063 FOR FURTHER DETAILS

Essex Tiny Basic System

- * RS232 Interface
48 I/O Lines
- * Powerful National
INS 8073 Processor
- * Autostart Operation
with Watchdog Timer
- * Up to 16K Byte EPROM
EPROM Programmer
- * Accommodates Instant
ROM Modules

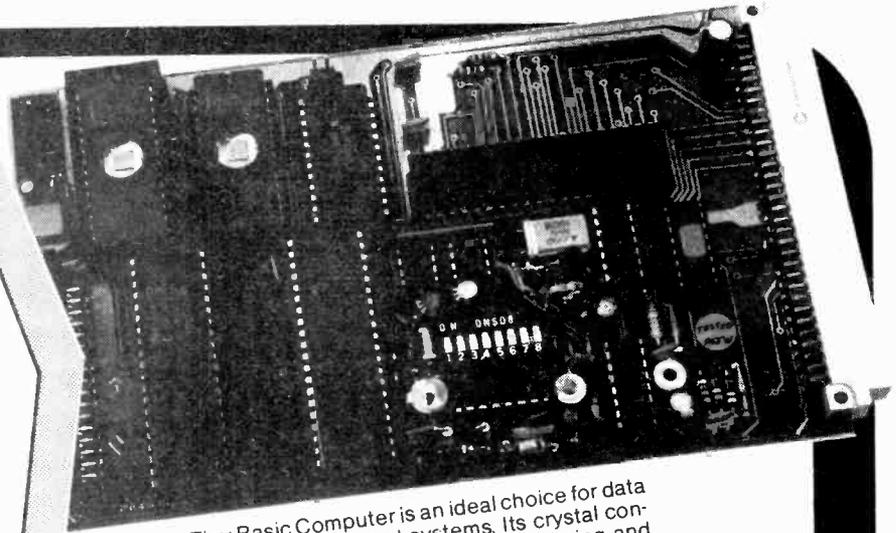PRICE EXCLUDING VAT: £185
CARRIAGE WITHIN THE UK £2



The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal, and then be copied into EPROM. Alternatively, Instant ROM modules may be used both during development and for program storage.

'INSTANT ROM' is the trademark of Greenwich Instruments
— PLEASE SEND FOR FULL INFORMATION

* NOW AVAILABLE

The Essex Buffer/Timer Board 24 Buffered Inputs & 16 Buffered Outputs & 4 Hardware Timers


Provides easy interfacing to the computer



Essex Electronics Centre

Wivenhoe Park, Colchester, Essex CO4 3SQ
Telephone: Colchester (0206) 865089

WW - 046 FOR FURTHER DETAILS

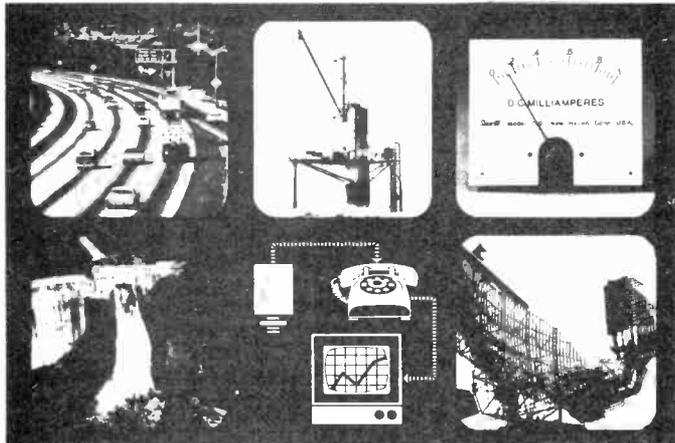

Visual monitoring of anything, anywhere, by phone, in seconds, with Robot Phonline TV.

Robot's Phonline TV systems provide a low-cost, efficient solution to the problem of visually monitoring remote installations, meters, gauges, traffic, weather, water levels, or any subject, large or small. The Phonline TV equipment works well with standard CCTV equipment and converts the broadband video signal from the camera to narrow band audio tones for transmission via the dial telephone network or voice grade radio, then to a video signal again for display on a monitor at the receiving end. The entire process takes as little as 4 seconds and costs only the amount of the phone call. Since one or more cameras can be fed to one or more monitoring stations for viewing sequentially or simultaneously, and since the system can be fully automated, there is an almost infinite number of PLTV system configurations possible. Permanent storage is available by recording the transmissions on audio cassette tapes. For fast, uncomplicated, inexpensive visual monitoring of any subject anywhere, Robot Phonline TV is the answer. Write or call for more information and descriptive literature.

Robot (UK) Ltd., Building 33
East Midlands Airport
Castle Donington, Derby DE7 2SA
Tel: (0332) 812446. Telex: 37522

World Leaders in Phone Line Television and Image Processing Systems

ROBOT
ROBOT RESEARCH INC

WW - 049 FOR FURTHER DETAILS

Happy Memories

Part type	1 off	25.99	100 up
4116 200ns77	.69	.66
4116 250ns70	.63	.60
4816 100ns For BBC comp.....	2.25	2.01	1.95
4164 200ns	3.99	3.56	3.42
2114 200ns Low power	1.15	1.00	.90
2114 450ns Low power95	.85	.80
4118 250ns	3.25	2.85	2.85
6116 150ns CMOS	3.55	3.20	2.95
2708 450ns	2.60	2.25	2.10
2716 450ns 5 volt.....	2.35	2.10	2.02
2716 450 ns three rail.....	5.75	5.00	4.65
2732 450ns Intel type.....	3.50	3.15	3.00
2532 450ns Texas type.....	3.70	3.30	3.00

Z80A-CPU	£3.95	Z80A-PIO	£2.99	Z80A-CTC	£2.99
6522 PIA	£3.70	7002 A-D	£4.60	3691	£2.75
88LS120	£2.20	7805 reg.....	.50	7812 reg.....	.50

Low-profile IC sockets:	Pins	8	14	16	18	20	22	24	28	40
	Pence	9	10	11	14	15	18	19	25	33

Soft-sectored floppy discs per 10 in plastic library case:					
5-inch SSSD	£17.00	5-inch SSDD	£19.25	5-inch DSDD	£21.00
			£26.25		
8-inch SSSD	£19.25	8-inch SSDD	£23.65	8-inch DSDD	£25.50

74LS Series TTL: Large stocks at low prices with D.I.Y. discounts starting at a mix of just 25 pieces — write or phone for list.

Please add 50p post and packing to orders under £15 and VAT to total
Access & Visa welcome. 24-hour service on (054 422) 618
Government and educational orders welcome. £15 minimum
Trade accounts operated — phone or write for details

HAPPY MEMORIES (WW)
Gladestry, Kington
Herefordshire HR5 3NY
Telephone: (054 422) 618 or 628

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, heavy duty brush assembly, continuously rated.
25 WATT 10/25/50/100/150/250/500/1K Ω /1.5k Ω
£3.10 + 50p P&P (**£3.91** inc. VAT).
50 WATT 250 Ω **£5.50** + 50p P&P (**£6.90** inc. VAT).
100 WATT 1/5/10/25/50/100/250/300/500/1k Ω /1.5k Ω /2.5k Ω /3.5k Ω
£7.25 + 75p P&P (**£8.20** inc. VAT).
Black Silver Sintered Knob calibrated in Nos. 1-9, 1/2in dia. brass bush. Ideal for above Rheostats 30p ea. + VAT.

SOLID STATE E.H.T. UNIT

Input 230V A.C. Fully isolated. Approx. 15KV. Built-in 10 sec. Timer. Easy modified for 20 sec. 30 sec. to continuous operation. Size 155x85x50mm. Price **£5** + 75p P&P (Total inc. VAT **£6.61**).

240V A.C. SOLENOID VALVE

Designed for Air/Gas at 0-7. Water 0.5 psi. Inlet/outlet 3/8". Forged brass body. Manuf. Dewraswitch Asco. Price: **£5.50** + 75p P&P (**£7.10** inc. VAT). N.M.S.

METERS (New) - 90mm DIAMETER

AC Amp. Type 62T2: 0, 1A, 0-5A, 0-10A.
 AC Volt. 0-150V, 0-300V.
 DC Amp. Type 65C5 0-5A, 0-10A, 0-50A, 0-100A. DC Volt 30V. All types **£3.60** ea + P&P 75p (**£5.00** inc. VAT) except 0-50A DC, 0-100A DC. Price **£5.00** + 75p P&P (**£6.61** inc. VAT).

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt **£8.70** inc. VAT **£10.00** (callers only).
2ft 20 watts **£8.20**. Post **£1.25** (**£9.57** inc. VAT & P).
 (For use in standard bi-pin fittings).
12in 8 watt **£3.00**. + 45p (**£3.97** inc. VAT P&P).
9in 8 watt **£2.50**. + 45p (**£3.39** inc. VAT P&P).
6in 4 watt **£2.50**. + 45p (**£3.39** inc. VAT P&P).
 Complete ballast unit for either 6V, 9V or 12V tube 230V AC op. **£5.50**
 Post 55p (**£6.96** inc. VAT P&P). Also available for 12V DC **£5.50** Post 55p
 (**£6.96** inc. VAT P&P).

BLACK LIGHT BULBS

Self-ballasted Mercury U.V. 175W Bulbs. Available for either B.C. or E.S. fitting. Price incl. p&p & VAT **£11.50**.
400W UV LAMP AND BALLAST complete **£38.80** Post **£3.50** (**£47.73** inc. VAT & P). **400W UV LAMP** only **£14.00**. Post **£2.00** (**£16.40** inc. VAT & P).

SOLENOIDS

230V A.C. approx 20lb pull, heavy duty **£7.50** + **£1.50** p&p (**£10.35** inc. VAT).
 240V A.C. approx 10lb pull. **£1.93** + 50p p&p (**£2.79** inc. VAT).
 12V D.C. approx 1/2lb pull. **£1.86** + 40p p&p (**£2.36** inc. VAT).

CONTACTOR

AMF 230V AC 2 c/o 25A. **£5.50** + 75p p&p (**£7.19** inc. VAT).
 AEG, Arrow-Hart, etc. from stock. Phone your enquiries

Stockists for
 Finnigans Hammerite paint and Waxoyl products



Ample parking space
 Showroom open
 Monday-Friday

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB, 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10

N.M.S. - New Manufacturers' Surplus.
 R&T - Reconditioned and Tested.

Personal callers only. Open Saturdays

**9 Little Newport Street
 London WC2H 7JJ
 Tel: 01-437 0576**

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-260V

200W 1 amp inc. a.c. voltage	£15.00
0.5 KVA (2 1/2 amp MAX)	£19.00
1 KVA (5 amp MAX)	£25.00
2 KVA (10 amp MAX)	£41.00
3 KVA (15 amp MAX)	£49.00
5 KVA (25 amp MAX)	£79.00
10 KVA (50 amp MAX)	£174.00
15 KVA (75 amp MAX)	£270.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual input 200-240V or 380-415V. Star connected
 3 KVA 5 amp per phase max **£113.40**
 6 KVA 10 amp per phase max **£170.10**
 10 KVA 16 amp per phase max **£345.45**

All plus carriage and VAT

Comprehensive range of L.T., AUTO (110-240V), ISOLATION TRANSFORMERS available for immediate delivery. Leaflet on request.

EPROM ERASURE KIT

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case, to include 12" 8 watt 2537 Argon Tube. Ballast unit, pair of bi-pin leads. Neon indicator, safety microswitch, on/off switch and circuit.
 LESS CASE. Price: **£13.80** + 75p P&P (Total incl. VAT **£16.50**).
 Warning: Tube used in this circuit is highly dangerous to the eyes. Unit MUST be fitted in suitable case.

FROM STOCK AT PRICES THAT DEFY COMPETITION!

AC GEARED MOTORS
 DC MOTORS
 MICROSWITCHES
 RELAYS
 REED SWITCHES
 SOLENOIDS
 PROGRAMME TIMERS

C.F. BLOWERS
 AC CAPACITORS
 STROBE KITS
 FLASHTUBES
 CONTACTORS
 SYNCHRONOUS MOTORS

Phone in your enquiries


SERVICE TRADING CO

LOW COST PROFESSIONAL TEST INSTRUMENTS

sabtronics
FREQUENCY METERS
 100MHz, 600MHz, and 1GHz Models
 from £67

elemic
 Hand Held
 Analogue and
 Digital
 Multimeters

16 Models
 from £18.75

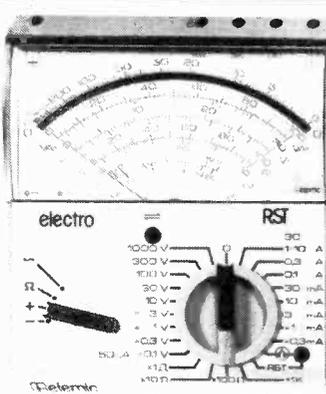

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list

Black Star Ltd.
 9A, Crown Street
 St. Ives, Huntingdon
 Cambs. PE17 4EB
 Tel: (0480) 62440 Telex 32339

WW - 047 FOR FURTHER DETAILS

WE PURCHASE

Surplus component stocks, redundant materials, obsolete computers, for cash.

We also collect - distance no object. Just call:

C. T. Electronics (Acton) Ltd.

267 & 270 Acton Lane, London W4 5DG

Telephone: 01-747 1555; 01-994 6275. Telex: 291429

WW - 071 FOR FURTHER DETAILS

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, 24 hour format, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BST and leap year, can expand to Years, Months and Milliseconds and work as STOPCLOCK, parallel BCD (including Weekday) output for alarm etc and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000K range, GET the RIGHT TIME, £69.60.

60KHZ RUGBY RECEIVER, as in MSF Clock, serial data output for computer etc, decoding details and Basic listings, £22.20. Each fun-to-build kit (ready made to order) includes all parts, printed circuit, case, instructions, by-return postage etc, money back assurance so GET yours NOW.


CAMBRIDGE KITS

45 (WQ) Old School Lane, Milton, Cambridge

Telephone: 860150

Marconi Type R1020 Hinged Antenna Column.

Easy to raise
Easy to lower

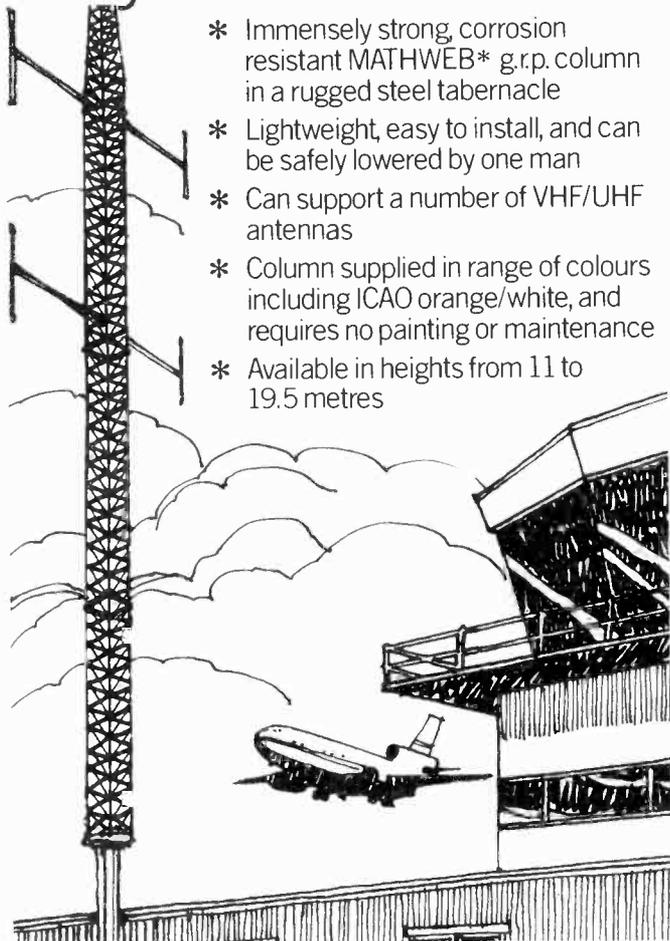

- * Immensely strong, corrosion resistant MATHWEB* g.r.p. column in a rugged steel tabernacle
- * Lightweight, easy to install, and can be safely lowered by one man
- * Can support a number of VHF/UHF antennas
- * Column supplied in range of colours including ICAO orange/white, and requires no painting or maintenance
- * Available in heights from 11 to 19.5 metres

OTHER MARCONI SUPPORT STRUCTURES

Include the MATHWEB* Lattice Antenna Mast Type R1010, and the Triangular Section Tubular Steel Self Supporting Tower Type R1060.

For more information talk to Chris Pettitt, Marketing Manager, Antenna Systems Division.

* MATHWEB is a registered trademark of the BP Group

Marconi

Communication Systems

Antenna Systems Division

Marconi Communication Systems Limited,
Lane Works, Waterhouse Lane, Chelmsford CM1 2QX, England
Tel: 0245 353221 Telex: 99108



A GEC-Marconi Electronics Company

WW - 022 FOR FURTHER DETAILS

CHILTERN ELECTRONICS

INCREDIBLE SCOOP PURCHASE OF
SUPERB HIGH RESOLUTION

9" VIDEO MONITORS

Look at these features:

- ★ 18Mhz Bandwidth
- ★ Over 85 Chars/line resolution
- ★ P31 Green Screen
- ★ Composite Video i/p
- ★ Mains 230v
- ★ Antireflective Faceplate
- ★ Attractively styled case

Why pay £120 or more?

**BRAND NEW IN MAKER'S CARTONS AT
THE AMAZING BARGAIN PRICE OF £78
vat extra, carriage £5**

**Quantity discounts/dealer enquiries
welcome**

THE IDEAL MATCH FOR YOUR MICRO

**High Street, Chalfont St Giles, Bucks
HP8 4QH**

Telephone 02407 71234. Telex 262284

WW - 068 FOR FURTHER DETAILS

TELEVISION

Well worth a closer look

The only magazine in Britain that gives the amateur enthusiast and professional engineer alike a comprehensive up-to-date coverage of TV technology.

In the March issue
SERVICING THE SONY KV1810UB
Restoring these now ageing sets is more simple than it looks. David Botto describes how to go about it.

JUNKING FOR JOY
Stripping down old sets can be a great source of spares.

VINTAGE TV
The unusual circuitry and various servicing problems of the Pye Model V4.

PLUS!
Test Report: The Unahm colour bar generator
Our regular servicing features
GET A COPY TODAY 90p


QUALITY, PERFORMANCE, VALUE ...the extra is DURABILITY

HH 103 . . . £158
Single trace 2mV/cm
10MHz, Component
Tester.

HM203-4 . . . £264
Dual trace 2mV/cm
20MHz, Alg Add, Invert
X-Y, Component Tester.

HM204... £365
Dual trace 2mV/cm
20MHz, Alg Add, Invert
Delay T/B, Var hold-off
Peak Auto Trig to 50MHz,
X-Y, Single Shot, Z Mod,
Component Tester.

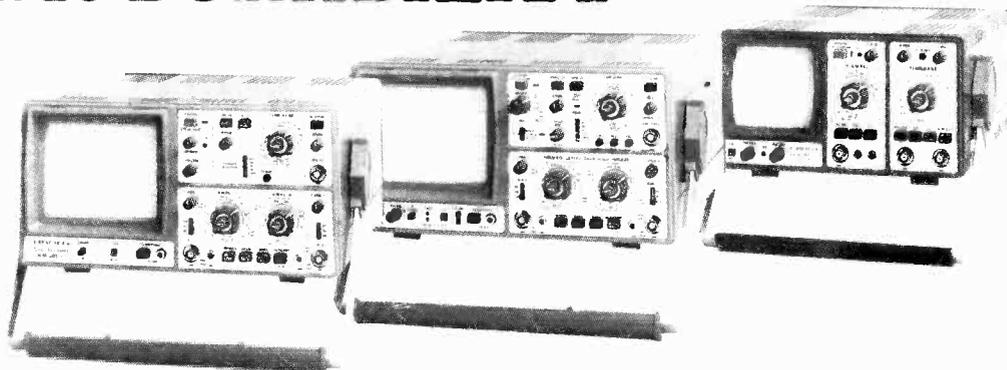HM705 . . . £588
Dual trace 2mV/cm
70MHz, Alg Add, Invert,
Signal Delay, Delay T/B,
Single Shot, Var hold-off,
14KV P.D.A. C.R.T.



For free data sheets of the full range contact:

Prices U.K. list ex. VAT

HAMEG

England
HAMEG LTD.
74-78 Collingdon Street,
Luton, LU1 1RX
Tel: (0582) 413174/Telex: 825484

France
HAMEG S.A.R.L.
5-9 Avenue de la Republique
94800 Villejuif,
Tel: 678.09.98/Telex: 270705

Spain
HAMEG IBERICA S.A.
Villaruel 172-174,
Barcelona-36
Tel: 230.15.97

West Germany
HAMEG Gmbh
6 Frankfurt am Main 71,
Kelsterbacher Str. 15-19
Tel: 0611/676017 Telex: 0413866

United States
HAMEG, INC.
88-90 Harbor Rd.,
Port Washington, N. Y. 11050
Phone: 516.883.3837/516.883.6428

WW - 051 FOR FURTHER DETAILS

WHAT ARE YOU DRIVING?

INDUCTION LOOP TRANSMITTERS
VIBRATOR/SHAKERS
SERVOMOTORS
MAGNETS

CRIMSON ELEKTRIK POWER AMP MODULES HAVE DONE IT ALL

CHOOSE our acclaimed Bipolar Modules for the best in Hi-Fi. These modules have been widely used by professional bodies. They are high slew, low t.h.d. devices without need for the output fuses that spoil fidelity. They have instantly resettable 'electronic fuse' and are L-bracket mounting for flexi installation.

CHOOSE Our Mosfet Modules for the most difficult loads. These modules are rugged and make ideal line step-up transformer drivers. They respond down to d.c. and make excellent servo-driving devices. They have low d.c. offset drift due to j fet inputs.


B I P O L A R	M O S F E T	TYPE	MAX. O/P POWER	SUPPLY TYP.	VOLTAGE MAX.	THD TYP.	PRICE INC. V.A.T. & POST
		CE 608	60W/8Ω	± 35	± 40	< .01%	£21.50
		CE 1004	100W/4Ω	± 35	± 40	< .018%	£25.00
		CE 1008	120W/8Ω	± 45	± 50	< .01%	£28.00
		CE 1704	200W/4Ω	± 45	± 63	< .015%	£35.50
		CE 1708	180W/8Ω	± 60	± 63	< .01%	£35.50
		CE 3004	320W/4Ω	± 60	± 63	< .02%	£49.50
		FE 908	90W/8Ω	± 45	± 60	< .01%	£30.00
		FE 1704	170W/4Ω	± 45	± 60	< .025%	£39.00

Export - no problem. Please write for quotation or quote your Visa/Master Charge card number.




Crimson Elektrik

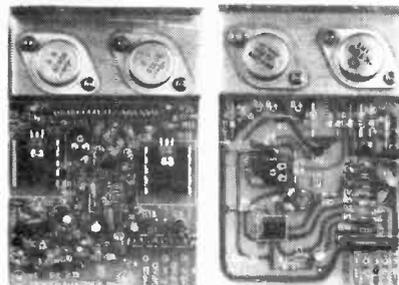FREEPOST, 9 Claymill Road, Leicester, LE4 7JJ, England



POWER AMPLIFIERS


POWER AMPLIFIERS

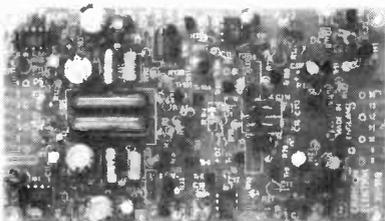

PRE-AMPLIFIERS




ACTIVE CROSSOVERS

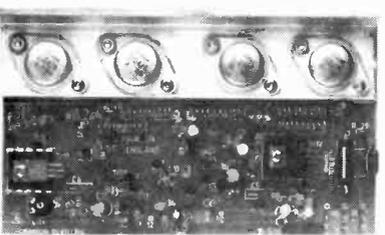

HEAVY DUTY POWER AMPLIFIERS

BBC Micro Computer

Please phone for availability

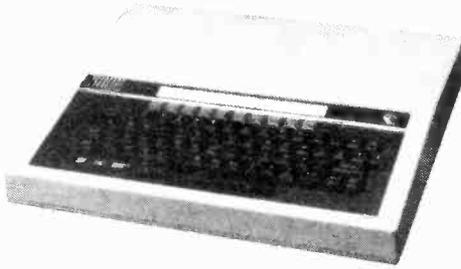

BBC Model A £299
 BBC Model B £399
 (incl. VAT)
 Carr £8/unit
 Model A to Model B
 upgrade kit £50
 Fitting charge £15
 Individual upgrades also
 available

WORD PROCESSOR 'VIEW'
 16K ROM £52

TELETEXT ADAPTOR £195
 PRESTEL ADAPTOR £90
 2nd PROCESSOR 6502/Z80 £170

ACORN SOFT/BBC SOFT/GAMES PADDLES IN STOCK

OFFICIAL **BBC** DEALER

FLOPPY DISC INTERFACE
 incl. 1.0 0.5
£95 & £20 installation

Phone or send for our BBC leaflet

BBC FLOPPY DISC DRIVES
 Single Drive 5¼" 100K £235+£6 carr.
 Double Drive 5¼" 800K £799+£8 carr.

BBC COMPATIBLE DRIVES
 These are drives with TEAC FD50 mechanism
 and are complete with power supply
 SINGLE: 100K £190; 200K £260; 400K £340
 DUAL: 200K £360; 400K £490; 800K £610

CASSETTE RECORDER

Ferguson 3T07
 £26.50 + £1.50 carr
 Cassette Leads £3.50
 Computer Grade Cassettes £0.50 each
 £4.50 for 10 + £1 carr

MONITORS

BMC BM1401 14"
 Colour Monitor RGB input
 £265 & £8 carr
 KAGA RGBI 12" Colour Monitor
 RGB input £235 & £8 carr
 KAGA 12" High Res Green Monitor
 £170 & £6 carr

MICROVITEC 1431 M/S 14"
 Colour Monitor £269 & £8 carr
 Hi Res Green Monitor £99 & £6 carr
 RGB Lead for BMC/KAGA £10
 Composite Video Lead £3.50

ACORN ATOM

Basic Built £135. Expanded £175
 (Carr £3 per unit)
 Atom Disc Pack £299 + £6 Carr
 3A 5v Regulated PSU £26 + £2 Carr
 Phone or send for our BBC Atom list

NEC PC 8023 BE - C


100CPS, 80 cols
 Logic Seeking, Bi-
 directional,
 Forward and Reverse
 Line Feed,
 Proportional Spacing,
 Auto Underline,
 Hi-Res and Block
 Graphics, Greek Char.
 Set.
 Only £320+£8 carr.



PRINTERS

SEIKOSHA GP 100A
 80 cols 30 CPS
 Full ASCII & Graphics
 10" wide paper
 Now only £175+£6 carr.
 Ask for details on GP 250A

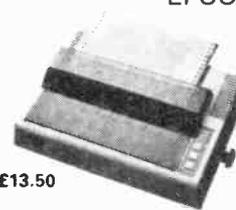Parallel Printer lead for BBC/Atom to most printers £13.50
 Variety of interfaces, ribbons in stock.
 2,000 fan fold sheets 9½" x 11" £13.50 x £3 p&p



EPSON MX 80 and 100F/T3

MX 80 80CPS 80 cols
 MX 100 100CPS
 136 cols
 Logic Seeking, Bi-
 directional,
 Bit Image Printing, 9
 x 9 Matrix
 Auto Underline
 MX 80 F/T3 £325
 MX 100 F/T3 £430
 (£8 Carr/Printer)

RUGBY ATOMIC CLOCK

This Z80 micro controlled clock/calendar receives
 coded time data from NPL Rugby. The clock never
 needs to be reset. The facilities include 8 independ-
 ent alarms and for each alarm there is a choice of
 melody or alternatively these can be used for
 electrical switching. A separate timer allows
 recording of up to 240 lap times without interrupt-
 ing the count. Expansion facilities provided.

See July/August ETI for details.
 Complete Kit £120 + £2 p&p

CONNECTOR SYSTEMS

ID CONNECTORS
 (Speedblock type)

No of ways	Header Plug	Receptacle	Edge Conn.
10	90p	90p	200p
20	145p	125p	240p
26	175p	150p	300p
34	200p	160p	380p
49	220p	190p	550p
50	235p	200p	600p

JUMPER LEADS

24" Ribbon Cable with Headers			
1 end	14pin	16pin	24pin
2 ends	145p	165p	240p
	210p	230p	345p

24" Ribbon Cable with Sockets			
1 end	20pin	26pin	34pin
2 ends	160p	210p	270p
	290p	385p	490p

Ribbon Cable with D. Conn.
 25-way Male 500p. Female 550p

AMPHENOL CONNECTORS

36 way Solder Type Plug (centronix type)	550p
36 way Solder Socket (centronix type)	550p
36 way IDC Plug (centronix type)	500p
24 way Solder Plug (IEEE type)	500p
24 way Solder Socket	500p
24 way IDC Plug	485p

RIBBON CABLE

(Grey)	
10 way	60p
14 way	80p
16 way	90p
20 way	105p
26 way	140p
34 way	220p
40 way	265p
50 way	330p
64 way	370p

MICROTIMER

6502 Based Programmable clock timer with
 ★ 224 switching times/week cycle
 ★ 24-hour 7-day timer
 ★ 4 independent switch outputs directly
 interfacing to thyristor/triacs
 ★ 6 digit 7 seg. display to indicate real time,
 ON/OFF and Reset times
 ★ Output to drive day of week switch and
 status LEDs.
 Full details on request. Price for kit £57

D CONNECTORS

No. of ways			
MALE			
Solder	90p	130p	160p
Angled	180p	230p	265p

FEMALE			
Solder	110p	160p	210p
Angled	175p	240p	310p
Hoods	95p	95p	125p

RS 232 CONNS

(25 way D)	
24" Single end Male	£5.50
24" Single end Female	£6.00
24" Female-Female	£11.00
24" Male-Male	£10.00
24" Male-Female	£11.50

DIL HEADERS

Solder		IDC	
Type	Type	Type	Type
14pin	40p	100p	100p
16pin	50p	110p	110p
24pin	100p	150p	150p
40pin	200p	225p	225p

EURO CONNECTORS

DIN STD	Plug	Skt.
41617 21 way	170p	170p
41617 31 way	180p	180p
41612 2x32 way	250p	320p
Angled 2x32 way	325p	375p
41612 3x32 way	275p	380p
Angled 3x32 way	—	400p
2x32 way IDC a+c	—	525p

(for 2x32 way specify a+b or a+c)


EDGE CONNECTORS

0.1"		0.156"	
2x18 way	—	140p	140p
2x22 way	200p	170p	170p
2x23 way	210p	—	—
2x25 way	225p	220p	220p
1x43 way	260p	—	—
2x43 way	395p	—	—
2x50 way	—	—	—
1x77 way	700p	—	—
S100 Conn.	—	600p	600p

MICRODOCTOR

£295

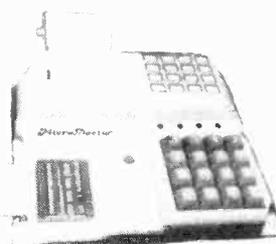This is not a logic analyser or an oscilloscope. It tests a microsystem and gives a printed reprint on RAM, ROM and I/O - it will print memory map, search for code, check dataline shorts and operates peripherals. Microdoctor complete with psu, printer probe cable and two configuration board.



SOFTY II INTELLIGENT PROGRAMMER

The complete microprocessor development system for Engineers and Hobbyists. You can develop programs, debug, verify and commit to EPROMS or use in host computer by using softy as a romulator. Powerful editing facilities permit bytes, blocks of bytes changed, deleted or inserted and memory contents can be observed on ordinary TV. Accepts most +5v Eproms
 Softy II complete with PSU, TV Lead and Romulator lead £169

SPECIAL OFFER

2114L	80p
2716 (+5v)	250p
2532	350p
4116-2	80p
4164-2	450p
6116P	350p

UV ERASERS

UV1B up to 6 Eproms £47.50
 UV1T with Timer £60
 UV140 up to 14 Eproms
 £61.50
 UV141 with Timer £78
 (Carr £2/eraser)
 All erasers are fitted with
 mains switches and safety in-
 terlocks.

TRAINER KITS

6502 Junior Computer.....£85
 6802 Nancomp I.....£80
 6809 Nancomp II.....£80
 1802 Micro Trainer.....£64
 Z80 Menta.....£115
 (fully built and documented)
 Full details on request

BOOKS

(No VAT p&p £1)
 CMOS Cook Book.....£7.75
 CRT Controller H/Book.....£5.95
 Programming the Z80.....£11.50
 Z80 Microcomp Handbook.....£6.95
 6502 Programming the 6502.....£10.25
 6502 Assy. Lang.....£12.10
 6502 Applications.....£10.20
 6502 Software Design.....£9.05
 6502 Games.....£10.25
 Large selection of databooks, interfac-
 ing books, books on BBC, etc in stock.
 Ask for our list. WW-12

**NEW COMPREHENSIVE CATALOGUE AVAILABLE
 PLEASE SEND FOR PRICE LIST**

CIRCUIT MODELLER for CP/M

by Harcourt Systems

For the first time a CAD package for CP/M* microcomputers to carry out accurate, fast designs of linear circuits.

CIRCUIT MODELLER can find voltage gain, phase shift, Z_{in} and Z_{out} for most linear electrical and electronic circuits. The limits of capacity are set by the microcomputer RAM, which must be at least 60 KBytes. This gives a capacity of 32 nodes, 101 resistors, 101 capacitors, 101 inductors, 31 mutual inductors, 31 simple operational amplifiers and 31 controlled sources.

Features include:

- ADD & EDIT** to construct and alter circuit
- LOAD & SAVE** to save and recover circuit from disk
- GAIN** to display gain and phase
- ZIN** to display in and output impedances
- BW** to find centre frequency and -3dB Av points of circuit
- SEARCH** to find frequency corresponding to given gain
- PRINT** to print synopsis of circuit diagram sufficient for its precise reproduction.

Operating Speed

CIRCUIT MODELLER is an all-compiled package with seven overlays in which the inner two loops of pivotal condensations are written in Z80 assembler. This means that whereas microcomputer CAD is usually slow, **CIRCUIT MODELLER** can solve a four hybrid-pi amplifier in a few seconds.

Graphics



PLOT is an optional extra extension to **CIRCUIT MODELLER** enabling an ordinary 132 column printer to plot both dB gain and phase angle against frequency for the circuit. A log/log plot is obtained with automatic axis scaling.

Themselves designers of high performance electronic equipment, Seasim Controls have recognised the importance of **CIRCUIT MODELLER** which they are making available in association with Harcourt Systems. **CIRCUIT MODELLER** is priced at £125 + VAT and **PLOT** at £35 + VAT. Order, or send for more details from

SEASIM CONTROLS LIMITED

The Paddocks, Frith Lane, Mill Hill, London NW7 1PS
Telephone: (01) 346 9271 - Telex: 28915


*CP/M is a trademark of Digital Research

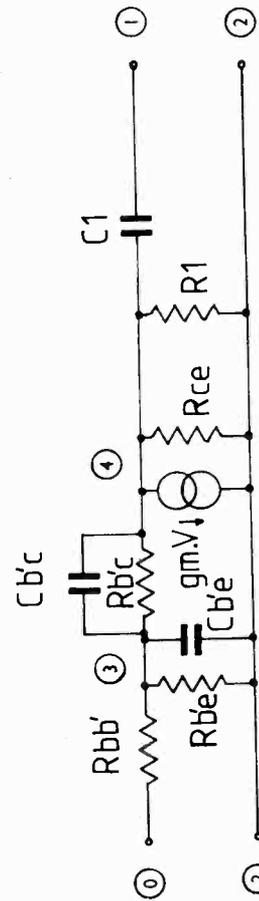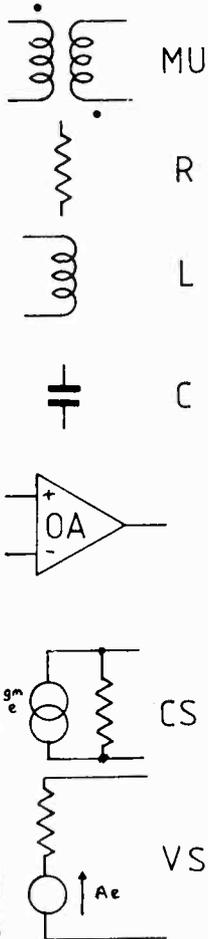

WW - 054 FOR FURTHER DETAILS

FYLDE

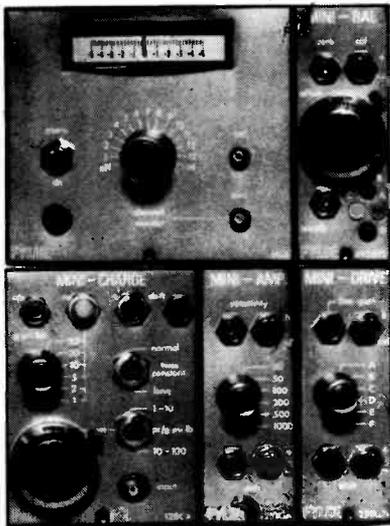TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

WW - 034 FOR FURTHER DETAILS

LAST CHANCE AT THIS PRICE. METALFILM RESISTORS 1% Tolerance, 1/4 Watt

100R	1k	10k	100k
110R	1k1	11k	110k
120R	1k2	12k	120k
130R	1k3	13k	130k
150R	1k5	15k	150k
160R	1k6	16k	160k
180R	1k8	18k	180k
200R	2k	20k	200k
220R	2k2	22k	220k
240R	2k4	24k	240k
270R	2k7	27k	270k
300R	3k	30k	
330R	3k3	33k	330k
360R	3k6	36k	
390R	3k9	39k	
430R	4k3	43k	
470R	4k7	47k	470k
510R	5k1	51k	
560R	5k6	56k	560k
620R	6k2	62k	
680R	6k8	68k	680k
750R	7k5	75k	
820R	8k2	82k	820k
910R	9k1	91k	910k

ONLY 3p EACH

High Quality High Stability.
Huge Strength.

Minimum order £20
Minimum 5 pcs per value
89 Values (E24)

VAT, p&p inclusive.

SPECIAL OFFER
10 PCS of EACH (890 RESISTORS)
£23.00

ORION SCIENTIFIC PRODUCTS LTD.

16 Orange Street
London WC2

WW - 016 FOR FURTHER DETAILS

SALE* P.&R. COMPUTER SHOP SALE*

IBM GOLFBALL PRINTERS from £70 EACH + V.A.T.

- *BRAND-NEW LA36 DEC WRITERS—SALE £200 EACH
- *BRAND-NEW LA180 DEC WRITER—SALE £300 EACH
- CENTRONIC 779 PRINTERS—£325 + V.A.T.
- CENTRONIC 781 PRINTER—£350 + V.A.T.
- POWER UNITS, 5-VOLT 6-AMP—£20 EACH
- FANS, PCBs, KEYBOARDS AND LOTS MORE

COME AND LOOK AROUND

**SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, MALDON, ESSEX
PHONE MALDON (0621) 57440**

WW - 025 FOR FURTHER DETAILS

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER £18 Post £2
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13 1/2 x 11 1/4 in. 3 speeds. Above motor board 3 3/4 in. Below motor board 2 1/2 in. Cut out Mounting Board £1 extra



HEAVY METAL PLINTHS Post £2
Cut out for most BSR or Garrard decks. Silver grey finish, black trim. Size 16x13 3/4 in. £4

DECCA TEAK VENEERED PLINTH. Post £1.50
Superior finish with space and panel for small amplifier. Board is cut for B.S.R. 18 3/4 in. x 14 1/4 in. x 4 in. Black/chrome fascia trim. Also with boards cut out for Garrard £3. Tinted plastic cover £5

TINTED PLASTIC COVERS Post £2

17 7/8 x 13 7/8 x 3 1/4 in.	£5	18 1/4 x 12 1/2 x 3 in.	£5
17 1/4 x 9 3/8 x 3 1/2 in.	£5	14 3/8 x 12 1/2 x 2 7/8 in.	£5
16 1/2 x 15 x 4 1/2 in.	£5	16 3/8 x 13 x 4 in.	£5
17 x 12 7/8 x 3 1/2 in.	£5	14 1/2 x 13 3/8 x 2 3/4 in.	£5
22 5/8 x 13 7/8 x 3 in.	£5	17 1/4 x 13 3/4 x 4 1/8 in.	£5
21 1/2 x 14 1/4 x 2 1/2 in.	£5	21 x 13 7/8 x 4 1/8 in.	£5
23 3/4 x 14 x 3 1/8 in.	£5	30 3/4 x 13 3/8 x 3 1/4 in.	£5

BSR SINGLE PLAYER DECKS
BSR P170 RIM DRIVE QUALITY DECK £20 Post £2
Manual or automatic play. Precision ultra slim arm. Black with silver trim, stereo ceramic cartridge



BSR P204 SINGLE PLAYERS SPECIAL OFFERS Post £2
Two speed 33/45 r.p.m. hi-fi decks with stereo cartridges, cueing device and snake arm. Ceramic - 240V AC £15 or 9V DC £18
Magnetic - 240V AC £20 or 12V DC £24

THE "INSTANT" BULK TAPE ERASER £9.50 Post 95p
Suitable for cassettes and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools and computer tapes.
Head Demagnetiser only £5.



BATTERY ELIMINATOR MAINS TO 9 VOLT O.C.
Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5x3 1/4 x 2 1/2 in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models. £4.50. Post 50p.

DE LUXE SWITCHED MODEL STABILISED. £7.50. PP £1.
3-6-7 1/2-9 volt 400ma DC max. Universal output plug and lead. Pilot light, mains switch, polarity switch.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy build kit. Controls up to 480 watts AC mains. £3. PP 65p.
DE LUXE MODEL READY-BUILT 800 watts. Front plate fits standard box, £5. Post 65p.

EMI 13 1/2 x 8 in. LOUDSPEAKERS £8 Post £1.50
Model 450, 10 watts R.M.S. with moving coil tweeter and two-way crossover; 3 ohm or 8 ohm. "Final Clearance". Sale Price
SUITABLE BOOKSHELF CABINET Post £1.50
£6.50. Size 18 x 11 x 6 in. Post £1.50.



RELAYS. 6V DC 95p. 12V DC £1.25. 18V £1.25. 24V £1.30
ALUMINIUM CHASSIS. 6x4 - £1.75; 8x6 - £2.20; 10x7 - £2.75; 12x8 - £3.20; 14x9 - £3.60; 16x6 - £2.50; 16x10 - £3.80.

ALUMINIUM PANELS. 6x4 - 55p; 8x6 - 90p; 14x3 - 90p; 10x7 - £1.15; 12x8 - £1.30; 12x5 - 90p; 16x6 - £1.30; 14x9 - £1.75; 12x12 - £1.80; 16x10 - £2.10.

ALUMINIUM BOXES. 4x4 x 1 1/2 £1.20. 4x2 x 2 £1.20. 3x2 x 1 £1.20. 6x4 x 2 £1.90. 7x5 x 3 £2.90. 8x6 x 3 £3.30. 10x7 x 2 1/2 £3.60. 12x5 x 3 £3.60. 12x8 x 3 £4.30.

BRIDGE RECTIFIER 200V PIV 2a £1. 4a £1.50. 6a £2.50.
TOGGLE SWITCHES SP 40p. DPST 50p. DPDT 60p.
MINIATURE TOGGLES SP 40p. DPDT 60p.

RESISTORS. 10Ω to 10M. 1/4W, 1/2W, 1W, 2P. 2W 10p.
HIGH STABILITY. 1/2W 2% 10Ωms to 1 meg. 10p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 20p.
PICK-UP CARTRIDGES SONOTONE 9TAHC £3.80.
BSR Stereo Ceramic SC7 Medium Output £2. SC12 £3.

PHILIPS PLUG-IN HEAD. Stereo Ceramic. AU1020 (G308 GP310 - GP233 - AG3306, £2. A.D.C., QLM 30/3 Magnetic £5. GOLDRING G850 £8.50, G800 £8.50. STYLUS most Ceramic Accos, Sonatone, BSR, Garrard Philips Diamond £1.20 ea.

MAGNETIC STYLUS, Sony, JVC, Sanyo, Goldring £4.
LOCKTITE SEALING KIT DECCA 118. Complete £1.
VALVE OUTPUT Transformers (small) 90p. Medium £1.50.

SUB-MIN MICROSWITCH, 50p. Single pole changeover.
ANTEX SOLDERING IRON "C" 15W £4.60. 25W X25 £4.70.
JACK PLUGS Mono Plastic 25p; Metal 30p.
JACK PLUGS Stereo Plastic 25p; Metal 35p.
JACK SOCKETS Mono 25p. Stereo 30p.

FREE SOCKETS - Cable end 30p. Metal 45p.
2.5mm and 3.5mm JACK SOCKETS 25p. Plugs 25p.
DIN TYPE CONNECTORS

Sockets 3-pin, 5-pin 15p. Free Sockets 3-pin, 5-pin 25p.
Plugs 3-pin 20p; 5-pin 25p; Speaker plugs 25p; Sockets 15p.
PHONO PLUGS and SOCKETS ea. 20p.
Free Socket for cable end 20p. Screened Phono Plugs 25p.

B.N.C. PLUGS £1. Sockets £1. Free Sockets £1.10.
UHF PLUGS 50p. Sockets 50p. Reducers 20p.
300 ohm TWIN RIBBON FEEDER 10p yd.
300 ohm to 75 ohm AERIAL MATCHING TRANSFORMER £1.

U.H.F. COAXIAL CABLE SUPER LOW LOSS. 25p yd.
COAX PLUGS 30p. COAX SOCKETS 20p. Lead Sockets 65p.
NEON INDICATORS 250V, round 40p. Rectangular 45p.

POTENTIOMETERS Carbon Track
5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5K. SP 45p.

MINI-MULTI TESTER NEW
De Luxe pocket size precision moving coil instrument. Impedance + Capacity - 4000 o.p.v. Battery included. 11 instant ranges measure: DC volts 5.25, 250, 500. AC volts 10, 50, 500, 1000. £6.50
DC amps 0-250µA, 0-250mA. Post 50p
Resistance 0 to 600K ohms.



De Luxe Range Doubler Model, £50,000 o.p.v. £18.50. 7x5x2in. Post £1

NEW PANEL METERS £4.50
50µa, 100µa, 500µa, 1ma, 5ma, 50ma, 100ma, 500ma, 1 amp, 2 amp
25 volt, VU Meter.
2 1/4 x 2 x 1 1/4 Post 50p
Stereo VU meter £3
3/4 x 1 1/2 x 1 in.



RCS SOUND TO LIGHT CONTROL BOX £27
Complete ready to use with cabinet size 9x3x5in. 3 channel, 1000 watt each. For home or disco
Input 200mV to 100 watt. AC 200/250V. Post £1.
OR KIT OF PARTS £19.50. LESS CABINET £15
Disco bulbs 100 watt, blue, green, yellow, red, amber, screw or bayonet £1.85 each. Post £1.50 per six.
Rope lights, 4 channel, 11ft with controller £33. PP £1.
"FUZZ" lights, red, blue, green, amber, 240V AC. £23.
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights, Edison Screw. 6 for £4, or 12 for £7.50. Post £1.50. Suitable panel mounting holders 85p.

RCS "MINOR" 10 watt AMPLIFIER KIT £14
This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Specification 10W per channel; size 9 1/2 x 3 1/2 in. SAE details. Full instructions supplied. 240V AC mains. Post £1.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board. Can be ganged to make multi-way stereo mixers. £3.50 Post 65p

MAINS TRANSFORMERS Post

250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A	£6.00	£2	
350-0-350V 250mA, 6.3V 6A CT	£12.00	£2	
220V 25ma 6V 1amp £2.50	220V 45ma 6V 2 Amp	£4.00	£1
250V 60ma, 6V 2A		£4.75	£1

AUTO 115V to 240V 150W £9. 250W £11. 400W £11. 500W £12.00 £2

GENERAL PURPOSE LOW VOLTAGE Price Post

Tapped outputs available			
2 amp 3, 4, 5, 8, 9, 10, 12, 15, 18, 25 and 30V		£6.00	£2
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£8.00	£2
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£10.50	£2
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£12.50	£2
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£16.00	£2
5-8-10-16V 1/2 amp	£2.50	£1	
15-0-15V 2 amps	£4.50	£1	
6V 1/2 amp	£2.00	£1	
20V 1 amp	£4.00	£1	
6-0-6V 1/2 amp	£3.50	£1	
20-0-20V 1 amp	£4.50	£1	
9V, 250ma	£1.50	£1	
20-40-80V 1 amp	£4.50	£2	
9V-9V, 50ma	£1.50	£1	
25-0-25V 2 amps	£4.50	£1	
10-0-10V, 2 amps	£4.00	£1	
28V 1 amp Twice	£6.00	£2	
10-30-40V, 2 amps	£4.50	£1	
30V 5 amp and	£4.50	£1	
12V, 100ma	£1.50	£1	
17-0-17.2A	£5.50	£2	
12V, 750 ma	£2.50	£1	
35V 2 amps	£4.50	£1	
12V 3 amps	£4.50	£1	
TOROIDAL 30-0-30V 4A	£10.00	£2	
12-0-12V, 2 amps	£4.50	£1	
and 20-0-20V 1/2A			
CHARGER TRANS	Post		
6-12 volt 3a	£4.00	£2	
6-12 volt 4a	£6.50	£2	
6-12 volt 2a	£1.10	£0.80p	
6-12 volt 4a	£2.00	£0.80p	

OPUS COMPACT SPEAKERS £22 pair Post £2
TEAK VENEERED CABINET
11x8 1/2 x 7 in, 15 watts
50 to 14,000 cps. 4 ohm or 8 ohm
OPUS TWO 15x10 1/2 x 7 1/4 in 25 watt 2-way system £39 pair. Post £3

LOW VOLTAGE ELECTROLYTICS Wire ends 10p

1 mf, 2 mf, 4 mf, 8 mf, 10 mf, 16 mf, 25 mf, 30 mf, 50 mf, 100 mf, 250 mf. All 15 volts. 22 mf/6V/10v; 25 mf/6V/10v; 47 mf/10v; 50 mf/6v; 68 mf/6v/10v; 16v/25v; 100 mf/10v; 150 mf/6v/10v; 200 mf/10v/16v; 220 mf/4v/10v/16v; 330 mf/4v/10v; 500 mf/6v; 680 mf/6v/10v; 1000 mf/2.5v/4v/10v; 1500 mf/6v/10v/16v; 2200 mf/6v/10v; 3300 mf/6v; 4700 mf/4v. 500mf 12V 20p; 25V 20p; 50V 30p; 1200mf 76V 80p. 1000mf 12V 20p; 25V 35p; 50V 50p; 100V 70p. 2000mf 6V 25p; 30V 42p; 40V 60p; 1500mf 100V £1.20. 2200mf 63V 90p. 2500mf 50V 70p. 3000mf 50V 65p; 4500mf 64V £2. 4700mf 63V £1.20. 4700mf/30V 75p.
--

HIGH VOLTAGE ELECTROLYTICS

2/500V 45p	32-32-16/350V 90p	8+8/500V	£1
8/450V 45p	100+100/275V 65p	8+16/450V	75p
16/350V 45p	150+200/275V 70p	16-16/350V	80p
32/500V 95p	220/450V	95p	32+32/350V 85p
32/350V 50p	32-32+32/325V 75p	32+32/500V	£1.80
50/450V 95p	50+50+50/350V 95p	50+50/300V	50p

CAPACITORS WIRE END High Voltage

.001, .002, .003, .005, .01, .02, .03, .05 mfd 400V 5p.	
.1MF 200V 5p. 400V 10p. 600V 15p. 1000V 25p.	
.22MF 350V 12p. 600V 20p. 1000V 30p. 1750V 50p.	
.47MF 150V 10p. 400V 20p. 630V 30p. 1000V 60p.	
TRIMMERS 30pF, 50pF, 10p, 100pF, 150pF 20p, 500pF 30p.	
MICROSWITCH SINGLE POLE CHANGEOVER 40p.	
TWIN GANG, 120pF £1. 500+200pF £1. GEARED TWIN GANGS 25pF 95p. 365+365+25+25pF £1.	
BRASS SPINDLE EXTENDERS 85p. Couplers 65p. Vernier drive dials, 36mm £2.25, 50mm £2.75.	
TRANSISTOR TWIN GANG. Japanese Replacement £1	
SOLID DIELECTRIC 100pF £1.50, 500pF £1.50	

HEATING ELEMENTS, WAFER THIN (Semi Flexible)
Size 11x9 x 1/8 in. Operating voltage 240V, 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, Propagation, etc. Must be clamped between two sheets of metal or ceramic, etc.
ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

NEW baker Star sound
high power full range quality loudspeakers British made exceptional reproduction. Ideal for Hi-Fi, music P.A. or discotheques. These loudspeakers are recommended where high power handling is required with quality results. The high flux ceramic magnet ensures clear response.



MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£16	£2
DELUXE MK II	12	8	15	HI-FI	£16	£2
SUPERB	12	8-16	30	HI-FI	£26	£2
AUDITORIUM	12	8-16	45	HI-FI	£24	£2
AUDITORIUM	15	8-16	60	HI-FI	£37	£2
GROUP 45	12	4-8-16	45	PA	£16	£2
GROUP 75	12	4-8-16	75	PA	£20	£2
GROUP 100	12	8-16	100	Guitar	£26	£2
OISCO 100	12	8-16	100	Oisco	£26	£2
GROUP 100	15	8-16	100	Guitar	£35	£2
OISCO 100	15	8-16	100	Oisco	£35	£2

BAKER AMPLIFIERS BRITISH MADE
NEW PA150 MICROPHONE PA AMPLIFIER £129
4 channel 8 inputs, dual impedance, 50K-500 ohm 4 channel mixing, volume, treble, bass. Presence controls, Master volume control, echo/send/return socket. Slave sockets. Post £3.
BAKER 150 Watt AMPLIFIER 4 Inputs £99
For Discotheque, Vocal, Public Address. Three speaker outlets for 4, 8 or 16 ohms. Four high gain inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing, 150 watts 8 ohms R.M.S. Music Power. Slave output 500 M.V. 25K ohm. Response 25 Hz - 20KHz ± 3db. Integral Hi-Fi preamp separate Bass & Treble. Size - 16" x 8" x 5 1/2". Wt - 14lb. Master volume control. British made. 12 months guarantee. 240V A.C. mains or 120V to order. All transistor and solid state. Post £2.
MONO SLAVE VERSION £80. 100 Volt Line Model £104. Post £2.
New Stereo Slave Model 150 + 150 watt £125. Post £24.



BAKER £69 50 WATT AMPLIFIER Post £2
Ideal for PA systems, Discos and Groups. Two inputs, Mixer, Volume, Controls, Master Bass, Treble Gain.



RCS offers MOBILE PA AMPLIFIERS. Outputs 4-8-16 ohms
20-watt RMS 12V DC, AC 240V, 3 inputs 50K £46 PP £2.
40-watt RMS 12V DC, AC 240V, 4 inputs 50K £75 PP £2
Mic 1; Mic 2; Phono; aux. outputs 4 or 8 or 16 and 100v line
60-watt RMS, Mobile 24 volt DC & 240-volt AC mains, inputs 50K. 3 mics + 1 music. Outputs 4-8-16 ohm + 100 volts line £95 PP £2

Battery only Portable PA Amplifier 10w max. Includes mike and speaker, OK for meetings, crowd control, stalls, fetes, traders, parties, etc. Batteries included (6 of U2) £27.50 post £2

R.C.S. 100 watt Robust VALVE AMPLIFIER
4 Channel mixing. Master treble, bass and volume controls. 5 Speaker outlets, suits 4, 8, 16 ohm. Disco group. £125. Carr. & ins. £15.

FAMOUS LOUDSPEAKERS "SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
SEAS	TWEETER	4in	50	8	£9.50	£1
GOODMANS	TWEETER	3 1/2in	25	8	£4	£1
AUOX	TWEETER	4in	30	8	£6.50	£1
SEAS	MIO-RANGE	4in	50	8	£7.50	£1
SEAS	MIO-RANGE	4 1/2in	100	8	£12.50	£1
AUOX	WOOFER	5 1/2	25	8	£10	£1
GOODMANS	HIFAX	7 1/2 x 4 1/4	100	4/8-16	£27	£2
GOODMANS	WOOFER	8in	25	4/8	£6.50	£1
GOODMANS	HB	8in	60	8	£12.50	£1
WHARFEOALE	WOOFER	8in	30	8	£9.50	£2
AUOX	WOOFER	10in	50	8	£16	£2
GOODMANS	HPG	12in	120	8/15	£29.50	£2
GOODMANS	GR12	12in	90	8/15	£27.50	£2
GOODMANS	HPD	12in	120	8/15	£29.50	£2
GOODMANS	HPO	18in	230	8	£80	£4

SPEAKER COVERING MATERIALS. Samples Large S.A.E.
B.A.F. LOTUSPEAKER CABINET WOODING 18in wide 35p ft.

MOTOROLA PIEZO ELECTRIC HORN TWEETER, 3 3/8in. square £5
100 watts. No crossover required. 4-8-16 ohm, 7 1/2 x 3 1/4 in. £10

CROSSOVERS TWO-WAY 3000 cps/30 watt £3. 100W £4.
3-way 950 cps/3000 cps. 40 watt rating £4. 3 way 60 watt £6. 100W £8.
LOUDSPEAKER BARGAINS. Please enquiry, many others.
3 ohm, 5in, 7x4in, £2.50; 6 1/2in, 8x5in, £3; 8in, £3.50, 10in, £5.
8 ohm, 2 1/2in, 3in, £2; 5x3in, 6x4in, 7x4in, 5in, £2.50; 6 1/2in, 8x5in, £3; 8in, £4.50; 10in, £5; 12in, £6.
15 ohm, 2 1/4in, 3 1/2in, 5x3in, 6x4in, £2.50; 6 1/2in 10W £5. 8in £4.
25 ohm, 3in, £2; 5x3in, 6x4in, 7x4in, £2.50. 120 watt, 3 1/4 in dia. £1.
CAR CASSETTE MECHANISM. 12V Controlled Motor Stereo Head £5

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £3.95. Post 65p
All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7 1/2 or 9 or 12V d.c. up to 100mA or less. Please state voltage required.

Dept 1, 337 WHITEHORSE ROAD, CROYDON
Open 9-6. Closed all day Wed.

HEMMINGS ELECTRONICS AND MICROCOMPUTERS

16 BRAND ST
HITCHIN
HERTS
SG5 1JE

Tel: (0462) 33031
Shop open Mon.-Sat. 9 a.m.-5.30 p.m.
Closed all day Wednesday



Professional quality electronic components, brand new and fully guaranteed. Mail order by return of post. Cash/Cheque/POs or Banker's Draft with order, payable to Hemmings Electronics Ltd. Official orders from schools, colleges and universities welcome. Trade and export enquiry welcome. P.&P. add 45p to all orders under £10. Telephone your Access orders, using our 24-hr. Ansaphone service. Please send SAE for full price list.

VAT - All prices exclusive of VAT - Please add 15% to total cost including P.&P.
No VAT on export orders or books.

COMPUTER ICs		CONNECTIONS		MAINS CONNECTORS	
6502	350p	AY-3-8912	435p	Bulgin P551 8 Pin Plug	220p
6522	340p	AY-3-8912	620p	Bulgin P552 8 Pin Socket	75p
6800	290p	AY-5-1230	450p	Cassette Mains Lead 2m	70p
68000	450p	709	35p	Reversible Connector	70p
6802	345p	741 8 pin	25p	Cassette Mains Plug	28p
6805	845p	741 14 pin	25p	Non-reversible	28p
68089	1350p	741S	55p	IEC Chassis Plug 6A 250V	45p
6809E	1295p	747	85p	IEC Cable Socket 6A 250V	66p
6810	120p	748	35p	IEC Cable Socket with 2m	74p
6821	160p	CA3080E	70p	Integral Lead	74p
68B21	215p	CA3130E	75p	MOLEX KK SERIES 0.1" PITCH	
6840	390p	LA4422	295p	Terminal Housing	
68B40	580p	LF355	80p	22-01-2025 2 Pole	5p
6844	1295p	LF356	80p	22-01-2035 3 Pole	6p
6845	795p	LF357	100p	22-01-2045 4 Pole	6p
6850	140p	LM301A	26p	22-01-2025 5 Pole	7p
6852	250p	LM307	50p	22-01-2065 6 Pole	8p
6854	680p	LM307A	50p	22-01-2075 7 Pole	8p
6875	490p	LM338A	95p	22-01-2085 8 Pole	9p
8T26A	120p	LM311N	86p	22-01-2095 9 Pole	10p
8T28	120p	LM324	86p	22-01-2105 10 Pole	11p
8T95	90p	LM339	50p	22-01-2125 12 Pole	12p
8T96	90p	LM348	75p	22-01-2155 15 Pole	14p
8T97	90p	LM358	60p	Crimp Contacts for Housings	
8T98	90p	LM380	95p	08-50-0136	30p
8035L	340p	LM381	160p	Pack of 100 19p	
8039L	290p	LM393	90p	PCB Wafer Straight Square Pin	38p
8080A	380p	LM3909	85p	22-03-2151 15 Pole	38p
80R5A	450p	MC1310P	210p	PCB Wafer Right Angle Pin	50p
8155	450p	MC1455	68p	22-05-2151 15 Pole	50p
8212	155p	MC1456	135p	PHONO	
8216	100p	MC1458	35p	Plug Blue, Yellow, Red, Black	15p
8224	180p	MC3242A	830p	Plug Screened	22p
8226	195p	MC3302	95p	Line Socket Blue, Yellow	15p
8228	250p	MC3340	120p	Red, Black, White, Green	15p
8243	210p	MC3401	65p	Chassis Socket	25p
8251	300p	MC3403	70p	4 Way In-line Socket	30p
8253	450p	MC3456	107p	Socket/Socket Adaptor	30p
8255	280p	MC3480	580p	TEST PROBE (CLIP-ON)	
8257	450p	MC34001	58p	Pair Miniature Test Probes	110p
8258	450p	NE555	16p	Spring Loaded Hook Grip	80p
8279	460p	555CMOS	90p	Red/Black Length 55mm	80p
75451	85p	NE556	59p	Length 90mm	110p
75452	85p	NE565	155p	Length 135mm	210p
75491	70p	NE567	140p	UNIT SERIES	
75492	70p	TA7205A	125p	Free Plug PL259	50p
AY-5-1015D	300p	TBA4800Q	175p	Reducer for 5.3mm Cable	15p
AY-5-1013A	300p	TBA5300Q	140p	Reducer for 6.4mm Cable	15p
MC1408	285p	TBA5400Q	130p	MISCELLANEOUS	
MC1488	55p	TBA5500Q	280p	Aerial Splitter Low Loss	120p
MC1489	55p	TBA5600Q	160p	Non-resistive	140p
MC3459	285p	TBA750	280p	Surface Mounted Switched	40p
Z80ACPU	350p	TBA800	90p	Car Power Plug	40p
Z80APIO	300p	TBA820	95p	Crocodile Clips	8p
Z80ADCT	300p	TBA820M	85p	Miniature Red or Black	8p
Z80ADART	750p	TBA920	190p	Standard	20p
		TBA990Q	190p	FM Plug	10p
		TC6580	390p	Power Plug 4 way 2.5mm,	20p
		TC9A10	180p	3.5mm Jack, 2.1mm, 2.5mm,	80p
		TC9A1004	290p	DC Connector	20p
		TL061	40p	Terminal Block 2A 12 way	20p
		TL062	80p	TV Coax Plug	20p
		TL064	98p	TV Coax Line Socket	45p
		TL071	30p		
		TL072	50p		
		TL074	100p		
		TL081	25p		
		TL082	45p		
		TL084	95p		
		UPC575	149p		
		UPC1167	158p		
		UPC2002V	285p		
		UPD7002	450p		
		ZN414	100p		

MEMORIES
2114L 90p
2708 220p
2718 210p
2532 380p
2732 380p
4116 85p
4184 500p
6116 390p
6116L 480p

LINEAR ICs
AY-3-1270 725p
AY-3-1350 350p

LIQUID CRYSTAL DISPLAY MODULES
PCM177 Frequency Counter
5 Digits, 0.35" FFL SW, MW, MHz, KHz Annunciators
Sample and Hold Capability
Reset Capability
25 Selectable IF Offsets
Prescaler Available
Incandescent Backlighting
Supply Voltage 5v
Operating Current 4mA

£17.15
PCIM 176 Digital Meter Module
3 1/2 digits, 0.5"
+/- and Decimal Point
200mV Full Scale Input
True Differential Input
Guaranteed '0' Reading
Single 9v Operation
Power Consumption 20mW
Accuracy 0.15%, +/- 1 Count
Temperature drift 60ppm/C
Low Battery Indicator
Incandescent Backlighting

£22.50
All modules are supplied with Data Sheet.

FIBRE OPTIC POLYMER CABLE
A 10m coil of 1mm core optical fibre cable sheathed in black polyethylene for protection £4.95

8" FLOPPY DISK DRIVES
Secondhand, manufactured by CDC - 400KByte, SSSD - perfect condition with data.
Only £90 inc. VAT
Carriage £3

ALFAC ETCH RESIST TRANSFERS
Make your own Printed Circuit Boards with our PCB transfers
★ Draw your artwork on 0.1" grid
★ Transfer to copper board using carbon paper
★ Burnish the Alfac transfers to the board using a spatula using carbon marks to assist in accurate alignment
★ Use Alfac chemical eraser to correct mistakes
★ Etch in Ferric Chloride

EC900/1 0.1" Edge Connector
EC902/1 0.156" Edge Connector
EC940 0.016" Lines
EC941 0.031" Lines
EC942 0.039" Lines
EC943 0.049" Lines
EC944 0.061" Lines
EC945 0.079" Lines
EC946 0.100" Lines
EC947 0.124" Lines
EC950/1 0.031" 90° Bends
EC950/2 0.061" 90° Bends
EC952/1 0.031" 30°, 45°, 60° Bends
EC952/2 0.061" 30°, 45°, 60° Bends
EC908 0.063" Pads
EC910 0.094" Pads
EC911 0.189" Pads
EC960/1 TO-5 Transistor Pads
EC993/1 IC Pads
EC997/1 IC Pads with tracks between pads
5 identical sheets in sealed pack

Individual sheets 196p
Spatula AR4 for burnishing 45p
Alfac knife 185p
Spare Blades (pack of 10) 280p
Alfac Eraser 40p
Alfac Precision Grids: Polyester film, matt finish 0.14mm thickness, 20 lines/in. A3 199p A4 100p
Double Sided Fibreglass Board 1/16" thickness, 1oz Copper, 5" x 4" 25p; 5" x 8" 45p

LIGHT EMITTING DIODES (LED)
3mm Red TIL209 10p
3mm Green LD37C 15p
Panel Clip 4p
3mm Chrome Bezel 35p
5mm Red CQV40L 10p
5mm Green, Yellow 15p
Panel Clip 4p
5mm Chrome Bezel 42p
5mm Square Red 25p
Green, Yellow 30p
Tri-colour V51BP 70p
Red Flashing CQX21 3Hz at 5V 45p

INFRARED
TIL32 Emitter 54p
TIL38 Emitter 45p
TIL78 Phototransistor 54p
TIL100 Photodiode 70p

EPSON MX800/T TYPE III PRINTER
80 Characters per Second, Friction and Tractor Feed, High Resolution 960 Dots/Line, Auto Underlining, Subscripts and Superscripts
£320
Securicor £5

GO FORTH AND MULTIPLY
much quicker with the JUPITER ACE
Available from stock
£89.95 inc. VAT

VIC-20 COLOUR COMPUTER
★ SPECIAL OFFER ★
VIC-20 Colour Computer
C2N Cassette Deck
Programmers Reference Guide
Games Tapes
Demonstration Tape
10 Blank Cassettes
VIC Computing Magazine
£195 inc. VAT
Securicor £6

Toroidal Transformers

THE COTSWOLD "BUDGET RANGE" OFFERS BUILT-IN QUALITY COUPLED TO A RELIABLE DELIVERY SERVICE MOST TYPES FROM STOCK

IEC 65
VDE 0550
BS 415
TO ORDER

PHONE
TELEX, WRITE
FOR DATA SHEET
AND PRICE LIST

Cotswold Electronics LTD.
Unit T1, Kingsville Road, Kingsditch Trading Estate, Cheltenham GL51 9NX
Tel: 0242-41313
Sales Office in U.S.A. AVEL LINDBERG INC. Peacock Alley 116, 1 Padanaram Road, Danbury, CT 06810 U.S.A. 203-797-8698. Telex: 710-456-9984

WW - 017 FOR FURTHER DETAILS

FOR YOUR PMR REQUIREMENTS CONTACT

South Midlands Communications Ltd.
SM House, Osborne Road, Totton
Southampton, England
Tel: 0703 867333 Tlx. 477351 SMCOMM G

EPSON MX800/T TYPE III PRINTER
80 Characters per Second, Friction and Tractor Feed, High Resolution 960 Dots/Line, Auto Underlining, Subscripts and Superscripts
£320
Securicor £5

BASE STATIONS MOBILES HANDHELD


LOW BAND HIGH BAND

UHF

WW - 010 FOR FURTHER DETAILS

The SCOPEX SG315

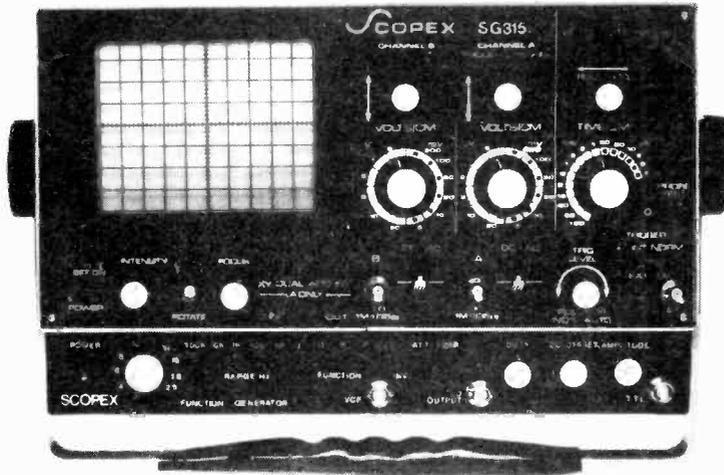A new range of test capabilities
 Combined Oscilloscope and Function Generator
 in one Precision Instrument



SCOPEX Instruments Limited
 Pixmore House, Pixmore Avenue, Letchworth,
 Herts. SG6 1HZ Tel: (04626) 72771 Telex: 825644

The Scope
 15 MHz bandwidth
 5 mV sensitivity
 Timebase range
 1 μ s-100 ms/cm
 8x10 cm screen
 vertical display
 A+B, B invert
 X-Y display,
 X deflection
 through A channel
 for max.
 sensitivity
 Normal, TV and ext.
 trigger

**The Function
 Generator**
 0.2 Hz-250 KHz
 Sine
 Square
 Triangular
 DC offset variable
 Duty cycle variable
 Output 20v,
 600 ohms
 20 dB attenuator
 plus variable
 VCF input
 TTL sync output

Function Generator can be supplied
 separately for you to fit to any Scopex
 Dual Trace scope, just state type when
 ordering, FG4, FG14/25.

Function Generator also available in an
 instrument case, FG1.

Prices:

SG315—£270+VAT. Price includes
 Probes and Mains Plug and carriage UK
 mainland.

Function Generator for mounting
 on Scopex Dual Trace Scopes:
 FG4, FG14/25—£59+VAT

Function Generator: FG1—
 £69+VAT

**NEW!
 SG315**

WW - 041 FOR FURTHER DETAILS

pantechnic

**THE POWERFET
 SPECIALISTS**

POWERFET AMPLIFIER MODULES

MODEL	POWER RANGE (Continuous RMS)	TYPICAL LOADS	PRICES (one off)
PFA 100	50W-150W	4 Ω , 8 Ω	£17.35
PFA 200	100W-300W	4 Ω , 8 Ω	£23.87
PFA 500	250W-600W	2 Ω , 4 Ω , 8 Ω	£42.00
PFA HV	200W-300W	4 Ω , 8 Ω , 16 Ω	£34.30

Key features:

- **RELIABLE** — Powerfet freedom from thermal runaway and secondary breakdown
- **LINEAR** — THD zero, IM/THD < 0.01% full power (mid-band THD down to 0.0015%)
- **FAST** — Slew rate >30V/ μ S (45V/ μ S typical)
- **QUIET** — Signal to noise ratio 120dB
- **BRIDGEABLE** — Without extra circuitry
- **STABLE** — Unconditionally
- **LOW COST** — 10 watts to 20 watts per £, depending on model and quantity

As they stand these modules suit most P.A. and industrial applications and satisfy all foreseeable audiophile requirements. (The HV is aimed at digital audio.) Where aspects of performance fail to meet specific requirements (e.g. in speed or power) low-cost customising is often a possibility. Alternatively entirely new boards can be produced.

ALSO—
 PAN 20—Ultra-low-noise/distortion, mono preamp board, £6.76
 PAX 2/24—2-way active crossover board (24dB/octave) plus regulators, £9.70
 THE HEAT EXCHANGER—New, super-efficient heatsink; handles 300W or 1.2kW when blown; 7in. x 4in. x 2 1/4in., £7.50

This is just a fraction of the new products available from Pantechnic—check us out!

Prices exclude V.A.T.

Carriage 75p

Price and Delivery
PANTECHNIC (Dept WW3)
 17A WOOLTON STREET
 LIVERPOOL L25 5NH
 Tel: 051-428 8485

Technical Enquiries
 contact
 Phil Rimmer
 on
 01-900 6667

WW - 058 FOR FURTHER DETAILS

C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG
 Tel: 01-747 1555/01-994 6275 — Telex: 291429
 9.30 a.m.-6 p.m. MONDAY to SATURDAY CONTINUOUS

**30,000 LOUSPEAKERS TO CLEAR
 ALL SHAPES AND SIZES
 BRAND NEW AND BOXED
 SEND FOR LIST OR PHONE FOR DETAILS**

**30,000 RELAYS TO CLEAR
 BRAND NEW AND BOXED
 SEND FOR LIST OR PHONE FOR
 DETAILS**

This advertisement is mainly of our excess stockholding. We also have excellent stocks of semiconductors, hardware, cables, etc. For further details send for our lists and retail price catalogue, phone or visit our shop. All prices are exclusive of VAT (and P&P). Minimum Mail Order £5+P&P+VAT. Government departments, schools, colleges, trade and export welcome.

WW - 078 FOR FURTHER DETAILS

Accurate Digital Multimeters at Exceptional Prices


NEW ANALOGUE METER WITH CONTINUITY BUZZER AND BATTERY SCALE

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

SPECIFICATION MODELS 6010 & 7030

- 10 amp AC/DC
- Battery: Single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm.
- Weight: 400g inc. battery.
- Mode Select: Push Button.
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 2MΩ
- Input Impedance: 10MΩ
- Display: 3½ Digit 13mm LCD
- O/Load Protection: All ranges

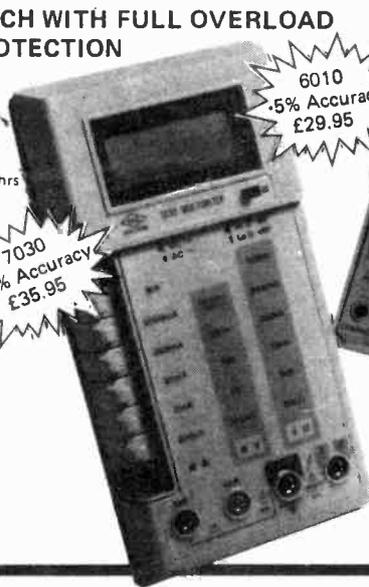OTHER FEATURES: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



6010
±5% Accuracy
£29.95

7030
±1% Accuracy
£35.95

NEW
HM102 BZ
£13.00

NEW HM 102 BZ SPECIFICATION

- DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500µA, 0-5, 50, 500mA
- Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.

HM 101 POCKET SIZE MULTIMETER SPECIFICATION

- DC & AC Voltage: 0-10, 50, 250, 1000 volts, 2000 ohms/volts
- Decibels: -10 to +22dB
- DC Current: 0-100mA
- Ohmmeter: 0-1 Megohm in 2 ranges, 60 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 90 x 60 x 29mm, 92gr. incl. battery
- Price: £5.50


Add 15% to your order for VAT. P&P is free of charge. Quantity discount for trade on application.



ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England
Telephone 01-9024321 (3 lines) TELEX No 923985

WW - 075 FOR FURTHER DETAILS

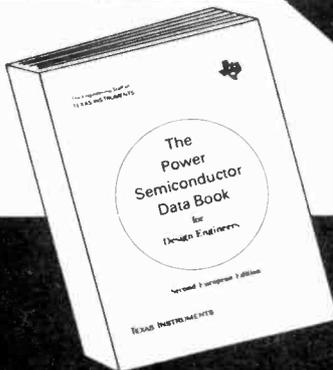

1983
EDITION

Powerful bestseller

The new 1983 edition of the Texas Instruments Power Semiconductor Data Book contains full data on the complete range of TI Power Transistors, Darlingtons, Triacs and Thyristors. Complete the coupon to receive a copy of this 900 page, bestseller ex-stock. Price £9.00 plus p& p.

TEXAS INSTRUMENTS

Please send me _____ copy/copies of the 1983 TI Power Data Book.
I enclose a cheque for £ _____ (including £1.50 p&p per order).
Name _____
Company _____
Address _____
Postcode _____
Mail to: Texas Instruments Ltd., PO Box 50, Market Harborough, Leicestershire.
Registered Office: Texas Instruments Ltd., Manron Lane, Bedford MK41 7PA.
Registered number: 574102 England. WW/1

WW - 077 FOR FURTHER DETAILS

CIRCUIT ANALYSIS ON PET/CBM

An all-machine code program for the rapid analysis of linear electronic circuits.

This package can find voltage gain, current gain, input impedance and output impedance in magnitude phase angle form.

32K RAM required but some 14K available for program development.

Some program features:
Capacity 20 Nodes, 40 passive components, 10 active sources.

Handles transistors, F.E.T., OP-AMP, transformer, transmission line, etc.

Handles hybrid-pi, h, y, s, parameters, etc.

Hardcopy of all results, including graphs.

Graph axes may be LIN/LOG/dB as appropriate with automatic scaling.

Simple, rapid component or parameter changes.

Comprehensive instructions with many examples.

State model number and disc or cassette.

S. J. BRANSON
111 PARK ROAD
PETERBOROUGH PE1 2TR
Tel: (0733) 67604

£80
inclusive
No V.A.T.
or send
for details

C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG
Tel. 01-747 1555/01-994 6275. Telex: 291429

9.30am-6pm
MON. to SAT.
CONTINUOUS

Stabilised Power Supplies.
Switched-mode and Linear.
Brand New, Unbeatable Prices.
Hundreds in stock.
Coutant, Gould, Lambda, Farnell, ITT, Grasham etc.
S.A.E. for latest list.

POWER SUPPLY UNITS

Supplier	Volt	Amps O/H	Price	Supplier	Volt	Amps O/H	Price
COUTANT 240							
ASC200	18	2A 5	22.00	GRESHAM			
ASA1000	5	10A 8	40.00	30/1	12	3.0A 3	31.00
ASB200	12	2A 6	16.00	GX15/2	15	2A 4	26.00
	6	5A 6	28.00	GX60/2C	60	2A 2	28.00
ATB200	15+15	2A 1	16.00	GX15/5B	15	5A 1	35.00
ICL035	10	2A 1	14.00	GX033	12	1A 1	
ASA500	6	5A 2	28.00	ELEC/ASSO			
ASA1000	5	10A 12	44.00	10/0017	12	1A 2	
ASA20018	16-24	2A 1	18.00	GOULD 110			
ASA5006	3-8	5A 2	26.00	MG5	5	60A 27	95.00
QA2	15	0.1A 217	12.00	MG24	24	8A 44	41.00
OA5	12	1A 3	14.00	ADVANCE			
IC200	5	2A 4	16.00	PMA35	15	5A 16	32.00
ED500	12	5A 1	24.00	PMA34	30	10A	70.00
SOL20/5	5	20A 1	80.00	PMA17	7	3A 10	24.00
				PMA46	50	1A 32	28.00
LAMBDA							
LMCC28	30	3A 1	22.00	COUTANT			
LOTX5152	12	0.5A 1	15.00	KSG500	6	5A 1	27.00
LJ51150V	5	20A 1	42.00	ASA1000	5	10A 59	44.00
LOSYS	5	6A 2	28.00	QA2		1A 4	
LXSA5	5	4A 16	22.00	QA3	+/-12-15	2.5A 11	18.00
LM219263	22-32	1A 1		ESM3	12-24	3A 4	21.00
LM219v	22-32	1.2A 1	24.00	EEM57	12-24	7A 1	36.00
FARNELL							
15/25	15	2A 56	18.00	ESM15	12-24	15A 12	49.00
15/25	6	15A 1	62.00	IC200	5	0.3A 4	16.00
15/25	28	10A 2	52.00	LXSCC50V	5	16A 11	60.00
A15	12-17	0.1A 8	12.00	LMCC20	20	5A 1	43.00
15/25	15	2A 19	18.00	LAMBDA			
30/15	20	1A 26	15.00	LXSC12R	12	6.5A 3	44.00
A15		25	15.00	LCSC24	24	3.6A 19	26.00
APTTSU	20	3A 2	24.00	LMD20	20	7.5A 2	36.00
73SC	5	3A 211	15.00	LXDD152R	7.5	5A 3	43.00
SSB MH	40	2A 1		LXDD152R	12-15	6.2A 9	48.00
VOLSTAT	9-5	3.5A 2	21.00	LXB12R	12	3.8A 1	28.00
ITT							
MR20AS51	5	20A 4	45.00	LXSD15R	15	14A 1	60.00
MR5AS51	5	5A 1	30.00	LMMCC5	5	10A 1	48.00
MQ10AS15	15	10A 2	48.00	LXSA50VR	5	4A 14	27.00
MQ3BS301	30	3A 2	20.00	FARNELL			
MR10AS4	4-5	10A 2	44.00	15/25	15	2A 3	18.00
MQ5AS151	15	5A 2	24.00	5D15002T	5	150A 1	14.00
PC250A15	+/-12-15	2.5A 1	15.00	NCR/31505059	4	15A 1	38.00
DIGIVUE		2		GOULD/MG5	5	40A 47	80.00
AE00101	24	3.5A 5	64.00	ACO/SE50	5	100A 1	8.00
BRANDENBURG							
374		20	30.00	ITT/PM65A151	15	65A 12	8.00
375		2	30.00	APT13334	+20v	5A 1	35.00
376		4	30.00	BRANDENBURG			
GOULD							
MG24	24	15A 20	48.00	374	117	45	30.00
WELWYN STRAIN GAUGE.							
(Precision Micro-Measurements). Romulus Michem type MA-09-500B4-350. Our price £1.25 ea. List price £3.85. Large quantities available.							

Also
Large stocks of relays, ribbon, multicore cables, S.A.E. or phone for lists and prices.

D TO A CONVERTERS 15MHz, 8 BIT

By Micro Consultants Ltd, 50Ω cable drive op. Linearity 0.25%, max. 0.125% typ. Settling time; 2V step 70nS typ. 2MV step 50nS colour television transmission standard. Diff. gain 0.5% diff phase shift 0.5% types rad 802 and MC2208/8. Unused. Ex-maker's pack.

SPECIAL OFFER PRICE £10.00

TRANSFORMERS

3-0-3V 100mA	£1.06
5-0-5V 400mA	£1.25
6-0-6V 100mA	£1.14
6-0-6V 250mA	£1.16
0/6-0/6 280mA	£2.00
8-0-8V 400mA	£1.25
9-0-9V 75mA	£1.14
9-0-9V 3A	£3.00
11V 2A, 22V 1A	£2.00
12-0-12 50mA	£1.18
12-0-12V 100mA	£1.48
12V 130mA	£0.80
12-0-12V 250mA	£1.94
12V 1A5	£1.25
13V+6.5V Sec 2 Amp	£2.00
0-12-0-12 96VA	£8.00
15V 100mA	£1.00
0/12-0/12 500+500mA	£2.96
9-0-9V 1 Amp	£2.64
12-0-12V 1 Amp	£3.36
15-0-15V 1 Amp	£3.62
15V 100mA	£1.00
17V 300mA	£1.50
30,24,20,15,12,2 Amp	£4.84
6.3V 1.5 Amp	£2.64
6-0-6V 1.5 Amp	£3.20
20-0-20 400mA	£1.80
22-0-22 50mA	£1.00
24V 100mA	£1.00
24V 250mA	£1.50
25V+6.2V Sec 1.6 Amp	£1.90
30,24,20,15,12,2 Amp	£7.96
9-0-9 2 Amp	£4.70
12V 2 Amp	£4.84
20-0-20V 2 Amp	£6.98
30-0-30V 2 Amp	£7.96
30V 250mA	£1.50
30-25-0-25-30 1A6	£6.00
0-2-4-6-8-10 5A	£6.00

☆ ☆ ☆ ☆ ☆ ☆ ☆

VIDEO GAME BOARD FIELD GOAL VIDEO GAME

by Taito a top quality board, complete with 6800 CPU system system with 2715 EPROMS with circuit diagram plus all connections for either colour or Black & White monitors (TV Sets). Price £20.00 + VAT £3, P&P £2.55

POWER SUPPLY KIT
to suit + circuit diagram.
Price: £15.00
+ VAT £2.25, P&P £3.45

2x22 Way Gold Plated Double Sided D.156" edge Connectors
to suit Video Boards.
Price: £1.60 per pair.
+ VAT 24p P&P included
The Complete Kit £46.00 inc.
Full Details on Application. ☆

ALUMINIUM BOXES

AB7 5.25x2.50x1.50in. (133.4x63.5x38.1mm)	£0.96
AB8 4x4x1.5in. (101.6x101.6x38.1mm)	£0.96
AB9 4x2.25x1.5in. (101.6x57.2x38.1mm)	£0.96
AB10 4x5.25x1.5in. (101.6x133.4x38.1mm)	£1.12
AB11 4x2.50x2in. (101.6x63.5x50.8mm)	£0.96
AB12 3x2x1in. (76.2x50.8x25.4mm)	£0.70
AB13 5x4x2in. (152.4x101.6x50.8mm)	£1.38
AB14 7x5x2in. (177.8x127.0x50.8mm)	£1.64
AB15 8x6x3in. (203.2x152.4x76.2mm)	£1.98
AB16 10x7x3in. (254.0x177.8x76.2mm)	£2.70
AB17 10x4.50x3in. (254.0x114.3x76.2mm)	£2.28
AB18 12x5x3in. (304.8x127.0x76.2mm)	£2.52
AB19 12x8x3in. (304.8x203.2x76.2mm)	£3.04

BLUE REXINE. COVERED ALUMINIUM BOXES

RB1 6x4.50x2.5in. (152.4x114.3x63.50mm)	£1.96
RB2 8x5x3in. (703.2x127.0x76.2mm)	£2.52
RB3 9x5x3.50in. (228.6x127.0x88.9mm)	£2.72
RB4 11x6x4in. (279.4x152.4x101.5mm)	£3.14
RB5 11x7.50x4.50in. (279.4x190.5x114.3mm)	£3.98

Switchcraft Cannon Connectors 3-pin plug. Free hanging £1.20

A3F 3-pin socket. Free hanging with lock. £1.32

D3F 3-pin Socket. Female chassis mounting with lock £1.60

D3M 3-pin Socket. Male chassis mounting £1.10

Switchcraft XLR Connectors always in stock. Discounts on quantity.

BLACK PLASTIC BOXES

75x50x25mm	£0.65
80x60x40mm	£0.92
90x70x40mm	£0.99
115x75x30mm	£0.90
110x90x45mm	£1.18
170x100x50mm	£1.65
200x120x80mm	£3.55

FILTERS

3 Phase 20 AM Filters 433V 50/60Hz Phase to Phase 250V AC 50/60Hz Phase to Neutral mfr. by Corcom Chicago II., USA., £15 each.
Single Phase Filter 30 Amps 125V 60Hz by Potter £5.00
Sprague Filter 2 x 30 Amp 250V AC 60Hz £10.00
Erie Mains Filters 3 and 5 Amp 250V AC 50Hz £4.00
All the above mentioned Filters are brand new. Carriage extra.

SPECIAL OFFER! 0.1% TOL
resistors. The following values available. 2K, 3K, 10K, 30K, 1 Mega ohms. Welwyn or Filmet. Price 30p each.

CERMET PRESETS 15p each

10A 250V AC ILLUMINATED ROCKER SWITCH
Red, DP ST 26x30mm rectangular snap-in type. £0.75
16A 250V AC ILLUMINATED ROCKER SWITCH
(Amber). 14x30mm rectangular snap-in type. SPST £0.30
LICON ILLUMINATED SWITCHES
01-800 Rectangular snap-in series
2PCO Latching £1.50
2PCO Momentary £1.50
Indicator only £0.50
Lenses available in red or white only.

MAIL ORDER: Gds + 15% VAT, plus VAT inclusive Ad M/pkg/post:
1/4kg 1.30 4kg 3.90
1/2kg 1.70 5kg 4.20
3/4kg 2.20 6kg 4.40
1kg 2.55 6-10kg 5.00
2kg 3.00 Over 10kg: Quote
3kg 3.45

This advertisement is mainly of our excess stockholding. We also have excellent stocks of semiconductors, hardware, cables etc. etc. Four further details send for our lists and retail price catalogue, phone or visit our shop. All prices are exclusive of VAT (and P&P) Minimum Mail Order £5.00 + P&P + VAT. Government departments, schools, colleges, trade and export welcome.

WW - 072 FOR FURTHER DETAILS

Pye Europa MF5FM high-band sets, complete but less mike and cradle. **£90 each plus £2 p.p. plus VAT.**
 Pye M294 high-band FM sets, complete but less mike, speaker and cradle. **£150 each plus £2 p.p. plus VAT.**
 Pye Reporter MF6 AM high-band sets, complete but less speaker and cradle. **£120 each plus £2 p.p. plus VAT.**
 Pye Olympic M201 AM high-band sets, complete but less mike, speaker and cradle. **£90 each plus £2 p.p. plus VAT.**
 Pye Westminster W15 FM G band 42-54 MHz sets, unused and like new, but less mike, speaker and cradle. **£85 each plus £2 p.p. plus VAT.**
 Pye Westminster W15 AMD mid-band multi-channel sets, no mikes, speakers or cradles. **£45 each plus £2 p.p. plus VAT.**
 Pye Westminster W15 AMD mid-band crystallised and converted to 129.9 MHz, 130.1 MHz, 130.4 MHz. Very good condition. **£120 each plus £2 p.p. plus VAT.**
 Pye Westminster W15 AMD high-band and low-band sets available. Sets complete but less mikes, speakers and cradles. **£70 each plus £2 p.p. plus VAT.**
 Pye Westminster W30 AM low-band sets only, no control gear. Sets complete and in good condition. **£45 each plus £2 p.p. plus VAT.**
 Pye base station F30 AM, low band and high band available, remote and local control. Prices from **£220 plus VAT.**
 Pye base station F401 high-band AM, local control, fully solid state, complete but less mike. **£275 each plus £15 p.p. plus VAT.**
 Pye base station receiver R402 high-band FM 148-174MHz, single channel, 12.5 KHz channel spacing. **£95 each plus £5 p.p. plus VAT.**
 Pye base station F9U, remotely controlled, 5 Watt output, UHF (440-470 MHz), single channel. **£90 each plus £5 p.p. plus VAT.**
 Pye base station F412 UHF (440-470 MHz), 25KHz channel spacing, single channel, local control. **£250 each plus £15 p.p. plus VAT.**
 Good second-hand Pye radiotelephones WANTED for cash.
 Pye base station receiver F27 AM, crystallised on 116.46 MHz, can be recrystallised on air band. Unused condition. **£15 each plus £5 p.p. plus VAT.**

Pye AC200 mains power unit for Olympic or Reporter, automatic standby power facility with trickle charging and built-in quartz digital clock. **£95 each plus £5 p.p. plus VAT.**
 Pye AC power supply unit AC25PU, specially designed for use with the Europa series mobiles, power output 13.2 volt 5 amp. New condition. **£45 each plus £5 p.p. plus VAT.**
 Pye PC1 radiotelephone controller, good condition, two only at **£50 each plus £2 p.p. plus VAT.**
 Pye Tulip microphone as used on most base stations and PC1, 2400 ohm with ptt switch. **£15 plus £1 p.p. plus VAT.**
 Pye PF1 UHF FM Pocketone receiver, 440-470 MHz, single channel, int. speaker and aerial. Requires 9-volt battery. With service manual. **£8 each plus £1 p.p. plus VAT.**
 Pye PF2 Pocketone 70, all types available, AM, FM, UHF, completed with battery, mike and aerial. **£85 each plus £2 p.p. plus VAT.**
 Pye PF1 Pocketone battery-charger type BC14, 12 way with meter. **£10 each plus £1 p.p. plus VAT.**
 Pye PFS012 UHF handhelds, crystallised on 466 MHz, complete with n-cads. **£140 each plus £2 p.p. plus VAT.**
 Pye Vanguard/Cambridge control leads, 18 way, with plugs and sockets, unused. **£4 each plus £1 p.p. plus VAT.**

MAINS TRANSFORMERS

0-240V input tapped 5000V 0.125 amp. **£20 plus £8 p.p. plus VAT.**
 0.240V input 50V 20 amp. **£25 plus £8 p.p. plus VAT.**
 0-240V input tapped 14KV 2mA. **£20 plus £8 p.p. plus VAT.**
 0-240V input tapped 700V 1.2 amp. **£20 plus £8 p.p. plus VAT.**
 Mains isolating transformer, 500VA 240V input, 240V C.T. output, housed in metal box. **£15 each plus £6 p.p. plus VAT.**
 Mains isolating transformer, 240V tapped input, 240V 3 amp, plus 12V 0.5 amp output. **£20 each plus £8 p.p. plus VAT.**
 Advance Volstat transformers, type CVN200/5, input 24 or 28V DC via inverter, output 220 or 240V RMS 150 watt, 50Hz. **£10 each plus £4 p.p. plus VAT.**
 Variacs 2 amp, 5 amp, 8 amp, 15 amp, 25 amp, used but good condition. From **£10 each.**

Marconi AM/FM signal generator, type TF995A/3/S (CT402), 1.5-220 MHz, good condition with copy of service manual. **£95 each plus £15 p.p. plus VAT.**
 Avo valve tester, type CT160 (22 valve bases) with copy of manual. **£20 each plus £6 p.p. plus VAT.**
 Scopex oscilloscope, type 4D10, 10 MHz dual beam, used but good condition. **£160 each plus £10 p.p. plus VAT.**
 Rhode & Schwarz UHF test receiver BN1525, 280-940 MHz. **£50 each plus £15 p.p. plus VAT.**
 Marconi universal bridge, type FT868, 10pf-100mf. **£50 plus £10 p.p. plus VAT.**
 Servomex AC voltage stabiliser, type AC2, 240V @ 9 amp. **£45 each plus £15 p.p. plus VAT.**
 Servomex AC voltage stabiliser, type AC7, 240V @ 20 amp. **£75 each plus £15 p.p. plus VAT.**
 Samwell & Hutton T.V. Wobulator, type 78M, 16-230 MHz. **£35 each plus £15 p.p. plus VAT.**
 Marconi RF power meter, type TF1152/1, 25 watt, 50 ohm. **£30 plus £5 p.p. plus VAT.**
 Meguro signal generator, type MSG-230E, 16 KHz-50 MHz. **£130 plus £10 p.p. plus VAT.**
 Solartron oscilloscope, type CD1740, 50 MHz, fitted with camera mount, good condition. **£285 plus £10 p.p. plus VAT.**
 Computer-grade electrolytic capacitors, screw terminals, 25,000mfd., 33 volts, brand new. **£1 each plus 50p p.p. plus VAT.**
 60 amp alternator and general noise filters for use in vehicles. **£1 each plus 50p p.p. plus VAT.**
 Modern telephones, type 746, with dials, colour grey, used but good condition. **£8 plus £1 p.p. plus VAT.**
 Cigar lighter plug with lead. **£1 each plus 30p p.p. plus VAT.**
 IC test clips, 28-way and 40-way, gold plated. **£2 each plus 30p p.p. plus VAT.**
 Equipment wire, size 7/0.2mm, colour yellow, 500-metre reels. **£4 plus £1 p.p. plus VAT.**
 Z80-CPU, Z80-P10, Z80-CTC. **£1.85 each plus 30p p.p. plus VAT.**
 Scotch video tape, 1" x 10" (25.40mm x 910mm), brand new. **£5 each plus £2 p.p. plus VAT.**
 Power units, 70 volt @ 8 amp, 20 volt @ 3 amp. Brand new but no details. **£20 each plus £8 p.p. plus VAT.**
 Beryllium block mounts for CCS1 valves, etc. **£10 each plus £1 p.p. plus VAT.**

B. BAMBER ELECTRONICS

GOVERNMENT AND MANUFACTURERS' SURPLUS

5 STATION ROAD
 LITTLEPORT CAMBS CB6 1QE
 Telephone: Ely (0353) 860185

ELECTRONIC COMPONENTS
 TELECOMMUNICATION EQUIPMENT
 TEST GEAR



WW - 073 FOR FURTHER DETAILS

MANUFACTURERS & DISTRIBUTORS



MATCHED PAIR DYNAMIC/STEREO MICROPHONES AND STANDS wired into one 3 pin 180° Din plug, approx. 2m separation, 200ohm. **£20 for 10 + VAT, £90 for 50 + VAT, £162 for 100 + VAT, £730 for 500 + VAT, £1,400 for 1,000 + VAT.** Sample sent for **£2.50 + 50p P&P** (£3.45 inc. VAT).

MONO DYNAMIC MICROPHONE AND STAND. 3.5mm J plug fitted to approx. 1m lead. **£7 for 10 + VAT, £32 for 50 + VAT, £60 for 100 + VAT, £270 for 500 + VAT, £500 for 1,000 + VAT.** Sample sent for **£1 + 50p P&P** (£1.28 inc. VAT).

CAR STEREO SHELF-MOUNTING SPEAKERS. Moulded black plastic cabinet for vertical or horizontal mounting. Imp 8ohm power handling, 5watt (nom.), 8watt (max.). Dims. 152mm x 222mm x 85. **£25 for 10 pr. + VAT, £115 for 50 pr. + VAT, £210 for 100 pr. + VAT, £390 for 200 pr. + VAT, £900 for 500 pr. + VAT.** Sample pair sent for **£3 + 75p P&P** (£4.32 inc. VAT).

MINIATURE ROUND SPEAKER. 2 1/4" 8ohm 1/2watt. **£35 for 100 + VAT, £165 for 500 + VAT, £315 for 1,000 + VAT, £600 for 2,000 + VAT.** Sample 10 sent for **£4 + £1 P&P** (£5.75 inc. VAT).

150WATT HINCHLEY TRANSFORMERS. 220/240V.A.C. input, 30-0-30V output + 14V. Tap size 96mm x 90mm, weight approx. 2.7kg. **£75 for 10 + VAT, £350 for 50 + VAT, £620 for 100 + VAT, £2,800 for 500 + VAT.** Sample sent for **£9 + £2 P&P** (£12.65 inc. VAT).

6V.A. MINIATURE TRANSFORMER. 240V.A.C. input, 12-0-12V output. P.C. mounting + internal thermal overload protection. **£2.50 for 10 + VAT, £115 for 50 + VAT, £210 for 100 + VAT, £950 for 500 + VAT.** Sample sent for **£3 + 75p P&P** (£4.31 inc. VAT).

JUST IN. P.C.B. Mounting Transformer - split bobbin - 6VA, 240V.A.C. input, 12-0-12V output. Size 43mm x 36mm x 32mm approx. **£12.50 for 10 + VAT, £58 for 50 + VAT, £105 for 100 + VAT, £480 for 500 + VAT, £920 for 1,000 + VAT, £4,150 for 5,000 + VAT, £7,500 for 10,000 + VAT.** Sample sent for **£1.50 + 50p P&P** (£2.30 inc. VAT).

FRIEDLAND UNDERDOME BELL. 10" dia., 200/250V.A.C., 0.04amp. **£45 for 5 + VAT, £85 for 10 + VAT, £155 for 20 + VAT, £280 for 40 + VAT.** Sample sent for **£10 + £2 P&P** (£13.80 inc. VAT).

Terms C.W.O. Please add 5% to all orders for carriage plus 15% VAT. Export enquiries welcome. We find it impossible to advertise all our stock. Please telephone or write for further details. Personal callers always welcome.

ELECTRONIC EQUIPMENT Co.

SPRINGFIELD HOUSE
 TYSSSEN ST., LONDON E8
 TEL. 01-249 8217
 TELEX 0863888 EECO.G

WW - 074 FOR FURTHER DETAILS

<p>D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts. Sealed base. Ideal for programming. 6-position at less than half manufacturer's price. ONLY 75p Will fit into 14-pin dil socket Ten at 65p ea. per 100 55p ea.</p>	<p>HONEYWELL PROXIMITY DETECTOR integral amplifier, 8v D.C. £3.50 ea. PHOTO CONDUCTIVE CELL. £1.25. High-power CdS cell, 600MW, for control circuits. Resistance 800 ohm to 4k. Max. volts 240. Size 1 1/2 x 1/2in. RIBBON MICROPHONE with pre-amp. on chassis. £1.75.</p>	<p>MULLARD MODULES LP1171 AM, FM LP1179 AM, FM "F. Strip Front end Pair £7.75 Complete with Data LP1186 LP1157 varicap Med. & Long Tuner £5.00 CRYSTALS COLOUR TV 4 433619 mcs £1.25 Miniature type sealed</p>	<p>ULTRA SONIC TRANSDUCERS 40KC/S. Complete on 18in. Screened cable. £1.75 each, pairs £2.95 ULTRA SONIC TRANSMITTER. Complete unit (uncased requires 1.5V). £3.25. FOSTER DYNAMIC MICROPHONES. 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.</p>
<p>U.H.F. MODULATORS Latest type, adjustable, ideal for computers with data circuit. Size 3 x 2 1/2 x 1 inch. In screened case. Only £3.50</p>	<p>LM380 Amplifier 85p LM318 Hi-Slew Op Amp £1.50 LM323K, 5v 3-amp, reg. £3.50 LM310N Volt. Follower. Amp. £1.20 LM311H High Perf. Volt. Comparator £1.00 LM384N, 5-watt Amp £1.20 LM339N Dual Comp. 50p 7905 Reg. -5v 75p</p>	<p>MINIATURE HIGH-QUALITY FANS "Whisper Model" by Roton. Low-power consumption (less than 10 watts). Silent running. 115v (two in series for 230v.). 50/60Hz. Size 4 1/2 x 4 1/2 x 1 1/2in. ONLY £6.50 EACH incl. VAT. BRAND NEW 60% less than manufacturer's price</p>	<p>STEREO CASSETTE MECHANISMS 6 or 12 volt. Complete with Heads + Erase and Solenoid. Brand new. £5.50 ea.</p>
<p>MONSANTO Half-inch + 1 Display High Intensity £1 each set of 4 £3.50 Common anode 14 Pin Dil Package</p>	<p>STEREO CASSETTE TAPE HEADS. Quality replacement for most recorders with mounting plate Record/Replay £2.80 MARRIOTT TAPE HEADS Quarter track Type XRPS18 Record/Replay (each) £2.00 XRPS36 Record/Replay (each) £3.00 XES11 Erase (each) £1.00</p>	<p>HEWLETT-PACKARD DISPLAYS 5082-7650 HIGH EFFICIENCY AND VERY BRIGHT. Only £1.00 each Set of 6 for £5 Half-inch red common anode will replace DL70/14-pin Dil.</p>	<p>EX-MOTOROLA 5 + 5-WATT CAR STEREO AMPLIFIERS Complete and tested units Medium and Long Wave. Supplied as two built units (5 x 2 x 2in.) with circuit and data. Only £5 pair. Includes pre-amp</p>
<p>BRIDGE RECTIFIER 800 PIV 35 amps 1 1/2 x 1 1/2 x 1/2in. £3.50</p>	<p>NATIONAL P 8090A Chips £2.95 8216 £1.75 INTEGRAL DIODES Full spec. but no polarity band. Per 1,000. £10 MINIATURE M.P.C. POTENTIOMETERS. Model M2 High quality. 5% tolerance, 2-watt, with lin. spindles. All values. 49 ohms 47k only 60p each per 10; 50p each per 100; 40p each</p>	<p>RECHARGEABLE BATTERIES VARTA 3.6 volts DEAC M/AH 225 £1.50 DRYFIT 6-volt, 4.5 amp. £7.50</p>	<p>"CHERRY" ADD-ON KEYPAD A compact 12-button keypad suitable for use with Keyboard extend its functions plus four extra keys. Supplied brand new LIST PRICE £22.00 OUR PRICE ONLY £7.50 incl. V.A.T.</p>

QUANTITY DISCOUNTS on ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW (unless otherwise stated). DELIVERY from stock - Add post 35p per order.

Henry's


EXPORT enquiries invited

TELEX 262284
 Transonics
 Mono 1400

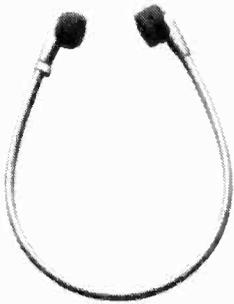01-723 1008/9

Callers to: 404 EDGWARE ROAD, LONDON W2 1ED
 ALL MAIL ORDERS/EXPORT ENQUIRIES 11/12 PADDINGTON GREEN, LONDON, W2

DANAVOX ARE ALWAYS COMING UP WITH SOUND IDEAS.



STETOCLIP
JUNIOR 60
HEADSET




STETOCLIP
LIGHTWEIGHT
HEADSET




SENIOR
STETOCLIP
HEADSET



STETOCLIP
GEMINI
HEADSET

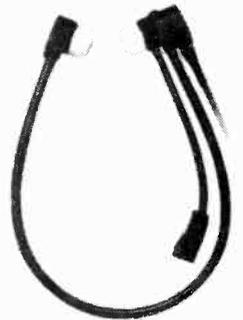

STETOMIKE
HMT 808

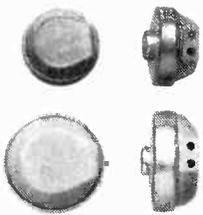


STANDARD &
SUB-MINOR
EARPHONES




PLASTIC
EARHANGERS




DANAMIC FIDELITY
EARSET

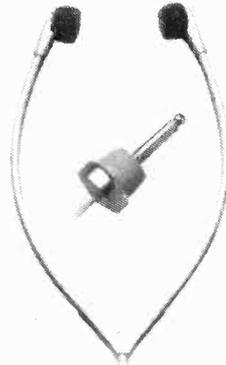

STETOTUBE
HEADSET &
SOUND PLUG

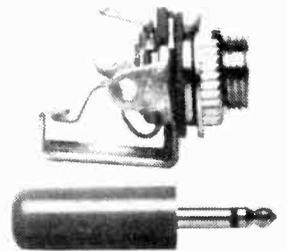

2,5mm 3,5mm
JACK PLUGS &
SOCKETS

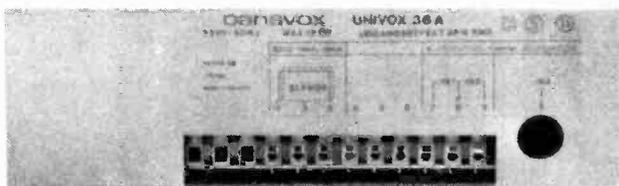

INDUCTIVE LOOP AMPLIFIER TYPE 36A



FIELD STRENGTH
TESTER FSI



DANASOUND
HEADSET



SUBMINIATURE
SWITCHES

The Danavox policy has always been one of constant improvement.

Our refinement, development and research has enabled us to offer an advanced range of components and accessories for dictation machines, tape recorders, tele-communications, hearing aids and electro-acoustic equipment.

All our products are built with care and precision.

And all carry the Danavox guarantee.

For more information about any Danavox product, contact John Carter.

Danavox

DANAVOX (Gt. Britain) Ltd.,
1 Cheyne Walk, Northampton. NN1 5PT
Tel: (0604) 36351 Telex 312395

WW - 070 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS
Now available with
3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC
OUTPUT 2: 0-70v, 10A AC
OUTPUT 3: 0-250v, 4A AC

ALL
Continuously
Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW - 028 FOR FURTHER DETAILS

reprints

If you are interested in a particular article / special Feature or advertisement published in this issue of

WIRELESS WORLD

why not take advantage of our reprint service.

Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)

For further details contact
Michael Rogers, IPC Electrical-Electronic Press Ltd. Phone 01-661 3036 or simply complete and return the form below.

To Michael Rogers, Reprints Department
Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS

I am interested in _____ copies of the article / advertisement headed _____ featured in

WIRELESS WORLD

on page(s) _____ in the issue dated _____

Please send me full details of your reprint service by return of post.

Name _____

Company _____

Address _____

Tel. No. _____

BARCLAYCARD
VISA

Master Charge

PM COMPONENTS LTD

VALVE & COMPONENTS SPECIALISTS

INTEGRATED CIRCUITS

AN124	2.50
AN2140	2.50
AN240P	2.90
AN612	2.15
AN7150	2.95
BA521	3.35
ETT6016	1.75
HA1366W	1.96
LA1230	1.15
LA4031P	2.70
LA4102	2.95
LA4400	4.15
LA4422	2.50
LC7120	3.25
LC7130	3.50
LC7131	5.50
LC7137	5.50
LM324N	0.45
LM380N	0.95
LM383T	2.95
LM390N	1.95
M51513L	2.30
M51515L	2.95
MB3712	2.00
MC1307P	1.00
MC1310P	1.50
MC1327	0.95
MC1327Q	0.95
MC1330P	0.95
MC1349P	1.20
MC1350P	0.75
MC1351P	1.50
MC1352P	1.25
MC1357	2.35
MC1358	1.58
MC1495	3.00
MC1496	1.25

MC14011BCP	0.32
MC1723	0.50
MC3357	2.25
ML231B	1.75
ML232B	1.75
ML237B	1.95
ML238B	4.20
ML920	4.12
M5M5807	6.75
PLLO2A	5.75
SAA1025	7.25
SAA5000A	3.05
SAA5010	0.35
SAS560S	1.75
SAS570S	1.75
SAS580	2.85
SL901B	2.05
SL917B	6.65
SL1310	1.80
SL1327	1.10
SL1327Q	1.10
SN76033N	1.95
SN76013N	1.95
SN76013ND	1.95
SN76023N	1.65
SN76033N	1.65
SN76101N	0.85
SN76131N	1.30
SN76226DN	1.55
SN76227N	1.05
SN76532N	1.40
SN76533N	1.65
SN76544N	1.65
SN76650N	1.15
SN76660N	0.80

SN76666N	0.70
TA7061AP	3.95
TA7106P	1.90
TA7120P	1.65
TA7130P	1.50
TA7146	2.95
TA7203	2.95
TA7204P	2.15
TA7205AP	1.50
TA7222AP	1.80
TA7227P	4.25
TA7310P	1.80
TA7313AP	2.95
TA7611AP	2.95
TAAS70	0.25
TAA570	1.95
TAA661B	1.20
TAA700	1.70
TAA630S	3.50
TBA120B	0.95
TBA120S	0.70
TBA120SA	0.70
TBA120SQ	0.70
TBA120T	1.05
TBA120U	1.00
TBA231	1.25
TBA395	1.50
TBA396	0.75
TBA440N	2.55
TBA480Q	1.25
TBA510	2.50
TBA5100	2.50
TBA520	1.10
TBA520Q	1.70
TBA530	1.10
TBA530C	1.10
TBA540	1.25
TBA540Q	1.35
TBA550Q	1.45
TBA560C	1.65
TBA560CQ	1.45
TBA570	1.00

TBA641A12	2.50
TBA641BX1	3.00
TBA641-B11	3.00
TBA651	1.75
TBA720A	2.45
TBA750Q	2.65
TBA800	0.89
TBA810AS	1.36
TBA820Q	1.45
TBA890	2.50
TBA920	1.65
TBA920Q	1.65
TBA950	2.35
TBA950/2X	2.35
TBA990	1.49
TBA990Q	1.49
TBA1441	2.15
TCA270	1.10
TCA270SQ	1.10
TC A650	2.50
TC A900	2.15
TCA830S	1.40
TCA940	1.65
TDA440	2.20
TDA1004A	2.20
TDA1006A	2.50
TDA1010	2.15
TDA1037	2.50
TDA1037	1.95
TDA1170	1.95
TDA1170S	1.95
TDA1190	2.15
TDA1270Q	3.95
TDA1327	1.70
TDA1352B	1.43
TDA1412	0.85
TDA2002	1.95
TDA2020	2.45
TDA2030	2.80

TDA2522	1.95
TDA2523	1.95
TDA2524	1.95
TDA2530	1.95
TDA2532	1.95
TDA2540	1.25
TDA2541	2.15
TDA2560	2.15
TDA2581	2.25
TDA2590	2.95
TDA2591	2.95
TDA2593	2.95
TDA2600	3.50
TDA2610	2.50
TDA2611A	1.95
TDA2640	2.90
TDA2690	1.35
TDA3560	3.95
TDA3950	1.95
UPC566H	2.95
UPC575C2	2.75
UPC1001H	2.50
UPC1025H	2.50
UPC1028H	1.95
UPC1156H	2.75
UPC1167C2	1.15
UPC1181H	1.25
UPC1182H	2.95
UPC1185H	3.95
UPC1350C	2.95
UPC2002H	1.95
ZTK33B	0.50
556	0.95
566	0.42
723	0.50
747	0.35
747	0.50
748	0.35
4042	0.50
7805	0.80

SEMICONDUCTORS

AAV12	0.25
AC126	0.22
AC127	0.20
AC128	0.20
AC128K	0.32
AC141	0.28
AC141K	0.34
AC142K	0.30
AC176	0.22
AC176K	0.31
AC187	0.25
AC187K	0.28
AC188	0.25
AC188K	0.37
AD142	0.90
AD143	0.82
AD149	0.90
AD161	0.39
AD161/2	0.90
AF115	0.75
AF124	0.34
AF125	0.35
AF126	0.32
AF127	0.32
AF139	0.40
AF150	0.42
AF239	0.42
AU106	2.00
AU107	1.75
AU110	2.00
AU113	2.95
BC107	0.10
BC107A	0.11
BC107B	0.11
BC108	0.10
BC108A	0.11
BC108B	0.12
BC109	0.10
BC109B	0.12
BC109C	0.12
BC114	0.11
BC116A	0.15
BC117	0.19
BC119	0.24
BC125	0.25
BC140	0.31
BC141	0.25
BC142	0.21
BC143	0.24
BC147	0.09
BC147B	0.09
BC148A	0.09
BC148B	0.09
BC149	0.09
BC157	0.12
BC158	0.09
BC159	0.09
BC160	0.28
BC161	0.28
BC170B	0.15
BC171	0.09
BC171A	0.10
BC171B	0.10
BC172	0.10
BC172B	0.10
BC172C	0.10

BC173B	0.10
BC174A	0.09
BC177	0.15
BC178	0.15
BC182	0.10
BC182LB	0.10
BC183	0.10
BC183L	0.09
BC184LB	0.09
BC204	0.10
BC207B	0.13
BC208B	0.13
BC212	0.09
BC212L	0.09
BC212LA	0.09
BC213	0.09
BC213L	0.09
BC214	0.09
BC214C	0.09
BC214L	0.09
BC237	0.10
BC237A	0.09
BC237B	0.09
BC238	0.09
BC239	0.12
BC251A	0.12
BC252A	0.15
BC258	0.09
BC258A	0.39
BC284	0.30
BC300	0.30
BC301	0.30
BC303	0.28
BC307	0.09
BC307A	0.09
BC307B	0.09
BC327	0.10
BC328	0.10
BC337	0.10
BC338	0.09
BC347A	0.13
BC461	0.35
BC478	0.20
BC527	0.20
BC547	0.10
BC548	0.10
BC549A	0.08
BC550	0.08
BC557	0.08
BC557A	0.08
BC557B	0.08
BC558	0.10
BCY33A	1.60
BD115	0.30
BD116	0.60
BD124P	0.59
BD131	0.32
BD132	0.35
BD133	0.40
BD135	0.30
BD136	0.30
BD137	0.32
BD138	0.30
BD139	0.32
BD140	0.30
BD144	1.10

BD159	0.85
BD166	0.85
BD173	0.72
BD182	0.70
BD201	0.83
BD202	0.85
BD203	0.78
BD204	0.70
BD222	0.48
BD223	0.48
BD225	0.48
BD232	0.35
BD233	0.35
BD234	0.35
BD246	0.85
BD237	0.40
BD238	0.40
BD241	0.40
BD242	0.50
BD246	0.85
BD376	0.32
BD410	0.55
BD434	0.55
BD437	0.50
BD438	0.60
BD530	0.50
BD508	0.40
BD520	0.65
BD538	0.75
BD597	0.85
BD597	1.10
BD639	1.10
BD707	0.80
BDX32	1.50
BF115	0.35
BF127	0.24
BF154	0.12
BF158	0.27
BF160	0.27
BF167	0.24
BF173	0.22
BF177	0.38
BF178	0.28
BF179	0.28
BF180	0.29
BF181	0.29
BF182	0.29
BF183	0.29
BF184	0.28
BF185	0.28
BF194	0.11
BF195	0.11
BF196	0.11
BF197	0.11
BF198	0.11
BF199	0.14
BF200	0.40
BF241	0.15
BF245	0.30
BF246	0.28
BF256/LC	0.34
BF257	0.28
BF258	0.28
BF259	0.28
BF271	0.28
BF273	0.13
BF336	0.34
BF337	0.29
BF338	0.32
BF355	0.37

BF362	0.38
BF363	0.38
BF371	0.20
BF394	0.19
BF422	0.32
BF457	0.32
BF458	0.28
BF459	0.36
BF595	0.23
BF597	0.25
BF599	0.23
BF640	0.23
BF641	0.28
BF688	0.30
BF690	1.55
BF691	1.75
BF742	0.28
BF743	0.28
BF792	0.85
BFX29	0.30
BFX29	0.26
BFX85	0.32
BFX86	0.30
BFX88	0.25
BFY90	0.21
BFY91	0.21
BFY92	0.25
BFY92	0.77
TV106/2	1.50
BR100	0.26
BR101	0.30
BRC4443	0.85
BT106	1.21
BT108	1.22
BT116	1.20
BT119	1.85
BT120	1.65
BU105	1.22
BU108	0.69
BU124	1.25
BU125	1.25
BU126	1.60
BU204	1.55
BU205	1.30
BU208	1.52
BU208A	1.52

PHONE
0474 813225
3 LINES

P. M. COMPONENTS LTD
SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
966371
PM COMP



A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 18.50	EA79 1.95	EF183 0.65	G237 4.50	PCF87 0.40	QY5-500 115.00	UJ7 8.00	2B7 1.50	6BR8A 2.15	10C2 0.70	92AG 11.85
A1998 11.50	EA81 0.60	EF184 0.65	1A0 1.00	PCF80 1.25	115.00	UY41 3.50	2D21 0.95	6BS7 4.50	10D2 1.25	92AV 11.85
A2087 11.50	EABC80 0.68	EF731 1.80	HABC80 0.90	PCF201 1.35	QZ06-20 32.50	UY85 0.70	2D21W 2.50	6BS8 2.50	10F1 0.75	95A1 6.50
A2134 14.95	EAC91 2.50	EF732 1.80	HBC90 0.75	PCF800 0.40	R10 4.00	V339 3.50	2E26 7.95	6BW4 1.50	10G6 1.95	108C1 1.50
A2293 6.50	EAF42 1.20	EF800 11.00	HBC91 0.80	PCF801 1.35	R16 12.00	VP561 10.95	2J42 93.00	6BW6 5.35	10H14 2.50	150B2 3.95
A2426 17.50	EAF60 1.40	EF804S 9.85	HF93 0.75	PCF802 0.60	R17 1.50	VP228 2.50	2K25 24.95	6BW7 1.50	10I10 1.50	150C2 1.50
A2521 21.00	EB34 1.50	EF805S 9.85	HF94 0.60	PCF805 1.48	R18 2.50	VP4A 4.50	3A/147J 7.50	6BW8 4.00	10L12 0.65	155UG 25.00
A2599 37.50	EB41 3.00	EF806S 9.85	HK90 1.05	PCF808 1.25	R20 1.20	VP4B 2.50	3A2 3.95	6BX7GT 3.50	10L21 1.85	158BT 1.50
A2900 11.50	EB91 0.52	EF812 0.85	HL2 1.50	PCL200 1.10	RG1-125 4.95	VP41 2.50	3A3A 3.95	6BZ6 2.00	11E3 55.00	205F 12.00
A3042 24.00	EB93 2.50	EF1200 1.50	HL3 3.50	PCL82 0.80	RG1-240A 14.50	VP133 2.00	3A4 1.10	6BZ7 2.95	12A6E 0.85	257A 6.00
A3283 24.00	EB94 1.95	EH90 0.72	HL33/DD 3.50	PCL84 2.50	RG3-250A 25.00	VR7 1.50	3A5 0.95	6BZ8 0.95	12AG8 1.50	307 5.00
B5450 67.00	EB95 0.85	EL81 0.90	HL33/DD 3.50	PCL85 0.80	RG3-1250A 52.50	VR7/30 3.00	3A6 1.95	6C4 0.80	12AL5 1.00	329 5.00
ACP 4.00	EB99 0.75	EL82 0.58	HL32 0.95	PCL805 0.80	RK2K25 62.50	VR91 1.50	3A6 1.95	6C6 0.50	12AT6 0.59	388A 17.50
AC/TH 4.00	EB99 0.75	EL83 4.00	HL32 0.95	PCD50 3.50	RG4-1000 12.00	VR101 2.00	3A7 1.50	6C8 1.50	12AT7 0.85	408A 4.00
AC/VP2 4.00	EBF33 2.50	EL84 0.69	HL32 0.95	PCF808 1.00	RK-20A 12.00	VR150/30 1.50	3A8 1.20	6C9 1.50	12AT7WA 2.50	425A5 4.00
AH221 39.00	EBF80 0.50	EL85 4.50	HL33 Mullard 9.50	PCF809 1.00	RL 1.50	VR150/30 1.50	3A8 1.20	6C9 1.50	12AU6 1.50	431U 2.00
AH238 39.00	EBF83 0.50	EL86 0.86	KT33C 3.50	PCF809 1.00	RPL16 12.00	VR150/30 1.50	3A9 1.20	6C9 1.50	12AV6 0.80	705A 8.00
AL50 6.00	EBF85 0.95	EL87 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12AX4GT 1.00	708A 8.00
ARP12 0.70	EBF89 0.70	EL88 0.86	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12AX7 0.65	715A 6.00
ARP34 1.25	EBF93 0.95	EL89 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12AX7WA 2.50	715C 45.00
ARP35 2.00	EBL1 1.50	EL90 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12AY2 4.00	801A 2.00
AZ31 2.00	EBL21 2.00	EL91 6.00	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	803 14.95
BL5 2.00	EBL31 3.95	EL92 0.58	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	807 1.50
B15450 67.00	EBL31 3.95	EL93 0.70	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	810 55.00
BT5 49.50	EBL31 3.95	EL94 0.69	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	811A 12.95
BT19 32.50	EBL31 3.95	EL95 0.70	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	812 18.50
BT79 12.50	EBL31 3.95	EL96 0.86	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	813 USA 59.50
CIK 16.00	EBL31 3.95	EL97 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	814 115.00
C108 16.00	EBL31 3.95	EL98 0.86	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	815 3.95
C1108 16.00	EBL31 3.95	EL99 0.86	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	816 3.95
C1134 17.50	EBL31 3.95	EL100 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	817 3.95
C1148A 60.00	EBL31 3.95	EL101 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	818 3.95
C1149/1 89.00	EBL31 3.95	EL102 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	819 3.95
C134 32.00	EBL31 3.95	EL103 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	820 3.95
CL31 2.00	EBL31 3.95	EL104 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	821 3.95
CCA 2.60	EBL31 3.95	EL105 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	822 3.95
CL30 2.00	EBL31 3.95	EL106 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	823 3.95
CL33 2.00	EBL31 3.95	EL107 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	824 3.95
CMG25 9.00	EBL31 3.95	EL108 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	825 3.95
CV Nos Prices on request	EBL31 3.95	EL109 1.25	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	826 3.95
DE3 1.20	EBL31 3.95	EL110 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	827 3.95
DAF91 0.45	EBL31 3.95	EL111 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	828 3.95
DAF96 0.65	EBL31 3.95	EL112 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	829 3.95
DC70 1.75	EBL31 3.95	EL113 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	830 3.95
DCX4-1000 12.00	EBL31 3.95	EL114 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	831 3.95
DCX4-5000 25.00	EBL31 3.95	EL115 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	832 3.95
DET10 6.00	EBL31 3.95	EL116 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	833 3.95
DET22 22.00	EBL31 3.95	EL117 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	834 3.95
DET24 39.00	EBL31 3.95	EL118 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	835 3.95
DET25 28.00	EBL31 3.95	EL119 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	836 3.95
DF91 0.70	EBL31 3.95	EL120 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	837 3.95
DF92 0.60	EBL31 3.95	EL121 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	838 3.95
DF96 0.65	EBL31 3.95	EL122 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	839 3.95
DH63 1.20	EBL31 3.95	EL123 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	840 3.95
DH77 0.90	EBL31 3.95	EL124 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	841 3.95
DH79 0.56	EBL31 3.95	EL125 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	842 3.95
DH149 2.00	EBL31 3.95	EL126 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	843 3.95
DK91 0.90	EBL31 3.95	EL127 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	844 3.95
DK92 1.20	EBL31 3.95	EL128 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	845 3.95
DK96 2.50	EBL31 3.95	EL129 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	846 3.95
DL35 1.00	EBL31 3.95	EL130 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	847 3.95
DL63 1.00	EBL31 3.95	EL131 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	848 3.95
DL70 2.50	EBL31 3.95	EL132 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	849 3.95
DL73 2.50	EBL31 3.95	EL133 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	850 3.95
DL91 1.50	EBL31 3.95	EL134 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	851 3.95
DL92 0.60	EBL31 3.95	EL135 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	852 3.95
DL93 1.10	EBL31 3.95	EL136 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	853 3.95
DL96 2.50	EBL31 3.95	EL137 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	854 3.95
DL97 1.50	EBL31 3.95	EL138 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	855 3.95
DL98 1.50	EBL31 3.95	EL139 1.10	KT36 2.00	PCF809 1.00	RPY13 2.50	VR150/30 1.50	3A9 1.20	6C9 1.50	12B7A 1.75	856 3.95

A COMPETITION OPEN TO ALL WIRELESS WORLD READERS WITH £8000 IN CASH PRIZES

Design an Electronic Device to help the Disabled

Could you design a piece of equipment to help a disabled person? If so, you would — in addition to undertaking this worthy task — be eligible to win a substantial cash prize.

Our competition is open to individuals or groups resident in the UK. You register your entry using the form below, sending it to the Editor to arrive at his office not later than June 30th 1983. The designs themselves must be submitted to his office by 1st October 1983.

Entries, which will be judged by a group of eminent engineers and doctors, must consist of the following: - a statement of the design objectives; an overall description of the device; detailed circuit descriptions and diagrams; a model of the device or a model of a unique aspect of the design sufficient to demonstrate its feasibility.

The finalists will be invited to London to talk over their entries with the judges and be awarded their prizes. The prizes are:

1st prize £2,500 and the 4 runners up will be awarded prizes each of **£1,000**
2nd prize £1,500

To make sure you have the maximum time to undertake your design, return your entry form now!

"DESIGN AN ELECTRONIC DEVICE TO HELP THE DISABLED" LIST OF RULES

1. The competition is open to U.K. residents only.
2. Entrants can be individuals or groups.
3. All participants must register their interest in entering the competition on the form provided which must be returned to the Wireless World Editorial Department by the 30th June 1983.
4. All entrants agree to give Wireless World first serial publication rights to an article describing the entry.
5. All entrants indemnify Wireless World from any liability in respect of injury to people or damage to property arising from the use of the design.
6. All submitted designs must be the original work of the entrant or entrants and must not infringe the rights of third parties in anyway.
7. All submissions should consist of:
 - a) A statement of design objectives
 - b) An overall description of the device
 - c) Detailed circuit descriptions and diagrams
 - d) A model of the device or the unique aspect of the design sufficient to demonstrate its feasibility.
8. The design will be judged on:
 - a) Originality and benefit to the handicapped
 - b) Potential for production
 - c) Elegance of engineering design
 - d) Electronics content
 - e) Design reliability
 - f) Simplicity of operation
 - g) Freedom from excessive maintenance
 - h) Safety.
9. Software only solutions are not accepted.
10. The judges' decision is final.
11. All designs must be submitted to the Wireless World Editor by the 1st October 1983.
12. Shortlisted entrants must be prepared to travel to a venue in London sometime during November and December 1983 to demonstrate their design. All costs will be paid by the journal.
13. Employees of Business Press International are not allowed to enter this competition.

wireless
world

COMPETITION
ENTRY FORM

"Design an electronic device to help the disabled"

Name of competitor _____

Address _____

Telephone (home) _____

(business) _____

I intend to enter the competition and to abide by the rules as laid down in the March 1983 issue of Wireless World.

I understand that, in order to qualify, my entry must be in the hand of the judges by 1st October 1983.

Signature _____

Date _____

Please send this form, as soon as possible, to:

The Editor, WIRELESS WORLD
Room L302, Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS.

Receipt of the form will be acknowledged.

Ex-STOCK TRANSFORMERS

Despatch by return

Price correct 1/2/83

OTHER PRODUCTS

OVER 150 TYPES OF TRANSFORMERS CONTINUOUS RATINGS

MAINS ISOLATORS

Pri 0-120; 0-100-120V. Sec 0-CT-115Vx2

Ref.	VA (Watts)	£	P&P
07★	20	5.32	1.50
149	60	8.84	1.60
150	100	10.06	1.84
151	200	13.69	2.12
152	250	16.31	2.64
153	350	20.34	2.12
154	500	25.02	2.90
155	750	35.91	OA
156	1000	45.89	OA
157	1500	60.52	OA
158	2000	72.43	OA
159	3000	101.12	OA
161	6000	203.65	OA

30 VOLT RANGE

Sec volts available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 2X SECS or 15V-0-15V

Ref.	30v	15v	£	P&P
112	0.5	1	1.19	1.20
79	1	2	4.32	1.40
3	2	4	6.99	1.60
20	3	6	8.10	1.85
21	4	8	9.67	1.90
51	5	10	11.95	2.00
117	6	12	13.52	2.02
88	8	16	18.10	2.26
89	10	20	20.88	2.24
90	12	24	23.20	OA
91	15	30	26.80	3.00
92	20	40	36.84	4.83

SCREENED MINIATURES

Ref.	mA	Sec Volts	Pri 240V	£	P&P
238	200	3-0-3		3.11	.90
212	1A, 1A	0-6, 0-6		3.45	1.20
13	100	9-0-9		2.59	.80
235	330, 330	0-9, 0-9		2.41	.90
207	500, 500	0-8-9, 0-8-9		3.36	1.20
208	1A, 1A	0-8-9, 0-8-9		4.27	1.40
236	200, 200	0-15, 0-15		2.41	.90
239	50MA	12-0-12		3.11	.90
214	300, 300	0-20, 0-20		3.39	1.20
221	700 (DC)	20-12-0-12-20		4.13	1.20
203	500, 500	0-15-20, 0-15-20		5.60	1.60
203	500, 500	0-15-27, 0-15-27		4.83	1.50
204	1A, 1A	0-15-27, 0-15-27		7.30	1.60

AVO & MEGGERS: FULL RANGE STOCKED

NEW RANGE:

2000 Hand Held DMM 3 1/2 LCD	£122.10
1000V, 2A AC/DC, 20m. res., diode test; cont. buzzer, fused, £71.40.	£49.30
2001 1000V 10A AC/DC/20m. res., safety fuses, £87.40.	£68.90
2002 Vehicle Testing, DC, to 20A, 1.500A with probe, 200V DC 500V AC 200k res., buzzer for continuity testing, £99 + P&P + VAT 15%.	£43.60
Megger Battery BM7	£58.50
MMS Minor	£81.90
DA211 LCD Digital	£131.30
DA116 LCD Digital	£187.00
DA117 Autorange LCD	£101.50
Megger Battery BM7	£71.60

8 Mk. 5 latest Model 71 (Handy) 73 (Portable Size) £49.30 £68.90

Avo Cases and Accessories P&P £1.60 + VAT 15%

12 or 24-VOLT RANGE

2x12V windings Pri 220-240V

Ref.	12v	24v	£	P&P
242	0.3	150mA	2.41	.90
213	1	0.5	3.19	1.20
71	2	1.0	4.25	1.20
18	4	2.0	4.91	1.60
85	5	2.5	6.78	1.50
70	6	3.0	7.69	1.40
108	8	4.0	8.98	1.64
72	10	5.0	9.82	1.80
116	12	6.0	10.89	1.90
17	16	8.0	12.97	2.12
115	20	10.0	17.46	2.44
187	30	15.0	21.89	2.64
226	60	30.0	44.46	OA

60 VOLT RANGE

Pri 0-120Vx2
2x30V tapped secs volts available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V, or 24V-0-24V or 30V-0-30V

Ref.	60v	30v	£	P&P
124	0.5	1	4.70	1.50
126	1	2	7.15	1.50
127	2	4	9.20	1.90
125	3	6	13.31	2.02
123	4	8	15.15	2.26
120	5	10	19.16	2.24
120	6	12	21.86	2.64
121	8	16	30.72	OA
122	10	20	35.76	OA
189	12	24	41.22	OA

AUTO TRANSFORMERS

Volts available 105, 115, 190, 200, 210, 220, 230, 240. For step up or step down.

Ref.	VA (Watts)	TAPS	£	P&P
113	15	0-10-115-210-240V	2.39	1.20
64	80	0-10-115-210-240V	4.94	1.40
4	150	0-10-115-200-220-240V	6.48	1.60
67	500	0-10-115-200-220-240V	13.30	2.24
84	1000	0-10-115-200-220-240V	22.70	2.80
93	1500	0-10-115-200-220-240V	28.17	OA
95	2000	0-10-115-200-220-240V	42.14	OA
73	3000	0-10-115-200-220-240V	71.64	OA
80	4000	0-10-115-200-220-240V	93.01	OA
57	5000	0-10-115-200-220-240V	108.30	OA

MAINS BATTERY ELIMINATORS

No wiring, ready to plug into 13A socket. 3, 4.5V, 6, 7.5V, 9, 12V DC @ 300mA £5.10 + £1.20 P&P + VAT 15%.

ANTEX SOLDERING IRONS 15W CCN2400 or C. £5.	£1.75
Safety stand	£5.30
12V 25W car soldering kit	£5.30

P&P 50p + VAT

Precision De-Solder Pumps for one hand working. Large £5.86. P&P 35p + VAT. Small £5.17. P&P 30p + VAT.

Telephones: Trimphone £24.50. Desk 746 £10. Wall phones £12.50 + £1.50 P&P + VAT.

50 VOLT RANGE

2x25V tapped secs. Volts available 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40 or 20V-0-20V or 25V-0-25V

Ref.	50v	25v	£	P&P
102	0.5	1	4.13	1.40
103	1	2	5.03	1.40
104	2	4	8.69	1.84
105	3	6	10.36	1.90
106	4	8	14.10	2.12
107	6	12	18.01	1.84
118	8	16	24.52	2.70
119	10	20	30.23	OA
109	12	24	36.18	OA

CASED AUTOS

240V cable input USA 115V outlets

VA	Price	P&P	Ref
20	£7.21	1.25	56W
80	£9.35	1.50	64W
150	£12.10	1.84	4W
250	£14.73	1.60	69W
500	£22.14	2.24	67W
1000	£33.74	2.80	84W
2000	£60.47	OA	95W

400/440V ISOLATORS

400/440 to 200/240V

VA	Ref.	£	P&P
60	243	8.11	1.50
250	246	16.07	OA
350	247	19.88	OA
500	248	24.77	OA
1000	250	50.53	OA
2000	252	74.79	OA
3000	253	104.86	OA
6000	254	207.92	OA

CABLE & WIRE

Instrument wire, coax cable, screened singles, etc.

PANEL METERS

43mm x 43mm...£6.70 p&p 80p + VAT
82mm x 78mm...£7.37 p&p 80p + VAT
0.50uF, 0.500uA, 0.1mA, 0.30V, 100NA, 100mA, 1A, 5A, 10A, 15V, 100V available

Ventilated Steel Transformer Cases. Wall or free-standing - grey

EDUCATIONAL METERS: I) 0-10A; II) 0-30V
75 x 78mm free-standing. Top screws terminal, simple. £4.50 + 66p p&p + VAT

Specialist transformer winding services for batch production

SPECIAL OFFER: SOLDERING IRONS, 240V BARGAIN: £1.75

+30p. p. & p. + V.A.T.

Constant Voltage Transformers

500VA	£198.90
1KVA	£278.40

+ carriage + VAT 15%

BRIDGE RECTIFIERS

200v	2A	45p	200v	4A	85p
400v	2A	55p	400v	4A	85p
100v	25A+	£2.10	400v	6A	£1.40
100v	35A	£2.80	500v	12A	£2.85

P&P 20p. VAT 15%

INVERTERS

12- or 24-volt d.c. input; 240v. a.c. output
100W £46.20
250W £101.50
500W £180.40
1kW £240.40 (24V input)

Continuous rating
+ carriage at cost + V.A.T. 15%

Barrie Electronics Ltd.
3 THE MINORIES, LONDON EC3N 1BJ
TELEPHONE 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST
WWW.6

OVERSEAS ENQUIRIES WELCOMED

Prices correct at time of print

WW - 006 FOR FURTHER DETAILS


PLUGS - SOCKETS - BOOKS - SEMI-CONDUCTORS - VALVES

AMAZING VALUE

TWO NEW HANDHELD DIGITAL MULTIMETERS

200µA - 10 AMP AC-DC

28 Ranges each with full overload protection

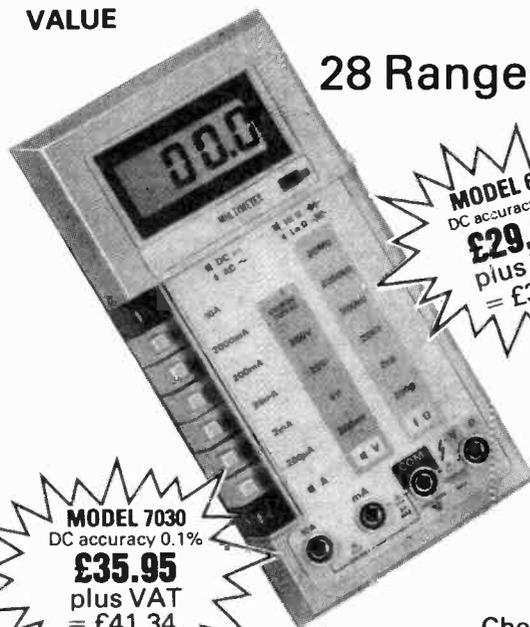

MODEL 6010
DC accuracy 0.5%
£29.95
plus VAT
= £34.44

MODEL 7030
DC accuracy 0.1%
£35.95
plus VAT
= £41.34

SPECIFICATION

- MODE SELECT:** Push button
- AC DC CURRENT: 200µA to 10A - 6 Ranges
 - AC VOLTAGE: 200mV to 750V - 5 Ranges
 - DC VOLTAGE: 200mV to 1000V - 5 Ranges
 - RESISTANCE: 200Ω to 200MΩ - 6 Ranges
 - INPUT IMPEDANCE: 10MΩ
 - DISPLAY: 3 1/2 Digit 13mm LCD
 - O/LOAD PROTECTION: All ranges
 - BATTERY: Single PP9 Type (included)
 - BATTERY LIFE: 200 hours
 - DIMENSIONS: 170 x 89 x 38mm
 - WEIGHT: 400g inc battery
- OTHER FEATURES:**
Auto polarity, auto zero, battery-low indicator, ABS plastic case with tilt stand, battery and test leads, spare fuse and operator's manual included.
Optional carrying case.

Cheques/PO please to

AFDEC ELECTRONICS LTD.

Kempshott Lane, Basingstoke Hants RG22 5LT

PLEASE SUPPLY (All prices include VAT & P&P)

PLEASE PRINT CLEARLY

MODEL 6010£34.44

NAME.....

MODEL 7030£41.34

ADDRESS.....

CARRYING CASE.....£2.00

TOTAL.....

COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RK05, NOVA, TEXAS etc.
Front load £550.00 - Top load £295.00
PSU type ME3029 for 2 drives £125.00
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details.

5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 newsletter. Suppression Devices SD5A £5.95.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 99XUOI Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard £9.95.
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95
BUHNER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

DON'T MISS THOSE BARGAINS CALL NOW, IT'S FREE!

01-683 1133 7 days per week 84 hrs. per day

COMPUTER 'CAB'



All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" w 10.5" h 11.5" d. Also available LESS PSU with internal dim. 19" w, 16" d, 10.5" h. £19.95. Carriage & insurance £9.50.

8" FLOPPY DISK DRIVES



Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality!! The 7100 single sided and 7200 double sided drive accept hard or soft sectoring IBM or ANSI standard formats giving a massive 0.8 MB (7100) 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMANS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. Carriage and insurance £9.75.
7100 Single sided £225.00 + Carr. 7200 Double sided £295.00 + Carr.
Optional accessories: Full technical manual £20.00 alone. £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

VIDEO MONITORS

MOTOROLA 9" open chassis monitor. Standard 240 v AC with composite 75 ohm video input, bandwidth in excess of 18 mhz. Monitors are ex equipment and although unguaranteed they are all tested prior to despatch, and have no visible burns on the screens. Dim approx. 9" x 9" x 9". Supplied complete with mains and input lead. Ideal ZX81 etc or giving the tele back to the family! Black and white phosphor. **£35.00 + £9.00 Carr.**

12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**

14" COLOUR superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL RGB with separate sync, and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col. definition. Brand new and guaranteed. Complete with full data & circuit. 240 v AC working. Dim. 14" x 13" x 13". **ONLY £199.00 PLUS £9.50 CARR.**

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499+ VAT

Made to the very highest spec. the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUIME compatibility plus Bi-directional printing, 10 or 12 pitch, 136 or 163 chars per line, full width 381 mm friction or single sheet paper. - order now or call sales office for more information and print sample. Please specify RS232 or CENTRONICS interface. Supplied complete with FREE dust cover and daisy wheel. Optional extras: RS232 data cable £10.00 - Tech. manual £7.50. Carriage & Ins. (UK) £12.50. - Tractor feed option £120.00



TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR + VAT
Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud. 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order
Options: Floor stand £12.50 + VAT
KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator. Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00** pp £1.95 Data sheet on request

RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v 2.5 ah. will deliver over 300 amps on short circuit!! Brand new at only £2.95

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 13A compact, a sync, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only £75.00
MODEM 2B/C Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. £85.00
MODEM 20-1 Compact unit for use with PRESTEL or full duplex 2 wire link. 75 baud transmit - 1200 baud receive. Auto answer. £130.00
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. £130.00
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. £130.00. Carriage. 13A £4.50. 2B/C & 20 £9.50.
For more details contact sales office.

D.C. POWER SUPPLY SPECIALS

Experimentors PSU Ex-GPO unit all silicon electronics. Outputs give +5v @ 2 amps +12v @ 800 ma. -12v @ 800 ma. +24v @ 350 ma. 5v @ 50 ma. floating Dim 160 x 120 x 350 mm. All outputs fully regulated and short circuit proof. Removed from working equipment, but untested. Complete with circuit. Transformer guaranteed. Only **£14.50 + £2.50 pp.**
CUSTOM POWER CO55 5v @ 3 amp. Very compact unit dim. approx 60 x 90 x 190 mm. Semi open chassis, full crowbar overvoltage protection. Tested Ex Equipment. **£11.95 + pp £1.25**
MINI SYSTEM PSU Ex equipment unit ideal for the small micro. Outputs give 5v @ 3 amps. +12v @ 1 amp and -12v @ 300 ma. Crowbar overvoltage protection and current limit. Fully tested. Dim 70 x 165 x 320 mm. Complete with Circuit only **£12.95 + £2.00 pp.**
PERIPHERAL SYSTEM SUPPLY. Fully cased unit supplied in a Brand new or little used condition. Outputs give 5v @ 11 amps. "+- 15-17v @ 8 amps. "- 15-17v @ 8 amps and "+ 24v @ 4 amps. All outputs are crowbar protected and the 5 volt output is fully regulated. Fan cooled. Supplied tested, with circuit. **£55.00 + £8.50 carr.**
MAIN FRAME SUPPLY. A real beefy unit designed for MINI or MAINFRAME use outputs give 5 volts @ 50 amps. +12v @ 5 amps. -12v @ 10 amps. All output are fully regulated with crowbar overvoltage protection on the 5v output. Supplied with circuit and tested. Ex-Equip. 110v AC input. Only **£49.95 + carr. £10.50.**

66% DISCOUNT ELECTRONIC COMPONENTS & EQUIPMENT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you play plus we always include something from our ads. for unbeatable value!! Sold by weight.

2.5kls £4.25 + pp £1.25
10kls £10.25 + pp £2.25
5kls £5.90 + pp £1.80
20kls £17.50 + pp £4.75

ALL PRICES PLUS VAT

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec. with manufacturer's markings, fully guaranteed. **50+ £2.95 100+ £5.15**
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. **100+ £6.90 200+ £12.30 200+ £19.50**

OLIVETTI TE300 REDUCED TO CLEAR

Complete input output terminal with integral B hole paper tape punch and reader. Unit operates at 150 baud in standard ASCII. Ideal as a cheap printer for a MICRO etc. 120 columns, Serial data i/o. Supplied complete with data, untested, unguaranteed **£65.00 + £11.50 carr.**

DISPLAY
-ELECTRONICS-

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts, Schools, Universities and established companies £20.00 Where post and packing not indicated please ADD 80p + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey
01-689 7702 - 01-689 6800 Telex 27924



**A MAJOR COMPUTER EXHIBITION IN
THE HEART OF INDUSTRIAL WALES.**

**COMPEC
WALES**

UNIVERSITY COLLEGE, CARDIFF MARCH 22-24, 1983

For the first time in March 1983 professionals residing in Wales and the West of England have an unequalled opportunity to see and compare the whole range of equipment and services available for today's specifiers and purchasers.

With many stands showing a comprehensive range of mini- and micro-computers, small business systems, printers, software, terminals and other peripherals, telecom equipment, word processors — as well as the many

ancillary services and equipment available — COMPEC WALES offers you the most effective way of bringing yourself up-to-date with everything the computer industry can offer.

Computer users, suppliers, systems and software houses, the OEM industry, consultants — and particularly those considering the use of a computer system for the first time, are all assured of seeing equipment relevant to their varied applications demonstrated by professionals familiar with your business in your area.

Apply for as many
FREE advance
registration tickets
as you will need.

Clip the coupon
NOW!

Applications not accepted after March 7

COMPEC WALES is a
ComputerWeekly
Exhibition.

**COMPEC
WALES**

Return to:
COMPEC WALES '83
Tickets,
IPC Exhibitions Ltd.,
Surrey House,
1 Throwley Way,
Sutton, Surrey,
SM1 4QQ

Please send.....FREE advance registration tickets for COMPEC WALES to:

Name

Job Title


Company

Address

.....

.....

WW

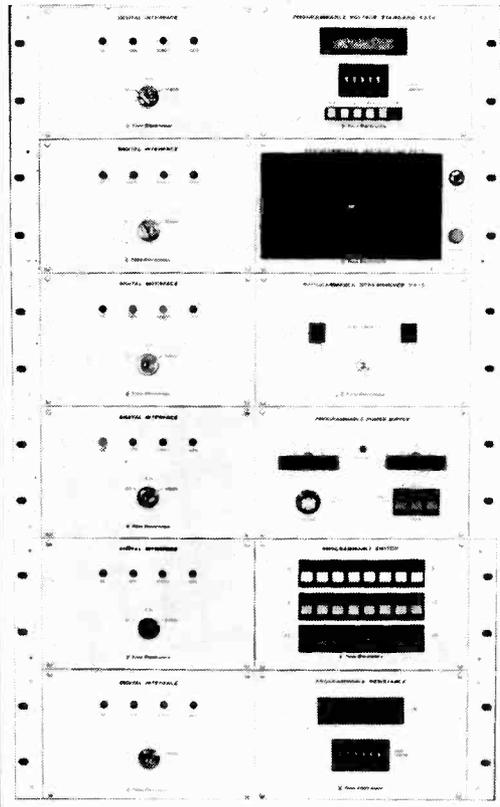

IEEE PROGRAMMABLES from TIME

9814 IEEE PROGRAMMABLE VOLTAGE STANDARD

A higher performance voltage standard with 4 ranges from 0.1 volt to 10 volt output. Accuracy is 0.01% and the resolution of setting is 1 in 200,000. Output resistance is less than 0.01 ohms, and output current adjustable 20mA-200mA. Temperature coeff is less than 20ppm/°C and long term stability better than 50ppm per year. Full manual control is available via front panel controls. Available for benchtop use or 19" rack mounting.

9816 IEEE PROGRAMMABLE VOICE

A high quality speech synthesizer which has a 280 word vocabulary. By suitable programming via the IEEE bus it is possible to output single words, phrases and sentences. The vocabulary has been chosen to be applicable to many ATE applications.

9815 IEEE PROGRAMMABLE SCREWDRIVER

The unit has been designed to overcome the problems of adjusting large numbers of multi-turn trimmers in ATE systems. The screwdriver is fully programmable via the IEEE bus with 3 speeds of rotation and 2 selectable torque values available. The unit is supplied complete with a flexible drive shaft and drill chuck into which various adjusting tools can be located.

9810 IEEE/PROGRAMMABLE POWER SUPPLY

0-33V in 0.1V steps. Local or remote (IEEE) operation. Fully programmable on the IEEE bus with 3 settable current limits 1mA, 10mA and 1.1A. A dual version of the 9810 is also available. The unit is 3 Euro units high and standard 19" rack mounting width.

9812 IEEE PROGRAMMABLE SWITCH

24 double pole changeover switches are available with full IEEE control. Each switch is rated at 1 Amp, 30V dc or 100V ac. Thermal emfs have been minimised to less than 1µV per switch. All outputs are on the rear panel along with the IEEE address selector switch and bus connector. Manual control of the switches is also provided via a set of front panel switches which also incorporate LED indicators.

9811 IEEE PROGRAMMABLE RESISTANCE

0-1 Megohm in 1 Ohm steps, fully programmable via the IEEE bus. Accuracy is 0.1% over most of the resistance range. Resistors are rated at 1 watt each. An attractive feature is the option to switch to local operation when the output resistance can be set up manually via front panel switches.

TIME ELECTRONICS LTD, Botany Industrial Est., Tonbridge, Kent, England TN9 1RS. Tel: (0732) 355993. Telex: 95481

WW - 079 FOR FURTHER DETAILS

ELECTRIC SHOCK

ACT AT ONCE - DELAY IS FATAL
BE READY TO SAVE A LIFE. SOMEONE MIGHT SAVE YOURS

ELECTRIC SHOCK ACT AT ONCE - DELAY IS FATAL

make sure it is safe to approach

If the casualty is not safe to approach, do not attempt to approach. If the casualty is safe to approach, do not attempt to approach until you are sure that the casualty is safe to approach.

If the casualty is breathing

Place the casualty in the recovery position and call a doctor.

If the casualty is NOT breathing

start artificial respiration - speed is essential


1. Check for breathing. If the casualty is not breathing, start artificial respiration. If the casualty is breathing, do not start artificial respiration.
2. Press hard and fast with one hand on the lower part of the breastbone, slightly to the left, with a clenched fist.

if AFTER FOUR INFLATIONS casualty does not respond to artificial respiration

Check for and give external heart compression. If the casualty is not breathing and has no pulse, start external heart compression. If the casualty is breathing and has a pulse, do not start external heart compression.

external heart compression

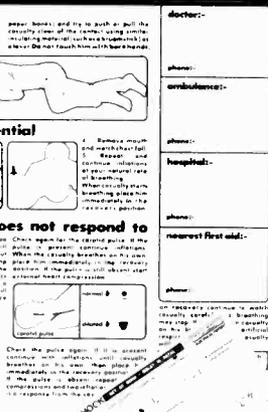Place the heel of your hand on the lower part of the breastbone. Press hard and fast with one hand on the lower part of the breastbone, slightly to the left, with a clenched fist.



Check for breathing. If the casualty is not breathing, start artificial respiration. If the casualty is breathing, do not start artificial respiration. If the casualty is not breathing and has no pulse, start external heart compression. If the casualty is breathing and has a pulse, do not start external heart compression.

ELECTRICAL REVIEW Shock First Aids
To General Sales Dept., Room 108
Quadrant House, Sutton, Surrey SM2 5AS.

Please send me:

- pocket cards at 70p each
- paper charts at £1.00 each
- card charts at £2.00 each
- plastic charts at £3.00 each

I enclose cheque/money order for £..... payable to IPC Business Press Ltd.

Post free in UK; overseas rates apply Tel. 01-661 8668; Telex 892084 BISPRS G.

Name

Address

WALL CHART:
356 x 508 mm.

POCKET CARD: 92 x 126mm.

HART

LINSLEY-HOOD 300 SERIES AMPLIFIERS



These latest designs from the drawing board of John Linsley-Hood, engineered to the very highest standard, represent the very best that is available on the kit market today. The delicacy and transparency of the tone quality enable these amplifiers to outperform on a side-by-side comparison, the bulk of amplifiers in the commercial market-place and even exceed the high standard set by his earlier 75-watt design.

Three versions are offered, a 30-watt with Darlington output transistors, and a 35- and 45-watt, both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2.

As with all HART kits the constructor's interests have been looked after in a unique way by reducing the conventional (and boring) wiring almost to the point of extinction. Any of these kits represents a most cost-effective route to the very highest sound quality with the extra bonus of the enjoyment of building a sophisticated piece of equipment.

30-watt Darlington amplifier, fully integrated with tone controls and magnetic pick-up facility. Total cost of all parts is £81.12. Special offer price for complete kits is £72.

35-watt Mosfet amplifier. Total cost of parts £98.41. Special offer for complete kits £87.40.

45-watt Mosfet amplifier. Total cost of parts £104.95. Special offer price for complete kits £94.80.

(Reprints of original Articles from Hi-Fi News 50p. Post free. No VAT.)

Reprints of MOSFET article 25p. No V.A.T. Post free.

'P.W. WINTON' TUNER AND AMPLIFIER



Snazzy matching slimline tuner and amplifier in beautiful wooden cabinets. These Ted Rule designs are for the enthusiast. Tuner covers LW, MW, SW, FM and TV sound Digital frequency readout with clock and timer features. FM has 6 section front end and switchable bandwidth for exceptional fringe area performance. Amplifier has Toroidal transformer, Mosfet output stages, 50 watts per channel and got a cracking review in Practical Wireless.

Tuner, Complete Kit..... £123
Amplifier, Complete Kit..... £98

LINSLEY-HOOD CASSETTE RECORDERS



We have done two kits to this design, one using the original car cassette mechanism and the newer version using a very high quality front loading deck. This new deck has an excellent W & F performance and fitted with our latest Sendust Alloy Super Head gives an incredible frequency range (with good tape you can see 23KHz on ours!).

Linsley-Hood Cassette Recorder 1..... £75.00
Linsley-Hood Cassette Recorder 2..... £94.90
Reprints of "WW" Articles..... 70p. No VAT



Please Note: New Phone Number after Feb. 26th (0691) 652894
Personal callers are always very welcome but please note that we are closed all day Saturday

THIS MONTH'S SPECIAL OFFER


LINSLEY-HOOD 300 Series Amplifiers reduced in price

30 Watt Darlington
Output
£65

35 Watt MosFet
Output
£79.50

45 Watt MosFet
Output
£83.50

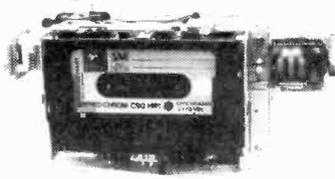FEED YOUR MICRO BYTES WITH OUR SOLENOID CONTROLLED CASSETTE DECK



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

LINSLEY-HOOD 100 WATT POWER AMPLIFIER

Our complete kit for this brilliant new design is the same size as our Linsley-Hood Cassette Recorder 2. Kit includes all parts for two power amplifiers with large heatsink area, huge power supply and speaker protection circuitry. Total cost of all parts is £114.46 but our special introductory price for all parts bought together is only £105.50.

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks..... £4.25

HM90 High Beta Permalloy Head. A hard-wearing, higher performance head with metal capability..... £5.20

HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response..... £3.20

HC551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head..... £7.40

Please consult our list for technical data on these and other Special Purpose Heads.

STUART TAPE CIRCUITS

(For reel-to-reel decks)
These circuits are just the thing for converting that old valve tape deck into a useful transistorised recorder. Total system is a full three head recorder with separate record and replay sections for simultaneous off tape monitoring. We also stock the heads. This kit is well engineered but does not have the detailed instructions that we give with our more recent designs. We would not therefore recommend it to beginners. Reprints of the original three articles 45p. Post free. No VAT.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £3.80 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy cassette size mains operated unit prevents build up of residual head magnetisation causing noise on playback..... £3.88

CASSETTE MOTORS

Brand New Governed 12v DC Tape Drive Motor Type MMI-6A2LK.
As used in SF925 and many other decks. 40mm Dia x 35mm Long. Shaft 10.5mm long x 2mm Dia. 6 x 2.5mm Mounting Holes on 26mm PCD on shaft end face. Anti-clockwise rotation at rated speed of 2200 RPM. Free run current 25mA. £4.95 each.
Lenco CRV/FFR.
We have a small quantity of spare motors for these decks at £6 each complete with drive pulley. Spare belts for FFR or CRV 90p (Large), 30p (Small).

Full details of the entire range of HART products is contained in our illustrated lists.
Ask for your FREE copy NOW.
Enquiries for lists are also welcome from overseas but please let us have three IRCs to cover the cost of surface post or 5 IRCs for airmail.
In a hurry? A telephone order with credit card number placed before 3 p.m. will be despatched THAT DAY!
Please add part cost of post, packing and insurance as follows:

INLAND	OVERSEAS
Orders up to £10 - 50p	Postage at cost plus £2
Orders £10 to £49 - £1	documentation and handling
Orders over £50 - £1.50	

ALL PRICES PLUS VAT



Northern Amateur Radio Societies Association

The Society is holding its 21st Exhibition at Pontins Holiday Village, Southport, on Saturday, 19th March and Sunday, 20th March, 1983. This was formerly the Belle Vue exhibition. The Exhibition will open at 11 a.m. each day.

It will include an inter club quiz, construction contest, grand raffle, R.S.G.B. book-stall, amateur computers, N.A.R.S.A. stands and trophy. Trade stands, featuring all types of Radio/Electronic equipment; Demonstration station.

The following traders will be present J. Birkett; Radiotronics; Amateur Radio Exchange; John's Radio; New Cross Radio; Wilson Valves; C.B. Electronics; S.O.T.A.; The Computer Junk Shop; W. H. Westlake; D. S. Electronics; Arrow Electronics Ltd; Green's Telecom; Royd Electronics; Newton Engravers; Leeds Amateur Radio; Macro Trading; R.A.I.B.C.; Micro Print Ltd; 2 J Sound; Gemini Communications; Radio Surplus; B.N.O.S. Electronics; D. Currie (Printer); G. Jackson; W. E. Griffiths; Waters & Stanton; Ham Radio Today; Garax Electronics; P.L.M. Communication Supplies; Tricon Supply Co.; Electro-Supplies.

Admission to the Exhibition will be 60p per day or £1 for two days.

Lots of 20 tickets or more booked in advance from Mike Bainbridge GAGS7, 7 Rothburg Close, Bury BL8 2TT, Lancs can be obtained at a 20% discount by sending the appropriate cash and s.a.e.

Chalets are available if booked direct from Pontins. Tel: 0704 77165 and can be equipped for self catering if you so wish. Charges vary from £10 + VAT (for 2 person chalet) to £26 + VAT (for a six person chalet). Larger family chalets are available.

Family entertainment will be available during the day while 'Residents' will be able to enjoy evening entertainment.

Talk in will be on S22 and other available simpler channels.

Car parking is free but please follow the parking attendants instructions and the notices to prevent congestion.

Enjoy yourself at this family Week End Exhibition.

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner
Telephone 445 2713/0749 (9461)

WW - 062 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Thursday, March 1st, for April issue, subject to space available.

DISPLAYED APPOINTMENTS VACANT: £15.50 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £3 per line, minimum £20 (prepayable).
BOX NUMBERS: £3 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS).
PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to IPC Business Press Ltd.



ALWAYS AHEAD WITH THE BEST!

£5,000-£13,000

- ★ **Experienced in:** Mini/Microprocessor Hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ **Where does your interest lie:** Image Processing; Automation; Datacomms; Radar; Nav-Aids; Video; Medical: Telemetry; Simulation; Satcom; Local Area Nets; Computers; Weapons; Communications?
- ★ **There are opportunities in:** Design; Test; Service; Sales; Systems; Production; Quality and Research for Engineers and Managers.
- ★ **First call:** MIKE GERNAT or JOHN SANDERS on 076 384 676/7.

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
 148-150 High St., Barkway, Royston, Herts SG8 8EG.

(1926)

POTENTIAL LEADER for SUNNY CALIFORNIA

An organisation in the San Francisco area is seeking a person fully competent in all aspects of software design and production, capable of leading others in this field and integrating with the hardware development and production groups.

The organisation and its environment offers advantages for advancement and living and disposes of adequate funds to ensure that any of its projects can be implemented and profitable.

The self-motivating person we seek needs to be capable of inspiring others and to possess the determination to bring projects to the market place.

Experience in communications and in navigation will be an advantage.

The organisation will ensure that the successful candidate is satisfactorily relocated and rewarded.

Replies to Box No. 1989



CAPITAL
 APPOINTMENTS LTD

CAPITAL HOUSE
 29-30 WINDMILL
 STREET
 LONDON W1P 1HG
 TEL: 01-637 5551

THE UK's No. 1 ELECTRONICS AGENCY

Design, Development and Test to £14,000
 Ask for Brian Cornwell

SALES to £15,000 plus car
 Ask for Maurice Wayne

FIELD SERVICE to £12,000 plus car
 Ask for Paul Wallis

We have vacancies in ALL AREAS of the U.K.

Ask for a Free Jobs List

Telephone: 01-637 5551 (3 lines)

(291)



Senior Projects Engineer — Service

We are looking for someone who can supervise our Service workshops and undertake in depth investigations into our Customers' service problems. We also need someone who can present and demonstrate our company's products. Do you think you are the one for the job? Then read on.

Firstly, you will need formal qualifications to degree standard.

You will also need to have a good few years experience in TV broadcast engineering tucked under your belt in installation, operation and maintenance, and a specialist knowledge of cameras, vision mixers, video recorders or assignment systems is essential.

All this, plus a current driving licence and the ability to work on your own initiative at home or abroad? Yes? We can't wait to hear from you.

Write to me enclosing a C.V. and tell me why you think you should be offered this important post. In return I can give you further details about our modern facilities, the advantages of working for a member of the Philips organisation and the opportunity of living in a beautiful city like Cambridge.

I'm Lynn Osborne, Personnel Officer, at Pye TVT Limited, Coldhams Lane, Cambridge.



Pye TVT Limited
 The Broadcast Company of Philips

(1993)

Electro-Acoustic

Product Development Engineer

c. £11,000

North London

The advent of digital switching systems allied to the rapid development in microprocessor technology means that tomorrow's telephone will provide a highly versatile communications medium. "New Generation" telephones will incorporate such aspects as large scale data memory, automatic call and recall options, visual displays, loud speaking facilities etc.

Our client, an international market leader in the field of telephone design and manufacture, is committed to an exciting product development programme and now needs to strengthen its engineering team through the appointment of an experienced Electro-Acoustic Engineer.

This position will be of interest to qualified engineers, degree level or equivalent, with several years' relevant experience in the design and development of electro-acoustic products. Successful applicants will be expected to demonstrate a high degree of design innovation to meet the critical low cost requirement associated with the high volume production of moulded components and small electro-mechanical assemblies while ensuring optimum acoustic performance.

This represents an exceptional

opportunity to join a small, multi-disciplined team of professional engineers working within the framework of a large organisation situated in the North London area. In addition to an attractive salary, the company offers relocation expenses where appropriate.

RF Development Engineers

Our client would also like to meet RF Development Engineers to work on a future range of Personal Communications products incorporating state-of-the-art technology up to 1GHz.

Whatever your level of experience, if you are qualified to degree level or equivalent and have a sound knowledge of analogue r.f. circuit design, our client would be interested in hearing from you.

In the first instance please telephone for an application form or write with full c.v. stating in a covering letter any companies to whom you do not wish your application forwarded, to: B. Kelly,

Moxon Dolphin & Kerby Ltd.,
178-202 Great Portland Street,
London W1N 5TB.
Tel 01-631-4411 quoting
ref: BK/955/W.

**MOXON
DOLPHIN
& KERBY LTD**

(2000)

SENIOR SERVICE ENGINEERS (Consumer Electronics)

Mitsubishi Electric (UK) Limited is a rapidly expanding and very successful division of the multi-national Mitsubishi Corporation.

In order to maintain and increase our present rate of growth we need to appoint additional Service Engineers to work on our wide range of consumer goods, including audio, T.V. and VHS video products. The appointments will be based at our modern Service Depot in Watford and offer excellent career opportunities.

The positions require at least five years experience of servicing the relevant equipment but offer opportunities for the successful applicant to expand his/her experience as the Company grows. Applicants should have a good technical qualification, ideally HND/HNC or HTEC Diploma (Electronics) and preferably some previous supervisory experience as well as a high level of self motivation.

A first class salary package is available including free BUPA cover and a twice yearly bonus scheme. Please telephone for an application form or send c.v. to:

Alan Freemantle,
Personnel and Administration Manager,
Mitsubishi Electric (UK) Limited,
Otterspool Way, Watford, Herts, WD2 8LD.
Tel: Watford 34618.

 **MITSUBISHI ELECTRIC**
(2002)

"HI-FLIERS" WANTED READY FOR "TAKE-OFF"

Senior Development Engineer to take design of real time microprocessor systems for video picture processing all the way from specification through to de-bugged delivery to client covering hardware (P.C.B. layout and prototype construction included) and software (high level and Assembler). Must be highly qualified with experience of microprocessors, vast memories, and L-S-I techniques, while knowledge of broadcasting video and display techniques would be useful.

Surrey

To £12,000

Computer Hardware Engineers to design digital and analogue interfaces for peripherals to mini and micro computers. Must be graduates with at least four years' experience of microcoding signal processing and embedded software, and simulator or trainer knowledge much appreciated.

Central Berks

Salary up to £12,000 p.a.

Commissioning and Test Engineers for a wide range of signal processing and digital video standards converters. Must have video and digital test experience and at least O.N.C.

London

To £10,000 p.a.

Senior Design Engineers to work on industrial data acquisition monitoring and control systems with associated test equipment with an emphasis on hardware with at least two years' experience of real time microprocessors and knowledge of assembler and high level structured languages. Must have H.N.C. at least and R.C.A. 1802 background would help.

Northants

And the salary? GOOD

Charles Airey Associates

Tempo House, 15 Falcon Road, Battersea, London SW11 2PJ
Telephone: 01-223 7662 or 228 6294

(1357)

ELECTRONICS APPOINTMENTS £6,000 - £16,000

ANALOGUE, RADIO, MICROWAVE
DIGITAL, MICROPROCESSOR, COMPUTER
DATA COMMS, MEDICAL

Design, Test, Sales and Field Service Engineers -
to use our free, confidential service and improve your salary and career prospects. UK and overseas, contact:

 **Technomark**
Engineering & Technical Recruitment

11 Westbourne Grove, London W2. Tel: 01-229 9239

(1935)

Appointments

ENGINEERING MANAGERS TV Broadcasting

We are looking for two Engineering Managers, for senior positions at our Birmingham and Nottingham studio centres. They will be responsible to the Chief Engineer for the work of electronic and mechanical engineers involved in the evaluation, design, installation, commissioning and maintenance of technical equipment.

Applicants must have extensive experience of modern electronic engineering, including the application of digital and computer techniques: a TV studio engineering background would be preferred, but relevant industrial experience could be of value. Suitable candidates are likely to have had a formal education leading to a professional qualification, but the primary requirement is practical technical knowledge and ability.

A high level of managerial skill and judgement is required, together with the potential to make a significant contribution to the future development of the company. Likely age range 35 - 40.

These are senior appointments, and the high salaries will reflect the responsibilities involved and the qualities expected of the successful candidates.

Application forms from:-
The Recruitment Officer,

Central Independent Television Plc,
Central House, Broad Street, BIRMINGHAM B1 2JP
(Please quote Vacancy No: 115(WW) and state preference for Birmingham/Nottingham).



CENTRAL (2007)

CAMBRIDGESHIRE COLLEGE OF ARTS AND TECHNOLOGY
ARE YOU MAKING THE MOST OF YOURSELF?

HAVE YOU CONSIDERED FURTHERING YOUR TRAINING IN ELECTRONICS ?

We offer:

CNA A BSc in Electronic Engineering

A four-year part-time degree for mature students, includes study of Digital, Telecommunications and Control Systems.

Entry qualifications: HNC or equivalent in Electrical and Electronic Engineering or Applied Physics. This degree is considered by the Council of Engineering Institutions as meeting their C.Eng academic requirements.

HND in Electrical and Electronic Engineering

A 2½-year sandwich course, including study of Electrical, Electronic and Communication Engineering, combined with control Engineering and Digital Techniques. Entry qualifications: 1 A Level in Mathematics or Physics.

For further details and application forms, contact The Department of Engineering, Cambridgeshire College of Arts and Technology, Cambridge CB1 2AJ. Telephone (0223) 63271. (2005)

TRAINEE RADIO OFFICERS

First-class, secure career opportunities.

A number of vacancies will be available in 1983/84 for suitable qualified candidates to be appointed as Trainee Radio Officers.

If your trade or training involves Radio Operating, you qualify to be considered for a Radio Officer post with the Composite Signals Organisation.

Candidates must have had at least 2 years' radio operating experience or hold a PMG, MPT or MRGC certificate, or expect to obtain this shortly.

On successful completion of between 36 and 42 weeks specialist training, promotion will occur to the Radio Officer grade.

Registered disabled people may be considered.

SALARY & PROSPECTS

TRAINEE RADIO OFFICER: £4,357 at 19 to £5,203 at 25 and over. On promotion to Radio Officer: £5,968 at 19 to £7,814 at 25 and over. Then by four annual increments to £10,662 inclusive of shift working and Saturday and Sunday elements.

For full details please contact our Recruitment Officer on Cheltenham (0242) 21491 Ext. 2269.

Recruitment Officer, Government Communications Headquarters, Oakley, Priors Road, Cheltenham, Gloucestershire GL52 5AJ

(1531)

GCHQ

INDEPENDENT TELEVISION NEWS LIMITED

ELECTRONIC DESIGN ENGINEER

£14,000 - £17,000

ITN

A vacancy exists in the Electronics Design and Development laboratory at ITN's Studio Centre situated in the West End of London.

The Section's recent design projects have included a state of the art computer graphics system now in daily use with ITN's programmes, minimal bandwidth digital sound and analogue vision fibre optic links.

Candidates for this interesting post should have considerable analogue circuit design experience related to the broadcasting industry and should have academic qualifications in electronic engineering to at least HND standard.

A salary in the range from £14,000 to £17,000 per annum is offered according to experience. A contributory pension scheme and subsidised canteen facilities also operate.

Application forms are available from the Personnel Department on 01-637 3144 quoting reference number 307002.

ITN is an equal opportunities employer. (2009)

BORED ?

Then change your job!

- 1) Test Equipment Controller**
Plan and procure test equipment and control a team of test equipment engineers. To £12,670 - Hants.
- 2) Maintenance Engineer**
Start an in-house test of communications equipment - then move to field service when fully conversant. To £8,000 + car - London.
- 3) Service Engineer**
Analogue and digital detection and alarm systems. Middx-Essex - to £8,000.
- 4) Test Engineer**
In-house work on modems and data communications systems. To £7,500 - Bucks.
- 5) Service Personnel**
(RAF, RN, Army)
We have many clients interested in employing ex-service fitters and technicians at sites throughout the UK. Phone for details.
- 6) £500 per week**
We are paying very high rates for contract design and test engineers who have a background in RF, MICROWAVE, DIGITAL, ANALOGUE or SOFTWARE, at sites throughout the UK.

Hundreds of other Electronic and Computer Vacancies to £12,500

Phone or write:

Roger Howard, C.Eng., M.I.E.E., M.I.E.R.E.

CLIVEDEN CONSULTANTS

87 St. Leonard's Road, Windsor, Berks.
Windsor (07535) 58022 (5 lines)

(1646)

CLIVEDEN

UNIVERSITY OF THE WITWATERSRAND, JOHANNESBURG

Applications are invited from suitably qualified persons regardless of sex, race, colour or national origin for appointment to the following immediately available post:

TELEVISION ENGINEER

R12 252-R17 880 p.a.
(£1 = R173 approx.)

A vacancy exists in the Central Television Service for a suitably qualified Studio Engineer. The University operates two full-colour television studios and a campus distribution system.

The main activities are making educational training programmes for the University and commerce and industry. Duties include the maintenance of television studio equipment, campus distribution system and associated equipment. Also studio operation duties as and when required.

Applicants should have a number of years' relevant experience in Television Engineering.

The University offers salary commensurate with qualifications and experience plus 13th cheque, pension, medical aid and housing subsidy for eligible applicants, congenial and dynamic environment, continuous opportunities for education and training, generous leave. There is a possibility of a salary supplementation.

Applicants should write to the Deputy Registrar (Non-Academic Staffing) University of the Witwatersrand, 1 Jan Smuts Avenue, Johannesburg 2001 giving full personal and career details, as well as the names and addresses of at least two referees.

Applications should be lodged by 15 March, 1983. (1984)

LOGEX ELECTRONICS RECRUITMENT

Specialists in Field & Customer Engineering appointments, all locations and disciplines.

Logex House, Burligh, Stroud
Gloucestershire GL5 2PW

0453 883264 & 01-290 0267

(24 hours)

EXPERIENCED SERVICE ENGINEER

wanted to repair and service Amateur, Private, Mobile and Marine equipment. Previous experience is necessary. Salary approximately £7,500/negotiable per year, plus car for personal use.

Apply to:

Communique, Communications House
Purley Avenue, London NW2
Tel: 01-450 9755

(2001)

CHANCE FOR YOUNG ENTHUSIAST WITH TOP BRITISH MICRO MAKER

TECHNICAL SUPPORT (SALES)

UP TO £5-7.6K, OXFORD-BASED

Research Machines is one of the leading British manufacturers of microcomputers. Thousands of users of our 380Z, ranging from school teachers and scientists to technicians and DP professionals, regard it as an essential tool of their trade. Satisfying their hardware and software information needs and solving their problems — by telephone and letter — is the first job of Technical Support.

But there's a lot more to this interesting and challenging vacancy than that. In addition to sales and technical support to customers, you will also give technical support to the sales team; support the Sales team at exhibitions and demonstrations; provide feedback to relevant departments on technical matters and sales trends; and liaise between customers and maintenance engineers. In the process you will get plenty of opportunity for hands-on experience of our range of hardware and software.

We are looking for a computer enthusiast to join this young, small team in our Sales Department. The successful candidate will probably:

- be capable of programming in a high-level language — preferably BASIC;
- have a real interest in microcomputing and some knowledge of electronics;
- be educated to at least 'A' level;
- have some admin or sales office experience.

Starting salary is between £5,000 and £7,600 depending on age and experience, and we also offer a number of valuable benefits such as free BUPA, life and disability insurance, and a pension scheme.

If you are interested in this vacancy please contact Polly Keane, by phone or letter, for an application form, quoting TS/WW

RESEARCH MACHINES MICROCOMPUTER SYSTEMS

RESEARCH MACHINES LTD Mill Street, Oxford OX2 0BW, Tel: (0865) 726136

(1999)

SENIOR RF ENGINEER

Western Home Counties

c £12-£14,000

Our client is a remarkable company with an enviable record of success and development.

Although they recruit infrequently they have identified a need for one Senior RF Engineer.

Ideally you will have attained Project Leader status and be able to work within a highly innovative environment.

You will have exacting, technical and commercial deadlines to meet and will therefore frequently work under pressure within a small department of very highly skilled and qualified people.

The prospects for promotion and career development are excellent as the company is commercially aggressive and has a number of unique qualities.

They are part of a successful multinational group covering a range of communications equipment.

To discuss this position contact PAUL HECQUET on Lewes (07916) 71271 or write with brief C.V. to the address given below.

(1990)



The Electronics
Recruitment Company

Temple House
25 26 High Street, Lewes
East Sussex BN7 2LU
Tel: Lewes (07916) 71271

Appointments

Premier international electronics companies – very secure and expanding in North, South, East and West of London and Home Counties – require professional senior staff (including departmental heads). Re-location allowance up to £3,000.

ELECTRONIC ENGINEERS

Electronic engineers required with degree – H.N.C. – tech. cert. – O.N.C. Almost any background required but software and hardware experience will bring salary of absolute minimum of £6,500 p.a. and could be up to £11,000 p.a.

ELECTRONIC DESIGN/DEVELOPMENT

Engineers required with experience of circuit or component design or development for microwave equipment or digital logic or computer peripherals or electronic packaging or film technology or telecommunications. Also above for up-dating in modern techniques. Salaries up to £11,000.

SOFTWARE PROGRAMMERS & ENGINEERS

Engineers or mathematicians required for development of commissioning and design proving programmes from assistant to team leader level. Salaries up to £12,000 p.a.

Please contact by telephone, or letter, to discuss companies and possibilities. Rickmansworth 770431 (Ansafone after 5 p.m.) or telephone Watford 49456 any time.

GORE MANAGEMENT SERVICES LTD

SELECTION & TRAINING CONSULTANTS
111 High Street, Rickmansworth, Herts
Rickmansworth 770431



Applications are invited from suitably qualified persons regardless of sex, race, colour or national origin for appointment to the following immediately available post:

TELEVISION ENGINEER

R12 252 - R17 880 p.a.

A vacancy exists in the Central Television Service for a suitably qualified Studio Engineer. The University operates two full-colour television studios and a campus distribution system.

The main activities are making educational training programmes for the University and commerce and industry. Duties include the maintenance of television studio equipment, campus distribution system and associated equipment. Also studio operation duties as and when required.

Applicants should have a number of years' relevant experience in Television Engineering.

The University offers salary commensurate with qualifications and experience plus 13th cheque, pension, medical aid and housing subsidy for eligible applicants, congenial and dynamic environment, continuous opportunities for education and training, generous leave. There is a possibility of a salary supplementation.

Applicants should write to the Deputy Registrar (Non-Academic Staffing), University of the Witwatersrand, 1 Jan Smuts Avenue, Johannesburg, 2001, South Africa, giving full personal and career details as well as the names and addresses of at least two referees. Applications should be lodged by 15th April, 1983.

**UNIVERSITY OF THE WITWATERSRAND,
JOHANNESBURG**

(1987)

ELECTRONIC DESIGN ENGINEERS

We are a small highly successful manufacturing company specialising in RF communications, digital and low frequency analogue equipment.

We require young highly motivated engineers wishing to develop their experience. The ideal candidate must have complete confidence in his ability.

- Starting salary £10K + (neg).
- 37½-hour week. Overtime available.
- Pay reviews every 6 months.
- Pleasant working environment.
- Location near City of London.

Contact Keith Penny on (01) 250 0894


(1983)

TECHNICAL VIDEO SALES

Rapidly growing video division need sales person to sell sophisticated military airborne video and image processors to U.K. Aerospace and Government research laboratories and with our agents in Europe.

Applicants should be qualified to HNC and should have experience in Aerospace or video background. Preference will be given to applicants in their early or mid twenties. Salary £9,000 plus car and other benefits.

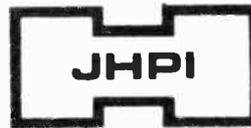Write for full description and application form to:



Mrs M. Berrow
Personnel & Training Manager
John Hadland (PI) Ltd.
Newhouse Road
Bovingdon
Hemel Hempstead
Herts HP3 0EL

(1988)



SALES ENGINEER

We require a first class sales engineer with experience in test and measuring instruments or microwave components to cover the South East and South of England – that is Essex to Hampshire, south of the Thames. If you know you would meet our needs – or think you would – we would like to hear from you.

We offer an interesting range of products – life will never be dull – a small company atmosphere, a basic salary of £8,500 per annum plus bonus and more if you are worth it, together with company car and free BUPA membership for you and your family.

Applications to: Philip Westwood, Managing Director
WESSEX ELECTRONICS LIMITED
114-116 NORTH STREET, DOWNEND, BRISTOL BS16 5SE
Telephone: (0272) 571404

(2014)

PHONE
YOUR CLASSIFIEDS TO
IAN FAUX ON
01-661 3033

DEVELOPMENT ENGINEER - ACOUSTICS

c £9500 + BONUS

Senior Engineer required by leading manufacturers situated in pleasant South Coast area. To be responsible for design and development of electro-acoustic devices/products for volume production in telecommunications or related industry.

Ideally, applicants (M/F) should be of degree standard (with acoustics endorsement) with experience of design of transducers for electro-acoustic applications. However, good experience may offset lower academic qualifications. Age range 25-40 years.

Write in first instance to:



21 CHURCH ROAD
HOVE
SUSSEX BN3 2FA
BRIGHTON 779574

(1994)

Brompton Hospital

Trainee Medical Electronics/ Physics Technician

We require a Trainee Technician with an interest in medical electronics. Training and day release to study for O and H TEC will be provided. During the first year the technician appointed will be expected to spend at least half his/her time working in the Intensive Care Units where they will gain experience of the clinical environment. The work will be of a varied but routine nature. The remaining time will be spent in the Department of Medical Electronics.

The post is likely to suit those with science 'A' levels who have a desire to make a career in medical electronics/physics.

The post is for one year in the first instance. Salary will be according to age and qualifications.

Further information and application form available from Miss J. A. Jenks, Personnel Manager, Brompton Hospital, Fulham Road, London SW3 6HP. Telephone: 01-352 8121 Ext. 4357. Completed application forms to be returned as soon as possible.

(1985)



APPLICATIONS ARE INVITED FOR THE POST OF

SERVICE TECHNICIAN

AT OUR HEAD OFFICE IN LONDON

The principal responsibility will be for maintenance of multi-standard television receivers and video cassette recorders.

The successful applicant will have considerable experience of colour television receiver and video cassette recorder servicing probably with a major television rental company in the industrial or domestic sectors. Knowledge of the V.H.S. format would be an advantage.

Candidates should be prepared to work with the minimum of supervision and be capable of using their own initiative.

Qualifications are less important than practical ability but we would expect City and Guilds Full Technological Certificate to have been gained. The salary will depend upon qualifications and experience. Conditions of employment include a 35-hour week, 20 days' holiday per annum, and a contributory pension scheme.

Application forms may be obtained from: Mr. G. J. Atkins, Technical Services Manager, Walport Telmar International Ltd., Walport House, 62/66 Whitfield Street, London, W1P 6JH. Telephone: 01-631 4373. (2010)

FIELD SERVICE ENGINEERS

(Based in Italy)

Exciting opportunities for qualified Electronics Engineers to work on the installation and maintenance of Television Studio Equipment at customer sites throughout Italy and Africa.

Key requirements are:

- ★ A sound knowledge of Electronic Engineering – Degree/HNC or equivalent
- ★ At least 3 years' experience in a Television Studio/Production environment, with specific experience of both Quad and Helical Scan, VTR, TV Camera and Switcher Engineering
- ★ Availability to travel extensively throughout Italy and Africa and ability to work on own initiative while away from base

Attractive salary package and other benefits to include overseas allowances and relocation expenses.

AMPEX

Please write or 'phone
Maureen Brake at:
Amplex Great Britain Limited
Acre Road, Reading RG2 0QR
Berkshire, England
Tel: Reading (0734) 875200

(1995)

Satellite Operations Coordinator

The International Telecommunications Satellite Organization is a rapidly growing organization offering challenging career opportunities and comprehensive salary and benefits packages which include five weeks' paid vacation and free medical and dental coverage.

Position available as Operations Centre Coordinator to assist in providing real time guidance to earth stations operating in an international satellite communications system. Duties include network control, system performance monitoring and implementation of telecommunications services through coordination with domestic and international earth stations and telecommunications entities.

Applicants should have 3-5 years of experience in satellite earth station operations or international communications network control facilities at a supervisory or senior technician level. A strong background in satellite system operations with recent maintenance experience and technical training are required. The ability to engage in effective liaison with international telecommunications entities and acceptance of shift work assignments are required.

Position is based in Washington D.C. For more information about this exciting opportunity please forward your resume including salary history to:

INTERNATIONAL TELECOMMUNICATIONS SATELLITE ORGANIZATION

ATT: Personnel Department Box C
490 L'Enfant Plaza S.W. Washington D.C. 20024

(2004)



Medical Physics Technical Officers

Saudi Arabia

c.£13,500-£18,000 p.a. inc. tax free

Allied Medical Group are the British consultants to the prestigious Riyadh Al-Kharj Hospital Programme in Saudi Arabia which provides the best of health care to the armed forces of Saudi Arabia and their families. The two hospitals which comprise the Programme – totalling approximately 660 beds – are new, superbly equipped, mainly U.K. staffed and enjoy a full range of paramedical and other support services. Within the next three years the Programme will expand to 1,000 beds and will become a principal referral centre in the Kingdom.

The Bio-Engineering Division, within the Medical Physics Department, is responsible for servicing a wide range of bio-medical equipment. We are now seeking Medical Physics Technical Officers to specialise in the maintenance of an extensive range of laboratory equipment covering clinical chemistry, haematology, microbiology and histo-pathology. Most of the equipment is maintained within the well-equipped workshop with sophisticated items being handled in conjunction with service agents.

Applicants should possess an HNC or equivalent qualification in electronics or another appropriate subject with at least 2-3 years' experience of maintaining hospital laboratory equipment. Three years' post-qualification experience would be an advantage.

Quote Ref: RKH 462

Junior and senior posts have also arisen within other areas of the mechanical workshop and more general applications are invited.

Quote Ref: RKH 463

Posts are offered on a two year renewable contract basis and attract one of the best benefits packages in the Middle East.

For further details please write, quoting the appropriate reference number to: Theresa Sutherland, Senior Personnel Officer, Allied Medical Group, 18 Grosvenor Gardens, London, SW1W 0DZ. Alternatively, call our 24-hour answering service on 01-730 5339, quoting appropriate reference number.

All applications will be dealt with in the strictest confidence.

INFORMAL OPEN DAYS – SCOTLAND

Please come along and see us. We'll be able to answer all your questions about living and working in Saudi Arabia.



Date	Location	Time
Wednesday, 16th March	North British Hotel George Square, Glasgow	2-8pm
Thursday, 17th March	North British Hotel Princess Street, Edinburgh	2-8pm

Allied Medical Group

The best of British Health Care in the Middle East

Guys Hospital DEPARTMENT OF CLINICAL PHYSICS AND BIOENGINEERING

This active, well established and well-equipped Department provides a physical sciences service for a number of clinical departments in the Hospital. We require a technician to join our electronics servicing group. This work includes the maintenance and servicing of a varied range of medical electronic equipment and covers all aspects of patient orientated equipment from fixed installations to small portable instruments.

Experience in this type of work would be an advantage but candidates with HM Forces experience or having a good background of TV servicing are encouraged to apply.

An ONC/HNC or equivalent qualification, followed by at least three years' technical experience, are required. The appointment will be on the Medical Physics Technician Grade 3 Scale. Salary: £6,468 p.a. - £8,087 p.a. inclusive.

Application forms may be obtained from the Personnel Department, Mary Sheridan House, Guy's Hospital, St Thomas' Street, London SE1 9RT. Telephone: 01-407 7600 Extn 3471 quoting Ref. PZ.

Closing date for completed applications: 4th March, 1983.

PRESTON POLYTECHNIC SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING. Applications are invited for the post of Senior Laboratory/Workshop Technician. Salary Scale: T3/4 (DLW) £5973 to £7545 plus up to £114 per annum for possession of appropriate qualifications. Applicants must possess a recognised electrical/electronic technician qualification and have experience in electronic design and construction. Application forms and further details obtainable from the Personnel Officer, Preston Polytechnic, Corporation Street, Preston PR1 2TQ. Tel: Preston 262027. Reference No: NT/82/83/19. Closing date: 3rd March 1983. (1192)

R & D OPPORTUNITIES. Senior level vacancies for Communications Hardware and Software Engineers, based in West Sussex. Competitive salaries offered. Please ring David Bird at Rediffusion Radio Systems on 01-874 7281. (1162)

ARTICLES FOR SALE

HYDROKIT Hydraulic Flypress Conversion



Complete Hydraulic Kits comprising: Power Pack, Control Valve, Ram, Hoses and Fittings. Suitable for many applications including Flypress Conversions. Working pressure 2,000 p.s.i. 2-10 tons. Stroke 4in. Adjustable relief valve. Power pressure and return.


PRICE FROM £428

"HYDROKITS" ARE COMPLETE
Just remove arm of press and operate screw shaft, fit hydraulic ram assembly with manual valve (all supplied), fill with hydraulic oil and connect to power source, 13 amp or 3-phase. Send details of press or ask for questionnaire.



TAWISHELM HYDRAULICS INTERNATIONAL LIMITED
Hypress House, Station Close, Potters Bar, Herts. EN6 1TL. Tel. Potters Bar (0707) 43434 (1735)

ARTICLES FOR SALE

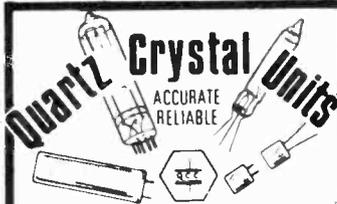

Private enquiries send 13p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY 01-942 0334 & 2988

(8493)

ENCAPSULATING EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regunning metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

VALVES, PROJECTOR Lamps, 6000 types, list £75, world wide export. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Phone (024 366) 2023. (1991)

LAMPS AND CABLE. Large amount of lamps and cable for sale – all types and sizes, domestic and industrial. Telephone MIRAGE LIGHTING on HITCHIN (0462) 733388 between 10am-7pm. (1809)

BRIDGES, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators – sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236. (1627)

TV TUBE Rebuilding Plant. Due to frustrated export order many items of latest plant and equipment available at half price. Western-Whybrow Engineering, The Square, Marazion, Cornwall. Telephone (0736) 710456. (1986)

WIRELESS WORLD 1968-81. (Few missing). Excellent condition. £40 + carriage. 15 copies 1930's, 40's including 2 RF straight set, Williamson Amplifier, Golden Jubilee issue. £10. Phone Bristol (0272) 733 837. (1982)


SULLIVAN Thermistor Bridge £59.
Heterodyne Bridge Detector £39.
EMI Disc Recording blanks 100 – £150.
Laboratory oven £49.
Lab-gear TV Pattern Generator £45.
Small compressor pump £20.
500lbs/sq.in. receiver £25.
Watson lab microscope £89.
Centrifuge £49.
Brinell Hardness Tester £98.
Ultrasonic Leak Detector £59.
4KW Diesel Generator £195.
Water pumps £12-£98.
Sullivan Mirror Galvanometer £39.
Audio Analyser £65.
220MHz Sweep Generator £79.
EMI Audio Sweep Generator £65.
Record Clip-on Ammeter/voltmeter/Recorder £79.
Marconi TF I225A Noise Receiver £59.
Plug-ins Cossor 1078 £15 ea.
Pye 200,000 M/ohm meter, EIL twenty-million M/ohm meter £35 ea.
A few oscilloscopes and other RF, AF, sweep generators

040-376236 (2000)

ARTICLES FOR SALE

RACAL COMMUNICATIONS RECEIVERS

500 Kc/s - 30Mc/s 1MHz wide. RA17L - £175. RA117E - £225. A few sets available as new at £75 extra. All receivers are air tested and calibrated in our workshop, supplied with full manual, dust cover, in fair used condition. New black metal louvered cases for above sets £25 each. RA98D - ISB - SSB - £75. RA21B - SSB - ISB and fine tune for RA117 - £50. TRANSMITTER DRIVE UNIT RA79. 1.5mc/s - 30mc/s - SSB - ISB - DSB - FSM - CW - £150. AERIAL TUNING UNIT and protection unit MA197B - £25 to £50. DECADE FREQUENCY GENERATOR MA350B Solid state synthesiser for MA79 or RA117 - RA217 - RA1217 - £150 to £200. MA250G - 1.6mc/s to 31.6mc/s - £150 (New). MA259G - precision frequency standard - 5mc/s 1mc/s 100kHz - £100 to £250. RACAL MA152 - Standing wave ratio indicator. FX2mc/s - 25mc/s Power up to 1000watts - 50 ohms - Auto trip switch - Transistor mains 100 - 250AC, new and boxed - £40. RACAL COUNTER 836 (9036) 32mc/s TTL circuit design - tested with manual - £50 to £75. OSCILLOSCOPES COSSOR CDU150 - 35mc/s - Twin Beam - Solid State - £175 with manual. TEXTRONIC OSCILLOSCOPE 647 and 647A Solid State - 50mc/s and 100mc/s bandwidth - £250 and £350. Tested, circuit and instructions. RACAL COUNTER 801 M-125 Mc-S £50. IMAGE INTENSIFIERS - Mullard - G.E.C. or E.E. Type XX 1060 very high gain self-focusing image intensifier assembly for night vision systems. Minimum luminance gain 35,000. Supplied as received from Government supplies in original box (used) with data sheets - £12 ea. (P&P+VAT=£5.25). All items are bought direct from H.M. Government, being surplus equipment. Price is ex-works. SAE for all enquiries. Phone for appointment for demonstration of any item. John's Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel: (0274) 684007. V.A.T. and Carriage extra. (848)

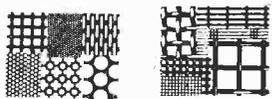

Perforated Metals - Screens, Plastics, Wire Meshes, Sifting Media, Cable Tray, Gratings, direct from Manufacturer's Stock. We can cut to size.

We specialise in one-offs or large quantities.

GRAEPEL PERFORATORS LTD

Unit 1-B, CHARLES STREET Dept WS, WALSALL, STAFFS WS2 9LZ. Tel. 0922 611644/611414. Telex 335291

POWER V MOS-FET TECHNOLOGY

We specialise in all aspects of this important subject. A comprehensive service is offered to individual or OEM users, including:

- ★ Hitachi Supertex and RCA V MOS-FET from stock.
- ★ V MOS-FET power modules from stock.
- ★ Competitive prices (120 watt modules £15.45, 1 off).
- ★ Printed circuits and kits.
- ★ Data books and application notes.
- ★ Design, evaluation and advice service. Catalogue/sample data sent free (50p stamp appreciated towards post and packing). Phone 02514 22303 and ask Richard Walsh about your application requirement or write:

AUDIO TECHNOLOGY
Freepost, Church Crookham
Aldershot, Hants. GU13 0BR

DC-DC CONVERTER, 5V input to 25V output, output current 50mA maximum, ripple level 80mV pk-pk, measuring 35x40x19mm. £10 each plus 60p P&P. - K.H. P'ng, 30 Queensbury Road, Alpertown, Middlesex HA0 1LU. Tel: Egham 34300, ext. 208 or 01-997 9708 eves. (2013)

QUARTZ CRYSTALS IN 24 HOURS ANY FREQUENCY 2-50 MHz FOR £4 inc

New fast service for C.W.O. only (state holder style). Clock oscillators for microprocessors in stock from £9.30.

Mcknight Crystal Co Ltd, Hardley Industrial Estate
Mythe, Southampton SO4 6ZY Tel. 0703 848961 (2008)

SITUATIONS VACANT

We'd like to read your autobiography

And this is your chance to write it. Just register your career data with us and our sophisticated computer bank does the rest. Using complex matching techniques, we scan the register every day to see which of the many vacancies suit you exactly. Once the right one - or more - has been identified, our clients contact you direct. It's the fastest most effective way of putting two decision makers together and it's free!

The Lansdowne Appointments Register

Park House, 207 The Vale,
London W3 7QB. Tel: 01-743 6321
(24 hr answering service)

Name _____
Job Title _____
Address _____

WW 15 2

Enough said.

As an ambitious Electronics Engineer, you can't devote as much time to furthering your career as you'd like to - so why not let someone else do it on your behalf? Simply complete the coupon and you're on your way to a new, more rewarding future.

A selection of some of the current vacancies we have for qualified people are:

- Senior Design Engineers ● Chief Engineers ● Project Leaders/Planners
- Engineers: ATE/Applications/Packaging/Test/Design & Development (Satellite Comms)/Quality/Systems/Software/Hardware/Microwave/Semi-Conductor/Sales/Custom Service/Audio Communications

Salaries range from £6000-£16000, with ages from 20-40, at various locations in the UK.

As an example, Digital, the worlds leading minicomputer manufacturer, has asked us to look for a Pncipal Hardware Engineer. A degree and 10 years experience, 6 in computer related design, are required.

digital

To be considered for this and other important career positions all you need to do is post the coupon today to Stuart Tait, The Lansdowne Appointments Register, Park House, 207 The Vale, London W3 7QB. Tel: 01-743 6321 (24 hr answering service).

All posts are open to men and women and our service is completely confidential for companies and jobseekers.

(1978)

The Lansdowne Appointments Register

ARTICLES FOR SALE

Obsolete stock of three MFE 6-channel Heat-type Strip Chart Recorders plus 30 12v DC Solenoid Valves. - Ring 0788 61638. (1996)

EX WD Radio equipment and test equipment. Over 500 sets in stock from £8. Send 50p for illustrated catalogue (including £1 voucher). Weirhead Ltd. 129 St. Albans Road, Watford, Herts. Tel: Watford (0923) 49456. (1974)

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC. LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc. ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE

TELEPHONE: 445 0749/445 2713

BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, North Finchley, London, N.12
(5 minutes from Tally Ho Corner)

(1613)

SITUATIONS VACANT

شركة أبوظبي العاملة في المناطق البحرية (أدما-العاملة)
 Abu Dhabi Marine Operating Company (ADMA-OPCO)

OIL COMPANY REQUIRES ARAB TELECOMMS PERSONNEL TO WORK IN THE UNITED ARAB EMIRATES IN ONSHORE AND OFFSHORE LOCATIONS AGE RANGE 25-45 YEARS

A long-established major oil company operating in the United Arab Emirates is seeking to augment its employees to meet its expanding needs by the recruitment of a number of Telecommunications Engineers and Technicians to work in a wide range of disciplines.

ENGINEERS should have a Degree or qualification in Telecommunications, with at least five years' experience in a large communications organisation in the installation and repair of some of the following:

Tropospheric Scatter equipment; Microwave Radio Relay; FDM/TDM Multiplex; MF, HF, VHF, and UHF Radio; Telephone Exchanges using stored programme control.

TECHNICIANS should have Part II City and Guilds Telecommunications Certificate or equivalent with at least three years' relevant experience.

SALARY will depend on relevant experience, but in the following ranges:

ENGINEERS: Dh. 94,100/- to Dh. 116,300/- per annum.
TECHNICIANS: Dh. 81,800/- to Dh. 101,300/- per annum.
 £ is approximately 6.2 Dh.

OFFSHORE POSTING (Das Island and Platforms) will be on bachelor status with free messing and accommodation with generous leave scheme.

ONSHORE POSTINGS (Abu Dhabi town) will be on bachelor or married status with free furnished accommodation.

The United Arab Emirates is a rapidly developing country. The capital, Abu Dhabi, is a modern city offering a full range of sports and social facilities. Primary and secondary schools are available.

APPLICATIONS with CVs and copies of educational and experience certificates should be sent to both:

Senior Personnel Officer (CPA)
 ADMA-OPCO
 Abu Dhabi
 United Arab Emirates

Department of Petroleum
 P.O. Box 9
 United Arab Emirates

More information can be obtained from Snr. Personnel Officer (CPA) on request. Priority in employment will be given to UAE Nationals.

(1997)



ARTICLES FOR SALE

PRINTER STANDS and TRAYS



HANDSOMELY CRAFTED IN 6mm TINTED PERSPEX
 ★ PSS for Microline 80/82/83, Epson MX80, Sheiksha GP100, etc.
 £16.95 + £3.50 p.p. + V.A.T.
 ★ PSL for Microline 84, Epson MX82/100, etc.
 £19.95 + £3.50 p.p. + V.A.T.
 ★ POT Tray for Fanfold paper up to 12in. long per fold
 £16.95 + £3.50 p.p. + V.A.T.



CAMBRIDGE
 MICROELECTRONICS LTD
 One Milton Road, Cambridge
 CB4 1UY
 (0223) 314 814 (1785)

PCBS & PANEL LABELS to your requirements. Design - Prototypes - Production. G. N. Slee Custom Products, 78 Derry Grove, Thurnscoe, Rotherham, Yorks SG3 0TP. Telephone (0709) 89525. (1892)

INTEGRATED 30+30 WATT STEREO AMPLIFIERS. Small quantity of full spec ILP HY6-6HY60 fully packaged amplifiers for sale. Size 11 x 8 x 2.5", complete with volume/tone/balance controls, £75 delivered. Send s.a.c. for particulars. Martin Welsh, Glassel Lodge, Banchory, Kincardineshire AB3 4DD. (2015)

PROTOTYPE PLASTIC CASINGS, vacuum formed to your requirements. Four-D Ltd., 25 Burnett Park, Harlow, Essex. Phone 0279 29246. (1725)

BILLINGTON VALVES

We are an established Valve and vintage service. No one should miss our new valve list (1,000 types) available on receipt of an SAE.

Our speciality is the supply of rare/extinct vintage radio valves, we also have huge stocks of 'industrial' valves. Every popular type listed at competitive prices.

We are keen to clear the following and have reduced our retail list price. Trade/bulk inquiries invited.

3B28, 4CX250B, 5B/254M, 5B/255M, 5R4, 6BH6, 6CH6, 6F11, 5F12, 6F33, 10F18, 12E1, 19H4, 19H5, CV4024, DA42, DET22, EB91, EC91, ECC81-2-3 high quality, EF37A, EF92, EY84, G232, G237, G1802M, KT66, OA2WA, PCC189, QV2-250C, S11E12, UL41.

Used and high quality versions available. We also stock transistors. Trade/bulk inquiries only stating specific requirements.

Please send 10p + SAE for our clearance list of radio components. Mailing address only (no callers): BILLINGTON VALVES, 23 Irwin Drive, Horsham, W. Sussex RH12 1NL

Special Offer: New 12E1 valve £16.40 plus 40p post. (1992)



TRACKBALL!

At last! A Trackball unit to add to ANY computer. The unit incorporates a high quality ball assembly and has self-contained logic. A standard TTL level interface with handshaking is provided, RS232C available as an option. Encoded 8 key pad option available giving 3/8 code.

Pricing: Basic Unit £129; RS232 option £20
 Encoded 8 Key Pad £30

SEA for further details to: PIXEL-PLUS, 2 Lupin Close, Hinckley, Leics. LE10 2UJ. Tel: 0455 635621 (1980)

The VINTAGE WIRELESS COMPANY

NOSTALGIA - COLLECTING
 1900-1950s
 Publishers of The Antique Wireless Newsheet (Sample on Request)



Suppliers of: Valve Radio sets & Amplifiers
 • Valves, Components
 • Repairs & Restorations
 • Service Data & Manuals
 • Historical Data
 • New and Used Books/Magazines

The complete service for the collector and enthusiast of Vintage Radio
 THE VINTAGE WIRELESS COMPANY
 94 Broad Street, Staple Hill, Bristol BS16 5NL
 Tel Bristol 0272 565472. 24 hour Ansaphone Closed Mondays. (1977)

ARTICLES FOR SALE

THE SCIENTIFIC WIRE COMPANY

P.O. Box 30, London, E.4
 ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	.80	.60
30 to 34	3.20	1.80	.90	.70
35 to 40	3.40	2.00	1.10	.80
41 to 43	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.50	6.30	3.69

SILVER PLATED COPPER WIRE
 14 to 30..... 6.50 3.75 2.20 1.40

TINNED COPPER WIRE
 14 to 30..... 3.30 2.36 1.34 .90

Prices include P&P, VAT and Wire Data. SAE for list. Dealer enquiries welcome.
 Reg Office: 22 Coningsby Gardens (90631)

RIBBON CABLE, PLUGS AND CONNECTORS

The very best quality. Proven manufacturer. Plugs and connectors sold singly or in quantities. Cable sold by the metre or by the roll.

Ring or write:
 T.A.D. SUPPLIES
 5-10 Eastman Road
 London W3
 Tel: 740 0058 (1840)

LINSLEY HOOD DESIGNS

75-100w AMPLIFIERS
 AUDIO SIG. GENERATORS
 DISTORTION ANALYSERS
 SAE for leaflets

TELERADIO ELECTRONICS
 325 Fore St., Edmonton N9 0PE
 TEL: 807 3719 (1762)

ARTICLES WANTED

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, and quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO

86 Bishopgate Street
 Leeds LS1 4BB
 0532 35649

WANTED

Scrap and re-usable mainframe computer and industrial electronic equipment.

E.M.A. Telecommunications Engineers, Orford, Woodbridge, Suffolk. Tel. 039-45 328. (1720)

SURPLUS

Top prices paid for surplus, redundant and obsolete test equipment, factories cleared.

Also quantities of components. Immediate settlement. We will call anywhere in the United Kingdom.

TIMEBASE
 94 Alfriston Gardens
 Shelling, Southampton SO2 8FU
 Telephone: (0703) 431 323 (1852)

WANTED


Redundant/surplus electronic components and equipment. Telephone and computer spares.

Prompt service and payment.

J. B. PATTRICK
 (Electronics)
 191/193 London Road
 Romford, Essex
 Romford 44473 (1979)

The world's most advanced low-cost bench multimeter

Thurlby 1905a £298+VAT

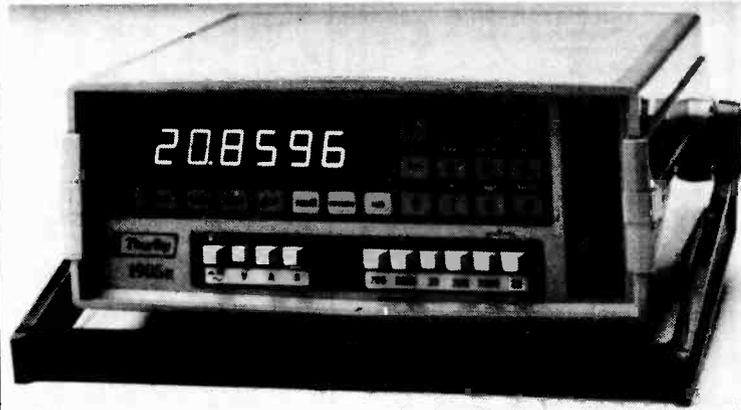

- A complete high performance bench DMM**
- 5½ digits; 0.015%; 1µV, 1mΩ, 1nA.
 - Full ac and current functions as standard
- A sophisticated computing and logging DMM**
- Linear scaling with offset; null/relative
 - Percentage deviation; running average
 - dBV, dBm, general logarithmic calculations
 - Limits comparison; min and max storage
 - 100 reading timed data logging

Thurlby Electronics Ltd
 Coach Mews, St. Ives, Cambs. PE17 4BN
 Tel: (0480) 63570

Thurlby 
 designed and built in Britain

WW - 044 FOR FURTHER DETAILS

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 110-119

	PAGE		PAGE		PAGE
AFDEC Electronics	105	Galatrek International Ltd.	4	Pantechnic	102
All Electronics Show	22, 23	Global Specialities Corp. (UK) Ltd.	9	PM Components	102, 103
Ambit International	19	GP Industrial Electronics Ltd.	16, 17	P. & R. Computer Shop	94
Analogue Associates	2			Radford Laboratory Instruments Ltd.	20
Armon Electronics Ltd.	98	Hall Electric Ltd.	21	Radio Component Specialists	95
Audio Electronics	15	Hameg Ltd.	91	Radio Society of G.B.	9
Avel Lindberg (Cotswold Electronics)	96	Happy Memories	88	Ralfe, P. F. Electronics	20
		Harris Electronics (London)	13	Reprints	102
Bamber, B. Electronics	100	Harrison Bros.	4	Research Communications Ltd.	25
Barrie Electronics Ltd.	105	Hart Electronic Kits Ltd.	109	Robot (UK) Ltd.	88
Black Star Ltd.	89	Hemmings Electronics and Microcomputers	96	RST Valves	85
Branson, S. J.	98	Henry's Radio	24, 100	Sagin, M. R.	4
Broadfield & Mayco Disposals	109	House of Instruments Ltd.	19	Sandwell Plant Ltd.	14
				Sche Tronics Ltd.	86
Cambridge Kits	89	ILP Electronics Ltd.	6, 7, 87	Scopex Instruments Ltd.	97
Carston Electronics	Loose Insert	Integrex Ltd.	25	Seasim Controls Ltd.	94
Chiltern Electronics	90	Interface Quartz Devices Ltd.	14	Service Trading Co. Ltd.	89
Circuit Services	13			Seyker Ltd.	24
Clef Products (Electronics) Ltd.	14	Keithley Instruments	13	South Midlands Communications Ltd.	96
Compec Wales	107			Sowler, E. A. Ltd.	84
Crimson Elektrik	91	Langrex Supplies Ltd.	85	Special Products (Distributors) Ltd.	20
C. T. Electronics (Acton)	89, 97, 99	L. J. Electronics Ltd.	12	Stewart of Reading	84
				Surrey Electronics Ltd.	86
Danavox (Gt. Britain) Ltd.	101	Magenta Electronics	20	Technomatic Ltd.	92, 93
Display Electronics	106	Maplin Electronic Supplies	Cover iv	Television Magazine	90
		Marconi Communication Systems	90	Texas Books	98
Easibind Ltd.	86	Microprocessors & Microsystems	86	Thander Electronics	26
Eddystone Radio Ltd.	18	Middle East Wire & Wireless	8	Thanet Electronics	87
Electrical Review Shock Cards	108	Midland Computer Fair	56	Thurlby Electronics (Reltech Instruments)	24, 120
Electronic Brokers Ltd.	3, 5, 54, 55	Midwich Computer Co. Ltd.	15	Timebase Ltd.	87
Electronic Equipment Co.	100			Time Electronics Ltd.	108
EMAP (Electronics & Computing Monthly)	83	Northern Amateur Radio	109	T. O. Supplies (Export)	2
Essex Electronics Centre	88			Valradio Ltd.	102
		Olson Electronics Ltd.	18	Vigilant Communications Ltd.	14
Farnell Instruments	Cover iii	Opus Supplies	84	Watford Electronics	10, 11
Fylde Electronic Laboratories Ltd.	94	Oric Products International Ltd.	Cover ii	White House Electronics	24
		Orion Scientific Products Ltd.	94	Wireless World Competitions	104
				Xtec Ltd.	12

OVERSEAS ADVERTISEMENT

AGENTS:

France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Mrs Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget.
 Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
 Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106.
 Telephone: (03) 585 0581.

United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080, Telex: 238327.

Mr Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.

Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1919.
 Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
 Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305, Telephone: (404) 237 7432.
 Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.

Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.

* Also subscription agents.

Directional power meter TM10

leads by a head



For colour brochure contact:

FARNELL INSTRUMENTS LIMITED
WETHERBY LS22 4DH
TELEPHONE (0937) 67961
TELEX 557294 FARIST G



Farnell

- Single detector head covers wide frequency and power band
- 25MHz to 1GHz ■ 20mW to 100W and VSWR from 1 to 3
- Head can be used 1.5m from meter (e.g. inside closed car boot)
- Fully portable – works from internal battery or vehicle battery
- Mains adaptor/charger and rechargeable battery available
- Manufactured, tested and inspected to Min. Def. Std. 0524.



WW-002 FOR FURTHER DETAILS

TRADE PRICES

from

MAPLIN

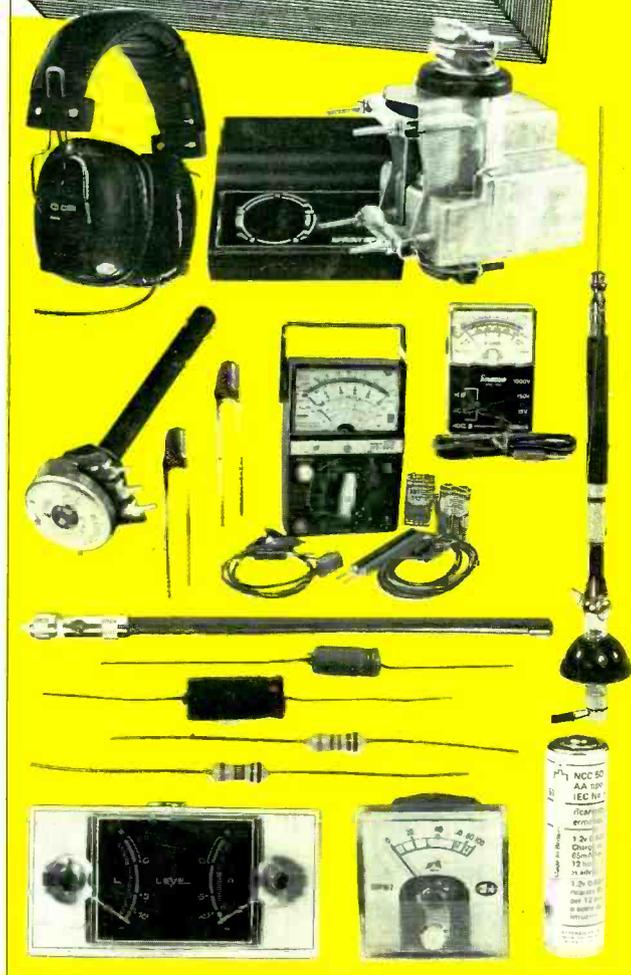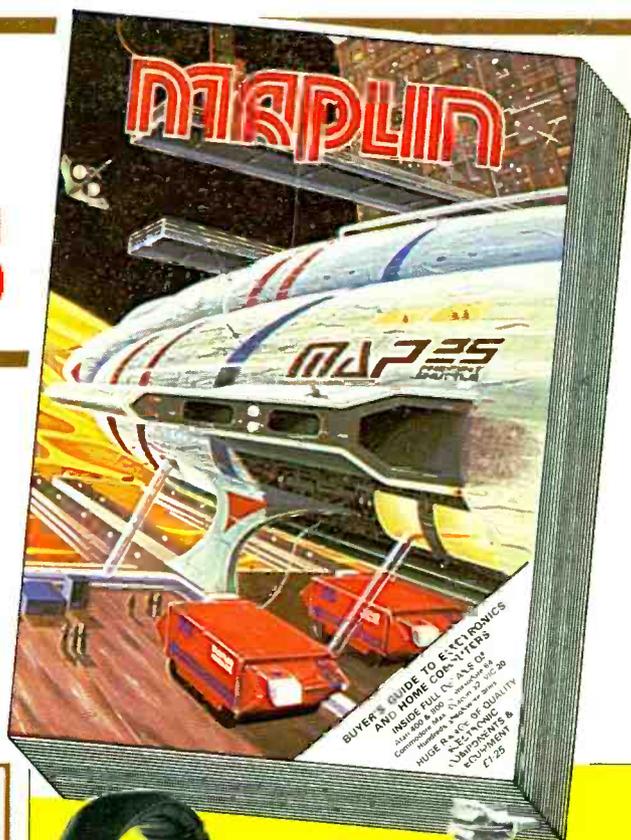Look at these examples
from our huge range.



Copies of our catalogue are available in all branches of W.H. Smith, price £1.25. In case of difficulty, send £1.50 to our mail-order address. Overseas price £1.90.

Maplin Electronic Supplies Ltd.

All mail to P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel. (0702) 552911.
Shops at 159 King St., Hammersmith, W6. Tel. 01-748 0926.
Lynton Square, Perry Barr, Birmingham. Tel: 021-356 7292.
284 London Road, Westcliff-on-Sea, Essex. Tel. (0702) 554000.
Shops closed all day Monday.

WW/3/83

Code	Description	Cat. Page	Retail Price Incl. VAT	Min. Trade Qty.	Price Each for Min. Tr. Quantity excl. VAT
XB54J	Aerial Rotator	25	£39.95	5	£29.00
YG00A	Ni-Cad AA 500mAh	26	£1.25	50	75p
FB15R	Electrolytic 2.2uF 63V	90	10p	500	4.5p
FB22Y	Electrolytic 10uF 25V	90	9p	1000	3.5p
FB49D	Electrolytic 100uF 25V	90	14p	500	6.5p
FB73Q	Electrolytic 470uF 25V	90	30p	250	12p
FB83E	Electrolytic 1000uF 25V	90	40p	250	17p
FB96E	Electrolytic 4700uF 25V	90	£1.25	50	58p
YG41U	27MHz Rubber Duck	99	£4.75	25	£2.95
XG13P	1.5m CB Aerial	99	£13.95	5	£8.45
LB72P	2-Station Intercom	102	£8.75	10	£4.95
HF85G	1/4in. Jack Plug plastic barrel	142	19p	500	9p
HF88V	1/4in. Jack Plug stereo plastic barrel	142	28p	250	15p
HF87U	1/4in. Jack Plug metal barrel	142	39p	250	18p
HF89W	1/4in. Jack Plug stereo metal barrel	142	45p	250	22p
RW67X	13A nylon Mains Plug British	157	79p	100	45p
WL27E	LED 0.2in. Red	182	12p	500	6p
WL28F	LED 0.2in. Green	182	19p	500	10p
WL29G	LED 0.2in. Orange	182	33p	250	19p
WL30H	LED 0.2in. Yellow	182	17p	500	9p
RK07H	Panel Meter 100uA	197	£2.95	25	£1.95
RK09K	Panel Meter 1mA	197	£2.95	25	£1.95
RK19V	Panel Meter VU	197	£2.95	25	£1.95
YQ47B	Dual VU Meter	197	£3.90	25	£2.30
YR84F	Professional Plugblock	201	£6.95	10	£4.95
RX96E	20mm Fuse Holder	250	45p	250	24p
M10R-M1M	Metal Film 0.4W 1% Resistor	262	2p	1000	1p
FW00A-FW09K	Rotary Potentiometers linear	265	45p	250	32p
FW21X-FW29G	Rotary Potentiometers log	265	45p	250	32p
QL80B	1N4148	270	4p	1000	2p
QL22Y	741C 8-pin DIL	270	23p	500	12p
QH66W	NE555	270	21p	500	12p
QQ06G	4164 64K dynamic RAM	271	£5.99	100	£3.84
BL18U	DIL Socket 14-pin	336	11p	500	7.5p
BL17T	DIL Socket 8-pin	336	9p	1000	4.5p
WF14Q	Stereo Headphone with slide volume controls	342	£7.99	10	£4.95
FH00A	Sub-min Toggle Switch SPDT	347	70p	100	45p
FH04E	Sub-min Toggle Switch DPDT	347	99p	100	59p
FF73Q-FF76H	Rotary Switch break before make	348	74p	100	46p
FH42V-FH45Y	Rotary Switch make before break	348	70p	100	42p
YW93B	1000 ohm per volt Multimeter	362	£4.85	25	£2.95
YW68Y	20,000 ohm per volt Multimeter with Transistor Tester	363	£16.25	5	£10.45
BR75S	Box-joint Insulated 4 1/2in. Cutters	370	£6.93	10	£4.45
BR78K	Box-joint Insulated 4 1/2in. Pliers	371	£5.72	10	£3.95

Retail prices guaranteed until 12th February 1983. Quantity prices shown are subject to change without notice. Please check with us before ordering.

Most items in our catalogue are available at competitive trade prices; the bigger the quantity the better the price. If you find the example prices attractive, then contact us now with your requirements for a quotation. Phone Southend (0702) 552911 or write to us at P.O. Box 3, Rayleigh, Essex, SS6 8LR. Please ask for trade sales desk.