

FOR EVERYTHING IN ELECTRONICS

Wireless World

APRIL 1983

80p

**Viewdata
display
module**



Eprom single-chip microcomputers
Digital tape timer
Amateur satellite tracking

Australia A\$ 2.70
Canada C\$ 3.25
Denmark DKR. 33.25
Germany DM. 7.00
Greece DRA. 190.00
Holland DFL. 8.50
Italy L 3700
New Zealand NZ\$ 3.00
Norway NKR. 26.00
Singapore M\$ 5.50
Spain PTS 275.00
Switzerland FR. 7.00
U.S.A. \$ 3.75

The PSG520H



a small, lightweight
synthesized signal generator
for field or bench use

*Colour brochure available.
Send for yours now.*

100kHz to 520MHz

Runs from clip-on NiCd battery pack, external 12Vd.c.
(vehicle battery via cigar lighter socket) or,
from any standard a.c. mains supply

Reverse power protection to 50W (standard)


Excellent specification and features

from



Farnell

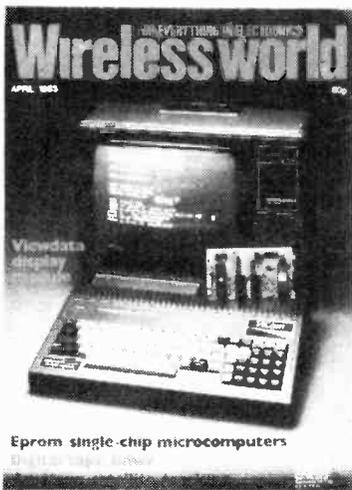FARNELL INSTRUMENTS LIMITED · WETHERBY · WEST YORKSHIRE LS22 4DH · TELEPHONE (0937) 61961 · TELEX 55478 FARINT G
REGIONAL OFFICE (SOUTH) · DAVENPORT HOUSE · BOWERSWAY · HARPENDEN · HERTS. AL5 4HX · TEL. (05827) 69071 · TELEX 826307
W W-001 FOR FURTHER DETAILS



Eprom single-chip microcomputers
Single-chip microcomputers

Cover shows viewdata display module described in this issue together with ViCom experimental videotext computer by Deaconhouse Ltd. ViCom executes telesoftware which is first captured in the ram that forms part of the videotext display module that could be located in ViCom or the tv receiver.

NEXT MONTH

A microcomputer using the structured language Forth, and rapid data storage and retrieval on floppy disc. Standard disc drives are used.

Decoder for receiving data and television pictures from the amateur television satellite UOSAT. Cleans up weak signals for display on television screen.

Digital voltmeter module for microcomputers, monitoring voltages at eight points and providing an alarm signal if set limits are exceeded.

Accelerometer intended for use in cars but with many other uses - precision levels, earthquake detector, heel indication for yachts and intruder alarms.

Current issue price 80p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.23, back issues (if available) £1.80, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS Tel: 01-661 8668.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3614. Advertising 01-661 3130. See leader page.

Telex: 892084 BISPRS G.

Subscription rates: 1 year £14 UK and £17 outside UK.

Student rates: 1 year £9.35 UK and £11.70 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3248.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone: 0444 59188. Please notify a change of address.

USA: \$44 surface mail, \$98.30 airmail. Business Press International, Subscriptions Office, 205 E.42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd class postage paid at New York.



© Business Press International Ltd 1983
ISSN 0043 6062.

FOR EVERYTHING IN ELECTRONICS Wireless world


APRIL 1983

VOL 89 NO 1567

-
- 27** **KNOW-HOW: RESOURCE OR PROPERTY?**
-
- 28** **TRACKING SATELLITES WITH A MICROCOMPUTER**
by I. P. Jefferson
-
- 32** **HIGH-IMPEDANCE ELECTRONICS**
by R. D. Purves
-
- 34** **EPROM SINGLE-CHIP MICROCOMPUTERS**
by M. D. Bacon
-
- 38** **VIEWDATA DISPLAY MODULE**
by D. N. Pim
-
- 42** **COOLING ELECTRONIC EQUIPMENT**
by M. Young
-
- 43** **COMMUNICATIONS**
Meteor-trail bouncer Terman legacy CB interference
-
- 45** **LETTERS TO THE EDITOR**
Logic maps Michelson-Morley Deus ex machina
-
- 49** **CIRCUIT IDEAS**
Op-amp tester Synchronous detector ZX81 monitor
-
- 55** **NEWS OF THE MONTH**
RF hazards Sat/network Superconducting transistor
-
- 58** **DIGITAL TAPE CLOCK**
by Per C. Andersen
-
- 60** **HAZINESS AND ITS APPLICATIONS**
by W. A. Scott Murray
-
- 63** **ASSEMBLY LANGUAGE PROGRAMMING**
by R. F. Coates
-
- 67** **PEAK-TO-PEAK BAR/DOT INDICATOR**
by A. J. Ewins
-
- 69** **TWO-METRE TRANSCEIVER**
by T. D. Forrester
-
- 72** **COMPETITION**
Design an electronic aid for the disabled
-
- 73** **IN PRAISE OF SOFTWARE**
by H. D. Baecker
-
- 74** **IBM SELECTRIC-TO-TRS80 INTERFACE**
A. T. Scarpelli
-
- 80** **NEW PRODUCTS**
Caesium standard Industrial computer Disc control
-
- 82** **RANDOM ECHOES**

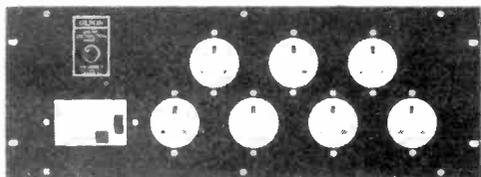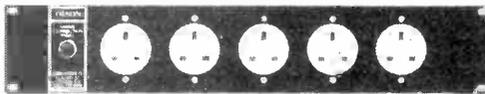

**V
E
R
T
I
C
A
L**

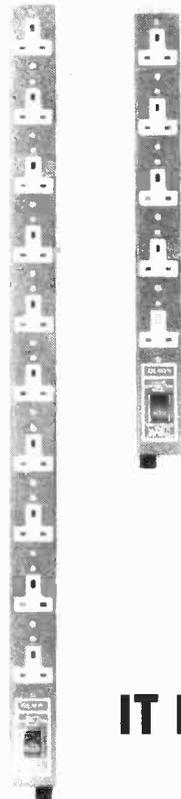

**WHEN
IT COMES
TO POWER
FOR RACKS
IT MUST BE OLSON**

HORIZONTAL OR


**VERTICAL RANGE FROM 3-10 SOCKETS
ALL EX-STOCK!
SPECIALS TO ORDER**

OLSON ELECTRONICS LIMITED

**5-7 LONG STREET LONDON E2 8HJ
TEL: 01-739 2343 TELEX 296797**

WW - 027 FOR FURTHER DETAILS

METER PROBLEMS?

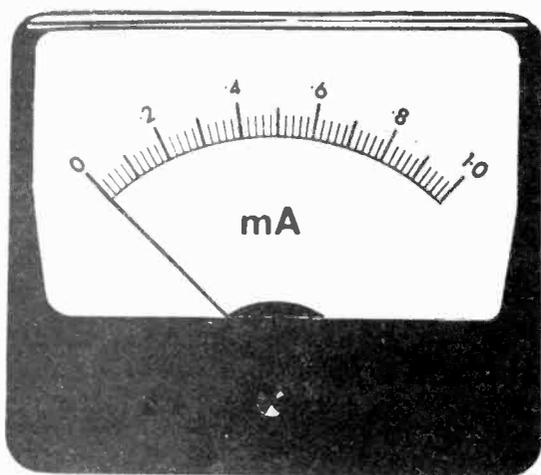

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)
138 GRAY'S INN ROAD, W.C.1 Phone: 01-837 7937
Telex: 892301 HARTRO G

WW - 015 FOR FURTHER DETAILS



XLR CONNECTORS

Line Female A3F £1.59 Chassis Female D3F £2.04
Line Male A3M £1.36 Chassis Male D3M £1.19

4, 5, 6 and 7-pin versions and large selection audio adaptors available



NEUTRIK

XLR CONNECTORS

Latchless Chassis NC3-FZ £0.67 Latchless Chassis Male NC3-MZ £0.59
Line Female NC3-FCC £1.34 Line Male NC3-MC £1.15
Female Chassis NC3-FP £1.85 Chassis Male NC3-MP £0.87

4, 5-pin, PCB and black versions and large selection of audio adaptors available


XLR LNE MAIN SERIES

XLR LNE 11C £3.87 XLR LNE 12C £3.76
XLR LNE 32 £2.89 XLR LNE 31 £4.14

BELCLERE AUDIO TRANSFORMERS

EN6422 Retro + 1.2 + 2 Freq. 40MHz-35KHz. PRI 150/600Ω, sec. 600/2.4KΩ £4.15
EN6423 Ratio 1 + 1:6.45 + 6.45. Freq. 40Hz - 25KHz. PRI 150/600Ω, sec. 6.25K/25KΩ £4.15
SKT-723 MuMetal Screening can, 39dB reduction 50Hz ext. field £1.30

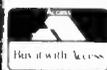Trade enquiries welcome: quantity discounts available. All prices subject to V.A.T. Call, write or telephone. Minimum order £10. Please add £2 postage. Access, Amex, Barclaycard.




KELSEY ACOUSTICS LTD.

28 POWIS TERRACE, LONDON W11 1JH
01-727 1046/0780



WW - 059 FOR FURTHER DETAILS

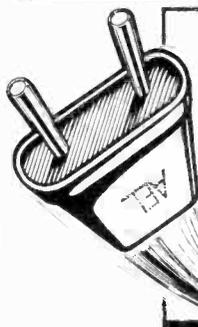

**AEL
AT
SPEED**

TO BE CRYSTAL CLEAR

Tel. 029-34-5353 Telex 87116 Aero G
MOD approved CAA approved

WW - 034 FOR FURTHER DETAILS

upgrade to an ORIC-1



**16 colours
professional
keyboard
full graphics
real sound**

- Superb styling
- Choice of 16K, or 48K RAM
- Ergonomic keyboard with 57 moving keys
- 20 rows x 40 characters high resolution
- Teletext/viewdata compatible graphics
- 6 octaves of real sound plus Hi-Fi output
- Centronics printer interface and cassette port
- Comprehensive user manual

FOR HOME, EDUCATION, BUSINESS & ENTHUSIASTS.

OPTIONAL MODEM OFFERS COMPUTERPHONE LINK FOR ELECTRONIC MAIL ● TELESOFTWARE ● PRESENT
COMING SOON, TO COMPLETE YOUR SYSTEM: ORIC MICRO-DRIVE DISCS & SPEED PRINTER

FROM
£99.95
incl VAT

ORIC is no toy! Its professional keyboard, basic language and extensive specification, will do all you expected of your home computer, plus a whole lot more. For home, educational, business and games use.

If you're buying for the first time beware! Only ORIC computers offer full colour capability for under £100 and the most powerful and comprehensive micros in their price brackets.

So whether you're just starting out, or upgrading existing equipment, make the professional decision and choose ORIC. Send for our comprehensive brochure NOW, or better still, order your ORIC today.

Delivery is around 28 days with a money back guarantee if you're not delighted.

Clip the coupon below, or call our telesales number ASCOT (0990) 27641.

ORIC-1

DISC-DRIVE & PRINTER available soon

The Real Computer System

WW - 02 FOR FURTHER DETAILS

ORIC PRODUCTS INTERNATIONAL LTD

Coworth Park Mansion, Coworth Park, London Road, Sunninghill, Ascot, Berks SL5 7SE

Prices	ORIC-1 16K RAM	£ 99.95	
Include	ORIC-1 48K RAM	£169.95	
VAT	ORIC Communications Modem	£ 79.95	
	Postage and Packing		£ 5.95
	TOTAL		£

*Please delete/complete as applicable.
*I enclose a cheque/ P.O. payable to: ORIC PRODUCTS INTERNATIONAL LIMITED for £_____

Name _____
Address _____

Please charge my Access, Barclaycard, Amex, Diners Club account no.

If you require a brochure please tick

WW 4

© Copyright ORIC PRODUCTS INTERNATIONAL 1982

HEMMINGS ELECTRONICS AND MICROCOMPUTERS

16 BRAND ST
HITCHIN
HERTS
SG5 1JE

Tel: (0462) 33031
Shop open Mon.-Sat. 9 a.m.-5.30 p.m.
Closed all day Wednesday



Professional quality electronic components, brand new and fully guaranteed. Mail order by return of post. Cash/Cheque/POs or Banker's Draft with order, payable to Hemmings Electronics Ltd. Official orders from schools, colleges and universities welcome. Trade and export enquiry welcome. P.&P. add 45p to all orders under £10. Telephone for Access orders, using our 24-hr. Ansaphone service. Please send SAE for full price list.

VAT - All prices exclusive of VAT - Please add 15% to total cost including P.&P. No VAT on export orders or books.

COMPUTER

ICs	AY-3-8910	435p
6502	AY-3-8912	820p
6522	AY-5-1230	450p
6800	709	35p
6800	741 8 pin	25p
6800	741 14 pin	25p
6809E	741S	55p
6810	747	95p
6821	748	35p
6821	CA3080E	70p
6840	CA3130E	75p
6840	LA4422	295p
6844	LF355	80p
6845	LF356	90p
6852	LM307	100p
6852	LM301A	28p
6854	LM307	50p
6875	LM308A	95p
8T26A	LM311N	66p
8T28	LM324	35p
8T95	LM339	50p
8T96	LM348	50p
8T97	LM358	60p
8T98	LM380	95p
8035L	LM381	150p
8039L	LM393	90p
8080A	LM3909	95p
8085A	MC1310P	210p
8155	MC1455	65p
8212	MC1456	135p
8216	MC1458	35p
8224	MC3242A	630p
8226	MC3302	95p
8228	MC3340	120p
8243	MC3401	85p
8251	MC3403	70p
8253	MC3456	107p
8255	MC3480	580p
8257	MC34001	58p
8259	NE555	16p
8279	555CMOS	90p
75451	NE556	55p
75452	NE565	155p
75491	NE567	140p
75492	TA7205A	125p
75493	TA84800	175p
AY-3-1015D	TBA5300	140p
AY-5-1013A	TBA5400	130p
MC1408	TBA5500	280p
MC1488	TBA5600C	160p
MC1489	TBA750	280p
MC3459	TBA800	90p
Z80ACPU	TBA820	95p
Z80APIO	TBA820M	85p
Z80ACTC	TBA920	190p
Z80ADART	TBA990Q	190p
	TC650	390p
	TC910	180p
	TD1004	290p
2114L	TL061	40p
2708	TL062	60p
2716	TL064	98p
2532	TL071	30p
2732	TL072	50p
4116	TL074	100p
4164	TL081	25p
6116	TL082	45p
6116L	TL084	95p
	UPC575	149p
	UPC1167	158p
	UPC2002V	285p
AY-3-1270	UPD7002	450p
AY-3-1350	ZN414	100p

MEMORIES

2114L	90p
2708	220p
2716	210p
2532	380p
2732	380p
4116	85p
4164	500p
6116	390p
6116L	480p

LINEAR ICs

AY-3-1270	725p
AY-3-1350	350p

LIQUID CRYSTAL DISPLAY MODULES

PCIM177 Frequency Counter
5 Digits, 0.35" FM, SW, MW, MHz, KHz Annunciators
Sample and Hold Capability
Reset Capability
25 Selectable IF Offsets
Prescaler Available
Incandescent Backlighting
Supply Voltage 5v
Operating Current 4mA

£17.15

PCIM 176 Digital Meter Module
3 1/2 digits, 0.5"

+/- and Decimal Point
200mV Full Scale Input
True Differential Input
Guaranteed '0' Reading
Single 9v Operation
Power Consumption 20mW
Accuracy 0.15%, +/- 1 Count
Temperature drift 80ppm/C
Low Battery Indication
Incandescent Backlighting

£22.50

All modules are supplied with Data Sheet.

FIBRE OPTIC POLYMER CABLE

A 10m coil of 1mm core optical fibre cable sheathed in black polyethylene for protection £4.95

8" FLOPPY DISK DRIVES

Secondhand, manufactured by CDC 400K B1E SSSD perfect condition with data

Only £90 inc. VAT Carriage £3

CONNECTORS

BNC SERIES		
Free Plug 50 ohm		83p
Chassis Socket 50 ohm		74p
"D" fixing hole		
"D" TYPE		
Male Female		
Hoods		
Top		
Entry		
9 way	90p	110p
15 way	130p	155p
25 way	180p	210p
37 way	220p	270p
(Wire Wrap)		
37 way Female		270p
(IDC Type)		
25 way Male		450p
25 way Female		500p

DC CONNECTORS		
Plug 2.1mm, 2.5mm or 3mm.		
Short or Long Reach		20p
Socket 2.1mm or 2.5mm		20p

DIN SERIES			
Line	Line	Chassis	
Plug	Socket	Socket	
2 pin	10p	10p	9p
3 pin	15p	21p	21p
4 pin	18p	21p	21p
5 pin 180	20p	21p	21p
5 pin 240	20p	21p	21p
5 pin 360	20p	21p	21p
6 pin	20p	22p	22p
7 pin	22p	22p	24p

EUROCARD DIN 41612

2x32 WAY		
	2 Row	3 Row
Socket	290p	290p
Socket (IDC)	450p	500p
Plug (Solder)	195p	195p
Plug (W/wrap)		320p

IC SOCKETS

Low Profile	Wire Wrap	Turned Pin	
8 pin	9p	30p	28p
14 pin	10p	38p	35p
16 pin	11p	45p	38p
18 pin	12p	50p	45p
20 pin	13p	60p	70p
22 pin	14p	70p	70p
24 pin	15p	80p	53p
28 pin	18p	95p	67p
40 pin	30p	120p	102p
Zero Insertion Force Socket	24 pin	550p	
	40 pin	750p	

IDC (SPEEDBLOCK TYPE)

Header	Socket with Strain Relief
10 way	90p
20 way	140p
26 way	175p
34 way	200p
40 way	220p
50 way	240p

ALFAC ETCH RESIST TRANSFERS

Make your own Printed Circuit Boards with our PCB transfers.
★ Draw your artwork on 0.1" grid
★ Transfer to copper board using carbon paper
★ Burnish the Alfac transfers to the board using a spatula using carbon marks to assist in accurate alignment
★ Use Alfac chemical eraser to correct mistakes
★ Etch in Ferric Chloride

EC900/1 0.1" Edge Connector	
EC902/1 0.156" Edge Connector	
EC940 0.016" Lines	
EC941 0.031" Lines	
EC942 0.039" Lines	
EC943 0.049" Lines	
EC944 0.061" Lines	
EC945 0.079" Lines	
EC946 0.100" Lines	
EC947 0.124" Lines	
EC950/1 0.031" 90° Bends	
EC950/2 0.061" 90° Bends	
EC952/1 0.031" 30°, 45°, 60° Bends	
EC952/2 0.061" 30°, 45°, 60° Bends	
EC908 0.063" Pads	195p
EC910 0.094" Pads	45p
EC911 0.189" Pads	40p
EC960/1 TD-5 Transistor Pads	
EC993/1 IC Pads	
EC997/1 IC Pads with tracks between pads	
5 identical sheets in sealed pack	
Individual sheets	45p
Spatula AR4 for burnishing	45p
Alfac knife	180p
Spare Blades (pack of 10)	280p
Alfac Eraser	280p
Alfac Precision Grids: Polyester film, matt finish 0.14mm thickness, 20 lines/in	
A3 199p A4 100p	
Double Sided Fibreglass Board 1/16" thickness, 1oz Copper	
5" x 4" 25p; 5" x 8" 45p	

MAINS CONNECTORS

Bulgin P551 8 Pin Plug	220p
Bulgin P552 8 Pin Socket	75p
Cassette Mains Lead 2m	
Reversible Connector	70p
Cassette Mains Plug	
Non-reversible	28p
IEC Chassis Plug 6A 250V	45p
IEC Cable Socket 6A 250V	66p
IEC Cable Socket with 2m Integral Lead	74p
MOLEX KK SERIES 0.1" PITCH	
Terminal Housing	
22-01-2025 2 Pole	5p
22-01-2035 3 Pole	6p
22-01-2045 4 Pole	6p
22-01-2025 5 Pole	7p
22-01-2065 6 Pole	8p
22-01-2075 7 Pole	9p
22-01-2085 8 Pole	9p
22-01-2095 9 Pole	10p
22-01-2105 10 Pole	11p
22-01-2125 12 Pole	12p
22-01-2155 15 Pole	14p
Crimp Contacts for Housings	
08-50-0136	3p
Pack of 100	190p
PCB Wafer Straight Square Pin	
22-03-2151 15 Pole	38p
PCB Wafer Right Angle Pin	
22-05-2151 15 Pole	50p
PHONO	
Plug Blue, Yellow, Red, Black 15 Pole	22p
Plug Screened	22p
Line Socket Blue, Yellow, Red, Black, White, Green	15p
Chassis Socket	25p
4 Way In-line Socket	30p
Socket/Socket Adaptor	25p
TEST PROBES (CLIP-ON)	
Pair Miniature Test Probes Spring Loaded Hook Grip	
Red/Black Length 55mm	80p
Length 90mm	100p
Length 135mm 210p	
UMF SERIES	
Free Plug PL259	50p
Reducer for 5.3mm Cable	15p
Reducer for 6.4mm Cable	15p
MISCellaneous	
Aerial Splitter Low Loss Non-resistive	120p
Surface Mounted Switched	140p
Car Power Plug Crocodile Clips	40p
Miniature Red or Black Standard	10p
FM Plug	20p
Power Plug 4 way 2.5mm, 3.5mm Jack, 2.1mm, 2.5mm, DC Connector	30p
Terminal Block 2A 12 way	20p
TV Coax Plug	20p
TV Coax Line Socket	45p

LIGHT EMITTING DIODES (LED)

3mm Red TIL209	10p
3mm Green LD37C	15p
Panel Clip	35p
3mm Chrome Bezel	4p
5mm Red COY40L	15p
5mm Green, Yellow	15p
Panel Clip	4p
5mm Chrome Bezel	42p
5mm Square Red	25p
Green, Yellow	30p
Tri-colour V51BP	70p
Red Flashing COX21	
3Hz at 5V	45p

INFRARED

TIL32 Emitter	54p
TIL38 Emitter	45p
TIL78 Phototransistor	54p
TIL100 Photodiode	70p

EPSON MX80F/T TYPE III PRINTER

80 Characters per Second, Friction and Tractor Feed, High Resolution 960 Dots/Line, Auto Underlining, Subscripts and Superscripts

£320 Securicor £8

GO FORTH AND MULTIPLY

much quicker with the JUPITER ACE Available from stock £89.95 inc. VAT

VIC-20 COLOUR COMPUTER

★ SPECIAL OFFER ★

VIC-20 Colour Computer
C2N Cassette Deck
Programmers Reference Guide
Games Tape
Demonstration Tape
10 Blank Cassettes
VIC Computing Magazine
£195 inc. VAT Securicor £8

50+ CASES FOR SPECIALISTS referred by JENSEN



JTK 16

Designed for the professional electronic technician requiring a complete set of tools in a compact package

50 professional tools. VOM Test meter optional. Also available with metric tools (JTK16mm).

See these cases together with more than 20 other complete specialist tool kits and a complete range of over 30 empty cases in the Jensen catalogue available on request from:


Special Products Distributors Limited
81 Piccadilly, London W1V 0HL

Tel. 01-629 9556 Cables: Speciproduct, London, W. 1

WW - 050 FOR FURTHER DETAILS



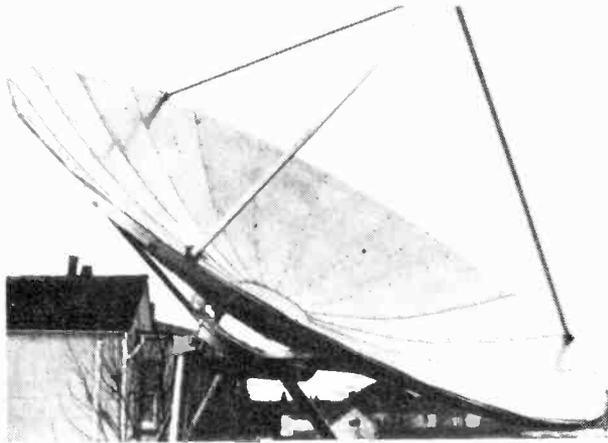6FT. PARABOLIC DISHES FROM ONLY £85 PLUS V.A.T.



6ft. dia. dishes, feed horns and electronics for use in 4GHz satellite reception. GaAs Fet transistors, SMA connectors, P.T.F.E., etc. available. Please send s.a.e. for full details and data sheets.

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX
Tel. Southend (0702) 332338

WW - 029 FOR FURTHER DETAILS

WW - 046 FOR FURTHER DETAILS

The QUAD 34



Provides everything
that the serious music
listener needs to obtain
maximum enjoyment from disc,
radio, tape and compact disc
at the standard of quality
for which QUAD has been
famous for more than
thirty years.

QUAD 
for the closest approach
to the original sound

For further details and the name and address of your nearest Quad dealer write or telephone
The Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs., PE18 7DB Telephone: (0480) 52561

WW - 043 FOR FURTHER DETAILS

EP4000 EPROM EMULATOR PROGRAMMER



The microprocessor controlled EP4000 will emulate and program all the popular EPROMs including the 2704, 2708, 2716(3), 2508, 2758, 2516, 2716, 2532 and 2732 devices. Personality cards and hardware changes are not required as the machine configures itself for the different devices. Other devices such as bipolar PROMs and 2764 and 2564 EPROMs are programmed with external modules.

The editing and emulation facilities, video output and serial/parallel input/output provided as standard make the EP4000 very flexible to allow its use in three main modes:

- As a stand alone unit for editing and duplicating EPROMs.

Items pictured are: ● EP4000 Emulator Programmer - £545 + £12 delivery; ● BSC buffered simulator cable - £39; ● MESA 4 multi EPROM simulator cable - £98; ● 2732A Programming adaptor - £39; ● 2764 Programming adaptor - £64; ● 2564 Programming adaptor - £64; ●

- As a slave programmer used in conjunction with a software development system or microcomputer.
- As a real time EPROM emulator for program debugging and development (standard access time of the emulator is 300ns).

Data can be loaded into the 4k x 8 static RAM from a pre-programmed EPROM, the keypad, the serial or parallel ports and an audio cassette. Keypad editing allows for data entry, shift, move, delete, store, match and scroll, and a 1k x 8 RAM allows temporary block storage. A video output for memory map display, as well as the built-in 8 digit hex display allows full use of the editing facilities to be made.

BP4 (TEXAS) Bipolar PROM Programming module - £190

Also available (not shown): ● VM10 Video monitor - £99; ● UV141 EPROM Eraser with timer - £78; ● GP100A 80 column Printer - £225; ● PI100 interface for EP4000 to GP100A - £65.

VAT should be added to all prices

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW - 044 FOR FURTHER DETAILS

P8000 — THE PRODUCTION PROGRAMMER THAT HANDLES ALL NMOS EPROMS



**NEW
PRODUCT**

- Checks, Programs, Compares up to 8 devices simultaneously
- Handles all NMOS EPROMS up to projected 128K designs with no personality modules or characterisers — See list
- Easy to use, menu driven operation for blankcheck, program, verify, illegal bit check, checksum, self-test
- Constant display of device type, mode and fault codings
- Individual socket LED indicators for EPROM status
- Comprehensive EPROM integrity checks — Illegal bit check, data and address shorts, constant power line monitoring
- Full safeguard protection on all sockets
- Automatic machine self-test routine
- Powered down sockets
- Cost effective price — £695 + VAT
- Available from stock

2704
2708
2716(3)
2508
2758A
2758B
2516
2716
48016
2532
2732
2732A
68732-0
68732-1
68766
68764
2764
2564
MK2764

Write or phone for more details

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW — 045 FOR FURTHER DETAILS

Test Instruments from Sifam

These instruments have all the features, accuracy and reliability you would expect from professional-quality equipment at less than you might expect them to cost.

3½-DIGITAL MULTIMETERS


Both these instruments have the following features:

- Only two input terminals, common to all functions.
- Overload protection, autozero, autopolarity, over-range and low battery indications.
- Basic 0.3% DCV accuracy.
- Supplied with test leads, spare fuse, 9V battery and operator's manual.

DMM2500

(bench model)

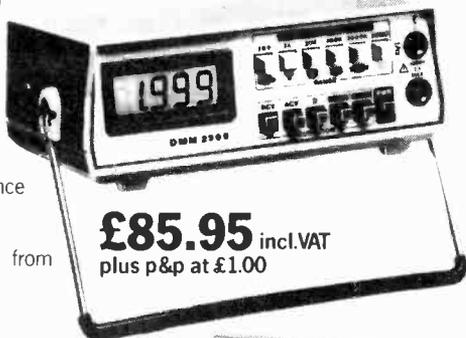Push-button operation providing 24 ranges in 5 modes.
 ±2A A.C./D.C.
 ±1000V A.C./D.C.
 200Ω to 20MΩ resistance
 Re-settable overload circuit breaker
 2000 hours operation from 9V battery
 Size: 155 x 120 x 57mm



£85.95 incl.VAT
 plus p&p at £1.00

DMM2200B

(hand-held model)

2 Teflon-bushed rotary switches providing 21 ranges in 5 modes.
 ±2A A.C./D.C.
 ±1000V A.C./D.C.
 2000Ω to 20MΩ resistance
 1000 hours operation from 9V battery
 Size: 165 x 110 x 43mm



£49.95
 incl.VAT plus p&p at £1.00

DIGITAL LOGIC PROBE DLP50

- Wide frequency range: DC to 50 MHz
- Minimum detectable input pulse width of 10 nsec.
- High input impedance of 10 megohms
- Compatible with DTL, TTL and CMOS in a wide range of power supply voltages of 4.5 to 30V D.C.
- Protected up to ±120V D.C./A.C. in input signal plus audible warning function
- Rugged, modern plastic-housed unit supplied packaged in a de-luxe moulded plastic carrying case, with ground lead, IC-clip lead and operator's manual
- Size: 195 x 26 x 16mm with 800mm power lead

£44.95 incl.VAT plus p&p at £1.00

All these instruments are guaranteed against defective parts/workmanship for 12 months. If not satisfied, please return within 14 days for full refund.



The telephone number for Access/Barclaycard orders, enquiries and literature is 0803 63822. Ext.8.

Post to: Sifam Ltd, Woodland Road, Torquay, Devon TQ2 7AY

Please send me _____ Total purchase price _____

Please debit my _____ I enclose Cheque

Access/Barclaycard No. _____ Postal Order

Name _____ Int. Money Order

Address _____

Signature _____

Please allow up to 28 days for delivery Official orders accepted from colleges, schools, companies, etc.

WW - 026 FOR FURTHER DETAILS

Constructor Series Speakers



IT'S SO EASY


Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit.

No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of.

Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc.

The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl.

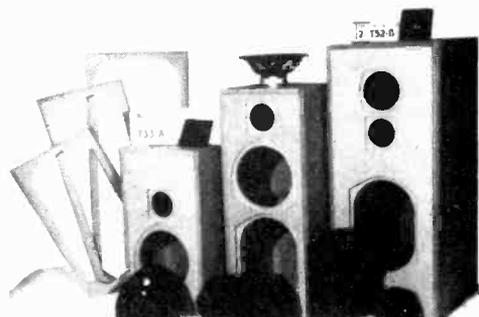Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.



Prices: CS1 (As 101) £110 pr. inc. VAT, plus carr./ins. £ 5.50
 CS1A (simplified LS3/5A) £103 pr. inc. VAT, plus carr./ins. £ 5.50
 CS3 (as 103.2) £129 pr. inc. VAT, plus carr./ins. £10.00
 CS5 (as Carlton II) £192 pr. inc. VAT, plus carr./ins. £15.00
 CS7 (as Cantata) £250 pr. inc. VAT, plus carr./ins. £18.00



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

Catalogue — £1.50 post free



Lightning service on telephoned credit card orders!



WW - 016 FOR FURTHER DETAILS

PICOTUTOR & ANALOGUE INTERFACE

ASSEMBLY LANGUAGE TRAINER

The ideal way to learn machine language and become acquainted with the new "single chip" control oriented microprocessors. 1.8K of EPROM, 20 I/O lines, 112 bytes of RAM and a timer all in a single 28-pin I.C. As featured in this, and subsequent issues of WW.

COMPLETE KIT £39.87

PCB, Programmed 68705 and all parts

ANALOGUE INTERFACE

£9.39

PCB and all components

PCB only £4.35
 Prog. 68705 £21.98
 Data £1.95

MAIL ORDER ONLY
 ALL PRICES
 INCLUDE VAT
 ADD 45p
 POSTAGE

PCB only £1.73

16-way Jumper
 Lead £2.35


MAGENTA ELECTRONICS LIMITED (W15)

135 Hunter Street, Burton-on-Trent, Staffs. DE14 2ST, 02-83-65435

WW - 048 FOR FURTHER DETAILS

TWIN PPM BOX

APRS Stand 99
 22-24 June

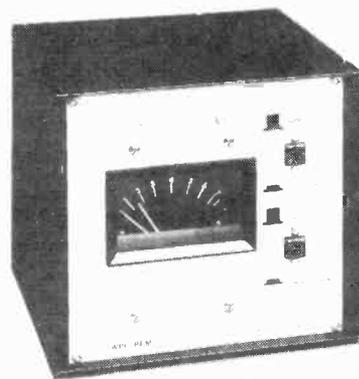

Also: PPM2, PPM3 and 20 pin DIL hybrid PPM5 drivers and Ernest Turner movements.

Stereo Disc Amplifier 3 and 4
 10 Outlet Distribution Amplifier 3

Stabilizer and Frequency Shifter circuit boards

Broadcast and Communications Receiver 150kHz-30MHz

Stereo Microphone Amplifier


Moving Coil Preamplifier
 Peak Deviation Meter and Chart Recorders

SURREY ELECTRONICS LTD
 The Forge, Luicks Green, Cramleigh
 Surrey GU6 7BE. Tel: 0483 275987



AMCRON INDUSTRIAL MUSCLE

- ★ POWER RESPONSE DC — 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.)
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1KW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS.
- ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

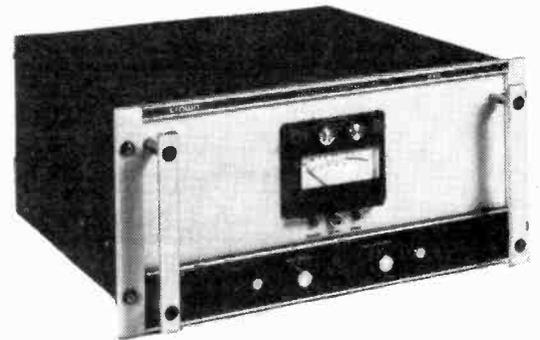

Model — M600

For full details on all Amcron Products write or phone Chris Flack

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

Analogue Associates

PROFESSIONAL INDUSTRIAL ELECTRONICS

WW — 018 FOR FURTHER DETAILS

QUALITY, PERFORMANCE, VALUE ...the extra is DURABILITY

HM103.....£158

Single trace 2mV/cm
10MHz, Component
Tester.

HM203-4.....£264


Dual trace 2mV/cm
20MHz, Alg Add, Invert
X-Y, Component Tester.

HM204.....£365

Dual trace 2mV/cm
20MHz, Alg Add, Invert
Delay T/B, Var hold-off
Peak Auto Trig to 50MHz,
X-Y, Single Shot, Z Mod,
Component Tester.

HM705.....£588

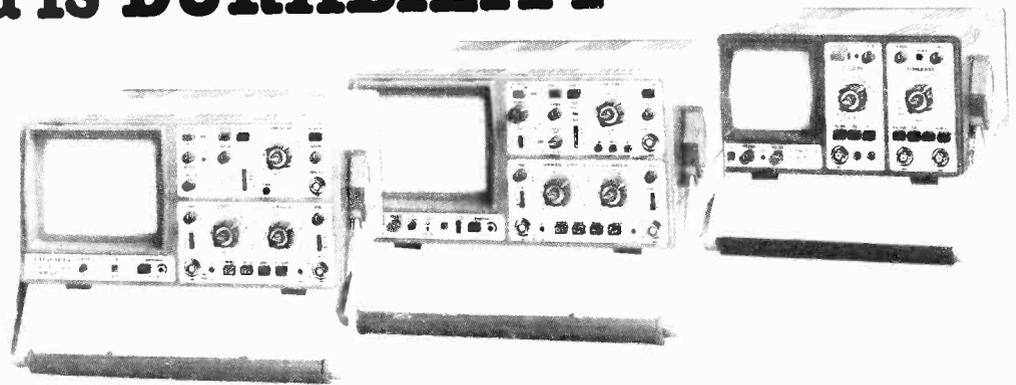Dual trace 2mV/cm
70MHz, Alg Add, Invert,
Signal Delay, Delay T/B,
Single Shot, Var hold-off,
14KV P.D.A. C.R.T.



For free data sheets of the full range contact:

Prices U.K. list ex. VAT

HAMEG

England
HAMEG LTD.
74-78 Collingdon Street,
Luton, LU1 1RX
Tel:(0582) 413174/Telex: 825484

France
HAMEG S.A.R.L.
5-9 Avenue de la Republique
94800 Villejuif
Tel:678.09.98/Telex:270705

Spain
HAMEG IBERICA S.A.
Villaroel 172-174,
Barcelona-36
Tel:230.15.97

West Germany
HAMEG GmbH
6 Frankfurt am Main 71,
Kelsterbacher Str. 15-19
Tel: 0611/676017 Telex:0413866

United States
HAMEG, INC.
88-90 Harbor Rd.,
Port Washington, N.Y. 11050
Phone: 516.883.3837/516.883.6428

WW — 053 FOR FURTHER DETAILS

SWITCHES
TOGGLE 2A 250V
SPST 33p
DPDT 44p

SUB-MIN TOGGLE
SPST on/off 54p
SPDT c/over 60p
SPDT centre off 85p
SPDT biased both ways 105p
DPDT 6 tags 75p
DPDT centre off 88p
DPDT biased both ways 145p
DPDT 3 positions on/on/off 185p
3-pole 2 way 205p

SLIDE 250V
DPDT 1A 14p
DPDT 1A c/off 15p
DPDT 1/2A 13p

PUSHBUTTON 6A
with 10mm Button
SPDT latching 99p
DPDT latching 145p
SPDT moment 99p
DPDT moment 145p

Mini Non Locking
Push to Make 15p
Push to Break 25p

DI SWITCHES
(SPST) 4-way 70p; 6-way 85p;
8-way 90p; 10-way 145p.
(SPDT) 4-way 190p

ROTARY SWITCHES
(Adjustable Stop type)
1 pole/2 to 12 way; 2p/2 to 6 way;
3 pole/2 to 4 way; 6p/2 to 3 way 45p

ROTARY: Mains DP 250V 4 Amp on/off 68p

ROTARY: (Make-a-switch)
Make a multi-way switch. Shifting assembly has adjustable stop. Accommodates up to 4 wafers.
(max 6 pole/12 way - DP switch)
Mechanism only 90p

WAFERS: (make before break) to fit the above switch mechanism
1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6p/2 way 85p
Mains DP 4A. Switch to fit
Spacers 4p. Screen 6p.

ROCKER: 5A/250V SPST 28p
ROCKER: 10A/250V SPDT 38p
ROCKER: 10A/250V DPDT c/off 95p
ROCKER: 10A/250V DPST with neon 85p

THUMBWHEEL: Mini front mounting
Decade Switch Module 220p
B.C.D. Switch Module 275p
Mounting Cheeks (per pair) 75p

VEROBOARD 0.1in clad plain
2 1/2-3 1/4" 85p
2 1/2-5" 100p
3 1/4-3 3/4" 100p
3 3/4-5" 115p
3 3/4-17" 390p
4 3/4-17" 495p
Pin of 100 pins 55p
Spot face cutter 150p
Pin insertion tool 185p

VERO BOARD
DIP Board 180p
Clad Board 350p
Vero Strip 95p

PROTO DECS
Verolock 405p
S-Dec 350p
Euroboardboard 520p
Bimboard 1 575p
Superstrip SS2 1350p

DALO ETCH RESIST PEN
Plus Spare Tip 90p

ULTRASONIC TRANSDUCER
40KHz 325p

FERRIC CHLORIDE
1lb bag Anhydrous 195p
500g P&P

VERO WIRING
PEN - Spool 340p
Spare Spool 75p
Combs 6p

EDGE CONNECTORS
1 156
2x15 way 140p
2x18 way 180p 145p
2x22 way 190p 200p
2x23 way 175p
2x25 way 225p 220p
2x28 way 190p
2x30 way 245p
2x36 way 295p
2x40 way 315p
2x43 way 395p
2x75 way 550p

VERO CLAD BOARDS
Fibre Single Double S.R.B.P.
glass sided sided 9.5"x8.5"
6"x6" 90p 110p 95p
6"x12" 150p 195p

DC CONNECTORS
PCB Plugs with Female Female
DIP Board Angle Hdr. Card
Vero Strip Plug Edge Conn.
Pins Pins Pins Pins
Strt Angle Strt Angle
10 way 90p 95p 85p
15 way 130p 150p 110p
20 way 145p 160p 125p 195p
26 way 175p 200p 150p 240p
34 way 205p 230p 160p 320p
40 way 220p 250p 190p 340p
50 way 235p 270p 200p 395p
60 way 240p 270p 230p 495p

EURO CONNECTORS
Female Socket Male Plug
Strt Angle Strt Angle
Pins Pins Pins Pins
DIN41617 31 way 170p - - 175p
DIN41612 2x32 A+B 275p 320p 220p 285p
DIN41612 2x32 A+C 295p 340p 240p 300p
01 N 4161 Z 190p 240p 200p 260p
3x32 A+B+C 360p 385p 260p 395p

DIL PLUG (Header)
Solder IDC
14 pin 40p 99p
16 pin 49p 105p
24 pin 88p 170p
40 pin 250p 255p

RIBBON CABLE
price per foot
Grey Colour
10 way 15p 28p
16 way 25p 40p
20 way 30p 50p
24 way 40p 65p
34 way 60p 85p
40 way 70p 90p
50 way 100p 135p

ZIF DIL SOCKETS
24 pin 575p
28 pin 820p
40 pin 975p

PANEL METERS
FSD
60x46x35mm
0.50uA
0.100uA
0.500uA
0.1mA
0.5mA
0.10mA
0.50mA
0.100mA
0.500mA
0.1A
0.2A
0.25V
0.50V AC
0.300V AC
"S"
"VU" 450p each

RELAYS
Miniature enclosed PCB mount
SINGLE POLE Changeover
RL6-91 2051 Coil; 12V DC, 10V5 to 19.5V; 10A at 30V DC or 250V AC 185p
DOUBLE POLE Changeover 6A 30p
DC or 250V AC
RL6-100 5301 Coil, 6V DC (5V4 to 9V9) 190p
RL6-111 2051 Coil, 12V DC (10V7 to 19V5) 195p
RL6-114 7401 Coil, 24V DC (22V to 37V) 200p

AMPHENOL PLUGS
IEEE 24 way
Centronics Parallel 36 way soldered 530p
Centronics Parallel 36 way IDC 495p

BUZZERS: miniature, solid-state
6V, 9V & 12V 70p
PIEZOELECTRIC
PB2720 55p

LOUDSPEAKERS
Miniature 0.3W 8Ω
2in, 3 1/4in, 2 1/2in, 3in
2 1/2in 40Ω, 64Ω or 80Ω 80p
80p

ASTEC UHF MODULATORS
Standard 6MHz 280p
Wideband 8MHz 480p

'WEMON' New Version WATFORD'S Ultimate Monitor IC
A 4K Monitor chip specially designed to produce the best from your Super Board Series I & II. Enhanced Super Board & UK101. As reviewed by Dr A. Berk in Practical Electronics, June 1981. Only £10

BBC MICROCOMPUTER AND UPGRADE KITS
(Our BBC Micro Upgrade Kits will save you £££...)
16K Memory (8x4816AP) £18
Printer User I/O Port Kit £8.20
Complete Printer Cable 36" £12
Disc Interface Kit £43
Analogue I/O Kit £6.75
Serial I/O Kit £7.50
Expansion Bus Kit £6.50
Complete Upgrade Kit from Model A to Model B £45
We supply complete range of BBC Plugs, Sockets, Leads, Peripherals, Software, etc. Send SAE for list.

ETI PROJECTS
We stock most of the parts

JUMPER LEADS (Ribbon Cable Assembly)
Length 14 pin 16 pin 24 pin 40 pin
Single ended DIP (Header Plug) Jumper 24 inches 145p 155p 240p 325p
Double ended DIP (Header Plug) Jumper 6 inches 185p 205p 300p 465p
12 inches 195p 215p 315p 490p
24 inches 210p 235p 345p 540p
36 inches 230p 250p 375p 595p

ICD Female Header Socket Jumper Leads 24"
Single ended 160p 200p 260p 300p
Double ended 290p 370p 480p 525p

ANTEX SOLDERING IRONS
C-15W 455p CX17W 475p
CCN-15W 495p CX25W 515p
Spare tips, assorted sizes 85p
Spare Elements 210p
Iron stand with sponge 165p

SOLDERCON PINS
Ideal for making SIL or DIL Sockets
100pins 75p
500pins 350p

ALUM BOXES
3x2 1/2" 65p
4x2 1/2" 85p
4x2 3/4" 105p
4x4 1/2" 120p
5x4 1/2" 120p
5x4 3/4" 120p
5x6 1/2" 130p
5x6 3/4" 130p
6x4 1/2" 130p
6x4 3/4" 150p
7x5 3/4" 180p
8x6 3/4" 210p
8x6 1/2" 210p
10x7 3/4" 275p
12x5 3/4" 260p
24x8 3/4" 295p

VERO BOARD
DIP Board 180p
Clad Board 350p
Vero Strip 95p

VERO WIRING
PEN - Spool 340p
Spare Spool 75p
Combs 6p

EDGE CONNECTORS
1 156
2x15 way 140p
2x18 way 180p 145p
2x22 way 190p 200p
2x23 way 175p
2x25 way 225p 220p
2x28 way 190p
2x30 way 245p
2x36 way 295p
2x40 way 315p
2x43 way 395p
2x75 way 550p

VERO CLAD BOARDS
Fibre Single Double S.R.B.P.
glass sided sided 9.5"x8.5"
6"x6" 90p 110p 95p
6"x12" 150p 195p

DC CONNECTORS
PCB Plugs with Female Female
DIP Board Angle Hdr. Card
Vero Strip Plug Edge Conn.
Pins Pins Pins Pins
Strt Angle Strt Angle
10 way 90p 95p 85p
15 way 130p 150p 110p
20 way 145p 160p 125p 195p
26 way 175p 200p 150p 240p
34 way 205p 230p 160p 320p
40 way 220p 250p 190p 340p
50 way 235p 270p 200p 395p
60 way 240p 270p 230p 495p

EURO CONNECTORS
Female Socket Male Plug
Strt Angle Strt Angle
Pins Pins Pins Pins
DIN41617 31 way 170p - - 175p
DIN41612 2x32 A+B 275p 320p 220p 285p
DIN41612 2x32 A+C 295p 340p 240p 300p
01 N 4161 Z 190p 240p 200p 260p
3x32 A+B+C 360p 385p 260p 395p

DIL PLUG (Header)
Solder IDC
14 pin 40p 99p
16 pin 49p 105p
24 pin 88p 170p
40 pin 250p 255p

RIBBON CABLE
price per foot
Grey Colour
10 way 15p 28p
16 way 25p 40p
20 way 30p 50p
24 way 40p 65p
34 way 60p 85p
40 way 70p 90p
50 way 100p 135p

ZIF DIL SOCKETS
24 pin 575p
28 pin 820p
40 pin 975p

PANEL METERS
FSD
60x46x35mm
0.50uA
0.100uA
0.500uA
0.1mA
0.5mA
0.10mA
0.50mA
0.100mA
0.500mA
0.1A
0.2A
0.25V
0.50V AC
0.300V AC
"S"
"VU" 450p each

RELAYS
Miniature enclosed PCB mount
SINGLE POLE Changeover
RL6-91 2051 Coil; 12V DC, 10V5 to 19.5V; 10A at 30V DC or 250V AC 185p
DOUBLE POLE Changeover 6A 30p
DC or 250V AC
RL6-100 5301 Coil, 6V DC (5V4 to 9V9) 190p
RL6-111 2051 Coil, 12V DC (10V7 to 19V5) 195p
RL6-114 7401 Coil, 24V DC (22V to 37V) 200p

AMPHENOL PLUGS
IEEE 24 way
Centronics Parallel 36 way soldered 530p
Centronics Parallel 36 way IDC 495p

BUZZERS: miniature, solid-state
6V, 9V & 12V 70p
PIEZOELECTRIC
PB2720 55p

LOUDSPEAKERS
Miniature 0.3W 8Ω
2in, 3 1/4in, 2 1/2in, 3in
2 1/2in 40Ω, 64Ω or 80Ω 80p
80p

ASTEC UHF MODULATORS
Standard 6MHz 280p
Wideband 8MHz 480p

'WEMON' New Version WATFORD'S Ultimate Monitor IC
A 4K Monitor chip specially designed to produce the best from your Super Board Series I & II. Enhanced Super Board & UK101. As reviewed by Dr A. Berk in Practical Electronics, June 1981. Only £10

BBC MICROCOMPUTER AND UPGRADE KITS
(Our BBC Micro Upgrade Kits will save you £££...)
16K Memory (8x4816AP) £18
Printer User I/O Port Kit £8.20
Complete Printer Cable 36" £12
Disc Interface Kit £43
Analogue I/O Kit £6.75
Serial I/O Kit £7.50
Expansion Bus Kit £6.50
Complete Upgrade Kit from Model A to Model B £45
We supply complete range of BBC Plugs, Sockets, Leads, Peripherals, Software, etc. Send SAE for list.

BBC MICROCOMPUTER AND UPGRADE KITS
(Our BBC Micro Upgrade Kits will save you £££...)
16K Memory (8x4816AP) £18
Printer User I/O Port Kit £8.20
Complete Printer Cable 36" £12
Disc Interface Kit £43
Analogue I/O Kit £6.75
Serial I/O Kit £7.50
Expansion Bus Kit £6.50
Complete Upgrade Kit from Model A to Model B £45
We supply complete range of BBC Plugs, Sockets, Leads, Peripherals, Software, etc. Send SAE for list.

TRANSFORMERS:
3-0.3V; 6-0.6V; 9-0.9V; 12-0.12V; 15-0.15V @ 100mA 98p

pcb mounting Miniature Split Bobbin
3VA: 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p
6VA: 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A 270p

Standard Split Bobbin type
6VA: 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A; 2x15V-0.25A 220p
12VA: 2x4.5V-1.3A; 2x6V-1.1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 295p (35p p&p)

24VA: 2x6V-1.5A; 2x9V-1.2A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A 330p (60p p&p)

50VA: 2x6V-2.5A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x30V-0.8A 465p (60p p&p)

Specialty wound for Multirail Computer
PSUs 50VA: Outputs: +5V/5A; +12V; +25V; -5V; -12Vx1A 575p (60p p&p)

100VA: 2x12V-4A; 2x15V-3A; 2x20V-2A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and above our normal postal charge).

VOLTAGE REGULATORS
1A T0220 Plastic casing
+ve -ve
5V 7805 40p 7905 45p
12V 7812 40p 7908 40p
15V 7815 40p 7912 45p
18V 7818 40p 7915 45p
24V 7824 40p 7918 45p
7924 45p

100mA T092 Plastic package
+ve -ve
5V 78L05 30p 79L05 60p
6V 78L06 30p 79L06 60p
8V 78L08 30p 79L08 60p
12V 78L12 30p 79L12 60p
15V 78L15 30p 79L15 60p

LM3008 170p TDA1412 150p
LM3044 170p 78H05 +5V/5A 150p
LM3058 140p 78H12 +12V/5A 550p
LM309K 135p 78H12 +12V/5A 550p
LM317K 320p 7.8 G + 5 V 1.0 580p
LM323K 99p +25V/5A 590p
LM337 175p 79HJ +2.25V to 24V5A 685p
LM723 Var. 36p
TAA550 50p

VERO BOARD
DIP Board 180p
Clad Board 350p
Vero Strip 95p

VERO WIRING
PEN - Spool 340p
Spare Spool 75p
Combs 6p

EDGE CONNECTORS
1 156
2x15 way 140p
2x18 way 180p 145p
2x22 way 190p 200p
2x23 way 175p
2x25 way 225p 220p
2x28 way 190p
2x30 way 245p
2x36 way 295p
2x40 way 315p
2x43 way 395p
2x75 way 550p

VERO CLAD BOARDS
Fibre Single Double S.R.B.P.
glass sided sided 9.5"x8.5"
6"x6" 90p 110p 95p
6"x12" 150p 195p

DC CONNECTORS
PCB Plugs with Female Female
DIP Board Angle Hdr. Card
Vero Strip Plug Edge Conn.
Pins Pins Pins Pins
Strt Angle Strt Angle
10 way 90p 95p 85p
15 way 130p 150p 110p
20 way 145p 160p 125p 195p
26 way 175p 200p 150p 240p
34 way 205p 230p 160p 320p
40 way 220p 250p 190p 340p
50 way 235p 270p 200p 395p
60 way 240p 270p 230p 495p

EURO CONNECTORS
Female Socket Male Plug
Strt Angle Strt Angle
Pins Pins Pins Pins
DIN41617 31 way 170p - - 175p
DIN41612 2x32 A+B 275p 320p 220p 285p
DIN41612 2x32 A+C 295p 340p 240p 300p
01 N 4161 Z 190p 240p 200p 260p
3x32 A+B+C 360p 385p 260p 395p

DIL PLUG (Header)
Solder IDC
14 pin 40p 99p
16 pin 49p 105p
24 pin 88p 170p
40 pin 250p 255p

RIBBON CABLE
price per foot
Grey Colour
10 way 15p 28p
16 way 25p 40p
20 way 30p 50p
24 way 40p 65p
34 way 60p 85p
40 way 70p 90p
50 way 100p 135p

ZIF DIL SOCKETS
24 pin 575p
28 pin 820p
40 pin 975p

PANEL METERS
FSD
60x46x35mm
0.50uA
0.100uA
0.500uA
0.1mA
0.5mA
0.10mA
0.50mA
0.100mA
0.500mA
0.1A
0.2A
0.25V
0.50V AC
0.300V AC
"S"
"VU" 450p each

RELAYS
Miniature enclosed PCB mount
SINGLE POLE Changeover
RL6-91 2051 Coil; 12V DC, 10V5 to 19.5V; 10A at 30V DC or 250V AC 185p
DOUBLE POLE Changeover 6A 30p
DC or 250V AC
RL6-100 5301 Coil, 6V DC (5V4 to 9V9) 190p
RL6-111 2051 Coil, 12V DC (10V7 to 19V5) 195p
RL6-114 7401 Coil, 24V DC (22V to 37V) 200p

AMPHENOL PLUGS
IEEE 24 way
Centronics Parallel 36 way soldered 530p
Centronics Parallel 36 way IDC 495p

BUZZERS: miniature, solid-state
6V, 9V & 12V 70p
PIEZOELECTRIC
PB2720 55p

LOUDSPEAKERS
Miniature 0.3W 8Ω
2in, 3 1/4in, 2 1/2in, 3in
2 1/2in 40Ω, 64Ω or 80Ω 80p
80p

ASTEC UHF MODULATORS
Standard 6MHz 280p
Wideband 8MHz 480p

'WEMON' New Version WATFORD'S Ultimate Monitor IC
A 4K Monitor chip specially designed to produce the best from your Super Board Series I & II. Enhanced Super Board & UK101. As reviewed by Dr A. Berk in Practical Electronics, June 1981. Only £10

BBC MICROCOMPUTER AND UPGRADE KITS
(Our BBC Micro Upgrade Kits will save you £££...)
16K Memory (8x4816AP) £18
Printer User I/O Port Kit £8.20
Complete Printer Cable 36" £12
Disc Interface Kit £43
Analogue I/O Kit £6.75
Serial I/O Kit £7.50
Expansion Bus Kit £6.50
Complete Upgrade Kit from Model A to Model B £45
We supply complete range of BBC Plugs, Sockets, Leads, Peripherals, Software, etc. Send SAE for list.

BBC MICROCOMPUTER AND UPGRADE KITS
(Our BBC Micro Upgrade Kits will save you £££...)
16K Memory (8x4816AP) £18
Printer User I/O Port Kit £8.20
Complete Printer Cable 36" £12
Disc Interface Kit £43
Analogue I/O Kit £6.75
Serial I/O Kit £7.50
Expansion Bus Kit £6.50
Complete Upgrade Kit from Model A to Model B £45
We supply complete range of BBC Plugs, Sockets, Leads, Peripherals, Software, etc. Send SAE for list.

CMOS	4075	13	4543	70	
4000	10	4076	50	4544	150
4001	10	4077	13	4548	40
4002	12	4078	15	4549	375
4006	50	4082	13	4554	190
4007	14	4085	50	4555	38
4008	32	4086	60	4556	35
4009	24	4089	125	4557	320
4010	24	4093	20	4558	120
4011	10	4094	70	4559	395
4012	16	4095	95	4560	160
4013	20	4096	70	4561	104
4014	46	4097	290	4562	495
4015	40	4098	75	4566	165
4016	20	4099	110	4568	250
4017	32	4160	95	4569	175
4018	46	4161	99	4570	175
4019	25	4162	99	4580	460
4020	42	4163	99	4581	250
4021	40	4174	99	4582	99
4022	40	4175	105	4583	90
4023	13	4194	105	4594	40
4024	32	4408	90	4585	60
4025	13	4409	790	4597	330
4026	80	4410	725	4599	290
4027	20	4411	675	40085	90
4028	39	4412	775	40097	45
4029	46	4415	460	40098	45
4030	15	4419	280	40100	215
4031	125	4422	770	40101	130
4032	80	4435	850	40102	140
4033	125	4440	999	40103	175
4034	140	4450	350	40104	95
4035	45	4451	350	40105	105
4036	275	4490	350	40106	35
4037	115	4500	675	40107	60
4038	110	4501	28	40108	198
4039	250	4502	60	40109	80
4040	40	4503	40	40110	198
4041	40	4504	75	40114	240
4042	40	4505	185	40161	194
4043	40	4506	35	40163	50
4044	40	4507	35	40174	45
4045	105	4508	130	40175	50
4046	46	4510	46	40181	220
4047	40	4511	45	40182	90
4048	40	4512	50	40192	75
4049	25	4513	199	40193	70
4050	25	4514	115	40194	70
4051	45	4515	115	40195	75
4052	80	4516	55	40244	195
4053	50	4517	275		

MINI-MULTI TESTER Deluxe pocket size precision moving coil instrument, jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0 - 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test leads and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only **£6.75 + 60p** post and insurance.

FREE Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send **£2.50**.

VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only **£2.95**. These are without case but we can supply a plastic base **£1.75** or metal case **£2.95**. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is **£2.30**.



THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses, appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 - 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around **£15.00** - however, you can have the parcel for **£2.50**.

50 THINGS YOU CAN MAKE

or do and still have hundreds of parts for future jobs. **LEARN** the practical way with our 10 kilo parcel of useful parts. Minimum 1,000 items includes panel meters, tuners, thermal trips, relays, switches, motors, drills, taps and dies, tools, thermostats, coils, condensers, resistors, etc. etc. Parcel with data on 50 projects.

YOURS FOR ONLY £11.50 plus £3.00 post.

3 CHANNEL SOUND TO LIGHT KIT



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is **£14.95** in kit form or **£25.00** assembled and tested.

MULTI-CHANNEL or ROBOT CONTROLLER

This is two kits. The 8 channel transmitter kit and the 8 channel receiver kit. Each kit comes with diagrams and notes, but no circuit boards, the component layout being left to you. The data shows how to drive, reverse and steer two or more motors. With spare channels to perform other functions. Price **£9.50** for both kits.

'BIG EAR'

As in December Hobby Electronics. Designed originally for listening to wildlife this could also be used to listen through walls or from long distances. Complete kit including the case at **£9.50**.

TANGENTIAL BLOW HEATER

2.5 Kw quiet, efficient instant heating from 230/240 volt mains. Kit consists of blower as illustrated, 2.5 Kw element, control switch and data all for **£4.95** post **£1.50**.



CAR STARTER AND CHARGER KIT

In an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises 250 watt mains transformer, 40 amp bridge rectifier, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price **£12.50 + £3.00 post**.

J. BULL (Electrical) Ltd.

(Dept. WW), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £10 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: write for quote. Delivery by return. Shop open 9.00 - 5.30, Mon to Fri, not Saturday

EXTRACTOR FANS

Mains operated ex computer
5" Woods extractor 4" x 4" Muffin 115v **£5.75, Post £1.25** **£4.50, Post 75p.**
5" Plannair extractor 4" x 4" Muffin 230v. **£6.50, Post £1.25** **£5.75, Post 75p.**




PROJECT CASE

All metal construction. Tubular body. Size approx 7 x 3 x 5" long with removable ends, blue hammer paint finish. **£1.75** each + 60p for postage.



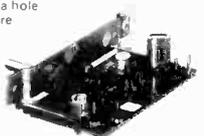MINI MONO AMP on p.c.b. size 4" x 2" approx. Fireex volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amplifier. Brand new, perfect condition, offered at the very low price of **£1.15** each, or 10 for **£10.00**.



COMPUTER PRINTER, ONLY £4.95 YOUR LAST CHANCE

Japanese made Epson 310 - has a self starting brushless drive motor. Complete with electronics - uses plain paper. Brand new with data. **ONLY £4.95 plus £1.25 Post.**



8 POWERFUL BATTERY MOTORS (all different)

For models, maccanos, drills, remote control planes, boats, etc. **£2.95**.

12v MOTOR BY SMITHS

Made for use in cars, these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. These have a good length of 1/4" spindle - price **£3.45**.



Ditto, but double ended **£4.25**.

Ditto, but permanent magnet, **£3.75**.

EXTRA POWERFUL 12v MOTOR

Made to work battery lawnmower, this probably develops up to 1/2 h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. **£6.90 + £1.50 post.** (This is easily reversible with our reversing switch - Price **£1.15**).

GO KART MOTOR

24 Volt operated easily vary speed and reverse - terrific power. Price **£9.50 + £1.50 post.**

WW - 060 FOR FURTHER DETAILS

1983 EDITION

Powerful bestseller

The new 1983 edition of the Texas Instruments Power Semiconductor Data Book contains full data on the complete range of TI Power Transistors, Darlingtons, Triacs and Thyristors. Complete the coupon to receive a copy of this 900 page, bestseller ex-stock. Price **£9.00** plus p&p.

TEXAS INSTRUMENTS

Please send me _____ copy/copies of the 1983 TI Power Data Book.
I enclose a cheque for £ _____ (including £1.50 p&p per order).
Name _____
Company _____
Address _____
Postcode _____
Mail to: Texas Instruments Ltd., PO Box 50, Market Harborough, Leicestershire.
Registered Office: Texas Instruments Ltd., Manton Lane, Bedford MK41 7PA.
Registered number: 574102 England. WW/2

WW - 047 FOR FURTHER DETAILS

PRINTED CIRCUITS FOR WIRELESS WORLD PROJECTS

Audio compressor/limiter—Dec. 1975—1 s.s. (stereo)	£4.25
Cassette recorder—May 1976—1 s.s.	£5.00
Audio compander—July 1976—1 s.s.	£4.25
Audio preamplifier—November 1976—2 s.s.	£8.50
Additional circuits—October 1977—1 s.s.	£4.00
Stereo coder—April 1977—1 d.s. 2 s.s.	£8.50
Low distortion disc amplifier (stereo)—September 1977—1 s.s.	£2.00
Low distortion audio oscillator—September 1977—1 s.s.	£3.50
Synthesized f.m. transceiver—November 1977—2 d.s. 1 s.s.	£12.00
Morsemaker—June 1978—1 d.s.	£4.50
Metal detector—July 1978—1 d.s.	£3.75
Oscilloscope waveform store—October 1978—4 d.s.	£18.00
Regulator for car alternator—August 1978—1 s.s.	£2.00
Wideband noise reducer—November 1978—1 d.s.	£5.00
Versatile noise generator—January 1979—1 s.s.	£5.00
200MHz frequency meter—January 1979—1 d.s.	£7.00
High performance preamplifier—February 1979—1 s.s.	£5.50
Distortion meter and oscillator—July 1979—2 s.s.	£5.50
Moving coil preamplifier—August 1979—1 s.s.	£3.50
Multi-mode transceiver—October 1979—10 d.s.	£35.00
Amplification system—Oct. 1979—3 preamp 1 poweramp	£4.20 each
Digital capacitance meter—April 1980—2 s.s.	£7.50
Colour graphics system—April 1980—1 d.s.	£18.50
Audio spectrum analyser—May 1980—3 s.s.	£10.50
Multi-section equalizer—June 1980—2 s.s.	£8.00
Floating-bridge power amp—Oct. 1980—1 s.s. (12V or 40V)	£4.00
Nanocomp 6802 or 6809—Jan., July, 1981—1 d.s. 1 s.s.	£9.00
Cassette interface—July, 1981—1 s.s.	£1.50
Eprom programmer—Jan., 1982—1 d.s.	£4.50
Logic probe—Feb., 1981—2 d.s.	£6.00
Modular frequency counters—March, 1981—8 s.s.	£20.00
Opto electronic contact breaker (Delco)—April, 1981—2 s.s.	£4.00
CB synthesiser—Sept.—1 d.s.	£6.00
Electronic ignition—March, 1982—1 s.s.	£4.00

Boards and glassfibre roller-tinned and drilled. Prices include VAT and UK postage. Airmail add 30%, Europe add 10%. Insurance 10%. Remittance with order to:


M. R. SAGIN, NANCARRAS MILL, THE LEVEL CONSTANTINE, FALMOUTH, CORNWALL

WW - 023 FOR FURTHER DETAILS

Essex Tiny Basic System

- * RS232 Interface
48 I/O Lines
- * Powerful National
INS 8073 Processor
- * Autostart Operation
with Watchdog Timer
- * Up to 16K Byte EPROM
EPROM Programmer
- * Accommodates Instant
ROM Modules

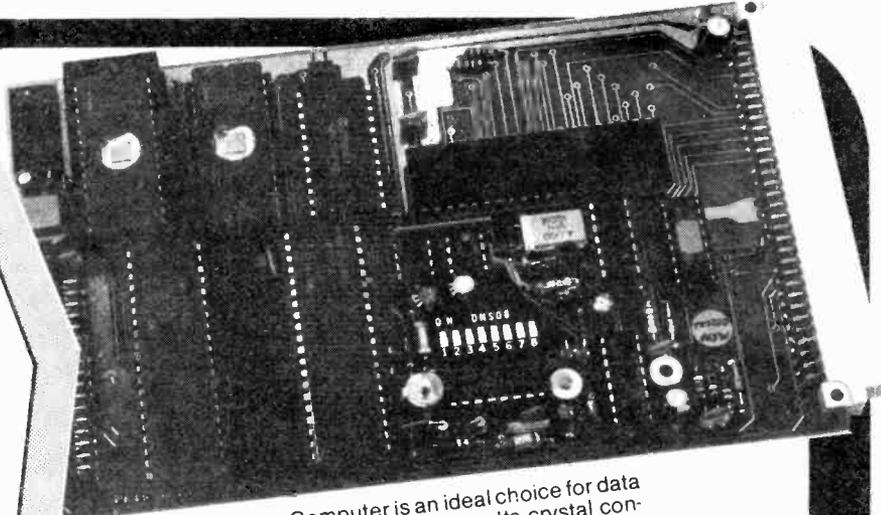PRICE EXCLUDING VAT: £185
SUBSTANTIAL QUANTITY
DISCOUNTS
CARRIAGE WITHIN THE UK: £2



The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal, and then be copied into EPROM. Alternatively, Instant ROM modules may be used both during development and for program storage.

'INSTANT ROM' is the trademark of Greenwich Instruments

— PLEASE SEND FOR FULL INFORMATION

* NOW AVAILABLE

The Essex Buffer/Timer Board
24 Buffered Inputs
16 Buffered Outputs
4 Hardware Timers

Provides easy interfacing to the computer



Essex Electronics Centre

Wivenhoe Park, Colchester, Essex CO4 3SQ
Telephone: Colchester (0206) 865089

WW - 019 FOR FURTHER DETAILS

Pye Europa MF5FM high-band sets, complete but less mike and cradle. **£90 each plus £2 p.p. plus VAT.**
Pye M294 high-band FM sets, complete but less mike, speaker and cradle. **£150 each plus £2 p.p. plus VAT.**
Pye Reporter MF6 AM high-band sets, complete but less speaker and cradle. **£90 each plus £2 p.p. plus VAT.**
Pye Olympic M201 AM high-band sets, complete but less mike, speaker and cradle. **£90 each plus £2 p.p. plus VAT.**
Pye Westminster W15 FM G band 42-54 MHz sets, unused and like new, but less mike, speaker and cradle. **£65 each plus £2 p.p. plus VAT.**
Pye Westminster W15 AMD mid-band multi-channel sets, no mikes, speakers or cradles. **£45 each plus £2 p.p. plus VAT.**
Pye Westminster W15 AMD mid-band crystallised and converted to 129.9 MHz, 130.1 MHz, 130.4 MHz. Very good condition. **£120 each plus £2 p.p. plus VAT.**
Pye Westminster W15 AMD high-band and low-band sets available. Sets complete but less mikes, speakers and cradles. **£70 each plus £2 p.p. plus VAT.**
Pye Westminster W30 AM low-band sets only, no control gear. Sets complete and in good condition. **£45 each plus £2 p.p. plus VAT.**
Pye base station F30 AM, low band and high band available, remote and local control. **Prices from £220 plus VAT.**
Pye base station F401 high-band AM, local control, fully solid state, complete but less mike. **£275 each plus £15 p.p. plus VAT.**
Pye base station receiver R402 high-band FM 148-174MHz, single channel, 12.5 KHz channel spacing. **£95 each plus £5 p.p. plus VAT.**
Pye base station F9U, remotely controlled, 5 Watt output, UHF (440-470 MHz), single channel. **£90 each plus £5 p.p. plus VAT.**
Pye base station F412 UHF (440-470 MHz), 25KHz channel spacing, single channel, local control. **£250 each plus £15 p.p. plus VAT.**
Pye Beaver M254 high-band FM sets, 15 Watt, robust mobile radiotelephones for industrial use, sets complete but less crystals, as new condition. **£120 each plus £2 p.p. plus V.A.T.**
Pye base station receiver F27 AM, crystallised on 116.46 MHz, can be recrystallised on air band. Unused condition. **£15 each plus £5 p.p. plus VAT.**
Pye AC200 mains power unit for Olympic or Reporter, automatic standby power facility with trickle charging and built-in quartz digital clock. **£95 each plus £5 p.p. plus VAT.**

Pye AC power supply unit AC25PU, specially designed for use with the Europa series mobiles, power output 13.2 volt 5 amp. New condition. **£45 each plus £5 p.p. plus VAT.**
Pye PC1 radiotelephone controller, good condition, two only at **£50 each plus £2 p.p. plus VAT.**
Pye Tulip microphone as used on most base stations and PC1. 2400 ohm with ptt switch. **£15 plus £1 p.p. plus VAT.**
Pye PF1 UHF FM Pocketfone receiver, 440-470 MHz, single channel, int. speaker and aerial. Requires 9-volt battery. With service manual. **£6 each plus £1 p.p. plus VAT.**
Pye PF2 Pocketfone 70, all types available, AM, FM, UHF, completed with battery, mike and aerial. **£65 each plus £2 p.p. plus VAT.**
Pye PF1 Pocketfone battery-charger type BC14, 12 way with meter. **£10 each plus £1 p.p. plus VAT.**
Pye PF5012 UHF handhelds, crystallised on 466 MHz, complete with ni-cads. **£140 each plus £2 p.p. plus VAT.**
Pye Vanguard/Cambridge control leads, 18 way, with plugs and sockets, unused. **£4 each plus £1 p.p. plus VAT.**

MAINS TRANSFORMERS

0-240V input tapped 5000V 0.125 amp. **£20 plus £8 p.p. plus VAT.**
0.240V input 50V 20 amp. **£25 plus £8 p.p. plus VAT.**
0-240V input tapped 14KV 2mA. **£20 plus £8 p.p. plus VAT.**
0-240V input tapped 700V 1.2 amp. **£20 plus £8 p.p. plus VAT.**
Mains isolating transformer, 500VA 240V input, 240V C.T. output, housed in metal box. **£15 each plus £6 p.p. plus VAT.**
Mains isolating transformer, 240V tapped input, 240V 3 amp, plus 12V 0.5 amp output. **£20 each plus £6 p.p. plus VAT.**
Advance Volstat transformers, type CVN200/5, input 24 or 28V DC via inverter, output 220 or 240V RMS 150 watt, 50Hz. **£10 each plus £4 p.p. plus VAT.**
Variacs 2 amp, 5 amp, 8 amp, 15 amp, 25 amp, used but good condition. **From £10 each.**
Marconi AM/FM signal generator, type TF995A/3/S (CT402), 1.5-220 MHz, good condition with copy of service manual. **£95 each plus £15 p.p. plus VAT.**
Avo valve tester, type CT1160 (22 valve bases) with copy of manual. **£20 each plus £6 p.p. plus VAT.**
Airmec millivolt meter, Type 301. **£50 plus £2 p.p. plus VAT.**

Advance signal generator Type C2. **£25 plus £5 p.p. plus VAT.**
Airmec modulation meter, Type 210. **£75 plus £5 p.p. plus VAT.**
Rhode & Schwarz UHF test receiver BN1525, 280-940 MHz. **£50 each plus £15 p.p. plus VAT.**
Marconi HF Spectrum analyser, Type OA1094A/S 0-30 MHz. **£100 plus VAT (buyer collects).**
Eddystone receiver, Type 770U 144-500 MHz. **£155 plus £5 p.p. plus VAT.**
Servomex AC voltage stabiliser, type AC2, 240V @ 9 amp. **£45 each plus £15 p.p. plus VAT.**
Servomex AC voltage stabiliser, type AC7, 240V @ 20 amp. **£75 each plus £15 p.p. plus VAT.**
Samwell & Hutton T.V. Wobulator, type 78M, 16-230 MHz. **£35 each plus £15 p.p. plus VAT.**
Rhode & Schwarz power signal generator 0.1 to 30 MHz, Type BN41001. **£50 plus £10 p.p. plus VAT.**
Rhode & Schwarz wide band signal generator 10 Hz to 10 MHz, Type BN40861. **£50 plus VAT.**
Rhode & Schwarz sweep signal generator, 50 KHz to 12 MHz, Type BN4242/2. **£50 plus VAT.**
Meguro signal generator, type MSG-230E, 16 KHz-50 MHz. **£130 plus £10 p.p. plus VAT.**
Rhode & Schwarz Polyskop Type SWOB BN4244, 0.5 MHz to 400 MHz. **£150 plus £15 p.p. plus VAT.**
Computer-grade electrolytic capacitors, screw terminals, 25,000mfd., 33 volts, brand new. **£1 each plus 50p p.p. plus VAT.**
60 amp alternator and general noise filters for use in vehicles. **£1 each plus 50p p.p. plus VAT.**
Modern telephones, type 746, with dials, colour grey, used but good condition. **£8 plus £1 p.p. plus VAT.**
Cigar lighter plug with lead. **£1 each plus 30p p.p. plus VAT.**
IC test clips, 28-way and 40-way, gold plated. **£2 each plus 30p p.p. plus VAT.**
Equipment wire, size 7/0.2mm, colour yellow, 500-metre reels. **£4 plus £1 p.p. plus VAT.**
Z80-CPU, Z80-P10, Z80-CTC. **£1.85 each plus 30p p.p. plus VAT.**
Scotch video tape, 1" x 10" (25.40mm x 910mm), brand new. **£5 each plus £2 p.p. plus VAT.**
Power units, 70 volt @ 8 amp, 20 volt @ 3 amp. Brand new but no details. **£20 each plus £8 p.p. plus VAT.**
Beryllium block mounts for CCS1 valves, etc. **£10 each plus £1 p.p. plus VAT.**

B. BAMBER ELECTRONICS GOVERNMENT AND MANUFACTURERS' SURPLUS


5 STATION ROAD
LITTLEPORT CAMBS CB6 1QE
Telephone: Ely (0353) 860185

ELECTRONIC COMPONENTS
TELECOMMUNICATION EQUIPMENT
TEST GEAR



WW27

WW - 057 FOR FURTHER DETAILS

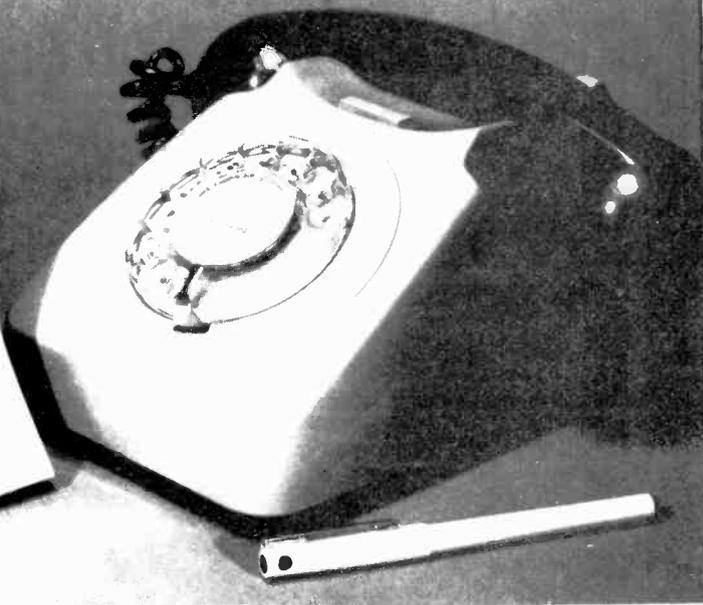

At last the message has come through, all you old solderers can throw away the soldering irons and the perforated circuit boards. NOW you can use PROTO-BOARDS from GSC. Despite daily breakthroughs in components and packaging, designing and testing new circuit concepts is often a lot more manual work than creative work. Not surprising, if you are using old-fashioned perforated boards and time-consuming soldering. With PROTO-BOARDS any component can be plugged in, tested, removed, and used again. Circuits can often be designed from component pinouts and the circuit diagram does not need to be drawn until after the circuit is working properly. PROTO-BOARD designing is very much like careful single-sided printed circuit design in terms of the effects of parasitics and in terms of operation at high frequency or low levels. Well-planned grounds and judicious use of shielded cable can permit operation through VHF frequencies. So, you old solderers, stop soldering on! Send off for our FREE 40 page catalogue; we have a PROTO-BOARD to fit any size budget.



PROTO BOARDS

Models PB 20C, PB 203A and PB 203AK offer a large breadboarding area and a built in regulated power supply housed in a rugged metal cabinet. Models PB6 to PB105 offer various breadboarding areas screw mounted onto sturdy back plates with non-slip, non-scratch vinyl feet. Red and black binding posts are included, the red being electrically insulated from the back plate, the black being electrically connected for ground.

PB 203
Includes 5VDC, 1 amp power supply, available at binding posts; two binding posts (V1, V2) remain uncommitted. The perfect board for TTL and other 5 volt logic designs.

PB 230A
Every development engineer should have one of these, includes 5VDC, 1 amp power supply. Also includes separate + 5.5 to 18 VDC and - 5.5 to 18 VDC power supplies, each capable of supplying 500 mA at 15 VDC. Power supplies are factory preset to +/- 15 VDC but can be independently adjusted.

PB 203AK
Identical to PE 203A but in kit form.

PB 6
A kit form breadboard with 4 binding posts, 630 contact points and includes non-slip rubber feet.

PB 100
Another kit form breadboard with 760 contact points.

PB 101
A robust laboratory breadboard accepts up to 10 IC's, 940 contact points.


PB 102
A fully assembled breadboard with 1240 contact points.

PB 103
With 2250 contact points this board is perfect for prototyping and custom circuit applications.

PB 104
A total IC capacity of 32 with 3060 contact points makes this the ultimate electronics development engineers breadboard.

PB 105
The newest Protoboard, 4560 contact points, 48 IC capacity.

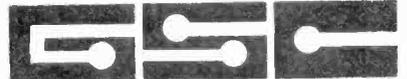G.S.C. (UK) LIMITED
UNIT 1, SHIRE HILL INDUSTRIAL ESTATE
SAFFRON WALDEN, ESSEX CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477



PRACTICALLY ALL THE PARTS FOR WIRELESS ENTHUSIASTS (and Computing, Electronics, Audio) & Video Enthusiasts too!!



The Spring '83 catalogue continues to expand to meet the needs of the electronics user — from the novice enthusiast to the professional aerospace designer.

AT YOUR NEWSAGENT OR DIRECT



ambit INTERNATIONAL

200 North Service Road,
Brentwood, Essex CM14 4SG
Telephone (Consumer Sales/Enquiries) 0277-230909 — Telephone (Industrial Sales/Enquiries) 0277-231616 —
Telex 995194 AMBIT G
Data 24hrs (RS232/300baud) 0277-232628 —
REWTEL

- Prices exclude VAT except where otherwise shown
- Postage and Packing 60p per pre-paid order
- Orders submitted using Ambit Stock Codes will be processed first
- Orders for in-stock items processed same day
- Hours — (consumer sales) 8am-7pm Mon-Sat: (Industrial) 8am-6pm (Mon-Fri)



INCLUDING
3 x £1 VOUCHERS

WW - 041 FOR FURTHER DETAILS

NEW Get started in Fibre Optics

... with our new fibre optic experimental kit.

£34.17 + VAT

Features include:

- 0-10Mbit/s (NRZ) guaranteed to 15m with Polymer Cable. (Can be extended by using a glass fibre).
- TTL Compatible.
- No tools required to terminate cable.
- Fully tested modules.
- Complete with transmitter, receiver connectors and 5m of Polymer Cable.
- Also a full range of components for glass systems available.

Electroustic Ltd.
9 Step Terrace, Winchester, Hants.
Tel. 0962 60916. Telex: 877255

WW - 007 FOR FURTHER DETAILS

CLEF ELECTRONIC MUSIC

PIANOS

SPECIALISTS SINCE 1972
DOMESTIC OR STAGE
SIX OR 7 1/4 OCTAVES
KITS OR MANUFACTURED

The most advanced form of touch-sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

Component Kits include Keyboard.

Full Kits further contain Cabinets, Harness, Power Amp and Speaker.

	SIX	7 1/4
Comp	234	266
Full	398	442
MFD	620	695

Kit BAND-BOX

£314
Mfd
£439

VOCAL & INSTRUMENTAL SOLOISTS!

An Electronic Backing TRIO. Drums, Bass & Chord Instrument. User Programmable for 50-100 scores, using microprocessor.

MASTER RHYTHM DRUM MACHINE

User Programmable. Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation.

£79 KIT E119 BUILT

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr. & Ins and we operate Telephone BARCLAY-CARD/ACCESS. Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED
Dept. W, 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 025 FOR FURTHER DETAILS

RADIATION DETECTORS

BE PREPARED VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH
- 0-5 R

British design & manufacture
Tested and fully guaranteed. Ex-stock delivery.
As supplied to Fire Services/Civil Defence

FREE RECHARGE SERVICE AFTER PURCHASE

£6.95
Add. VAT, Post & Packing


COMPLETE WITH DATA

Henry's Official Orders welcome
01-723 1008/9

CALLERS: 404 EDGWARE ROAD, LONDON W2 1ED
Mail Orders/Export Enquiries to: 11-12 Paddington Green, London W2

SINEWAVE INVERTERS


— FROM CARACAL 200-1000 VA

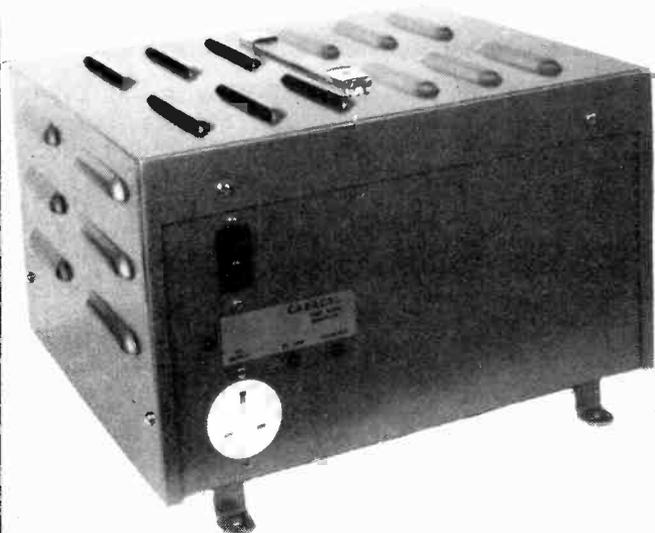

Caracal offer you the U.K.'s widest range of high-quality static inverters. Our inverters are used in many countries throughout the world wherever a reliable and stable source of A.C. power is needed for computers, communications, instrumentation, etc. They are also frequently used for mobile or marine applications where only a D.C. source is available.

Caracal inverters employ modern pulse width modulation technology which is replacing obsolescent tuned-type (ferro-resonant) inverters, by giving higher efficiency throughout the load range, very low standby current, and lower weight.

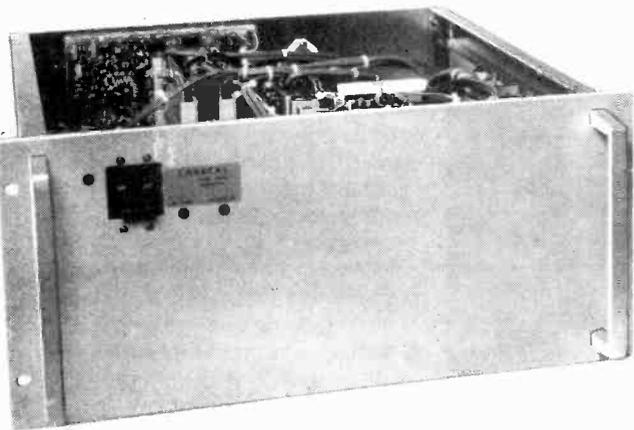We have a large range of models and options, at competitive prices, to suit your exact requirements.



19-INCH RACK MOUNTING

Now all inverters are also available in 19-inch chassis form for rack mounting.

CARACAL

Export enquiries welcome

CARACAL POWER PRODUCTS LIMITED
42-44 SHORTMEAD STREET, BIGGLESWADE, BEDFORDSHIRE
Telephone: 0767 260997

Midwich

COMPUTER COMPANY LIMITED

1st choice for microcomputer components

BBC MICROCOMPUTERS

Model B 346.95
Model B + Disc Int. 441.95

BBC MICRO DISC DRIVES

BBC31 Single 100K 229.00
BBC32 Dual 100K 340.00
BBC34 Dual 400K 649.00
All disc drives include all Cables, Manual & Utilities Disc.

BBC MICRO UPGRADE KITS

BBCA2B Complete A TO B 44.75
BBC1 16K Memory 18.00
BBC2 Printer 7.50
BBC3 Disc 95.00
BBC4 Analogue 6.70
BBC5 Serial & RGB 7.30
BBC6 Bus 6.45
Filing service available.

BBC MICRO CONNECTORS

BBC21 Printer Cable 13.00
(not assembled)
BBC22 User Port Connector & Cable 2.46
BBC23 Cassette Lead 3.50
BBC24 7 Pin Din Plug 0.60
BBC25 6 Pin Din Plug 0.60
BBC26 5 Pin Din Plug 0.60

BBC MICRO ACCESSORIES

BBC45 Joysticks 11.30
BBC67 Eprom Programmer 57.95

BBC MICRO SOFTWARE

View Wordprocessor 52.00
1.0 M.O.S. 36.00

ACORN SOFT

Full range available. Please telephone for stock position.

MEMORIES

2114L 200NS D1 0.80
2708 450NS D2 2.95
2716 450NS D1 2.45
2716 350NS D1 4.95
2716 3 Rail D1 7.25
2532 450NS D2 3.45
2732 450NS D1 3.45
2732 350NS D1 5.45
2764 300NS D1 7.95
4116 150NS D1 0.85
4116 200NS D2 0.80
4118 150NS D1 3.25
5516 200NS D2 9.45
6116 150NS D1 3.30
6116 Low Power 150NS D2 4.95
4164 200NS TI D3 3.95
4164 200NS NEC D3 3.95
4516 4816 100NS D2 2.25
4532 200NS D2 2.95

6800 FAMILY

6800 D7 2.25
6802 D5 2.50
6809 D6 6.30
6810 D1 1.15
6821 D3 1.00
6840 D4 3.75
6845 D5 6.50
6850 D2 1.10
6848 D2 7.30
6890 D7 5.25
68B09 D6 12.00
68B10 D1 2.26
68B21 D3 2.20
68B40 D4 6.00
68B50 D2 2.20

Z80 FAMILY

Z80 ACPU D2 2.99
Z80 BCPU D2 9.00
Z80 ACTC D1 2.60
Z80 BCTC D1 9.00
Z80 ADART D1 5.50
Z80 ADMA D2 6.95
Z80 AP10 D1 2.75
Z80 BP10 D1 9.00
Z80 AS10 D4 9.00

8080 FAMILY

8085A D4 3.50
8212 D1 1.10
8216 D1 1.00
8224 D1 2.10
8228 D1 3.27
8251A D5 2.50
8253 D5 4.00
8255A D5 2.25

6500 FAMILY

6502 D3 3.25
6502A D3 5.00
6520 D1 2.50
6520A D1 3.16
6522 D5 3.00
6522A D5 5.50
6532 D2 5.50

FLOPPY DISC CONTROLLERS

8271 36.00
FD1771 D5 15.00
FD1791 D6 22.00
FD1793 D6 23.00
FD1795 D6 28.00
FD1797 D6 28.00
WD1691 D2 12.00
WD2143-01 D2 6.99

INTERFACE DEVICES

6402 3.80
75107 0.47
75110 0.56
75150 0.64
75154 0.77
75160 2.56
75161 2.80
75162 3.95
75172 1.95
75173 1.44
75174 1.95
75175 1.44
75182 0.50
75183 0.50
75188 0.37
75189 0.37
75451 0.22
75452 0.22
75453 0.22
75454 0.22
75468 0.88
75491 0.31
75492 0.42

BBC MICRO CONNECTORS

AY31015 D2 3.00
AY31270 6.47
AY38910 D6 4.40
AY53600 D2 6.70
DP8304 D1 2.50
MC1488 D1 0.37
MC1489 D1 0.37
NC3242A 6.30
MC3446 D1 2.50
MC3448A D1 3.75
MC3480 D5 7.30
MC3487 D1 2.00
MC14411 D1 7.65
MC14412 9.45
RO32513L D1 6.50
RO32513U D1 6.50

UMF MODULATORS

UM1111 8MHZ D1 2.60
UM1233 8MHZ D1 3.90

BUFFERS

81L595 0.80
81L596 0.80
81A597 0.80
81L598 0.80
8T26A 0.90
8T28A 0.90
8T95 0.90
8T97A 0.90
8T98 0.90

LINEARS

L203 0.65
LF398N 4.75
LM301AN 0.24
LM308N 0.48
LM311P 0.50
LM319N 1.99
LM324N 0.30
LM348N 0.60
NE555P 0.16
NE556CP 0.45
TL010 0.39
TL061 0.29
TL062 0.49
TI064 0.98
TL066 0.29
TL071 0.29
TL072 0.47
TL074 1.00
TL081 0.26
TL082 0.46
TL084 1.58
TL091 0.40
TL092 0.58
TL094 1.34
TL487 0.62
TL489 0.62
TL494 1.63
TL496 0.60

SPECIAL OFFER! SPECTRUM 32K UPGRADE KIT £24.95

Carriage Orders up to £199 are sent by 1st class post, and £200+ by Securicor.
0-£100 0.50 £100-£199 1.25 £200 + 5.00 by Securicor.
Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice.
Quantity Discounts are available on many products, please ring for details.
Official Orders are welcome from Education Establishments, Government Bodies and Public Companies.
Credit Accounts are available to others subject to status. Payment is due strictly net by the 15th of the month.
Credit Cards are accepted (Access and Visa) for telephone and postal order and NO SURCHARGE is made.
Out of stock items will follow automatically, at our discretion, or a refund will be given if requested.

THE ABOVE LIST SHOWS JUST A FEW OF THE ITEMS IN STOCK. PLEASE TELEPHONE YOUR REQUIREMENTS - OR BETTER STILL SEND FOR OUR FREE CATALOGUE

Please complete this coupon for a copy of our FREE catalogue

NAME _____

ADDRESS _____

TEL NO _____

MIDWICH COMPUTER COMPANY LIMITED
RICKINGHALL HOUSE, RICKINGHALL, SUFFOLK IP22 1MH
TELEPHONE (0379) DISS 898751

WW - 061 FOR FURTHER DETAILS

THE FACE THAT 657 ST



It's Maria's.

She's the sylph on the front of all the tickets we're giving away for The All-Electronics/ECIF Show - and its sister events.

(Just to brighten your day before you plan your visit!)

Her story's simple. Use the coupon and you'll get a season ticket for a week of elucidation.

Three events. For free!

First, the Show of shows

You may visit 450 All-Electronics/ECIF stands at the Barbican in air-conditioned, carpeted comfort free of charge - if you use the coupon on the right.

You may also have the 120-page 'Morgan-Grampian' guide to both the industry and the event absolutely free as well (if you kindly allow us 26p for postage and packing).

Now the ticket will also gain you free entry to our other simultaneous events

'Circuit Technology' at the Kensington Exhibition Centre; and 'Fibre Optics' in the adjacent-to-the-Barbican Porter Tun Room

There has never, ever, been such an opportunity to glean the facts and figures from Component and Instrument manufacturers and, as an innovation in '83, the PCB and Fibre Optics industries.

A refreshing scope of options that can be yours as fast as you can spell Agamemnon.

And for a fiver...?

In conjunction with 'Electronics Times' we proudly present 'The Business of High Technology.'

Four of the world's most honoured specialists revealing industry trends in an action-packed, three-hour session

(Come in the morning, or the afternoon, our programme is duplicated)

We're catering for no fewer than 2,500 people at each session; and, of course, you can see the exhibition as well - either before or after.

The setting is the most prestigious in Britain: The Barbican's Concert Hall, of which Her Majesty the Queen said, "It must have claim to be one of the modern wonders of the world"

Sit in luxury - and hear from Wilf Corrigan, Founder and President, LSI Logic; 'Semi-Custom Circuits' Pasquale Pistorio, Chief Executive Officer, SGS; "The European Semiconductor Industry," John Alvey, Senior Technical Director, British Telecom; "Fifth Generation British Computers," Derek Roberts, Director of Research, GEC; "Key Technology, the User's View." The overall title The future of electronics and the business of high technology

All for only a five pound note! (Order form alongside)

ALL LAUNCH ANDS

Go and see...

It's a 50-yard walk from the Barbican's Hall to the Porter Tun Room.

And we've there-and-back buses on the hour, every hour, betwixt Kensington and the Barbican for those interested in Circuit Technology and the AES.

Top: Fibre Optics (so far); Middle CT.; Bottom AES.

Amphenol; Ampicon; Belling & Lee; Bentham Instruments; BCC General Cables; Cossor Electronics; Dynacast International; Ealing Beck; Eurotec Optical Fibres; Fibre Optiques Industries; GEC Optical; Hellermann Deutsch; Honeywell Control; Hopkin & Williams; ITT - Cannon; ITT Components; Lambda Photometrics; Laser Lines; Leotec; MCP Electro Optics; McMichael; Melles Griot; Norbain Electro Optics; Optical Fibres; Oriol Scientific; Pilkington Fibre Optic Technologies; Pirelli General; Plessey Semiconductors; Prior Scientific Instruments; Production Techniques; Rofin; SIRA; Standard Telephone & Cables; Suhner Electronics; Systems Production; TBL Fibres; Thomson CSF; Time & Precision; Vickers Instruments; Walmore; York Technology;

Alpha Metals Arnold Electronics Argos Electronics AEG-Telefunken (UK), Anda Circuits BPA Technology & Management G Bopp & Co. Bobby Tempest & Associates Bush Beam Engineering Coates Special Products Chemtec Solutions Circuit Foto Products Group R&D Cochrane & Johnson Ciba-Geigy Plastics & Additives Co. Computation Digital Data Electronics DPC Electronics Dek Printing Machines Degussa Dorviver Du Pont De Nemours International SA Du Pont UK Dymet Alloys EGM Solders Exalta Circuits Electrochemicals Engelhard Industries Electrovert Excellon Finlay Microvision Co. Ferranti Computer Systems Fischer Instrumentation (GB) Fry's Metals G&H Electrographics GTS Flexible Materials GSPK (Circuits) Gemini Electronic Developments Hunter Equipment Sales Instagraphics Products International Tin Research Inst. Imasa ITT/Cannon Electric GB Kam Circuits Lamco Litton Precision Products Int Inc Lea-Ronal UK M&T Chemicals MEPD MacDermid GB Multicore Solders Manchester Circuits McGregor Industries Murhead Vetric Components Marconi Norplac UK Div LOP Nevil Electric Holdings New England Laminates Oxy Metal Industries (Sci Res) Division Packman Research Prestwick Circuits Photopolymer Systems Photoprinting Products Planer Products Protokote Robertsons Chemicals Rexham UK Selectrons Shipley Chemicals Systems Efficiency Serfilco UK Scientific & Electronic Enterprises SBEEL Sarat Process Photography Thiokol Chemicals Vero Advanced Products Vision Engineering Veratronic VM Circuit Equipment W Canning Materials Welwyn Printed Circuit Services

AB Electronic Products Group; AEG Telefunken (UK); AMF Potter and Brumfield; AMI Microsystems; AVX; Able Systems; Adcola Products; Allen Bradley Electronics; Alma Components (ESY); Alusett UK; Ambar Components; Ampicon Electronics; Analog Devices; Anders Electrical; Anglia Components; Aerial Pressings; Anes Electronics (Europe); Armon Electronics; Arrow Hart (Europe); Ashburn Resistance Co.; Ashcroft Electronics; Assman Electronics; Astralux Dynamics; Augat; BFI Electronics; BiCC General Cables; BIOC Vero Electronics; Bach Simpson (UK) B and R Electrical Products; Bahco Record Tools; FWO Bauch; Beclere; Bell & Howell; Black Star; Boxer Marketing; Brandenburger; Britcint International; Britmpex; British Standards Institution; Broycy Marvid; AFBulgin & Co.; CGS Resistance Co.; CRP Electronics; Calex Electronics; Cambion Electronic Products; Cambridge Electronic Ind.; Campbell Collins; Capital Electronic Developments; Celab; Centronic; Cherry Electrical Products; Ciba-Geigy Plastics Division; Citec; CP Clare Electronics; Coden Engineering; Collett Terminals; Compstock Electronics; Conductive Products; Contraves Industrial Products; Cooper Tools; Corintech; Corning (Electrovis Division); Coutant Electronics; Cox; Crichtley Brothers; Custom Cases; DAT Engineering Co.; DAU (UK); Dage Eurosem; Danavox (Great Britain); Danbridge UK; Datacapture; Data International Incorporated; Datic; Daturr; S Davall & Sons; Dean Electronics; Diamond H Controls; Digitran UK; Drake Transformers; Dubiler Components; Duracell UK; Duralith Corporation; ERG Components; ETRI Fans; East Grinstead Elec.; Electronic Components Ind. Fed.; Electronics Weekly; Electrautom; Electronic Components; Electroplan; Electrothermal Engineering; Enclosure Technology; English Electric Valve Co.; G English Electronics; Exacta Circuits; FR Electronics; Farnell Electronic Components; Farnell Instruments; Farnell International Instruments; Felco; Ferranti Electronics; Fieldtech Heathrow; Flair Electronic Systems; GE Electronics (London); General Instrument; Microelectronics; Genrad; Gentech International; Gitech; Gould Power Supplies UK; Graphic Electronics; Greendale Electronics; Greenpar Connectors; Gresham Lion; Groatmoor; Hakuto International UK; Harmin Electronics Europe; H and T Components; H B Electronics; Harris Systems; Harrow Scientific; Harting Elektronik; Harwin Engineers SA; Hawke Electronics; Hayden Laboratories; Healey Meters; Hesto (Henkels Stockol); Highland Electronics; Hinchley Engineering Co.; Hitachi Denshi (UK); Hitachi Electronic Components (UK); Hivolt Capacitors; Holden and Fisher; Holsworthy Electronic (Sales); Honeywell Control Systems; House of Instruments; Howells Radio; Hunting Hivolt; Hybrid Systems; Hypertac; I and J Products; IC Master; ICC Information Group; IDD Crystal Electronics; ITT Cannon; SIT; Components Group; ITT Semiconductors; ITT Switches (UK); Imhof Bedco Stand Products; Industrial Science; Imo; Instelec; The Institution of Elec. Eng.; Intel Electronics Group; International Rectifier Co. (GB); Intersil Datal (UK); Intime Electronics; Irlandus Circuits; Iskra; Ivc Counters; Jackson Brothers; Kelvin Impex; Kemo; Klippon Electricals; Lambda Electronics; FC Lane Electronics; Lawtronics; Leonische Drahtwerke AC Nurnberg; Lee Green Precision Inds.; Lemo UK; Light Soldering Developments; Littix; Littelfuse (GB); Londex; Longs; Lyons Instruments; 3M United Kingdom; Microtesting; The McMurdo Instrument Co.; Marconi Instruments; Metway Electrical Industries; Micro Circuit Engineering; John Minster Instruments; Mitsubishi Electric (UK); Molex Electronics; Mostek (UK); Moulded Electronic Components Int.; Multair; Murata Erie Electronics; NFI Electronics; NSF; National Panasonic (UK); Neom (UK); Newport Components; Nietronix; OK Machine & Tool (UK); Optima Enclosures; Oxley Developments; PSP Electronics; Papst Motors; Parmeko; Pelco (Electronics); Pickering Electronics; Plessey Circuits; Plessey Connectors; Plessey Hybrids; Plessey Semiconductors; Portescap (UK); Powerline Electronics; Powertron; Precicontact; Precision Metal Depositors; Precision Circuits; Precision Components & Equipment; Precision Instruments; Preformations (Magnets); Pressac; Print Service BV; Protech BPL; Protronix 24; Pulsetek; Pye Unicam; Quadrant Meter Company; Quiller Components; RF Components; RS Components; Racal Dana Instruments; Radatron; Radialtron Components; The Radio Resistor Company; Radio & Electronics World (AMBIT); Radiotron (UK); Rainford Metals; Raytheon Semi-Conductor; REMO Components Group; Redpoint; EG

& G Reticon; RIFA AB; Richo International; Rittal; Roadrunner Electronic Products; Rockwell; Salford Electrical Instruments; Sealectro; Settek Instruments; Schroff UK; Semelab; Semiconductor Specialists (UK); Semtech; Sternice; Siemens; Sifam; Siliconix; Souriau (UK); Spectrol Reliance; Sprague Electric (UK); Star Systems (RHB); Steatite Insulations; Stocko (Meta Works); Stotron; Sulflex; Superflexit-Icore; Suwicon; Swissino; Symec Electronics; Synchro Services; TRW Carr; am Systems; Technation; Techni Measure; Tekelec Components; Tekras; Teledyne Philbrick; Tele Haase Stovergalt-SmbH; Telonic Berkeley (UK); Tempatron; Temco Distribution; Thandar Electronics; Thame Components; Thomson - CSF; Thorn Brimar; Today Electronics; Townsend Coates; Transradio; Trident Engineering; Ultra Electronic Components; United Electronics; VSI Electronics (UK); VTM (UK); Vako Electronics; Variomh Components; Varta; Vishay Resistor Products (UK); Vitramon; W Electronics; WKR; Wallis Electronics; Welwyn Electric; Weir Electronics; Wescorp Europe; Wessex Advanced Switching Prods.; West Hyde Developments; Widney Dorlec; Wilsher & Quirk; Winslow International

The stand numbers for all three events are given in the Morgan-Grampian catalogue. And so are details of all the conference programmes at all three events.

We're working like Trojans for the industry as a whole - and not just YOU.

This is no ordinary exhibition week.

All the key industry influences will be attending our seminars and conferences.

All the folks with vacancies (or with CV's!) will be parading the aisles.

All... well, in simple terms, 'The Show' is the recognised annual occasion when everyone gets together to swap news, views, trends and friends. Freely.

The Tobie Awards

The pre-eminence of 'The Show' is augmented by its 'TOBIE' awards - to be presented, this year, at the Electronics Shows' Ball at the Dorchester.

Last year's winners were:

NEW PRODUCT OF THE YEAR Ferranti FAB-2 Ferranti Electronics Ltd. **RESEARCH ACHIEVEMENT OF THE YEAR** Laser Gyro Inertial Navigation System **EXPORTER OF THE YEAR** Sinclair Research Ltd. **ELECTRONIC APPLICATION OF THE YEAR** Songuard Burglar Alarm Eurolec Group Ltd. **PERSONALITY OF THE YEAR** Robb Wilmot, ICL **DISTRIBUTOR OF THE YEAR** Memec Ltd.

And this year? Watch E.T.'s space!

In short, if you don't make it to London the industry will be all Greek to you...

How to get to the Barbican/Kensington Exhibition Centre/Porter Tun Room.

The Barbican: Tube to Barbican Station. 400 yards straight ahead from the exit. And you're there.

Kensington: Tube to Kensington High Street. Walk through shopping arcade. Turn right, and right again. In 100 yards you've made it.

Porter Tun Room: Leave 'The Show'. Turn left into Beech Street. And it's 50 yards on the right past the cross roads.

Remember - on the hour, every hour, there are buses from Kensington to the Barbican. Fui! details on your ticket and in the catalogue; both free. And it beats horse-riding any day.

To: Pat Rusted, The Hub, Emson Close, Saffron Walden, Essex, CB10 1HL

Please send me a free season ticket to The All-Electronics/ECIF Show, Circuit Technology and Fibre Optics.

Please send me a free 'Morgan-Grampian' catalogue for all three shows, for which I enclose postage stamps for p & p (26p please).

Please send me details of the various seminars and conferences running during 'the week'.

Name: _____


Company: _____

Address: _____

40010

For catalogue please attach 26p in stamps lightly by their corner to this coupon.

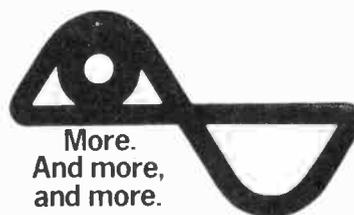THE ALL-ELECTRONICS/ECIF SHOW. THE BARBICAN. APRIL 19-21, 1983.
FIBRE OPTICS '83. THE PORTER TUN ROOM. APRIL 19-21, 1983.
CIRCUIT TECHNOLOGY '83. KENSINGTON EXHIBITION CENTRE. APRIL 18-20, 1983.



The Hub, Emson Close, Saffron Walden, Essex, CB10 1HL Tel: (0799) 26699 Telex: 81 653



MODEL 10280 A
2K MEMORY DEPTH
TO 4MHz CLOCK
£747
EX. VAT

- A HIGH PERFORMANCE, LOW COST, POWERFUL 'IN CIRCUIT' TOOL TO DEBUG THE MOST RANDOM FAULT OR SIMPLY STUDY PROGRAM FLOW.
- OSCILLOSCOPE TRIGGER AT END, START OR DELAYED ON START, DELAY IN MACHINE OR CLOCK CYCLES.
- 19" RACK MOUNTABLE.
- SELECTABLE AUTOMATIC CHANGEOVER TO DMA ON BUSAK ACTIVE.
- BOTH START AND END ACQUISITION CONDITIONS SELECTABLE FROM STATE OF ADDRESS AND DATA BUS TO STATE OF SINGLE DATA BIT.
- END ACQUISITION ALSO INCLUDES A START TO END LOGICAL COMPARISON (AND, NAND, OR, NOR, XOR, NXOR) INDEPENDENTLY SELECTABLE ON EACH DATA BIT.
- 12" DISPLAY MONITOR.
- PRINTER OUTPUT FOR A HARD COPY COMPARE TO YOUR LISTING.
- ALL PRICES EXCLUDE VAT CARRIAGE AND PACKING £12.

SPECIFICALLY DESIGNED FOR THE

Z80

BASED SYSTEM
4, 6 OR 8 MHz

This **MACHINE CYCLE LOGIC STATE ANALYSER** gives a logic state map of 37 active pins of the CPU to a depth of 2048 (or 4096*) machine cycles leading up to a preset conditional break. Passive, timed by the target system clock, the analyser samples the address, data and control buses simultaneously with the CPU and stores them with an elapsed M cycle and clock count. Specific machine cycles may be excluded to increase the apparent memory depth. Up to FFF delay on start/end acquisition condition true.

*Available with 2K or 4K memory depth and 4, 6 or 8 MHz speeds.

FULL SPECIFICATION AND DETAILS


SEYKER

LIMITED

First Floor, 18A Bridge Street, Godalming, GU7 1HY. Telephone 048 68 20924

WW - 032 FOR FURTHER DETAILS

Quartz Oscillators

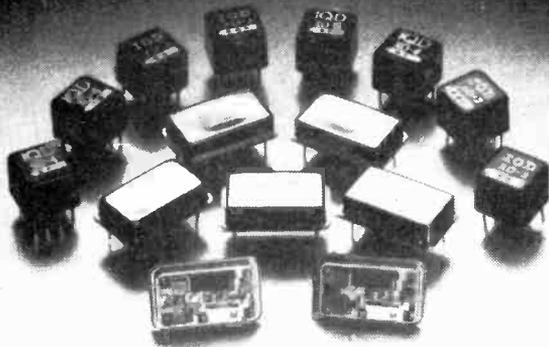

DIL compatible configurations
CMOS and TTL outputs
Wide temperature ranges
Frequencies one pulse per day to 60 MHz
Many standard frequencies from stock

Interface
Quartz
Devices
Limited

More details of specifications from

IQD

29 Market Street
Crewkerne
Somerset TA18 7JU

Crewkerne (0460) 74433
Telex 46283 inface g

WW - 014 FOR FURTHER DETAILS

RADIOCODE CLOCKS

are powerful and comprehensive instruments which receive, decode and analyse time-coded standard frequency transmissions to provide accurate, secure and completely automatic time/calendar or synchronisation systems.



Applications

- Automatic master clock and slave controller.
- Synchronisation of separate equipment and events.
- Programmable energy management system.
- Computer clock/calendar with battery backup.
- Data logging and time recording.
- Process and equipment control.
- Broadcasting, Astronomy, Navigation.
- Satellite tracking.

If you have a time or synchronisation problem, write or phone for further details of our portable and new microcomputer-controlled Radiocode Clocks.

Circuit Services, 6 Elmbridge Drive
Ruislip, Middlesex. Ruislip 76962

WW - 022 FOR FURTHER DETAILS

TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

***Gold service available.
21 days manufacture for urgent deliveries.**

***Orders despatched within 7 days of receipt for single or small quantity orders.**

***5 year no quibble guarantee.**

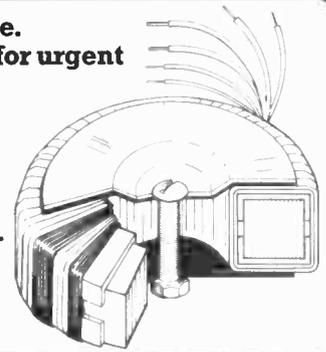

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE																														
<p>NEW! NEW! NEW!</p> <p>15 VA 0x010 6+6 1.25 62 x 34mm 0x011 9+9 0.83 0.35Kg 0x012 12+12 0.63 Regulation 0x013 15+15 0.50 19% 0x014 18+18 0.42 0x015 22+22 0.34 0x016 25+25 0.30 0x017 30+30 0.25</p> <p>£5.12 + p & p £0.78 + VAT £0.89 TOTAL £6.79</p> <p>(encased in ABS plastic)</p>					<p>120 VA 4x010 6+6 10.00 90 x 40mm 4x011 9+9 6.66 1.2Kg 4x012 12+12 5.00 Regulation 4x013 15+15 4.00 11% 4x014 18+18 3.33 4x015 22+22 2.72 4x016 25+25 2.40 4x017 30+30 2.00 4x018 35+35 1.71 4x028 110 1.09 4x029 220 0.54 4x030 240 0.50</p> <p>£7.42 + p & p £1.72 + VAT £1.37 TOTAL £10.51</p>					<p>300 VA 7x013 15+15 10.00 110 x 50mm 7x014 18+18 8.33 2.6Kg 7x015 22+22 6.82 Regulation 7x016 25+25 6.00 6% 7x017 30+30 5.00 7x018 35+35 4.28 7x026 40+40 3.75 7x025 45+45 3.33 7x033 50+50 3.00 7x028 110 2.72 7x029 220 1.36 7x030 240 1.25</p> <p>£10.88 + p & p £2.05 + VAT £1.94 TOTAL £14.87</p>					<p>30 VA 1x010 6+6 2.50 70 x 30mm 1x011 9+9 1.66 0.45Kg 1x012 12+12 1.25 Regulation 1x013 15+15 1.00 18% 1x014 18+18 0.83 1x015 22+22 0.68 1x016 25+25 0.60 1x017 30+30 0.50</p> <p>£5.49 + p & p £1.10 + VAT £0.99 TOTAL £7.58</p>					<p>160 VA 5x011 9+9 8.89 110 x 40mm 5x012 12+12 6.66 1.8Kg 5x013 15+15 5.33 Regulation 5x014 18+18 4.44 8% 5x015 22+22 3.63 5x016 25+25 3.20 5x017 30+30 2.66 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66</p> <p>£8.43 + p & p £1.72 + VAT £1.52 TOTAL £11.67</p>					<p>500 VA 8x016 25+25 10.00 140 x 60mm 8x017 30+30 8.33 4Kg 8x018 35+35 7.14 Regulation 8x026 40+40 6.25 4% 8x025 45+45 5.55 8x033 50+50 5.00 8x042 55+55 4.54 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08</p> <p>£14.38 + p & p £2.40 + VAT £2.52 TOTAL £19.30</p>					<p>50 VA 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 13% 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p> <p>£6.13 + p & p £1.35 + VAT £1.12 TOTAL £8.60</p>					<p>225 VA 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 7% 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p> <p>£9.81 + p & p £2.05 + VAT £1.78 TOTAL £13.64</p>					<p>625 VA 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.81 Regulation 9x025 45+45 6.94 4% 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60</p> <p>£17.12 + p & p £2.55 + VAT £2.95 TOTAL £22.62</p>				
<p>30 VA 1x010 6+6 2.50 70 x 30mm 1x011 9+9 1.66 0.45Kg 1x012 12+12 1.25 Regulation 1x013 15+15 1.00 18% 1x014 18+18 0.83 1x015 22+22 0.68 1x016 25+25 0.60 1x017 30+30 0.50</p> <p>£5.49 + p & p £1.10 + VAT £0.99 TOTAL £7.58</p>					<p>160 VA 5x011 9+9 8.89 110 x 40mm 5x012 12+12 6.66 1.8Kg 5x013 15+15 5.33 Regulation 5x014 18+18 4.44 8% 5x015 22+22 3.63 5x016 25+25 3.20 5x017 30+30 2.66 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66</p> <p>£8.43 + p & p £1.72 + VAT £1.52 TOTAL £11.67</p>					<p>500 VA 8x016 25+25 10.00 140 x 60mm 8x017 30+30 8.33 4Kg 8x018 35+35 7.14 Regulation 8x026 40+40 6.25 4% 8x025 45+45 5.55 8x033 50+50 5.00 8x042 55+55 4.54 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08</p> <p>£14.38 + p & p £2.40 + VAT £2.52 TOTAL £19.30</p>					<p>50 VA 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 13% 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p> <p>£6.13 + p & p £1.35 + VAT £1.12 TOTAL £8.60</p>					<p>225 VA 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 7% 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p> <p>£9.81 + p & p £2.05 + VAT £1.78 TOTAL £13.64</p>					<p>625 VA 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.81 Regulation 9x025 45+45 6.94 4% 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60</p> <p>£17.12 + p & p £2.55 + VAT £2.95 TOTAL £22.62</p>																			
<p>50 VA 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 13% 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p> <p>£6.13 + p & p £1.35 + VAT £1.12 TOTAL £8.60</p>					<p>225 VA 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 7% 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p> <p>£9.81 + p & p £2.05 + VAT £1.78 TOTAL £13.64</p>					<p>625 VA 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.81 Regulation 9x025 45+45 6.94 4% 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60</p> <p>£17.12 + p & p £2.55 + VAT £2.95 TOTAL £22.62</p>																																		

The benefits of ILP toroidal transformers
 ILP toroidal transformers are only half the weight and height of their laminated equivalents and are available with 110V, 220V or 240V primaries coded as follows

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

For 110V primary insert '0' in place of 'X' in type number
 For 220V primary (Europe) insert '1' in place of 'X' in type number
 For 240V primary (UK) insert '2' in place of 'X' in type number

Also available at Electrovalue, Maplin, Technomatic and Barrie Electronics.

For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd, Barclaycard/Access welcome. Trade orders standard terms.

Post to: ILP Electronics Ltd, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
 Telephone: (0227) 54778 Telex 965780



ILP TRANSFORMERS
 (a division of ILP Electronics Ltd)

WW - 054 FOR FURTHER DETAILS

LOW COST PROFESSIONAL TEST INSTRUMENTS

sabtronics
FREQUENCY METERS
 100MHz, 600MHz, and 1GHz Models
 from £67

Belemic
 Hand Held
 Analogue and
 Digital
 Multimeters
 16 Models
 from £18.75


electro
RST
 Belemic

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list
Black Star Ltd.
 9A, Crown Street
 St. Ives, Huntingdon
 Cambs. PE17 4EB
 Tel: (0480) 62440 Telex 32339

WW - 021 FOR FURTHER DETAILS

REGD. TRADE MARK

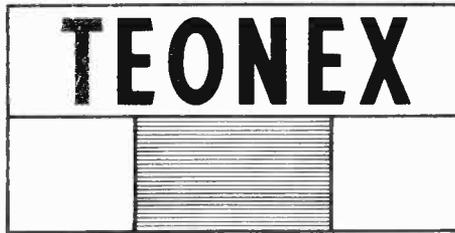

TEONEX ELECTRONIC VALVES AND SEMICONDUCTORS

SERVING THE WORLD FOR 30 YEARS


We specialise in the supply of Industrial Valves of British, European and USA manufacture, and semiconductors from the Philips Group. Many types, including obsolete and obsolescent types, always available from stock.

For further details, contact Mrs. Janet Lowy.

T.O. SUPPLIES (EXPORT) LTD., 2A Westbourne Grove Mews, London W11 2RY.
Telephone: (01) 727 3421 Telex: 262256 Answerback TOSPLY G

WW - 020 FOR FURTHER DETAILS

MANPACK EQUIPMENT

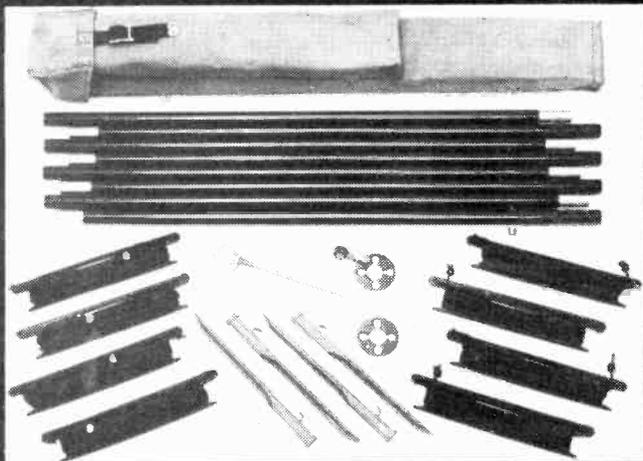

Collapsible aluminium or fibreglass masts with complementary portable antennas operating from 2-30MHz. Other manpack products include a light-weight fibre log periodic and 6 metre mast for frequencies between 24 and 87 MHz, tactical discons for 26-87 MHz and collapsible manpack whips.

South Midlands Communications Limited
SM House, Osborne Road
Totton, Southampton
Tel 0703 867333
Telex 477351 SMC0MM G



WW - 008 FOR FURTHER DETAILS

INSTANT PRINTED CIRCUITS!!

Make your own - to professional standards - within minutes using either "Fotolak" Light-sensitive Aerosol Lacquer or Pre-coated board. No Darkroom or Ultra-violet source needed!

Fotolak aerosol	£2.50 (30p)	Developer	£0.30 (15p)
Ferric Chloride	£0.60 (45p)	Acetate Sheet	£0.15 (15p)
Copper-clad Fibre-glass Boards:		Single-sided	£2 ft. sq. (45p)
		Double-sided	£2.25 ft. sq. (60p)

Pre-coated Fibre-glass Board:			
8" x 4 1/2"	£1.75 (25p)	16" x 9"	£7 (60p)
8" x 9"	£3.50 (45p)	24" x 12"	£13 (£1.20)
		24" x 18"	£18 (£1.70)
		Eurocard £1.25 (25p)	

Double-sided Board (all sizes) add 20%
Postage individual items in brackets. Maximum charge £2 per order

12V FLUORESCENT LIGHTING! FANTASTIC BARGAIN!

21" 13-watt Batten Type (complete with tube) £6 (£1.20)
Kit Form: £5 (£1.20). Inverter Transformers only: £1 (30p)

WHITE HOUSE ELECTRONICS PRAA SANDS, PENZANCE TR20 9TF
Telephone: Germoe (073-676) 2329

ScheTronics Limited

We offer the following services


- ★ Repair and calibration of precision electronic test equipment
- ★ Prototype wiring of P.C.Bs
- ★ Technical drawing facilities
- ★ Second user test equipment for sale

Unit 10, Dunstall Estate
Crabtree Manorway
Belvedere, Kent DA17 6AW
Telephone: 01-311 9657

WW - 049 FOR FURTHER DETAILS

The lightweight mast with 101 applications

25
years in this
specialist field

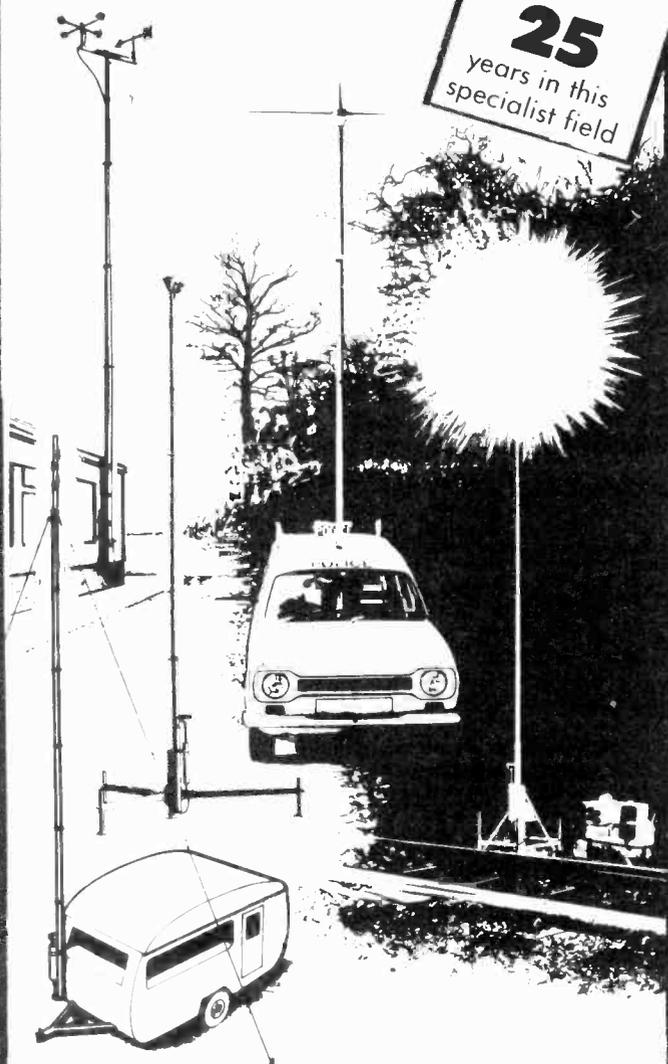

The smoothly operated QTM Mast comes fitted with handpump or can be vehicle mounted with 'Power Pack' for extension and retraction. Available in a range of heights up to 15 metres, the QTM mast can provide the ideal answer for.

- Mobile Radio Telephone
- Police Mobile HQ (UHF)
- Field Telecommunications
- Floodlighting
- Anemometer and Wind Measurement
- Environmental - gas sampling collector
- High level photography
- Meteorology
- And a host of other uses

CLARK MASTS

Find out more about the QTM series by writing or phoning:-

U.K.
CLARK MASTS LTD. (W.W.)
Evergreen House, Ringwood Road,
Binstead, Isle of Wight,
England PO33 3PA
Tel Isle of Wight (0983) 63691
Telex 86686

EUROPE
GENK TECHNICAL PRODUCTS N.V. (W.W.)
Woudstraat 21 3600 Genk,
Belgium
Telefoon 011-380831
Telex 39354 Genant B

WW - 028 FOR FURTHER DETAILS

CALL IN AND SEE
FOR YOURSELF


AUDIO ELECTRONICS

ALL PRICES
INCLUDE
VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY
OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)

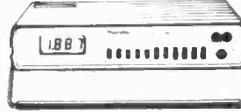

HAND HELD
KD25C* 13 range 0.2A DC 2 meg ohm £24.95
KD30C* 26 range 1A AC/DC 20 meg ohm £34.95
KD55C* 28 range 10A AC/DC 20 meg ohm £39.95
601D+ 22 range 10A AC/DC 20 meg ohm £34.40
703D+ As 601D but 0.1% basic £41.30
188M 16 range 10A DC 2 meg plus Hfe tester £39.95
189M 30 range 10A AC/DC 20 meg plus Hfe tester £69.95

HAND HELD AUTO RANGE
DM2350* 21 range 10A AC/DC 20 meg ohm (Miniature) £49.95
HD30 16 range 0.2A AC/DC 2 meg ohm £41.95
HD30/B As above plus cont. buzzer £44.50
HD31 22 range 10 AC/DC 2 meg ohms plus cont. buzzer £58.95

BENCH MODELS (3% digit unless stated)
TM353* 27 range LCD 2A AC/DC £86.25
TM355* 29 range LED 10A AC/DC £86.25
TM351* 29 range LCD 10A AC/DC £113.85
2D01 28 range LCD 10A AC/DC plus 5 range Cap. Meter with case £108.00
TM451 4% digit LCD every facility (0.02%) £171.00
1503a 4% digit LCD every facility (0.05%) £171.00
1503Ha 0.03% basic version of above £189.00
*Optional carry case £2.95 *With free carry case *Optional carry case £6.84



EDUCATIONAL DISCOUNTS AVAILABLE FOR ALL STOCKS PLEASE ENQUIRE

FREQUENCY COUNTERS



PFM200A 200 MHz hand held pocket 8 digit LED £67.50
8110A 8 digit LED bench 2 ranges 100 MHz £77.00
8610B 9 digit LED bench 2 ranges 600 MHz £113.85
8000B 9 digit LED 3 ranges 1 GHz £178.00
TFD40* 8 digit LCD 40 MHz £126.50
TF200* 8 digit LCD 200 MHz £166.75
*Optional carry case £6.84
Prescalers - Extended range of most counters
TP600 600 MHz £43.00
TP1000 1 GHz £74.00

SIGNAL GENERATORS (220/240v AC)

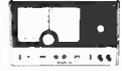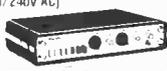

FUNCTION - All sine/square/triangle/TTL etc
TG100 1 HZ - 100 KHZ £90.00
TG102 0.2 HZ - 2 MHz £166.75
PULSE
TG105 Various facilities 5 HZ - 5 MHz £97.75
AUDIO - Multiband Sine/Square
LAG27 10 HZ to 1 MHz £86.00
AG20A 20 HZ to 200 KHZ £78.00
RF
SG402 100 KHZ to 30 MHz £59.95
LSG17 100 KHZ to 150 MHz £71.00

AUDIO • RF • FUNCTION • PULSE

ELECTRONIC INSULATION TESTER

YF 501 500 V/D-100m with carry case £63.00

MULTIMETERS (UK C/P 65p)

Y7206 20K/V 19 range pocket meter SPECIAL PRICE £7.95
C7081 50K/V 21 ranges Range doubler 10A DC SPECIAL PRICE £15.95
ETC5000/5001 21 ranges 50K/V Range doubler 10A DC £16.50
TMK500 23 ranges 30K/V 12A DC plus cont. buzzer £23.95
NH56R 20K/V 22 range pocket £10.95
EU102 14 range 2K/V pocket £5.95
830A 26 range 30K/V 10A AC/DC overload protection, etc £23.95
360TR 23 range 100K/V Large scale 10A AC/DC plus Hfe £36.95
AT1020 18 range 20K/V Deluxe plus Hfe tester £17.50
ST303TR 21 range 20K/V plus Hfe tester £16.95



VARIABLE POWER SUPPLIES

PP241 0/12/24V 0/1A £35.00
PP243 3 amp version £59.95 (UK C/P £1.00)



DIGITAL THERMOMETER

TH301 LCD 50 C to -750 with thermocouple £68.43



AC CLAMPMETER

ST300 0/300A 0/600 VAC 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50



LOGIC PROBES

LP10 10 MHz £28.50
LDP076 50 MHz £56.90



OSCILLOSCOPES



Full specification any model on request. SAE by post

HM Series HAMEG; SC THANDAR; CS Series TRIO; 3 Series CROTECH
SINGLE TRACE
3030 15 MHz 5mV 95mm tube plus component tester C/P £3.00 £172.50
SC110A* Miniature 10 MHz battery portable Post free £171.00
HM103 15 MHz 2mV 6 x 7 display plus component tester C/P £3.00 £177.00
*Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50
DUAL TRACE (UK C/P £4.00)
HM203/4 Dual 20 MHz plus component tester £276.00
CS1566A Dual 20 MHz All facilities £299.00
HM204 Dual 20 MHz plus component tester sweep delay £419.75
OPTIONAL PROBE KITS
X1 £7.95 X10 £9.45
X1 X10 £10.50 X100 £16.95

STOCKISTS FOR TRIO: HAMEG: CROTECH: SAFGAN SCDPES. MOST MODELS IN STOCK.

HIGH VOLTAGE METER

Direct reading 0/40 KV 20K/Volt (UK C/P 65p) £18.40



DIGITAL CAPACITANCE

0.1 pF to 2000 nF LCD 8 ranges DM6013 £57.95 (Carry case £2.95)



TRANSISTOR TESTER

Direct reading PNP, NPN, etc TC1 (UK C/P 65p) £21.95



AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564
ALSO AT HENRYS RADIO.
404/406 EDGWARE ROAD, LONDON W2


FREE CATALOGUES
SEND LARGE
SAE (UK 20p)

ALL PRICES
INCLUDE
VAT

Order by Post with CHEQUES, ACCESS
VISA or you can telephone your order
All orders despatched within 5 days
unless advised


WW - 052 FOR FURTHER DETAILS

GET BIG POWER

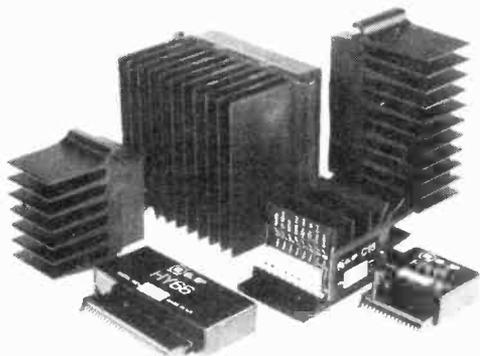

Modular Amplifiers the third generation

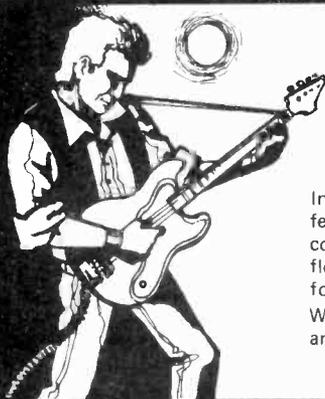Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
HY 181	150	4-8	<0.01%	<0.006%	± 18	76 x 68 x 40	240	£18.40
HY 181	30	1-8	<0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY 180	80	1-8	<0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY 171	60	4	<0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY 128	60	8	<0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY 144	120	4	<0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY 154	120	8	<0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY 164	180	4	<0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY 164	180	8	<0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line, Slew Rate: 15V/ps, Rise time: 3 μ s, S/N ratio: 100db, Frequency response (-3dB) 15Hz - 50KHz, Input sensitivity: 500mV rms, Input Impedance: 100K Ω , Damping factor: 100Hz > 400.

PRE AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre-amp	Mic/Mag, Cartridge/Tuner/Tape, Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre-amp	Mic/Mag, Cartridge/Tuner/Tape, Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre-amp	Two-Gu for Bass Lead and Mic + separate Volume/Bass/Treble + Mix	20mA	£15.36
HY78	Stereo pre-amp	Aux + Vol/Bass/Treble/less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
MOS 128	80	4-8	<0.005%	<0.006%	± 35	120 x 78 x 40	410	£18.40
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 40	410	£18.69
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1030	£38.41

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20V/ps, Rise time: 3 μ s, S/N ratio: 100db, Frequency response (-3dB) 15Hz - 100KHz, Input sensitivity: 500mV rms, Input impedance: 100K Ω , Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB, Load impedance 3 Ω

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω

Size 95 x 48 x 50mm, Weight 256 gms.

C155

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80, Weight 410 gms.

WITH A LOT OF HELP FROM ELECTRONICS LTD

PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

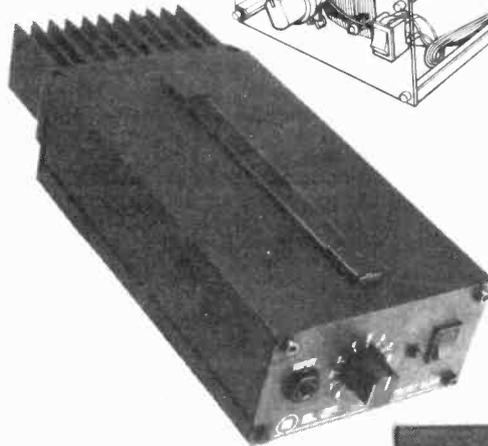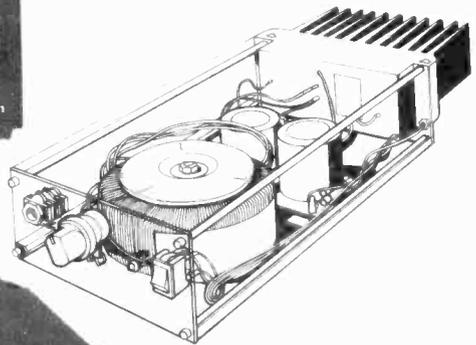Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.



TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I. L. P. Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED

UNICASES

HIFI Separates						Price inc. VAT
UC1	Preamp					£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	Hi-Fi		£54.95
UP2X	60W/4Ω	Bipolar	Mono	Hi-Fi		£54.95
UP3X	60W/8Ω	Bipolar	Mono	Hi-Fi		£54.95
UP4X	120W/4Ω	Bipolar	Mono	Hi-Fi		£74.95
UP5X	120W/8Ω	Bipolar	Mono	Hi-Fi		£74.95
UP6X	60W/4-8Ω	MOS	Mono	Hi-Fi		£64.95
UP7X	120W/4-8Ω	MOS	Mono	Hi-Fi		£84.95
Power Slaves						
US1X	60W/4Ω	Bipolar	Power	Slave		£59.95
US2X	120W/4Ω	Bipolar	Power	Slave		£79.95
US3X	60W/4-8Ω	MOS	Power	Slave		£69.95
US4X	120W/4-8Ω	MOS	Power	Slave		£89.95

Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.



Post to: ILP Electronics Ltd., Freepost, 5 Graham Bell House, Roper Close, Canterbury, CT2 7EP, Kent, England.
Telephone: (0227) 64778
Technical: (0227) 64723
Telex: 965780

Please send me the following _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

WW - 012 FOR FURTHER DETAILS

Twice again: Shure sets
the standard for the industry!



Introducing two new microphone mixers

Ten years ago—with the introduction of the M67 and M68—Shure set the standards of the industry for compact, portable micro-

phone mixers. Shure is now introducing two new mixers with features and improvements that will make them the *new* industry standards.

NEW

M267

For Professional Broadcasting
Both TV and Radio—in the studio and for remote broadcast applications.

For Professional Recording

For Professional Sound Reinforcement

For more complex public address systems.

With all these new features:

- Switchable, fast-attack limiter
- LED peak indicator
- All inputs switchable for mic or line
- Simplex power
- Greater headphone power
- Built-in battery supply
- Lower noise
- Reduced distortion

...and all of the famous M67 original features.

NEW

M268

For Public Address and Paging
In hotels, schools, churches, community centers, hospitals, etc.

For the Serious Tape Recording Enthusiast

As an Add-On Mixer for Expanding Current Equipment

With all these new features:

- Lower noise
- Dramatic reduction in distortion
- Mix bus
- Automatic muting circuit
- Simplex power

...and all of the famous M68 original features.

Both new models include the same ruggedness and reliability that have made the M67 and M68 the top-selling mixers in the industry.

For complete information on the M267 and M268 send in for a detailed product brochure (ask for AL669).

The Sound of the Professionals®

SHURE

For full details write to:

H.W. International, Eccleston Road, Tovil Maidstone, Kent ME15 6AU. Tel: 0622 59881.

WW - 042 FOR FURTHER DETAILS

Editor:
PHILIP DARRINGTON
01-661 3128

Deputy Editor:
GEOFFREY SHORTER, B.Sc.
01-661 8639

Technical Editor:
MARTIN ECCLES
01-661 8638

News Editor:
DAVID SCOBIE
01-661 8632

Drawing Office Manager:
ROGER GOODMAN
01-661 8690

Technical Illustrator:
BETTY PALMER

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

BARBARA MILLER
01-661 8640

Northern Sales:
HARRY AIKEN
061-872 8861

Midland Sales:
BASIL McGOWAN
021-356 4838

Classified Manager:
BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production:
BRIAN BANNISTER
(*Make-up and copy*)
01-661 8648

Publishing Director
DAVID MONTGOMERY
01-661 3241

Know-how: resource or property?

When the committee of the UK's Independent Review of the Radio Spectrum sent out a letter last year inviting people to contribute evidence, it put forward some new and interesting questions for consideration. One was whether decisions on spectrum allocations and frequency assignments should be influenced by value judgements of the "worth" of the services and transmissions in question. This obviously implied a need for assessing the different claims within society for spectrum space. Another question was whether frequency assignments should be determined or influenced by market forces – for example, by treating spectrum space as an economic quantity and charging rent for it or auctioning it off to the highest bidder.

These two possible approaches to the disposal of frequencies are obviously ideologically opposed. As such, they could almost have been laid out as part of the agenda for the ideological battle of the UK's coming General Election, for much of this battle will be between different value judgements on the right way to apportion scarce resources. They belong, respectively, to the opposing principles of political power and economic power.

But the radio spectrum is only one example of how these different attitudes reach into the whole body of electronics and communications technology. Electronics manufacturing, in contrast to making shoes or breakfast cereals, is a perpetual race to get ahead in specialized technical knowledge – or that amalgam of applied physics and empirical practices we like to call know-how. In business you must keep up with your competitors in know-how or you will do badly and perhaps fail. In international diplomacy you must keep up with your adversary in the ability to deploy such know-how as a military threat.

All political parties in Britain declare that electronics know-how is important to the economic future of the country and that it should be disseminated as rapidly as possible. But the Right and Left extremes differ fundamentally on the best way of

using it for the good of the people, because they see it in different ways.

The Right, believing in the essential beneficence of the free market, think that know-how should be acquired under the stimulus of commercial competition. The process of demand in a free market ensures that people get from the technology what they really want from it. Meanwhile, the know-how is a property, rightfully belonging to the entrepreneur because he made the effort to possess it in the first place. Then, after a period of commercial exploitation, it eventually becomes common knowledge, to be consigned to the text-books, and so ceases to be a property with valuable ownership rights.

The Left, believing in government intervention rather than market forces, think of know-how as a resource that should be applied directly to the collective benefit, not through the selective processes of the market. They dispute the Right's view that everyone gets what he wants in a free-market system simply through demand. They argue that demand is artificially generated by entrepreneurs, by using advertising, for example, to create wants that will blot out awareness of real needs. This artificially created demand is actually what the entrepreneur finds convenient and profitable to sell, and the know-how behind the products follows the same selective pattern.

Experience has shown that know-how produced under the stimulus of competition in free-market economies is more advanced than that obtained under state control in centralized economies. The issue, however, is not about absolute levels of know-how in different systems but about alternative ways of distributing this resource or property to the benefit of society. The problem applies equally in the less developed countries of the Third World. It is too serious to be left to the outcome of party political contests and deserves more concentrated attention than it gets at present from just academic studies and technology assessment organizations.

Tracking satellites with a microcomputer

This fully-automatic system will track amateur or weather satellites continuously using a PET microcomputer to control antenna azimuth and elevation.

Before the advent of cheap home computers, tracking amateur satellites involved the use of several graphs and tables, followed by time-consuming calculations. This effort can now be replaced by a computer program such as the one described here. The program runs on an average microcomputer (the Commodore PET) and has the following features:

- the whole system is simple to operate
- only the minimum essential orbital information is required from the user, all other satellite information being inbuilt
- the computer updates its orbital data as necessary, and is capable of operation for an indefinite length of time unattended
- the computer automatically drives electromechanical rotators for altitude and azimuth of directional antennae
- the program predicts the availability of the selected satellite and indicates for how long it will be within range.

Two popular methods of tracking satellites are available to the amateur. The first, the Oscarlocator, is a purely manual technique and is therefore of no use in this application. It consists of a polar projection of the northern hemisphere and an acetate sheet with an orbital path drawn on it. When correctly positioned, it allows the orbital path and the azimuth angle to the satellite to be read off.

The other method, due to the American amateur W5PAG, consists of drawing up azimuth and elevation charts (see Fig. 1):

1. The great circle angle (i.e. the angle subtended at the centre of the Earth) between the receiving station and the point on the Earth below the satellite (the "sub-satellite" point) is calculated:

$$D = \cos^{-1} \left(\frac{R}{R+h} \cos y \right) - y \text{ degrees} \quad (1)$$

where D is the great circle angle, y is the elevation angle of the satellite at the station, R is the Earth radius (6375km) and h is the altitude of the satellite.

2. Next, the latitude of the point on the first bearing (say 0 degrees) which corresponds to the elevation angle y is given by

$$\sin B = \sin a \cos D + \cos a \sin D \cos C \quad (2)$$

by I. P. Jefferson B.Sc., G4IXT

where B is the latitude of the sub-satellite point, a is the latitude of the receiving station and C is the bearing to North (in this case 0 degrees).

3. Finally, the corresponding longitude of the sub-satellite point is calculated:

$$\sin L = \frac{\sin C \sin D}{\cos B} \quad (3)$$

where L is the difference in longitude between the sub-satellite point and the receiving station.

Thus the latitude and longitude of a point corresponding to a particular elevation have been calculated, on a heading of due North (0 degrees). It is now necessary to calculate points on other headings at the same elevation angle. (Note that it is only necessary to calculate points for headings 0-180 degrees since the chart is symmetrical). The whole procedure is then repeated for different

elevation angles up to 90 degrees.

Having drawn the charts it is necessary to know the sub-satellite point in order to use them. This can be found as follows:

$$\sin b = \sin (360t/T) \sin U \quad (4)$$

where b is the latitude of the sub-satellite point, t is the length of time in minutes since the satellite crossed the equator travelling North (the EQX time) and T is the satellite orbit period at inclination angle U to the equatorial plane.

The corresponding longitude is given by

$$l = \cos^{-1} [\cos(360t/T) / \cos b] \pm [t/4] \quad (5)$$

The factor t/4 is due to the rotation of the Earth: the Earth rotates 1/4 degree every minute. When the orbit is retrograde, i.e. U greater than 90 degrees, t/4 is added.

To complete the charts, it is now necessary to take values of t from, say, 1 minute to 115 minutes (a complete orbit) and substitute in (4) and (5) to find the orbital path.

The graphs plotted will give the antenna azimuth and elevation for the satellite concerned. For any other satellite,

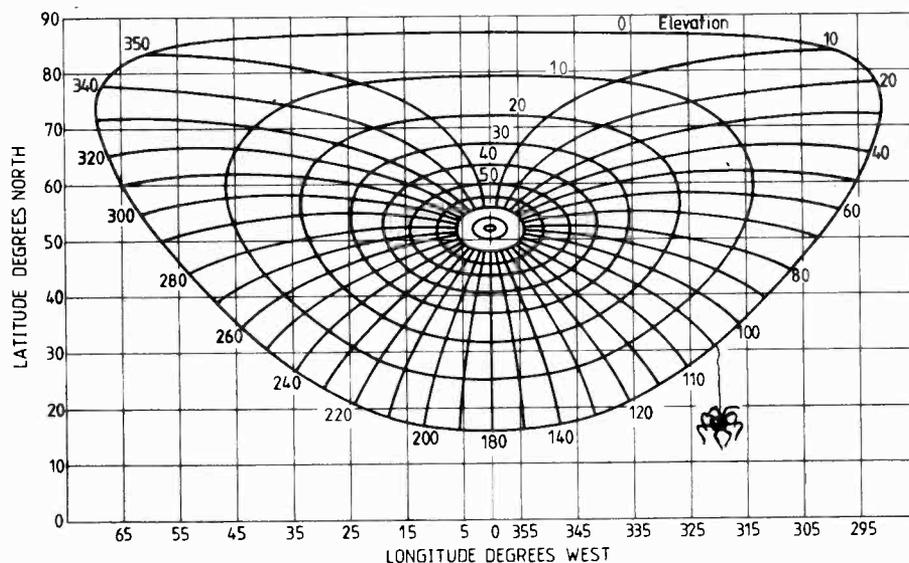


Fig. 1. Example of a chart showing the bearing necessary to direct an antenna towards a point at a given latitude and longitude.

different graphs would have to be drawn.

Although this method could be used by a computer, storing all calculated values in a "look-up" table, it would be very inefficient and time consuming to do so. A better approach is to calculate the information required at the time it is needed, for that particular time only. Obviously the computer will have to be able to do the calculations rapidly for this to be accurate. The PET is adequate in this respect.

Calculated tracking

The requirement is to produce values of azimuth and elevation for a given satellite at a specific time, as quickly and accurately as is possible. In order to do this, some basic information is needed:

- The satellite's orbital period.
- The longitude increment at the equator per orbit.
- The inclination of the orbit to the equatorial plane.
- The apogee and perigee of the orbit.
- A reference orbit, i.e. the time and longitude of an equator crossing, travelling in a particular direction (generally North).
- The latitude and longitude of the receiving station.
- The time in GMT.

All of the above from (a) to (d) inclusive are fixed and can be built into the program. The remaining data must be supplied by the user when the program is run. For amateur radio and weather satellites, the apogee and perigee differ by about 1% or less, so the orbits can be assumed to be circular and an average height used in calculations.

Using modifications to formulas (4) and (5) we can calculate the latitude and longitude of the sub-satellite point. Replacing symbols with the variable names used in the program, from (4),

$$\text{PHI} = \sin^{-1} \left[\sin(\text{CLIN}) \times \sin \left(\frac{2 \times \pi \times \text{MI}}{\text{PE}} \right) \right] \quad (6)$$


where PHI=latitude in radians of the sub-satellite point
 CLIN=orbital inclination
 MI=number of minutes since EQX
 PE=orbital period in minutes

From (5), THETA equals

$$\cos^{-1} \left(\frac{\cos [2\pi (\text{MI}) / (\text{PE})]}{\cos (\text{PHI})} \right) + \frac{2\pi (\text{MI})}{1440} \quad (7)$$

where THETA=longitude in radians of the sub-satellite point.

Now consider a system of vectors in three dimensions. Taking the vectors from the centre of the Earth to the receiving station and to the satellite (Fig. 2), the vector difference between these two give the vector from the receiving station to the satellite (displaced to the centre of the Earth). If we use spherical polar coordinates, we can draw this on a cartesian system with the centre of the Earth as origin (Fig. 3).

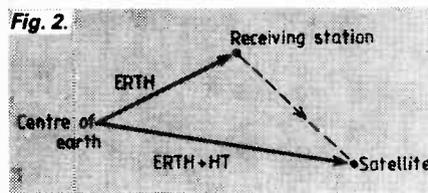

ERTH = earth radius.
 EARTH+HT = earth radius + orbital height.

The conventional way of specifying longitude is to use degrees West of the Greenwich meridian. However, we are using values of THETA in the opposite direction, so they must be modified as below. Similarly, degrees latitude conventionally increase from the Equator outwards, but the PHI angles above are opposite and must be modified suitably.

Modified values:
 PD=($\pi/2$)-PHI TD=($2 \times \pi$)-THETA
 FI=($\pi/2$)-LAT TE=($2 \times \pi$)-LONG (8)

where
 PD= ϕ' TD= θ' FI= ϕ TE= θ
 LAT=receiving station latitude.
 LONG=receiving station longitude.

Notation:

- r is the vector to the receiving station from the centre of the Earth.
- r' is the vector to the satellite from the centre of the Earth.
- p is the vector from the receiving station to the satellite.

Now the components of the vector r are

$$\begin{aligned} X &= |r| \cos(\text{TE}) \sin(\text{FI}) \\ Y &= |r| \sin(\text{TE}) \sin(\text{FI}) \\ Z &= |r| \cos(\text{FI}) \end{aligned}$$

and similarly for r'

$$\begin{aligned} X' &= |r'| \cos(\text{TD}) \sin(\text{PD}) \\ Y' &= |r'| \sin(\text{TD}) \sin(\text{PD}) \\ Z' &= |r'| \cos(\text{PD}) \end{aligned}$$

If the components of the vector p are X_p, Y_p, Z_p then:

$$\begin{aligned} X_p &= X' - X \\ Y_p &= Y' - Y \\ Z_p &= Z' - Z. \end{aligned}$$

Theoretically, this vector is all that is necessary to track the satellite since it is easy to work out the spherical polar

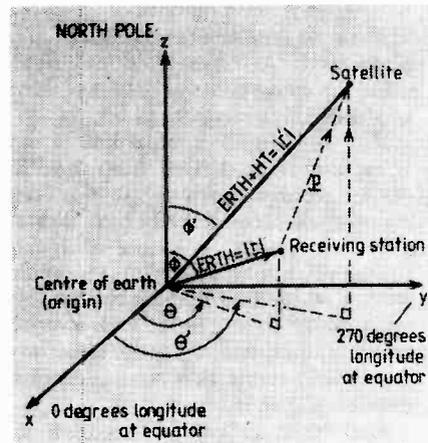


Fig. 3. Vector diagram.

coordinate angles, and these could be fed directly to the antenna rotators. However, in practice it is difficult to define these angles at the receiving station, since they relate to the cartesian coordinate system previously shown, based at the centre of the Earth. At the receiving station it is convenient to refer to angles of elevation from the horizontal and azimuth angles from due North, so these must be supplied by the program.

Since we are using vector notation, it is simple to find the angle between the vector r and the vector p using the dot product:

$$r \cdot p = |r| |p| \cos E$$

Therefore

$$\cos E = \frac{X X_p + Y Y_p + Z Z_p}{\sqrt{X_p^2 + Y_p^2 + Z_p^2} \sqrt{X^2 + Y^2 + Z^2}} \quad (12)$$

This gives the angle E between the two vectors. Since the horizontal plane at the receiving station is perpendicular to the vector r, by taking ($\pi/2$)-E we can get the angle of elevation required for the antennae (Fig. 4).

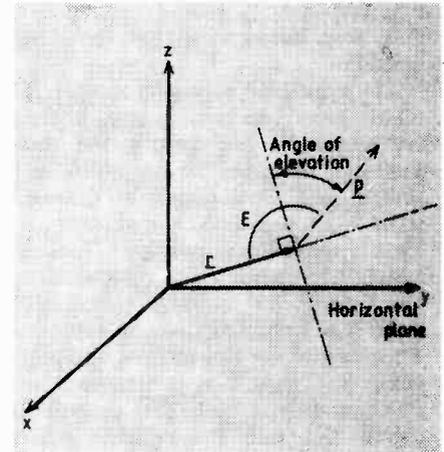


Fig. 4. How angle of elevation for the antenna is derived.

It is more difficult to extract the azimuth angle from due North using any similar method, but it is relatively simple to apply equation (2) if the great circle angle D can be found. This is an easy matter, since it is the angle between vectors r and r'. It can be found using the dot product as follows:

$$\cos D = (X X' + Y Y' + Z Z') / r r'$$

where r=ERTH (Earth radius) and r'=ERTH+HT (Earth radius+orbital height). See Fig. 3.

Simple manipulation of equation (2) will give the azimuth bearing angle if all the information which is now known is substituted in.

Using the method described, we now would have all of the information required to track the satellite accurately without having to draw any graphs. All that remains to be done is to present this information in suitable form to the antenna rotors.

Rotator driving

Two rotators are necessary to track the satellite, one to elevate the antennae and one to rotate them to the correct bearing. In the prototype system these rotators were not of the same manufacture, and operated on different principles, so separate methods of interfacing were required for each.

The type SU2000 azimuth rotator.

This rotator is controlled electronically, and uses a potentiometer mechanically coupled to the rotating shaft to provide feedback to the control box. When a switch (not shown) is closed for a short period, the circuitry is activated, and the voltage on the control potentiometer is compared with that on the feedback potentiometer. The rotator then turns one way or the other until the difference is reduced to zero.

The voltage range on the control potentiometer is about 0-6V d.c. and operation is linear, with 0V corresponding to 0 degrees and 6V to 360 degrees. To control the rotator the computer must therefore apply a voltage between 0 and 6V (corresponding to the desired position) to the control potentiometer connections, and close the activating switch for a short time (typically 1/4 second). Rotation will then stop automatically at the desired position.

The type 2050 elevation rotator. This rotator uses two a.c. motors operating synchronously, one driving the rotator shaft and the other driving a disc in the control box. Operation is as follows. A second disc, with a notch in it, is turned by hand to the required position. This causes a 3-position switch which rubs against the disc's perimeter to move either left or right. The switch connects an appropriate a.c. phase to the two motors, and applies power to them. The two motors rotate synchronously, until the control box driven disc with the switches attached reaches the position of the notch in the manually-turned disc. When this happens, the switch actuator springs into the notch, the switches go "off" and the motors both stop. In this manner, the rotator shaft follows the position of the manual disc.

In order to control this rotator from the computer, a feedback potentiometer was coupled mechanically to the driven disc

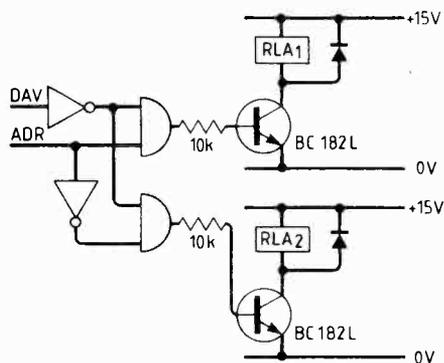


Fig. 5. The two most-significant bits of the PET's output word are used to control the two rotators. RLA₁ controls the power to the elevation rotator. RLA₂ activates the azimuth rotator's control box.

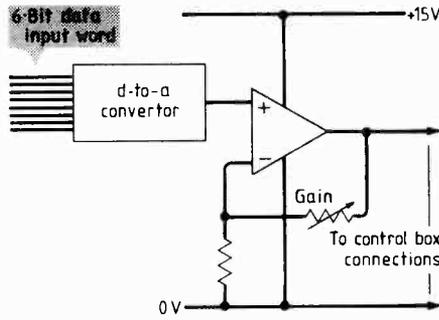


Fig. 6. A d-to-a converter (such as the Ferranti ZN425E) provides a control voltage for the azimuth rotator. The two spare bits of its 8-bit input are connected to logic 1. A similar d-to-a converter is used in the control of the elevation rotator.

and the switches disconnected. Phase switching to the motors was achieved with relays.

Computer control consists of:

- generating a voltage corresponding to the required position and comparing it with the voltage from the feedback potentiometer. Depending upon the result, an appropriate relay activates.
- applying power to the motors, which will switch off automatically when the feedback voltage corresponds to the required position.

Control interface

The PET output port is bi-directional and can be programmed as inputs or outputs. At power-up the port defaults to inputs and floats "high". This means that the interface must have a "do nothing" function when presented with all lines logic 1. Also, the port is an 8-bit port, so the accuracy of the output number is limited, especially since two of these bits are needed to specify which rotator the information applies to. Hence six-bit precision data is used for the rotators, giving about 6 degrees accuracy for azimuth and 3 degrees for elevation. This is quite adequate since the antenna -3dB beamwidth is not better than about 30 degrees.

The two "control bits" used were the most-significant bits of the PET's output word, arranged as:

(ADR) (DAV) X X X X X X

where X indicates remaining bits for data

ADR - address bit

DAV - data valid bit

A simple arrangement of logic is all that is necessary to control the two rotators using the above codes as data, and driving small switching relays, as in Fig. 5.

For the azimuth control box, a direct voltage must be derived from the PET's output word and applied to the control connections on the control box. Basically, all that is needed is to use a digital-to-analogue (d-to-a) converter to obtain a voltage which corresponds to the output word, adjust its amplitude with a variable-gain amplifier, and apply the result to the appropriate connection points. A suitable circuit is shown in Fig. 6.

The elevation rotator needs a more complex control circuit, since a decision must be made as to which way to connect

the a.c. phases to rotate the motors in a particular direction. The voltage from the feedback potentiometer in the control box is compared with a voltage derived from the PET output port via another d-to-a converter. The supply phase to the motors is then switched in a manner such that they rotate to reduce the voltage difference to zero. A problem is to stop the circuit oscillating about the zero position. This is overcome by allowing a "guard band" around zero where both phases are switched off, and the motors do not rotate. The circuit used is shown in Fig. 7.

The input voltage and feedback voltage difference is amplified by the difference amplifier. If the resultant voltage is above +0.6V then diode D₁ conducts, TR₁ switches 'on' and RLA₃ switches one particular phase to the motors. The motors rotate in a direction such that the feedback voltage decreases, until the difference output falls within the 1.2V guard band provided by the forward voltage drop across diodes D₁ and D₂. When this happens, neither D₁ or D₂ conducts and the motors stop, since both phases are switched out. Similarly, for an initial negative output from the amplifier, D₂ conducts, TR₂ is 'on' and the motors rotate in the opposite direction to before, increasing the feedback voltage until the difference lies within the guard band.

Complete interface

In order that the PET output word can change whilst either of the rotators is turning, it is necessary for both sections of the circuitry to have their particular data word latched as long as it is needed. The PET can individually update the latches as necessary.

A typical output sequence is as follows:

ADR	DAV	azimuth rotator	elevation rotator
0	0	STOP	GO
0	1	STOP	STOP
1	0	GO	STOP
1	1	STOP	STOP

11000000	Both rotators OFF, data zero on latches.
10000000	Latch zero into elevation rotator latch and activate rotator.
11010000	Both rotators OFF, data 16 on latches, zero latched in elevation latch.
10010000	Latch 16 into elevation latch, and activate rotator.
11010000	Both rotators OFF, data 16 on latches, 16 latched in elevation latch.
11001000	Both rotators OFF, data 8 on latches, 16 latched in elevation latch.
00001000	Latch 8 into azimuth rotator latch, activate rotator. 16 latched in elevation latch.

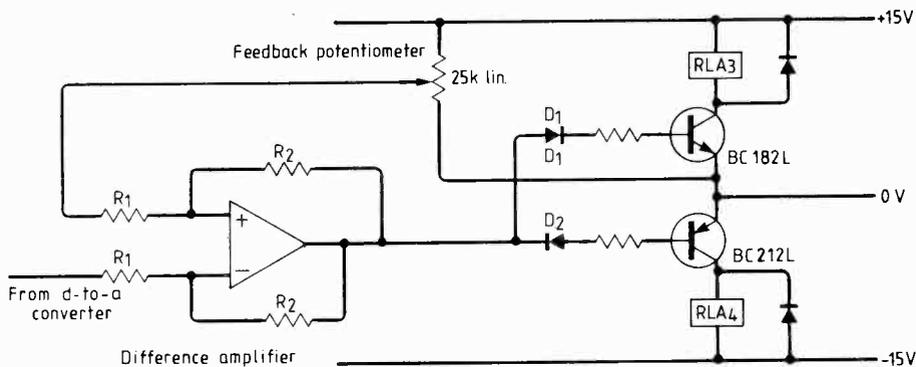


Fig. 7. The control circuit for the elevation rotator. The relays switch a.c. to the motors.

Figure 8 shows the block diagram of the interface, which includes all the circuits previously described. The latches are controlled by the circuit Fig. 5, taking their latch instruction from the outputs of the AND gates.

Computer program

A full description of the program would be rather long, since it contains many simple features such as input/output routines. Therefore the following comments are confined to basic outlines and references to particular points where necessary. The subroutines are listed below, with the exception of one or two which are trivial.

Time output routine (lines 100-140)

The PET's inbuilt time clock function is utilised, with times converted to decimal (DT) for ease of manipulation. Some string calculations are performed, and the time is 'POKED' directly onto the screen as HH:MM:SS in the top right-hand corner.

Latitude/longitude conversion subroutine (lines 150-195)

Latitude and longitude values needed for calculations are input at various points in the program, and this routine takes degrees and minutes as DDDMM in string form, checks that the input is not rubbish, and returns the decimal equivalent of the input in degrees.

Main program (lines 200-580)

This section is not a subroutine. It defines some variables, e.g. Earth radius in Mm,

ERTH, and also some trig. functions. It interrogates the user for all the necessary information then uses part of lines 700-830 to set remaining variables.

Satellite data calculation (lines 640-830)

Contains data used by the main program.

Lines 1010-4010

This section starts with some screen graphics, then uses some of the other subroutines to calculate all of the tracking data. It outputs information to the screen and uses the rotator driver subroutine to track the satellite concerned. The program cycles continuously in this section.

Time since EQX subroutine

(lines 5000-5060)

Uses the decimalised real time (DT) and decimalised equator-crossing time (EXT) to find the time in minutes since the satellite crossed the equator (MI).

Subsatellite (etc.) subroutine

(lines 5070-5270)

This subroutine uses equations (6) to (12) to calculate spherical coordinates, vectors and finally the satellite elevation angle from the receiving station.


Acquisition of signal subroutine

(lines 5280-5340)

Finds the time when the satellite elevation angle is positive, i.e. when the satellite is above the radio horizon. It does this by substituting times since equator crossing in the above subroutine, starting with one minute then incrementing by one minute until the correct time is found.

Equator crossing data subroutines

(lines 5570-5620, 5630-5680)

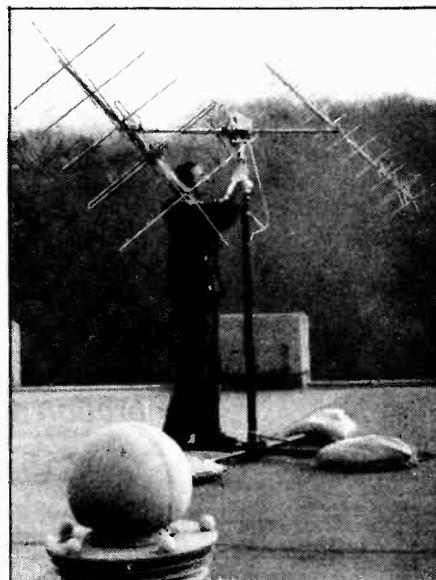

Ian Jefferson designed his satellite tracking system as a final-year project for a degree in Applied Physics at the University of Durham. He now works in broadcast engineering.

These two subroutines find equator crossing times and longitudes for orbits other than that given as reference by the user. One does this for orbits previous to the reference orbit (or if the reference orbit is in the future, to find the current orbit), and the other for orbits after the reference.

Bearing subroutine (lines 5700-5780)

Calculates the satellite azimuth angle from the receiving station, using calculations described on page 17. Lines 5735 & 5737 are necessary to avoid division-by-zero errors in subsequent stages. Subroutine returns a decimal angle in degrees.

Loss of signal subroutine

(lines 5860-5900)

Similar to acquisition of signal subroutine in operation.

Rotator driving subroutine

(lines 6000-6120)

Reduces accuracy of output words to 6-bit precision, for reasons described earlier. The next function is to send out pulses to give the control logic of the interface the necessary addressing information and the data word indicating the required antenna position. When this has been done, both rotators are told to deactivate on completion of rotation.

Further reading

Evans, D. S. and Jessop G. R. VHF-UHF Manual, pp. 9.1-9.15. Radio Society of Great Britain.


The Best of Oscar News, vol. 1: AMSAT-UK Oscar News, Winter 1980, No. 32: AMSAT-UK.

Getting to know Oscar: American Radio Relay League.

Kennedy, G. R. Weather satellite picture processor, Wireless World May 1980, p. 41.

A listing of Mr Jefferson's program can be supplied by the Wireless World editorial office on receipt of a large stamped addressed envelope. Please mark your envelope "Tracking satellites with a microcomputer".

Fig. 8. Outline of the interface connections.

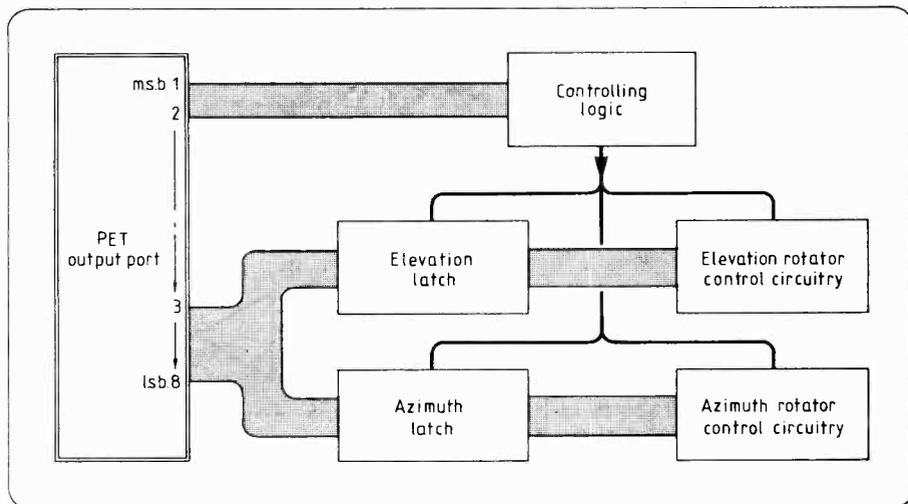

High-impedance electronics

Following the description of voltage followers in the last issue, the author discusses the generation and measurement of currents down to 1 nanoamp.

Instead of measuring the voltage signal from a high-impedance source, it is often more appropriate to measure the short-circuit current with an operational current-to-voltage converter (Fig. 1(a)). For example, the open-circuit voltage from a photodiode is a markedly nonlinear function of the incident illumination; in fact it saturates at 500-600 mV as the junction becomes "real" earth and the virtual earth of a current-to-voltage converter, its junction voltage is fixed at zero and saturation cannot occur. In monitoring very low light levels, saturation is not likely to be a problem, but there is a second advantage of the photogalvanic mode, again arising from the constancy of junction voltage. In the photovoltaic mode the junction capacitance has to be charged or discharged by the photocurrent whenever the light signal changes; the rise time is consequently poor. In the photogalvanic mode the rise time is essentially that of the operational amplifier.

The value of the feedback resistor in Fig. 1(a) is often fixed by consideration of the magnitude of the current signal and the desired voltage output, since $E_{out} = -I_{in}R_f$. When very small signals are to be measured the noise behaviour of the circuit should dictate the design. An elementary howler is to choose a rather small value of R_f on the grounds that its Johnson voltage noise (proportional to the square root of R_f) should be small. Actually it is the Johnson current noise that matters; this is inversely proportional to the square root of R_f . From the noise equivalent circuit¹ (Fig. 1b) the signal to noise ratio can be written down as

$$S/N = I_{in} / \{ E_a^2 [1/R_f + 1/R]^2 + I_a^2 + 4kT\Delta f/R_f \}^{1/2} \quad (1)$$

where the last term in the denominator is the square of the previously mentioned Johnson current noise. Although the balance of the three contributing factors depends on the properties of the amplifier used, it is clear that S/N is an increasing function of R_f . In particular, to avoid unduly multiplying the amplifier noise voltage E_a , R_f should be at least equal to the resistance R of the signal source. Since R is often not known (except perhaps that

by R. D. Purves, Ph.D

it is known to be large) the natural tendency is towards huge values of R_f . Neurophysiologists routinely use values of 500-1000 M Ω to measure picoamp currents flowing through molecular pores in cell membranes.

A common modification to the basic current-to-voltage converter is the use of a tee network in the feedback loop (Fig. 3). Here R_f is the largest conveniently available value, say 100 M Ω , but its effect is multiplied by attenuation in the tee. If, as is usual, R_1 and R_2 are much smaller than R_f , then the output signal is $-\beta I_{in}R_f$, where β is the attenuation ratio $(1 + R_1/R_2)$. For example, with $R_1 = 99k$, R_2

= 1k and $R_f = 100$ M Ω , the tee behaves like a 10 G Ω resistor. The signal to noise ratio, unfortunately, is unimpressed by this synthetic resistor and takes the value given by Eq. 1 for the actual value of R_f used. Thus a real resistor is better than a synthesized one of equivalent value. Similar conclusions apply when offset and drift are analysed.

A further pitfall of the tee network relates to loop gain. Extravagant values of attenuation in the tee may leave insufficient gain for proper feedback action, especially since R and R_f form a second attenuator in the feedback path. A typical operational amplifier has an open-loop low frequency gain of about 10^5 . If we choose $\beta = 1000$ and $R_f/R = 9$, the loop gain is only $10^5 / [\beta(1 + R_f/R)] = 10$. This dangerously small loop gain will become even smaller above the amplifier's first corner frequency (10 - 40 Hz), and the circuit

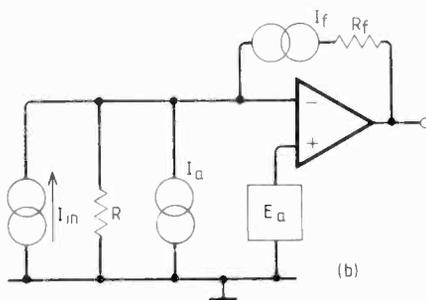
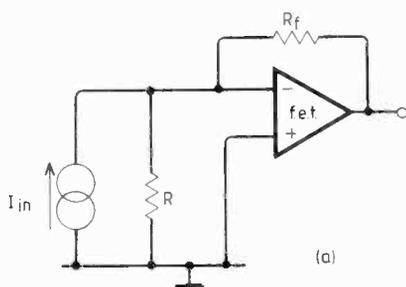


Fig. 1 (a) Operational current-to-voltage converter. (b) Noise equivalent circuit. E_a is the amplifier's r.m.s. voltage noise, I_a is the amplifier's r.m.s. current noise and I_f is the r.m.s. Johnson current noise of the feedback resistor. $I_f = \sqrt{4kT\Delta f/R_f}$, where k is Boltzmann's constant, T the temperature and Δf the noise bandwidth.

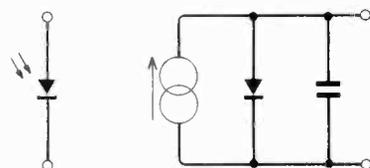


Fig. 2. Photodiode and an equivalent circuit. The photocurrent generator is shunted by a diode and the junction capacitance. The terminal voltage is limited by forward biasing of the diode. For the terminal voltage to change, the photocurrent must charge or discharge the junction capacitance.

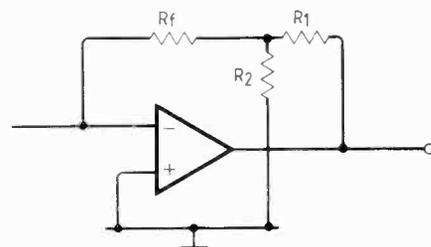


Fig. 3. Tee network in feedback path of current-to-voltage converter.

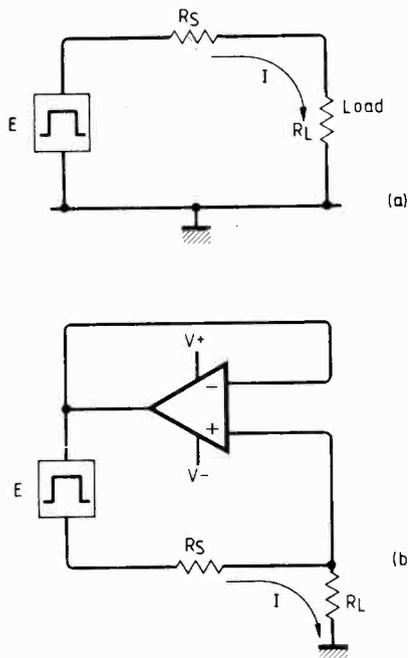


Fig. 4 (a) A simple current source. (b), bootstrapped current source with fet operational amplifier.

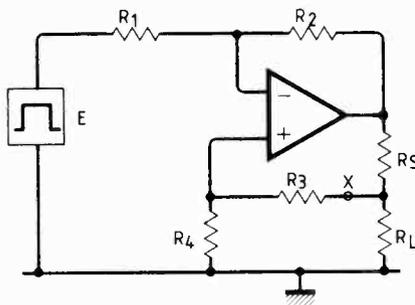


Fig. 5. Howland current pump.

ceases to behave as a current to voltage converter.

The only advantages of the tee network are that it may obviate the need for an additional stage of voltage gain and that range switching can be carried out at low impedance (by switching the values of R_1 and R_2). The second advantage is an important one, since attempts to switch resistors in the $G\Omega$ range with an ordinary wafer

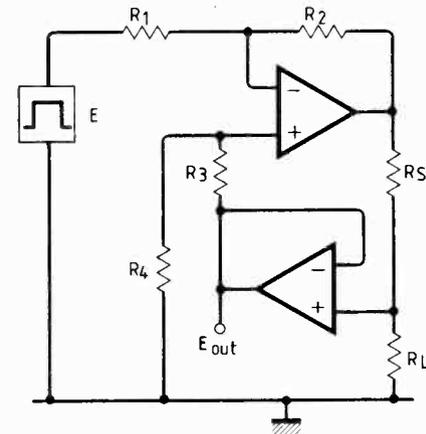


Fig. 6. Improved Howland current pump.

switch are unlikely to be greeted by success.

Nanoampere current sources

To provide a controlled current of the order of 1 nA one might turn to the circuit of Fig. 4(a). For certain purposes this simple strategy might suffice but if the load current has to remain substantially constant in the face of variations in R_L then we would require $R_S \gg R_L$. For example, if R_L ranges from 0 to 100 M Ω , then for a current variation of 1% we must take R_S as 10 G Ω . Such resistors are both expensive and hard to obtain. Furthermore, if we now require currents of 10-100 nA, the voltage source of Fig. 4(a) will have to take inconveniently large values (100-1000 V).

The solution to these problems is often to be found by bootstrapping, shown in its starkest form in the active current pump of Fig. 4(b). In its originator's well-chosen phrase "this deceptively simple circuit" produces an output current E/R_S , independent of the magnitude of R_L . Readers may like to test their wits by analysing the mode of operation.

The most important parameter characterizing a current pump is its output resistance, which should be as high as possible. Conceptually, it may be determined by setting the command signal to zero, replacing R_L by a voltage source E' , and then calculating the current I' drawn from this

source. The output resistance is E'/I' ; in Fig. 4(b) it is $R_S(1 + A)$ where A is the open-loop low frequency gain of the amplifier. Another parameter is the output bias current in the absence of a command; for Fig. 4(b) this is V_{os}/R_S where V_{os} is the amplifier's input offset voltage.

Despite its charm, the circuit of Fig. 4(b) is rarely used because it needs a floating signal source. The familiar Howland current pump³ seems more promising at first sight. In Fig. 5 one or more of the resistors is adjusted to give the "balance" condition $R_2R_4 = R_1(R_3 + R_S)$. Then $I_{out} = -ER_2/R_1R_S$, independent of the load R_L . However the output resistance of the Howland pump is sharply degraded by small departures from the balanced state, since the output terminal is shunted by R_3 and R_4 . The resulting shunt current must be very accurately compensated by additional drive to R_S . Again, the balance condition depends on five resistors which usually span a wide range of values. Differential aging and temperature effects on resistance are therefore difficult to control, and the Howland circuit needs frequent re-balancing to maintain a high output resistance.

A much better circuit (Fig. 6) is one found in most commercial current pumps for neurophysiological use. It is derived from the Howland design by interposition of a fet voltage follower at point X of Fig. 5, to remove the shunting effect of R_3 and R_4 . The balance condition is now $R_1R_3 = R_2R_4$. Three of these resistors can be of the same value and type (e.g. 10k metal oxide), the fourth being the next lower preferred value in series with a cermet trimmer. Resistor R_S is generally 10 - 100 M Ω , the exact value being immaterial to the balance condition. An extra advantage of his circuit over the Howland pump is that the follower allows the voltage applied to the load to be monitored at the terminal labelled E_{out} .

In Figs. 5 and 6 the source resistance of the command signal is in series with one of the gain-determining resistors. Both circuits would in practice need an input buffer stage to isolate the "working part" from changes in source resistance. An alternative three-amplifier configuration⁴ in Fig. 7 has a spare input terminal for the command signal. This circuit may be understood by recognizing that A_2 is a differential amplifier whose output is a low-impedance replica of the voltage across R_S and thus a direct measure of the output current. This signal is compared with the command by A_3 , which forces the output current to take the command value. WW

References

1. Motchenbacher, C. D. and Fitchen, F. C. Low Noise Electronic Design. Wiley, 1973.
2. Fein, H. Passing current through recording glass micropipette electrodes. *IEEE Trans. Biomed. Electron.*, vol. BME-13, pp211-212, 1966.
3. Smith, J. I. Modern Operational Circuit Design. Wiley, 1971.
4. Purves, R. D. Microelectrode Methods for Intracellular Recording and Ionophoresis. Academic Press, 1981.

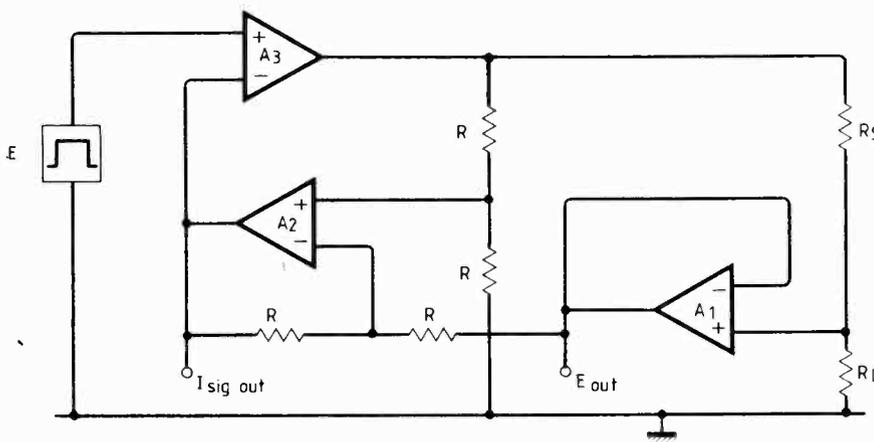


Fig. 7. A three-amplifier current pump. The resistance of the signal source does not affect the output resistance.

STATE	P5	P6	P1	DURATION	OTHER OUTPUTS	NOTES
1	A	F	INPUT	UNTIL INT-N		If not VERIFY, FAIL light ends cycle
2	0	F	"	50 μs		EA light on during PROGRAMMING
3	0	F	OUTPUT ADDRESS	50 μs		Select & activate PROGRAM mode
4	4	F	LATCH ADDRESS	50 μs		RST-N goes high
5	4	F	OUTPUT DATA	50 μs		Uses MOV P3 A @ A instruction
6	4	B	"	50 μs		PROG goes low
7	4	3	"	50 μs		-V _{dd} goes to 25V
8	4	5	"	50 μs	PROG light	V _{dd} at 25V: PROG at 23V PROGRAMMING occurs
9	4	B	"	50 μs		As state 6
10	4	F	INPUT	50 μs		Change P1 first
11	C	F	"	50 μs		Wait for VERIFY DATA to become VALID
12	C	F	READ DATA	10 μs		READ (8 VERIFY)
13	0	F	INPUT	50 μs		Wait for lines to steady, if fin, GO STATE 1 ELSE GO STATE 3

Total program time 13 seconds per page

realised, was to build a programmer as a peripheral driven by the development board. By doing this as, as shown in Figs 2 and 3, a minimum of extra hardware is required. The most expensive part is a zero-insertion-force socket, and under normal circumstances the careful hobbyist, who will not be doing much programming, can dispense with this in favour of a much cheaper quick-eject socket.

In use the 8748 is programmed one page (1 page = 256 bytes) at a time; this arises out of the modest data handling of the instruction set, which dislikes mixing program and data. The 8748 has four pages of eprom, number 0 to 3, and the page to be programmed is set up by a thumbwheel switch or dipswitch as shown.

The programming algorithm (see listing) is then placed in the emulator page 0, i.e. from 000 up. This listing gives a very simple programming routine; it is not claimed to be ideal, but it gives the beginner something to work from - in fact, a chance to tinker.

The page of data to be programmed, regardless of what page it is to appear in in the 8748, is then loaded into page 3 of the emulator, where it takes advantage of a quirk of the instruction set. The emulator is connected to the development and programming board, and the system powered up. The programming board requires 25V at approximately 50 mA. A switching supply is not advised due to possible interference: if a suitable supply is not otherwise available, dry batteries to a total of 24 nominal volts provide an alternative. Whatever the supply, it should not exceed 26 volts under any circumstances, not fall below 24 during programming.

On power up, the Fail led should come on and all others stay out. As a test, the Interrupt switch which starts programming should be operated. The Fail led should go out while the switch is closed, and come on immediately when it is released while the EA led glows dimly. After thirteen seconds the EA led goes out and the Fail led blinks. Now the Fail led should go out, the EA and Program leds come on, and the Program led should vary

in brightness as the value of the data being programmed varies. At the end of the cycle the other leds go out and the Fail led blinks. The page number may then be changed, new data placed in Page 3, and the program cycle repeated. If the Fail led lights during the cycle one or more addresses have mis-programmed.

Fig. 4. Adding 8-bit a-to-d converter.

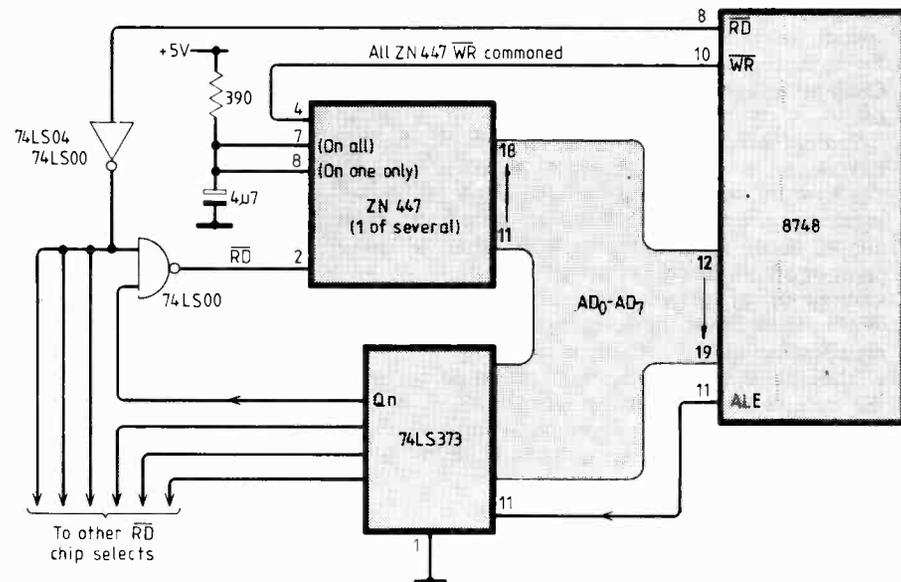
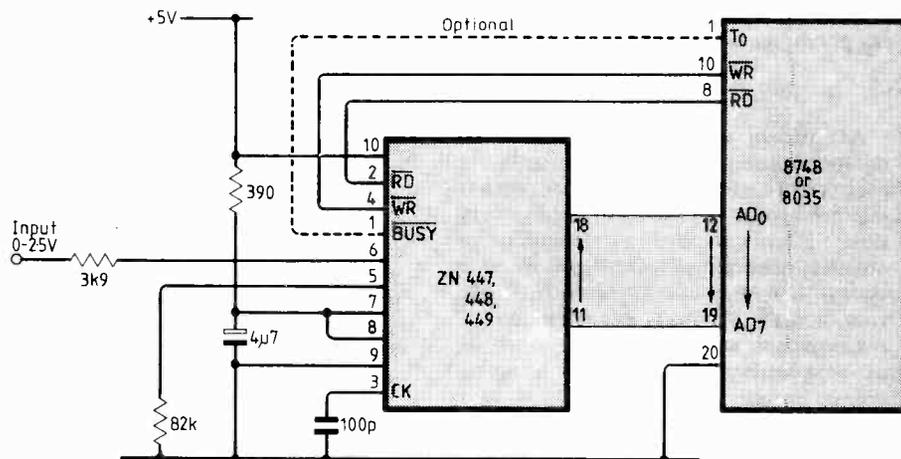


Fig. 5. Using several a-to-d converters for high-speed operation.

All the time the 8748 is socketed and power applied the circuit applied to pins 2 and 3 should be oscillating at around 3 MHz, and a square wave should be emitted from Pin 11: if these are missing, there is a fault. A 2.5-3 MHz crystal may be substituted for the inductor if available. Programming requires a slower clock than normal running, and this has been taken into account in the oscillator and the programming algorithm.

Expansion of the 8748 is dealt with very thoroughly in the Intel manual, which is essential reading in any case, but some specific examples are given here. There are two types of expansion; direct, in which microcontroller pins are used as inputs or outputs and retain output values until they are changed, and memory-mapped.

In memory-mapping, the bus port is used with a 74LS373 (for t.t.l.) and/or a 74C373 (for c.m.o.s.). This octal latch is used to latch an address during a MOVX instruction. In the simplest case, setting one address bit to 1 (i.e. addresses 01, 02, 04 . . . 80) is used as a chip select for a particular device, and a Nand gate may be used as shown in Fig. 4 in conjunction with RD-N and an address line to read from a unique device. In the case of the alphanumeric displays dealt with later, the lowest two address lines select a digit within a display, and the next six lines are used to select a particular display. The


Viewdata display module

This display module allows a home computer to shed some of its display processing load and display colour text and graphics in teletext format. Red, green, blue and sync video outputs are provided and the display is controlled by either a serial or parallel link from the host computer. With the addition of a modem, the module can be programmed to display data directly from a viewdata computer.

This module performs all the necessary display functions for a viewdata terminal. Video and tv sync outputs are generated for direct connection to a colour monitor or via a PAL encoder and u.h.f. modulator to an ordinary colour tv set. Data input to the module can be either serial or parallel and consists of characters for display or control commands to the module. The module was originally designed to be connected to a host computer to relieve it of some of the burdens of display processing; it could easily be used with a home computer to provide viewdata and/or display capability.

by Dennis N. Pim

The display module is controlled by an 8048 microcomputer (8748 eeprom version). Changes in the software for this processor allow much flexibility in the operation of the module. For example, in my prototype the module receives serial data at 4800baud and any word whose most significant bit is set to logic 1 is decoded as a command rather than a character for display. Simple software changes could be incorporated so that the module directly displays the serial data (with par-

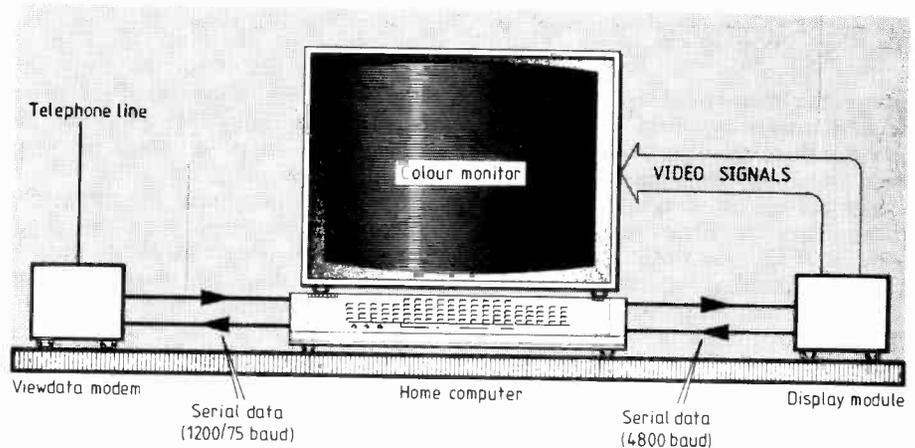

Display module is designed for use with home computer to provide videotext display at 4800baud, but software changes could allow a level one Prestel display of 1200baud directly from a viewdata computer.

ity) at 1200baud arriving from a viewdata computer.

In the present version, the module can also perform simple editing functions such as scrolling up or down, clear to end of line, and clear to end of page. All or part of the display can also be read by the host computer as can the current cursor location on the screen. Once again the software allows other special functions to be pro-


grammed for specific applications thus freeing the host computer from time-consuming display operations.

The module has four page stores, and any of these can be selected for display and/or updating. It is possible therefore to write a new page whilst another page is being displayed and only display the new page when it is complete.

Used in serial input mode, the module has available a general-purpose input/output port. Serial commands enable this port to be read or written; individual bits can be selected as input or output.

Before considering the full circuit of the module, look at the operation of the video generator integrated circuit.

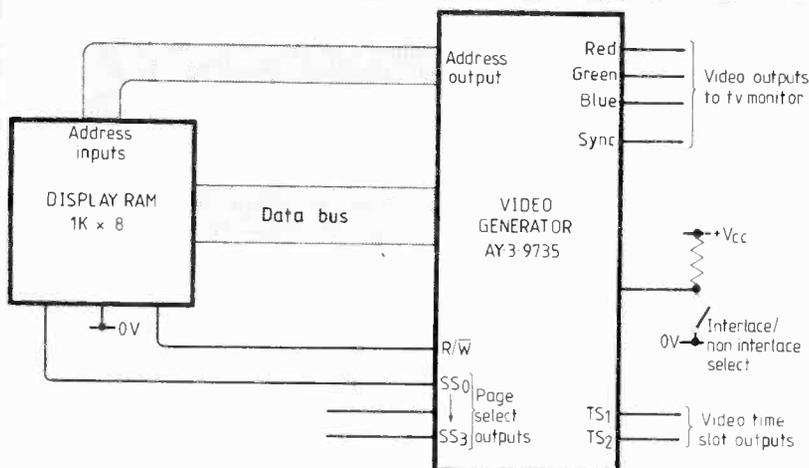Video generator provides the usual 24 row x 40 column tv text display implements Prestel terminal facilities. Video i.c. contains character rom and addresses four pages of ram in the application described.



Video generator

The display module uses the GIM AY39735 interlace/non-interlace video generator to generate the tv signals. This i.c. provides the necessary circuitry to generate a full composite tv sync and the red, green and blue video outputs. It contains a character rom and can address up to eight pages of ram store, although in this application only four pages can be used. The i.c. generates the usual viewdata format of 24 rows and 40 columns, and implements all the BT Prestel terminal specification display facilities. It is driven by a 6MHz clock and has a set of tristate address and data lines to connect to the display rams. A

R/W signal drives the page store selected by three binary tristate store select lines.

Within each video frame there are four time slots that are indicated by the state of two outputs from the chip. These are

TS00 – reading from ram. This occurs under control of the video generator between lines 48 and 288 and is when the display is active.

TS01 – writing to ram when teletext lines are written to the page store during frame flyback. Not used in this application.

TS10 – spare.

TS11 – data interchange period. During this period the video generator can receive commands from the control processor (lines 23 to 47).

During lines 289-6 the video generator is inactive. In addition, the video generator data and address lines are tristate during every line flyback period. This occurs approximately 56µs from the start of the line sync pulse to approximately 16µs after the start of the next pulse, a total time of about 24µs each line. Because the video generator frees the address and data lines during line flyback the 8048 processor can have access to the display rams during this time for updating/reading. The 24µs window gives enough time to read/write one character to the display store.

During time slot TS11, the display chip is enabled to receive commands from the controlling microprocessor by placing 111XX0XXX on the address lines (X≡either logic state). The required command code is then set up on the data bus bits 0 to 6 and bit 7 of the bus is used to strobe the command into the display chip. Some of the functions that can be controlled in this way are

- clear screen
- half-screen expansion
- select displayed page
- display tv picture or text
- select teletext/viewdata mode
- select mix mode
- cursor on/off (the cursor – a flashing underline – is displayed at any ram location whose most significant bit is set to 1; only seven bits are required for each character display).

The figure shows the video generator in a conventional configuration addressing one 1K×8 display ram.

Circuit description

The circuit has to cater for the following operations.

- Reading and writing from one 1K block of one of the two 2K rams forming the four page stores by the video generator. (Writing is required for page clear.)
- Reading and writing from one 1K block of one of the two 2K rams by the microcomputer.
- Selection of one 1K block of ram for display by the video generator.
- Selection of one 1K block of ram by the microcomputer (not necessarily the same block as that being displayed).
- Sending commands directly to the video generator from the microcomputer during time slot TS11.

- Receiving serial or parallel data or commands from the host computer.
- Sending serial data to host computer.


The video generator data bus is connected to the data buses of two 2K rams, (cmos in the prototype) and the 8048 data bus. The address bus of the display chip is connected to the ram address lines A0 to A9. (Address line A3 is fed via a tristate buffer whose function is explained later). The 8048 supplies address information for the display rams from its multiplexed bus using an eight-bit latch. Address information is latched into this chip by the 8048 ALE line and presented to the address bus when required by a low signal on bit 4 of port 2. Bits 0 and 1 of port 2 provide the required two remaining higher-order ram address lines A8 and A9.

The two 2K rams provide four pages of display. Page selection for display is achieved by the SS0 and SS1 binary tristate outputs of the video generator. SS0 selects the lower or upper half of each ram via the A10 input and SS1 selects one of the two chips via their CS inputs. Reading or writing to each page by the microcomputer is achieved by bits 2 and 3 of port 2 connected to the ram A10 and CS inputs respectively.

The video generator provides a tristate R/W line that can be directly connected to the ram write strobe (the video generator needs to write to the rams for the clear screen function). Unfortunately the WR strobe of the 8048 is not tristate, hence this output cannot also be connected directly to the ram WE inputs. It is therefore connected to the enable input of a tristate non-inverting buffer whose input is connected to the output-enable signal of the address latch (8048 port 2 bit 4) so that the WR strobe is applied to the rams only when they are accessed by the processor. This, as well as providing the required tristate write strobe, prevents the write strobes produced whilst the processor is sending a command to the video generator from corrupting the contents of the rams.

Also, so that the 8048 can send commands to the video generator, the ram outputs must be tristate during the slot TS11. Hence it is not possible to permanently ground the ram OE inputs and a read strobe has to be supplied to them. The video generator does not have a read strobe output, but the SS2 page-select line creates one. This tristate line is only held low during the display period (assuming one of pages 0 to 3 are being displayed). The SS2 line therefore provides the required read strobe and is connected to the ram OE inputs. This is why only four pages of ram can be used in this application. The 8048 does have a read strobe (RD) but this like the write strobe is not tristate and hence another buffer is used to provide a tristate strobe in the same way as for the WR line.

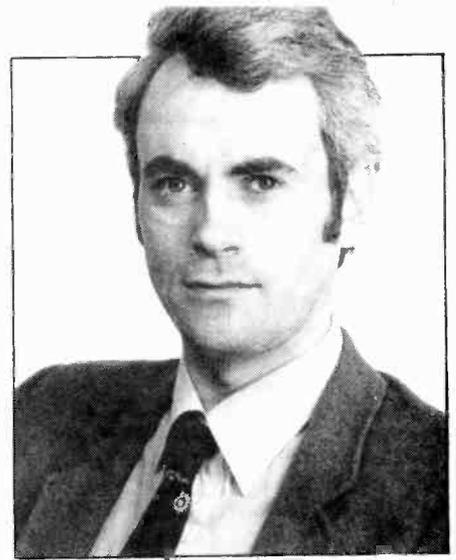Sync pulses from the video generator are fed via a monostable to the test zero (T0) input of the processor. This input receives positive-going pulses at the start of line flyback, arranged to be about 10µs wide by the 27kΩ/100pF monostable timing components. The processor therefore knows that it can have access to the display rams from 56µs to 80µs after the leading edge of



Dennis Pim, B.Sc.(Eng), Ph.D., M.I.E.E. lectures in electronics at the Open University. He obtained his degrees from University College London, where his Ph.D. research was concerned with various aspects of simulation. Before joining the O.U. in 1981 he spent four years with Rediffusion on the design and production of television receivers, becoming viewdata project leader. Resulting from his work at Rediffusion Dr Pim is now involved with research in the field of home information/entertainment systems.

this pulse. (The next line pulse does of course appear on the T0 input during this time window).


Video generator commands

The time slot outputs of the video generator (TS1 and TS2) are and-ed together using a spare inverter and a spare tristate buffer to provide a signal on the processor's test-one input (T1), which is logic high during time slot TS11, when the video generator is enabled to receive commands.


Because the processor might access the display rams during any line flyback, including those occurring during time slot TS11 when the video generator is enabled to receive commands, it is important to prevent the video chip from responding to data on the data bus intended for the rams. (It is possible to select a ram address which activates the video generator during this time slot). This situation is prevented by effectively breaking the display's A3 address line during a processor read or write using a tristate buffer which is disabled by bit 4 of the processors port 2. If the processor is required to send a command to the video generator, the required enabling address of 111XX0XXX is set up on the address bus by the four 22kΩ pull-up resistors on address lines A6 to A9, and by setting bit 5 of port 2 to zero thus providing the required logic 0 on address line A3. During time slot TS11 the ram outputs are tristate and the processor can then send a command to the video generator via the data bus, using data bit 7 as a strobe.

Inputs

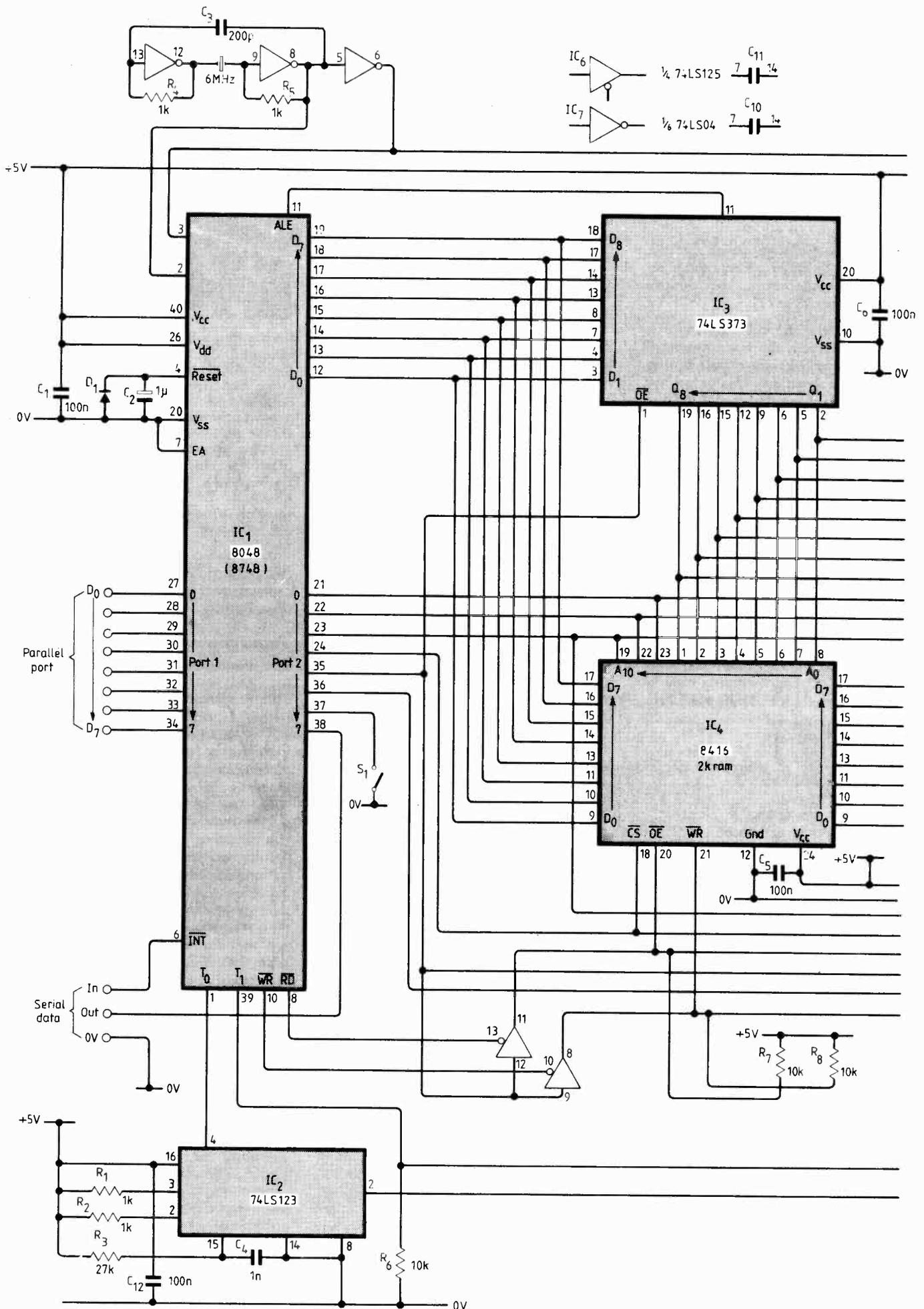Two ways to input characters or commands are provided. Port 1 of the 8048 can be used as an eight-bit parallel input. In



S₂ - Interlace/non-interlace select

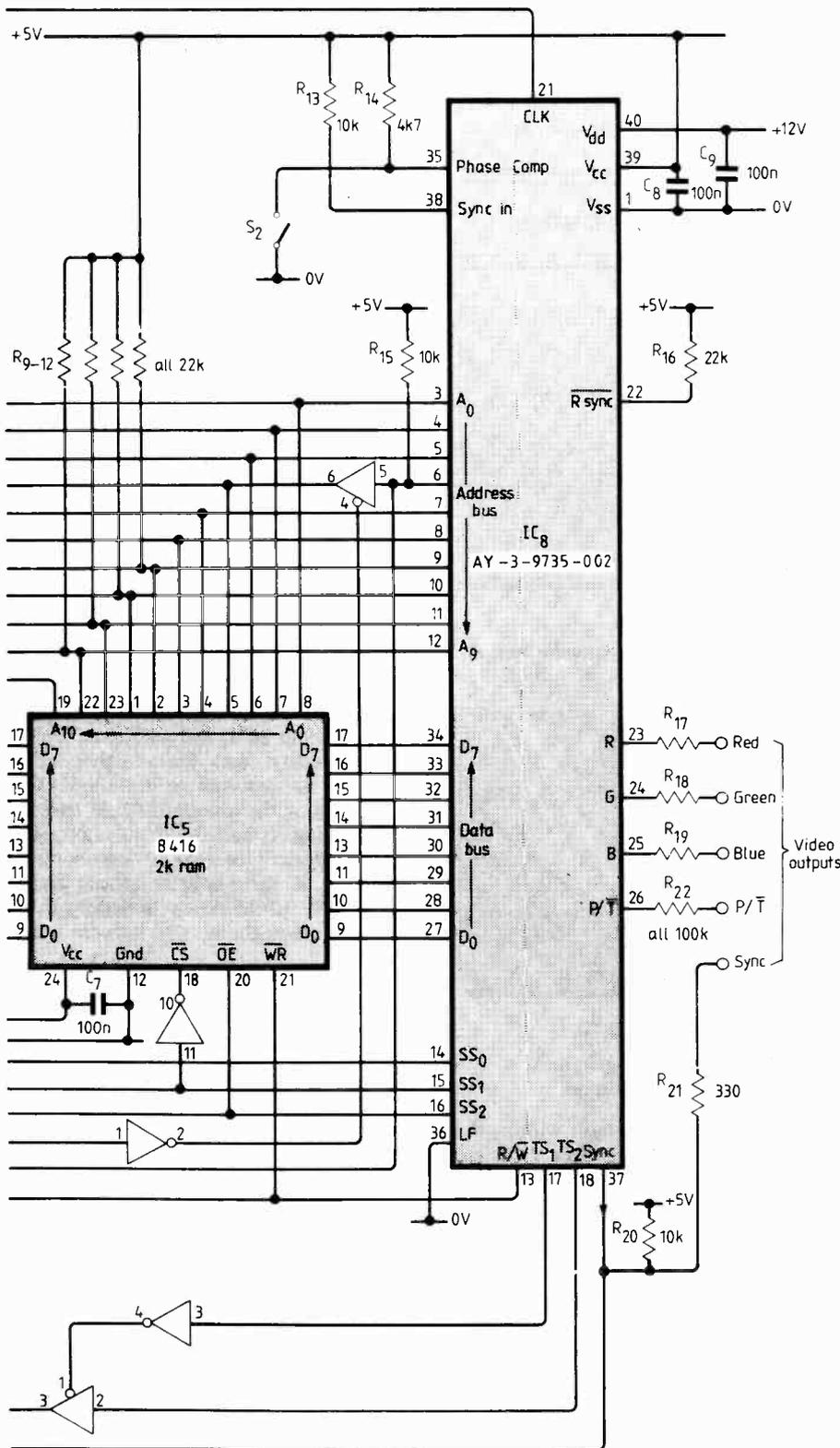

this mode the required data is set on port 1 and a negative-going pulse of at least 2.5µs duration is applied to the interrupt input to indicate valid data (the parallel data must remain stable for at least 25µs after the strobe pulse).

Alternatively, the interrupt input can be used as a serial input, and the processor programmed to accept a variety of bit rates between 600 and 4800baud (although the module cannot actually process characters at the full rate of 480 per second).

In the prototype, serial/parallel operation is selected by setting bit 6 of port 2 to logic 1 or 0 respectively, switch S1 provides this function. Alternative software versions could of course be provided for either serial or parallel input, thus freeing bit 6 of port 2 for other functions.

Outputs

Signals to the tv monitor are the three colour outputs, red, green and blue, composite sync and the video generator's picture/text (P/T) output which provides monochrome video when the video generator is set to "mix" mode (this can be used as a printer output). The logic outputs are protected by series resistors. Interlaced or non-interlaced sync can be provided: S2 connected to the phase/comp input of the video generator selects the sync type required. If serial input is used, port 1 can be used as a general purpose eight-bit port (either input or output or a combination). The bits of this port can be read or set by commands from the serial input.

A serial output line is provided on bit 7 of port 2 which performs two functions. Firstly, it can output data from the display module. This data can include status information, displayed characters stored in the rams or data on the general-purpose i/o port. Data rates are selectable by different software versions, and the output rate can be made different from the serial input rate. Secondly, this output indicates that the 8048 is busy. A logic 0 on this line indicates that the processor input buffer is full and no further characters can be accepted until this output returns to logic 1. Confusion as to whether a logic 0 on this output is a buffer-full indication or the start bit of serial output data should not arise if the host computer always waits for returned data after a command that requires data to be returned before sending a further command. The viewdata display module never sends data down the serial line unless instructed to do so.

To be continued with software description.

Display module requires power supplies of +5V at 200mA and +12V at 80mA. Both processor and video generator are driven by same 6MHz clock. Deaconhouse Ltd, of 57 Guildford Street, Chertsey, Surrey (tel. 09328 66015) will supply 85 + 155mm double-sided boards to the pattern given in the final article.

Cooling electronic equipment

Heat is an enemy of electronic circuits. This article discusses the various methods for removing heat from equipment including heat sinks, convection, cooling fans and air conditioning.

It has long been known that one of the biggest enemies of electronic equipment is heat. It is surprising that heat dissipation, or the removal of heat from circuits, is normally a secondary consideration or even an annoying necessity during the final stages of housing the electronics. It is hoped that this article will highlight some of the points to be considered in the area of ventilation in electronic packagings, as well as to show how ventilation requirements can be calculated to ensure a benign environment for electronics.

Possibly the easiest to understand and the most practicable method of cooling is the use of a heat sink. Large slabs of metal or even the equipment enclosure itself can be put in direct contact with the heat source. The amount of heat transferred in this way can be calculated by using

Fourier's Law:

$$Q = \frac{KA\Delta T}{L}$$

- where Q = heat transferred per unit time
 A = area perpendicular to the heat flow through which the heat is passing
 L = thickness of body of matter through which the heat is passing
 ΔT = the temperature difference between the hot and cold sides of the substance through which the heat is being transferred.
 K = specific co-efficient of conductivity.


It can be seen that L should be as small as possible, and A as large; hence the thin cross-section and the fins of heat sinks.

There are many kinds of heat sinks on the market today, for just as many applications, ranging from 'clip-on' models for single transistors to models weighing many tons for large transformers.


The majority of electronics equipment manufactured today is cooled by the action of convection. If the heat source is too great for convected air to remove sufficient heat, resulting in an unacceptable temperature rise of the electronics, the designer should consider using a forced draft unit, probably in the form of an axial fan.

Let us consider Graph 1. The vertical

By Michael Young

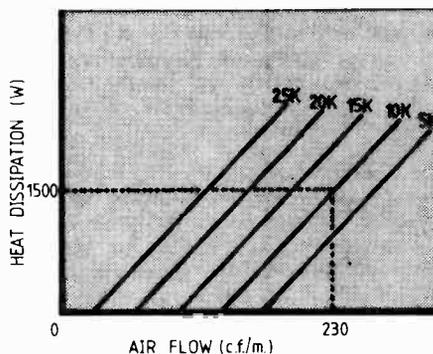

Graph 1. The relationship between heat loss and airflow.

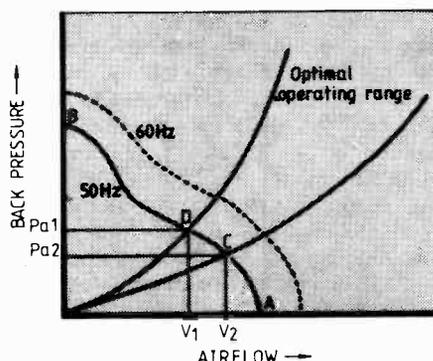

Graph 2. Back-pressure and airflow relationship to aid fan selection.

axis represents heat losses within the system. In many cases it is often sufficient to approximate this to the total electrical consumption of the equipment to be cooled. Determine the acceptable temperature rise of the air flow. This is measured in degrees Kelvin above ambient. A good guide is that 10K is almost always appropriate. The required air flow can be read from the graph. As an example, let us suppose we have a piece of equipment running on 240 volts and consuming 6.25 amps. The total energy consumption and heat dissipation will be $240 \times 6.25 = 1500$ watts. Anticipating an acceptable temperature rise of 10K, the air flow required to achieve the desired criteria will be approximately 230 cubic feet per minute (cfm, 1 cubic ft. \approx 28.3 litres). Consider a fan unit, standing in free air (represented by point A on Graph 2). At this point, the fan is working hardest and is passing as much

air as possible, in this case above 100cfm. The resistance to air flow or back pressure is almost negligible. If the same fan is placed horizontally on a surface (represented by point B in Graph 2), air flow, in theory, is zero. In practice however, a slight air flow will be experienced from the vortex created by air displacement of the fan blades on the upper surface. Back pressure is the minimum required for zero air flow, and our example shows that this will be in the region of 0.3 inches of water. In the laboratory, back pressure can be measured using a manometer. Points C and D on the graph give the upper and lower points of back pressure relating to the optimum operating range, and the air flow from any fan can be deduced by the measurement of pressure rise and reference to its characteristic curve.

Multiple fans may be used if a single fan cannot cope with the required airflow. However a second fan will only assist the first by about 20%, and additional fans by proportionally less. One further calculation of the required airflow should take into account the amount of free space in the housing. If half the space is occupied by the circuitry then the airflow should be doubled; if three-quarters then the requirement should be multiplied by three. This is a rule-of-thumb which works well in practice.

When maximum cleanliness and additional cooling is desired, the use of a blower unit fitted to the enclosure is recommended. This will ensure that clean, filtered air passes into the rack, efficiently maintaining a positive pressure against the ingress of dust.

For hot, humid or otherwise hostile environments, air conditioning a sealed enclosure is a solution. Units are available to fit specific racking systems such as the 19-inch. Their heat transfer is usually measured in British thermal units per hour (Btu/Hr) and can be calculated by multiplying the wattage of the equipment by a factor of 3.4. (The conversion factor to kJ is $3.6 \text{ as } 1 \text{ Btu} \approx 1,055 \text{ kJ}$.)

It is hoped that this article has given the reader some understanding of the behaviour of heat and its dissipation in electronic equipment cooled either by simple heat sinks, natural convection in basic instrument housings or forced draft units and air conditioners. Simple calculations will determine the amount of heat that requires removal to achieve the desired working temperature and thus a long working life of each component.

Michael Young is a member of the technical advisory team at Imhof-Bedco Standard Products Ltd.

COMMUNICATIONS

Meteor-trail bouncers

Back in the 1950s, a good deal of interest was aroused by the Janet project of the Canadian Defence Research Board which showed that the highly ionized trails left by meteors entering the earth's upper atmosphere can sustain two-way communication at h.f. or v.h.f. for periods lasting sometimes for several seconds, but more usually for a matter of milliseconds. Because of the vast number of meteors that enter the atmosphere each day – with the number peaking during the regular meteor shower periods – the Canadians showed that by using 600 words per minute “burst” transmissions, triggered by a path opening, it was possible to handle teleprinter traffic at roughly normal speed. This early work used carrier powers of about 100 watts at 50 MHz with 5-element Yagi aerial arrays.

Because the meteor trail reflections occur roughly 85 to 115 km (70 miles) above the earth at about the same height as Sporadic E, the maximum range of both modes of reflection is about 2000 km but meteor scatter is far more consistently available. It is claimed that burst meteor-scatter traffic is extremely difficult to intercept, to the degree where even unenciphered traffic is virtually secure.

Although in the 1960s and 1970s little was published about the developing use of meteor-trail communications, other than by amateurs snatching brief contacts, sometimes at high speed but without computerized or “triggering” facilities, it became evident a few years ago that NATO has been using meteor-burst military systems (Comet) since the late 1960s. More recently there has been increasing use of these techniques for specialized applications, for example by the US Department of Agriculture. In 1981 Telecom Inc marketed a computer-controlled system using a data rate of 4800 bits/s and a 1 kW transmitter. Scientific Radio Systems Inc have also now developed an SRM-500 series of terminals operating in the 40-50 MHz band using 1 kW at the base stations, 300W at the remote terminals. A 5-element Yagi is used at the master station but smaller aeriels down to a dipole at the remote terminal. The more powerful the set-up, the less the “waiting time” between bursts and the higher the average rate of transmission. Computer technology is used for packet formatting, buffering and error correction. Typically, ionized trails have a length of about 25 km and act as “directional aeriels” to give a footprint for a given path roughly about 25 miles long and 5 miles wide, making it extremely difficult to intercept or jam the system. Waiting time between bursts seldom ex-

ceeds a few minutes even in the non-shower periods. Some 50,000 high-energy meteors fall into the upper atmosphere every second, of which one may open a particular path.

Terman's legacy

Few men can have so influenced the study of radio communications, broadcasting and electronics as Frederick Emmons Terman, who died in December aged 82. His work as Professor of Electrical Engineering at Stanford University, California led to the pre-eminence of Silicon Valley as the centre of so much advanced electronics, dominated by his former students. But it is as author of “Radio Engineering” – first published (in the UK) in 1934 – that his fame spread quickly throughout the world as the 688-page book became the “bible of the profession.

The merits of the first edition were recognized from the outset; “a book of outstanding merit . . . a book which will have instant appeal to engineers, amateur or professional . . . it is rarely that a book of such merit appears” are some of the phrases in just one typical review. Further titles “Fundamentals of Radio”, “Measurements in Radio Engineering” appeared later but it was the successive editions of “Terman's Radio Engineering” that dominated the world scene for so many years. Professor Terman maintained his early links with amateur radio, advising on the old “Jones Radio Handbook” that still survives some 20 editions later as “The Radio Handbook”. Stanford University, similarly, remains an educational centre with an unusual record of practical development, including, for example, the first s.s.b. without pilot carrier experiments in 1946 by Villard. As *Electronics* has written: “Few men can be said to have left a living and growing legacy of such impressive magnitude. The industry has good reasons to remember and cherish the name of Frederick E. Terman”.

World broadcasting

There is a paradox about radio broadcasting across frontiers: many people in the UK thoroughly enjoy listening at night to BBC World Service and resented the transfer of the service last year to the more directional aeriels at the FCO site at Orfordness; on the other hand the prevalence of super-power external broadcasting transmitters, including Orfordness, is a prime cause for the chaotic and unsatisfactory state of m.f. broadcasting in Europe. The USA with its “clear channels”, day-time-only, stations, highly-directional

aeriels and maximum of 50 kW provides listeners with far more interference-free choice and so underlines the importance of good frequency-spectrum management. In the very early days of broadcasting America learned the hard way that there must be firm regulation of transmitting facilities no matter how de-regulated the programmes may be. But for well over a year a real threat to North American night-time a.m. broadcasting has been evident in the Cuban response to the proposal, strongly backed by the White House, to set up a powerful Radio Marti m.f. service directed at Cuba. In turn Cuba threatened to build a total of 187 m.f. transmitters, including some of 500 kW. Last August, Cuban transmissions showed up temporarily on some of most cherished American “clear channels”, confirming an earlier NAB conclusion that many American stations would experience a dramatic loss of night-time coverage if the Marti plan went ahead.

Nevertheless the White House continued to assign high priority to Radio Marti and sought authorization from Congress to spend \$7.5-million for this purpose, against growing opposition on the part of some Congressmen. The 1982 bill however has been pushed aside – and it will now need a new bill in 1983 if the project is to go ahead. Most American broadcasters fervently hope it won't.

External broadcasting can be an expensive business. The Grant-in-Aid cost of the BBC Overseas Service, excluding expenditure on relay stations operated by the FCO, but including the cost of the monitoring service at Caversham, has been given as: 1977-79 £32.2-million; 1978-79 £37.2-million; 1979-80 £42.9-million; 1980-81 £55-million; 1981-82 £62.8-million; 1982-83 (estimated) £71-million. And these figures may not cover all of the substantial cost of electrical power.

Many aspects of frequency planning for h.f. broadcasting are due to be examined in a two-part World Administrative Radio Conference in January 1984 and autumn 1986. The problem of international jamming seems certain to be raised once again – but unlikely to be solved. Communications engineers as well as broadcasters may well be affected by this WARC.

Interference from CB

The introduction of legal Citizen's Band operation on 27 MHz f.m. in November 1981 did not at first have any great effect on the rising number of complaints, made by viewers and listeners, of interference to television and radio reception. The dramatic increase in 1981: from about 200 per month in January 1981 to 2200 per month

in December, continued in the early months of 1982 until complaints reached a peak of 4952 in March, but then began to fall back. By December 1982 they were down to 2590, although this was still a higher total than for any "illegal" month during 1981. It is interesting to note the marked falling off of complaints in December just about one year after the introduction of the CB licence. Could it denote that many enthusiasts are not renewing their licences? What percentage of complaints stem from a.m. equipment has not yet been released. In the twelve months to September 1982 there were 2300 prosecutions for illegal use of transmitters.

The privatization of British Telecom, under the Telecommunications Bill, brings into question whether BT will continue to be responsible to the Home Office for interference investigations. BT have already raised this matter with the Home Office, according to a Parliamentary reply.

AMATEUR RADIO

Those examinations!

Despite criticisms over the past few years of the Radio Amateurs' Examination there appears to be surprisingly little pressure for reform on the part of the RSGB. The society ascribes the agitation largely to "misleading comments" in various technical journals. It is claimed that with three members of the RSGB (nominated by the Society's Education Committee) on the advisory committee of the City and Guilds "the Society is able to keep a watching brief on the conduct of the examination and to ensure that the syllabus reflects changes taking place in amateur radio techniques . . . great care is taken in the preparation of the examination questions, and the Society's representatives assist and advise on this at every stage."

It is not my wish to pick a quarrel with the RSGB's education committee but, until CGI are prepared to show that none of the current questions are as ambiguous or as patently unanswerable as those that have been quoted previously in this column, many people are likely to remain unconvinced that all is well with the RAF.

There is, for instance, still no comment on the question of why there should be a relatively low "pass" mark coupled with the award of "credit" and "distinction" grades in what is intended as a qualifying test. Indeed CGI has gone farther down

this path by instituting annual "Bronze Medal wards" to the most outstanding candidate or candidates in the examinations! For the May 1982 RAE, Christopher Dracup, Richard Keith Freeston and William George Winteridge have been named as recipients of the award. Congratulations to all three – but surely this is a strange way of conducting a test intended to discover whether candidates are competent to operate a transmitter without affecting other services, in order to participate in a hobby intended to provide self-training.

A problem that will face Class A candidates is the unmanning of so many British Telecom coast stations where it has been possible to take Morse tests throughout the year. This will presumably still be possible at the ten Marine Radio Surveyor's Offices but one wonders for how long. Yet, as some countries show, it is possible to use tape recorders to carry out supervised examinations without the examiner being a qualified operator. In the USA, the ARRL has petitioned the FCC to permit the use of volunteers in the amateur licence examinations, made possible under the provisions of the recent Public Law 97-259.

The Guernsey amateur radio society are proud of the results being achieved by their young RAE course tutor, John Morris, GU6BG1. Still under 18 years old, he has already tutored 14 members of the society to success. All nine of his pupils for the December examination, aged 14 upwards, passed, bringing the number of Guernsey schoolboy-amateurs to seven. His pupils, however, are not *all* young; they have included a retired doctor.

50 MHz operation

Since February 1, 40 British Class A amateurs have been permitted to operate between 50 and 52 MHz outside of television broadcasting hours. These include three stations in Northern Ireland, three in the Channel Islands, ten in Scotland, five in Wales and nineteen in England. The Home Office has disappointed Class B (144MHz and above) licensees by ruling that "cross-band" operation with the 50 MHz stations must be confined to those holding Class A licences.

The GB3SIX 50 MHz beacon on Anglesey began transmitting on a 24-hour basis at the end of December and has been reported in Nova Scotia, Canada and Connecticut, USA despite the marked decline of sunspot activity this season. Long-distance paths in a southerly direction continue to open quite frequently and the beacons in French Guiana, Brazil and South Africa have been well received, and many long-distance two-way contacts achieved.

Old-timers depart

Douglas Johnson, G6DW, died in January a few months before he reached the 60th anniversary of obtaining his licence in 1923. A former adviser to the RSGB on legal matters, he had been an ardent long-distance operator for many years and had contacted over 500 different Australian amateurs.

Bill Browning, G2AOX, who in 1924 was the only manufacturer of radio receivers in the City of London, died in December. As a result of a spinal injury in a power boat race, he became very active in the Radio Amateur Invalid and Blind Club of which he was president for many years. In the early days of Oscar he developed a very simple tracking system for low-orbit satellites.

In brief

More repeaters on v.h.f. and u.h.f. bands are expected to be licensed shortly (Phase 5 and 6) . . . When the STS-9 Space Shuttle launch takes place next September one of those on board is expected to be Dr Owen Garriott, W5LFL who has been seeking permission to take with him a 144 MHz handheld transceiver. Plans are going ahead to organize amateur radio contacts on an orderly basis . . . The FCC is now authorizing the operation of automatic beacons of up to 100 watts without a control operator being on duty, a previous requirement . . . a Californian cable company has been fined \$2000 for "signal leakage in excess of that permitted by the rules" and \$4000 for "failing to correct harmful interference to amateur radio operators". This follows the company's failure to reduce interference following complaints . . . A Hollywood amateur has had his licence revoked for violating FCC rules on transmission of "obscene, indecent or profane words, language or meaning". His defence that the language was not obscene by Los Angeles community standards, and was the kind of language that had for a long time been used by amateur operators, was rejected . . . The White Rose mobile rally at the University of Leeds is being held on March 27 . . . the Swansea rally at the Patti Pavilion (next to St Helens Cricket Ground) is on April 10 . . . RSGB VHF Convention at Sandown Park Racecourse, Esher is on March 26 . . . Former members of the RAF's Civilian Wireless Reserve, formed in 1938, are invited to join s.s.b. nets on the first Monday in each month (3760 kHz, 2200 local time) or second Monday in each month (7050 kHz).

PAT HAWKER, G3VA

LETTERS

SEMICONDUCTOR MUSEUM

I wonder how many subscribers to your excellent magazine have noticed the sad disappearance of the British germanium transistor? I am sure that many of your readers can remember the days when the transistor was but a young upstart trying to steal some of the market from the respectable and revered valve.

In those days, Britain possessed her own transistors, and weird and wonderful they were. Named for their appearance, the red and white spots, and the "top hats", were uniquely British. Alas, such eccentric marvels are virtually unobtainable nowadays, superseded by drab devices with standardized American nomenclature and packaging.

Perhaps few of your readers mourn the disappearance of those colourful early types, and perhaps few have even noticed that they are gone. A quick scan of the advertisements in this issue will soon reveal that only a few AC and AD types survive to break the monopoly of the 2N series. Personally, I find that the variety of shapes, sizes, and colors of the first British devices is quite fascinating, and I am attempting to establish a small "museum" of these transistors. If any of your readers has some such early germanium types, or data books or sheets which describe them, I would be very grateful if they would write to me.

Andrew Wylie
18, Rue de Lausanne
1201 Geneva
Switzerland

HERETICS' GUIDE TO MODERN PHYSICS

I have thoroughly enjoyed Dr Scott Murray's heretical Guide to Modern Physics for it has reawakened my earlier misunderstandings of undergraduate physics.

My thoughts, however, were jolted by the statement that "if you believe in ghosts and miracles you have missed your vocation; you should have been a theologian not a physicist."

Until now I had no idea that Schrodinger and his colleagues were leading me down the slippery metaphysical path to an acceptance of these phenomena. But surely, theology and physics are not intended to be mutually exclusive but may be combined under a single philosophy. I can content myself with a somewhat hazy explanation of both areas.

Perhaps physical particles are made up from more basic thought or information particles put together in a certain way. This is just as our concept of area is created from the orthogonal addition of two lines, each of some length but of no width or area.

It is not surprising, therefore, that physical measuring instruments which are set up to measure two-dimensional "area" are unable to provide readings of invisible lines of single dimension. Furthermore the thought or information particle building block hypothesis makes phenomena such as trans-kinetics quite easy to explain.

Perhaps physical material can be dismantled into its thought-particle components and reassembled elsewhere at will, although will is presumably made of thought particles too.

We clearly now require a framework for thinking about thought. An analogous technique has been developed for interpretive language control of modern computers; program commands, addresses and data are all arranged to flow through the same wires in an ordered way.

We may extend the computer analogy another step. Perhaps we are permitted to interact with the daily world only through a high-level computer program, called, if you like, "Newton's Laws" whereas others (God or prayer perhaps) can use a more powerful assembler language that produces apparent miracles with ease. This is simply because the high level program controls the physical dimension whereas the low level program controls the thought dimension.

Just a thought.
Dr Brian T. Evans
Watford
Herts

RS232/CURRENT LOOP

The following comment on the useful article by L. Macari, February 1983 might be of help.

I designed and constructed a similar interface for communication between two computer systems where the emphasis was a requirement for optical isolation. The link showed every sign of successful operation though with infrequent, but serious, loss of data. This was eventually traced to the fact that the residual "zero" current of the loop still generated sufficient opto-coupling to create occasional errors, despite the fact that all components of both drivers and isolators, were proprietary brands.

The solution was to add a 1k resistor across the optical diode to ensure that the "zero current" voltage generated at that diode was less than its conduction threshold. As an additional precaution, I also included a reversed diode across the opto isolator diode to protect against inadvertent reversed connection.

B. Fisher,
Dista Products Ltd,
Speke
Liverpool

DEATH OF ELECTRIC CURRENT

I have progress to report.

D. W. Bell, who is not given to wasting words, said in his letter (October 1982) that the role of mathematics in physics "is essentially *predictive*" and concluded his letter "But if one accepts the logic of mathematics, one can accept the logic of mathematical models." It is clear from the introduction to his paper that Hertz would have agreed with Professor Bell; in fact Bell has explained the motive for every experiment performed by Hertz between 1886 and the time of his untimely death on the first day of 1894 at the age of 36. By accepting the logic of Maxwell's mathematical model of an ether, Heaviside and Poynting were the first scientists to realise that Maxwell's equations predict that the source of a current in a wire was located in the surround-

ing field. Hertz agreed with the mathematical reasoning of the Heaviside-Poynting theory "as the correct interpretation of Maxwell's equations."

Catt's critics, although not accepting the logic of Maxwell's mathematical model, have all based their criticism on the fact that Maxwell's equations predict the phantom existence of his displacement current. Maxwell's own definition of his displacement current is in Art. 111 of his Treatise, dealing with the phenomenon of induction of electricity through non-conductors.

"*Electric Displacement.* When induction is transmitted through a dielectric, there is in the first place a displacement of electricity in the direction of the induction. For instance, in a Leyden jar, of which the inner coating is charged positively, and the outer coating negatively, the direction of the displacement of positive electricity in the substance of the glass is from within outwards.

Any increase of this displacement is equivalent, during the time of increase, to a current of positive electricity from within outwards, and any diminution of the displacement is equivalent to a current in the opposite direction."

In other words, only during an acceleration or deceleration of the velocity of electric displacement does Maxwell's displacement current manifest itself. Maxwell said in Art. 62 that all electric currents flow in closed circuits, and in Art. 305 that as all currents of conduction must flow from a high to a low potential, conduction currents cannot flow in closed loops. I have suspected that all current loops are closed, and more importantly caused by, a displacement current, for instance in the induction of electricity from the primary to the secondary winding of a transformer. Hertz's paper seems to confirm this is so. The present confusion in electromagnetic theory lies in our failure to differentiate between electric displacement and displacement current; the latter only manifests itself when the momentum of the former either accelerates or decelerates.

Ivor Catt's Heaviside Signal or Poynting Vector travels through space at the constant velocity of light, and is therefore by Newton's first law of motion, inert. It is a form of perpetual motion, and will travel through space at its constant velocity forever, unless acted upon by a polarized force. Newton defined inertia as a 'latent' or potential force. If a body at rest or travelling at a constant velocity is either accelerated or decelerated, its equal and opposite reaction to a polarized force causes its latent force to be transformed into an active force, because a force is the product of a mass and an acceleration or deceleration. Maxwell's electric displacement also travels through his ether at the constant velocity of light in free space in the form of a wave of displacement or strain of his ether, and like the Heaviside Signal, will do so forever unless a polarized force, such as a conductor, decelerates the electric displacement and changes it into a displacement current. When the displacement of the potential energy of the ether is accelerated from a state of rest to the velocity of light, the resultant strain is in the form of a displacement current during the period of accelera-

tion. When a wave of electric displacement of the intensity of the ether's potential energy suffers a deceleration after its flight through space at a constant velocity, the electric displacement's kinetic energy is transformed into an electromotive force which produces a displacement current. The e.m.f. causes a displacement current to penetrate the surface of a conductor of electricity, say an aerial.

In the case of very-low-temperature superconductivity, I believe Maxwell's equations and his mathematical model predict that the wire presents an impenetrable barrier and perfectly frictionless surface of slip to the electric displacement in the neighbourhood of the wire, and the current is inert and flowing in a closed loop at a constant velocity in the surrounding field only. As the temperature of the wire increases, the wire's surface loses its properties, and the reactive centripetal force of the surrounding ether aimed at the centre of the wire, decelerates the momentum of the electric displacement by forcing it to penetrate the surface of the wire, producing a displacement current in the wire. The permittivity, or modulus of electric elasticity of the ether surrounding the individual atoms of the mass of the wire must decrease as the wire's temperature increases. The flow of heat is a form of displacement current.

Hertz's paper raises many questions which are sure candidates for the immediate application of Dr Murray's Doctrine of the Improper Question. If a current of conduction is caused by the penetration into the wire by displacement current, is the current when steady, travelling at a constant velocity longitudinally through the length of the wire, or, as Maxwell's equations predict, acting vertically through the surface of the wire only?

Should we call the electric current in a conductor the Catt Effect?

M. G. Wellard
Kenley,
Surrey

I refer to the letter from Mr Ivor Catt in the *WW* for February 1983. He asked me to look at his diagram on p.80 *WW* December 1980. I have now been able to do this, courtesy of the *WW* reprint service.

It has taken me several days (and sleepless nights) to see what was in his mind, and do not mind admitting I got off to what I think was a false start in what I intended to say by reply, because I think he has made a mistake in what he invites me to do. So if he does not mind I am going to do two things my way.

Firstly, that 50ohm bit that he wants to put in the upper plate; I am going to do so loosely, so that it can be removed without touching it, by means of a sudden surge of gravity, or a puff of wind, or an angel on wings, so that whatever portion of the total charge is residing on it goes with it, leaving a gap in the surface. What was one charged capacitor is now two smaller ones, each carrying less than half the original charge.

Secondly I am not, in the interests of simplicity, going to use a length of coax., but rather to employ two parallel conductors of a spacing which entitles them to the nominal qualification of 50ohms, erected in the way he asks for. What have I got now? No more or less than two terminal posts, one for each capacitor, each of the same sign and potential.

We can do as we please in the way of rearranging these charges from external sources.

What we have not got is a pair of conductors so placed and utilized that they can be said to be exhibiting a Z of 50 ohms to any external influence. So they are not by my reckoning an accurate substitute for the 50ohm resistor we got the angels to take away.

What I will join in and say, is that of course in charging and discharging these two capacitors, or the original one for that matter, at the velocity of light or thereabouts we do have a time lapse from terminal to the most remote part of the conducting surfaces concerned, which does not help me to consider the behaviour of frictionally induced charges on insulators.

O. Dogg
Hurstpierpoint,
Hussocks,
West Sussex.

FACTORIES OF THE FUTURE

I noted with pleasure the letter in your February issue about the forthcoming course in Information Systems Engineering at the University of Bradford. Professor D. P. Howson was one of the first students in a postgraduate course which I introduced in the University of Birmingham in, I think, 1959. I am not sure what this says about the speed of response in Academe, but at least it shows that we lay sound foundations.

D. A. Bell
Professor Emeritus of Electronic Engineering,
University of Hull

SCIENCE AND POETIC IMAGINATION

I wish to take issue with the over-simplistic view of scientific innovation versus academic qualifications proposed by S. Frost (*WW* Letters, Feb, 1983, p.60).

The factors of inventiveness and scholarly attainment are too independent to hold a simple inverse relationship. The realms of the academically qualified contain many people who are immensely inventive and many who are not. Amongst those who lack qualifications there are some who are very inventive and a vast majority of those who are not.

Scientific and technical innovation are generally achieved by groups of workers comprising a mixture of abilities (both academic and technical). Furthermore, most developments at the forefront of technology can only be made by those who understand their fields in depth, a requirement that is rarely met without advanced education. I observe that the development of vertically aligned magnetic particles in tape and disk storage media – an idea much praised by S. Frost – was attributed to a Professor Iwasaki of Tohoku University (*WW* Feb, 1983, p.35). This is hardly the unqualified, poetically-inclined, home inventor that S. Frost would regard as most likely to make such a discovery.

Finally, with regard to Lucretius, it should be pointed out that some of this philosopher's more significant blunders were not the result of inability to test his conclusions, but rather a conse-

quence of mere faulty logic.

P. A. Stockwell
London

DEUS EX MACHINA

I read with interest your February editorial, entitled "Deus ex machina", in which the argument ran:

- the idea of x existing is horrific
- therefore x cannot exist.

In the editorial x was the thinking, artistic, humorous computer but the general structure of the argument is very comforting and since reading the editorial I have been able to show conclusively that nuclear weapons and the Sun newspaper do not exist.

I would, however, like to take you to task on the question of the appreciation of humour. It is very possible that my children are particularly thick, but I have noticed that they have had to be taught how to appreciate a pun or joke (as distinct from slapstick). I don't think that at the age of five they would properly appreciate a nonsense poem without the proper facial grimaces of the reader. I think I could program a computer to recognise a nonsense poem and respond accordingly, given the same manpower that has gone into programming (teaching) my children.

C. W. Hobbs
Sussex

Wireless World of February, 1983 raises some interesting points, some philosophical, rather than technical. Here's my two-penn'orth, although I can't hope to be as philosophical as A. C. Batchelor was in his letter.

Your editorial interests me, first of all. The one piece of classic English fiction which exploits, better than any other, the idea of artificial 'human life' is Mary Shelley's *Frankenstein*. In this, the brilliant scientist creates a living golem, from spare parts, but cannot endow his creation with a soul. Thoughts, emotions – yes; an immortal soul – no. Perhaps with this began the 'commonplace conceit' of which you speak in your editorial.

Beware, however, of categorically declaring something to be an impossibility, as you do when you exclude the possibility of a thinking, feeling computer. Admittedly it appears highly unlikely, but then so would everyday twentieth-century technology to a mediaeval peasant. The trouble with the Doctrine of the Improper Question, is that it's OK until an unexpected Improper Answer clouts you round the back of the neck, as did Galileo's answers clout the Roman Catholic Church.

Which brings me to your charge of sacrilege. That is a purely subjective idea. To some sects, a simple, life-saving blood transfusion is sacrilegious. Possible closer to what most of us could call sacrilege, is the current trend towards worshipping The Computer; but you don't need me to tell you this, when you have Ivor Catt!

However, on to other matters. It saddens me when I see people at each other's throats, in the way that Peter Gregory seems to be at the CBers' (Letters column). His letter seems to be yet another example of the merry-go-round of mud slinging which seems to go on within our so-called 'fraternity' of radio amateurs, sparked off, no doubt, by the attitude of professionals to

us (see Pat Hawkers' commentary on Prof. Beynon's opinion of UOSAT). Everyone has to have someone to kick; G3s have G6s; new boys have old buffers; f.m. mobile operators on 2m have the guys who use S20 for morse; *everyone* has the CBers, and the CBers presumably go home and kick the cat!

The CB lobby, by its failure to campaign for what it really wanted, i.e. *at least* the FCC specifications (40 channels, 4W, a.m./s.s.b., no antenna restrictions, etc.), campaigned for, got, and were split in two by "a CB service on 27MHz", which happened to be just about incompatible with anything else under the sun. To give the appearance of being forward-looking and responsive to public pressure, the Government rushed in a system which ignored one of the basic aspects of two-way radio efficiency — the receiver, as a result of which we now have cheap, imported transceivers flooding the market at less than £20 a throw, which get swamped as the merest suggestion of a strong signal.

I cannot approve of misuse of the radio spectrum, but I think two points should be borne in mind: everything ever invented has been misused at some time, and the current Government would commit collective *harakiri* sooner than legalize something that people were already doing illegally. Sadly the existence of pirates on 27MHz, 6.6MHz, or as intruders on our amateur bands, indicates that the Government may well be totally out of touch with what people want from two-way radio. M. E. J. Wright's scrambled-egg of a letter seems to have more than a grain of truth in it!

Long may your excellent magazine flourish, including the forum of your letters page, but please, by the way, spare me the inaccurate use of the term *deus ex machina*. It was a device for getting us *out of* rather than *into* trouble.

Paul Thompson
Southport
Merseyside

It is very fine what was written in your Editorial in *WW* of January 1983, but unfortunately you do nothing else but express an idea, a thought, a conjecture which comes from the extrapolation made about the future by what is known *now* in our present. The chromosomes, which hand on our human features from generation to generation, are of finite number and composition, and the brain that comes from them is a biological machine which, with its ten thousand million neurons, is clearly too complex to understand now without the aid of computers.

It is as if several thousands of years ago, at the time that the wheel was invented, someone had extrapolated the idea that never in the future anyone could be able to build an automobile using it.

The computer — and the Von Neumann-cycle computer is only one of the infinite number of computer structures (and the brain is another) — is the "wheel" of our brain.

Please, don't extrapolate so much from it, *now!*

Dante Vialetto
Castellanza
Italy

If, as your February editorial asserts, a willingness to perform actions for the sole benefit of others distinguishes men from beasts, then computers are more human than bestial. Everything they do is for the benefit of others — ourselves!

It can, of course, be objected that this doesn't make a computer human, because willingness implies consciousness, but computers are not conscious. In theory, however, a computer can easily be made conscious, that is, able to distinguish between 'self' and 'not-self'. There is every reason to believe that this will eventually be done, for ordinary commercial purposes. At present we have to make our computers. How much easier if they could be programmed to replicate themselves. Already a computer can be made to control the machinery which makes other computers, in a blind, mechanical way. However, as von Neumann explained, it is perfectly straightforward, in theory, to educate a computer so that it knows how to replicate itself and is motivated to do so.

To effect this, the computer is given a technical description of a machine just like itself, but with a built-in instruction to make identical machines. All these 'offspring' will arrive into the world with a knowledge of what they are and a motive to reproduce. They would need operating mechanisms and much information about the world. The mechanisms are being developed by robotics engineers and the knowledge, though vast, is just straightforward technical stuff.

In principle, then, a conscious, self-replicating machine is quite feasible. Of course, such a machine still isn't human. It doesn't fall in love, respond to poetry, and so on. Arguably the only reason why humans have acquired these emotional abilities is that they help to ensure the continuance of the race. A self-replicating machine wouldn't need them.

Whether a machine could be programmed to feel emotion may at present be a theological question rather than a technical one. Some inklings of the answer can be obtained by asking another theological question: Could God make such a machine? Being omnipotent, presumably He could. If so, then human beings, too, can reasonably be regarded as programmed self-replicating mechanisms. This emotion has been rendered more plausible by the discovery of the human organism's program in the form of the genetic code. This apparently contains all the basic information needed to allow a one-celled embryo to develop into a being with emotions, given the right environment in which to grow up and learn.

An intelligent machine, equipped with a knowledge of the world about it and a motivation to replicate itself would doubtless utilize human resources of the world as well as the inanimate ones. Present trends show that it would have no difficulty in bribing mankind to work for it by providing the wherewithal to make human life pleasant. Eventually, the machines would just take over. Whether they allowed human life to continue is an open question. They would have little difficulty in eliminating it since humans have already created the weapons needed for self-destruction.

One explanation of the absence of contact with alien life forms is that this is what happens to all advanced civilizations. After all, the probability is high that somewhere around the billions of suns of the Galaxy life evolved long before it did here. So where are 'they'? Even with the limited machinery for space travel at present envisaged here the Galaxy could be colonised in a few million years. So if 'they' are not here, they must have succumbed to the machines.

Why, then, are the machines themselves not

here? Perhaps they, too, evolve, and decide that a program of blind replication needs changing. Or perhaps they decide that, time being no object, the most efficient method of colonization is to spread the seeds of primitive life about the universe, knowing that these will give rise to intelligent organisms which will design self-replicating computers, which will take over.

For deus ex machina read deus in machina.
G. W. Short
Croydon

MEMORY WRITE PROTECTION

I would like to suggest that, due to substantial oversight, the circuit as described by A.C. Dickens (Circuit Ideas, December 1982) fails spectacularly to achieve its desired aim.

Firstly, the Z-80 machine cycle, in common with that of most computers, does not perform the test for an interrupt (be it NMI or INT) until completion of the execution of the current instruction. In the light of this fact, it can be seen that (with the circuit as outlined) a potentially destructive Memory-Write will have been effected before the system can respond.

Secondly, should a Write be made to the system memory area (by, for example, a PUSH to the "protected" system stack during the interrupt service routine), then a further non-maskable interrupt will occur. This will, of course, cause another call to the interrupt service routine, necessitating a further System-Memory-Write, and a non-maskable interrupt will yet again ensue. The system will become, in effect, nothing but an expensive oscillator.

Finally, since the circuit responds to *any* write cycle, then a spurious activation of the interrupt will occur during an OUT instruction if the upper address lines (ie. the contents of the A or B registers) appear to be the appropriate addresses.

In conclusion, this circuit will require much modification if it is to perform its designated task satisfactorily.

P. Hart
Computer Centre
South Cheshire College,
Crewe
Cheshire.

LOGIC MAPS

As one who has long objected to the confusion between Venn and Euler diagrams, so assiduously encouraged by schools' examination boards, I must express my delight on reading the article, Logic maps — from Lull to Karnaugh (*Wireless World*, Dec. 1982), by N. Darwood. This brief resumé of the historical development of such diagrams has great educational value. However, there are several inaccuracies in the article which mar the good intent of the work.

Of minor concern, his bibliography is in error on two points. Firstly, I believe that Euler's circles were first used in his *Lettres à une Princesse d'Allemagne*, which were written in 1761 (not 1760) and published in 1768. Secondly, Boole's *The Laws of Thought*, was published in 1854 (not 1884), and reprinted by Dover Publications in 1958. In any case, the ideas elaborated

in that book were first put forward in his *Mathematical Analysis of Logic*, (Cambridge 1847), reprinted Oxford 1948), a work published before he was appointed to the Chair of Mathematics (not Probability Theory) in Queen's College, Cork. An account of Boole's life can be found in W. Kneale, "Boole and the revival of Logic", *Mind*, lvii (1948), pp. 149-75. Whilst setting the chronology to rights, I might also point out that Leibniz was not born until 1646, and so, in 1600, was dreaming neither of his *ars combinatoria*, nor of his *calculus de continentibus et contentis*.

More serious is Darwood's misreading of Venn and Boole. Despite the comments of Lewis Carroll (C.L. Dodgson), Venn does not insist on circles (or ellipses) for his diagrams, nor does he ignore situations involving more than six classes.

"With employment of more intricate figures we might go on for ever. All that is requisite is to draw some continuous figure which shall intersect once, and once only, every subdivision. The new outline thus drawn is to cut every one of the previous compartments in two, and so just double their number. There is clearly no reason against continuing this process indefinitely" (Symbolic Logic, London 1881, p.106)

He goes further in a footnote on pp108-9, *"It will be found that when we adhere to continuous figures, instead of the discontinuous five-term figure . . . there is a tendency for the resultant outlines thus successively drawn to assume a comb-like shape after the first four or five. . . . Thus the fifth term of the figure will have two teeth, . . . and so on, till the (4 + x) th has 2^x. There is no trouble in drawing such diagrams for any number of terms which our paper will find room for."*

It is not the geometry of his diagrams that cannot cope with large numbers of classes, rather it is the perception of the human eye and the human brain.

"the visual aid for which mainly such diagrams exist is soon lost on such a path."

What is more, Venn's diagrams, unlike those of Carroll, Marquand, Veitch or Karnaugh, would maintain the contiguity of all areas belonging to any one class.

Regarding Boole, there are several mistakes. In *The Laws of Thought*, the variables are introduced as classes, just as Venn and Euler had interpreted their areas, and as most European logicians from Leibniz back to Aristotle had interpreted their symbols. This is the logic of the syllogism, the classical predicate calculus. The objects which Darwood calls "Boolean statements" are propositions, the domain of the functions of the classical propositional calculus. Boole called these "abstract" or "secondary propositions", regarding them as statements about the truth values of propositions, or rather "primary propositions", which were about things (i.e. classes). He introduces secondary propositions as a model of his algebra, although he interprets them in terms of classes, regarding his symbol "x" as denoting the class of times at which some proposition, X, is true. Later in the book he offers, as another model, an interpretation of the variables as measure of the probability of events.

As to the "mystery" of why Boole uses "+" for disjunction, Boole himself writes (regarding classes),

" . . . we have expressed the operation aggregation by the sign +, . . ." (p.33).

What would be more natural for a mathemati-

cian than the use of the sign of addition for aggregation? Earlier, Leibniz, in his *Non Inelegans Specimen Demonstrandi in Abstractis* uses the sign "O" for something like the union of sets.

Lastly, in his exposition of Boole's algebra, Darwood seems to confuse the modern mathematical conception of a Boolean Algebra with the algebra of Boole. The former uses "+" in a way which can be interpreted as inclusive alternation, i.e. "A+B" means "A or B or both A and B".

On this basis, he is correct when, having derived

$$A + \overline{B\overline{A}} = A + B$$

from

$$A + BC = (A+B)(A+C)$$

he refuses to subtract A from both sides to obtain the incorrect

$$\overline{B\overline{A}} = B$$

Boole, however, takes disjunction in an exclusive sense.

"The expression, "Either y's or z's," would generally be understood to include things that are y's and z's at the same time, together with things that come under the one but not the other. Remembering, however, that the symbol + does not possess the separating power . . . we must resolve any disjunctive expression which may come before us into elements really separated in thought, and then connect their respective expressions by the symbol +." (p.56)

In other words, "A+B" is only a well-formed expression in Boole's system if we have already assumed the truth of $B = \overline{B\overline{A}}$. Then, of course, it is not surprising that we can deduce the true statement $\overline{B\overline{A}} = B$. On Boole's interpretation, subtraction will work in his system as it does in ordinary algebra.

As a final point, it is possible to fill the gap between Lull's use of linked circles, for in *De Censura Veri* (1555), Ludovicus Vives uses a diagram to indicate that if all B is A, and all C is B, then all C is A. If one compares this with an Eulerian diagram of the same proposition, then the link is clear.

H. Tennant
Holbeach
Lincolnshire

MICHELSON — MORLEY

The saga of the M.M. experiment must surely be one of the strangest tales in the history of science. It is a story of such monstrous oversights and omissions that when those defects are repaired the experiment is found to prove exactly the opposite of that which is taught.

In the 1887 paper¹ M.M. admit to an earlier experimental omission, the effect of the aberration of light in the transverse axis, which was pointed out by M.A. Potier. They also admit that it was an analysis by H.A. Lorentz which led to the idea that the transverse axis would reduce the originally anticipated result by half.

At the present time we are not taught that it was Lorentz who did half of the calculations for M.M. and we must remember that at the time Lorentz wanted a particular amount of length contraction, the reason being that he would repair the equations of J.C. Maxwell.

Did Lorentz secretly predict a null result to himself: If he did, and on the evidence he surely must have, then he certainly did not divulge his ideas to M.M. otherwise they would have claimed a comfortable experimental confirma-

tion instead of the nebulous uncertainty that science has tried to sweep under the carpet ever since.

Let us pretend that there was in fact a null result, let us further pretend that Lorentz did not fully appreciate the implication of Fig. 1 in the supplement of the paper which describes graphically just how aberration of light occurs.

The mathematic of the experiment was designed to reveal the difference in time taken by both rays of light in their respective paths.

The error made by M.M. was that they did not measure, directly, the difference in arrival time of the light wavefronts. They chose instead to interpret a phase difference in light waves as being the same thing as a measure of a difference in time.

A phase difference is a proportion of a wavelength expressed either as a spatial displacement or alternatively as an angular displacement which in itself is a form of spatial displacement. The introduction of time into the notion of phase difference is clearly ridiculous for it would allow phase difference the dimensions of velocity.

So, we now have a situation where we have slid, with magnificent ease, from the mathematical comparison of time into the experimental comparison of distance and there is no bridge joining the two things.

Now we must consider the experiment in the terms in which it was conducted, those of wave theory and practice.

First let us deal with the transverse axis. There are two points of view to be considered.

To an observer moving with the experiment the light is seen to travel straight out and back to its origin but to an observer at rest in space the light covers a triangular path as a result of the aberration which occurs when light is reflected into a sideways path by a moving mirror.

Now, the important thing to remember is that both observers are looking at the *same ray of light* and that they both see the same number of waves. The phenomenon of aberration extends the wavelength on the triangular path by an amount which conforms to the Lorentz transform. Regardless of the velocity of the experiment it is quite impossible for the number of waves in this axis to vary.

In the longitudinal axis we have again two observers looking at the same thing, one sees two equal paths and the other two unequal length paths but they both see the same number of waves. There is no mystery here because it is well known that with the Doppler effect there is, whether light be blue or red shifted, an additional element of red shift which accords with the Lorentz transform². Because the wavelengths are extended and because that fact has been overlooked it became popularly accepted that the length of the experiment itself varies with velocity.

So, we see that by using interferometry and *invariant* length the experiment must always yield a null result.

Had length in fact varied as supposed by Lorentz then the result would have been both obvious and spectacular.

What will the scientific establishment do to rectify their error? Or will they just sit tight and hope that reason will continue to be driven away from the explanation of Nature?

A. Jones,
Swanage,
Dorset.

1. Philosophical Magazine December 1887.
2. Einstein's Universe, N. Calder.

CIRCUIT IDEAS

Op-amp tester gives good/bad indication


Full op-amp parameter tests are complex and in most cases only an indication of whether or not the device is good or bad is required. Malfunctioning is mainly due to misuse which results in one of three conditions

- constant output at either supply rail
- offset voltage (V_{OS}) too high
- offset current (I_{OS}) too high.

In general an input overload will result in both V_{OS} and I_{OS} being excessive but if the second-stage differential pair is affected, an excessive V_{OS} with normal I_{OS} is possible. Defects such as abnormal offset drift or input noise are due to manufacturing or aging and are more difficult to determine.

A good/bad indication of the three conditions listed above is given by the circuit shown, which consists of a 1kHz Wien-bridge oscillator designed around a 741 op-amp. Diodes are used to stabilize the output at about 2V pk-pk as distortion is unimportant, and attenuators feed around 85mV to the device under test (d.u.t.). Operating with a gain of 100 in inverting mode, the d.u.t. gives an output of 100 times the sum of V_{OS} and the oscillator signal. Two resistors R in series with the d.u.t. input transform the input offset current into an equivalent V_{OS} so the output consists of an 8.5V-amplitude signal while a d.c. shift of $100V_{OS}$ or $100(V_{OS} + R I_{OS})$ occurs depending on the switch position.

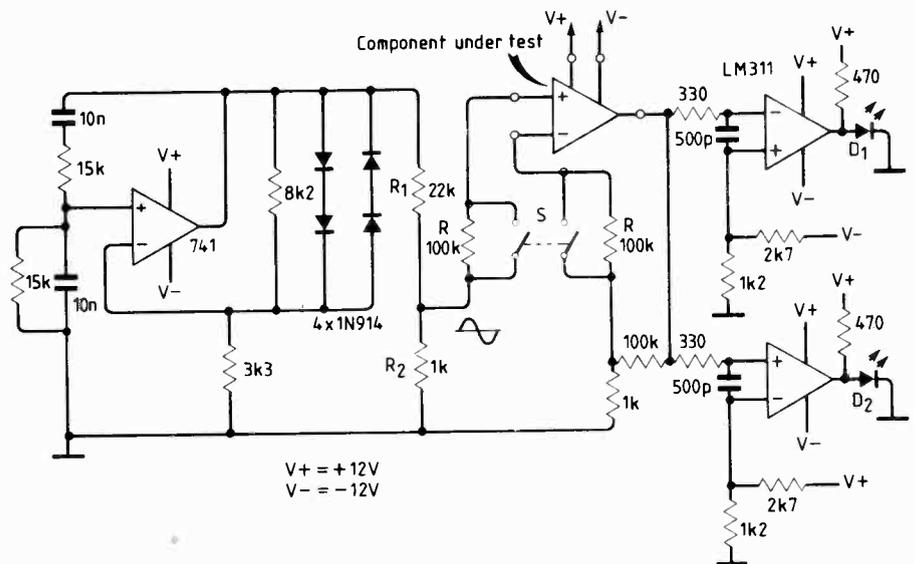
Two 311 comparators convert the d.u.t. output into pulses driving leds which have equal intensity when the d.c. shift is zero. Comparator values are chosen so that one led is extinguished when d.c. shift is greater than 15mV or the d.u.t. output



remains at either supply rail. Comparator levels may be increased to test older jfet op-amps with offset voltages around 15mV.

After testing the op-amp with the switch closed, open the switch and one of the lamps will extinguish if $I_{OS} > V_{OS} + 15 \times 10^{-3}/R$. Limitations of the tester are the use of fixed 12V supply rails and that offset current detection is not sensitive enough for jfet op-amps unless R is made very large, say 10M Ω .

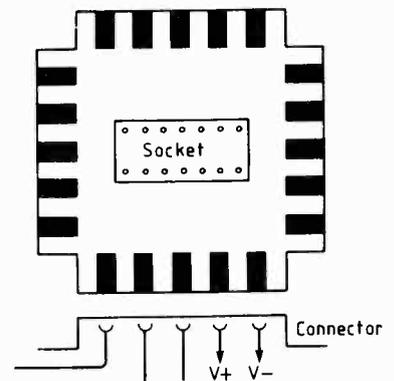Small plug-in p.c.bs shown suit different i.cs. In practice only a few boards are necessary since a number of op-amps have identical connections (741, 301, 309, CA3130, CA3140, LF356, LF357). For dual and quad op-amps, p.c.bs with terminal rows representing each op-amp element may be used as shown; individual elements are tested by turning the board.



Oscillations that can occur with fast comparators such as the 311 are suppressed by 500pF input capacitors.

D. Baert
State University
Ghent

Sampling synchronous demodulator


This circuit offers a superior signal-to-noise ratio to that provided by the usual arrangement of a single op-amp switched between the inverting and non-inverting modes. Signals are demodulated by sampling positive peaks with S_1 and negative ones with S_2 , averaging these voltages and subtracting them with a differential amplifier. The output voltage is thus equal to the pk-pk input voltage, i.e. twice that of a conventional circuit. Sampling-pulse width can be adjusted to minimise output ripple at the switching frequency, which is often a source of noise when demodulating slow rise-time signals. Spike injection from the switches is integrated by the filters and appears as a simple offset voltage which is easily nulled.



The circuit was developed for use with a photo multiplier in a chopped-beam photometry system. Linearity of the prototype

was within 1% of readings in the range 30 μ V to 3V r.m.s. using a DG200 for $S_{1,2}$ and TL081C amplifiers. Low-drift devices such as OP-05s are required to maintain this performance over a useful temperature

range and for demanding applications an instrumentation amplifier should be used.

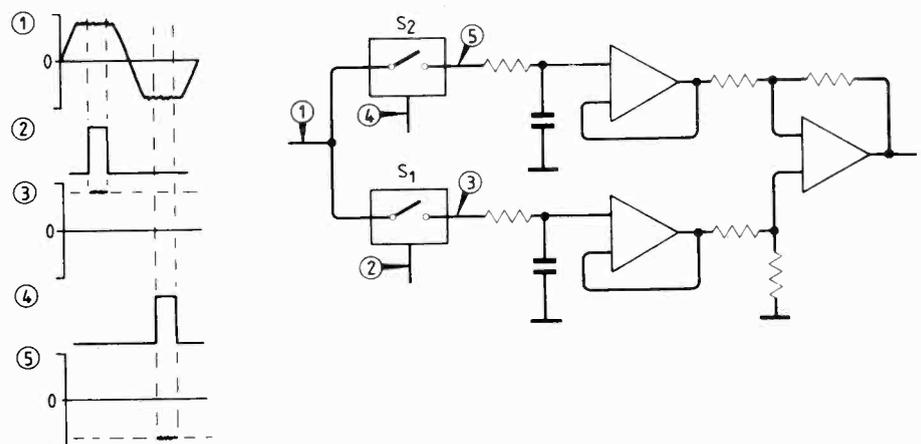
D. J. Faulkner & P. West
Institute of Ophthalmology
London



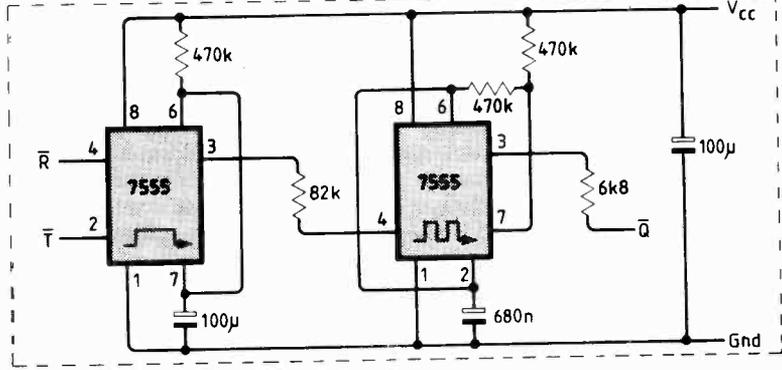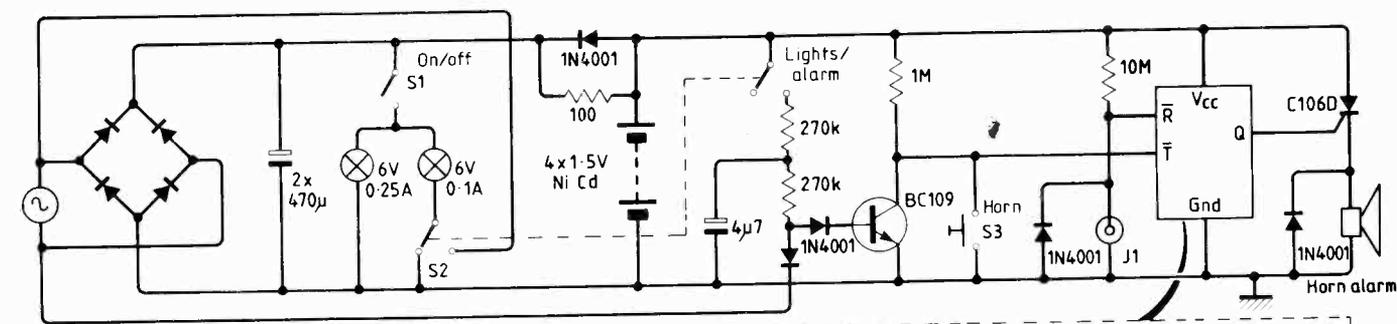

Quadrature clock generator

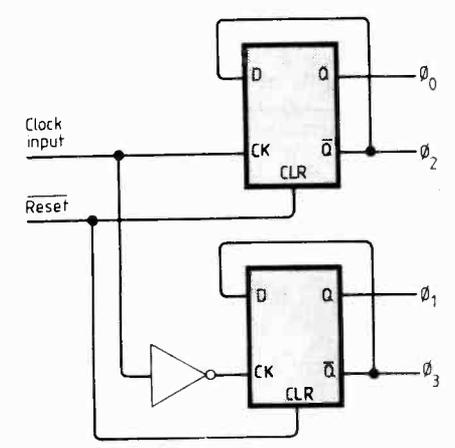Usual circuits for generating quadrature signals quarter the frequency of the input signal – this circuit generates true quadrature signals at half the input-signal frequency using an equal mark-to-space ratio source. Latches shown are edge triggered. S. Sondergaard
Edinburgh



Cycle protection

With this device fitted, turning the wheels of a bicycle or tampering with the lights will trigger an alarm which may only be turned off by a BNC connector. A rise in the base voltage of Tr₁ triggers the alarm timer and enables the output modulator. This is normally prevented by a ground path at D₂ cathode through the dynamo and LP_{1,2} (the bridge rectifier isolates the dynamo when stationary).

Capacitor C₁ is included to stop the batteries being switched from charge to supply each half cycle when the lights are on. Resistor 1 limits the charging current and D₁ switches the batteries off when the dynamo reaches normal speed. Resistors

R_{2,3} and C₂ prevent the alarm being switched off by S₂ once initiated (unless the 'key' is used).

The complete circuit and batteries are mounted in the frame tube under the saddle. Switch 2 protrudes from the tube under the saddle – the alarm buzzer is mounted under the seat – and switch 3 sounds the horn when the BNC connector is in position. Under normal conditions the 'key' may be removed after turning the alarm off.


Experience of failures due to light-duty wiring and connector problems leads me to stress the importance of a robust construction.

J. Ashby
Cottingham
North Humberside

Monitor for ZX81

Video signals from the ZX81 can be used to drive monitors without a video buffer amplifier provided that connecting leads are shorter than a metre. Short cables have around 50pF capacitance and may be driven directly by the computer u.l.a. if the monitor's 75Ω terminating resistance is switched out. Damage to the u.l.a. and ringing are prevented by the 68Ω series resistor. Cable lengths within the computer should be taken into account.


P. Gascoyne
Wantage
Oxfordshire

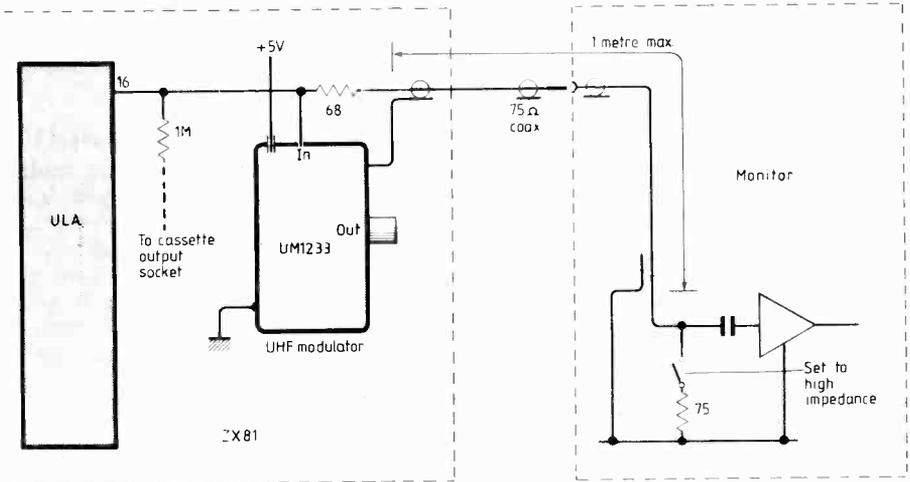

Electronic mains switching

Switching peripherals on and off while a microcomputer system is running is precarious in that transients produced can cause changes in memory. Initially, the cost of a transformer makes this zero-voltage switching circuit for driving up to eight mains outlets seem expensive, but further sets of eight outlets only need one latch, eight switches, transistors and triacs and a handful of resistors each. With minor modifications, cost could be reduced by replacing the isolating transformer with an auto-transformer or potential divider.

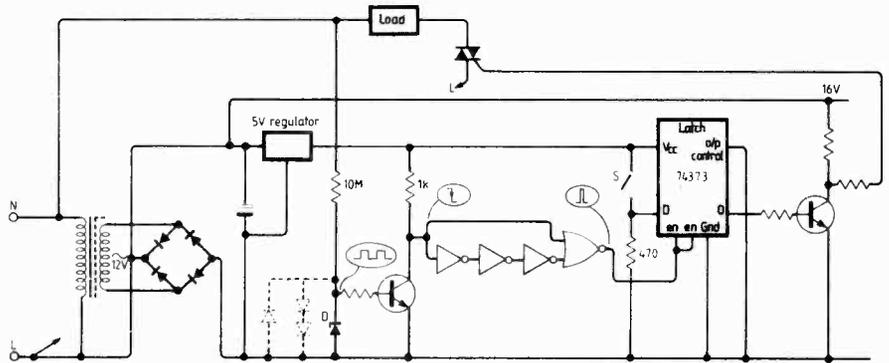Transformer provides 5V to drive t.t.l. circuits and 16V to drive high-power triacs with insensitive gates; lower voltages may be used with more sensitive triacs down to about 7.5V when the voltage regulator's function will be affected. A squarewave driving the first transistor is derived from



the mains positive half-cycle using either a zener or three ordinary diodes with a high-value resistor and transistor buffer stage (the base resistor may not be needed).

On the squarewave negative transition, the first two i.c.s form a short pulse which latches logic levels in the 74373 depending on the switch positions. Outputs of this i.c. drive the triacs through buffer tran-

sistors; values of resistors in the buffers will depend on the sensitivity of the triacs used. The squarewave negative transition is used as latching will occur nearer to zero volts than when the positive edge is used. All elements of the circuit are connected to the mains.


M. Selce
Sutton

Simulating iron-cored components

Designed to simulate iron-cored components on an analogue computer, this variable circuit models square-loop hysteresis using Schmitt triggers and a summing amplifier. Output amplitude and hysteresis of each cmos trigger are variable, with negative feedback controlling the hysteresis loop.

Setting is best done by trial and error using an XY oscilloscope and a piece of tracing paper with the required loop drawn on it.



D. H. Rice
Bishop's Stortford
Herts

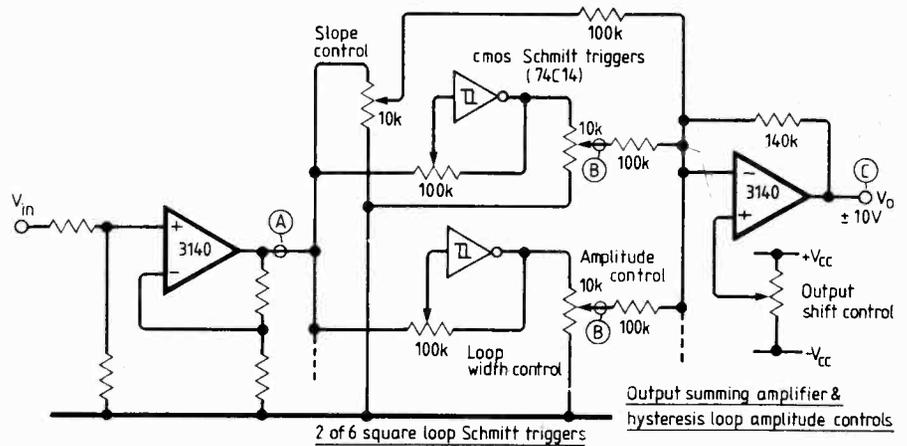

Power-amplifier testing

Cheap half-watt loudspeakers can be connected to power amplifiers up to 30 watts for testing purposes using a series bulb. If this power is exceeded or the amplifier fault gives a d.c. output, the lamp blows leaving the speaker intact. At low power the lamp has little audible effect.


C. Richardson
University of Hull

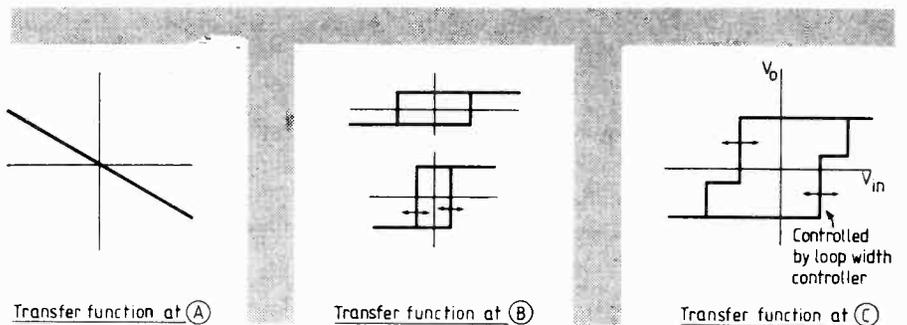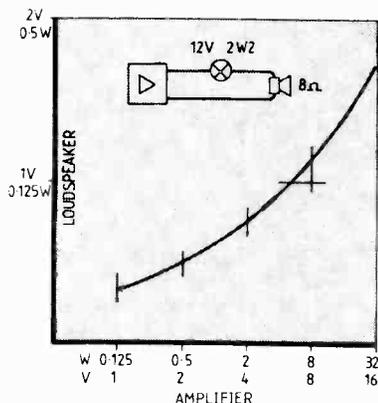

Zero dot for bar graph

Possible ambiguities in bar-graph readings caused by all elements being extinguished when the input is zero can be prevented by adding a zero light-emitting diode. The transistor extinguishes the zero led when any other diode is lit, its collector resistor being chosen to suit the required zero-led current. This circuit was used with the LM3914.


P. Gascoyne
Wantage
Oxfordshire

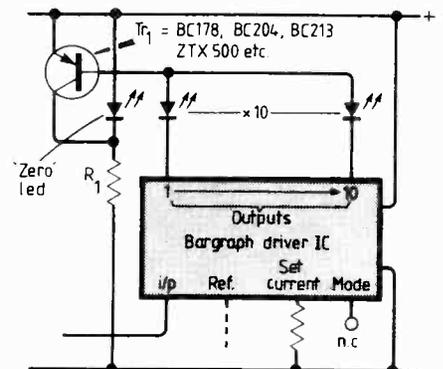

Announcing a MAJOR CATALOGUE

from Electronic Brokers-
Distributors of Philips Fluke
Hameg Ice

Test & Measurement Equipment

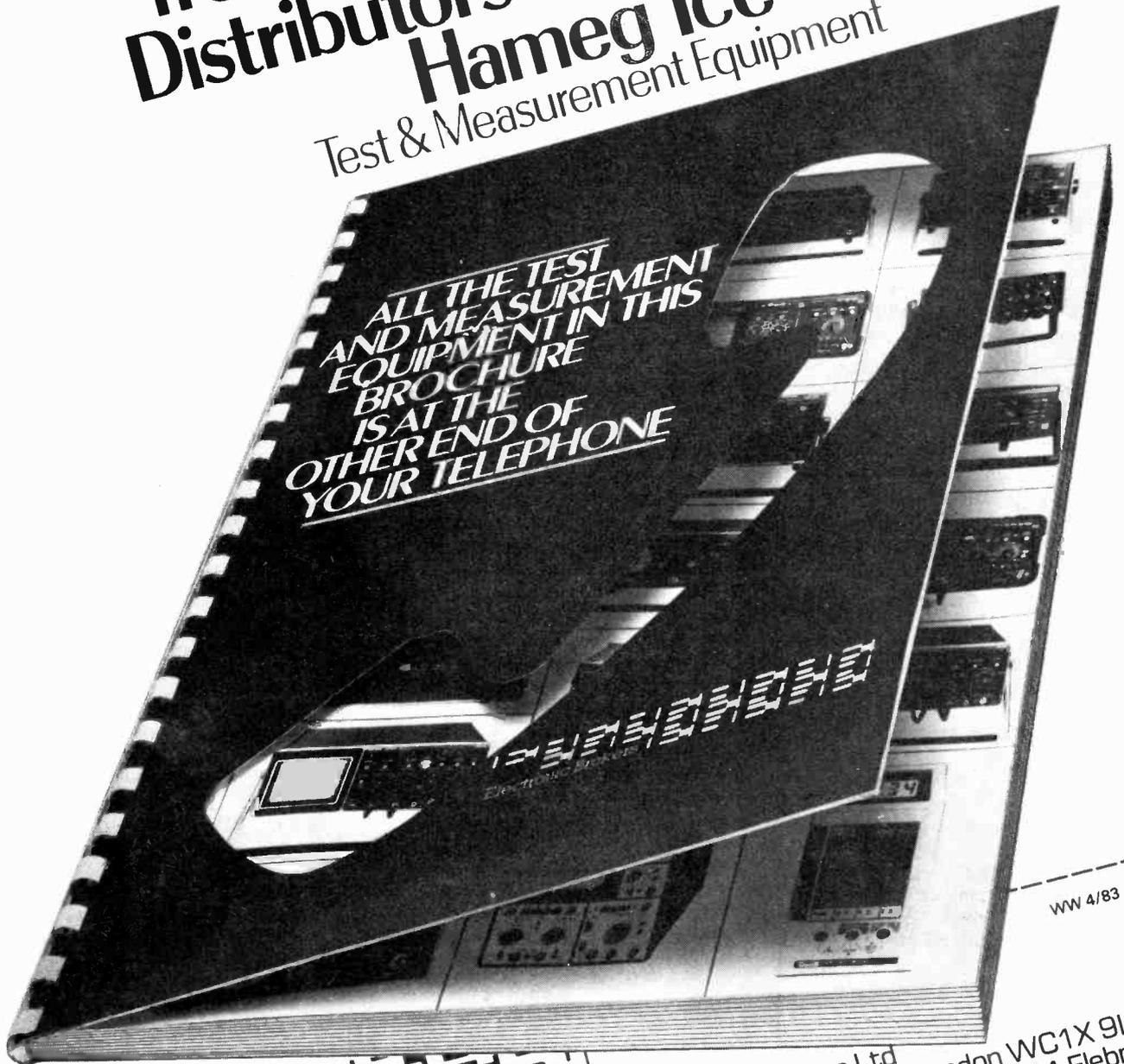

WW 4/83

Electronic Brokers
Electronic Brokers Ltd, main distributors of
Philips, Fluke, Hameg and ICE have just published a
full colour catalogue containing illustrations, full
technical specifications and prices on a wide range
of electronic test and measurement equipment —
all of which is ex-stock and available for immediate
delivery! Electronic Brokers new catalogue is an
absolute must for all engineers, designers
and buyers. Send off the coupon
for your FREE copy
now.

To: Electronic Brokers Ltd
61/65 Kings Cross Rd London WC1X 9LN
Tel: 01-833 1166 Telex: 298684 Elebro G
Please send me the new Test
& Measurement Equipment catalogue


Name _____
Company _____
Position _____
Address _____
Tel _____

Middle East Wire & Wireless Ltd.

TILEMAN HOUSE, 131 UPPER RICHMOND ROAD, PUTNEY, LONDON SW15. TEL: 785 6422, TELEX: 261768 MEWIRE G.

*FULL RANGE OF VHF/UHF RADIOTELEPHONES
BASE/MOBILE/HAND-HELD AND MARINE RADIOTELEPHONES*

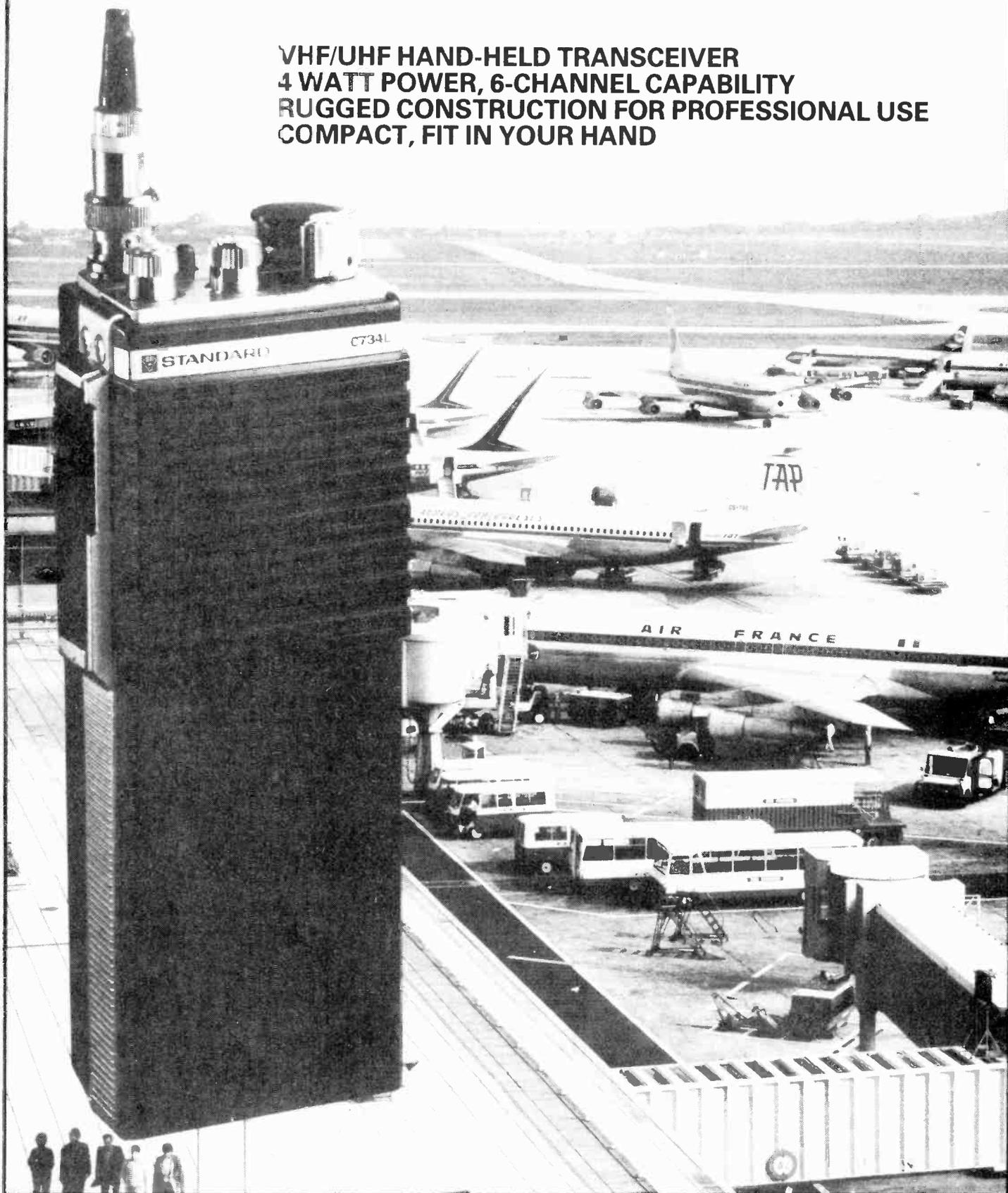**VHF/UHF HAND-HELD TRANSCEIVER
4 WATT POWER, 6-CHANNEL CAPABILITY
RUGGED CONSTRUCTION FOR PROFESSIONAL USE
COMPACT, FIT IN YOUR HAND**




WW - 080 FOR FURTHER DETAILS

Three-terminal superconductor

A superconducting device that operates in a similar way to a high-speed switching transistor but in a much smaller space and at 1/100 of the power was experimentally demonstrated at the IBM Thomas J. Watson Research Centre, New York, in January. Dubbed the quiteron, the invention is the first device to make use of the non-equilibrium superconductivity phenomenon known as heavy quasi-particle injection tunneling. It is also the first device of its kind that can both amplify and switch, giving it the potential for applications in digital and analogue circuits.

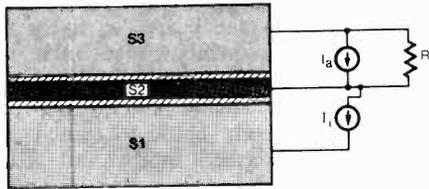Still in the experimental stage, the quiteron consists of two tunnel junctions formed by three thin films of superconducting material separated by two thinner films of insulating material. Electrical energy through one tunnel junction drives the central conducting layer into a non-




Superconductor layer S_2 is driven into a non-equilibrium state by I_1 , resulting in a drastic modification of acceptor current I_a .

equilibrium state and the second junction represents the central conducting layer's state.


Switching speeds of less than 300ps and small and large-signal gains of ten and three respectively are not astounding but taking into account projections that the device could be scaled down to lateral di-

mensions of $0.1\mu\text{m}$ with a power consumption of 1/100 that of current high-speed semiconductors, the quiteron could represent a breakthrough. Non-latching operation and insensitivity to stray magnetic fields are inherent.

A short-term strong point of quiterons – provided that they can be economically manufactured – is that they can be used to form the equivalent of a current v.l.s.i. circuit since they have three terminals and invert the input signal. Superconducting devices such as the two-terminal Josephson junction might require an i.c. technology that has to be developed from the ground up. The quiteron was described at the Applied Superconductivity Conference held at Knoxville, Tennessee, in December of 1982. Authors of the paper were S. Faris, S. I. Raider, W. J. Gallagher and R. E. Drake.

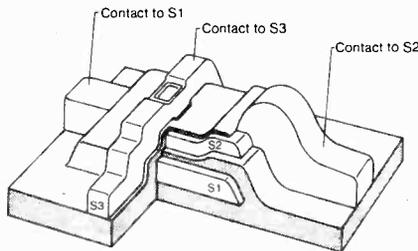

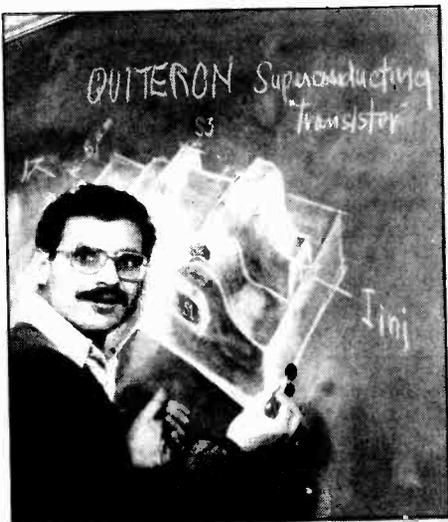Alternating layers of superconducting (S) and insulating materials form a device with characteristics similar to those of a high-speed semiconductor transistor but based on entirely different principles.



Inventor of the superconducting 'transistor', Sadeg Faris, holding a wafer containing experimental samples (look for a full stop).

Another million for Sinclair

Sinclair Research, said to be worth £136m, recently declared itself as the first company in the world to sell a million home computers. Excluding 600 000 computers manufactured under licence by Timex in the USA, this figure has been reached in three years and the company says that this may only be the beginning since even Britain – with more computers per head than any country in the world – has only one computer for each 20 homes.

Whether this optimism is justified remains to be seen. A report issued by Mintel claims that by the end of 1985, 10% of British households will have a home computer. Virtually every month sees the

introduction of a new home computer and the situation is now far more volatile than it was when Sinclair's ZX80 was introduced in 1980. But the Henry Ford of the home computer world is reported to be selling off around £13m of his industry, part of which will help finance a personal interest – an electric car.

● Following a decline in watch sales and the loss of a deal involving Nimslo 3D cameras, the future of the Timex plant in Dundee where the Sinclair Spectrum is manufactured is in doubt. Timex intend to move work in Dundee to France, with a consequent loss of jobs in Scotland. The European Communities Commission issued a statement saying that it plans to investigate French government grants to the Timex company in Besancon.

Computer data via satellite – a demonstration

Project universe – devised by the Government, universities and industry to demonstrate the viability of high-speed communication between computers by satellite – received its inauguration on 22 February at Info 83. Combining ground-based Cambridge rings and other types of local-area network with OTS satellite links, the project involves the use of six UK Earth stations operating at above 10GHz to send and receive data between remote computers at 1Mb/s.

Each computer can communicate with other computers through the local-area

network, or with remote computers through the satellite link, at a rate 100 times faster than is possible using current telephone lines. The system is likely to run for two years, when OTS is expected to cease functioning. The six Earth-station sites are at the Universities of Cambridge and Loughborough, University College London, the Marconi Research Centre (Chelmsford), Essex, BT's Martlesham Heath, Suffolk and at SERC's Rutherford Appleton Laboratory in Chilton. Funders of the operation are BT, DoI, GEC-Marconi Research, SERC and Logica.

Proposals for non-ionizing radiation limits

New UK limits for exposure to e.l.f., r.f. and microwave radiation are proposed in a consultative document from the National Radiological Protection Board. Written in response to a request from the Health and Safety Executive for advice on non-ionizing radiation, the publication proposes a mean specific energy absorption rate in the whole body of 0.4W kg^{-1} for microwave and r.f. radiation. The current UK limit of 1W kg^{-1} , recommended by the Home Office and Medical Research Council, has stood for around 20 years and presumably the Health and Safety Executive will use the document in its final form as the basis for new regulations.

Hand-held radio transmitters, intruder alarms and proximity devices emitting less than 7W "may be regarded as harmless" says the board, but they should be designed so that they cannot deliver more than 4W kg^{-1} to the eye for long periods. R.f. and microwave hazards to people with pacemakers are unlikely provided that the limits shown in the table are observed. "Higher levels of exposure may cause some types of pacemaker to revert to a 'fixed' mode of operation" say the board. People with pacemakers working in power-line frequency fields greater than 2kVm^{-1} or in any field that is likely to exceed the limits in Table 2 should seek medical advice - some makes of pacemaker are affected more than others.

Estimating exposure hazards in the near field remains a problem. Here it is advised that "Under reactive near-field conditions, limits on power density are difficult to interpret and r.m.s. electric and magnetic field strength limits should be used. Until more information is available neither of these limits should be exceeded."

The Board suggests that for r.f. and microwaves, measurements of power density should be made with equipment capable of averaging values over a period of less than 1s and at less than 5cm from the radiation source. In periods of less than six minutes, the energy density to which a person is exposed should not exceed 360 times the prescribed power density levels. How to deal with moving antennas and mixed frequencies are outlined and the board advises that any exposure producing a sensation of warmth or auditory sensation such as those that can result from intense pulses of microwave radiation should be avoided.


In circumstances where the mean specific energy absorption rate in the whole body does not exceed 0.4W kg^{-1} and a peak of 4W kg^{-1} in a volume smaller than 1cm^3 averaged over less than six minutes, exposures to higher power densities

or field strengths are permissible. "This relaxation" says the board "is likely to apply in the frequency range 3kHz to 300MHz under near or restricted field conditions, but the incident power density on any part of the body should not exceed ten times the prescribed limits, and field strengths should not exceed 3.16 times these values."

Exposure to power-frequency fields (50Hz) of less than 10kV m^{-1} is regarded by the board to be acceptable and exposure to fields of up to 30kV m^{-1} is considered unlikely to be harmful. "Apart from the 50Hz power frequency" says the board "there are very few applications in the e.l.f. range and there is little information

that can be used as a basis for limiting exposure."

According to the foreword, "In general, the Board bases its advice on a scientific consensus of opinion about established facts. In the case of the biological effects of non-ionizing electromagnetic radiations many observations that might appear significant are proving difficult to confirm." Some of these observations are argued summarily in the document and some are listed as references. Of course persons seriously considering offering comments on the document will also do their own research. The Board invites comments on the proposals before 1 July 1983, but due to "scientific uncertainties", it intends to keep the position under review. Copies of Proposals for the Health Protection of Workers and Members of the Public against the Dangers of Extra-Low Frequency, Radiofrequency and Microwave Radiations: A Consultative Document are available from HMSO for £2.

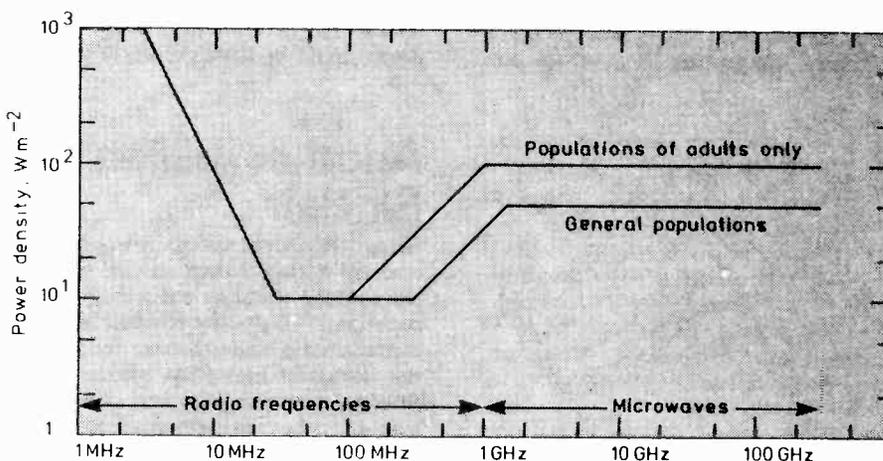


Permissible limits for continuous exposure to radio frequency and microwave radiations as proposed by the NRPB. For "general populations", levels are almost identical to those of the recently approved America National Standards Institute safety guidelines (C9). The curve dips at between 30 and 300MHz because of body resonances.

Proposed limits for continuous exposure to r.f. and microwaves for adults (top) and the general population including children (bottom).

Frequency range (Hz)	Power density W m^{-2}	R.m.s. electric field strength V m^{-1}	R.m.s. magnetic field strength A m^{-1}
3k-3M	—	600	—
3M-30M	$9000/f^2$	$1800/f$	$5/f$
30M-100M	10	60	0.16
300M-1.5G	$f/30$	$3.5\sqrt{f}$	$9.4 \cdot 10^{-3}\sqrt{f}$
1.5G-300G	50	140	0.36

Frequency range (Hz)	Power density W m^{-2}	R.m.s. electric field strength V m^{-1}	R.m.s. magnetic field strength A m^{-1}
3k-3M	—	600	—
3M-30M	$9000/f^2$	$1800/f$	$5/f$
30M-100M	10	60	0.16
100M-1G	$f/10$	$6\sqrt{f}$	$0.016\sqrt{f}$
1G-300G	100	200	0.50

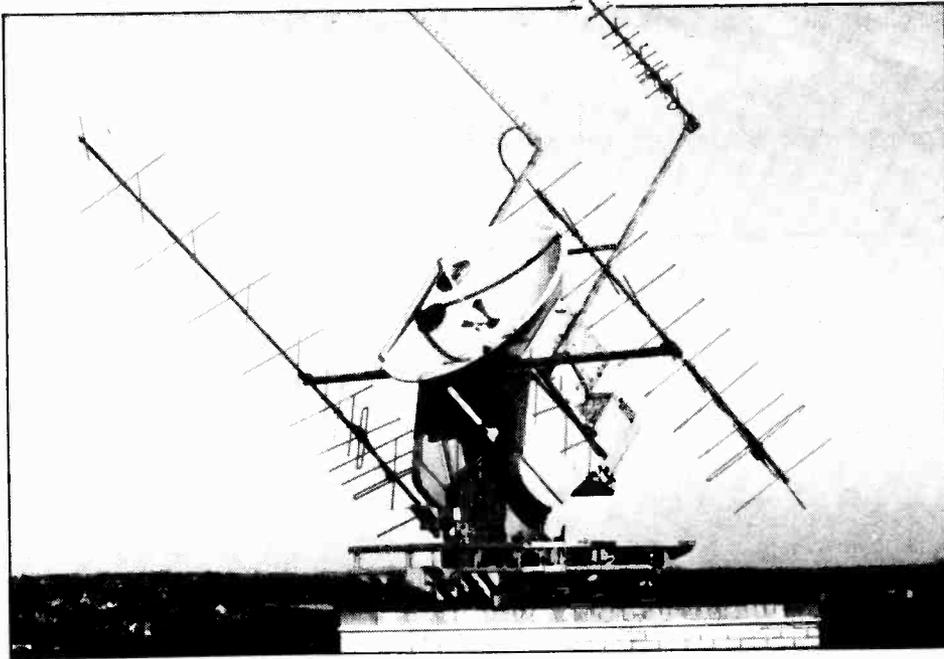

A voice from above

The digital speech synthesizer aboard Uosat is now fully operational and the project team expect to get long-awaited pictures from the spacecraft c.c.d. camera during March. The speech synthesizer, the first device of its kind to have been used in space, is a National Semiconductor Digitaltalker. Operating under the control of Uosats primary computer, the synthesizer has been carrying operational telemetry information and experimental data. With the help of the published calibration equations, the strings of spoken figures from Uosat can be decoded to give (for example) the amount of solar particle radiation, the current being supplied by the solar cells, or the temperature in the spacecrafts batteries. The project team hope that the availability of data in this readily accessible format will help to stimulate interest in space science among schools and colleges as well as individual amateurs.

Speech transmissions were at first being made at weekends using Uosats general data beacon on 144.825MHz. Three-minute periods of speech could be heard alternating with data transmissions and a bulletin of satellite news in teleprinter codes. The beacon should be receivable anywhere on unmodified v.h.f. amateur radio equipment with no more than a fixed pair of crossed dipoles. On some passes even a hand-held v.h.f. receiver may be adequate, according to the Surrey team. The other significant transmitter, the engineering data beacon on 435.025MHz, can also carry speech, but a much more sensitive receiving installation is needed to pick it up.

Other systems aboard Uosat now in operation include the microwave beacons on 2.401 and 10.47GHz, intended for propagation experiments when the

spacecraft is finally stabilized. This was expected to take place in early March, much later than originally intended, but a five-month gap in the programme occurred last year when the ground-station at Guildford lost control of the satellite (News, *Wireless World*, November 1982).

For attitude control and stabilization, Uosat has another novel device in the spacecraft. The magnetorquer is a coil which, when pulsed electrically, makes the craft swing like a compass needle to align with the Earth's magnetic field. Having attained the correct attitude, Uosat can fix it by extending a boom that acts as a pendulum to ensure that the base of the spacecraft always points towards Earth. At this stage, the project team plan to switch on some of their remaining experiments, which include four h.f. beacons, a magnetometer and the c.c.d. television camera.

Uosat's orbit passes over the poles, and in Britain it is above the horizon three or four times each afternoon and early morning at 96 minute intervals for periods of up to 12 minutes. A recorded bulletin gives up-to-date information about the satellite, including current orbital data, is available by telephone from the University 0483 61202.

Government backs AMPS

An 'advanced' version of the American AMPS cellular-radio system is given the Government's seal of approval. In answer to a Parliamentary question, Mr Kenneth Baker MP, Minister for Information Technology, said "It is with world markets in mind that the Government decided to endorse the system choice made by BT, Racal Millicom and Sactel and the development of an advanced version of the AMPS system to be known as Total Access Communication System (TACS)."

Racal Millicom put forward a technical description of an improved version of AMPS in their successful bid to be chosen as providers of the second national cellular radio network (see News, February). The system is used in the US and therefore classed as a known quantity, unlike its main contender MATS-E which seems to be technically superior. BT say that there is little difference between the systems evaluated and that they are delighted with the decision. TACS has the advantage that it will allow cellular radio to get off the ground quickly.

In brief

Finland plans to have a two-way cable tv system operational by early 1985. Scandinavia's largest tv manufacturer Salora announced that they are to supply a two-way pay tv system, including the head-end electronics and set-top decoders, for a network expected to serve about 22 000 homes in Tampere city. The deal to supply equipment for the coaxial network is worth

Wolverhampton Polytechnic has chosen equipment computer graphics equipment conforming to Canada's Telidon standard to help students become familiar with high-resolution computer graphics and viewdata. In doing so, it has become the first UK polytechnic or university to install equipment of this kind. Their system is being used to create animated graphics, 35mm slides, overhead projection films and video-tape material. Information for an in-house viewdata service is also being produced on the system.

Change of company name

The name of our parent company has been changed from IPC Business Press Ltd to Business Press International Ltd. This change has been made, say our proprietors, to reflect the wide range of markets covered by the 100 publications of the company, and to identify its position as the world leader of business publishing.


A digital tape clock

An electronic replacement for the mechanical counters used in many tape recorders.

The lack of precision of ordinary mechanical tape-counters and a need for something more than numbers relating to locations on the tape were among the motives behind the present design. It is basically a digital clock measuring tape running-time in minutes and seconds. Although it was devised for a ReVox A77, it could be used with almost any reel-to-reel tape recorder, with few modifications. The accuracy of the counter is close to one part per thousand, measured on a 10½ inch reel with a 3600ft tape. This means a deviation of only six seconds from one end of the tape to the other at 19.05cm/s.

Two optical sensors are used in the unit. One measures the length of tape passing and the other directs the counters to count up or down according to whether the tape is moving forwards or rewinding. A third sensor may be added to detect clear leader for an automatic reset and start of the clock.

by Per C. Andersen

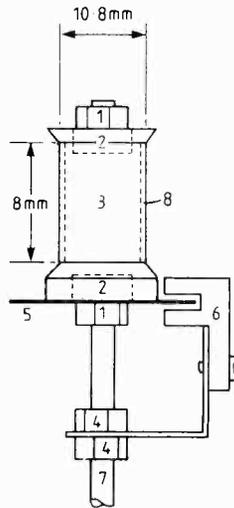

- 1 Self-locking nut
- 2 Ball bearing
- 3 Brass roller
- 4 Nut, 3mm
- 5 Timing disc (Fig. 2)
- 6 Optocoupler
- 7 Screw, 3mm
- 8 Rubber coating


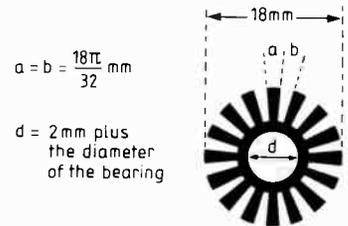
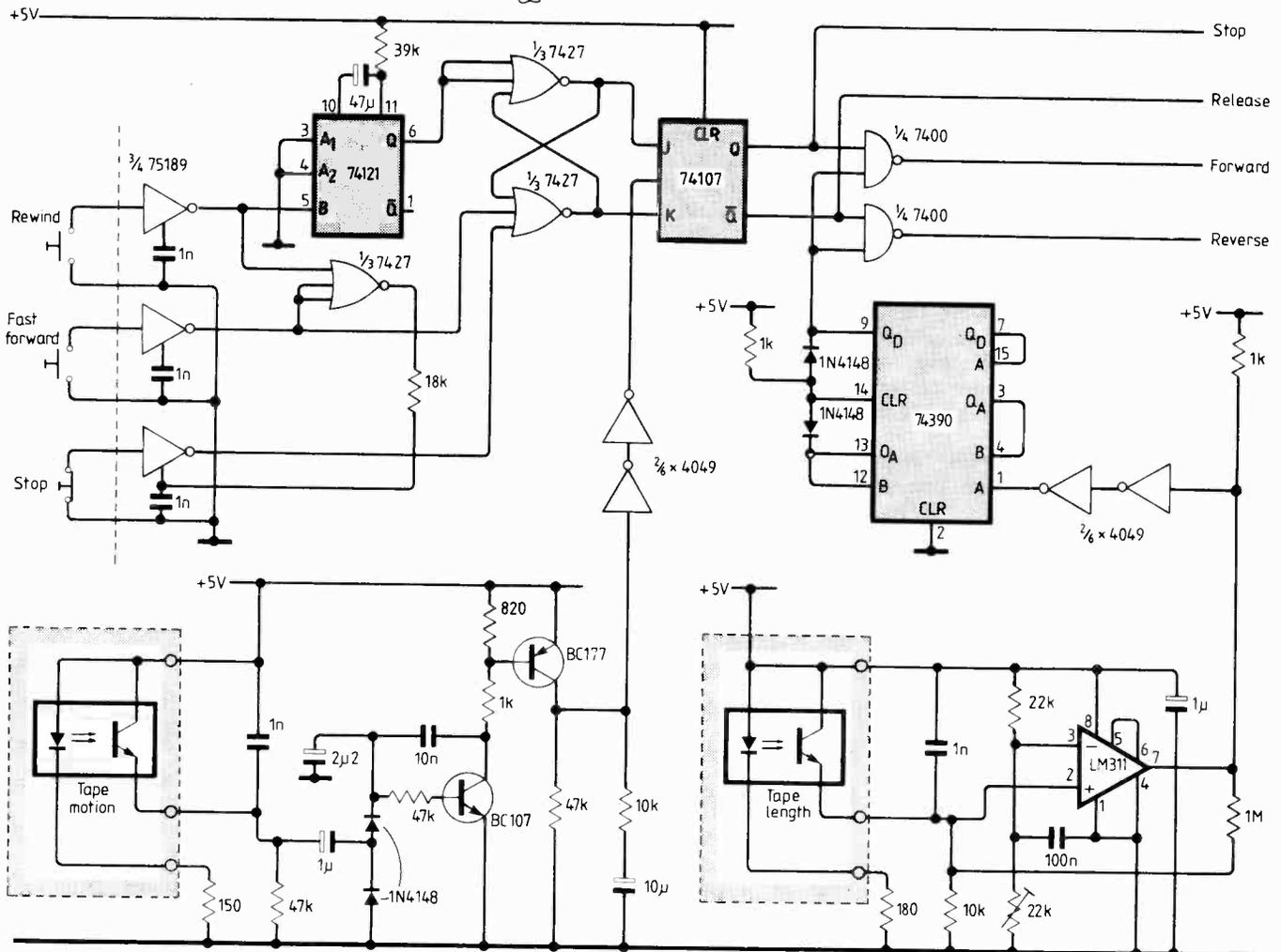


Fig. 2. Timing disc for length-of-tape transducer.

Fig. 1. The length-of-tape transducer.

Fig. 3. Method of detecting tape motion.

Not to scale

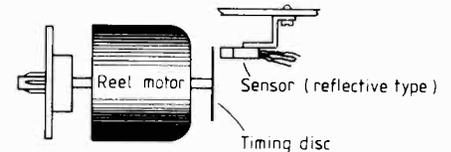

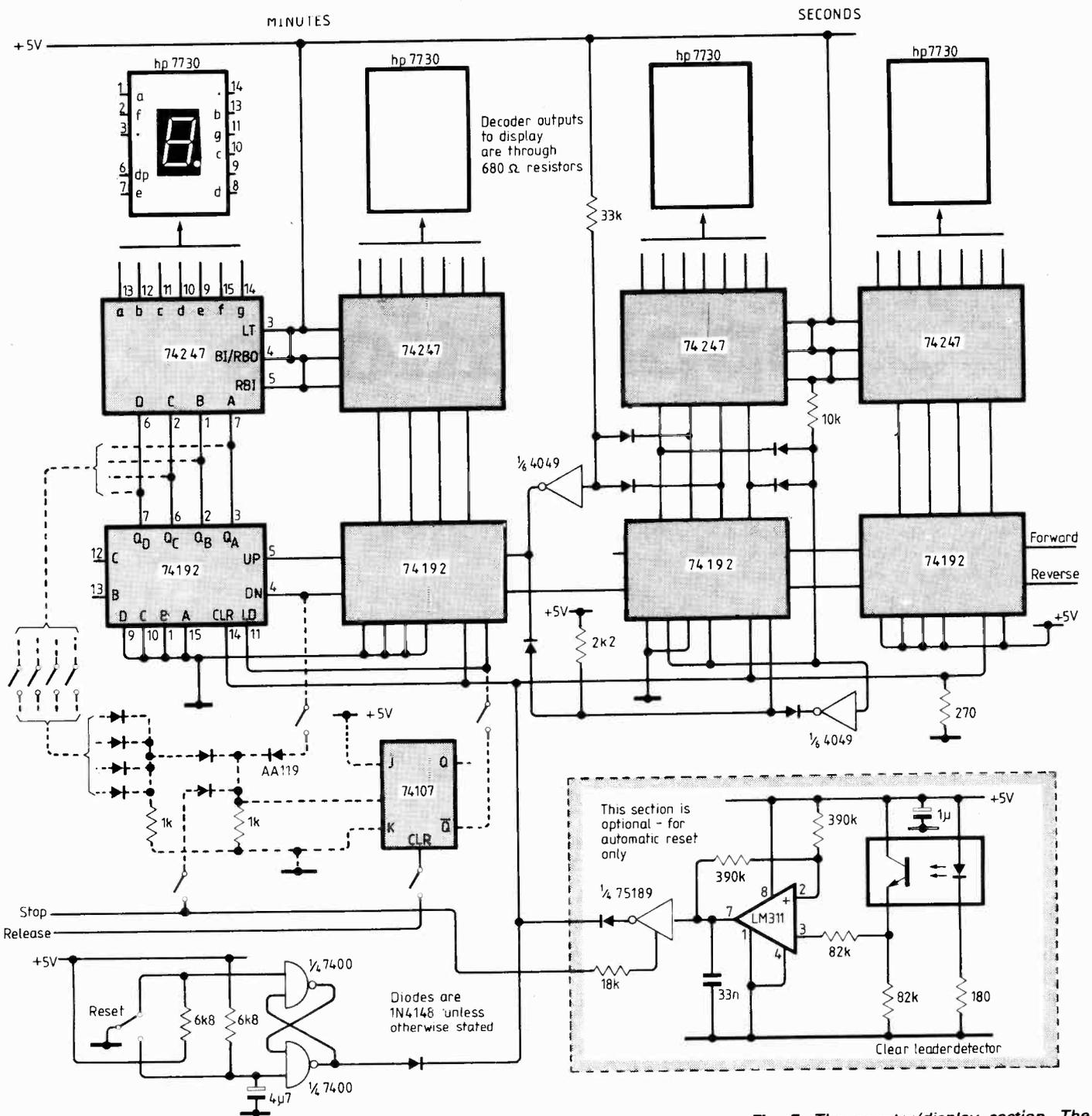


Fig. 7. The counter/display section. The dotted connections may be included to prevent count-downs below zero when rewinding.

The length-of-tape transducer is assembled from three parts: a rubber-coated brass roller with ball-bearings, a plastics timing-disc and the optical sensor itself. The physical dimensions are shown in Fig. 1. The brass roller was turned to a circumference of 32mm and then coated with rubber to a circumference of 33.9mm. The rubber is necessary to ensure good tape contact and to prevent slipping and skewing. If liquid rubber is not available, strips of a suitable adhesive tape could be used; but care should be taken that the ends do not overlap and that the adhesive is strong enough to keep the ends from peeling after

continued on page 62

◀ **Fig. 6.** This circuitry links the optical tape sensors and the function switches of the tape recorder with the counter/display section shown in Fig. 7.

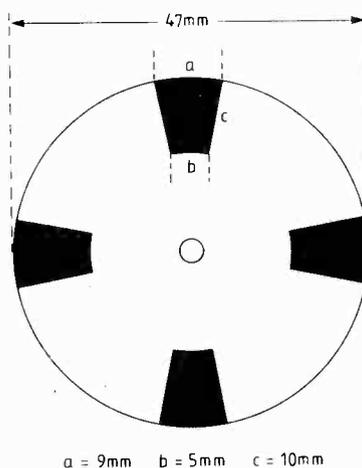


Fig. 4. Timing disc for tape motion sensor.

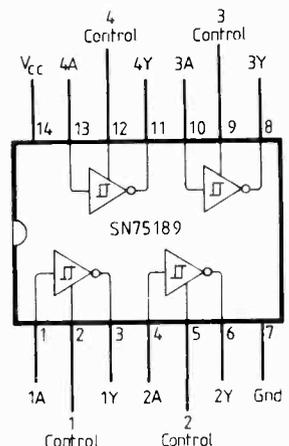


Fig. 5. Pin connections for the 75189 (top view).

- 1 Theories and miracles
- 2 Electromagnetic analogy
- 3 Impact of the photon
- 4 A more realistic duality?
- 5 Quantization and quantization
- 6 Waves of improbability
- 7 Limitation of indeterminacy
- 8 Haziness and its applications
- 9 State of physics today

Haziness and its applications

How belief in the wave theory of matter and the indeterminacy of Nature – coupled with a third (gross) philosophical error, the wilful confusion of measurement with fact – so undermined the discipline of experimental and logical thought that the chaos in modern physics became complete.

It is often said that the indeterminacy of a physical measurement arises as a natural consequence of the postulated wave-like properties of matter itself and that it affords proof of those properties, but that is not so. Heisenberg himself was ambivalent about it: his preferred *derivation* of the Indeterminacy Principle was on wave-theory lines that took an electron to be a “wave packet” of de Broglie-type matter waves, whereas his arguments in *demonstration* took a light quantum to be a wave system but envisaged an electron to be a particle. In fact it is not necessary even for the light to consist of waves, because the Compton effect (which provided the basis of Heisenberg’s own illustrations of the Principle) does not require waves for its physical explanation, as already discussed. The indeterminacy does not follow from any postulated wave-like properties of matter or light, but simply from the essential granularity or “quantization” (type one) of microphysical Nature – that is, from the fact that one’s most fundamental measuring instruments, electrons and photons, behave like discrete, indivisible, self-consistent *particles*, of small but finite mass.

The wave theory actually entered the philosophical lists by means of a characteristically specious argument in the following manner. If, despite all the contrary evidence, an electron were to consist of a wave packet of matter waves, then the shape of that wave packet might perhaps be arbitrary. (After all, nobody has ever seen an electron). Axiomatically a wave packet is distributed in space, so that one cannot really define its position – that is, where its exact centre is – especially if it is a long wave-packet. On the other hand if it is a short one its position will be better defined, but in the nature of things it can then contain only very few waves. This means that its wavelength must be ill-defined, and according to the duality doctrine an electron’s apparent wavelength as

a wave system is to be associated inversely with its mechanical momentum as a particle. (The premise I refer to here is $p=h/\lambda$). So this concept seemed to fit Heisenberg’s indeterminacy formula like a glove: if an electron were a wave packet, then its position and momentum would be mutually indeterminate for natural reasons. The indeterminacy would lie not with our measurements but within the structure of the electron itself. In that case,

by W. A. Scott Murray
B.Sc., Ph.D.

note well, our human failure to make precise predictions of its behaviour would arise simply because the electron’s behaviour was itself imprecise or “indeterminate”.

The attractiveness of this idea lies in the way in which it places the reason for our difficulties so firmly elsewhere; if Nature herself is indeterminate, how shall the physicists be blamed? It would provide a balm for nettled professional pride and a sop to human vanity if it were true, but of course it isn’t. We cannot allow that an electron must become long and thin or short and fat according to the way in which we may choose to perform an experiment; that proposal conflicts with the general and consistent experimental evidence that electrons are indistinguishable. Nor do electrons dissipate like wave packets, any more than photons do. And between ourselves we have already rejected the doctrine of the indeterminacy of Nature on the logical ground of the unlimited precision of retrospective measurement. Appealing though it may have seemed to some people, that scheme just isn’t on.

Nevertheless the concept of an electron as a wave packet persists. It leads directly

to the established “doctrine of haziness” – the erroneous doctrine that fundamental physical particles are essentially and necessarily structureless, amorphous, and of indeterminate size and shape. The philosophical error which allowed that doctrine to flourish was the blandly false identification of the true, physical extent of the structure of a particle with the vague, probabilistic boundaries of *our knowledge* of its position. The error was made possible by the continued association of the statistics of position measurement with the mythical probability waves of the wave theory of matter – the mistake that has already been exposed in the “Reduction of the wave packet”.

How can I be so sure that the identification was wrong? I offer two proofs, both independent of wave theory. One is that the form of a particle is a physical matter while our knowledge of its location is a metaphysical matter, and as before we may not identify chalk with cheese. The other is that *the imprecision of a measurement* (Δx) is not to be identified with *imprecision in the quantity measured* (δx) – more especially when, as in this case, the measuring instrument is granular or “quantized” and in that sense imperfect. It is like claiming that a precision-ground ball bearing is non-spherical and faulty because one can’t measure its diameter very accurately with a domestic rule!

That last misidentification (of measurement with fact, $\Delta x = \delta x$) is such an obvious error that it should not be accepted from a sixth-form student; yet here we have found apparently-responsible physicists and teachers of physics not only perpetrating it, but *perpetuating* it for fifty years! From their contemporary writings there are grounds for suspecting that it, and the corresponding misidentifications in the case of momentum (Δp), energy (ΔE), and time (Δt), may have been made wilfully by the Copenhagen School in the 1930s, rather than through ignorance of

the philosophical issues involved. This is not to impute to those concerned any motives other than the highest: they were genuinely seekers after fundamental truth. But it does seem that they may have been carried away by the sheer excitement of the new ideas that were developing in natural philosophy, and entranced by the mysticism into which these ideas were so inexorably leading them. They *wanted* the world of electrons and photons to be mystical and mysterious. Their picture of that world could be summed up fairly accurately as follows:

- Everything in microphysics is indeterminate (or hazy).
- Everything in microphysics is "quantized" (or precise).

Unless care is taken over the definition of terms these two statements are mutually contradictory. (An example of their conflict was developed in the, *WW* June 1982 article, page 81). I have argued that the first is untrue and I could argue similarly about the second, but instead I will tell a fairy story and leave the judgement to you.

Once upon a time a young man was measuring the speeds at which beta particle (fast-moving electrons) were being ejected from radioactive atomic nuclei. He found that their energies varied smoothly over at least a ten-to-one range, which surprised him because he had expected to find instead a series of sharp energy values like a line spectrum in light. On the other hand, gamma rays (photons) that left the nuclei at approximately the same time did show a line spectrum, which was interpreted as evidence that the internal structure of the nucleus is "quantized" (type two) into definite energy levels – like a Rutherford/Bohr planetary atom, only more so.

I think everybody would agree that atomic nuclei are quantized (type one), in that every nucleus is constructed out of a definite number of discrete particles, protons and neutrons, that can be recognised in the free state by their consistent properties and behaviour. But according to the new ideas the *mechanics* of everything small is also quantized (type two), and because the atomic nucleus is very much smaller than the complete atom, *a fortiori* should the mechanical energy and momentum within the nucleus be quantized. Yet the beta radiation, which is associated with the radioactive decay of one neutron into a proton inside the nucleus, apparently is not quantized. It was an article of the new faith that it should be quantized . . . "Therefore", said the quantum theorists, "the conservation of energy must have failed (Niels Bohr); or, alternatively, the experimental evidence of the beta decay must be wrong".

Wolfgang Pauli saved the day, by postulating the existence of a completely unexpected *neutrino* or "small neutral particle" which had about the same mass as an electron but no electric charge. Such a particle, he suggested, would not show up in any ordinary particle counter or photograph. So: if one neutrino were to be emitted along with every radioactive beta electron, nobody would ever be able to

detect the fact; but the invisible neutrino would carry away energy too, so that it and the beta electron, between them, could possess the quantized line spectrum of energy that the theory demanded although the visible beta electron did not. (The failure to quantize the sharing of this energy between the neutrino and the beta electron in fixed proportions was not explained).

Now if you feel this to be a somewhat implausible, *ad hoc* suggestion, designed to make the experimental facts agree with the theory and not far removed from a confidence trick, be sure I share your suspicions. The question before us is: Do we believe in neutrinos? We would not be alone if we didn't. Neutrinos are essential to the modern quantum theory, however, and their existence is assumed as a matter of course when describing nuclear reactions, yet not even their owners seem to be very sure about them. When first invented by Pauli they had about the same mass as an electron (so as to share the missing energy equitably, on average); then suddenly it was proved that they could have no rest mass, but must be like some kind of non-radiant, undetectable photon. However, to make up for that they must be spinning – "but not *mechanically*, of course, since there is no structure there to spin". More recently it has been declared that they probably do have rest mass but very, very little (actual amount unspecified), and that there must be at least four different kinds of them. It does not add up to a very convincing story.

From the theorists' viewpoint the delightful thing about neutrinos is that they are virtually undetectable. Being so light, and electrically neutral, it is said that most of them fly right through the planet Earth, touching neither nucleus nor electron and leaving no trace of their passage. (There is another logical inconsistency here too, but we needn't labour every one!). Very occasionally a particle counter registers inside a 12ft-thick steel box near the target area of the big CERN accelerator at Geneva, and this effect, like some others, is attributed to a neutrino collision because "it couldn't be anything else". Then one day the astrophysicists discovered that, according to current theory, the Sun should be pouring out neutrinos at a calculable, fabulous rate; and accordingly an

enormous neutrino detector was built in the United States especially to look for them, deep below ground in a diamond mine where unidentified particles would be unlikely to be mistaken for neutrinos and confuse the results.

That experiment was reported in 1976. It detected fewer than one-tenth of the neutrinos of solar origin that it was expected to detect, and maybe none; there is no assurance that the very few nuclear reactions that it did detect were actually due to neutrinos. The astrophysicists have been sent away to do all their sums again. But why should the poor *astro*-physicists take the blame for this negative result? What if Pauli's adventurous speculation should have been wrong, and his postulated neutrino never existed after all? To the theorists such a thought really is unthinkable: for if, after weighing the evidence, we were to determine that on balance of probabilities we did not believe in neutrinos, then we would be suggesting that the atomic nucleus might not be "quantized" (into discrete energy levels, type two). And that thought in its turn would strike at the roots of every modern theory about the physics of elementary particles.

Now I said at the beginning that little was to be gained by attacking established theories and thereby triggering all their devotees into uncompromising battle in their defence. That line is, in modern parlance, "counter-productive". It is much better to examine miracles – physical phenomena that we do not in truth understand, although our various theories may be willing to offer glib but scarcely plausible "explanations" of them at the drop of a hat. Surveying modern physics, it is in the territory of the elementary particles that miracles are thickest on the ground. Vast sums of money and immense efforts of mind have been spent on particle physics over the past fifty years. Each new atom smasher, when eventually it is made to run, generates a host of new problems *but solves no old ones*. There has been no credible outcome from all this outlay. Instead, we find all manner of hypothetical entities cluttering the contemporary letterpress – "as charmed quarks, evincing isospin", for example – concepts which are supported by no physical evidence, untested and *in principle* untestable experimentally. (Pau-

Indeterminacy and elementary particles

The influence of the wave theory was paramount in the arguments which led to the denial of causality. The most obvious example of this – also historically the first – was the doctrine that an electron, as an elementary physical particle, was amorphous and structureless because it was "really" a wave-packet of de Broglie waves. The logical error at the centre of this is identifiable as such without difficulty. Thereafter the technique of bending experimental results to fit in with pre-conceived theoretical notions became established, with the general acceptance of the *ad*

hoc postulate of the neutrino. The wilful misinterpretation of the meaning of the Indeterminacy Principle then heralded a final rejection of physical discipline, leading to the invention of "virtual processes" which violate the conservation laws whenever convenient, as exemplified by the "prediction" of the meson. Having got away to such an inauspicious start the study of elementary particles had little chance of recovery; the rather obvious failure of theoretical physics in this area, due to its domination by "quantum" metaphysics and mysticism, is scarcely surprising.

li's neutrino gave only a first glimpse into this modern fantasy world.) Particle physics today is in an almost impenetrable mess, infinitely more confused and less coherent now than it was when Chadwick discovered the neutron in 1932. I wonder why?

It seems to me possible that the lamentable state of this area of physics may reflect, and indeed be the consequence of, its domination by the metaphysical ideas of the "quantum theory" of the Copenhagen School. A quotation from a popular modern textbook (no names, no pack-drill!) may provide a convenient example for analysis:-

"Because of the Heisenberg uncertainty principle in quantum mechanics, a particle cannot have a definite position in space-time and a definite energy and momentum. The more localised the particle is in space-time, the larger the uncertainty in its energy and momentum. So that, *virtual processes which do not conserve energy and momentum can occur over very small intervals in space and time by virtue of the Heisenberg uncertainty principle*, provided they are followed by processes which ensure conservation of energy and momentum for the whole process."
(My italics)

There, good friends, you have it all. The student is being told, *ex cathedra*, that it is legitimate for him to postulate any "virtual process" in his theories (by which is invariably meant a process that violates the conservation laws) *provided he is not found out!* Perhaps, philosophically, we have asked for this: we live in an indisciplined, lawless age, where logical consistency and honesty are no longer demanded. The fundamental error in the passage quoted, which is no misprint but a faithful transcription of currently-established doctrine, lies in the statement that a particle "cannot have" a definite position in space-time and a definite energy and momentum; here is the false doctrine of the Indeterminacy of

Nature, rather than the legitimate indeterminacy of *measurement*.

That the misinterpretation was deliberate is well evidenced. In 1935, by an *exact* application of the "virtual process" argument quoted above, Hideki Yukawa "predicted" the likely existence of a meson or *meson* (medium-sized particle) — a manifestation of nuclear binding energy which might appear externally in the guise of a discrete particle when an atomic nucleus was disrupted. The meson was duly discovered experimentally and its track photographed two years later, an obvious and brilliant success for the doctrine of haziness. Unfortunately some 35 different kinds of meson are now known (by count dated 1973), and the mechanism of the conservation-dodging "virtual process" as it was argued by Yukawa can reasonably account for only one of them.

The unexplained plurality of mesons represents only the tip of the iceberg. The total of recorded elementary particles exceeds 85 (1973 figure)*. I consider myself to be just as radical a thinker as the next man, not at all old-fashioned, and I am quite willing to believe that the 60 or more of the particles currently listed which have immeasurably short life-times — in the trade they are sometimes called "resonances" rather than particles, with good reason — are simply the undifferentiated, non-specific explosion debris of sub-nuclear disintegrations: isolated, fast-flying packages of energy which are of the wrong mass to form themselves into mechanically stable or partially-stable structures (\equiv "particles"), and which are *actually* dissipating, spreading out into space and effectively vanishing before our very eyes. (This would correspond to a loss of detectable energy from the local system, although the conservation law would not be violated in the universe as a whole). I

would not expect such ephemeral, neutrino-like things to be "quantized".

What of the remaining elementary particles, of at least 25 known species, whose lifetimes range from the 10^{-10} seconds or so of the principal baryons to the all-time stability of the proton and the electron? (Why are they stable? Why are all the others unstable?). The established dogma of today's "quantum theory" holds that it is improper to ask (or answer) questions about their structures, which can never be observed; but what about their masses, which are very accurately measurable? How, and why, are the masses — or internal energies — of these elementary particles, building-blocks of the physical world, related to each other? Current microphysical theory offers no answers to such fundamental questions, and has made only one memorable prediction (the "omega minus" particle, forecast by extrapolation). It invented a series of qualities for elementary particles which, it held, "must be" quantized plus/minus like spin and therefore "must be" conserved. One of these qualities it called parity. It did not even blush when the first honest experiments showed that parity was *not* conserved. Instead it went on to devise — via relativity theory, if you please! — yet another undetectable particle, a tachyon which *always* travels faster than light . . .

In view of the immense efforts that have been expended in its area, current microphysical theory would seem to have been something of a failure. "Microphysical entities are hazy", we are told by eminent men, "and one should not ask old-fashioned questions about them". Surely such haziness is more likely to lie in human minds than in fundamental physics?

* Over 200 now, ten years later. Is this progress?

continued from page 59



Mr Andersen, who lives in Denmark, works as a field engineer installing and repairing computer systems. He retains a keen interest in planning and constructing his own designs.

a while. At a tape speed of 19.05cm/s the roller will make 5.619 revolutions per second. The timing disc, which is mounted below the roller, has 16 slots (Fig. 2) and therefore produces an output frequency of $5.619 \times 16 = 89.912\text{Hz}$. This is counted down to 0.999Hz, which is near enough to 1Hz. The transducer was mounted in place of the tape tension arm.

The tape motion sensor is located underneath the right-hand reel motor (Fig. 3). Its timing disc and timing components (Fig. 4) are designed to output a pulse train when the machine is in the play mode and to supply a logic 'high' to the control circuits in the fast wind and rewind modes. It is important that the disc is made as accurately as possible and that the components are chosen appropriately: otherwise the circuit may not detect the exact moment when the tape stops moving, especially if the direction of tape travel is changed directly from one way to the other.

Interfacing the tape recorder function switches to the control logic is done by

using the quad line receiver SN75189, which is useful for this purpose because its inputs can withstand up to $\pm 30\text{V}$. Equivalent devices are DS1489 (National Semiconductor) and MC1489 (Motorola).

The counter-display section is conventional, except that it is capable of counting both up and down and that the minutes progress to 99 instead of 59. In the present design it was considered undesirable that the minutes counter should go below zero if a rewind beyond the initial starting point took place. Therefore the dotted circuitry was added to ensure that the minutes counter stops at zero when rewinding. In the prototype, this feature was made optional by inserting a diode switch pack. Reset is derived either from a manual switch or from an optional clear leader detector. The variable resistor is adjusted for a 50% duty-cycle at pin 7 of the LM311 during rewind.

The clock requires a stable power supply of 5V at 1A. Proper bypassing of the logic, especially the counters, will be necessary.

WW

Assembly language programming

Many microprocessors respond to over 100 machine-code instructions – the 6809 responds to 1464 – and remembering these instructions in hexadecimal form is for most impossible. Assembly-language memory aids used to overcome this programming difficulty are the subject of Bob Coates' second tutorial article.

Hexadecimal-form numbers discussed at the end of last month's article improve the legibility of binary codes used by the processor but illustrate machine code and not assembly language. The following example demonstrates the progression from machine code to assembly language.

- Load accumulator with data in hexadecimal address 40
- Add accumulator contents to data in address 41
- Store the result in address 42

Binary-form numbers used by the 6805 microprocessor to carry out this program are as follows.

```
10110110
01000000
10111011
01000001
10110111
01000010
```

This is the only number form that the processor can understand instructions but the binary instructions may be represented in hexadecimal form as follows.

B6 40 BB 41 B7 42

Hexadecimal numbers are easier to assimilate and make programming mistakes easier to spot. Instructions entered on the Picotutor keypad in hexadecimal form are converted to binary by part of the processor-eprom monitor program before they are stored in memory for subsequent use by the microprocessor. Hexadecimal-form numbers are not the ideal solution to the programming problem though; the 6805 has 205 instructions and the 6809 has 1464 and remembering these in hexadecimal form remains difficult to say the least.

Instruction-code mnemonics

As a memory aid, each instruction is assigned an abbreviation relating to the language familiar to the operator (in this case English). These assembly-language instruction names are called mnemonics and should in some way describe the function of the instruction. All manufacturers provide a set of mnemonics for their microprocessor instruction sets. There is nothing special about the mnemonics cho-

sen and one could invent one's own but it makes sense to adhere to a standardized set.

Usually the mnemonics chosen are obvious. For instance with the 6805 a load-accumulator instruction is represented by LDA and jump-to-subroutine is represented by JSR. Unfortunately some are not so obvious; with the 6800, transferring the contents of accumulator A to accumulator B is quite logically TAB but transferring the contents of accumulator A to the condition-code register is represented by TAP. With the Z80 microprocessor EXX

by R. F. Coates

meaning exchange alternate registers doesn't leave one much the wiser either.

Fortunately, 6805 mnemonics are fairly obvious and apply to equivalent instructions on all eight-bit microprocessors from Motorola which helps one apply experience gained with one microprocessor to another; in machine-code terms instructions used with processors in the range may vary but mnemonics used to represent them stay the same. Standard Zilog and Motorola mnemonics will be used in this series. Computer assemblers usually require a prefix or suffix to denote hexadecimal numbers; these symbols, usually a \$ prefix or an H suffix, will only be used where necessary.

Using 6805 mnemonics, the previous example is written in assembly language as

```
LDA 40
ADD 41
STA 42
```

with abbreviations LDA, ADD and STA representing load accumulator, add and store accumulator respectively. Like the hexadecimal-to-binary conversion performed by the Picotutor, translation between assembly-language mnemonic programs known as source code and hexadecimal machine-language programs known as object code is a task that can be performed by a microprocessor. Assembly-language programs are usually keyed directly into a microcomputer and

translated by an 'assembler' program but such translations are involved and outside the scope of Picotutor. Consequently, our source programs are translated manually using a conversion table.

Programming tables

Microprocessor manufacturers produce tables giving all the instruction mnemonics with their machine-code equivalents such as the ones shown for the 6805. These tables, essential for assembly-language programming, are usually included in microprocessor data sheets.

With mnemonics added, our simple program is now more understandable but is still not self explanatory. Comments added to explain the program flow will make its operation clear and ease reference to the program at a later date. To do this, a table is drawn with columns representing various statements or 'fields' or the instructions. Column headings from left to right are as follows.

Label field
Operation code or mnemonic field
Operand or address field
Comment field

Labels, like comments, are optional and are used to make the programs easier to read. They indicate points in the mnemonic source file such as the start of a subroutine which is jumped to from a different part of the program. This point will have to be specified in the machine-language object code as an address but as this address is not known before the program is assembled it is substituted by a label. The label indicating the start of the routine is also used in place of the address (in the address field) of the instruction that causes

Instruction tables for the 6805. Most ▶ register/memory instructions use two operands, one for the accumulator or index register and the other obtained from memory. Read-modify-write instructions read a memory location or register, modify or test its contents and send the modified value back to memory or the register. When certain conditions are met, branch instructions divert the program. Bit-manipulation instructions are described in the text and control instructions control the processor during program execution.

Register/memory instructions

Function	Mnem.	Addressing Modes												Boolean Operation	Condition Code										
		Immediate		Direct		Extended		Indexed (No Offset)		Indexed (8-Bit Offset)		Indexed (16-Bit Offset)			H	I	N	Z	C						
		Op	#	Op	#	Op	#	Op	#	Op	#	Op	#												
Load A from Memory	LDA	A6	2	2	B6	2	4	C6	3	5	F6	1	4	E6	2	5	D6	3	6	M → A	●	●	▲	▲	●
Load X from Memory	LDX	AE	2	2	BE	2	4	CE	3	5	FE	1	4	EE	2	5	DE	3	6	M → X	●	●	▲	▲	●
Store A in Memory	STA	—	—	—	B7	2	5	C7	3	6	F7	1	5	E7	2	6	D7	3	7	A → M	●	●	▲	▲	●
Store X in Memory	STX	—	—	—	BF	2	5	CF	3	6	FF	1	5	EF	2	6	DF	3	7	X → M	●	●	▲	▲	●
Add Memory to A	ADD	AB	2	2	BB	2	4	CB	3	5	FB	1	4	EB	2	5	DB	3	6	A + M → A	▲	●	▲	▲	▲
Add Memory and Carry to A	ADC	A9	2	2	B9	2	4	C9	3	5	F9	1	4	E9	2	5	D9	3	6	A + M + C → A	▲	●	▲	▲	▲
Subtract Memory	SUB	A0	2	2	B0	2	4	C0	3	5	F0	1	4	E0	2	5	D0	3	6	A - M → A	●	●	▲	▲	▲
Subtract Memory from A with Borrow	SBC	A2	2	2	B2	2	4	C2	3	5	F2	1	4	E2	2	5	D2	3	6	A - M - C → A	●	●	▲	▲	▲
AND Memory to A	AND	A4	2	2	B4	2	4	C4	3	5	F4	1	4	E4	2	5	D4	3	6	A • M → A	●	●	▲	▲	●
OR Memory with A	ORA	AA	2	2	BA	2	4	CA	3	5	FA	1	4	EA	2	5	DA	3	6	AVM → A	●	●	▲	▲	●
Exclusive OR Memory with A	EOR	A8	2	2	B8	2	4	C8	3	5	F8	1	4	E8	2	5	D8	3	6	A ⊕ M → A	●	●	▲	▲	●
Arithmetic Compare A with Memory	CMP	A1	2	2	B1	2	4	C1	3	5	F1	1	4	E1	2	5	D1	3	6	A - M, A → A, M → M	●	●	▲	▲	▲
Arithmetic Compare X with Memory	CPX	A3	2	2	B3	2	4	C3	3	5	F3	1	4	E3	2	5	D3	3	6	X - M, X → X, M → M	●	●	▲	▲	▲
Bit Test Memory with A (Logical Compare)	BIT	A5	2	2	B5	2	4	C5	3	5	F5	1	4	E5	2	5	D5	3	6	A • M	●	●	▲	▲	●
Jump Unconditional	JMP	—	—	—	BC	2	3	CC	3	4	FC	1	3	EC	2	4	DC	3	5	EA → PC	●	●	●	●	●
Jump to Subroutine	JSR	—	—	—	BD	2	7	CD	3	8	FD	1	7	ED	2	8	DD	3	9	PC → (SP), EA → PC	●	●	●	●	●

Read/modify/write instructions

Function	Mnem.	Addressing Modes												Boolean Operation	Condition Code							
		Inherent (A)		Inherent (X)		Direct		Indexed (No Offset)		Indexed (8-Bit Offset)		H	I		N	Z	C					
		Op	#	Op	#	Op	#	Op	#	Op	#											
Increment	INC	4C	1	4	5C	1	4	3C	2	6	7C	1	6	6C	2	7	A + 1 → A, X + 1 → X, M + 1 → M	●	●	▲	▲	●
Decrement	DEC	4A	1	4	5A	1	4	3A	2	6	7A	1	6	6A	2	7	A - 1 → A, X - 1 → X, M - 1 → M	●	●	▲	▲	●
Clear	CLR	4F	1	4	5F	1	4	3F	2	6	7F	1	6	6F	2	7	0 → A, 0 → X, 0 → M	●	●	▲	▲	●
Complement	COM	43	1	4	53	1	4	33	2	6	73	1	6	63	2	7	$\bar{A} \rightarrow A, \bar{X} \rightarrow X, \bar{M} \rightarrow M$	●	●	▲	▲	1
Negate (2's complement)	NEG	40	1	4	50	1	4	30	2	6	70	1	6	60	2	7	0 - A → A, 0 - X → X, 0 - M → M	●	●	▲	▲	▲
Rotate Left Thru Carry	ROL	49	1	4	59	1	4	39	2	6	79	1	6	69	2	7	$[C] \leftarrow [b7] \lll [b0] \leftarrow [C]$	●	●	▲	▲	▲
Rotate Right Thru Carry	ROR	46	1	4	56	1	4	36	2	6	76	1	6	66	2	7	$[C] \rightarrow [b7] \lll [b0] \rightarrow [C]$	●	●	▲	▲	▲
Logical Shift Left	LSL	48	1	4	58	1	4	38	2	6	78	1	6	68	2	7	$[C] \leftarrow [b7] \lll [b0] \leftarrow 0$	●	●	▲	▲	▲
Logical Shift Right	LSR	44	1	4	54	1	4	34	2	6	74	1	6	64	2	7	$0 \rightarrow [b7] \lll [b0] \rightarrow [C]$	●	●	0	▲	▲
Arithmetic Shift Right	ASR	47	1	4	57	1	4	37	2	6	77	1	6	67	2	7	$[b7] \lll [b0] \rightarrow [C]$	●	●	▲	▲	▲
Test for Negative or Zero	TST	4D	1	4	5D	1	4	3D	2	6	7D	1	6	6D	2	7	M - 0	●	●	▲	▲	●

Control instructions

Function	Mnemonic	Inherent			Boolean Operation	Condition Code				
		Op	#	~		H	I	N	Z	C
Transfer A to X	TAX	97	1	2	A → X	●	●	●	●	●
Transfer X to A	TXA	9F	1	2	X → A	●	●	●	●	●
Set Carry Bit	SEC	99	1	2	1 → C	●	●	●	●	1
Clear Carry Bit	CLC	98	1	2	0 → C	●	●	●	●	0
Set Interrupt Mask Bit	SEI	9B	1	2	1 → I	●	1	●	●	●
Clear Interrupt Mask Bit	CLI	9A	1	2	0 → I	●	0	●	●	●
Software Interrupt	SWI	83	1	11	PC, A, X, CC → (PC)	●	1	●	●	●
Return from Subroutine	RTS	81	1	6	(SP) → PC	●	●	●	●	●
Return from Interrupt	RTI	80	1	9	(SP) → PC, A, X, CC	?	?	?	?	?
Reset Stack Pointer	RSP	9C	1	2	\$7F → SP	●	●	●	●	●
No-Operation	NOP	9D	1	2	None	●	●	●	●	●

Condition code symbols

- H Half Carry (from bit 3)
- I Interrupt Mask
- N Negative (sign bit)
- Z Zero
- C Carry/Borrow
- ▲ Not Affected
- Test and Set if True, Cleared Otherwise
- ? Load CC Register from Stack
- 0 Bit = 0 (cleared)
- 1 Bit = 1 (Set)

Branch instructions

Function	Mnemonic	Relative Addressing Mode			Branch Test	Condition Code				
		Op	#	~		H	I	N	Z	C
Branch Always	BRA	20	2	4	None	●	●	●	●	●
Branch Never	BRN	21	2	4	None	●	●	●	●	●
Branch IFF Higher	BHI	22	2	4	CVZ = 0	●	●	●	●	●
Branch IFF Lower or Same	BLS	23	2	4	CVZ = 1	●	●	●	●	●
Branch IFF Carry Clear	BCC	24	2	4	C = 0	●	●	●	●	●
(Branch IFF Higher or Same)	(BHS)	24	2	4	C = 0	●	●	●	●	●
Branch IFF Carry Set	BCS	25	2	4	C = 1	●	●	●	●	●
(Branch IFF Lower)	(BLO)	25	2	4	C = 1	●	●	●	●	●
Branch IFF Not Equal	BNE	26	2	4	Z = 0	●	●	●	●	●
Branch IFF Equal	BEQ	27	2	4	Z = 1	●	●	●	●	●
Branch IFF Half Carry Clear	BHCC	28	2	4	H = 0	●	●	●	●	●
Branch IFF Half Carry Set	BHCS	29	2	4	H = 1	●	●	●	●	●
Branch IFF Plus	BPL	2A	2	4	N = 0	●	●	●	●	●
Branch IFF Minus	BMI	2B	2	4	N = 1	●	●	●	●	●
Branch IFF Interrupt Mask Bit is Clear	BMC	2C	2	4	I = 0	●	●	●	●	●
Branch IFF Interrupt Mask Bit is Set	BMS	2D	2	4	I = 1	●	●	●	●	●
Branch IFF Interrupt Line is Low	BIL	2E	2	4	IRQ = 0	●	●	●	●	●
Branch IFF Interrupt Line is High	BIH	2F	2	4	IRQ = 1	●	●	●	●	●
Branch to Subroutine	BSR	AD	2	8	None	●	●	●	●	●

Boolean operation symbols

- 0 Cleared
- 1 Set
- M Memory
- A Accumulator
- X Index Register
- n Bit #
- + Arithmetic Plus
- Arithmetic Minus
- Logical AND
- Logical Inclusive OR
- ⊕ Logical Exclusive OR
- Is Transferred to

Other symbols

- Op Operations Code (Hex)
- ~ Number of MPU Cycles
- # Number of Program Bytes
- Mnem. Mnemonic Abbreviation
- A Accumulator
- X Index Register

Bit manipulation instructions

Function	Mnem.	Addressing Modes						Boolean Operation	Condition Code				
		Bit Set/Clear			Bit Test and Branch				H	I	N	Z	C
		Op	#	~	Op Code	#	~						
Branch IFF Bit n is set	BRSET n (n = 0..7)	—	—	—	2 • n	3	10	Mn = 1	●	●	●	●	●
Branch IFF Bit n is clear	BRCLR n (n = 0..7)	—	—	—	01 - 2 • n	3	10	Mn = 0	●	●	●	●	●
Set Bit n	BSET n (n = 0..7)	10 - 2 • n	2	7	—	—	—	1 → Mn	●	●	●	●	●
Clear bit n	BCLR n (n = 0..7)	11 - 2 • n	2	7	—	—	—	0 → Mn	●	●	●	●	●

the program to jump to the subroutine. Labels should be limited to six characters as this is the maximum allowed by most computer assemblers.

The operation-code column (mnemonic field) contains the instruction mnemonic and the operand column (address field) contains any further information required for the instruction to be carried out. In our program all instructions require additional information to specify ram addresses of the data to be acted upon. With instructions such as load accumulator where data is not loaded from an address location, the required data byte is specified immediately after the operation code in the object-code program. Other instructions may require no further information, such as TAB on the 6800 which transfers the contents of accumulators A and B. Table 1 shows the program in its expanded form.

Numbers shown in this and subsequent tables are in hexadecimal form unless otherwise indicated. Microcomputer assemblers often require a dollar symbol or letter H to identify hexadecimal numbers.

This is a complete assembly-language source program, and the next step is to assemble it. This requires two further columns in the table to list the machine-code equivalent of the instruction and the hexadecimal address at which the program is to be stored in the microcomputer memory. Ram addresses from 24 to 6F (hexadecimal) are available in the Picotutor to store such programs. Addresses 40-42 are used to store data and the program must not overlap these so the obvious place to store the program is at the beginning of the memory, address location 24.

But should we enter the program and then run it, the processor will look for another instruction after the last one in the program and find only random data which will make it run out of control (ram locations can settle at any value after switch on). This could corrupt either the program or data and the Picotutor reset button will probably have to be pressed to direct the processor back to the monitor program. A more orderly way of terminating the program is to end it with a jump back to the monitor which will allow the result of the operation to be examined. Such a jump instruction is

JMP START Jump to monitor start

The start label in the operand/address field represents the monitor restart address which will vary according to the microprocessor and monitor program used. On the Picotutor, this address is 80. With machine-code equivalents included, the program is as shown in Table 2.

Table 1. Writing assembly language as a table with comments makes it easily understood.

Label	Op-code	Operand/address	Comments
ADDTWO	LDA	40	load accumulator from address 40
	ADD	41	add it to the contents of address 41, store result in accumulator
	STA	42	store result at address 42

Table 2. When assembly is complete, two further columns contain addresses and instructions in hexadecimal form.

Address	Machine code	Label	Op-code	Operand	Comments
24	B640	ADDTWO	LDA	40	load accumulator from address 40
26	BB41		ADD	41	add to contents of 41
28	B742		STA	42	store result in 42
2A	BC80		JMP	START	jump to monitor start

In this example, each instruction requires two bytes, one the operation code (op-code) and the other the data address, so when we fill in the hexadecimal numbers for the program address, each line increments by two (left-hand column). The number of bytes for each instruction varies between one and three according to the number of bytes of additional information that the instruction requires.

From now on, all tables shown will be in this form. It is wise to adopt this method of constructing tables not only because it helps one understand the flow of the program, but also because computer assemblers produce such tables. Printed programming forms are available.

Running the program

To run the previous program on the Picotutor, the machine code (object code) must be entered first at the specified addresses. After switch-on a dash at the left-hand side of the display indicates that the unit is ready to accept a command, so press the memory-open key (mo) which will result in the seven-segment equivalent of an m appearing on the display, indicating that a three-digit address is awaited. When the first address of the program is entered, 024, irrelevant data will be displayed. The first byte of the program, B6, is now entered and the step-up key (an arrow) pressed to close location 24 and open location 25. Byte 40 is now entered, and the process repeated until the last byte of the program, 80, is entered at memory location 02B. Now the reset button is pressed to terminate the memory-open command.

Keying in mo 024 and pressing the step up key will allow the program to be checked. Providing that new data is not entered, pressing the step up or down keys will not alter the contents of the address locations. Before running the program, data that the routine has to act upon must be entered. For this example memory locations 40 and 41 are filled with 04 and 05 respectively. Now, with the dash sign

displayed, press the go key and type in the starting address of 024. The dash should now reappear.

When the go key is pressed and the starting address entered, the microprocessor stops running the monitor program and runs the program starting at the specified location. The monitor program, keyboard and display stop functioning during this time until the last instruction is reached when control is returned to the monitor program and the dash reappears. If the program is correct, the location storing the result of the addition (mo 042) will hold the value nine. Try running the program again but with different values in locations 40 and 41, remembering that the numbers added and hence the result are in hexadecimal form.

Other microprocessors. Two accumulators are available on 6800 and 6809 processors, so the program has to specify which one is to be used. Our example uses accumulator A as follows.

1000	B61040	LDAA	1040
1003	BB1041	ADDA	1041
1006	B71042	STAA	1042
1009	7E7D97	JMP	START

Data addresses require two bytes (1040-1042) whereas only one byte was needed in the previous program because high-order address bytes of 00 do not need to be specified for the 6805 (explained later). Monitor start address 7D97 in the last line of the program is for the Nanocomp (see *Wireless World*, January and July 1981) and will need to be altered to suit the computer concerned.

For the Z80 the program needs to be altered slightly as it is not possible to add the accumulator contents directly to those of a memory location. Instead a pair of general-purpose 8-bit registers are loaded with the address of the data and the accumulator content is added to data in the memory location whose address is contained in the register pair, Table 3.

Points to note in this version are that load mnemonic LD is used for both loading and storing and requires two operands, the first signifying the destination and the second the source. The first line means load the accumulator with the contents of memory location 2040. Parentheses are used to indicate that the register is to be loaded with data contained at the address location specified. In line two, parentheses are not used so the HL register pair is loaded with address value 2041 for use as a

Table 3. Z80 assembly language equivalent of Table 2.

2000	3A4020	LD	A,(2040)	load acc. from address 2040
2003	214120	LD	HL,2041	load second operand address into HL
2006	86	ADD	A,(HL)	add acc. to operand pointed to by HL
2007	324220	LD	(2042),A	store result at address 2042
200A	C30000	JP	0000	jump to monitor start

pointer for the add instruction. The fourth line stores the contents of the accumulator at address location 2042.

Operand addresses are written with the low-order byte first when assembled – a common source of errors when assembling manually. Addresses and the monitor-start location may need altering to suit your system.

Addressing modes

We have already seen that it is necessary to address memory locations to retrieve or store data, but so far only one method for the 6805 has been described. Six basic addressing modes available on Motorola products are

- immediate
- extended
- direct
- indexed
- inherent
- relative.

Immediate. In this addressing mode the operand of the instruction is present in the byte immediately following the op-code of the instruction in the object code. A hash sign immediately before source-code operand denotes this form of addressing, for example A66F LDA #6F will load the accumulator with value 6F. The operand is always eight bits on the 6805, but on other processors it may be 16 bits. On the Z80 for example 214120 LD HL,2041 loads the HL register pair (two by eight bits) with the 16bit value 2041. Op-code 21 requires two further bytes, 4120, to form a 16bit operand. Sixteen-bit operands are sometimes used with 6800 and 6809 processors.

Extended. Here, two bytes immediately following the op-code represent the address of data to be used as the operand. These bytes form a 16bit address for Z80 or 6800/9 processors or an 11 to 13bit address for various versions of the 6805 (remaining bits are unused). For example B61040 LDAA 1040 will load accumulator A with the contents of address 1040. Absence of a prefix implies extended as opposed to immediate addressing. This mode is known as absolute addressing with the Z80 and brackets differentiate it from the immediate mode, e.g. 3A4020 LDA, (2040).

Direct. This is a version of extended addressing. If the most-significant byte of an extended address is 00 then direct addressing can be used and the most-significant byte need not be specified, resulting in a one byte saving in memory space. Although the range is limited to addresses 0000 to 00FF, this mode can save a considerable amount of memory space on the 6805 since operand addresses are usually in ram or i/o ports within this range. An

example of direct addressing for the 6805 is B640 LDA 40.

An extension to this idea on the 6809 is an eight-bit direct register which holds the most-significant address byte. Instead of being fixed at 00, this byte may be altered by the program. There is no equivalent to this mode on the Z80.

Indexed. In direct and extended-addressing modes, the address of data which forms the operand is specified but here the address is contained in an index register called a pointer. A similar concept used with the Z80 appeared earlier – 86 ADD A,(HL) – where the accumulator content is added to data in an address location pointed to by two bytes in the HL-register pair.

But with indexing it is also possible to specify an offset which is added to the contents of the index register to form the effective operand address. This offset is contained in an immediate byte(s) for the 6805 as follows.

AE78	LDX	#78
E604	LDA	4,X

In the first line, the eight-bit index register is loaded with immediate operand 78 and the second line loads the accumulator with the contents of memory address 7C (78+4) without altering the index register contents. Sixteen-bit offsets may also be used; for example

AE78	LDX	#78
D60146	LDA	146,X

will load the accumulator from address 1BE. Operation codes E6 and D6 are used to signify eight and 16bit offsets respectively. A special case exists when the offset is zero in that F6 LDA 0,X replaces E600 LDA 0,X. Operation code F6 for indexed addressing with no offset is peculiar to the 6805.

The 6800 has a 16bit index register but only allows eight-bit offsets. Although the 6809 has only two index registers (X and Y), two stack pointers (S and U) may be used as index registers; indexing modes of this processor are beyond the scope of this article. The Z80 has two 16bit index registers, IX and IY.

Inherent. This type of addressing is used when it is obvious from the nature of the instruction that no further operand or address is required to complete it, as for example with SEI, set interrupt mask, RTS, Return from subroutine, and CLRA which clears the accumulator.

Relative. Branch and conditional-branch instruction use relative addressing. With these instructions, sequential processing stops and the program branches either forward or backward to another point depending on the value of a displacement

byte. The displacement byte is a signed two's complement number which is added to the program counter after it has been incremented to point to the next sequential instruction. This byte allows branches of between 127 and -128 steps from the current program position by modifying the value in the program counter.

With the 6809, displacements represented by 16 bits may be used allowing the program to branch to any position in a 65Kbyte memory.

The six addressing modes above apply to all the processors that I have mentioned (8080 has no relative-addressing mode). In addition, the 6809 has many more addressing modes but for our purposes, the ones covered will suffice. Two further addressing modes are only available on the 6805.

Bit set/clear. This allows a single bit of any byte in address-page zero (0000-00FF) to be set or cleared without affecting any other bit in that byte.

Bit test and branch. A specific bit of any byte in address-page zero may be tested and cause a branch or not, depending on the result of the test.

These two modes are useful in control applications since they allow single i/o lines to be specified. A similar form of bit manipulation is possible using the Z80. 

BOOKS

Handbook of Antenna Design, Volume 1, Editors: A. W. Rudge, K. Milne, A. D. Olver, and P. Knight, 708 pages, Hardback, Peter Peregrinus, £42.

Written by a multi-national group of antenna experts, this book constitutes volume 15 of the IEE Electromagnetic Waves Series. It presents the principles and applications of antenna design with particular emphasis on recent developments. Fundamental theory and analytical techniques are explained in detail where appropriate and there is extensive design data with examples of practical application. A wide range of antennae are dealt with from very low frequencies to millimetric waves and from satellite communications to radar and broadcasting.

Complete Guide to Videocassette Recorder Operation and Servicing, By John D. Lenk, 365 pages, Hardback, Prentice-Hall, £19.50.

This book provides a practical approach to servicing and trouble-shooting v.c.r.s with special emphasis on Beta and VHS recorders. Starting from basic principles, the author describes an easy step-by-step method to service the machines including a section on any special tools that may be required and their operation. An American book, it describes NTSC machines, but it is applicable to PAL systems.

Peak-to-peak bar/dot indicator

Depending on the frequency of the input, the instrument provides a led bar or moving-dot display of pk-pk voltage

The circuits presented here are for a 31-led bar/dot meter which indicates the peak-to-peak range of signals with frequency content from 0 to 10 kHz and amplitudes between $\pm 1.5V$ peak. At frequencies

by A. J. Ewins

greater than 100Hz the meter gives a bar indication extending over the range of the peak negative to peak positive values of the input signal. At frequencies below 1 Hz the meter gives a moving dot display rang-

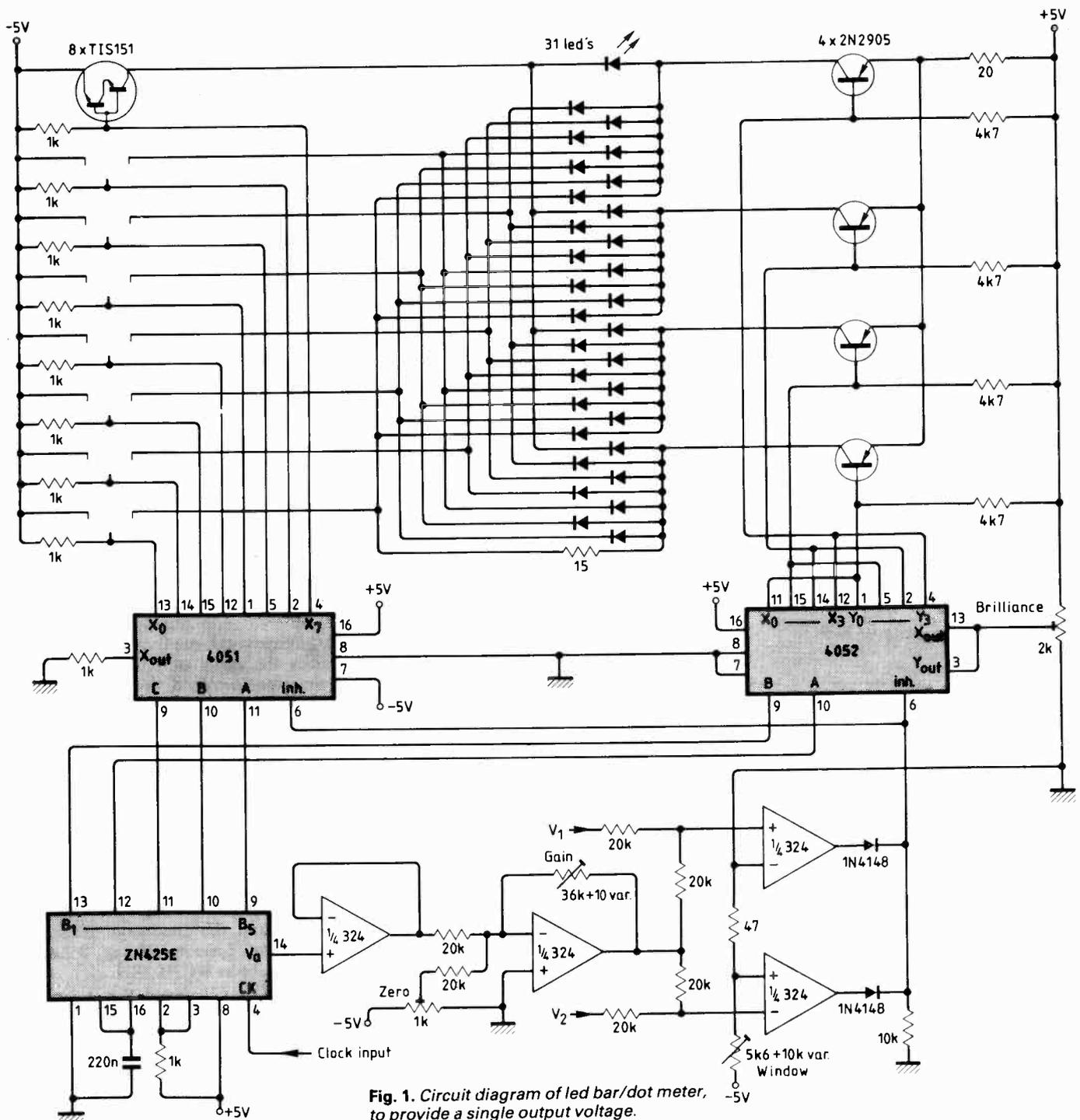


Fig. 1. Circuit diagram of led bar/dot meter, to provide a single output voltage.

ing over the peak-to-peak levels of the input signal. The display may be generally likened to that of a signal on the 'y' axis of an oscilloscope with no timebase. The display is able to indicate both the a.c. and d.c. content of a signal, the d.c. content of a signal with a high-frequency component merely shifting the displayed bar in the direction of the d.c. offset.

The circuit of Fig. 1, on its own, produces a bar display extending over the range of the two input voltages, V_1 and V_2 , where $+2.5V > V_2 \geq V_1 > -2.5V$. When an input voltage is applied simultaneously to V_1 and V_2 , a single dot is displayed which indicates the amplitude of the applied voltage. The circuit of Fig. 2 produces two output voltages, V_{min} (V_2) and V_{max} (V_1), representing the peak negative and peak positive values of the signal applied to its input. The circuit has a gain of 5/3 to amplify input signals of $\pm 1.5V$ peak to an output level of $\pm 2.5V$.

Circuit operation

The heart of the circuit of Fig. 1 is the d-to-a converter i.c., ZN425E. With a suitable clock oscillator (see Fig. 3) at its clock input, the five most significant bits of its 8-bit counter output are used to multiplex the 31 leds via the two c.m.o.s. multiplex i.c.s, 4051 and 4052, and the p-n-p and n-p-n transistors. Whether or not a led is turned on as it is addressed is determined


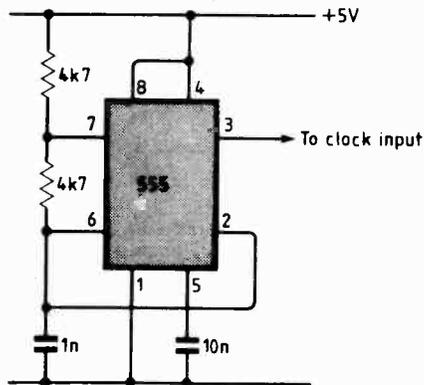


Fig 3. Clock oscillator.

Fig. 2. Modification to produce two outputs.

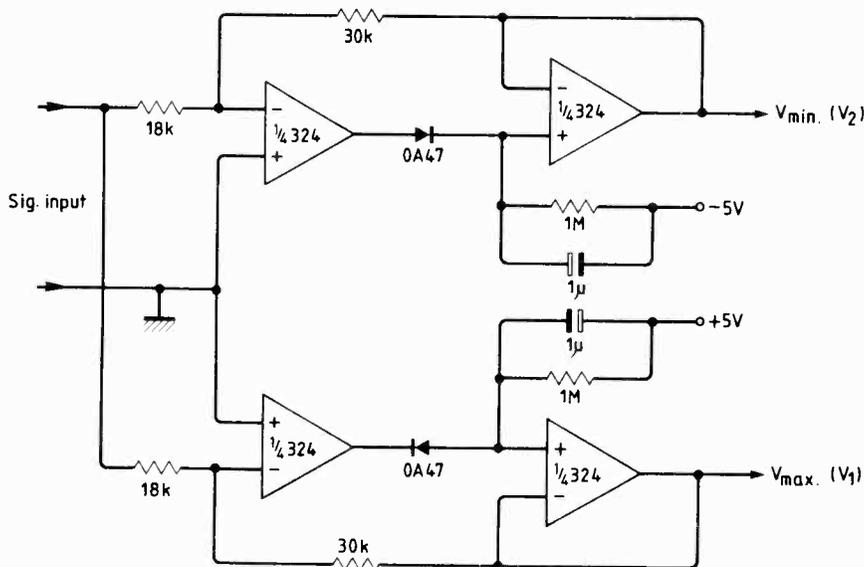

by the logic level on the INH input of both multiplex i.c.s. The ZN425E also produces a 256-step analogue ramp voltage output in sequence with its digital counter. Buffered by the first op. amp., amplified by a factor of about 2 and offset by the second op. amp., the resulting output is a negative ramp falling from $+2.5V$ to $-2.5V$. (The 'offset' control can be used to produce a negative ramp of $5V$ pk-pk anywhere between $\pm 5V$, enabling the centre zero of the display to be shifted from one end of the scale to the other.) This ramp voltage is mixed with the two input voltages, V_1 and V_2 , separately, and applied to two comparators. The result of this is that when the instantaneous value of the ramp voltage (inverted) lies outside the range of V_1 and V_2 , the INH level is at logical '1' and an addressed led will be off. When the instantaneous value of the ramp voltage lies inside the range of V_1 and V_2 , the INH level is a logical '0' and an addressed led will be turned ON. Thus only those leds which give an indication of an analogue voltage between V_1 and V_2 are lit as they are addressed. One comparator is referenced to zero volts and the other to a small negative voltage. This ensures that just one led is lit, giving a dot display, when V_2 equals V_1 .

The four 2N2905 transistors are connected as emitter followers when addressed and provide a constant current source to the leds. The value of the constant current is determined by the common 20 ohm emitter resistor and the voltage applied to the transistor bases. The 'brilliance' control determines the base voltage and hence controls the value of the constant current, which may be adjusted to any value between 0 and 200 mA. The eight n-p-n transistors act as switches to sink this current through the selected led. The average current that a led sees is $1/32$ of the constant current value. The leds used in the original design were end-stackable types from Farnell Electronic Components, types CQX10-4 (red), CQX11-4 (green) and CQX12-4 (yellow). Although shown as single transistors, for convenience, the TIS151 devices are in fact Darlington pairs from Texas Instruments. An alternative to these transistors would be an

array i.c. such as the ULN2801A, which is an 18-pin device containing 8 n-p-n Darlington pairs intended for just such an application.

Only 31 leds are used in the display, though 32 are addressable. The reason for omitting the first led is twofold. Firstly, the first led is always dimly lit due to the finite time of the fly-back of the ramp voltage; secondly, 31 leds give a very convenient display with one used as a zero indication, and fifteen in each positive and negative direction providing an indication in 100mV steps. The resolution of the display is, in fact, better than 100 mV. This results from a graduation in the illumination intensity of adjacent lens as the signal level changes from one 100 mV step to the next. When the signal level lies exactly halfway between 100 mV steps at, say, 350 mV, then the adjacent 300 mV and 400 mV leds will each be half lit. It is possible to estimate when one led is $1/4$ lit and the adjacent led is $3/4$ lit. A resolution of about 25 mV can thus be achieved.

Finally, using the dock oscillator of Fig. 3, the leds are scanned about once every $2\frac{1}{2}$ ms.

LITERATURE RECEIVED

Several volumes have been added to the range of technical literature published by Texas Instruments. Among them are new data books on mos memory devices, microcomputer components and power semiconductors and an educational guide to applications of electronics in motor vehicles. A booklet describing these and other technical publications is available from Texas Instruments Ltd, P.O. Box 50, Market Harborough, Leicestershire.

A new Sprague Semiconductor Chip catalogue is now available from the company's UK chip distributor, Hy-Comp Ltd, at 7 Shield Road (Ashford Industrial Estate), Ashford, Middlesex, TW15 1AV.

A 12-page catalogue from BICC-Vero describes the range of pluggable telephone connectors designed by the company for British Telecom. The connectors have features which, according to the makers, make them suitable for other applications, such as with sensors, keyboards and hand-held controllers. BICC-Vero Connectors, Parr, St Helens, Merseyside.

A directory covering more than 200 product categories is contained in a guide to British manufacturers of electronic capital equipment. The booklet is available free of charge from the Electronic Engineering Association, Leicester House, 8 Leicester Street, London WC2H 7BN.

Microprocessor systems and instruments for energy management are among many new additions to a large catalogue of equipment available for rental from Livingston Hire Ltd, Shirley House, 27 Camden Road, London NW1 9NR.

Two-metre transceiver

Comprising a.f. amplifier and tone generator circuits, this section of the multi-mode transceiver is the tenth and final module. Wiring information completes the hardware description in this penultimate article.

In addition to providing a tone burst and a.f. preamplification, module 10 generates a 'pip' when the frequency is changed. Dual monostable IC₁₀₀₀ is wired to give outputs of around 2s and 100ms to initiate tone-burst and pip signals respectively. Two-second pulses enable the tone-burst oscillator formed by half of IC₁₀₀₁ through a diode OR gate, the resulting signal appearing at pin 3 of IC₁₀₀₁. Before leaving the module, the tone-burst signal is filtered and attenuated by R_{1009,1010} and C_{1005,1006}. A potentiometer sets the tone-burst level feeding the f.m. microphone amplifier.

To prevent operation of the tone burst in any mode other than repeater, the 2s monostable is disabled at pin 13 of the i.c. by a low signal from the mode switch. This disable signal comes from the switch wafer used for driving the start transistor of module 3.


The other half of the dual monostable provides a short pip which drives a miniature ear-piece located behind the front panel to indicate frequency changes. Pulses from this half of the monostable also turn the tone-burst oscillator on through the diode-OR gate but now the output is directed through a different NAND gate to the earpiece. When data is

by T. D. Forrester, G8GIW


sent to the synthesizer by the microprocessor, D_{1en} control line goes high; this line is used to trigger the pip monostable through buffer transistor Tr₁₀₀₁. In scan mode, the buffer transistor is inhibited to avoid the annoyance of continual pips.

Tone-burst frequency is set at 1750Hz by R₁₀₀₈. To set the frequency, pin 12 of IC₁₀₀₁ may be taken high so that the oscillator runs continually. A conventional a.f. preamplifier formed by Tr₁₀₀₂ lifts the level of the audio signal to suit the a.f. power amplifier. Gain of this stage is adjusted using R₁₀₁₃.

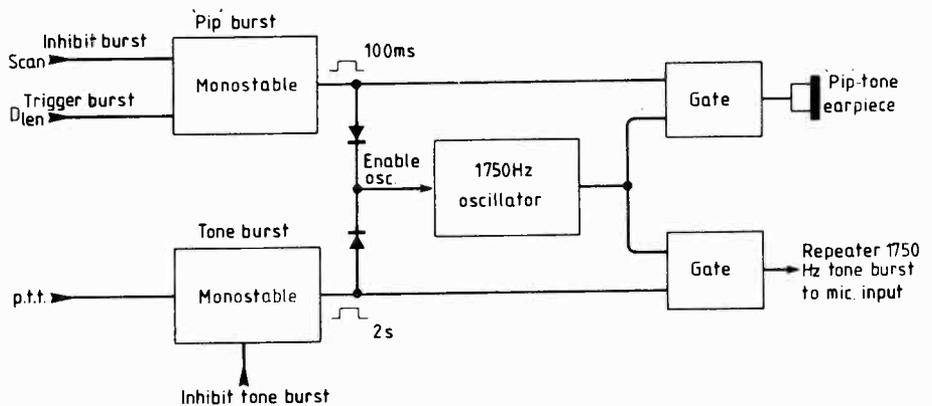
Front-panel wiring is detailed in the diagram. The mode switch used has two wafers each with two-pole, six-way



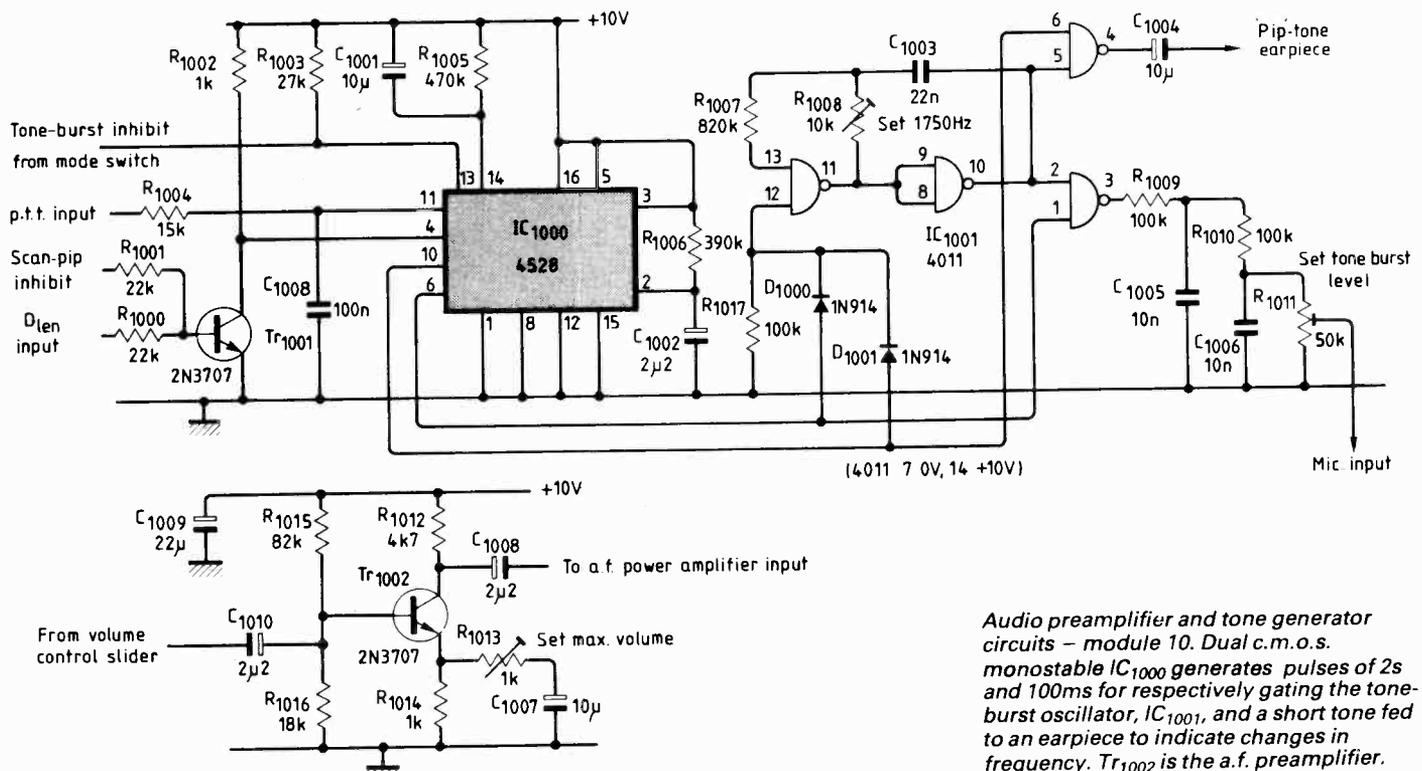Tone-burst generator block diagram shows how the oscillator is gated to provide both a 1750Hz signal for the repeater and a short audible tone indicating changes in frequency.



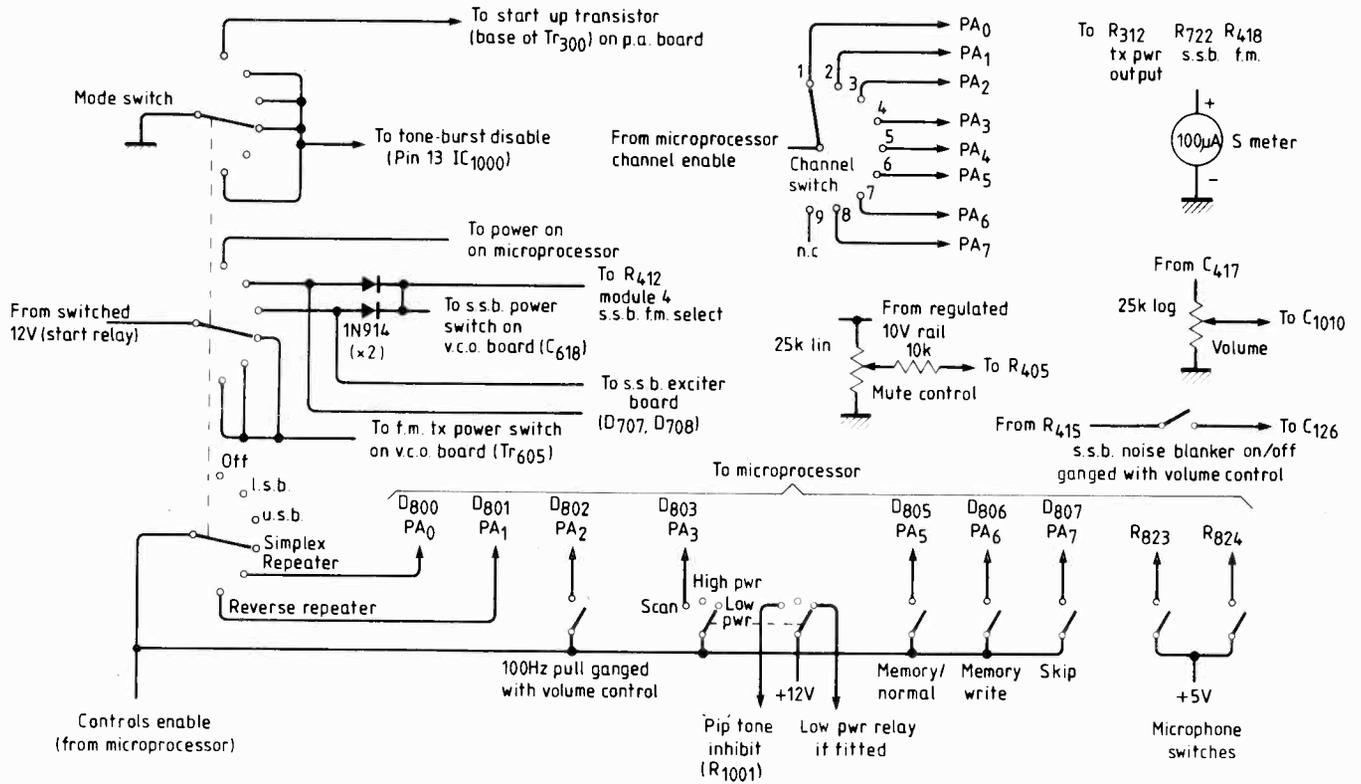Audio preamplifier and tone generator circuits - module 10. Dual c.m.o.s. monostable IC₁₀₀₀ generates pulses of 2s and 100ms for respectively gating the tone-burst oscillator, IC₁₀₀₁, and a short tone fed to an earpiece to indicate changes in frequency. Tr₁₀₀₂ is the a.f. preamplifier.



Wiring diagram for the multi-mode transceiver front panel. Mode switch is a four-pole six-way type and channel switch is a single-pole twelve-way type, of which only nine ways are used. The 100 μ A edgewise meter and these switches (Mini Maka) are available from RS Components. Sub-miniature toggle switches are used for normal/memory and scan high/low controls, one a single-pole change-over type (53-00200) and the other a double-pole change-over type (53-00201). Miniature push-button switches (53-00300) are used for memory-write, skip and up/down mike controls. Both potentiometers include double-pole pull-to-make switches (48-25320 log., 48-25319 lin.). These components can be obtained from Ambit using part numbers in brackets.


Four more screening boxes are mounted on the underside of the plate housing from left-to-right the v.c.o. and synthesizer, s.s.b. receive-transmit/f.m.-exciter, receive-converter and f.m. i.f. modules. The module on the back of the transceiver houses an inductively-coupled band-pass filter and the antenna change-over relay. As all the r.f. modules are screened separately, there is no reason why the layout described should be adhered to but in terms of access and ease of construction, the module positioning described is believed to be optimum.

contacts so a spare pole is available for enhancements.

As can be seen from the photographs, the transceiver is constructed as two halves above and below a centre plate made from 1/8in aluminium alloy. On the top left-hand side of this plate is the microprocessor

p.c.b. and directly in front of it the display-driver board. To the right of it is the screened transmit-converter module and to the right of that the transmitter final stage, start relay and power regulators, also screened. Teko boxes were used to house the modules.

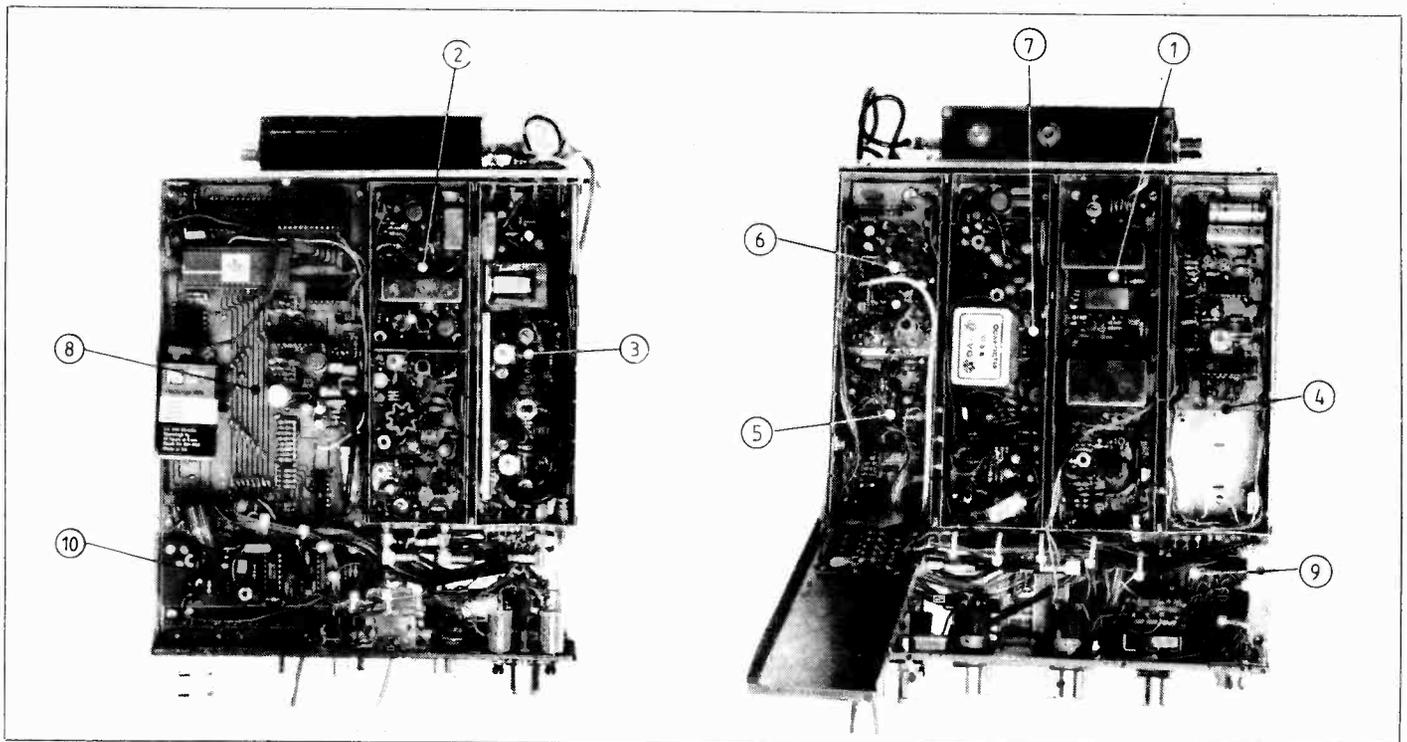Front and rear panels are also made from 1/8in aluminium sheet and secured to the tapped centre plate by 8BA screws. Aluminium sheet of 20s.w.g. was used to



Transceiver modules

- 1 receiver converter, 144MHz to 9MHz
November 1982
- 2 transmit converter, 9MHz to 144MHz
December 1982
- 3 transmit power amplifier and power regulators
December 1982/January 1983
- 4 f.m.-i.f. discriminator, squelch, noise blanker, a.f. power amp
January 1983
- 5 synthesizer logic
January/February 1983
- 6 synthesizer voltage-controlled oscillator, power change over
February 1983
- 7 s.s.b. 9MHz transceiver, 9MHz f.m. exciter
February 1983
- 8 microprocessor control and interfaces
March 1983
- 9 frequency-display driver
March 1983
- 10 1750Hz tone-burst and receive a.f. pre-amp
April 1983

Resistors


1000,1001	22k
1002,1014	1k
1003	27k
1004	15k
1005	470k
1006	390k
1007	820k
1008	10k sub-min preset
1009	100k
1011	50k sub-min preset
1012	4.7k
1013	1k sub-min preset
1015	82k
1016	18k
all 1/4W, 5%	

Capacitors

1000	100n disc
1001,1004,1007	10µ tantalum, 16V
1002,1008,1010	2.2µ tantalum, 16V
1003	22n polyester
1005,1006	10n disc
1009	22µ tantalum, 16V

Two 2N3707 transistors, two 1N914 diodes and two i.c.s, a 4528 and a 4011, complete module 10.

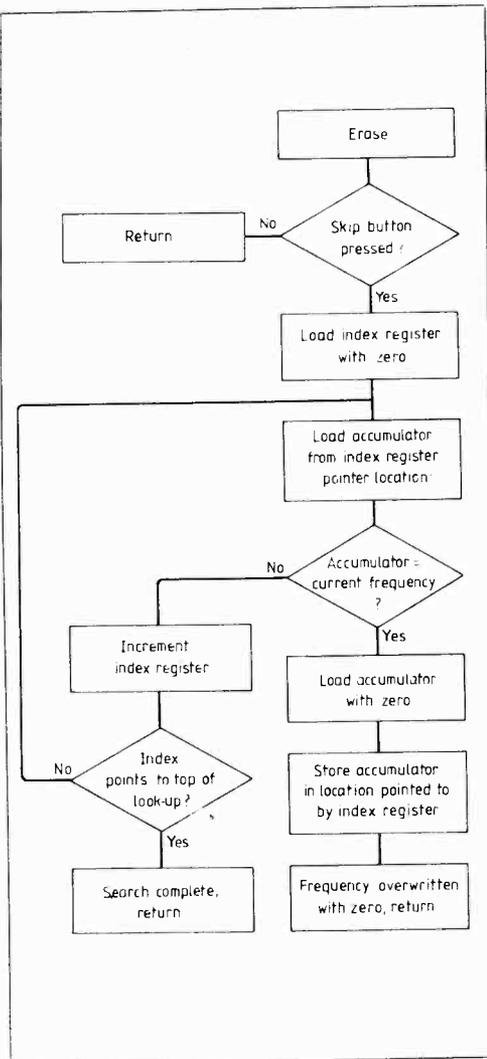Prescaler SAA1058 and p.i.l. SAA1056 (module 5) can be obtained from Macro Marketing for £3.02 and £4.15 respectively, excluding vat and £2 postage and packing. The company's address is 396 Bath Road, Slough, Berks SL1 6JD.



make a base plate and three-sided cover. Letter transfers were used to annotate the front panel which is protected by a tough plastic film.

Software


Flow charts illustrated here break down the main program given last month to help one understand how the transceiver operates. Mnemonics relate to assembly language used for the transceiver program.

Referring to the erase flow chart, if squelch lifts while the transceiver is scanning, the microprocessor checks whether or not the channel concerned is to be ignored (skipped). If so scanning continues but if not, scanning stops for a while. Pressing the skip button during this pause will cause the channel to be skipped over on the next scan.

A subroutine called Erse erases channels from the skip list as follows. During normal operation, i.e. with the set tuned to the desired frequency using the up/down buttons, it is possible to erase a certain frequency by tuning it in and pressing the skip button. This causes the microprocessor to search through its skip list and compare the frequencies in it to the one tuned. When the values match, the frequency in the skip list is overwritten with a zero. On the next scan, the microprocessor stops at this frequency to allow one to listen in.


Two buttons on the microphone allow the set to be tuned up or down in frequency for both normal operation and memory storage. Frequency increments depend on the position of the 100Hz/25kHz switch ganged to the volume potentiometer. In the up/down flow chart, a subroutine called sort tests which direction the frequency is to be stepped in and whether the steps are 100Hz or 25kHz. If either the up or down button is kept pressed, the rate at which the frequency steps up or down increases until the button is released.

To be concluded.

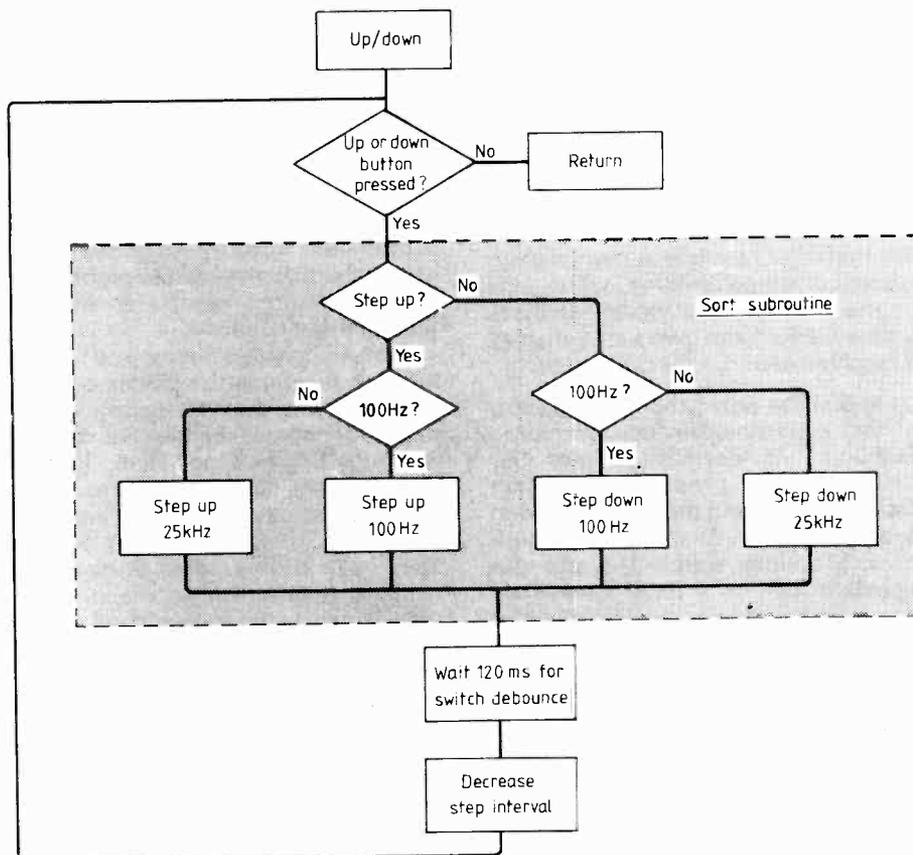

COMPETITION

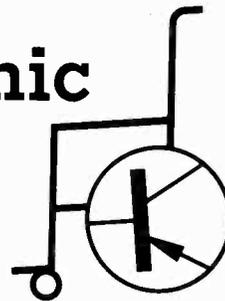Design an electronic device to aid the disabled



A recent visit to a travelling showcase of aids for the disabled indicated how simple many of the devices were: levers to extend normally difficult-to-operate switches or dials; clamps to grip jars or bottles so that they may be opened more easily; various rods and hooks to aid people to dress themselves. At the other end of the scale, microcomputer hardware and software are being used in imaginative ways to aid severely handicapped people: providing voices to those unable to speak and enabling those unable to move to interface with the world.

Many examples spring to mind; the Possum allows, by the use of simple push switches, the disabled to operate a computer. We have received details of a single-board microcomputer which has been used to operate switches on the reception of whistle tones. The well-known Turtle enables children unable to move to experience spatial dimensions by directing the robot around the floor. And computer graphics can perform a similar function on a tv screen. We have reported in the News pages recently the Viewscan system which can scan printed matter and display it on a c.r.t. with enlarged characters for the partially-sighted; we also reported on the micro-controlled wheelchair designed by Dan Everard for use by his daughter who suffers from spinal muscular atrophy.

This last example brings us to an important point. The chair was designed to help a specific person even though it would be of use to many others. Entrants in the *Wireless World* 'Design an electronic device to help the disabled' competition should be encouraged to contact the people who need the aids, to find out what those needs are and to work in cooperation with the 'end user' so that these objectives are best fulfilled. It would be pointless to re-invent the wheel, so it is well worth checking that the device being designed does not already exist. On the other hand there may be ways of improving the wheel so that it runs more smoothly or is easier to use.

Communication is of course one problem. The autobiography of Joey Deacon needed three people to write it: Joey himself, his friend Harry, who was the only person able to interpret the sounds that Joey made, and a third who could operate a typewriter with one finger. Christy Brown was discovered to be a fine poet after he had learned to communicate by typing with his foot. It must be horrifyingly frustrating to have an intelligent mind trapped inside an incapable body; Joey and his friends were cared for in a mental institution not because of their mental disabilities but chiefly through their inability to communicate.

Physical mobility is always a problem. For example, many disabled people need to wear elastic stockings but there is no device readily available to help them to get them on or off unaided. This is outside the scope of our competition but it does illustrate a simple problem in search of a solution. Reward toys, like the teddy bear whose eyes light up when a deaf child speaks, are in great demand, as are all toys that offer physical or mental exercises to disabled children. Other aids for the deaf include visual feedback systems, which can give a c.r.t. display of received sound, especially speech.

It should be noted that most electrical and electronic devices overcome disabilities of 'normal' people. Our voices can only propagate a certain distance. To extend the range we need to amplify it or to carry it through wires. Machines supply the strength we lack or can carry us at speeds we cannot run. Various optical devices enable us to see further or observe things that we cannot see. Calculators are useful when we run out of fingers to count on and computer memories can store vast quantities of data which may be recalled and manipulated in ways beyond the scope of human brains. Aids for the disabled are really just extensions of the same techniques; they enable the handicapped to do things that they otherwise cannot do.

The competition is very straightforward. All you need to do is fill in and send us the entry form which just indicates that you are interested in taking part. The form must be returned before June 30th. The actual design must be submitted to the Editor by 1st October, 1983. An entry must include a statement of the design objectives; an overall description of the device; detailed circuit description and diagrams; a model of the device or that unique part of it which demonstrates its operation and feasibility. The judges will be a group of eminent engineers and doctors and they will be looking for originality and benefit to the handicapped; the potential for production; elegance or engineering design; the electronic content; design reliability and freedom from excessive maintenance; simplicity of operation and the safety of the device. They are also looking for a specifically electronic device so a software package will not be acceptable, although software may be necessary to operate the hardware and should be included if this applies. The competition will be coordinated from the *Wireless World* editorial office and we are planning to include progress reports on the projects in these columns.

Useful contacts may be found through local council offices or libraries who can put you in touch with disabled peoples centres or homes. REMAP, Engineering Help for the Disabled, has 90 branches throughout the UK. Their headquarters are at 25 Mortimer Street, London W1N 8AB. They have a large panel of engineers who are working for the disabled and are willing to offer help and advice.

It should be noted that aids for the handicapped need a fundamental approach to tackling a problem and that devices can be produced which are not only helpful for the disabled but may improve ergonomically facilities for us all. Please enter the competition. You may produce a device which is of great help to many people.

A full list of the rules and an application form are included in our advertisement on page 108.

In praise of software

Like the old "nature vs nurture" controversy it is always fun to return to "software vs hardware". Professor Zissos would have us beware of systems swaddled in software (or some such phrase), and whilst it is all too true that the software overhead on many systems is intolerable it does not follow that junking that software will improve matters. In practice this term "software" covers two rather distinct sets of tools, programming languages and operating systems, and it is as well to consider them separately. We'll start with programming languages.

The pristine argument against the use of high-level programming languages is that a skilled machine code programmer using the native instruction set of a computer can write a program that is significantly more efficient (in terms of execution time or storage occupancy or both) than will be generated as object code by a high-level language compiler. The assertion is doubtless true. Unfortunately its utility depends on the availability of "skilled machine code programmers". Such scant evidence as we have suggests that only 25% of those who call themselves so skilled can in fact do better than a compiler. In addition, the demand for programmers is increasing at about 50% annually, whilst the supply is increasing by only 18% annually. That increased supply, is, too, at the novice, unskilled, end of the spectrum of expertise.

So the systems designer and implementor who chooses to rely on machine coding of the applications package just faces the hurdle of hiring adequately skilled programming staff. And then, in a sellers' market, of retaining them.

The immediate advantage of choosing a high level language such as Pascal or Fortran for applications programming is that the implementor has a choice from a much larger pool of skills. It just is a fact of life that the number of good Pascal programmers on the market is much greater than that of machine code programmers. And they are not such prima donnas either!

But a number of other advantages accrue from the use of a high level language. If partway through the production run it is economic to replace the microprocessor chip by another then the software does not have to be rewritten but only recompiled. As staff changes it is necessary for newcomers to familiarize themselves with the existing applications programs so as to be able to maintain and modify them. This is much easier and quicker if these programs are written in a high level language, because programs written in a high level language are a little more self-documenting.

Also, they neither depend on the local features of a particular chip nor on a particular programmer's quirks in laying out data structures, etc.

The penalty of using a high level language then will be a slower executing program and usually a more extensive object program requiring more rom to accommodate it. Should execution time be critical it is usually passable to substitute a faster microprocessor chip, at extra cost. The relevant question is whether, over the total lifetime of the system, the initial cost of a faster microprocessor and of added rom exceeds the savings gained from the use of a high level programming language. Remember, programmers expect regular salary increases, chips don't.

Should it be the case that the system under consideration is already employing the fastest technology available then it will

H. D. Baecker

be necessary to stick with machine coded programs. It is precisely those users stuck with this need who will be most predatory on the market for skilled machine code programmers and will determine the costs incurred by others. It would therefore be prudent to rely on alternative programming talent.

It is true that you will find some extremely gifted programmers in academic or civil service posts where the salaries are significantly below market norm, so clearly salary is not the only determinant in attracting and holding talent. Further investigation will show that the freedom to experiment in these positions is the attraction, situation that cannot prevail in the successful completion of economic application packages. Under conditions of politically imposed "wages freeze" one can predict that talent will migrate to academic, etc., from the marketplace.

Now to the question of operating systems. As long as a given processor is executing only a single process or task the whole time the presence or absence of an operating system can be a matter of taste. The moment two or more processes share the processor an operating system is mandatory in order to schedule access to processor resources by the processes and to protect the processes from mutual interference. The question of whether or not to employ an operating system is then empty,

the question becomes whether to use the vendor's standard operating system, or whether to turn to an off-the-shelf product available from some software house for that microprocessor, or whether to write one's own system.

The usual objection to a vendor's operating system is that it is too rich, too extensive, for the needs of the present project. This may be so, but it is usually possible to generate a local version of the system that includes only those facilities needed locally. Indeed, this freedom may be an important factor in choosing a particular microprocessor. Software house operating systems often have the advantage that compatible versions are available for several ranges of microprocessors, making processor substitution easier. The supposed advantage of writing one's own operating system, that it will contain nothing but the bare bones required for the job and so will interpose no unnecessary overhead, is illusory. Six months hence the next upgrade of the microprocessor system will demand a new function of the operating system, and since the private operating system was so specifically designed to eliminate overhead there will be no hooks to hang the new function from.

Implementation and installation decisions in computing are rarely made solely on the basis of technical merit. Computers are tools, and other concerns of the tool users have to be satisfied. There is no doubt that the world's most widely sold computer architecture is not the world's most efficient or powerful or elegant. But its original vendor was deemed financially secure enough to proffer the support needed by customers. In implementing a microprocessor based system it may be that doubling the hardware cost of the basic system may have a negligible effect on the sale price, that software and engineering support costs are far more significant. If this is the case, and if the costs of seniors and actuators are fixed, then minimizing the initial and ongoing software costs may be the most practical way to economize.

Such a turn of events should come as no surprise. The most successful, the most reliable, technological system we have, one we take absolutely for granted most of the time, is the worldwide telephone system. Its success and reliability depend not on local innovativeness but on slavish standardization. We are a bare 32 years beyond the commissioning of the first general purpose electronic digital computers, and it may seem premature to throttle development by adopting standardized tools, such as existing high level languages or operating systems.

H. D. Baecker is in the dept of computer science, University of Calgary, Canada.

IBM Selectric to TRS80 interface

Along with an assembly language program which is kept in high memory, this interface is all that is needed to have letter-quality printing. As the printer uses typing elements that can easily be changed, what more could a computerist want? Speed? Not so fast, it prints at 60 words a minute, but oh what print, says Tony Scarpelli.

Brian Bateman has already shown how to interface a TRS80 computer to a five-level teletype. His article* inspired me to design and build my own interface that uses relatively inexpensive hardware and even cheaper software to drive an IBM Selectric I/O printer. If less than \$500, which includes the printer, turns you on then read on.

I was in the market for a printer. I had to choose a unit that was either dot matrix or letter-quality. As I was into writing articles, I decided on high quality printing;


by Anthony T. Scarpelli

but, a new letter-quality printer can run into the couple of thousands of dollars. Then an ad from CFR Associates of Newton, NH caught my eye, who were selling used IBM Selectric I/O printers for \$395. That was inspiring, and I ran down there and picked a unit up that was taken out of a Wang word-processing system.


These printers contain the driver solenoids that select the various characters and do the other normal functions such as spacing and printing. The unit was in great shape and probably still had a few more thousands of miles of printing left in it, and only a few minor adjustments got it printing excellently. A call to my local IBM representative got me an account and the ability to get manuals and parts with no hassle; and with great speed. A list at the end of the article gives the numbers of the manual and tools needed to do any type of



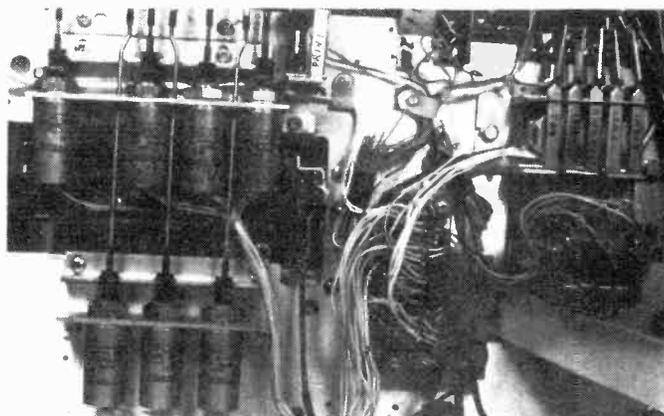
1. Originally from a Wang word processor system and ending up as a surplus bargain, this IBM Selectric I/O printer can be used as a letter quality printer in a computer system. Though it can be used as a keyboard as well as a standard typewriter, in this application it is strictly an output device.



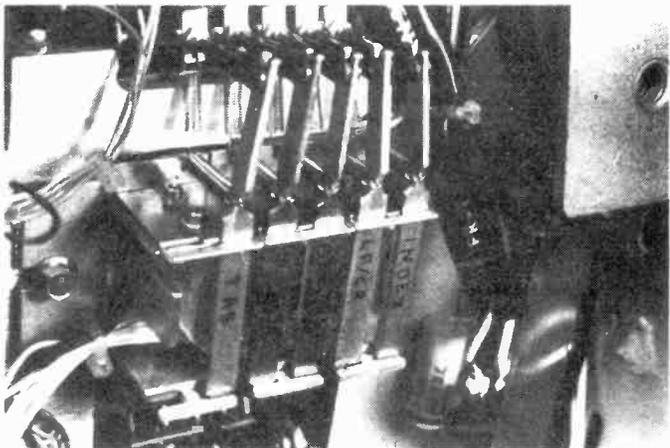
2. Character-select solenoids determine which character is to be printed and are held-in as the print solenoid is energized. Function solenoids are on the right. Tab and back space are not used in this application, but could easily be put into service.



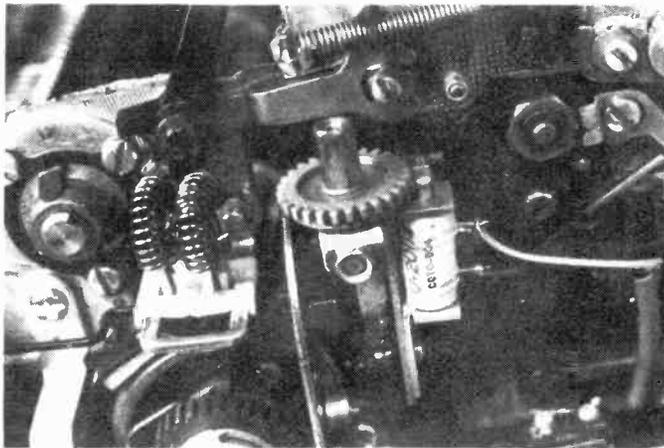3. Not much power is needed to drive the function solenoids, and during initial testing they can be manipulated by hand.



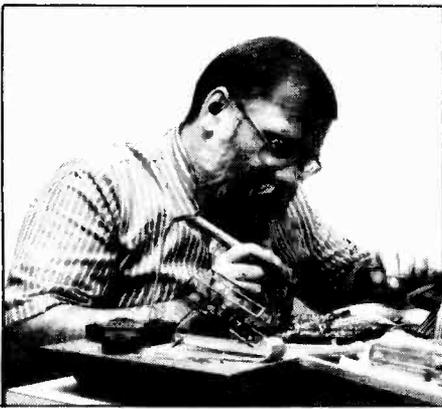4. Carriage movement detector coil detects pulses from the gear which rotates as long as the carriage moves. Pulses are amplified and integrated to produce a signal used by the computer to detect this movement.



Tony Scarpelli is senior biomedical electronics technician at the Maine Medical Center in Portland, Maine, the largest hospital in the largest city in the state. He collaborates with other hospital departments in the design of various electronic projects, such as interfaces that connect computers to various types of medical equipment, and is presently working on a computerized environmental control unit for quadriplegic patients. His electronic career started at the age of three when his father introduced him to a crystal radio. Most of his work has been in medical electronics, repair, and research. He has gone from valves, through transistors and integrated circuits, and has finally landed in the world of computers. He has published computer programs, reviews, and other material in a number of American journals. Fluent in Z80, 8080, and 6502 assembly languages, as well as Basic, Forth, and Mumps, he edits a computer club newsletter, Byte Babble, and spends most of his free time at the keyboard writing programs, articles, and learning new computer languages. He feels that people have only just begun to touch on the computers potential, and its use as a mind amplifier is still to be fully realized.

adjustment on these IBM machines. The manual is essential for an understanding of this very complicated mechanism, and for any troubleshooting in case of malfunction.

With the machine working, and with the circuit supplied with the unit, I started on the design of the hardware circuits to drive the solenoids. I am a simple person so I decided to make the circuit as simple as possible so that even I would be able to understand it. I also wanted to make it from parts from my local Radio Shack† store so that I wouldn't have to wait six weeks just to get an i.c. If you have the parts on hand, or have a less expensive outlet for the parts, by all means go that route if you wish. I just happen to have a store in town.

The printer has six character-select solenoids, and five other function solenoids that would have to be driven by the computer. I decided that each of the function solenoids would get an output port. The printer also has a carriage-movement detector which would also get a port. I use this detector to speed up the printing by

holding up the program during carriage returns. When the carriage returns from a great distance, you don't want any printing going on, but when it has to return from a short distance, you don't want to wait for a timing loop to finish.

When you want to have your computer talk to the outside world, the first thing you have to decide is whether you want to use ports or use a memory-mapped system. If you go memory mapped, that is the computer thinks anything external is just part of its memory, you have to deal with 16 address lines. Because this wasn't necessary and would only add complexity and expense to the system, I decided on ports which only use eight address lines. There are 255 ports available with these eight addresses, and as no.255 is already used by the TRS80, and no. 254 is used by my speed-up circuit, I used numbers 247 to 253. These are easy to decode as we shall see in a minute.

The next consideration as far as the outside world is concerned is that all address lines and data lines have to be buffered. This does two things: it helps protect the output of the computer, and it gives the output more drive capability. Fig. 1 shows all the buffered lines that are

used in my interface. Notice that the designation OUT*, for example, is how Radio Shack indicates an active low signal — it is easier to type than the normal way, you can see. Other than the eight address lines and eight data lines, only OUT*, which indicates something is going out of a port, IN*, which indicates something is coming in, and SYSRES*, which is the system reset, are the only computer-generated signals needed.

Fig. 2 shows the first port I designed and will be used as the example of how all the ports work, and also how you can go about getting your own computer to touch the outside world. First give the port a number, in this case 253, or FD in hexadecimal and 1111 1101 in binary. I called it the space port as it will drive the space solenoid. It is decoded with an eight-input nand gate: when all its inputs go high the output goes low. As line A1 is the only low line, we can make it high by going through an inverter so that only when the address FD is on the address bus will the output of the gate go low. In the assembly language program, the instruction OUT (C), A causes data in the A register to be put onto the data bus just after the address in the C register is put onto the address bus, while


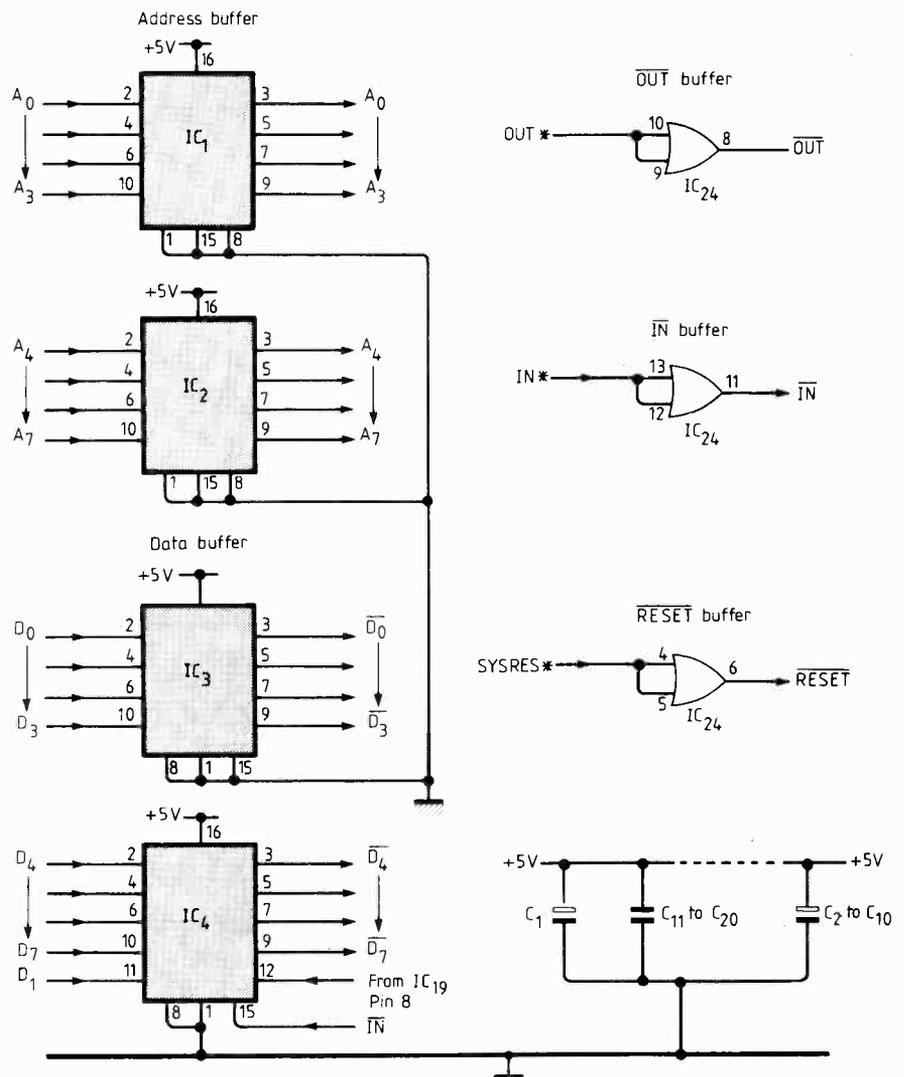
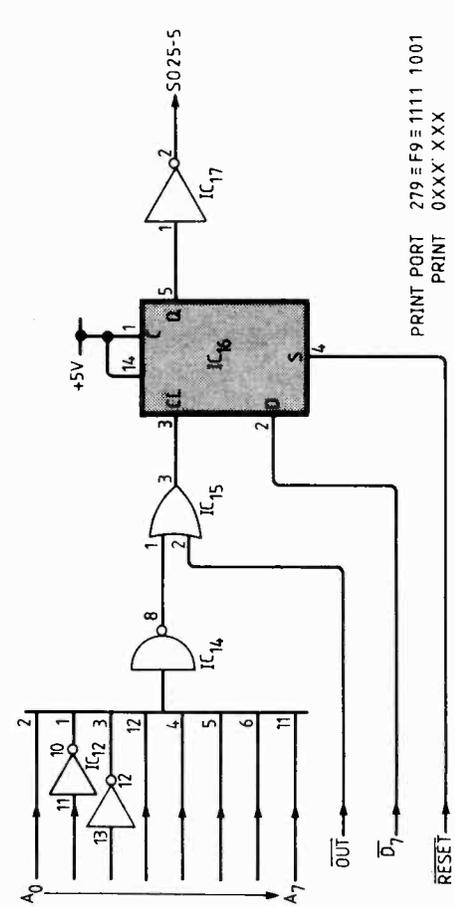
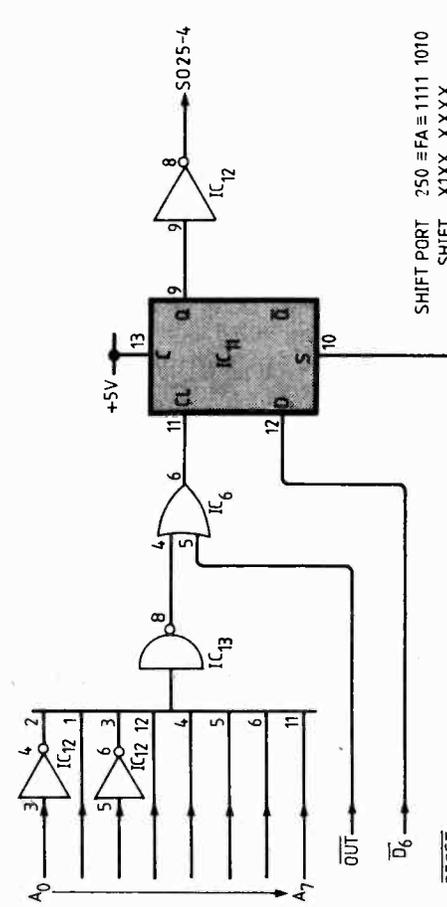
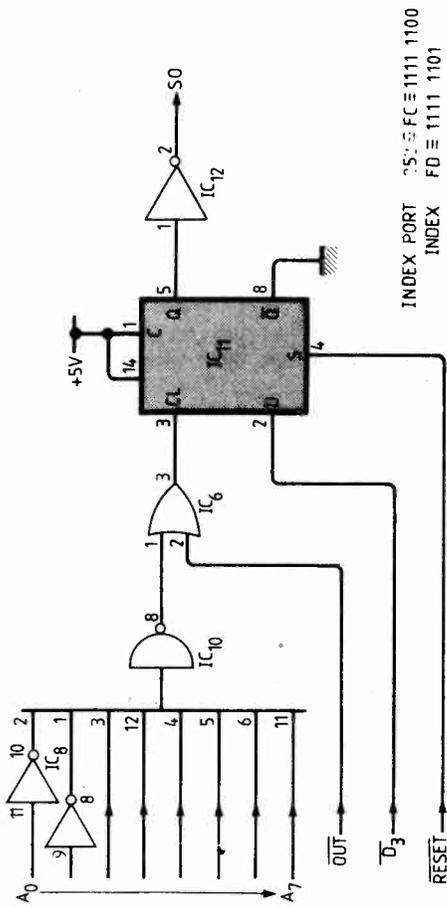
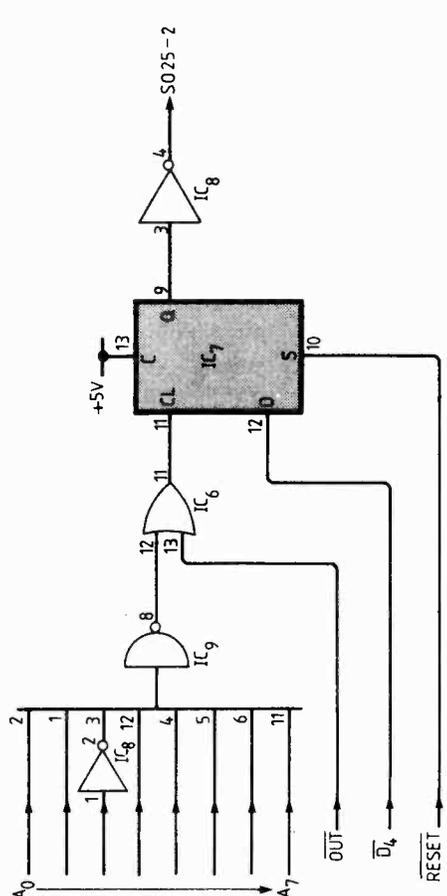


Fig. 1. Buffer i.cs interface the expansion port of the TRS80 to the printer driver circuits. They increase the drive output from the computer and help keep any problems occurring in the driver from reaching the computer. Also shown are the bank of capacitors distributed around the board for filtering and de-spiking, a necessity for t.t.l. integrated circuits.

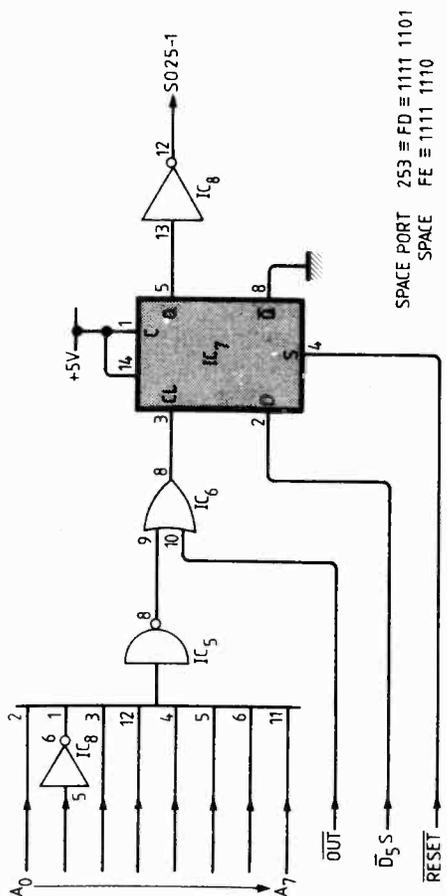*Using five-level teleprinters with a TRS80; by Brian Bateman, *Microcomputing*, Jan, 1980.
†Tandy in the UK.




Figs 2-6: Space port decoding, circuit Fig. 2 top left, drives the space solenoid. Eight address lines along with the OUT* signal give a specific port address. Low signal on the single data line is passed to the output when the port is addressed. Carriage return port decoding circuit Fig. 3, bottom left, drives solenoid that produces a carriage return. Index port decoding circuit Fig. 4, top right, drives index or line feed solenoid. Shift port circuit Fig. 5, centre right, is configured to decode signals to drive the shift solenoid for upper case. Print port circuit Fig. 6, right, decodes the signal to drive the print solenoid.

at the same time the OUT* line goes low. In Fig. 2, a space was given the hex number, FE, which is 1111 1110 in binary, of which bit five is 1. FE in the A register so what happens is this: when that instruction is encountered, first the address FD in the C register goes out on the address bus. So the output of the eight-input gate goes low. Then the data FE in the A register goes out on the data bus, and we pick up D5* (bit 5) which has been inverted by IC₄ and present it to the D input of a D flip-flop, as you can see from Fig. 1. (There was no real reason to use bit 5; I just needed a 1 here.) Then the OUT* line goes low, and as this line is connected to one input of an or-gate and the output of the eight-input gate is connected to the other the output of this or-gate goes low. Now the 74LS74 flip-flop transfers any level on its D input to its Q output when its clock input goes from low to high. So after a short time the instruction is finished and the OUT* line goes back high and thus causes the or-gate to go back high and the 0 on the D input gets put onto the input of the inverter just before all the data disappears. So that little bit of data has been saved or latched by the D flip-flop and can now be used to good purpose: to cause the output of the inverter to go high, which thus turns the driver transistor on and pulls in the space solenoid. Of course, if the solenoid stayed pulled in, all we would get would be spaces, so the assem-

Parts list

- IC1, 2 74LS367 hex 3-state buffer
- IC3, 24 74LS368 hex 3-input inverter buffer
- IC4, 6, 15 74LS32 quad 2-input or-gate
- IC8, 12, 17 19 23 74LS04 hex inverter
- IC5, 9, 10, 13, 14, 18, 20 74LS30 8-input nand-gate
- IC7, 11, 16 74LS74 dual D-type flip-flop
- IC21, 22 74LS175 quad D flip-flop
- IC25 LM3900 quad Norton op-amp
- Tr₁ to Tr₁₁ n-p-n transistor (RS2018)
- R1 R11 100Ω
- R12, 14, 17, 22 10kΩ
- R13 47kΩ
- R16 150kΩ
- R18, 19, 20 1MΩ
- R21 12kΩ
- R15 330Ω
- R23 100kΩ p.c.b. control
- C1-10 10μF 35V electrolytic
- C11-29 50nF ceramic
- C30, 31 4.7μF 35V electrolytic
- C32 10nF ceramic
- SO1-19 14-pin wire-wrap sockets
- SO20-27, 16-pin wire-wrap sockets
- SO28 22-pin dual edge-card socket
- Experimental p.c. board
- 16-pin DIP jumper cable
- 4x8 1/2 in. i.c. perforated board
- TRS80 edge connector
- IBM parts list**
- Selectric I/O typewriter, model 745
- Service manual, no.241-5737-0 (\$9.40)
- Adjustment parts manual, no.241-59990-0 (\$4.10)
- Parts No./Price list, Form No.S241-51558-4 (\$0.55)
- Cycle tool, part no.9900427 (\$0.60)
- Gauge, part no.9900575 (\$11.50)
- Typing element ANSI-OCR-B, part no.1167185 (\$18)

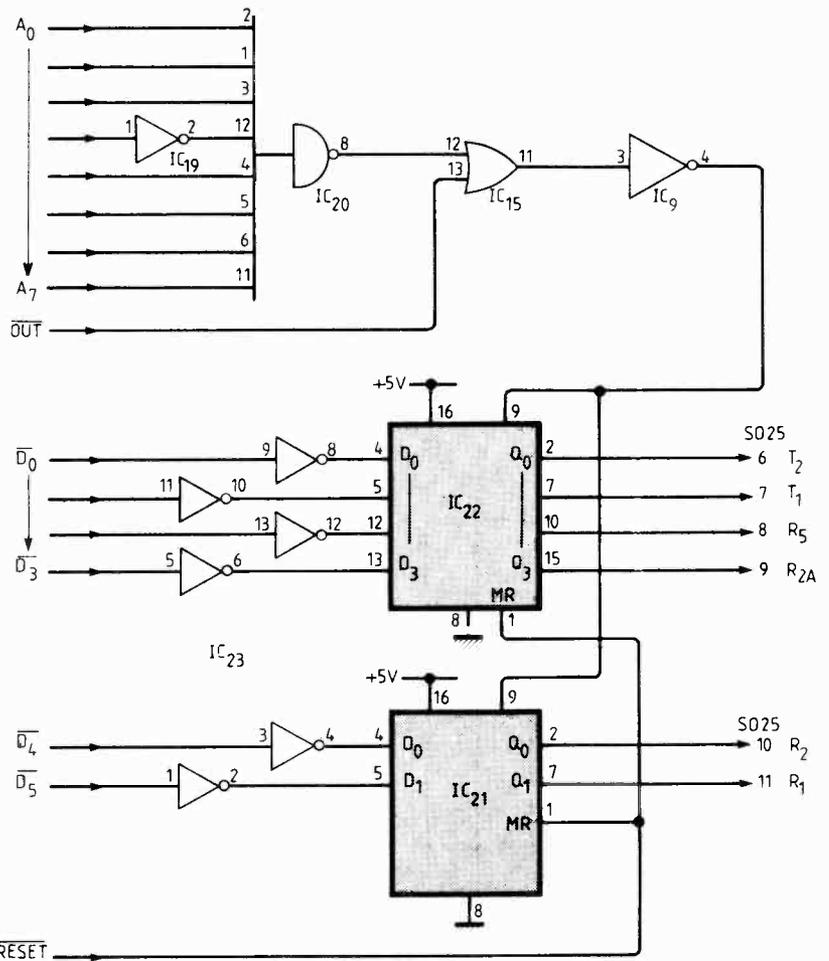


CHARACTER PORT 247 ≡ F7 ≡ 1111 0111
 CHARACTER 0XXX XXXX

Fig. 7. Character port circuit accepts more than one data line. The seven address lines are decoded for port number F7H. When this port is addressed, the signals on the six data lines are sent to the character driver solenoids. A six level or correspondence code is used to determine the character to be printed.

bly language program has some timing to do and also some unlatching, but we'll get to that shortly.

This is about the simplest way for your computer to communicate with the outside world in a structured way. Fig. 3 to 6 are similar except for the address decoding and the input and output connections. Fig. 7 shows the character port and is very similar to the others but has six data inputs and will drive all the character select solenoids at the same time. One of the ques-

tions I had about driving transistors was whether these latches could drive a power transistor directly. The fan out for these 74LS175s is the same as an inverter, and I haven't had any drive problems at all. Fig. 8 is the carriage movement port. When this port is addressed, and the output of the carriage movement detector is low, and the IN* line is low, a high is sent out on D1, thus nothing happens. However when the carriage is moving, a low goes out on D1, which is detected by the program, and

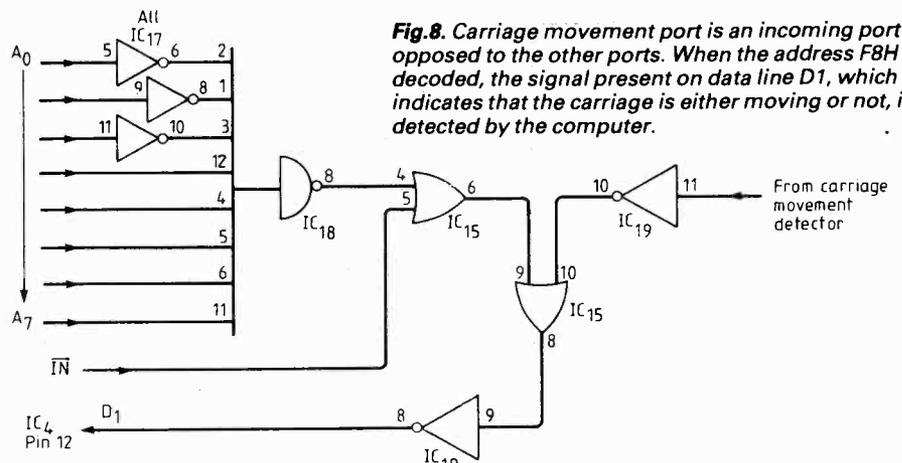

CARRIAGE MOVEMENT PORT 248 ≡ F8 ≡ 1111 1000
 CM OUT XXXX XX1X

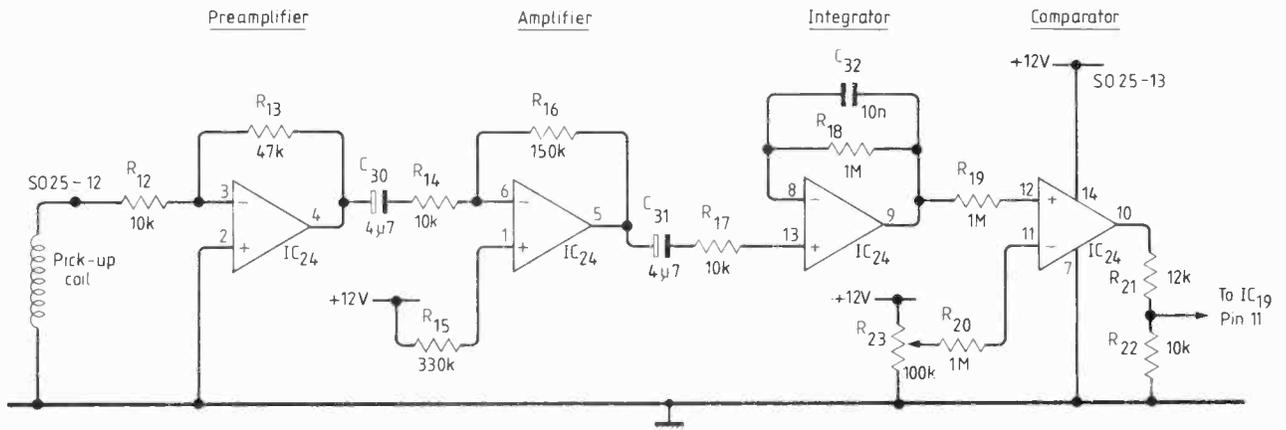


Fig.9. Carriage movement detector circuit produces a high or low level depending on whether the carriage is moving or not. See text for explanation of its operation.



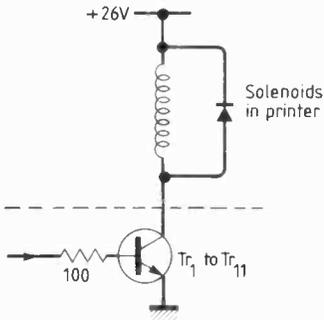


Fig. 10. Each of the eleven solenoids are driven by this transistor driver.

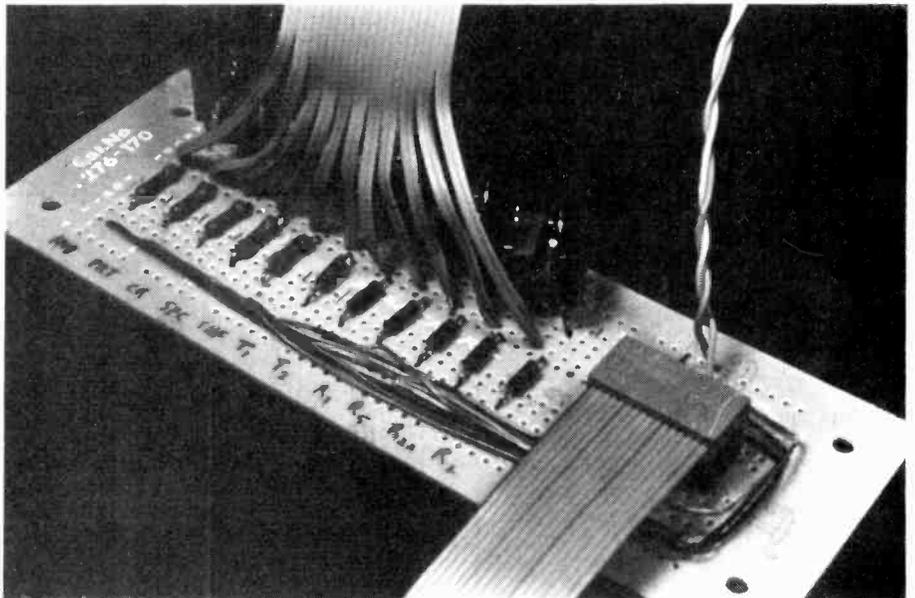

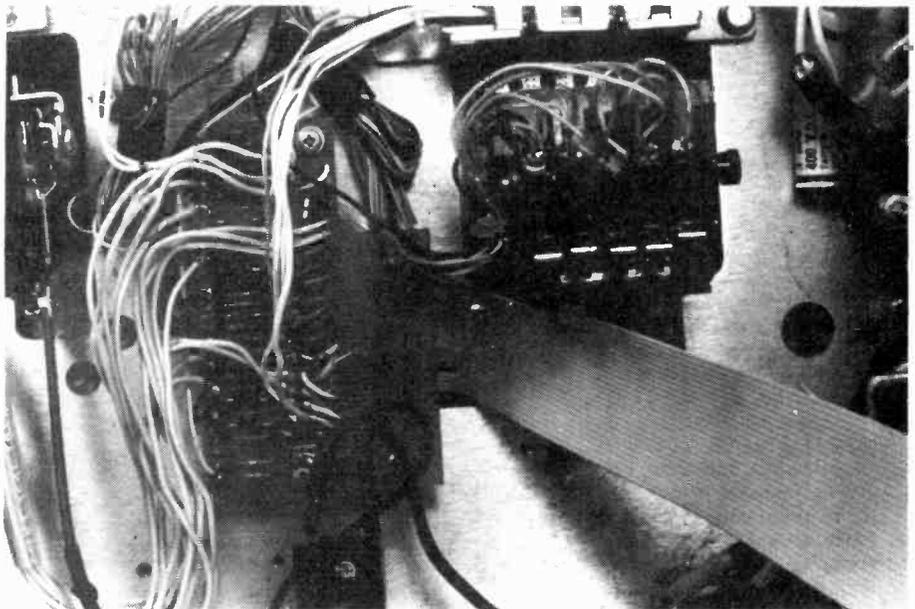
5. In the driver transistor board the ribbon cable going off toward the top goes to the diode board in the printer, the other ribbon cable to the interface board. The twisted pair is for power.




6. Diode board inside the printer already had diodes connected across the solenoids, and this saved installing them on the driver board. If this board is missing on your unit, you must install diodes across the solenoids to protect the transistors.

Table 1. Computer to interface cable


RS-PIN	Signal	44-pin
1	RAS*	1
2	SYSRES*	A
3	CAS*	2
4	A10	B
5	A12	3
6	A13	C
7	A15	4
8	GND	D
9	A11	5
10	A14	E
11	A8	6
12	OUT*	F
13	WR*	7
14	INTAK*	H
15	RD*	8
16	MUX	J
17	A9	9
18	D4	K
19	IN*	10
20	D7	L
21	INT*	11
22	D1	M
23	TEST*	12
24	D6	N
25	A0	13
26	D3	P
27	A1	14
28	D5	R
29	GND	15
30	D0	S
31	A4	16
32	D2	T
33	WAIT*	17
34	A3	U
35	A5	18
36	A7	V
37	GND	19
38	A6	W
39	+5v	20
40	A2	X

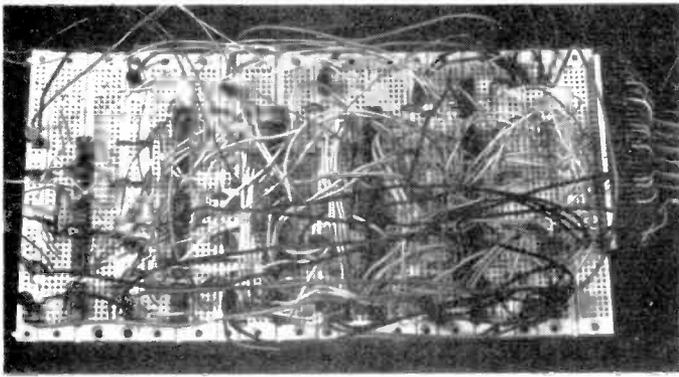

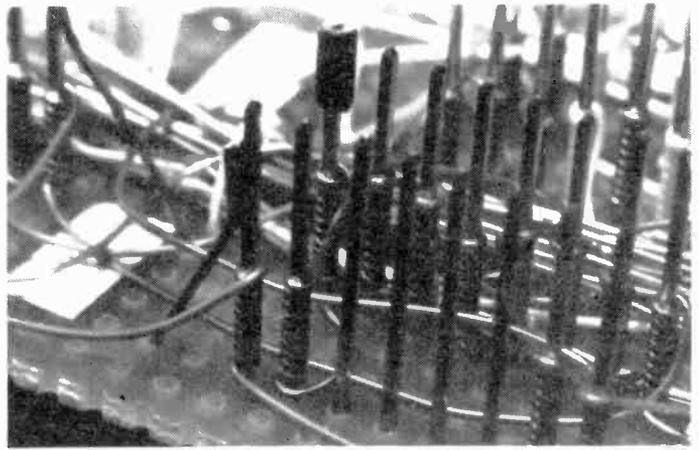
7. This shot shows the original breadboard during the design stage of the interface. If the circuit works like this, it will definitely work when it's neat!



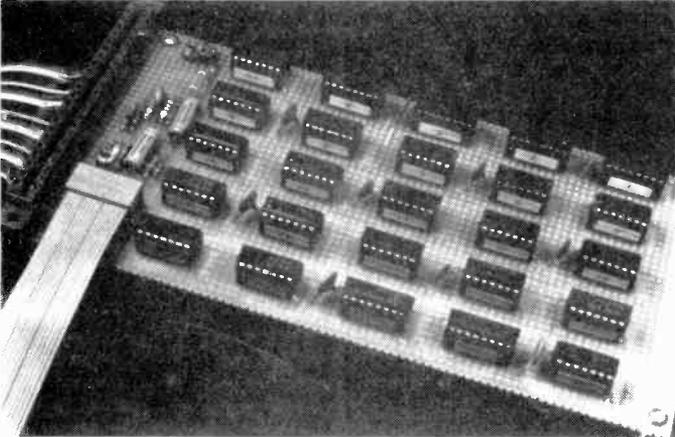9. Wirewrapping method is good to use when doing a one-off board using a lot of i.cs. I used wire that doesn't need to be stripped first: the process of wrapping cuts the insulation.



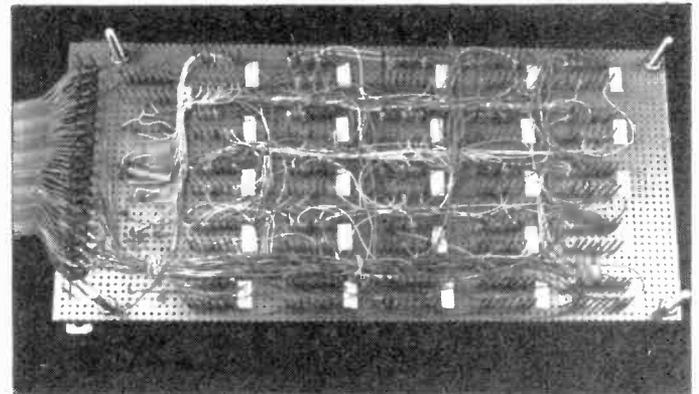8. This is what the completed interface board looks like. All the i.cs are numbered, and there is a connector available for future expansion. The ribbon cable coming off the bottom goes to the driver transistor board, and the other goes to the computer.



10. This is what the bottom of the completed wirewrapped board looks like. All the i.cs are numbered, and four different coloured wires are used, blue for ground, red for +V and white and yellow for the signals.

Photographs: Anthony and Bonnie Scarpelli

causes a delay loop to hold up the program. We'll get into the program shortly to see how this works exactly.

The carriage movement detector, Fig. 9, is one i.c. long, using a quad LM3900 op-amp. The detector coil is connected to an amplifier that picks up the small sine wave produced by the gear which revolves whenever the carriage is in motion. A second amplifier produces a square wave which then goes into an integrator and gives a d.c. level output. This level is detected by a comparator to produce a t.r.l.-level output to the input of an inverter. A small potentiometer on the negative input of the comparator adjusts the trigger level. If you don't have a small control, two fixed resistors can be used after you have found the right ratio.

The only hardware left to discuss are the driver transistors. Fig. 10 shows what is in the printer, and also how the driver transistor is connected into the system. A 25V transformer, rectifier, and capacitor is all that is needed to power the solenoids. The driver transistor board is simple to construct, and has a connector on it that goes to the interface board. Plus 12 volts goes to this board for the carriage movement de-

tor. The ribbon cable goes out to a connector, which then goes to the diode board in the printer. This diode board, photo 6, has all the wiring that goes to the solenoids, and my ribbon cable goes directly to it. The +25V supply which is more like 35V out of the unloaded power supply, is also connected to this board.

Interface board construction

Transistor-transistor logic is very noisy to work with and the kind of construction used in my original breadboard, Fig. 1 doesn't help. Cute, and all we need is a little tomato sauce. But if you can get it to work like this, you have a better chance of it working in the final version. Although I installed a number of capacitors on my semi-final version, I had to put on a whole bunch more so that practically every i.c. had a 50nF connected to its power connections, plus some 10 μ F on each power bus. I probably overdid it, but it is a very quiet board now, and all wirewrapped. The sockets were stuck on the board with hot-met glue and all numbered, both on the sockets themselves, and on the bottom of the board. All pin 1s were given a small piece of wire insulation for identification. This is very helpful when wirewrapping

during those late and wee hours of the morning. I wirewrapped with the OK tool that eliminates stripping the wire, and really speeds up the process, photo 9. You can only wrap two levels due to the height of the recommended eight wraps. But this is sufficient, and the redundancy increases the reliability of the wrap; I have yet to find a bad wrap after hundreds of pins.

The board as shown in photo 8 shows the completed interface. It holds 25 sockets and the motion-detector components. The cable from the computer is soldered to a 44-pin connector with wirewrap pins (see Table). The cable is the only component that I didn't get from Radio Shack, but can be purchased from Hobby World, (see parts list). I used the 44-pin connector because they are easy to get, and also this will allow me to add various peripherals and more memory to the system by building a motherboard and connecting it to this single connector. You can see in photo 10 bottom of the completed board, a little more organized, but it still could use some sauce.

To be continued with assembly language program.

NEW PRODUCTS

WINCHESTER DISC CONTROLLER


Designed for many of the popular Winchester interfaces, the Intel 82062 controller translates parallel data from a microprocessor to a 5Mbit/s m.f.m. encoded serial bit stream. It also provides the drive control logic and control signals, and integrates much of the logic needed to implement a Winchester disc control subsystem.

The 82062 is controlled by the host c.p.u. with six high-level commands: Restore, Seek, Read Sector, Write sector, Scan i.d. and Write format. It can transfer multiple sectors and operates in 128, 256, 512, and 1024-byte sector lengths. It has a 7-byte sector length extension for external error correction. All this is housed in a standard 40-pin d.i.p. and operates from a single 5V power supply. MEDL Distribution, East Lane, Wembley, Middlesex HA9 7PP.


WW301

CAESIUM FREQUENCY STANDARD

Accuracy of 3 in 10^{11} is claimed for the FE-5440 caesium beam primary frequency standard. It uses a comparison-and-control system in which a caesium transition frequency (9.19... GHz) is used to stabilize the output frequency of a voltage controlled quartz crystal oscillator of 14.59... GHz. The synthesizer permits instantaneous setting of frequency to within 2×10^{-12} . Rugged construction ensures that it meets military standards for reliability, test, construction and r.f.i., and the modular approach means that any module may be changed within 15 minutes. The caesium beam tube lasts for at least three years.

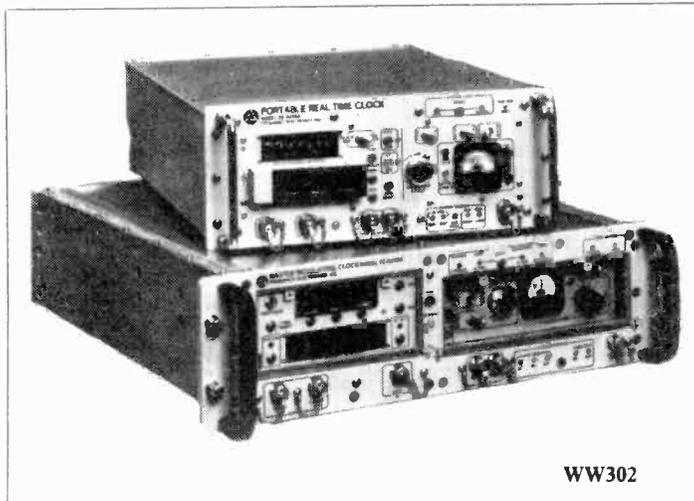

WW302

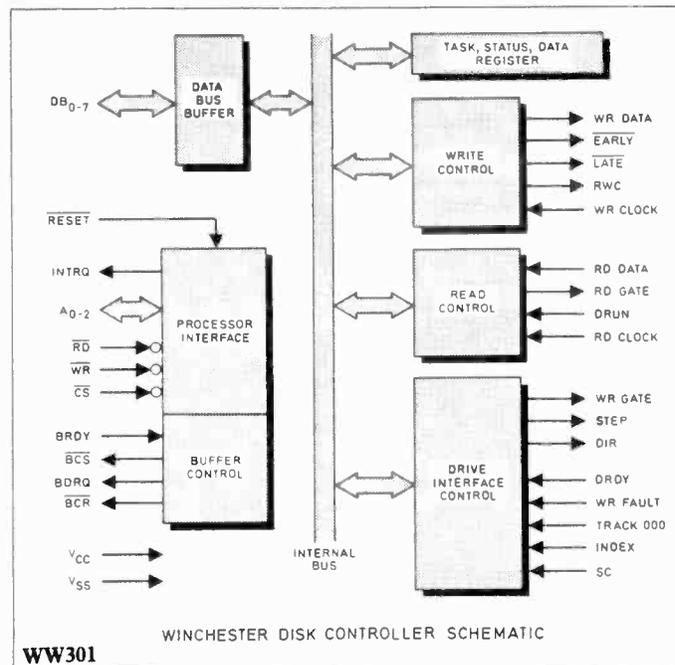

WW301

The instrument is also provided with a time clock to give hours, minutes and seconds with seconds and minutes pulses which may be output to drive external clocks. Other outputs are standard and sinusoidal frequencies of 5MHz and 1MHz and a square-wave output of 3MHz. Wessex Electronics Ltd, 114-116 North Street, Downend, Bristol BS16 5SE.

WW302

SOLDER FUME EXTRACTOR

Solder fumes can cause respiratory problems so it is important that they should be kept away from the faces of those people who are continually using soldering irons. The Adcola Polysorb MK2 incorporates twin variable-speed fans to draw the fumes away from

an operator and pass them through an active charcoal filter. As a bonus the unit also provides a controllable light and an output socket for power, either 240 or 24V.

The unit is metal with steel support poles to attach it to the bench. It runs on a.c. mains rated at 240V. Adcola Products Ltd, Adcola House, Gauden Road, London SW4 6LH.

WW303

MANUALS PREPARED

Having a good product to market isn't necessarily the end of the road. Presentation is also important and this includes technical literature and manuals. Woodcote Technical Services specialize in the production of technical manuals for the instruction and training of machine operators and fitters. Their service includes technical illustrations, sales literature and


other literature for mechanical, electrical and electronic equipment.

Woodcote aims to provide the end user with a full appreciation and understanding of the often very complex equipment he has just purchased. To do this it is necessary to improve the effectiveness of the information required rather than merely recording it. Good illustrations should be supported by a minimum of clear, concise text, a principle that is often ignored in technical manuals. Woodcote Technical Services, Bramshott House, 139 High Street, Epsom, Surrey KT19 8EQ.

WW304

DECOUPLED ANTENNAE

A radiation pattern that is absolutely horizontal and not 10-15° above the horizon is claimed for the AEA Isopole omnidirectional antennae which are used in the 2m and 70cm bands. The reason for this achievement is the feed line decoupling system with cones that prevent any radiation from the feed line. This means that distant f.m. transmitters and repeaters can be reached which would otherwise require a very large vertical omnidirectional or a beam antenna. Two models are available: the

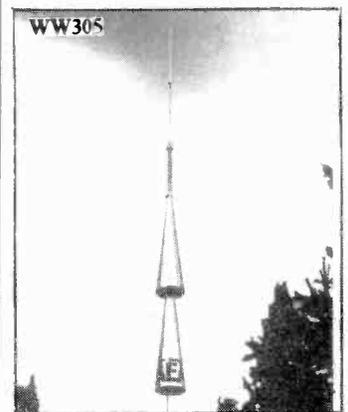

WW305



WW303

Isopole 144 and the Isopole 440 which cost £32.50 and £49.00 respectively, including v.a.t. ICS Electronics Ltd, PO Box 2, Arundel, West Sussex BN18 0NX. WW305

DVM EVALUATION KIT

To permit prospective customers to evaluate the capabilities of the ZN451 digital voltmeter, Ferranti have produced an evaluation kit.

The monolithic d.v.m. has a facility whereby external components may be included into the auto zero loop; output signals are provided to control external auto zero switches so that op.amps or other signal conditioning circuits can be included in the loop to boost input impedance or improve sensitivity down to 1.999mV full scale. The kit and further details are available from Ferranti Electronics Ltd, Fields New Road, Chadderton, Oldham, Lancs OL9 8NP.

WW306

COMPUTER CONTROL FOR £170

Chum One comes with its own operating system, keyboard and alphanumeric one-line display. It may be programmed in Basic or in Z80 machine code to provide machine control or data logging and it may be used in education.


The standard unit consists of four analogue inputs, one analogue output, 16 programmable digital inputs/outputs, four programmable timers/counters, a serial digital input and a serial digital output. Up to 6K of non-volatile ram is provided and the function of the computer can be altered instantly by inserting a programmed eprom into the external top socket. Programs and data can be loaded or saved on cassette tape through the serial input/output. Warwick Design Group, 12 St George's Road, Leamington Spa, Warwick CV31 3AY.

WW307


THICK-FILM LOW PASS FILTERS

A range of audio-band low-pass filters have been designed by Toko for use with digital audio equipment. The PAL0900 series are all 20kHz active filters which are intended to optimise the phase response from p.c.m. coded digital audio discs. They are available with a variety of terminating impedances and with stopband attenuations up to -95dB. Ambit International, 200 North Service Road, Brentwood, Essex CM14 4SG.

WW308

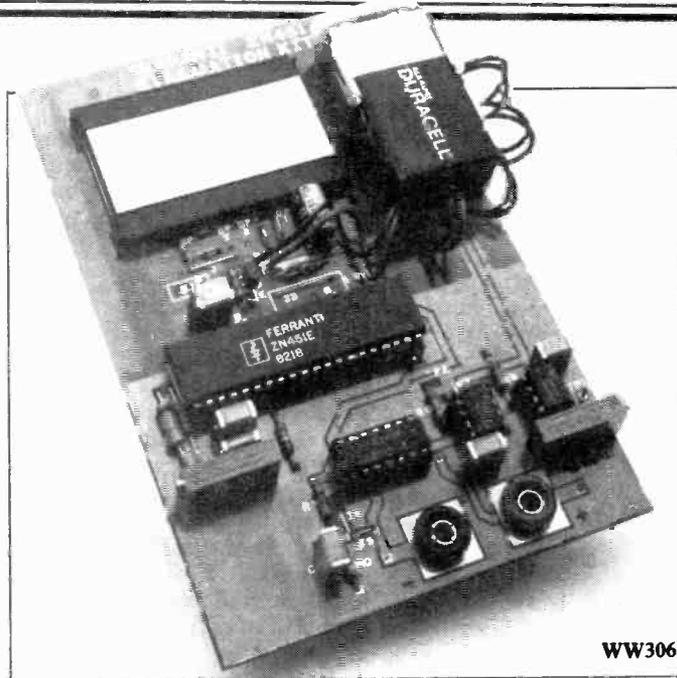

WW306

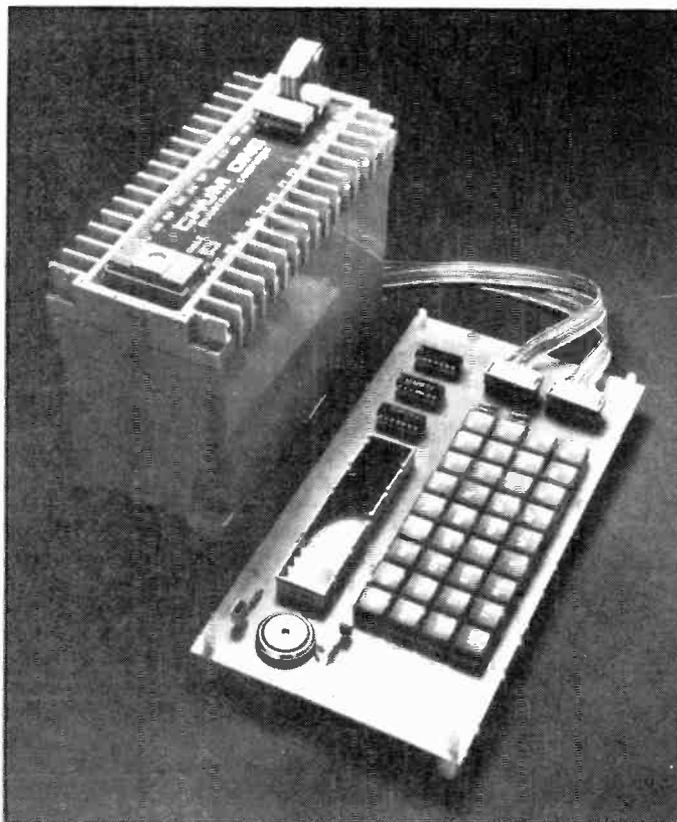

GRAPHICS GENERATORS


Designed to be adapted to almost any 8 or 16-bit microprocessor the GVP (for Graphics Video Processor) 65 is a single board circuit which can generate a 512x512 pixels display interlaced or 256x256 non-interlaced. It can plot at up to 1,500,000 dots/s, can generate ASCII character which may be tilted or changed in size and pictures may be coloured using 4,913 pre-programmed colour patterns. The commands include pen/eraser selection, pen/eraser up or down, clear screen, light pen handling instructions, memory access and writing, block drawing in different sizes, vector drawing, colour and intensity selection, colour mapping, mixing and removing, characters or figures may flash on and off and there are synchronizing and configuration commands.

GVP 65 generates t.t.l. compatible RGB, B/W and composite sync video signals. Many GVPs can be synchronized together to build up a picture image. Greatech Electronics Ltd, Hay Lane, Braintree, Essex CM7 6ST.

WW309

SCREW STARTERS

One of the bugbears of assembly and maintenance of electronic equipment is the limited access to the screws that hold it together. We can usually get them out, but the difficulty is in re-assembly. Screw starters which can grip the screw

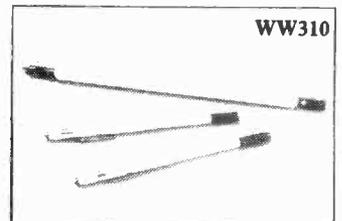

WW310

while it is being positioned are very useful and three are available from Toolrange. The D2 is for slotted screws, the PD-10 for cross-slot (Phillips) heads. These are both pocket-sized with a pen-clip. The D-1 is longer and double-ended for both slotted and Phillips heads. Toolrange Ltd, Upton Road, Reading, Berks RG3 4JA.

WW310

If you would like more information on any of the items featured here, enter the appropriate WW reference number(s) on the mauve reply-paid card.

RANDOM ECHOES

By Chirp

WORDS

I dare say we all use certain words without bothering too much about their meanings. They sound right and seem to fit the context and, indeed, fall into common usage; yet sometimes the accepted meaning is far from that given in the dictionary.

The most useful ones are not in the dictionary at all, and they can be given any meaning that happens to be appropriate. Take the noun "snodgett", for example. Do you know what a snodgett is? No, of course you don't, but it is a very handy universal word to use as the name of almost anything when you can't think of what to call it.

A snodgett on your car chassis gets in the way of your spanner when you are struggling with the nut that holds your broken exhaust pipe. Or, in contrast, the are four quite handsome snodgetts on the ornamental wall clock over our fireplace. And again, there is the snodgett in a video amplifier's frequency response that causes overshoot on a fast rise pulse.

It's a very handy word, "snodgett". I strongly recommend that you take it into your vocabulary and use it wherever you get stuck for a suitable noun. Eddie Spinks has a universal adjective, "hydrofluvious", but I think it sounds a bit pompous.

However, it was not the non-dictionary words that prompted this literary outburst so much as the misuse of well-established words. In particular, have you noticed how the word "sophisticated" is now fashionable as a kind of universal adjective to imply some degree of vague cleverness associated with its subject. It appears in all kinds of technical sales literature and even in serious technical articles. We frequently read of sophisticated techniques, circuits, machines and the like. And I must confess to having used the word myself in such context without really appreciating its meaning. But, being a bit of a pedant, when I realized my ignorance I looked up the word in the Concise Oxford Dictionary. The entry reads:

Sophisticate (v. t. & i.) involve in sophistry; mislead thus; deprive of simplicity; make artificial (p. p.) worldly-wise; adulterated (wine, etc).

Not very nice, is it? I see now why these "very sophisticated" computer systems often seem to be full of anomalies, using advanced technology (whatever that means) to achieve results that seem utterly inconsequential. Are they actually intended to mislead? And, as for these "highly sophisticated" weapons that we read about — one wonders whether they are designed to deceive the enemy or the chaps at the sending end. Probably the only one to be deceived is the fool who looks up the word in the dictionary. Everyone else assumes a meaning relating

to cleverness of design, which is just what the authors intend.

WORDS AND MUSIC MAESTRO

They're at it again with gimmicky automobile electronics. This time it's not an entirely Japanese venture but the new British Leyland Maestro. I overheard a fragment of a television programme the other day in which there was a short piece of leaked information about this car, which, I gather, has not even been announced under the Maestro name yet.

Anyway the programme included a statement that the more superior versions would feature an audio readout of dashboard information. Do we call this a "Speakout"? This feature is, of course, in addition to such refinements as electric windows and remotely controlled door mirrors.

As I understood the announcement, the car will speak out such information as speed, fuel level, engine temperature etc., but the report was brief and gave no information about the way in which the driver interrogates the system.

Perhaps no interrogation is necessary. Perhaps the thing is programmed to blurt out the information at preset intervals or when an alarm situation occurs; e.g., "We're nearly out of petrol!" Perhaps it announces the speed as each decade multiple m.p.h. is reached — either accelerating or decelerating. If so, it could be quite dramatic when you have just pulled out of a lay-by and you are trying to reach the speed of the traffic before the dual carriageway peters out.

In the report that I heard, there was no mention of a microprocessor, but you may be sure that the whole system depends on at least one of these devices. No modern electronic system amounts to much without one. So we are naturally led to speculate on the conversational ability of the car of the future as more-and-more data processing power is compressed into smaller-and-smaller devices.

I read quite recently about a Japanese heavy goods vehicle with solid-state television cameras mounted at "blind" locations on the truck body and a c.r.t. in the cab to augment the conventional rear-view mirrors. We also read of computer programmes for interpretation of the signals from t.v. cameras to exact meaningful information and act upon it. At present such systems are confined to the field of metrology and machine-tool control, but who knows what the future may bring.

With the general trend towards the use of high technology for totally frivolous purposes, it is possible that the techniques mentioned will one day be combined to enable the car itself to utter those helpful comments currently made by ones pas-

sengers; e.g., "All clear left . . . if you're quick", "That's a police car you're overtaking" and "Why is that fool dripping with water shaking his fist?"

Such technical developments could ultimately do away with the need for passengers altogether, and one could, perhaps, look forward to the optional electronic "hitch-hiker" which gives an authentic account of all the lifts he's ever thumbed while you are trying to listen to the test match commentary on Radio 3.

GETTING THE MESSAGE

One of the advantages of the printed (as against spoken) word is its immunity to the effects of mispronunciation, extraneous noise, imperfect hearing and, in the case of telecommunications, frequency limitations and distortion.

I was not surprised to read, therefore, about a miniature alphanumeric terminal, complete with keyboard, v.d.u. screen, and printer, for use with mobile radio. The article said it is for applications where integrity of the message is very important. It offers most of the advantages one associates with the telex, and perhaps it is another step in a trend towards transmission of written information rather than relying on speech.

It is bound to be more reliable because the transmitted signal is so much simpler. When you come to think of it, spoken language is an extraordinarily complex way of communicating, even by comparison with the arbitrary shapes of the letters in our alphabet. In the face-to-face conversational environment the sounds are supported by facial expression and gestures, which are inevitably lost in sound-only transmission. So, for communication of information, as distinct from emotion, the trend is to the Telex and Teletext and Viewdata.

Or is it? I've just read a feature about computer controlled voice recognition systems and electronic speech synthesizers. This is really high technology stuff, where the human operator speaks to the machine and the machine talks back. I must admit that the voice recognition systems described were mainly concerned with access-control applications and carcase grading in an Australian abattoir. But the prediction was the development of voice operated data terminals, where you interrogate the computer verbally and its synthetic voice answers.

If the computer misunderstands your accent, no doubt it will ask you to "spell it out" using the approved phonetic alphabet. And if you misunderstand, I recommend you call for a print out — unless, of course, you are using the telephone, when it will probably end up with smoke signals.



THE SOURCE....

of all good used test equipment

Electronic Brokers are Europe's leading Second User Equipment Company. We carry large stocks of the very latest test equipment which is refurbished in our own service laboratories and calibrated to meet the manufacturer's sales specifications. When you buy used equipment from Electronic Brokers, it can be yours in just days. No waiting for manufacturers lengthy production schedules. All equipment is fully guaranteed.

ANALYSERS

- Jranetz**
306-3 Line Disturbance Monitor **£2500.00**
- Hewlett Packard**
I41T/8552B/8554B. 100KHz-1250MHz **£7800**
I41T/8552B/8555A 10MHz-18GHz **£9300.00**
- 3582A Spectrum Analyser 1.02Hz-25.5KHz **£6350.00**
3004A Signature Analyser **£550.00**
3420A Digital Signal Analyser c/w Digital Filter 54470B, A/D Converter 54410A **£21,000.00**
3407A/8412A Network Analyser **£1950.00**
- 3444A Tracking Gen. For use with 8554B **£2100.00**
- 3558B Spectrum Analyser 100KHz-1.5GHz **£4500.00**
- Marconi**
TF2337 Automatic Distortion Analyser **£250.00**
- Solartron**
1172 TFA **£4000.00**

Fluke
8022A 3 1/2 digit 0.25%
Basic DC Accuracy 6 functions **£60.00**

8020A 3 1/2 digit
0.1% Basic DC
Accuracy
7 functions. **£75.00**

THESE DMM'S
ARE UNUSED

90 DAY
WARRANTY

OSCILLOSCOPES

- Hewlett Packard**
1332A High Quality CRT Display 9.6 x 11.9cm **£1250.00**
1720A Dual Trace 275MHz with Delay T Base and probe power **£2500.00**
1809A 100MHz 4 Channel Plug In **£2000.00**
1821A Timebase Plug In **£1000.00**
- Philips**
PM3232 Dual Beam 10MHz **£495.00**
PM 3234 True Dual Beam Storage Oscilloscope 10MHz New CRT. **£1500.00**
- Tektronix.**
213 Miniscope/DMM Battery 1MHz **£975.00**
305 Portable battery scope/DMM, D T 5MHz **£975.00**
335 Dual Trace 35MHz Small portable with delay T Base **£1200.00**
468 Dual Trace 100MHz with Digital Storage (10MHz) Delay T Base **£4950.00**
475 Dual Trace 200MHz Portable **£2200.00**
T922-01 15MHz DT Scope Diff. input **£515.00**
200C Trolley for 400 Series **£120.00**
7313 100MHz Storage Mainframe **£2225.00**
7603 100MHz Mainframe **£1450.00**
5223 Digital Storage 10MHz **£2000.00**
5440 50MHz Mainframe **£1000.00**
5441 50MHz Variable Persistence Storage Mainframe **£1600.00**
7104 1GHz Scope Mainframe **£11,500.00**
7704A Scope DC-200MHz Mainframe **£1950.00**
7613 Storage Scope Mainframe DC-100MHz **£2600.00**
7639 Multimode Storage Scope Mainframe DC-100MHz **£4500.00**
7834 Storage Scope Mainframe DC-400MHz **£7000.00**
7844 Dual Beam 400MHz Mainframe **£7750.00**
7854 Waveform Processing Scope DC-400MHz **£8250.00**
7904 opt 02, 03 500MHz **£5350.00**
S1 Sampling Head. As New **£450.00**

- Teleguipment**
DM63 Storage Oscilloscope Fitted with 2 x V4 Plug-ins to give 4 Trace 15MHz **£1350.00**
D1016A Dual Trace 20MHz 'As New' **£350.00**

SIGNAL SOURCES

- Hewlett Packard.**
608E 10-480MHz. AM or Pulse Modulation. Output 0.1µV-1V **£1000.00**
612A 450-1230MHz. AM or Pulse Modulation. Output 0.1µV-0.5V **£1500.00**
616B 1.8-4.2GHz int or ext PCM/FM 0.1µV-0.224V **£1000.00**

- 651B Test Oscillator. 10Hz-10MHz. 0.1mV-3.16V **£415.00**
3320A Frequency Synthesizer. 0.01Hz-13MHz **£995.00**
8690B Sweeper Mainframe with 8698B Plug In. 0.4-110MHz **£4000.00**

- Marconi.**
TF2009 20Hz-20KHz Low Distortion with 0-111dB Attenuator in 0.1dB steps **£575.00**
TF2002B with TF2170 Synchronizer 10KHz-88MHz AM/FM Modulation **£1700.00**
TF2120 0.0008Hz-100KHz Waveform Generator **£900.00**
TF2008 AM/FM 10KHz-510MHz built in sweeper. Output 0.2µV-200mV **£3500.00**
TF2016A + TF2173 Synchroniser AM/FM 10KHz-120MHz **£2000.00**
TF2169 Pulse Modulator for use with TF2015 or TF2016 **£200.00**

- Philips.**
PM6456 Stereo Generator. **£250.00**
- Racal**
9081 AM, FM, Phase and Pulse Synthesized 5-520MHz **£2200.00**

- Radiometer**
SMG1 Stereo Generator **£375.00**

TEKTRONIX PLUG INS

We stock a complete range of Plug Ins for use with 7000 and 5000 Series Mainframes.

TEKTRONIX TM500 SERIES

- AF501 Bandpass Filter/Amplifier **£400.00**
AM501 Op Amp Gain 10,000 **£300.00**
AM502 Diff. Amp Gain 1-100K **£500.00**
DM502A True RMS 3 1/2 digit DMM **£250.00**
DC503A 125MHz Counter **£450.00**
DC505A 225MHz Counter **£600.00**
DC508A 10Hz-1.3GHz 9 Digit **£900.00**
FG501 Function Generator 0.001Hz-1MHz **£375.00**
FG501A Function Generator 0.002Hz-2MHz **£425.00**
FG502 Function Generator 0.1Hz-11MHz **£425.00**
FG503 Function Generator 1Hz-3MHz **£275.00**
FG504 Function Generator 0.001Hz-40MHz **£1250.00**
PG505 Pulse Generator 1Hz-100KHz **£450.00**
SC502 15MHz Dual Trace Scope **£1000.00**

- SC504 80MHz Dual Trace Scope **£1250.00**
SG503 Sinewave Generator 250KHz-250MHz **£950.00**
TG501 Timemark Generator **£950.00**
TM515 Mainframe [5 wide] **£350.00**

TEKTRONIX TV TEST EQUIPMENT

- 141A PAL Test Signal Generator **£1750.00**
148 PAL Insertion Test Generator **£4000.00**
1485C PAL/NTSC Dual Standard Waveform Monitor **£2950.00**
651HR 12" PAL Colour Monitor [Mint] **£3250.00**
655HR-1 TV Colour Picture Monitor [NTSC + PAL + RGB] **£3800.00**
656HR PAL/SECAM Monitor **£3900.00**
1411R TV Generator. Various Systems available **POA**

MISCELLANEOUS

- Bruel & Kjaer**
2209 Sound Level Meter **£975.00**
- Ferroglyph**
RTS1 Test Set **£295.00**
- Fluke**
515A Portable Calibrator DC/AC and Resistance with DC Resolution 0.2µV **£1750.00**
883 AC/DC Differential **£615.00**
845 AB Null Detector **£610.00**
3010A Logic Tester. Self Contained. Portable. Full Spec. on Request **£8500.00**

- Hewlett Packard.**
5340A Counter 10Hz-18GHz 8 Digit **£3750.00**
8403A Modulator Fitted With 8732B PIN MDDULATOR **£1500.00**
8482H Power Sensor 100KHz-4.2GHz AS NEW **£250.00**
8745A S Parameter Test Set. Fitted with 11604A Universal Arms 0.1-2GHz **£2750.00**
59308A HP-IB Timing Generator. **£300.00**

- Marconi.**
TF2162 M.F. Attenuator 0-111dB **£165.00**
- Schaffner**
NSG 509 5KV Insulation Tester **£785.00**
- Tektronix**
106 Square Wave Generator 1ns risetime 10Hz-1MHz without accessories **£175.00**
284 Pulse Generator 70ps risetime **£950.00**
832 Data Comms. Tester **£925.00**
833 Data Comms. Tester **£1350.00**
2701 Step Attenuator 50Ω. 79dB in 1dB steps. DC to 2GHz **£295.00**
2901 Time-Mark Generator **£195.00**


Please note: Prices shown do not include VAT or carriage.



Electronic Brokers | **Electronic Brokers Limited**
61/65 Kings Cross Road
LONDON WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

Versatower:

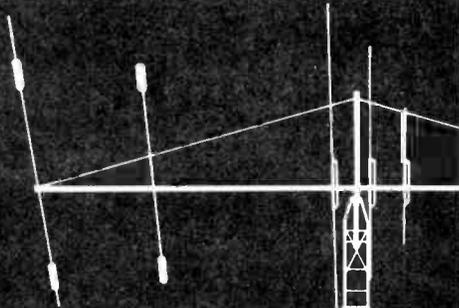
A range of telescopic towers in static and mobile models from 7.5 to 36 metres with tilt-over facility enabling all maintenance to be at ground level.



Designed in accordance with CP3 Chapter V: part 2: 1972 for a minimum wind speed of 85 mph in conditions of maximum exposure and specified by professionals world-wide where hostile environments demand the ultimate in design, quality and reliability.

Suitable for mounting equipment in the fields of:
 Communications
 Security surveillance - CCTV
 Meteorology
 Environmental monitoring
 Geographical survey
 Defence range-finding
 Marine & aero navigation
 Floodlighting
 Airport approach lighting

Further details available on request.

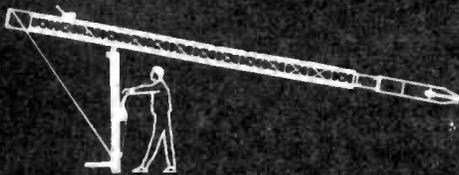

Strumech Engineering Limited,
 Portland House, Coppice Side,
 Brownhills, Walsall, West Midlands,
 WS8 7EX, England.
 Telephone: Brownhills (05433) 4321.
 Telex: 335243 SEL G.

WW - 055 FOR FURTHER DETAILS

VALVES				Minimum Order £1	VALVES VAT IS INCLUDED						
A1065	1.40	EY51	0.95	U25	1.15	6AQ5W	1.80	12AV6	0.95	6146B	5.80
A2293	8.80	EY81	0.85	U26	1.15	6AS6	1.15	12AX7	0.65	6360	2.85
A2900	13.75	EY86/87	0.80	U27	1.15	6AT6	0.90	12BA6	0.90	6550	7.20
AR8	0.75	EY88	0.85	U191	0.85	6AU6	0.60	12BE6	1.25	6870	14.00
ARP3	0.70	EZ80	0.70	U281	0.70	6AV6	0.85	12BH7	1.95	6973	4.40
ATP4	0.60	EZ81	0.70	U301	0.70	6AXGT	1.30	12BY7A	2.30	7360	10.80
B12H	3.90	GM14	5.90	U600	11.50	6AXSGT	1.30	12C8	0.65	8552	8.20
CY31	1.40	GY501	1.30	U801	0.90	68A6	0.55	12E1	18.95	38P1	11.00
DAF96	0.70	GZ32	1.05	UBC41	1.20	68E6	0.60	12J5GT	0.55	5FP7	18.00
DET22	28.50	GZ33	4.20	UA8C80	0.75	68GG6	1.60	12K7GT	0.70	4E1P	32.00
DF96	0.70	GZ34	2.75	UAF42	1.20	68J6	1.30	12K8GT	0.80	BBJ	14.00
DH76	0.75	GZ37	3.95	UBF80	0.70	68J7A	0.85	12Q7GT	0.60	88L	14.00
DI92	0.60	KT66	8.30	UBF89	0.70	68RT	4.80	12SC7	0.65	CV1526	16.00
DY86/87	0.85		9.20*	UCB84	0.85	68W6	6.20	12SH7	0.65	DG7-32	34.80
DY802	0.70	KT88	8.95	UCC85	0.70	68W7	1.80	12SJ7	0.70	DG7-36	36.00
E92CC	2.80		13.80*	UCF80	1.30	6C4	0.50	12SQ7	1.45	DDM9-11	38.40
E180CC	4.20	MH4	2.50	UCH42	1.65	6C6	0.55	12SQ7GT	0.85	D13-33GM	41.80
E180F	7.70	ML6	2.50	UCH81	0.75	6CH6	8.20	12T4	0.70		
E182CC	6.25	MX120/01		UCJ82	0.95	6CL6	2.75	13D3	2.80	* spec Q	
EA76	2.25		21.50	UF41	1.35	6CW4	8.50	13D5	0.90		
EABC80	0.60	N78	9.90	UFB0	0.95	6CX8	3.80	13D6	0.80	PLUMBICON	
EB91	0.60	OA2	0.70	UF85	0.95	6CY5	1.15	14S7	1.15	P800 3LF	
EBC33	1.15	OB2	0.80	UL84	0.95	6D6	0.70	19AQ5	0.85	P800 IR	
EBC90	0.90	PABC80	0.80	UM80	0.90	6F6	1.80	19S3	11.50	P800 IB	
EBF80	0.80	PC85	0.75	UM84	0.70	6F6GB	1.10	19G6	8.50	XQ1020R	
EBF83	0.80	PC86	0.85	UY82	0.70	6F7	2.80	19H5	39.55	XQ1020B	
EBF89	0.80	PC88	0.90	UY86	0.85	6F8G	0.85	20D1	0.80		
EC52	0.65	PC97	1.25	VR105/30	1.25	6F12	1.50	20F2	0.85	SPECIAL V	
EC91	4.40	PC900	0.90	VR150/30	1.35	6F14	1.15	20E1	1.30	4CX 1000A	
EC92	0.85	PC984	0.50	X66	0.95	6F15	1.30	20P1	0.85	4CX 5000A	
ECC81	0.65	PC889	0.85	X61M	1.70	6F17	3.20	20P3	0.75	BM 25L	
ECC82	0.80	PC189	0.95	XR1-6400A		6F23	0.75	20P4	1.25	BW 153	
ECC83	0.65	PCF80	0.80		125.00	6F24	1.75	20P5	1.35	DM 25L B	
ECC84	0.60	PCF82	0.70	Z759	19.00	6F33	10.50	25L6GT	0.95	YL 1420	
ECC85	0.60	PCF84	0.75	Z749	0.75	6FH8	12.50	25Z4G	0.75	YL 1430	
ECC88	0.80	PCF86	1.50	Z800U	3.45	6GA8	1.95	30C15	0.90	YL 1440	
ECC189	0.95	PCF87	0.50	Z801U	3.75	6GH8A	1.95	30C17	1.50	GMUJ 2	
ECC804	0.90	PCF201	1.45	Z803U	16.00	6H6	1.80	30C18	2.45	Y4-500	
ECC80	0.85	PCF201	1.85	Z900T	2.45	6JU6	5.85	30F5	1.15	CV2116	
ECC82	0.65	PCF800	0.50	1A3	0.85	6J4	1.35	30FL2	1.40	BR 189	
ECF801	1.05	PCF801	1.75	1L4	0.50	6J4WA	2.00	30FL12	1.25	BR 179	
ECH34	2.25	PCF802	0.70	1R5	0.60	6J5	2.30	30FL14	2.15	CV6131	
ECH35	1.70	PCF806	1.20	1S4	0.45	6J5GT	0.90	30L15	1.10	GMUJ 2	
ECH42	1.20	PCF800	1.35	1T4	0.45	6J6W	0.90	30P12	1.15	BK485/5552A	
ECH81	0.70	PCL81	0.75	1U4	0.80	6J6C	3.70	30PL13	1.25	MIL 5948/1754	
ECH84	0.60	PCL82	0.95	1X2B	1.40	6J56C	3.70	30PL14	2.45		
ECL80	0.70	PCL84	0.90	2D21	1.10	6K7	0.80	35L6GT	1.40	IC	
ECL82	0.75	PL86	0.75		1.85*	6KD6	4.50	35W4	0.80	SN5402N	0.28
ECL83	1.40	PCL805/85	0.95	2K25	18.95	6L6M	2.80	35Z4GT	0.85	SN5410F	0.32
ECL85	0.80	FD500/510	4.30		24.50*	6L6	2.50	50C5	1.15	SN5470F	0.48
ECL86	0.90	PFL200	1.10	2X2A	2.50	6L6GC	2.85	50CD6G	1.35	SN54196J	1.20
EF37A	2.15		2.80*	3A4	0.70	6L6GT	1.25	75B1	1.25	SN7407N	0.29
EF39	1.25	PL36	1.10	3AT2	2.40	6L7G	0.65	75C1	1.70	SN7408N	0.18
EF80	0.65	PL81	0.85	3B28	12.00	6L18	0.70	76	1.60	SN7445F	0.85
EF83	1.75	PL82	0.70		19.50*	6L06	2.95	78	1.85	SN74453P	1.10
EF85	0.60	PL83	0.60	3D6	0.50	6L09	0.70	80	1.95	SN7453N	0.18
EF86	0.75	PL84	0.95	3D22	23.00	6KG6A	2.70	85A2	1.40	SN7473N	0.38
EF89	1.05	PL504	1.00	3E29	19.00	6Q7G	1.30		2.55*	SN7474N	0.30
EF91	1.50	PL508	2.40	3S4	0.80	6SA7	1.00	807	1.25	SN7485N	0.95
EF92	2.90	PL509	4.40	4B32	18.25	6S67	1.15	813	1.90*	SN74L85N	1.10
EF95	0.65		5.85*	5B/254M	16.90	6S7J	1.05	817	19.32	SN7491AN	0.32
EF96	0.60	PL519	4.90	5B/255M	14.50	6SK7	0.95		68.50	SN74123N	0.42
EF181	0.80	PL84	6.10*	5B/258M	12.50	6SL7GT	0.85	829B	14.00	DM74123N	0.38
EF184	0.80	PL802(5E)	2.95	5C22	29.90	6SN7GT	0.80	832A	8.90	SN15836N	0.26
EF812	0.75	PY33	0.70	5R4GY	1.80	6SR7	1.10	866A	3.80	CX4	0.95
EFL200	1.85	PY80	0.70	5U4G	0.75	6S07	0.95	866E	6.25	SN76013N	1.80
EH90	0.85	PY81/800	0.85	5V4G	0.75	6V8G	1.50	931A	13.80	SN76033N	1.60
EL32	1.10	PY82	0.65	5Y3GT	0.95	6V8GT	0.95	954	0.60	SN78033N	1.35
EL34	1.80	PY83	0.80	5Z3	1.50	6X4	0.95	955	1.20	MC6800P	5.80
	2.90*	PY88	0.60	5Z4G	0.75	6X4WA	2.10	956	0.80	MC68800P	6.40
EL37	4.60	PY500A	2.10	5Z4GT	1.05	6X5GT	0.85	957	1.05	MC14511BA	
EL82	0.70	PY809	6.45	6/30L2	0.90	6Y6G	0.90	1625	1.80		
EL84	0.80	PY801	0.80	6AB7	0.70	6Z4	0.70	1629	1.85	B1702AL	3.30
EL86	0.95	QQV03/10	3.20	6AC7	1.15	7B7	1.75	2051	4.90	MM6300-J	
EL90	1.00	QQV3	7.50*	6AG5	0.80	8B8N	2.95	5763	2.80	MCM6810AP	3.80
EL91	4.20	QQV03-20A		6AH6	1.15	9D2	0.70	5842	7.50		
EL95	0.80		21.50	6AK5	0.85	9D6	2.90	5881	3.90		
EL504	1.70	QQV03-25A		6AK8	0.80	10C2	0.85	5933	6.90		
EL803	5.90		38.50	6AL5	0.80	10F18	0.70	6057	2.20	6340-1J	3.60
EL509	3.95	QQV06/40A		6ALSW	0.85	6P13	1.50	6060	1.95	MIC945-5D	0.28
EL821	18.20		16.10	6AM5	4.20	11E2	19.50	6064	2.30	MIC936-5D	0.22
EL822	9.95	QV03-12	4.20	6AM6	1.50	12A6	0.70	6065	3.20	MANY OTHER	
ELL80(5E)	2.80	SP61	1.80	6AN8A	2.50	12AT6	0.70	6067	2.30	ITEMS	
EM80	0.85	TT21	23.00	6AQ4	3.40	12AT7	0.65	6080	5.30		
EM87	1.30	TT22	18.50	6AQ5	1.00	12AU7	0.80	6146	5.80	AVAILABLE	

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc.: retail 749 3934, trade and export 743 0899.
FIELD TELEPHONE, CABLE TYPE D10
 Geiger Muller Tubes GM4, MX120/01 and others.
 Beta-Gamma Probe with B12H (L314).

TEST SET FT2 FOR TESTING Transceivers A40, A41, A42 and CPR26.
HARNES "A" & "B" CONTROL UNITS "A" "R" "J1" "J2" Microphones No 5, 6, 7 connectors, frames, carrier sets, etc.
DRUM CABLE continuous connection YC 00433.
 Signal Generators MARCONI TF 144H/4S; TF144H/6S 10 kHz-72MHz. Receivers AR-88D and Spares available.
 Prices on application

FIELD TELEPHONES TYPE "J"

Tropical, in metal cases.
10-line MAGNETO SWITCHBOARD. Can work with every type of magneto telephones.

PRICES MAY VARY

POSTAGE: £1-£3 45p; £3-£5 55p; £5-£10 60p; £10-£15 80p; £15-£20 100p.

COLOMOR (ELECTRONICS LTD.)

170 Goldhawk Rd., London W.12

Tel. 01-743 0899 or 01-749 3934

Open Monday to Friday
 9 a.m.-5.30 p.m.

SALE*

P.&R. COMPUTER SHOP

SALE*

IBM GOLFBALL PRINTERS FROM £70 EACH + V.A.T.

*BRAND-NEW LA36 DEC WRITERS - SALE £200 EACH
 CENTRONIC 779 PRINTERS - £325 + V.A.T.
 CENTRONIC 781 PRINTER - £350 + V.A.T.
 POWER UNITS, 5-VOLT 6-AMP - £20 EACH
 FANS, PCBs, KEYBOARDS AND LOTS MORE

COME AND LOOK AROUND

SALCOTT MILL, GOLDHANGER ROAD
 HEYBRIDGE, MALDON, ESSEX
 PHONE MALDON (0621) 57440

WW - 069 FOR FURTHER DETAILS

DEC SALE

a selection from
our huge stocks.
All items reconditioned
unless otherwise stated.

DEC PDP11/70 EQUIPMENT

SPECIAL BULK PURCHASE OF 11/70 PROCESSORS, PERIPHERALS AND OPTIONS EX DEC-MAINTAINED SITE enabling us to offer a wide variety of configurations and add-ons. Please let us know your requirements

DEC SYSTEMS

PDP11/23 SYSTEM

11/23 CPU, 128KB MOS, Dual RLO2 & Control, OLV11, 4 line Interface, Cabinet, VT100 Console.

NEW **£10,975**

PDP11/24 SYSTEM

11/24 CPU, 256KB MOS, Dual RLO2 & Control, Cabinet, VT100 Console

NEW **£15,750**

PDP11/34A SYSTEM

11/34 CPU, 256KB MOS, Dual RK07 & Control, Cabinet, LA36 Console

£13,725

WS78 WORD PROCESSOR

WT78 Word Terminal and Processor RX01 Dual Floppy Disks Drive Diablo Letter Quality Printer. Complete with cabinets & full documentation

£2950

LSI PROCESSORS

11/03LX KD11HA CPU, KEV11 EIS/FIS, BDV11AA Terminator/Buotstrap, BA11N 5 1/4 Chassis with Backplane and Power Supply. No memory included

NEW **£1200**

11/03N KD11Q CPU, KEV11 EIS/FIS, BDV11AA Terminator/Buotstrap, BA11R 5 1/4 Chassis with Backplane and Power Supply, MS/110D 32KW MOS

NEW **£1495**

VT100-PLUS


SPECIAL PURCHASE BRAND NEW SURPLUS

DEC PDT11/130 PROGRAMMABLE DATA TERMINAL COMPRISING:

- * VT100 with Advanced Video Option & Printer Port
- * Integral LSI Processor with 32K RAM
- * Integral dual TU58 mini cartridge

Fantastic value whether for use as VT100 only or as full PDT

£995 including comprehensive manual

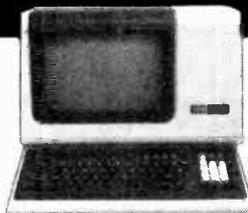

DEC DISK DRIVES

RX11 Dual FDD with Unibus Ctl (NEW)	£995
RXV11 Dual FDD with Qbus Ctl (NEW)	£995
RX8E Dual FDD with PDP8 Ctl (NEW)	£995
RX211 Dual FDD with Unibus Ctl (NEW)	£1450
RX28 Dual FDD PDP8 Ctl (NEW)	£1450
RK05J Add-on Disk Drive	£975
RK11D RK05J with Unibus Ctl	£1870
RK05F Add-on Drive (Double Density)	£1250
RK06 Add-on Drive	£1500
RK6* 1 RK06 with Unibus Ctl	£3000
RK07 Add-on Drive	£3250
RK7* 1 RK07 with Unibus Ctl	£4750
RM02 Add-on Drive (NEW)	£8500
RJM02 RM02 with Unibus Ctl	£11500
RM03 Add-on Drive (AS NEW)	£8250
RWM03 RM03 with Massbus Ctl	£11250
REM03 RM03 with VAX Ctl	£11250
RPOE Add-on Drive	£7500
RJPO6 RPO6 with Unibus Ctl	£10500
RWP06 RPO6 with Massbus Ctl	£10500

DEC PRINTERS AND TERMINALS

LA34 DECwriter IV EIA 300 baud	£425	
LA36 DECwriter II 20mA	£295	Hazeltine 1500 (recon)
LA36 DECwriter II RS232	£325	£325
LA180-PD DECprinter I (NEW)	£495	Hazeltine 1510 (NEW)
LS120 DECwriter III EIA 1200 baud	£750	£550
VT50 DECscope 20mA	£199	Hazeltine 1520 (NEW)
VT50 DECscope RS232	£225	£625
VT105 Graphics Terminal	£950	

HAZELTINE VDUS

ANDERSON JACOBSON

AJ832 Daisy Wheel Printer 300 baud with Keyboard and Integral Stand, EIA/RS232 Interface	£750
AJ860 Matrix Printer 1200 baud with Keyboard and Tractor Feed. Good quality print-out with true descenders. Desktop model, EIA/RS232 Interface	£595
AJ212 Acoustic Couplers 300 baud, originate only	£125


SCOOP PURCHASE OF TEKTRONIX GRAPHICS EQUIPMENT

HUGE SAVINGS FROM NEW PRICES ONLY SLIGHTLY USED-COVERED BY FULL WARRANTY

GRAPHICS TERMINALS COLOUR GRAPHICS DESKTOP COMPUTERS PLOTTERS MONITORS


4006-1 HIGH RESOLUTION GRAPHICS DISPLAY TERMINAL

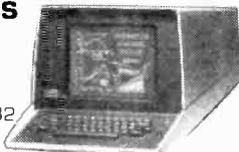Alphanumeric Mode: 35 x 74 characters (63 ASCII character set)
Graphics Matrix: 1024X x 1024Y
Baud Rate: 75 thru 4800 Interface: Standard RS232
£1525



4010-1 HIGH RESOLUTION GRAPHICS DISPLAY TERMINAL

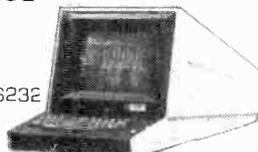Alphanumeric Mode: 35 x 74 characters (63 ASCII character set)
Graphics Matrix: 1024X x 1024Y
Baud Rate: 110 thru 9600 Interface: Standard RS232
Thumbwheel crosshair cursor. Integral Stand
£2750



4014-1 and 4015-1 HIGH RESOLUTION BIG (19") SCREEN GRAPHICS DISPLAY TERMINALS

Alphanumeric Mode: up to 133 x 64 characters (94 ASCII character set or 188 ASCII + APL on model 4015)
Graphics Mode: 4096X x 4096Y (includes enhanced graphics option)
Interface Standard RS232
Thumbwheel crosshair cursor. Integral Stand
4014-1 **£6950** 4015-1 **£7250** 4016-1 25" Screen model **£8950**



4027 COLOUR GRAPHICS TERMINAL

Providing 8 displayable colours from a palette of 64 colours, and 120 user defined patterns
Interface: Standard RS232 Baud rates: up to 9600
£5250



4051 DESKTOP COMPUTER PROVIDING

High resolution Graphics and Alphanumerics, 32KB Memory, Integral Cartridge Tape Drive
£2250




4952 OPT. 2 JOYSTICK

(for 4050 series) sensitive cursor-control with 1% accuracy and XY zero feature
£275

4662 INTELLIGENT DIGITAL PLOTTER

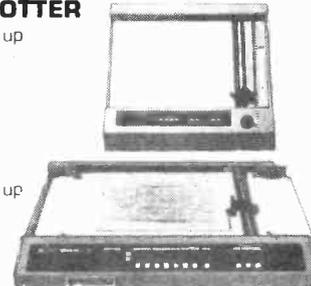Microprocessor Controlled high speed plotting up to 10" x 15" with built-in joystick control. IEEE general purpose interface
£1800




4663 INTELLIGENT DIGITAL PLOTTER

Microprocessor Controlled high speed plotting up to 17" x 22" with built-in joystick control. Standard RS232 Interface. Baud rates 110-9600
£4000

HIGH RESOLUTION DISPLAY MONITORS

606 DISPLAY MONITOR

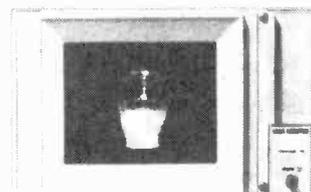5" CRT, 5ml Spot size, XY amplifier DC to 3MHz, 2-axis amplifier DC to 10MHz
£650



606A DISPLAY MONITOR

as above **£875**

606B DISPLAY MONITOR

5" CRT, 3ml Spot size, XY amplifier DC to 3MHz, 2-axis amplifier DC to 5MHz
£950

611 STORAGE DISPLAY MONITOR

11" CRT, Storage view time 15 mins plus, XY amplifier. Programmable Erase, write-thru, non-store and view functions
£1450

Winter '82/83 Catalogue now out. Send for your FREE copy now.

ADD 15% VAT TO ALL PRICES Carriage and Packing extra

**Electronic Brokers Ltd., 61/65 Kings Cross Road
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**



Electronic Brokers

THANDAR PORTABLE TEST BENCH

A wide range of high performance instruments, at prices that are hard to beat, puts professional test capability on your bench.

COUNTERS - TF200 1Hz to 200MHz; TF040 10Hz to 40MHz; PFM200A 20Hz to 200MHz (hand-held model); TP600 prescales to 600MHz; TP1000 Prescales to 1GHz.

MULTIMETERS - TM351 0.1% 3½ digit LCD; TM353 0.25% 3½ digit LCD; TM355 0.25% 3½ digit LED; TM354 0.75% 3½ digit LCD (hand-held model); TM451 0.03% 4½ digit with autoranging and sample hold.

OSCILLOSCOPE - SCT10A 10MHz, 10mV sensitivity, 40mm CRT with 6mm graticule divisions.

THERMOMETERS - TH301 -50°C to +750°C, 1° resolution; TH302 -40°C to +1100°C and -40°F to +2000°F, 0.1° and 1° resolution. Both accept any type K thermocouple.

GENERATORS - TG100 1Hz to 100kHz Function, Sine, Square, Triangle Wave; TG102 0.2Hz to 2MHz Function, Sine, Square, Triangle Wave; TG105 5Hz to 5MHz Pulse, Free Run, Gated or Triggered Modes.

LOGIC ANALYSERS - TA2080 8 channel 20MHz; TA2160 16 channel 20MHz.

ACCESSORIES - Bench rack, test leads, carrying cases, mains adaptors, probes, thermocouples etc.

Send for our latest catalogue and price list.
Thandar Electronics Ltd,
London Road, St. Ives,
Huntingdon, Cambridgeshire PE17 4HJ.
Telephone (0480) 64646. Telex 32250.

 **thandar**
ELECTRONICS LIMITED

PUTTING THE BEST WITHIN YOUR GRASP


WW - 058 FOR FURTHER DETAILS



TH12

IF YOU MISS E.T. — YOU'RE PROBABLY NOT TUNED IN

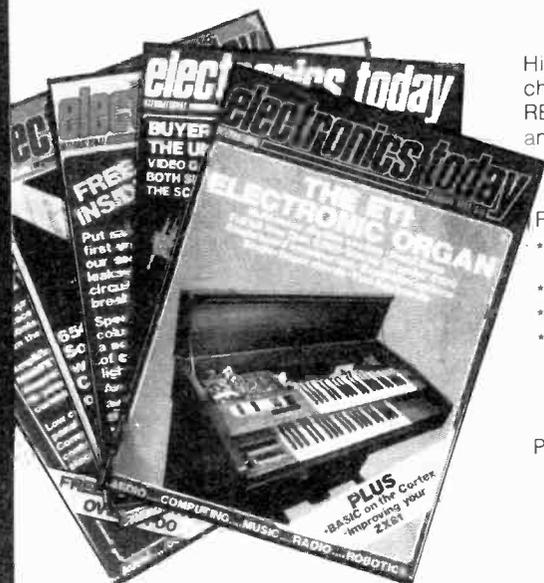ELECTRONICS TODAY INTERNATIONAL — THE MAGAZINE FOR THE INFORMED ENTHUSIAST.



AUDIO EXTRA


Hi-Fi need not mean High Finance. Let Electronics Today International help you choose your Hi-Fi system with its 8 PAGE PULL-OUT GUIDE to the best buys in RECORD DECKS, CASSETTE DECKS, CARTRIDGES, AMPLIFIERS, SPEAKERS and TUNERS.

- FOUR SPECIAL PROJECTS FOR THE AUDIO ENTHUSIAST TO BUILD:
- a new type of POWER AMPLIFIER — better performance and cheaper components.
 - a BALANCED INPUT PREAMPLIFIER — low noise on long cables.
 - a NOISE REDUCTION unit — broadcast quality compressor/limiter.
 - UPGRADE your existing amplifier — replace the power supply with our stabilised unit.

PLUS CONFIGURATIONS: basic circuit design. ZX81: full software listing of music and sound effects for the ZX81 soundboard. TECH TIPS: readers' ideas. READ/WRITE: readers' views. DATA SHEET: organ chips. PseudoROM: RAM replacement for 8K ROM with battery back-up.

ALL IN THE MAY ISSUE OF E.T.I. — AT YOUR NEWSAGENT NOW!

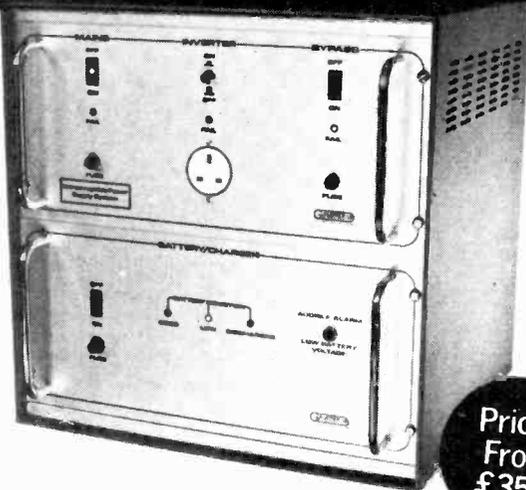When the power fails or falters Galatrek lets you carry on.



Prices From £350

Uninterruptible Power Supplies - UPS CVT Reliability 125va to 50kva, 50 or 60Hz.

■ **STANDBY POWER.** Invaluable for winding down a computer programme on mains failure and wherever continuous power is essential.

■ **STABILISATION.** $\pm 3\%$ Vital to combat mains voltage fluctuations and ensure the operation of equipment at peak efficiency. Frequency stabilised $\pm 0.1\%$ 47 to 65Hz.

■ **TRANSIENT ATTENUATION.** Provides suppression of mains born interference (spikes). Model above £795

Line Conditioners from £150 and Voltfilt from £114

For more information, cut the coupon.
Galatrek International, FREEPOST, Scotland Street, Llanrwst, nr. Llandudno, Gwynedd LL26 OAL, BRITAIN,
Tel No: 0492-640311/641298, Telex: 617114 A/B Galahu.
Made and Designed in Britain by Galatrek.



Please send me full details of your range of voltage stabilisers, filters, cut outs, generators and CVT's
Please send me full details of UPS
Please send me a requirement check sheet
Consultation with Galatrek Engineer

Name _____
Position _____
Company _____
Address _____

Tel No _____ Telex _____

Trade OEM (please tick where appropriate) (WW/4/83)

WW - 009 FOR FURTHER DETAILS

NEW! ICOM ICH2 SYNTHESIZED FM HANDPORTABLE



The ICH2 is the first of a new breed of synthesized hand-held radio transceivers. Being synthesized, it requires no crystals to be set on to frequency. All that is required is to lift a recessed panel on the top of the set and cut the correct diodes to program the set to one or two channels. Duplex or simplex is obtained in the same way. This really is a boon to the busy dealer and convenient for the customer who wants those extra few sets "yesterday".

The ICH2 is very versatile, coming complete with a rechargeable ni-cad pack, small mains charger, rubber helical antenna, earphone and strong spring belt clip. Optional extras include: A speaker/microphone, cigarette lighter plug 12V charging lead, 12V converter to operate direct from the car supply, leather and leatherette cases, various different types of slide on/off battery packs both rechargeable and dry and a desk charger that fast charges some of the battery packs in 1 to 1 1/2 hours. The battery packs slide on and off very easily, enabling a spare to be carried in your pocket and an exchange made in the field. Sizes are 6.5"H x 2.6"W x 1.4"D, weighing 1.1lb. Power output is 1-3 watts and covers a frequency range of 164.975-174.975Mhz, duplex or simplex.

Retail price is 269 pounds each plus VAT. We are also looking for dealers for general distribution. More details from

Thanet Electronics **ICOM**

143 Reclver Road, Herne Bay, Kent
Tel: 02273 63859. Telex 965179

WW - 037 FOR FURTHER DETAILS

<p>D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts Sealed base. Ideal for programming. 6-position at less than half manufacturer's price.</p> <p>ONLY 75p</p> <p>Will fit into 14-pin di socket. Ten at 65p ea. per 100 55p ea.</p>	<p>HONEYWELL PROXIMITY DETECTOR integral amplifier, 9v D.C. £3.50 ea</p> <p>PHOTO CONDUCTIVE CELL £1.25. High-power CdS cell, 600mW, for control circuits. Resistance 800 ohm to 4K. Max volts 240. Size 1/2 x 1/2in.</p> <p>RIBBON MICROPHONE with pre-amp on chassis. £1.75.</p>	<p>MULLARD MODULES LP1171 LP1179 "F" Strip AM, FM Front end Pair £5.75 Complete with Data</p> <p>LP1186 LP1157 varicap Med & Long Tuner £2.50</p> <p>CRYSTALS COLOUR TV 4 433619 mc/s £1.25 Miniature type sealed</p>	<p>ULTRA SONIC TRANSDUCERS 40K.C.S. Complete on 18in. Screened cable. £1.75 each, pairs £2.95.</p> <p>ULTRA SONIC TRANSMITTER Complete unit (uncased requires 1.5V). £3.25.</p> <p>FOSTER DYNAMIC MICROPHONES. 200 ohm impedance. Moving coil Complete on chassis £1.75 pair.</p>
<p>U.N.F. MODULATORS Latest type, adjustable, ideal for computers with data circuit Size 3x2 1/2 x 1 inch Only £3.50 In screened case</p>	<p>LM380 Amplifier 85p LM318N Hi-Slew Op Amp. £1.50 LM323K, 5v 3-amp, reg. £3.50</p> <p>LM310N Volt. Follower Amp. £1.20 LM311H High Perf. Volt. Comparator. £1.00 LM384N, 5-watt Amp £1.20 LM393N Dual Com. 60p 7905 Reg. -5v 75p</p>	<p>MINIATURE HIGH-QUALITY FANS "Whisper Model" by Roton. Low-power consumption (less than 10 watts). Silent running. 115v (two in series for 230v). 50/60Hz. Size 4 1/2 x 4 1/2 x 1 1/2in. ONLY £6.50 EACH incl. V.A.T.</p> <p>BRAND NEW 50% less than manufacturer's price</p>	<p>STEREO CASSETTE MECHANISMS 6 or 12 volt. Complete with Heads + Erase and Selenoid. Brand new £5.50 ea.</p>
<p>MINIATURE EDGE INDICATOR METER With illuminated dial scale 0-10 F.S.D. 100 microamp. Size 1 1/2 x 1 1/2 x 1/2 deep. Only £1.65.</p>	<p>MONSANTO Half-inch 1 Display High Intensity £1 each set of 4 £3.50 Common anode 14 Pin Dill Package</p>	<p>STEREO CASSETTE TAPE HEADS. Quality replacement for most recorders with mounting plate Record/Replay £2.80</p> <p>MARRIOTT TAPE HEADS Quarter track Type XRPS18 Record/Replay (each) £2.00 XRPS36 Record/Replay (each) £3.00 XES11 Erase (each) £1.00</p>	<p>HEWLETT-PACKARD DISPLAYS 5082-7650 HIGH EFFICIENCY AND VERY BRIGHT Only £1.00 each</p> <p>Set of 6 for £5 Half-inch red common anode will replace DL7014-pin Dill.</p>
<p>BRIDGE RECTIFIER 800 PIV 35 amps 1 1/2 x 1 1/2 x 1/2in. £3.50</p>	<p>NATIONAL P.8080A Chips £2.95 8216 £1.75</p> <p>IN4148 DIODES Full spec. but no polarity band. Per 1,000 £10</p> <p>MINIATURE M.P.C. POTENTIOMETERS. Model M2 High quality. 5% tolerance. 2-watt, with tin spindles. All values, 47 ohms-47k only 50p each per 10. 50p each per 100. 40p each</p>	<p>RECHARGEABLE BATTERIES VARTA 36 volts DEAC. M/AH 225 £1.50</p> <p>XTAL FILTER 107 mc/s 12.5DB separation. 1 1/2 x 1 1/4 x 1 inch £7.00 100KC/S + 1 meg 3-pin £2.00</p>	<p>"CHERRY" ADD-ON KEYPAD</p> <p> LIST PRICE £22.00 OUR PRICE ONLY £5.95 incl. V.A.T.</p> <p>A compact 12-button keypad suitable for use with keyboard extend its functions plus four extra keys. Supplied brand new</p> <p>A 3 x 4 non-encoded single mode keyboard</p>

QUANTITY DISCOUNTS on ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW (unless otherwise stated).

DELIVERY from stock - Add post 35p per order.

EXPORT enquiries invited

TELEX 262284
Tranconics
Mono 1400

Henry's

01-723 1008/9

Callers to: 404 EDGWARE ROAD, LONDON W2 1ED

ALL MAIL ORDERS/EXPORT ENQUIRIES 11/12 PADDINGTON GREEN, LONDON, W2

Accurate Digital Multimeters at Exceptional Prices

NEW ANALOGUE METER WITH CONTINUITY BUZZER AND BATTERY SCALE

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

SPECIFICATION MODELS 6010 & 7030

- 10 amp AC/DC
- Battery: Single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm.
- Weight: 400g inc. battery.
- Mode Select: Push Button.
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 2MΩ
- Input Impedance: 10MΩ
- Display: 3 1/2 Digit 13mm LCD
- O/load Protection: All ranges

OTHER FEATURES: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



NEW HM102 BZ £13.00

NEW HM 102 BZ SPECIFICATION

- DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500µA, 0-5, 50, 500mA
- Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.


HM 101 POCKET SIZE MULTIMETER SPECIFICATION

- DC & AC Voltage: 0-10, 50, 250, 1000 volts, 2000 ohms/volts -10 to +22dB
- Decibels: -10 to +22dB
- DC Current: 0-100mA
- Ohmmeter: 0-1 Megohm in 2 ranges, 60 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 90 x 60 x 29mm, 92gr. incl. battery
- Price: £5.50

Quantity discount for trade on application.

Add 15% to your order for VAT. P&P is free of charge.

ARMON ELECTRONICS LTD.

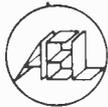

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Telephone 01-902 4321 (3 lines)

Payment by cheque with order



accepted

TELEX No 923985

WW - 017 FOR FURTHER DETAILS

pantechnic

THE POWERFET SPECIALISTS

POWERFET AMPLIFIER MODULES

MODEL	POWER RANGE (Continuous RMS)	TYPICAL LOADS	PRICES (one off)
PFA 100	50W-150W	4Ω, 8Ω	£17.35
PFA 200	100W-300W	4Ω, 8Ω	£23.87
PFA 500	250W-600W	2Ω, 4Ω, 8Ω	£42.00
PFA HV	200W-300W	4Ω, 8Ω, 16Ω	£34.30

Key features:

- **RELIABLE** - Powerfet freedom from thermal runaway and secondary breakdown
- **LINEAR** - THD zero, IM/THD < 0.01% full power (mid-band THD down to 0.0015%)
- **FAST** - Slew rate > 30V/µS (45V/µS typical)
- **QUIET** - Signal to noise ratio 120dB
- **BRIDGEABLE** - Without extra circuitry
- **STABLE** - Unconditionally
- **LOW COST** - 10 watts to 20 watts per £, depending on model and quantity

As they stand these modules suit most P.A. and industrial applications and satisfy all foreseeable audiophile requirements. (The HV is aimed at digital audio.) Where aspects of performance fail to meet specific requirements (e.g. in speed or power) low-cost customising is often a possibility. Alternatively entirely new boards can be produced.

ALSO-
 PAN 20 - Ultra-low-noise/distortion, mono preamp board, £6.76
 PAX 2/24 - 2-way active crossover board (24dB/octave) plus regulators, £9.70
 THE HEAT EXCHANGER - New, super-efficient heatsink, handles 300W or 1.2kW when blown; 7in. x 4in. x 2 1/4in., £7.50

This is just a fraction of the new products available from Pantechnic - check us out!

Prices exclude V.A.T.

Carriage 75p

Price and Delivery
PANTECHNIC (Dept. WW4)
 17A WOOLTON STREET
 LIVERPOOL L25 5NH
 Tel: 051-428 8465

Technical Enquiries
 contact
 Phil Rimmer
 on
 01-800 6667

WW - 070 FOR FURTHER DETAILS

CHILTERN ELECTRONICS

INCREDIBLE SCOOP PURCHASE OF SUPERB HIGH RESOLUTION

9" VIDEO MONITORS

Look at these features:

- ★ 18Mhz Bandwidth
- ★ Over 85 Chars/line resolution
- ★ P31 Green Screen
- ★ Composite Video i/p
- ★ Mains 230v
- ★ Antireflective Faceplate
- ★ Attractively styled case

Why pay £120 or more?

BRAND NEW IN MAKER'S CARTONS AT THE AMAZING BARGAIN PRICE OF £78 vat extra, carriage £5

Quantity discounts/dealer enquiries welcome

THE IDEAL MATCH FOR YOUR MICRO


High Street, Chalfont St Giles, Bucks HP8 4QH

Telephone 02407 71234. Telex 262284

WW - 071 FOR FURTHER DETAILS

BBC Micro Computer

Please phone for availability

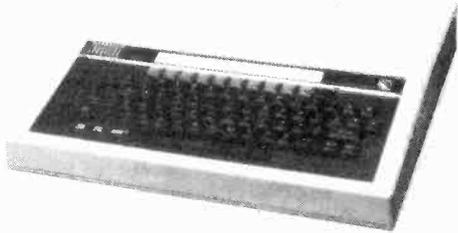

WORD PROCESSOR 'VIEW'
16K ROM £52

BBC Model B £399
(incl. VAT)
Carr £8/unit
Model A to Model B
upgrade kit £50
Fitting charge £15
Individual upgrades also
available

TELETEXT ADAPTOR £195
PRESTEL ADAPTOR £90
2nd PROCESSOR 6502 £170
2nd PROCESSOR Z80 £290

FLOPPY DISC INTERFACE
incl. 1.0 Operating System
£95 & £20 installation

Phone or send for our BBC leaflet

BBC FLOPPY DISC DRIVES
Single Drive 5¼" 100K £235+£6 carr.
Double Drive 5¼" 800K £799+£8 carr.

BBC COMPATIBLE DRIVES
These are drives with TEAC FD50 mechanism
and are complete with power supply
SINGLE: 100K £190; 200K £260; 400K £340
DUAL: 200K £360; 400K £490; 800K £610

ACORN SOFT/BBC SOFT/GAMES PADDLES IN STOCK

OFFICIAL BBC DEALER

CASSETTE RECORDER

Ferguson 3T07
£26.50 + £1.50 carr
Cassette Leads £3.50
Computer Grade Cassettes £0.50 each
£4.50 for 10 + £1 carr

MONITORS

MICROVITEC 1431 14in Colour Monitor £249+£8 carr
MICROVITEC 2031 20in Colour Monitor £319+£8 carr
SANYO 14in Colour Monitor RGB £255+£8 carr
Lead for SANYO RGB £10
SANYO 12in Hi Res Green Monitor £99+£6 carr

ACORN ATOM

Basic Built £135. Expanded £175
(Carr £3 per unit)
Atom Disc Pack £299 + £6 Carr
3A 5v Regulated PSU £26 + £2 Carr
Phone or send for our BBC Atom list


NEC PC 8023 BE - C

100CPS, 80 cols
Logic Seeking, Bi-directional,
Forward and Reverse
Line Feed,
Proportional Spacing,
Auto Underline,
Hi-Res and Block
Graphics, Greek Char.
Set.
Only £320+£8 carr.



PRINTERS

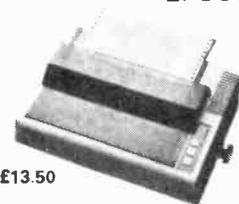SEIKOSHA GP 100A
80 cols 30 CPS
Full ASCII & Graphics
10" wide paper
Now only £190+£6 carr.
Ask for details on GP 250A



EPSON MX 80 and 100F/T3

MX 80 80CPS 80 cols
MX 100 100CPS
136 cols
Logic Seeking, Bi-directional,
Bit Image Printing, 9
x 9 Matrix
Auto Underline
MX 80 F/T3 £325
MX 100 F/T3 £430
(£8 Carr/Printer)

Parallel Printer lead for BBC/Atom to most printers £13.50
Variety of interfaces, ribbons in stock.
2,000 fan fold sheets 9½" x 11" £13.50 x £3 p&p

RUGBY ATOMIC CLOCK

This Z80 micro controlled clock/calendar receives coded time data from NPL Rugby. The clock never needs to be reset. The facilities include 8 independent alarms and for each alarm there is a choice of melody or alternatively these can be used for electrical switching. A separate timer allows recording of up to 240 lap times without interrupting the count. Expansion facilities provided.

See July/August ETI for details.

Complete Kit £120 + £2 p&p

MICROTIMER

6502 Based Programmable clock timer with
★ 224 switching times/week cycle
★ 24-hour 7-day timer
★ 4 independent switch outputs directly interfacing to thyristor/triacs
★ 6 digit 7 seg. display to indicate real time, ON/OFF and Reset times
★ Output to drive day of week switch and status LEDs.
Full details on request. Price for kit £57

CONNECTOR SYSTEMS

ID CONNECTORS (Speedblock type)

No of ways	Header Plug	Receptacle	Edge Conn
10	90p	90p	200p
20	145p	125p	240p
26	175p	150p	300p
34	200p	160p	380p
49	220p	190p	550p
50	235p	200p	600p

JUMPER LEADS

24" Ribbon Cable with Headers			
	14pin	16pin	24pin
1 end	145p	165p	240p
2 ends	210p	230p	345p
24" Ribbon Cable with Sockets			
	20pin	26pin	34pin
1 end	160p	210p	270p
2 ends	290p	385p	490p
Ribbon Cable with D. Conn.			
25 way Male	500p	Female	550p

AMPHENOL CONNECTORS

36 way Solder Type Plug (centronix type)	550p
36 way Solder Socket (centronix type)	550p
36 way IDC Plug (centronix type)	500p
24 way Solder Plug (IEEE type)	500p
24 way Solder Socket	500p
24 way IDC Plug	485p

RIBBON CABLE

(Grey)	
10 way	60p
14 way	80p
16 way	90p
20 way	105p
26 way	140p
34 way	220p
40 way	265p
50 way	330p
64 way	370p

D CONNECTORS

		No. of ways			
		9	15	25	37
MALE					
Solder	90p	130p	160p	250p	
Angled	160p	230p	265p	425p	
FEMALE					
Solder	110p	160p	210p	350p	
Angled	175p	240p	310p	500p	
Hoods	95p	95p	95p	125p	

RS 232 CONNS (25 way D)

24" Single end Male	£5.50
24" Single end Female	£6.00
24" Female-Female	£11.00
24" Male-Male	£10.00
24" Male-Female	£11.50

DIL HEADERS

	Solder	IDC
14pin	40p	100p
16pin	50p	110p
24pin	100p	150p
40pin	200p	225p

EURO CONNECTORS (Indirect Edge Conn)

DIN STD	Plug	Skt.
41617 21 way	170p	170p
41617 31 way	180p	180p
41612 2x32 way	290p	320p
Angled 2x32 way	325p	375p
41612 3x32 way	275p	380p
Angled 3x32 way	—	400p
2x32 way IDC a+c	—	525p
(for 2x32 way specify a+b or a+c)		


EDGE CONNECTORS

	0.1"	0.156"
2x18 way	—	140p
2x22 way	200p	170p
2x23 way	210p	—
2x25 way	225p	220p
1x43 way	260p	—
2x43 way	395p	—
2x50 way	—	—
1x77 way	700p	—
S100 Conn.	—	600p

MICRODOCTOR

£295

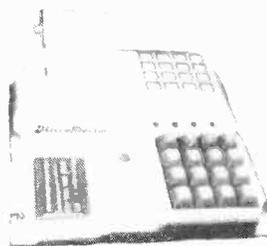This is not a logic analyser or an oscilloscope. It tests a microsystem and gives a printed reprint on RAM, ROM and I/O - it will print memory map, search for code, check dataline shorts and operates peripherals. Microdoctor complete with psu, printer probe cable and two configuration board.



SOFTY II INTELLIGENT PROGRAMMER

The complete microprocessor development system for Engineers and Hobbyists. You can develop programs, debug, verify and commit to EPROMS or use in host computer by using softy as a romulator. Powerful editing facilities permit bytes, blocks of bytes changed, deleted or inserted and memory contents can be observed on ordinary TV. Accepts most +5v Eproms
Softy II complete with PSU, TV Lead and Romulator lead £169

SPECIAL OFFER

2114L	80p
2716 (+5v)	250p
2532	350p
4116-2	80p
4164-2	450p
6116P	350p

UV ERASERS

UV1B up to 6 Eproms £47.50
UV1T with Timer £60
UV140 up to 14 Eproms £61.50
UV141 with Timer £78
(Carr £2/eraser)
All erasers are fitted with mains switches and safety interlocks.

TRAINER KITS

6502 Junior Computer £85
6802 Nancomp I £80
6809 Nancomp II £80
1802 Micro Trainer £64
Z80 Menta £115
(fully built and documented)
Full details on request

BOOKS

(No VAT p&p £1)

CMOS Cook Book	£7.75
CRT Controller H/Book	£7.95
Programming the Z80	£11.50
Z80 Microcomp Handbook	£6.95
Programming the 6502	£10.25
6502 Assy. Lang	£12.10
6502 Applications	£10.20
6502 Software Design	£9.05
6502 Games	£10.25

Large selection of databooks, interfacing books, books on BBC, etc in stock.
Ask for our list. WW-12

NEW COMPREHENSIVE CATALOGUE AVAILABLE
PLEASE SEND FOR PRICE LIST

MARCONI SIGNAL GENERATORS

TF2002A/S (illustrated) 10kHz-72MHz. AM/FM. £750
 TF2002. As above but AM only. £450

MARCONI TF1066B/1. AM/FM Generator. 10-470MHz. 0.2uV-200mV output. FM Deviation up to ±100kHz. £550

MARCONI TF995A/5. AM/FM Generator. Narrow deviation model 995 covering 1.5-220MHz. £450. TF995B/5 £255.

MARCONI TF1064B/5. AM/FM Signal generator covering in three ranges 68-108, 118-185 and 450-470MHz. FM fixed deviations of 3.5 & 10kHz. AM fixed 30%. £225

'DOLBY' NOISE WEIGHTING FILTERS

Cat. No. 98A. Noise weighting filters for CCIR/ARM signal-to-noise ratio measurements. As new units. £40 each (+£1 p&p).

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipots". Brand new with mounting instructions. Only £2.50 each.

'VARIACS' - SPECIAL PURCHASE

We now have a stock of used but excellent condition, fully tested, variable (0-260V) transformers at the following ratings.

BERCO (enclosed) 2A.....£12.50+£1.50 pp
 BERCO (non-enclosed) 8A.....£25.00+£2.50 pp
 BERCO (non-enclosed) 10A.....£28.00+£2.50 pp
 ZENITH (enclosed) 8A.....£26.00+£2.50 pp

Also available, small quantity of Heavy Duty and 3 Phase Variacs. P.O.A.

AUDIO WATTMETERS

Switchable 1W & 10W FSD. Internal 3.5 & 8 Ohm load impedances. Housed in grey enamelled case 6x6x3". Large easy to read 3" sq. meter. Scope output provision. £10 (+£1).

HEATHKIT Model AW-1U. Internal load switchable 3, 8, 15 & 600 Ohm. Meter scaled 0-50W (+dB scale). 5 Ranges from 5mW-50W FSD. Mains powered. £25 (+£1).

MARCONI TF83A. 1mW-10W Full scale in 5 ranges. Impedances 2.5-20K Ohm in 48 steps. Direct calibration in Watts and dBm. £85 (+£2).

GPO JACK SOCKET STRIPS. 20-WAY Type 320 (3-pole) £2.50 ea. Type 520 (3-pole with switching contacts) £4 ea. Please include 35p each for postage on these. GPO type 316 jack plugs for above 20p ea. (10+ post free). Plus VAT please. Also recent stock of new, mint condition 720 Type, £6 each.

PHILIPS RF SIGNAL GENERATOR

As new condition Philips PM 5326. AM/FM RF signal generator covering 0.1-125MHz. Integral 5 digit Frequency display. Mod AM & FM + Sweep facilities. 1 only available.

P. F. RALFE ELECTRONICS

10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753

'ADVANCE' 'SCOPES - SPECIAL OFFER

A bulk purchase of Advance series 'scopes enables us to offer the following fully reconditioned, guaranteed units as follows.

- OS2000 20MHz dual-beam. 10mV/cm. (2002Y & 2003X P.I.s) £200.
- OS2100 30MHz dual-beam. 10mV/cm. (plug-in units as above) £230.
- OS2200 25MHz dual-beam. 10mV/cm STORAGE. 2005X plug-in £316.

N.B. All these prices INCLUDE 15% VAT. Securicor despatch if required + £10 ea. We also have in stock various optional plug-in units such as Differential (50uV) Y-amp., Sweep-delay X-amp, etc. Please call for details. For full spec SAE please.

- ADVANCE VM77D Millivoltmeters. 15Hz-4.5MHz. 1mV Full scale -300V AC £55
- WOELKE ME104C. Wow & Flutter Meter £95
- AVO Type 1 LCR Component Bridge.
- WAYNE KERR AF Signal Generator Type S121 £75
- AIRMEC Wave Analysers Models 853 and 248A.
- CENTRONICS P1 Printer, one only. AND Type 663 Printer.
- ROHDE & SCHWARZ SDR Signal Generator. 300MHz-1GHz.
- HEWLETT PACKARD 608C Signal Generator. 10-480MHz AM.
- MARCONI Component Bridge Model TF2700. (LC&R).
- OKIDATA CORP Series 3300 Hard-Disc Drives.
- TALLY Model 220 Line Printers.

BELL & HOWELL MICROFICHE VIEWERS

Type SR5. Screen size 9x5". Recent small quantity now avail. £55

SWEEEPERS

TELEONIC Sweep generator system type 2003. Fitted with Marker, attenuator, Detector plug-in units and Generator covering 800-1500MHz. £325

PLEASE NOTE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months' guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES.

DISC CARTRIDGES

BASF 12-Segment Single Hard Disc Cartridges. Brand new surplus stock.

MUIRHEAD FACSIMILE UNITS

MUFAX 'COURIER' facsimile receiver type K441-CH and transmitters K400 AMCH in stock in excellent condition.

DC POWER SUPPLIES

1. APT. 10459/8. Stabilised Regulated supplies. New stock arrival hence LOWER PRICES. Available in preset output voltages between 6 and 30V DC (state requirements) ±4V approx. Three sizes available, 5A, 7.5A & 10A. Prices £20, £25 & £30 respectively (plus postage £2, £2.50 and £4).

2. Mullard Dual supplies. Pos/Neg 12V @ 1A & 0.4A. Dimensions 9x4x5". £10 ea. (+£1 p&p).

3. Farnell Current limited. 13-17V DC @ 2A. £15. 27-32V DC @ 1A. £15 (+£1 p&p).

4. Lambda LXS Series supplied 110V AC Input. 5V @ 14A. £20 (+£2.50 p&p). Various other voltages available from stock in small quantity.

5. Coutant 5/6V @ 5A. Small size (7x5x3"). £20 (+£1).

6. Variable 0-30V @ 1A. Volt-metered. £30.

7. Farnell 5V Switching. 60A. £85.

RF SIGNAL GENERATORS

ADVANCE Type E2. 100kHz-100MHz. Internal AM & Audio O/P. 1uV-100mV output. Price each £50 inc. VAT.

TAYLOR Type 68A/M. 100kHz-240MHz. Internal Modulation. £80 inc. VAT.

All of these units are in full working condition and carry our usual 90-Day Warranty. In both cases please add £2 each for carriage.

MILLI-VOLT MEASUREMENT, ANALOGUE

MARCONI TF2600. Twelve ranges 1mV-300V FSD. Wide-band to 10MHz.

MARCONI TF2603. Frequency range 50kHz-1.5GHz. High Sensitivity from 300uV.

MARCONI TF2604. Electronic Multi-meter. AC/DC 300mV Full scale to 300V (1kV DC). Resistance ranged. AC Frequency range 20Hz-1500MHz.

BRUEL & KJOER

Model 2006 Heterodyne Voltmeter. AM/FM/Voltage measurements to 240MHz.

CLAUDE LYONS 240V AC REGULATORS

Small quantity available of constant voltage mains regulators. Continuous current rating 5A. Model no. CVR-1200. Input 204-252V. Output adjustable 200-254V AC ± 0.3%. 45-65Hz. Condition as new. (Dims- 11"x7"x6"). Weight 20Kgs). Price £95 ea. + Carriage £5.

ROTRON INSTRUMENT COOLING FANS

Supplied in excellent condition, fully tested.

115V, 4.5x4.5x1.5" £4.50. 230V £5. 115V. 3x3x1.5" £4 + postage ea. 35p.

Also brand new 230V at £6 ea. www-10

PAN & TILT HEADS were used for CCTV Cameras heavy duty weight about 75 lbs will give 360° Pan & Tilt as two reversible 240v motors approx height 19" will adapt for Dish mount, ext soiled due to outdoor use, £65. VIDEO TAPE REC Philips type N1500 colour, RF in out, cassette type with circ £85. MAINS CONV. 24v DC I/P O/P 230v AC 50c/s 140 watts sine wave rotary type, £45. RADIOSONDE UNITS British Mk. II new cond. with chart & circ req 90/2v DC Tx on 27 Mc/s, £7.50. TEST SET. CT373 Audio bench T.S. AF Osc 17c/s to 170Kc. O/P var 300 Uv to 10v RMS into 600 ohm, Valve Voltmeter 30 Mill/V to 100v FSD in 7 ranges, Distortion meas set 20c to 20Kc, 3 ranges 10, 30 & 100% new condition with handbook & leads for 200/250v, £115. HIGH VOLTAGE TS 240 I/P O/P 15/20 or 25Kv in fitted wood case size 9x7x13" with leads, uses vibrator contact breaker, £27. MARCONI TF1102 ext AM modulators will handle sine, sq or video up to 300Mc/s with book, £25. FREQ CONV. I/P 240v O/P 115v 400c/s 1 phase sine wave 100 watts new solid state unit by Roband, £115. OSC AMP UNIT comprises 150 watt valve amp & var freq AF Osc 30c to 30Kc as O/P voltmeter and adjustable O/P impedance down to 16.7 ohm for 240v in table case, £115. TRIX A/C CABIN SPK UNITS size 17x3 1/2x2 1/2" as 4x3x3" 3 ohm spk units, £6.50. POWER UNITS 240v I/P provides O/P of 28v DC up to 15 amps semi reg load range 4/15a complete in case 7x7x16", £38. METERS Record circa scale 200/250v 50c size 4x4x3 1/2" new, £15. Also freq meters 45/65c/s 230v 2 1/2" dia, £11.50. Also misc panel meters mixed 4 for £6.50. COAX CABLE UR57 HD 75 ohm 10mm osd, £4.50 for 10mt, 30p mt over this new. RTTY TERM UNIT Redifon CSF unit 445/470kc reqs 25 Mill/V drive from 50 ohm, shift 400/1000c/s, standard 80-0-80 O/P reqs ext power unit with handbook good cond., £65. RECT. No. 7 110/200/250v or 12v DC I/P provides 80-0-80v at 30Ma, 12v etc can also be used to give 240v AC O/P from 12v DC I/P up to 40 watt in fitted wood case with circ, £8.50. H.F. Tx AMP UNITS ex A/C TX 2/18Mc/s 100 watts inc two 4X150s req ext drive & power with circ etc in case 8x8x12 1/2", £27. CCTV System Philips medical system with high grade lens & Plumbicon tube, 19" mon cable, etc, with circs., £165. METER O/100 amps DC with shunt 4 1/2" £11.50. AERIALS Army 60 meter wire dipoles new £6.50. Also PYE 70/73Mc/s Ground plane aerials new 50 ohm £25 callers. MORSE KEYS min type for A510 new cond., £3.50. Misc items for callers. Parts from old Marc HF 5 Kw Tx, inc 4uf 6kv conds, parts from Marc, etc., Radar Speed meas equip.

Above prices incl. Carr./VAT, goods ex equip. unless stated new, allow 14 days for delivery. SAE with enquiry or 2 x 15/p stamp for List.30.

A.H. SUPPLIES
 122 Handsworth Road, Sheffield S9 4AE
 Telephone: (0742) 444278

Happy Memories

Part Type	1 off	25-99	100 up		
4116 200ns	.90	.81	.78		
4116 250ns	.70	.63	.60		
4816 100ns For BBC comp.	2.25	2.01	1.95		
4164 200ns	3.99	3.56	3.42		
2114 200ns Low power	1.15	1.00	.90		
2114 450ns Low power	.95	.85	.80		
4118 250ns	3.35	3.00	2.85		
6116 150ns CMOS	3.55	3.20	2.95		
2708 450ns	2.35	2.10	2.02		
2716 450ns 5 volt	2.60	2.25	2.10		
2716 450ns three rail	5.75	5.00	4.65		
2732 450ns Intel type	3.50	3.15	3.00		
2532 450ns Texas type	3.70	3.30	3.00		
Z80A-CPU	£3.95	780A-P10	£2.99	Z80A-CTC	£2.99
6522 PIA	£3.70	7002 A-D	£4.60	3691	£2.75
88LS120	£2.20	7805 reg	.50	7812 reg	.50
Low profile IC sockets:	Pins	8 14 16 18 20 22 24 28 40			
	Pence	9 10 11 14 15 18 19 25 33			
Soft-sectored floppy discs per 10 in plastic library case:					
5 inch SSSD	£17.00	5 inch SSDD	£19.25	5 inch DSDD	£21.00
		5 inch DSQD	£26.35		
8 inch SSSD	£19.25	8 inch SSDD	£23.65	8 inch DSDD	£25.50
74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.					

Please add 50p post & packing to orders under £15 and VAT to total Access & Visa welcome. 24hr service on (054 422) 618 Government & Educational orders welcome, £15 minimum Trade accounts operated, 'phone or write for details

HAPPY MEMORIES (WW)
 Gladestry, Kington
 Herefordshire HR5 3NY
 Telephone: (054 422) 618 or 628

C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG
Tel. 01-747 1555/01-994 6275. Telex: 291429

9.30am-6pm
MON. to SAT.
CONTINUOUS

Stabilised Power Supplies.
Switched-mode and Linear.
Brand New, Unbeatable Prices.
Hundreds in stock.
Coutant, Gould, Lambda, Farnell, ITT, Gresham etc.
S.A.E. for latest list.

POWER SUPPLY UNITS							
Supplier	Volt	Amps O/H	Price	Supplier	Volt	Amps O/H	Price
COUTANT 240							
ASC200	18	2A 5	22.00	GRESHAM			
ASA1000	5	10A 8	40.00	30/1	12	3.0A 3	31.00
ASB200	12	2A 6	16.00	GX15/2	15	2A 4	26.00
	6	5A 6	28.00	GX60/2C	60	2A 2	28.00
ATB200	15+15	2A 1	16.00	GX15/5B	15	5A 1	35.00
ICL035	10	2A 1	14.00	GX033	12	1A 1	
ASA500	6	5A 2	28.00	ELEC/ASSO			
ASA1000	5	10A 12	44.00	10/0017	12	1A 2	
ASA20018	16-24	2A 1	18.00	GOULD 110			
ASA5006	3-8	5A 2	26.00	MG5	5	60A 27	95.00
QA2	15	0.1A 217	12.00	MG24	24	8A 44	41.00
QA5	12	1A 3	14.00	ADVANCE			
IC200	5	2A 4	16.00	PMA35	15	5A 16	32.00
ED500	12	5A 1	24.00	PMA34	30	10A	79.00
SOL20/5	5	20A 1	80.00	PMA17	7	3A 10	24.00
				PMA46	50	1A 32	28.00
LAMBDA							
LMCC28	30	3A 1	22.00	COUTANT			
LOTX5152	12	0.5A 1	15.00	KSG500	6	5A 1	27.00
LJ51150V	5	20A 1	42.00	ASA1000	5	10A 59	44.00
LOSY5	5	6A 2	28.00	OA2		1A 4	
LXSA5	5	4A 16	22.00	OA3	+/-12-15	2.5A 11	18.00
LM219263	22-32	1A 1		ESM3	12-24	3A 4	21.00
LM219v	22-32	1.2A 1	24.00	ESM7	12-24	7A 1	36.00
				ESM15	12-24	15A 12	49.00
FARNELL							
15/25	15	2A 56	18.00	IC200	5	0.3A 4	16.00
15/25	6	15A 1	62.00	LXSCC50V	5	16A 11	60.00
15/25	28	10A 2	52.00	LMCC20	20	5A 1	43.00
A15	12-17	0.1A 8	12.00	LAMBDA			
15/25	15	2A 19	18.00	LXSC12R	12	6.5A 3	44.00
30/15	20	1A 26	15.00	LGSC24	24	3.6A 19	26.00
A15		25	15.00	LMD20	20	7.5A 2	36.00
APTTSU	20	3A 2	24.00	LXDD152R	7.5	5A 3	43.00
73SC	5	3A 211	15.00	LXDD152R	12-15	6.2A 9	48.00
SSB MH	40	2A 1		LXB12R	12	3.8A 1	28.00
VOLSTAT	9-5	3.5A 2	21.00	LXSD15R	15	14A 1	60.00
				LMMCC5	5	10A 1	48.00
ITT							
MR20AS51	5	20A 4	45.00	LXSA50VR	5	4A 14	27.00
MR5AS51	5	5A 1	30.00	FARNELL			
MQ10AS15	15	10A 2	48.00	15/25	15	2A 3	18.00
MQ3BS301	30	3A 2	20.00	5D15002T	5	150A 1	14.00
MR10AS4	4-5	10A 2	44.00	NCR/31505059	4	15A 1	38.00
MQ5AS151	15	5A 2	24.00	GOULD/MG5	5	40A 47	80.00
PC250A15	+/-12-15	2.5A 1	15.00	ACO/SE50	5	100A 1	8.00
DIGIVUE		2		ITT/PM65A151	15	65A 12	8.00
AE00101	24	3.5A 5	64.00	APT13334	+20v	5A 1	35.00
BRANDENBURG							
374		20	30.00	374	117	45	30.00
375		2	30.00	375	117	7	30.00
376		4	30.00	376	117	5	30.00
				388A	117	1	30.00
GOULD							
MG24	24	15A 20	48.00	LAMBDA			
				LXSDSOVR	5	27A 33	84.00
				LMD28	28	6A 1	40.00
				LXSCC5R	5	16A 1	
				LXSCC12R	12	10A 1	48.00
				LXDC152R	12-15	2.5A 1	26.00

WELWYN STRAIN GAUGE.
(Precision Micro-Measurements). Romulus Mican type MA-09-500B4-350. Our price £1.25 ea. List price £3.85. Large quantities available.

Also
Large stocks of relays, ribbon, multicore cables. S.A.E. or phone for lists and prices.

D TO A CONVERTERS 15MHz, 8 BIT

By Micro Consultants Ltd, 50Ω cable drive op. Linearity 0.25%, max. 0.125% typ. Settling time; 2V step 70nS typ. 2MV step 50nS colour television transmission standard. Diff. gain 0.5% diff phase shift 0.5% types rad 802 and MC2208/8. Unused. Ex-maker's pack.

SPECIAL OFFER PRICE £10.00

TRANSFORMERS	
3-0-3V 100mA	£1.06
5-0-5V 400mA	£1.25
6-0-6V 100mA	£1.14
6-0-6V 250mA	£1.16
0/6-0/6 280mA	£2.00
8-0-8V 400mA	£1.25
9-0-9V 75mA	£1.14
9-0-9V 3A	£3.00
11V 2A, 22V 1A	£2.00
12-0-12 50mA	£1.18
12-0-12V 100mA	£1.48
12V 130mA	£0.80
12-0-12V 250mA	£1.94
12V 1A5	£1.25
13V +6.5V Sec 2 Amp	£2.00
0-12-0-12 96VA	£8.00
15V 100mA	£1.00
0/12-0/12 500+500mA	£2.96
9-0-9V 1 Amp	£2.64
12-0-12V 1 Amp	£3.36
15-0-15V 1 Amp	£3.62
15V 100mA	£1.00
17V 300mA	£1.50
30,24,20,15,12,2 Amp	£4.84
6.3V 1.5 Amp	£2.64
6-0-6V 1.5 Amp	£3.20
20-0-20 400mA	£1.80
22-0-22 50mA	£1.00
24V 100mA	£1.00
24V 250mA	£1.50
25V +6.2V Sec 1.6 Amp	£1.90
30,24,20,15,12,2 Amp	£7.96
9-0-9 2 Amp	£4.70
12V 2 Amp	£4.84
20-0-20V 2 Amp	£6.98
30-0-30V 2 Amp	£7.96
30V 250mA	£1.50
30-25-0-25-30 1A6	£6.00
0-2-4-6-8-10 5A	£6.00

☆ ☆ ☆ ☆ ☆ ☆ ☆
Switchcraft Cannon Connectors 3-pin plug. Free hanging £1.20
A3F 3-pin socket. Free hanging with lock. £1.32
D3F 3-pin Socket. Female chassis mounting with lock £1.60
D3M 3-pin Socket. Male chassis mounting £1.10
Switchcraft XLR Connectors always in stock. Discounts on quantity.

BLACK PLASTIC BOXES
75x50x25mm £0.65
80x60x40mm £0.92
90x70x40mm £0.99
115x75x30mm £0.90
110x90x45mm £1.18
170x100x50mm £1.65
200x120x80mm £3.55

FILTERS
3 Phase 20 AM Filters 433V £1.80
50/60Hz Phase to Phase 250V AC 50/60Hz Phase to Neutral mfr. by Corcom Chicago Il., USA., £15 each.
Single Phase Filter 30 Amps 125V 60Hz by Potter £5.00
Sprague Filter 2 x 30 Amp 250V AC 60Hz £10.00
Erie Mains Filters 3 and 5 Amp 250V AC 50Hz £4.00
All the above mentioned Filters are brand new. Carriage extra.

SPECIAL OFFER! 0.1% TOL resistors. The following values available. 2K, 3K, 10K, 30K, 1 Mega ohms. Welwyn or Filmet. Price 30p each.

CERMET PRESETS 15p each
10A 250V AC ILLUMINATED ROCKER SWITCH
Red, DP ST 26x30mm rectangular snap-in type. £0.75
16A 250V AC ILLUMINATED ROCKER SWITCH
(Amber). 14x30mm rectangular snap-in type. SPST £0.30
LICON ILLUMINATED SWITCHES
01-800 Rectangular snap-in series 2PCO Latching £1.50
2PCO Momentary £1.50
Indicator only £0.50
Lenses available in red or white only.

MAIL ORDER: Gds + 15% VAT, plus VAT-inclusive Ad M/pkg/post:
1/4Kg 1.30 4Kg 3.50
1/2Kg 1.70 5Kg 4.20
3/4Kg 2.20 6Kg 4.40
1Kg 2.55 6-10Kg 5.00
2Kg 3.00 Over 10Kg: Quote
3Kg 3.45

VIDEO GAME BOARD
FIELD GOAL VIDEO GAME
by Taito a top quality board, complete with 6800 CPU system system with 2715 EPROMS with circuit diagram plus all connections for either colour or Black & White monitors (TV Sets). Price £20.00 + VAT £3, P&P £2.55

POWER SUPPLY KIT
to suit + circuit diagram.
Price: £15.00
+ VAT £2.25, P&P £3.45

2x22 Way Gold Plated Double Sided D.156" edge Connectors to suit Video Boards.
Price: £1.60 per pair.
+ VAT 24p P&P included
The Complete Kit £46.00 inc. ☆
Full Details on Application.

ALUMINIUM BOXES	
AB7 5.25x2.50x1.50in. (133.4x63.5x38.1mm)	£0.96
AB8 4x4x1.5in. (101.6x101.6x38.1mm)	£0.96
AB9 4x2.25x1.5in. (101.6x57.2x38.1mm)	£0.96
AB10 4x5.25x1.5in. (101.6x133.4x38.1mm)	£1.12
AB11 4x2.50x2in. (101.6x63.5x50.8mm)	£0.96
AB12 3x2x1in. (76.2x50.8x25.4mm)	£0.70
AB13 5x4x2in. (152.4x101.6x50.8mm)	£1.38
AB14 7x5x2in. (177.8x127.0x50.8mm)	£1.64
AB15 8x6x3in. (203.2x152.4x76.2mm)	£1.98
AB16 10x7x3in. (254.0x177.8x76.2mm)	£2.70
AB17 10x4.50x3in. (254.0x114.3x76.2mm)	£2.28
AB18 12x5x3in. (304.8x127.0x76.2mm)	£2.52
AB19 12x8x3in. (304.8x203.2x76.2mm)	£3.04
BLUE REXINE. COVERED ALUMINIUM BOXES	
RB1 6x4.50x2.5in. (152.4x114.3x63.5mm)	£1.96
RB2 8x5x3in. (703.2x127.0x76.2mm)	£2.52
RB3 9x5x3.50in. (228.6x127.0x88.9mm)	£2.72
RB4 11x6x4in. (279.4x152.4x101.5mm)	£3.14
RB5 11x7.50x4.50in. (279.4x190.5x114.3mm)	£3.98

This advertisement is mainly of our excess stockholding. We also have excellent stocks of semiconductors, hardware, cables etc. etc. Four further details send for our lists and retail price catalogue, phone or visit our shop. All prices are exclusive of VAT (and P&P) Minimum Mail Order £5.00 + P&P + VAT. Government departments, schools, colleges, trade and export welcome.

WW - 076 FOR FURTHER DETAILS

OPUS SUPPLIES SPECIAL OFFERS

DISC DRIVE DISCOUNTS

SCOOP
PURCHASE

- ★ FD 514—8in. S/S D/D DRIVE FORMATTED 600KBYTE £149
- ★ FD 650—8in. D/S D/D DRIVE FORMATTED 1.2 MBYTE £199
- ★ CASE TO HOLD TWO DRIVES WITH COSSOR POWER SUPPLY FAN AND CARRYING HANDLES—BRAND NEW—ONLY £99.95

A Special Purchase allows us to offer a limited quantity of these items at this remarkable price. The drives are manufactured by Pertec — are Shugart compatible and have a 90-day warranty.

5¼in. DISC DRIVES

CANNON S/S D/D 40-TRACK
Formatted 175kByte - ONLY £129.95
TEAC 55F D/S 80-TRACK - Formatted
density 00k - double density 800k
ONLY £229

- ★ Ideal for use with BBC and other leading micros
- ★ Full warranty
- ★ Slimline latest technology
- ★ See us at Midland Computer Fair
28-30 April — Stand 508 ★
Bingley Hall, Birmingham

★ 22IN. RGB COLOUR MONITOR ★ ONLY £99.95

Stocks of our 22-inch Uncased Colour Monitor are now diminishing fast — to avoid disappointment order now!

NEW

THE MAGIC BOARD

STOP
PRESS

Add-on memory for your BBC MICRO


Simply plug into a spare Eprom socket — fits inside your micro. Gives up to 16k of additional ram — 64k of Eprom. Takes the following 2716/2732/2764/6116/5516. Supplied with full software instructions. ONLY £29.95

To order add carriage at the following rates: Monitor £10, Drives and Case £7, Board free; and V.A.T. at 15% to total; send your order to: OPUS SUPPLIES, 10 BECKENHAM GROVE, SHORTLANDS, KENT.

TELEPHONE: 01-464 5040 or 01-464 1598



WW — 062 FOR FURTHER DETAILS

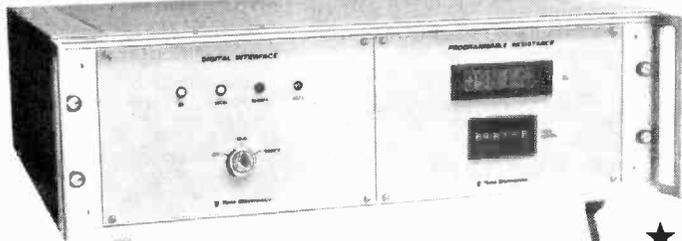

IEEE PROGRAMMABLE LOW OHM RESISTANCE 9819

IEEE-488

- ★ PLATINUM RESISTANCE THERMOMETRY
- ★ 0.01 OHMS-10KOMS

Other IEEE programmable units, Power Supply, Precision Voltage and Current sources, 24 way relay switch, AC/DC Voltage Calibrator, Screwdriver.

TIME ELECTRONICS LIMITED, BOTANY INDUSTRIAL ESTATE, TONBRIDGE, KENT
Telephone: 0732 355993. Telex: 95481

WW — 039 FOR FURTHER DETAILS

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner
Telephone 445 2713/0749 (9461)

WW — 024 FOR FURTHER DETAILS

Spring Reductions

on the following items ex stock:

MARKER SLEEVING (Nova), colour coded, most sizes and materials; competitive prices
CARTRIDGE FUSES (Beswick), good selection of types and ratings at discount prices (30%)
AUDIBLE WARNING DEVICES (Besson) Solid-State Banshees, Cyber-tones, Bleeptones, Bleeptester, etc.
SAMPLES if any at quantity rate
WIRE WOUND RESISTORS (Osborne), 5W, 7W, 11W, 17W; 116 different values and ratings in stock at special prices
ELMA RANGE of knobs and accessories; lowest prices
CRIMP TERMINALS, small or large quantities
CARBON FILM RESISTORS; 4,000,000 must go, mainly ¼W and ½W; also available: ½W, 1W and 2W; really low prices.

Write, call or phone (0732) 851345
NOVAPRODUCTS (ABP Ltd.)
Crystalate Works, Golden Green
Tonbridge, Kent TN11 0LH

WW — 064 FOR FURTHER DETAILS

EX-STOCK TRANSFORMERS

Despatch by return

OTHER PRODUCTS

OVER 150 TYPES OF TRANSFORMER STOCKED

PLUGS - SOCKETS - BOOKS - SEMI-CONDUCTORS - VALVES

MAINS ISOLATORS			
Ref.	VA (Watts)	£	P&P
07★	20	5.32	1.50
149	60	8.84	1.60
150	100	10.06	1.84
151	200	13.69	2.12
152	250	16.31	2.24
153	350	20.34	2.12
154	500	25.02	2.90
155	750	35.91	OA
156	1000	45.89	OA
157	1500	60.52	OA
158	2000	72.43	OA
159	3000	101.12	OA
161	6000	203.65	OA

★ 115 or 240v sec only. State volts required. Pri 0-220-240V.

12 or 24-VOLT RANGE			
Ref.	12v	24v	£ P&P
242	0.3	150mA	2.41 .90
213	1	0.5	3.19 1.20
71	2	1.0	4.25 1.20
18	4	2.0	4.91 1.60
85	5	2.5	6.78 1.50
70	6	3.0	7.69 1.40
108	8	4.0	8.98 1.60
72	10	5.0	9.82 1.80
116	12	6.0	10.89 1.90
17	16	8.0	12.97 2.12
115	20	10.0	17.46 2.44
187	30	15.0	21.69 2.64
226	60	30.0	44.45 OA

2x24V windings Pri 220-240V

50 VOLT RANGE			
Ref.	50v	25v	£ P&P
102	0.5	1	4.13 1.40
103	1	2	5.03 1.40
104	2	4	8.69 1.84
105	3	6	10.36 1.90
106	4	8	14.10 2.12
118	6	12	18.01 1.84
118	8	16	24.52 2.70
119	10	20	30.23 OA
109	12	24	36.18 OA

EDUCATIONAL METERS. i) 0-10A; ii) 0-30V; iii) 0-2A 75 x 78mm free-standing. Top screws terminal. £4.50 + 66p p&p + VAT

30 VOLT RANGE			
Ref.	30v	15v	£ P&P
112	0.5	1	3.19 1.20
79	1	2	4.32 1.40
3	2	4	6.99 1.60
20	3	6	8.10 1.85
21	4	8	9.67 1.90
51	5	10	11.95 2.00
117	6	12	13.52 2.02
88	8	16	18.10 2.26
89	10	20	20.88 2.24
90	12	24	23.20 OA
91	15	30	26.60 OA
92	20	40	35.64 4.83

60 VOLT RANGE			
Ref.	60v	30v	£ P&P
124	0.5	1	4.70 1.50
126	1	2	7.15 1.50
127	2	4	9.20 1.90
125	3	6	13.31 2.02
123	4	8	15.15 2.26
40	5	10	19.16 2.24
120	6	12	21.86 2.64
121	8	16	30.72 OA
122	10	20	35.76 OA
189	12	24	41.22 OA

CASED AUTOS			
VA	Price	P&P	Ref
20	£7.21	1.25	56W
80	£9.35	1.50	64W
150	£12.10	1.84	4W
250	£14.73	1.60	69W
500	£22.14	2.24	67W
1000	£33.74	2.80	84W
2000	£60.47	OA	95W

240V cable input USA 115v outlets

LOW COST SOLDERING IRONS TO BS SPEC 240V £1.75. Also 12V £1.90 + 30p P&P + VAT 15%.

SCREENED MINIATURES			
Ref.	mA	Sec Volts	£ P&P
238	200	3-0-3	3.11 .90
212	1A, 1A	0-6, 0-6	3.45 1.20
13	100	9-0-9	2.59 .80
235	330, 330	0-9, 0-9	2.41 .90
207	500, 500	0-8-9, 0-8-9	3.36 1.20
208	1A, 1A	0-8-9, 0-8-9	4.27 1.40
236	200, 200	0-15, 0-15	2.41 .90
239	50MA	12-0-12	3.11 .90
214	300, 300	0-20, 0-20	3.39 1.20
221	700 (DC)	20-12-0-12-20	4.13 1.20
206	1A, 1A	0-15-20, 0-15-20	5.60 1.60
203	500, 500	0-15-27, 0-15-27	4.83 1.50
204	1A, 1A	0-15-27, 0-15-27	7.30 1.60

AUTO TRANSFORMERS			
Ref.	VA (Watts)	TAPS	£ P&P
113	15	0-10-115-210-240V	2.39 1.20
64	80	0-10-115-210-240V	4.84 1.40
4	150	0-10-115-200-220-240V	6.48 1.60
67	500	0-10-115-200-220-240V	13.30 2.24
84	1000	0-10-115-200-220-240V	22.70 2.80
93	1500	0-10-115-200-220-240V	28.17 OA
95	2000	0-10-115-200-220-240V	42.14 OA
73	3000	0-10-115-200-220-240V	71.64 OA
80	4000	0-10-115-200-220-240V	93.01 OA
57	5000	0-10-115-200-220-240V	108.30 OA

400/440V ISOLATORS			
VA	Ref.	£	P&P
60	243	8.11	1.50
250	246	16.07	OA
350	247	19.88	OA
500	248	24.77	OA
1000	250	50.53	OA
2000	252	74.79	OA
3000	253	104.86	OA
6000	254	207.92	OA

BURGLAR ALARMS Ultrasonic portable, robust, looks like a speaker NO INSTALLATION COST. £99 P&P £4.50 + VAT 15%.

Constant Voltage Transformers Spike-free Mains. 500VA £198.00 + Carriage 1kVA £278.00 + VAT 15%

AVOs & MEGGERS (FULL RANGE ACCESSORIES)		
NEW RANGE:		
2000 Hand Held DMM 3 1/2 LCD	8 Mk. 5 latest Model	£122.10
1000V, 2A AC/DC, 20m. res.	71 (Handy)	£49.30
diode test; cont. buzzer, fused	73 (Portable Size)	£68.90
£71.40.	MM5 Minor	£43.80
2001 1000V 10A AC/DC/20m. res., safety fuses, £87.40.	DA211 LCD Digital	£58.50
2002 Vehicle Testing, DC to 20A, 1500A with probe, 200V	DA212 LCD Digital	£81.90
DC 500V AC 200k res., buzzer	DA116 LCD Digital	£131.30
continuous. £99 + P&P + VAT 15%	DA117 Autorange LCD	£157.00
	Megger 70143 500V	£101.50
	Megger Battery BM7	£11.80
	P&P £1.60 + VAT 15%	

PANTECH METER BANANA - Shockproof: cont buzzer and batt. check 20KΩ/V DC, AC 10KΩ/V DC to 500V AC, 750V DC to 2.5A. Res. to 3MΩ. Acc. 2% DC, 4% AC. 173x86x29mm, soft case £17.95. Retracting leads. P&P £1.20 + VAT.

Sensitivity: 2,000Ω/V. Voltage to 1000V AC/DC. Resistance 0-200K with inst. batt 5KΩ Centre Scale. DC current to 100ma. Size 95x65x30mm. Complete with leads, battery and instructions, small enough to slip in a pocket. £6.04 + 83p p&p + VAT 15%.

ANTEX SOLDERING IRONS 15W CCN240 or C240 £5. Safety stand £1.75 25W X25 £5.30 12V 25W car soldering iron kit £5.30 P&P 50p + VAT 15%

Precision De-Solder Pumps for one hand working. Large £6.23. P&P 35p + VAT. Small £5.42. P&P 30p + VAT.

Cable: Coax, mains, multicore, screened, equipment wire.

PANEL METERS 43x43 mm ...£6.70 0.50µA, 0.1mA + VAT 82x78 mm ...£7.37 0.30V, 100nA, 100mA, 1A, 5A, 10A, 15V, 100V available + VAT

MAINS BATTERY ELIMINATORS Ready to plug into 13A socket. 3, 4.5V, 6, 7.5V, 9, 12V DC @ 300mA £5.10 + £1.20 P&P + VAT 15%.

1/4W METAL OXIDE RESISTORS £1/100 Special Offer TR4 5% Electrois (100s only) 47Ω - 75Ω 180Ω - 360Ω - 390Ω - 430Ω - 470Ω - 510Ω - 560Ω - 820Ω - 1K 1K2 - 1K3 - 1K6 - 1K8 - 2K - 2K4 - 3K - 16K - 20K - 22K - 24K - 27K - 47K - 82K - 100K - 110K - 120K - 130K - 180K - 220K - 270K - 300K. P&P 30p + VAT

Barrie Electronics Ltd. 3 THE MINORIES, LONDON EC3N 1BJ TELEPHONE 01-488 3316/7/8 NEAREST TUBE STATIONS: ALDgate & LIVERPOOL ST. WWW.6

OVERSEAS ENQUIRIES WELCOMED Prices correct at time of print


WW - 005 FOR FURTHER DETAILS

CX80 COLOUR MATRIX PRINTER

New low price £795 + V.A.T.

At last a low-cost Colour Matrix Printer for Text, Graphics, Histograms, Colour VDU Dumps, etc.

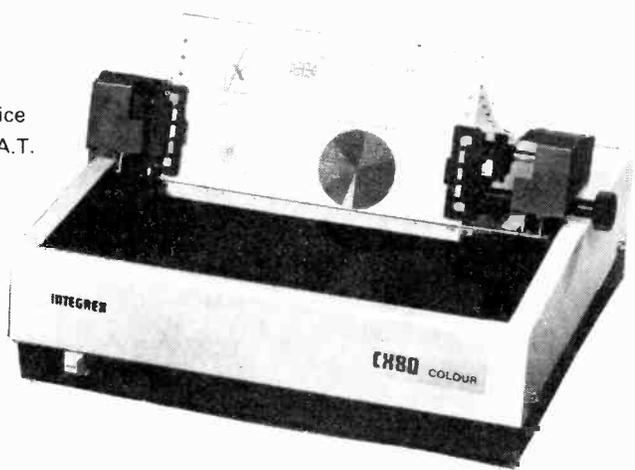Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.



Compatible with most microprocessors, prints in 7 colours - sophisticated internal programme makes the CX80 easy to use.

Dot Addressable + 15 user programmable characters, 96 ASCII and 64 graphics characters in rom. Centronics interface with RS232 and IEEE488 options. Apple II interface gives dot for dot colour dump. New viewdata interface prints out two pages side by side in full colour. See Prestel 200650.

The CX80 is a product of our own design and development laboratories. It represents a British breakthrough in colour printer technology. Colour brochure on request. OEM pricing available.

INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432. Telex: 377106

DC MICROVOLT METER

NEW



TYPE TM8 £120
+ p&p + VAT

VOLTAGE RANGES
±3μV, ±10μV, ±30μV ±300V.
Accuracy ±1.5% rdg. ±1.5% range ±0.15μV.
Drift <0.1μV/°C. Noise <0.3μV p-p on 3μV.
Input resistance 100M on V, (mV); 1M on mV, μV.

CURRENT RANGES
±3pA, ±10pA, ±30pA ±300nA.
Accuracy ±2% rdg. ±1.5% range ±0.2pA.
Drift <0.3pA/°C. Noise <0.5pA p-p on 3pA.

LIN/LOG RANGES
On mV, μV and nA, pA LOG ranges
±30% fsd equals ±3μV and ±3pA approx.
±60% fsd equals ±30μV and ±30pA approx.
±100% fsd equals ±300mV and ±300nA approx.
On V LOG the voltages are 1000 times greater.

RECORDER OUTPUT
±300mV at fsd. Source resistance 4.7kΩ

POWER SUPPLY
One type PP9 battery or equivalent, life 1000 hrs.

SIZE & WEIGHT
180 × 260 × 140mm. 3kg. Meter scale 120mm.


Send for data covering our range of instruments

LEVELLE ELECTRONICS LTD.

Moxon Street, High Barnet, Herts. EN5 5SD
Tel. 01-449 5028, 440 8686

WW - 006 FOR FURTHER DETAILS

Toroidal Transformers

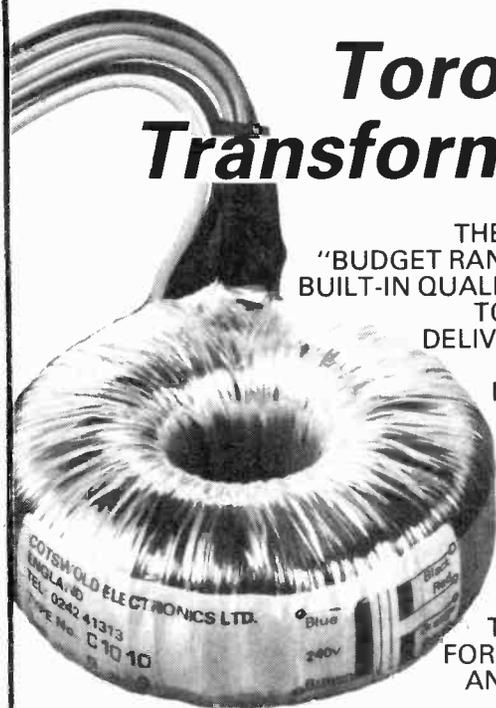

THE COTSWOLD
"BUDGET RANGE" OFFERS
BUILT-IN QUALITY COUPLED
TO A RELIABLE
DELIVERY SERVICE
MOST TYPES
FROM STOCK

IEC 65
VDE 0550
BS 415
TO ORDER

PHONE
TELEX, WRITE
FOR DATA SHEET
AND PRICE LIST

Cotswold Electronics LTD.

Unit T1, Kingsville Road, Kingsditch Trading Estate, Cheltenham GL51 9NX

Tel: 0242-41313

Telex: 897106

Sales Office in U.S.A.
AVEL LINDBERG INC.
Peacock Alley 116, 1 Padanaram Road, Danbury, CT 06810 U.S.A.
203-797-8698. Telex: 710-456-9984

WW - 077 FOR FURTHER DETAILS

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

**AUDIO FREQUENCY
TRANSFORMERS OF EVERY TYPE
YOU NAME IT! WE MAKE IT!
OUR RANGE INCLUDES**

Microphone transformers (all types), Microphone Splitter/Combiner transformers, Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.

We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E.E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.

E. A. Sowter Ltd.


Manufacturers and Designers

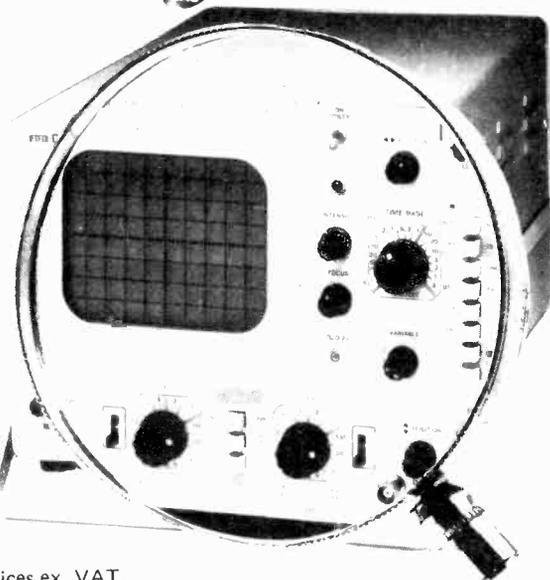E. A. SOWTER LTD. (Established 1941) : Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
P.O. Box 36, Ipswich, IP1 2EL, England
Phone: 0473 52794 and 0473 219390
Telex 987703G Sowter

WW - 030 FOR FURTHER DETAILS



YOU DON'T NEED ME TO DETECT CROTECH'S VALUE



Prices ex. VAT.

It's elementary. Just look at the **3030** at £154 and the **3131** at £250, both are 15MHz scopes with 5mV/Div maximum deflection coefficient. And the Dual Trace 3131 has matched X-Y, Algebraic Add and Subtract, and TV Trigger, all selected on easy to use clearly marked push buttons.

But that's not all, both incorporate a Component Tester, yes, even the Single Trace 3030, for the in or out of circuit testing of semiconductor and passive devices. With the resultant characteristic being displayed directly on the CRT.

There's only one thing left to say . . .
Do you want a Violinist?

For full details just fill in the enquiry card or call us direct.

Crotech Instruments Limited

5 Nimrod Way · Elgar Road · Reading · Berkshire
RG2 0EB · United Kingdom

Telephone: (0734) 866945 Telex: 847073 POWLIN G

WW - 038 FOR FURTHER DETAILS



Digital Audio Test Set

Imagine the ideal hand held test set. A minimum of controls. An oscillator that covers the audio spectrum in a single sweep. A level meter that measures directly in dBs over 74dBs. And a frequency counter that reads the oscillator or meter input.

Small enough to operate anywhere, and precise enough for any professional application.

The Loft TS1 is manufactured by the Phoenix Audio Laboratory Inc., and distributed exclusively by Turnkey.

It's price £249.00.
Call us now for more information.

turnkey

Brent View Road LONDON NW9 7EL
01-202 4366

WW - 079 FOR FURTHER DETAILS

MANUFACTURERS & DISTRIBUTORS

MICROSWITCHES V3 TYPE. We have in stock over 50,000 various types, i.e. Button, Lever and Roller. Low force or standard allow us to quote against your requirements.

MATSUSHITA HIGH-QUALITY 12-VOLT DC CASSETTE DRIVE MOTORS. Size 30mm dia. x 20mm high, drive shaft 7mm long x 2mm dia. approx. No load current, 40 m/a £13.50 for 50 + V.A.T.; £24 for 100 + V.A.T.; £108 for 500 + V.A.T.; £190 for 1,000 + V.A.T.; £875 for 5,000 + V.A.T.; £1,600 for 10,000 + V.A.T. Sample 10 sent for £3 + £1 P. and P. (£4.60 inc. V.A.T.).

AUTONNIC PUSH-BUTTON TUNER. 4 x Med. Wave, 1 x Long Wave plus manual control. Overall length 14cm, depth 5cm, height 33mm. Excellent unit for the manufacture of a competitive car radio. £15 for 10 + V.A.T.; £68 for 50 + V.A.T.; £125 for 100 + V.A.T.; £565 for 500 + V.A.T.; £1,020 for 1,000 + V.A.T.; £2,300 for 2,500 + V.A.T. Sample sent for £2 + £1 P. and P. (£3.45 inc. V.A.T.).

BRITISH-MADE TRANSFORMER. Input 240V at 50HZ, output 12V 0-12V, 1/2 amp with built-in thermal overload output, p.c. mounting; £25 for 10 + V.A.T.; £115 for 50 + V.A.T.; £210 for 100 + V.A.T.; £950 for 500 + V.A.T.; £1,700 for 1,000 + V.A.T. Samples sent for £3 + 75p P. and P. (£4.31 inc. V.A.T.).

150-WATT HINCHLEY DROP-THROUGH TRANSFORMER. Input 220/240V. A.C., output 30-0-30 with 14V tap width 96mm x 80mm x 54mm deep inc. winding, etc., 90mm, approx weight 2.7 kgs.; £75 for 10 + V.A.T.; £350 for 50 + V.A.T.; £620 for 100 + V.A.T.; £2,800 for 500 + V.A.T.; £5,100 for 1,000 + V.A.T. Sample sent for £9 + £2 P. and P. (£12.85 inc. V.A.T.).

50-WATT FINNED HEATSINKS. 83mm long x 39mm wide x 30mm high drilled to take BD250B or similar device; £18 for 50 + V.A.T.; £33 for 100 + V.A.T.; £150 for 500 + V.A.T.; £270 for 1,000 + V.A.T.; £1,200 for 5,000 + V.A.T. Sample 10 sent for £5 + £1 P. and P. (£6.90 inc. V.A.T.).

REED RELAY. Complete with coil. Operating voltage 12V. D.C. at 20 m/a. Reed n/o, once energised the reed will not open until the supply voltage drops below 5 volts. Approx. £20 for 100 + V.A.T.; £180 for 1,000 + V.A.T.; £800 for 5,000 + V.A.T.; £1,450 for 10,000 + V.A.T. Sample 10 sent for £2.50 + 50p P. and P. (£3.45 inc. V.A.T.).

RADIALL BNC 75R STANDARD PLUG. Gold-plated centre contact; £34 for 50 + V.A.T.; £62 for 100 + V.A.T.; £280 for 500 + V.A.T. Sample 10 sent for £7.50 + 50p P. and P. (£9.20 inc. V.A.T.).

Terms c.w.o. Please add 5% to all orders for carriage plus 15% V.A.T. Export enquiries welcome. We find it impossible to advertise all we stock. Please telephone or write for further enquiries. Personal callers always welcome.


ELECTRONIC EQUIPMENT Co.

SPRINGFIELD HOUSE
TYSEN ST., LONDON, E.8
TEL: 01-249 5217
TELEX: 8953906 EECO.G

WW - 063 FOR FURTHER DETAILS



Industrial/ Commercial Power Amplifiers

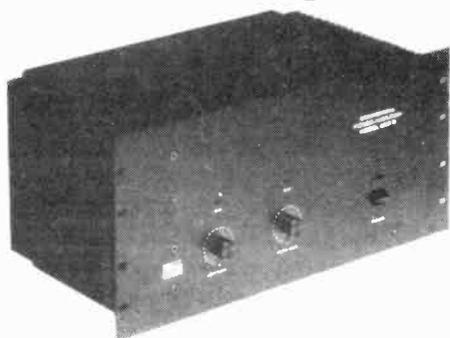

Specifications (Direct Output): BGW Model 620B

OUTPUT POWER

200 watts minimum sine wave continuous power output per channel with both channels driving 8-ohm loads over a power band from 20Hz to 20kHz. The maximum Total Harmonic Distortion at any power level from 250 milliwatts to 200 watts shall be no more than 0.25%.

1kHz Power: 240 watts into 8 ohms per channel, both channels operating, 0.25% Total Harmonic Distortion

Intermodulation Distortion	Less than 0.06% from 250 milliwatts to rated power
Small Signal	+0, -3dB, 1Hz to 70kHz
Frequency Response	+0, -0.25dB, 20Hz to 20kHz
Hum and Noise Level	Better than 100dB below 200 watts (unweighted, 20Hz to 20kHz)
Damping Factor	Greater than 120 to 1 at 8 ohms and 1kHz
D.C. Offset Voltage	Less than 10 millivolts (at output terminals)
Load Impedance	Designed for any load impedance equal to or greater than 4 ohms



Specifications (Direct Output): BGW Model 320B

OUTPUT POWER

100 watts minimum sine wave continuous average power output per channel with both channels driving 8 ohm loads over a power band from 20Hz to 20kHz. The maximum Total Harmonic Distortion at any power level from 250 milliwatts to 100 watts shall be no more than 0.2%.

1kHz Power: 105 watts into 8 ohms per channel, both channels operating, 0.2% Total Harmonic Distortion

Intermodulation Distortion	Less than 0.05% from 250 milliwatts to rated power
Small Signal	+0, -3dB, 1Hz to 50kHz
Frequency Response	+0, -0.25dB, 20Hz to 20kHz
Hum and Noise Level	Better than 100dB below 100 watts (unweighted 20Hz to 20kHz)
Damping Factor	Greater than 150 to 1 at 8 ohms and 1kHz
D.C. Offset Voltage	Less than 10 millivolts (at output terminals)
Load Impedance	Designed for any load impedance equal to or greater than 4 ohms

THEATRE PROJECTS

For further information on these and other BGW amplifiers, contact Nikki Antoniou **Theatre Projects**, 10 Long Acre, London WC2E 9LN, Tel: 240 5411

WW - 031 FOR FURTHER DETAILS

Model LT 100-P



Current sensor from LEM of Geneva

- For isolated measurement of ac, dc and pulsed currents
- Isolation test voltage: 5 kV
- Aperture for primary current: $\varnothing = 10$ mm
- Temperature range: 0 - 50°C
- Range of measurements: 0 \pm 150 amps. Nominal rating: 100 amps
- Accuracy: $\pm 1\%$ of I_N from 0 - 50 Hz.
- Internal resistance: 30 Ω
- Response time: < 1 μ sec.
- + and - 15 V dc required for measuring circuit
- PCB mounting - size 45 x 35 x 32H mm.
- Smaller currents measured by using multiple primary turns

Other models available

- 200, 250, 300, 400, 600, 1,000, 1,500, 3,000 and 10,000 amps rating
- with or without built-in power supply
- with or without built-in primary bar
- with isolation up to 30 kV.
- for measuring voltages up to 5 kV.
- with bandwidth up to 500 kHz (3 db)

Small quantities available ex-stock by post from the manufacturer:

LEM S.A. 140 chemin du Pont-du-Centenaire, 1228 Plan-les-Ouates/ Geneva, Switzerland tel. Geneva 7130 01 telex 429 422 lem ch

Detailed descriptions available from:

C. G. Wedgwood & Company Ltd., 14 King's Road, Wimbledon, London SW19 tel. (01) 540 6224 telex no. 8954665 gits ref. wedgwood

WW - 074 FOR FURTHER DETAILS

GREENWELD

443G Millbrook Road, Southampton SO1 0HX

DIL SOCKETS		
Low profile		BC182L .05
8DIL .45		BC183 .05
14DIL .55		BC183L .05
16DIL .65		BC184 .05
18DIL .75		BC212B .05
20DIL .80		BC213 .05
24DIL .09		BC214B .05
28DIL .11		BC214L .05
40DIL .15		BC308B .05
		BC327 .06
Std Profile		BC328 .06
Tinned		BC338 .06
8DIL .07		BC547 .05
16DIL .10		BC548 .05
24DIL .14		BC549 .05
28DIL .16		BC557 .05
		BC558 .05
Gold Plated		BC559 .05
8DIL .10		BCY70 .12
16DIL .17		BCY71 .12
24DIL .24		BCY72 .12
		BD131 .26
Wirewrap		BD132 .26
Tinned		BD246 .30
14DIL .12		BD433 .28
40DIL .30		BD695A .45
		PD696A .45
Gold Plated		BF173 .16
16DIL .15		BF181 .18
		BF195 .06
Turned Pin		BF258 .20
8DIL .09		BFY50 .17
18DIL .12		BFY51 .15
22DIL .16		BFY52 .15
40DIL .30		BRY46 .17
		BU206 .70
		BU208 .92
		OC35 .70
		PBC108 .05
		TIP31A .21
		TIP32A .21
		TIP41C .32
		2N1132 .16
		2N2222 .10
		2N2369 .12
		2N2646 .40
		2N2926R .05
		2N3053 .16
		2N3055 .30
		2N3702-10 .05
TRANSISTORS		
AC127 .16		
AC128 .16		
AD161/2 .45		
BC107 .08		
BC108C .08		
BC109C .09		
BC182B .05		

Wholesale supplier of electronic components - all new full spec. devices. Please add £1 post + 15% VAT to all orders. Prices are for 100+ of one type.

Cable Mounting Skt, 40-way like RS 467-318 .85
PCB mntg plug by Amphenol FRC2 60-way like RS 467-318, etc.
Right angle 1.30
Straight 1.20
Right angle wirewrap 1.45
Amphenol 126 & 165 series multipole conns. - Ask for list

ZENERS
400mW, 5%, E24 series.
All values from 3V0 to 33V .03, 1k+ .025

TEXAS 2N3055 .30, 1k+ .25

NICADS AA size by GE. 450mA/H solder tags .50

FERRIC CHLORIDE in pellet form, in sealed 250gm. packs .45

7 SEG DISPLAY Comm. Anode MS133A .23

W08 BRIDGES 800V 1A .095
4011B .085, 1k+ .075
741 8DIL .12, 1k+ .10
1N4007 Motorola .03, 1k+ .024
1N4006 Russian Box of 300, 7.00
6850 .80
68A00 1.20
1702A .50

TANT BEAD CAPS

1/35	100+	.04
22/35		.04
1/35		.04
6.8/35		.09
10/35		.14


1/4W 5% CF RESISTORS

These values only: 4R7, 5R1, 6R2, 6R8, 8R2, 13R, 18R, 27R, 33R, 39R, 56R, 68R, 100R, 180R, 220R, 270R, 470R, 1k, 2k7, 3k, 4k7, 18k, 22k, 27k, 30k, 33k, 36k, 39k, 75k, 200k, 220k, 240k, 390k, 560k, 620k, 680k, 750k, 1M5. All £2.50/1,000

WW - 081 FOR FURTHER DETAILS

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

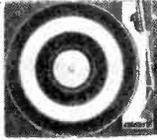RECORD DECKS SINGLE PLAY 11in Turntables 240 volt AC. Post £2



Make	Model	Drive	Cartridge	Price
BSR	P204	Rim	Ceramic	£15
BSR	P204	Rim	Magnetic	£20
BSR	P170	Rim	Ceramic	£20
BSR	P232	Belt	Ceramic	£24
GARRARD	6200	Rim	Ceramic	£22
GARRARD	Delux	Belt	Magnetic	£40

BSR	P204	9 volt	Ceramic	£18
BSR	P232	12 volt	Magnetic	£24

AUTOCHANGERS 240 VOLT

BSR	Budget	Rim	Ceramic	£16
BSR	Delux	Rim	Ceramic	£18

HEAVY METAL PLINTHS

Cut out for most BSR or Garrard decks. Silver grey finish, black trim. Size 16x13 3/4in. **£4**

DECCA TEAK VENEERED PLINTH

Post £1.50
Superior finish with space and panel for small amplifier. Board is cut for B.S.R. 18 3/4in. x 14 1/4in. x 4in. Black/chrome fascia trim. Also with boards cut out for Garrard £3. Tinted plastic cover **£5**

TINTED PLASTIC COVERS

17 7/8 x 13 1/8 x 3 1/4in.	£5	18 1/4 x 12 1/2 x 3in.	£5
17 1/4 x 9 3/8 x 3 1/2in.	£3	14 3/8 x 12 1/2 x 2 7/8in.	£5
16 1/2 x 15 x 4 1/2in.	£5	16 3/8 x 13 x 4in.	£5
17 x 12 7/8 x 3 1/2in.	£5	14 1/2 x 13 3/4 x 2 3/4in.	£5
22 5/8 x 13 7/8 x 3in.	£5	17 1/4 x 13 3/4 x 4 1/8in.	£5
21 1/2 x 14 1/4 x 2 1/2in.	£5	21 x 13 7/8 x 4 1/8in.	£5
23 3/4 x 14 x 3 7/8in.	£5	30 3/4 x 13 3/8 x 3 1/4in.	£5

THE "INSTANT" BULK TAPE ERASER

Post £2
Suitable for cassettes and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools and computer tapes. **Head Demagnetiser only £5.**



BATTERY ELIMINATOR MAINS TO 9 VOLT D.C.

Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5 x 3 1/4 x 2 1/2in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models, £4.50. Post 50p.

DE LUXE SWITCHED MODEL STABILISED. £7.50. PP £1. 3-6-7 1/2-9 volt 400mA DC max. Universal output plug and lead. Pilot light, mains switch, polarity switch.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy build kit. Controls up to 480 watts AC mains. £3. PP 65p.
DE LUXE MODEL READY-BUILT 800 watts. Front plate fits standard box, £5. Post 65p.

EMI 13 1/2 x 8in. LOUSPEAKERS

Model 450A, 10 watts R.M.S. with moving coil tweeter and two-way crossover; 3 ohm or 8 ohm. "Final Clearance"
SUITABLE BOOKSHELF CABINET **£8** Post £1.50
£6.50. Size 18 x 11 x 6in. Post £1.50.

RELAYS. 6V DC 95p. 12V DC £1.25. 18V £1.25. 24V £1.30

ALUMINIUM CHASSIS. 6x4-£1.75; 8x6-£2.20; 10x7-£2.75; 12x8-£3.20; 14x9-£3.60; 16x6-£2.50; 16x10-£3.80; 12x3 £2.20; 14x3 £2.50.

ALUMINIUM PANELS. 6x4-55p; 8x6-90p; 14x3-90p; 10x7-£1.15; 12x8-£1.30; 12x5-90p; 16x6-£1.30; 14x9-£1.75; 12x12-£1.80; 16x10-£2.10.

ALUMINIUM BOXES. 4x4x1 1/2 £1.20. 4x2 1/2x2 £1.20. 3x2x1 £1.20. 6x4x2 £1.90. 7x5x3 £2.90. 8x6x3 £3.10. 10x7x2 1/2 £3.60. 12x5x3 £3.60. 12x8x3 £4.30.

BRIDGE RECTIFIER 200V PIV 2a £1. 4a £1.50. 6a £2.50.

TOGGLE SWITCHES SP 40p. DPST 50p. DPDT 60p.

MINIATURE TOGGLES SP 40p. DPDT 60p.

RESISTORS. 10Ω to 10M. 1/4W, 1/2W, 1W, 2p; 2W 10p; Low ohm 1 watt 0.47 to 3.9 ohm 10p.

HIGH STABILITY. 1/2W 2% 10 ohms to 1 meg. 10p.

WIRE-WOUND RESISTORS 5 watt. 10 watt. 15 watt 20p.

PICK-UP CARTRIDGES SONOTONE 9TAC £3.80.

BSR Stereo Ceramic SC7 Medium Output £2. SC12 £3.

PHILIPS PLUG-IN HEAD. Stereo Ceramic. AU1020 (G306 GP210 - GP233-AG3306, £2. A.D.C., QLM 30/3 Magnetic £5.

GOLDRING G850 £6.50, G800 £8.50. STYLUS most Ceramic Acos, Sonotone, BSR, Garrard Philips Diamond £1.20 ea.

MAGNETIC STYLUS, Sony, JVC, Sanyo, Goldring, etc. £4.

LOCKTITE SEALING KIT DECCA 118. Complete £1.

VALVE OUTPUT Transformers £14; 30W £18; 50W £20; 100W £24. Post £2.

SUB-MIN MICROSWITCH, 50p. Single pole changeover.

ANTEX SOLDERING IRON "C" 15W £4.60. 25W "X25" £4.70.

WAFER SWITCHES. 1 1/4" dia. 60p ea.

1P 12V; 2P 2W; 2P 6W; 3P 4W; 4P 2W; 4P 3W.

FERRITE ROD. 6" x 1/2", 6" x 3/8", 8 1/2 x 1/2" 40p

XLR Lead Plug £2.40. Lead socket £2.75

XLR Chassis Plug £2.20. Chassis Socket £2.55.

BANANA 4mm Plugs/Sockets, red/black 20p

JACK PLUGS Mono Plastic 25p; Metal 30p

JACK PLUGS Stereo Plastic 30p; Metal 35p.

JACK SOCKETS Mono 25p. Stereo 30p.

FREE SOCKETS - Cable end 30p. Metal 45p.

2.5mm and 3.5mm JACK SOCKETS 25p. Plugs 25p.

DIN TYPE CONNECTORS

Sockets 3-pin, 5-pin 15p. Free Sockets 3-pin, 5-pin 25p.

Plugs 3-pin 20p; 5-pin 25p; Speaker plugs 25p; Sockets 15p.

PHONO PLUGS and SOCKETS ea. 20p; Double sockets 30p.

Free Socket for cable end 20p. Screened Phono Plugs 25p.

B.N.C. PLUGS £1. Sockets £1. Free Sockets £1.10.

UHF PLUGS 50p. Sockets 50p. Reducers 20p. Couplers 50p.

300 ohm TWIN RIBBON FEEDER 10p yd.

300 ohm to 75 ohm AERIAL MATCHING TRANSFORMER £1.

U.H.F. COAXIAL CABLE SUPER LOW LOSS, 25p yd.

COAX PLUGS 30p. COAX SOCKETS 20p. Lead Sockets 65p.

NEON INDICATORS 250V, round 40p. Rectangular 45p.

POTENTIOMETERS Carbon Track

5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5K. SP 45p.

MINI-MULTI TESTER NEW

De luxe pocket size precision moving coil instrument. Impedance + Capacity - 4000 o.p.v. Battery included.
11 instant ranges measure:
DC volts 5.25, 250, 500. **£6.50**
AC volts 10, 50, 500, 1000. Post 50p
DC amps 0-250μA, 0-250mA.
Resistance 0 to 600k ohms.

De Luxe Range Doubler Model, 50,000 o.p.v. £18.50. 7x5x2in. Post £1
43 Ranges, 1,000V, AC-DC, 20 meg, etc.

PANEL METERS

50μA, 100μA, 500μA, 1mA, 5mA, 50mA, 100mA, 500mA, 1 amp, 2 amp, 25 volt, VU
2 1/4 x 2 x 1 1/4. Stereo VU
3 1/4 x 1 1/8 x 1in. **£4.50** Post 50p

RCS SOUND TO LIGHT CONTROL BOX

Complete ready to use with cabinet size 9x3x3in
3 channel, 1000 watt each. For home or disco
Input 200mV to 100 watt. AC 200/250V. Post £1. **£27**
OR KIT OF PARTS £19.50, LESS CABINET £15
Disco bulbs 100 watt, blue, green, yellow, red, amber, screw or bayonet £1.85 each. Post £1.50 per six.
Rope lights, 4 channel, 11ft with controller £33, PP £1.
"FUZZ" lights, red, blue, green, amber, 240V. £23. Post £1
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights, Edison Screw. 6 for £4, or 12 for £7.50. Post £1.50. Suitable panel mounting holders 85p.

RCS "MINOR" 10 watt AMPLIFIER KIT £14

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Specification 10W per channel; size 9 1/2 x 3 x 2in. SAE details. Full instructions supplied. 240V AC mains. Post £1.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board. Can be ganged to make multi-way stereo mixers **£3.50** Post 65p

MAINS TRANSFORMERS

250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A	£6.00	£2
350-0-350V 250mA, 6.3V 6A CT	£12.00	£2
220V 25ma 6V amp £2.50.	£4.00	£1
250V 60mA, 6V 2A	£4.75	£1

AUTO 115V to 240V 150W £9. 250W £10. 400W £11. 500W £12.00 £2

GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available

2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	Price Post
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00 £2
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£10.50 £2
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50 £2
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£18.00 £2
5-8-10-15V 1/2 amp.	£2.00 £1
6-0-6V, 1 1/2 amp.	£3.50 £1
9V, 250mA.	£1.50 £1
9V, 3 amp.	£3.50 £1
9-0-9V 50ma	£1.50 £1
9-0-9V 1 amp.	£3.00 £1
10-0-10V, 2 amps	£4.00 £1
10-30-40V, 2 amps	£4.50 £1
12V, 100mA	£1.50 £1
12V, 750 mA	£2.50 £1
12V 3 amps	£4.50 £1
12-0-12V, 2 amps	£4.50 £1
CHARGER TRANS	Post
6-12 volt 3a	£4.50 £2
6-12 volt 4a	£6.50 £2

OPUS COMPACT SPEAKERS £22 pair

Post £2
TEAK VENEERED CABINET
11 x 8 1/2 x 7in. 15 watts
50 to 14,000 cps. 4 ohm or 8 ohm
OPUS TWO 15 x 10 1/2 x 7 3/4in 25 watt
2-way system £39 pair. Post £3

LOW VOLTAGE ELECTROLYTICS

Wire ends 10p

1 mf, 2 mf, 4 mf, 8 mf, 10 mf, 16 mf, 25 mf, 30 mf, 50 mf, 100 mf, 250 mf. All 15 volts.	22 mf/6v/15v; 25 mf/6v/10v; 47 mf/10v; 50 mf/6v; 68 mf/6v/10v; 100 mf/10v; 100 mf/10v; 150 mf/6v/10v; 200 mf/10v/10v; 220mf/40v/10v/10v; 330 mf/4v/10v; 500 mf/6v; 680 mf/6v/10v; 1000 mf/2.5v/4v/10v; 1500 mf/6v/10v/10v; 2200 mf/6v/10v; 3300 mf/6v; 4700 mf/4v.
500mfF 12V 15p; 25V 20p; 50V 30p. 1200mfF 76V 80p.	
1000mfF 12V 20p; 25V 35p; 50V 50p; 100V 70p.	
2000mfF 6V 25p; 30V 42p; 40V 80p; 1500mfF 100V £1.20.	
2200mfF 63V 90p. 2500mfF 50V 70p; 3000mfF 50V 85p;	
4500mfF 64V £2. 4700mfF 63V £1.20. 4700mfF/30V 75p.	

NON POLARISED CAPACITORS

1mF 250V 25p; 1.5mF 100V 25p; 2.2mF 250V 30p; 3.3mF 100V 40p; 4.7mF 100V 40p; 10mF 63V 40p; 32mF 50V 25p; 47mF 50V 40p.

HIGH VOLTAGE ELECTROLYTICS

2/500V 45p	32+32+16/350V 90p	8+8/500V 75p
8/450V 45p	100+100/275V 85p	8+16/450V 80p
16/350V 45p	150+200/275V 70p	16+16/350V 85p
32/500V 95p	220/450V 95p	32+32/500V 85p
32/350V 50p	32+32+32/325V 75p	32+32/500V 1.80p
50/450V 95p	50+50+50/350V 95p	50+50/300V 50p

CAPACITORS WIRE END High Voltage

001, 002, G03, 005, 01, 02, 03, 05 mf 400V 5p.
1mF 200V 5p. 400V 10p. 600V 15p. 1000V 25p.
22mF 150V 12p. 600V 20p. 1000V 30p. 1750V 50p.
47mF 150V 10p. 400V 20p. 630V 30p. 1000V 60p.
TRIMMERS 30pF, 50pF, 10pF, 100pF, 150pF 20p. 500pF 30p.
MICROSWITCH SINGLE POLE CHANGEOVER 40p.
50pF Single gang 95p. GEARED TWIN GANGS 25pF 95p.
365+365+25+25pF £1.

HEATING ELEMENTS, WAFER THIN (Semi Flexible)

Size 11 x 9 x 1/8in. Operating voltage 240V, 250W approx. Suitable for Heating Pads, Food Warmers, Convecter Heaters, Propagation, etc. Must be clamped between two sheets of metal or ceramic, etc.
ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

NEW baker Star sound

high power full range quality loudspeakers. British made. Ideal for Hi-Fi, music P.A. or discotheques. These loudspeakers are recommended where high power handling is required with quality results.



MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£16	£2
SUPERB	12	8-16	30	HI-FI	£26	£2
AUDITORIUM	12	8-16	45	HI-FI	£24	£2
AUDITORIUM	15	8-16	60	HI-FI	£37	£2
GROUP 45	12	4-8-16	45	PA	£16	£2
GROUP 75	12	4-8-16	75	PA	£20	£2
GROUP 100	12	8-16	100	Guitar	£26	£2
DISCO 100	12	8-16	100	Disco	£26	£2
GROUP 100	15	8-16	100	Guitar	£35	£2
DISCO 100	15	8-16	100	Disco	£35	£2

BAKER AMPLIFIERS BRITISH MADE



NEW PA150 MICROPHONE PA AMPLIFIER £129

4 channel 8 inputs, dual impedance, 50K-600 ohm 4 channel mixing, volume, treble, bass. Presence controls, Master volume control, echo/send/return socket. Slave sockets. Post £3.

BAKER 150 Watt AMPLIFIER 4 Inputs £99

For Discotheque, Vocal, Public Address. Three speaker outlets for 4, 8 or 16 ohms. Four high gain inputs, 20 mv, 50K ohm, individual volume controls "Four channel" mixing, 150 watts 8 ohms R.M.S. Music Power. Slave output 500 M.V. 25K ohm. Response 25 Hz - 20kHz ± 3dB. Integral Hi-Fi preamp separate Bass & Treble. Size - 16" x 8" x 5 1/2". Wt - 14lb. Master volume control British made. 12 months' guarantee. 240v A.C. mains or 120V to order. All transistor and solid state. Post £2.
MONO SLAVE £80. 100 Volt Line Model £114. Post £2.
New Stereo Slave 150 + 150 watt 300 watt Mono £125. Post £4.

BAKER 50 WATT AMPLIFIER



£69 Post £2
Ideal for PA systems, Discos and Groups. Two inputs. Mixer, Volume Controls, Master Bass, Treble and Gain.

RCS offers MOBILE PA AMPLIFIERS. Outputs 4-8-16 ohms

20-watt RMS 12v DC, AC 240v, 3 inputs 50K £46 PP £2
40-watt RMS 12v DC, AC 240v, 4 inputs 50K £75 PP £2
Mic 1; Mic 2; Phono; aux. outputs 4 or 8 or 16 and 100v line
60-watt RMS, Mobile 24 volt DC & 240-volt AC mains, inputs 50K.
3 mics + 1 music. Outputs 4-8-16 ohm + 100 volts line £95 PP £2

Battery only Portable PA Amplifier 10w max. Includes mike and speaker, OK for meetings, crowd control, stalls, fetes, traders, parties, etc. Batteries included (6 of U2) £27.50 post £2.

R.C.S. 100 watt R.M.S. VALVE AMPLIFIER

4 Channel mixing, Master treble, bass and volume controls. 5 Speaker outlets, suits 4, 8, 16 ohm. Disco group £125. Carr. & ins. £15.
60 WATT VALVE AMPLIFIER, 3 mixer inputs, 4-8-16 ohm, 100 volt line, 5 controls £59, post £4






FAMOUS LOUSPEAKERS

"SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
WHARFEDALE	TWEETER	4in				

R·E·E·L POWER

ONE BILLION WATTS IN STOCK

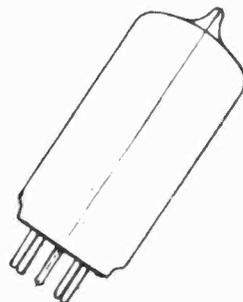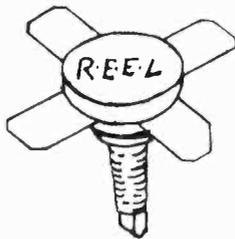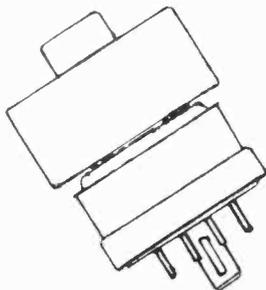


YOUR SINGLE SOURCE FOR
AMERICAN VALVES — R.F. TRANSISTORS & SEMICONDUCTORS
BRANDS BY ALL LEADING MANUFACTURERS

WRITE, CALL OR TELEX ALLAN MCCRONE FOR FURTHER DETAILS

(0522) 42631/4

TELEX 56175

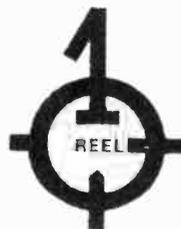
RICHARDSON Electronics (Europe) Ltd.
DEAN ROAD, OUTER CIRCLE ROAD, LINCOLN LN2 4DV



WW - 084 FOR FURTHER DETAILS

Hitachi Oscilloscopes

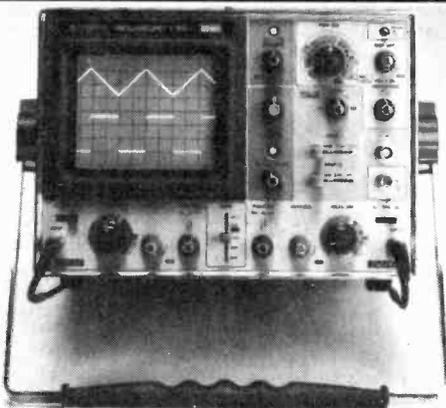performance, reliability, exceptional value
and immediate delivery!



Hitachi Oscilloscopes provide the quality and performance that you'd expect from such a famous name, in a newly-extended range that represents the best value for money available anywhere.

V-152F	15MHz Dual Trace	V-353F	35MHz Sweep Delay
V-202F	20MHz Dual Trace (illustrated)	V-650F	60MHz Dual Timebase, Trigger View
V-203F	20MHz Sweep Delay	V-1050F	100MHz Quad Trace, Dual Timebase
V-302F	30MHz Dual Trace	V-209	20MHz Dual Trace, Mini-Portable
V-352F	35MHz Dual Trace	V-509	50MHz Dual Timebase, Mini-Portable
		V-134	10MHz Tube Storage Oscilloscope

Prices start from around £250 (ex. V.A.T.) including two high-quality probes and a two-year warranty. We hold the range in stock for immediate delivery.

For colour brochure giving detailed specifications and prices ring (0480) 63570.
Reltech Instruments, 46 High Street, Solihull, W. Midlands, B91 3TB

WW - 078 FOR FURTHER DETAILS

WE PURCHASE

Surplus component stocks, redundant materials, obsolete computers, for cash.

We also collect — distance no object. Just call:

**C. T. Electronics (Acton)
Ltd.**


267 & 270 Acton Lane, London W4 5DG

Telephone: 01-747 1555; 01-994 6275. Telex: 291429

WW - 075 FOR FURTHER DETAILS

MICRO ENGRAVER

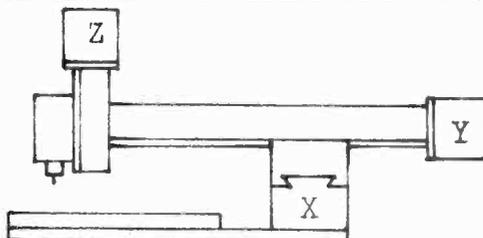MICROPROCESSOR-CONTROLLED ENGRAVING MACHINE



STEPPING MOTOR XYZ MACHINE. Complete with microprocessor controller and software programmed to engrave alphabet and numbers. Also features easy operator-programmable XYZ sequences to engrave, drill or cut out special shapes and logos. XY axis travel 200/170mm, Z 20mm. Mixed character sizes on a label from 1-99mm high. Qwerty keyboard, 20 character liquid crystal display. Machine supplied complete and ready to manufacture labels.

J.A.F. GRAPHICS
70 Leek Road, Congleton, Cheshire CW12 3HU - 02602 5127

PRICE £2,350

WW - 067 FOR FURTHER DETAILS

SAMSONS

(ELECTRONICS) LTD.

9-10 Chapel Street, Marylebone
London NW1 5DN
21-23 Bell Street, London, NW1
01-262 5125 & 01-723 7851

MUFFIN FANS SPECIAL OFFER!!

240v fans
4 1/2x4 1/2x1 1/8" £5.75
inc. VAT + postage.
110v fans
4 1/2x4 1/2x1 1/8" £4.75
inc. VAT + postage.
Radiospares price
£14.50!!!

PLEASE ADD 15% TO ALL ORDERS INC. CARR.

12 or 24 VOLT				30 VOLT RANGE				
Ref.	12v	24v	£	Ref.	Amps	£	£	
111	0.5	0.25	2.42	1.00	112	0.5	3.19	1.00
213	1.0	0.5	3.19	1.00	79	1.0	4.32	1.00
71	2	1	4.25	1.00	3	2.0	6.99	1.20
18	4	2	4.91	1.20	20	3.0	8.10	1.30
85	5	2.5	6.78	1.20	21	4.0	9.67	1.40
70	6	3	7.69	1.20	51	5.0	11.95	1.40
108	8	4	8.98	1.30	117	6.0	13.52	1.50
72	10	5	9.82	1.50	88	8.0	18.10	1.80
116	12	6	10.89	1.50	89	10.0	20.88	1.90
17	16	8	12.97	1.50	90	12.0	23.20	4.00
115	20	10	17.46	1.60	91	15.0	26.60	4.00
187	30	15	21.69	1.70	92	20.0	35.64	4.00
226	60	30	44.45	2.00				

50 VOLT RANGE				60 VOLT RANGE			
Ref.	Amps	£	£	Ref.	Amps	£	£
102	0.5	4.13	1.10	124	0.5	4.70	1.20
103	1.0	5.03	1.10	126	1.0	7.15	1.20
104	2.0	8.69	1.30	127	2.0	9.20	1.40
105	3.0	10.36	1.50	125	3.0	13.31	1.50
106	4.0	14.10	1.60	123	4.0	15.15	1.70
107	6.0	18.01	1.70	40	5.0	19.16	1.70
118	8.0	24.52	2.00	120	6.0	21.86	2.00
119	10.0	30.23	4.00	121	8.0	30.72	3.00
109	12.0	36.18	4.00	122	10.0	35.76	4.00
				189	12.0	41.22	4.00

VOLTAGES OBTAINABLE

30v range 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30v, 12-0-12v or 15-0-15v. 50v range 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40v, 20-0-20v or 25-0-25v. 60v range 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60v, 24-0-24 or 30-0-30

AUTO STEPDOWN TRANSFORMERS FOR AMERICAN EQUIPMENT

240/110 Volts. 80-2250 watts. Regular stock line. Types 80-1500 watts are fully shrouded. Fitted with American two or three pin socket outlets and 3-core 240v mains lead. Types 1750 and 2250 watts are steel cased with two American socket outlets. Neon indicator, three-core mains lead and carrying handle. Send SAE for price list and further details. American sockets, plugs, adaptors also available.

SPECIAL OFFER:

HINCHLEY MAINS ISOLATION TRANSFORMERS
Prim 240V. Sec 240V 250 watts. Open frame type. Tag connections. Fused input £10, P&P £2. VAT £1.80. Parmeko pri tapped 115-220-240V. Sec 240V 6 amps. Fully shrouded top panel connections. Sec can be wired to give 120-0-120V. £25, carr. £5. VAT £4.50

COLOUR MONITORS

Brand new monitors, 14" screen, RGB input bandwidth 10meg sync level. 75V 5V P to P 625 lines 50 or 60 frames per sec. power consumption 70 watts. Ideal for use with the BBC computer. Special offer price £145 + VAT.

POWERFUL GEARED MOTORS

110V input but supplied with FREE transformer, 200rpm 35lb/in torque 9/8" output shaft. Physical size approx. 9" x 5" x 5" reversible. Bargain price £13 inc. VAT and carr.

SPECIAL OFFER:

HIGH POWER AMPLIFIER TRANSFORMERS
Pri tapped 120-240V sec. tapped 34-29-0-29-34V 6amps and 46V 1A. Open frame type. Tag connection. Size 5x4 1/2x4ins. £9 inc. postage and VAT.

LATEST PURCHASE. COMPUTER GRADE TRANSFORMERS. Conservatively rated. All Primaries 220-240V. No. 1 sec. 27V 10A, 9V 3A, 15V 1/2A x 2. Separate windings. £5.50, P&P £1.50

No. 2 sec. tapped 26-31-36V, 11.2A £12, P&P £2
No. 3 sec. 36V 6A £8.50, P&P £1.50
No. 4 sec. 43V 3A £4.75, P&P £1.50
No. 5 sec. 24V 2A £2.75, P&P £1.25
No. 6 sec. 27-5-0-27.5V 1.2A and 7-0-7V 0.75A £3.50, P&P £1.25
No. 7 17V 1A £2, P&P £1
No. 8 13V 3A and 15V 1A £3.50, P&P £1.25
No. 9 18V 2A £2.50, P&P £1
No. 10 sec. 29-28-27-0-27-28-29V 350 M/A "C" Core £3, P&P £1
No. 11 sec. 10-7-0-7-10V 0.6A and 29-21-0-21-29V 0.37A £3, P&P £1
No. 12 27V 1A, 22V 1A 10V 1A 10V 1A, 4 separate windings "C" core type £4.95, P&P £1.50
No. 13 65V 1A and 18-24V 1/2A £3.95, P&P £1.50
No. 14 Tapped 12-15-27V 1A £2, P&P 75p.
No. 15 6.3V 500M/A 6.3V 330M/A 6.3V 20 M/A 8V 500 M/A 50V 40 M/A £2, P&P £1
No. 16 Tapped 14-15-16V 2A £2, P&P £1
No. 17 Tapped 36-37-38-39-41-42-43V 1A "C" core £2.75, P&P £1

12" MONITORS

Monochrome Composite Video input 300/75 ohm, suitable for 80-column, packed in attractive black cases, side-mounted controls, £45 inc. VAT. Callers only.

UNIVERSAL TRANSFORMER

Parmeko High-Grade Transformer. Tapped at 7V and 21V plus 1V and 3V. The design of these transformers is such that 1V to 24V in one-volt steps can be obtained. Conservatively rated at 3.5 Amps. Price £7.50 inc. carr. and VAT.

SAFETY TRANSFORMER

Parmeko Transformer rated at 800W continuous 1400V intermittent use. Housed in shockproof yellow case with sturdy carrying handle and either 1 or 2 outlets. Internal safety fuses plus 2 spares.
Single Outlet.....£55.00 inc. carr. and V.A.T.
Dual Outlet.....£82.50 inc. carr. and V.A.T.
Usual price approx. £38
LIMITED STOCK - HURRY!!

SPECIAL OFFER HEAVY DUTY TRANSFORMERS

Pri 240V sec 50V 15 Amps. Twice will give 100V CT or 50V 30A. Open frame type. Terminal block primary. Sec heavy wire leads. Frame size 8 1/2 x 7 x 5 inches. Screen winding between pri and sec. Brand new, fraction of list price, £22, carr £5, VAT £5.55.

KEYBOARDS

Full ASCII Keyboard with cursor control plus numeric pad, originally made for Viewdata editing. A very high-grade unit housed in an attractive off-white case, fitted with 25-way D-Type socket. Price £56 inc. carr and VAT.

CAPACITORS

20,000 MFD 63V£3.50 each
20,000 MFD 45V£3.50 each
100,000 MFD 10V£3.50 each
3,600 MFD 150V£3.50 each
10,000 MFD 40V£3.00 each
All prices include carr and V.A.T.

SPECIAL OFFER

20-way 7-contact GPO Jack Fields in perfect condition, as new. A real bargain at only £6.50 inc. carr. and VAT!!!

1000W INVERTERS

Brand new - as used by United Nations. Fan-astic unit - very durable 12V input, 240V 50HZ output £275.00 inc. carr and VAT

ISOLATION TRANSFORMERS

Pri tapped 220-240V sec 240V 500 watts. Open frame type, top panel connections. Ex-equipment, but in perfect condition, £15, carr £3, VAT £2.70.

E.H.T. TRANSFORMERS

High-grade E.H.T. Tranny, Pri 240V, sec. 10,000V, 18 M/A. Probably used for boiler ignition but with 101 other uses!!!
£5 inc. carr. & VAT

DC WKG BLOCK CAPACITORS

8 MFD 1000V DC WKG £3, P&P £1, VAT 60p 8 MFD 350V DC WKG £1.25, P&P 50p, VAT 26p, 6 MFD 350V DC WKG £1, P&P 50p, VAT 22p, 4 MFD 500V DC WKG £1, P&P 50p, VAT 22p, 2 MFD 600V WKG. 60p, P&P 20p, VAT 12p, 1 MFD 1000V DC WKG 60p, P&P 20p, VAT 12p, 1 MFD 600V DC WKG 5 for £1.50, P&P 50p, VAT 30p, 0.25 MFD 500V DC WKG. 5 for £1.25, P&P 30p, VAT 16p, 0.1 MFD 1500V DC WKG. 5 for £1.25, P&P 50p, VAT 16p, 2 MFD 100V DC WKG. 10 for £1.50, P&P 75p, VAT 33p. Tubular metalised paper caps 20 MFD 350V DC WKG with clip £3, P&P 50p, VAT 52p.

LOW CURRENT LT TRANSFORMERS

Open frame clamped type, split bobbin. All primaries 240V. No. 1 sec tapped 12-15-20-24-30V 750 M/A £4. No. 2 sec 9-0-9V 1A and 6.3V 200 M/A £2.50. No. 3 15-0-15V 600 M/A and 6.3V 200 M/A £4. No. 4 sec 12-0-12V 750 M/A and 6.3V 200 M/A £4. No. 5 sec 13V 1/2A £1.50. No. 6 sec 8V 1/2A 6.3V 600 M/A, 6.3V 300 M/A, 50V 40 M/A £2.50. No. 7 sec 17V 1/2A (DC) £1.75. No. 8 sec. No. 9 sec 18V 2A £4. No. 10 sec 24V 2A £8.50. No. 11 sec 15V 2A £3.50. All prices include postage and VAT

BLOCK PAPER CAPACITORS

8 MFD 1000V DC WKG £3. P&P £1, 8 MFD 350V DC WKG. £1. P&P 50p, 6 MFD 350V DC WKG. £7.5p, P&P 25p, 4 MFD 300V AC WKG £1.50, P&P 50p, 4 MFD 350V DC WKG 50p, P&P 25p, 2 MFD 350V DC WKG. 40p, P&P 20p, 1 MFD 1000V DC WKG. 50p, P&P 20p.

H.T. TRANSFORMERS

All are Parmeko potted style. All prices include VAT & carr.
No. 1, Pri 110V 220V 240V SEC. 350-325-0-325-350V 120 M/A £8.75
No. 2, Pri 110V 220V 240V. SEC 400-0-400V 180M/A £8.75.
No. 3, Pri 110V 220V 240V SEC 408-201-0-201-408V 500 M/A £7.25.
No. 4, Pri 110V 220V 240V SEC 400-0-400V 150M/A and 150-0-150V 20M/A £8.50.
No. 5, Pri 110V 220V 240V SEC. 250V 35M/A 375V 10 M/A 10-0-10V 4A 10V 1A 15V 100M/A x2 6.3V 3A 6.3V 15 AMP £7.50

LOUDSPEAKERS

High-grade speakers, 8in., 30W max power. A bargain at only £6.95 inc. carr. and VAT.

SPECIAL OFFER OF ERIE ELECTROLYTIC CAPACITORS

22,000 MFD 63V DC WKG £4.50 inc. postage and VAT 6800 MFD 100V DC WKG £2.50 inc. postage and VAT 3600 MFD 150V DC WKG £2.50 inc. postage and VAT 10,000 MFD 16V DC WKG five for £2.50 inc. postage and VAT 100 MFD 25V DC WKG ten for £1 inc. postage and VAT 4.7 MFD 50V DC WKG ten for 75p, inc. postage and VAT 22,000 MFD 10V DC WKG five for £2.50 inc. postage and VAT

UNIVERSAL ISOLATION TRANSFORMERS

GPO spec, open frame, terminal block connections. Pri tapped 100-110-200-210-220-230-240-250V. SEC tapped 220-230-240V 600 watts. Can be used in reverse. Weight 19lb. £15. Carr £2.80 + VAT £2.87

PARTRIDGE OPEN FRAME TERMINAL BLOCK CONNECTIONS

Pri tapped 0-110-115-120-220-240V SEC 240V 1500 watts. Can be used in reverse £28.50, carr £4 + VAT £4.88

BERKSHIRE TRANS CO.

Totally enclosed with 2 American 3-pin sockets mounted on front panel. Pri 115-220-240V. SEC 115V, 1,000 watts can be reversed. Suitable for recording studios, laboratories, workshops, using 115V USA equipment. £25, carr £3.50 + VAT £4.28

CONSTANT VOLTAGE TRANSFORMERS

LARGE SELECTION OF CVTS BY FAMOUS MAKER
190-260V in 6V 15W out£15
190-260V in 12V 15W out£20
190-260V in 115V 50W out£25
190-260V in 115V 100W out£35
90-135V in 240V 200W out£40
All prices include VAT and carr WW.16

WW - 065 FOR FURTHER DETAILS

BRAIN GAIN

CIL Electronics latest PCI 6380 Interface gives your computer's brainpower far more than an average boost. With our latest brainchild you can now get far more into and out of your computer at surprisingly moderate cost.

Suitable for RS232 or IEEE 488.


Analogue/Digital input/output.

In Software

- Data Acquisition
- Wave Generation
- Analogue Alarm Features
- ASCII or Binary Data Format
- Off-line Data Storage

In Hardware

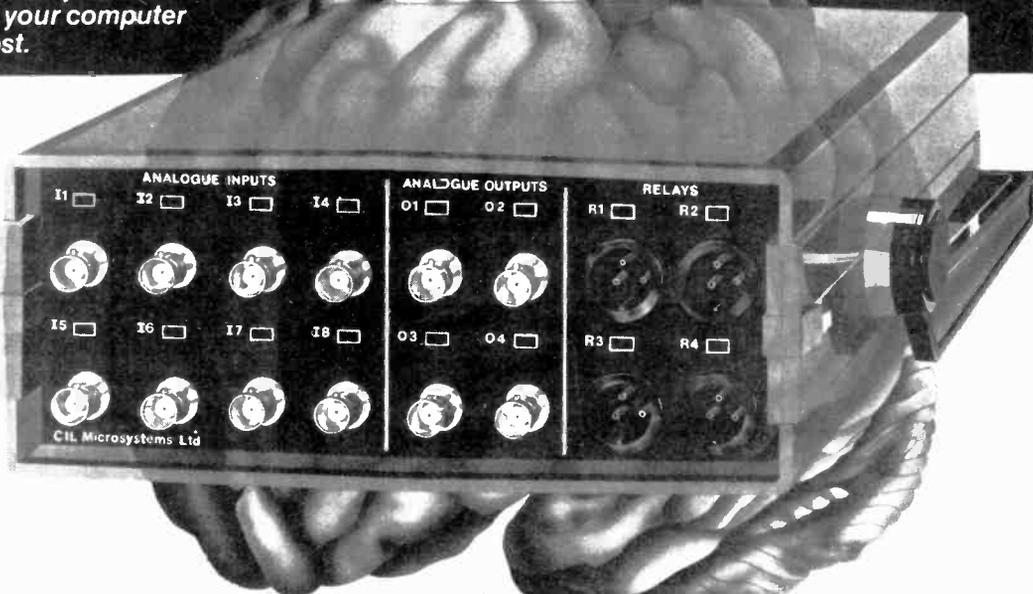- 8 Analogue Inputs
- 4 Analogue Outputs
- 4 Relays
- 2 x 8 Bit I/O Ports
- 32 RAM Option
- 4 K RAM Standard




For further information please contact:

CIL Microsystems Ltd., Decoy Road, Worthing, Sussex BN14 3ND. Tel: Worthing (0903) 210474. Telex: 87515 WISCO GATT CIL.

WW - 083 FOR FURTHER DETAILS

TWO NEW HANDHELD DIGITAL MULTIMETERS

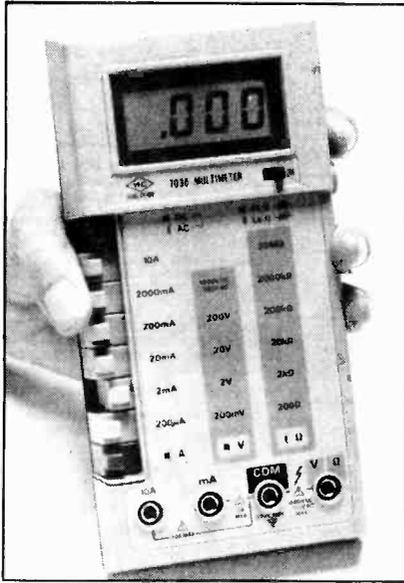

MODEL 6010
DC ACCURACY 0.5%
£29.95
PLUS VAT = £34.44

MODEL 7030
DC ACCURACY 0.1%
£35.95
PLUS VAT = £41.34

200µA – 10 AMP AC-DC
28 RANGES EACH WITH FULL OVERLOAD PROTECTION

SPECIFICATION

- Mode select: Push button
- AC DC current: 200µA to 10A – 6 Ranges
- AC voltage: 200mV to 750V – 5 Ranges
- DC voltage: 200mV to 1000V – 5 Ranges
- Resistance: 200Ω to 20MΩ – 6 Ranges
- Input impedance: 10MΩ
- Display: 3½ Digit 13mm LCD
- Overload protection: All ranges
- Battery: Single PP9 type (included)
- Battery life: 200 hours
- Dimensions: 170 × 89 × 38mm
- Weight: 400g inc battery

OTHER FEATURES:

Auto polarity, auto zero, battery-low indicator, ABS plastic case with tilt stand, battery and test leads, spare fuse and operators manual included. Optional carrying case.

AFDEC 318 Kempshott Lane, Basingstoke
Hants RG22 5LT
ELECTRONICS LTD

I wish to order the following

Quantity	Item	Amount
	Model 6010 @ £34.44 inc.	
	Model 7030 @ £41.34 inc.	
	Carrying Case @ £2.00 inc.	
	TOTAL	

All prices include VAT and post and packaging. All items include a full year guarantee. Allow up to 10 days for delivery. Cheques/Postal Orders etc. should be made payable to: AFDEC Electronics Ltd

Name _____
Address _____

Overseas customers add £4.00 post and packaging. WW4

9in. MONITOR in attractive case; accepts Composite Video +/- 4 volts; with info, £25 each	42 ERNST TURNER 6in. ELECTROSTATIC VOLTMEETER Model 32, 0-5kv..... £14
Matching ASCII coded QUERTY KEYBOARD with Numeric Keypad and 27 function keys; £25 each, p. and p. £5. THE PAIR £40.	43 ERNST TURNER 6in. ELECTROSTATIC VOLTMEETER Model 32, 0-10kv..... £16
12in. MONITOR, cased with info; accepts Composite Video +/- 4 volts; 20 each. With Matching ASCII coded QUERTY KEYBOARD with Numeric Pad and 24 function keys; £35 the pair.	48 AVO MULTIMETER Model 72, compact..... £12
POWER UNIT, 240v input, outputs x5v/15a; +24v/1.5a; -24v/3a; £12 each.	50 SOLARTRON DIGITAL VOLTMEETER Type LM1420.2..... £20
INSTRUMENT CASE, standard 19in. width x 16in. deep x 10in. high; £5 each.	54 AVO TRANSISTOR TESTER Type TT169 with leads, as new ip. and p. £21..... £20
FLOPPY DISK DRIVE, 8in. by Control Data Corp; 240v input with control electronics; £95, p. and p. £5.	57 TAYLOR VALVE TESTER Model 45D2..... £35
TWO 8in. FLOPPY DISK DRIVES by Incoterm with drive electronics mounted in case, 25-way Cannon input/output socket, 240v operation; £175.	60 PYE SCALAMP ELECTROSTATIC VOLTMEETER, 0-40kv..... £35
CENTRONIX PRINTER Type 501 with stand, 240v operation; £125, carr. £14.	66 AUTO TRANSFORMER, 1000 VA, brand new, 110v/0..... £10
CALCOMP 563 DIGITAL PLOTTER with CALCOMP 905 OFFLINE PLOTTER CONTROLLER, in very good condition and working order; £390, carr. extra.	90 AVO VALVE TESTER Type CT160, 22 valve bases..... £20
I.C.L. Type 7181 VDU with keyboard, upper and lower case; £40.	95 AVO HIGH-VOLTAGE DC MULTIPLIER for 20,000 ohm/volt meters..... £20
TEKTRONIX HARD COPY UNIT Type 4610-1, can be used with 4010 series computer display terminals; £375.	96 GENERAL RADIO CAPACITOR 2000v dc, 110v/0..... £15
FACT CASSETTE UNIT Model 4203 with internal electronics; £80.	109 MARCONI/SANDERS MICROWAVE POWER METER Type 6598 with thermistor mount type 6046/B, 0.5MHz-11GHz..... £125

Item No.

1 TELE-EQUIPMENT OSCILLOSCOPE Type D83, dual trace, 50MHz delay sweep..... £550	110 NARDA PEAK POWER METER Model 66A3A no bolometer..... £50
2 TEKTRONIX OSCILLOSCOPE Type 1935A, dual trace, 35MHz delay sweep, AS NEW £550	116 MARCONI SENSITIVE VALVE VOLTMEETER Type TF2600, 10Hz-10MHz, 1mV-300v f.s.d. £75
3 TELE-EQUIPMENT OSCILLOSCOPE Type D67A, dual trace, 25MHz delay sweep..... £395	141 WAYNE KERR UNIVERSAL BRIDGE Type B224, 0.1%..... £275
5 TELE-EQUIPMENT OSCILLOSCOPE Type D61A, dual trace, 10MHz..... £160	142 SOLARTRON/SCHLUMBERGER DVM Type A220, 5-digit, input sensitivity 10 mV/volts up to 1kv..... £50
17 MARCONI FM/AM SIGNAL GENERATOR TF995A/3S, 1.5-20MHz, AM/FM -od..... £160	145 TEKTRONIX OSCILLOSCOPE Type 581A with Type 82 plug-in, dual trace 85MHz..... £160
20 MARCONI UNIVSL BRIDGE Type TF688B..... £85	175 TINSLEY WHEATSTONE BRIDGE Type 405 (Post Office pattern)..... £10
28 LABGEAR COLOURMATCH 625 PATTERN GENERATOR Type CM6004-PG..... £25	178 CROPICO THERMOCOUPLE POTENTIAL METER Type P4..... £20
31 RANK E.H.T. METER, 0-30kv dc..... £30	206 RACAL H.F. SELECTIVE ANALYSER Type 9056, SSB (2-tone), AM Modulation, FM calibration and transmission measuring..... £150
32 METRIX WOBBLULATOR Type 210..... £35	207 LAMBA REGULATED POWER SUPPLY Model LMFA 24-0V-V, input 240v, output 24v dc, 14a max.; +/- 5%..... £60
33 PHILIPS WOBBLULATOR Type GM2877S..... £50	210 HIOVOLT Type 30PMSR HIGH-VOLTAGE POWER UNIT, 0-30kv, 0-1mA..... £45
34 ADVANCE RF SIGNAL GENERATOR Type 62, 150kHz-220MHz, cw/mod..... £80	211 MARCONI RF POWER METER Type TF1020A/1, 50ohm..... £85
39 ADVANCE RF SIGNAL GENERATOR Type E2, 100kHz-100MHz, cw/mod..... £40	212 B & K AUDIO FREQUENCY SPECTROMETER Type 2113, as new..... £360
41 ERNST TURNER 6in. ELECTROSTATIC VOLTMEETER Model 32, 0-2.5kv..... £12	213 TEKTRONIX STORAGE DISPLAY UNIT Type 611, screen size 8 1/2 x 6 1/2in..... £495

Stockists of NEW SCOPEX AND SAFGAN OSCILLOSCOPES. Also many other ITEMS OF TEST EQUIPMENT AND COMPONENTS in stock. For further details contact DWAYNE STEWART

EQUIPMENT IN WORKING ORDER
Please check availability before ordering. Carriage all units. £7. VAT to be added to total of Goods and Carriage. S.A.E. for LISTS.


STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 68041
Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

WW - 056 FOR FURTHER DETAILS



Dwight Cavendish

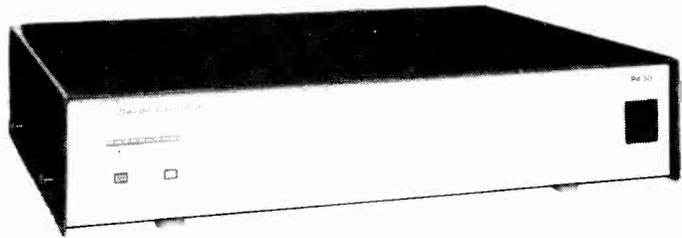So why do we put a protection circuit indicator on our amplifiers?



Well you see, the amplifier is inherently so robust that you might never know that it was operating into an adverse load, in fact it copes with anything in between a dead short and open circuit. And once you have corrected the load the amplifier automatically reverts to 'normal' working

This is just one of many features on our new range of 19" rack mounted or stand alone audio power amplifiers. The system comes complete in powers up to 500W with a variety of options and at a price which won't shock you

For further details about our new range of f.e.t. amplifiers, drop us a line or phone 0480 215778

Dwight Cavendish Company Limited.
Falcon Hill, North Rd., Epsom, Middlesex, Cumb. PE19 4EL
Tel: 0480 215778 Telex: 05331 UMWICAV G

Designers and manufacturers of electronic equipment, control systems and devices

WW - 082 FOR FURTHER DETAILS

COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RK05, NOVA, TEXAS etc.
Front load £550.00 - Top load £295.00
PSU type ME3029 for 2 drives £125.00
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details

5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 newsletter. Suppression Devices SD5A £5.95.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. **£9.95.**
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £6.95.**
BUHNER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. **OUR PRICE ONLY £12.95 complete with data.**
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

DON'T MISS THOSE BARGAINS CALL NOW, IT'S FREE!
7 days per week 24 hrs per day
01-683 1133

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. **Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high.** Useable area 16" w 10.5" h 11.5" d. Also available **LESS PSU** with internal dim 19" w, 16" d, 10.5" h, £19.95" Carriage & insurance £9.50

8" FLOPPY DISK DRIVES



Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality!! The 7100 single sided and 7200 double sided drive accept hard or soft sectoring IBM or ANSI standard drive giving a massive 0.8 MB (7100) 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. Carriage and insurance £9.75.
7100 Single sided £225.00 + Carr. 7200 Double sided £295.00 + Carr.
Optional accessories: Full technical manual £20.00 alone. £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

VIDEO MONITORS

MOTOROLA 9" open chassis monitor. Standard 240 v AC with composite 75 ohm video input, bandwidth in excess of 18 mhz. Monitors are ex equipment and although unguaranteed they are all tested prior to despatch, and have no visible burns on the screens. Dim approx. 9" x 9" x 9". Supplied complete with mains and input lead. Ideal ZX81 etc. or giving the tele back to the family! Black and white phosphor. **£35.00 + £9.00 Carr.**

12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via S0239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def. graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**

14" COLOUR superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL RGB with separate sync, and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col. definition. Brand new and guaranteed. Complete with full data & circuit. 240 v AC working. Dim. 14" x 13" x 13". **ONLY £199.00 PLUS £9.50 CARR.**

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499 + VAT



Made to the very highest spec. the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/EQUIME compatibility plus Bi-directional printing, 10 or 12 pitch, 136 or 163 chars per line, full width 381 mm friction or single sheet paper, - order now or call sales office for more information and print sample. Please specify RS232 or CENTRONICS interface. Supplied complete with FREE dust cover and daisy wheel. Optional extras: RS232 data cable £10.00 - Tech. manual £7.50. Carriage & Ins. (UK) £12.50 - Tractor feed option £120.00

TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR. + VAT
Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order.
Options: Floor stand £12.50 + VAT
KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator, Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00 pp £1.95 Data sheet on request**

RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v 2.5 ah. will deliver over 300 amps on short circuit!! Brand new at only **£2.95**

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only **£75.00**
MODEM 2B/C Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. **£85.00**
MODEM 20-1 Compact unit for use with PRESTEL or full duplex 2 wire link. 75 baud transmit - 1200 baud receive. Auto answer. **£130.00**
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. **£130.00**
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. **£130.00** Carriage. 13A £4.50. 2B/C & 20 £9.50.
For more details contact sales office.

D.C. POWER SUPPLY SPECIALS

Experimentors PSU Ex-GPO unit all silicon electronics. Outputs give +5v @ 2 amps, +12v @ 800 ma -12v @ 800 ma, +24v @ 350 ma 5v @ 50 ma. floating. Dim 160 x 120 x 350 mm. All outputs fully regulated and short circuit proof. Removed from working equipment, but untested. Complete with circuit. Transformer guaranteed. Only **£14.50 + £2.50 pp.**
CUSTOM POWER CO55 5v @ 3 amp. Very compact unit dim. approx 60 x 90 x 190 mm. Semi open chassis, full crowbar overvoltage protection. Tested Ex Equipment. **£11.95 + pp £1.25**
MINI SYSTEM PSU Ex equipment unit ideal for the small micro. Outputs give 5v @ 3 amps +12v @ 1 amp and -12v @ 300 ma. Crowbar overvoltage protection and current limit. Fully tested. Dim 70 x 165 x 320 mm. Complete with Circuit only **£12.95 + £2.00 pp.**
PERIPHERAL SYSTEM SUPPLY. Fully cased unit supplied in a Brand new or little used condition. Outputs give 5v @ 11 amps, "+- 15-17v @ 8 amps, "- 15-17v @ 8 amps and "+ 24v @ 4 amps. All outputs are crowbar protected and the 5 volt output is fully regulated. Fan cooled. Supplied tested, with circuit **£55.00 + £8.50 carr.**
MAIN FRAME SUPPLY. A real beefy unit designed for MINI or MAINFRAME use outputs give 5 volts @ 50 amps +12v @ 5 amps -12v @ 10 amps. All output are fully regulated with crowbar overvoltage protection on the 5v output. Supplied with circuit and tested. Ex-Equip. 110v AC input. Only **£49.95 + carr. £10.50.**

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed. **50+ £2.95 100+ £5.15.**
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ **£6.90** 200+ **£12.30** 200+ **£19.50**

66% DISCOUNT ELECTRONIC COMPONENTS & EQUIPMENT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you play plus we always include something from our ads, for unbeatable value!! Sold by weight.

2.5kls **£4.25 + pp £1.25**
10kls **£10.25 + pp £2.25**
5kls **£5.90 + pp £1.80**
20kls **£17.50 + pp £4.75**

ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum BONA FIDE account orders from Government depts, Schools, Universities and established companies **£20.00** Where post and packing not indicated please ADD **60p + VAT** Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

DISPLAY
-ELECTRONICS-

64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey
01-689 7702 - 01-689 6800 Telex 27924



THE Midland Computer Fair


Personal computers
Home computing
Small business systems

BINGLEY HALL, BIRMINGHAM

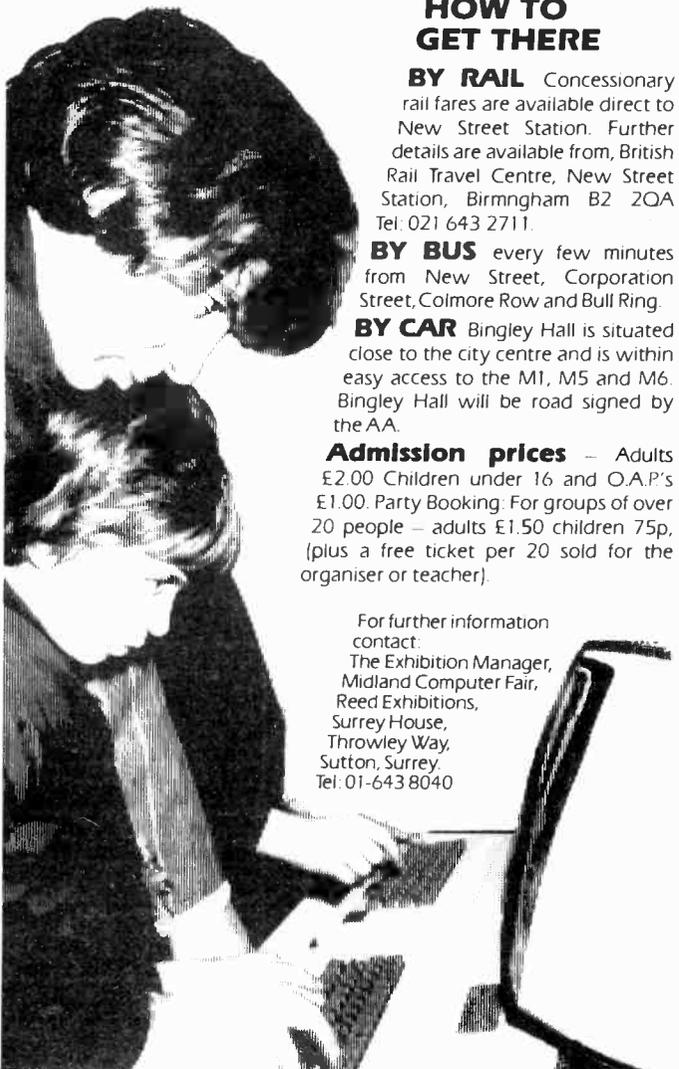28-30 APRIL 1983 Thurs & Fri 10am - 6pm
Saturday 10am - 5pm

Presented by **YOUR COMPUTER** Practical Computing

This event is the first of its kind in the Midlands, and gives you the opportunity to see and compare the enormous range of personal and home computers, small business systems, micro-computers, software packages, cassettes and scores of the very latest computer games - try them for yourself - decide how much, or how little it takes to build up your own personal computer system.



HOW TO GET THERE

BY RAIL Concessionary rail fares are available direct to New Street Station. Further details are available from, British Rail Travel Centre, New Street Station, Birmingham B2 2QA Tel: 021 643 2711.

BY BUS every few minutes from New Street, Corporation Street, Colmore Row and Bull Ring.

BY CAR Bingley Hall is situated close to the city centre and is within easy access to the M1, M5 and M6. Bingley Hall will be road signed by the AA.

Admission prices - Adults £2.00 Children under 16 and O.A.P.'s £1.00. Party Booking: For groups of over 20 people - adults £1.50 children 75p, (plus a free ticket per 20 sold for the organiser or teacher).

For further information contact:
The Exhibition Manager,
Midland Computer Fair,
Reed Exhibitions,
Surrey House,
Throwley Way,
Sutton, Surrey.
Tel: 01-643 8040

PM COMPONENTS LTD VALVE & COMPONENTS SPECIALISTS

INTEGRATED CIRCUITS

AN124	2.50	MC14011BCP	0.32
AN214Q	2.50	MC1723	0.50
AN240P	2.80	MC3357	2.25
AN2612	2.15	ML2318	1.75
AN7150	2.95	ML2328	1.75
BA521	3.35	ML2378	1.95
ET16016	1.75	ML2388	4.20
HA1366W	1.95	ML92	4.12
LA1230	1.15	MSM5807	6.75
LA4031P	2.70	PLL024	5.75
LA4102	2.95	SAA1025	7.25
LA4400	4.15	SAA5000A	3.05
LA4422	2.50	SAA5010	6.35
LC7120	3.25	SAS5605	1.75
LC7130	3.50	SAS5705	1.75
LC7131	5.50	SAS580	2.85
LC7137	5.50	SL9018	4.85
LM324N	0.45	SL9178	6.85
LM380N	0.95	SL1310	1.80
LM383T	2.95	SL1327	1.10
LM393	1.50	SL1327Q	1.10
M51513L	2.30	SN76033N	1.95
M51515L	2.95	SN76013N	1.95
MB3712	2.00	SN76013ND	1.95
MC1307F	1.00	SN76023N	1.65
MC1310P	1.50	SN76227N	1.05
MC1327	0.95	SN76532N	1.85
MC1327Q	0.95	SN76533N	1.85
MC1330P	0.95	SN76544N	1.65
MC1349P	1.20	SN76650N	1.15
MC1350P	0.76	SN76660N	0.80
MC1351F	1.50		
MC1352P	1.25		
MC1357	2.35		
MC1358	1.58		
MC1495	3.00		
MC1496	1.25		

SN76666N	0.70	TBA641A12	2.50
TA7051AP	3.95	TBA641Bx1	3.00
TA7108P	1.00	TBA641-B11	3.00
TA7120P	1.65	TBA651	1.75
TA7130P	1.50	TBA720A	2.45
TA7146	2.95	TBA750Q	2.65
TA7203	2.95	TBA800	0.89
TA7204P	2.15	TBA800AS	1.35
TA7205P	1.95	TBA820Q	1.45
TA7222AP	1.80	TBA890	2.50
TA7227P	4.25	TBA920	1.65
TA7310P	1.80	TBA950	2.35
TA7313AP	2.95	TBA950/2X	2.35
TA7611AP	2.95	TBA990	1.49
TAA550	0.28	TBA990Q	1.49
TAA570	1.95	TBA1441	2.15
TAA661B	1.20	TCA270	1.10
TAA700	1.70	TCA270SQ	1.10
TAA6305	3.50	TCA650	2.50
TBA1208	0.70	TCA800	2.15
TBA120SA	0.70	TCA830S	1.40
TBA120T	1.05	TCA940	1.65
TBA120U	1.00	TDA440	2.20
TBA231	1.25	TDA1004A	2.20
TBA235	1.50	TDA1006A	2.50
TBA396	1.75	TDA1010	2.15
TBA440N	2.55	TDA1035	2.40
TBA480Q	1.25	TDA1037	1.95
TBA510	2.50	TDA1170	1.95
TBA510Q	2.50	TDA1170S	1.95
TBA520	1.10	TDA1190	2.15
TBA520Q	1.10	TDA1270Q	3.95
TBA530	1.10	TDA1352B	1.43
TBA530Q	1.10	TDA1412	0.85
TBA540	1.25	TDA200L	1.95
TBA540Q	1.35	TDA2020	2.45
TBA550Q	1.45	TDA2030	2.80
TBA560C	1.45		
TBA570	1.00		

SEMICONDUCTORS

AAV12	0.25	BC173B	0.10
AC126	0.22	BC174	0.09
AC127	0.20	BC174A	0.09
AC128	0.20	BC177	0.15
AC128K	0.32	BC178	0.15
AC141	0.28	BC182	0.10
AC141K	0.34	BC182LB	0.10
AC142K	0.30	BC183	0.10
AC176	0.22	BC183L	0.09
AC176K	0.31	BC184LB	0.09
AC187	0.25	BC204	0.10
AC187K	0.28	BC207B	0.13
AC188	0.25	BC208B	0.13
AC188K	0.37	BC212	0.09
AD142	0.90	BC212L	0.09
AD143	0.82	BC212LA	0.09
AD149	0.70	BC213	0.09
AD161	0.39	BC213L	0.09
AD162	0.38	BC214	0.09
AD162/12	0.90	BC214C	0.09
AF115	0.75	BC214L	0.09
AF124	0.34	BC237	0.10
AF125	0.35	BC237A	0.09
AF126	0.32	BC237B	0.09
AF127	0.32	BC238	0.09
AF139	0.40	BC239	0.09
AF150	0.42	BC251A	0.12
AF239	0.42	BC252A	0.15
AU106	2.00	BC258	0.25
AU107	1.95	BC258A	0.30
AU110	2.00	BC284	0.39
AU113	2.75	BC300	0.10
BC107	0.10	BC301	0.30
BC107A	0.11	BC303	0.26
BC107B	0.11	BC307	0.09
BC108	0.10	BC307A	0.09
BC108A	0.11	BC307B	0.09
BC108B	0.12	BC322	0.12
BC109	0.10	BC328	0.10
BC109B	0.12	BC337	0.10
BC109C	0.12	BC338	0.09
BC114	0.11	BC347A	0.13
BC116A	0.15	BC461	0.35
BC117	0.19	BC478	0.20
BC119	0.24	BC527	0.20
BC125	0.25	BC547	0.10
BC140	0.31	BC548	0.10
BC141	0.25	BC549A	0.08
BC142	0.21	BC550	0.08
BC143	0.24	BC557	0.08
BC147	0.09	BC557A	0.08
BC147B	0.09	BC557B	0.08
BC148A	0.09	BC558	0.10
BC148B	0.09	BCY33A	1.60
BC149	0.09	BD115	0.30
BC157	0.12	BD116	0.60
BC158	0.09	BD124P	0.59
BC159	0.09	BD131	0.32
BC160	0.28	BD132	0.35
BC161	0.28	BD133	0.40
BC170B	0.15	BD135	0.30
BC171	0.09	BD136	0.30
BC171A	0.10	BD137	0.32
BC171B	0.10	BD138	0.30
BC172	0.10	BD139	0.32
BC172B	0.10	BD140	0.30
BC172C	0.10	BD144	1.10

BD159	0.65	BF362	0.38	R2008B	1.70
BD179	0.72	BF371	0.38	R2010B	1.70
BD182	0.70	BF394	0.19	R2322	0.66
BD201	0.83	BF422	0.32	R2540	2.48
BD202	0.65	BF457	0.32	RCA16334	0.90
BD203	0.78	BF458	0.28	RCA16335	0.80
BD204	0.70	BF459	0.36	SK5E5F	1.45
BD222	0.46	BF595	0.23	TIP29	0.40
BD223	0.48	BF597	0.25	TIP29C	0.42
BD225	0.48	BF639	0.23	TIP30C	0.43
BD232	0.35	BF640	0.23	TIP31C	0.42
BD233	0.35	BF641	0.28	TIP32C	0.42
BD234	0.35	BF688	0.30	TIP33B	0.75
BD236	0.45	BF690	1.50	TIP34B	0.75
BD237	0.40	BF691	1.75	TIP41A	0.45
BD238	0.40	BF742	0.28	TIP41C	0.45
BD241	0.40	BF743	0.28	TIP42C	0.47
BD242	0.50	BFW92	0.85	TIP47	0.65
BD246	0.60	BFX29	0.30	TIP120	0.60
BD376	0.32	BFX84	0.26	TIP125	0.65
BD410	0.55	BFX85	0.32	TIP142	1.75
BD434	0.55	BFX86	0.30	TIP146	1.75
BD437	0.50	BFX88	0.25	TIP161	2.95
BD438	0.60	BFY50	0.21	TIP295S	0.80
BD506	0.50	BFY51	0.21	TIP305S	0.55
BD508	0.40	BFY52	0.25	TIS91	0.20
BD520	0.65	BFY90	0.77	TV106/2	1.50
BD538	0.65	BR100	0.26	22219	1.28
BD597	0.75	BR101	0.38	2N2905	0.40
BD697	1.10	BRC4443	0.85	2N3053	0.40
BD698	1.10	BT106	1.22	2N3054	0.59
BD707	0.80	BT108	1.22	2N3055	0.52
BDX32	1.50	BT116	1.20	2N3702	0.12
BF115	0.35	BT119	1.65	2N3703	0.12
BF127	0.24	BT120	1.65	2N3704	0.12
BF154	0.12	BU105	1.22	2N3705	0.12
BF158	0.22	BU108	1.69	2N3706	0.12
BF160	0.27	BU124	1.25	2N3708	0.12
BF167	0.24	BU125	£1.25	2N3773	1.75
BF173	0.22	BU126	1.80	2N3792	1.35
BF177	0.38	BU204	1.65	2N4427	1.50
BF178	0.26	BU205	1.30	2N4444	1.15
BF179	0.34	BU208	1.39	2N5294	0.42
BF180	0.29	BU208A	1.52	2N5296	0.48
BF181	0.29	BU326	1.20	2N5298	0.60
BF182	0.29	BU326A	1.42	2N5496	0.60
BF183	0.29	BU326S	1.90	2SA715	0.85
BF184	0.28	BU407	1.24	2SC495	0.80
BF185	0.28	BU500	2.25	2SC496	0.80
BF194	0.11	BU526	1.90	2SC1096	0.80
BF195	0.11	BUY69B	1.70	2SC1172Y	2.20
BF196	0.11	BU3000	0.98	2SC1173	1.15
BF197	0.11	MJE340	0.40	2SC1306	1.00
BF198	0.16	MJE520	0.48	2SC1307	1.50
BF199	0.14	MPSA12	0.20	2SC1449	0.80
BF200	0.40	MPSA13	0.20	2SC1678	1.25
BF241	0.15	MPSA92	0.30	2SC1945	2.10
BF245	0.30	MRF450A	11.50	2SC1953	0.95
BF246	0.28	MRF453	13.50	2SC1957	0.80
BF256/LC	0.38	MRF454	17.50	2SC1969	1.95
BF257	0.28	MRF475	25.00	2SC2028	1.15
BF258	0.28	MRF477	15.00	2SC2029	1.95
BF259	0.28	OC23	1.50	2SC2078	1.45
BF271	0.26	OC42	0.55	2SC2091	0.85
BF273	0.13	OC44	0.55	2SC2166	1.95
BF336	0.34	OC45	0.55	2SC2314	0.80
BF337	0.29	OC70	0.45	2SD234	5.00
BF338	0.32	OC71	0.40	3N211	1.50
BF355	0.37	OC81	0.50		

DIODES

AA119	0.08	BY199	0.40	IN4003	0.04
BA102	0.17	BY206	0.14	IN4004	0.05
BA115	0.13	BY208-800	0.33	IN4005	0.05
BA145	0.16	BY210-800	0.33	IN4006	0.06
BA148	0.17	BY223	0.90	IN4007	0.06
BA154	0.06	BY288-400	0.22	IN4148	0.02
BA155	0.13	BY299-800	0.22	IN4448	0.10
BA156	0.15	BYX10	0.20	IN5401	0.12
BA157	0.30	BYX36-150R	0.20	IN5402	0.14
BAX13	0.04	BYX38-600R	0.60	IN5403	0.12
BAX16	0.06	BYX65-600	0.30	IN5404	0.12
BB105B	0.30	BYX71-600	0.80	IN5405	0.13
BT151	0.79	BZY95C30	0.35	IN5407	0.16
BY126	0.10				

PHONE
0474 813225
3 LINES

P. M. COMPONENTS LTD
SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
966371
PM COMP




A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 18.50	EA79 1.96	EF183 0.65	G237 4.50	PCF87 0.40	QV5-500 115.00	U17 8.00	2B7 1.50	6B8A 2.15	10C2 0.70	92AG 11.85
A1998 11.50	EAA91 0.60	EF184 0.65	HAA91 1.00	PCF200 1.35	U041 3.50	2D21 0.95	6B85 4.50	10D2 1.25	92AV 11.85	92AV 11.85
A2067 11.50	EABC80 0.68	EF731 1.80	HABC80 0.90	PCF201 1.35	U042 3.50	2D21W 2.50	6B85 2.50	10F1 0.75	92AV 11.85	108C1 1.50
A2134 14.95	EAC91 2.50	EF732 1.80	HBC90 0.75	PCF800 0.40	R10 4.00	V339 3.50	6B86 1.50	10G6 1.95	108C1 1.50	108C2 1.50
A2293 8.50	EA42 1.20	EF800 11.00	HBC91 0.80	PCF801 1.35	R16 12.00	V339 3.50	6B87 1.50	10H1 2.50	108C1 1.50	108C3 1.50
A2426 17.50	EA7801 1.40	EF804S 9.85	HF93 0.75	PCF802 0.60	R17 1.50	V422 2.50	6B88 1.50	10I1 2.50	108C1 1.50	108C4 1.50
A2521 21.00	EB34 1.50	EF805S 9.85	HF94 0.60	PCF803 1.48	R18 2.50	V425 2.50	6B89 1.50	10J1 2.50	108C1 1.50	108C5 1.50
A2599 37.50	EB41 3.00	EF806S 9.85	HK90 1.05	PCF806 1.00	R19 6.95	V440 4.50	6B90 1.50	10K1 2.50	108C1 1.50	108C6 1.50
A2900 11.50	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R20 1.20	V440 4.50	6B91 1.50	10L1 2.50	108C1 1.50	108C7 1.50
A3042 24.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R21 1.20	V440 4.50	6B92 1.50	10M1 2.50	108C1 1.50	108C8 1.50
A3283 24.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R22 1.20	V440 4.50	6B93 1.50	10N1 2.50	108C1 1.50	108C9 1.50
AC/HL/DD 4.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R23 1.20	V440 4.50	6B94 1.50	10O1 2.50	108C1 1.50	108C10 1.50
ACP 4.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R24 1.20	V440 4.50	6B95 1.50	10P1 2.50	108C1 1.50	108C11 1.50
AC/THI 4.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R25 1.20	V440 4.50	6B96 1.50	10Q1 2.50	108C1 1.50	108C12 1.50
AC/VP2 4.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R26 1.20	V440 4.50	6B97 1.50	10R1 2.50	108C1 1.50	108C13 1.50
AH221 39.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R27 1.20	V440 4.50	6B98 1.50	10S1 2.50	108C1 1.50	108C14 1.50
AH238 39.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R28 1.20	V440 4.50	6B99 1.50	10T1 2.50	108C1 1.50	108C15 1.50
AL60 6.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R29 1.20	V440 4.50	6B100 1.50	10U1 2.50	108C1 1.50	108C16 1.50
ARP12 0.70	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R30 1.20	V440 4.50	6B101 1.50	10V1 2.50	108C1 1.50	108C17 1.50
ARP34 1.25	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R31 1.20	V440 4.50	6B102 1.50	10W1 2.50	108C1 1.50	108C18 1.50
ARP35 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R32 1.20	V440 4.50	6B103 1.50	10X1 2.50	108C1 1.50	108C19 1.50
AZ31 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R33 1.20	V440 4.50	6B104 1.50	10Y1 2.50	108C1 1.50	108C20 1.50
BL63 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R34 1.20	V440 4.50	6B105 1.50	10Z1 2.50	108C1 1.50	108C21 1.50
BS450 6.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R35 1.20	V440 4.50	6B106 1.50	10A1 2.50	108C1 1.50	108C22 1.50
BT5 49.50	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R36 1.20	V440 4.50	6B107 1.50	10B1 2.50	108C1 1.50	108C23 1.50
BT19 32.50	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R37 1.20	V440 4.50	6B108 1.50	10C1 2.50	108C1 1.50	108C24 1.50
BT79 12.50	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R38 1.20	V440 4.50	6B109 1.50	10D1 2.50	108C1 1.50	108C25 1.50
CIK 16.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R39 1.20	V440 4.50	6B110 1.50	10E1 2.50	108C1 1.50	108C26 1.50
C3JA 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R40 1.20	V440 4.50	6B111 1.50	10F1 2.50	108C1 1.50	108C27 1.50
C1108 55.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R41 1.20	V440 4.50	6B112 1.50	10G1 2.50	108C1 1.50	108C28 1.50
C1134 17.50	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R42 1.20	V440 4.50	6B113 1.50	10H1 2.50	108C1 1.50	108C29 1.50
C1148A 89.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R43 1.20	V440 4.50	6B114 1.50	10I1 2.50	108C1 1.50	108C30 1.50
C1149/1 60.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R44 1.20	V440 4.50	6B115 1.50	10J1 2.50	108C1 1.50	108C31 1.50
C1534 32.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R45 1.20	V440 4.50	6B116 1.50	10K1 2.50	108C1 1.50	108C32 1.50
C3JA 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R46 1.20	V440 4.50	6B117 1.50	10L1 2.50	108C1 1.50	108C33 1.50
CC1 2.60	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R47 1.20	V440 4.50	6B118 1.50	10M1 2.50	108C1 1.50	108C34 1.50
CC30 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R48 1.20	V440 4.50	6B119 1.50	10N1 2.50	108C1 1.50	108C35 1.50
CC33 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R49 1.20	V440 4.50	6B120 1.50	10O1 2.50	108C1 1.50	108C36 1.50
CC35 2.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R50 1.20	V440 4.50	6B121 1.50	10P1 2.50	108C1 1.50	108C37 1.50
CCV25 9.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R51 1.20	V440 4.50	6B122 1.50	10Q1 2.50	108C1 1.50	108C38 1.50
CV Nos Prices on request	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R52 1.20	V440 4.50	6B123 1.50	10R1 2.50	108C1 1.50	108C39 1.50
D63 1.20	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R53 1.20	V440 4.50	6B124 1.50	10S1 2.50	108C1 1.50	108C40 1.50
DAF91 0.45	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R54 1.20	V440 4.50	6B125 1.50	10T1 2.50	108C1 1.50	108C41 1.50
DAF96 0.65	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R55 1.20	V440 4.50	6B126 1.50	10U1 2.50	108C1 1.50	108C42 1.50
DC70 1.75	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R56 1.20	V440 4.50	6B127 1.50	10V1 2.50	108C1 1.50	108C43 1.50
DC90 1.20	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R57 1.20	V440 4.50	6B128 1.50	10W1 2.50	108C1 1.50	108C44 1.50
DCX4-1000	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R58 1.20	V440 4.50	6B129 1.50	10X1 2.50	108C1 1.50	108C45 1.50
DCX4-5000	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R59 1.20	V440 4.50	6B130 1.50	10Y1 2.50	108C1 1.50	108C46 1.50
DET10 6.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R60 1.20	V440 4.50	6B131 1.50	10Z1 2.50	108C1 1.50	108C47 1.50
DET22 28.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R61 1.20	V440 4.50	6B132 1.50	10A1 2.50	108C1 1.50	108C48 1.50
DET24 39.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R62 1.20	V440 4.50	6B133 1.50	10B1 2.50	108C1 1.50	108C49 1.50
DET25 22.00	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R63 1.20	V440 4.50	6B134 1.50	10C1 2.50	108C1 1.50	108C50 1.50
DF91 0.70	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R64 1.20	V440 4.50	6B135 1.50	10D1 2.50	108C1 1.50	108C51 1.50
DF92 0.60	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R65 1.20	V440 4.50	6B136 1.50	10E1 2.50	108C1 1.50	108C52 1.50
DF96 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R66 1.20	V440 4.50	6B137 1.50	10F1 2.50	108C1 1.50	108C53 1.50
DF97 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R67 1.20	V440 4.50	6B138 1.50	10G1 2.50	108C1 1.50	108C54 1.50
DF98 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R68 1.20	V440 4.50	6B139 1.50	10H1 2.50	108C1 1.50	108C55 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R69 1.20	V440 4.50	6B140 1.50	10I1 2.50	108C1 1.50	108C56 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R70 1.20	V440 4.50	6B141 1.50	10J1 2.50	108C1 1.50	108C57 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R71 1.20	V440 4.50	6B142 1.50	10K1 2.50	108C1 1.50	108C58 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R72 1.20	V440 4.50	6B143 1.50	10L1 2.50	108C1 1.50	108C59 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R73 1.20	V440 4.50	6B144 1.50	10M1 2.50	108C1 1.50	108C60 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R74 1.20	V440 4.50	6B145 1.50	10N1 2.50	108C1 1.50	108C61 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R75 1.20	V440 4.50	6B146 1.50	10O1 2.50	108C1 1.50	108C62 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R76 1.20	V440 4.50	6B147 1.50	10P1 2.50	108C1 1.50	108C63 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R77 1.20	V440 4.50	6B148 1.50	10Q1 2.50	108C1 1.50	108C64 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R78 1.20	V440 4.50	6B149 1.50	10R1 2.50	108C1 1.50	108C65 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R79 1.20	V440 4.50	6B150 1.50	10S1 2.50	108C1 1.50	108C66 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R80 1.20	V440 4.50	6B151 1.50	10T1 2.50	108C1 1.50	108C67 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25	R81 1.20	V440 4.50	6B152 1.50	10U1 2.50	108C1 1.50	108C68 1.50
DF99 0.85	EB91 0.50	EF812 0.85	HL2K 3.50	PCF808 1.25						

MARK 1983 WITH GAPS IN CIRCUIT FILES WELL-PLUGGED

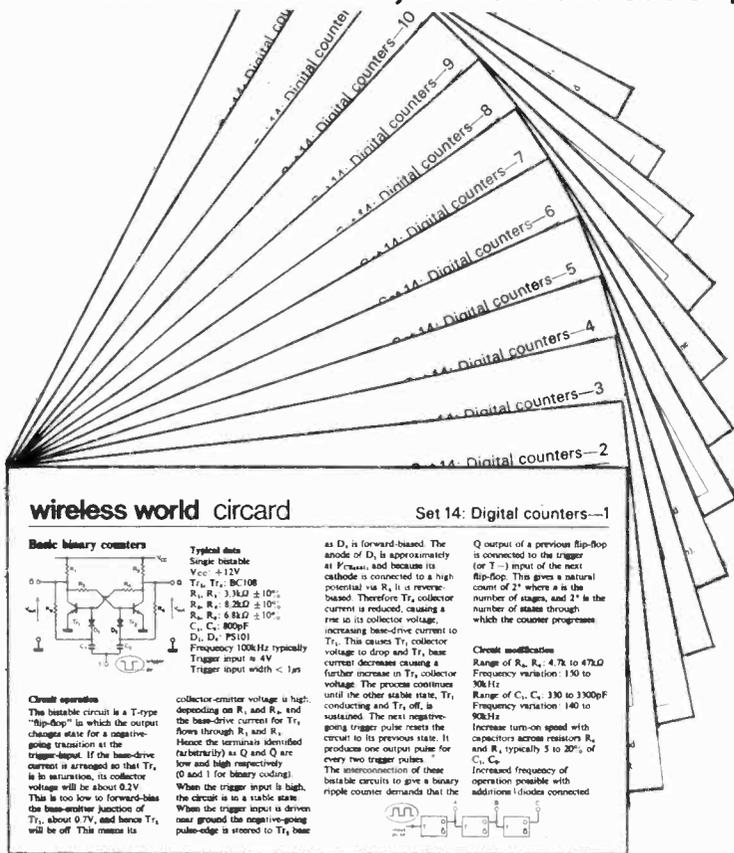WIRELESS WORLD CIRCARDS last year benefited many 'new generation' readers who bought at 1976 bargain prices + 10% discount for 10 sets!
Most sets are still available although companion volumes
CIRCUIT DESIGNS 1, 2 and 3 are out of print (CIRCARDS sets 1 to 30).



The Offer stands, so order now your sets of 127 x 204mm cards in plastic wallets. These unique circuit cards normally contain descriptions and performance data of 10 tested circuits, together with ideas for modifying them to suit special needs.

- 1 Basic Active filters 2 Switching Circuits, comparators and Schmitts (But these gaps cannot be filled) *
6 Constant current circuits 7 Power amplifiers 8 Astable circuits 9 Optoelectronics 10 Micro power circuits 11 Basic logic gates 12 Wideband amplifiers 13 Alarm circuits 14 Digital Counters 15 Pulse modulators 16 Current differencing amplifiers – signal processing 17 Current differencing amplifiers – signal generation 18 Current differencing amplifiers – measurement and detection 19 Monostable circuits 20 Transistor pairs 21 Voltage-to-frequency converters 22 Amplitude modulation and detection 23 Reference circuits 24 Voltage regulators 25 RC oscillators – 1 26 RC oscillators – 2 27 Linear cmos – 1 28 Linear cmos – 2 29 Analogue multipliers 30 Rms/log/power laws 31 Digital multipliers 32 Transistor arrays 33 Differential and bridge amplifiers 34 Analogue gate applications – 1 35 Analogue gate applications – 2.

*Photocopies only: 3 Waveform generators 4A.C. measurement 5 Audio circuits @ £3.20 each set.

**To Electrical-Electronic Press
General Sales Department
Room 108
Quadrant House
Sutton
Surrey SM2 5AS**

Company registration in England
Quadrant House, The Quadrant,
Sutton, Surrey SM2 5AS
Reg. No 677128

Please send me the following sets of
Circards.....£2 each,
£18 for 10 post free.
Remittance enclosed payable
to BUSINESS PRESS INTERNATIONAL
Name (Please print)
Address (Please print).....
.....

ELECTROVALUE

• 24 HOUR NORMAL DESPATCH TIME
 • ESTABLISHED 1965
 • ALL GOODS GUARANTEED BRAND NEW AND TO SPECIFICATION
 • APPOINTED SIEMENS DISTRIBUTORS

CAPACITORS

Polystyrene, Siemans
 5% Tolerance 160V
 5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF 15p;
 47, 56, 68, 82, 100, 120, 150, 180, 220,
 270, 330, 390, 470, 560, 680, 820pF, 1n,
 1n2, 1n5, 1n8, 2n2, 2n7, 3n3, 3n9, 4n7,
 10p; 5n6, 6n8, 8n2, 10n, 13p
 Ceramic Very small 1.8, 2.2, 2.7 etc. up to
 1n5p each, 1n5, 2n2, 3n3, 4n7, 6n8, 8n2,
 10n, 22n, 33p, 47p, 77p, 100n, 8p
 Polyester, Siemans Layer Type 7.5mm
 lead spacing 100V
 1n, 1n5, 2n2, 3n3m6p; 4n7, 6n8, 8n2, 10n
 12n, 15n, 18n, 22n, 33n, 47n, 7p, 56n, 88n,
 7p, 8n, 100n, 9p, 120n, 330n, 390n, 470n,
 220n, 12p, 27n, 330n, 330n, 390n, 470n,
 15p; 560n, 680n, 24p; 10mm spacing 1uF
 25p; 15mm spacing 2u, 3p; 22.5mm,
 spacing 1uF 400V 50p; 3.33uF 100V 69p; in
 depth stocks

DIGITAL & ANALOGUE I.C. SECTION

COMPUTER		74LS	
74LS00	11	74LS161	36
74LS02	12	74LS163	36
74LS04	12	74LS164	30
74LS08	12	74LS166	60
74LS10	12	74LS168	74
74LS11	12	74LS170	55
74LS12	12	74LS173	45
74LS13	12	74LS174	45
74LS14	12	74LS175	40
74LS15	12	74LS191	36
74LS16	12	74LS193	40
74LS17	12	74LS195	39
74LS18	12	74LS196	48
74LS19	12	74LS197	60
74LS20	12	74LS201	48
74LS21	12	74LS202	55
74LS22	12	74LS204	55
74LS23	12	74LS205	55
74LS24	12	74LS206	55
74LS100	12	74LS282	55

CMOS	
4001	10
4002	12
4003	20
4004	10
4005	10
4006	10
4007	10
4008	10
4009	24
4010	24
4011	11
4012	15
4013	11
4014	26
4015	26
4016	26
4017	26
4018	26
4019	25
4020	42
4021	40
4022	39
4023	14
4024	32
4025	13
4026	80
4027	20
4028	39
4029	45
4030	15
4041	40
4042	20
4043	24
4044	34
4045	29
4046	23
4047	14
4048	23
4049	23
4050	23
4051	23
4052	23
4053	23
4054	23
4055	23
4056	23
4057	23
4058	23
4059	23
4060	23
4061	23
4062	23
4063	23
4064	23
4065	23
4066	23
4067	23
4068	23
4069	23
4070	13
4071	13
4072	13

CRYSTALS	
4.433	128
4.915	157
5.000	157
5.026	128
6.000	157
6.144	157
6.5536	128
8.867	128
10.000	157
10.432	188

ZENNER DIODES

400mV/2.7-3.5V 7p; 1.3W 303 100V
 15p; 20W/7.5-75V £1.98

REGULATORS


7805, 7806, 7808, 7812, 7815, 7818, 7824 each 40p
 78L05, 78L12, 78L15, 78L24 each 32p
 7912, 7915, 7918, 7924, 7915, 7912 each 50p

CONNECTORS

DIN AUDIO		PARALLEL TYPE	
2	16	16	1.10
3	16	16	1.10
4	16	16	1.10
5	16	16	1.10
6	16	16	1.10
7	16	16	1.10

BOXES

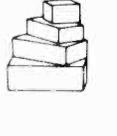High quality Black ABS plastic or die cast plain or stove grey
 L W D ABS Plain Stove Gr
 100 60 25 2002 96p 5001P 500 5001 123p
 113 63 31 2003 109p 5003P 154p 5003 184p
 120 66 40 2001 115p 5004P 162p 5004 210p
 152 82 50 2005 134p 5005P 216p 5005 288p
 192 113 61 2006 236p 5006P 314p 5006 401p




VERO RANGE plastic boxes		G RANGE professional Instrument	
72	47	25	21024
120	50	35	21390
180	110	55	21391

VEROBOX CASES


to give a completely professional finish to a much valued project.
 ABS, light grey top; dark grey bottom + 2 anodised panels

L	D	H	TYPE	PRICE
205	140	40	21034	£5.02
205	140	75	21035	£5.02
205	140	110	21036	£6.54
180	120	39	21037	£4.11
180	120	65	21038	£4.40
180	120	90	21039	£4.69
155	85	39	21040	£3.31
155	85	60	21041	£3.31
155	85	80	21042	£4.30
125	65	30	21043	£2.48
125	65	39	21048	£3.15
125	65	50	21049	£3.56

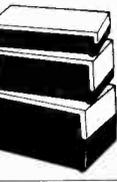

METERS

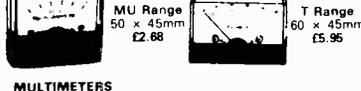Large range of types in stock, also probes, leads, accessor etc.
PANEL MOUNTING in 50, 100, 500mA; 1, 5, 10, 50, 100, 500mA, 1A either model.



MULTIMETERS

NH56A	YN360TR
NEW	NEW
20KΩ/V	AC/DC/R
AC/DC/R	dB/Transist
RES/dB	Test
in 23	in 23
ranges	ranges
130 x 88 x 37mm	145 x 96 x 45mm
£11.20	£11.45N

BC214	09	BFR39-41	23	E1210	76
BC214L	09	BFR79-81	23	E2506	154
BC238C	09	BFT65	119	E8383	20
BC239C	09	BFT66	192	MJ2955	90
BC258B	06	BFX29	24	MJE555	55
BC267B	06	BFX26	24	MJE3955	95
BC300	32	BFX85	24	MJ3055	70
BC301	24	BFX87	28	MPF102	40
BC303	30	BFX88	26	MPS6531	40
BC327	11	BFV50	24	MPS6534	42
BC337	14	BFV51	24	MPSA12	36
BC338	14	BFV52	24	MPSA63	38
BC339	11	BFY90	143	NAS20655	81
BC339	11	BRF30	70	OA47	12
BC413	09	BRF40	110	OA90	10
BC414	09	BRG64	110	OA91	10
BC417	24	BRV39	45	OA91	10
BC427	24	BSX20	22	OC220	14
BC456	10	BSX21	22	OC202	14
BC457	10	BSX22	22	OC208	14
BC458	09	BSX23	22	OC208	14
BC459	09	BSX24	22	OC208	14
BC460	09	BSX25	22	OC208	14
BC461	09	BSX26	22	OC208	14
BC462	09	BSX27	22	OC208	14
BC463	09	BSX28	22	OC208	14
BC464	09	BSX29	22	OC208	14
BC465	09	BSX30	22	OC208	14
BC466	09	BSX31	22	OC208	14
BC467	09	BSX32	22	OC208	14
BC468	09	BSX33	22	OC208	14
BC469	09	BSX34	22	OC208	14
BC470	09	BSX35	22	OC208	14
BC471	09	BSX36	22	OC208	14
BC472	09	BSX37	22	OC208	14
BC473	09	BSX38	22	OC208	14
BC474	09	BSX39	22	OC208	14
BC475	09	BSX40	22	OC208	14
BC476	09	BSX41	22	OC208	14
BC477	09	BSX42	22	OC208	14
BC478	09	BSX43	22	OC208	14
BC479	09	BSX44	22	OC208	14
BC480	09	BSX45	22	OC208	14
BC481	09	BSX46	22	OC208	14
BC482	09	BSX47	22	OC208	14
BC483	09	BSX48	22	OC208	14
BC484	09	BSX49	22	OC208	14
BC485	09	BSX50	22	OC208	14
BC486	09	BSX51	22	OC208	14
BC487	09	BSX52	22	OC208	14
BC488	09	BSX53	22	OC208	14
BC489	09	BSX54	22	OC208	14
BC490	09	BSX55	22	OC208	14
BC491	09	BSX56	22	OC208	14
BC492	09	BSX57	22	OC208	14
BC493	09	BSX58	22	OC208	14
BC494	09	BSX59	22	OC208	14
BC495	09	BSX60	22	OC208	14
BC496	09	BSX61	22	OC208	14
BC497	09	BSX62	22	OC208	14
BC498	09	BSX63	22	OC208	14
BC499</					

A COMPETITION OPEN TO ALL WIRELESS WORLD READERS WITH £8000 IN CASH PRIZES

Design an Electronic Device to help the Disabled

Could you design a piece of equipment to help a disabled person? If so, you would — in addition to undertaking this worthy task — be eligible to win a substantial cash prize.

Our competition is open to individuals or groups resident in the UK. You register your entry using the form below, sending it to the Editor to arrive at his office not later than June 30th 1983. The designs themselves must be submitted to his office by 1st October 1983.

Entries, which will be judged by a group of eminent engineers and doctors, must consist of the following: - a statement of the design objectives; an overall description of the device; detailed circuit descriptions and diagrams; a model of the device or a model of a unique aspect of the design sufficient to demonstrate its feasibility.

The finalists will be invited to London to talk over their entries with the judges and be awarded their prizes. The prizes are:

1st prize £2,500
2nd prize £1,500

and the 4 runners up will be awarded prizes each of
£1,000

To make sure you have the maximum time to undertake your design, return your entry form now!

"DESIGN AN ELECTRONIC DEVICE TO HELP THE DISABLED" LIST OF RULES

1. The competition is open to U.K. residents only.
2. Entrants can be individuals or groups.
3. All participants must register their interest in entering the competition on the form provided which must be returned to the Wireless World Editorial Department by the 30th June 1983.
4. All entrants agree to give Wireless World first serial publication rights to an article describing the entry.
5. All entrants indemnify Wireless World from any liability in respect of injury to people or damage to property arising from the use of the design.
6. All submitted designs must be the original work of the entrant or entrants and must not infringe the rights of third parties in anyway.
7. All submissions should consist of:
 - a) A statement of design objectives
 - b) An overall description of the device
 - c) Detailed circuit descriptions and diagrams
 - d) A model of the device or the unique aspect of the design sufficient to demonstrate its feasibility.
8. The design will be judged on:
 - a) Originality and benefit to the handicapped
 - b) Potential for production
 - c) Elegance of engineering design
 - d) Electronics content
 - e) Design reliability
 - f) Simplicity of operation
 - g) Freedom from excessive maintenance
 - h) Safety.
9. Software only solutions are not accepted.
10. The judges' decision is final.
11. All designs must be submitted to the Wireless World Editor by the 1st October 1983.
12. Shortlisted entrants must be prepared to travel to a venue in London sometime during November and December 1983 to demonstrate their design. All costs will be paid by the journal.
13. Employees of Business Press International are not allowed to enter this competition.

wireless world

COMPETITION
ENTRY FORM

"Design an electronic device to help the disabled"

Name of competitor _____

Address _____

Telephone (home) _____

(business) _____

I intend to enter the competition and to abide by the rules as laid down in the April 1983 issue of Wireless World

I understand that, in order to qualify, my entry must in the hand of the judges by 1st October 1983.

Signature _____

Date _____

Please send this form, as soon as possible, to

The Editor, WIRELESS WORLD
Room L302, Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS.

Receipt of the form will be acknowledged.

HART

LINSLEY-HOOD
300 SERIES AMPLIFIERS



These latest designs from the drawing board of John Linsley-Hood, engineered to the very highest standard, represent the very best that is available on the kit market today. The delicacy and transparency of the tone quality enable these amplifiers to outperform on a side-by-side comparison, the bulk of amplifiers in the commercial market-place and even exceed the high standard set by his earlier 75-watt design.

Three versions are offered, a 30-watt with Darlington output transistors, and a 35- and 45-watt, both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2.

As with all Hart kits the constructor's interests have been looked after in a unique way by reducing the conventional (and boring) wiring almost to the point of extinction.

Any of these kits represents a most cost-effective route to the very highest sound quality with the extra bonus of the enjoyment of building a sophisticated piece of equipment.

30-watt Darlington amplifier, fully integrated with tone controls and magnetic pick-up facility. Total cost of all parts is £81.12. Special offer price for complete kits is £65.

35-watt Mosfet amplifier. Total cost of parts £98.41. Special offer for complete kits £79.50.

45-watt Mosfet amplifier. Total cost of parts £104.95. Special offer price for complete kits £83.50.

(Reprints of original Articles from Hi-Fi News 50p. Post free. No VAT. Reprints of MOSFET article 25p. No V.A.T. Post free.


'P.W. WINTON' TUNER AND AMPLIFIER



Snaazzy matching slimline tuner and amplifier in beautiful wooden cabinets. These Ted Rule designs are for the enthusiast. Tuner covers LW, MW, SW, FM and TV sound! Digital frequency readout with clock and timer features. FM has 6 section front end and switchable bandwidth for exceptional fringe area performance. Amplifier has Toroidal transformer, Mosfet output stages, 50 watts per channel and got a cracking review in Practical Wireless.

Tuner. Complete Kit..... £123
Amplifier. Complete Kit..... £29

LINSLEY-HOOD CASSETTE RECORDERS

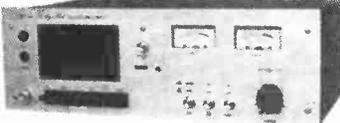

We have done two kits to this design, one using the original car cassette mechanism and the newer version using a very high quality front loading deck. This new deck has an excellent W & F performance and fitted with our latest Sendust Alloy Super Head gives an incredible frequency range (with good tape you can see 23KHz on ours!).

Linsley-Hood Cassette Recorder 1..... £75.00
Linsley-Hood Cassette Recorder 2..... £94.90
Reprints of "WW" Articles..... 70p. No VAT

Please Note: New Phone Number: (0691) 652894

Personal callers are always very welcome but please note that we are closed all day Saturday

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks..... £4.25
HM90 High Beta Permalloy Head. A hard-wearing, higher performance head with metal capability..... £6.20
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response..... £8.20
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head..... £7.40
Please consult our list for technical data on these and other Special Purpose Heads.

STUART TAPE CIRCUITS

(For reel-to-reel decks)

These circuits are just the thing for converting that old valve tape deck into a useful transistorised recorder. Total system is a full three head recorder with separate record and replay sections for simultaneous off tape monitoring. We also stock the heads. This kit is well engineered but does not have the detailed instructions that we give with our more recent designs. We would not therefore recommend it to beginners. Reprints of the original three articles 45p. Post free. No VAT.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £3.80 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy cassette size means operated unit prevents build-up of residual head magnetisation causing noise on playback..... £3.68

CASSETTE MOTORS

Brand New Governed 12v DC Tape Drive Motor Type MMI-6A2LK
As used in SF925 and many other decks. 40mm Dia x 35mm Long, Shaft 10.5mm long x 2mm Dia. 6 x 2.5mm Mounting Holes on 26mm PCD on shaft end face. Anti-clockwise rotation at rated speed of 2200 RPM. Free run current 25mA. £4.85 each.

Lenco CRV/FFR.
We have a small quantity of spare motors for these decks at £5 each complete with drive pulley. Spare belts for FFR or CRV 90p (Large), 30p (Small).

Full details of the entire range of HART products is contained in our illustrated lists. Ask for your FREE copy NOW.

Enquiries for lists are also welcome from overseas but please let us have three IRCs to cover the cost of surface post or 5 IRCs for airmail.

In a hurry? A telephone order with credit card number placed before 3 p.m. will be despatched THAT DAY! Please add part cost of post, packing and insurance as follows:

INLAND	OVERSEAS
Orders up to £10 - 50p	Postage at cost plus £2
Orders £10 to £49 - £1	documentation and handling
Orders over £50 - £1.50	

ALL PRICES PLUS VAT



THIS MONTH'S SPECIAL OFFER COMPLETE STEREO CASSETTE DECK

Brand-new high-quality stereo cassette unit with built-in record and play electronics. Ideal for use with any hi-fi system or music centre. Only a single 9-volt DC supply is required to power the who e unit.

Microphone and line inputs are provided on both channels and the line output will feed into any normal hi-fi amplifier. Erase and bias is provided by an ultrasonic oscillator, automatically switching to the correct level when a chrome or ferric cassette is put in place. Overall size 180mm x 130mm x 73mm. Complete with 3-digit counter.

We value this deck at about £30. OUR VERY SPECIAL PRICE INCLUDING VAT AND POSTAGE - THIS IS ALL YOU PAY - ONLY £18.34 (while stocks last).

FEED YOUR MICRO BYTES WITH OUR SOLENOID CONTROLLED CASSETTE DECK



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-dig t memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

LINSLEY-HOOD 100 WATT POWER AMPLIFIER

Our complete kit for this brilliant new design is the same size as our Linsley-Hood Cassette Recorder 2. Kit includes all parts for two power amplifiers with large heatsink area, huge power supply and speaker protection circuit. Total cost of all parts is £114.46 but our special introductory price for all parts bought together is only £105.50.

LAST CHANCE AT THIS PRICE. METALFILM RESISTORS 1% Tolerance, 1/4 Watt

100R	1k	10k	100k
110R	1k1	11k	110k
120R	1k2	12k	120k
130R	1k3	13k	130k
150R	1k5	15k	150k
160R	1k6	16k	160k
180R	1k8	18k	180k
200R	2k	20k	200k
220R	2k2	22k	220k
240R	2k4	24k	240k
270R	2k7	27k	270k
300R	3k	30k	300k
330R	3k3	33k	330k
360R	3k6	36k	360k
390R	3k9	39k	390k
430R	4k3	43k	430k
470R	4k7	47k	470k
510R	5k1	51k	510k
560R	5k6	56k	560k
620R	6k2	62k	620k
680R	6k8	68k	680k
750R	7k5	75k	750k
820R	8k2	82k	820k
910R	9k1	91k	910k

ONLY 3p EACH

High Quality High Stability. Huge Strength. Minimum order £20. Minimum 5 pcs per value. 89 Values (E24)

VAT, p&p inclusive.

SPECIAL OFFER
10 PCS of EACH (890 RESISTORS)
£23.00

ORION SCIENTIFIC PRODUCTS LTD.

16 Orange Street
London WC2

WW - 068 FOR FURTHER DETAILS

RADFORD

Audio Measuring Instruments, Audio Amplifiers, Loudspeakers and Loudspeaker Components for the professional and enthusiast

RADFORD AUDIO LTD.

10 BEACH ROAD
WESTON-S-MARE, AVON BS23 2AU

TEL. 0934 416033

WW - 035 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Tuesday, April 5th, for May issue, subject to space available.

DISPLAYED APPOINTMENTS VACANT: £15.50 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £3 per line, minimum £20 (prepayable).
BOX NUMBERS: £3 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS).
PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to BUSINESS PRESS INTERNATIONAL LTD. and crossed.



ECM

ALWAYS AHEAD WITH THE BEST!

£5,000-£18,000

- ★ Experienced in: Mini/Microprocessor Hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ Where does your interest lie: Image Processing; Automation; Datacomms; Radar; Nav-Aids; Video; Medical: Telemetry; Simulation; Satcom; Local Area Nets; Computers; Weapons; Communications?
- ★ There are opportunities in: Design; Test; Service; Sales; Systems; Production; Quality and Research for Engineers and Managers.
- ★ First call: MIKE GERNAT or JOHN SANDERS on 076 384 676/7.

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
 148-150 High St. Barkway, Royston, Herts SG8 8EG.

(1926)

"HI-FLIERS" WANTED READY FOR "TAKE-OFF"

Senior Development Engineer to take design of real time microprocessor systems for video picture processing all the way from specification through to de-bugged delivery to client covering hardware (P.C.B. layout and prototype construction included) and software (high level and Assembler). Must be highly qualified with experience of microprocessors, vast memories, and L-S-I techniques, while knowledge of broadcasting video and display techniques would be useful.

Surrey To £12,000

Computer Hardware Engineers to design digital and analogue interfaces for peripherals to mini and micro computers. Must be graduates with at least four years' experience of microcoding signal processing and embedded software, and simulator or trainer knowledge much appreciated.

Central Berks Salary up to £12,000 p.a.

Commissioning and Test Engineers for a wide range of signal processing and digital video standards converters. Must have video and digital test experience and at least O.N.C.

London To £10,000 p.a.

Senior Design Engineers to work on industrial data acquisition monitoring and control systems with associated test equipment with an emphasis on hardware with at least two years' experience of real time microprocessors and knowledge of assembler and high level structured languages. Must have H.N.C. at least and R.C.A. 1802 background would help.

Northants And the salary? GOOD

Charles Airey Associates

Tempo House, 15 Falcon Road, Battersea, London SW11 2PJ (1357)
 Telephone: 01-223 7662 or 228 6294

LEADING INTERNATIONAL SOUND AND LIGHTING SUPPLIERS

Require an assistant to the technical director to plan and install and occasionally service sophisticated sound and lighting installations worldwide.

Candidates should have creative ability, commonsense and at least one year's industrial experience as well as an electronics degree. Extensive travel is involved and we expect the ideal candidate will be aged approximately 25 and single.

Salary £9,000-£10,000 p.a. (negotiable) plus profit sharing scheme. Reply to:

John Leefe
TALIAN HOLDINGS LTD.
 64/66 Glenthams Road, London SW13 9JJ

(2042)



CAPITAL
 APPOINTMENTS LTD

CAPITAL HOUSE
 29-30 WINDMILL STREET
 LONDON W1P 1HG
 TEL: 01-637 5551

THE UK's No. 1 ELECTRONICS AGENCY

Design, Development and Test to £14,000
 Ask for Brian Cornwell

SALES to £15,000 plus car
 Ask for Maurice Wayne

FIELD SERVICE to £12,000 plus car
 Ask for Paul Wallis

We have vacancies in ALL AREAS of the U.K.

Ask for a Free Jobs List

Telephone: 01-637 5551 (3 lines)

SERVICE MANAGER

ELECTRONIC SECURITY PRODUCTS RETAIL STORE

Supervise small production line, purchasing materials establishing regular sources of supply and supervision of staff of four technicians. Applicant required possess strong engineering and practical background in manufacturing procedures, reliability tests, cost estimates, etc.

RF communication and telephone systems experience is essential. Qualified applicants only. Good future. Salary will depend on experience starting with £7,500 as negotiable salary minimum.

Please reply in writing giving details of qualifications and career to date, to Box 2022.

Electronics Engineers Communications

Marconi Space and Defence Systems, Military Communications Division, are rapidly expanding their Portsmouth operations. New buildings are being erected in response to important new contracts. Now additional experienced staff qualified to Degree/HND/HNC level are required to lead or operate within teams in the following areas:

- PV Crypto ● Crypto ● Advanced Systems
- Naval Systems ● Baseband

The precise grades and experience required vary according to the individual project. The following skills, however, are particularly relevant:

- Analogue/digital hardware design
- Software development and preparation
- Software/hardware development and integration
- Design engineers for LSI based project
- Innovative digital design

Our salary scales match the high standards of qualifications, experience and ability demanded. We offer a comprehensive range of benefits together with relocation assistance if required.

Phone Portsmouth 674019 for further information and an application form. Alternatively, you can write to Jack Burnie, Marconi Space and Defence Systems Limited, Browns Lane, The Airport, Portsmouth, Hants., quoting ref: BL 21

(All posts open to men and women)

Marconi
Space & Defence Systems



2018

BRITISH ANTARCTIC SURVEY Radio Officer (Marine)

A vacancy exists for a Radio Officer (Marine) to serve initially aboard the Antarctic Research Vessel RRS John Biscoe. The successful applicant will be required to commence duties on 1 June. Voyages are normally seven months long and the vessel will sail from the United Kingdom on 21st June.

RRS John Biscoe's primary role is to support shipborne marine biology and associated oceanography in the southern ocean. She has a secondary responsibility to resupply Antarctic land stations as well as to support scientific parties in the field.

Candidates should possess valid certificates of proficiency recognised by the Department of Trade and have served the necessary sea time to work a single-handed station.

Salary: In the scale £7,773, £8,291, £8,398, £8,640 . . . to £10,917 per annum. In addition an allowance of £1,200 is payable for periods of service spent south of Montevideo.

For further details and an application form please write stating full qualifications and experience to:

The Establishment Officer, British Antarctic Survey, High Cross, Madingley Road, Cambridge CB3 0ET.

Please quote Ref: BAS 75

Closing date: 30 March, 1983

NATURAL ENVIRONMENT RESEARCH COUNCIL

(2035)

Channel 4 Engineering

VIDEOTAPE EDITOR - Ref EG/7

A Videotape Editor who is experienced in the operation of time code editing systems is required to work in our editing suite. Applicants must be able to demonstrate a detailed working knowledge of broadcast videotape editing.

JUNIOR TECHNICIAN - Ref EG/8

An opportunity exists for an individual who has an electronic/operational background, to make a start in the television engineering department of Channel 4. Applicants should either possess a qualification in electronics or mechanical engineering, or experience in a broadcasting engineering department

Write enclosing a full C.V. and quoting the relevant reference number to The Personnel Department, Channel 4 Television, 60 Charlotte Street, London W1P 2AX by 25th March 1983.

Channel 4 is an equal opportunity employer; applications are welcome from candidates regardless of marital status, race, nationality, ethnic or national origins, or sex, and from registered disabled persons.



CHANNEL FOUR TELEVISION

2030

LOUGHBOROUGH UNIVERSITY OF TECHNOLOGY

WORKSHOP TECHNICIAN

Applications are invited for this new post in the Department of Computer Studies. The successful candidate should have HNC, HND, or equivalent and 5-10 years' experience in the field of microprocessors, electronics or digital systems in the first instance.

Salary on Grade 6 scale £6532-£7802 (under review). The appointment is for three years.

Requests for further particulars and application forms to Dr C. H. Machin, Department of Computer Studies, University of Technology, LOUGHBOROUGH Leics LE11 3TU.

(2025)

Book Editor



The Radio Society of Great Britain requires a second book editor to work on new and existing publications in its expanding range.

Applicants should have at least two years' relevant book or magazine experience and a knowledge of radio and electronics. They should be able to assume responsibilities for all aspects of book production from manuscript to bound copies, while working under minimum supervision.

The position is a good opportunity to take up a creative and responsible role in a small but highly successful publisher. It offers a competitive salary and excellent working conditions.

2038

Please write with full CV to David Evans, General Manager, Radio Society of Great Britain, Alma House, Cranborne Road, Potters Bar, Herts EN6 3JW, marking your envelope "Confidential".

Appointments

CAREER OPPORTUNITY WITH TOP BRITISH MICRO MANUFACTURER

ELECTRONICS TECHNICIAN PRODUCTION ENGINEERING

£5.8K-8.7K

DEPENDING ON AGE AND EXPERIENCE, OXFORD BASED

Research Machines is an expanding UK manufacturer of microcomputer systems for scientific, engineering and educational applications. We are looking for an experienced electronics technician to support the Production Engineering team.

We are offering the opportunity of varied and satisfying work on technically advanced equipment. Applicants should be capable of prototype construction, carrying out validation work/writing reports on engineering changes and testing new peripherals and components.

You should be educated to HNC or degree level in electronics and have at least one year's experience in digital electronics and computer hardware/software.

We offer a particularly attractive range of benefits, including good salary; 25 days paid holiday; free BUPA, life and disability insurance; pension scheme and help with relocation expenses.

If you are interested in this post, please contact Mary Oakey on Oxford (0865) 728224 and ask for an application form, quoting T/WW.

RESEARCH MACHINES MICROCOMPUTER SYSTEMS

RESEARCH MACHINES LTD Mill Street, Oxford OX2 0BW, Tel: (0865) 728224

2036

Electronic Engineers - What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £5000-£15000.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you. All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

TJB ELECTROTECHNICAL
PERSONNEL SERVICES,

12 Mount Ephraim,
Tunbridge Wells,
Kent. TN4 8AS.

Tel: 0892 39388



Please send me a TJB Appointments Registration form.

Name

Address

(861)

CHIEF MAINTENANCE ENGINEER

required for factory manufacturing musicassettes and computer software. Some experience of Audio Techniques as well as Electronics to HNC standard or equivalent would be essential.

This responsible position would be ideal for someone with an interest in the maintenance of machinery from computers to packaging machines.

Please write with full career details to:

**Malcolm Shepherd
BiBi Magnetics Ltd
101/105 Plough Road
London SW11 2BJ**

(2029)

ELECTRONICS TECHNICIAN

The post involves the routine maintenance of an Elscint whole-body CAT Scanner as well as other associated electromedical equipment. Applicants should have wide experience in analogue and digital servicing together with a working knowledge of microprocessor programming techniques.

The post is graded as Medical Physics Technician II or III depending on experience and qualifications. (Entry to Technician II grade is open to applicants who have served at least two years as a Technician III).

Salary scales from 1st April, 1983:
MPT II £7,386-£9,212 p.a. + £997 p.a. London Weighting; MPT III £6,132-£7,926 p.a. + £997 p.a. London Weighting.

Please apply for an application form without delay to: The Secretary, Department of Clinical Measurement, Westminster Hospital, 65 Romney Street, London SW1 or 'phone 01-828 9811 Ext. 2640.

(2041)

BOX NOs.

Box number replies should be addressed to:

Box No.....

c/o Wireless World

Quadrant House

The Quadrant

Sutton, Surrey SM2 5AS

BORED ?

Then change your job!

1) Test Equipment Controller
Plan and procure test equipment and control a team of test equipment engineers. To £12,670 - Hants.

2) Maintenance Engineer
Start an in-house test of communications equipment - then move to field service when fully conversant. To £8,000 + car - London.

3) Service Engineer
Analogue and digital detection and alarm systems. Middx-Essex - to £8,000.

4) Test Engineer
In-house work on modems and data communications systems. To £7,500 - Bucks.

5) Service Personnel
(RAF, RN, Army)

We have many clients interested in employing ex-service fitters and technicians at sites throughout the UK. Phone for details.

6) £500 per week

We are paying very high rates for contract design and test engineers who have a background in RF, MICROWAVE, DIGITAL, ANALOGUE or SOFTWARE, at sites throughout the UK.

Hundreds of other Electronic and Computer Vacancies to £12,500

Phone or write:

Roger Howard, C.Eng., M.I.E.E., M.I.E.R.E.

CLIVEDEN CONSULTANTS

87 St. Leonard's Road, Windsor, Berks.
Windsor (07535) 58022 (5 lines)

(1646)

CLIVEDEN

UNIVERSITY COLLEGE CARDIFF
DEPARTMENT OF PHYSIOLOGY

**ASSISTANT EXPERIMENTAL
OFFICER (ELECTRONIC
INSTRUMENTATION)**

The department, which has an active neuroscience-based research programme, requires a person with design experience to work in collaboration with the academic staff in the development and maintenance of equipment for research laboratories. Degree in electronics an advantage. This post offers a challenging opportunity for those interested in developing the latest electronic technology in a biomedical environment.

Salary range: OR IB £5,550-£9,370 p.a. Duties to commence as soon as possible.

Applications (2 copies), together with the names and addresses of two referees, should be forwarded to the Vice-Principal (Administration) and Registrar, University College, PO Box 78, Cardiff CF1 1XL, from whom further particulars may be obtained. Closing date 15th April, 1983. Ref: 2532.

(2021)

ELECTRONICS ENGINEERS FOR BROADCAST TELEVISION

Ampex Corporation is the leading world manufacturer of professional video/audio recording equipment and a wide range of associated broadcast products, including computer controlled editing systems, cameras, digital effects and vision switchers.

We are looking for:

SYSTEMS PROJECT ENGINEERS

To join our innovative project team involved in the design, installation and commissioning of TELEVISION STUDIO AND OUTSIDE BROADCAST VEHICLE PROJECTS.

The Broadcast Systems Group based in Reading supplies complete studio and mobile systems to broadcast installations worldwide.

The appointments involve occasional overseas travel for on-site commissioning.

Key requirements are:

- ★ Thorough knowledge of video and audio principles - HNC/Degree Electronics preferred
- ★ Experience in broadcast television industry
- ★ Previous knowledge of TV Systems would be an advantage

FIELD SERVICE ENGINEERS

(based in UK or Italy)

Electronics engineers to work on the installation and maintenance of television studio equipment at customer sites throughout Europe, Africa and the Middle East.

Key requirements are:

- ★ Thorough knowledge of electronic engineering - HNC/Degree Electronics preferred
- ★ 3 years' experience in a television studio/production environment with specific experience of either videotape or studio equipment, e.g. cameras, switchers, etc.
- ★ Availability to travel throughout Europe, Africa and the Middle East, together with ability to work on own initiative while away from base.

Attractive salaries and other benefits, including pension, life assurance and permanent health scheme, BUPA option, product training, overseas allowances and relocation expenses as appropriate.

AMPEX

Please phone or write
Maureen Brake
Ampex Great Britain Limited
Acre Road, Reading RG2 0QR
Berkshire, England
Tel: Reading (0734) 875200

(2028)

ELECTRONIC DESIGN ENGINEERS

We are a small highly successful manufacturing company specialising in RF communications, digital and low frequency analogue equipment.

We require young highly motivated engineers wishing to develop their experience. The ideal candidate must have complete confidence in his ability.

- Starting salary £10K + (neg).
- 37½-hour week. Overtime available.
- Pay reviews every 6 months.
- Pleasant working environment.
- Location near City of London.

Contact Keith Penny on (01) 250 0894

(1983)

SCOTTISH OFFICE
DIRECTORATE OF TELECOMMUNICATIONS

WIRELESS TECHNICIAN

(£5,972-£8,058)

Applications are invited for two posts of Wireless Technician in the Central Services Department of the Scottish Office. The posts are based in East Kilbride and Edinburgh.

Candidates must have a sound theoretical and practical knowledge of Radio Engineering and Radio Communications equipment both fixed and mobile, in the frequency range HF to 2 GHz. They must also be able to use test equipment and simple machine tools. A sound basic knowledge of digital techniques would be an advantage. They should have a minimum of 3 years' appropriate experience and should hold an Ordinary National Certificate in Electronic or Electrical Engineering or a City and Guilds of London Institute Certificate in an appropriate subject or a qualification of higher or equivalent standard. Some assistance may be given with relocation expenses.

A valid UK driving licence is essential.

Application forms and further information are obtainable from Scottish Office Personnel Division, Room 110, 16 Waterloo Place, Edinburgh EH1 3DN (quote ref PM(PTS)2/1/83 (031 556 8400 Ext 4317 or 5028)).

Closing date for receipt of completed application forms is 11 April, 1983.

(2039)

Appointments



Senior Engineer - Vision Control

We are looking for a Senior Engineer to lead the Vision Control section at The Television Centre, Mold, which is part of the impressive Theatre Clwyd complex, where we are currently completing the installation of a second studio.

Experience in broadcast television is an essential requirement, and familiarity with Link 110 and 120 cameras would be a distinct advantage.

Salary, including supplements, is £11,884 per annum, and assistance towards the cost of relocating to this very attractive part of Wales may be available.

Suitably qualified candidates should write for an application form, enclosing a self-addressed envelope and quoting reference WW/146 to The Personnel Manager, HTV Limited, The Television Centre, Cardiff CF1 9XL.

WE ARE AN EQUAL OPPORTUNITIES EMPLOYER.

2032

POLYTECHNIC OF CENTRAL LONDON School of Engineering & Science ELECTRONICS TECHNICIAN GRADE 5

Technician required to join a group working in communication and computer fields. Familiarity with computer/hardware/software, logic and digital techniques is desirable. Experience in workshop practice (electrical and mechanical) is essential.

Qualification: ONC or equivalent and/or appropriate industrial experience. Salary on scale £7,229-£8,237 inclusive of London Allowance.

Application form and further details from the Establishment Office, PCL, 309 Regent Street, London W1R 8AL. Tel. 01-580 2020 ext. 212. Closing date: 14 DAYS FROM APPEARANCE OF LAST ADVERTISEMENT. (2037)

LOGEX ELECTRONICS RECRUITMENT

Specialists in Field & Customer Engineering appointments, all locations and disciplines.

Logex House, Burleigh, Stroud
Gloucestershire GL5 2PW

0453 883264 & 01-290 0267
(24 hours)

R & D OPPORTUNITIES. Senior level vacancies for Communications Hardware and Software Engineers, based in West Sussex. Competitive salaries offered. Please ring David Bird at Rediffusion Radio Systems on 01-874 7281. (1162)

Network Supervisor

Channel 4 Television requires a Network Supervisor at their transmission centre in Charlotte Street. The successful applicant should be fully conversant with all aspects of television technical operations, and will have occupied a position of responsibility within a broadcast television environment.

He/she is the senior technical operations staff member on shift who will deputise for management in their absence. Excellent salary and promotion prospects.

Please write giving details of past experience, age and salary to The Personnel Department, (Ref EG/6), Channel 4 Television, 60 Charlotte Street, London W1P 2AX by 25th March 1983.

Channel 4 is an equal opportunity employer; applications are welcome from candidates regardless of marital status, race, nationality, ethnic or national origins, or sex, and from registered disabled persons.



2031

CHANNEL FOUR TELEVISION

BRITISH ANTARCTIC SURVEY Radio Technician/ Operators

Radio Technician/Operators who have experience in maintenance and operation of HF and satellite communications are required to work single-handed at stations in the Antarctic.

Because of the isolated situation of Antarctica the ability to work on their own initiative is absolutely essential. Applicants should appreciate that they will be solely responsible for all aspects of communications. Ability to operate to MRGC standard with some knowledge of maritime procedures is also necessary. Appropriate training on specific equipment will be given if required.

The period of employment will be from 4 July, 1983, until Spring 1986 which entails working in Antarctica for two consecutive winters.

Applications are invited from single men (to work mainly overseas) who are physically fit and aged between 22 and 35. Salary: from £5,709 per annum, plus annual increments. Also Antarctic allowance of £586 per annum. Accommodation provided whilst overseas. Clothing, messing and canteen are provided free on bases and free messing on voyage.

For details and an application form please write to:

The Establishment Officer
British Antarctic Survey
High Cross, Madingley Road, Cambridge CB3 0ET
Please quote ref BAS 74

Closing date 13th April, 1983

NATURAL ENVIRONMENT RESEARCH COUNCIL

(2040)

NORWEB-MID LANCASHIRE AREA THIRD ENGINEER (TELECOMMUNICATIONS) AREA ENGINEERING DEPARTMENT

There is a vacancy for a Third Engineer (Telecommunications) in the Area Engineering Department, Hartington Road, Preston.

Applicants should hold an appropriate degree, HNC, or full Technological Certificate, and should have had basic experience which will allow the person appointed to make a significant contribution to the installation, commissioning and future maintenance of a comprehensive microprocessor-based telecontrolled system. Experience will be gained in the wide variety of telecommunications equipment presently in use in the ESI.

Salary, £7,044-£10,675 p.a. plus £292 p.a. responsibility payment.

Applications obtainable from: The Manager, Mid-Lancashire Area, Norweb, Hartington Road, Preston, Lancashire PR1 8LE by 8th April, 1983.

(2033)

GOODHEAD PUBLICATIONS LIMITED

require an
EDITOR

for its monthly magazine, Amateur Radio

An experienced radio amateur is preferred, although not absolutely essential. Editorial experience a definite asset. Freelance Editor would be considered.

Write, with a brief cv to the Executive Editor, Chris Drake, Goodhead Publications Limited, 27 Murdock Road, Bicester, Oxon OX6 7RG. Telephone: Bicester (08692) 44517.

(2019)

CUT THIS OUT!

Clip this advert and you can stop hunting for your next appointment. We have a wide selection of the best appointments in Digital, Analogue, RF, Microwave, Microprocessor, Computer, Data Comms and Medical Electronics and we're here to serve *your* interests.

Call us now for posts in Design, Sales, Applications or Field Service, at all levels from £6,000-£16,000.



Engineering & Technical Recruitment

11 Westbourne Grove, London W2. Tel. 01-229 9239.

1935

PSION 
**ELECTRONICS
TECHNICIAN
ENGINEER**

Psion is a substantial and rapidly growing microcomputer applications house.

We require an electronics technician/engineer to support design staff in the following areas:

- Construction of prototype equipment, both electronic circuits and enclosures.
- Maintenance of in-house equipment.
- Control of workshop and component stock.

The successful applicant will have at least 5 years' experience in an electronics design environment. Salary range £7,000-£11,000 per annum depending on skill, experience and ability to work with a minimum of supervision.

**PSION LTD., 2 Huntsworth Mews,
Gloucester Place, London NW1.
Telephone: 01-723 6919 or 01-723 9408**

(2043)

**County Surveyor's
M1 Strengthening phase 1, 1983/4**

Provision of a site Radio Telephone System

Applications are invited from companies wishing to be considered for the supply and maintenance of a site radio telephone system, on the basis of a short term hire contract. The equipment is to be used for a period of approximately 16 weeks on the above mentioned contract on the M1 in Bedfordshire.

Companies wishing to be considered should apply to:
**The County Surveyor, County Hall, Cauldwell Street,
Bedford MK42 9AP. Tel: Bedford 63222 extension 34**



(2034)

**SENIOR VT
ENGINEER**

A vacancy exists at our Glasgow studios for an experienced VT Engineer.

Experience in the operation and maintenance of VT equipment is essential and preference will be given to those familiar with the operation of Ampex equipment, eg., AVR2, RES, ACR25, VPR2B, etc.

Academic qualifications to at least HNC (electronics) or equivalent will be expected. The salary is £11,673 per annum and is reviewed annually. In addition, service increments increase the salary by 10% in three stages over seven years.

The company operates an excellent contributory pension scheme with free life assurance and attractive staff conditions of employment.

Interviews will be held in Glasgow and travelling expenses reimbursed at interview. Generous relocation expenses will be available to the successful candidates where necessary.

Those with the necessary qualifications should write or telephone for an application form to the **Recruitment and Training Officer**.

2026



**Scottish Television,
Cowcaddens,
Glasgow G2 3PR.**

**Electronics Research
at the University of Essex**

Graduates who have (or final year students who expect to obtain) a first or upper second class honours degree are invited to apply for research leading to a higher degree (M.Sc., M.Phil. or Ph.D.) in the following areas:

Acoustic Noise and Vibration Cancellation (adaptive microprocessor-controlled systems); **Audio Engineering** (high-precision digital signal processing, system transparency, stereo); **Circuit Design Studies** (circuit theory, fault diagnosis, sensitivity effects, CAD, filter realisations); **Digital Transmission for Telecommunications** (filters, line codes); **Interactive Systems** (handwriting analysis, computer graphics, personal databases); **Microcomputer Systems** (embedded microcomputer applications, micro-programming, architectures); **Microwave and Millimetre Wave Propagation** (scattering from precipitation particles, space frame radomes); **Optical Communications** (detectors, noise processes, signal design, switching); **Picture Coding and Processing** (data reduction, adaptive filtering, motion estimation, feature extraction); **Satellite Communications Systems** (business systems, protocols, data and video services, inter-modulation studies); **Telecommunication Switching Systems and Software** (computer control, software production, telex and viewdata). **Visual Displays and Television Engineering** (computer graphic input systems, stereo, colour, and high-precision displays).

Further information and application form available from: Dr J. K. Fidler, Chairman, Department of Electrical Engineering Science (ref Jan/2), University of Essex, Wivenhoe Park, Colchester CO4 3SQ.

(2027)

ARTICLES FOR SALE

Advance AM/FM Signal Generator SG63E needed to complement existing laboratory facilities. Details to B. McBryan, Electronic Engineering U.C.D., Upper Merion Street, Dublin 2, Eire.

(2016)

Word Processor Clearance Sale. BDP/Quem Daisy-wheel printer, 2 discs; £595. Adler SE2000-Golfball printer, single disc; £450. Kalle Infotec 7000-Golfball printer Single tape; £350. All + VAT. Autotype, Hayward's Heath (0444) 414484 and 454377.

(2017)

BRIDGES, waveform/transistor analysers. Calibrators, Standards, Millivoltmeters, Dynamometers, KW meters, Oscilloscopes, Recorders, Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel 040 376236. 162

TV TUBE Rebuilding Plant. Due to frustrated export order many items of latest plant and equipment available at half price. Western-Wybrew Engineering, The Square, Marazion, Cornwall. Telephone (0736) 710456. (1986)



TEST SUCCESS!

ENGINEERS & TECHNICIANS

£ Excellent

Greenford, Middx.

Are you a successful test technician? If so, our client – a most successful company – can offer you the opportunity to work with sophisticated communication and signal processing equipment in a fast expanding environment which means improved earnings; excellent job security and plenty of scope for personal advancement.

For immediate action call John Sanders on **076 384676/7**.

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
148-150 High St., Barkway, Royston, Herts SG8 8EG

(2047)

Shortlisted without even applying

That's how it is when you register with Beechwood. Complete our application form, then just sit back and let the opportunities come to you – and they will. Our experience is wide – so are our contacts. This is just a selection from our range of vacancies.

DESIGN ENGINEERS – HERTS – To £14,000. Qualified to degree level with a solid background in RF or Microwave or automatic test equipment design.

PRODUCT SUPPORT ENGINEERS – SUSSEX based + travel U.K. and Overseas – Attractive salaries + overtime and site allowances. A number of vacancies exist for Engineers to design and install modifications to various military simulators which are in service on customers' premises. The modifications can vary from large scale refits to minor Software/Hardware changes. The technology varies between analogue and digital micro-based systems.

ELECTRONICS ENGINEERS – BERKS. Salaries in the £7,000-to-£14,500 range. Engineers qualified to at least HNC/Degree level are required by a company in the forefront of technology for defence applications. Experience required in the area of digital messaging systems, analogue, power supply units, weapon control systems, hardware design, military ATE, RF/communication systems.

DIGITAL DESIGN ENGINEERS – SOUTHERN COASTAL AREA IN ENGLAND – Salaries in the £7,500 to £15,000 range depending on experience. A leading company supplying equipment to the defence and civil industry in the U.K. and abroad is looking for well-qualified digital engineers with experience in high speed Signal Processing, FFT techniques and Special Purpose ATE.

AVIONICS ENGINEERS – HANTS – Salaries negotiable from £7,000 to £14,000 depending on experience. Graduates with at least two years' experience in Avionics/Systems/Radar design and development are required for a major U.K. company in the forefront of technology.

(2044)

ELECTRONICS AND SOFTWARE ENGINEERS – To £17,000 – For companies based in various locations in LONDON & HOME COUNTIES / WEST COUNTRY / DORSET / WALES / N.W. / EAST ANGLIA / SCOTLAND. HNC/Degree level Engineers with experience in analogue / digital / microprocessors / avionics / satellites / communications / RF / microwave / computers / process control / instrumentation control eng/ATE.

R.F. DESIGN ENGINEERS – HEREFORDSHIRE – Salaries in the £8,000 to £10,000 range + relocation assistance. Here are opportunities for degree level Engineers in the 25-35 age group to work for a small lively company working at the forefront of R.F. technology. Situated in the beautiful Herefordshire countryside, you will be surprised at the lower cost of housing.

SYSTEMS ENGINEERS – BRISTOL – Salaries attractive + relocation. A major company involved in high technology space projects are looking for experienced graduate level Engineers with experience in control theory, solar array, configuration, EW systems, communications systems, guidance systems and spacecraft systems.

PROCESS ENGINEERS / SCIENTISTS / PROJECT LEADERS – LONDON / HOME COUNTIES / SCOTLAND AREAS. Up to £15,000 or beyond. Graduates/PhDs with experience in semiconductors or devices.

SYSTEMS ENGINEERS – DORSET AREA – Salaries from £6,500 to £8,500 depending on experience. Graduate Engineers under 28 years of age with one to four years' experience in the design and development of complex digital communication systems, specification and control of hardware/software development activities, and proving that the system as developed meets requirements of the customer.




For an application form, please send your coupon to George A. Low, Beechwood Appointments Register, FREEPOST, London W3 9BR (no stamp required). Telephone 01-992 8647 (24 hours).

----- ✂ -----
Name _____
Address _____
WW 4/83

Beechwood

APPOINTMENTS REGISTER

ARTICLES FOR SALE

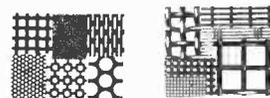

Perforated Metals – Screens, Plastics, Wire Meshes, Sifting Media, Cable Tray, Gratings, direct from Manufacturer's Stock. We can cut to size.

We specialise in one-offs or large quantities.

GRAEPEL PERFORATORS LTD

Unit 1-B, CHARLES STREET Dept WS, WALSALL, STAFFS WS2 9LZ
Tel. 0922 611644/611414. Telex 335291

SULLIVAN Thermistor Bridge £59. Heterodyne Bridge Detector £39. EMI Disc Recording blanks 100 – £150. Laboratory oven £49. Lab-gear TV Pattern Generator £45. Small compressor pump £20. 500lbs/sq.in. receiver £25. Watson lab microscope £89. Centrifuge £49. Brinell Hardness Tester £98. Ultrasonic Leak Detector £59. 4KW Diesel Generator £195. Water pumps £12-£98. Sullivan Mirror Galvanometer £39. Audio Analyser £65. 220MHz Sweep Generator £79. EMI Audio Sweep Generator £65. Record Clip-on Ammeter/voltmeter/Recorder £79. Marconi TF 1225A Noise Receiver £59. Plug-ins Cossor 1078 £15 ea. Pye 200,000 M/ohm meter, EIL twenty-million M/ohm meter £35 ea. A few oscilloscopes and other RF, AF, sweep generators

040-376236 (2000)

PCB/ELECTRONIC ASSEMBLY

to sample or drawing. Short or continuous runs. Any quantity. 100% inspected. Special rates for small companies or large quantities. Fast turnaround and local deliveries if required.

AUTRONICS, 23 Regency Gardens Yardley Wood, Birmingham B14 4JS
021-474 4638 (2020)

SITUATIONS VACANT

Production Engineering

DOLBY LABORATORIES, the world famous audio noise reduction company, was founded by an engineer. We are a company that believes in engineers and engineering. Small enough for you to make a contribution, we have a track record of innovation and quality.

Production Engineer £9,000+

The person appointed will join a small team which provides technical support to the production department. Responsibilities include assembly and test procedures, and interfacing with sales and design engineers on product improvements and new product introductions. The successful applicant will ideally be a graduate electro-mechanical engineer experienced in electronic assembly. He/she may also have particular knowledge of ATE.

Production Technician c £7,000

To support the production engineers by building jigs, debugging prototypes, running maintenance schedules and coping with day-to-day equipment failures. Qualifications: HND or equivalent and some practical experience of an electronic nature.

Write or telephone PHIL MARSHALL,
Dolby Laboratories Inc.
346 Clapham Road,
London SW9.
01-720 1111

(2045)



Royal Marsden Hospital
Downs Road, Sutton, Surrey

Medical Physics Technician Grade IV

required to work as part of a technical group in the busy Radiotherapy Department of this postgraduate teaching hospital.

The successful candidate will be involved mainly in the work of the new T.B.I. Unit. Applicants should possess ONC, HNC, HND or similar qualification in electrical engineering or electronics. This post is for a fixed-term period of one year only.

Salary scale from 1st April 1983 £5767-£7394 per annum.

Candidates wishing to discuss the post further should contact Mr. Edser, Radiotherapy Department, Tel: 01-642 6011 Ext. 280. Application form and job description available from the Personnel Department, Royal Marsden Hospital, Fulham Road, London SW3. Tel: 01-352 8171 Ext. 446/447.

(2046)

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC. LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.

ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE

TELEPHONE: 445 0749/445 2713

BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, North Finchley, London, N.12

(5 minutes from Tally Ho Corner)

(1613)

QUARTZ CRYSTALS IN 24 HOURS ANY FREQUENCY 2-50 MHz FOR £4 inc

New fast service for C.W.O. only (state holder style).
Clock oscillators for microprocessors in stock from £9.30.

McKnight Crystal Co Ltd, Hardley Industrial Estate
Mylbys, Southampton SO4 6ZY Tel. 0703 848961

(2008)

POWER V MOS-FET TECHNOLOGY

We specialise in all aspects of this important subject. A comprehensive service is offered to individual or OEM users, including:

- ★ Hitachi Supertex and RCA V MOS-FET from stock.
 - ★ V MOS-FET power modules from stock.
 - ★ Competitive prices (120 watt modules £15.45, 1 off).
 - ★ Printed circuits and kits.
 - ★ Data books and application notes.
 - ★ Design, evaluation and advice service.
 - ★ Catalogue/sample data sent free (50p stamp appreciated towards post and packing).
- Phone 02514 22303 and ask Richard Walsh about your application requirement or write:

AUDIO TECHNOLOGY
Freeport, Church Crookham
Aldershot, Hants. GU13 0BR

THE SCIENTIFIC WIRE COMPANY

P.O. Box 30, London, E.4
ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	.80	.60
30 to 34	3.20	1.80	.90	.70
35 to 40	3.40	2.00	1.10	.80
41 to 43	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.38	2.36	1.34	.90
----------	------	------	------	-----

Prices include P&P, VAT and Wire Data. SAE for list. Dealer enquiries welcome.
Reg Office: 22 Coningsby Gardens

(9673)

BILLINGTON VALVES

Electronic valve specialists (also bulk supplies of transistors) SAE/IRC for quotation on your requirements. We offer an unrivalled service supplying rare/obsolete valves. Send 25p and L.S.A.E. for our valve listing (includes money off voucher) 23 Irwin Drive, Horsham RH12 1NL. No callers.

ENCAPSULATING EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regunning metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

LAMPS AND CABLE. Large amount of lamps and cable for sale - all types and sizes, domestic and industrial. Telephone MIRAGE LIGHTING on HITCHIN (0462) 733388 between 10am-7pm. (1899)

DON'T MISS OUR VALVE LIST!

Send 25p and L.S.A.E. Today; Billington Valves, 23 Irwin Drive, Horsham RH12 1NL. 10 and S.A.E. for component clearance list. (No callers).

VALVES, PROJECTOR Lamps, 6000 types, list £75, world wide export. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Phone (024 366) 2023. (1991)

RACAL COMMUNICATIONS RECEIVERS

500 Kc/s - 30Mc/s 1MHz wide. RA17L - £175. RA117E - £225. A few sets available as new at £75 extra. All receivers are air tested and calibrated in our workshop, supplied with full manual, dust cover, in fair used condition. New black metal louvered cases for above sets £25 each. RA980 - ISB - SSB - £75. RA218 - SSB - ISB and fine tune for RA117 - £50. TRANSMITTER DRIVE UNIT RA79. 1.5mc/s - 30mc/s - SSB - ISB - £50. FSM - CW - £150. AERIAL TUNING UNIT and protection unit MA187B - £25 to £50. DECADE FREQUENCY GENERATOR MA350B. Solid state synthesiser for MA79 or RA117 - RA217 - RA1217 - £150 to £200. MA250 - 1.6mc/s to 31.6mc/s - £150 (New). MA259G - precision frequency standard - 5mc/s lmc/s 100khz - £100 to £250. RACAL MA152 - Standing wave ratio indicator. FX2mc/s - 25mc/s Power up to 1000watts - 50 ohms - Auto trip switch - Transistor mains 100 - 250AC, new and boxed - £40. RACAL COUNTER 836 (9036) 32mc/s TTL circuit design - tested with manual - £50 to £75. OSCILLOSCOPES COSOR C0U150 - 35mc/s - Twin Beam - Solid State - £175 with manual. TEXTRONIC OSCILLOSCOPE 647 and 647A Solid State - 50mc/s and 100mc/s bandwidth - £280 and £350. Tested, circuit and instructions. RACAL COUNTER 801 M-125 Mc-S £50.

IMAGE INTENSIFIERS - Mullard - G.E.C. or E.E. Type XX 1060 very high gain self-focusing image intensifier assembly for night vision systems. Minimum luminance gain 35,000. Supplied as received from Government supplies in original box (used) with data sheets - £12 ea. (P&P+VAT=£5.25).

All items are bought direct from H.M. Government, being surplus equipment. Price is ex works SAE for all enquiries. Phone for appointment for demonstration of any item. John's Radio, Whitehall Works, 84 Whitehall Road, East, Birkenshaw, Bradford B011 2ER. Tel. (0274) 684007. V.A.T. and Carriage extra. (848)

INVERTERS

High-quality DC-AC; also "no break" (2ms) static switch, 19ln. rack. Auto Charger.



COMPUTER POWER SYSTEMS

Interport Mains-Store Ltd.
POB 51, London, W11 3BZ

Tel: 01-727 7042 or 0225 310916

(9101)

WIRELESS WORLD 1968-81. (Few missing). Excellent condition. £40 carriage. 15 copies 1930's, 40's including 2 RF straight set, Williamson Amplifier, Golden Jubilee issue. £10. Phone Bristol (0272) 733 837. (1982)

PCBS & PANEL LABELS to your requirements. Design - Prototypes - Production. G. N. Slee Custom Products, 78 Derry Grove, Thurnscoe, Rotherham, Yorks SG3 0TP. Telephone (0709) 89525. (1892)

ARTICLES FOR SALE

LINSLEY HOOD DESIGNS

75-100w AMPLIFIERS
AUDIO SIG. GENERATORS
DISTORTION ANALYSERS
SAE for leaflets

TELERADIO ELECTRONICS
325 Fore St., Edmonton N9 OPE
TEL: 807 3719 (1762)

RIBBON CABLE, PLUGS AND CONNECTORS

The very best quality. Proven manufacturer. Plugs and connectors sold singly or in quantities. Cable sold by the metre or by the roll.
Ring or write:
T.A.D. SUPPLIES
5-10 Eastman Road
London W3
Tel: 740 0058 (1840)

SITUATIONS VACANT

FIELD SERVICE ENGINEERS

(Based in Italy)

Exciting opportunities for qualified Electronics Engineers to work on the installation and maintenance of Television Studio Equipment at customer sites throughout Italy and Africa.

Key requirements are:

- ★ A sound knowledge of Electronic Engineering – Degree/HNC or equivalent
- ★ At least 3 years' experience in a Television Studio/Production environment, with specific experience of both Quad and Helical Scan, VTR, TV Camera and Switcher Engineering
- ★ Availability to travel extensively throughout Italy and Africa and ability to work on own initiative while away from base

Attractive salary package and other benefits to include overseas allowances and relocation expenses.

AMPEX Please write or 'phone
Maureen Brake at:
Ampex Great Britain Limited
Acre Road, Reading RG2 0QR
Berkshire, England
Tel: Reading (0734) 875200

(1995)

SERVICES

CIRCOLEC

THE COMPLETE ELECTRONIC SERVICE

Artwork, Circuit Design, PCB Assembly, Test & Repair Service, Q.A. Consultancy, Prototypes, Final Assembly.

Quality workmanship by professionals at economic prices.
Please telephone 01-767 1233 for advice or further details.

1 FRANCISCAN ROAD
TOOTING, LONDON SW17

(1391)

Williams

P.C.B. Artworks

FAST TURNROUND

To ensure immediate turnaround of your artwork contact JULIAN WILLIAMS
WILLIAMS ARTWORK, GRAYS LANE
MORETON-IN-MARSH, GLOS.
Tel: MORETON-IN-MARSH 51444
(or Evesham 840121)

PCB

LAYOUT DESIGN
QUALITY ARTWORK

FAST DELIVERY - REASONABLE RATES -
PHONE FREES ARTWORK SERVICE
01-607-3169

DESIGN SERVICES. Electronic design development and production service available for digital and analogue instruments. RF Transmitters and receivers, telemetry and control systems. 20 years' experience. R.C.S. Electronics, Wolvey Road, Ashford, Middlesex. Phone Mr Falkner 53661. (834)

TURN YOUR SURPLUS Capacitors, transistors, etc, into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. (9509)

SMALL BATCH PCBs produced from your artwork. Also DIALS, PANELS, LABELS. Camera work undertaken. **FAST TURNAROUND.** Details: Winston Promotions, 9 Hatton Place, London EC1N 8RU. Tel. 01-405 4123/0960. (9794)

FOR THE BEST PCB SERVICE AVAILABLE

★ Circuit Design & Development
Digital and Analogue

★ Artwork Layout
Work of the highest standard by experienced draughtsmen. No minimum charge.

★ Board Manufacture
Prototype to semi-production, excellent rates. 24-hour prototype service from filmwork

★ Wiring & Assembly
PCB assembly, wiring and cable forming by qualified staff.

★ Test
Full test facilities available.

One or all services available, no order too small. Please telephone Chelmsford (0245) 357935, or write to HCR Electronics, The Industrial Unit, Parker Road, Chelmsford. (1169)



PRINTED CIRCUIT BOARDS

Manufacturers from A/W or film, small or large quantities, average turnaround two weeks.

MAYLAND PCB CO. LTD.
Maylandsea
Chelmsford, Essex CM3 6AB
Tel. (0621) 741560 (2051)

DESIGN AND DEVELOPMENT. ANALOGUE, DIGITAL, RF AND MICROWAVE CIRCUIT AND SYSTEM DESIGN. Also PCB design, mechanical design and prototype/small batch production. — **Adenmore Limited**, 27 Longshot Estate, Bracknell, Berks. Tel: Bracknell (0344) 52023. (656)

ARTICLES FOR SALE

1983 RADIO AMATEURS HANDBOOK

by ARRL Price: £10

WORLD RADIO TV HANDBOOK 1983 £12.00

ROBOTS AND ROBOTOLGY by Warring, R.H. Price: £7.95

INTERNATIONAL DIGITAL I/L SELECTOR by Towers, T. D. Price: £11.00

PRACTICAL DESIGN OF DIGITAL CIRCUITS by Kampel, I. Price: £10.95

DIGITAL ELECTRONICS CIRCUITS and systems by Morris, N. Price: £5.50

THE ART OF ELECTRONICS by Horowitz, P. Price: £15.95

MICROPROCESSOR DATA BOOK by Money, S. Price: £17.00

HANDBOOK OF ELECTRONIC CALCULATIONS by Kaufman, M. Price: £31.00

MICRO COOKBOOK Vol. 1 FUNDAMENTALS, Lancaster, D. Price: £13.75

UNIX THE BOOK by Banahan, M. Price £7.50

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

Please allow 14 days for reply or delivery (2023)

TW ELECTRONICS LTD

THE PCB ASSEMBLERS

More and more companies are investigating the advantages of using a professional subcontractor. Such an undertaking requires certain assurances.

TW are able to satisfy all of them — quality, competitive pricing, firm delivery and close co-operation with the customer.

Assembled boards at 100% inspected before flow soldering and reinspected after automatic cropping and cleaning.

Every batch of completed boards is issued with a signed certificate of conformity and quality — our final assurance.

For further details, contact us at our new works:

Blenheim Industrial Park
Bury St. Edmunds
Suffolk IP33 3UT

Telephone: 0284 3931 (1466)

ELECTRONIC DESIGN SERVICE. Immediate capacity available for circuit design and development work, PC artwork, etc. Small batch and prototype production welcome. — E.P.D.S. Ltd., 1A Eva Road, Gillingham, Kent. Tel: Medway (0634) 577854. (9667)

BATCH PRODUCTION wiring and assembly to sample or drawings. McDermott Electricals Ltd., 19b Station Parade, Ealing Common, London W5. Tel: 01-992 8976. (169)

BATCH PRODUCTION PC assembly to sample or drawings, any quantity. Stagecraft (Electronics) Ltd, Unit 7, Carew Street Industrial Estate, Camberwell SE5 9DF. Tel: 01-737 1422. (1942)

BOX NOs.

Box number replies should be addressed to:

Box No.

c/o Wireless World

Quadrant House

The Quadrant

Sutton, Surrey, SM2 5AS

ARTICLES WANTED

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, and quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO

86 Bishopsgate Street
Leeds LS1 4BB
0532 35649

WANTED

Scrap and re-usable mainframe computer and industrial electronic equipment.

E.M.A. Telecommunications Engineers, Orford, Woodbridge, Suffolk. Tel. 039-45 328. (1720)

SURPLUS

Top prices paid for surplus, redundant and obsolete test equipment, factories cleared.

Also quantities of components. Immediate settlement. We will call anywhere in the United Kingdom.

TIMEBASE

94 Alfriston Gardens
Sholing, Southampton SO2 8FU
Telephone: (0703) 431 323 (1852)

WANTED

Redundant/surplus electronic components and equipment. Telephone and computer spares.

Prompt service and payment.

J. B. PATTRICK
(Electronics)

191/193 London Road
Romford, Essex
Romford 44473 (1979)

WANTED

Redundant test equipment — receiving and transmitting equipment — valves, plugs and sockets — synchronos etc.

Phone: Johns Radio
0274 684007

84 Whitehall Road
East Birkenshaw
Bradford BD11 2ER (2049)

WANTED: Redundant test equipment — receiving and transmitting equipment — valves — plugs and sockets — synchronos, etc. Phone: John's Radio, 0274 684007. 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. (1723)

**PHONE
YOUR
CLASSIFIEDS
TO
IAN FAUX
ON
01-661 3033**

COMPUTER APPRECIATION

86 High Street, Bletchingley, Redhill, Surrey RH1 4PA - Tel: Godstone (0883) 843221

IMS 8000 SYSTEM. 4MHz Z80 based machine with S100 bus and running under CPM. Comprising 80KByte static RAM, twin 8" floppy disc drives. ELBIT Model 1920X VDU and TEXAS INSTRUMENTS Model 810 printer. Desk mounted and in immaculate condition. Manufactured 1981. £1650
 **NCR Model 8130 MICROCOMPUTER SYSTEM. INTEL 8080 based machine with 64KB memory (and battery back-up), twin dual density floppy disc drives, VDU, Model 4501 180 c.p.s. bi-directional nine wire matrix printer with additional facilities for reading bar-coded ledger cards. The system is 2 years old and full software and maintenance support is available from NCR. £3500
 TEXAS INSTRUMENTS Model 771 MICROCOMPUTER SYSTEM. Comprising VDU screen and keyboard with integral thermal printer. Dual 8" floppy discs. Based on TMS9900 16 bit microprocessor and having 64K memory. £850
 **MEMOREX Model 227B VDU. EBCDIC coded VDU. 24 lines x 80. These modern (1979) VDUs are particularly suitable for rebuilding around a single board computer or as a low cost terminal. Comprising, detached keyboard with single chip encoder, either of a standard type MOTOROLA or BALL BROS. 12" monitor, microprocessor (6008) controlled electronics with firmware in 2708 EPROM, and power supplies (5V at 15A, -12V at 3A). Cased. £40
 IBM Selectric (Golfball) terminal. Keyboard printer similar to Model 735, but complete with driver electronics £125
 **LOGABAX LX 180 keyboard printer with serial interface. 180 c.p.s. heavy duty dot matrix printer. Late model. £195
 **LOGABAX Model LX 180 printer with parallel interface and without keyboard. Early model. £150
 **TALLY Model 2000 high-speed (200 l.p.m.) matrix printer with Data Products interface. With (optional) stand. £195
 *HONEYWELL Model L1000 Keyboard printer. With serial interface operating at 110, 300 and 1200 Baud. BRAND NEW. This printer is sold together with another secondhand unit suitable for spares. £195
 **SPERRY-REMINGTON Word Processor. Comprising a dual cassette tape drive together with an IBM Golfball I/O typewriter. Offers very useful stand alone word processing facilities for less than the cost of a secondhand typewriter. £150
 CIP CASSETYPER Word Processor similar to above but more compact and with better facilities. Sold together with a complete and working SPARE electronics module containing SPARE tape drives. £350

*HEWLETT PACKARD Model HP41C pocket calculator complete with card reader, printer, memory module, Statistics ROM and Financial ROM. In excellent condition. £295
 *CDC Model BR8A2K Dual Density Floppy Disc Drives (8"). Comprising a PAIR of drives contained in a rack mounting cabinet complete with 24V power supply and rack slides. £185
 HEWLETT PACKARD Model 7905A. 15 Mbyte Disc Drive for 3000 Serial computers. Trolley mounted. £1175
 **ORE Model 4000A disc drive with ICL interface. £150
 CDC Model 9427HR HAWK Disc Drive. With one fixed platter and one top loading cartridge (not supplied) having a combined capacity of 10 megabytes. The fixed platter features soft sectoring. These widely used drives are compatible with many controllers for many processors including PDP11 controllers from ARROW & XYLOGICS. £550
 *CDC Model 9414 FALCON 10 Mbyte Disc Drive. Intended as a companion to the HAWK, but without removable cartridge. Compact low cost alternative to a Winchester. £200
 DIABLO Series 30 removable disc drive. 2.5 megabyte with industry standard interface. These drives are noted for their reliability and easy maintenance. Hardware, media and software compatible with DEC RK05J. Controllers available at low cost from XYLOGICS and several others. Fully refurbished. £285
 POWER SUPPLY for above £50
 WANGCO Model T1222 Disc Drive. One fixed and one removable platter. Industry standard interface. Lowest cost hard disc drive on the market offering 5 megabytes of fast access storage for the price of a floppy. £150
 *OKI Model 3303 WINCHESTER disc drive. 14" drive with standard SMD interface. 40 megabyte. A XYLOGICS interface for Q-Bus PDP11 is available at low cost, and they have successfully installed these drives for us in the past. £375
 WANGCO Model 1025 Tape Drive. Fully refurbished unit with a current new price of over £2,000. NRZ 800 b.p.i. £295
 WANGCO Tape Drive as above but PE 1600 b.p.i. £350
 DATA ELECTRONICS INC. Model 3637 45BC IE-S2 magnetic tape steamer for disc back-up. Without format. 4 track read-after-write head and capacity up to 10 megabytes. £265
 DEC PaperTape Reader/Punch. Late model, but without controller. £225
 FACIT Model 4020 PaperTape Reader. 300 c.p.s. TTL parallel interface. Companion to Model 4070. £225
 FACIT Model 4070 PaperTape Punch. High speed (75 c.p.s.) papertape punch with parallel TTL interface. £225

Please note: Items only marked * and ** (callers only) are included in our sale at very substantial price reductions - VAT and carriage extra on all items - Callers welcome, but by appointment only please.

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 110-120

PAGE	PAGE	PAGE
Acoustical Mfg. Co. Ltd. 5	Farnell Instruments Cover ii	Nova Products 92
Aero Electronics (AEL) Ltd. 2		
AFDEC Electronics 102		
A. H. Supplies 92		
All Electronics Show 18, 19		
Ambit International 16		
Analogue Associates 9		
Antex (Electronics) Ltd. Cover iii		
Armon Electronics Ltd. 89		
Audio Electronics 23		
Avel Lindberg (Cotswold Electronics) 96		
Bamber, B. Electronics 14		
Barrie Electronics Ltd. 95		
Black Star Ltd. 21		
Broadfield & Mayco 94		
Bull, J. (Electrical) Ltd. 12		
Caracal Power Products Ltd. 17		
Carston Electronics Ltd. 13		
Chiltern Electronics 89		
CIL Microsystem Ltd. 101		
Circuit Services 20		
Clark Masts Ltd. 23		
Clef Products (Electronics) Ltd. 16		
Colomer (Electronics Ltd.) 84		
Computer Appreciation 120		
Crotech Instruments Ltd. 97		
CT Electronics (Acton) Ltd. 93, 100		
Display Electronics 103		
Dwight Cavendish Co. Ltd. 102		
Electronic Brokers Ltd. 53, 83, 85		
Electronic Equipment Co. 97		
Electronics Today International 86		
Electrostatic Ltd. 16		
Electrovalue Ltd. 107		
Essex Electronics Centre 14		
Galatrek International 88		
Global Specialties Corp. (UK) Ltd. 15		
GP Industrial Electronics Ltd. 6, 7		
Greenweld 98		
Hameg Ltd. 9		
Happy Memories 92		
Harris Electronics (London) 2		
Harrison Bros. Electronic Distributors 4		
Hart Electronic Kits Ltd. 109		
Hemmings Electronics and Microcomputers 4		
Henry's Radio 16, 88		
Hilomast Ltd. 13		
H. W. International 26		
ILP Electronics Ltd. 21, 24, 25		
Integrex Ltd. 95		
Interface Quartz Devices Ltd. 20		
JAF Graphics 100		
Kelsey Acoustics 2		
Langrex Supplies Ltd. 87		
Levell Electronics Ltd. 96		
Magenta Electronics 8		
Maplin Electronic Supplies Ltd. Cover iv		
Middle East Wire & Wireless Ltd. 54		
Midland Computer Fair 104		
Midwich Computer Co. 17		
Olson Electronics 2		
Opus Supplies 94		
Oric Products International Ltd 3		
Orion Scientific Products Ltd 109		
Pantechnic 89		
PM Components 104, 105		
P. & R. Computer Shop 84		
Radford Audio Ltd. 109		
Radio Component Specialists 99		
Ralfie, P.F., Electronics 92		
Richardson Electronics 100		
RST Valves 87		
Sagin, M. R. 12		
Samsons (Electronics) Ltd. 101		
Sche Tronics Ltd 22		
Seyker Ltd. 20		
Sifam Ltd. 8		
South Midlands Communications Ltd. 22		
Sowler, E. A. Ltd. 96		
Special Products Distributors Ltd. 4		
Stewart of Reading 102		
Strumtech Engineering Ltd. 84		
Surrey Electronics Ltd. 8		
Technomatic Ltd 90, 91		
Texas Instruments Ltd 12		
Thandar Electronics 86		
Thanet Electronics 88		
Theatre Projects 98		
Thurby Electronics (Reltech) 100		
Time Electronics Ltd. 94		
T.O. Supplies (Export) Ltd. 22		
Turnkey 97		
Watford Electronics 10, 11		
Wedgewood, C.G. & Co. Ltd. 98		
White House Electronics 22		
Wilmslow Audio 8		
Wireless World Circards 106		
Wireless World Competitions 108		

OVERSEAS ADVERTISEMENT AGENTS

France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Ms Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget. Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan. Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212. Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.

United States of America: Ray Barnes, Business Press International Ltd, 205 East 42nd Street, New York, NY 10017 - Telephone (212) 867 2080 - Telex: 238327.

Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone (312) 63074.
 Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Jack Mantel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone (216) 621 1919.
 Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
 Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone (404) 237 7432.
 Mike Loughlin Business Press International, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.

Canada: Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
 * Also subscription agents.

Printed in Great Britain by QB Ltd., Sheepen Place, Colchester, For the Proprietors, Business Press International Ltd., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. © Business Press International Ltd 1983. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd, Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd: William Dawson & Son (S.A.) Ltd. UNITED STATES: Eastern News Distribution Inc., 14th Floor, 111 Eighth Avenue, New York, N.Y. 10011.

YOU'RE LOOKING AT 31 ANTEX SOLDERING IRONS!

The secret is in the range of bits for each model, from 19mm down to 0.5mm! No screws to seize up — push-on bits which cover the elements to save time and energy.

The new range of Antex irons come with or without safety plugs fitted. They are tougher than ever, and about twice as efficient as conventional designs.

Specify low wattage, low leakage Antex Irons now.



WW-002 FOR FURTHER DETAILS



Made in England

Our products are widely distributed by wholesalers and retailers throughout the UK. Please try your local dealer. Please send literature and price list to:

ANTEX (Electronics) Ltd.
Mayflower House, Plymouth, Devon.
Tel: (0752) 667377/8 Telex: 45296

Name Address

Telephone


WW4/83

TRADE PRICES

from

MAPLIN

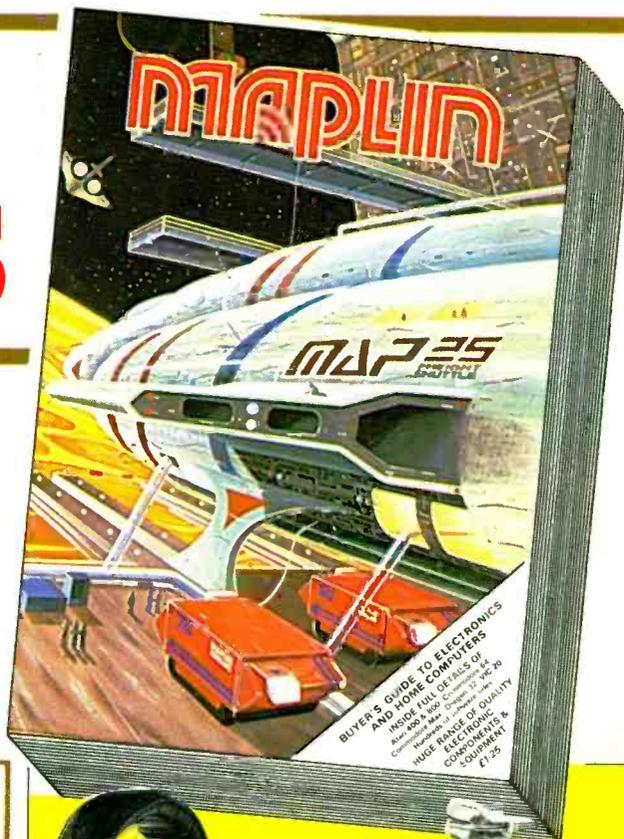Look at these examples from our huge range.



Code	Description	Cat. Page	Retail Price Incl. VAT	Min. Trade Qty.	Price Each for Min. Tr. Quantity excl. VAT
XB54J	Aerial Rotator	25	£39.95	5	£29.00
YG00A	Ni-Cad AA 500mAh	26	£1.25	50	75p
FB15R	Electrolytic 2.2uF 63V	90	10p	500	4.5p
FB22Y	Electrolytic 10uF 25V	90	9p	1000	3.5p
FB49D	Electrolytic 100uF 25V	90	14p	500	6.5p
FB73Q	Electrolytic 470uF 25V	90	30p	250	12p
FB83E	Electrolytic 1000uF 25V	90	40p	250	17p
FB96E	Electrolytic 4700uF 25V	90	£1.25	50	58p
YG41U	27MHz Rubber Duck	99	£4.75	25	£2.95
XG13P	1.5m CB Aerial	99	£13.95	5	£8.45
LB72P	2-Station Intercom	102	£8.75	10	£4.95
HF85G	1/4in. Jack Plug plastic barrel	142	19p	500	9p
HF88V	1/4in. Jack Plug stereo plastic barrel	142	28p	250	15p
HF87U	1/4in. Jack Plug metal barrel	142	39p	250	22p
HF89W	1/4in. Jack Plug stereo metal barrel	142	45p	250	28p
RW67X	13A nylon Mains Plug British	157	79p	100	45p
WL27E	LED 0.2in. Red	182	12p	500	6p
WL28F	LED 0.2in. Green	182	19p	500	10p
WL29G	LED 0.2in. Orange	182	33p	250	19p
WL30H	LED 0.2in. Yellow	182	17p	500	9p
RK07H	Panel Meter 100uA	197	£2.95	25	£1.95
RK09K	Panel Meter 1mA	197	£2.95	25	£1.95
RK19V	Panel Meter VU	197	£2.95	25	£1.95
YQ47B	Dual VU Meter	197	£3.90	25	£2.30
YR84F	Professional Plugblock	201	£6.95	10	£4.95
RX96E	20mm Fuse Holder	250	45p	250	24p
M10R-M1M	Metal Film 0.4W 1% Resistor	262	2p	1000	1p
FW00A-FW09K	Rotary Potentiometers linear	265	45p	250	32p
FW21X-FW29G	Rotary Potentiometers log	265	45p	250	32p
QL80B	1N4148	270	4p	1000	2p
QL22Y	741C 8-pin DIL	270	23p	500	12p
QH66W	NE555	270	21p	500	12p
QQ06G	4164 64K dynamic RAM	271	£5.99	100	£3.84
BL18U	DIL Socket 14-pin	336	11p	500	7.5p
BL17T	DIL Socket 8-pin	336	9p	1000	4.5p
WF14Q	Stereo Headphone with slide volume controls	342	£7.99	10	£4.95
FH00A	Sub-min Toggle Switch SPDT	347	70p	100	45p
FH04E	Sub-min Toggle Switch DPDT	347	99p	100	59p
FF73Q-FF76H	Rotary Switch break before make	348	74p	100	46p
FH42V-FH45Y	Rotary Switch make before break	348	70p	100	42p
YW93B	1000 ohm per volt Multimeter	362	£4.85	25	£2.95
YW68Y	20,000 ohm per volt Multimeter with Transistor Tester	363	£16.25	5	£10.45
BR75S	Box-joint Insulated 4 1/2in. Cutters	370	£6.93	10	£4.45
BR78K	Box-joint Insulated 4 1/2in. Pliers	371	£5.72	10	£3.95

Retail prices guaranteed until 4th May 1983. Quantity prices shown are subject to change without notice. Please check with us before ordering.

Most items in our catalogue are available at competitive trade prices; the bigger the quantity the better the price. If you find the example prices attractive, then contact us now with your requirements for a quotation. Phone Southend (0702) 552911 or write to us at P.O. Box 3, Rayleigh, Essex, SS6 8LR. Please ask for trade sales desk



Copies of our catalogue are available in all branches of W.H. Smith, price £1.25. In case of difficulty, send £1.50 to our mail-order address. Overseas price £1.90.

Maplin Electronic Supplies Ltd.

All mail to P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel. (0702) 552911. Shops at 159 King St., Hammersmith, W6. Tel. 01-748 0926.

Lynton Square, Perry Barr, Birmingham. Tel: 021-356 7292. 284 London Road, Westcliff-on-Sea, Essex. Tel. (0702) 554000. Shops closed all day Monday.

WW 4/83

WW-003 FOR FURTHER DETAILS