

FOR EVERYTHING IN ELECTRONICS

Wireless World

SEPTEMBER 1983 80p

**RTTY on a Nascom
Process control**

**Current
dumping**

**Better
stereo**

**Electronics and
mental handicap**

Australia A\$ 2.70
Canada C\$ 3.25
Denmark DKR. 33.25
Germany DM. 7.00
Greece DRA. 190.00
Holland DFL. 8.50
Italy L 3700
New Zealand NZ\$ 3.00
Norway NKR. 26.00
Singapore M\$ 5.50
Sweden SEK. 275.00
Switzerland SFR. 7.00

Directional power meter TM10

leads by a head



For colour brochure contact:


FARNELL INSTRUMENTS LIMITED
WETHERBY LS22 4DH
TELEPHONE (0937) 61961
TELEX 557294 FARIST G

- Single detector head covers wide frequency and power band
- 25MHz to 1GHz ■ 20mW to 100W and VSWR from 1 to 3
- Head can be used 1.5m from meter (e.g. inside closed car boot)
- Fully portable – works from internal battery or vehicle battery
- Mains adaptor/charger and rechargeable battery available
- Manufactured, tested and inspected to Min. Def. Std. 0524.



Farnell

WW-001 FOR FURTHER DETAILS

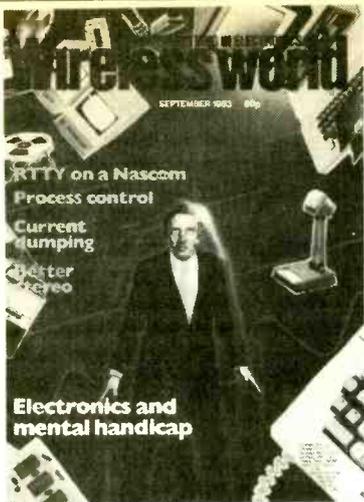

New concepts of system modelling such as 'data marshalling' and 'thinking fatigue' are linked to hyperautism - this month's cover depicts the 'shell' condition - in R. E. Young's perceptive analysis.

NEXT MONTH

Low-frequency stereo imaging is improved using simple delay technique.

Professor MaCausland finds persistent inconsistencies in Einstein's Special Theory of Relativity

Ray Macario shows a need for monitoring the accuracy of world time standards.

Complementing his description of a 6809-based Forth computer, Brian Woodroffe starts to describe the Forth language.

Flow diagrams enable a program for ladder network insertion loss and delay equalization for a ZX81 to be modified for other computers.

Current issue price 80p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.23, back issues (if available) £1.80, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS Tel: 01-661 8668.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3614. Advertising 01-661 3130. See leader page.

Telex: 892084 BISPRS G.

Subscription rates: 1 year £15 UK and £19 outside UK.

Student rates: 1 year £9.35 UK and £11.70 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3248.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone: 0444 459188. Please notify a change of address.

USA: \$44 surface mail, \$93.80 airmail. Business Press International (USA). Subscriptions Office, 205 E. 42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd class postage paid at New York.

© Business Press International Ltd 1983
ISSN 0043 6062.

FOR EVERYTHING IN ELECTRONICS Wireless World


SEPTEMBER 1983

VOL 89 NO 1572

-
- 21 TECHNOLOGY AND PEOPLE**
-
- 22 COMMUNICATIONS COMMENTARY**
Meteor scatter Polarization modulation Batteries
-
- 24 MENTAL HANDICAP AND ELECTRONICS**
by R. E. Young
-
- 30 RTTY ON A NASCOM**
by I. H. Wade
-
- 36 COMMON-MODE REJECTION EXPLAINED**
by B. L. Hart
-
- 39 CURRENT DUMPING REVIEW-1**
by M. McLoughlin
-
- 44 AUTOMATIC LOUDNESS COMPENSATION**
Microphone samples s.p.l.
-
- 45 ASSEMBLY LANGUAGE PROGRAMMING**
by R. F. Coates
-
- 50 LETTERS TO THE EDITOR**
Rechargeable h.l. battery Recording teletext More Heretics
-
- 54 PROCESS CONTROL BY PERSONAL COMPUTER**
by E. Bertra et al.
-
- 60 NEWS OF THE MONTH**
Merriman reports Cable tv bids Teletext by cable
-
- 63 TYPEWRITER PRINTER**
by N. Duffy
-
- 64 FORTH COMPUTER DISC DRIVES**
by B. Woodroffe
-
- 67 COMPLEMENTARY CURRENT MIRROR**
by I. M. Filanovsky
-
- 68 CIRCUIT IDEAS**
Acoustic timer 555 mark/space control RF notch filter
-
- 70 GENERAL PURPOSE MICROCOMPUTER BOARD**
by M. Shragai
-
- 73 NEW PRODUCTS**
Flat screen 'scope - d.v.m. B-H meter
-
- 104 INDEX TO ADVERTISERS**

RF LINEAR POWER AMPLIFIERS

LOW NOISE GASFET PREAMPLIFIERS

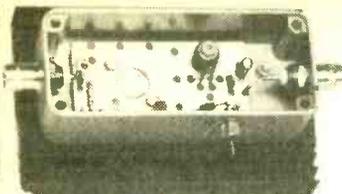

TYPE 9045

V MOS WIDEBAND LINEAR POWER AMPLIFIERS
4 watts and 20 watts max.
RF output. Without tuning.
Power gain 10 dB


TYPE 9045 10KHz - 100 MHz. 4 watts	£49.50 + £2.50 p&p
TYPE 9050 20 MHz - 200 MHz. 4 watts	£49.50 + £2.50 p&p
TYPE 9066 10 KHz - 100 MHz. 20 watts	£120 + £5 p&p
TYPE 9064 As above with integral mains power supply unit	£180 + £10 p&p
TYPE 9067 20 MHz - 200 MHz. 20 watts	£120 + £5 p&p
TYPE 9065 As above with integral mains power supply unit	£180 + £10 p&p



TYPE 9100 in 9010

THREE STAGE GASFET STRIPLINE PREAMPLIFIERS
Television bands IV or V.
Channel group 'A' 21-34,
'B' 39-51 or 'CD' 48-68.


TYPE 9100 Three stage Gasfet preamplifier. N.F. 0.7 dB. Gain 25 dB. High Q filter. 12V. + DC	£85 + £2 p&p
TYPE 9102 UHF three stage Gasfet preamplifier. N.F. 0.6 dB. Gain 25 dB. Aligned to your specified frequency in the range 250-500 MHz. High Q filter. 12V. + DC	£85 + £2 p&p
TYPE 9012 Gasfet preamplifier mains power supply unit	£24.50 + £3 p&p
TYPE 9010 Masthead weatherproof unit	£6.50 + £2 p&p

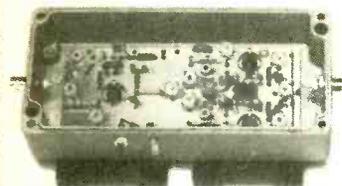

TYPE 9052

TELEVISION LINEAR POWER AMPLIFIERS
Bands IV or V.
Channel group 'A' 21-34, 'B' 39-51, or 'CD' 48-68.


TYPE 9061 150 mV. input. 10 mW. output. Adjustable gain	£120 + £5 p&p
TYPE 9052 10 mW. input. 500 mW. output. Adjustable gain	£120 + £5 p&p
TYPE 9059 500 mW. input. 5 watts output	£150 + £5 p&p

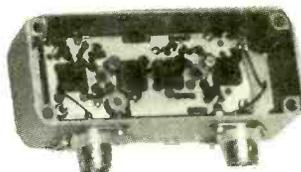

TYPE 9026

GASFET/MOSFET RF PREAMPLIFIERS
Aligned to your specified frequency in the range 1-250 MHz.
Masthead/local use.

TYPE 9026 N.F. 1.0 dB. Gain 10-40 dB. variable	£39.50 + £2 p&p
TYPE 9026FM As above. Band II 88-108 MHz	£39.50 + £2 p&p
TYPE 9006 Gasfet. N.F. 0.6 dB. Gain 10-40 dB. variable	£65 + £2 p&p
TYPE 9035 Mains power supply unit for above	£24.50 + £3 p&p

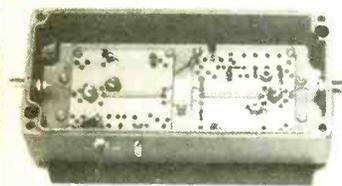

TYPE 9054

V MOS LINEAR POWER AMPLIFIERS
Tuned to your specified frequency in the range 1-250 MHz.

TYPE 9054 200 mW. -2 watts input. 20 watts output. Gain adjustable 10-20 dB	£120 + £5 p&p
TYPE 9060 As above with integral mains power supply unit	£180 + £10 p&p
TYPE 9068 1-8 watts input. 80 watts output. Gain adjustable 10-20 dB	£160 + £5 p&p
TYPE 9057 As above with integral mains power supply unit	£210 + £10 p&p
TYPE 9084 FM TRANSMITTER. 88-108 MHz. 50 watts RF output. 24V. + supply. Complete modular system	£345 + £15 p&p
TYPE 9085 As above with integral mains power supply unit	£395 + £20 p&p

IF YOU REQUIRE EQUIPMENT MODIFIED TO SPECIFICATION PLEASE CONTACT OUR TECHNICAL DEPARTMENT

RESEARCH COMMUNICATIONS LTD.
UNIT 3, DANE JOHN WORKS, GORDON ROAD, CANTERBURY, KENT CT1 3PP
TELEPHONE: CANTERBURY (0227) 56489

ALL EQUIPMENT IS DESPATCHED BY FIRST CLASS RECORDED DELIVERY

WW - 040 FOR FURTHER DETAILS

FREQUENCY COUNTERS

HIGH PERFORMANCE
HIGH RELIABILITY
LOW COST


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz - 1.2GHz
- ★ Sensitivity < 50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100 (100MHz)	£104.07
METEOR 600 (600MHz)	£133.97
METEOR 1000 (1GHz)	£184.57

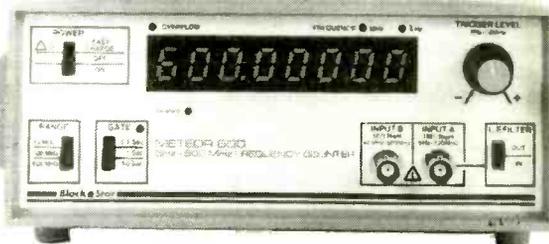Illustrated colour brochure with technical specification and prices available on request.



Designed and manufactured in Britain

Black Star

BLACK STAR LTD, 9A Crown Street, St.Ives, Huntingdon, Cambs. PE17 4EB, England.
Tel: (0480) 62440 Telex: 32339

WW - 056 FOR FURTHER DETAILS

SALE* P.&R. COMPUTER SHOP SALE*

IBM GOLFBALL PRINTERS from £70 EACH + V.A.T.

INTERFACE FOR IBM GOLFBALL £40 + V.A.T.
*BRAND-NEW LA36 DEC WRITERS - SALE £200 EACH + V.A.T.
CENTRONIC 779 PRINTERS - £325 + V.A.T.
CENTRONIC 781 PRINTER - £350 + V.A.T.
POWER UNITS, 5-VOLT 6-AMP - £20 EACH
FANS, PCBs, KEYBOARDS AND LOTS MORE
8-INCH IBM FLOPPY DISC DRIVES.

COME AND LOOK AROUND

SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, MALDON, ESSEX
PHONE MALDON (0621) 57440

WW - 049 FOR FURTHER DETAILS

FUSES, WIREWOUND RESISTORS

British-made by Beswick, Osborne
Stock items available at 30% extra discount
Also Carbon film resistors (Asian) stock items available at 50% extra discount
Send or phone for stock lists

Our regular lines always available:
Audible Warning Devices (single sample price including vat and postage shown in brackets)
Banshees (£23), Cybertones (£11), Solotones (£4), Bleepones (£7), Minibleeps (£8), Multimounts (£3.50)
Markers Sleeves - pvc, silicone rubber, neoprene, etc., printed or plain
Elma range of Collet knobs, dials, etc.
Crimp terminals. R.f. Chokes (Greendale)
Pcb self-adhesive guides, 18.5mm wide x any length


Write, call or phone (0732) 851345

NOVAPRODUCTS (APB Ltd)
Crystalate Works, Golden Green, Tonbridge, Kent TN11 0LH
Member Crystalate Group

WW - 046 FOR FURTHER DETAILS

FYLDE

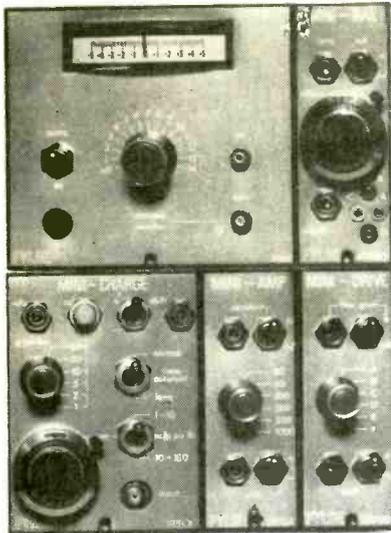TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE


Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

WW - 018 FOR FURTHER DETAILS

KONTAKT

The European name of Aerosol Excellence. Special cleaners for all electrical contacts and switches.

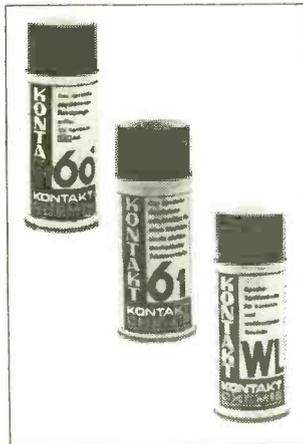

Kontakt 60

Dissolves oxides and sulphides, removes dirt, oil, resin and traces of metal abrasion. Protects against erosion. Ensures perfect contacts.

Kontakt 61

Special cleaning, lubricating and anti-corrosion fluid for NEW (non oxidised) and specially sensitive contacts. An excellent lubricant for all electrical and electro mechanical systems.

Spray Wash WL

A rapid cleaner for reliable washing and degreasing of electrical equipment and components. For removal of dirt, grease, oil, soldering residues and other impurities.

ALSO AVAILABLE:

A COMPLETE RANGE OF INDUSTRIAL AEROSOL SPRAYS

SK10 Soldering Lacquer, K75 Cold Spray, K70 Plastic Spray, K88 Oil Spray, K701 Vaseline Spray, K90 Video Spray, K33 Graphite Spray, K100 Antistatic Spray, K101 Fluid Spray and, of course, Positiv 20 positive photo resist for printed circuits.

Details from:

Special Products Distributors Ltd.

81 Piccadilly, London, W1V 0HL
Tel: 01-629 9556. Telex: 26500 (answerback RACEN). Cables: Speciproduct, London, W1

WW - 028 FOR FURTHER DETAILS

WIRELESS WORLD SEPTEMBER 1983

THE SOURCE OF ALL GOOD USED TEST EQUIPMENT

ANALYSERS

Drantz	
606 3 Line Disturbance Monitor	£2500.00
Hewlett Packard	
1615A/001 Logic Analyser	£4750.00
5004A Signature Analyser	£550.00
8407A/8412A Network Analyser	£1800.00
Marconi	
TF2303 Mod Meter	£460.00
Tektronix	
AA501 opt 01 Distortion 10Hz - 100KHz to Less than 0.0025%	£1450.00
DAS 9103 opt 01 02 Logic Analyser	£11,000.00
DF1 Display Formatter For 7D01	£850.00
308 Portable 8 Channel 20MHz Data Analyser	£2100.00
491 Spectrum Analyser 10MHz-40GHz	£7500.00
492 [opt 01, 08] Spectrum Analyser 50KHz-21GHz	£13000.00
492P [opt 01, 2, 3] Programmable Version of 492	£20000.00
7L5 Spectrum Analyser with opt 25 (Tracking Gen) and L3 [50Ω input] 20Hz - 5MHz	£7300.00
7L12 Spectrum Analyser 100KHz-1.8GHz	£8000.00
7L13 Spectrum Analyser 1KHz-1.8GHz	£7500.00
7L14 Spectrum Analyser 10KHz-1.8GHz	£8450.00
7L18 Spectrum Analyser 1.5GHz-60GHz	£7500.00
TR502 Tracking Generator (for 7L12, 13 & 14)	£3200.00
TR503 Tracking Generator (for 492/496 series)	£3250.00
5L4N Spectrum Analyser 20Hz-100KHz	£2350.00
7D01 16 Channel 100MHz Sample Rate	£2450.00
7D02/01 Logic Analyser	£3950.00

OSCILLOSCOPES

Hewlett Packard	
1332A High Quality CRT Display 9.6 x 11.8cm	£1250.00
1809A 100MHz 4 Channel Plug In	£2000.00
1821A Timebase Plug In	£1000.00
Philips	
PM3232 Dual Beam 10MHz	£495.00
Tektronix	
PM3232 Dual Beam scope/DMM, D T 5MHz	£975.00
335 Dual Trace 35MHz Small portable with delay T Base	£1300.00
465 100MHz Portable	£1,550.00
200C Trolley for 400 Series	£120.00
7313 100MHz Storage Mainframe	£2225.00
7603 100MHz Mainframe	£1850.00
5440 50MHz Mainframe	£1000.00
5441 50MHz Variable Persistence Storage Mainframe	£1800.00
7704A Scope DC-200MHz Mainframe	£2500.00
7613 Storage Scope Mainframe DC-100MHz	£3250.00
7834 Storage Scope Mainframe DC-400MHz	£7200.00
7844 Dual Beam 400MHz Mainframe	£7750.00
7854 Waveform Processing Scope DC-400MHz	£9000.00
7904 opt 02, 03 500MHz	£5350.00

TEKTRONIX TM500 SERIES

We stock a very wide range of these versatile modular equipments

Please note: Prices shown do not include VAT or carriage.

**Electronic Brokers Ltd., 61/65 Kings Cross Road,
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**

Electronic Brokers

TEKTRONIX PLUG IN'S

We stock a complete range of Plug In's for use with 7000 and 5000 series Mainframes.

TEKTRONIX TV TEST EQUIPMENT

148 Sig Gen	£4000.00
141A Sig Gen	£1500.00
1485R Waveform Monitor	£3200.00
651HR PAL Monitor	£2100.00
655HR-1 Monitor	£3800.00
656HR PAL/SECAM Monitor	£3900.00
671 PAL Monitor	£1800.00

MISCELLANEOUS

Bruel & Kjaer	
2209 Sound Level Meter	£850.00
Datalabs	
DL901 Transient Recorder	£750.00
DL905 Transient Recorder	£995.00
Fluke	
515A Portable Calibrator	£1750.00
883 AC/DC Differential	£815.00
845 AB Null Detector	£610.00
931B Diff V Meter	£1,000.00
2020A -3-6 Printer	£500.00
3010A Logic Tester: Self Contained, Portable, Full Spec. on Request	£8500.00
8921A DMM	£695.00
Hewlett Packard	
3200B Oscillator	£950.00
467A Amplifier	£725.00
415E VSWR Meter	£950.00
214A Pulse Gen	£850.00
3556A Psophometer	£850.00
435A Power Meter	£850.00
3552A Trans Test Set	£1,500.00
5300B/5306A DMM/Counter	£1,200.00
5340A Counter 10Hz-18GHz 8 Digit	£3750.00
8013B Pulse Generator	£750.00
8350A/83525A Sweeper System	£9,500.00
4815A Vector Impedance Meter	£3650.00
11720A Pulse Modulator	£1950.00
Marconi	
TF1313A LCR Bridge	£775.00
TF2120 Waveform Gen	£850.00
TF2603 RF Millivoltmeter	£750.00
TF2300B Mod Meter	£1500.00
TF2000 Oscillator	£575.00
TF2015/2 + TF2171 AM/RM Sig Gen	£1950.00
Racal	
9301A RF Millivoltmeter	£495.00
Tektronix	
106 Square Wave Generator 1ns risetime 10Hz-1MHz without accessories	£175.00
832 Data Comms. Tester	£825.00
833 Data Comms. Tester	£1350.00
2701 Step Attenuator 50Ω 0.79dB in 1dB steps. DC to 2GHz	£295.00
2901 Time-Mark Generator	£195.00

See us at **TESTMEX '83**
Stand 86
Grosvenor House
Sept 13-15



STOP PRESS
New Catalogue
Just Out
Send for your
free copy now

WW - 202 FOR FURTHER DETAILS

Be on a Winner!

A.R.R.A.

presents the

TWELFTH

AMATEUR RADIO AND ELECTRONICS

EXHIBITION

BIGGER AND BETTER THAN EVER...

on

6th, 7th & 8th OCTOBER, 1983

at

THE EXHIBITION CENTRE

DONCASTER RACECOURSE

(LEGER WAY)

MAGNIFICENT EXHIBITION HALL

EXCELLENT CATERING AND BARS

FREE CAR PARKING

ADMISSION: £1.50

OAPs & CHILDREN £1

**PARTIES OF 15 AND OVER:
£1.25 (inc. postage)**

Contact:

**FRED HOPEWELL (G4PGC)
48 GLADSTONE STREET
LOUGHBOROUGH
LEICESTERSHIRE LE11 1NS**

**THE ODDS ARE 100-1 YOU
WILL ENJOY THE SHOW!**

£500

VOUCHER PRIZES

IN

FREE


RAFFLE!

(Open 10am to 6pm)

TALK-IN BY G3UER

(S22 & SU8)

See you at Doncaster!

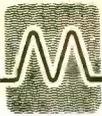

MICROWAVE MODULES LTD

TUNE INTO THE WEATHER . . .

USING OUR COMPLETE 'METEOSAT' WEATHER SATELLITE RECEPTION SYSTEM

We supply the complete system from antenna to video monitor, at the lowest price ever imagined for such a comprehensive system. View the entire globe on your video screen, or select any enlarged portion of the earth, for example Europe, as seen by the satellite from 20,000 miles above the earth. Both visible light pictures and infra-red pictures can be selected, the latter giving useful temperature information.

Our complete system consists of the following items:-

- 1. ANTENNA:** 1.1 metre diameter parabolic dish with feed, supplied in kit form to reduce costs and make transportation easier.
- 2. ANTENNA PREAMPLIFIER:** Gasfet low-noise preamplifier to be bolted on to the antenna, to overcome feeder losses and provide maximum sensitivity.
- 3. 1690 MHz CONVERTER:** Frequency converter from 1690 MHz to 137.5 MHz to allow a conventional receiver to be utilised.
- 4. 137 MHz RECEIVER:** The FM receiver, which demodulates the received encoded signal. Orbiting satellites on the 136-138 MHz band can also be received using this receiver.
- 5. DIGITAL FRAME STORE:** The audio signal from the receiver is stored in a large Dynamic RAM memory, which then drives the monitor to provide a continuous display.
- 6. VIDEO MONITOR:** A high quality black-and-white monitor, with 25 MHz bandwidth, ideal for displaying this type of image with excellent definition.

The above items are all that are necessary to obtain first-class pictures from Meteosat. **ALL FOR £1,295+VAT.**

Individual items from the above system are also available.

Write or phone for further details.

MICROWAVE MODULES

BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND

Telephone: 051-523 4011 Telex: 628608 MICRO G

WW - 050 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS

Now available with
3 OUTPLTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC

OUTPUT 2: 0-70v, 10A AC

OUTPUT 3: 0-250v, 4A AC

ALL
Continuously
Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW - 019 FOR FURTHER DETAILS

DEC SALE

a selection from our
huge stocks. All items
reconditioned unless
otherwise stated.

**NEW
AUTUMN' 83
CATALOGUE**
now out
send for your
free copy



SPECIAL PURCHASE OF PDP11/34A PROCESSORS

11/34A CPU
MS11JP 64KB MOS Memory
DL11W Console Interface
KY11LB Programmers Panel,
M9312 Bootstrap
BA11L 5 1/4" Chassis
ONLY £2,500

DEC LSI PROCESSORS

11/03LX KD11HA CPU,
KEV11 EIS/FIS, BDV11AA
Terminator/Bootstrap.
BA11N 5 1/4" Chassis with
Backplane and Power Supply.
No memory included.
NEW £1200
11/03N KD11G CPU,
KEV11 EIS/FIS, BDV11AA
Terminator/Bootstrap. BA11R
5 1/4" Chassis with Backplane
and Power Supply, MSV11DD
32KW MOS
NEW £1495

DEC MAG TAPE

TE16 Slave **£4,500**
TE16 Master with TM02 **£5,750**
TE16 Master with TM03 **£6,250**
TS11 Inc. Unibus Ctl
NEW **£6,250**
TU77 Master with TM03
NEW **£14,500**
All above include DEC Cabinet

DEC MUX AND COMMS

DH11AC Multiplexor **£1,500**
DH11AD Multiplexor **£2,750**
DH11AE Multiplexor **£2,400**
DM11DA Line Adaptor **£525**
DMC11AL I/P Link **£975**
DMC11AR Network Link **£995**
DMC11DA EIA Link **£675**
DMC11MD Int. Modem Link **£925**
DZ11B Multiplexor **£995**
DZ11D Multiplexor **£995**

DEC DISK DRIVES

RK07ED 28MB **£2,500**
RK07PD 28MB **£2,500**
RL01A 5MB **£995**
RM02AD 67MB NEW **£6,250**
RM03AD 67MB NEW **£6,250**
RM05AD 256MB NEW **£14,750**
RM80 124MB **£9,500**
RX11BD Dual Floppy **£995**
RX211BD Dual Floppy **£1,725**

DECSCOPE TERMINALS

VT50AB 20mA **£199**
VT50-AF EIA **£225**
VT52-AB 20mA **£350**
VT52-AF EIA **£395**
VT55-EB 20mA **£450**
VT55-EF EIA **£495**
VT55-FB + Copier, 20mA **£710**
VT55-FF + Copier, EIA **£750**

SCOOP PURCHASE OF


TEKTRONIX GRAPHICS EQUIPMENT

EX-DEMONSTRATION STOCK IN ORIGINAL MANUFACTURER'S
PACKAGING, HUGE SAVINGS ON NEW PRICES
ONLY SLIGHTLY USED - COVERED BY FULL WARRANTY

HIGH RESOLUTION BIG SCREEN GRAPHICS DISPLAY TERMINALS

4014-1, 4015-1 and 4016-1
19in. Screen providing 4096x by
3120Y displayable points or 8512
alphanumerics (models 4014 and
4015). 25in. Screen providing 4096x
by 3120Y displayable points or
15,000 alphanumerics (model 4016).
APL Character Set (model 4015).
Plot-10 compatible. Prices include
Enhanced Graphics Option. Extra
Memory Option and Programmable
Keyboard Option.
4014-1 **£6,950.** 4015-1 **£7,250.**
4016-1 **£8,950.**

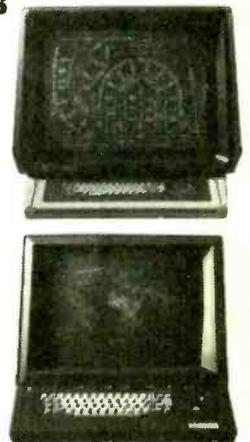Other Tektronix graphics equipment
currently available includes 4006-1,
4010-1, 4027, 4051, 4952,
606/606A/606B and 611.




ADD 15% VAT TO ALL PRICES Carriage and Packing extra

**Electronic Brokers Ltd, 61/65 Kings Cross Road,
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**



WW - 203 FOR FURTHER DETAILS

REGD. TRADE MARK

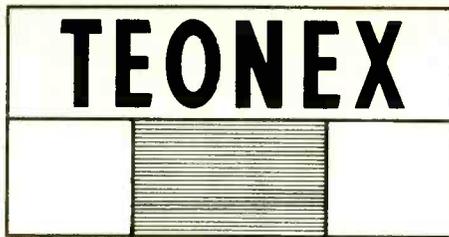

TEONEX ELECTRONIC VALVES AND SEMICONDUCTORS

SERVING THE WORLD FOR 30 YEARS

We specialise in the supply of Industrial Valves of British, European and USA manufacture, and semiconductors from the Philips Group. Many types, including obsolete and obsolescent types, always available from stock.

For further details, contact Mrs. Janet Lowy.

T.O. SUPPLIES (EXPORT) LTD., 2A Westbourne Grove Mews, London W11 2RY.
Telephone: (01) 727 3421 Telex: 262256 Answerback TOSPLY G

WW - 009 FOR FURTHER DETAILS

EASIBINDERS

Quick, neat and easy!



It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold six issues and is attractively bound and blocked with the WIRELESS WORLD logo.

Price U.K. £4.30 including postage, packing and V.A.T.

Overseas orders add 35p per binder
Nat. Giro No. 5157552.

Please allow 3/4 weeks for fulfilment of order.

Payment by ACCESS/BARCLAYCARD/VISA. Send coupon below detailing credit card no. and signature.

Why not place your order now? Send the completed coupon below with remittance payable to:

EASIBIND 42 Hoxton Square
London N1 6NS

Order Form WIRELESS WORLD

I enclose P.O./cheque value..... for..... binders

Years required.....
BLOCK LETTERS PLEASE

Name.....
Address.....

Date..... Registration No. 735718

9in. MONITOR in attractive case, non standard input with info. £25.	24 MARCONI SIGNAL GENERATOR TF1060/2. 450-1200MHZ. Late style. £150
Matching ASC 11 coded QUERTY KEYBOARD with Numeric Keypad and 27 function keys. £25 each. P&P £5. THE PAIR £40.	26 MARCONI FM/AM SIGNAL GENERATOR TF995A/5. 1.5-220MHZ. AM/FM Mod. £225
12in. MONITOR cased, non-standard input, with info. £20 each.	27 MARCONI UNIVERSAL BRIDGE TF868B. £120
With matching ASC 11 coded QUERTY KEYBOARD with Numeric Keypad and 24 function keys. £35.	28 MARCONI RF POWER METER TF1152 range. 50 ohm. £50
INSTRUMENT CASE, standard 19in. width x 16in. deep x 10in. high. £5 each.	29 MARCONI SIGNAL GENERATOR TF2002A/5. AM/FM 10KHZ-72MHZ. AM/FM Mod. £475
FLOPPY DISK DRIVE bin. by MEMOREX with control electronics. £75 each P&P £5.	30 MARCONI SIGNAL GENERATOR TF2002. As above. AM only. £250
HARD DISK DRIVES by DATA RECORDING. Series 30. Front load with info. £125 each.	31 MARCONI POWER METER TF893A. 20HZ-35KHZ. £75
TEKTRONIX STORAGE DISPLAY UNIT type 611. Screen size 8 1/2in. x 6 1/2in. £495.	32 MARCONI VACUUM TUBE VOLTMETER TF1041B. £20
AZTEC 20in. black and white monitor. Video in £50. TV style 20in. monitors. £30.	33 MARCONI CARRIER DEVIATION METER TF1910. 4-1024MHZ. £95
COSSOR VDU type CDD3000. 12in. green screen. £60.	34 MARCONI SENSITIVE VALVE VOLTMETER TF2600. 10HZ-10MHZ. 1mV-300 Volts. £75
CREED 75 TELEPRINTER Very good condition. £25 each. Carriage £7.	36 MARCONI DISTORTION FACTOR METER TF142F. 100-800HZ. £85
	37 MARCONI VHF SIGNAL GENERATOR TF1064B/5M. 68-108/118-185-450-470MHZ. £95
	38 MARCONI AUTOMATIC DISTORTION METER TF2337. £225
	44 H.P. VHF SIGNAL GENERATOR type 608C 10-480MHZ. £150
	46 H.P. 431B POWER METER with head type 8478B. 10MHZ-18GHZ. £250
	48 H.P. LOG VOLTMETER AMPLIFIER type 7563A. £95
	51 WAYNE KERR SOURCE & DETECTOR SR268. £75
	52 WAYNE KERR VHF ADMITTANCE BRIDGE type B801B. £95
	53 H.P. UHF SIGNAL GENERATOR type 612A 450-1230MHZ. £175
	61 AIRMEC MODULATION METER type 210. 3-300MHZ. £125
	68 ADVANCE FM/AM SIGNAL GENERATOR SG63A. 7.5-230MHZ. £75
	72 ADVANCE SIGNAL GENERATOR type J1A 15HZ-50KHZ. £35
	87 JERROLD SWEEP GENERATOR SYSTEM Model SS-300-5B. 0-300MHZ. £350
	100 KAY SWEEP & MARKER GENERATOR type 1500C. 20HZ-200KHZ. £125
	111 BRADLEY OSCILLOSCOPE CALIBRATOR type 156. £175
	113 RADIOMETER type AFM1 MODULATION METER. 3.5-320MHZ. £150
	125 BONTON POWER AMPLIFIER type 230A. 10-500MHZ. RF Output 0-30V. £100
	62 AIRMEC WAVE ANALYSER type 248. 5-300MHZ. £75
	65 AIRMEC SIGNAL GENERATOR type 365. AM/FM. 1-302MHZ. £130
	84 R&S SWEEP SIGNAL GENERATOR SWH BN4242/4. 50KHZ-12MHZ. £95
	85 R&S NOISE GENERATOR SKTU BN4151/2/75. 1-1000MHZ. £50
	88 FLUKE DIFFERENTIAL VOLTMETER Model 821A. £50

Item No.

1	TEKTRONIX OSCILLOSCOPE type T935A. Dual Trace 35MHZ. Delay Sweep. As New. £500
2	TEKTRONIX STORAGE OSCILLOSCOPE type 564B with 3A5 and 3B3. £395
3	TEKTRONIX OSCILLOSCOPE type 545B with 1A2. Dual Trace 33MHZ. Dual TB. £160
4	SE LABS OSCILLOSCOPE type SM111. Dual Trace 20MHZ. Solid State. £225
5	COSSOR OSCILLOSCOPE type CDU110. Dual Trace 20MHZ. Solid State. £150
6	SOLARTRON OSCILLOSCOPE type CD1400. Dual Beam 15MHZ. Delay Sweep. £90
7	MINISTRY OSCILLOSCOPE type CT436. Dual Beam. DC-6MHZ. £60
8	B&K AUDIO FREQUENCY SPECTROMETER type 2113. Unused. £850
9	B&K ELECTRONIC VOLTMETER type 2409 2HZ-200KHZ. £50
10	B&K MICROPHONE AMPLIFIER type 2604. £50
11	B&K FREQUENCY ANALYSER type 2105. £150
12	B&K AUDIO FREQUENCY SPECTROMETER type 2109. £125
15	B&K RANDOM NOISE GENERATOR type 1402. £125
16	MARCONI UNIVERSAL BRIDGE type TF2700. £225
17	MARCONI RF ELECTRONIC MILLIVOLTMETER type TF2603 50KHZ-1.5GHZ. £175
18	MARCONI SIGNAL GENERATOR type TF144H/4. 10KHZ-7MHZ. £125
20	MARCONI FM/AM SIGNAL GENERATOR TF1066B/1. 10-470MHZ. Int and Ext. AM/FM Mod. £250
21	MARCONI FM/AM SIGNAL GENERATOR TF995A/3S. 1.5-220MHZ. AM/FM Mod. £150
23	MARCONI RF POWER METER TF1020A/1. 50 ohm. DC-250MHZ. £75

Stockists of NEW SAFGAN OSCILLOSCOPES. Also many other ITEMS OF TEST EQUIPMENT AND COMPONENTS in stock. For further details contact DWYANE STEWART.

EXECUTIVE TELEPHONES - PUSH BUTTON
Many functions including 10 number memory, repeat dialling, etc. Will connect to GPO System. Brand New. £25 each. P&P £4.

EQUIPMENT IN WORKING ORDER
Please check availability before ordering. Carriage all units. £7. VAT to be added to total of Goods and Carriage. S.A.E. for LISTS.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 68041

Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

WW - 037 FOR FURTHER DETAILS

TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

*Gold service available.
21 days manufacture for urgent deliveries.

*Orders despatched within 7 days of receipt for single or small quantity orders.

*5 year no quibble guarantee.

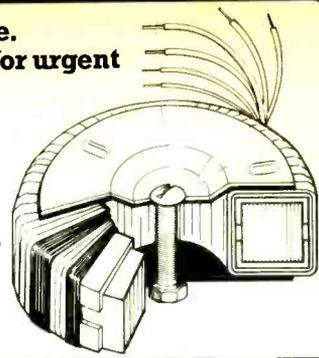

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE																														
<p>NEW! NEW! NEW!</p> <p>15 VA 0x010 6+6 1.25 62 x 34mm 0x011 9+9 0.83 0.35Kg 0x012 12+12 0.63 Regulation 0x013 15+15 0.50 £5.12 19% 0x014 18+18 0.42 + p & p £0.78 0x015 22+22 0.34 + VAT £0.89 0x016 25+25 0.30 TOTAL £6.79 0x017 30+30 0.25</p> <p>(encased in ABS plastic)</p>					<p>120 VA 4x010 6+6 10.00 90 x 40mm 4x011 9+9 6.66 1.2Kg 4x012 12+12 5.00 Regulation 4x013 15+15 4.00 £7.42 11% 4x014 18+18 3.33 + p & p £1.72 4x015 22+22 2.72 + VAT £1.37 4x016 25+25 2.40 TOTAL £10.51 4x017 30+30 2.00 4x018 35+35 1.71 4x028 110 1.09 4x029 220 0.54 4x030 240 0.50</p>					<p>300 VA 7x013 15+15 10.00 110 x 50mm 7x014 18+18 8.33 2.6Kg 7x015 22+22 6.82 Regulation 7x016 25+25 6.00 £10.88 6% 7x017 30+30 5.00 + p & p £2.05 7x018 35+35 4.28 + VAT £1.94 7x026 40+40 3.75 TOTAL £14.87 7x025 45+45 3.33 7x033 50+50 3.00 7x028 110 2.72 7x029 220 1.36 7x030 240 1.25</p>					<p>30 VA 1x010 6+6 2.50 70 x 30mm 1x011 9+9 1.66 £5.49 0.45Kg 1x012 12+12 1.25 + p & p £1.10 Regulation 1x013 15+15 1.00 + VAT £0.99 18% 1x014 18+18 0.83 TOTAL £7.58 1x015 22+22 0.68 1x016 25+25 0.60 1x017 30+30 0.50</p>					<p>160 VA 5x011 9+9 8.89 110 x 40mm 5x012 12+12 6.66 1.8Kg 5x013 15+15 5.33 Regulation 5x014 18+18 4.44 £8.43 8% 5x015 22+22 3.63 + p & p £1.72 5x016 25+25 3.20 + VAT £1.52 5x017 30+30 2.66 TOTAL £11.67 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66</p>					<p>500 VA 8x016 25+25 10.00 140 x 60mm 8x017 30+30 8.33 4Kg 8x018 35+35 7.14 Regulation 8x026 40+40 6.25 £14.38 4% 8x025 45+45 5.55 + p & p £2.40 8x033 50+50 5.00 + VAT £2.52 8x042 55+55 4.54 TOTAL £19.30 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08</p>					<p>50 VA 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 £6.13 13% 2x014 18+18 1.38 + p & p £1.35 2x015 22+22 1.13 + VAT £1.12 2x016 25+25 1.00 TOTAL £8.60 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p>					<p>225 VA 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 £9.81 7% 6x016 25+25 4.50 + p & p £2.05 6x017 30+30 3.75 + VAT £1.78 6x018 35+35 3.21 TOTAL £13.64 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p>					<p>625 VA 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.14 Regulation 9x025 45+45 6.94 £17.12 4% 9x033 50+50 6.25 + p & p £2.55 9x042 55+55 5.68 + VAT £2.95 9x028 110 5.68 TOTAL £22.62 9x029 220 2.84 9x030 240 2.60</p>				
<p>30 VA 1x010 6+6 2.50 70 x 30mm 1x011 9+9 1.66 £5.49 0.45Kg 1x012 12+12 1.25 + p & p £1.10 Regulation 1x013 15+15 1.00 + VAT £0.99 18% 1x014 18+18 0.83 TOTAL £7.58 1x015 22+22 0.68 1x016 25+25 0.60 1x017 30+30 0.50</p>					<p>160 VA 5x011 9+9 8.89 110 x 40mm 5x012 12+12 6.66 1.8Kg 5x013 15+15 5.33 Regulation 5x014 18+18 4.44 £8.43 8% 5x015 22+22 3.63 + p & p £1.72 5x016 25+25 3.20 + VAT £1.52 5x017 30+30 2.66 TOTAL £11.67 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66</p>					<p>500 VA 8x016 25+25 10.00 140 x 60mm 8x017 30+30 8.33 4Kg 8x018 35+35 7.14 Regulation 8x026 40+40 6.25 £14.38 4% 8x025 45+45 5.55 + p & p £2.40 8x033 50+50 5.00 + VAT £2.52 8x042 55+55 4.54 TOTAL £19.30 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08</p>					<p>50 VA 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 £6.13 13% 2x014 18+18 1.38 + p & p £1.35 2x015 22+22 1.13 + VAT £1.12 2x016 25+25 1.00 TOTAL £8.60 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p>					<p>225 VA 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 £9.81 7% 6x016 25+25 4.50 + p & p £2.05 6x017 30+30 3.75 + VAT £1.78 6x018 35+35 3.21 TOTAL £13.64 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p>					<p>625 VA 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.14 Regulation 9x025 45+45 6.94 £17.12 4% 9x033 50+50 6.25 + p & p £2.55 9x042 55+55 5.68 + VAT £2.95 9x028 110 5.68 TOTAL £22.62 9x029 220 2.84 9x030 240 2.60</p>																			
<p>50 VA 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 £6.13 13% 2x014 18+18 1.38 + p & p £1.35 2x015 22+22 1.13 + VAT £1.12 2x016 25+25 1.00 TOTAL £8.60 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p>					<p>225 VA 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 £9.81 7% 6x016 25+25 4.50 + p & p £2.05 6x017 30+30 3.75 + VAT £1.78 6x018 35+35 3.21 TOTAL £13.64 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p>					<p>625 VA 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.14 Regulation 9x025 45+45 6.94 £17.12 4% 9x033 50+50 6.25 + p & p £2.55 9x042 55+55 5.68 + VAT £2.95 9x028 110 5.68 TOTAL £22.62 9x029 220 2.84 9x030 240 2.60</p>																																		

The benefits of ILP toroidal transformers
ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows


IMPORTANT: Regulation — All voltages quoted are FULL LOAD Please add regulation figure to secondary voltage to obtain off load voltage

For 110V primary insert "0" in place of "X" in type number
For 220V primary (Europe) insert "1" in place of "X" in type number
For 240V primary (UK) insert "2" in place of "X" in type number

Also available at Electrovalue, Maplin, Technomatic and Barrie Electronics.

For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.

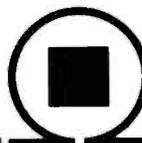Post to ILP Electronics Ltd, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 54778 Telex 965780



ILP TRANSFORMERS
(a division of ILP Electronics Ltd)

WW - 025 FOR FURTHER DETAILS

RECHARGEABLE BATTERIES

PRIVATE & TRADE ENQUIRIES WELCOME


Full range available to replace 1.5 volt dry cells and 9 volt PP type batteries, SAE for lists and prices. £1.45 for booklet, "Nickel Cadmium Power," plus catalogue.

★ COMPLETE RANGE OF CHARGERS

SANDWELL PLANT LTD.
2 Union Drive, Boldmere
Sutton Coldfield, West Midlands, 021-354 9764
After hours: LICHFIELD 57977
Now open Saturday morning 9.30 to 12.30

WW - 021 FOR FURTHER DETAILS

METER PROBLEMS?

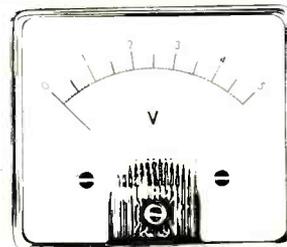

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)
138 GRAY'S INN ROAD, W.C.1 Phone: 01-83-7937
Telex: 892301

WW - 022 FOR FURTHER DETAILS

AVO 1001 £28.50


The new AVO 1000 Series of analogue testers feature a breakthrough in design.

A slot in the handle is the key to simple lead stowage, but that's only one aspect of our breakthrough. This series, designed and built in Britain, also features top entry leads with right angled fittings, moulded channels to contain spare prods and clips; easy-to-read analogue scales; simple range selection, a separate battery and fuse compartment and a handy tilt stand. The specification is equally outstanding.

The AVO 1001, for instance, offers voltage testing to 1kV (a.c. and d.c.), current up to 1A d.c. and resistance up to 2M Ω .

See your usual distributor for further information and a demonstration.

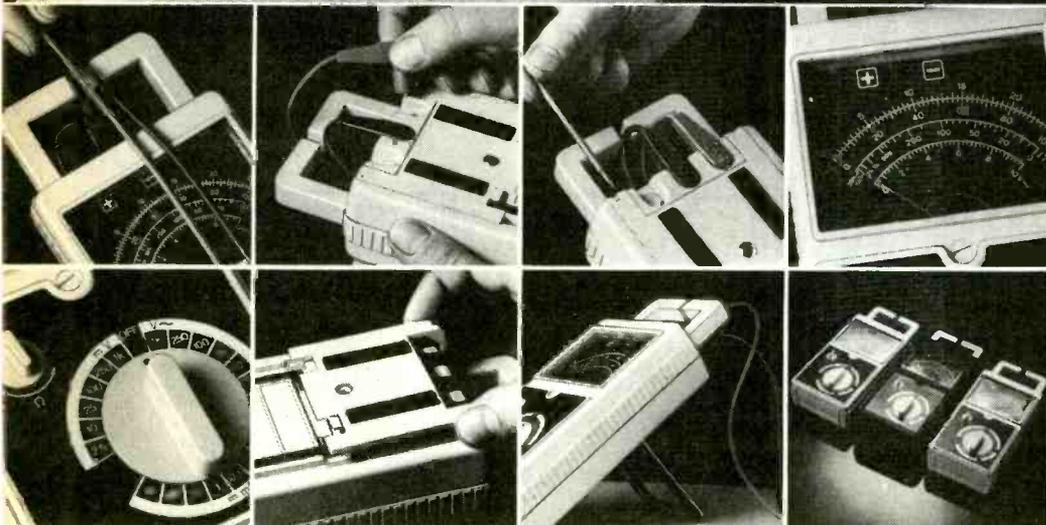Chances are you'll want to drop it into your toolbag right away. Which is fine, we've designed them for precisely that.



The test of ability




THORN EMI Instruments Limited

Archcliffe Road, Dover, Kent CT17 9EN. Telephone: 0304 202620. Telex: 96283

WW - 046 FOR FURTHER DETAILS

FIBED

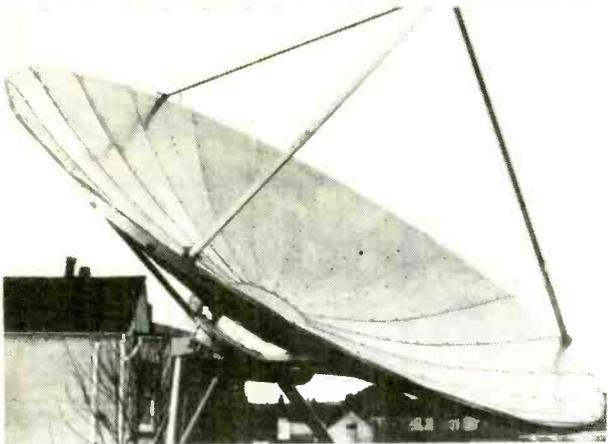6FT. PARABOLIC DISHES FROM ONLY £85 PLUS V.A.T.



6ft. dia. dishes, feed horns and electronics for use in 4GHz satellite reception. GaAs Fet transistors, SMA connectors, P.T.F.E., etc. available. Please send s.a.e. for full details and data sheets.

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX
Tel. Southend (0702) 332338


WW - 010 FOR FURTHER DETAILS



GAIN ANTENNAS FOR PMR Windsor Range 60-500MHz

ANTENNAS

SMC77 SMC582

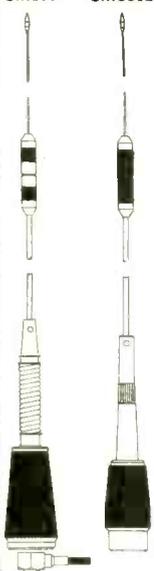

LOW BAND $\frac{3}{8}\lambda$ HIGH GAIN

SMC-370F 66-74 MHz } Fold over
SMC375F 71-79 MHz } bases whips
SMC383F 78-88 MHz }

HIGH BAND $\frac{1}{2}\lambda$ HIGH GAIN

SMC77FL 160-166 MHz Foldover
SMC77FH 166-172 MHz Foldover

or the sprung versions
SMC77SL 160-166 MHz
SMC77SH 166-172 MHz

HIGH BAND $\frac{5}{8}\lambda$

SMC910 Fixed
SMC920 Foldover
SMC930 Sprung

HIGH BAND $\frac{1}{2}\lambda$

SMC910 Fixed
SMC920 Foldover
SMC930 Sprung

UHF $\frac{5}{8}\lambda$ + $\frac{5}{8}\lambda$ COLINEAR

6DBi GAIN
SMC582H 454-464 MHz
SMC582L 427-441 MHz

All antennas in the WINDSOR RANGE are fully interchangeable (on any base option) giving complete and easy choice from the wide range available. Unique low band $\frac{3}{8}$ being probably the first improvement on the $\frac{1}{2}$ wave low band ever. All antennas are available in commercial quantities.

BASE OPTIONS



WING MOUNT



GUTTER MOUNT



MAGNETIC MOUNT



TRUNK MOUNT



BODY MOUNT

SOUTH MIDLANDS COMMUNICATIONS LTD.

RUMBRIDGE ST., TOTTEN
SOUTHAMPTON SO4 0DP

Telex: 477351 SMCMM G
Tel: Totton (0703) 867333

WW - 035 FOR FURTHER DETAILS

Midwich

COMPUTER COMPANY LIMITED

1st choice for microcomputer components

BBC MICROCOMPUTERS Model B 346.95 Model B + Disc Int. 431.95 BBC MICRO DISC DRIVES BBC31 Single 100K 195.00 BBC32 Dual 100K 335.00 BBC34 Dual 400K 525.00 All disc drives include all Cables, Manual & Utilities Disc. BBC MICRO UPGRADE KITS BBCA28 Complete A TO B 44.75 BBC1 16K Memory 18.00 BBC2 Printer 7.50 BBC3 Disc 84.95 BBC4 Analogue 6.70 BBC5 Serial & RGB 7.30 BBC6 Bus 6.45 Fitting service available. BBC MICRO CONNECTORS BBC21 Printer Cable 7.50 (not assembled) BBC22 User Port Connector & Cable 2.46 BBC23 Cassette Lead 3.50 BBC24 7 Pin Din Plug 0.80 BBC25 6 Pin Din Plug 0.60 BBC26 5 Pin Din Plug 0.60 BBC MICRO ACCESSORIES BBC45 Joysticks 11.30 BBC MICRO SOFTWARE View Wordprocessor 52.00 1-2MOS 10.00 ACORNSOFT Full range available. Please telephone for stock position.	INTERFACE DEVICES 6402 3.80 75107 0.47 75110 0.56 75150 0.64 75154 0.77 75160 2.56 75161 2.80 75162 3.95 75172 1.95 75173 1.44 75174 1.95 75175 1.44 75182 0.50 75183 0.50 75188 0.37 75189 0.37 75451 0.22 75452 0.22 75453 0.22 75454 0.22 75468 0.88 75491 0.31 75492 0.42 AY31015 D2 3.00 AY31270 D1 6.47 AY38910 D6 4.40 AV53600 D2 6.70 DP9304 D1 2.50 MC1488 D1 0.37 MC1489 D1 0.37 NC3242A D1 6.30 MC3446 D1 3.75 MC3448A D1 3.75 MC3480 D5 3.00 MC3487 D1 2.00 MC14411 D1 7.65 MC14412 D1 9.45 RO32513L D1 6.50 RO32513U D1 6.50 UMF MODULATORS UM1111 6MHZ D1 2.60 UM1233 8MHZ D1 3.90 BUFFERS 81L595 0.80 81L596 0.80 81A597 0.80 81L598 0.80 8T26A 0.90 8T28A 0.90 8T95 0.90 8T97A 0.90 8T98 0.90 MEMORIES D1 0.80 D2 2.95 D1 2.45 D1 4.95 D1 7.25 D2 3.45 D1 3.45 D1 5.45 D1 7.95 D1 0.85 D2 0.80 D1 3.25 D2 9.45 D1 3.30 D1 4.95 D3 3.95 D3 3.95 D2 2.25 D2 2.95 6800 FAMILY D7 2.25 D5 2.50 D6 6.30 D1 1.15 D3 1.00 D4 7.75 D5 6.50 D2 1.10 D7 7.30 D6 12.00 D1 2.26 D3 2.20 D4 6.00 D2 2.20 Z80 FAMILY D2 2.99 D2 9.00 D1 2.60 D1 9.00 D1 5.50 D2 6.95 D1 2.75 D1 9.00 D4 9.00 8080 FAMILY D4 3.50 8085A 1.10 8216 1.00 8224 2.10 8228 3.27 8251A D5 2.50 8253 4.00 8255A D5 2.25 6500 FAMILY D3 3.25 D3 5.00 D1 2.50 D1 3.16 D5 3.00 D5 5.50 D2 5.50 FLOPPY DISC CONTROLLERS 8271 48.00 FD1771 D5 15.00 FD1791 D6 22.00 FD1793 D6 23.00 FD1795 D6 28.00 FD1797 D6 28.00 WD1691 D2 12.00 WD2143-01 D2 6.99	TL507 1.33 725 1.60 741 0.14 747 0.48 748 0.27 REGULATORS 78L05 0.30 78L12 0.30 78L15 0.30 7805 0.40 7812 0.40 7815 0.40 7905 0.45 7912 0.45 7915 0.45 LM309K 1.20 LM317K 2.40 LM323K 4.50 LM338K 6.25 DATA CONVERTORS UPD7002 D1 4.26 ZN425 D1 3.45 ZN426 D1 3.00 ZN427 D1 5.99 ZN428 D1 4.75 ZN429 D1 2.10 ZN432 D1 13.00 ZN449 D1 2.55 CRYSTALS 1MHz 2.75 1.8432 MHz 1.92 4MHz 0.64 8MHz 0.86 DIL SOCKETS Pins Tin Gold W/W 8 7 16 25 14 10 26 35 16 10 29 40 18 13 33 50 20 15 37 60 22 17 38 65 24 21 46 70 28 24 55 80 40 30 76 99 ZIF SOCKETS 24 Pin 5.75 28 Pin 8.20 40 Pin 9.75 LINEARS TL203 0.65 TL398N 4.75 LM301AN 0.24 LM308N 0.48 LM311P 0.50 LM319N 1.99 LM324N 0.30 8T37A 0.60 LM348N 0.60 NE555P 0.16 NE556CP 0.45 TL010 0.39 TL061 0.29 TL062 0.49 TL064 0.98 TL066 0.29 TL071 0.29 TL072 0.47 TL074 1.00 TL081 0.26 TL082 0.46 TL084 1.58 TL091 0.40 TL092 0.58 TL094 1.34 TL487 0.62 TL489 0.62 TL494 1.53 TL496 0.60 SPECIAL OFFER! SPECTRUM 32K UPGRADE KIT £24.95 Carriage Orders up to £199 are sent by 1st class post, and £200+ by Securicor. 0-£100 0.50 £100-£199 1.25 £200+ 5.00 by Securicor. Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice. Quantity Discounts are available on many products, please ring for details. Official Orders are welcome from Education Establishments, Government Bodies and Public Companies. Credit Accounts are available to others subject to status. Payment is due strictly net by the 15th of the month. Credit Cards are accepted (Access and Visa) for telephone and postal order and NO SURCHARGE is made. Out of stock items will follow automatically, at our discretion, or a refund will be given if requested.
-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

Data sheets are available on items marked D. Prices are as follows:
 D1 0.75 D5 2.00
 D2 1.00 D6 3.00
 D3 1.25 D7 4.00
 D4 2.00 D8 5.00

THE ABOVE LIST SHOWS JUST A FEW OF THE ITEMS IN STOCK PLEASE TELEPHONE YOUR REQUIREMENTS - OR BETTER STILL SEND FOR OUR FREE CATALOGUE

Please complete this coupon for a copy of our FREE catalogue

NAME _____


ADDRESS _____

TEL NO _____

MIDWICH COMPUTER COMPANY LIMITED
 RICKINGHALL HOUSE, RICKINGHALL, SUFFOLK IP22 1HH
 TELEPHONE (0379) DISS 898751


WW - 023 FOR FURTHER DETAILS

GET BIG POWER

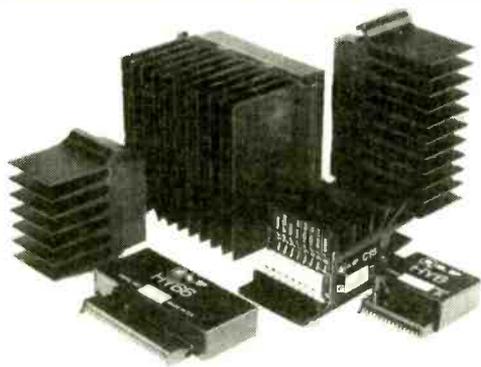

Modular Amplifiers the third generation

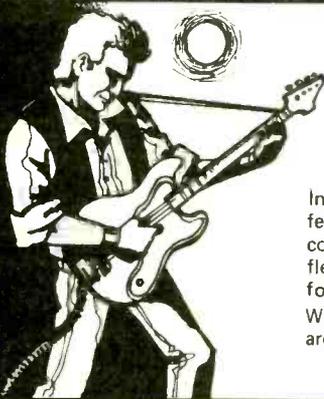Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
HY 30	15	4-8	<0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY 60	30	4-8	<0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY 120	60	4	<0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY 128	60	8	<0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY 244	120	4	<0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY 248	120	8	<0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY 164	180	4	<0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY 368	180	8	<0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15V/ μ s. Risetime: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre-amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre-amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp.

A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6 - HY13 £1.05 (inc. VAT) and the B66 for modules HY66 - HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.94
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£11.40
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£19.80
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.00

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20V/ μ s. Rise time: 3 μ s. S/N ratio: 100db.

Frequency response (-3dB) 15Hz - 100KHz. Input sensitivity: 500mV rms.

Input impedance: 100K Ω . Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz.

S/N ratio (DIN AUDIO) 80dB. Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

WITH A LOT OF HELP FROM





PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

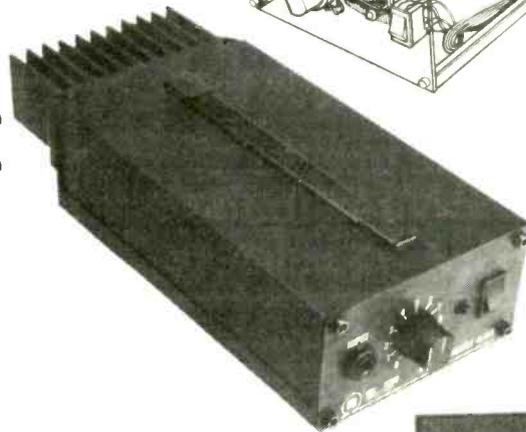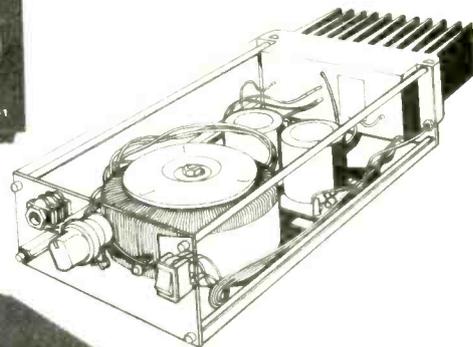Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.

UNICASES

HI-FI Separates					Price inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	Hi-Fi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	Hi-Fi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	Hi-Fi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	Hi-Fi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	Hi-Fi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	Hi-Fi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	Hi-Fi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.96
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.). All units except UC1 incorporate our own toroidal transformers.

TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. If sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED



Post to: ILP Electronics Ltd., Freepost, 5 Graham Bell House, Roper Close, Canterbury, CT2 7EP, Kent, England. Telephone (0227) 54778. Technical (0227) 64723. Telex 965780.

Please send me the following _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

WW - 024 FOR FURTHER DETAILS



HF COMMUNICATIONS RECEIVERS

FOR

POINT TO POINT/TRANSPORTABLE

AND

MARINE SYSTEMS

DESIGNED AND MANUFACTURED TO HIGHEST INTERNATIONAL SPECS

Fully Synthesised

10Hz or 100Hz steps

Continuously Tuned 50KHz to 30MHz

Modes LSB/USB/CW/AM/FSK

Stability ± 1 part in 10^7 °C

Tuning Keypad/Spin/Decade

Power Supplies
110V/240V AC and 24V DC

WE ANNOUNCE NEW MODELS

- (a) SR 520 To meet new C.E.P.T. Spec for Ships Main Receiver.
 - (b) SR 522 with Preselector for Point to Point/Transportable.
 - (c) SR 530 As (a) above but MICROPROCESSOR/KEYPAD controlled, 200 channel memory, Scanning.
 - (d) SR 532 As (c) above but for Point to Point/Transportable
- OPTIONS. Full Remote Control by VHF Radio or Telephone Line, Dual Diversity, FSK Demodulator and 600 ohm Line Amplifiers.

SEND FOR TECHNICAL BROCHURES TO:

VIGILANT COMMUNICATIONS LTD, UNIT 5, PONTIAC WORKS, FERNBANK ROAD, ASCOT, BERKS, ENGLAND

TELEPHONE: (0344) 885656

TELEX: 849769 VIGCOM G

WW - 052 FOR FURTHER DETAILS

Greatech LTD
Electronics
DISPLAY & COMMUNICATION PRODUCTS

Hay Lane,
Braithree,
Essex CM7 6ST

Telephone: (0376) 327117
Telex: 987911
24-Hour Ansaphone Service

R.F. POWER TRANSISTORS Many other types available				NEW VALVES National, Varian, Mullard, RCA, ITT...			
2N3375	5.85 SD 1005	6.48 MRF 221	12.05	E80CC	15.00 8AU6A	2.30	
2N3553	1.50 SD 1006	1.80 MRF 231	9.36	E80F	13.30 8AU5GA	4.25	
2N3733	3.20 SD 1012FL	7.50 MRF 234	13.80	E88CC	4.50 6AW8A	2.85	
2N3866	1.00 SD 1013	7.50 MRF 237	2.75	E180F	8.00 6B8	3.10	
2N3926	9.85 SD 1088	23.00 MRF 238	12.60	EC91	8.65 6BA8A	3.40	
2N3927	11.02 SD 1089	25.64 MRF 239	15.00	ECC81	1.19 6BH6	2.55	
2N4416	0.75 SD 1098	32.82 MRF 240	18.55	ECC82	1.19 6BQ7A	3.45	
2N4427	1.00 SD 1127	2.60 MRF 243	28.08	ECC83	1.19 6BR8A	3.50	
2N4440	6.50 SD 1135	8.42 MRF 245	30.10	ECC88	2.30 6B28	2.50	
2N5016	6.72 SD 1136	11.80 MRF 247	34.00	ECC91	3.75 6CB6A	2.30	
2N5090	16.80 SD 1143	8.50 MRF 250	5.00	EC9H1	2.50 6CD8GA	4.65	
2N5109	2.01 SD 1219	11.40 MRF 261	7.00	EF86	1.35 6CL6	3.45	
2N5179	0.86 SD 1229FL	7.80 MRF 262	10.40	EL34	2.88 6CW4	6.85	
2N5485	0.62 SD 1272	10.20 MRF 264	11.00	EL84	1.00 6DK6	2.65	
2N5486	0.66 SD 1272FL	10.20 MRF 314	25.06	KT77	6.80 6D05	5.50	
2N5589	4.70 SD 1407	22.50 MRF 401	10.84	PC92	4.00 6D06B	4.00	
2N5590	6.85 SD 1410	19.68 MRF 406	11.83	PCF802	1.60 6E8A	2.50	
2N5591	8.90 SD 1412	27.18 MRF 421	31.57	PCL805	1.00 6GK6	2.46	
2N5635	5.20 SD 1416	30.00 MRF 422	35.52	PL509	4.75 6J4	4.20	
2N5636	9.70 SD 1418	26.22 MRF 449A	14.00	PL519	4.75 6J5	4.30	
2N5637	11.25 SD 1428	23.00 MRF 450A	11.40	PY500A	2.98 6J6A	4.90	
2N5641	5.35 SD 1429	13.98 MRF 453	13.30	QQV02-6	6JB6A	4.05	
2N5642	7.90 SD 1444	3.00 MRF 454A	16.80	/6939	15.75 6JS6C	5.00	
2N5643	13.00 SD 1488	26.25 MRF 455	13.80	QOV03-10	6K6GT	2.75	
2N5913	2.10 2SC730	3.84 MRF 460	15.78	/6360	9.50 6KD6	5.60	
2N5944	6.90 2SC1165	5.88 MRF 464	31.57	QOV03-20A	6LQ6	6.00	
2N5945	8.95 2SC1177	16.14 MRF 472	2.50	/6252	63.00 65N7GTB	2.75	
2N5946	11.40 2SC1308	1.44 MRF 475	2.40	QOV06-40A	6080	11.00	
2N6080	5.10 2SC1307	2.34 MRF 476	1.71	/5894	45.00 6146A	7.70	
2N6081	6.75 2SC1678	1.44 MRF 477	10.70	QVO3-12	6146B	7.70	
2N6082	8.45 2SC1946A	18.54 MRF 515	2.70	/5763	5.80 6159B	18.00	
2N6083	8.75 2SC1947	9.24 MRF 604	1.60	UCL 82	1.60 6201	6.30	
2N6084	11.70 2SC1970	2.76 MRF 607	2.20	2D21	2.85 6360	6.00	
2N6094	5.00 2SC1971	7.50 MRF 629	4.10	3B28	14.95 6550A	6.70	
2N6095	6.90 2SC1972	10.32 MRF 646	26.24	4CX250B	37.10 6688	9.80	
2N6096	8.40 2SC2237	15.00 MRF 648	35.14	4CX350A	69.50 6689	12.24	
2N6097	13.30 2SC2538	1.62 MRF 901	2.58	5U4GB	2.50 6883B	7.70	
				5670	3.40 6973	3.85	
				5726	2.40 7360	9.50	
				5763	4.05 7551	5.90	
				5814A	3.50 7558	9.50	
				5842	11.20 7591A	3.80	
				5965	3.25 7868	3.95	
				6AH6	4.75 811A	14.75	
				6AK5	3.55 812A	18.55	
				6AK6	2.00 813A	60.00	
				6AN5	4.40 866A	15.00	
				6AN8A	3.20 872A	15.65	
				6AQ5A	2.15 8298A	4.90	
				6AS6	5.10 8417	5.80	
				6ASTG	6.45 931A	18.20	
				6AT6	1.35 12AY7	3.75	
				6AU5GT	4.50 12BY7A	2.60	

Normally stock items are shipped by return post.
We can supply nearly ANY TYPE OF VALVE or R.F. POWER TRANSISTOR - ring for quotation.

TERMS: Cash, Postal Order or Cheque with order
CREDIT: Accounts available subject to approved references
POSTAGE: Add 60p to order
VAT: All prices are excluding VAT, please add 15% to order
GUARANTEE: All goods brand new and to specification

WW - 041 FOR FURTHER DETAILS

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, parallel BCD (including Weekday) output for alarm etc and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, only 15x5x8cm, built-in antenna, 1000Km range, GET the RIGHT TIME, £72.70.

60KHZ RUGBY RECEIVER, as in MSF Clock, serial data output for computer, decoding details and Basic listings, £24.20.

Audio Oscillator, 10Hz-200KHz, sine, square, £21.60.

Each fun-to-build kit (ready made to order) includes all parts, printed circuit, case, instructions, by-return postage etc, money back assurance, so GET yours NOW.

CAMBRIDGE KITS

45 (WW) Old School Lane, Milton, Cambridge. Tel 860150

Bird Electronic


THRULINE® Wattmeters

TERMALINE® loads

and accessories from stock

Aspen Electronics Limited

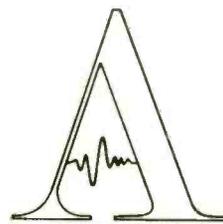The exclusive
UK representative for Bird Electronic
2/3 Kildare Close, Eastcote,
Ruislip, Middlesex HA4 9UR
Telephone: 01-868 1188
Telex: 8812727




WW - 033 FOR FURTHER DETAILS

Essex Tiny Basic System

The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal, and then be copied into EPROM. Alternatively, Instant ROM modules may be used both during development and for program storage.


£185

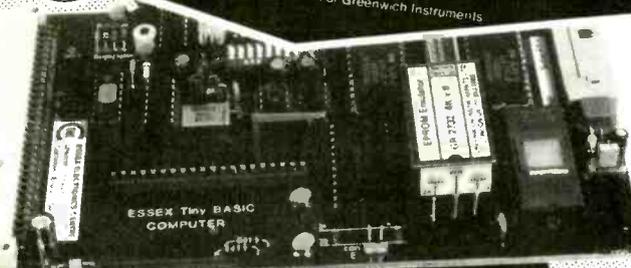

Essex Buffer Timer

A convenient means of buffering the I/O lines of the Essex Tiny BASIC Computer provides 24 inputs, 16 outputs and four hardware timers.


£78

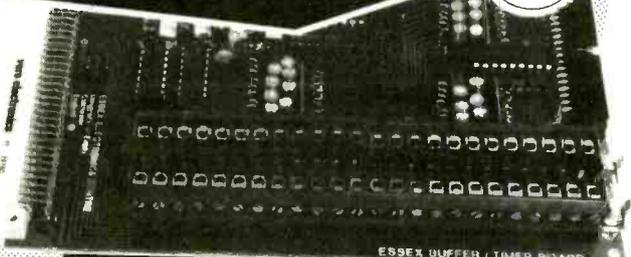

Essex Opto-Isolator

Connects to the Essex Tiny BASIC System bus to provide an additional 12 opto-isolated inputs and 12 opto-isolated outputs per card for safe connection to external equipment, isolation voltage = 1500 volts.

£150

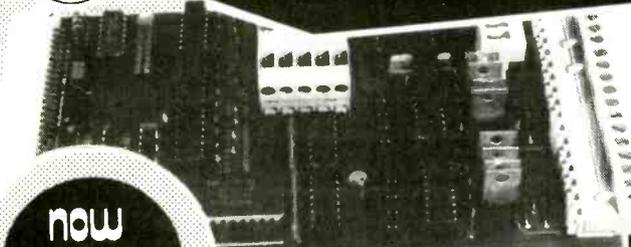

now available...

Essex Backplane

A four slot backplane with printer and terminal connectors to accept these cards. **£35**

Alex

A powerful software utilities package that provides the user with an enhanced editor and all the tools needed to program efficiently in assembly language.

* Text Editor * Assembler
* Disassembler * Debug Monitor
Supplied as a 4K EPROM with comprehensive manual. **£65**

all prices exclude V.A.T.
* substantial quantity discounts available
* carriage within U.K. £2

Essex Electronics Centre

Wivenhoe Park, Colchester, Essex CO4 3SQ
Telephone: Colchester (0206) 865089

CALL IN AND SEE FOR YOURSELF


AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)

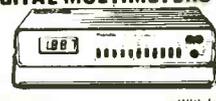

ALL MODELS 3 1/2 DIGIT UNLESS STATED



HAND HELD	With free carry case etc.	Beckman T110 As T100 plus Cont. test.	£67.85
K025C = 13 range 0.2A DC 2 meg ohm	£24.95	Sifam 2200B 21 range 2A AC/DC 20 meg ohm	£39.95
K030S = 16 range 10A DC 2 meg ohm	£34.95		
K030C = 26 range 1A AC/DC 20 meg ohm	£39.95		
K055C = 28 range 10A AC/DC 20 meg ohm	£34.40		
6010+ 28 range 10A AC/DC 20 meg ohm	£41.30		
7030+ As 6010 but 0.1% basic.	£39.95		
K0615 = 16 range 10A DC 2 meg plus Hfe tester	£69.95		
189M 30 range 10A AC/DC 20 meg plus Hfe tester	£41.95		
H030 16 range 0.2A AC/DC 2 meg ohm	£44.50		
H030/B As above plus cont. buzzer	£58.95		
H031 22 range 10 AC/DC 2 meg ohms plus cont. buzzer	£49.95		
DM2350 = 21 range 10A AC/DC 20 meg ohm miniature hand held auto range	£56.35		
Beckman T100 34 range 10A AC/DC 20 meg ohm			

FREQUENCY COUNTERS

P FM200A MHz hand held pocket 8 digit LED	£77.60
8110A 8 digit LED bench 2 ranges 100 MHz	£77.00
8610B 9 digit LED bench 2 ranges 800 MHz	£113.85
8000B 9 digit LED 3 ranges 1 GHz	£178.00
TF040 = 8 digit LCD 40 MHz	£126.50
TF200 = 8 digit LCD 200 MHz	£186.75
Prescalers - Extended range of most counters	
TP600 600 MHz	£43.00
TP1000 1 GHz	£74.00

SIGNAL GENERATORS (220/240V AC)

FUNCTION: All sine/square/triangle/TTL, etc	TG100 1 Hz - 100 KHz	£90.00
	TG102 0.2 Hz - 2 MHz	£168.75
PULSE	TG105 Various facilities 5 Hz - 5 MHz	£97.75
AUDIO: Multiband Sine/Square	LAG27 10 Hz to 1 MHz	£90.85
	AG202A 20 Hz to 200 KHz (List £94.50)	£83.50
	RF	
	SG402 100 KHz to 30 MHz (List £79.50)	£89.50
	LSG17 100 KHz to 150 MHz	£78.35

ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100m with carry case **£63.00**

MULTIMETERS (UK C/P 65p)

HM102Z 20K/V 10A DC 22 range & cont. buzzer	£13.50
HM102Z 20K/V 22 range & cont buzzer	£14.95
ETC5000/5001 21 ranges, 50K/V, Range doubler, 10A DC.	£18.95
TMK500 23 ranges 30K/V, 12A DC plus cont. buzzer.	£24.75
NH56R 20K/V, 22 range pocket	£10.95
ETU102 14 range 2K/V pocket	£6.50
830A 26 range 30K/V, 10A AC/DC overload protection, etc.	£23.95
360TR 23 range 100K/V, Large scale 10A AC/DC plus Hfe	£39.95
AT1020 18 range 20K/V, Deluxe plus Hfe tester	£18.95
YM 360TR 19 range 20K/V plus Hfe tester	£15.95
Matrix Professional multimeters in stock 3 models from	£74.75

VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP241 0/12/24V, 0/1A	£35.00
PP243 3 amp version	£59.95
P8 1307S 8/15V 7 amp twin meter	£24.95

DIGITAL THERMOMETER

TH301 LCD -50°C to +750°C with thermocouple **£68.43**

AC CLAMP METER

ST300 0/300A, 0/600 VAC, 0/1 Kohm 9 ranges With carry case (UK C/P 65p) **£28.50**

LOGIC PROBES

LP10 10 MHz **£28.50**
OLP50 50 MHz with carry case and accessories **£52.33**

OSCILLOSCOPES

Full specification any model on request. SAE by post.	
HM Series NAMEG: 'SC' THANOAR: 'CS' TRIO: '3' CROTECH 'DT' Saigpan	
SINGLE TRACE UK C/P £3.00	
3030 15 MHz 5mv, 95mm tube plus component tester C/P £3.00	£177.10
SCI10A = Miniature 10 MHz battery portable	£171.00
Post free	
HM103 15 MHz 2mv, 6 x 7 display plus component tester C/P £3.00	£181.70
Optional carry case £6.84 AC adaptor £6.69	
Nicads £12.50	
DUAL TRACE (UK C/P £4.00)	
DT 520 Dual 20 MHz	£241.50
HM203/4 Dual 20 MHz plus component tester	£303.60
CS1562A Dual 10 MHz (List £321.00)	£269.50
3131 Dual 15 MHz + component tester	£276.00
CS1566A Dual 20 MHz All facilities (List £401.35)	£349.50
HM204 Dual 20 MHz plus component tester sweep delay	£419.75
CS1820 Dual 20 MHz with extra facilities (List £508.30)	£485.00
OX710 Matrix dual 15 MHz + component tester	£304.75

OPTIONAL PROBE KITS

X1 £7.95 X1 - X10 £10.50 X10 £9.45 X100 £16.95

HIGH VOLTAGE METER

Direct reading 0/40 KV, 20K/Volt. (UK C/P 65p) **£23.00**

DIGITAL CAPACITANCE METER

0.1 pf to 2000 mfd LCD 8 ranges OM6013 **£52.75** (Carry case £2.95)

TRANSISTOR TESTER

Direct reading PNP, NPN, etc. TC1 (UK C/P 65p) **£21.95**

AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON W2 1BN, TEL: 01-724 3564
ALSO AT HENRYS RADIO,
404/406 EDGWARE ROAD, LONDON, W2, TEL: 01-724 0323
HENRY'S COMPONENT SHOP, TEL: 01-723 1008

FREE CATALOGUES SEND LARGE SAE (UK 20p)

ALL PRICES INCLUDE VAT

WW - 013 FOR FURTHER DETAILS

WW - 039 FOR FURTHER DETAILS

If you can buy it cheaper we'll refund the difference*

This month's offer is another winner – a consignment of 14" R.G.B. colour monitors manufactured by J.V.C. – at prices never seen before in the U.K. Suitable for use with BBC Micro, Lynx, Oric, Apple II, Apple III and IBM, etc.

It's a safe to put a cheque in the post today. Because, if you find someone who's cheaper, we'll refund the difference.

RGB MEDIUM RES £199


Resolution, 370x235 Pixels.
Display, 80 charactersx25 lines. Slot Pitch .63mm.
Input, Video – RGB Analogue with TTL input.
SYNC – Separate SYNC on RGB. Features, On/Off switch with pilot light. Brightness control.
Power 220/240V 50/60HZ.

RGB HIGH RES £299

Resolution, 580x235 Pixels.
Display, 80 charactersx25 lines. Slot pitch .41mm.
Input, Video – RGB Analogue with TTL input
SYNC – Separate SYNC on RGB.
Features, On/Off switch with pilot light.
Brightness control. Power, 220/240V 50/60HZ.

IBM COMPATIBLE £349

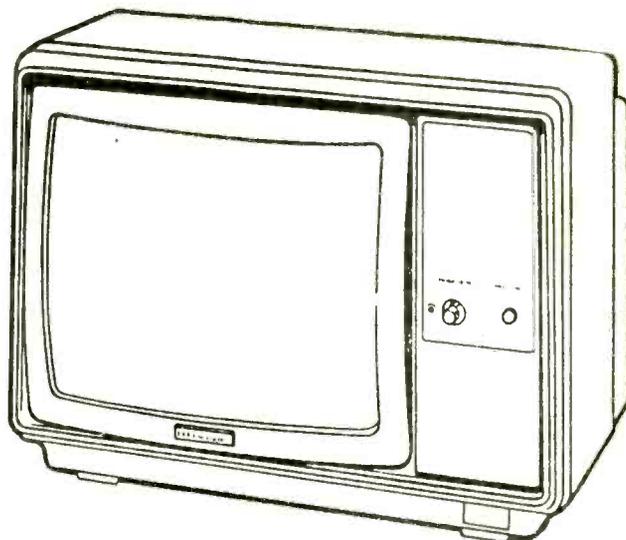Specifications as above with IBM interface.



VIEW DATA TERMINALS PRESTEL. Built-in modem Slimline design



ONLY £199
LIMITED QUANTITY

Green characters/black background
24 lines x 40 characters

NASHUA FLOPPY DISCS

Minis		8" Discs	
S/S S/D	£16.95 for 10	S/S S/D	£17.95 for 10
S/S D/D	£19.95 for 10	S/S D/D	£23.95 for 10
D/S D/D	£22.95 for 10	D/S D/D	£24.95 for 10
S/S 80 Track	£24.95 for 10		
D/S 80 Track	£26.95 for 10		

With full 5 year warranty. All mini discs have hub rings and a FREE plastic library case.

12" GREEN SCREEN MONITOR

One year warranty, ex stock delivery, 18MHz, Phono connector. Limited quantity **only £69.95**

Lead to connect to BBC **£5.95**

8" DISC DRIVES SHUGART COMPATIBLE

FD514 S/S Dual density. Formatted 600K Byte **only £149.00**

FD650 D/S Dual density. Formatted 1.2M Byte **only £199.50**

Certec 90-day warranty.

Case to hold 2 drives – complete with power supply and fan **only £99.95**

TEAC DISC DRIVES

TEAC 55F D/S 80-TRACK DRIVE

* Single drive in case complete with all leads **only £249.95**

(Gives single density 400K, double density 800K)

* Dual drive in case with own P.S.V. and all leads **only £499.95**

(Gives single density 800K, Double density 1.6Mb)

* Uncased drive **£229.00**

Ribbon leads: single £12; dual £15

Power leads: single £5; dual £6

DUAL CASE WITH PSU & BLANKING PLATE **£39.95**

JAPANESE DISC DRIVES

TEAC 55A/CANON MDD 6106

S/S 40-TRACK **FROM £129.95**

Formatted single density 100K

Double density 200K

Case to hold single drive **£9.95**

*Our price pledge only applies to the JVC monitor

To order: Add carriage at the following rates:

Discs 85p. Other goods £7 Add VAT at 15% to total and send your order to:

OPUS SUPPLIES

158 Camberwell Road, London SE5 0EE

Tel: 01-701 8668 (3 lines) 01-703 6155/6/7

Government and educational orders welcome



LOOK AHEAD!

MONOLITH
electronic products

WITH MONOLITH MAGNETIC TAPE HEADS -


VIDEO HEAD REPLACEMENT KIT



DOES YOUR VCR GIVE WASHED OUT NOISY PICTURES - IT'S PROBABLY IN NEED OF A NEW HEAD - FAST FROM OUR EX-STOCK DELIVERIES.

SAVE ££'s ON REPAIR CHARGES. OUR UNIVERSAL REPLACEMENT VIDEO HEADS FIT ALL MODELS OF VHS OR BETAMAX VCR's. FOLLOWING OUR REPLACEMENT GUIDE AND WITH A PRACTICAL ABILITY, YOU CAN DO THE WHOLE JOB IN YOUR OWN HOME WITH OUR HEAD REPLACEMENT KIT.

ALL YOU NEED!

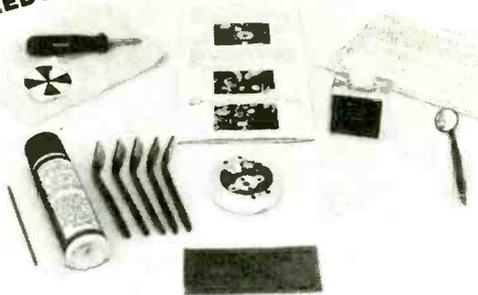

HOW TO ORDER,

PLEASE STATE CLEARLY THE MAKE AND MODEL OF YOUR RECORDER. THERE ARE TWO VERSIONS OF THE VHS HEAD AND YOUR ORDER CAN BE PROCESSED FASTER IF YOU CHECK THE SIZE OF THE CENTRE HOLE OF THE HEAD WHICH WILL BE EITHER 5mm OR 15mm DIAMETER.

CATALOGUE

For our full Catalogue of Replacement Video and Audio Cassette/Reel to Reel Heads, Motors, Mechanisms etc. Please forward 50p P. & P.

KIT CONTAINS - NEW VIDEO HEAD, 5 CLEANING TOOLS, HEAD CLEANING FLUID, CAN OF AIR BLAST, INSPECTION MIRROR, ANTISTATIC CLOTH, VHS/BETAMAX MAINTENANCE MANUAL, CROSS HEAD SCREWDRIVER, HANDLING GLOVES, MOTOR SPEED DISC, SERVICE LABEL, HEAD REPLACEMENT GUIDE.


VHS KITS £53.25
BETAMAX KIT £85.25
Prices include P. & P. and V.A.T.

THE MONOLITH ELECTRONICS CO. LTD


5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0460) 74321
Telex 46306 MONLTH G

MONOLITH THE SPECIALISTS
SUPPLIER TO MOST OF THE U.K.'s LEADING DISTRIBUTORS AND SERVICE ORGANISATIONS

WW - 007 FOR FURTHER DETAILS

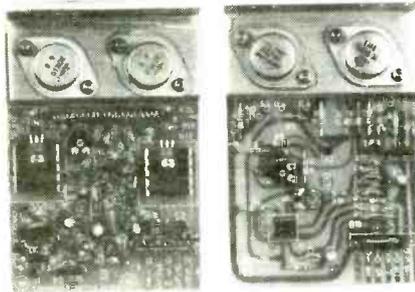

BI POLAR & FET POWER AMPLIFIERS

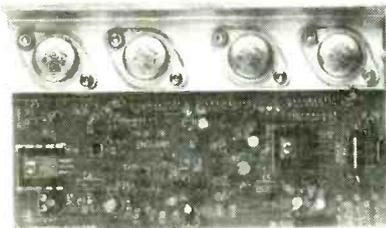

HEAVY DUTY POWER AMPLIFIERS

CRIMSON AMPLIFICATION: First Choice of the Professionals!

Whatever your application, Crimson Modular Amplification provides a simple, efficient, and reliable solution. As many engineers in production, development and research will testify, when you need a particular amplifier you need to deal with a company who can answer your queries and supply a working unit quickly. - CRIMSON will do exactly that!

We supply a standard range of power amplifier modules (both Bipolar and Mosfet) which can be incorporated in most systems from recording studios to home hi-fi or for more difficult loads such as induction loop transmitters, vibrators, servos and line transformers. For really complex applications, our technical department can usually supply a dedicated module on request.

All modules are guaranteed for two years and offer outstanding performance and value. If you would like more details please return the coupon with a s.a.e.

STANDARD MODULES

BI POLAR	TYPE	MAX. O/P POWER	SUPPLY TYPE	VOLTAGE		THD TYP.	PRICE INC. V.A.T. & POST.
				MAX.			
BI POLAR	CE 608	60W/8Ω	± 35	± 40	< .01%	£21.50	
	CE 1004	100W/4Ω	± 35	± 40	< .018%	£25.00	
	CE 1008	120W/8Ω	± 45	± 50	< .01%	£28.00	
	CE 1704	200W/4Ω	± 45	± 63	< .015%	£35.50	
	CE 1708	180W/8Ω	± 60	± 63	< .01%	£35.50	
	CE 3004	320W/4Ω	± 60	± 63	< .02%	£49.50	
MOS	FE 908	90W/8Ω	± 45	± 60	< .01%	£30.00	
	FE 1704	170W/4Ω	± 45	± 60	< .025%	£39.00	

All prices include V.A.T., Post and Packing (quantity discounts available).

To order send c.w.o. or quote Access/Mastercharge card no. All modules are available from Bradley Marshall Ltd., 325 Edgware Road, London. Export: Please write for a proforma.

Please send me details on -

- POWER AMPLIFIER MODULES
 HI FI KIT AMPLIFIERS
 19IN. RACK MOUNTING P.A. AMPLIFIERS

I enclose a S.A.E.

Name

Address

WW9/83

Send to: **Crimson ElektriK Stoke, Phoenix Works, 500 King Street, Longton, Stoke-on-Trent.**



CRIMSON ELEKTRIK STOKES
PHOENIX WORKS, 500 KING STREET, LONGTON
STOKE-ON-TRENT, STAFFS. - Tel: 0782 330520

LANGREX SUPPLIES LTD

Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

RST

Tel: 01-677 2424 Telex: 946708

RST

SEMICONDUCTORS

AA115 0.10	AA130 0.10	AA145 0.13	AA155 0.15	AA170 0.15	AA185 0.15	AA200 0.15	AA215 0.15	AA230 0.15	AA245 0.15	AA260 0.15	AA275 0.15	AA290 0.15	AA305 0.15	AA320 0.15	AA335 0.15	AA350 0.15	AA365 0.15	AA380 0.15	AA395 0.15	AA410 0.15	AA425 0.15	AA440 0.15	AA455 0.15	AA470 0.15	AA485 0.15	AA500 0.15	AA515 0.15	AA530 0.15	AA545 0.15	AA560 0.15	AA575 0.15	AA590 0.15	AA605 0.15	AA620 0.15	AA635 0.15	AA650 0.15	AA665 0.15	AA680 0.15	AA695 0.15	AA710 0.15	AA725 0.15	AA740 0.15	AA755 0.15	AA770 0.15	AA785 0.15	AA800 0.15	AA815 0.15	AA830 0.15	AA845 0.15	AA860 0.15	AA875 0.15	AA890 0.15	AA905 0.15	AA920 0.15	AA935 0.15	AA950 0.15	AA965 0.15	AA980 0.15	AA995 0.15
------------	------------	------------	------------	------------

VALVES

A1834 9.00	A2087 13.50	A2134 17.50	A2299 16.00	A2426 18.75	A2521 22.50	A2900 22.50	A3343 45.00	A331 2.75	A4241 2.60	BK448 114.90	BK484 58.00	B5452 60.00	B5810 60.00	B75 58.95	BT117 151.00	BT119 44.00	BT29 349.15	BT69 354.80	BT95 129.00	CB131 4.00	CL33 4.00	CY31 4.00	CLK 20.00	C3A 22.00	C3JA 22.00	DA41 25.00	DA42 18.70	DAF9 1.75	DAF96 1.75	DET22 35.00	DET24 49.00	DF91 1.75	DF96 1.75	DK91 1.75	DK92 1.75	DK96 1.75	DL92 2.00	DL94 1.75	DL96 1.75	DL98 1.75	DL99 1.75	DL10 1.75	DL15 1.75	DL16 1.75	DL17 1.75	DL18 1.75	DL19 1.75	DM70 2.00	DM71 2.00	DM160 4.75	DM87 1.50	DM92 2.00	E5L 22.00	E80C 8.81	E80F 13.58	E80L 13.37	E81C 8.00	E81L 12.57	E83C 8.10	E83E 8.40	E86C 8.25	E88C 8.25	E88CC 8.00	E89CC 8.61	E90F 9.90	E91H 6.25	E92CC 8.75	E99F 9.10	E130L 18.50	E180CC 10.50	E182CC 13.25	E186F 11.50	E188CC 8.25	E280F 22.51	E283CC 12.00	E288CC 17.50	EAS2 32.25	EAS7 2.25	EAB8C0 1.25	EAC91 3.50	EAF24 1.50	EAF800 2.00	EB41 4.00	EB91 1.50	EB93 2.50	EB94 2.50	EB95 1.50	EB96 1.50	EB97 1.50	EB98 1.50	EB99 1.50	EBF80 1.50	EBF83 1.75	EBF89 1.50	EBL31 4.00	EC90 1.25	EC91 1.25	EC92 1.75	EC157 325.40	EC33 4.50	EC35 4.50	EC36 4.50	EC37 4.50	EC38 1.75	EC39 1.75	EC40 1.75	EC677 1.75	EC678 1.
------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-----------	------------	--------------	-------------	-------------	-------------	-----------	--------------	-------------	-------------	-------------	-------------	------------	-----------	-----------	-----------	-----------	------------	------------	------------	-----------	------------	-------------	-------------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	------------	-----------	-----------	-----------	-----------	------------	------------	-----------	------------	-----------	-----------	-----------	-----------	------------	------------	-----------	-----------	------------	-----------	-------------	--------------	--------------	-------------	-------------	-------------	--------------	--------------	------------	-----------	-------------	------------	------------	-------------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	------------	------------	------------	------------	-----------	-----------	-----------	--------------	-----------	-----------	-----------	-----------	------------	------------	------------	------------	----------



MICROWAVE MODULES LTD

DO YOU HAVE A REQUIREMENT FOR VHF/UHF RECEIVERS OR TRANSMITTERS?

We have a comprehensive range of professional quality FM receiver and transmitter units, which can be supplied either as working printed circuit boards for inclusion as a sub-assembly in a more complex unit or as complete encased products, to operate in the frequency ranges: 130-180 MHz and 400-500 MHz.

UNIT TYPE	AR21	AR71
Description	VHF FM Receiver	UHF FM Receiver
Frequency Range	130-180 MHz	400-500 MHz
Number of Channels Available	2 (6ch also available)	2 (6ch also available)
Sensitivity	0.25µV P.D. for 20dB Sinad	
Selectivity	>80dB at ±25kHz	
Input Impedance	50 ohm	50 ohm
Audio Output Power	3 watts into 4 ohms	
Squealch Range	0.2-1.0µV	0.2-1.0µV
Supply Voltage	12.5 volts (11v min, 15.6v max)	
Current Consumption	50-600mA dependent on audio level	
Dimensions	135x123x26mm	

UNIT TYPE	AT25	AT75
Description	VHF FM Transmitter	UHF FM Transmitter
Frequency Range	130-180MHz	400-500MHz
Power Output	4 watts (normal) 0.5 watts (reduced)	2 watts (normal) 0.5 watts (reduced)
Output Impedance	50 ohm	50 ohm
Supply Voltage	12.5 volts (11v min, 15.6v max)	
Current Consumption	0.8 amps for 4w output 0.5 amps for 1w output	0.6 amps for 2w output 0.4 amps for 0.5w output
Dimensions	135x102x26mm	

UNIT TYPE	PRICE (exc. VAT)
AR21 VHF FM Receiver	£149
AR71 UHF FM Receiver	£177
AT25 VHF FM Transmitter	£84
AT75 UHF FM Transmitter	£110

The above items carry a 12 month guarantee, and we normally carry good stocks to ensure the minimum of delivery delays. If you have a requirement, or would be interested in quantity discounts, please contact our sales department.

MICROWAVE MODULES
BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND
Telephone: 051-523 4011 Telex: 628608 MICRO G

WW - 051 FOR FURTHER DETAILS

"Instruments for Industry"



This superb range of hand-held and bench multimeters offers a unique choice of 3½ or 4½ digit specifications and features. Engineering excellence at competitive prices with numerous supporting accessories to suit design, production and service needs. Now available ex-stock from one of the U.K.'s most experienced electrical measurement specialists. The complete range of Anders instruments and panel meters

is described in the "Instruments for Industry" catalogue.

For your personal copy contact:




ANDERS ELECTRONICS LIMITED
48-56 Bayham Place
London NW1 0EU
Tel: 01-387 9092. Telex: 27364

WW - 017 FOR FURTHER DETAILS

RADIOCODE CLOCKS SOLVE PROBLEMS

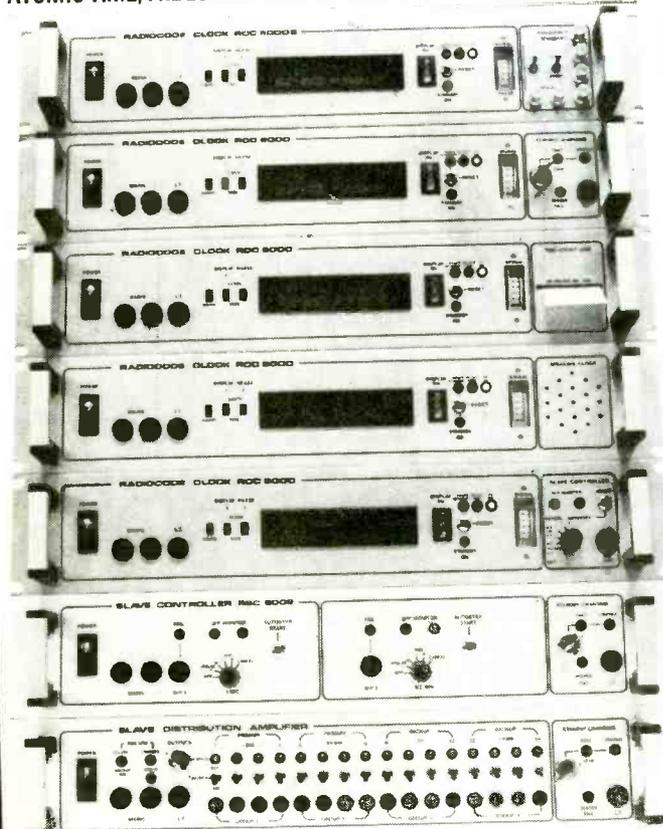ATOMIC TIME, FREQUENCY AND SYNCHRONISATION EQUIPMENT



NEW PHASE-MODULATION SYSTEMS

Until recently, atomic time and date information was only available on v.l.f. transmissions using amplitude modulation. The RCC 8000AM series of equipment uses these transmissions to offer high noise immunity and high accuracy, particularly at very long range.

The new RCC 8000PM series of equipment uses, for the first time, phase modulated transmissions with massive radiated powers of up to 2 Mega-Watts to offer long range, excellent noise immunity and no scheduled maintenance periods.

NEW PRODUCTS

The AM and PM series of Radiocode Clock equipment has been further expanded to include seven new models (from top) 8000S - combined clock, frequency standard and optional stopclock. **Internal standby power supply** - with dual rate constant current charger. **Time-event log** - prints hours, minutes, seconds, milliseconds and day of year, on receipt of a log pulse. **Speaking clock** - time announcement or audio recording. **Slave controller** - total control of single-standard master/slave systems ie one pulse/sec. **Dual standard slave controller** - total control of two different and independent slave systems, ie. one pulse/sec and one pulse/half min. **Slave distribution amplifier** - maximum flexibility for the largest master/slave installations requiring dual standard operation, multiple circuits and complete master/slave backup.

NEW OPTIONS

A continuously expanding range of fully integrated software and hardware is available for both series of Radiocode Clock equipment. Standard options now include:


- IRIG B precision serial o/p
- RS232/V24 1mS resolution
- General purpose parallel o/p
- FSK record/replay system
- Keypad entry of alarm times
- Keypad entry of time/date
- Time code generators
- Intelligent slave systems
- Standard frequency outputs
- Stopclock operation
- Calibrated systems for increased accuracy

Radiocode Clocks Ltd*
Unit 19, Parkengue, Kernick Road Industrial Estate
Penryn, Falmouth, Cornwall. Tel: Falmouth (0326) 76007
(*A Circuit Services Associate Co.)

WW - 047 FOR FURTHER DE? ILS

AMATEUR WIRELESS BEFORE 1914

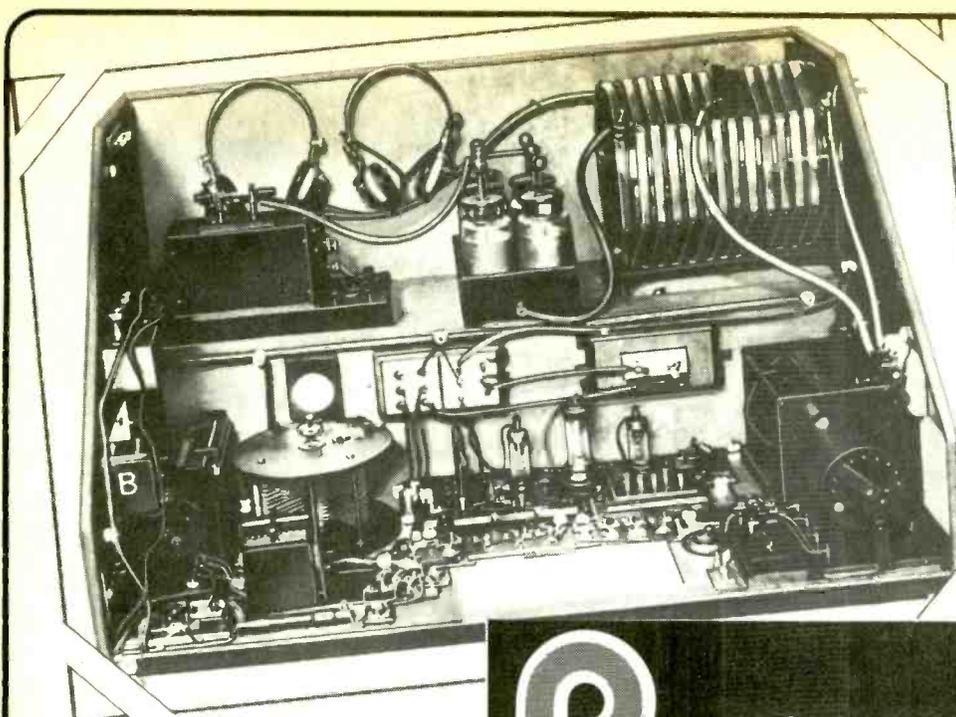George Jessop G6JP begins a nostalgic look at the hobby in the days when you not only built your own equipment, you had to make most of the components too.



SEPTEMBER ISSUE 90p

Practical Wireless

ON SALE NOW THE RADIO MAGAZINE

Basic QSOs in Spanish

How to talk to Spanish-speaking amateurs in their own language.

Ring-Beam Antenna for 144 MHz

A new design by F. C. Judd G2BCX, giving 8dB gain over a dipole with a very clean radiation pattern

The Wings Appeal Fund helps to maintain the RAF Association Home for Disabled and Chronic Sick. Care is essential for those who have served their country and who are in need. So please help by giving all you can for an emblem in WINGS WEEK in September or send a donation to show that you care.



Give as they Gave



Space donated by
Wireless World

To: Royal Air Forces Association,
Appeals Dept., (DS) Portland Rd.,
Malvern, Worcs. WR14 2TA.

I enclose a donation of _____
for the Wings Appeal Fund.

Name _____

Address _____

Please tick if receipt required
or information on RAFA
Membership

CLEF ELECTRONIC MUSIC

PIANOS



SPECIALISTS SINCE 1972
DOMESTIC OR STAGE
SIX OR 7¼ OCTAVES
KITS OR MANUFACTURED

The most advanced form of touch-sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

Component Kits include Keyboard.

Full Kits further contain: Cabinets, Harness, Power Amp and Speaker.

DOMESTIC PRICES

£	SIX	7¼
Comp	234	266
Full	398	442
MFD	620	695



VOCAL & INSTRUMENTAL SOLOISTS!

MASTER RHYTHM DRUM MACHINE
User Programmable
Twenty-four patterns.
Eight parallel tracks.
Twelve instruments sequence operation.

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr., & ins, and we operate Telephone BARCLAY-CARD/ACCESS. Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED

Dept. W, 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 043 FOR FURTHER DETAILS

RADFORD

Audio Measuring Instruments,
Audio Amplifiers, Loudspeakers and
Loudspeaker Components for the
professional and enthusiast

RADFORD AUDIO LTD.
10 BEACH ROAD
WESTON-S-MARE, AVON BS23 2AU
TEL. 0934 416033

WW - 011 FOR FURTHER DETAILS

HEMMINGS ELECTRONICS AND MICROCOMPUTERS

16 BRAND ST
HITCHIN
HERTS
SG5 1JE

Tel: (0462) 33031
Shop open Mon.-Sat. 9 a.m.-5.30 p.m.
Closed all day Wednesday



Professional quality electronic components, brand new and fully guaranteed. Mail order by return of post. Cash/Cheque/POs or Banker's Draft with order, payable to Hemmings Electronics Ltd. Official orders from schools, colleges and universities welcome. Trade and export enquiry welcome. P.&P. add 45p to all orders under £10. Telephone your Access orders, using our 24-hr. Ansaphone service. Please send SAE for full price list.

VAT - All prices exclusive of VAT - Please add 15% to total cost including P.&P. No VAT on export orders or books.

COMPUTER ICs	MEMORIES	CRYSTALS
6502 350p	Static RAM	32.768KHz 100p 6.000MHz 180p
6522 340p	2114L-200nS	1.000MHz 320p 6.1440MHz 180p
6800 290p	6116P3-150nS	3.432MHz 240p 6.880MHz 240p
6800A 450p	390p	2.000MHz 225p 8.000MHz 160p
6802 345p	6116LP3-150nS	2.4576MHz 225p 10.000MHz 170p
6805 845p	450p	3.000MHz 240p 16.000MHz 190p
6809 1350p	Dynamic RAM	3.5795MHz 120p 18.432MHz 150p
6809E 1295p	4116-200nS	3.884MHz 240p 19.660MHz 240p
6810 120p	75p	4.000MHz 150p 20.000MHz 200p
6821 160p	4164-200nS	4.194MHz 190p 27.000MHz 170p
6821A 215p	450p	5.0688MHz 240p 48.000MHz 170p
6840 390p		
68B40 580p		
6844 1295p		
6845 795p		
6850 140p		
6852 250p		
6854 680p		
6875 490p		
8126A 120p		
8128 120p		
8195 90p		
8196 90p		
8197 90p		
8198 90p		
8035L 340p		
8039L 290p		
8080A 360p		
8085A 450p		
8155 450p		
8212 155p		
8216 100p		
8224 160p		
8226 195p		
8228 250p		
8251 300p		
8253 450p		
8255 280p		
8257 450p		
8259 450p		
8279 450p		
75107 90p		
75108 90p		
75110 88p		
75112 160p		
75182 95p		
75450 85p		
75451 50p		
75452 50p		
75453 72p		
75461 40p		
75491 70p		
75492 70p		
AY-3-1015D 300p		
AY-5-1013A 300p		
MC1408 295p		
MC1488 55p		
MC1489 55p		
MC3455 265p		
UPD7002 450p		
Z80ACPU 350p		
Z80APIO 300p		
Z80ACTC 300p		
Z80ADART 750p		

COMPUTER ICs	MEMORIES	CRYSTALS
2 x 15V at 100mA		
2 x 20V at 67mA		
6VA 2 x 6V at 500mA		
2 x 12V at 250mA		
2 x 15V at 250mA		
2 x 20V at 150mA		
		275p

CHASSIS MOUNTING

6-0-6V at 100mA	120p
9-0-9V at 100mA	125p
12-0-12V at 100mA	145p
15-0-15V at 0.5A	350p
9-0-9V at 1A	270p
12-0-12V at 1A	320p
15-0-15V at 1A	395p
30-0-30V at 0.5A	395p

PCB TRANSFERS
Make your own Printed Circuit Boards with Alflec Etch Resist PCB Transfers

- ★ Draw your artwork on 0.1" grid
- ★ Transfer to copper board using carbon paper
- ★ Burnish the Alflec transfers to the board using a spatula using carbon marks to assist in accurate alignment
- ★ Use Alflec chemical eraser to correct mistakes
- ★ Etch in Ferric Chloride

★ EPSON FX-80 ★
We now have in stock the new Epson printer, the FX-80, which replaces the MX80 F/T III. If you thought the MX80 was good, you will agree that the FX-80 is brilliant. All the MX80 features are there plus the following extras:

- ★ 160 cps print speed
- ★ 80 cps special quiet mode
- ★ Prole character set which can be downloaded from your computer
- ★ 9 different bit image modes up to 1920 dots per line
- ★ Print styles emphasised, condensed, proportional, elite, italic and all MX80 styles
- ★ Program control of skip-over perforation, number of columns, character sets
- ★ Fully compatible with MX80 control codes

£395 + VAT SECURICOR £8

PRINCE MONITOR
A 12" monochrome monitor 24MHz video bandwidth ideal for most personal computers, word processing, scientific work etc.

INPUT VIDEO
1 volt p composite video

INTERNAL CONTROLS
Contrast, brightness, vertical hold, on/off

INTERNAL CONTROLS
Horizontal width, linearity, frequency, phase, focus, black level, vertical height and linearity

TECHNICAL CHARACTERISTICS
Scan 625 lines/50Hz, Deflection 110°, Character display 80 by 24 lines, Video input PHONO, X-ray radiation to IEC spec no 65

SCREEN PHOSPHORS
Black/white, green, or orange Green or orange filters available to order

£98 + VAT SECURICOR £8

THE COMMODORE 64
MEMORY SIZE
System memory 20K ROM 3K RAM
User area 38K RAM or 54K If BASIC Interpreter is not used

SCREEN DISPLAY
Full colour display 25 by 40
25 combinations of screen and border colours
16 Text/Character colours displaying alphanumerics or PET graphics

Connection to a TV set or a colour or monochrome monitor UHF modulator internal to the computer

GRAPHICS
High resolution graphics 320 x 200 pixels
62 predefined graphic symbols available from the keyboard displayed in normal or reverse in all 16 colours

SPRITE GRAPHICS
High resolution moveable object blocks 24 pixels wide by 21 pixels deep
Up to 8 Sprites which can be layered for 3D effects
Sprites can be one of 8 colours or multicolour up to 4 different colours in one sprite
Sprites can be moved independent of text, graphics or other Sprites

SOUND
Music Synthesis chip provides 3 voices, 8 octaves 4 waveforms - sawtooth, triangle, pulse or noise
Programmable attack, decay, sustain and release
Programmable filter - low pass, band pass, high pass or notch outputs
Variable resonance and master volume control

INPUT/OUTPUT
User port with RS232C
Cartridge port for games and ROM based software
2 joystick/paddle/light pen ports

LANGUAGE
BASIC interpreter future options are BASIC, Pascal, COMAL, LOGO and FORTH

TEMPERATURE METER
A fully self-contained digital temperature meter, battery operated with an LCD display

- ★ Temperature range 0-99.9°C
- ★ Accuracy 0.40°C +/- 0.2°C
- ★ 40.70°C +/- 0.4°C
- ★ 70.99.9°C +/- 1.0°C
- ★ Battery 9v alkaline. Lifetime approx. 1 year
- ★ External temperature probe

£19.95

TRANSFORMERS
PCB MOUNTING TYPE
All types have dual primaries of 0.120, 0.120 or inputs of 120V or 240V - Primary and Secondary wound on a Split Bobbin providing superior Isolation

3VA 2 x 6V at 250mA
2 x 12V at 125mA

NOW ONLY £199 + VAT SECURICOR £8

The Keithley 179A



NEW!

A MEASURE OF ACHIEVEMENT.

Specification... Versatility... Accuracy... Price. In almost every major area the new 179A - a 4 1/2 digit bench/portable DMM - from Keithley Instruments sets some pretty impressive standards:

- 20 amp capability
- Full function: 27 ranges including true RMS AC Measurement
- Year's guarantee on spec
- 0.04% DC accuracy
- IEEE option
- Large display and 10µV dc resolution.

For those requiring 10 times more sensitivity and an analogue output there's the 177, a unit with similar specification to the 179A. Both models are part of a vast range of test equipment from one of the world's leading manufacturers. For more information fill in the coupon at the bottom of the page.

Alternatively, phone our Instant Information Service on 0734 861287 now.

KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047



I'd like to know more...

Name _____

Position _____

Company _____

Address _____


Telephone _____

WW/9

WW - 008 FOR FURTHER DETAILS

WW - 053 FOR FURTHER DETAILS

Test it on Test on Site

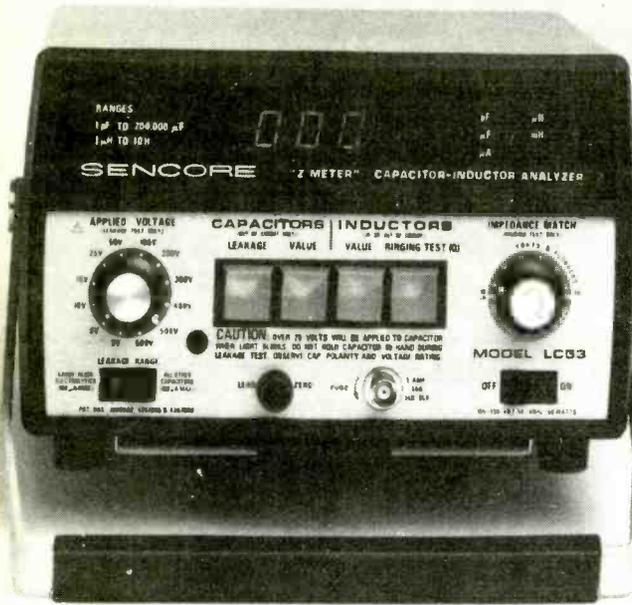

The "Z Meter" capacitor-inductor Analyser, from Sencore, now gives you the fastest, most accurate means of batch testing even from semi-skilled operators — **and we're prepared to come round and prove it.**

For an on-site test and more information:-
Mike Dawson 01-897 6446.




**Fieldtech
Heathrow**

Fieldtech Heathrow Limited
Huntavia House 420 Bath Road
Longford Middlesex UB7 0LL
Telex: 23734 FLDTEC G

WW - 015 FOR FURTHER DETAILS

PROVED IN SERVICE THROUGHOUT THE WORLD EDDYSTONE MODEL 1837/2

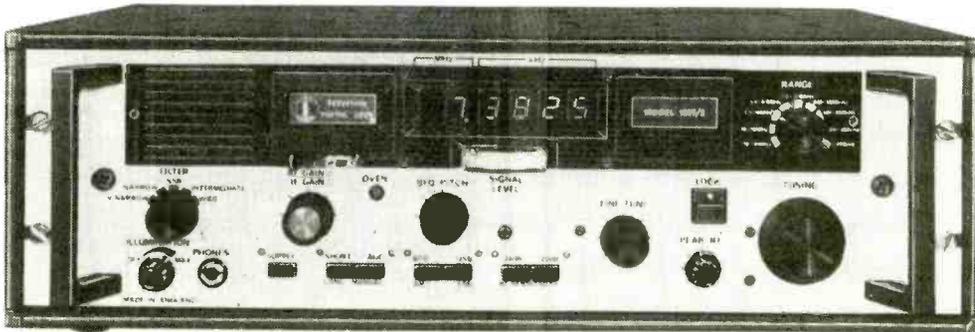LOW COST, HIGH STABILITY COMMUNICATIONS RECEIVER 100kHz to 30MHz



- * Capable of operation under the most stringent conditions of service, professional and military
- * Manual tuning plus accurate digital frequency readout and high stability working with Eddystone patent digital lock

- * Complies fully with MPT Specifications 1201, and 1204: CEPT Draft Recommendations and DEF 133/L2
- * Provides inexpensive teleprinter terminal when fitted with Model 1529 FSK Unit

Details on request

Eddystone Radio Limited

Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England
Telephone: 021-475 2231 Telex: 337081

60 YEARS OF
DEPENDABLE
SERVICE
1923 - 1983



WW - 038 FOR FURTHER DETAILS

Editor:

PHILIP DARRINGTON
01-661 3128

Deputy Editor:

GEOFFREY SHORTER, B.Sc.
01-661 8639

Technical Editor:

MARTIN ECCLES
01-661 8638

Projects Editor:

RICHARD LAMBLEY
01-661 3039

News Editor:

DAVID SCOBIE
01-661 8632

Drawing Office Manager:

ROGER GOODMAN
01-661 8690

Technical Illustrator:

BETTY PALMER

Advertisement Manager:

BOB NIBBS, A.C.I.I.
01-661 3130

BARBARA MILLER
01-661 8640

Northern Sales:

HARRY AIKEN
061-872 8861

Midland Sales:

BASIL MCGOWAN
021-356 4838

Classified Manager:

BRIAN DURRANT
01-661 3106

IAN FAUX

01-661 3033

Production:

BRIAN BANNISTER
(Make-up and copy)
01-661 8648

Publishing Director

DAVID MONTGOMERY
01-661 3241

Technology and people

As has perhaps been mentioned before on this page, it can be extremely dispiriting to take stock of society's scale of values, particularly when technology is the subject for discussion. Offensive weaponry, expensive trivia and the means to dispense one-way 'communications' constitute the overwhelming majority of applications in the field of electronics while other, more pressing, needs go unattended.

All the more encouraging, then, to report work which is supportive rather than sinister and which is designed to assist instead of to anaesthetize. In this issue, R. E. Young writes of his investigations into the alleviation of mental handicap by the breaking down of the communications barrier which is one of the symptoms of hyper-autism — the 'shell', as it has been called. The work stems from enquiries into human behaviour during unexpected emergencies,* in which people can exhibit some of the characteristics of mental handicap.

The use of technology to gain an insight into the ways in which humans operate and to alleviate abnormalities in behaviour illustrates the similarities between electronics and the human mind — if that is the word to use. It is possible that the similarities are contrived because we work in electronics and tend to think of most processes in electronic terms, but the

correlation is quite marked. Young refers to "gating interfaces", "delay time", "inversion" and the blocking effect caused by the accumulation of too much data for a handicapped person to accept, sort and act upon.

Whatever the connexion, it is evident that even the most severely handicapped autistic has a latent capability and can be assisted to break the shell by a deeply understanding approach — one which recognises that communication is the basic problem and that removal of stress and help in carrying out even simple actions to achieve some kind of pride in performance are beneficial, particularly when previously considered to be impossible.

Electronics and other technologies can be of great and increasing help to workers in this field, since the similarities between the mind and electronic systems enable the patient to be included in a system, so that small irregularities in behaviour can be discovered in a reasonable time. Simple, continuous observation of behaviour is not of great value, since irregularities must be encouraged by conditions, and detection must be certain.

One of the most remarkable aspects of this research is the persistence shown in the face of disbelief, and the insight to recognise the 'concealed person' on the basis of extremely slight evidence — some of it offered diffidently for fear of ridicule. This is an important and humanitarian application of engineering skill and deserves ultimate success.

* Crisis control, R. E. Young, WW June, July, 1982

Better batteries

There can be few areas of more consequence to the future progress of portable communications, lightweight television production equipment and consumer-electronics equipment than the development of higher-density and/or more cost-effective batteries. Current progress is reported from the USA on the standard carbon-zinc cell, including the use of a zinc chloride electrolyte and oxidation-resistant coated-paper separator, (according to Ralph Brodd of Broddays Inc.) that is claimed, at low and medium drain over protracted periods, to provide performance comparable to the considerably more expensive alkaline cells. For low-power consumption over very short periods in microminiature applications, mercury-zinc and mercury-silver cells offer extremely high efficiency, but recent zinc-air button-cells are claimed to offer much higher power densities, of up to 15 watts per cubic inch. A disadvantage of the zinc-air button-cell is a life limited to about one month, due to continuous energy consumption once it has been put into use.

The rechargeable lead-acid cell appears to be gaining renewed interest for use in portable equipment as a result of the development of new forms of sealed, maintenance-free batteries, in addition to the older jelly-acid ("gel") cells: in some recent "flooded" designs the electrolyte is soaked in porous pads. With these starved acid-lead cells there is no emission of gases or acid, as oxygen released from the positive plate when the cell is overcharged reacts at the negative plate to reform water.

Layer batteries. In the 1930s there was a widespread belief that a long-lasting match had been invented, but that the match-box firms had brought up the patent and blocked production. I have no idea whether there was any foundation for this story, though it circulated widely. In "The Secret War of Charles Fraser-Smith" (Michael Joseph, 1981) a somewhat similar anecdote appears relating to improved dry batteries.

Charles Fraser-Smith, as an official in the wartime Ministry of Supply, was responsible for obtaining a wide variety of items for use by the intelligence, escape and special operations organizations. One of his tasks was to acquire miniature radio receivers that could be smuggled into the prisoner-of-war camps, so that morale could be raised by reception of news from Allied radio stations (though the news in the first few years could seldom have done much for morale!).

For this purpose he arranged for the production of some miniature receivers but encountered a "distinct lack of enthusiasm" when he approached the management of a large battery firm seeking more

compact, longer-life batteries. He was told firmly that this was "not feasible". However when he later met the firm's chief engineer the immediate response was that this could certainly be done, with an improvement of about three-to-one on existing batteries. The book claims that when the management heard what had been promised one of them remarked "Don't let on to the Board of Trade. . . . If these ever get on to the regular market we'd lose a fortune . . . customers would need only one in place of three ordinary ones. And they cost about the same." What emerged was a battery of layer-type construction instead of the former round-cell h.t. batteries! These did reach the public post-war, but initially in the USA.

Polarization modulation?

In one of the now traditional "April Fool" articles in a recent amateur radio magazine, an elaborate spoof was based on a complex "polarization modulation" technique. However this reminded a reader, Eric Harman of the IBA, that back in 1968, Mark Epstein of the Radioscience Laboratory of Stanford University published a report of experiments in "communication by polarization modulation" (*Proc. IEEE*, June 1968, pp.1114-5) in which he suggested that channel capacity on h.f. could be doubled by the use of antennas that launch and receive waves whose polarizations correspond to the limiting polarizations of the magneto-ionic modes.

Experimental results over a 1900-km path from Lubbock, Texas to Stanford, California using signals switched alternately between left-hand and right-hand circular polarization showed a better than 15dB separation on one-hop signals. This suggested to Epstein the possibility of increasing channel capacity by modulating the transmitted wave polarization of existing on-off and f.s.k. telegraphy systems — two communications channels instead of one. That was 15 years ago but there seems to have been little follow up to this system — except as the basis of the April Fool article! Polarization diversity is an established h.f. technique, as is the use of mixed polarization to combat fading due to Faraday rotation — so why not polarization modulation?

III-V semiconductors

Further developments in III-V semiconductor technology have been reported from the Central Research Laboratories of Thomson-CSF. Following work on indiumphosphide (InP) metal semiconductor field-effect-transistors (InP mesfets) for microwave power amplification, the laboratories have recently produced de-

vices in which the gate is insulated by a silicon-oxide (SiO₂) layer. The InP misfet devices have achieved power outputs at 9GHz with 4dB gain of up to 1 watt, representing 3.5W/mm power per unit gate width, or roughly double that achieved with experimental gallium arsenide mesfet devices. The laboratory has also proposed a new form of GaAs enhancement-mode transistor with metal-insulated-metal gate. It is claimed that mim-gate fets would combine the advantages of both GaAs mesfet and GaAs misfet devices. Experimental devices have shown an enhancement current handing capability double that of more conventional mesfet devices.

Meteor aero-radio

Last April we noted the growing interest in the USA in meteor-trail communications for civilian as well as for secure military systems. The large number of meteors that enter the earth's atmosphere create short-lived ionized trails roughly 70 miles above earth. With computer-controlled high-speed burst transmissions it is possible to sustain teleprinter traffic at roughly normal speed, provided that the link is not required to provide instant access.

R. E. Martin of Guildford has pointed out that a good deal of work into extending the use of meteor-scatter systems has also been carried out in the UK, both for the NATO military systems and with a view to specialized civilian systems. Last year, at ICAP2, Dr H.P. Williams noted the potentiality of meteor-trail systems for medium-distance links over distances of up to about 2000km, using high frequencies when these are above the m.u.f. and therefore under-utilized. Dr Williams' paper (briefly noted on this page in July, 1982) pointed out that frequencies as low as 14 MHz or so can be used for these systems.

R. E. Martin points out that meteor-trail systems appear most attractive for providing, for example, economical r.t.t.y. networks for administrative purposes for power authorities, especially in developing countries. In such places there are often only inadequate PTT networks and distances of one or two-thousand kilometres are frequently involved. Provided that short delays are acceptable and speech communication is not required, the meteor systems have the cost advantage of not requiring any costly powered microwave repeater sites, can utilize low v.h.f. (or even above-the-m.u.f. h.f.) and do not encounter so many of the usual problems in obtaining frequencies.

R. E. Martin also draws attention to one of the curiosities of meteor communications — the greater number of meteors that enter the atmosphere in the morning than in the evening, due to the effect of the rotation of the Earth.

COMMENTARY

This point has also been noted in the investigations into meteor-scatter currently being made at the Royal Aircraft Establishment with a view to the use of meteor-trails for air-ground communication, as first suggested by A. J. Hannum *et al* (*IRE Trans. Com. Syst.* vol. 8, pp.113-133) in 1960. In a paper ("Meteor scatter communication in an air-ground environment") given at ICAP3, P.S. Cannon and G. Richardson of RAE note that the arrival rate is random with a 4:1 variation between the maximum in August (a "shower" period) and minimum in February. There is also a 4:1 variation between a maximum at around 0600 local time and a minimum at 1800 local time. Unlike amateur-radio use of meteor-scatter, which usually seeks to use only the longer-lasting "over-dense" trails created by the larger particles, commercial/military burst systems utilize the underdense trails which provide scattered signals that are "remarkably space and time-coherent", and are affected by the local time variations.

The RAE experiments have been based on an h.f. (27MHz) link between Kinloss, Scotland and Farnborough, Hampshire — a ground path length of 712km, with path losses of about 178dB, and a median "waiting time" of two seconds. The 27MHz frequency was chosen because of equipment available but future work is to concentrate on v.h.f. where less interference is likely. Cannon and Richardson conclude that the close correspondence between predicted and experimental results for a ground-to-ground link provides confidence in the prediction equations; they note however that the design of an airborne meteor-scatter system will be more difficult than, and different from, a ground-based system. Aircraft-to-ground communication is expected to be easier than ground-to-air; Faraday rotation of polarization is foreseen as a problem.

AMATEUR RADIO

Spiralling up

The cost to UK radio amateurs of "top-of-the-market" American and Japanese amateur-radio equipment has been rising at many times the official "inflation rate" due to the changes in the exchange rates, and the frequent up-dating of designs to include more and more "new technology".

Nowadays retailers and distributors, particularly in the USA, are increasingly coy about publishing prices, with list prices often heavily discounted. However a quick check shows that the top-grade Collins KW380 h.f. transceiver is now likely to cost a British purchaser almost £2200

compared with about £1600 a year ago — an increase of around 30 per cent. The comparative price in the USA (without vat) is around \$2850. The Drake TR7A transceiver is about £1200 in the UK, under \$1400 in the USA, whereas a year ago the earlier TR7 model, with power supply unit, could be bought new in the UK for under £1000. Japanese equipment prices have risen less steeply but are some 12-15% higher than at this time last year: the Yaesu FT-One, for example, has gone from just under £1300 to about £1450. There are signs that the present high cost of top-grade h.f. equipment is depressing demand despite the continued rise in the number of British licences. A more welcome change is the number of home-construction projects now appearing, although it is recognised that an h.f. transceiver design fully equivalent to the top factory models represents a major project beyond the capabilities of most home constructors. Although all-solid-state linear power amplifiers of up to about 1 kW rating are now possible using modules based on either bipolar or power mosfet devices, there still appears to be a cost differential of at least two-to-one on the higher power units in favour of valve amplifiers. The solid-state models base their appeal primarily on being wideband designs permitting band-changing without retuning. Also appearing are increasing numbers of aerial tuning or matching units with automatic tuning, but here again it is clear that operating convenience costs real money.

R.f radiation

Not all doubts surrounding possible behavioural ("non-thermal") effects of r.f. radiation have disappeared despite repeated efforts by the National Radiological Protection Board to stress that the only proven hazards of non-ionizing radiation are thermal, and that the safety limit of 10mW/cm² is entirely adequate. The consultative document issued by NRPB in December 1982 proposes a reduced limit of 1mW/cm² between 30 and 100MHz, where dipole resonances of the body reduce the safety factor. It even accepts that "an auditory effect occurs for some individuals when exposed to intense and sharp pulses of microwave radiation" but adds that "there appear to be no harmful effects resulting from this phenomenon".

At ICAP3 last April, however, Leonard S. Taylor of the department of electrical engineering and radiation oncology of the University of Maryland devoted part of his paper on "Therapeutic applications of electromagnetic radiation" to a balanced appraisal of conflicting views on whether long-term exposure to very low-level microwave radiation can be harmful. In doing so he presented a viewpoint significantly different from that of NRPB, although he accepts that "the significance of much of the experimental evidence is ques-

tionable". He notes the evidence of increased calcium ion efflux both *in vitro* and *in vivo* chick and cat brain tissues at levels down to 0.05mW/cm² and considers this substantiates the influence of u.h.f. and microwave fields on the brain-cell microenvironment.

Here and there

Apart from the Syledis and Maxiran position-locating radio-navigational systems, the 430 to 440 MHz amateur band (with its "secondary" status in the UK) appears to be coming under increasing pressure from other users, including the Ministry of Defence. MoD have established a radio-communications network ("Mould") connected with civil defence between 433.0 and 433.5MHz. There have also been unconfirmed rumours that the Belgian authorities have reduced their amateur allocation to 435 to 439MHz and closed all microwave bands to Belgian amateurs.

By the time these notes appear, the Oscar 10 satellite, the first of the Phase 3 series, launched last June, should be in its final high orbit. The apogee motors were due to be fired about July 14. An early problem with the solar array also needs to be overcome or Oscar 10 could have an operational life of only a few months. The c.w. beacon is on 145.81MHz.

In brief

The RRL membership has confirmed overwhelming opposition to code-free licences even on v.h.f. bands. . . . At the annual Dayton, Ohio convention two operators were able to read Morse at 68 words per minute, 4 word/min short of Ted McElroy's pre-war "world record" of 72 word/min. . . . A draft new constitution for the International Amateur Radio Union was drawn up at an Administrative Council meeting in Tokyo and is to be further considered at a second meeting later this year. . . . A "wireless museum" in Orkney features radio communications equipment of World War 2 as used by the Services in Orkney during that period. Research and restoration was carried out by James McDonald, GM88FG. . . . New Zealand amateurs have made a 545km contact on 3.4GHz between Cape Reinga (North Island) and Mount Egmont using one-watt output and 4 ft dish aerials. . . . Since May 22, American phone allocations in the 14MHz have extended down to 14,150kHz with 14,150 to 14,175kHz reserved for "extra class" licences 14,175 to 14,225kHz reserved for "advanced" and "extra" licences. . . . The Scottish Amateur Radio Convention is to be held on August 27 at Cardonald College, Mossbank, Glasgow followed by a dinner/dance at the Bellahouston Hotel. . . . The Welsh Amateur Radio Convention is at Oakdale Community College, Blackwood on September 25.

PAT HAWKER, G3VA

Mental handicap and electronics

Stemming from enquiries into human behaviour during unexpected emergencies – reported in the author's previous Crisis Control article – R. E. Young writes of his investigations into the alleviation of the communication breakdown of hyperautism with the help of electronic systems, and proposes a new specialized mental handicap unit.

What was little more than an abstract idea has been taken to a development-backed set of proposals for setting up an operational complex. A project that grew on an ever-increasing scale from its mental-handicap base to make contributions in other fields, both humanitarian and technological, and in its own right, progressed towards the establishment of a research-based care unit for the severely handicapped¹. The aims of this unit are firstly to arrest the deterioration (regression) which is almost without exception taken to be inevitable with these 'most disadvantaged' people; and secondly to proceed to rehabilitation, with their development continuing from within.

In view of the picture of mental handicap presented by the media it would seem that to attempt to stop the retreat into the isolation of the blank-look shell of non-talker is just not 'on', still less 'on' is any effort to reverse the trend. Nevertheless, these things have been done, albeit on a limited basis. In the two-part article in *Wireless World*, where mental handicap was linked with the stress conditions of crisis control², a brief outline was given of some of the methods adopted to bring-out the handicapped and, in particular, to help them to communicate from within. This question of communication is vital, and, as shown on the flow chart (phase 3) the statement of mental handicap being in essence a communication problem constituted the beginning of a defined research programme on the disability.

This does not mean that the work of phases 1 and 2 was not research nor that it was relatively unimportant. In the event, the development of the main project has demonstrated how far-reaching this earlier work has proved to be. Primarily it brought out the fact that there were people in the UK and other countries, notably Australia, who – by virtue of their own thinking and observation – held the conviction that "something was there" with even the most severely handicapped. Two major points emerged during this period.

- These people were almost invariably widely separated from one another (i.e. were isolated), and in general were surrounded by quite understandable scepticism. Despite these and other adverse factors, they had persisted in their be-

by R. E. Young

B.Sc. (Eng.), F.I.E.E., M.R.Ae.S.

lief; and the importance of this cannot be over-emphasized, especially in relation to the almost insuperable difficulties of building-up any real observational data on mental handicap (see next section).

- Not only had this observational data to be gathered purely on a human basis, but it also had to be expressed in these human terms.

The full implications of this statement do not become clear until one looks at the circumstances surrounding these potential 'witnesses'. First, because of their isolation and the difficulty of putting words to phenomena which very often they had seen only fleetingly, 'data acquisition' could not be carried out by direct questioning. It had to be a matter of establishing contact in some way, a problem in itself, and then almost literally waiting for the information to 'come out'. The other, much more obstructive, aspect was the natural reticence to talk about something which was almost totally intangible and in addition was surrounded by incredulity. An associate of some years' standing – and responsible for the highly descriptive name of 'false handicap' – recently admitted that he had had moments of doubt – "have I got it wrong?" when thinking over some manifestation he had seen of the person behind the handicap.

Another major obstacle was the 'set-back' of regression which is so easily brought about without the cause being obvious; and which, unless countered, made positive observation impossible.

But this basic information *did* emerge from these early activities, and it says much for the 'quality' (and even more for those who produced it) that the resulting statements remain, in effect, as some of the guidelines in the proposals for the unit. Furthermore, the point was reached where, as indicated for phase 3, it appeared possible to attempt to make an attack on mental handicap from an entirely new base.

The position at the end of phase 1 was that considerable insight had been gained

into this "most mysterious of all human complaints"; but that the evidence would remain intangible until, as a minimum, a "language" (technical vocabulary) had been evolved to enable some of the features of the disability to be identified and consequently described. In yet other words produced at the time: "If we had something to get hold of we could at least talk about it."

This was one of the first occasions on which it was possible to combine the 'thinking' from independent sources and to link this with the technological approach to the problem which had begun to take shape and which was eventually to form part of the 'human electronics' around which the remainder of this article is centred.

Human electronics

The term system modelling and hyper-austistic effects such as 'delay time', and distortion of speech by 'inversion', are representative of the technical vocabulary shown as being developed in phase 3; but the outstanding importance of them is that they had been predicted from the results of system modelling. In one sense this process came into being with the development of the concept of mental handicap being a communication engineering problem; and which, in common with others of these concepts, was introduced initially as a form of extended working hypothesis. But it soon became evident that the 'communication approach' was opening up other lines of attack which could be linked with the observations of phases 1 and 2; and, not only reinforced them but – most significantly – began to explain them. Thus it was in the context of electronically-based communication that 'clutter' – as a new concept – was developed.

Clutter, with the definitions it carried, provided an important bridge between electronic technologists and those who were looking for 'something to get hold of' in the intangibility of mental handicap. It was, however, the 'human electronics' contribution that was then built up which produced the full electronic approach and which has been recognized by non-technologists as virtually the only way in which the 'deceptive' nature of mental handicap could have been overcome, certainly within an acceptable time. Full tribute must be paid to the medical authorities

Human electronics – project flow chart for mental handicap

Taken up to the point of publication of the proposals for a new 'Research Care Unit' for the mentally handicapped

	Phase 1 Build-up of observational data	Phase 2 'Enlarging the view'	Phase 3 Establishing technological base (essentially electronic)	Phase 4 Statement of areas of research	Phase 5 Development and assessment of specialised techniques
Direct Project Action	Making contact with 'witnesses'	Bringing-in 'associates' outside the immediate field	Statement of main concepts, initially 'a communication problem'	Identification of electronic-type 'mechanisms' involved, including 'system modelling'	Construction of electronically-based equipment, and trials under 'research care' conditions
			Developing original 'technical' vocabulary and overall picture	Full coordination of this work and all observational results	Expansion of main concepts, production of integrating reports
Indirect Project Action	Analysis of 'Human' position	Feed-in of 'human' aspect into direct project	First – largely exploratory – publications in the press	Correlation with 'outside' areas e.g. deafness and geriatric care	Extension of correlation to other fields, particularly with 'crisis control'; and with maximum two- way 'spin-off' flow Second – selective publications in the press

who, despite all these difficulties, had set up the facilities which already existed in the UK. That the 'new thinking' has been made possible – and has taken place – is largely by virtue of the environment so soundly established by these authorities in the past.

The human electronics has been described, again by a non-technologist, as providing the equivalent of a "... microscope on mental handicap". System modelling is shown on the project flow chart (phase 4) as being concerned with the "identification of (electronic-type) mechanisms" involved in such effects as 'thinking fatigue' and 'delay in response'. Although system modelling does not appear on the chart until phase 4, investigation and analysis of this kind had been going on during the earlier phases. It was not until phase 4 that sufficient correlation of the information has been obtained for this process to be regarded as a 'firm' section of the work.

Examples of these early findings included the identification of (telegraph-type) 'start-stop' working and 'thinking fatigue'. The first-mentioned has been selected to show how a comparatively minor point was made to yield confirmatory and other information for application in the main programme. First, the underlying principle is simple: for communication, the transmission of a message entails the sending of a start alerting signal and of a corresponding stop signal for 'end of message'. It was found that a similar practice could be useful in certain circumstances when communicating verbally with the severely handicapped; and this information was fed in to, and coordinated with, the other data which was beginning to give a picture of some of the elements entering the hyper-autistic condition. Also

it had been possible, even at the stage, to "separate-out" some of the factors involved in the hyper-autistic state; and, as such an identified factor, 'start-stop' brought clarification both in itself and in respect of other effects as exemplified by the various aspects of clutter.

It will be realized that the work heavily depended on observation, and – not so obviously – on the way in which the findings were translated into action with ('handling') the individual. Thus, continuing with start-stop as a representative example, it was vital that usage of it should not be imposed on the person, but should be introduced only when it corresponded with something 'coming from within'.

A large number of interlocking issues are involved here; and some of these are examined later in the context of a specialised unit and in relation to its staffing. This treatment is preceded by descriptions of some of the new methods and techniques which have been used in the various phases of the project, and which form much of the basis for the Proposals for the unit.

To complete this brief review, it is relevant to show how the role of the observer, while remaining central to the whole project, changed in character as electronics moved more and more into what had become an entirely unique form of systems engineering.

Initially, observation had to be accepted as being 'passive' in that near-infinite periods could elapse between any manifestations of the person behind the handicap. Indeed the only way to overcome the randomness of these occurrences was to provide "utterly continuous observation" (ref. 1); and in other than exceptional cases only parents were in a position to approach this. The whole attitude to mental handi-

cap was such that any suggestion by them of the existence of concealed capability was almost certain to have been dismissed, bearing in mind the evidence available and (always present) the dangers of raising false hopes.

The first step was therefore to set up conditions for the controlled observation which favoured occurrence and also made detection much more likely. The last-mentioned point was made a matter of giving some indication of where and when to look for these occurrences, and which was made possible by elementary system modelling, itself founded on the correlated (observational) information which by then was available.

Thus in phase 4, it had been established that interconnected gating type systems – 'gating interfaces' – appeared to be involved in the thinking process in such a way that the physical condition of mental handicap reduced the transfer efficiency between interface levels and also, in effect, reduced the isolation between channels required for 'multi-channel' thinking². When correlated with direct observation in this and other fields such as crisis control emergencies, there were two far-reaching conclusions.

● That 'inversion' of speech could take place largely as the result of 'imperfect read-out'. Inversion as used here covers a variety of distortion effects, including stuttering. In one relatively common form, syllables in a single word are transposed, sometimes with a loss of one or more, e.g. "poose" may be "spoon". As in all work on inversion, these transpositions are difficult to detect, particularly with loss of part of the original word (they are not, in general, classical spoonerisms); but even more difficult to pick out is the composite word made up of the end of one word and the

beginning of the next. A specific example which combined the features of both cases was afforded by "byer" which was traced to "fire burn". Of course, distortion may be so great that only what appears to be a noise or succession of noises is produced. Here again, as shown later (see full system modelling) detection may be achieved, especially if a benign atmosphere can be set up to encourage attempts at communication.³

● The other major aspect – 'data marshalling' – which arises here has effects such as 'delay in response' and 'thinking fatigue' associated with it, and from the point of view of the outside world is seen as a condition ranging from a severe lack of confidence to the shell of the total non-talker. This aspect is therefore linked with the stress condition under which the mentally handicapped can live for long periods; and which can be explained in relation to system modelling, largely in terms of data marshalling.

Data marshalling (refs 2 and 4) may be defined in the present context as the "streaming" and "sorting" of "masses of data". A full definition also includes the systematic presentation of the data, and it is in this final transfer *outward* that the handicapped often find the most difficulty.

Only just recently this last problem was demonstrated most dramatically by a young man who is easily driven into the non-talking state. On this occasion he selected a gramophone record which, from the sleeve, he knew to be of a piano; but instead of saying the word as usual he mouthed it – there is no ambiguity when lip-reading "piano". Although he could be sensed to be making an intense effort to achieve the transfer to voice production the pressures were such that he found it impossible.

Apart from its importance in providing direct evidence of something that cannot be detected in most circumstances – the failure to transfer – this incident carries a number of other important implications. Outstanding is the single aspect of delay-time which it covers (the "microscope" mentioned earlier). This specific element is part of the general build-up of delay which seems to be associated with the checking process of streaming and sorting which enter into data marshalling in the hyper-autistic condition. The evidence is sufficiently widespread to justify the statement that every new step – even for an action – has to be checked and re-checked before the individual feels that he can carry it out, unless some assurance which is acceptable has been given beforehand. However, the main reason for quoting this incident is that it gives an example of the "control" which is a feature of full system modelling. The chances of picking up an isolated event of this character are infinitesimal without some control of the attendant circumstances. To set up such controlled circumstances demands prediction by "primary" system modelling; and in this case the use of the gramophone provided a form of control (see later for an account of this approach) while experience combined with knowledge of the individual gave a likely time for observation. It

is the inability to obtain repetition of such incidents which has made it so difficult to maintain continuous lines of research. This difficulty has been fully recognised as one of the problems facing the specialised unit¹ and in effect forms one of the "design criteria" for it.

Similar lines of argument had to be followed to derive the remainder of these design criteria or the equivalent; and that the course of their development was linked with:

- the corresponding phases of the project itself and
- the progress of the trials which have been carried out with electronically-based techniques and equipment and which have underlain, and have been correlated with, the project as outlined in the foregoing description.

It is hoped that this has given at least an indication of the difficulties facing anyone entering this field and having to assimilate all the new concepts which have been introduced. Again briefly, it does seem that the only real solution is through on-the-job study and experience (see ref. 2 for link with training for emergency control) so that overall perspective and atmosphere can be gained. This general requirement has been covered in the proposals for the specialised unit in that allowance is made for high-calibre learners to work alongside the permanent research-care staff. These learners would thus be favourably placed for "... coming to grips with so many new concepts" and "... in building up their own know-how" (ref. 1). It is envisaged that they would spend at least a year in the nominal learning role, and then as part of the general policy for the unit would undertake the passing-on of their know-how and relevant experience to others.

How these possibilities would be realized in the unit is perhaps best shown by giving some account of the techniques and

equipment which have already been developed. This account is concluded with a description of an advanced language laboratory which would provide facilities – already tried out in principle – to enable individual aspects of hyper-autism to be investigated in the controlled circumstances of total system modelling.

It cannot be stressed too highly that, although the laboratory would provide unique facilities for research into various aspects of mental handicap which have already been "separated out", the basic objective would remain to develop ever-improving care for the handicapped. And in so doing to remove the worry and the other pressures from them, which is utterly obligatory if this work is to be at all successful – quite apart from the humanitarian issues which arise. It has been suggested that the present methods could be expanded and could feed this "source" information into a health authority organization "concerned with all vulnerable members of the community"¹

Magnetic board

The first piece of equipment specially designed to provide research-based care ("research-care") facilities for a young woman who suffered from a mental handicap and multiple physical handicap was the magnetic board. Full tribute must be paid to the staff who worked with Christina. They had established a rapport despite her inability to do more than make a small range of noises, while communication through the hands was near-impossible because of severe malformation of her wrists.

Nevertheless, it did seem that the last-mentioned avenue of communication might be investigated, and that this might even yield some spin-off; and full acknowledgement must be made to the head of the unit in that this spin-off was of a major character especially in terms of some basic principles that have been brought into the design of the advanced language lab.

The so-called magnetic board consisted of a square of sheet iron faced with 0.2mm-thick plastics over which converted magnetic door-latch pieces could be moved by

Christina at work with the magnetic board – tutorial techniques being established in parallel.



a magnetic stick. The first decision taken – to have “words” rather than individual letters as the movable pieces – though simple, was of major importance in other applications. Thus in practice, the speed of selection was found to be matched to Christina’s concealed capability and – as confirmed by other examples – the alternative of letter-by-letter build-up was tedious and time-consuming. This is of interest in those control systems employing speech synthesis⁴ and, as will be seen, in the human electronics of the advanced language lab.

In the same way, the results of the attack on the problem of the physical handicap – to enable the pieces to be moved by Christina – were of wider interest because severe mental handicap is frequently accompanied by some form of physical disability and, as with Christina, this calls for courage and determination of the highest order. (The mentally handicapped have been described as “the most courageous people on earth”.)

Similar considerations also applied to the development of the “ruggedized gramophone” (see below), where one of the aims was to enable those with an appreciable degree of physical handicap to do something, hitherto accepted as quite impossible, *themselves*. Furthermore, as has been shown to be crucial for progress and to help offset the effects of their difficult circumstances, they are working with a mature objective.¹

As a practical example of the attention needed for the apparently simple component design required in these instances, with their human implications, it may be useful to consider the “magnetic stick” as finally adopted. As the result of a series of trials – which helped Christina to supplement her own efforts to improve her command of the stick – its dimensions, found to be quite critical, were 25cm long and a diameter of 8mm. The actual configuration was tee-shaped with a croupier-type end tipped with a small permanent magnet. The magnet was selected, in conjunction with the rake end, to provide the push/pull action required to move the words against the magnetic “sticktion” of the board.

Ruggedized gramophone

In its do-it-yourself role, the ruggedized gramophone is noteworthy for the large amount of spin-off that was gained from it. Developed specially for this application, the basic design aim was to provide a unit which could be operated by the most severely handicapped individual; and, as implied by its original title, would stand up to any form of clumsy handling that could be envisaged. Provision was made to restrict access to the turntable and pick-up when a record was being played. Thus the mechanical design of the box was extremely robust with power interlocks on the lid which had to be shut before playing. On the operational side, “start” was by a plunger-type control external to the box; while an alternative cone-shaped spindle provided easy juke-box centring for compatible records where physical

handicap made this difficult.

When this unit was brought into service a definite break-out from the shell was produced with *every member* of the group concerned, and that this could be repeated. This meant that concealed capability could be demonstrated effectively “to order” for the first time. This depended upon the maintenance of stable conditions i.e. by preventing disturbance, particularly by avoiding intrusion by strange visitors.²

That this point had been reached was of particular significance in terms of intensifying research, because it proved that it was possible to set up the equivalent of the controlled conditions which were being evolved even then, on the basis of rather more indirect evidence; and not to have to depend entirely on random – passive – observation for firm vital data.

On the human (care) side a summary of the position is perhaps best achieved by quoting from statements made by the staff at the time:

“It (the gramophone) has given them great satisfaction being able to do something completely by themselves” and

“... expressions change and the mentally handicapped start to communicate more freely than they have ever done before”.

The statement that “... people there was little hope for, who remained silent throughout long periods ... progress from gestures to more comprehensive sounds and words ... and more awareness of what is going on around them” is given as being representative of the evidence that has been collected from many witnesses. However in this instance there are two vital differences: firstly that the evidence is for *all* of a group and secondly that it has been obtained in a controlled, non-random fashion.

The last statement quoted also includes a reference to “. . . clearer voices . . .” (when progress is being made with communication). These may be regarded as being early manifestations of “second voice” (and “super-second voice” effects which are covered elsewhere.³ By their very nature they are difficult to detect, but work continues on this aspect of “the person underneath”.

On the technical side, the bringing into operation of the gramophone may be said to have marked the beginning of system modelling proper. The composite system – planned to produce certain research answers – consisted of the individual with a “thinking mechanism” sub-system, the sound-track “data content” of the record and the instructions (roughly software) given to the student.

With regard to this last aspect, one element in the control programme was that the student selected “his” record by looking for his photograph on the sleeve which also carried his name (for possible “subliminal” recognition); and, for instance, information could be obtained on delay time which was “tied” to a specific parameter and set of circumstances.

Continuing with this example, the next step now could be to look into gating interface blockages, for example, when suffi-

cient linking information had become available. Thus, analysis of delay times in telephone communication with, say, variation in side-tone content could be made – assuming isolation had been achieved from such effects as “back-comparison” time.

The crystal transducer and amplifier unit were used with a small hand-held loudspeaker unit for the original speech reinforcement development. In the proposed advanced language lab application, the speech output would be fed into the laboratory loudspeaker system (page 00); and it is of interest that a similar arrangement might be adopted for the main operating space for “two-tier” full emergency control.²

The unit gave remarkably good quality, and as far as the main problem of acoustic feedback was concerned, this could be kept below the howl-back threshold for all but the maximum loudspeaker volume. The initial speech reinforcement requirement was set at a minimum of increasing the intelligibility-content of sounds produced by the less-heavily mentally handicapped who were prevented physically from making almost any form of utterance. (Precedents with the non-mentally handicapped have been seen.) Accompanying this initial requirement was the hope that the work would encourage attempts to produce sounds which were more speech-like; and in the trials that were possible this did indeed take place.

With regard to improvement of speech sound production a basis was established the work planned in this area for the a.l. lab. Taking advantage of the early magnetic board findings, it appeared possible to “fill-in” words such as those produced as little more than exclamations by a word on the board and vice versa.

This has been taken further in planning to include in the a.l. lab. a ‘talking typewriter’ for ‘filling-in’ by the handicapped person with words instead of individual letters on the keys – following the principle accepted for the magnetic board. This does mean that only a very restricted vocabulary is available; but in many cases this is desirable, especially in cases where system modelling is being carried out and where mental search time has to be kept to a minimum.

The lightly handicapped occupy a special place in the proposals in that it is suggested that they should be made part of the unit’s back-up staff, acting as contact helpers. Information has been collected from a variety of sources on their ability to interpret the distorted (e.g. inverted) speech of those at a lower level of attainment; and in undertaking this work they would derive enormous benefit for themselves from doing something that is adult, carries recognizable responsibility, and – perhaps for the first time – shows them that they can be successful at doing this mature work. Experience can be quoted than the resultant enthusiasm is then transmitted to the others; and this access of confidence – as opposed to a dread of ‘getting it wrong’ – can be seen in their ability to act as team-leaders to the more handicapped. They are, in fact, achieving the equivalent of rehabilitation in bringing

themselves and their team out of the hyper-autistic shell.

Such a successful arrangement should not be disturbed; continuity and hence stability are vital even for those at the higher levels of attainment if they are to retain this position. Also, they still require highly sensitive guidance and particularly, encouragement, as with all the handicapped.

Language laboratory tutorial scheme

As envisaged the first application of the tutorial system would be to the talking typewriter scheme. It is assumed that the move to this scheme would be preceded by a build-up of contact experience where interpretation would become increasingly tripartite in character, i.e. students, helpers and main care staff would develop more and more mutual understanding, and as time went on more and more interdependent.


Such an arrangement could be made more formal with, say, the d.i.y. gramophone operating with a definite team programme. To prepare for the final scheme, individual members of the team might be introduced to basic language lab. conditions with the use of the telephone under controlled conditions². Thus, providing the telephone is accepted, the student can be expected to gain in confidence and in facility of verbal communication.

This question of acceptance of the unfamiliar (with the anxiety it may cause) is perhaps where the helper can make his greatest contribution. Association of ideas effects¹ are often enough to prevent such acceptance in these circumstances; but the trust placed in the helper may enable him to smooth the way to compliance. It should be added that non-compliance usually takes the form of entrance into the isolation of the shell for an indefinite period (and which should not be confused with sulking).

With this background, it becomes more than evident that human considerations must always be given absolute priority in the design of these systems and in planning their operation. Thus human electronics takes on its full meaning; with failure even to avoid, say, an unsuitable shape of a control liable to vitiate the whole scheme.

Something of the way in which these principles are applied may be seen with the talking typewriter development. This scheme is centred round a word-keyboard speech synthesizer with software arranged to display the words being keyed-in. In the word mode, the words would be spoken as they were keyed-in. In the phrase mode, they would still be displayed word-by-word, but not put out as speech until a speak button was pressed for the group of words to be transmitted out from store.

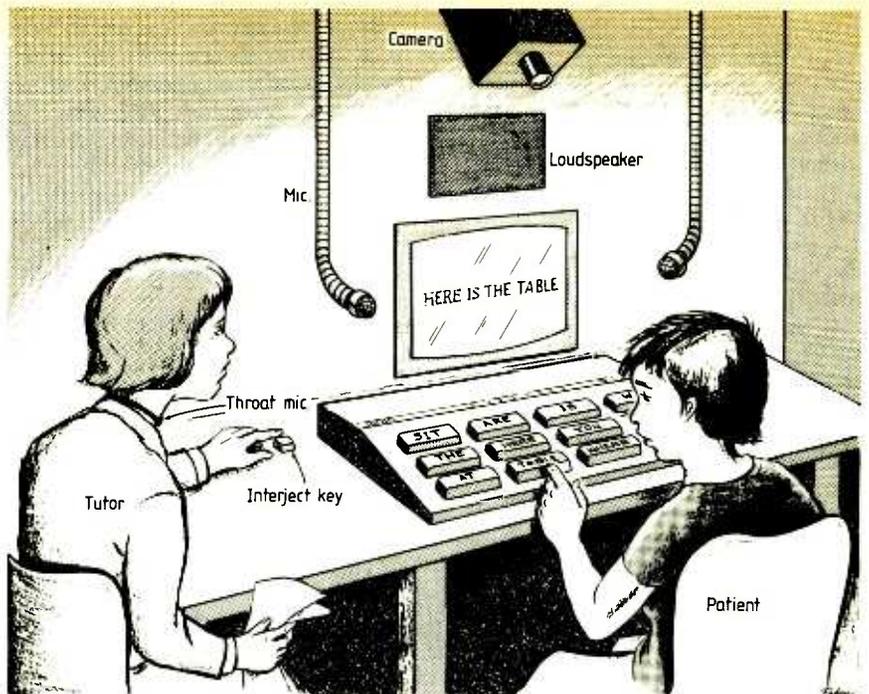Insert mode would have two sub-modes. In the first, this button would bring in a throat microphone worn by a tutor to give an insert (interject) facility for 'filling-in'. In the second sub-mode, this interject facility would be made available to both tutor and student so that the tutor could back up any attempts made by the student to produce coherent speech by mixing his



own sounds into the controlled, synthesized speech. In general this would only be used by lightly handicapped students (they will accept the throat microphone) particularly by those who were potential tutors; but as the result of experience it might be possible to evolve a simplified version of this system for the more handicapped.

The aim throughout is to develop 'subliminal' methods for learning to read, combined with improvement of speech. Not long ago it would have seemed astonishing that systems of this kind were being suggested for the mentally handicapped. Now, as has been shown, more than sufficient evidence exists to justify further extension of these advanced methods; and in the last system to be described, the extension is taken into 'visual mathematics'. This concept has been evolved in the context of mental handicap, and not least in the light of an interest in numbers that has been detected.

The ideas entering into this concept come from several areas, and started with an aerospace calibrated display system⁵. This continued with the suggestion that this system – essentially for multi-channel 'histogram' working – would be made in single-channel form to meet a specific requirement in crisis control. A further development for operation under 'survival' control conditions⁶ appeared to offer possibilities in the evolution of visual mathematics; and in view of the interest being shown in this area, the principle was applied to the tutorial side. As in other instances of this kind, spin-off flow built up in both directions.

In its original form the calibrated display enabled the time-division multiplexed output from several transducers – appearing as a histogram – to be shown simultaneously with an adjustable calibration line on a c.r.t. display. Histogram and calibration line were shown on alternate strokes of the time base, and thus

'Tutorial' position in advanced language laboratory as envisaged for the talking typewriter. Tutor operating with throat microphone and 'interject' button. Demonstration/teaching c.c.tv camera and microphones overhead.

measurements in terms of calibration frequency were made on common equipment. The calibration – and therefore the accuracy of measurement – were thus independent of changes in the chain because the calibration and histogram signal were fed into it at the same point.

This same basic principle is used in the crisis control application. Here the raw data output from a single 'frequency' transducer is measured by moving the calibration line to coincide with the top of the pulse representing the transducer output value. In the illustration, the pulse is shown as repeated in order to read more easily through 'locked' interference; while the sine wave shown below the calibration line is a direct representation of the transducer output.

This last feature has been added for visual mathematics where the idea of number might be associated initially with this picture of a variable-frequency tone reproduced on a loudspeaker. This would be related to the numerical value shown on the calibration adjustment control at a suitable point as judged by the tutor, with this followed appropriately by interchange of setting and reading between him and the student. It is envisaged that this facility might be extended to more computer-like displays; but this would only be after a protracted exploratory period. And the outcome of this work might only reveal a logical aptitude; but this alone would be worthwhile, as in a comparable case when one discovers that a non-communicator is making himself understood with words which it was not known that he had mastered.

Project summary

The position now reached with this project as shown in the five phases of the flow chart can be stated in terms of 'research-care' and the developments which have stemmed from the establishment of a technological (essentially electronic) base - phase 3.


The growth in the wider aspects of research-based care has been maintained throughout the project; the most important element in it continuing to be information (observational data) obtained from witnesses at all levels, and giving direct insight into the concealed capability of the mentally handicapped. The work of interpretation of these reports and their correlation has been strengthened with the development of the required technical vocabulary; and has been increasingly interlocked with the results of trials which it has been possible to carry out, particularly during the latter part of the programme.

It has become increasingly clear with the progress of the project that over-riding priority must always be given to the human considerations. Thus, although the accepted research-care is an abbreviation of research-based care, and although research is fundamental to the whole concept of the unit, it must be made subordinate to care at all times. This principle has already been stated with regard to the design of electronic equipment for use by the handicapped themselves, where disregard of their special requirements is quite likely to result in non-acceptance and consequent entry into the shell.

Therefore, broadening this principle not only to include system design but also to include the planning of any research it becomes clear that a close watch must always be kept for any signs of the development of set-back, not least for the serious economic penalty that can be incurred with the inordinate amount of time and effort that may have to be expended to restore the position.

Precautions can be taken to reduce the chances of set-back conditions being set

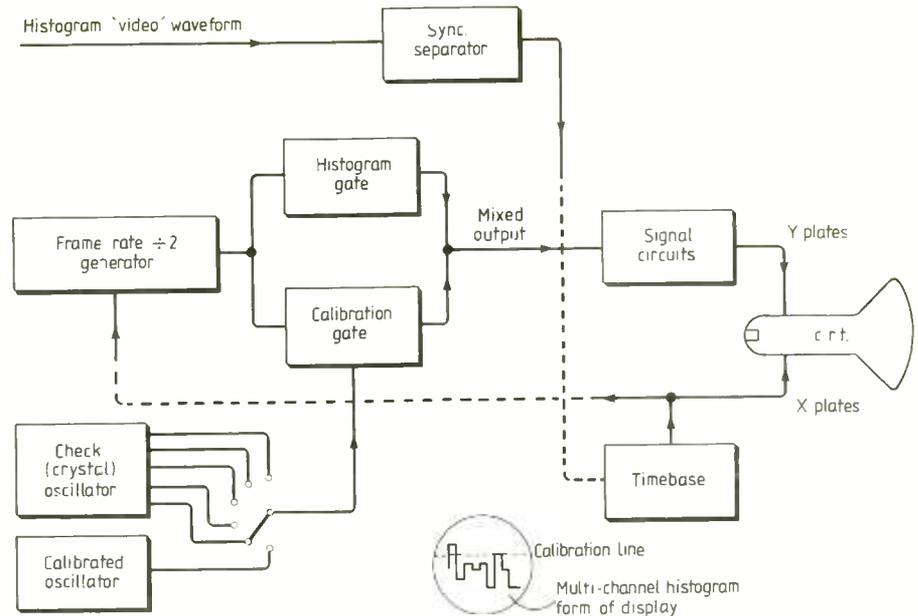Laboratory equipment arranged for 'visual mathematics' display. In tutorial use, auxiliary traces would be shown on separate displays. Photo by Manchester Polytechnic.



up; and one part of this approach is to make sure that a step forward in a programme is not taken until the current step has been understood and accepted. This is vital, particularly where research is being carried out by indirect methods designed to pick up answers to questions arising from, say, system modelling, and where it is difficult to separate-out the factors.

Some of this has already been outlined in the earlier sections on tutorial techniques; and can be seen in more detail by taking the case of the young man who failed to make the final transfer to audible speech. The question of "Could failure to transfer always be traced to the last interface (or at others?)" could be tackled by an indirect approach using suitable facilities available in the advanced language lab. These might well include observation of delay time with the 'talking typewriter' and the telephone with its side-tone effects; and would involve finding how representative these students were, in order to avoid causing distress to individuals not immediately capable of using these pieces of equipment.

Original calibrated display for multi-channel working.

Such a research investigation would be complex, but could be kept under control; and could give valuable information in a number of fields such as ordinary autism and geriatric ability to speak, and, of course, for getting a better picture of this aspect of mental handicap communication.

Acknowledgements. Special acknowledgement must be made of the part in this project played by Dr Gordon Avery, District Medical Officer of the South Warwickshire Health Authority, particularly with regard to the publication of proposals for a specialised unit, which is approved and backed by him. A personal acknowledgement is made to Professor Harold C. A. Hankins of the University of Manchester Institute of Science and Technology for his major contribution to this work both with continuous practical interest and with full-ranging discussion throughout. Finally, full recognition must be given to Peter Watts and the UMIST Medical Engineering Unit for the originality shown in the design and development of the ruggedized gramophone and throat microphone, and for the research done on the microphone. 

References

1. Mental Handicap - Proposals for South Warwickshire Specialised Unit, by R. E. Young, 1982. Communication to South Warwickshire Health Authority, available in its original form from *Wireless World*.
2. Crisis control by R. E. Young *Wireless World*, June and July 1982.
3. Mental Handicap - The New Thinking, by G. M. and R. E. Young, August 1981.
4. Control in Hazardous Environments, by R. E. Young and Peter Peregrinus (IEE), 1982.
5. Analogue telemetry equipment and systems by S. Poole, A. Potten, C. O. Titley, - Pt 2, *Electron. Eng.* Vol. 33, 1961 no. 396.
6. Crisis control - the background, by R. E. Young, *Nuclear Engineer*, Vol 24, July/August 1983.

RTTY on a Nascom

Now that home microcomputers are replacing the old-style electromechanical teleprinters, interest in transmitting teleprinter messages by amateur radio (RTTY) is on the increase. Ian Wade describes how a Z80-based Nascom microcomputer can be used for RTTY, and includes full details of the special hardware and software required. Most of the techniques apply to any micro-based system.

Despite the fact that the Z80-based Nascom microcomputer was first introduced several years ago, many of these excellent machines are still in use today in amateur radio stations. About two years ago I decided to build a rtty system around a Nascom, and this article describes how it was done. The package started life as a small collection of rudimentary subroutines performing little more than conversion between the ascii and Baudot character codes, but as operational experience increased, more and more software and hardware facilities were progressively added until the system eventually assumed its present form. The panel opposite lists the features now incorporated in the system.

The first part of this article summarizes the basic operation of the system, and then covers suggested hardware modifications to make the Nascom function as a rtty terminal. Each of the modifications is accompanied by a short test program, so that the changes can be checked out individually before running the rtty program proper. The second part describes the software in detail, and includes a machine code listing of the rtty program. Whilst some of the material is naturally specific to the Nascom, most of the techniques described are equally applicable to any micro-based rtty system, and may be adapted for use on other machines.

by Ian Wade

BSc(Hons) MBCS G3NRW

RTTY system

Starting at the top left-hand corner of the simplified block diagram, Fig. 1, the two-tone audio output from the receiver is passed through the terminal unit, in this case a home-made version of the well-known ST5 design¹. The output from the terminal unit is a stream of ± 5 volt pulses, $-5V$ corresponding to a mark (1445Hz) and $+5V$ corresponding to a space tone (1275Hz). These serial pulses, representing Baudot characters, are then input to the uart in the Nascom. The rtty software now takes over, converting the Baudot characters into their ascii equivalents, and saving them in the ascii text buffer. From there they are sent to the tv screen, and optionally, to a printer connected to the parallel interface (p.i.o). In the reverse direction, characters to be transmitted are typed in at the keyboard and saved in the ascii text buffer. These characters are displayed on the screen and again optionally printed, before being converted to Baudot for transmission, via the uart, to the two-tone generator¹. The audio output from the generator is connected to the

The author

Along with other holders of G3N callsigns, Ian Wade is fast approaching his first quarter century as a licensed amateur, and has dabbled in most aspects of this fascinating hobby at one time or another. His particular interest is in data communication, satellites and very low power operation, but other of his sessions include photography, music (from Bach to Heavy Metal, but drawing the line at Harpsichords) and linguistics. Professionally, he is managing director of the software house Dowermain Ltd, specializing in industrial, process control and telecommunication systems.

microphone input of the transmitter, which operates in vox mode.

The single-bit drive output from the Nascom (normally used to control a cassette tape recorder motor when saving programs on tape) is used in the rtty system to switch the two-tone generator on and off. When DRIVE is asserted low, the generator operates normally, sending mark and space tones to the transmitter. When DRIVE is asserted high, however, no tones are generated at all. Thus the drive output controls transmit/receive changeover, and when used in conjunction with vox there is no need to make any direct control connection to the transceiver. In

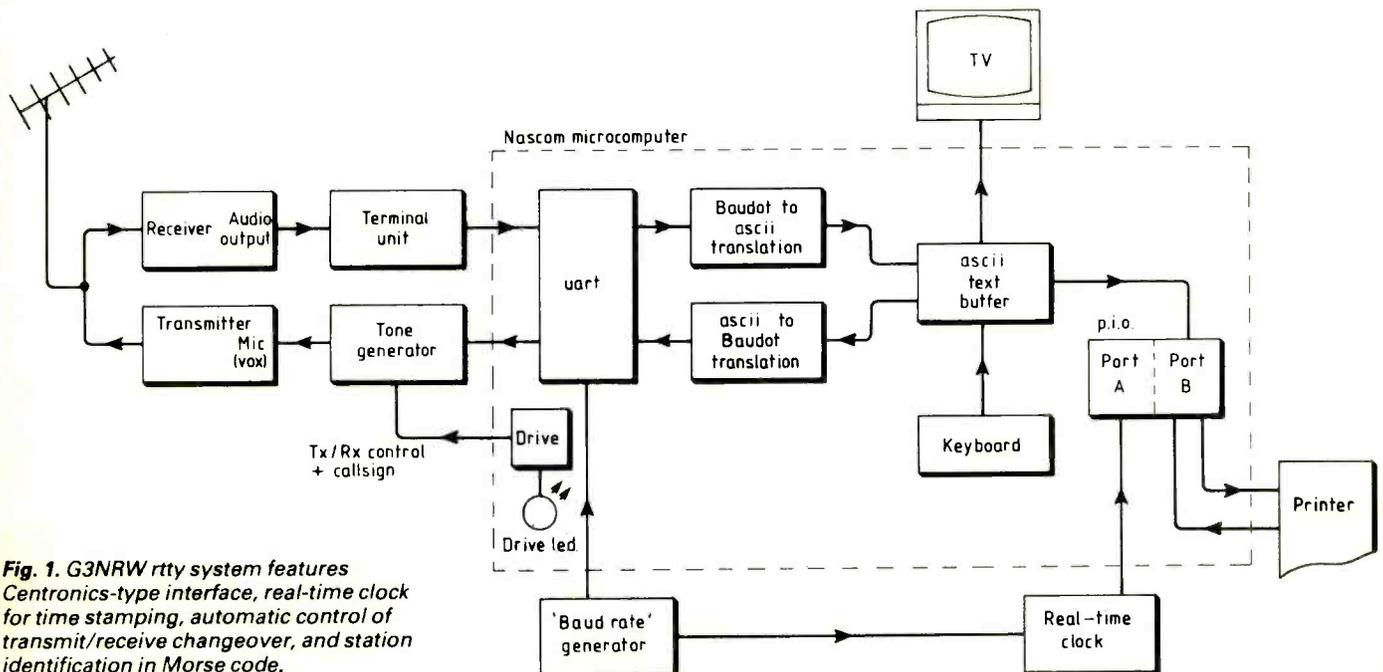


Fig. 1. G3NRW rtty system features Centronics-type interface, real-time clock for time stamping, automatic control of transmit/receive changeover, and station identification in Morse code.

FEATURES OF THE G3NRW NASCOM RTTY SYSTEM

The rty program runs on a basic Nascom 1 or 2 microcomputer, under the standard Nas-Sys Monitor, and occupies just 896 bytes of user ram (in the address range 0C80 to 0FFF).

Only minor hardware changes are required to the Nascom hardware, to make the uart handle five-bit characters at 45.45baud. An alternative uart clock generator covering all the standard rates is also described.

Supports an external real-time clock, operating under interrupt, allowing the current time to be displayed on the tv screen and to be included in messages.

Supports a Centronics-compatible printer via the parallel i/o (p.i.o.) interface, also operating under interrupt, to provide hard copy of all transmitted and received messages.

Uses the drive output from the Nascom to control transmit/receive changeover, and to transmit the station callsign in Morse code for identification.

When transmitting, provides:

- keyboard buffering, allowing type-ahead
- automatic carriage return/line feed insertion, to prevent overprinting at the end of a line
- automatic insertion of shift character after a space
- automatic transmission of a pre-defined message (e.g. a CQ call)

When receiving, provides:

- automatic carriage return/line feed insertion
- facility to insert a Letter Shift or Figure Shift character into incoming text, to correct characters being received in the wrong shift
- automatic testing of uart status, with rejection of invalid characters (i.e. characters having overrun or framing errors)
- facility to set up a message for later transmission

Received message text is displayed on the tv screen in lower case letters, and transmitted text in upper case, to allow easy distinction between incoming and outgoing messages.

In addition, the system has a command which causes the drive output to be keyed with the station's callsign in Morse code, for identification.

The optional real-time clock interrupts the processor at regular intervals, and forms the basis of a time-of-day clock which is displayed on the screen and which can also be transmitted as part of a message if desired.

The computer in my system is a basic Nascom 1, with 896 bytes of user memory, and running under the standard Nas-Sys Monitor program. All of the options listed above work in this system, but any of them

can be omitted if the corresponding hardware is not available.

Hardware modifications

The essential modifications to the Nascom are

- to provide a uart clock running at 727Hz for 45.45baud operation (or 800Hz for 50baud), and
- to set up the uart control inputs for 5 bits per character and 1½ stop bits.

The remaining modifications (i.e. for the printer, real-time clock and drive control) are optional, but once fitted can be used in a wide range of other applications apart

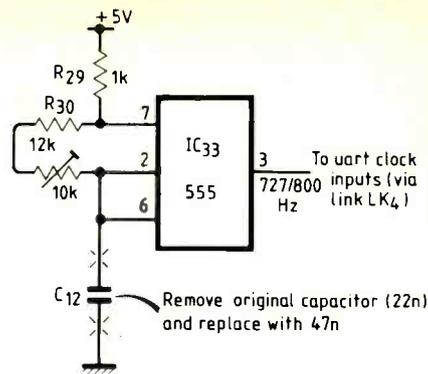


Fig. 2. Modification to 555 clock generator to run the uart at 44.45/50baud. Component numbers refer to those in the Nascom 1 manual.

from rty. The modifications are described in detail below, and are suitable for both the Nascom 1 and 2 computers. The test programs to check out the changes are keyed in from the keyboard, using the Nas-Sys modify memory (M) command, and they all start at address 0C80; i.e. execution is started with the command EC80. All references to memory addresses and their contents, here and elsewhere in the article, are in hexadecimal.

UART clock

Two methods of providing a uart clock are described. The first involves a minor modification to the existing 555 clock generator (which normally runs at 1760Hz for 110baud operation), and the second is an external clock which produces all of the standard clock rates from 45.45 to 9600baud.

To make the 555 clock run at 727 or 800Hz, it is only necessary to replace the existing 22nF timing capacitor (C₁₂ in Fig. 2) with a 47nF capacitor. This should be a

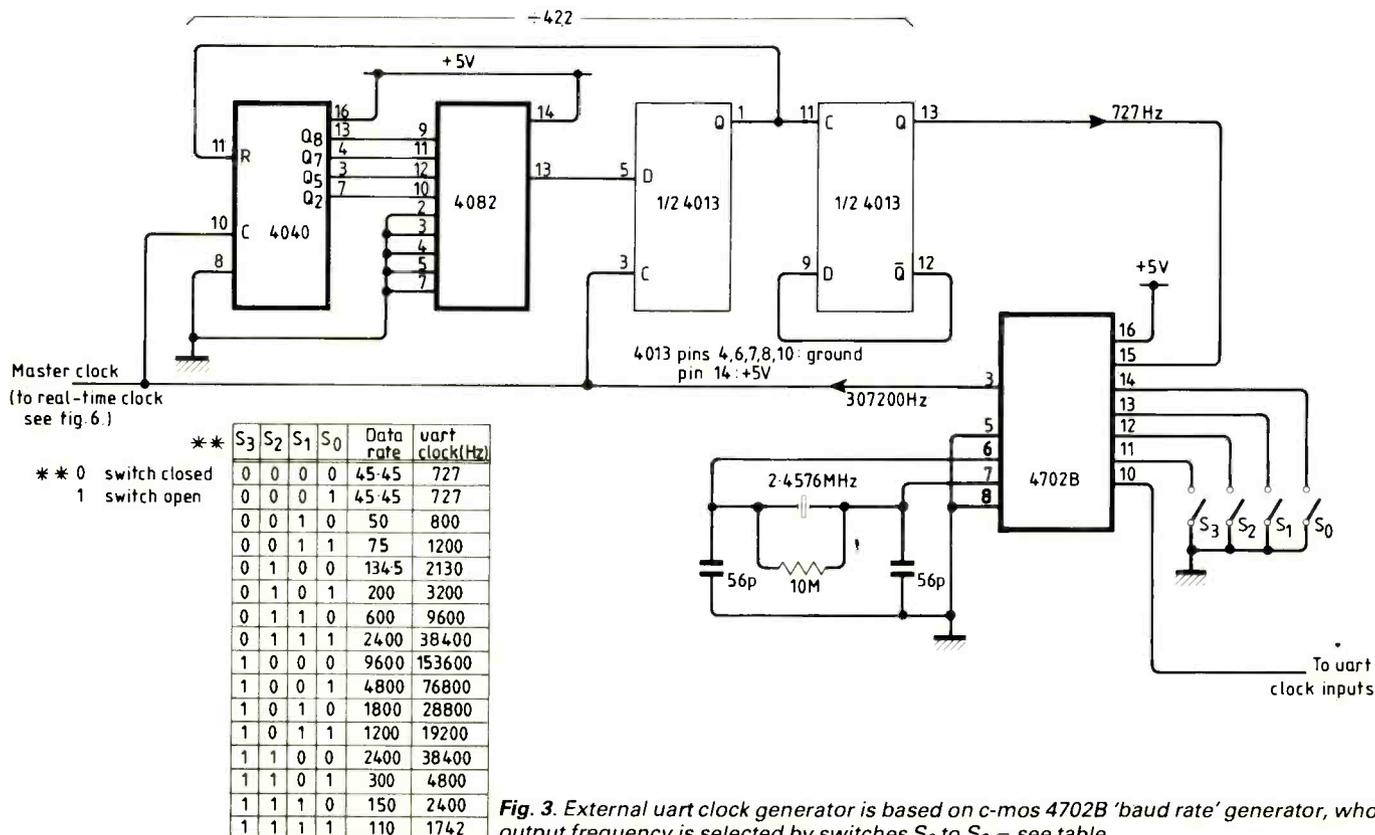


Fig. 3. External uart clock generator is based on c-mos 4702B 'baud rate' generator, whose output frequency is selected by switches S₀ to S₃ - see table.

polycarbonate film type or similar to reduce thermal drift. It is then a matter of adjusting the preset, ideally using a frequency counter, until the desired frequency is achieved. This modification was used successfully for several months, but does of course have the minor disadvantage that it is not then possible to revert to 110baud operation without having some means of switching the timing capacitor back to its original value.

To overcome this disadvantage, an external uart clock generator was developed (Fig. 3). This is based on the cmos 4702B 'baud rate' generator chip, whose output frequency can be selected by means of the four s.p.s.t. switches S0 to S3, according to the table shown in the diagram. The basic 4702B chip provides all of the standard clock rates for operation from 50 to 9600baud, and the three additional cmos chips produce the clock for 45.45baud by dividing the master clock frequency (307200Hz) by a factor of 422. The four clock select switches do not require pull-up resistors. Pin 4 of the 4702B chip is normally left unused, but if it is grounded the clock output on pin 10 is disabled.

The unit can be built on a small piece of stripboard and requires no setting up. After construction, the output frequency should be checked with a frequency counter for each of the 16 possible combinations of the clock select switches, and should be within a few Hz of the values given in the table. The 'unusual' frequencies for 110 and 134.5baud arise from limitations in the design of the chip, but are still well within acceptable limits for the uart.

UART control

The uart control inputs (pins 35 to 39) need to be set up for five-bit character operation. This requires these pins to be connected as follows (corresponding to 5 data bits, 1½ stop bits, no parity):

- Pin 35: high
- 36: high
- 37: low
- 38: low
- 39: high or low (does not matter).

To achieve this, it is required first to remove the existing connections to these pins, if necessary by breaking the p.c.b. tracks. Then the pins can be connected to s.p.s.t. switches with pull-up resistors, as shown in Fig. 4, so that any combination of control inputs can be set up.

Printer interface

The rty program will drive a Centronics-compatible printer to provide hard copy of all received and transmitted messages (Fig. 5). The printer is connected to port B of the p.i.o. and operates under interrupt. When the printer is ready to receive a character, its acknowledge output (and therefore the BSTB input to the p.i.o.) goes low, thus causing the interrupt. The data strobe from the p.i.o. to the printer is connected to the B7 data pin of the p.i.o. because the print strobe is generated by software.

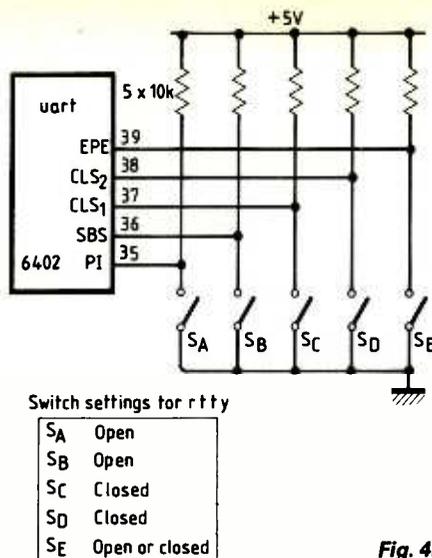


Fig. 4.

To test the printer, load the program listed in Table 1, and start it running with the EC80 command. Then type any characters on the keyboard. As each key is struck, the program outputs the corresponding character via the p.i.o. to the printer. Having accepted the character,

Table 1. Printer test program.


```

OC80: 21 86 0C E5 ED 4D 3E 0F
OC88: D3 07 3E AC D3 07 3E 87
OC90: D3 07 3E 0C ED 47 ED 5E
OC98: FB DF 7B 32 B9 0C CB FF
OCA0: D3 05 CB BF D3 05 CB FF
OCA8: D3 05 18 EC AE 0C 08 3A
OCB0: B9 0C 32 F9 0B 08 FB ED
OCB8: 4D
  
```

the printer should then respond with an interrupt, and the interrupt service routine in the test program now echoes the character at the top right-hand corner of the screen. If no characters are echoed, the printer is not interrupting correctly. Note that although the characters are echoed on the screen, nothing is actually printed until carriage return is typed (or 132 characters have been input).

Real-time clock

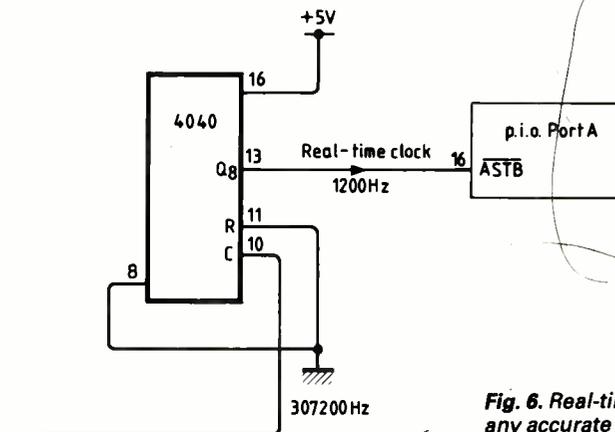A real-time clock can be connected if desired to the ASTB input of the p.i.o. The clock could be at 50Hz, derived via a suit-



Master clock (from Fig. 3.)

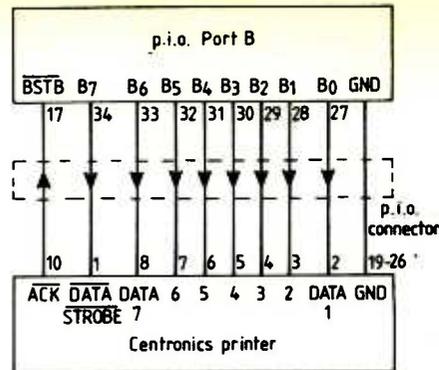


Fig. 5. Program will drive a Centronics-compatible printer to provide hard copy of messages.

able step-down transformer from the mains, or could be generated by a crystal oscillator. Any frequency in the range 1Hz to about 1500Hz could be used, provided that it is accurately known and stable. In the G3NRW system, the clock is obtained from the uart master clock, which is divided by 256 to give a square-wave output at 1200Hz; see Fig. 6. This frequency was chosen to allow the Nascom to run Amtor, but that is another story!

To test the clock, first load the program listed in Table 2, setting locations 0CAC and 0CAD (indicated by Y and X in the program) to correspond to the clock frequency in use. X is the most significant byte of the frequency and Y is the least significant byte. Examples of the hexadecimal values of X and Y for various clock frequencies are shown in Fig. 6. Now start the program with the EC80 command. If the clock is working correctly, the two-byte counter at locations 0BF7 and 0BF8 will be decremented after every individual clock interrupt, and the counter at location 0BF9 will be incremented once per second. As these three memory locations correspond in fact to the last three character positions on the top line of the tv screen, the counters can be observed very easily. Thus the first two of these characters will be changing at the clock rate (and hence will be quite blurred except for very low clock frequencies), whereas the last character on the top line will only change once per second. If these characters do not change at all, the clock is not interrupting correctly.

Real-time clock program constants		
Frequency Hz	X	Y
1	00	01
25	00	19
50	00	32
100	00	64
1000	03	E8
1200	04	B0

Fig. 6. Real-time clock could be driven by any accurate frequency between 1Hz and 1500Hz; in the G3NRW set-up clock is obtained from uart and divided by 256 to give rectangular-wave output at 1200Hz.

Table 4. G3NRW rtty program to run under Nas-Sys 3. To run under Nas-Sys 1, change location 0CDE from 7C to 82 and 0D8E from 80 to 86. Real-time clock frequency XY is at 0FD0 (Y) and 0FE1 (X). Callsign constants occupy locations 0FD4 to 0FDF.

```

0C80: 21 98 0C E5 ED 4D 0D 0A 20 54 49 4D 45 20 30 30
0C90: 30 30 20 55 54 43 20 20 2E 0E 11 91 0C 3E 30 CD
0CA0: C4 0F 23 CD C4 0F 2E 86 11 CA 0B 01 12 00 ED B0
0CB0: AF CD 56 0E 2A 86 0C 22 F7 0B 3E 0B 32 C0 0E CD
0CC0: CD 0F 3E 0F D3 06 D3 07 ED 47 3E 87 D3 06 D3 07
0CD0: 3E C0 D3 04 D3 06 3E C2 D3 07 ED 5E FB 3E 7C CD
0CE0: 34 0E CF 4F FE 20 38 39 FE 74 CA 8D 0D FE 6C 28
0CF0: 4C FE 66 28 43 FE 7A 28 1B FE 78 28 1E 3A F9 0B
0D00: B7 28 DF 2A 0E 0C 3E F7 95 20 02 2E DC 71 23 22
0D10: 0E 0C 18 CE 3E 0D CD 56 0E 18 C7 AF 32 F9 0B 18
0D20: C1 DB 02 E6 0E 28 04 3E 20 18 23 47 79 B7 28 B2
0D30: FE 1F 28 09 FE 1B 20 0D 21 61 0F 18 03 21 41 0F
0D40: 22 10 0C 18 9D 2A 10 0C 09 7E FE 0A 28 94 CD 68
0D50: 0E F3 0F 65 FB FE 0D 20 89 CD 50 0E 3E 0A 18 EE
0D60: AF 4F 21 04 0F 16 08 5E B3 28 2C CB 13 38 16 CB
0D70: 79 CB F9 20 04 F3 DF 5F FB AF 06 06 CD 40 00 15
0D80: 20 E9 23 18 E0 CB 79 CB B9 28 EE 18 E8 3E 80 CD
0D90: 34 0E 3E 1F 32 1D 0C DF 5F DF 62 30 30 FE 69 28
0DA0: BF FE 72 28 23 FE 68 20 01 AF CD 68 0E FE 0D 20
0DB0: 07 CD 50 0E 3E 0A 18 F2 FE 0A 20 04 3E 20 18 EA
0DC0: FE 20 20 09 3E 1F 18 E2 DF 5F C3 DD 0C DB 02 E6
0DD0: 40 28 5E 2A 12 0C ED 5B 14 0C CD AD 0E FB 28 31
0DE0: ED 53 14 0C 22 12 0C 4F FE 1F 28 31 FE 0D 20 04
0DF0: 3E 08 18 29 FE 0A 20 04 3E 02 18 21 06 00 21 61
0E00: 0F 09 7E 21 1D 0C CB 7F 28 0B CB 56 28 0F CB 96
0E10: 7E D3 01 18 1C CB 56 20 04 CB D6 18 F3 D3 01 79
0E20: FE 1F 28 04 F3 DF 65 FB 3A 12 0C CD 9F 0E 32 12
0E30: 0C C3 99 0D 32 75 0C 21 2E 0C 22 16 0C 22 12 0C
0E40: 22 18 0C 21 41 0F 22 10 0C AF 32 1E 0C 32 F9 0B
0E50: 3E C0 32 1C 0C C9 32 F9 0B 21 DC 0B 22 0E 0C 06
0E60: 1B 3E 2E 77 23 10 FC C9 F3 4F 21 1C 0C 34 20 0A
0E70: 06 FF 70 FE 20 20 03 3E 0D 4F ED 5B 16 0C 12 7B
0E80: CD 9F 0E 3E 16 0C 5F 3A 1E 0C B7 20 0F 3C 32 1E
0E90: 0C 79 B7 28 04 ED 53 18 0C CD 34 0F 79 FB C9 3C
0EA0: FE 61 20 03 3E 2E C9 FE FA CD 3E CA C9 F3 3A 16
0EB0: 0C 95 C8 7E B7 C0 CB 54 28 08 7D CD 9F 0E 6F 11
0EC0: DB 0B EB 18 E8 D9 08 DD E5 3E CA 32 C0 0E 2A 0C
0ED0: 0C 2B 22 0C 0C AF 47 4F ED 42 20 2D CD CD 0F 3A
0EE0: F9 0B ED 44 32 F9 0B 21 1F 0C 34 3E 3C BE 20 19
0EF0: AF 77 21 D5 0B 06 04 DD 21 BB 0F 34 7E DD 23 DD
0F00: BE 00 20 05 36 30 2B 10 F2 DD E1 08 D9 FB ED 4D
0F10: D9 08 2A 18 0C ED 5B 1A 0C CD AD 0E 28 11 ED 53
0F20: 1A 0C CD 34 0F 7D CD 9F 0E 6F 22 18 0C 3E 01 32
0F30: 1E 0C 18 D7 CB FF D3 05 CB BF D3 05 CB FF D3 05
0F40: C9 00 65 0A 61 20 73 69 75 0D 64 72 6A 6E 66 63
0F50: 6B 74 7A 6C 77 68 79 70 71 6F 62 67 00 6D 78 76
0F60: 00 00 33 0A 2D 20 27 38 37 0D 24 34 27 2C 21 3A
0F70: 28 35 2B 29 32 23 36 30 31 39 3F 26 00 2E 2F 3D
0F80: 00 04 8D 85 94 89 00 9A 85 8F 92 00 91 8C 83 9C
0F90: 9D 96 97 93 81 8A 90 95 87 86 98 8E 9E 8F 9E 9C
0FA0: 99 00 03 19 0E 09 01 0D 1A 14 06 0B 0F 12 1C 02
0FB0: 18 16 17 0A 05 10 07 1E 13 1D 15 11 3A 36 3A 33
0FC0: C5 0E 10 0F ED 67 12 1B ED 67 12 1B C9 2A E0 0F
0FD0: 22 0C 0C C9 3A 88 0E E8 AB B8 E8 BA 2E E0 00 00
0FE0: B0 04 B8 AA 56 FC FA 0B 48 0C 79 02 B8 01 0C 0C
0FF0: 6B 07 0C 0C 00 00 34 0C FC 03 35 00 FD 03 05 00
    
```

Table 2. Real-time clock test program. Clock frequency=XY.

```

0C80: 21 86 0C E5 ED 4D 3E 0F
0C88: D3 06 3E 9E D3 06 3E 87
0C90: D3 06 3E 0C ED 47 ED 5E
0C98: AF 47 4F FB 18 FE A0 0C
0CA0: 2A F7 0B 2B 22 F7 0B ED
0CA8: 42 20 0A 21 B0 04 22 F7
0CB0: 0B 21 F9 0B 34 FB ED 4D
    
```



Drive control

To control the transmit/receive changeover of the transceiver, and to allow the callsign to be sent in Morse code, the drive output from the Nascom can be used to switch the

tone generator on and off. The output is — intermittently low and high when sending the callsign (low corresponds to the 'on' or audible elements of the callsign) — continuously high during receive — continuously low during transmit.

To check for proper operation of the drive and generator outputs, load the program listed in Table 3, press the reset key and start the program running with the EC80 command. Then strike any key on the keyboard. This should cause the drive l.e.d. to light, indicating that the drive output is low, and the tone generator should be enabled. Then strike another key. Now drive should go high, the drive l.e.d. should go out, and the tone generator output should be inhibited. Repeated

entry of keyboard characters in this manner will toggle the drive output from high to low and back again as many times as required.

Table 3. Drive output test program.

```
0C80: DF 61 30 FC DF 5F 18 F8
```

RTTY software

The main features of the rtty program are described followed by the operating instructions, illustrating the start-up of the program and the various commands used in transmitting and receiving messages. The machine code version of the rtty program is listed in Table 4. Copies of the full assembly listing, which runs to some 20 pages, are available direct from the author.

Receive mode

The main functions of the receive section of the rtty program are to translate incoming Baudot characters to ascii, to deposit them in the ascii text buffer, and to display them on the tv screen. In addition, the characters can be output from the text buffer to the printer. Several features have been included in the receive section of the program to allow error correction and to allow reply messages to be prepared for later transmission.

- The program tests the uart status as each character is received. If a status error (i.e. framing or overrun error) is detected, the received character is discarded and replaced by a space character. This is very useful under noisy conditions, or when receiving characters at the wrong speed, considerably reducing the number of garbled characters displayed and printed.
- If an incoming letter shift or figure shift character is corrupted so that subsequent characters are displayed in the wrong shift, it is possible to inject a shift correction character via the keyboard to restore the correct shift. For example, if a series of numbers are displayed, and it is suspected that they should be letters, the <SHIFT> L (lower case L) command can be typed. This inserts a Baudot letter shift into the character stream, and all following characters will then be displayed as letters (until, of course, a figure shift character is received, or a <SHIFT> F command is typed at the keyboard). This feature is again extremely useful under noisy conditions particularly when the transmitting station sends line after line of plain text without shift characters.
- The program automatically inserts carriage return/line feed (CRLF) into the incoming message stream, at the first space following the first 64 characters on a line. Thus when using the printer, overprinting at the end of the line is prevented.
- All received message characters are displayed in lower case on the screen to distinguish them from transmitted characters which are displayed in upper case.
- When receiving messages, it is possible


0C. Larger values of the constant will reduce the speed of callsign transmission, and smaller values will increase it.

Using the program

The rty program is now ready for use. After loading it into memory, strike 'reset' and start the program running at address 0C80, using as usual the EC80 command, followed by the time in hours and minutes (24-hour clock) if the real-time clock is fitted;

for example: EC80 1715.

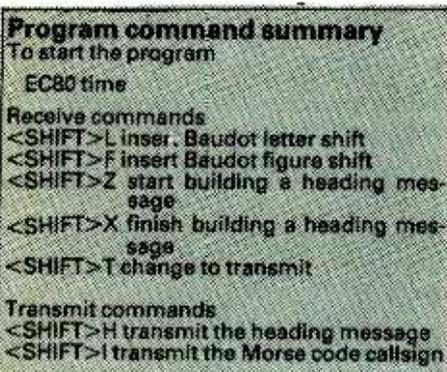The time, as set up above, will be displayed on the top line of the screen and will be updated every minute thereafter. If the clock is not fitted, simply type the EC80 command by itself to start the program.



Receiving rty messages

On start-up, the program goes automatically into receive mode, and incoming Baudot characters are translated to ascii and displayed in lower case on the screen. If the printer is fitted, the ascii characters will also be printed.

When in receive mode, there are five command characters which can be entered from the keyboard. Each of these characters is a shift character; that is, to enter a command, hold down the <SHIFT> key, strike the command key, then release the <SHIFT> key. The commands are

- <SHIFT>L: insert Baudot letter shift into the incoming message
- <SHIFT>F: insert Baudot figure shift into the incoming message
- <SHIFT>Z: start building a heading message
- <SHIFT>X: finish building a heading message
- <SHIFT>T: change to transmit.

The <SHIFT> L and <SHIFT> F commands are very useful for changing the Baudot shift of incoming message characters when previous shift characters have not been received correctly.

The <SHIFT> Z and <SHIFT> X commands are used to set up the one-line heading message on the top line of the display. This message can then be transmitted later when in transmit mode. To set up the message, input the <SHIFT> Z command. This causes a flashing arrow to appear at the top right hand corner of the screen, signifying that the system is ready to accept a new message. Also, a row of dots is displayed on

the top line, indicating the maximum extent of the message area.

Now type in the message. As each character is input, it will appear on the top line. When the end of the line is reached, the next character will appear back at the beginning of the message area. If a typing mistake is made, give the <SHIFT> Z command again and retype the line from the beginning.

When the message is complete, input the <SHIFT> X command. The flashing arrow will then disappear, and any further keyboard characters (except commands) will be ignored.

The heading message can be set up or changed at any time whilst in receive mode. Note that when setting up the message, incoming Baudot characters are still displayed on the remaining lines of the screen without interruption. Therefore it is possible to tune in to a station, ascertain its callsign, then set up an appropriate reply, all without missing any incoming characters.

Transmitting rty messages

The <SHIFT> T command changes the program from receive to transmit mode, whereupon the drive output from the Nascom goes low. To send a message, simply type in the required text at the keyboard. As each character is transmitted via the uart, it appears in upper case on the screen, and hard copy is produced on the printer.

In transmit mode there are three command characters:

- <SHIFT>H: transmit the heading message
- <SHIFT>I: transmit the station identification in Morse code
- <SHIFT>R: change to receive mode.

The <SHIFT> H command causes the top line of the display to be transmitted (the whole line, including the time, if the real-time clock is fitted, or the message only if the clock is not fitted). The command causes the line to be transmitted once; to transmit it more than once, simply type <SHIFT> H as many times as required.

The <SHIFT> I command causes the program to transmit the Morse callsign to identify the station, and can be used at any time whilst transmitting.

The <SHIFT> R command causes the program to change back to receive mode, and the drive output goes high.

The final test

Before using the rty program on the air, it can be tested using a cassette recorder in place of the transceiver. That is, messages are 'transmitted' to the recorder, and then 'received' by playing back the tape. This method of operation was used extensively when developing the program, to make sure that the message characters were being transmitted exactly as expected (and this technique has proved to be even more useful in developing other data communications programs such as Amtor which transmit and receive synchronous bit streams).

Experience

On the air, the system described in this article has been in regular use at G3NRW for over a year, and many very interesting contacts have been made on h.f. and v.h.f. Low power operation on 20m has been particularly rewarding – you simply can't beat the thrill of getting a 539 report from Italy when running 50 milliwatts of rty to a dipole – and the many features built in to the program have more than proved their worth.

There are, of course, limitations in the software, arising mainly from the very small memory available. With not one single byte to spare there was just no room, for example, to store a library of standard messages (such as 'RYRYRY' or station description), which would considerably reduce typing effort on transmit. However, the whole exercise has been extremely instructive, in that it forced me to find out exactly how Nas-sys works and how it could be used to maximum efficiency in supporting the required input/output functions.

On the hardware front, few problems were experienced in making the computer system work by itself, but the fun really started when the system was attached to the h.f. transceiver. On receive, r.f. hash from the computer virtually blotted out all but the strongest signals, and on transmit an output power greater than about 15 watts caused the computer to stop running. Eventually, after much experimentation with ferrite beads, decoupling capacitors, r.f. chokes and screened leads, almost all of the interference in both directions was cured by connecting a single 150pF capacitor between the +12V d.c. supply and ground. A simple remedy, but it took a long time to find.

Finally a special thankyou to Bob, EA5CNG (perhaps better known in the UK as G3FXG). Bob has been using the program on his Nascom 2 for several months and has provided much useful feedback and suggestions for further development. Incidentally, the program itself was originally transmitted to Bob over the air, Nascom to Nascom on 20m, and since then several other experiments in direct computer-to-computer communication between the UK and Spain have been carried out. But that is yet another story!

References

- 1 'RTTY The Easy Way'. A popular booklet describing how to build simple rty terminal units and two-tone generators. Published by the British Amateur Radio Teleprinter Group (BARTG) at £1.15 including packing and postage. Available from the BARTG Secretary, 27 Cranmer Court, Richmond Road, Kingston-upon-Thames, Surrey.
- 2 Assembly listing of the G3NRW RTTY Program. Available direct from the author at £2 to cover stationery, photocopying and mailing at 7 Daubeney Close, Harlington, Dunstable, Beds.
- 3 'Two-tone terminal unit'. A three-part article describing an a.m. terminal unit, published in the *BARTG Newsletter*: March/June/September 1979. 

Common-mode rejection explained

Common-mode-rejection ratio characterizes the ability of a differential amplifier to discriminate between the differential-mode and the common-mode components of a signal. It is often conveniently ignored in amplifier circuit analysis because in many op-amp applications – perhaps the majority – the non-inverting input is connected to earth and a large amount of d.c. negative feedback forces the inverting input to be close to earth, so the common-mode component is insignificant, even in second-order calculations. But there are some practical op-amp circuits, such as direct-coupled voltage followers, in which the finite c.m.r.r. cannot be ignored. This article clarifies the c.m.r. properties of an op-amp – its origin and meaning, its graphical interpretation and its representation by a voltage generator for circuit calculations. A second article deals with practical aspects of c.m.r. and explains how c.m.r.r. can be measured directly.

Classification of op-amps

An understanding of the origin of common-mode rejection of a real op-amp can be built up by introducing a classification system. Postulate initially the existence of an almost perfect op-amp having the symbol shown in Fig. 1(a). This symbol is almost the same as that used for any differential voltage amplifier but the vertical side of the triangle is thickened to denote that the amplifier characteristics depart from the conventional 'ideal' (infinite input impedance output admittance and bandwidth) in that there is a finite voltage gain A . The total instantaneous input signal V_+ and V_- can be considered as two parts, (b), a c.m. component V_C given by $(V_+ + V_-)/2$, and a d.m.c. V_D defined as $V_+ - V_-$. There is general agreement in the literature that the meaning of c.m.c. is the algebraic average of V_+ and V_- , as just defined. There is an alternative choice for d.m.c. of $(V_+ - V_-)/2$ which corresponds to $V_D/2$. This is certainly useful in analysis, as shown by redrawing (a) in the form of (c).

The quasi-perfect op-amp, which I shall term a Class 1, is completely specified by a single transfer characteristic, (d). For all values of V_C this is a straight line $a_0 b_0$ with slope $+A$ that passes through the origin of co-ordinates on a plot of V_0 vs V_D . So $V_0 = AV_D$. A is clearly the d.m. gain, i.e. $A = A_D$. In elementary analyses a Class 1 op-amp is implied, usually with the additional assumption $A_D \rightarrow \infty$ corresponding to a transfer characteristic coincident with the vertical axis.

The gain A_C for the c.m.c. is zero. Thus

by B. L. Hart

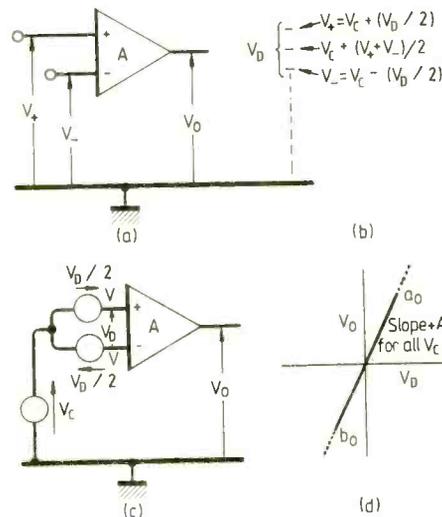


Fig. 1. Symbol for 'quasi-perfect' op-amp uses thickened line to denote non-ideal behaviour (a). Signals V_+ and V_- can be split into common-mode component V_C and differential component V_D (b). Redrawn version (c) emphasizes significance of V_C and V_D . This class 1 op-amp is completely specified by transfer characteristic (d).

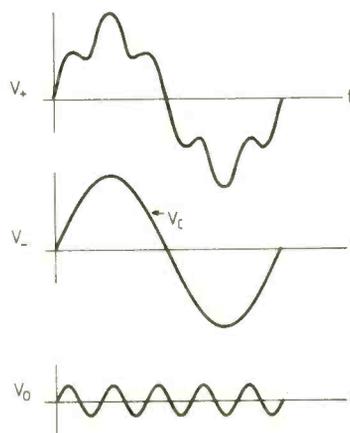


Fig. 2. Common-mode gain for class 1 op-amp is zero so if V_+ and V_- have the form indicated, V_0 is an amplified version of V_D only.

if V_+ and V_- have the form indicated in Fig. 2, V_0 is an amplified version of V_D only; V_C is totally rejected. This is an ideal never achieved in practice. The reason for this rejection is that though V_+ and V_- are applied at different input points to the amplifier they undergo identical magnifi-

The author

Bryan L. Hart is currently senior lecturer in charge of the electronics group in the School of Electrical and Electronic Engineering at North East London Polytechnic, where his principal research interests are device modelling and analogue integrated-circuit design techniques. Graduating in physics from Queen Mary College, London University, in 1951 and following national service in the Royal Signals, he obtained a postgraduate diploma in electronics and radio from Edinburgh University in 1954. After a period in industry as a radar research engineer with the Marconi Company he entered teaching in 1964.

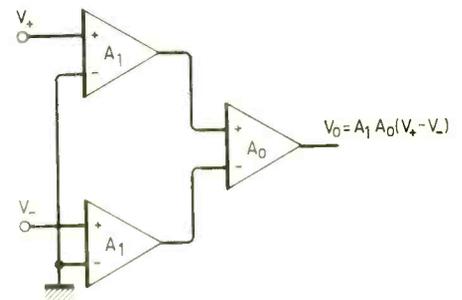


Fig. 3. Common-mode signal is rejected due to identical magnifications, though the signal paths are different, as indicated.

cation in their passage through it. (Magnification means an increase in signal amplitude without regard to polarity.) To emphasize the fact that the initial signal paths are different we can imagine the op-amp as comprising three separate units for which $A_D = A = A_1 A_0$, Fig. 3.

Class 2

A second class of op-amp is best defined graphically. For all magnitudes of V_C there is a single transfer characteristic – a straight line $a_1 b_1$ with slope $+A$ and intercept OX_1 on the V_D axis, Fig. 4. By definition OX_1 , arbitrarily shown as positive, is the input offset voltage and its

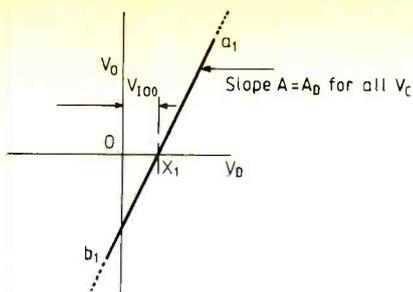


Fig. 4. Class 2 op-amps have straight-line transfer characteristic with intercept on the V_D axis, equal to the input offset voltage, V_{I00} , arising simply from small differences in the active devices.

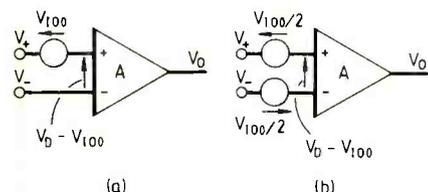


Fig. 5. Class 2 op-amp is represented by a class 1 with an offset voltage generator in either of its inputs (a). Alternatively, for analysis, offset voltage can be split into equal components one in series with each input (b).

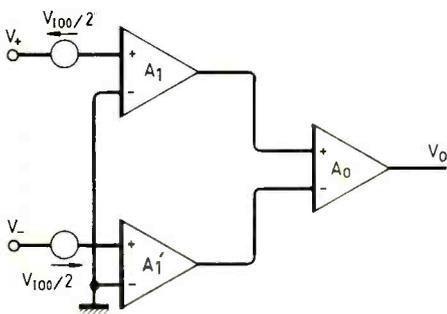


Fig. 6. Unequal magnifications of V_+ and V_- together with offset voltage are taken into account in this class 3 equivalent circuit.

magnitude is V_{I00} . The cause is due to a number of factors, including the nature of the active devices used in the amplifier and it could arise merely through a small difference in the emitter areas of two otherwise identical bipolar junction transistors forming part of a long-tailed pair in the input stage.

A Class 2 op-amp can be represented by a Class 1 op-amp with an offset voltage generator in series with either of its input terminals as shown in Fig. 5(a), in which the non-inverting input terminal is arbitrarily chosen. For analytical convenience, V_{I00} can equally well be split into two equal components, one in series with each input terminal, as in Fig. 5(b). Then

$$V_0 = A \{ V_+ - (V_{I00}/2) \} - A \{ V_- + (V_{I00}/2) \}$$

and substituting for V_+ and V_- gives

$$V_0 = A_D (V_D - V_{I00}) \quad (1)$$

Notice that $A_D (=A)$ now relates to changes in V_0 and V_D i.e. $A_D = \Delta V_0 / \Delta V_D$. V_{I00} , unless zero, causes a d.c. offset at the output. V_C is still completely rejected as V_+ and V_- are magnified equally in passing from input to output.

Class 3

Complications must be expected when the signals V_+ and V_- are magnified by unequal amounts in their passage through the amplifier, as is the case in practice. Taking V_{I00} into account, the equivalent circuit representation of a Class 3 op-amp is shown in Fig. 6. In this case

$$V_0 = A_0 \{ V_+ - (V_{I00}/2) \} - A_0 \{ V_- - (V_{I00}/2) \} A_1'$$

Substituting for V_+ and V_-

$$V_0 = \{ A_0(A_1 + A_1')/2 \} \{ V_D - V_{I00} \} + A_0(A_1 - A_1') V_C$$

which can be rewritten

$$V_0 = A_D (V_C - V_{I00}) + A_C V_C \quad (2)$$

where by definition

$$\begin{aligned} A_D &= \text{d.m. gain} \\ &= \Delta V_0 / \Delta V_D \text{ with } V_C \text{ constant} \\ &= \{ A_0(A_1 + A_1')/2 \} = A_0 \bar{A}_I \\ A_C &= \text{c.m. gain} = \Delta V_0 / \Delta V_C \quad V_D \text{ const.} \\ &= A_0(A_1 - A_1') = A_D \Delta A_I. \end{aligned}$$

The voltage V_0 contains an undesirable c.m.c. because of the existence of a non-zero gain difference ΔA_I . This arises through unbalanced passive and active component parameters.

A quantitative description of the extent to which a differential amplifier rejects the c.m.c. in favour of the d.m.c. is the common-mode rejection ratio ρ or k_{CMR} , the usual definition of which is

$$\rho = |A_D / A_C| \quad (3)$$

Thus $\rho = |\bar{A}_D / \Delta A_I| \quad (4)$

Although this indicates an origin for c.m.r.r. its potential usefulness to a device designer or circuit engineer for calculating ρ to any degree of accuracy depends on the particular amplifier configuration. One circuit for which this is applicable is the single-stage resistively-loaded fet long-tailed pair differential amplifier shown in Fig. 7, in which the output in question is taken from the drain of Tr_2 .

The low-frequency incremental output resistance of the tail current generator is assumed infinite: the nominally matched n-channel j-fets have voltage amplification factors μ_1 and μ_2 . It can be shown (see Part 2, in which a derivation is given for completeness) that

$$A_1 = \lambda \mu_1 / (1 + \mu_1) \text{ and } A_1' = \lambda \mu_2 / (1 + \mu_2)$$

where λ is a constant fixed by a resistor ratio. Putting

$$(\mu_1 + \mu_2)/2 = \mu (\gg 1) \text{ and } \mu_1 - \mu_2 = \delta \mu (\ll \mu)$$

it follows that

$$1/\rho = |\delta \mu / \mu^2|. \quad (5)$$

As μ usually only weakly depends on operating current, so does ρ . Equation 5 will be familiar if you recall the use of matched thermionic valves in d.c. amplifiers for biomedical applications. Accord-

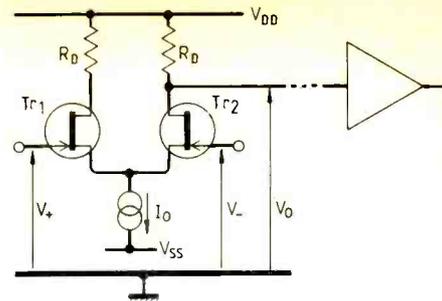


Fig. 7. Typical circuit for which common-mode rejection is quantitatively given by the ratio of the mean amplifier gain to the difference in gains.

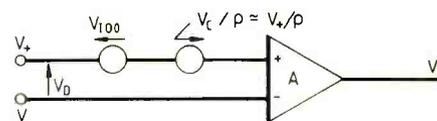


Fig. 8. Effect of finite c.m.r. can be allowed for by including a voltage generator V_C/ρ in series with one of the inputs.

ing to Middlebrook¹, effectively the same result was obtained — though by a different analytical technique — for a valve stage by, among others, Parnum² as long ago as 1945. What is perhaps not generally appreciated is that this equation also applies to the case of a single-stage resistively-loaded and voltage-driven long-tailed pair amplifier using bipolar transistors. This can be shown by an extension of the proof given in the Appendix, or alternatively follows from a different approach³.

For the case of bipolar transistors $\mu = g_m r_{ce}$ where $g_m \approx 40 I_c \text{ mS}$, the quiescent collector current I_c being expressed in mA, and r_{ce} in $k\Omega$ is the low frequency collector incremental output resistance with base-emitter voltage drive. Values for r_{ds} for a fet and r_{ce} for a bipolar transistor are normally comparable in magnitude but $g_m \gg g_{fs}$ at similar operating current levels. As a result, for a modern planar bipolar transistor, μ is considerably greater than that for a fet, typically about 5000. Consequently, for a given percentage match in μ , ρ for the bipolar stage exceeds that for the fet stage. Actually, the majority of op-amp input stages are not simple long-tailed pairs: ingenious circuit design techniques attempt to obtain a ρ superior to that given by equation 5. Nevertheless equation 4 is still a useful relationship from a system viewpoint. As specified by device manufacturers, ρ is obtained from measurements on production samples and is commonly expressed in dB: even low-cost op-amps typically have $\rho \sim 80 \text{ dB}$.

Equations 2 and 3 give a clue to the equivalent circuit representation of c.m.r. as we can combine them to obtain

$$V_0 = A_D \{ V_D - V_{I00} + V_C/\rho \} \quad (6)$$

Like offset voltage, the effect of finite c.m.r. can be allowed for by including a voltage generator (V_C/ρ) in series with one of the input terminals of the op-amp, as in Fig. 8. The positive sign for the third term, as with the negative sign for the second, arises through an arbitrary choice.

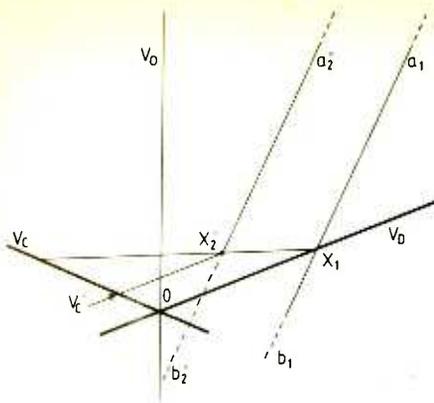


Fig. 9. 'Three dimensional' characteristic plane displays functional dependence of V_0 on the two dependent variables V_D and V_C . As A_D and A_C are presently assumed constant, equation 2 is the equation of a plane surface that is defined by any two parallel straight lines such as a_1b_1 , corresponding to $V_C=0$ and $a_2'b_2'$ for $V_C=V_C$, that cut the plane $V_0=0$ at points X_1 and X_2' respectively. As V_{I00} is constant the incremental form of equation 2 is

$$\Delta V_0 = A_D \Delta V_D + A_C \Delta V_C \quad (7)$$

A geometrical interpretation is given in Fig. 10, in which a_2b_2 is the projection of $a_2'b_2'$ on the plane $V_C=0$ and $a_1'b_1'$ is the projection of a_1b_1 on the plane $V_C=V_C$. Suppose, initially, we are biased at the point P. Then an increase in both V_D and V_C can be imagined to occur in two separate steps. The change from P to Q with V_C constant (at zero) gives $\Delta V_{01}(=A_D \Delta V_D)$; similarly, the change from Q to R at constant V_D gives $\Delta V_{02}(=A_C \Delta V_C)$. Point S is the projection of R on the plane $V_C=0$.

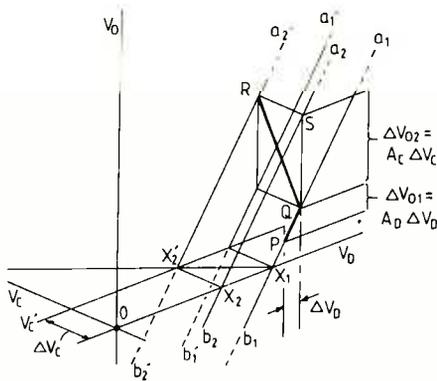


Fig. 10. With V_{I00} constant, the incremental form of the V_0 equation is as shown.

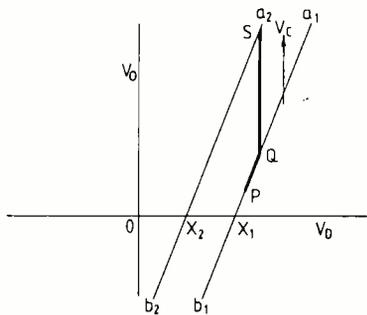


Fig. 11. Transfer characteristic of class 3 op-amp comprises a series of parallel lines, two of which are shown, corresponding to the projection of lines such as $a_2'b_2'$ on the plane

The way in which the sign-uncertainty is dealt with in practice will be considered later (Part 2). For calculation, equation 6 is unnecessarily complicated and can be simplified. Thus from equation 6

$$V_+ - V_- = V_D = (V_0/A_D) + V_{I00} - V_C/\rho$$

$$\text{or } V_- = V_+ - (V_0/A_D) - V_{I00} + V_C/\rho$$

substituting $V_- = 2V_C - V_+$ in this expression gives

$$V_C = V_+ - (V_0/2A_D) - (V_{I00}/2) + V_C/2\rho$$

$$\text{or } V_C = [V_+ - (V_0/2A_D) - V_{I00}/2] / [1 - 1/2\rho]$$

Typically, $V_0 < 10V$, $A_D > 80dB$, $\rho \gg 1$, $V \sim 1mV$. Hence, if $V_+ \gg V$, then $V_C \approx V_+$ and $V_C/\rho \approx V_+/\rho$.

Mathematically, equation 2, unlike 1, indicates that V_0 is a function of two dependent variables, V_D and V_C . So to display the functional dependence we must plot in three dimensions. In Fig. 9 the axis for V_C is perpendicular to the V_0 and V_D axes. As A_D and A_C are presently assumed constant, equation 2 is the equation of a plane surface that is defined by any two parallel straight lines such as a_1b_1 , corresponding to $V_C=0$ and $a_2'b_2'$ for $V_C=V_C$, that cut the plane $V_0=0$ at points X_1 and X_2' respectively. As V_{I00} is constant the incremental form of equation 2 is

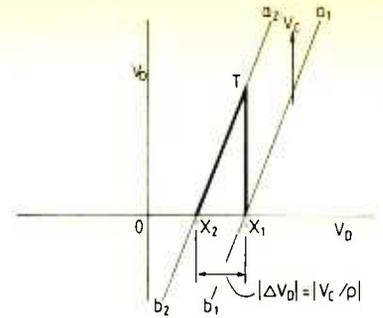


Fig. 12. Construction not only gives information about line spacing but also leads to an alternative definition of common-mode rejection that is useful for measurement.

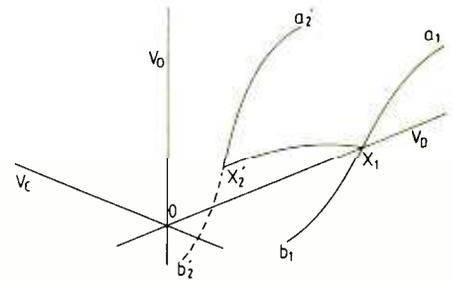


Fig. 13. Class 4 op-amps are defined by non-planar characteristic surface such as that shown.

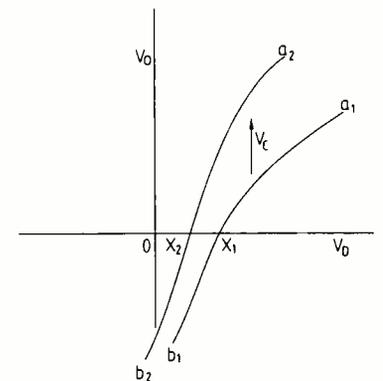


Fig. 14. Family of Class 4 transfer characteristics associated with Fig. 13 obtained by projection onto the plane $V_C=0$ are now neither straight nor parallel.

The transfer characteristics of a Class 3 op-amp comprise a series of parallel straight lines – two of which are shown in Fig. 11 – corresponding to the projection of lines such as $a_2'b_2'$ on the plane $V_C=0$. The lines are equally spaced because $|A_C|$ is constant: a_2b_2 is drawn to the left of a_1b_1 because we are assuming $A_C > 0$. The construction in Fig. 12 not only gives information about the spacing of the parallel characteristics but also leads to an alternative definition of c.m.r.r. that is useful for measurement.

Suppose we operate at $V_0=0$ corresponding to $V_C=0$ and $V_D=V_{I00}$, i.e. point X_1 . If $\Delta V_0=0$ when V_D and V_C both change, then the path traced out is X_1 to T (V_D constant, V_C changes) and T to X_2 (V_C constant, V_D changes). From equation 7,

$$0 = A_D \Delta V_D + A_C \Delta V_C$$

The spacing of the characteristics in Fig. 12 is thus

$$|\Delta V_D| = |\Delta V_C/\rho| \approx |\Delta V_+/\rho|.$$

The same result would, of course, be obtained had we started with $V_0=V_0'=0$ and again made changes in V_D and V_C , this time for $\Delta V_0'=0$. Now V_D for $V_0=0$ is defined as the input offset voltage V_{I0} , so the reciprocal of ρ is the rate of change of input (offset) voltage with common mode input voltages. Thus

$$1/\rho = |\Delta V_D/\Delta V_C| \text{ for } V_0 \text{ constant at zero} \\ = |\Delta V_{I0}/\Delta V_C| \quad (8)$$

On data sheets the input offset voltage is commonly given two subscripts, e.g. V_{os} or V_{I0} : an additional subscript (0) is used in this article to refer to the usual practical measurement condition $V_C=0$. In general

$$V_{I0} = V_{I00} \pm V_C/\rho \approx V_{I00} \pm V_+/\rho.$$

The negative sign applies for $\Delta A_T > 0$. Notice for comparison, that in a Class 2 opamp $V = f(V_C)$ so for that case the line

X_1X_2' in Fig. 9 would be parallel to the V_C axis.

Class 4

A fourth class is defined by a non-planar characteristic surface such as that shown in Fig. 13. The associated family of transfer characteristics obtained by projection on to the plane $V_C=0$ are now neither straight nor parallel, Fig. 14.

A_D , A_C and ρ are all dependent on the d.c. operating conditions but can be considered sensibly constant if the changes in V_0 , V_D and V_C about the selected bias point are small enough for the characteristic surface to be well-approximated by a tangent plane. Then

$$A_D = \partial V_0/\partial V_D \text{ at constant } V_C \\ A_C = \partial V_0/\partial V_C \text{ at constant } V_D \\ 1/\rho = |\partial V_{D0}/\partial V_C| \text{ at constant } V_0.$$

To be continued

Current dumping review — 1

Crossover distortion is a problem in designing any class B audio amplifier. Bias current provides the basis for the usual solution, but introduces the threat of thermal instability. Current dumping is an alternative to bias current, aiming to abolish crossover distortion without further difficulty.

In his original article in this periodical (December 1975), P. J. Walker explains a new technique for abolishing crossover distortion in audio amplifier output stages. His ideas are backed by the commercial success of the Quad 405 amplifier, and the subsequent 1978 Queen's Award for technological achievement.

Seven years have now passed, but the discussion continues unabated. The early contributions in these pages were from practitioners in the audio field, including many well-known names, while later material has come from universities over the world. This article presents in good order the results so far obtained. The discussion reads rather like an epic, full of sudden reversals of fortune.

As the new method is often referred to as something of a mystery, it will first be related in terms of familiar ideas. Walker's own explanation is in terms of the circuit of Fig. 1. For small output currents the driver amplifier A itself supplies the load Z_L directly, via Z_3 . Larger currents turn on a dumper, and as Z_4 is chosen to be small the dumper then supplies the bulk of the output current. Then A never has to supply much power, and so it can operate in class A, with no crossover distortion. Indeed, A is just the usual driver amplifier, and we shall refer to it as such.

It is therefore appropriate to call the output transistors in Fig. 1 the "current dumpers", and the substantial distortion which remains will be their crossover distortion. Walker has shown how to choose circuit values that result in complete cancellation of this distortion. It is this choice which is the heart of the matter.

Feedback explanation

To start detailed discussion of Fig. 1 with an intuitive idea of its working, that offered by P. Baxandall (July 1976) relies on the most familiar ideas.

He starts from a circuit similar to that of Fig. 2, with S_1 closed and Z_4 shorted as drawn. Now imagine Z_3 removed. There will be no feedback, and the V_{out}/V_{in} characteristic will look like that of Fig. 3, except that the central segment will be horizontal. This occurs while V_{in} makes progress across the dead region, while the output of A is traversing the voltage gap

by Michael McLoughlin

between the levels required to drive the transistor bases. Adding Z_3 assists matters: while this gap is being crossed there is still some output to the load, as shown by the reduced but positive slope of the central segment.

Now open S_1 of Fig. 2, to provide 100% voltage feedback to A. The variation in open-loop gain shown will be violently assaulted, and the ratio of the gains in the dumpers-off and dumpers-on regimes will be very close to unity. There is now scarcely any crank between the three segments of Fig. 3. (Also the horizontal scale has changed dramatically.)

Baxandall observes that there is now a way to make all three segments line up perfectly. All that is needed is a little extra feedback in the dumpers-on regime, to reduce the gain slightly to that found at the central segment. Then the outer segments tilt gently on their point of meeting with the central section, to provide a perfect straight line!

To provide the extra feedback it suffices to remove the short on Z_4 . When the dumpers are off this resistor has no influence on feedback, but when they are on the hotter end of Z_4 carries more output voltage than the load itself. So there is now extra feedback when the dumpers are on, as required. Naturally, Z_4 must be chosen with care to produce just the correct flexing in Fig. 3.

If desired, Z_2 may be connected between N and B in Fig. 2. It is however clearly quite unnecessary. Indeed its contribution to total feedback at N is retrograde, actually feeding back more of V_{out} when the dumpers go off. But if Z_2 is inserted, its harmful effect can readily be cancelled by an increase in Z_4 , to boost the desired feedback as necessary.

When the correct Z_4 is in circuit the transfer characteristic is perfectly linear. As a result the grounded terminal of the signal source V_{in} may now be connected instead to V_{out} , and the signal source made to float. Of course, much less signal will

Michael McLoughlin is a mathematics teacher at Haberdashers' Aske's School, Elstree.

now be required for a given output.

Following Baxandall closely we have arrived at Walker's circuit in Fig. 1, with S_1 as drawn. And when S_1 is switched the essential invention now appears as the introduction of Z_4 , to provide a little extra feedback in the dumpers-on regime to counter the extra gain introduced into the system when the dumpers bypass Z_3 .

Algebra

Baxandall's intuitive explanation can easily be extended into algebra, to derive the Walker balance condition on the four bridge components. The discussion will now centre on Fig. 1, taking the floating "zero volts" rail as zero for the discussion of all voltages. It should be helpful initially to think of this line as "earth", and to regard Z_3 and Z_4 as amplifier load resistors connected to this.

We shall study the total load current I flowing to "earth", and deduce the balance condition in three short paragraphs. Before starting define F as that fraction of output voltage across Z_3 fed back to the negative input terminal of A. And recall that for an amplifier of infinite gain the closed-loop gain is inversely proportional to F.

(A) When a dumper is on, its base-emitter junction cannot support voltage variations, so $F=1$. But when the dumper goes off the junction is an open circuit, and $F=Z_1/(Z_1+Z_2)$. So F has been multiplied by this last fraction. As A has infinite gain, the closed-loop gain to B promptly multiplies by the inverse fraction, namely $1+Z_2/Z_1$.

(B) However, as the dumper goes off the load impedance which controls I rises from $Z_3||Z_4$ to Z_3 . Dividing, we see that load impedance has been multiplied by $(Z_3+Z_4)/Z_4$, which is $1+Z_3/Z_4$.

(C) There is no change in gain through to I when the dumper goes off if the gain multiplies by the same factor as the load impedance. The relevant factors are at the ends of the two previous paragraphs, and concur if the Walker condition is met:

$$Z_2/Z_1 = Z_3/Z_4 \quad (1)$$

Actually the argument neglects two minor factors. When F was established for the dumpers-off condition in (A), the effect of Z_4 on the potential division was neglected.

impedance will be very small. In terms of algebra this bridge model is very powerful, and also in terms of intuition. Fig. 5 with an inductor at Z_4 and a capacitor opposite shows that the basic idea is just to balance a traditional LC bridge, according to $L=R_1R_3C$.

Feedforward explanation

It may seem strange that current dumping claims to cancel distortion completely. Certainly in normal correction of error by negative feedback the distortion can never be totally eliminated because a residue must be left to be sensed and so drive the amplifier into opposing the source of distortion. But what if one sensed the distortion in the output current (by comparing it with input voltage) before it was fed into the load, and then injected a further correction current into the load, but forward of the sensing element? The difficulty disappears, because correction does not now reduce sensing and so perfect cancellation of error is then theoretically possible. For example, the crossover distortion of a heavy-duty class B amplifier can be corrected perfectly in principle by a small class A amplifier of high quality.

In practice resistor tolerances do impose serious limitations, though these do not often seem to be analysed. In contrast to feedback, this type of error correction is called feedforward, and has sometimes been aired here (May 1972, October 1974, twice in May 1978). But suppose only four 5% resistors are used in the defining chains. Then the correction may be 20% out. One would do better to increase the

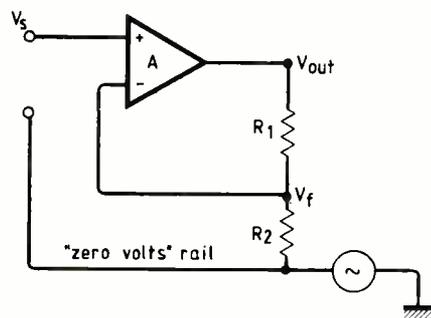


Fig. 4. Amplifier of infinite gain must produce V_f equal to V_s even when a voltage source drives the floating "zero volts" rail with respect to which these quantities are measured. Think what would happen if V_f fell short.

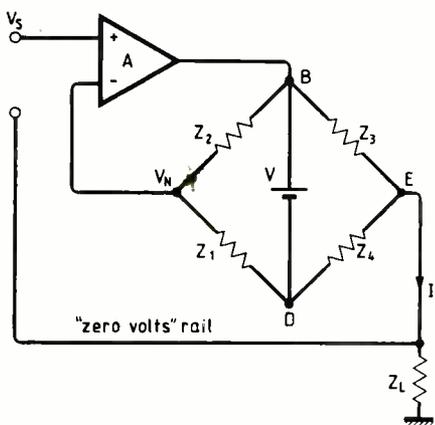


Fig. 5. Modelling the dumpers of Fig. 1 as a voltage source V_f , Vanderkooy & Lipshitz redraw the circuit as a bridge.

gain of the main amplifier by a factor of five, and then use feedback to cut it back again. And this is a great deal easier to do. Nevertheless, the idea of feedforward demonstrates that a claim to perfection of error correction is not objectionable in principle.

Does current dumping use feedforward? Following Baxandall we have presented it entirely in terms of feedback. Imagine Z_4 of Fig. 1 shorted: then the transfer characteristic returns to the style of Fig. 3. The solution was to consider the slope of the central section as basic, and to insert just the right Z_4 to adjust into line the gain of the outer segments. The picture is one of negative feedback being adjusted during the cycle, to make the gain conform to its value at the centre. This is not classical feedback, because the feedback fraction is varied during the cycle, but it is negative feedback, and no further picture is required.

Walker's explanation

In his original article, however, Walker gives a perfectly valid discussion of Fig. 1, which is entirely feedforward in style. He regards Z_4 as the output sensing element, and compares V_s with the sensor voltage I_4Z_4 . His argument may be simplified and presented as follows.

A is taken to have infinite gain, so the voltage between its input terminals is zero. Now think of both input terminals as a new "zero volts" point for reference. Viewed from here, $-V_s + I_4Z_4$ appears at the far end of Z_1 . As usual when such a signal is fed to the negative input terminal of an amplifier, it reappears at the output terminal but multiplied by $-Z_2/Z_1$. To obtain this output voltage relative to the floating rail of Fig. 1, it is only necessary to add V_s again. (Ignore the expression V_B in Fig. 1.)

So $V_s - I_4Z_4$ is heavily amplified, and if I_4Z_4 is at all sluggish in following V_s , a large protest voltage will appear at the output of A, forcing extra current through Z_3 forward of the sensing element Z_4 . We have just found the output voltage, so we may choose Z_3 and then write down I_3 . Then add I_4 to obtain the total output current, which is just

$$\frac{1}{Z_3} \left[\frac{Z_2}{Z_1} (V_s - I_4Z_4) + V_s \right] + I_4.$$

It is now clear that if Z_3 is chosen according to (1) then I_4 actually cancels out in this expression! Whatever particular I_4 the dumpers choose to allow at any particular time, the output current will remain untouched, provided just the right Z_3 has been fitted.

The language used here is entirely feedforward, though the situation is not classical, for two reasons. Firstly, the protest volts generated by A do actually power the sensing element Z_4 as well as the sensor bypass Z_3 . Also Z_3 is not a pure bypass element, but reports back to the amplifier via Z_2 , as can be seen clearly in the dumpers-off condition.

Mr Walker's accompanying discussion seems to take as basic the gain when the

dumpers are on, feeding current through $Z_3||Z_4$. Of course there will be a short departure from these arrangements during crossover. And during this brief period of error a suitable correction will be fed through Z_3 . The whole picture is perfectly valid, and indeed nothing more than this feedforward is required to explain current dumping.

Much binding

Suppose a tuned circuit is energized at its resonant frequency. Then the circulating current is large, compared with its value at adjacent frequencies. Bloggs explains that this is because C is cancelling the high impedance offered by L. Smith objects that this could not be more false. It is L that is cancelling the high impedance offered by C! And so they rattle on.

Obviously high farce has effected an entry. This illustration establishes the principle that a complex situation may sometimes be viewed quite validly in alternative ways. In this case the fullest understanding seems to be obtained when one has seen both explanations, seen that they are both valid, and grasped that they are complementary views of the same situation.

There seems to have been a similar division of opinion about the operation of Walker's amplifier: does it use feedback or feedforward? In good part the discussion seems to stem from a resolve to class a new and hybrid idea as one or the other of the two existing categories. But a major factor might be a failure to realize that a complex idea can sometimes be explained in several different ways. Our own view is that current dumping may be adequately explained by feedback, or by feedforward, or as a bridge, or as a measuring instrument (see below).

Everyone agrees that use of (1) aligns the three segments of Fig. 3. But it is fruitless to argue whether this is because the correct Z_4 has been chosen to make the outer segment slope equal to that found at the centre (feedback), or because the correct Z_3 has been chosen to ensure that the central section slope concurs with the outer parts (feedforward). We followed Baxandall initially as a matter of taste (indeed so does Walker in November 1976): the feedback ideas involved are more familiar.

In their most recent article (cited later) Vanderkooy and Lipshitz again insist that feedforward alone is the only correct explanation. Their argument consists of a logical structure presenting a "conceptual development of current dumping from feedforward." But one has to ask "whose concepts?" An equally clear set of concepts is the basis for Baxandall's feedback explanation. (It is a mistake to list Baxandall's letter here in support of feedforward.) In short, an explanation in terms of feedforward, however clear, does nothing to exclude other explanations.

An objection

In Fig. 1 the value of Z_4 is carefully chosen to yield the correct additional feedback when the dumpers are on. But how can a single value of Z_4 cancel perfectly the

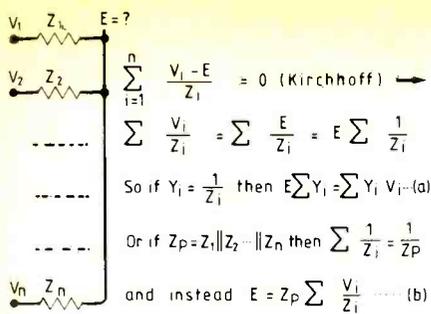


Fig. 6. Millman's theorem allows ready calculation of the voltage E at which a junction will settle. Strictly speaking it is result (a), stated in terms of admittances, and it is useful to abolish denominators in difficult algebra. Form (b) is more useful in easier cases.

peculiar vagaries of dumper V_{bc} ? And how can anyone assert such a thing without examination of the vagaries concerned?

The objection could easily be met by observing that the result is already secured by different thinking. But it can also be met directly and on the intuitive level by presenting the circuit as a measuring instrument. The dumper behaviour from instant to instant is measured by Z_4 , which controls the feedback accordingly to hold the gain constant. Naturally any talk of gain variation within a cycle refers to incremental gain. This intuition is built into a rigorous proof below. We shall not impose the detail on the printer, and all except enthusiasts are urged to bail out at once, as far as the next heading.

Replace the dumpers of Fig. 1 by a resistor R , to stand for the small-signal emitter input resistance of the operating dumper; this variable R connects from Z_2 to Z_4 . Now measure all voltages relative to the floating zero rail. Then for unit increment of V_B there will be an increment of V_N given by

$$\frac{Z_4 + \frac{Z_1}{Z_1 + Z_2} [R / (Z_1 + Z_2)]}{Z_4 + R / (Z_1 + Z_2)}$$

Add $1/A$ to this to yield ΔV_s . Now the ΔI resulting from the unit change in V_B is just the reciprocal of the impedance from B to E : write down this simpler expression. Then solve $\Delta V_s = K \Delta I$ in such a way that K does not depend on the varying R . This constant proportionality will provide an undistorted output. Provided it is noticed early that R only occurs as $R / (Z_1 + Z_2)$ and this quantity is labelled x , a page of work will produce a rigorous proof of (2). This time, Z_4 has been regarded as a measuring instrument, noting how much current R passes in response to changes of voltage at B , and then controlling gain accordingly.

There is the usual fallacy in that argument, which it is easier to correct after deriving the result. If the output volts of A rise one unit relative to the floating conductor, then relative to true ground they rise an additional $Z_L \Delta I$. This must be taken into account when calculating ΔV_s , which must therefore be augmented by a further $Z_L \Delta I / A$. But this addition does not contain R and is already proportional to

ΔI , so provided K has the value found as above a relationship of proportionality will still prevail between ΔV_s and ΔI .

This analysis is really an extension of Baxandall's feedback approach, showing that it can be extended to include any transistor behaviour, even when A is finite.

Algebraic explanations

In an attempt to dispel mystery the above-mentioned arguments have remained close to intuition, even at the cost of complexity. But we shall now study straight algebra, and discover much simpler arguments.

The obvious method of studying Fig. 1 is to regard Z_2 and Z_1 as a potential divider, whose lower end is at $I_4 Z_4$ volts and whose upper end is maintained a further $I_3 Z_3 - I_4 Z_4$ volts higher. Ignoring the expression in Fig. 1 an expression for V_N is therefore

$$I_4 Z_4 + \frac{Z_1}{Z_1 + Z_2} (I_3 Z_3 - I_4 Z_4)$$

Take A large: then this can be taken as an expression for V_s and tidied:

$$V_s = \frac{Z_1 Z_3 I_3 + Z_2 Z_4 I_4}{Z_1 + Z_2}$$

Suppose now $Z_1 Z_3 = Z_2 Z_4$ as in (1). Then the coefficients of I_3 and I_4 are equal in this expression for V_s . So the output current $(I_3 + I_4)$ has been locked into a proportionality relation with V_s , and the output is undistorted.

An even briefer analysis seems to underlie the remarks of J. Halliday (April 1976). He appears to rely on the circuit theorem of Fig. 6, which gives in two convenient forms the potential adopted at the meet of several impedances. We shall rely heavily on this theorem henceforward.

When Fig. 6 (form b) has been mastered, it will be easy to verify the expression for V_N marked in Fig. 1, where only two arms Z_1 and Z_2 are connected to marked voltages. Now $V_s = V_N$ because the gain of A is large. Simply by looking at that expression for $V_s = V_N$ it is clear that if $Z_4 / Z_1 = Z_3 / Z_2$ then V_s and $(I_3 + I_4)$ are trapped in a linear relation.

Given the expressions of Fig. 1, the last sentence provides a fifth proof that cancellation of distortion is possible, and gives the condition for it.

Output current

For practical reasons Z_4 is much smaller than Z_3 , and provided the balance condition holds then

$$Z_3 \gg Z_4 \Rightarrow Z_2 \gg Z_1 \Rightarrow Z_p \approx Z_1$$

(Strictly speaking the first four symbols should have modulus signs.) So the $V_s = V_N$ of Fig. 1 now simplifies to

$$V_s = V_N = (I_3 + I_4) \frac{Z_4}{Z_1} \cdot Z_p$$

and if $I = I_3 + I_4$ we have

$$V_s \approx I Z_4 \quad (3)$$

In other words the output current can be calculated simply by supposing that V_s is

applied to Z_4 , and it can be modelled by the output current I in the emitter follower circuit of Fig. 7 (with S_1 as drawn.)

The operator H

Before entering on our conclusions we have a duty to look at the difficult article of H. S. Malvar (March 1981). Its early algebra can be much simplified, as shown by K. G. Barr (June 1981). The article relies heavily on a multiplier B , which it will be safer here to call H , and it is used to relate two voltages of our Fig. 1 according to $V_D = H V_B$. This H is the most general possible multiplier, and it changes with V_B as necessary, to maintain the above equation true to what happens in an amplifier. Certainly if one makes a printout of these two voltages at small increments of either, then H could be listed in a third column. Indeed for a given amplifier H could be presented as a list opposite small increments of input signal to the amplifier. But of course such a system leaves the list for H violently dependent on any variations in driver gain that are being considered.

Well, briefly, there is no need to consider what happens when H is off-course by ΔH . The course is defined as above by what H does, and it cannot be off-course. ΔH is meaningless and should be set at zero throughout (equation 8 misleading). If this is not liked, then an alternative description of H must be given. Also it is clear from the above equation that one may not reason on the basis that $H=0$ when the dumpers are off (equation 12 wrong). And when A is allowed to tend to infinity, then his (6) requires either that R_3 does likewise, or R_4 tends to zero (equation 9 wrong). Finally, once it is admitted that a change in driver gain will cause shifts in H , the Maclaurin expansion used is not only incorrectly computed (equation 10 wrong) but quite invalid in method (H has been treated as a constant in the differentiation.)

Quad 405

Walker explains that he takes (1) as the basic design equation for the Quad 405 design, with $Z_1 = R_1$ and $Z_3 = R_3$, so that both are straight resistors. But Z_4 is an inductor L and Z_2 is a capacitor C . Ingeniously enough, substituting the necessary $j\omega L$ and $1/j\omega C$ in (1) yields nevertheless the frequency-independent balance condition found in the bridge model:

$$L = R_1 R_3 C \quad (4)$$

This ensures that the coefficients of I_3 and I_4 found at V_N in Fig. 1 are equal and will stay equal to each other at all frequencies.

But it does nothing to ensure that these coefficients remain constant as frequency varies, and disaster has in fact struck at this point. Indeed, simply by looking at (3) one can see that if Z_4 is an inductor then output current is inversely proportional to frequency. In circuit terms, what happens to the frequency response in Fig. 7 if Z_4 is an inductor?

This conclusion can be confirmed by substituting R_1 , $1/j\omega C$, R_3 and $j\omega R_1 R_3 C$

for the four bridge values in V_N of Fig. 1 and simplifying, to obtain

$$V_N = \left[\frac{j\omega R_1 R_3 C}{1 + j\omega C R_1} \right] I.$$

The bracketed factor is almost constant when ω is large, but its modulus does fall with frequency. Indeed, with $R_1=500\Omega$ and $C=120\text{pF}$ as in the Quad 405, the denominator is essentially unity below 1MHz. Hence V_N varies as f in the audio range, and output varies as $1/f$ there.

The use of L and C in the bridge has resulted in a ferocious dependence of gain on frequency. The solution applied is the use of massive negative feedback, applied in the usual way by switching S_1 in Fig. 1. This can be modelled by switching similarly in Fig. 7. In this figure Z_4 now causes no attenuation of output across Z_L at low frequencies, but at 20kHz it may reduce output noticeably. Suppose we decide that at 20kHz we will tolerate a 0.1% reduction in output volts. Then if $Z_L=8\Omega$, $Z_4=0.36\Omega$ inductive, so $L=2.85\mu\text{H}$. Actually $3\mu\text{H}$ is fitted.

Many pairs of L and C would satisfy (4), and there has been no explanation of the choice made. It seems that feedback is unable to overcome the effect on gain if L is any larger, even when the amplifier gain is infinite. It follows that above 20kHz the performance of this amplifier must begin to deteriorate, and this explains the exhortation not to make tests with square waves.

Somersaults

The operation of the circuit in Fig. 1 may now be summarized in a sentence. Firstly bridge values are balanced to ensure that $V_N \propto I$, and then the driver amplifier is used to ensure that $V_N = V_s$, thus locking into proportionality V_s and I.

This full discussion of current dumping equips us to examine the controverted points, and we shall now witness three successive somersaults before the end of this article.

Firstly Halliday, supported by Olsson (July 1976), rides in from the flank. He agrees with all that has been said, but points out that it is entirely superfluous. We have just seen that the method depends on deriving a feedback V_N proportional to $(I_3 + I_4)$. Then why not derive it from a small resistor in series with the load at r in Fig. 1?

Indeed, supposing that (1) holds and examining V_N of Fig. 1, the value of r required to give identical feedback voltage is readily seen to be $Z_P Z_4 / Z_1 \approx Z_4$. (The accurate figure is Z_3 / Z_4 .) And J. G. Bennett (April 1976) drives the nail home. Such an r will provide feedback strictly proportional to I, but Walker's bridge owing to tolerances cannot be expected to balance perfectly the two coefficients in V_N in Fig. 1. The bridge will not produce a feedback strictly proportional to I, and current dumping is actually worse than the simpler conventional approach proposed.

Walker in his reply does not oppose these arguments. He points instead to the real case where A is finite, and quotes

result (5) below, in a slightly different algebraical form. The result may readily be derived, by noting that if A is finite then a voltage V_B/A exists between the input terminals of A in Fig. 1. This yields a second expression for V_N , given on the left below and equated to that of Fig. 1:

$$V_s - \frac{I_3 Z_3}{A} = \left(\frac{I_3 Z_3}{Z_2} + \frac{I_4 Z_4}{Z_1} \right) Z_P \\ \Rightarrow V_s = Z_P \left[I_3 \left(\frac{Z_3}{Z_2} + \frac{Z_3}{AZ_P} \right) + I_4 \frac{Z_4}{Z_1} \right]$$

So V_s is again locked linearly to $(I_3 + I_4)$ if

$$\frac{Z_4}{Z_1} = \frac{Z_3}{Z_2} + \frac{Z_3}{AZ_P} \quad (5)$$

The usual difficulty arises from the floating zero-volts rail of Fig 1. The real output voltage of the amplifier is not just V_B : in fact $(I_3 + I_4)Z_L$ needs to be added. Divide by A and use the result to alter the figure used above for volts between the amplifier input terminals. But the extra term has I_3 and I_4 already balanced, leaving unaltered the above balancing requirement (5).

Thus the current dumping circuit can still provide freedom from crossover distortion with finite A. Further, fixing an eye on (5) and examining V_N of Fig. 1, it is now clear that the coefficients of I_3 and I_4 in that expression are no longer equal. Hence V_N cannot now be derived from a resistor in series with the load. Current dumping is sound after all, because Halliday's objection only applies when A is infinite.

But Walker does not go on to revise his explanation of the Quad 405 to show how he has used (5) instead of (1). Indeed, it would appear that he did use the last mentioned. For a start, his explanation is in terms of (1), and also of (4) which is a form of it. Further, the driver in the Quad 405 is a current output device whose working load adopts three values over the cycle. According to (5) there is still a solution: make the gain very large, and then the last term can be dismissed, together with its several gyrations. Then variations in A during the cycle will not upset the bridge balance. Now whether one thinks of A as infinite or merely as large, neglect of the third term of (5) means that the coefficients of V_N of Fig. 1 are set equal. And so identical feedback can be derived from the small resistor mentioned earlier. Halliday's criticism is sound: the Quad 405 would work better without its current dumping. These matters will recur in Part 2.

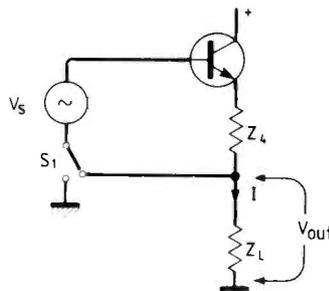


Fig. 7. Dumper output model.

In principle, however, current dumping is now once more of value, provided that A is not taken as large, but is allowed instead to influence (5). The dumpers may do as they please as the cycle progresses, provided only that A is not given too much work. So any crossover distortion caused by the dumpers, or indeed any other harmonics, noise, hum or delays that they introduce into the circuit will all cancel perfectly.

Tolerances

All that is theory, however, and the position is reversed for the third time when practical considerations are taken into account. Components do not have their nominal values, but are produced to tolerances. It follows that if A is large, the designer cannot give any serious weight to the last term in (5), whose contribution will be overrun by tolerance errors in the other terms. He might as well specify $Z_4/Z_1 = Z_3/Z_2$, and once this is done Halliday's observation on V_N recovers all its power. Such an amplifier would do better to abandon current dumping.

What sort of amplifier could use current dumping with advantage? Certainly not one where A is so high that the third term of (5) disappears under the tolerance of its predecessor. If this has happened then a designer attempting to allow for the third term will actually do harm to a proportion of his production run. The critical value of A is the figure which reduces the third term in (5) to 10% of the value of the previous term, because the third term is then getting inside the 10% uncertainty of its predecessor. (We are assuming 5% components, as in the Quad 405.)

Indeed the noose can now tighten, if variation of the first term of (5) is taken into account. Now the third term must not fall below 20% of its predecessor. So the critical value of A satisfies

$$\frac{Z_3}{AZ_P} = \frac{1}{5} \frac{Z_3}{Z_2} \Rightarrow A \approx \frac{5Z_2}{Z_1} \approx \frac{5Z_3}{Z_4}$$

(where really the moduli are under consideration).

We are kinder to current dumping if this upper limit on A is set high. But Z_4 cannot really be made smaller than 0.1Ω , or the resistance of the soldered joints will get into the act. And Z_3 might be 47Ω as in the Quad 405. In which case the upper limit on A is around 2,500 or so. If A exceeds this no designer can allow for it because of tolerances. In particular, the circuit is no use if the driver is an op-amp.

To recapitulate, if A is thought of as large and the last term of (5) neglected, the current dumping circuit is actually worse than normal negative feedback. Indeed, even if A is linear, and known, and used in (5), tolerances defeat the designer's efforts unless A is under 2,500 or so. There might just be a window of gain up to this figure where current dumping could be useful. This point is pursued in part 2 of this article. Meanwhile, it appears that reactive components should be kept out of the bridge.

To be continued

Automatic 'loudness' compensation uses microphone

Using a microphone-derived control signal to adjust the response of electronic filters, Swede Eric Jansson has produced a circuit that gives loudness compensation at all listening levels, regardless of the listening environment, source-signal levels and loudspeaker impedance.

Sound pressure is sensed by the microphone and the amplified signal rectified to feed a voltage-controlled loudness-compensation filter which processes the source signal. The output signal is now compensated for the equal-loudness contours but so are sound pressure levels sensed by the microphone, so to correct this a subfilter whose function is the inverse of the main filter is connected between the microphone and rectifier. Output of the active subfilter also depends on

the control voltage so the signal feeding the rectifier is effectively uncompensated.

Positioning of the microphone is not critical as loudness compensation mainly affects frequencies below 1kHz. Components C_1 and R_1 form a 48Hz high-pass filter before the voltage amplifier which feeds the subfilter. Output of the subfilter feeds rectifier IC_{2C} . A comparator, IC_{2B} , causes analogue switch IC_3 to short the control voltage at C to point A when sound pressure level is above 86dB. When these points are shorted the control voltage is



zero and both filters have a flat amplitude response. Resistor R_2 sets the control voltage; at 0dB sound pressure level the voltage over points A and C should be 310mV and above 86dB the reading should be zero. Circuit IC_1 is a quad voltage-controlled filter; two sections of the device are loudness filters for each channel and a third section forms the subfilter.

The circuit is designed for a microphone sensitivity of 0.56mV/ μ bar. Jansson has applied for a patent for his circuit.

WW

A microphone-derived signal controls the electronic loudness filter and a further voltage-controlled filter removes loudness compensation from the microphone signal.

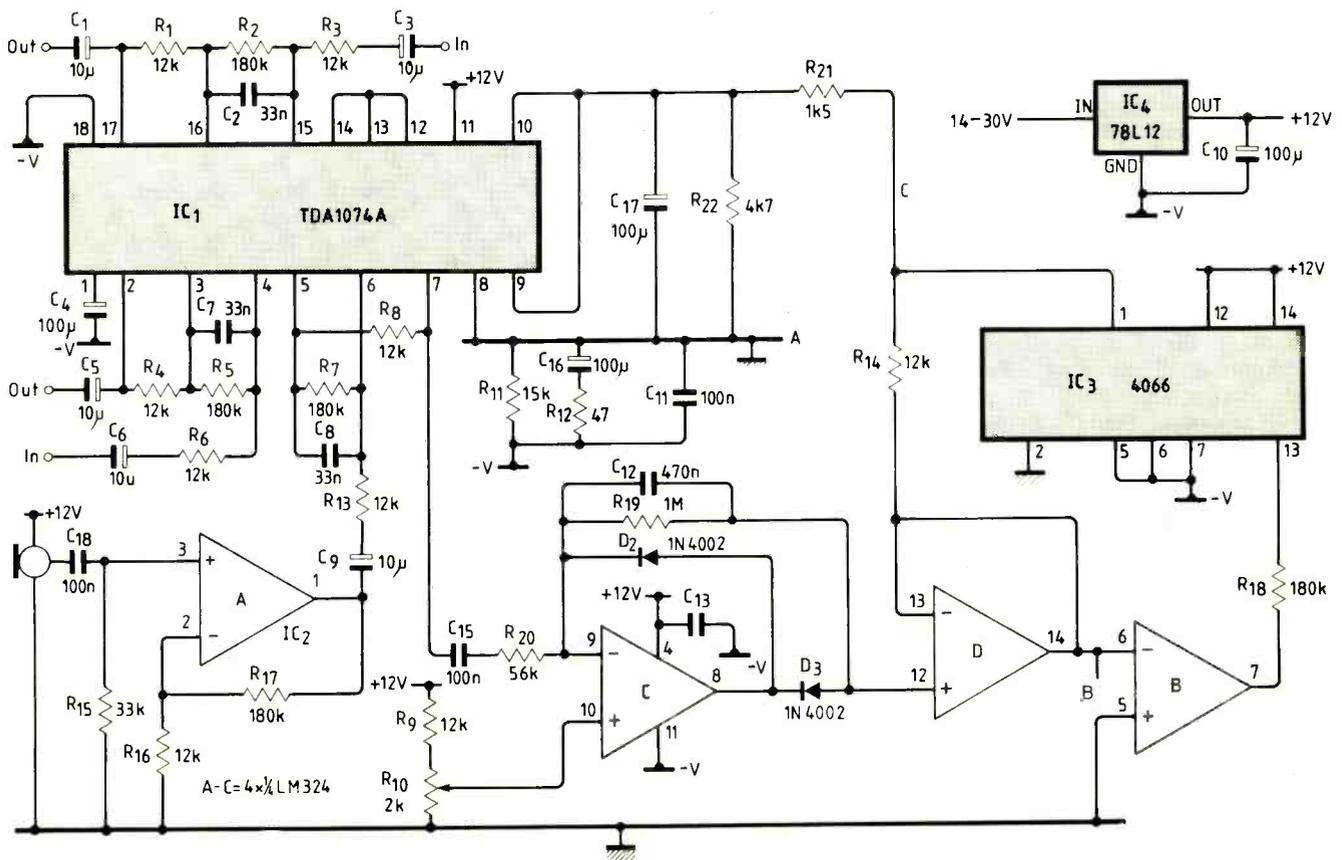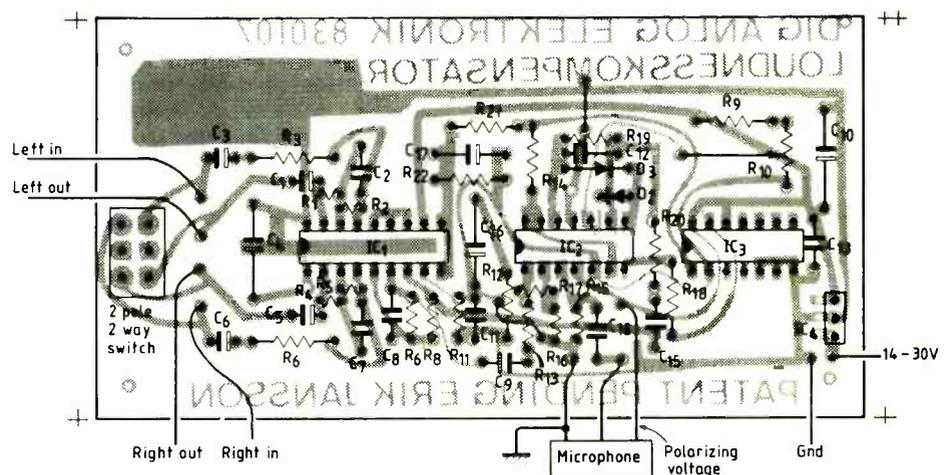Loudness compensation governed by sound pressure levels and independent of listening environment, source level and loudspeaker impedance is claimed for this circuit.



Assembly language programming

Emphasizing the use of flow diagrams to aid programming, Bob Coates illustrates how microprocessors perform arithmetic in his sixth tutorial.

Flow charts provide a pictorial representation of a procedure. A simple programming loop illustrates how flow charts are applied as an aid to assembly-language programming, see diagram below. Programmers use flow charts to help program writing and to provide documentation for future reference. When constructing flow charts, one must first decide how much detail is required; charts can range from a brief outline to a highly detailed description. Textbooks often expound that the 'correct' method for program writing is to draw up a neat flow chart using all the proper symbols — of which there are many — but in practice few programmers work in this way. Flow charts are an aid to writing programs and should be constructed in the way that suits you.

If a section of a chart proves difficult to sort out it is useful to consider the section as one block and to work the block out later using a second flow chart. Things can get a little disjointed but it doesn't matter as long as you understand what is happening. The time to write a flow chart conforming to the rules for future reference is when the program works correctly.

Summing numbers

As a first example, consider a simple looping program. Requirement of the program is to sum eight-bit binary numbers stored in successive memory locations and store the result in a specified location. The number of binary values is specified by a value in a memory location. Memory locations for the Picotutor* are


```
024 start of program
050 result store
051 number of values
052 first 8-bit value
053 second 8-bit value
054 ...
```

and so on. Flow diagram 'Summing of numbers' represents the operation required, and you can see how this chart corresponds to the basic structure shown earlier. The job of this program is to circulate the loop section once for each eight-bit value, adding each value to the result. Using the index register as a pointer, as-

*Picotutor is a low-cost assembly-language trainer described in *Wireless World* December 1982 and January 1983. A Picotutor kit is available from Magenta, see advertisers index.

by R. F. Coates


Program loop structure

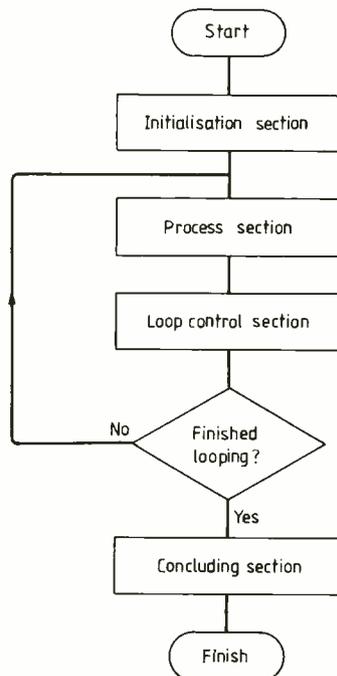

sembly language for the program is shown in List 1.

Two instructions which clear the summing register and set the pointer to the first data-byte location form the initialisation section of the program. The processing section is the single ADD instruction which adds the contents of the memory location addressed by the index register to the accumulator. INCX updates the pointer so that the next iteration adds the next value to the summing register. To keep track of the number of iterations still to be carried out, DEC VALUE decre-

Summing of numbers

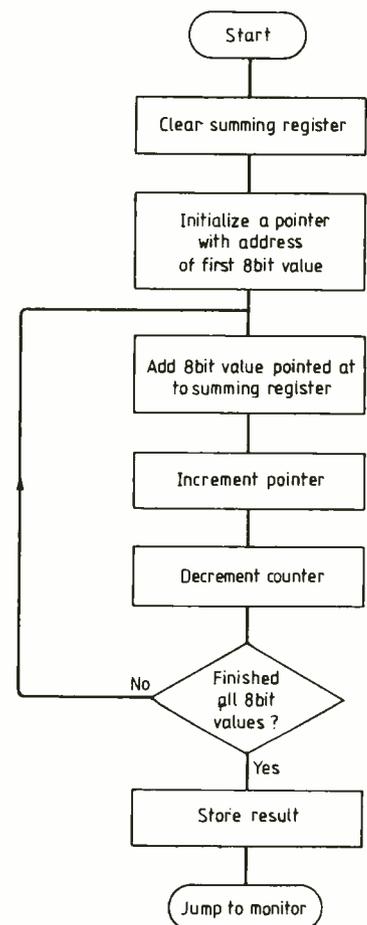

ments the location containing the number of values. BNE causes a branch if the zero flag is not set. Offset is a twos complement number which when added to the program counter causes a branch to the address of label LOOP. If the zero flag is set the next instruction in sequence, STA RESULT, is executed. The last instruction affecting the zero bit before the branch instruction is DEC VALUES and branching continues

List 1. Assembly language for summing numbers on the Picotutor.

```

024 AF      CLR    A      CLEAR SUMMING REGISTER
025 A25D   LD     D      #VALUE,  INITIALISE POINTER
026 FE      ADD     0, D   ADD 1ST VALUE TO SUMMING REG.
027 FD      LOOP   INCX   INCR. PTR.
028 FD      LOOP   INCX   INCR. PTR.
029 1701   DEC     0, D   DECR. NO. OF VALUES
030 1701   DEC     0, D   DECR. NO. OF VALUES
031 1701   DEC     0, D   DECR. NO. OF VALUES
099 1701   DEC     0, D   DECR. NO. OF VALUES
100 1701   DEC     0, D   DECR. NO. OF VALUES
101 1701   DEC     0, D   DECR. NO. OF VALUES
102 1701   DEC     0, D   DECR. NO. OF VALUES
464 1701   DEC     0, D   DECR. NO. OF VALUES
465 1701   DEC     0, D   DECR. NO.
```

until this instruction causes the location called 'values' to decrement from 01 to 00. If the initial content of location 'values' is 02, two loops will be performed hence two numbers added.

Try filling the data locations with these values

```
052 08
053 13
054 2A
055 1C
```

and set the values location 051 to 04. Result location 050 should contain 61 when the program is completed and control is returned to the monitor.

Reassembling the program as shown in Lists 2 and 3 allows it to run on systems, using 6800 and 6809 microprocessors. The only significant difference is that there is no INX register incrementing instruction in the 6809. A more versatile load effective address instruction, LEA, replaces it. Here the effective index-register address is formed from the index-register value plus the two's complement offset. With an offset of one, one is added to the index register as with INX but the register is incremented or decremented using a single instruction which is not possible with the 6800 or 6805.

List 2. Summing numbers using the 6800.

```
1000 4F CLR A
1001 0E1052 LD B, #VALUES
1004 A200 LDCP ADDA B, A
1006 08 INX
1007 7A1051 DEC #VALUES
100A 02F8 BNE LDCP
100C 071050 STA RESULT
100F 7E7057 LMC START
```

List 3. Summing numbers using the 6809.

```
1000 4F CLR A
1001 0E1052 LEX #VALUES
1004 A200 LDCP ADDA B, A
1006 0001 LEAM INX
1008 7A1051 DEC #VALUES
100A 02F7 BNE LDCP
100C 071051 STA RESULT
100F 7E7057 LMC START
```


All of the examples shown depict just one way of performing a given operation and even the simplest programs may be reconstructed to perform the same operation. Generally, examples given are chosen because they indicate clearly what is happening. They are not necessarily the most efficient solutions. It may be wise to modify programming techniques for different processors, as can be seen by applying the summing example to the Z80, List 4.

With the Z80 there is no specific clear-accumulator instruction but it is possible to perform an exclusive-or function on the accumulator and any other register — including the accumulator. An exclusive-or operation on a number with itself gives all

List 4. Z80 number summing program.

```
2000 3A5120 LD A, (VALUES)
2003 47 LD B, A
2004 AF XOR A
2005 215220 LD HL, (VALUES)
2008 03 LDCP ADD A, (HL)
2009 28 INC HL
200A 10FD DJNZ LOOP
200C 225020 LD (RESULT), A
200F 030000 JP 0
```

8 x 8 multiplication

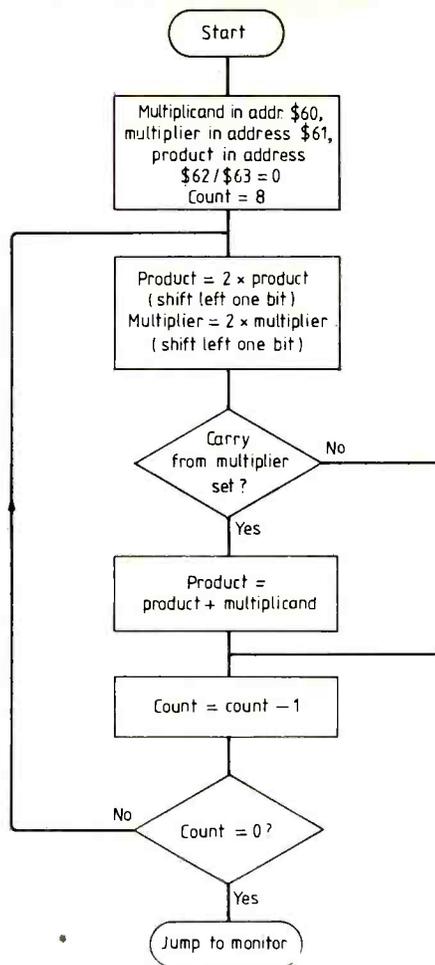

zeros so performing exclusive-or on the accumulator, XOR A, has the effect of clearing the accumulator. Secondly conditional jump DJNZ decrements the B register and causes a relative jump if the B register does not hold zero. This instruction replaces two in the 6800-series programs. The B register cannot be loaded on its own, only as a pair with the C register, so the A register is loaded with data which is subsequently transferred to the B register.

Four basic arithmetic functions are frequently carried out in further examples. Sixteen-bit addition and subtraction has already been illustrated, leaving multiplication and division to be explained.

8-bit multiplication

An algorithm for 8-by-8 bit multiplication in which two eight-bit numbers in locations 60 and 61 are multiplied and the eight most-significant bits of the result placed in location 62 is illustrated in the multiplication flow diagram. Eight bits of location 63 are set to one. How one can multiply when the processor can only add and subtract needs explaining. Consider these binary numbers

```
0101 multiplicand
0110 multiplier
```

To multiply these numbers, for each bit in the multiplier the multiplicand must be shifted left to realign with the bit in the multiplier. If the bit in the multiplier is set the shifted multiplicand is added to the value in a result register and if the bit is

clear no addition takes place. For the first bit in the multiplier the multiplicand is shifted left by one bit to give binary 1010 which is stored as a partial product. For the second bit the multiplicand is shifted left again to give 10100 which is added to the partial product, i.e.

```
first shift 1010
second shift 10100
total 11110
```

resulting in 1E (5x6=30 decimal giving 1E hex.). Consequently one only needs to shift and add in order to multiply.

Details in the flow-chart differ from this slightly because shifting an eight-bit multiplicand eight times would require a further byte to shift the value into. Instead the multiplicand is added to the product store and that is shifted left, saving a byte of ram. Program derived from the flow chart for the 6805 is shown in List 5.

List 5. Multiplication program for the 6805.

```
024 3F02 MUL CLR PROD
026 3F03 CLR PROD+1
028 AE0E LDX #E
02A 3863 MUL1 LSL PROD+1
02C 3962 ROL PROD
02E 3861 LSL MULTIPLIER
030 240B BCC MULD
032 8660 LDA MCAND
034 8263 ADD PROD+1
036 8760 STA PROD+1
038 4F CLR A
03E 8602 ADC PROD
038 8760 STA PROD
03D 5A MULD DECM
03E 03EA DNE DNE
040 03E0 LXP START
```

Sixteen-bit register PROD and PROD+1, which is initially cleared, holds the result. Counting is carried out by the index register which is set to the number of bits in the multiplier, in this case eight, to determine how many times the program will run.

Shifting of the 16-bit product store is required in the first part of the looping section but only eight-bit registers can be shifted (except with 6801/3 processors) so shift and rotate are used to give the same effect. Program section LSL PROD+1 shifts the first eight bits of the product left, placing bit seven into the carry position. ROL PROD then rotates the most-significant eight bits left and the previous carry indication moves into bit zero of PROD, resulting in a 16-bit left shift.

Next, the multiplier is shifted left to place each of its bits in the carry location where they can be tested for one or zero on each loop. A digital one causes the multiplicand to be added to the 16-bit partial product, the result being returned to the partial product locations, and a zero causes the add section to be skipped over by the BCC instruction. Decrementation of the loop counter then takes place and the program loop restarts if all eight bits of the multiplier have not been tested; otherwise looping ends with the partial-product locations containing the final result value.

15-by-7-bit division

Division on a microprocessor can be carried out using a series of trial subtractions. For each step in the division it must be determined whether or not the divisor can be subtracted from the remainder of eight

greater than 99 so 60 is added and the half-carry bit is set so a further six is added. With correction of 66 added, result E2 becomes 148, i.e. 48 with the carry indication set.

Because this algorithm is often used and ram space in Picotutor is limited the subroutine for this shown in List 7 is included in eprom at address 33. I used a different assembler for this program so entering of hexadecimal numbers is different; numbers entered are prefixed with H. List 8 illustrates how 99 and 49 are added using this subroutine. When the first SWI instruction is encountered, press the register key and check that the H bit is set, that the C bit is clear and that the accumulator contains E2. Leave register mode and press the cn key to continue the program. Pressing the register key should now indicate that the H bit is clear and the carry bit is set. The accumulator now contains 48 and multiple-precision addition may be carried out as described earlier using the carry indication.

Number conversion

Converting a decimal number to binary, manipulating it and converting it back to

List 8. Adding two numbers using the simulator of List 7.

```

004 1800 LDA #1800
005 1840 ADD #1100
006 00 SA1
007 00 JSR DAA
008 00 SA1

```

List 9. Converting decimal 2748 to binary form using Picotutor.

```

004 A627 LDA #27
006 B71A STA POINT
008 A648 LDA #48
00A B71B STA POINT+1
00C AEE0 LDX #60
00E BDB9 JSR BCDBIN
030 BC80 JMP START

```

List 10. Assembly language for Picotutor subroutine BCDBIN.

```

041 * BCDBIN - CONVERTS A 4 DIGIT PACKED DEC NUMBER IN
042 * POINT TO 14 BIT BINARY, AND PLACES
043 * RESULT IN POINT+1. BCD NUMBER
044 * UNALTERED. SETS CARRY IF A NON-DECIMAL
045 * DIGIT ENTERED.
046 *
047 BCDBIN CLR 0,X CLEAR REGISTER REGISTERS
048 CLR 1,X
049 BCLR 1,BITSTR CLEAR OVERFLOW FLAG
050 LDA POINT PUT 1000'S DIGIT IN POINTS
051 LSR#A
052 LSR#A
053 LSR#A
054 LSR#A
055 STA POINTS
056 BSR BCDCHK CHECK DIGIT IS <=9
057 BRZ BRANCH IF DIGIT <= 0
058 *
059 BCB1 LDA #3 ADD H'300' TO RESULT
060 ADD 0,X
061 STA 0,X
062 LDA #H'E8' ADD H'E8' TO RESULT
063 BSR BCDADD (TOTAL ADD=H'3E8', 1000 DEC)
064 BNE BCB1 BRANCH IF 1000'S NOT ZERO
065 *
066 *
067 BCB2 LDA POINT PUT 100'S DIGIT IN POINTS
068 AND #H'F
069 STA POINTS
070 BSR BCDCHK
071 BRZ BRANCH IF DIGIT <= 0
072 *
073 BCB3 LDA #H'54' ADD H'54' (100) TO RESULT
074 BSR BCDADD
075 BNE BCB3
076 *
077 *
078 BCB4 LDA POINT+1 PUT 10'S DIGIT IN POINTS
079 LSR#A
080 LSR#A
081 LSR#A
082 LSR#A
083 STA POINTS
084 BSR BCDCHK
085 BRZ
086 *
087 BCB5 LDA #H'A' ADD H'A' (10) TO RESULT
088 BSR BCDADD
089 BNE BCB5
090 *
091 *
092 BCB6 LDA POINT+1 ADD 1'S TO RESULT
093 AND #H'F
094 BSR BCDCHK
095 BSR BCDADD
096 *
097 *
098 CLR 1,BITSTR,BCB7 BRANCH IF NO ERROR
099 BSR SEC SET CARRY AS NON-DECIMAL NO.
100 BCB7 RTS RETURN, CONVERSION COMPLETE
101 *
102 *
103 *
104 *
105 BCDADD ADD 1,X ADD NUMBER IN A TO RESULT
106 STA 1,X
107 LDA #0
108 ACC 0,X PASS ON CARRY
109 STA 0,X
110 DEC POINTS DECREMENT THE DECIMAL DIGIT
111 *
112 *
113 *
114 *
115 BCDCHK CMA #0 SET ERROR FLAG IF DIGIT > 9
116 BLS BCDCHK
117 BSET 1,BITSTR SET FLAG
118 BCDCHK: TSTA
119 RTS

```

List 7. Simulation of the 6800 DAA instruction included in the Picotutor.


```

* DAA - THIS ROUTINE SIMULATES THE DAA INSTRUCTION OF THE
* 6800 ETC. IT SHOULD BE CALLED AFTER AN ADD OR ADC
* INSTRUCTION AS.... JSR DAA.
* UPON EXIT, A IS BCD CORRECTED AND C IS SET FOR
* MULTIPRECISION BCD ADD.
*
386 B71E DAA STA TEMP# SAVE INPUT VALUE
388 BF1F STX TEMPX
*
* CALCULATE CORRECTION FACTOR
*
38A 5F CLR#X BUILD CORRECTION IN X
38B 101D BSET 0,BITSTR SET CARRY STORE
*
38D 2506 BCS DAA#G
38F 111D BCLR 0,BITSTR BUT CLEAR CARRY STORE IF CARRY ISN'T SET
391 A199 CMP #H'99'
393 2302 BLS DAALOW INPUT <=H'99'
395 AE60 LDX #H'60' HIGH NIBBLE NEEDS CORRECTION
*
397 2906 DAALOW BHCS DAALG
399 A40F AND #H'F'
39B A109 CMP #5
39D 2304 BLS DAADNE NO LOW NIBBLE CORRECTION
39F 9F DAALG TXA
3A0 AB06 ADD #H'6' LOW NIBBLE CORRECTION
3A2 97 TAX TOTAL ADJUST BACK TO X
*
* CORRECT ACCUMULATOR NOW
*
3A3 9F DAADNE TXA CORRECTION GOES INTO A
3A4 BB1E ADD TEMP# AND IS ADDED TO ORIGINAL VALUE
3A6 BE1F LDX TEMPX
3A8 2504 BCS DAA2 BRANCH OUT IF CARRY ALREADY SET
3AA 011D01 BRCLR 0,BITSTR,DAA2 OR IF IT WAS CLEAR ON ENTRY
3AD 99 SEC BUT SET CARRY IF IT WAS ON ENTRY
3AE 81 DAA2 RTS

```

decimal form is the second alternative. These conversions are often used, for instance the d.v.m. program referred to in the January issue obtains an eight-bit binary value equivalent to the input voltage and converts it to decimal form for display. Subroutines for converting numbers in both directions are included in the Picotutor monitor as 'system calls'. How b.c.d. is converted to binary in its BCDBIN program is illustrated in the flow diagram shown. Here, for each of the thousands, hundreds and tens digits the equivalent hexadecimal number is added to a result register by the number of times equal to the number of the digit. Finally, units are added to the result. Table 1, system calls, shows that the b.c.d. number should be placed in POINT and POINT+1, the first being the ram register used by the monitor at address 1A and the last the next location, 1B. As these locations are used by the monitor they cannot be set up by the memory-open command (mo) which uses POINT for other purposes but must be set up within the user program. Setting up of the index register is also required so that it points to where the result of the conversion is to be placed.

BCD-to-binary conversion

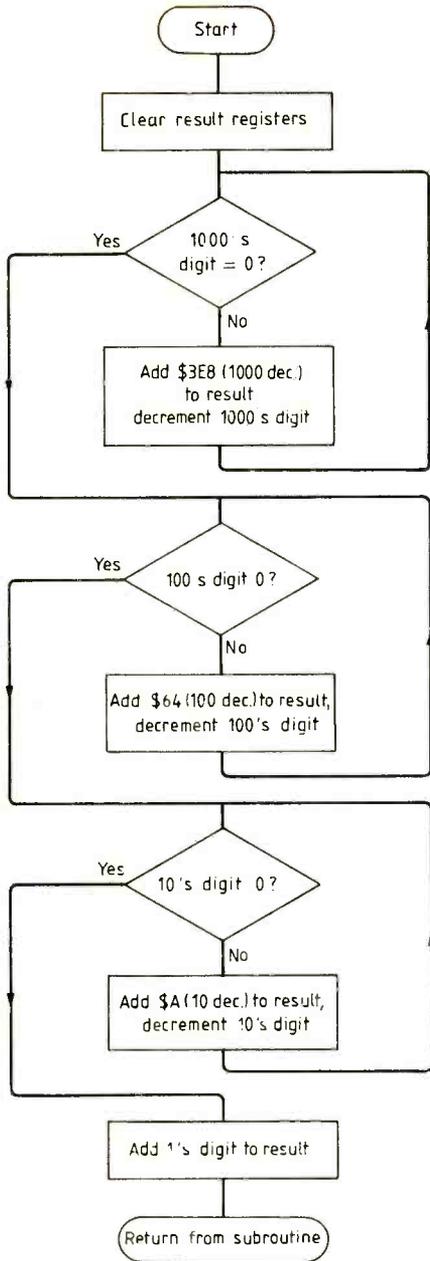

List 9 is a program example for converting 2748 to binary for representation in hexadecimal form. First POINT and POINT+1 are set up with the decimal value then the index register is loaded to point to result location 60. Subroutine BCDBIN is then called to convert the number to decimal and return control to the monitor. Examination of locations 60 and 61 using the memory-open key should

Table 1. System calls.

Add	Name	Function	Add	Name	Function
80	START	Re-enter monitor.	B6	BINBCD	Converts a 14-bit binary number in POINT/POINT+1 to a four-digit packed b.c.d. number in 0,X/1,X. Sets C if an overflow occurs.
83	DISKEY	Refreshes display with data in DISBUF then calls KEYIN.	B9	BCDBIN	Converts a four-digit packed b.c.d. number in POINT/POINT+1 to a 14-bit binary number in 0,X/1,X. Sets C bit if a non-decimal digit entered.
86	KEYIN	Scans keypad and returns with key code in A, 00 if no key pressed. Sets c.c.r. C bit if same key pressed, clears otherwise.	BC	BUILD4	Gets four hex. digits from keypad and packs them in POINT/POINT+1. Jumps to START if non-hex. key pressed.
89	DISGET	Repeatedly calls KEYIN until a new key is pressed, returns with key code in A.	BF	ADD	Adds two 16-bit binary numbers in POINT/POINT+1 and TEMPX1/TEMPX2. Result in POINT/POINT+1.
8C	DISHEX	Calls DISGET and converts key code to hex. if a 0-9 or A-F key and clears C bit. If non-hex., returns with original key code and sets C bit.	C2	SUB	Subtracts 16-bit number in TEMPX1/TEMPX2 from 16-bit binary number in POINT/POINT+1. Result in POINT/POINT+1.
8F	HEXCON	Converts key-code in A to hex (00-0F) and clears carry. If non-hex. key, returns with original code in A and sets carry.	C5	MUL	Multiplies two eight-bit binary numbers in TEMPX1/TEMPX2. 16-bit result in POINT/POINT+1.
92	BADDR	Builds three-digit address entered by keypad in POINT/POINT + 1.	C8	DIV	Divides 15-bit binary number in POINT/POINT+1 by seven-bit binary number in TEMPX1, puts quotient in POINT+1, remainder in POINT.
98	THEX	Gets two hex. digits from keypad and combines in A. Puts seven-segment equivalent of two digits in 0,X/1, X. Non-hex. keys cause jump to START.	CB	DVM	Digital voltmeter program (see Jan. 83 issue)
9B	LSEG	Converts m.s. nibble in A to seven-segment code.	CE	VGEN	Voltage generator program (see Jan. 83 issue).
9E	RSEG	Converts l.s. nibble in A to seven-segment code.			
AD	ERROR	Puts 'Error' in display until any key pressed then jumps to START.			
B0	CLRDIS	Clears display buffer ram DISBUF.			
B3	DAA	Simulates the 6800 DAA instruction.			

reveal the result 0ABC. List 10 is the b.c.d.-to-binary program in Picotutor. Try modifying the program to convert from binary in hexadecimal form to b.c.d. using Picotutor subroutine BINBCD.

System calls

Because of limited ram in Picotutor a collection of useful subroutines, or system calls, such as BCDBIN are included in the monitor eeprom, Table 1. By linking these to your programs fairly complex programs

can be used despite the small ram. Included are the routines for addition, subtraction, multiplication and division already described. Other routines will be described later; the list is included now to allow you to experiment.

Addresses of each call are only three bytes apart because the address merely contains a jump instruction which causes a jump to the actual routine address. There are two reasons for this. Firstly all these jumps can be contained in page zero eeprom locations which allows direct addressing and saves memory space. Secondly minor program modifications which alter address locations may be made without altering the jump addresses. An area of ram reserved for use by the monitor is also used by some of the system calls, indicated in Table 2.



Bob Coates concentrates on the 6805 and reveals some of Picotutors secrets in his next article.

Table 2. Reserved memory.

Address	Bytes	Name	Function
10	6	DISBUF	Store for seven-segment codes for each digit of display.
16	1	TIMEV	Timer interrupt vector. Program will jump to the direct address given here when a timer interrupt occurs.
17	1	IRQV	Same as TIMEV but for hardware interrupt.
18	1	LASKEY	Used by DISKEY.
19	1	POINTP	Used by monitor
1A	2	POINT	Used by monitor and for arguments of some system calls.
1C	1	POINTS	Used by monitor.
1D	1	BITSTR	Single bit flag store. Bit 0 used by DAA, bit 1 used by BINBCD and BCDBIN. Bits 2 to 7 reserved for future use.
1E	1	TEMPA	Used by monitor.
1F	1	TEMPX	Used by monitor.
20	1	TEMPX1	Used by monitor and for arguments of some system calls.
21	1	TEMPX2	Used by monitor and for arguments of some system calls.

LETTERS

DESIGN COMPETITION

In case anyone who has entered your design competition is still undecided about what to do, I would like to make a suggestion.

In a noisy environment the normal ear can shut out the unwanted sound, enabling a conversation to be carried on without much difficulty.

Interpose a hearing aid or any microphone – amplifier – receiver combination for that matter and the ability to discriminate is lost. All we hear is the loudest noise.

Anyone who can overcome this will earn the undying gratitude of the hard of hearing.

D. Wattson
Hayfield
Derbyshire

Over the years there have been several methods for the disabled to signal help when they are in difficulties – cords, bells, lights, whistles, etc. and, of course, the telephone. They are all so limited that they are virtually useless for the very people for whom they are most needed – the very severely disabled, including the frail elderly. When they fall to the floor, or are in similar difficulty, they are helpless; they cannot reach any of the communication aids presently suggested.

What is needed is a portable fail-safe alarm, a device that can be worn round the wrist or neck which the person can immediately operate, activating automatically the telephone or similar means of communication to an outside source of help. I have to say that there are one or two such devices on the market, but they, too, are limited and, I think, expensive.

If something really suitable could be produced it would be a tremendous boon for the increasing numbers of disabled people. There would be an enormous market amongst them, and Social Services department, especially with the increasing emphasis on community care.

I hope this will be taken up.
E. M. Cohen
Southend-on-Sea

'WASTE' OF A RESOURCE

May I suggest a new cause that *Wireless World* with its new-found sense of social responsibility may care to take up?

This is the almost incredible waste of a precious natural resource – the radio spectrum – on what can only be described as pap at its mildest and sheer rubbish at its worst. If one tunes across the medium-waveband in any part of this country today, all that can be heard is the same type of "chat-show, DJ, phone-in", repeated ad nauseam from what seems to be hundreds of stations, all identical except for their names and the occasional reference to some local event or other. Some put out adverts for local businesses and call themselves "independent" stations, others advertise themselves and claim to be the BBC. Radio 4 has absconded to long-wave, Radio 3 has been relegated to a single frequency and ruined by continuous fading even in daylight, and the scene is not even enlivened by the occasional "good music" station, as in the USA. In fact, as a frequent visitor to the USA, it seems to me that from a situation 20 years ago where we could be rightly proud of what the BBC was doing, we have completely degenerated to the point where almost any large

American city has more real choice than we do.

What I object to is the sheer waste of frequencies. We have been told repeatedly over many years whenever some new form of public service broadcasting was suggested that the real problem was lack of frequencies, so they never came to anything, yet now we seem to have found (by magic, apparently) that there are in fact huge numbers of channels totally unoccupied and just waiting for another pap station to occupy them.

I have in mind, particularly, continuous weather broadcasting of the "Airmet" variety. "Airmet", you may remember, was a long-wave station that transmitted continuous weather reports for a large number of stations throughout the UK, interspersed with interpretation by a forecaster. Nominally for the benefit of aircraft, it was chased off the air in 1950 by, supposedly, the Copenhagen Plan, which re-allocated its frequency (245 kHz) to Copenhagen. There was a considerable outcry at the time, quietened down somewhat by the reassurance that as soon as an alternative frequency could be found it would be re-instated. Needless to say it has not been.

Now this was a particularly useful bit of true public service broadcasting. Being in plain language, on an easily accessible frequency, it needed no specialised equipment and eliminated all the business we now have of trying to remember at what time on what channel the weather forecast is. Unless you happen to have specialised knowledge and can use the h.f./s.s.b. civil and military weather broadcasts, there is still no way to get up-to-date actual weather reports country-wide. And yet, how many disasters do we still have attributed to some poor chap's lack of knowledge of how the weather was developing? A continuous broadcast on the medium waveband might just prevent some of those hikers or sailors starting out in the first place, and save the expenditure of large sums by the rescue services.

Of course, none of the existing broadcasters would want to organise it – it is unglamorous and might not pay – but how about the Government itself doing it?

This is only one example, but there are many others. Come on, *Wireless World*, this one might even have a better chance of success than some of your other causes!

W. Blanchard
Dorking
Essex

TELECINE SCANNING

Is it not time that, even now, after all these years of the growth of tv, something could be done to adjust more sensibly the 35mm telecine scanners of both BBC and the IBA companies. I have the impression that for a large number of years the SMPTE standard has been used, but unfortunately this results in excessive underscanning of the film frame, titles becoming far too close to the picture edges, in some cases even being partially cut off. Credits such as "directed by" at times being the result. Even famous names have been "shortened" on occasion.

In cinemas in pre-CinemaScope days when screens were all 4 × 3 ratio this problem did not arise. When one considers that domestic tv receivers almost always overscan the picture tube (all the ones I've seen – except mine – do) the present excessive underscanning by the broadcasting authorities telecines is completely unwarranted.

Surely the solution is to line up to the traditional scanning area of standard 35mm projectors. This will result in correct framing and composition as intended by the original film makers. Incidentally there would be an added bonus (albeit only marginal) in that the definition would be improved.

Who will pursue this?
Arthur Dungate
Hounslow
Middlesex

BINAURAL RECORDING

I want to give some comment on Mr Kirkham's letter in *WW* June, 1983. First of all I want to deal with the "oddities" he discovered in the schematic diagram given in my article in *WW* November, 1982.

Driver stage for the 600Ω load


This stage was designed to operate with 1V_{peak} input voltage, with an overload margin of some 10 dB, and a flat frequency response up to 50 kHz. Therefore the output can make excursions between the power supply-lines. This requirement cannot be met by most op-amps, hence the class-B output stage. This opened the way to the use of a somewhat "funny" amplifier, the LM 3900, which is a Norton amplifier. This reduces the number of switch contacts, and reduces the number of resistors. The a.c. analysis of a typical Norton amplifier is given below.

This shows that the amplification of the first stages is 3 in both modes, and that the third stages are 1× amplifiers in both modes.


Second amplifier stage

The second amplifier has to have the following characteristics: low noise, because the output of the cross-feed circuit is 0.01× the input signal; frequency characteristic flat up to 50 kHz. These demands are met by the LM387, which has an equivalent noise voltage of 7nV/√Hz. This single supply amplifier however has a somewhat peculiar behaviour. The input presents a 1.2V d.c. level, which by means of d.c. feedback controls the d.c. output level. This explains the split between d.c. and a.c. feedback, and the 1μ capacitor on the input. Mr Kirkham is correct however, when he indicates that the switch was wrongly positioned. This was corrected in *WW* of January 1983.

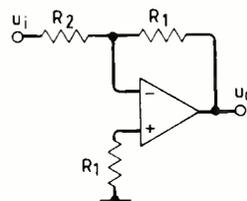The circuit as published in my article (*WW* Nov 1982) can be approved upon by using TL074 (or equivalent) because LM3900 is prone to high frequency instability, which generates noise. However, the circuitry has to be changed considerably, else you will end up with




$$u_o = -\frac{R_1}{R_2} u_i$$

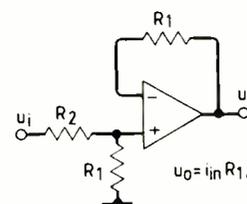

$$i_{in} = \frac{u_i}{R_2}$$
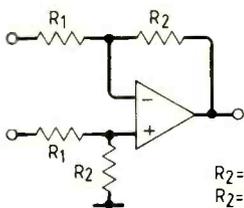
$$u_o = i_{in} R_1, \text{ hence } u_o = u_i = \frac{R_1}{R_2}$$



$R_2=3R_1$ for the input stage
 $R_2=R_1$ for the third stage

wrong amplification factors. Part of the circuit is given below.

Now about the use of the circuit described in *WW* November, 1982. It is intended to give loudspeaker-like reproduction on headphones, or headphone-like reproduction on loudspeakers. This is something totally different from what Mr Kirkham is looking for. He is looking for some "gadget" that enlarges the stereo-base. The circuit he provides does just that, and nothing more.

When Mr Kirkham suggests that a simple roll-off at 1kHz would very likely generate the same audible effect as my circuit, I think this will not be the case. This is caused by the fact that no account is given to the difference in arrival-time of the sound of a single source on the left and right ear, and that no account is given to the high frequency lift generated by the presence of the head. Because of the cross-feed circuit used by me (and developed by Mr Bauer of CBS in 1961) does just that, one ends-up with a good reproduction of dummy-head (*kunstkopf*) recordings via loudspeakers, and loudspeaker-like reproduction of conventional stereo via headphones. These are facts that the circuit given by Mr Kirkham cannot achieve.

J. H. Buijs
 Huizen
 Holland

WAVES IN SPACE

I refer to the correspondence in the August issue concerning Catt's "Waves in Space", (March, 1983).

Ivor Catt has, for some years, been proposing new explanations of electrical phenomena which many regard as already fully explained by classical e-m theory; theory which unfortunately has become dogma because few have bothered to question its tenets in those areas where its teachings give rise to curious and unexplained paradoxes.

Correspondents who try to put Catt down generally throw up a dogmatic smokescreen whilst often failing completely to address themselves to the apparently paradoxical events he has attempted to explain. The latest correspondence concerning "Waves in Space" is no exception. R. T. Lamb's letter gives no real explanation of the phenomena that Catt discussed and simply fluffs the issue of pulse duration with a remark about the charged line being an energy storage device rather than a source of e.m.f.

Timothy C. Webb's letter puts a finger on one important issue when he asks why Catt's contra-moving waves are not destroyed by line losses, but he fails to ask whether conventional energy dissipation due to line loss applies to these contra-moving waves. I suspect Catt thinks otherwise and it would be interesting to have his views.

In other respects Mr Webb's letter falls into the dogma trap. There is a resounding bit about

"The great body of scientific and engineering knowledge that has amply demonstrated . . ." etc., etc. Dr Catt has quite reasonably asserted that the great body of scientific and engineering knowledge has singularly failed amply to demonstrate some of the things it purports to explain! At the end of his letter Webb gives what I found to be an incomprehensible explanation of the pulse duration problem and then rounds this off with a remark about the "pleasing aspect of this argument . . ." etc. I was not very pleased because I could not make head nor tail of it!

Hodge's letter is perhaps more thoughtful but again it does not seem to explain the phenomena which Catt discussed in his article.

Catt's theories may be wrong but he is certainly right to shine lights into some of the dark and deceiving corners of classical e.m. theory. One would like to see more reasoned arguments advanced in refutation and less reliance on the "dogma must be right" approach which, incidentally, rather neatly mirrors the discussion on the "closed loop arguments", (said to be used to support relativistic dogma), given in an unrelated letter from A. H. Winterflood in the same issue of *Wireless World*.

Anyone who thinks he knows all about electricity should also read Professor Jennison's article on making a charge from a radio wave!
 M. G. T. Hewlett
 Midhurst
 W. Sussex

CRAFT AND TECHNOLOGY

In your July issue, under the above heading, Dr Smith purports to "discuss the role of the industrial designer". As a craftsman myself, with some experience in engineering and industrial design, I was disappointed to find that the discussion amounted to one paragraph, where he says that "a well structured p.c.b. with all the components colour-coded and laid out for strictly functional use can be aesthetically (though unintentionally) very pleasing (but) many mass-produced goods disguise themselves in poor design, however good the technology incorporated in them".

The main body of the article is entirely devoted to a "bracket clock of modern design, with fine traditional metalwork mounted in a handcrafted case of amber-tinted transparent acrylic (with) silvered chapter ring, brass spandrels and finials . . . finely engraved and hand finished . . . (giving) the impression of being a traditional English timepiece while using modern materials.

The maker of this article, which is shown in an illustration said, in answer to a question: "Contemporary artists and craftsmen must use modern materials and mould them to give a message of what we are doing now". The author justifies the printing of this article in *Wireless World* by saying that the clock "although it originated in a cottage industry established by a craftsman, uses a very up-to-date quartz drive . . . (and) bridges the gap between fine individually made objects and anonymous mass-produced (although highly technological goods)". He says "the success of this design encourages me".

Well, it doesn't encourage me! What if someone were to make a modern electric locomotive look like a steam loco. Or an automatic washing

machine like an old dolly-tub, or a steam smoothing iron look like the old flat-irons?

As a matter of contemporary fact, mass-produced pseudo-traditional clocks very like this handcrafted piece are the most astonishing feature of a modern city shopping centre. Industrial design seems to have by-passed clocks, except for the occasional pocket digital alarm-cum-stop-watch-cum-almost-everything in precision timing.

An instrumentation engineer myself, with somewhat disused craft skills of my own, I just love old clocks and measuring instruments, and the fine old instrument work that still lingers in a few old college laboratories. But this kind of modern mechanism deliberately dressed up in old clothing is the very antithesis of real craftsmanship, which in every age has always used the very best techniques and materials available at the time, and allowed the craftsman to express himself superbly without a single note of falseness or deference to an archaic traditionalism.

Does anyone suppose that clocks and other artefacts like the one described in this article will be admired by connoisseurs, or reproduced by artist-craftsmen one or two hundred years hence?

I am sure we are in for a resurgence of fine craftsmanship (if we survive long enough), if only to fill in the time of our structural unemployed. But I am equally sure it will not be dissipated in copying antique objects of beauty, or clothing high technology in resurrected 'traditional' forms.

R. Gill
 Derby

RECORDING TELETEX

Speaking recently by telephone to one of your technicians doubt was expressed about the possibility of recording teletext pages and subtitles on a domestic video recorder.

I thought that it might be of interest that I have quite successfully recorded using a teletext decoder from Ayr Viewdata of Byfleet, who advertise in your journal, this being simply tuned through a spare channel on my Toshiba V8600 video recorder.

There is a slight reduction in quality by using an adaptor rather than a teletext tv and, though pages are in full colour, subtitles are in black and white to save cost on the decoder. Results are pretty good and quite acceptable to the viewers.

This facility is valuable to people who are suffering from hearing problems and particularly those who would like to record a subtitle programme being shown at an unsociable hour or clashing with one on another channel.

Since it is available at approximately one third of the current price of a 22 inch teletext tv, I am amazed that manufacturers and dealers are not pressing sales of the decoder for people who already have a modern tv without the teletext facility.

N. Gibson
 Burgess Hill
 W. Sussex

IMPOSSIBLE LOYALTIES

Referring to your May editorial, the ethical problems of conflicting loyalties may have come to *Wireless World's* attention only in 'the perilous 1980s', but people have been grappling

with these questions for some thousands of years. To make a useful contribution, *Wireless World* should perhaps give them rather more careful thought than is evident in the editorial.

There seems no case for saying that loyalty can exist only between people. Loyalty is given to ideas and principles, not to people as structures of flesh, bones and hair nor to organizations as management structures. Ideas and principles may be embodied by organizations as much as by people: surely an organization such as The Red Cross must be allowed as an example of this.

The argument that organizations are motivated only by self-interest can be applied equally to people. One can say that any person's good action is done ultimately for the resulting glow of self-satisfaction, but this is a sterile line which puts an end to any useful debate.

Wireless World seems very ready to judge for us whether our loyalties are worthy or not. Are you, or is anybody, really in a position to dismiss as unacceptable the possible loyalty of a wife to her mass-murderer husband? In any case you are really suggesting only the replacement of conventional allegiances by loyalty to the concept of 'Engineers Against Evil.' If some engineers decided to uphold their principles with action rather than just words, you might even find yourselves advocating loyalty to a terrorist group!

D. P. Leggatt
Farnham,
Surrey.

DEATH OF ELECTRIC CURRENT

I believe Ivor Catt bases his theory on Heaviside's "the current in the wire is set up by the energy transmitted through the medium around it."

Chapter ten of Hertz's book 'Electric Waves' is a reprint of his paper 'On the Propagation of Electric Waves by Means of Wires' first published in 1889, a year after the experiments which made him famous. The purpose behind the experiments described in this later paper was to test Heaviside's and Poynting's theory that, as Hertz wrote, "the electric force which determines the current is not propagated in the wire itself, but under all circumstances penetrates from without into the wire. . . ." Hertz went on to say "As a matter of fact the theory was found to be confirmed by the experiments which are now to be described; and it will be seen that these few experiments are amply sufficient to support the conception introduced by Messrs Heaviside and Poynting."

Hertz then described a set of experiments which used his invention of the coaxial cable and the balanced feeder or transmission line, and concluded his paper, "On studying the experiments above described, the mode in which we have interpreted them, and the explanations of the investigators referred to in the introduction, one difference will be found especially striking between the conception here advocated and the usually accepted view. (Weber's theory of electricity carried by charged particles acting instantaneously at a distance.) In the latter, conductors appear as the only bodies which take part in the propagation of electrical disturbances - non-conductors as bodies which oppose this propagation. According to our conception, on the other hand, all propagation of electrical disturbances takes place through non-conductors; and conductors oppose this propagation with a resistance which, in the case of rapid alterna-

tions, is insuperable. We might almost feel inclined to agree to the statement that conductors and non-conductors should, according to this conception, have their names interchanged. . . ."

Hertz was even more specific in his Supplementary Note No. 24. "By the experiments in the following paper it is pretty plainly proved that in the case of rapid variations of current the changes penetrate from without into the wire. It is thereby made probable that in the case of a steady current as well, the disturbance in the wire itself is not, as has hitherto been assumed, the cause of the phenomena in its neighbourhood; but that, on the contrary, the disturbances in the neighbourhood of the wire are the cause of the phenomena inside it."

Catt's critics have a choice: either Hertz was a crank and a crackpot, or he was, as an experimenter and detective, in the same class as Faraday. If Hertz's diagnosis of his experiments with a transmission line is correct, the effect we call a current is caused by "the disturbances in the neighbourhood of the wire, is being disturbed? Maxwell's ether?

M. G. Wellard
Kenley Surrey

ELECTROMAGNETIC DOPPLER

If two objects have a relative velocity then the distance between them is changing (by definition). Anything that travels from one object to the other at regular intervals will travel different distances on successive trips. If the two objects are travelling away from each other then each trip will be longer (in distance) and will take longer (in time) unless the thing making the trip (wave crest, photon, bullet, or jogger for that matter) increases its speed to compensate for the increased distance. The fact that consecutive trips take longer (in time) means that consecutive arrivals are further apart (in time) than the corresponding departures. This is called the Doppler effect.

Special Relativity and Newtonian physics predict different values for the Doppler effect: they do not invoke different mechanisms. The mechanism is that unless you increase your speed you'll take longer to travel a greater distance.

You don't have to like Special Relativity but you must accept that it "explains" Doppler shift just as well as Newtonian physics does - indeed, the "explanation" is the same for both systems.

In your July issue, S. Kennaugh derives a formula for the magnitude of the Doppler effect. He describes his derivation as common-sense, elegant, but heretical. His derivation is Newtonian and relies on two assumptions (velocities can be added like pure numbers, and wavelength of an electromagnetic wave is constant to all observers) that are valid for Newtonian but not for special relativistic physics. Neither of these assumptions is needed - I offer the following: Observer B is receiving radio signals transmitted by A at frequency f . A is moving at velocity v relative to B. "Wave crests" are transmitted at intervals of $1/f$, during which time the distance from A to B increases by v/f . This extra distance is covered in time v/fc (c being the velocity of radio waves measured, like v , relative to B). Wave crests arrive at B at intervals of $(1/f + v/fc)$ which corresponds to a frequency of $fc/c+v$ - a Doppler frequency shift factor of $c/c+v$.

This derivation is correct for both Newtonian and Special Relativistic physics - provided that all values are observed by B. Note that (aside from the symbol 'c' for speed of wave propagation) there is nothing specific to electromagnetic Doppler in this derivation; it is equally correct for sound waves, or for any periodic transmission across an increasing distance.

In your July issue, J. Kennaugh raises another aspect of Special Relativity: suppose that the same radio wave is observed by two observers who are moving relative to each other. They each observe a different frequency for the wave but they observe the same propagation speed (c). Since $V = f\lambda$ holds good for all observers, these two observers obtain different wavelengths for the same wave. The two observers disagree about the length of the same physical "object". J. Kennaugh, it seems, does not like this prediction of Special Relativity. Although I can only agree with JK that Newtonian physics is simpler in many ways than Special Relativity, that doesn't make it correct.

In case your readers should think that I'm trying to avoid discussing the more disturbing predictions of Special Relativity, let me return briefly to the question of observed wavelengths. Special Relativity predicts (as pointed out by JK) that two observers of the same wave will see different wavelengths. Imagine now that one observer measures the time taken by the radio wave to travel between two objects at a distance of say in wavelengths apart. The other observer times the same radio wave travelling between the same two objects. Now Special Relativity predicts that the two observers measure a different distance (between the same two objects) traversed by the same wave at the same speed. They measure a different amount of time for the same physical event!

Predictions like these may be hard to understand and even harder to believe but it is important to realise that they are not contrary to logic. I'm sure that nothing I can say will shift JK (and many many others) from his view that Special Relativity contains some basic logical flaw, but if you are happy to continue publishing our letters then I am happy (for a while, at least) to continue defending Special Relativity.

Before I finish this letter I must challenge two things raised by James L. Smith also in your July issue. Firstly he suggests that the existence of a wave propagation medium (ether) changes the observed Doppler effect; as I've already explained, this is not true. Secondly he offers a choice between "Einsteinian" and "Non-Einsteinian" systems; this is a ludicrous oversimplification - Einstein proposed at least two systems (Special and General Relativity) and there are almost unlimited alternative (non-Einsteinian) systems - some predict an "ether", others do not.

S. J. Hobson
Hampton
Middlesex

HERETICS' GUIDE

It is reassuring to hear that the idea of the wave/particle duality or complementarity of light, "current half a century ago" (and chosen by Niels Bohr as his motto when knighted by the King of Denmark), is no longer a required belief in modern physics. Yet Mr Coleman (July 'Letters') continues to rely on the duality concept, even in this letter. In his fifth paragraph he refers to Doppler shift, a wave phenomenon (incidentally, is it really the ordinary conductivity electrons that radiate with

this Doppler shift, and how is it measured, please?); then he speaks of "a photon hitting the surface of a metal" and of "an area comparable with the square of its wavelength" in the same sentence. Duality may be dead but it seems reluctant to lie down!

I asked earlier why it was that only one of these (millions of) electrons is ejected by the impact of a single photon. Mr Coleman says the answer is simple, but he does not supply it. The work function (escape energy of a conductivity electron) from a metal surface is measurable, and no visible or ultra-violet photon carries more than a few times this escape energy. If that energy were distributed equally or even thermally among millions of electrons not one of them would have enough energy to escape — yet one of them does. Why? The quantum theory does not try to explain this but, characteristically, side-steps the real question by *assuming* the observed result.

The bunching of visual photons measured by Dontsov & Baz' (*WW* Letters, May, 1983) may perhaps assist in accounting for the interference phenomenon, but it is not required in order to explain the so-called "diffraction" of electrons or gamma-rays. (I have not felt entitled to ignore such facts — indeed, the early articles were concerned with little else!). The mechanism need not be wavelike. In a pin-ball game the ball bearings follow preferred tracks and finish up in preferred places that are predictable statistically but unpredictable individually. This is just what is observed when electrons and photons pass through crystals and are "diffracted". A pin-table doesn't look much like a diffraction grating to me.

W. A. Scott Murray
Kippford-by-Dalbeattie
Galloway


Dr Scott Murray on page 35 of the May 1983 issue of *Wireless World* uses the seepage of water through sand as an analogy for the tunnel effect. A more satisfactory analogy is that of frustrated total internal reflection of light waves.

N. A. de Bruyne
Princeton
New Jersey
USA

DARLINGTON DEVIATION

Mr Gray has pointed out (*WW*, March, 1983, p.62) the limitation of the Darlington in saturation and the advantage of the independent emitter-follower drive. When the main transistor is a power switch, and more especially when it is one of the devices which is operated at $I_b = I_c/5$, an intermediate configuration offers advantages.

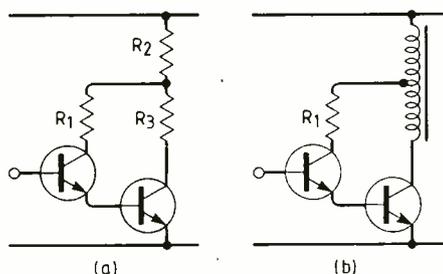The general form is shown in Fig. (a), and (b). In Fig. (a), R_2 and R_3 form the load to be heated. It is obvious that R_2 carries the total current in the two transistors. Provided that the first transistor is robust enough to accept a wide



tolerance of current, the drop in R_3 need only be ($V_{CE\text{ Sat } 1} + V_{BE2} - V_{CE\text{ Sat } 2}$), about half a volt, and the load current is then, for the typical case, increased by some 10-15%. The introduction of R_1 gives better control at the price of lower efficiency.

When an output transformer is used, the circuit of Fig. (b) allows the drive transistor to be limited to anywhere between V_{CC} , for the emitter follower form, and $2V_{CC}$ for the Darlington.

T. Roddam
Arundel
W. Sussex

SATELLITE TV AERIAL ALIGNMENT

I must agree with all the difficulties that N. L. H. Cresdee describes in directing a satellite aerial dish. The problems are especially acute using the 12GHz band, with necessarily large dishes at present in use. In addition, if the receiving lens or reflector is slightly off-focus or boresight, the lobe pattern of the aerial is quite disturbed and you can easily end up optimising for a false or poor maximum.

However, there is one invaluable aid, both to directing and focusing that was not mentioned, and that is the sun. Far from the rarity it would appear to be in the UK, a visual sighting of the sun reflected on to your receiver lens will give you a positional fix close to that of the satellite orbit. The accuracy of this fix depends solely on your ability to know or calculate the local Solar Time.

J. Emmett
Supervisory Engineer
Thames Television
Sundials: Their Theory and Construction. A. E. Waugh, Dover.

RECHARGEABLE H.T. BATTERY

OVER recent months it has been my task to sort over the "debris" of 60 years of life of one family in the one house. One particular item that I have "found" is a Milnes rechargeable h.t. battery (6x120 volt) that I know for fact has not been recharged or used in any way at all since 1956 — and almost certainly was last charged not later than 1952. Imagine my astonishment when a quick check with a multimeter revealed that several of the individual cells still — after 30 years or so — show a potential of at least one volt. I am writing to your journal because I know that your circulation penetrates those institutions where the "brains" are. Someone, somewhere — possibly engaged in storage battery research — could well be interested in this Milnes unit. I feel it would be criminal of me to cast it onto the rubbish heap without first making the effort to put it where it perhaps could be of use. I had over 35 years in radio communication and I only ever saw just two Milnes in my life — this one that my father bought sometime in the 1930's and one other where I first worked in 1943 at Somerton Radio Station: there cannot be very many in existence. I feel that a high percentage of those engaged in radio and electronics today would not even know what it was if one showed it them — hence my approach to you.

W. B. Pash
Somerton
Somerset

FORTH COMPUTER

In his article on a Forth Computer, Brian Woodroffe takes the dangerous step of comparing microprocessor c.p.us by preparing a number of examples of small isolated sections of code.

Whilst I do not wish to take a standpoint in favour of any particular device I would like to point out that this sort of comparison is, at best, worthless and can be misleading. To quote one counter example, the 8088 '+' operation could be carried out via the instructions:

```
POP AX
MOV BP, SP
ADD [BP] AX
```

equal to the 6809 in terms of instructions or, if BP has a fixed relation to SP as is the case in most executing programs:

```
POP AX
ADD [BP + α] AX
```

where X is an assembly time constant. I hasten to point out that I am not trying to challenge his choice of processor but simply to point out that his reasoning is flawed (I have no doubt that any software engineer (sorry Mr Catt) familiar with the other c.p.u. mentioned could improve upon the quoted examples.

J. O'Connor
Crewe

BBC ENGINEERING

May I reply to R. G. Brown (June 'Letters') whose letter I certainly take as constructive criticism rather than abuse.

First of all, most non-news recording in the BBC today is effected on 1 in helical machines, the earlier 2 in quadruplex equipment being progressively phased out. The technical quality obtained with the 1 in helical system is unquestionably superior to that on quadruplex.

Secondly, a lower standard of recording quality is sensibly accepted for e.n.g. work, in the interest of portability. But e.n.g. recording quality could not possibly be matched by a domestic video recorder.

So equipment and engineering standards can certainly not be blamed for Mr Brown's dissatisfaction.

On the other side of the coin, programme makers will always push their technical facilities to the limit. Any improvements in effective sensitivity (ie signal/noise ratio) or other technical parameters will tend to be exploited to give additional programme flexibility in the way of darker or higher-contrast scenes, even more multi-generation dubbing for editing purposes, and more complex special effects. This push for flexibility is very proper and it is the business of engineering to continue with improvements which offer it; but of course a balance must be struck between programme flexibility and technical quality, such that the major part of our audience is pleased with the former and content with the latter. I'm sorry if to Mr Brown's eye we have overstepped the line at times but the final judgements are subjective.

As engineers we remain continually vigilant to see that the flexibility/quality balance is about right. Comments such as those of Mr Brown are useful aids to this vigilance.

D. P. Leggatt
Engineering Information Department
BBC
London

Process control by personal computer

Although most of the general-purpose process control systems still use proportional-integral-derivative algorithms, control techniques which have been too expensive or too complicated to implement not long ago are now made possible using a microcomputer.

This article covers the operation, design procedures and the applications of a microcomputer-based digital dynamic control system (d.d.c.) and underlines how the addition of a simple analogue interface on a small personal computer allows the designer to become familiar with the digital dynamic control techniques in a real (not simulated) environment. The system described consists of an eight multiplexed input a-to-d converter, a d-to-a converter with power outputs and a six input adder. Thus multiple feedback controlling only one output variable is possible. Alternative interfaces are also described; their object is acquiring data and simplifying the software which the microprocessor needs to make data conversion.


Digital process control ousts analogue

The history of automatic control, from the use of ingenious pneumatic controllers to the present-day d.d. control systems, has spanned almost half a century. This evolution has not been the result of a continuous transformation but the consequence of an acceleration-stop process which has been technology's main characteristic since the second World War.

Neither has this evolution occurred without controversy: the technological changes have originated many and sometimes serious polarizations in the designer's opinion. They can be classified into two main controversial groups, the first being an immediate consequence of the technological change. Concerning the control hardware selection, it is generally solved assuming that the ultimate decision is purely a marketing decision. Innovations in hardware often act like perturbations in the decision system.

The theory-practice gap evident in many applications constitutes the second controversy and is the most relevant characteristic in the recent history of automatic control. On the other hand, theory and technology have evolved side by side; from the idea of feedback as a starting point, control theory has developed powerful analytical tools and efficient controllers

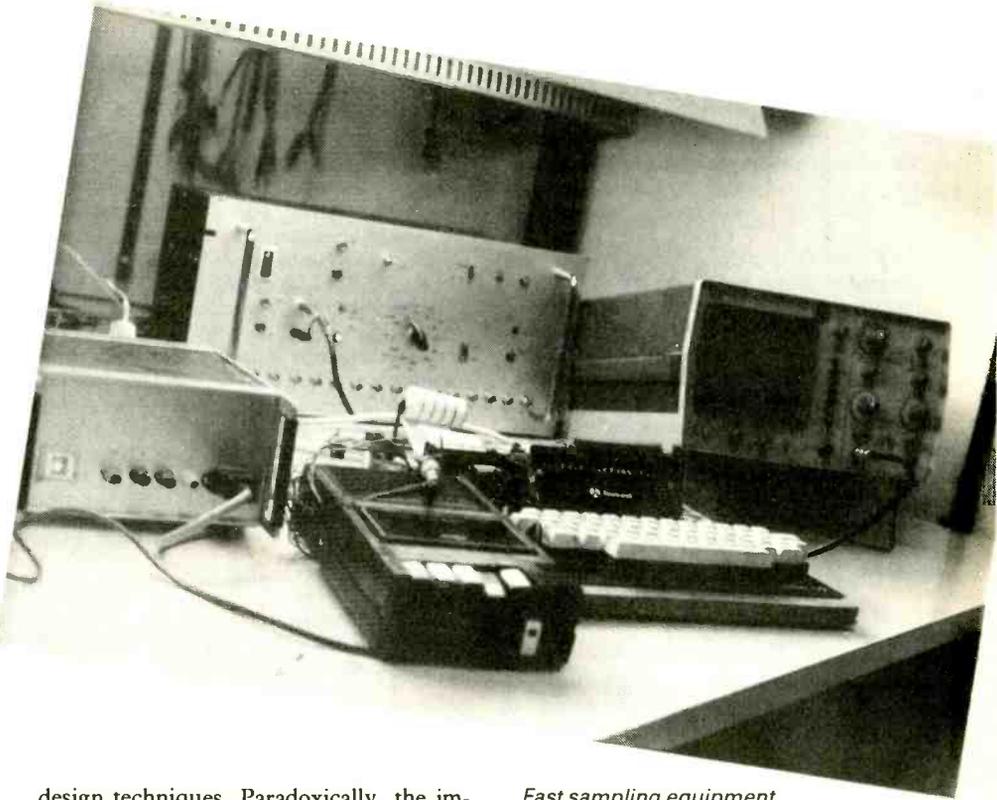Professor Bertrán and colleagues are in the Department de Sistemes de Control, Escuela Técnica Superior de Ingenieros de Telecomunicación, Barcelona, where they teach circuit theory and systems control.



design techniques. Paradoxically, the impact of these achievements has been almost insignificant in the field of industrial applications. Thus p.i.d. action – which has been the main process control algorithm since the beginning of automatic control – still has worldwide acceptance. An inquiry made in USA in 1978 into the control type used by the analogue controllers then in

**by E. Bertrán, L. Martínez,
J. Miguel and I. Munilla**

use revealed that 34 out of 37 listed controllers were p.i.d., either exclusively or with options for proportional-integral or proportional actions. Satisfactory performance in the properly tuned p.i.d. controllers caused other control options to be relegated, whereas electronic technology could have made them possible.

It has not been exclusively a problem of mistrust in the theoretical proposals; an algorithm more sophisticated than p.i.d. implies a more complex and expensive analogue controller. The close relationship between algorithm and hardware complexity didn't allow the practical application of most theoretical models until the introduc-

Fast sampling equipment together with rest of the microcomputer system – Rockwell Aim 65 keyboard, external memory, power supply and oscilloscope.

tion of the digital computer. But not until few years ago could designers count on a real, economical and flexible alternative to the use of p.i.d. analogue controllers. Thus microcomputer-based digital control is competitive even in the area of small applications.

In a direct digital control system the microprocessor performs the controller tasks. The control becomes control by program instead of hardware control by analogue filter. Algorithm complexity is no longer related to the system price but to the computation time, namely to the output delay which constitutes a basic parameter in closed-loop systems. Neither does control sensitivity depend on filter component tolerance, but on computation accuracy (round-off, number of bits representing every coefficient, etc.). Old restrictions disappear while new design factors arise. And finally, software flexibility allows selection of the appropriate algorithm, adoption of a control strategy which allows alternatives (for instance, starting and


steady-state), program linearization of transducer characteristics, etc.

The small personal computer is a very useful tool for designers' practical initiation into d.d.c. techniques and it is mostly used for running either standard programs (e.g. video-games, file-handling) or the users program. Its outer communication is basically limited to the input and storage of data and programs, and to the display. By adding appropriate input/output devices and by means of a special program, this computer can perform the real-time control of any outer device. The small personal computer can therefore be used as a calculator (analysis or design programs), as a simulator (simulation programs with graphical results), and as a controller (real-time control programs).

Equipment scheme and performance

An analogue control interface for the Rockwell Aim-65 microcomputer system has been implemented though the design is easily adaptable to any other computer. It uses eight multiplexed inputs and one output, and has been designed to control low-power devices. Its structure corresponds to the very general functional scheme of Fig. 1.

The analogue input consists of several modules whose performance is controlled by the microcomputer through an input/output port. The multiplexer selects one of its input signals and applies it to the sample and hold circuit whose aim is holding a sample at a fixed voltage during the a-to-d conversion time interval. The converter provides a digital representation of the value of every sample by using a limited number of bits (eight in this case). A decoder allows the microcomputer to read the digital samples through a specific memory address which belongs to the memory space not occupied by rom, ram or other addressable devices. The analogue output consists basically of a d-to-a converter. The microcomputer writes the digital values in an output port which is connected to the above-mentioned d-to-a converter. Finally, an analogue adder

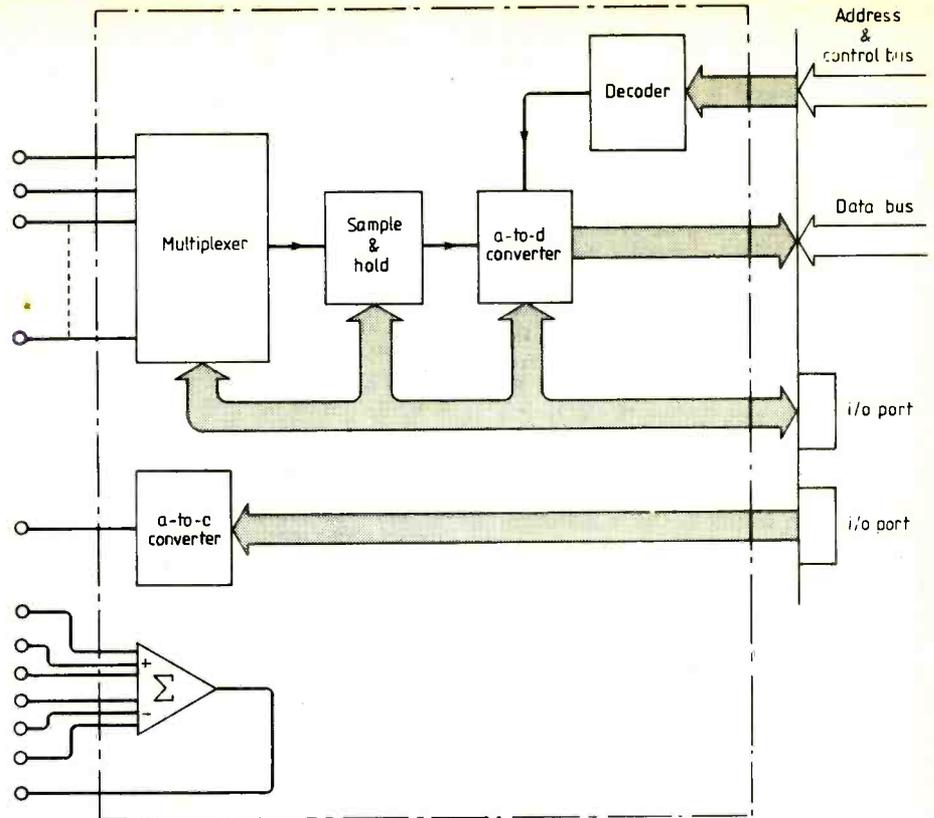

Figs 1 & 2. Functional scheme of the analogue interface (above) together with its detailed system performance (below).

(Σ) with three adding and three subtracting inputs has been incorporated.

The microcomputer system performs the control of the analogue input through the so-called v.i.a., a set of programmable input/output ports, owing to the use of the AIM-65 system. The sequence of tasks for the acquisition of one sample is given below:

- 1 *Programming of v.i.a. port A*, implies that PA₀, PA₁, PA₂ and PA₄ will be the outputs and PA₅ the input.
- 2 *Selection of an analogue input*. According to the binary combination PA₁, PA₀, PA₂, one of the eight possible inputs is chosen.
- 3 *Order of sampling*: A 'one' is loaded in PA₃.
- 4 *Acquisition time*. A minimum time t_A of



5 μ s is needed to ensure that the sample and hold output be equal to the input.

5 *Order of holding*. A '0' is loaded in PA₃.

6 *Delay of opening*. A minimum time t_H of 1 μ s is required to ensure a fixed voltage in the sample and hold output.

7 *Beginning of conversion*. Once the input signal analogue sample is obtained, i.e., t_H microseconds after the 'hold' order, the microcomputer gives the order 'begin of conversion' to the a-d converter by loading a '0' in PA₄.

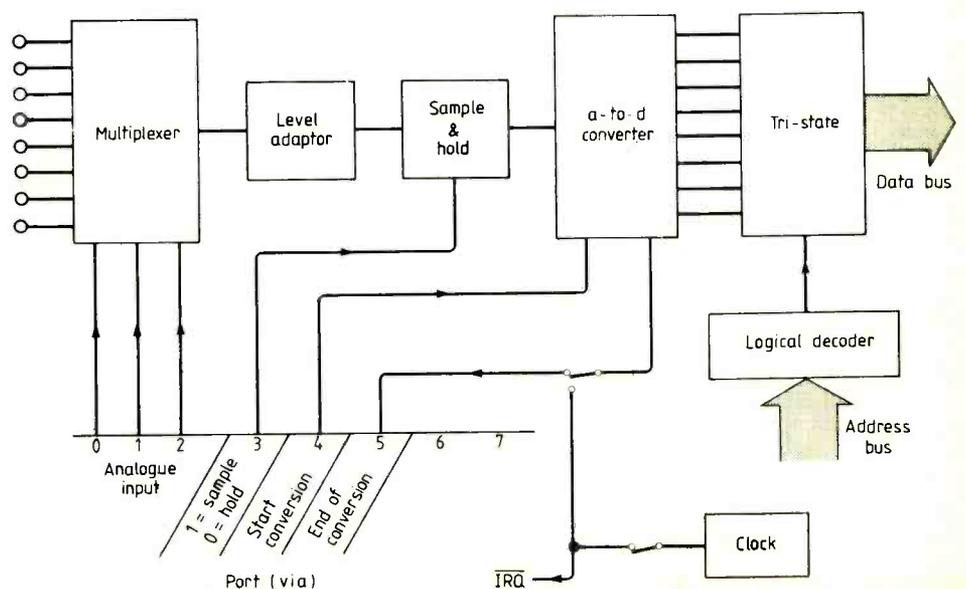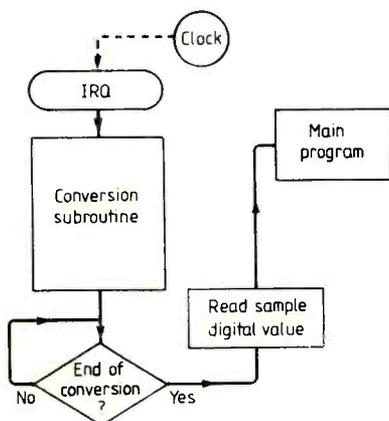8 *End of conversion*. The microcomputer remains in a waiting state until the end of digitization, indicated through PA₅. Therefore it will test either continuously that bit state. By varying the jumper position, the microcomputer may execute other program tasks without making any test since it would receive the end of conversion indication as if it were an interrupt request.



9 Reading of the sample. Once the end of a-to-d conversion is verified, the microcomputer reads the results in a memory position whose address is determined by the logical decoder. This decoder also activates the tristate buffer connected between the a-d converter output pins and the data bus. Fig. 2 shows the system performance when the sampling period is fixed by an external clock and the jumper applies the signal 'end of conversion' to PA₅. Port A is assumed to be initially programmed. Whenever a new clock edge is applied, the task (main program) is interrupted to execute the a-to-d conversion subroutine. As regards the analogue output, the R-2R d-a converter is directly coupled to v.i.a. port B which is output-programmed. Therefore, an analogue signal extracting program is an instruction or a set of instructions that can modify the contents of Port B. A detailed scheme of the acquisition and extracting modules for analogue signals is shown in Fig. 3.

Design alternatives


A similar equipment incorporating two cascaded monostables is shown in Fig. 4. Once the microcomputer gives the order of sampling, the orders 'hold' and 'beginning of conversion' are automatically generated after the necessary opening and holding times. This solution however, is not always optimal. In fact, in many cases it can be much more interesting not to use the monostables even at the cost of generating successively all the orders by microcomputer.

Another contribution of this equipment is the presence of a programmable gain amplifier which offers greater versatility by conforming the optimal range of the sample and hold performance to different possible multiplexor inputs.

Reading the digital code corresponding to the input analogue signal can be made in different ways. Fig. 5 describes the two most important ones, consisting either in the reading of the data as though it were a ram position, or in the reading through an i/o port. Choice of the method will depend on the application and, above all, on the limitations of the microcomputer.

In some applications, like supervision or processes identification, it can be interesting to dispose of a sampling unit with specific services. Fig. 6 shows the functional block diagram of an equipment for fast sampling which has been developed in the Department of Systems Control (E.T.S.I.T., Barcelona). Its performance also differs from the former because the

Fig. 3. Under control of port A, analogue input signals are processed by the multiplexer, amplifier and sample and hold circuit, and digitized by the AD570. Sample digital codes reach the data bus through the three-state 74245. DAC-08 performs the d-a conversion. An error adder is built separately with standard op-amps (LM324).

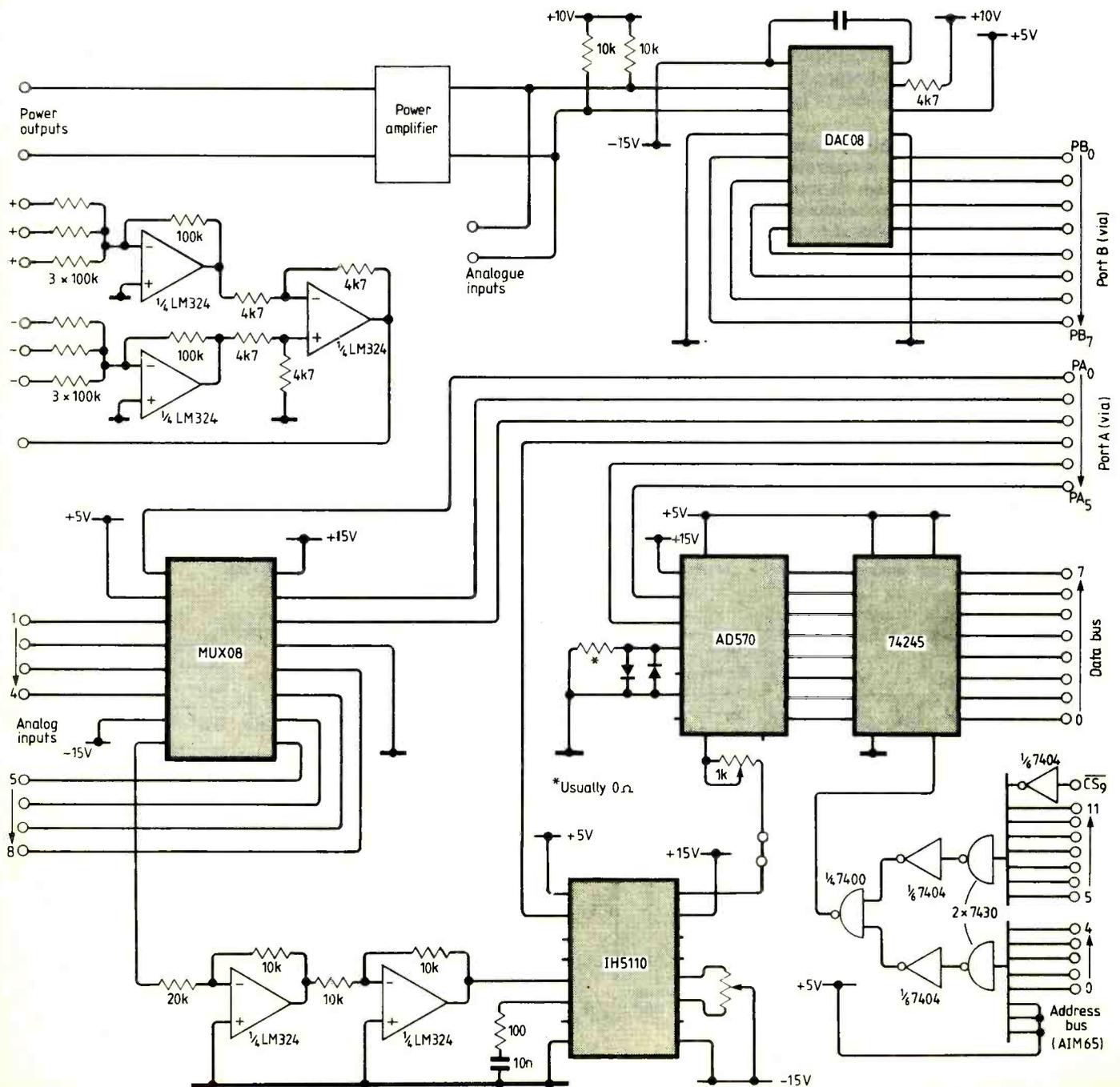

microcomputer initializes a counter by loading the number of consecutive wanted samples from the input signal. These samples are stored in the consecutive positions of a ram at the maximum speed allowed. While the input signal is being sampled, a d.m.a. controller carries the microcomputer to a state of waiting, this taking place only if the computer tries to accede to the ram, which is shared both by the computer and the acquisition system. Thus the information loss coming from the multiplexer is avoided.

With this equipment the rate of sampling can also be selected either automatically or by hand. It also allows sporadic transient phenomena to be registered in the ram, and pulse trains as well as different analogue signals to be generated.





Real time control constitutes the most stringent demand of the afore-described equipments. Computation lags, conversion times and operation accuracy now acquire a relevant design significance. So the basic criteria determining the microcomputer assignment can be classified as follows:

Precision grade — is proportional to the number of bits representing samples and coefficients. **Quantization** is modelled like an added noise to the

Fig. 4. Modified acquisition system automatically provides the delayed hold and beginning of conversion signals which follow the microcomputer sampling order. Two options of end-of-conversion indication can be switch-selected: a flag (bit 5) in the i/o port or an interrupt generation.

Fig. 5. Digital code-reading options: memory mapped or i/o mapped.

Fig. 6. This fast sampling equipment exploits the automatic generation conversion signal shown in Fig 4. The samples can be acquired by blocks of selectable length under control of the direct memory access arbiter.

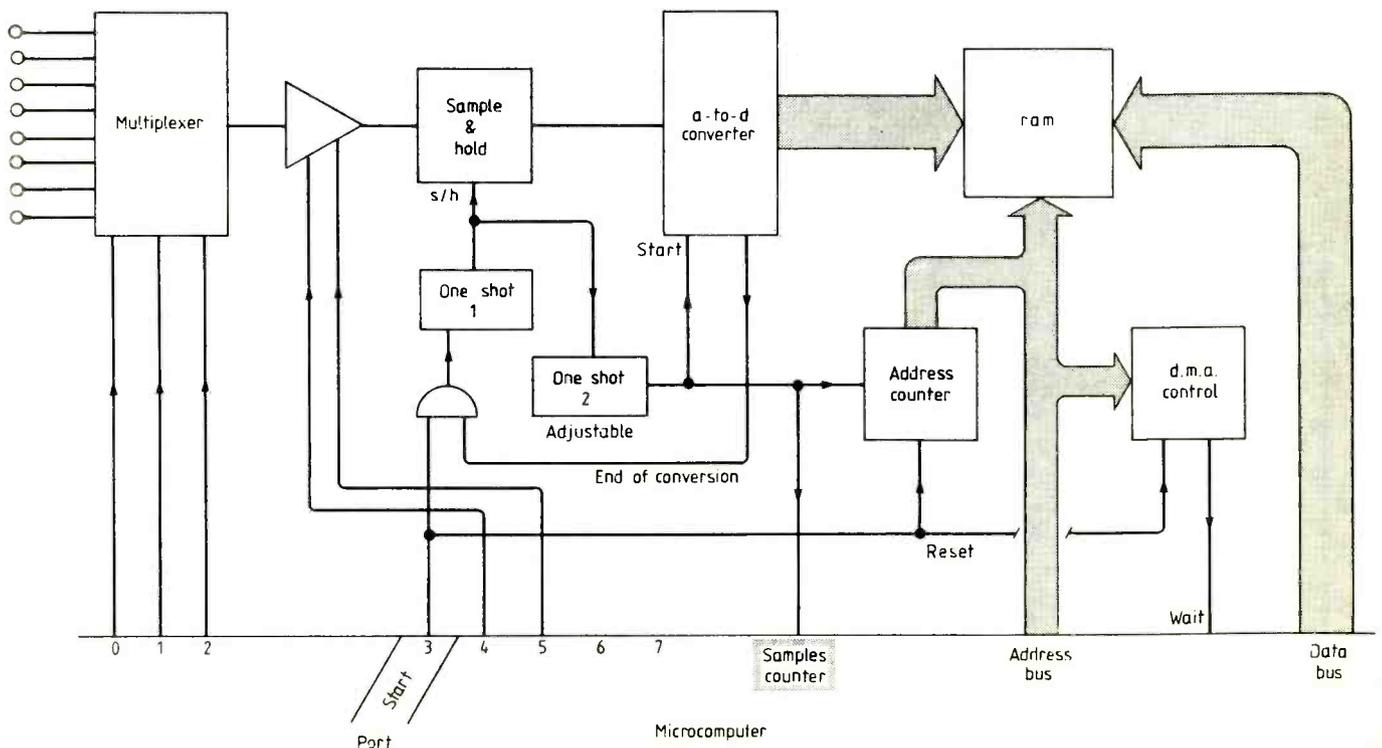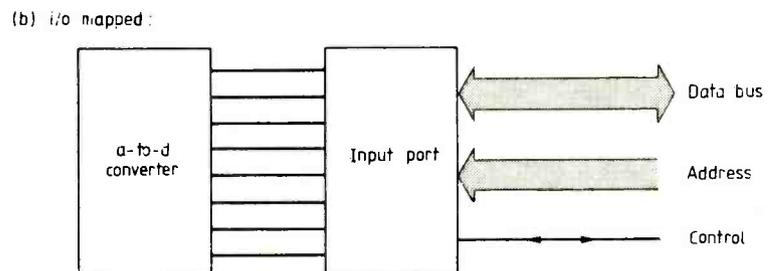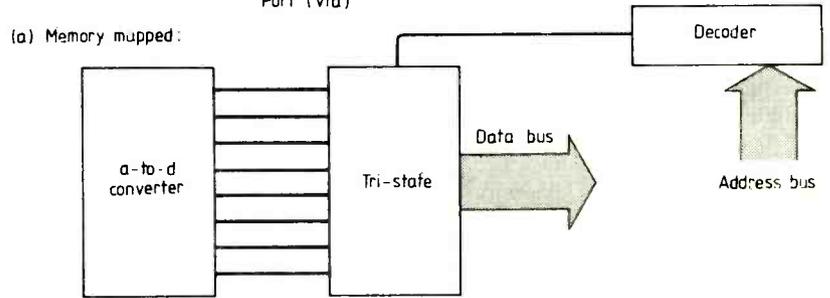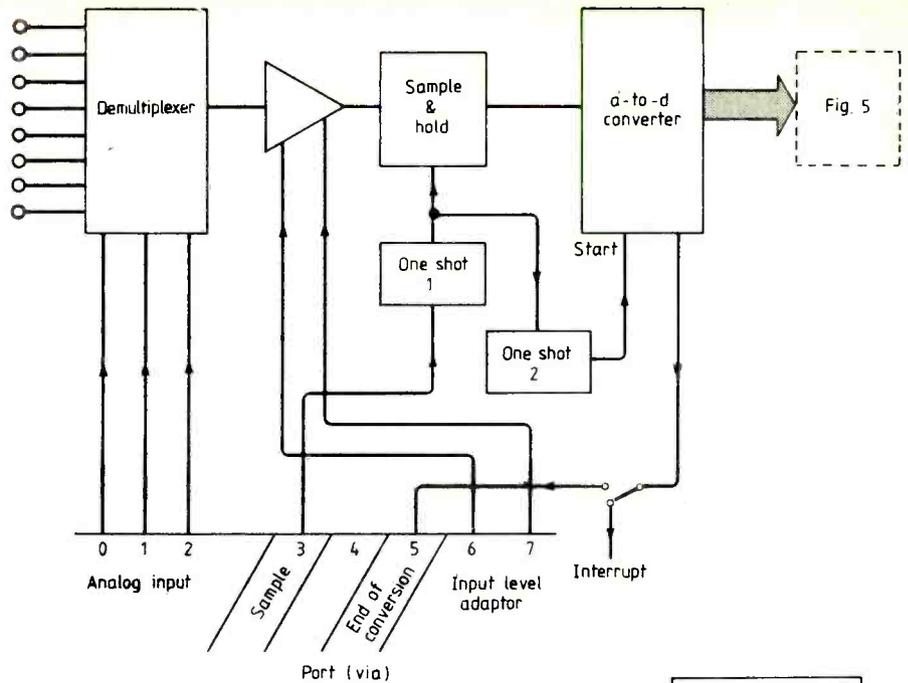

designed ideal filter. It represents the round-off and truncation, both from calculations and from the filter coefficients effective value.

Maximum processing speed — is the inverse of the minimum possible sampling period. This period is calculated by considering the a-to-d conversion time, the control algorithm computation time and the d-to-a conversion time.

Precision criteria

By assuming a uniform distribution of the input samples along the whole amplitude range, an equation can be derived by relating the number of bits (n) used in the a-to-d conversion to the quantization signal-to-noise ratio in the input filter:

$$S/N_q \approx 6n \text{ (dB)}$$

This equation applies exactly to an eight-bit converter. In general, the noise caused by internal operations can be neglected because calculations are usually made with a bigger precision (number of bits) than that used in converters. As regards the filter coefficients, if these have been calculated with a Q digits precision, P bits must be used to maintain that precision. This

Fig. 7. From the digital filter specification, $D(z)$, its corresponding recurrence equation can be obtained. This equation can be written in a more convenient form, substituting each digital sample by its N-bit two-complement representation. Computations will be greatly simplified using precalculated values of F as a function of $x_j^k, x_j^{k-1}, y_j^{k-1}$ (x_j^k being the j-bit of the digital sample $x(k)$, etc.).

Fig. 8. Using distributed arithmetic, the processing speed of an 8-bit microcomputer can be easily multiplied by a factor of 100. 16-bit microcomputers normally include a powerful set of instructions that reduces the differences between the distributed and conventional arithmetic processing. Digital signal processing microprocessors are devices specially suited to signal processing, reaching thus the highest possible speed.

yields the following condition:

$$P \geq 3.3Q.$$

To express the sign, a supplementary bit is used so coefficients internally will need P+1 bits.

If a high-order filter is implemented, then it will be useful to decompose it into second-order sections, either series or parallel-coupled. Thus, global filter behaviour will be less sensitive to quantization errors in computations or in coefficients.

Speed criteria



By using a high-level language (Basic, Fortran, PL1, Pascal, etc.) internal operations are made with great accuracy, and as a consequence processing speed is reduced. On the other hand, using assembler language makes the speed increase at the expense of implementing operations with large errors. This is due to the limitation to eight or 16 bits in the internal representa-

tion, which simplifies the operations; otherwise, speed would be also reduced.

A high processing speed without loss of precision can be obtained by means of a distributed arithmetic. Multiplications are substituted by accesses to table containing calculated values and additions, Fig. 7. Therefore, the best services of an eight-bit standard microprocessor can be obtained at the expense of employing a great memory space (look-up tables). Thus, the antonym speed-precision changes into memory occupation-precision while maintaining the speeds. An example of the effective minimum sampling times with the AIM 65 and the equipment of Fig. 1 are

- 0,2 seconds (Basic and conventional arithmetic)
- 1 millisecond (assembler and eight-bit distributed arithmetic).

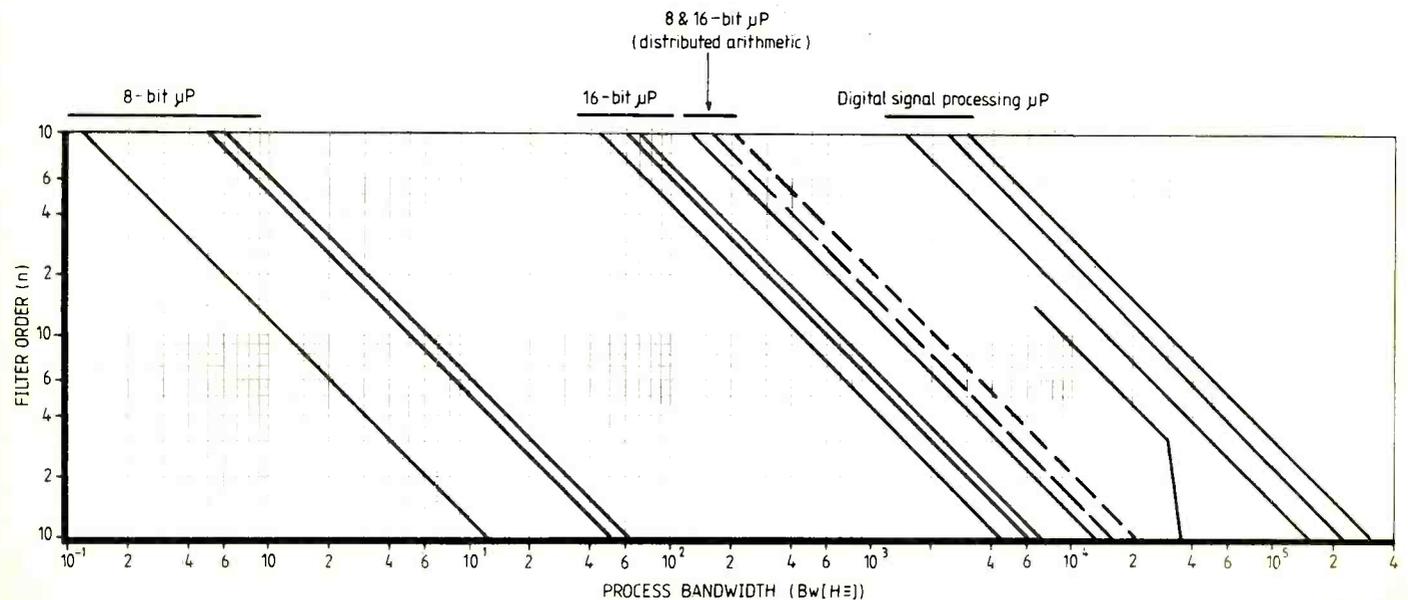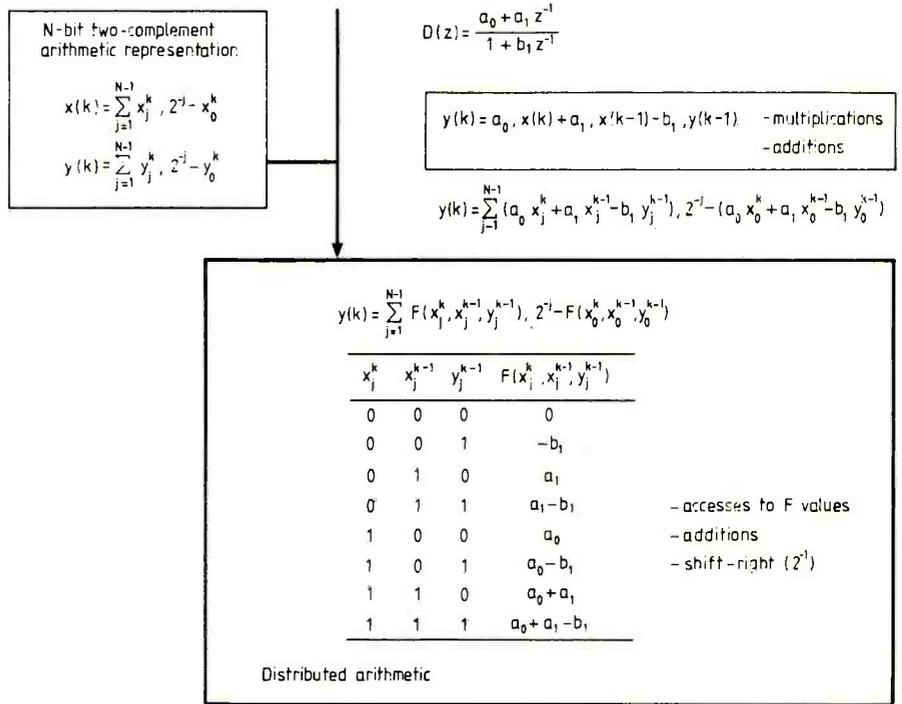These times include the conversions and the internal processing of a second-order correcting filter.



The microcomputer services can be evaluated when implementing a second-order filter; on the other hand, the microcomputer maximum processing speed for an nth-order filter will result from extrapolation as follows:

$$T_n \approx \frac{n}{2} \cdot T_2.$$

This equation means that the processing time of an nth-order filter (T_n) will be approximately $n/2$ times the processing time of a second-order filter (T_2). Decomposition in second-order sections, which is reasonable from the point of view of sensibility, justifies this estimation.

The process bandwidth (B) is a particularly useful parameter in the analysis of the microcomputer applicability to a particular case. This gives a measure of the process response speed to the control signal; a response time of 1 second implies $B \approx 1\text{Hz}$; 1 millisecond corresponds to $B \approx 1\text{kHz}$. According to the sampling theorem, this bandwidth will be related to the processing time as

$$B < \frac{1}{2T_n} = \frac{1}{nT_2}.$$

This condition allows the maximum bandwidth to be determined once the processing time of a second order filter (T_2) and the correct order are known. Figure 8 shows the results obtained in an approximate evaluation for different microprocessors. An important factor in the evaluation of B is the margin for the Nyquist's condition. For instance, $B < 1/10nT_2$ implies that the consequences of the delay computation on the controlled-system performance can be neglected.

Application examples

The main connections in the equipment in Fig. 3 are used for position control of a d.c. servomotor in Fig.9. Position feedback is obtained through the potentiometer transducer.

Fig.10 represents the functional block diagram of the control system. By using the

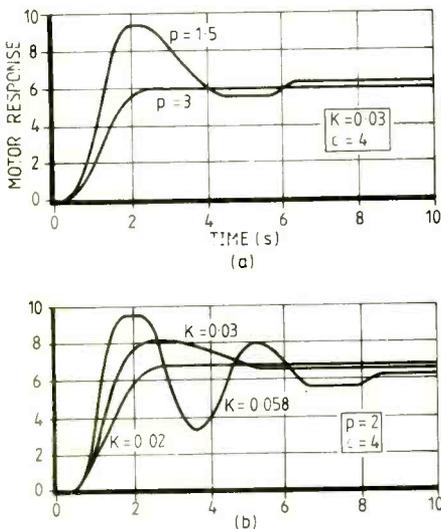


Fig. 11. Motor responses to a six-volt step in the set-point ($p=1.5;3$) - (a) compared with ($k=0.02, 0.03, 0.58$) - (b).


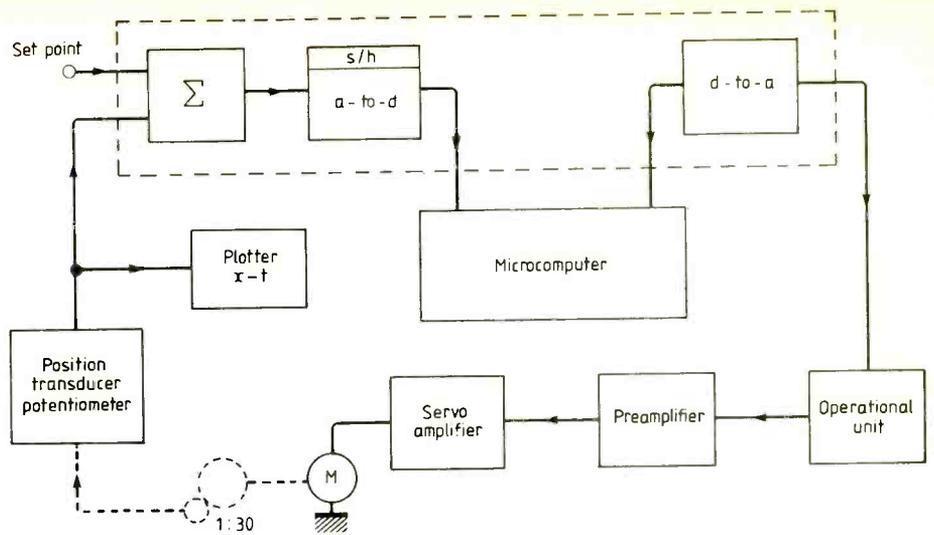


Fig. 9. Schematic representation of a laboratory experience intended to test the performance of the equipment described in Fig. 3 in the position control of a d.c. servomotor.

Fig. 10. Functional model block diagram of the control system implementation of Fig. 9(a).

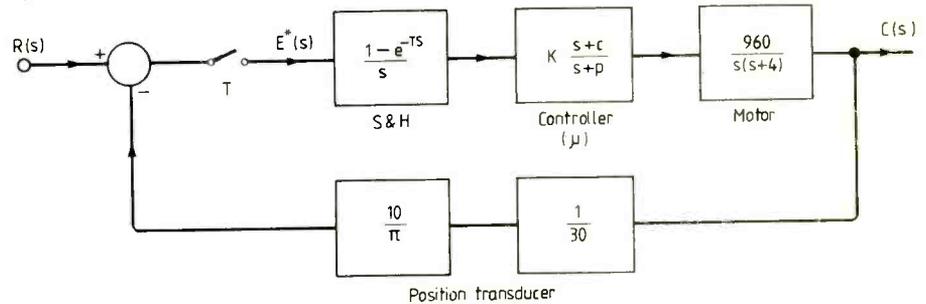

bilinear transformation a lag-lead controller has been programmed in the microcomputer, with the transfer function

$$G_a(s) = K \frac{s+c}{s+p}.$$

Finally motor responses to a six-volt step in the set-point have been obtained for different values of p , Fig.11(a), and K , (b). In spite of the simplicity of this system, it has not been difficult to verify

the importance of the computation time which must be reflected as a transport lag in the system. In fact, if the mechanical time constant of the motor is 0,38 seconds and the controller program execution time 0,16 seconds, Nyquist's condition will be only strictly accomplished. By comparing the real with the simulated response plots, it can be verified that only one of those simulated is correct - the one considering computation delay. WW

EVENTS

August 25-28

Acorn Computer Show (including the launch of the Electron); Cunard International Hotel, Hammersmith Broadway, London. Details from Susan Phipps, Telephone: 01-390 1612.

September 2-4

September Satellite Weekend: organised by the Institute of Broadcast Sound at the BBC Engineering Training Department, Evesham. Details from Jeff Baker, 14 Meadow Close, Marlow, Bucks.

September 2-11

Funkausstellung 83: International audio and video fair. Exhibition grounds and International Congress Centre, Berlin. AMK Berlin, Postfach 1917 40, Messedamm 22 D-1000 Berlin 19.

September 5-9

Many local further education colleges are enrolling for Radio Amateurs' Courses during this week.

Radio Spectrum Conservation

Techniques: IEE International conference, University of Birmingham. IEE, Tel: 01-240 1871 Ext 222.

September 6-8

Electronic Displays, Exhibition and conference, Frankfurt Intercontinental Hotel. Network Exhibitions. Tel: 028 02 5226.

September 6-10

Inteltec 83/Swissdata 83. Two exhibitions at the Swiss Industries Fair Halls, Basle, on industrial and technical electronics and on data processing in technical applications: SMB, CH-4021 Basel, Messeplatz, Switzerland.

September 13-15

Testmex 83: Test and measurement instrumentation technology, exhibition at the Grosvenor House Hotel, Park Lane, London. Details from Evan Steadman Communications, Tel: 0799 22612.

Continued on page 72

Merriman reports

More public accountability is needed in the allocation of slices of the radio spectrum. This is one of the conclusions of the Independent Review of the Radio Spectrum, chaired by Dr James Merriman. The main conclusion of the Merriman Report is that there should be a more positive approach to the regulation of the spectrum and this has already resulted in the transference of the Radio Regulatory Division (RRD) to the Department of Trade and Industry from the Home Office.

One of the main reasons for having the enquiry was to find extra space for land mobile bands and the Report says that although there is enough room to cope up to the late 1980s, problems thereafter are likely to become acute unless significant use can be made of other bands and/or use of 'new technology'. No mention is made of where these other bands may be found although the earlier, interim, Report re-allocated Bands I and III to land mobile use after the demise of the 405-line tv service.

For broadcasting it is recommended that the demand from the "enlarged community of programme makers" should be taken into account in policy formulation, and that the broadcasters should be encouraged to make the maximum use of the existing bands to accommodate their ancillary requirements. But there is "no justification for the provision of additional spectrum for terrestrial tv or sound services . . . in the light of the undoubted emergence of alternatives" [i.e. cable and satellite]. (Public broadcasting in the UK has the smallest allocation of frequencies in Europe.)

Despite outside criticism that the military are somewhat profligate with their frequency allocations, the Review body finds that "there is little scope for the reduction in defence spectrum usage".

Facing that saturation point is likely to be reached soon for fixed services, the Report recommends that early special arrangements be made with all parties concerned to review the policy and practice of frequency spectrum management so that an overall strategy may be developed.

In general the Report concludes that there is no prospect of any significant reserves of unused or underused spectrum being identified in the 30 to 960MHz range and reallocated, so any fundamental decisions need to be taken early on the relative priorities to be given to different services.

In the public accountability and information area the main recommendations

of the Review are to:

- produce an RRD annual report reviewing spectrum policy and management together with explanatory material
- institute regular reviews related to specific user groups
- publish the frequency allocation table
- establish a high-level advisory committee
- use spectrum costing and cost/benefit analysis in management decisions
- review defence usage by a small committee of Privy Councillors
- adjust licence fees periodically to give financial incentive to use more efficient equipment in less congested bands
- allocate adequate resources to spectrum monitoring to aid efficient usage and effective management.

Decisions of responsibility, wherever

practicable, should be delegated to common interest groups, reporting back to the RRD. Services should have some priority over individuals and fixed-term assignments could be adopted, as could short-term provisional assignments, to increase planning and development efficiency.


Because the RRD is understaffed and overworked, according to the Report, it is recommended that sufficient resources be made available for the Division so that it may carry out its duties, especially those activities in cooperation with the Science and Engineering Research Council and the Specially Promoted Programme into Radio Communications Systems.

Finally, the report recommends that radio regulation remains within Government, rather than being made the responsibility of a non-government body. There should be a separate ministerial department responsible for telecommunications or, failing that, responsibility for telecommunications be concentrated in a distinct unit with its own Minister, within an existing Government department.

Crack detection in offshore rigs

A method of testing for cracks in offshore platforms has been developed by British Gas at their Engineering Research Station. Hitherto it has been necessary clean back to the bare structure; removing all marine life and mineral deposits, but a new approach considers that important cracks are only those that let in water. To test if a rig member is full of water, an ultrasonic probe is clamped to the member magnetically and pulses transmitted by cable

from a remote controller on the surface. In a normal air-filled structure the only echo received is from the nearest surface. But if water is present inside, a second echo will be received from the opposite wall. The method requires the minimum of cleaning from the surface of the steel structure and can be handled by divers with no previous experience of n.d.t. Each test takes about a minute and a whole structure can be surveyed in a few days as opposed to months using former methods. The equipment, sensor and remote control/recorder, is being manufactured under licence by Wells-Krautkramer Ltd.

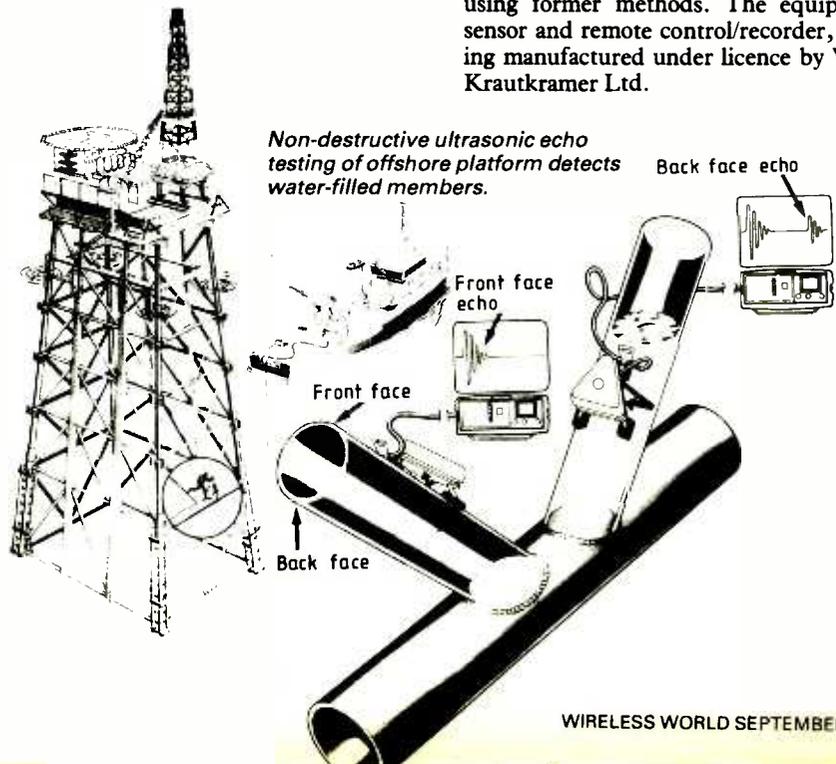

Book-size computer growth 'exponential'

Portable computers – those that fit into a carrying case with a keyboard, display and internal memory with stand-alone ability – are going to have an exponential increase in sales, according to a market research study by Venture Development. The provision of hard-copy as a built-in or add-on printer will be an important factor in differentiation between products, as will the operating system. The amount of memory storage is also considered to be important and yet users are demanding all this in as small a space as possible. This has resulted in the production of 'book-size' computers, the first of which on the market has been the Epson HX20. Many similar types will be introduced soon, but as they get smaller, users will need to choose between size and ease of use.

The survey found that the majority of users were in the scientific and engineering fields. A large proportion also used them for word processing, although portable computers with their inherently small displays do not seem to be particularly suitable for this. Business users like graphics displays for bar graphs and pie charts and the demand for graphics capabilities will increase. The use of electronic mail on portable computers is forecast to increase rapidly over the next five years. The full report, *The portable briefcase computer and terminal industry: A strategic analysis*, is published by Venture Development Corporation, 1 Washington Street, Wellesley, Massachusetts 02181, USA.

News in brief

The opening of a £1M factory marked the culmination of a business that started nine years ago in a kitchen sink. Brian Howard and John Edwards started by making small batches of printed circuit boards. As business expanded they moved to larger premises and eventually acquired Circuit Techniques Ltd. The new factory at Ashford, Middlesex, has two computer-aided design systems for the plotting and designing of multi-layer p.c.b.s. The plant also includes n.c. drilling equipment and the mechanical and optical devices needed to photo-print, align and bond all the layers. The company claims to produce a prototype single-layer board from a designer's sketch in 72 hours, and a 50-off preproduction set of boards within four weeks.

Button cell manufacture in Washington, Tyne & Wear, will no longer be carried out by the Timex Corp, as they have sold the factory to Ray-o-Vac, the US manufac-

More US-UK cable tv bids

A bid for a major share in the cable tv market in Britain has been launched by Plessey Scientific-Atlanta with the introduction of a so-called multistar distribution system designed to meet Government requirements for both 12 and 20-year franchises. The system is based on the conventional tree architecture, but can be upgraded to switched-star if required.

The basis of PSA's network is a three-tier hierarchy of switching nodes capable of servicing various sized groups of homes. A key element in the switched-star version is a new subscriber switch capable of delivering to 20 households as many as three simultaneous tv channels plus the entire 88-108MHz f.m. broadcast band. The three television channels are carried as system I PAL signals in the band 5 – 88MHz, the lower portion of which is allocated to two-way data communications and a 'reverse' video channel allowing contributions to be fed back to the head-end. With some reconfiguration, the switch could also carry the C-MAC transmission format developed by the IBA.

Besides radio-frequency equipment, the unit incorporates a number of microprocessors – one for every three households for control purposes, plus another to relay information from the cable system's central computer. Subscribers can be billed

turer of miniature batteries for use in electronic watches, calculators and hearing aids. Much new equipment is to be installed and the jobs of 85 employees are secure, say Timex.

The 1983 recipient of the Marconi International Fellowship is Francesco Carassa, professor of electrical engineering at the Polytechnic of Milan. The award recognises his 'outstanding contribution to radio-frequency communications, including both land and satellite communications using microwaves'. His experiments in v.h.f. satellite communications culminated in the launch of the Italian Sirio satellite which led to the use of new satellite technologies.

An agreement on basic specifications for magnetic discs to be used in electronic still-picture cameras has been reached by 20 companies in electronics, camera and magnetic tape industries. Over three quarters of the companies involved are Japanese but the alliance includes 3M, Philips and RCA and the specifications are being considered for submission to international organizations.

automatically for the 'pay-per-view' programmes and access to individual channels can be permitted or denied. Non-payers may be cut off instantly against loss of revenues through unauthorised use of the system without the signal degradation often associated with scrambling devices. The computer software for the switch is capable of handling a variety of additional services such as home banking and 'teleshopping'.

In view of the signal radiation problems experienced with some cable systems abroad, PSA's choice of frequencies for the subscriber drops should go some way towards allaying the fears of other spectrum users. The method of construction of the company's demonstration system may be reassuring too: the electronic modules and their switched-mode power supplies are enclosed in separately screened boxes and the outer casing of each unit is sealed with an r.f.-tight gasket.

Upstream from the subscriber switch would be a further node capable of handling 160 households; and above that in a full switched-star system there would be a 1500-point switch. Coaxial cable is to be used for the feeders initially, though the company envisages a change-over to optical fibre when costs have fallen. The capacity of the switching nodes is dictated by typical housing densities in the United Kingdom.

It is expected that the Government will award first batch of cable franchise during the autumn and PSA hopes to have system components ready for the successful applicants from the end of the year onward. The first networks could begin operation in mid-1984.

Plessey Scientific-Atlanta Ltd is owned jointly by Plessey Telecommunications and the American corporation Scientific-Atlanta, from which many of the system's components will at first be imported. However, the company intends to transfer production of the distribution equipment to England, leaving only a few specialised items for the network head-ends to come from the United States.

● Another Anglo-American alliance in the cable tv field has been formed by GEC-McMichael and the Jerrold division of the General Instrument Corporation. GEC Jerrold's activities are to include the design and supply of both switched-star and tree-and-branch systems. The new company will also be concentrating on business users, with products such as a video teleconference system which uses data-rate compression to obtain bandwidth reduction of up to 40:1.

Oric springs Forth

After what seems an interminable wait, some useful software has been published for the Oric-1 computer. There are the inevitable arcade games involving shooting things in space, though some of these do demonstrate the high-resolution colour graphics and high quality sound available. One package which caught our attention is an Oric Forth cassette program with an operation handbook. With it, the Basic-based system runs Forth. Standard FIG Forth is implemented with some additional words specific to the Oric. Programs may be stored in blocks of memory called screens, and a screen editor program is provided. When completed programs can be compiled into the Forth 'dictionary' or list of instructions and executed; they are not separate entities but part of Forth itself. Each instruction is linked to its component parts, which in turn are linked to their component parts, down to the machine-code primitives. This is why Forth is called a 'threaded interpretive language' - each instruction is threaded to others.

In addition to the Forth core and the screen editor, the cassette includes a

machine-code assembler to create primitive Forth words from assembly language mnemonics. This incidentally illustrates the efficiency of Forth; the assembler, written in Forth, occupies less than 4K of memory and yet includes all the 6502 mnemonics, allows the use of labels and macro-assemblies.

A further addition is the 'extension' program which is mostly concerned with specific commands for high-resolution graphics and three-voice music. This is extended by a music demonstration program, Tunemsmith, which enables music to be entered very easily and includes a demonstration tune in three-part harmony.

Loading from tape is slow but only a temporary discomfort as Forth is really designed to be run on disc and a 3in, 100K drive is to be added to the range.

Another addition is a £160 printer/plotter based on the Alps ball-pen mechanism. This has limitations; it is slow (eight character/s) and uses 120mm-wide paper. But it is low cost, has four colours and has a very clear print-out even in the tiny 80 characters/line mode.

Standardisation in gate arrays

Although semi-custom i.c.s are all individual many of them have certain elements in common. Professor Carver Mead and Lynn Conway of Xerox's Palo Alto Research Centre devised an approach to v.l.s.i. design which has been adopted in many universities and in the (American) technical press. The system treats parts of a design as building blocks which may then be arranged to produce the required design. The building blocks themselves are given hierarchical values and are arranged topologically to keep interconnections to a minimum. In a report on the *Mead-Conway approach and other routes to user-designed i.c.s*, the analogy is drawn that designing an i.c. is like designing a house; in a conventional custom i.c., the aim would be to get all the rooms into the least possible space and the first items to be designed would be the bricks and fittings. As a number of designers might be involved, the rooms could be of quite different styles and there may be no immediate connection between the dining room and the kitchen. Services and drains may be spread all round the house. By contrast, the Mead-Conway 'house' would start with blocks to represent the main rooms, as functional blocks and then move these

around so that there is minimal interconnection, with the services together. Device manufacturers are largely ignoring these methods but the report points out that with the appropriate c.a.d. design is passing into the hands of the customers who can use the structured methodology introduced by Mead and Conway. The report was prepared by Mackintosh Consultants Ltd, and is published by Benn Electronics Publications, Luton.

Full-page cable teletext

A version of their full-channel teletext system has been developed by Jasmin Electronics for use on the switched-star multi-channel cable tv system designed by Rediffusion. The use of a full channel rather than the unused lines of a tv raster enables the transmission of 500 pages per second. Another advantage is a very large database capacity. The system can accept pages from Prestel and other data services and can decode the Ceefax/Oracle signals that would be transmitted by the public networks. A subscriber scheme is envisaged and the service would provide at least 1000 pages.

Computer display for partially-sighted

The portable reading aid for the partially-sighted, Viewscan, has been extended to include an information handling system. Viewscan has been coupled to an Epson HX20 portable computer. The system may be used, as before, to scan printed text and produce an enlarged image on the screen (News, March 1982). The improvement means that the text so displayed may also be stored in the computer memory and text may also be entered through the keyboard, viewed on the screen, and edited and stored. The system would seem to be particularly useful to those wishing to gather information from libraries. The combined unit can be carried in a briefcase and can operate from battery or mains. Wormald International, 7 Musters Road, West Bridgford, Nottingham.

Better stereo

The article scheduled for this issue on increasing low-frequency spatial impression in stereo reproduction by Y. Hirata has unavoidably been held over. We received further information in particular details of a circuit applying Dr Hirata's technique too late to include in the article.

Did WW get it right? In Alan Chester's study of the statistical background to the Morse code on pages 62-64 of the August issue, two lines were inadvertently not typeset. So in line 14 of column 2, following 'eight bits', please insert: "On this basis a bit count for all letters of the . . .", and in line 13 of the text on page 64, column 1, after 'sending the passage normally', insert "in a given time. For random code letters are . . ." Finally, in line 14 of column 3 on page 62, 1 word/min=50/60baud, and not 50 to 60.

Crossword solution

	E'								
	C'								
	A'								
F' D' B'	4	2				1	1		
F' D' B		3	1			1	2	1	
F' D B'		3	1						4
F' D B	1		1			2	2	2	
F' D B'			5			3			
F' D B	2			1	1			1	3
F D B'				6				1	1
F D B	1			1	4				2

Clues

B' D' E' F' = 6 A' B D F' = 6
 B' D E' F = 4 B' D E = 6
 B D E F' = 6 A D' E F' = 3
 B D E F = 6 C E F = 8

N. Darwood's numerical crossword appeared on page 62 of the August issue.

Typewriter printer

In the July issue Neil Duffy showed how an electronic daisywheel typewriter could be fitted with an RS232 interface to enable it to double as a printer for a computer. This article describes a few simple changes to the circuit to provide it with a Centronics-compatible parallel interface so that it can be used with micros that don't provide a serial output port.

The design described in the July edition can be readily adapted to enable the typewriter/printer to be driven from a Centronics-compatible parallel port on a personal computer. The connection between the computer and the interface is designed to use a 26-way ribbon cable with alternative wires grounded to prevent cross talk between the signal cores. A 26-way insulation-displacement connector at the interface end is used rather than the more conventional Amphenol 36-way plug because of its lower cost and its compatibility with the Centronics port on the BBC Micro. As with the RS232 interface, correct operation of the handshake between the computer and the typewriter relies on the computer outputting both a line feed and carriage return character at the end of each line.

The main change to the original circuit consists of replacing the uart and the data rate generator (IC₂ and IC₃) with octal buffer IC₁₂ to buffer the incoming parallel data from the computer before feeding it to the existing eprom. The clear-to-send signal originally generated by Tr₂ is no longer needed and the handshake timer circuitry associated with IC₅ is modified to handle the strobe and acknowledge signals associated with the Centronics interface.

Circuit operation

The interface described here is Centronics-compatible, that is, it uses a minimum subset of the signals available on a full Centronics port. The signals actually used are

- seven data lines D₀ to D₆ which are active high and which carry data from the computer to the interface
- a strobe line driven from the computer and which pulses low to indicate that valid data is available
- an acknowledge signal sent from the interface to the computer. This signal pulses low to indicate that data has been received and that the typewriter is ready for the next data strobe.

Relationships during a data transfer to the typewriter are shown in the timing diagram. When a strobe pulse is received from the computer the latch formed by IC₁₃ is set and Tr₃ is turned off. After approximately 63ms (t₁) capacitor C₃ charges up to the threshold level of timer


by Neil Duffy

IC₅ causing its output to go low and reset the latch. Transistor 3 is now turned on again and discharges C₃ through R₂₆. After a further period of 63ms (t₂) the voltage on C₃ falls below the trigger level of the timer and its output goes high again. This causes R₂₄ and C₁₃ to generate a 10µs pulse which is buffered by one of the gates of IC₁₃ and sent to the computer as the acknowledge signal.


Latches IC₁₀ in the original circuit generate a halt signal during a typewriter carriage return or when the paper has run out. These latches are now clocked on the rising edge of the timer output signal. The halt signal is fed to flip-flop IC₁₄ which delays it until the next data word (a line feed) is transferred from the computer. The delayed signal on the output of IC₁₄ is used to prevent the subsequent acknowledge pulse from being generated until the halt condition is removed. This happens

when the line-feed-complete switch on the typewriter operates or when the paper-out condition is removed.

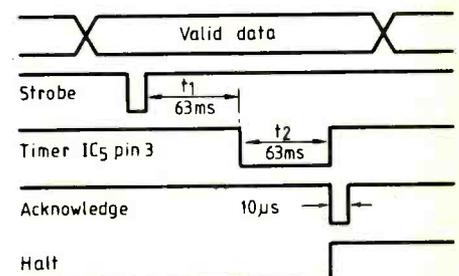Period t₁+t₂ in the timing diagram determine the maximum speed of data transmission between the computer and the typewriter. Because of the tolerance of C₃ it may be necessary to change the value of R₅ to set the speed to around eight characters per second.



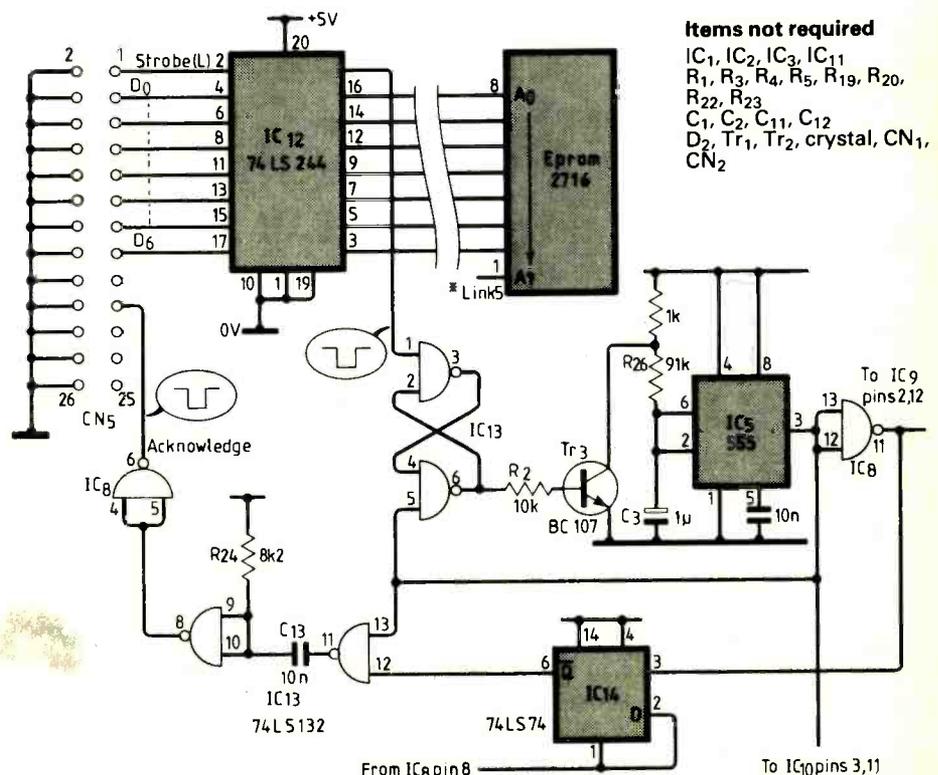In a Centronics parallel interface a strobe pulse from the computer signals that valid data is available. The computer must receive an acknowledge pulse from the peripheral device before any further data transfer can take place.



Forth computer

Exceeding Brian Woodroffe's earlier expectations, his 6809-based Forth computer can be used with disc drives requiring high data-transfer rates — including Sony's microdrive and 8in floppy-disc drives. Access times for standard drives can also be reduced using a minor hardware modification.

After using the computer for a while I became discontented with the disc system because the software caused a one second delay each time access to the disc was required. This waiting time is needed to allow the drive to reach its operating speed — the software doesn't know whether the disc is running or stopped before access — and much of the benefit of the virtual memory system is lost because of this delay. Forth keeps data from a number of disc sectors in memory. When data from a sector that is not in the main memory is requested by the program, Forth overwrites one of the buffers with the required data. But if data in the buffer has been changed Forth first sends the data back to the disc so there can be two 1s delays for one disc call.

Keeping the disc constantly rotating is the easiest way of avoiding this delay but this was rejected because it shortens the life of the drive even though the motor is a brushless d.c. type. The method chosen relies on the fact that disc access operations are not uniform in time i.e., they are likely to come in bursts, especially when loading or listing screens from a disc and as a result of the virtual-memory buffer replacement algorithm described above. Keeping the drive running for a short while after a disc access is made means that it is likely that the disc will be running when the next disc access is required.

Normally, the disc-drive motor is turned off by the disc-select signal going false (p.i.a. A port, D₆, 0 to 1) when the program finishes using the drive. In the modification the drive motor enable signal is held true for five seconds after the drive-select signal goes false by a monostable multivibrator triggered by the trailing edge of the p.i.a. signal. As the software always assumes that the drive is up to speed and available, even though the monostable i.c. might have completed its cycle, a means of ensuring that the WD1793 controller doesn't try to access the drive during the motor start period is required. During this period the ready signal is held false by a further monostable multivibrator fired by the drive-motor start signal. A low-pass filter after the NOR gate combines the two sources of motor-on signal to allow for the set-up time of the 5s monostable.

This small hardware modification, consisting of two s.s.i. devices relieves the software of all considerations of motor-start latency. To prevent erroneous trig-

by B. Woodroffe

gering the two monostable multivibrators should be grounded separately.

Interfacing 8in drives

I found it galling that my 1.5MHz 6809 Forth system could not be interfaced with faster 8in drives, especially as these are often available second-hand at bargain prices. I have not yet got an 8in drive but I have been fortunate enough to try one of the sub-5in drives from Sony which has the same data rate as 8in drives. There is as yet no *de jure* standard for microfloppy-disc drives¹ but within Hewlett Packard, the Sony drive is the *de facto* standard. The first problem is to build a data-service routine that services the disc at a rate better than 11µs/byte. Although nominal disc-data transfer normally takes 16µs/byte, Western Digital specify 11 and 13µs worst-case service times for write and read respectively.

The previously used software loop (*Wireless World*, June 1983) achieves far worse than 11µs, even with the M6809 direct-page register modified to make the

controller i.c. accessible through direct addressing. Analysing the software loop shows that two functions are being carried out — a byte is transferred between the WD1793 controller and ram, and bytes are counted to determine when the sector operation is completed. If the second function could be dispensed with the remaining loop would be much smaller and faster. There would be a small penalty in that the ability to read from and write to consecutive sectors would be lost as no byte count is kept. The problem now is how to break out of the disc-service software loop. Fortunately the controller gives hardware help here in that the IRQ line is activated on completion of every command; the DRQ line is activated for each byte transfer. DRQ, connected to the M6809 FIRQ line, is used in the data transfer loop to make the processor clear its SYNC state, thus synchronizing controller/processor transfers operations.

Interrupt request IRQ is tied to one of the other M6809 interrupt lines so that when a read or write-sector command is complete the processor aborts its current data-transfer loop activity and commences the interrupt routine. On application of the FIRQ signal the processor does not abort the data transfer loop and carry out the FIRQ routine because the program inhibits the FIRQ interrupt by holding the FIRQ mask bit in the condition-code re-


List 1. In this design the following Forth words are available.

LIT	EXECUTE	BRANCH	0BRANCH	(LOOP)	(+LOOP)
<DD>	I	T	K	DIGIT	(FIND)
ENCLOSE	EMIT	KEY	?TERMINAL	CR	CMOVE
UK	U*	U/	AND	OR	XOR
SP#	SP!	RP!	;	+	D+
ATRAUS	DRAINUS	1+	2+	1-	2-
*/MOD	*/	M/MOD	/MOD	/	MOD
R)	R	OVER	DROP	DABS	S->D
+!	!	CP	!	LEAVE	>R
-BUILDS	DOES)	:	:	SWAP	DUP
D	T	?	?	C!	TOGGLE
FIRST	LIMIT	USER	+ORIGIN	CONSTANT	VARIABLE
TIB	WIDTH	WARNING	FENCE	BL	C/L
BLK	TN	OUT	SCR	SR	RO
CURRENT	STATE	BASE	DPL	DP	VOC-LINK
R)	HD	COLUMNS	HERE	OFFSET	CONTEXT
TRAVERGE	LATEST	MIN	MAX	FLD	CSP
?LOADING	?ERROR	?COMP	?EXEC	ALLOT	<
DIGITAL	(CODE)	COUNT	TYPE	<	-DUP
PI	EXPECT	QUERY	DEPTH	<	NFA
MARKS	HOLD	PAD	X	<	?PAIRS
LITND	(ABORT)	ERROR	WORD	<	SMUDGE
LITERAL	DI LITERAL	INTERPRET	ID	<	-TRAILING
USE	PREV	ABORT	IMMEDIATE	<	?STACK
LOAD	THEN	+RDEF	COLD	<	FILL
ENDIF	AGAIN	DO	(LINE)	<	(NUMBER)
END	SPACES	REPEAT	FORGET	<	CREATE
CR	D.	?	LOOP	<	VOCABULARY
DUMP	VE IS!	B/BUF	IF	<	WARM
DRQ	DRI	EMPTY-BUFFERS	!	<	(LINE)
UPDATE	NOOP		?	<	BACK
			B/SCR	<	+LOOP
			DRIVE	<	ELSE
			FLUSH	<	?
				<	LIST
				<	SCR)BLK
				<	R/W
				<	FORTH
				<	MESSAGE
				<	INDEX
				<	USEBLK
				<	CODE
				<	TASK

Brian Woodroffe works in research and development at Hewlett Packard.

Drive	Density	WD1793 (pin 24)	Data separator
8 in	Double	2MHz	8MHz
	Single	2MHz	4MHz
5 1/4 in	Double	1MHz	4MHz
	Single	1MHz	2MHz

Additional circuits shown by tone

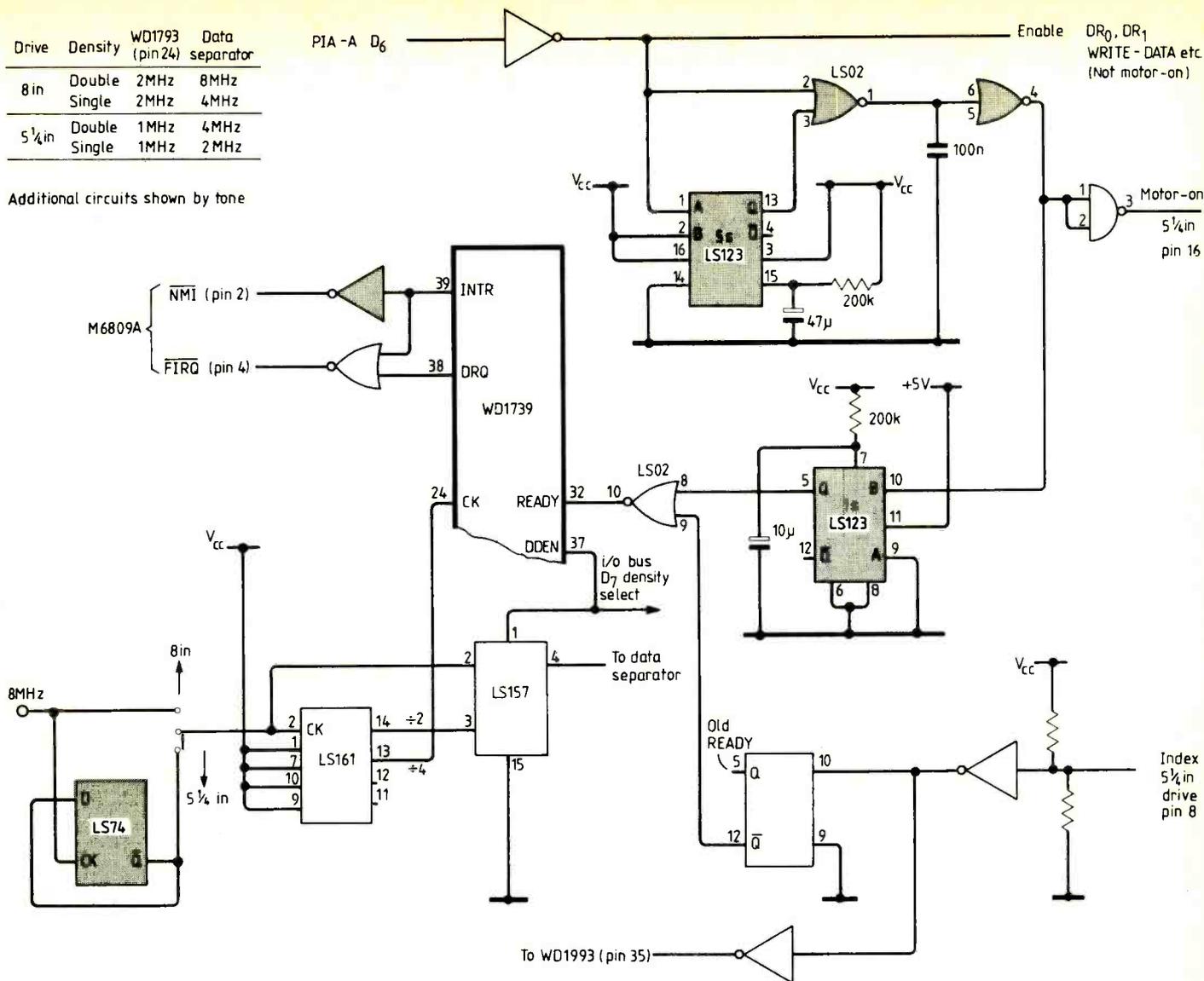


▲ **Disc interface modification speeds up overall access time by keeping the drive motor running for five seconds after the computer tells it to switch off. This significantly reduces the effect of a one second delay required for the motor to start up since disc-access operations tend to come in bursts.**

U.h.f. modulator connects to the video-controller circuit output (see June issue) so that the computer can be used with a standard tv set.


gister set. The controller interrupt-request line IRQ, being connected to the processor's non-maskable interrupt input NMI, can never be masked so when this line is true the processor must be interrupted and goes to the routine requested by IRQ. The processor IRQ interrupt-request input could have been used but I wanted to leave it free for expansion.

For sector read and write operations the disc controller interrupts on transfer of the last byte. In the case of a sector-write operation the data-transfer routine is finished when the last byte is written into the controller. In sector read operations the data transfer routine is finished not when the last byte is read from the controller, but when it is written into the ram sector buffer. So when a sector is written the

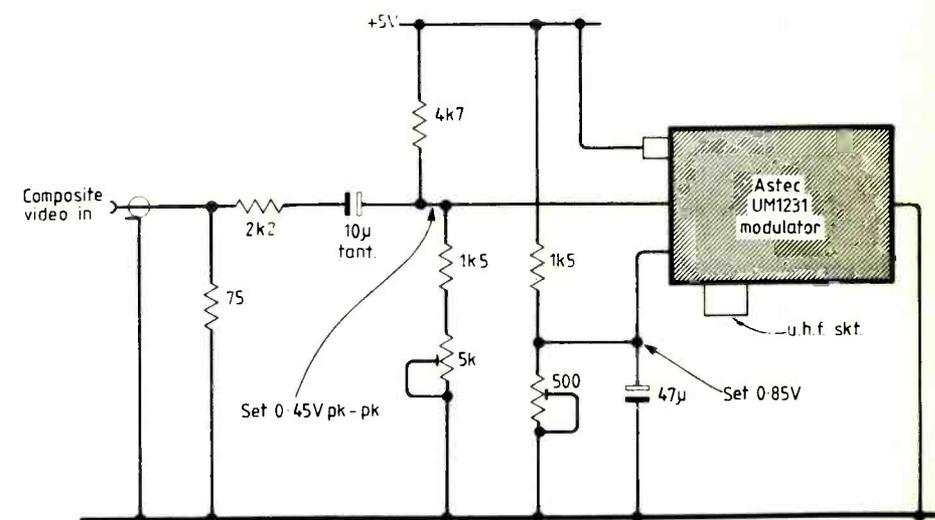

controller interrupts after all data transfers have taken place but when sectors are read the controller causes a jump out of the software loop before the last memory-storage operation is carried out. Worse still, latency before the controller interrupt is variable so when an interruption is made, whether or not the memory has been updated remains in doubt. The solution I chose was to code the data-transfer loop so as to maximize the time between reading data from the controller and writing it into

the memory. Inclusion of a no-operation, NOP, increases the data-transfer loop time to just under the allowable maximum of 13µs to ensure that the controller always interrupts before the processor can write the byte into memory; the first operation of the interrupt routine is to write that byte into memory. Unfortunately this writing operation done outside the data-transfer loop means that the interrupt routines for sector reading and writing must be different.

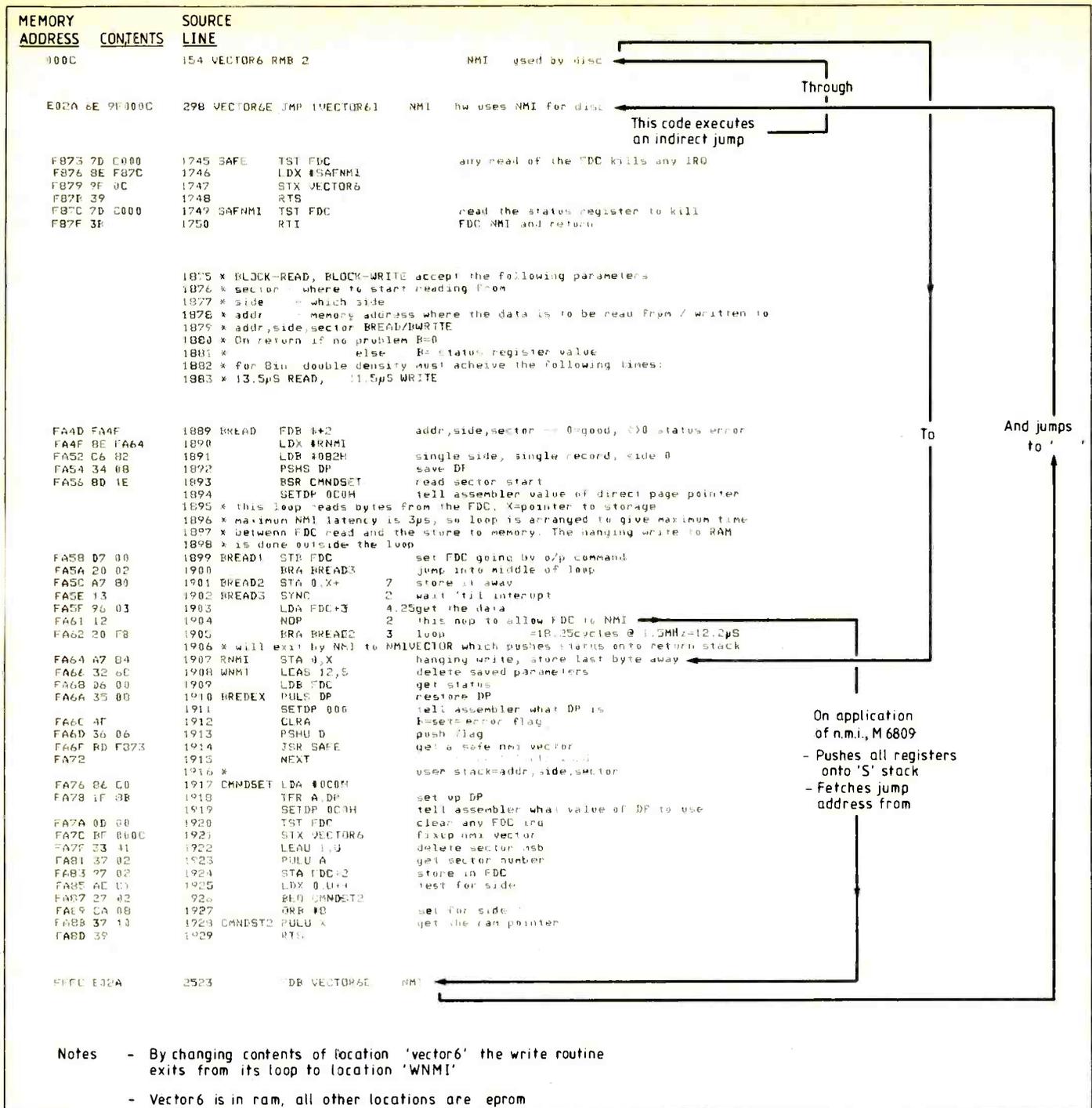

The processor starts its interrupt sequence by pushing appropriate registers onto the stack and jumping to code pointed to by a vector in high memory. In this Forth system high memory is eprom so the interrupt vectors cannot be changed to point to different routines. I remedied this by making the interrupt vectors point to code which executes a jump to a location determined by a value stored in ram. By changing data in the ram location the non-maskable interrupt vector can be altered during program execution. This practice is unstructured and therefore unfashionable, but it is highly effective.

Normally an interrupt routine is completed by a return-from-interrupt instruction which restores processor register values to those prior to the interrupt, i.e. restore context. In this case the interrupt vector is being used as a jump instruction to jump out of the data-transfer loop so the first operation in the NMI routine is to

Diagram of program flow during a sector read on the Forth computer.

delete saved registers (LEAS 12,S). As the controller is connected to the non-maskable interrupt line there is the potential for the occurrence of an interrupt when one is not required. To prevent this the NMI vector points to a safe routine when not in use which reads the controller status register, clearing the cause of the interrupt before carrying out a more normal return from interrupt, RTI, operation.

Extra signals to the disc drives, e.g. track 42, should be inverted and buffered using standard t.t.l. open-collector drivers (7438) as used for the WGATE signal. Extra input signals from the drive such as READY should be buffered using say two LS14 gates, and terminated as previously shown. I should have used the drive's ready signal, eliminating one of the monostable multivibrators connected to the index line but I did not. Also I connected my

motor-on signal (5.25in drive, pin16) to the Sony drive head-load line, pin 14, whereas I should have used hold, HLD on pin 28 of the controller. These minor modifications were made because I still intend to use 5.25in drives as they currently offer better value for money than the Sony drives at one-off prices.

The matter of write-precompensation has not yet been resolved. I found by trial and error that for the Sony drive at least write-precompensation is not mandatory. It might be necessary for older 8in drives, and in commercial products to minimize the number of attempts to read the disc. Details of precompensation circuits are given in the Western Digital handbook and reference two.

For drives that keep the disc rotating, such as Sony's and most 8in drives, the disc speed-up hardware previously described should not be fitted but the drive should be connected with the motor-on

List 2. Forth words specific to this system.

Note the movement of data onto and off the stack is shown thus
 s1 s2 ...ABC... r1 r2 r3
 Forth word 'ABC' takes two values off the stack (s2=top of stack) and produces three results (r3=new top of stack).

VEHIT,VKEY,V?TER = a user variable containing the execution vector for EMIT,KEY, ?TERMINAL respectively
 ..VEHIT..addr ..VKEY..addr ..V?TER..addr

DPMAX = a user variable containing the maximum address for the dictionary.
 ..DPMAX..addr

SMAX = a user variable containing the maximum depth of data stack allowed for this user
 ..SMAX..addr

PI,PE = a WORD to store a byte to, read a byte from one of the user ports
 data.addr..PI..addr..PE..data

DENSITY = a constant =0 for single density; -1 for double density
 ..DENSITY..boolean

DR-SEL = a WORD to select the drive value top of stack
 value..DR-SEL..

DE-SEL = a WORD to deselect the disc drives
 ..DE-SEL..

VERIFY = a variable which if true causes a read after write verify of disc writes
 ..VERIFY..addr

SIDE/DISC = a constant returning the number of sides per disc
 ..SIDE/DISC..value

SEC/TRK,TRK/SIDE = constants returning the number of sectors per track and tracks per disc respectively.
 ..SEC/TRK..value ..TRK/SIDE..value

SIDE = a WORD to select the side of the disc depending on the value at top of stack
 value..SIDE..

?WRITE = if disc is write-protected issue error message 10 and abort execution to return to terminal mode
 ..?WRITE..

CMND = a WORD to execute DOS/PC command at top of stack
 value..CMND..

RATE = a CONSTANT which equals the disc drive stepping rate as coded for the WD1793
 ..RATE..value

SEEK = steps the floppy drive to seek the track that is at top of stack
 value..SEEK..

STEP = a WORD to step the floppy disc, IN if TOS=1
 OUT if TOS=-1
 same direction if TOS=0
 value..SEEK..

R-ADR = reads the address mark off the disc, either returns a/ flag=true if unsuccessful (status of WD1793) b/ sector_type, sector, side, track, false flag
 ..R-ADR.. type sector side track 0 or
 ..R-ADR.. true

BREAD,RWRITE = similar to FORTH BLOCK_READ, BLOCK_WRITE except additional parameters are included; sector within a track.
 returns WD1793 status 0=successful
 address side sector ..BREAD.. status

SEC-R/W = similar to FORTH R/W except no limit checking is done. Returns to top of stack a flag: 0=successful operation
 1=disc error
 2=seek error
 3=not ready
 addr sector flag ..SEC-R/W.. status

TRK-WR = a WORD to write a whole track to disc; used in formatting a disc. Takes from the stack the address of the track image. Return WD1793 status: 0=successful
 addr..TRK-WR.. status

TRK-BLD = a WORD to build in memory a byte image of a track prior to be written out by TRK-WR. Takes as input the side and track number whose image is to be formed and produces the address of where the image is.
 side track ..TRK-BLD.. addr

?DISC = a WORD to find out what sort of disc is on the drive.
 sets CONSTANTS B/RUF,DENSITY,SEC/TRK to suit.
 ..?DISC..

MS = a WORD to delay execution by the number of milliseconds that is top of stack
 value..MS..

PREM = currently a no operation word, that can be patched to allow interleaving of the sectors when formatting a disc. Intended usage is that it will multiply the sector number currently at top of stack
 sector_num ..SKEW.. sector_num

signal permanently true, i.e. grounded.

Software issued (first revision) assumes the presence of disc speed-up hardware and includes the faster data-transfer loop. I will supply a drive pin connection list and format program for the Sony drive that can be modified for 8in drives to readers sending an s.a.e. to me at 632 Queensferry Road, Edinburgh. The Forth word BLD-TRK in eprom is only suitable for mini-floppy disc drives.

Thanks to Hewlett Packard for the use of their test equipment and Sony for the loan of a microdrive. Software used, based on the FIG model, was prepared on an HP64000 microprocessor development system.

Integrated circuits 87 and 88 were missing from last month's components list. They are 2114 static rams. In the photo-

graph of power-supply spikes, vertical sensitivity for all but the clock signal is 0.5V/div.

References

1. J. Bovin, Floppy incompatibility, *Systems International*, May 1983, p.61.
2. J. Hoepfner and L. Wall, Encoding/decoding techniques double floppy disc capacity, *Computer Design*, Feb. 1980, pp. 127-135. WWW

Brian Woodroffe plans to describe the Forth language in a subsequent series.

Wireless World Forth computer Introduction, c.p.u. and memory circuits, May 1983, pp. 53-8.

Circuit description, video-controller circuit and peripherals, June 1983, pp. 55-8.

Software, disc controller and power supply circuits, July 1983, pp. 58-61.

Construction tips, August 1983, pp.44,45.

Complementary current mirror

Current mirrors with transistors of the same type of conductance are well known¹ and widely used in integrated circuits². It is possible to create the configuration with similar properties using complementary transistors also, Fig. a. Accepting the usual assumptions² that

$$I_{C1} = I_{S1} \exp(V_{BE1}/V_T)$$

$$I_{C2} = I_{S2} \exp(V_{BE2}/V_T)$$

$$I_{B1} = I_{C1}/\beta_{F1}$$


and $I_{B2} = I_{S2}/\beta_{F2}$, the output current is

$$I_{C2} = \frac{I_0}{\left(1 + \frac{1}{\beta_{F1}}\right) \frac{I_{S1}}{I_{S2}} + \frac{1}{\beta_{F2}}}$$

with $|V_{BE1}| = V_{BE2}$. If the technology allows two complementary transistors with $I_{S1} = I_{S2}$, then

$$I_{C2} = \frac{I_0}{1 + \frac{1}{\beta_{F1}} + \frac{1}{\beta_{F2}}} \approx I_0 \left(1 - \frac{1}{\beta_{F1}} - \frac{1}{\beta_{F2}}\right)$$

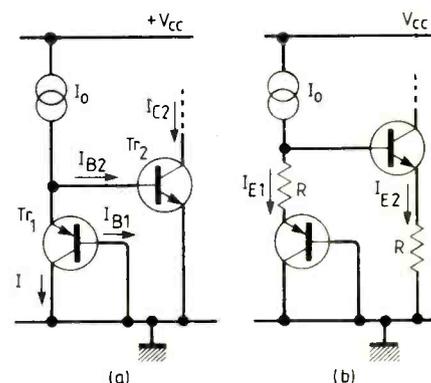as in the ordinary current mirror. Usually n-p-n and p-n-p transistors in an integrated technology are produced by different methods and parameters I_{S1} and I_{S2}



Complementary transistor current mirror with matched transistor (a) and matched emitter resistances (b).

are not matched. But the discrete current mirror with matched resistors in emitter circuits works reasonably well, Fig. b. In this circuit

$$I_{E1}R + |V_{BE1}| = V_{BE2} + I_{E2}R$$

and

$$I_{E1} = I_{E2} + \frac{|V_{BE1}| - V_{BE2}}{R}$$

If transistors are designed for complementary operation, say 2N4401 and 2N4403, and emitter resistors are matched to within 1% the error is 2 to 3% without preliminary transistor matching. The gain β_{F1} of a discrete p-n-p transistor is usually high and the collector currents happen to be matched also. — I. M. Filanovsky, University of Alberta.

1. F.J. Lidgey. Looking into current mirrors. *Wireless World*, October, 1979, vol. 68, pp. 51-58.

2. P. Gray, R. Meyer. Analysis and design of analog integrated circuits. Wiley, 1977. WWW

CIRCUIT IDEAS

555 mark/space control


The frequently used 555 astable circuit¹ with one capacitor (a) has the disadvantage that the capacitor C is charged through R_1 and R_2 and is discharged through R_2 . Any variation of R_2 will change both the charge and discharge time.

A circuit where the same capacitor is charged and discharged by independently controlled currents is shown at (b). In the first quasi-stable state C is charged by the current source Tr_1, Tr_2 when the switch Tr_5 is closed and the transistor Tr_3 of the discharging current source is off (the inner switch of the 555 timer is open). Charge current is $I_c \approx (V_{cc} - 0.7)/R_1$ and the mark duration is $T_1 = V_{cc}C/3I_c$. Capacitor C will be charged up to $2V_{cc}/3$. Then the inner switch of the 555 timer (pin 7) closes. Simultaneously the switch Tr_5 opens and the circuit flips to its second quasistable state. Potential on pin 7 becomes close to 0V. Capacitor C starts to discharge. The discharge current

$$I_d \approx \frac{(V_{cc} - 0.7)}{(R_2 + R_4)} \cdot \frac{R_4}{R_3}$$

and the space duration is $T_2 = V_{cc}C/3I_d$. When C discharges to $V_{cc}/3$ the circuit returns to the first quasistable state.

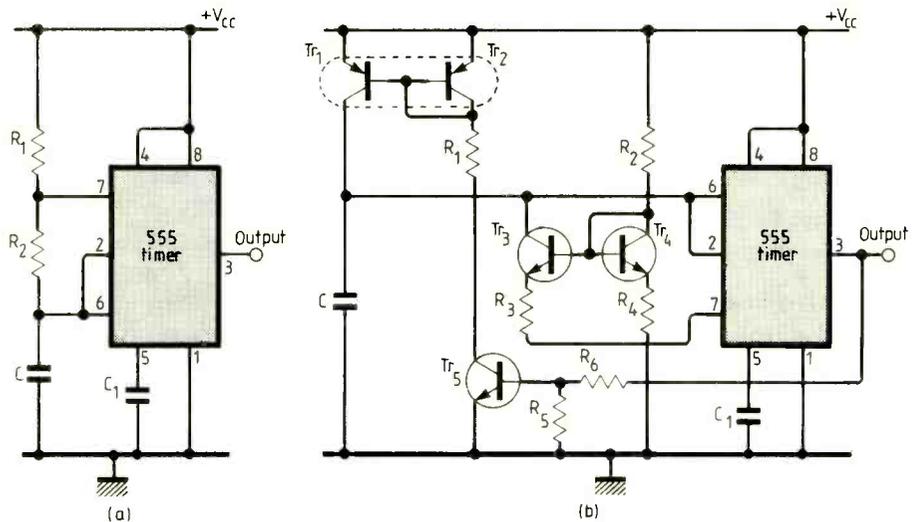This circuit can be used without matched transistors in the current source



Tr_1, Tr_2 . In this case we have to introduce resistors² in the emitter circuits of Tr_1 and Tr_2 as in Tr_3 and Tr_4 (the emitter resistor of Tr_1 in this case can be used for frequency control as well). For the current source Tr_3, Tr_4 the resistor R_3 and R_4 are necessary to compensate for the saturation voltage of the 555 inner switch (this voltage can be as large as 0.1V).

Mark/space ratio for this circuit is $T_1/T_2 = I_d/I_c$. It is easily controlled, and T_2/T_1 of the order of 10^{-3} can be achieved without difficulty, taking into consider-

ation practical limitations for transistor currents.

I. M. Filanovsky, V. A. Piskarev
University of Alberta
Canada

1. J.L. Linsley Hood 555-Type integrated circuits. *Wireless World*, April 1982, pp. 41-43.
2. U. Tietze, Ch. Schenk. *Advanced Electronic Circuits*. Springer-Verlag, 1978.
3. F.J. Lidgley. Looking into current mirrors. *Wireless World*, October 1979, pp. 57, 58, 68.

*Predictable relay oscillator. Switch S of this circuit in the August issue was the one at the top of the diagram.

Acoustic timer with bargraph display

Devised to monitor the response time of an acoustic impulse system, the start pulse in this circuit is derived from the stimulation and the stop pulse from a pressure sensor. As several supposedly identical sources were triggered simultaneously, and the important parameters were output phase and repeatability rather than absolute delay, a multiple bargraph display gave the best visual readout.

The most attractive feature is that only one control wire is needed to each bargraph display; no current-limiting resistors are needed and each display takes only 40mA of current irrespective of the number of segments lit. Calibration is unnecessary, device tolerances being well within the 10% display resolution.

The ZN425E is used in the counting d-to-a mode, and will accept clock rates of up to 1MHz. Using the internal 2.55V reference, one clock pulse gives an output step of 10mV. With full scale on the D634P needing 1.0V, this corresponds to 100 clock pulses; a 100kHz clock gives a full scale of 1ms, and the scale can be changed merely by changing the clock frequency.

The m.s.b. output will go high at a count of 128 (= 1.28V). By or-ing this with the stop input, the display will always give a "full house" reading when the stop pulse

is missing or outside the pulse window.


For measuring such items as pulse jitter about a mean, the effective accuracy of the display can be increased by introducing a fixed delay in the start pulse to bring it closer to the stop pulse, and increasing the clock frequency.

Trevor S. Smith
Stag Electronics
Hebden Bridge
W. Yorkshire

Don't waste good ideas

We prefer circuit ideas with neat drawings and widely-spaced typescripts, but we would rather have scribbles on "the back of an envelope" than let good ideas be wasted.

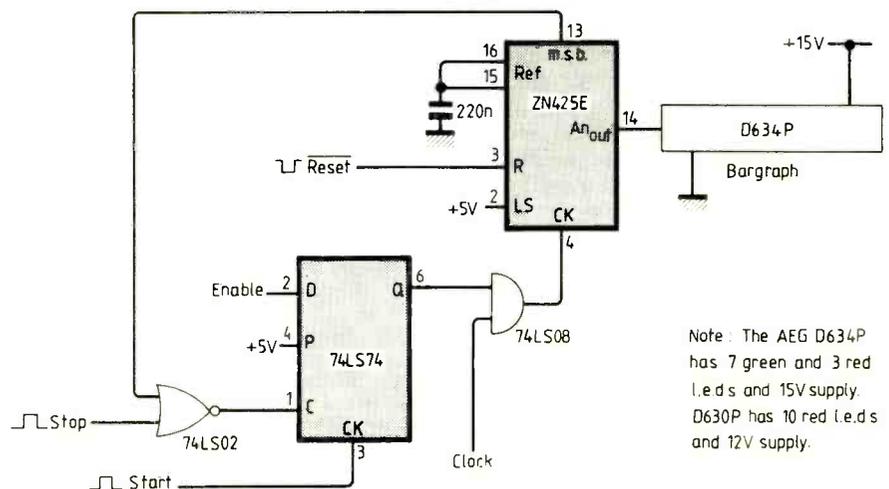Submissions are judged on originality or usefulness - not excluding imaginative modifications to existing circuits - so these points should be brought to the fore, preferably in the first sentence. Minimum payment of £20 is made for published circuits, normally early in the month following publication.



Simpler combination lock

This simple and cheap circuit has been in use for over three years on an entrance door to a clean-room and has suffered only one breakdown caused by "infant mortality" of a leaky BC108 transistor.

Three push-buttons have to be operated in sequence to open the lock. Pressing an incorrect button inhibits lock operation for approximately 20 seconds. A person trying to gain access without knowing the combination would not know how long to wait between attempts, and therefore might miss the successful combination. There are 700 possible combinations of 3 different keys from 10, so waiting 20 seconds between entries will take approximately 10 hours to try them all. If an authorized person hits a wrong key, the 20 seconds is not too long to wait until a new attempt can be made. Of course, the time delays or even the number of keys can be altered as appropriate for the security level required.


The code for the lock can be hard-wired by connecting the push-buttons directly to the circuit, or can be changed as shown in the circuit diagram by routing the connections through a 28-pin d.i.l. socket or any other appropriate patch plug. The three active push-buttons are jumpered across the first, second and third digit inputs, and

RF notch filter has wide range

Designed to operate from the low to the high radio-frequency range, this notch filter provides -76dB stopband attenuation. Basically a common-gate amplifier, at the notch frequency $f = \frac{1}{2\pi} \sqrt{LC}$, the parallel-tuned LC circuit effectively isolates the gate from ground and gain falls steeply at this frequency. L_1 and L_2 , bifilar-wound broadband toroid transformers,

can be replaced by simpler resistive coupling. Attenuation and Q are dependent on choice of fet, LC characteristics and circuit layout. A Q of 30 and stopband attenuation of -76dB were obtained at a cut-off frequency of 30MHz using an MPF102 field-effect transistor.

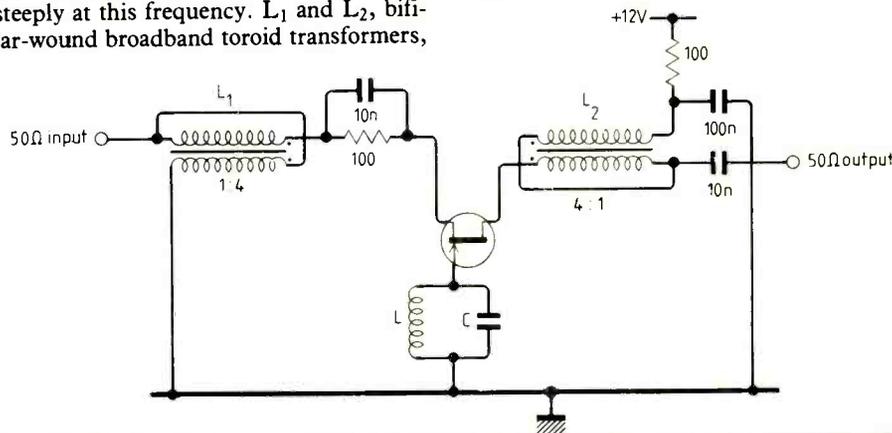A. Achong
University of the West Indies
Trinidad




the remainder are wired in parallel to the inhibit input. Note that push-buttons with separate access to both switch contacts must be used, and not the encoded matrix arrangement used on calculators etc.

The circuit could be extended for

greater security by adding further push-buttons across the inhibit input, or by adding another quad nor-gate for up to four more keys in the code chain.

A. F. Abbey
Stoney Stanton, Leics

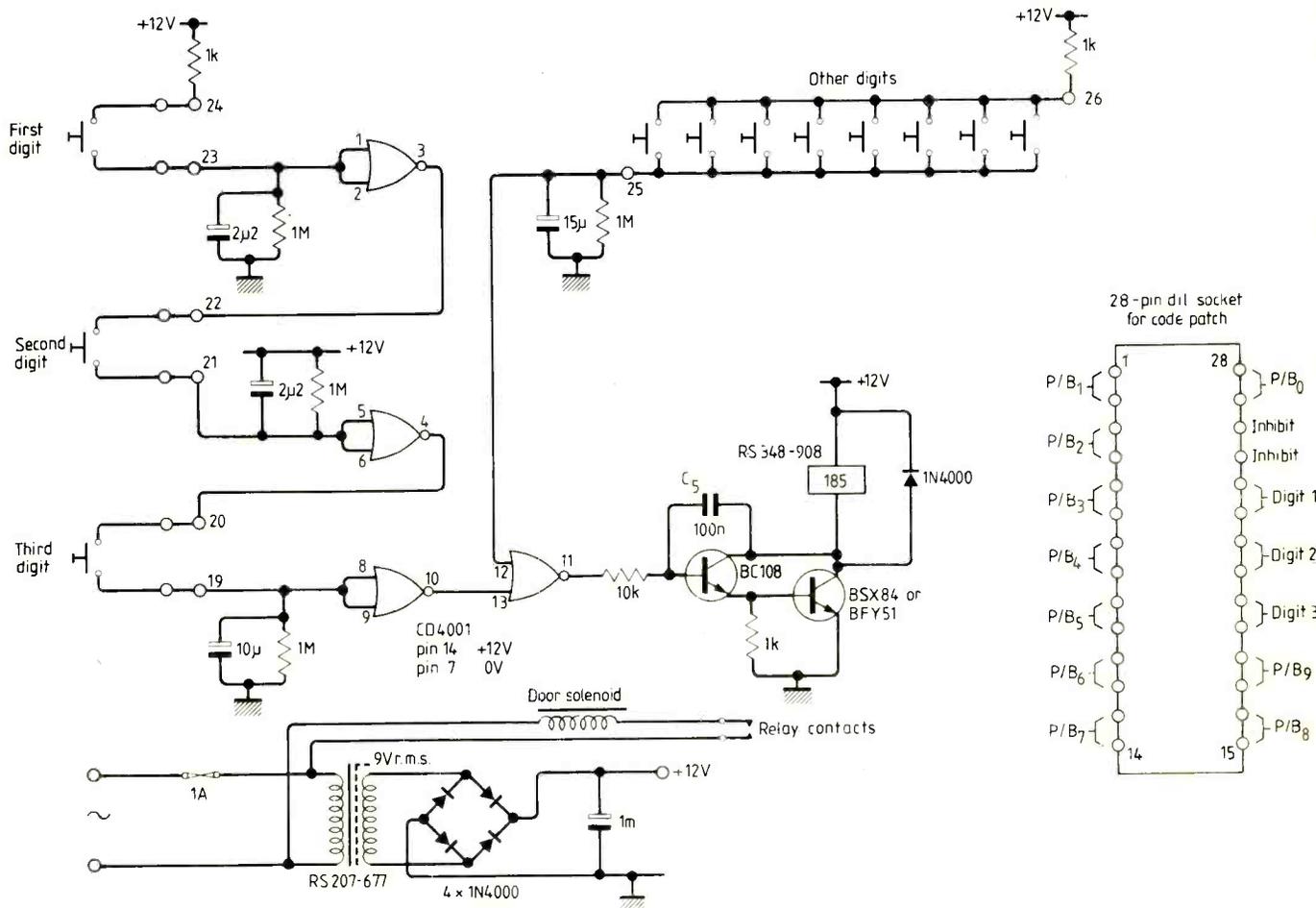

opto-couplers, data transmission being indicated by an led.


The prototype was connected to the outside world using four connectors - a 44 pin edge connector for address, data and control signals, a 16pin dill socket connected to the decoder, a 26 pin flat-cable connector carrying status signals and a 10pin connector for RS232/20mA signals. Automatic power-on reset is included, i.e. the program always starts from the beginning when the computer is switched on.

Software was developed on a PDP11/40 minicomputer and translation to machine code carried out by a MAC80 cross assembler. In my application ram is loaded from the host computer using a 'front panel' system. Loading is done in direct memory access mode after defining the memory region and the file name of the program to run in real time on the target microprocessor. The front panel has tracing and breakpoint capabilities to help debugging of the program.

Data-conversion application

This software and interface developed for the general-purpose microcomputer board were used to convert four-bit hexadecimal telephone traffic-control data into 300 baud RS232 serial data for sending to a remote terminal in ASCII or binary.

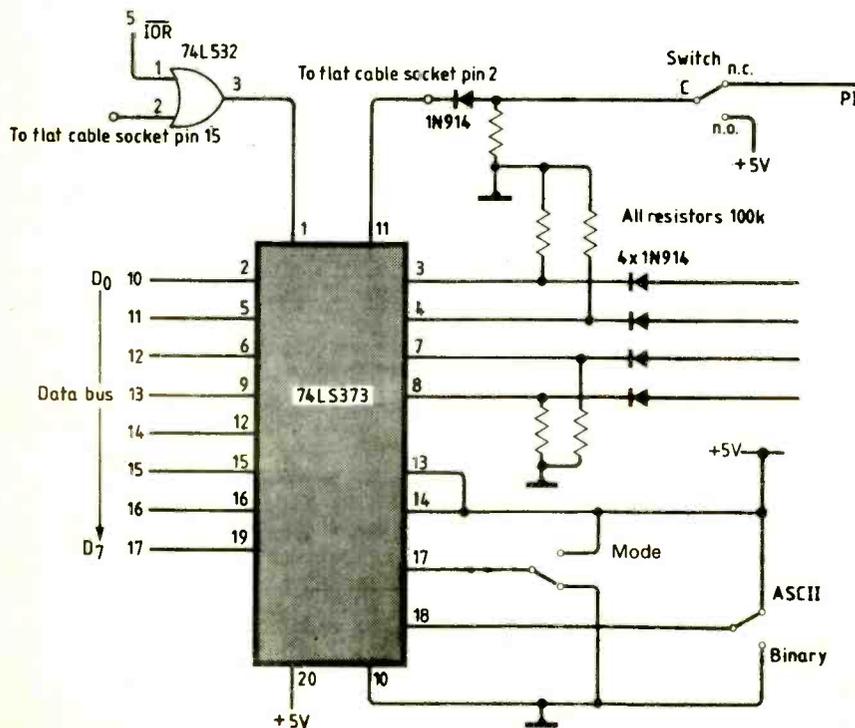Inputs to the conversion interface are four bits representing a hexadecimal word, punch-instruction select signal, ASCII/binary select and a signal representing operating mode, set using the unmarked switch.



```

LXI 24000,SP
JMP INIT
;BLK 66 ;Blank til address 74 oct.
INTR: JMP MSG ;Restart 7.5 address
INIT: MVI 77,A ;Set time for 300x16 baud
      OUT 43
      MVI 40,A
      OUT 40
      MVI 3,A
      OUT 40
      MVI 372,A ;Set uart for even parity
      OUT 1
      MVI 41,A
      OUT 1
      MVI 13,A ;Enable restart 7.5 only
      .BYTE 60
      EI ;Enable interrupt
      LXI HEADER,H ;Print header
      CALL TTYO
      JMP CRLF
EDM: DER E ;Print CR and LF
     MOV E,A ;LF & CR every 80 char.
     JZ CRLF
     MVI 113,A ;SOD low (ready signal)
     .BYTE 60
     HLT ;HALT: wait for interrupt
     JMP FOM
MSG: IN 1 ;Ready to transmit?
     ANI 001
     JZ MSG
     MVI 313,A ;SOD high (not ready)
     .BYTE 60
     IN 100 ;Input status
     RAL ;Rotate = 0 to check carry (switch pos.)
     JNC BINAR ;Jump according to switch position
ASCII: IN 100 ;Input parallel word
      ANI 17 ;and transmit serial ASCII
      ADI 60
      OUT 0
      EI
      RET
BINAR: IN 100 ;Input parallel word
      ANI 17 ;and transmit serial binary
      OUT 0
      EI
      RET
CRLF: IN 1 ;Print CR and LF
      ANI 001
      JZ CRLF
      MVI 12,A
      OUT 0
S2: IN 1
     ANI 001
     JZ S2
     MVI 15,A
     OUT 0
     MVI 80,,E
     JMP EDM
HEADER: .BYTE 12,15 ;Header transmit subroutine
        .ASC /TRAFFIC MEASUREMENT DEVICE/
        .BYTE 12,15
        .ASC /TELECOMMUNICATION RESEARCH CENTER/
        .BYTE 12,15
        .ASC /*****
        .BYTE 12,15,0
TTYO: IN 1
      ANI 001
      JZ TTYO
      MOV M,A
      OUT 0
      INX H
      ANA A
      RZ
      JMP TTYO
.END

```

EVENTS

Continued from page 59

September 16-17

Television tomorrow - costs and quality. Royal Television Society Convention, Kings College, Cambridge. RTVS Tel: 01-387 1970.

September 17-25

The great home entertainment spectacular: home entertainment electronic show. Olympia, London, Montbuild, Tel: 01-486 1951.

September 20-22

Sensors and their applications: European conference and exhibition at University of Manchester Institutes of Science and Technology. Organised by the Institute of Physics, Tel: 01-235 6111

September 26- 28

International electrical, electronics conference and exposition; Automotive Building, Exhibition Park, Toronto, Canada. Sponsored by the Canadian Region of the IEEE, 1450 Don Mills Road, Don Mills, Ontario M3B 2X7, Canada.


NEW PRODUCTS

BRITISH PRINTER FOR SCHOOLS AND SHIPS


Walters WM200 dot-matrix printer incorporates many of the features that make printers emanating from the Far East attractive. It has 9 by 9 dot-matrix printer head that prints in either direction at a speed of 120 characters/s. Four character sizes are available and much thought has been put into the design of the typeface which is very clear and legible. Sprocket-fed paper can be up to 254mm wide. The printer is provided with a Centronics, RS232 or IEEE488 interface and may be easily converted from one to another by changing a slot-in p.c.b. a 750-character internal buffer is supplied which may be expanded to 1800 characters. The printer's development was partly funded by the Department of Industry's Microprocessor Applications scheme and has been selected for use in schools as part of the extension to the 'micros in schools' project, and by the Ministry of Defence. £395 from Walters Microsystems International Ltd, Cetec House, Lincoln Road, Cressle Industrial Estate, High Wycombe, Bucks HP12 3QU. WW 301

FAST-RISE PULSE GENERATOR

Rise and fall times of 150ps are provided in Avtech pulse generators. AVMR-1 has a pulse width variable between 10 and 200ns and a repeat frequency of 5MHz which may be increased to 10MHz with a rise time of 1ns. AMVR-2 is similar but provides high pulse amplitude to 20V with 300ps rise time at 5MHz or 3ns at 10MHz. Both models are available as a bench instrument with internal clock, a line-powered instrument with external trigger or a compact module requiring 24V direct power and an external trigger. Prices start

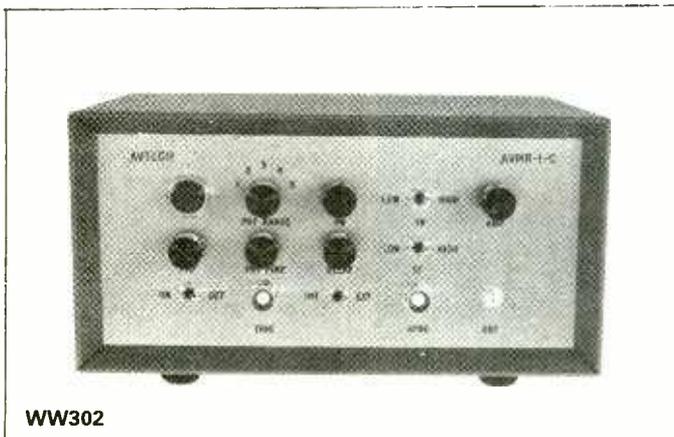

WW302

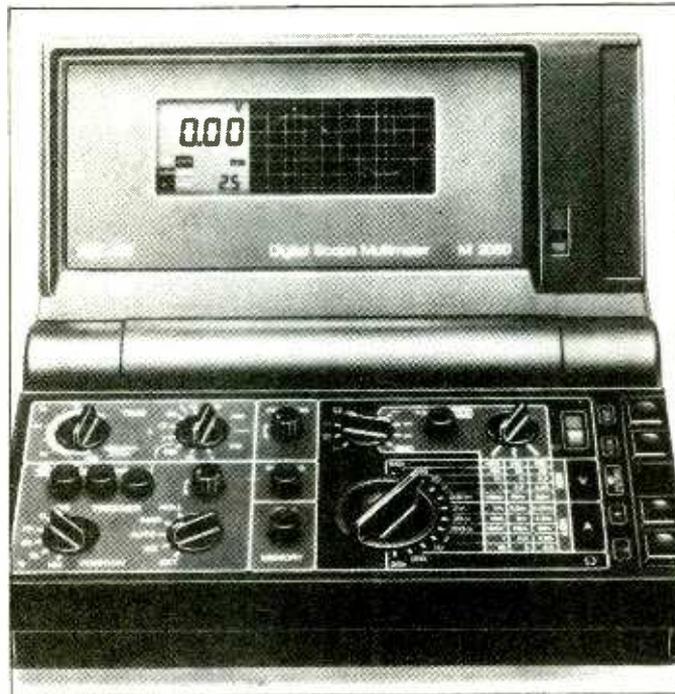


WW305

at £700. Lyons Instruments, Hoddesdon, Herts. WW 302

MAGNETIC HYSTERESIS MEASURED

A B-H meter which can be used directly to check the quality of magnetic recording tape and discs is the 7500A meter which can be used for process control by manufacturers of magnetic media. The microcomputer-controlled meter may be programmed (though two floppy discs) for a variety of applications. Analogue B and H measurements are digitised, stored, sorted and scaled in order to measure the desired parameter. A 50 or 60Hz magnetizing field is applied to the sample and a graphical plot of the Hysteresis curve is displayed on the c.r.t.

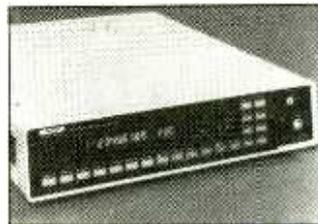

WW304

along with the computed parameters. The curves and data may be stored for later use or printed out on the optional printer-plotter. All fits into a convenient desk-sized unit. LDJ Electronics Inc. Unit 2, The Midlands, Holt, Trowbridge, Wilts BA14 6RU. WW 303

MICRO-CONTROLLED D.V.M.

A digital voltmeter with an 8½-digit readout with a resolution down to 10nV has been announced by Solartron. The heart of the system is a patented pulse-width modulated a-to-d converter. The scale length can be selected to give five or eight significant digits, each with a different integration time. On d.c. ranges the meter is claimed to have an accuracy to within 1.2 p.p.m. over a 24-hour period. The performance has been achieved, say Solartron, by close attention to the ageing of such components as zener diodes and resistors, with compensation circuits to allow for temperature stability of the zeners. True r.m.s. alternating voltages can be measured with six significant figures, resistances from 10μΩ to 1400MΩ. The lowest ohms range has the means of measuring any spurious e.m.f. and then compensating for this to give a 'true

ohms' reading. The control circuitry allows eight different ratio measurements and 17 data processing programs to calculate such parameters as the mean, standard deviation and variance of measurements, or for checking results against pre-defined limits. 1500 results may be stored and used for analysis or display. The meter has IEEE488 and RS232 interfaces and calibration may be carried out through these. The makers see the meter as of use in calibration labs and in automatic test gear as well as general lab and workshop use. The 7081 is from Solartron Instrumentation Group, Victoria Road, Farnborough, Hants GU14 7PW. WW 304

FLAT-SCREEN SCOPE WITH DVM

A combination of the functions of an oscilloscope, a transient recorder and a digital multimeter are all fitted into one portable unit. The 3½-digit multimeter has 32 ranges of current, voltage and resistance measurement. A flat screen liquid crystal display oscilloscope can run for up to eight hours on the internal battery. The transient recorder uses the integrated l.c.d., and there are two independent 0.5K-byte memories. Folding for carriage and storage the instrument is useful in the laboratory, workshop or for the field engineer. The M2050 costs £975 and can be provided with a printout when it would cost £1150. John Minster Instruments Ltd, 137 Sandgate Road, Folkestone, Kent CT20 2DE. WW 305

REMOTE CONTROL

A four-channel infra-red remote control costing £38.50 for both receiver and transmitter is available. The control provides a latched push-on/push-off function which may be used to operate several functions. Power switching relays may be added if required. Maximum operating range is 20m. The receiver preamplifier is fitted into a screened box mounted on to a p.c.b. with the remaining components, and a stabilized power supply which operates from 12 to 14V alternating supplies. Immunity from interference is provided with the use of coded signals. The transmitter uses four power infra-red l.e.d.s with reflectors and is powered by a 9V battery, all fitting into a hand-held case. The Velleman control is available from Electronic and Computer Workshop Ltd, 171 Broomfield Road, Chelmsford, Essex, CM1 1RY. WW 306

MICRO PRODUCTS

16-BIT FORTH

A Forth implementation for the Sage II computer includes an assembler for the 68000 processor which enables machine code languages to be developed through Forth. The versatility of Forth is illustrated by the development of the package; "To write this version of Forth we had to use an assembler that had certain shortcomings," says Tim Moore of Kuma. "We wrote a verbosely coded Forth and then used it to write a real assembler. Using that, we wrote the final version of Forth". Kuma intends to implement the Forth on as many different 68000-based computers as popular demand requires and are willing to undertake 'custom' versions for such applications as industrial robotics. The kernel conforms to FIG-Forth standard, the 68000 assembler uses standard mnemonics, a screen editor is provided and the system is supported by a tutorial manual. Kuma Computers Ltd, 11 York Road, Maidenhead, Berks SL6 1SQ.

WW 307

C-MOS 8086


A world first c-mos 16-bit processor is claimed for the Harris 80C86, a c-mos version of the Intel 8086. The 80C86 is completely compatible with its pattern and has the added advantages of lower power requirements, greater reliability and a wide temperature-operating range. The operating current of 10mA compares with 340mA for the 8086. This means that high speed portable computers may be manufactured with the full facilities of standard computers. The operating frequency of 5MHz is available now for versions with commercial, industrial or military temperature range requirements. 8MHz versions will be introduced toward the end of the year. Harris Systems Ltd, 153 Farnham Road, Slough, Berks SL1 4XD.

WW 308

8085 COMPUTERS USE Z80 SOFTWARE

... if a simple adaptor is used to replace the 8085 microprocessor with an NSC800 and a matching circuit. The plug-in unit fits the 8085 socket and itself has a socket for the NSC800. One drawback is that the serial input and serial output pins of the 8085 may not be used. The adaptor costs £12.90 from F. Braunschmid, Inzerdorferstrasse 119, A-1100 Vienna, Austria.

WW 309

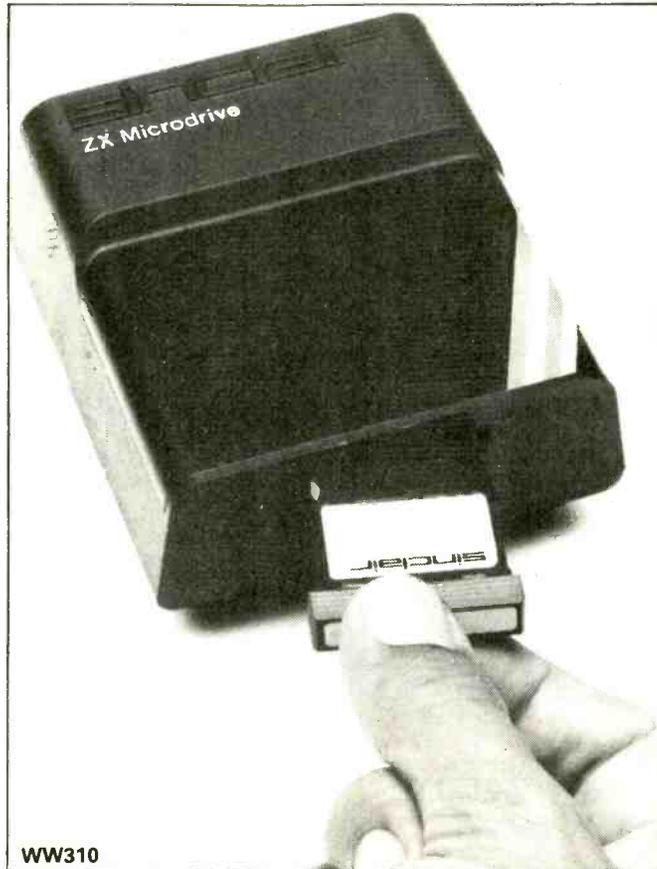

WW310


MICRODRIVE — AT LAST

Announced as 'coming soon' when the Sinclair ZX Spectrum was launched, the ZX Microdrive has just been launched, about a year later. The recording medium turns out to be a continuous loop of tape sealed in a removeable cartridge. Each cartridge can store over 85Kbytes with a typical access time of 3.5s and the Microdrive behaves rather like a miniature floppy disc drive. It interfaces with the computer through ZX Interface 1, which contains the control circuitry for up to eight Microdrives, giving a total storage capacity of 680Kbytes. Interface 1 also provides an RS232 interface so the Spectrum can communicate with other

networked Spectrums, or with other computers or peripherals. Transmission rates are software-selectable up to 19200baud. The local area network can link up to 64 Spectrums; it transmits at 100baud. Each transmitting terminal can select a receiver or broadcast to all open receivers. File exchanges and peripheral (i.e. printer) sharing are allowed for.

The ZX Microdrive costs £49.95, Interface 1 is £29.95 if bought with Microdrive or £49.95 on its own. Each cartridge costs £4.95. There is unlikely to be any available in the shops for a while; they are being offered, mail order, to the owners of ZX Spectrums in the order in which they were purchased. Sinclair Research Ltd, 25 Willis Road, Cambridge CB1 2AQ.

WW 310

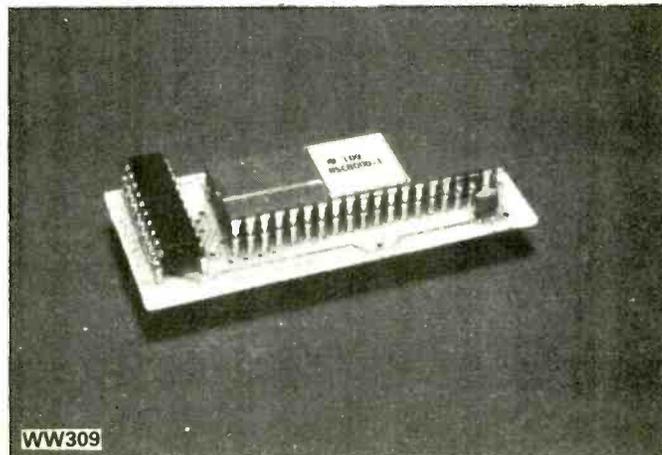


WW309

HIS MAESTRO'S VOICE

The speech synthesiser chip used in the BL Maestro car is now available to design engineers as an evaluation and support package. The Europcard Speechpak board is based on the Hitachi HD61885 speech synthesiser and includes an audio amplifier. Words and phrases can be input through a keyboard, or through an RS232 data link. It costs £180. There is also a software development service available and the distributors can provide production-quantity boards with the on-board rom mask-programmed to any requirement. Dialogue Distribution Ltd, Watchmoor Road, Camberley, Surrey GU15 3AQ.

WW 311

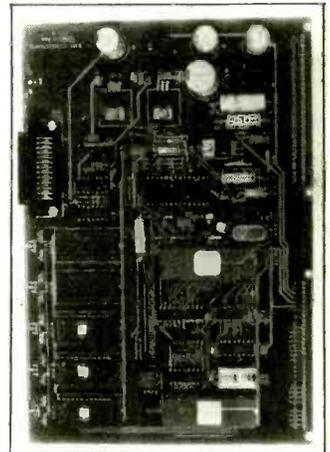

WW311


FAST FORTH FOR Z80

A CP/M disc version of Forth for the Z80 processor claims to be the only version which can compile high-level threaded code definitions into machine code primitives. This gives a two- to five-fold increase in speed according to the Quanta Corporation, who developed Q4TH. The standard Forth-79 set is implemented along with an interpreter, screen editor, assembler (using Zilog mnemonics) and the machine code compiler. The system is available in a number of disc formats and is supported by an update and newsletter scheme. A package of various utilities is included. Quanta Corporation, 2510 Sunset Boulevard, Los Angeles, California 90026, USA.

WW 312

If you would like more information on any of the items featured here, enter the appropriate WW reference number(s) on the mauve reply-paid card bound in this issue. Overseas cards require a stamp.

Testing..Testing..Testing anywhere!

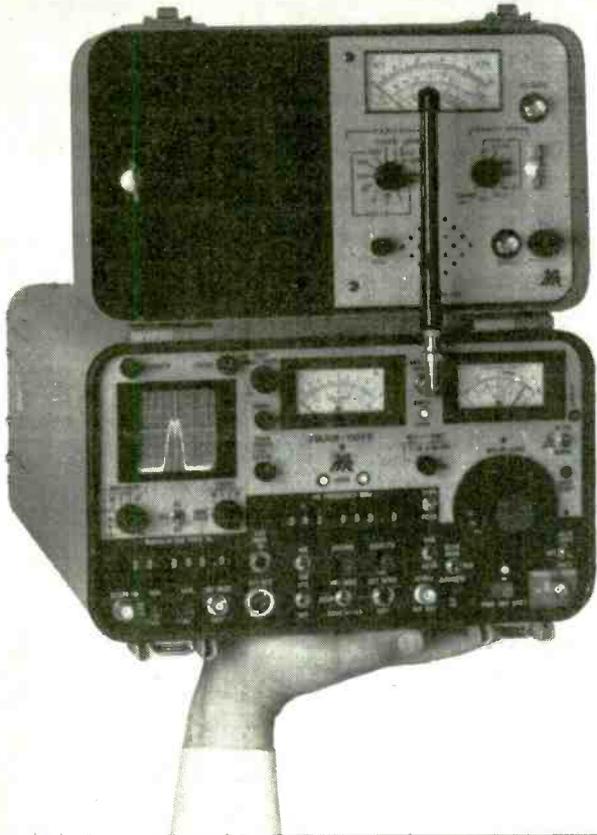

**FM/AM 1100S
with Spectrum Analyser.**
The most sophisticated portable
Communications Service Monitor
from IFR, with an unrivalled
versatility of integrated functions.

For a practical demonstration to prove our point contact:
Mike Dawson on 01-897 6446.



**Fieldtech
Heathrow**

Fieldtech Heathrow Limited
Huntavia House 420 Bath Road
Longford Middlesex UB7 0LL
Telex: 23734 FLDTEC G


WW - 016 FOR FURTHER DETAILS

Hitachi Oscilloscopes

performance, reliability, value

New Models!

immediate delivery!

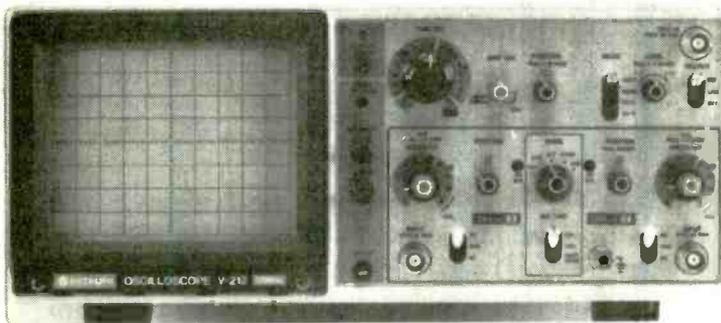

New from Hitachi are three low-cost bench 'scopes with bigger screens and extra features in a new slimline ultra-lightweight format. The range now extends to 13 models:—

- 4 dual trace single timebase models 20MHz to 40MHz
- 2 dual trace sweep delay models 20MHz and 35MHz
- 2 dual timebase multi-trace models 60MHz and 100MHz
- 2 miniature field portable models, 20MHz and 50MHz
- 3 storage models, one tube storage, two digital storage

Prices start at £295 plus vat (model illustrated) including 2 probes and a 2-year warranty. We hold the range in stock for immediate delivery.

For colour brochure giving specifications and prices ring (0480) 63570.

Reltech Instruments, 46 High Street, Solihull, W. Midlands, B91 3TB

WW - 055 FOR FURTHER DETAILS

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner
Telephone 445 2713/0749

WW - 027 FOR FURTHER DETAILS

10 OUTLET DISTRIBUTION AMPLIFIER 3



A compact mains-powered unit with one balanced input and ten a.c. and d.c. isolated floating line outputs.

- ★ Exemplary R.F. breakthrough specifications giving trouble-free operation in close proximity to radio telephones and links
- ★ Excellent figures for noise, THD, static and dynamic IMD
- ★ Any desired number of outlets may be provided at microphone level to suit certain video and audio recorders used at press conferences
- ★ Meets IEC65-2, BS415 safety and I.B.A. 'signal path' requirements

Also available as a kit of parts less the case and all XLR connectors for one or ten outlets.
Broadcast Monitor Receiver 150kHz-30MHz ★ Stereo Disc Amplifier 3 and 4 ★ Moving Coil Preamplifier ★ Illuminated PPM Boxes ★ PPM Drive Boards and Ernest Turner Movements ★ Stabilizer and Frequency Shifter Boards ★ Peak Deviation Meter ★ Programme and Deviation Chart Recorders ★ PPM5 20 pin DIL hybrid ★ Stereo Microphone Amplifier.

SURREY ELECTRONICS LIMITED
The Forge, Luck's Green
Cranleigh, Surrey GU6 7BG
Tel: 0483 275997

TEST EQUIPMENT

10cm Variable Airlines	£25
20cm Variable Airlines	£35
Electrohome 15" B&W X-Y Monitors - NEW (details available)	£25
Philips PM3244 4 Channel 50MHz Sweep Delay Scope	£895
Teleguipump D54 Dual Channel 10MHz Scope	£150
Tek. 465B 100MHz Scope with DM44 Option - complete with all probes, temp. probe, manuals and pouch - as new	£1800
Tek. Type 113 Delay Cable	£50
Tek. 7L18 Spectrum Analyser Plug-in 1.5 to 60GHz - as new	£7250
Tek. 2213 60MHz Scope - as new	£725
Tek. 7313 25MHz Storage Scope Mainframe	£995
Philips 2522A 4 1/2 digit DMM	£146
Fuke 8000A 3 1/2 digit DMM	£86
Fuke 8030A Battery/Meins 3 1/2 digit DMM	£95
Fuke 8600A 4 1/2 digit DMM	£155
Systrom Donner 6250A 8 digit Timer Counter BCD output	£135
Hewlett Packard 6920B Meter Calibrator, DC, AC, V & I	£195
Telonic 1205A Sweep Generator DC to 1500MHz Fitted with all usual TV servicing frequency markers	£695
Sinclair X81 Computer with 64K Memopak	£195
Telonic Type 12112" Display Unit	£195
Philips PM5508 TV Colour Bar servicing generator	£85
Racal 9514 100MHz Timer Counter with IEEE interface	£50
H.P. 7100B 2 pen chart recorder with 17500A & 17505A P.I.	£395
Avometers Model 8 Mk. 5 - as new	£85
Avometers Model 8 Mk. 3	£80
Avometers Model 7 Mk. 2	£85
Racal 9514 100MHz Timer Counter with IEEE interface	£395
Leader LB0510 4MHz single channel Scope - NEW	£95
Marconi TF144H Signal Generator 20KHz to 72 MHz	£195
Marconi TF2410 8 digit 120MHz Counter with 100 MHz Video Amp, 600MHz Converter and 3.4 GHz Converter P.I. units	£195
Tek. Type M4 Channel Plug-in	£80
Tek. Type CA, Z, P Plug-ins	£25
Tek. 564 10MHz Storage Scope with 3B3 & 2B67 Plug-ins	£200
Tek. 564B 10MHz Storage Scope with 3B3 and 2B67 Plug-ins	£225
Hewlett Packard 140 Scope complete	£395
Teleguipump D83 large screen 50MHz delayed sweep scope	£40
Tek. 3A7 Differential Plug-in	£35
Tek. 3A3, 3B3 and 2B67 Plug-ins	£35
Rhode & Schwarz Inductance Meter Type LRT 0.1µH-1H	£195
Tek. Type 184 Time Mark Generators (Lge. Qty. Available)	£125
Tek. Type 191 Constant Amplitude Generators (L.Q.A.)	£115
Tek. Type 106 Fast Rise Pulse Generators (L.Q.A.)	£95
Tek. Type 2901 Pulse Generators (Quantity available)	£295
Tek. Standard Amplitude Calibrators (L.Q.A.)	£195
Singer Synchro Resolver Test Set	£695
Hedin Furnace - 20" to 150"	£295
H.P. 184C 50MHz Storage Scope + 1825A & 1801A P.I.	£795
Tek. 2215 60MHz Scope - as new	£795
Fenn 0-90dBs X Band Variable Attenuators - unused	£175
Solelect Super 50 Multimeter	£45
R & S DPU 0-110dB 50 ohm Variable Attenuators 1.5GHz	£45
Houston DP10 Incremental Plotters	£175
Tek. 661 Sampling Scope with 5T3 & 451 Plug-ins	£185
Bendix Digitiser Complete with 3' x 4' Table	£250
DRI Series 30 2.5 MegaByte Disk Drives	£100
Full Size Draughtsman Table - Nesit	£125
Leader LFR-5600 Frequency Response Recorder	£595

Carriage additional. All prices exc. V.A.T.

TIMEBASE

94 ALFRISTON GARDENS, SHOLING, SOUTHAMPTON SO2 8FU
TELEPHONE: 431323 (0703)


Callers welcome

Access/Barclaycard: Telephone your order

WW - 058 FOR FURTHER DETAILS

PRECISION DUAL AXIS CONTROL STICK

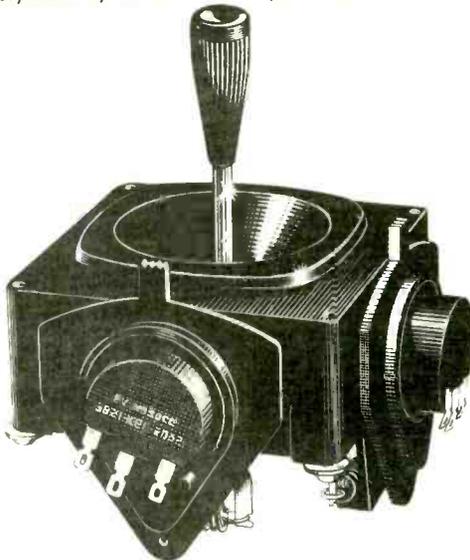Suitable for use with Computers, Robotics, Machine Tools
Widely used by Government departments and industry



SUPER SMOOTH PRECISE ACTION - SEPARATE FINE TRIM ADJUSTMENT - ACCURATE CENTRING - LONG-LIFE MOULDED NYLON PARTS

Available in kit form - easily assembled. Standard version - Carbon track pots. 1 off £8.50, P&P 75p. De luxe version - Conductive plastic film pots. 1 off £12.80, P&P 75p. Send SAE for full details of sticks and servos suitable for Robotics. OEM and trade enquiries invited, Barclaycard and Access accepted.

SKYLEADER, DEPT 9, AIRPORT HOUSE, PURLEY WAY CROYDON, SURREY CRO OXZ. 01-686 6688

WW - 057 FOR FURTHER DETAILS



PM COMPONENTS LTD

VALVE & COMPONENTS SPECIALISTS

INTEGRATED CIRCUITS

AN124 2.50	MC1495 3.00	SN76660N 0.80	TBA560C 1.45	TDA2522 1.95
AN214Q 2.50	MC1496 1.25	SN76668N 0.70	TBA5600 1.45	TDA2523 1.95
AN240P 2.80	MC14011BCP 0.32	TA7061AP 3.95	TBA570 1.00	TDA2524 1.95
AN612 2.15		TA7108P 1.00	TBA641A12 2.50	TDA2530 1.95
AN7150 2.95	MC145106P 7.95	TA7120P 1.85		TDA2532 1.95
BA521 3.35	MC1723 0.50	TA7130P 1.50	TBA641B1X1 1.50	TD2541 2.15
CA3123E 1.35	MC3357 2.25	TA7176AP 3.95	TBA651 1.75	TDA2560 2.18
ET76016 2.50	ML231B 1.75	TA7203 2.95	TBA720A 2.45	TDA2571 1.95
HA1156W 2.50	ML232B 2.50	TA7204P 2.15	TBA750Q 2.65	TDA2581 2.25
HA1366W 1.95	ML237B 1.95	TA7205AP 1.50	TBA800 0.85	TDA2590 2.95
LA1230 1.15	ML238B 4.20	TA7222AP 1.80	TBA810AS 1.35	TDA2591 2.95
LA4031P 2.70	ML920 4.12	TA7227P 4.25	TBA890Q 1.48	TD2593 2.95
LA4102 2.95	MSM5807 6.75	TA7310P 1.80	TBA920 2.50	TDA2600 3.80
LA4400 4.15	PLL02A 5.75	TA7313AP 2.95	TBA920 1.65	TDA2610 2.50
LA4422 2.50	SAA1025 2.75	TA7321P 2.25	TBA920Q 1.85	TDA2611A 1.95
LC7120 3.25	SAA5000A 3.05	TA7611AP 2.95	TBA950/2K 2.35	TDA2640 2.60
LC7130 3.50	SAA5010 6.35	TA7612P 1.80	TBA990 1.49	TDA2690 1.35
LC7131 5.50	TA6561B 1.20	TA7613P 1.80	TBA990Q 1.48	TD2698 2.95
LC7137 5.50	TA700 1.70	TA7614P 2.25	TBA1441 2.15	TDA2699 1.95
LM56CH 0.95	TAAG605 3.50	TA7615P 2.25	TBA120B 0.95	TDA2710 2.95
LM324N 0.45	TBA120B 0.95	TA7616P 2.25	TBA1205A 0.70	UPC1025H 2.50
LM380N 0.95	TBA1205A 0.70	TA7617P 2.25	TCA830S 1.40	UPC1028H 1.95
LM383T 2.95	TBA1205Q 0.70	TA7618P 2.25	TCA90 0.85	UPC1156H 2.75
LM390N 1.95	SL1310 1.80	TA7619P 2.25	TCA90 0.70	UPC1167C 1.15
M51513L 2.30	SL1327Q 1.10	TA7620P 2.25	TDA120T 1.05	
M51515L 2.95	SN76003N 1.95	TA7621P 2.25	TDA120U 1.00	
M5152L 1.50	SN76013N 1.95	TA7622P 2.25	TBA231 1.25	
MB3712 2.00	SN76023N 1.65	TA7623P 2.25	TBA395 1.50	
MC1307P 1.00	SN76033N 1.65	TA7624P 2.25	TBA396 0.75	
MC1327 0.95	SN76110N 0.89	TA7625P 2.25	TBA480Q 1.25	
MC1327Q 0.95	SN76131N 1.30	TA7626P 2.25	TBA510 2.50	
MC1330P 0.76	SN7626DN 1.55	TA7627P 2.25	TBA510Q 2.50	
MC1349P 1.20	SN76227N 1.05	TA7628P 2.25	TBA520 1.10	
MC1350P 0.95	SN76533N 1.65	TA7629P 2.25	TBA520Q 1.10	
MC1351P 1.50	SN76544N 1.65	TA7630P 2.25	TBA530 1.10	
MC1352P 1.25	SN76650N 1.15	TA7631P 2.25	TBA530Q 1.10	
MC1357 2.35		TA7632P 2.25	TBA540 1.25	
MC1358 1.58		TA7633P 2.25	TBA540Q 1.35	
		TA7634P 2.25	TBA550Q 1.45	

SEMICONDUCTORS

AAY12 0.25	BC173B 0.10	BD159 0.65	BF355 0.37	OC81 0.50
AC126 0.22	BC174 0.09	BD166 0.55	BF362 0.38	R2008B 1.70
AC127 0.20	BC174A 0.09	BD179 0.72	BF363 0.38	R2101B 1.70
AC128 0.20	BC177 0.15	BD201 0.83	BF371 0.20	R2322 0.58
AC128K 0.20	BC178 0.15	BD202 0.65	BF394 0.19	R2323 0.66
AC141 0.28	BC182 0.10	BD203 0.78	BF457 0.32	RCA16334 0.90
AC141K 0.34	BC182LB 0.10	BD204 0.70	BF458 0.28	RC1A6335 0.80
AC142K 0.30	BC183 0.10	BD222 0.48	BF459 0.36	SK5E5 1.45
AC176 0.22	BC183L 0.09	BD223 0.48	BF595 0.23	TIP29 0.40
AC176K 0.31	BC204 0.10	BD225 0.48	BF597 0.25	TIP29C 0.42
AC181 0.25	BC204 0.10	BD232N 2.65	BF599 0.23	TIP30C 0.43
AC187K 0.28	BC207B 0.13	BD233 0.35	BF640 0.23	TIP31C 0.42
AC188 0.25	BC208B 0.13	BD234 0.35	BF641 0.28	TIP32C 0.42
AC188K 0.37	BC212 0.09	BD236 0.45	BF681 0.25	TIP33B 0.75
AD142 0.79	BC212L 0.09	BD237 0.40	BF688 0.30	TIP34B 0.76
AD143 0.82	BC212A 0.09	BD238 0.40	BF690 1.50	TIP41A 0.45
AD149 0.70	BC213 0.09	BD241 0.40	BF691 1.75	TIP41C 0.45
AD161 0.39	BC213L 0.09	BD242 0.50	BF742 0.28	TIP42C 0.47
AD162 0.39	BC214 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
AD161/2 0.30	BC214C 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
AF115 0.75	BC214L 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
AF124 0.34	BC217 0.10	BD246 0.60	BF743 0.28	TIP47 0.85
AF125 0.35	BC237A 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
AF126 0.32	BC237B 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
AF127 0.32	BC238 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
AF139 0.40	BC239 0.12	BD246 0.60	BF743 0.28	TIP47 0.85
AF150 0.42	BC251A 0.12	BD246 0.60	BF743 0.28	TIP47 0.85
AF239 0.42	BC252A 0.15	BD246 0.60	BF743 0.28	TIP47 0.85
AU106 2.00	BC258 0.25	BD246 0.60	BF743 0.28	TIP47 0.85
AU107 1.75	BC258A 0.39	BD246 0.60	BF743 0.28	TIP47 0.85
AU110 2.00	BC284 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
AU113 2.95	BC300 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
BC107A 0.11	BC301 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
BC107B 0.11	BC303 0.26	BD246 0.60	BF743 0.28	TIP47 0.85
BC108 0.10	BC307 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
BC108A 0.11	BC307A 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
BC108B 0.12	BC307B 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
BC109 0.10	BC327 0.10	BD246 0.60	BF743 0.28	TIP47 0.85
BC109B 0.12	BC328 0.10	BD246 0.60	BF743 0.28	TIP47 0.85
BC109C 0.12	BC337 0.10	BD246 0.60	BF743 0.28	TIP47 0.85
BC114 0.11	BC338 0.09	BD246 0.60	BF743 0.28	TIP47 0.85
BC116A 0.15	BC347A 0.13	BD246 0.60	BF743 0.28	TIP47 0.85
BC117 0.19	BC461 0.35	BD246 0.60	BF743 0.28	TIP47 0.85
BC119 0.24	BC478 0.20	BD246 0.60	BF743 0.28	TIP47 0.85
BC120 0.25	BC527 0.20	BD246 0.60	BF743 0.28	TIP47 0.85
BC139 0.20	BC547 0.10	BD246 0.60	BF743 0.28	TIP47 0.85
BC140 0.31	BC548 0.10	BD246 0.60	BF743 0.28	TIP47 0.85
BC141 0.25	BC549A 0.08	BD246 0.60	BF743 0.28	TIP47 0.85
BC142 0.21	BC550 0.08	BD246 0.60	BF743 0.28	TIP47 0.85
BC143 0.24	BC557 0.08	BD246 0.60	BF743 0.28	TIP47 0.85
BC147 0.08	BC557A 0.08	BD246 0.60	BF743 0.28	TIP47 0.85
BC147B 0.08	BC557B 0.08	BD246 0.60	BF743 0.28	TIP47 0.85
BC148A 0.09	BC558 0.10	BD246 0.60	BF743 0.28	TIP47 0.85
BC148B 0.09	BCY33A 1.60	BD246 0.60	BF743 0.28	TIP47 0.85
BC149 0.09	BD115 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
BC157 0.12	BD116 0.60	BD246 0.60	BF743 0.28	TIP47 0.85
BC158 0.09	BD124P 0.59	BD246 0.60	BF743 0.28	TIP47 0.85
BC159 0.09	BD131 0.32	BD246 0.60	BF743 0.28	TIP47 0.85
BC160 0.28	BD132 0.35	BD246 0.60	BF743 0.28	TIP47 0.85
BC161 0.28	BD133 0.40	BD246 0.60	BF743 0.28	TIP47 0.85
BC170B 0.15	BD135 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
BC171 0.09	BD136 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
BC171A 0.10	BD137 0.32	BD246 0.60	BF743 0.28	TIP47 0.85
BC171B 0.10	BD138 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
BC172 0.10	BD139 0.32	BD246 0.60	BF743 0.28	TIP47 0.85
BC172B 0.10	BD140 0.30	BD246 0.60	BF743 0.28	TIP47 0.85
BC172C 0.10	BD144 1.10	BD246 0.60	BF743 0.28	TIP47 0.85

DIODES

AA119 0.08	BY199 0.40	IN4004 0.05
BA102 0.17	BY206 0.14	IN4005 0.05
BA115 0.13	BY208-800 0.33	IN4006 0.06
BA145 0.16	BY210	

PHONE
0474 813225
3 LINES

P. M. COMPONENTS LTD
SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
966371
PM COMP



A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 11.50	EAA91 0.60	EF731 1.80	HK90 1.05	PCL85 0.80	RG3-1250A 1.00	VR37 1.50	3A2 3.95	68X6 0.48	10D2 1.25	95A1 6.50
A1998 18.50	EABC80 0.68	EF732 1.80	HL23DD 3.50	PCL200 0.80	RG2K25 62.50	VR75/30 3.00	3A3A 3.95	68X7GT 3.50	10G1 0.75	108C1 1.50
A2087 11.50	EAC31 2.50	EF800 11.00	HL41 3.50	PCL800 0.80	RG4-1000 10.00	VR101 2.00	3AL5 0.95	68Z7 2.95	10G6 1.95	15082 3.95
A2134 14.95	EAF42 1.20	EF804S 11.00	HL41DD 3.50	PCL805 0.80		VR105/30 1.50	3AT2 3.35	68Z8 0.95	10G14 2.50	150C2 1.50
A2293 6.50	EAF801 1.40	EF815S 13.50	HL42DD 3.50	PD500 3.50		VR150/30 1.05	3AW2 3.35	6C4 0.80	10G18 0.78	150C4 2.15
A2521 21.00	EB34 1.50	EF806S 14.50	HL90 0.70	PD510 3.65	RLK-20A 12.00	V152 2.50	3B2 3.00	6C5 1.95	10G11 1.00	155UG 25.00
A2599 37.50	EB41 3.00	EF812 0.65	HL92 3.00	PL21 2.50	RL16 1.50	V152 2.50	3B2 3.00	6C6 1.95	10G12 0.65	185BT 1.50
A2900 11.50	EB91 0.52	EF1200 1.50	HL93 0.70	PL21 2.50	RPL16 12.00	VU39 1.50	3B7 4.50	6C8 0.50	11E2 16.50	205F 12.00
A3042 24.00	EB93 0.75	EH90 0.72	HL93/33DD 3.50	PL21 2.50	RS695 54.95	VX6120 5.00	3B8 1.50	6C9 1.50	11E3 55.00	257A 6.00
A3283 24.00	EB94 0.75	EK90 0.72	HR2 4.00	PL33 1.25	RS698 52.15	VX9133 5.00	3B8 1.50	6C11 2.50	12A2E6 0.85	307F 5.00
AC/HL/DD 4.00	EB95 0.75	EL33 4.00	HY90 1.00	PL36 0.95	RPY23 2.50	VX9181 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	329 5.00
ACP 4.00	EB96 0.75	EL34 2.25	HVR2 3.00	PL36 0.95	RPY25 3.00	VX9181 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	388A 17.50
AC/THI 4.00	EB97 0.75	EL34 Philips 3.15	K3118 85.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	425A5 8.00
ACT22 59.75	EBF33 2.50	EL36 3.15	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
AC/VP2 4.00	EBF80 0.50	EL37 9.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
AC/52 PEN3.50	EBF83 0.50	EL38 6.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
AH221 39.00	EBF85 0.95	EL38 6.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
AH238 39.00	EBF86 0.70	EL38 6.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
AL60 6.00	EBF93 0.95	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
ARP12 4.70	EBL1 2.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
ARP34 1.25	EBL21 2.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
ARP35 2.00	EC52 0.75	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
AR23 2.00	EC70 0.75	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
BS450 67.00	EC80 4.25	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
CIK 16.00	EC81 4.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
C3JA 16.00	EC86 1.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
C108 55.00	EC88 1.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
C1134 32.00	EC90 0.70	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
C1148A 115.00	EC91 7.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
C1149/1 130.00	EC92 1.25	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
C1150/1 135.00	EC93 0.80	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
C1534 32.00	EC95 7.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
CBL31 2.00	EC97 1.10	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
CCA 2.60	EC8010 6.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
CC3L 0.90	EC832 3.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
CL33 2.00	EC89 1.25	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
CMG25 9.00	EC835 3.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
CV Nos Prices on request	EC840 3.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
D63 1.20	EC881 0.95	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DAF91 0.45	EC882 0.55	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DAF96 0.65	EC883 Philips 1.10	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DC70 1.75	EC883 0.65	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DC90 1.20	EC883 Mullard 1.35	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DCX4-1000 26.00	EC883 Philips 1.10	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DCX4-5000 12.00	EC884 1.10	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DET10 6.00	EC885 0.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DET22 28.00	EC886 1.45	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DET24 39.00	EC888 0.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DET25 22.00	EC891 2.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DF91 0.70	EC880 0.72	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DF92 0.60	EC889 0.78	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DF96 0.65	EC890 0.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DH63 1.20	EC803S 3.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DH77 0.90	EC804 0.60	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DH79 0.56	EC807 2.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DH149 2.00	EC82000 12.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DK91 0.90	EC880 0.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DK92 1.20	EC891 0.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DK95 2.50	EC886 1.70	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL35 1.00	EC8200 1.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL63 1.00	EC8205 1.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL70 2.50	EC8801 0.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL73 2.50	EC8804 0.85	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL91 1.50	EC8805 1.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL92 0.80	EC8806 1.25	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL93 1.10	EC83 2.50	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL94 2.50	EC84 3.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL96 2.50	EC835 1.60	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL97 1.00	EC842 1.00	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DL98 10.00	EC843 1.70	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DM70 8.00	EC883 0.78	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C15 2.50	12AG6 1.50	431U 2.00
DM160 2.75	EC884 0.69	EL42 2.00	K3188 7.00	PL36 0.95	RPY25 3.00	W77 5.00	3C4 1.00	6C		

EuroCUBE 6502/6809—EuroBEEB—BEEBEX

The expanding range of CUBE control boards

BBC BASIC
now on
Eurocard

EuroCUBE is just one small 100x160mm Eurocard—but it is a single-board computer of exceptional power and versatility.


- 6809 or 6502 Microprocessors available.
- Four memory sockets, each 28 pin. Supports RAM, ROM, EPROM—from 2KB to 32KB each.
- Battery Back-up for CMOS RAM
- Dual CPU clock mode—2 MHz for memory, 1 MHz for i/o
- VIA provides 20 digital i/o channels.
- ACIA provides a bi-directional RS-232C 423/422 serial port. On-board programmable baud-rate generator.
- PROM address decoding.
- Machine Operating System included free of charge.

EuroBEEB—EuroCUBE with BBC BASIC—The MOS included on EuroCUBE, provides an environment in which languages can be run, and is available in two main versions:

- MOS A — supports ATOM BASIC
- MOS B — supports BBC BASIC

EuroCUBE fitted with MOS B can run BBC BASIC. In its simplest form, with 4KB RAM fitted for work space, a BBC BASIC program in EPROM could control the two 8-bit ports and the serial interface, in addition to any other cards connected to the CUBE expansion bus.

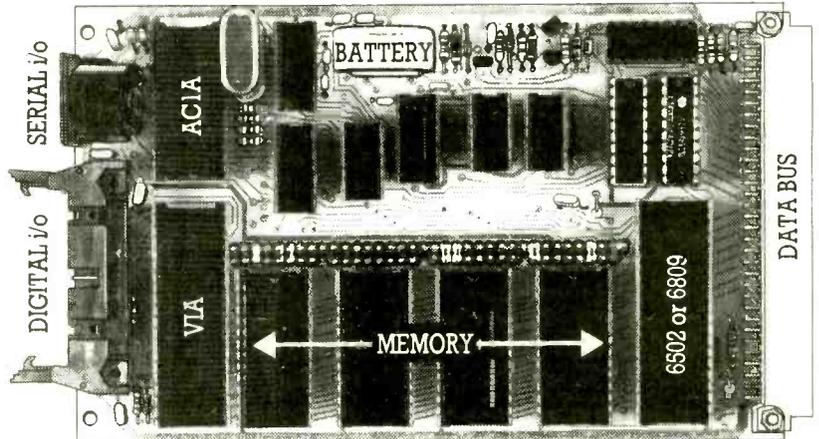BEEBEX, another recent addition to the CUBE range, is a simple, low-cost Eurocard which interfaces to the 1MHz bus connection on the BBC Microcomputer, enabling it to communicate with the entire range of CUBE Acorn Eurocards.



EuroCUBE £139.00

One-off price excluding VAT
No charge for Operating System Software

Control Universal's new 160 page catalogue and technical overview is now available free of charge. Explanatory leaflets are also available on the CUBE range, and on our Eurocard extensions to the BBC Microcomputer.

CUBE RANGE

includes video, analog & digital
i/o, prom programming, disks, etc.



Unit 2, Andersons Court,
Newnham Road, Cambridge CB3 9EZ
Telephone (0223) 358757
Telex 995801-G (C13)

WW - 030 FOR FURTHER DETAILS

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

Accurate Digital Multimeters at Exceptional Prices



7030
1% Accuracy
£35.95

6010
.5% Accuracy
£29.95

6010 & 7030 MODELS SPECIFICATION

- 10 amp AC/DC
- Battery: single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm
- Weight: 400g inc. battery
- Mode Select: Push Button
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 20MΩ
- Input Impedance: 10MΩ
- Display: 3 1/2 Digit 13mm LCD
- O/Load Protection: All ranges



NEW
HM102 BZ
£13.00

ANALOGUE HM102BZ WITH CONTINUITY BUZZER AND BATTERY SCALE

- DC Voltage: 0-25, 1, 25, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500µA, 0-5, 50, 500mA
- Ohmmeter: 0-6 Megohms in 4 ranges.
- 30 ohms Centre Scale.
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.

OTHER features: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road
Wembley, Middlesex HA9 8BH, England
Telephone: 01-902 4321 (3 lines). TELEX No. 923985

Quantity discount for trade on application
Add 15% to your order for V.A.T. P&P is free of charge
Payment by cheque with order



or accepted

WW - 006 FOR FURTHER DETAILS

METAL FILM RESISTORS

100R	1k	10k	100k
110R	1k1	11k	110k
120R	1k2	12k	120k
130R	1k3	13k	130k
150R	1k5	15k	150k
160R	1k6	16k	160k
180R	1k8	18k	180k
200R	2k	20k	200k
220R	2k2	22k	220k
240R	2k4	24k	240k
270R	2k7	27k	270k
300R	3k	30k	
330R	3k3	33k	330k
360R	3k6	36k	
390R	3k9	39k	
430R	4k3	43k	
470R	4k7	47k	470k
510R	5k1	51k	
560R	5k6	56k	560k
620R	6k2	62k	
680R	6k8	68k	680k
750R	7k5	75k	
820R	8k2	82k	820k
910R	9k1	91k	1M

1/4 Watt, 1% tolerance, 3p each. 89 Values, E24, see left. Minimum order £20. Minimum 10 pcs per value. VAT, P&P incl.

SPECIAL OFFER
10 pcs of each value, 890 pcs
£25.30

SPECIAL 'POP' PACK
100 pcs: 100R, 1K, 4K7, 10K, 47K,
100K, 1M. 50 pcs: 330R, 470R, 1K5,
2K2, 3K3, 22K. Total 1000 pcs. £28.50.

One of each
pack £50 only

ORION SCIENTIFIC LTD - 16 Orange Street - London WC2H 7ED

WW - 054 FOR FURTHER DETAILS

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV Tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology.

Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Sealoffs, and all other associated items for TV Tube Production. A Full Technical Back-up and Advisory Service is available to all customers Worldwide.

Please request our current catalogues and Data Information.

**GRIFTRONIC
EMISSION LTD**

2 SWAN STREET
ALCESTER
WARWICKSHIRE
B49 5DP
ENGLAND

Telephone: (0789) 764852/764100. Telex: 312354 Grifem G

WW - 044 FOR FURTHER DETAILS

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

RECORD DECKS SINGLE PLAY

Large Turntables
240 volt AC. Post £2



Make	Model	Drive	Cartridge	Price
BSR	P170	Rim	Ceramic	£20
BSR	P232	Belt	Ceramic	£24
GARRARD	6200	Rim	Ceramic	£22
GARRARD	Delux	Belt	Magnetic	£40

BSR	P232	12 volt	Magnetic	£24
AUTOCHANGERS 240 VOLT				
BSR	Budget	Rim	Ceramic	£16
BSR	Delux	Rim	Ceramic	£18
BSR	Delux	Rim	Magnetic	£26

MAINS PRE-AMP FOR MAGNETIC CARTRIDGES to low gain amplifier 10mv to 1/2 volt, mono £5, stereo £7. P&P £1

HEAVY METAL PLINTHS Post £1
Cut out for most Garrard decks. Black or silver grey finish. Size 16x13 1/4 in. **£4**

DECCA TEAK VENEERED PLINTH Post £1
Superior finish with space and panel for small amplifier. Board is cut for B.S.R. 18 1/4 in. x 14 1/4 in. x 4 in. Black/chrome fascia trim. Also with boards cut out for Garrard £3. Tinted plastic cover £5

TINTED PLASTIC COVERS	Post £1
17 1/8 x 13 1/8 x 3 1/4 in.	£5
17 1/4 x 9 3/8 x 3 1/2 in.	£3
16 1/2 x 15 x 4 1/2 in.	£5
17 x 12 7/8 x 3 1/2 in.	£5
22 5/8 x 13 7/8 x 3 in.	£5
21 1/2 x 14 1/4 x 2 1/2 in.	£5
23 3/4 x 14 x 3 1/8 in.	£5

THE "INSTANT" BULK TAPE ERASER £10.50 Post 95p
Suitable for cassettes and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools and computer tapes.
Tape Head Demagnetiser only £5



BATTERY ELIMINATOR MAINS TO 9 VOLT D.C.
Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5x3 1/4 x 2 1/2 in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models. £5. Post £1.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy build kit. Controls up to 800 watts AC mains with plastic case 4 x 3 x 1 1/2 in. £5, less case £4. For brush motors, power tools, drills and lighting. Post 65p.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £3.95. Post 65p
All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7 1/2 or 9 or 12V d.c. up to 100mA or less. Please state voltage required.

RELAYS. 6V DC 95p. 12V DC £1.25. 18V £1.25. 24V £1.30
ALUMINIUM CHASSIS. 2 1/2 in. deep 6x4—£1.75; 8x6—£2.20; 10x7—£2.75; 12x8—£3.20; 14x9—£3.60; 16x6—£3.16x10—£3.80; 12x3 £2.20; 14x3 £2.50; 13x9 £2.80.

ALUMINIUM PANELS. 6x4—55p; 8x6—90p; 14x3—90p; 10x7—£1.15; 12x8—£1.30; 12x5—90p; 16x6—£1.30; 14x9—£1.75; 12x12—£1.80; 16x10—£2.10.

ALUMINIUM BOXES. 4x4x1 1/2 £1.20. 4x2 1/2x2 £1.20. 3x2x1 £1.20. 6x4x2 £1.90. 7x5x3 £2.90. 8x6x3 £3. 10x7x3 £3.60. 12x5x3 £3.60. 12x8x3 £4.30.

ALI ANGLE BRACKET 6x3 1/4 x 3 1/4 in. 30p.

BRIDGE RECTIFIER 200V PIV 2a £1. 4a £1.50. 6a £2.50.

TOGGLE SWITCHES SP 40p. DPST 50p. DPDT 60p.

MINIATURE TOGGLE SP 40p. DPDT 60p.

RESISTORS. 10Ω to 10M. 1/4W, 1/2W, 1W, 2p; 2W 10p.

Low ohm 1 watt 0.47 to 3.9 ohm 10p.

HIGH STABILITY. 1/2w 2% 10 ohms to 1 meg. 10p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 20p.

PICK-UP CARTRIDGES SONOTONE STAHG £3.80.

BSR Stereo Ceramic SC7 Medium Output £2. SC12 £3.

PHILIPS PLUG-IN HEAD. Stereo Ceramic AG1020 (G306 - GP310-GP233-AG3306. £2. A.D.C. QLM 30/3. MAGNETIC £6.50

STYLUS most Ceramic Accos, Sonotone, BSR, Garrard Philips Diamond £1.50 ea.

MAGNETIC STYLUS, Sony, JVC, Sanyo, Goldring, etc. £4.

LOCK TITE SEALING KIT DECCA 118. Complete £1.

VALVE OUTPUT Transformers push/pull 15 watt £14; 30W £18; 50W £20; 100W £24. Post £2. 100V/Line 20W £3.75.

MICROSWITCH, 50p. Miniature £5p. SPDT.

ANTEX SOLDERING IRON 'C' 15W £5.25. 25W 'X25' £5.50.

WAFER SWITCHES. 1 1/4" dia. 60p ea.

1P 12W; 2P 2W; 2P 6W; 3P 4W; 4P 2W; 4P 3W.

FERRITE ROD. 6" x 1/2", 6" x 3/8", 8x5/16" 50p

XLR Lead Plug £2.40. Lead socket £2.75

XLR Chassis Plug £2.20. Chassis Socket £2.55.

BANANA 4mm Plugs/Sockets, red/black 20p

JACK PLUGS Mono Plastic 25p; Metal 30p. Sockets 25p.

JACK PLUGS Stereo Plastic 30p; Metal 35p. Sockets 30p.

FREE SOCKETS - Cable end 30p. Metal 45p.

2.5mm and 3.5mm JACK SOCKETS 25p. Plugs 25p.

DIN TYPE CONNECTORS

Sockets 3-pin, 5-pin 15p. Free Sockets 3-pin, 5-pin 25p.

Plugs 3-pin 20p; 5-pin 25p; Speaker plugs 25p; Sockets 15p.

PHONO PLUGS AND SOCKETS ea. 20p; Double sockets 30p.

Free Socket for cable end 20p. Screened Phono Plugs 25p.

B.N.C. PLUGS £1. Sockets £1. Free Sockets £1.10.

U.H.F. PLUG 50p. Socket 50p. Reducer 20p. Coupler 50p.

300 ohm TWIN RIBBON FEEDER 10p.

300 ohm to 75 ohm AERIAL MATCHING TRANSFORMER £1.

U.H.F. COAXIAL CABLE SUPER LOW LOSS. 75 ohm 25p.

COAX PLUGS 30p. COAX SOCKETS 20p. Lead Sockets 65p.

NEON INDICATORS 250V, round 40p. Rectangular 45p.

MORSE CODE TAPPER AND BUZZER SET £3.

CAR CASSETTE MECHANISM. 12V Motor Stereo Head £5.

POTENTIOMETERS Carbon Track
5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5k. SP 45p.

MINI-MULTI TESTER NEW
De luxe pocket size precision moving coil instrument. Impedance + Capacity - 4000 o.p.v. Battery included.
11 instant ranges measure:
DC volts 5.25, 250, 500. **£7.50**
AC volts 10, 50, 500, 1000. Post 65p
DC amps 0-250μA, 0-250mA.
Resistance 0 to 600K ohms.

De Luxe Range Doubler Model £19.50
50,000 o.p.v. 7 x 5 x 2 in. Post £1
43 Ranges, 1,000V, AC-DC, 20 meg. etc.

PANEL METERS
50μA, 10CμA, 500μA, 1mA, 5mA, 50mA, 100mA, 500mA, 1 amp, 2 amp, 25 volt, VU
2 1/4 x 2 x 1 1/4. Stereo VU
3 1/4 x 1 1/8 x 1 in. **£4.50** Post 50p

RCS SOUND TO LIGHT CONTROL BOX
Complete ready to use with cabinet size 9x3x5 in. 3 channel, 1000 watt each. For home or disco **£27**
OR KIT OF PARTS £19.50 Post £1
LIGHT BOXES. 20x9x9 in, red, yellow, blue, green, £15' p.p. £2.
Disco bulbs 100 watt, blue, green, yellow, red, amber, screw or bayonet £2 each. Post £1.50 per six.
"FUZZ" lights, red, blue, green, amber, 240V. **£28.** Post £1.
200 Watt Hear Reflecting White Light Bulbs. Ideal for Disco Lights, Edison Screw. 6 for £4, or 12 for £7.50. Post £1.50. Suitable panel mounting holders 85p.

RCS "MINOR" 10 watt AMPLIFIER KIT £14
This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. 10W per channel; size 9 1/2 x 3 1/2 in. SAE details. Full instructions supplied. 240V AC mains. Post £1.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board **£3.50** Post 65p
Can be ganged to make multi-way stereo mixers

MAINS TRANSFORMERS Post
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A **£6.00** £2
350-0-350V 250mA, 6.3V 6A CT **£12.00** £2
220V 25ma 6V 1amp **£3.00** £1
220V 45ma 6V 2 Amp **£4.00** £1
250V 60mA, 6V 2A **£4.75** £1

Step-Up 115V to 240V 150W **£9.** 250V to 110. 500W **£12.00** £2

GENERAL PURPOSE LOW VOLTAGE
Tapped outputs available Price Post
2 amp, 3, 4, 5, 8, 9, 10, 12, 15, 18, 25 and 30V **£8.00** £2
1 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 **£10.50** £2
2 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 **£12.50** £2
3 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 **£16.00** £2
5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 **£21.00** £2
5.8-10-16V 1/2 amp. **£2.50** £1
15-0-15V, 1 amp **£4.00** £1
6V 1/2 amp. **£2.00** £1
6V 1 1/2 amp. **£3.00** £1
9V 400ma **£1.50** £1
9V 3 amp **£4.50** £1
9-0-9V 50ma **£1.50** £1
9-0-9V 1 amp **£3.50** £1
10-0-10V 2 amps **£4.00** £1
10-30-40V 2 amps **£4.50** £1
12V 100ma **£1.50** £1
12V 750 ma **£2.50** £1
12V 3 amps **£4.50** £1
10-12V 2 amps **£4.50** £1

CHARGER TRANS Post
6-12 volt 3a **£4.50** £2
6-12 volt 4a **£6.50** £2

RECTIFIERS Post
6-12 volt 2a **£1.10** + 80p
6-12 volt 4a **£2.00** + 80p

OPUS COMPACT SPEAKERS £22 pair Post £2
TEAK VENEERED CABINET
11x8 1/2 x 7 in, 15 watts
50 to 14,000 cps. 4 ohm, 8 ohm or 16 ohm
OPUS TWO 15 x 10 1/2 x 7 3/4 in 25 watt
2-way system **£39 pair.** Post £3

LOW VOLTAGE ELECTROLYTICS Wire ends All 10p ea.
1 mf, 2 mf, 4 mf, 8 mf, 10 mf, 16 mf, 25 mf, 30 mf, 50 mf, 100 mf, 250 mf. All 15 volts. 22 mf/6V/10v; 25 mf/6V/10v; 47 mf/10V; 50 mf/6V; 68 mf/6V/10V/16V/25V; 100 mf/10V; 150 mf/6V/10V; 200 mf/10V/16V; 220mf/4V/10V/16V; 330 mf/4V/10V; 500 mf/6V; 680 mf/6V/10V; 1000 mf/2.5V/4V/10V; 1500 mf/10V; 2200 mf/6V/10V; 3300 mf/6V; 4700 mf/4V. 500mF 12V 15p; 25V 20p; 50V 30p. 1200mF 76V 80p. 1000mF 12V 20p; 25V 35p; 50V 50p; 100V £1.20. 2000mF 30V 42p; 40V 60p; 100V £1.40; 1500mF 100V £1.20. 2200mF 30V 90p. 2500mF 50V 70p; 3000mF 50V 65p; 4700mF 30V 75p; 40V £1; 63V £1.80.

NON POLARISED CAPACITORS - REVERSIBLE
1mF 250V 25p; 1.5mF 100V 25p; 2.2mF 250V 30p; 3.3mF 100V 40p; 4.7mF 100V 40p; 10mF 63V 40p; 32mF 50V 25p.

HIGH VOLTAGE ELECTROLYTICS
27500V 45p 32+32+16/350V 90p 8+16/450V 75p
8/450V 45p 100+100/275V 50p 16+16/350V 80p
16/350V 45p 150+200/275V 50p 32+32/350V 85p
32/500V 95p 32+32+32/325V 50p 32+32/500V £2
32/350V 50p 50+50+50/350V 95p 50+50/300V 50p
50/450V 95p 8+8/500V £1 50+50/350V 80p

CAPACITORS WIRE END High Voltage
.001, .002, .003, .005, .01, .02, .03, .05 mfd 400V 10p.
.1mF 400V 14p. 600V 15p. 1000V 25p.
22mF 350V 12p. 600V 20p. 1000V 30p. 1000V 60p.
47mF 150V 10p. 400V 25p. 630V 30p. 1750V 60p.
TRIMMERS 30pF, 50pF, 100pF, 100pF, 150pF 20p. 500pF 30p.
MICROSWITCH SINGLE POLE CHANGEOVER 40p.
GEARED TWIN GANGS 365+365+25+25pF £2.
BRASS SPINDLE EXTENDERS 85p. Couplers 65p.
VERNIER DRIVE DRIVES. 36mm £2.50, 50mm £3.
SLOW MOTION DRIVE 6:1 £1.50. Reverse Vernier drive 90p.
TRANSISTOR "WIN GAN" Japanese Replacement £1
SOLID DIELECTRIC 100pF £1

HEATING ELEMENTS, WAFER THIN (Semi Flexible)
Size 11x9x1/4 in. Operating voltage 240V, 250W approx. Suitable for Heating Pads, Food Warmers, Convectro Heaters, Propagation, etc. Must be clamped between two sheets of metal or ceramic, etc.
ONLY 60p EACH (FOUR FOR £2) POST 50p.

NEW **baker** Star sound

high power full range quality loudspeakers. British made. Ideal for Hi-Fi, music P.A. or discotheques. These loudspeakers are recommended where high power handling and quality is required.



MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£16	£2
SUPERB	12	8-16	30	HI-FI	£26	£2
AUDITORIUM	12	8-16	45	HI-FI	£24	£2
AUDITORIUM	35	8-16	60	HI-FI	£37	£2
GROUP 45	12	4-8-16	45	PA	£16	£2
DG 75	12	4-8-16	75	PA	£20	£2
GROUP 100	12	8-16	100	Guitar	£26	£2
DISCO 100	12	8-16	100	Disco	£26	£2
GROUP 100	15	8-16	100	Guitar	£35	£2
DISCO 100	15	8-16	100	Disco	£35	£2

BAKER AMPLIFIERS BRITISH MADE



NEW PA150 MICROPHONE PA AMPLIFIER £129
4 channel 8 inputs, dual impedance, 50K-600 ohm 4 channel mixing, volume, treble, bass. Presence controls. Master volume control, echo send return socket. Slave sockets. Post £3.

BAKER 150 Watt AMPLIFIER 4 Inputs £99
For Discotheque, Vocal, Public Address. Three speaker outlets for 4, 8 or 16 ohms. Four high gain inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. 150 watts 8 ohms R.M.S. Music Power. Slave output 500 M.V. 25K ohm. Response 25 Hz - 20KHz ± 3dB. Integral Hi-Fi preamp separate Bass & Treble. Size - 16" x 8" x 5 1/2". Wt - 14lb: Master volume control. British made. 12 months' guarantee. 240V A.C. mains or 120V to order. All transistor and solid state. Post £2.
100 Volt Line Model £114. MONO SLAVE £80.
New Stereo Slave 150 + 150 watt 300 watt Mono £125. Post £4.

BAKER MOBILE PA AMPLIFIER. All transistor, 60-watt RMS, 12v DC & 240-v AC, 4 inputs 50K, Aux + 2 mics + 1 phone, 4-8-16 ohm + 100 volt line. **£89 p.p. £2.**

BAKER PORTABLE DISCO 150W. Twin console + amplifier + mike and headphones + twin speakers **£330.** 300 watt version Complete. **£399.** Carriage **£30.** Concola with pre-amp only **£107**

ELECTRONIC ECHO CHAMBER £85. Post £2
BBD Delay System 30 m/sec to 200 m/sec. Variable echo and direct sounds. Maintenance free. 240V AC.

DISCO GRAPHIC MIXER EQUALISER £108. Post £2
4 Channel stereo, 5 band graphic, red + green LED. VU display, headphone monitor or Deluxe Model **£119.**

PA CABINET SPEAKERS, Complete. 8 ohm 60 watt 17x15x9 in. £25. Post £4. 4 or 8 or 16 ohm 75 watt 23 x 15 x 11 in. £50. 90 watt 32x15x11 in. **£63.** 120 watt **£77.** Carr. £10. Black vinyl-covered with handles.

WATERPROOF HORNS 8 ohms 25 watt £20. 30 watt £23. 40 watt £26. 40W plus 100 volt line £32. Post £2.

R.C.S. 100 watt R.M.S. VALVE AMPLIFIER
4 Channel mixing. Master treble, bass and volume controls. 5 Speaker outlets, suits 4, 8, 16 ohm. Disco group. **£125.** Carr. & ins. **£15.**
60 WATT VALVE AMPLIFIER.
3 m.xer inputs, 4-8-16 ohm, 100 volt line. 5 controls, 2 mic inputs plus 1 input switchable for mic, phone, aux. Treble and bass and 3 volume controls, 7 valves. **£69.** Post £3.



FAMOUS LOUSPEAKERS "SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	DHMS	PRICE POST
WHARFEDALE	TWEETER	4in 30	8		£7.50 £1
PEERLESS	TWEETER	3 1/2 in 60	8		£6.50 £1
AUDAX	TWEETER	4in 30	8		£6.50 £1
AUDAX	MID-RANGE	4in 50	8		£7.50 £1
SEAS	MID-RANGE	4 1/2 in 100	8		£14.50 £1
AUDAX	WOOFER	5 1/2 25	8		£10 £1
GOODMANS	HIFAX	7 1/2 x 4 1/4 100	4/8/16		£30 £2
GOODMANS	WOOFER	8in 25	4/8		£7.50 £1
GOODMANS	HB WOOFER	8in 60			

GET THE COMPLETE PICTURE

— ORDER YOUR COPY NOW —


★ STILL THE ONLY CATALOGUE FOR THE COMPLETE RANGE OF COMPONENTS. BATTERIES, CRYSTAL FILTERS, RF POWER, MOSFET, TOKO COILS, CHOKES, ALPS PLOTTERS, SOLENOID CASSETTE MECHS ETC.

SUMMER '83

COMPONENTS FOR ELECTRONICS, COMMUNICATIONS & COMPUTING

ambit[®]
INTERNATIONAL

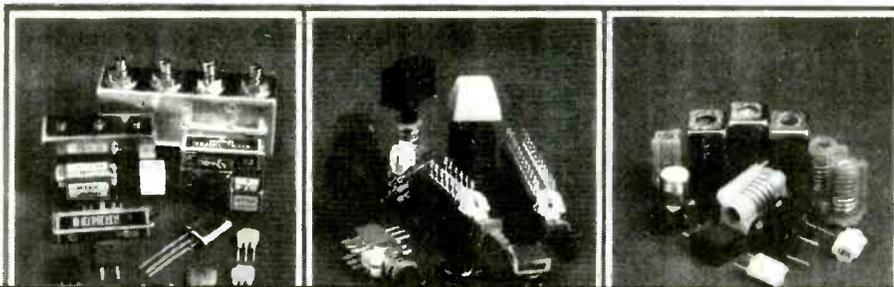WORLD OF RADIO & ELECTRONICS
— CATALOGUE —



80p
144 PAGES
3x£1 DISCOUNT VOUCHERS

- ★ FIRST WITH ON-LINE COMPUTER SHOPPING
- ★ FIRST FOR INNOVATION
- ★ FIRST FOR VALUE
- ★ FIRST FOR CHOICE
- ★ FIRST FOR SERVICE

ambit[®] INTERNATIONAL

200 North Service Road, Brentwood, Essex CM14 4SG
Tel: (Consumer Sales/Enquiries) 0277-230909.
Tel: (Industrial Sales/Enquiries) 0277-231616.
Tlx: 995194 AMBIT G. Data 24hrs (RS232/300 baud) 0277-232628.

WW - 060 FOR FURTHER DETAILS

ICOM ICR70



The professional communications receiver for point to point, ship to shore, and general coverage radio work. RANGE 100KHz-30MHz ★ MODES AM, SSB, CW, RTTY and optional FM ★ CPU based 10Hz step digital PLL synthesizer with DUAL VFO's ★ Frequency display 6 digit to 100Hz ★ STABILITY less than 50Hz after one hour ★ POWER SUPPLY 117 or 235V AC and optional 12V DC ★ IF - 1st 70.4515MHz, 2nd 9.0115MHz, 3rd 455KHz, 4th 9.0115MHz ★ Optional transceive units and filters available.

THIS SUPERB RECEIVER IS PRICED AT
£433.91 + VAT

Contact us for more details on this and other ICOM professional communications equipment.

PMR - MARINE - AMATEUR

Dealer enquiries welcome

Thanet Electronics 

143 Reculver Road, Herne Bay, Kent
Tel: 02273 63859. Telex 965179

WW - 034 FOR FURTHER DETAILS

ELECTROVALUE

Understandably
Britain's most popular
and relied-upon
suppliers of

SEMI-CONDUCTORS

I.C.s

COMPONENTS

COMPUTING EQUIPMENT

TOOLS, BOXES, CONNECTORS
and much, much more

OUR SUMMER PRICE LIST TELLS ALL

Send for your **FREE** copy by return
BETTER PRICES, BETTER CHOICE, BETTER SERVICE
Don't forget to mention **WIRELESS WORLD** with your request

ELECTROVALUE LTD.


Head Office: Mail Order Dept. and Shop
28 St Judes Road, Englefield Green, Egham, Surrey TW20 0HB
Telephone Egham (STD 0784; London 87) 33603; Telex 264475

Also in Manchester for personal shoppers at:
680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone 061-432 4945
Computing Shop:
700 Burnage Lane, Manchester. Telephone 061-431 4866

EMS POWER SYSTEMS

THE EASY SOLUTION TO YOUR POWER REQUIREMENTS

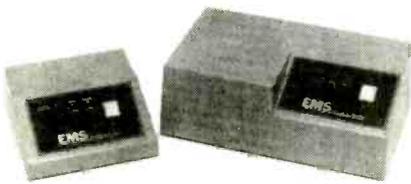Your previous Inverter/Charger requirements can now be sourced from the EMS Range.



EMS STANDBY POWER PACKS are suitable for any business machines including cash registers (including Scanners), weigh scales and small or large computers, in fact any equipment requiring constant AC power.

EMS STANDBY POWER PACKS — with automatic switching are designed to keep your electrical/electronic equipment running when there is no mains power, i.e. power failure, mobile or remote site.



Some typical Inverter types are:
 35IE 12V DC INPUT 35 Watts square wave output 115/230V AC
 120IE 12V DC INPUT 100 Watts square wave output 115/230V AC
 250IE 12V DC INPUT 250 Watts square wave output 115/230V AC
 200IS 12V DC INPUT 200 Watts sine wave output 115/230V AC
 500IS 12V DC INPUT 500 Watts sine wave output 115/230V AC
 1000IS 24V DC INPUT 1000 Watts sine wave output 115/230V AC

We also manufacture U.P.S. systems, power supplies and chargers.

For further details please contact:
E.M.S. Manufacturing Limited
 Chairborough Road
 High Wycombe, Bucks.
 Tel: (0494) 448484

WW - 063 FOR FURTHER DETAILS

hi! performance hi! competitive hi!

MORE ^{people are buying} TRIO

*** FOR *** MORE DISPLAY


nearly 50% more with the NEW LARGE 6 inch rectangular CRT with illuminated inner face graticule, 6KV accelerator voltage for a brighter, higher resolution display with guaranteed accuracy.

*** MORE SENSITIVITY

1 milli Volt per cm in the vertical axis, valuable for observing complex low level waveforms especially with 20 nano sec per cm Sweep Speed.

*** MORE FACILITIES

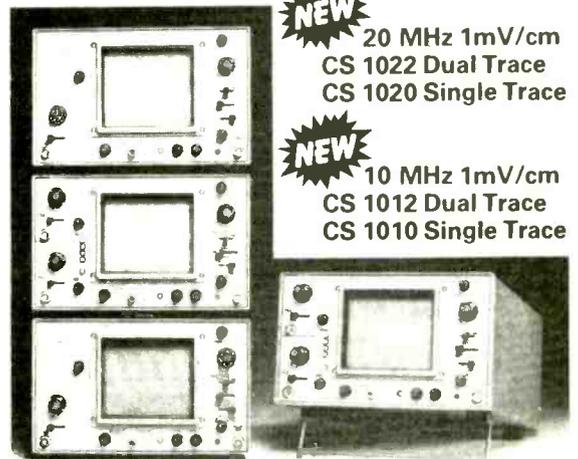like push-button MODES inc. Add, Sub, Alt and Chop - V mode trigger SOURCE - NEW super video sync - Front panel control of Astig, Trace rotation, Scale illum and X-Y - Chan I O/P, Int. Mod etc, etc.



NEW
20 MHz 1mV/cm
CS 1022 Dual Trace
CS 1020 Single Trace

NEW
10 MHz 1mV/cm
CS 1012 Dual Trace
CS 1010 Single Trace

AT REAL VALUE FOR MONEY PRICES

Fully Guaranteed for 2 years inc.
Free 'pick up' and 'return'



In a hurry? Then ring (0799) 24922

House of Instruments,
Clifton Chambers, 62 High Street,
Saffron Walden, Essex CB10 1EE
Telephone: (0799) 24922 Telex: 818750

Ask for FREE DATA

TRIO

hi!

hi! competitive hi!


House of Instruments Ltd.

WW - 059 FOR FURTHER DETAILS

BBC Micro Computer System

OFFICIAL DEALER

Please phone for availability

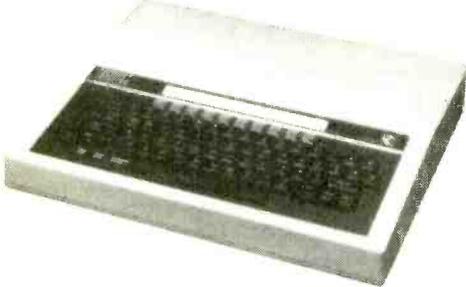

BBC Model B £399
(incl. VAT)
Carr £8/unit
Model A to Model B
upgrade kit **£50**
Fitting charge **£15**
Individual upgrades also
available
TELETEXT ADAPTOR £195
WORDWISE 8K ROM £39
TORCH Z80 DISC PACK £780
WORD PROCESSOR 'VIEW'
16K ROM £52

FLOPPY DISC INTERFACE
incl. 1.2 Operating System
£95 & £20 installation

BBC FLOPPY DISC DRIVES
Single Drive 5¼" 100K **£230**+£6 carr.
Double Drive 5¼" 800K **£699**+£8 carr.
BBC COMPATIBLE 5¼" DISC DRIVES
These drives are supplied in BBC matching colour
cases.
SINGLE DRIVES: 100K **£150**; 200K **£215** 400K **£265**
SINGLE DRIVES: with PSU 100K **£185**; 200K **£260***; 400K
£330
DUAL DRIVES: with PSU 200K **£355**; 400K **£475***; 800K
£595
***These drives are provided with a switch to change
between 40 and 80 tracks.**
DRIVE CABLES: SINGLE **£8**, DUAL **£12**.
DISC MANUAL & FORMATTING DISKETTE **£17.50**

BUSINESS, EDUCATION AND FUN SOFTWARE IN STOCK -

Phone or send for our BBC leaflet

CASSETTE RECORDER

SANYO Data Recorder DR101
A superior quality data recorder with dedicated
computer output and monitoring facility on
both record and play
£39.50 + £1.50 carr.
SLIMLINE Cassette Recorder complete with
counter and remote control
£24.50 + £1.50 carr.
Computer Grade Cassettes
£0.50 each, £4.50 for 10 + £1 carr
Cassette lead **£3.50**.

MONITORS

MICROVITEC 1431 14in Colour Monitor £249+£8 carr
MICROVITEC 2031 20in Colour Monitor £319+£8 carr
KAGA 12in RGB Monitor £255+£8 carr
Lead for KAGA/SANYO RGB £10
SANYO HI RES GREEN MONITOR £99+£6 carr
SANYO HI RES RGB MONITOR £445+£8 carr.

BBC BOOKS (no VAT; p&p £1)

Basic on BBC **£5.95**
30 House Basic **£5.95**
Programming the BBC Micro **£6.50**
BBC Micro An Expert Guide **£6.95**
Assy Lang Prog. for BBC **£8.95**
6502 Machine Codes for Beginners **£6.95**

NEC PC 8023 BE - C

100CPS, 80 cols
Logic Seeking, Bi-
directional
Forward and Reverse
Line Feed.
Proportional Spacing,
Auto Underline,
Hi-Res and Block
Graphics, Greek Char.
Set.
Only **£320 + £8 carr.**




PRINTERS

SEIKOSHA GP 100A

80 cols 30 CPS
Full ASCII and Graphics
10" wide paper
Now only **£175 + £6 carr.**
GP250A **£235 + £8 carr.**

Parallel Printer lead for BBC/Atom to most printers **£13.50**
Variety of interfaces, ribbons in stock.
2,000 fan fold sheets 9½" x 11" **£13.50 + £3 p&p**

EPSON RX80 and FX80

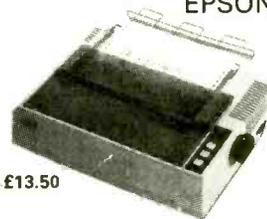

RX 80 100CPS 80 col
Tractor Feed **£290**

FX80 160CPS 80 col
F & T Feed **£389**

MX100 F/T3 **£425**
(Carr./printer **£8**)

Full speci-
fication on request

RUGBY ATOMIC CLOCK

This Z80 micro controlled clock/calendar receives
coded time data from NPL Rugby. The clock never
needs to be reset. The facilities include 8 independ-
ent alarms and for each alarm there is a choice of
melody or alternatively these can be used for
electrical switching. A separate timer allows
recording of up to 240 lap times without interrupt-
ing the count. Expansion facilities provided.

See July/August '82 ETI for details.
Built and tested **£145+£2 p&p**.

MICROTIMER

6502 Based Programmable clock timer with
★ 224 switching times/week cycle
★ 24-hour 7-day timer
★ 4 independent switch outputs directly
interfacing to thyristor/triacs
★ 6 digit 7 seg. display to indicate real time,
ON/OFF and Reset times
★ Output to drive day of week switch and
status LEDs.
Full details on request. Price for kit **£57**

CONNECTOR SYSTEMS

I.D. CONNECTORS

I.D. CONNECTORS (Speedblock Type)			
No of ways	Header Plug	Recep- tacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

D CONNECTORS No. of ways				
	9	15	25	37
MALE Solder	80p	105p	160p	250p
Angled	150p	210p	250p	365p
FEMALE				
Solder	105p	160p	200p	335p
Angled	165p	215p	290p	440p
Hoods	90p	85p	90p	100p
IDC 25-way plug 385p, Socket 450p				

TEXTPOOL ZIF

SOCKETS	24-pin	£5.75
	40-pin	£9.75
28-pin	£8.00	

DIL SWITCHES

4-way	70p	8-way	90p
6-way	85p	10-way	140p

JUMPER LEADS

24" Ribbon Cable with Headers				
	14-pin	16-pin	24-pin	40-pin
1 end	145p	165p	240p	350p
2 ends	210p	230p	345p	540p
24" Ribbon Cable with Sockets				
	20-pin	26-pin	34-pin	40-pin
1 end	160p	200p	280p	300p
2 ends	290p	370p	480p	525p

Ribbon Cable with D. Conn.
25 way Male 500p Female 550p

RS 232 JUMPERS

RS 232 JUMPERS (25-way D)	
24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female-Female	£10.00
24" Male-Male	£9.50
24" Male-Female	£9.50

DIL HEADERS

DIL HEADERS Solder Type IDC Type		
	40p	100p
14pin	40p	100p
16pin	50p	110p
24pin	100p	150p
40pin	200p	225p

AMPHENOL CONNECTORS

36-way plug Centronics Parallel
Solder **£5.25** IDC **£4.95**
36-way socket Centronics Parallel
Solder **£5.50** IDC **£5.20**
24-way plug IEEE Solder **£5**
IDC **£4.75**
24-way socket IEEE Solder **£5**

RIBBON CABLE

RIBBON CABLE (Grey/meter)		
	10-way	40p
	16-way	60p
	20-way	85p
	26-way	120p
	34-way	160p
	40-way	180p
	50-way	200p
	64-way	280p

EURO CONNECTORS

EURO CONNECTORS		
DIN 41617	Plug	Skt.
21-way	160p	165p
31-way	170p	170p
DIN 4161Z		
2x32-way St. Pin	220p	275p
2x32-way Ang. Pin	275p	320p
3x32-way St. Pin	260p	300p
3x32-way Ang. Pin	375p	350p

EDGE CONNECTORS

EDGE CONNECTORS		
	0.1"	0.156"
2x18-way	-	140p
2x22-way	190p	240p
2x23-way	175p	-
2x25-way	225p	220p
2x28-way	190p	-
1x43-way	260p	-
2x43-way	365p	-
1x77-way	600p	-
5100 Conn	-	600p

TEST CLIPS

14-pin	275p	16-pin	£3
40-pin	£6		

DISC DRIVES FOR THE FORTH COMPUTER

5¼" Teac FD55 Slim Line Mechanisms.
FD55A 40 track SSDD 250kbytes unformatted
Bare: **£135**; Cased: **£155**
2 x FD55A 40 track SSDD 500kbytes unformatted
Cased x psu **£350**
FD55E 80 track SSDD 500kbytes unformatted
Bare: **£180**; Cased: **£205**
2 x FD55E 80 track SSDD 1 Mbyte unformatted
Cased + psu **£475**
5¼" Mitsubishi M4853 Slim Line mechanism 80 track
DSDD 1 Mbyte unformatted Bare: **£225**; Cased: **£245**
2 x M4853 2 Mbytes Cased + psu **£590**
Single drive cable **£8**; Dual Drive cable **£12**
Other parts for FORTH COMPUTER available send SAE
for details.

SOFTY II INTELLIGENT PROGRAMMER

The complete microprocessor development system for Engineers and
Hobbyists. You can develop programs, debug, verify and commit to
EPROMS or use in host computer by using softy as a romulator. Power-
ful editing facilities permit bytes, blocks of bytes changed, deleted or
inserted and memory contents can be observed on ordinary TV.
Accepts most +5v Eproms.
Softy II complete with PSU, TV Lead and Romulator lead **£169**

★ SPECIAL OFFER ★

2532	350p
2732	350p
2764-25	450p
27128-25	£25
4164-2	450p
6116P-150NS	350p

UV ERASERS

UV1B up to 6 Eproms **£47.50**
UV1T with Timer **£60**
UV140 up to 14 Eproms
£61.50
UV141 with Timer **£78**
(Carr £2/eraser)
All erasers are fitted with
mains switches and safety in-
terlocks.

'WIRELESS WORLD' PROJECTS

Semiconductors inc.
I. Cs., Transistors,
Displays, Connectors and
Sockets for most projects
are stocked by us

BOOKS

(No VAT p&p £1)
CRT Controller H/Book.....**£8.50**
Programming the Z80.....**£11.50**
Z80 Microcomp Handbook.....**£6.95**
Programming the 6502.....**£10.25**
6502 Assy. Lang.....**£12.10**
6502 Applications.....**£10.20**
6502 Software Design.....**£9.05**
6502 Games.....**£10.25**
Large selection of databooks, interfacing
books, books on BBC, etc in stock.
Ask for our list. WW-12

NEW COMPREHENSIVE CATALOGUE AVAILABLE
PLEASE SEND FOR PRICE LIST

74 SERIES **4029** **45p** **4030** **15p** **4031** **125p** **4032** **80p** **4033** **125p** **4034** **100p** **4035** **275p** **4036** **275p** **4037** **110p** **4038** **110p** **4039** **230p** **4040** **40p** **4041** **40p** **4042** **40p** **4043** **40p** **4044** **40p** **4045** **105p** **4046** **50p** **4047** **45p** **4048** **50p** **4049** **24p** **4050** **24p** **4051** **24p** **4052** **60p** **4053** **50p** **4054** **90p** **4055** **90p** **4056** **90p** **4057** **225p** **4058** **14p** **4059** **45p** **4060** **45p** **4061** **27p** **4062** **27p** **4063** **27p** **4064** **27p** **4065** **27p** **4066** **27p** **4067** **27p** **4068** **14p** **4069** **14p** **4070** **14p** **4071** **14p** **4072** **14p** **4073** **14p** **4074** **14p** **4075** **14p** **4076** **48p** **4077** **16p** **4078** **16p** **4079** **16p** **4080** **16p** **4081** **16p** **4082** **16p** **4083** **16p** **4084** **16p** **4085** **125p** **4086** **125p** **4087** **24p** **4088** **24p** **4089** **24p** **4090** **24p** **4091** **24p** **4092** **24p** **4093** **24p** **4094** **24p** **4095** **75p** **4096** **75p** **4097** **290p** **4098** **90p** **4099** **100p** **4100** **50p** **4101** **50p** **4102** **50p** **4199** **50p** **4200** **50p**

7400	11p	7401	11p	7402	12p	7403	12p	7404	12p	7405	12p	7406	12p	7407	18p	7408	14p	7409	14p	7410	14p	7411	14p	7412	14p	7413	14p	7414	18p	7415	18p	7416	18p	7417	18p	7418	18p	7419	18p	7420	18p	7421	18p	7422	20p	7423	18p	7424	18p	7425	18p	7426	18p	7427	18p	7428	18p	7429	18p	7430	14p	7431	14p	7432	14p	7433	22p	7434	22p	7435	22p	7436	22p	7437	22p	7438	22p	7439	25p	7440	15p	7441	55p	7442A	30p	7443	70p	7444	70p	7445	50p	7446A	50p	7447A	30p	7448	45p	7449	15p	7450	15p	7451	15p	7452	15p	7453	15p	7454	14p	7455	14p	7456	15p	7457	25p	7458	25p	7459	25p	7460	15p	7461	30p	7462	30p	7463	30p	7464	30p	7465	30p	7466	30p	7467	30p	7468	18p	7469	18p	7470	18p	7471	18p	7472	18p	7473	18p	7474	18p	7475	18p	7476	25p	7477	25p	7478	25p	7479	25p	7480	48p	7481	120p	7482	66p	7483A	30p	7484	30p	7485	60p	7486	18p	7487	18p	7488	18p	7489	18p	7490	20p	7491	35p	7492A	25p	7493A	24p	7494	24p	7495A	35p	7496	35p	7497	90p	7498	90p	7499	90p	7599	90p	7600	90p
------	-----	------	-----	------	-----	------	-----	-------	-----	------	-----	------	-----	------	-----	-------	-----	-------	-----	------	-----	------	-----	------	-----	------	------	------	-----	-------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	-------	-----	-------	-----	------	-----	-------	-----	------	-----	------	-----	------	-----	------	-----

7601	90p	7602	90p	7603	90p	7799	90p	7800	90p
------	-----	------	-----	------	-----	------	-----	------	-----

4029	45p	4030	15p	4031	125p	4032	80p	4033	125p	4034	100p	4035	275p	4036	275p	4037	110p	4038	110p	4039	230p	4040	40p	4041	40p	4042	40p	4043	40p	4044	40p	4045	105p	4046	50p	4047	45p	4048	50p	4049	24p	4050	24p	4051	24p	4052	60p	4053	50p	4054	90p	4055	90p	4056	90p	4057	225p	4058	14p	4059	45p	4060	45p	4061	27p	4062	27p	4063	27p	4064	27p	4065	27p	4066	27p	4067	27p	4068	14p	4069	14p	4070	14p	4071	14p	4072	14p	4073	14p	4074	14p	4075	14p	4076	48p	4077	16p	4078	16p	4079	16p	4080	16p	4081	16p	4082	16p	4083	16p	4084	16p	4085	125p	4086	125p	4087	24p	4088	24p	4089	24p	4090	24p	4091	24p	4092	24p	4093	24p	4094	24p	4095	75p	4096	75p	4097	290p	4098	90p	4099	100p	4100	50p	4101	50p	4102	50p	4103	50p	4104	50p	4105	50p	4106	50p	4107	50p	4108	50p	4109	50p	4110	50p	4111	
------	-----	------	-----	------	------	------	-----	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	-----	------	-----	------	-----	------	-----	------	-----	------	------	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	------	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	------	------	------	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	------	------	-----	------	------	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	--

RADIO AND TELEVISION SERVICING

1982-83 MODELS

Editor: R. N. Wainwright, T. Eng (CEI), F.S.E.R.T.

This volume, like its predecessors, continues to provide the only comprehensive reference source for a large range of domestic entertainment products currently available from retail outlets.

The first part of this volume contains manufacturers' circuits and service information for the main classes in a wide selection of colour and monochrome receivers. The second section presents a selection from the numerous available types of audio equipment, including portable and clock radios, in-car units, cassette recorders, combinations and unit audio systems. The usual addendum gives cross-references to relevant information detailed in earlier volumes, together with supplementary servicing information abstracted from the technical bulletins issued by the manufacturers during the year.

Price: £22.50
On sale now

Previous volumes are still available. Enquiries to the Sales Department, Macdonald & Co.

From booksellers, or in case of difficulty, please use the coupon below:-

To: Cash Sales Dept. Macdonald & Co.,
Maxwell House, Worship Street, London
EC2A 2EN.

Please send me copy(ies) of RADIO AND TELEVISION SERVICING 1982-83 MODELS.

I enclose a cheque/PO made out to Macdonald & Co (Publishers) Ltd for
Please allow 28 days for delivery.

Name

Address

WW

Macdonald
a BPCC plc company

WW - 065 FOR FURTHER DETAILS

pantechnic

THE POWERFET SPECIALISTS

POWERFET AMPLIFIER MODULES

MODEL	POWER RANGE (Continuous RMS)	TYPICAL LOADS	PRICES (one off)
PFA 100	50W-150W	4Ω, 8Ω	£20.65
PFA 200	100W-300W	4Ω, 8Ω	£27.35
PFA 500	250W-600W	2Ω, 4Ω, 8Ω	£42.00
PFA HV	200W-300W	4Ω, 8Ω, 16Ω	£36.04

Key features:

- RELIABLE - Powerfet freedom from thermal runaway and secondary breakdown
- LINEAR - TID zero, IM/THD < 0.01% full power (mid-band THD down to 0.0015%)
- FAST - Slew rate > 30V/μS (45V/μS typical)
- QUIET - Signal to noise ratio 120dB
- BRIDGEABLE - Without extra circuitry
- STABLE - Unconditionally
- LOW COST - 10 watts to 20 watts per £, depending on model and quantity

As they stand these modules suit most P.A. and industrial applications and satisfy all foreseeable audiophile requirements. (The HV is aimed at digital audio.) Where aspects of performance fail to meet specific requirements (e.g. in speed or power) low-cost customising is often a possibility. Alternatively entirely new boards can be produced.

ALSO -

PAN 20 - Ultra-low-noise/distortion, mono preamp board, £7.61

PAX 2/24 - 2-way active crossover board (24dB/octave) plus regulators, £9.70

THE HEAT EXCHANGER - New, super-efficient heatsink; handles 300W or 1.2kW when blown; 7in. x 4in. x 2 1/4in., £7.50

This is just a fraction of the new products available from Pantechnic - check us out!

Prices exclude V.A.T.

Carriage 75p

Price and Delivery
PANTECHNIC (Dept. WW9)
17A WOOLTON STREET
LIVERPOOL L25 5NH
Tel: 051-428 8485

Technical Enquiries
contact
Phil Rimmer
on
01-800 6657

WW - 064 FOR FURTHER DETAILS

FILTERS

Custom-built to YOUR requirements

Solent Electronic Services Ltd. specialize in the custom design and manufacture of L/C and crystal filters in the 0-40 MHz range (0-1000 MHz under development).

Filters are designed, built and tested to meet the highest specifications, including those for telecommunications and defence.

Production is specifically geared to small quantities - from single units to small batches - at relatively low cost.

Phone or write for further information:



Solent Electronic Services Ltd.

15 Abshot Close Titchfield Common
Fareham Hants PO14 4LZ

Tel. 04895-82094

WW - 068 FOR FURTHER DETAILS

Give as they Gave

RAFA WINGS APPEAL






DURING SEPTEMBER



LEADER

Peak Performance Oscilloscopes

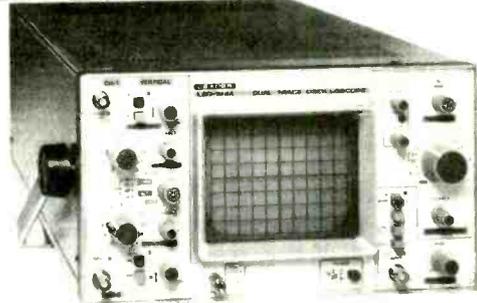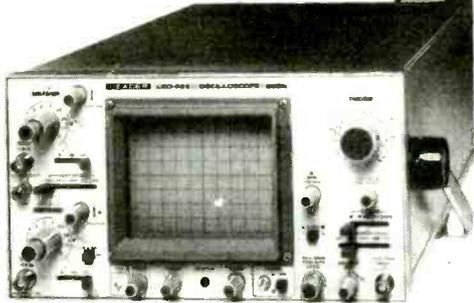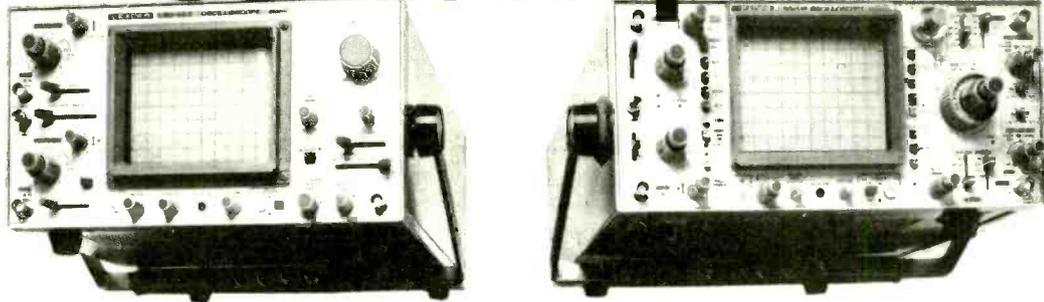

Professionals who know the difference prefer Leader peak performance oscilloscopes. Versatile, reliable and compact instruments. The LBO range of dual trace scopes includes a battery portable with 20MHz bandwidth, two low cost 15MHz and 20MHz models and 35MHz, 50MHz and 100MHz laboratory performance models with or without delayed sweep.

LBO-514A is a dual trace 50MHz bandwidth, 1Mv sensitivity, low cost general purpose oscilloscope.

LBO-522 is a dual trace 20MHz bandwidth 500 μ v sensitivity oscilloscope featuring X-Y, hold off variable plus full TV triggering.

LBO-523 is a 35MHz dual trace offering similar features to the LBO-522 plus internal graticule dome-mesh tube with 7Kv accelerations (pda).

LBO-524 is a 35MHz dual trace scope offering similar features to the LBO-523 plus the added facility of delayed sweep timebase.

LBO-517 is a 50MHz quad trace scope offering comprehensive triggering and timebase options.

LBO-518 is a 100MHz quad trace version of the LBO-517 including similar facilities.

LBO-308s is a small compact 20MHz dual trace battery or mains portable scope offering full triggering and timebase facilities.



thandar
ELECTRONICS LIMITED

Thandar Electronics Ltd.,
London Road, St. Ives,
Huntingdon, Cambs. PE17 4HJ, England.
Tel: (0480) 64646, Telex: 32250 Test.

PUTTING THE BEST WITHIN YOUR GRASP

WW - 029 FOR FURTHER DETAILS

TH03

HART

LINSLEY-HOOD 300 SERIES AMPLIFIERS



30 Watt Complete Kit £65
 35 Watt Complete Kit, MosFet O/P £79.50
 45 Watt Complete Kit, MosFet O/P £83.50
 Reprints of 30 Watt Article from 'Hi-Fi News' 50p
 Reprints of MosFet Postscript to above 30p

'P.W. WINTON' TUNER AND AMPLIFIER



Tuner, Complete Kit £183
 Amplifier, Complete Kit £99
 Amplifier Reprint £1.25

SOLENOID CONTROLLED HI FI/DIGITAL CASSETTE MECHANISM



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter, and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

LINSLEY-HOOD 100 WATT POWER AMPLIFIER

Our complete kit for this brilliant new design is the same size as our Linsley-Hood Cassette Recorder 2. Kit includes all parts for two power amplifiers with large heatsink area, huge power supply and speaker protection circuit. Total cost of all parts is £114.46 but our special introductory price for all parts bought together is only £105.50.


THIS MONTH'S SPECIAL OFFERS

DOLBY 'B' NOISE REDUCTION IC LM1011
 Marvellous opportunity for home experimenters, build your own noise reduction system. Supplied complete with circuit showing typical application. Absolute knockout price only £3.50 for two inc. VAT and post.

COMPLETE STEREO CASSETTE DECK
 Brand new high quality top-loading Cassette Deck complete with Record/Play electronics. Supplied with connection data and circuit diagram. Automatic chrome/ferric switching. Only needs 9v DC supply. Total price only £18.34 inc. VAT and post.

COMPLETE STEREO TUNER MODULE
 Three band LW/MW/FM Stereo Tuner fully assembled on PCB 165 x 85mm. Supplied with Ferrite rod aerial and band switch fully wired. Facility provided to drive tuning meter and stereo LED. Only needs 12v DC supply. FM sensitivity. 2.5uV. Price only £7.99 inc. VAT and post.

SUPER SLIM FLOPPY DRIVE

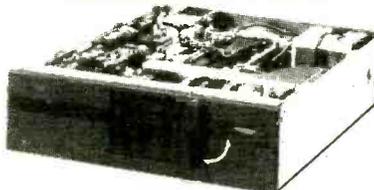

Very latest low consumption 5 1/4 in Disk Drives. Fit two in the space previously taken by one! Compatible with major standards. Connects directly to BBC and other microcomputers fitted with disk interface. The 80 track drive can be made switchable to read 40 or 80 track disks, very useful when upgrading to higher density storage.

40 Track Drive £154. 80 Track Drive £214

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC11 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £4.25
HM90 High Beta Permalloy Head. A hard wearing, higher performance head with metal capability £6.20
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £2.20
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £7.40
 Please consult our list for technical data on these and other Special Purpose Heads.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £3.80 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback £3.68

Full details of the entire range of HART products is contained in our illustrated lists.

Ask for your FREE copy NOW. Enquiries for lists are also welcome from overseas but please let us have three IRCs to cover the cost of surface post or 5 IRCs for airmail.

In a hurry? A telephone order with credit card number placed before 3 p.m. will be despatched THAT DAY!

Please add part cost of post, packing and insurance as follows:

INLAND
 Orders up to £10 - 50p
 Orders £10 to £49 - £1
 Orders over £50 - £1.50

OVERSEAS
 Postage at cost plus £2
 documentation and handling

PLEASE ADD VAT
TO ALL PRICES

HART

HART ELECTRONIC KITS LTD
 OSWESTRY, SHROPSHIRE
 SY18 9AF

Please Note: New Phone Number: (0691) 652894

Personal callers are always very welcome but please note that we are closed all day Saturday

reprints

If you are interested in a particular article / special Feature or advertisement published in this issue of

WIRELESS WORLD

why not take advantage of our reprint service.

Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)

For further details contact Michael Rogers, Electrical-Electronic Press. Phone 01-661 3457 or simply complete and return the form below.

To Michael Rogers, Reprints Department:
 Quadrant House, The Quadrant
 Sutton, Surrey SM2 5AS

I am interested in copies of the article / advertisement headed featured in

WIRELESS WORLD

on page(s) in the issue dated

Please send me full details of your reprint service by return of post.

Name

Company

Address

Tel. No.

FSK HIGH PERFORMANCE

Teletype Modems

HF/SSB

Selective Calling Systems

SOLID STATE 500W-1000W

Linear Amplifiers

COMPATIBLE WITH MOST EXISTING HF/SSB SYSTEMS.

AEL

Aero Electronics (AEL) Ltd.

Garwick House, Horley, Surrey, England RH6 9SU
 Telephone: Horley (02934) 5353 Telex: 871116 (Aero G)
 Cables: Aerocon Telex Horley

WW - 031 FOR FURTHER DETAILS

Modem Kit Only £39.95


- ★ CCITT standard
- ★ 300 baud full duplex
- ★ Direct connection - greatly reduces data loss associated with acoustic couplers
- ★ Powered from phone lines therefore no power supply required
- ★ Opto coupled data in and data out for intrinsically safe operation.

Build it yourself for £39.95 including VAT and postage (note - case not included).

Racom Ltd., Dept. B
 81 Cholmeley Road, Reading, Berks RG1 3LY
 Tel: 0734 67027

WW - 020 FOR FURTHER DETAILS

INSULATION TESTER

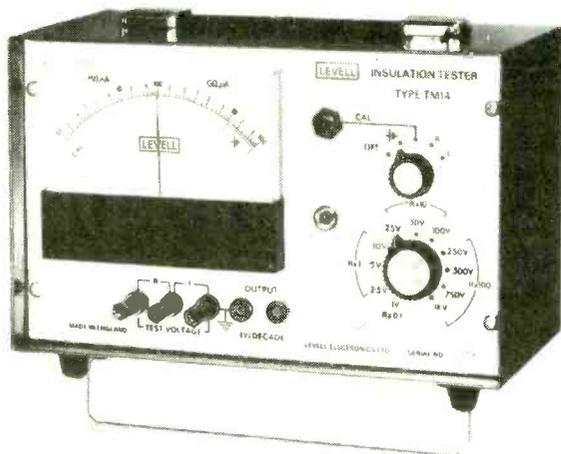

TYPE TM14 £190

+ P&P + VAT

A logarithmic scale covering 6 decades is used to display either insulation resistance or leakage current at a fixed stabilised test voltage. The current available is limited to a maximum value of 3mA for safety and capacitors are automatically discharged when the instrument is switched off or to the CAL condition. The instrument operates from a 9V internal battery.

RESISTANCE RANGES

10M Ω to 10T Ω (10^{13} Ω) at 250V, 500V, 750V and 1kV.

1M Ω to 1T Ω at 25V, 50V and 100V.

100k Ω to 100G Ω at 2.5V, 5V and 10V.

10k Ω to 10G Ω at 1V.

Accuracy $\pm 15\%$ + 800 Ω on 6 decade logarithmic scale.

Accuracy of test voltages $\pm 3\%$ ± 50 mV at scale centre.

Fall of test voltages $< 2\%$ at 10 μ A and $< 20\%$ at 100 μ A.

Short circuit current between 500 μ A and 3mA.

CURRENT RANGE

100pA to 100 μ A on 6 decade logarithmic scale.

Accuracy of current measurement $\pm 15\%$ of indicated value.

Input voltage drop is approximately 20mV at 100pA,

200mV at 100nA and 400mV at 100 μ A.

Maximum safe continuous overload is 50mA.

MEASUREMENT TIME

< 3 s for resistance on all ranges relative to CAL position.

< 10 s for resistance of 10G Ω across 1 μ F on 50V to 500V.

Discharge time to 1% is 0.1s per μ F on CAL position.

RECORDER OUTPUT

1V per decade $\pm 2\%$ with zero output at scale centre.

Maximum output ± 3 V. Output resistance 1k Ω .

Send for data covering our range of instruments.

LEVELL ELECTRONICS LTD.

Moxon Street, High Barnet, Herts. EN5 5SD
Tel: 01-449 5028/440 8686

WW - 005 FOR FURTHER DETAILS

CX80 COLOUR MATRIX PRINTER

New low price
£795 + V.A.T.

At last a low-cost Colour Matrix Printer for Text, Graphics, Histograms, Colour VDU Dumps, etc.

Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.



Compatible with most microprocessors, prints in 7 colours – sophisticated internal programme makes the CX80 easy to use.

Dot Addressable + 15 user programmable characters, 96 ASCII and 64 graphics characters in rom. Centronics interface with RS232 and IEEE488 options. Apple II interface gives dot for dot colour dump. New viewdata interface prints out two pages side by side in full colour. See Prestel 200650.

The CX80 is a product of our own design and development laboratories. It represents a British breakthrough in colour printer technology. Colour brochure on request. OEM pricing available.

INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432. Telex: 377106

AN OSCILLOSCOPE & DUAL POWER SUPPLY IN ONE PRECISION INSTRUMENT FOR JUST **£324 plus VAT**



Made in Britain

You can now buy a dual trace oscilloscope and dual power supply and have it delivered anywhere in the UK mainland for little more than £300. Alternatively, if you already have a Scopex dual trace scope, the power supply can be supplied separately for you to fit. Only Scopex offers this total add-on compatibility.

SCOPEX PS Combined oscilloscope and power supply £324 plus VAT
 PD151/4 & /14 Dual power supply for mounting on Scopex dual trace scopes £88 plus VAT
 PS151/1 Stand-alone dual power supply in instrument case £98 plus VAT

SCOPEX

the oscilloscope people

Scopex Instruments Limited, Poxmore House,
 Poxmore Avenue, Letchworth, Herts SG6 1HZ
 Telephone (04526) 72771

WW - 062 FOR FURTHER DETAILS

B. BAMBER ELECTRONICS

Rank Pullin Airport Weapon Detector Type 3 Walk-through Cabinet. Complete and good working order. **£150 plus VAT.**
 Marconi HF Spectrum Analyser Type OA1094A/S complete with Frequency Converter Type TM644B and mounted on trolley, 0-30 MHz **£90 plus VAT.**
 Systron Donner Spectrum Analyser Model 805 200 Hz - 1.6 MHz. POA.
 Hewlett Packard SHF Signal Generator Type 620B 1 - 11 GHz, FM, CW, & Square Wave, **£120 plus VAT.**
 Marconi AM Signal Generator Type TF 801D/8S 10 - 485 MHz, **£95 plus VAT.**
 Avo Valve Tester Mark IV complete with instruction book, **£45 plus VAT.**
 Tektronix Oscilloscope Type 545A Mainframes, **£85 plus VAT.**
 Tektronix Oscilloscope Type RM45A Rack Mount mainframes, **£50 plus VAT.**
 Tektronix Oscilloscope Type 551 Mainframes with Power Unit, **£75 plus VAT.**
 Tektronix Oscilloscope Type 555 Mainframes with Power Unit, **£85 plus VAT.**
 Tektronix Sampling Oscilloscope Type 661, fitted with 4S1 plug-in, **£120 plus VAT.**
 Tektronix Plug-In Units Type B, G, H, K, L. **£25 each plus VAT.**
 Avo Transistor Tester Type 2 with Battery and Mains Power Units, **£30 plus VAT.**
 Solartron Oscilloscope Type CD 1642.
 Solartron Oscilloscope Type CD 1014.3.
 Tequipment Oscilloscope Type D 61.
 Tequipment Oscilloscope Type D 43 R.
 Tequipment Storage Oscilloscope type DM 64.
 Solartron RC Oscillator Type CD 1004 10Hz - 1 MHz. **£25 plus VAT.**
 Advance Oscilloscope Type OS 2100 DC - 30 MHz. **£185 plus VAT.**
 Radiosonde RS 21 Meteorological Balloon Transmitter with Water Activated Battery. **£5 each plus VAT.**
 Pye Industrial pH Monitor Model 539 complete with Technical Manual. **£30 plus VAT.**
 Marconi AM/FM Signal Generator Type TF 995A/5, **£250 plus VAT.**
 Meguro Signal Generator Type MG6 - 230E 16KHz - 50 MHz. **£125 plus VAT.**
 Philips PAL Colour TV Pattern Generator Type PM 5508, **£185 plus VAT.**

Good secondhand equipment always wanted for cash

Pye Europa MF5FM High Band Sets, ideal for 2 M. 5 watt output 6 Ch. complete but less mike and cradle with circuit diagrams, **£60 each plus VAT.**
 Pye Reporter MF6 AM High Band Sets, single Ch. complete but less speaker with circuit diagrams, **£60 plus VAT.**
 Pye Motafone MF5AM Mid band 6 Ch. good condition with circuit diagram, **£15 plus VAT.**
 Pye Westminster W15AMD Mid Band Single Ch. complete but less speaker, mike and cradle, **£45 plus VAT.**
 Pye Westminster W15AMD Low and High Band Sets, complete but less speaker, mike and cradle, **£50 plus VAT.**
 Pye Westminster W30AM Low Band Sets, boot mounted, 30 W output, complete but less speaker, mike and leads, **£25 plus VAT.**
 Pye Olympic M201 AM High Band, complete but less mike, speaker and cradle. With circuit diagrams. **£40 plus VAT.**
 Pye Cambridge AM10D Low Band, few only **£15 plus VAT.**
 Pye Cambridge AM10B High Band, few only, **£10 plus VAT.**
 Pye Base Station F27 Low Band, **£40 plus VAT.**
 Pye Base Station F30 High Band, **£180 plus VAT.**
 Pye Base Station F401 High Band, **£220 plus VAT.**
 Pye Base Station F9U UHF. Remote. **£90 plus VAT.**
 Pye RTC Controller units for remotely controlling VHF and UHF fixed station radio telephones over land lines. **£10 plus VAT.**
 Pye PC1 Radiotelephone controller, good condition, **£50 plus VAT.**
 Pye Base Station Tx Type T406 100 W Low Band FM. **£150 plus VAT.**
 Pye Base Station Tx Type T100 100W FM 'G' Band 38.6-50 MHz, ideal for 6 M. New condition. **£100 plus VAT.**
 Pye Pocketfone Type PF5, UHF 'T' Band, complete with mike, good condition, **£45 plus VAT.**
 Pye Pocketfone PF5 Battery Charger Type BC16A, **£25 plus VAT.**
 Pye Pocketfone PF1 UHF Receiver, 440-470 MHz, single channel, int. speaker and aerial. Supplied complete with rechargeable battery and service manual. **£6 each plus £1 p.p. plus VAT.**
 Ni-Cad Batteries for Pye PF1 rx, used but good condition, **£2 each**, PF1 tx Batteries, **£3 each plus VAT.**

PLEASE NOTE: All sets are sold less crystals unless otherwise stated. Carriage on RT equipment - Mobiles £2 each. Base stations £15 each. Red Star available at cost.

SEMICONDUCTORS & VALVES p.p. 50p per order.
 PLEASE ADD VAT. 1N4148 10 for 25p, 741 4 for £1, 555 4 for £1, Z80-P10 £1.85, Z80-CTC £1.85, BC108 4 for 50p, BC109 4 for 50p, BC113 4 for 50p, BC148 4 for 50p, BC149 4 for 50p.
 QQV03 - 10 ex-equip. **£1.20**, QQZ03 - 10 new **£2.50**, QQV03 - 20a ex-equip **£5**, QQV06 - 40a **£15**, QQZ06 - 40a ex-equip. **£13**.
 VIDCON SCAN COILS 1" Transistor type but no details, complete with vidcon base. **£3.50 each plus 50p p.p. plus VAT.**
 Mains isolating transformer, 500VA 240V input, 240V C.T. output, housed in metal box. **£15 each plus £6 p.p. plus VAT.**
 Mains isolating transformer, 240V tapped input, 240V 3 amp, plus 12V 0.5 amp output, **£20 each plus 50p p.p. plus VAT.**
 Garrard Car Cassette Player Mechanisms, 12 V motor, stereo head, brand new, **£2.50 each plus 50p p.p. plus VAT.**
 Cigar Lighter Plug with lead, **£1 each p.p. plus VAT.**
 IC Test Clips, 28 way and 40 way, gold plated, **£2 each plus 30p p.p. plus VAT.**
 60 amp Alternator and Generator Noise Filters for use in vehicles, **£1 each plus 50p p.p. plus VAT.**
 Computer Grade Electrolytic Capacitors, screw terminals, 25000 mfd., 33 volt, brand new, **£1 each plus 50p p.p. plus VAT.**
 Mains Transformers 220 v Pri. 36 v @ 1.5 amp. Sec. **£1 each plus 50p p.p. plus VAT.**
 BASF Chromdioxid Video Cassette Tape for use with Philips N1500/1700 VCR. LVC30+5, 36 min. long play. **£5 each plus 50p p.p. plus VAT.**
 Mullard Vari-Cap Tuners Type ELC2003, UHF only, removed from brand new TV sets. **£3.50 plus 5p p.p. plus VAT.**
 2N3055 Transistors, Brand New, 4 for **£1 plus 20p p.p. plus VAT.**
 Beryllium Block Mounts for CCS1 valves. Brand new and boxed, **£10 each plus 50p p.p. plus VAT.**

All prices quoted exclude p/p and VAT unless otherwise stated




5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE
PHONE: ELY (0353) 860185



WW - 061 FOR FURTHER DETAILS

MARK 1983 WITH GAPS IN CIRCUIT FILES WELL-PLUGGED

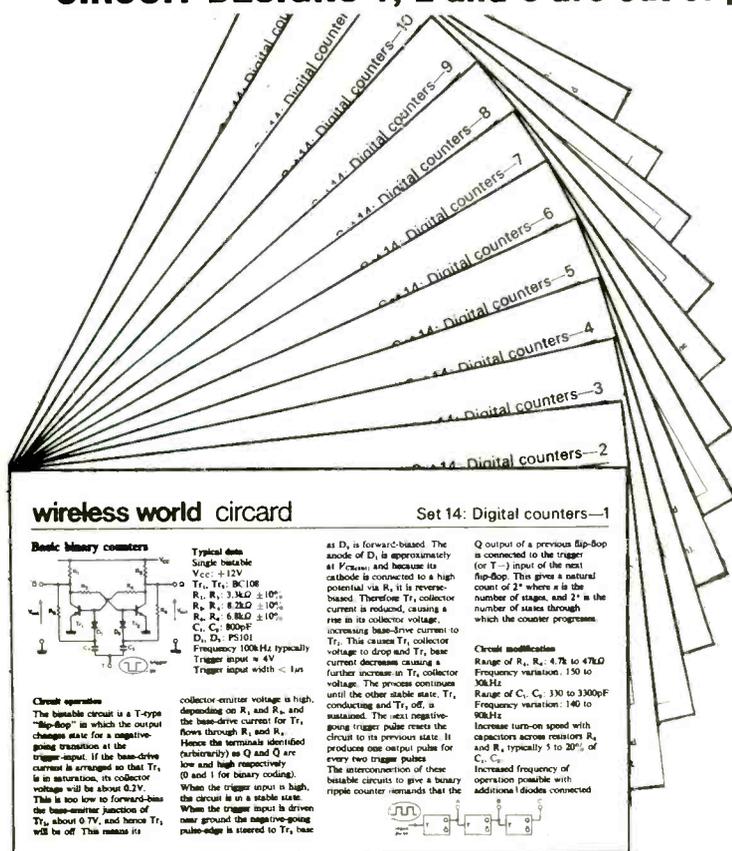WIRELESS WORLD CIRCARDS last year benefited many 'new generation' readers who bought at 1976 bargain prices + 10% discount for 10 sets! Most sets are still available although companion volumes CIRCUIT DESIGNS 1, 2 and 3 are out of print (CIRCARDS sets 1 to 30).



The Offer stands, so order now your sets of 127 x 204mm cards in plastic wallets. These unique circuit cards normally contain descriptions and performance data of 10 tested circuits, together with ideas for modifying them to suit special needs.

- 1 Basic Active filters 2 Switching Circuits, comparators and Schmitts (But these gaps cannot be filled) *
6 Constant current circuits 7 Power amplifiers 8 Astable circuits 9 Optoelectronics 10 Micro power circuits 11 Basic logic gates 12 Wideband amplifiers 13 Alarm circuits 14 Digital Counters 15 Pulse modulators 16 Current differencing amplifiers – signal processing 17 Current differencing amplifiers – signal generation 18 Current differencing amplifiers – measurement and detection 19 Monostable circuits 20 Transistor pairs 21 Voltage-to-frequency converters 22 Amplitude modulation and detection 23 Reference circuits 24 Voltage regulators 25 RC oscillators – 1 26 RC oscillators – 2 27 Linear cmos – 1 28 Linear cmos – 2 29 Analogue multipliers 30 Rms/log/power laws 31 Digital multipliers 32 Transistor arrays 33 Differential and bridge amplifiers 34 Analogue gate applications – 1 35 Analogue gate applications – 2.

*Photocopies only: 3 Waveform generators 4A.C. measurement 5 Audio circuits @ £3.20 each set.

**To Electrical-Electronic Press
General Sales Department
Room 108
Quadrant House
Sutton
Surrey SM2 5AS**

**Company Registered Number: 151537 (ENGLAND).
Registered Office: Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS**

Please send me the following sets of
Circards.....£2 each,
£18 for 10 post free.
Remittance enclosed payable
to BUSINESS PRESS INTERNATIONAL LIMITED
Name (Please print)
Address (Please print).....
.....

COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RK05, NOVA, TEXAS etc.
Front load £550.00 - Top load £295.00
PSU type ME3029 for 2 drives £125.00
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details.

5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 newsletter. Suppression Devices SD5A £5.95.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRANO NEW professional cooling fans.
ETRI 99XUOI Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95
BUHLER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.
MUFFIN-CENTAUUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60.

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

DON'T MISS THOSE BARGAINS CALL NOW, IT'S FREE!
7 days per week 24 hrs. per day
01-683 1133
8 BIT WORD - NO PARITY

COMPUTER 'CAB'



All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" w. 10.5" h. 11.5" d. Also available LESS PSU, with FANS etc. Internal dim. 19" w. 16" d. 10.5" h. £19.95. Carriage & insurance £9.50.

8" FLOPPY DISK DRIVES



Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality!! The 7100 single sided drive accepts hard or soft sectoring IBM or ANSI standard formats giving a massive 0.8 MB of storage. Absolutely SHUGART, BASF, SIEMENS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. 7100 Single sided £225.00 + Carriage and insurance £10.00.

Optional accessories: Full technical manual £20.00 alone. £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

RECHARGEABLE NICADS

SAFT VR2C 1.2v 'C' size nicads. 18 cells in ex equipment pack. Good condition - easily split to single cells. £9.50 + £1.90 post and packing.

VIDEO MONITORS

12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. ONLY £45.00 PLUS £9.50 CARR.

24" CASED. Again made by the KGM Co with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs, shops etc. Supplied in a used but working condition. ONLY £55.00 PLUS £9.50 CARR. & INS.

14" COLOUR superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL RGB with separate sync. and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col definition. Brand new and guaranteed. Complete with full data & circuit. 240 v AC working. Dim. 14" x 13" x 13". ONLY £19.00 PLUS £9.50 CARR.

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter

Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499 + VAT

Made to the very highest spec the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUME command compatibility and full control via CPM Wordstar etc. Many other features include bi directional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information. Optional extras: RS232 data cable £10.00. Tech manual £7.50. Tractor feed £140.00. Spare daisy wheel £3.00. Carriage & Ins. (UK Mainland) £10.00.



TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR + VAT
Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT. KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

SOFTY 2

The amazing SOFTY2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, VHF modulator, Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only £169.00 pp £1.95 Data sheet on request

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only £75.00
MODEM 2B/C Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. £85.00
MODEM 20-1 Compact unit for use with PRESTEL or full duplex 2 wire link 75 baud transmit - 1200 baud receive. Auto answer. £130.00
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. £130.00
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. £130.00 Carriage. 13A £4.50 2B/C & 20 £9.50.
DATA PUMP MODEM compact unit upto 1200 baud full duplex over 4 wires or half duplex over 2 wires. BELL specification with data i/o via RS232 25 way D socket, remote test etc. 240 v operation. Supplied complete with data £65.00 carr. £4.50.

For more information or details of other types of ex. stock modems contact sales office.

SPECIAL MODEM OFFER

EX TELECOM. Direct connect. 2 wire, European standard, 75/1200 baud data modems. Normally priced at £140.00, we have a limited quantity of guaranteed working, but cosmetically defective (ie scratches and scuffs on panels etc.) units at a super low price of only £49.95. Modems are made to the highest standard and conform to the CCITT tone spec. Ideal for MICRONET, PRESTEL or DISTEL's forthcoming high speed ports. Standard RS232 data i/o via 25 way D skt. With data.
MODEM 2A Early version of modem 2B/C 300 baud full duplex, send-receive, auto answer. RS232 i/o. With data but untested. End of line clearance. Only £35.00. Supplied complete with data. Carriage & Ins. £9.50

8" WINCHESTER price SLASH

S100 Bus 19 Mb. Subsystem. A cancelled order and change of policy by a major British disk drive manufacturer enables us to offer you 'last year's model' at a plug in and ready to go SUPER LOW PRICE. Our own custom controller pugs direct into the S100 bus and will control 2 disk drives, offering a total storage of OVER 36 Mbs! and at data transfer rates in excess of 7 Mb/sec seeing is believing!! Supplied complete with user configurable BIOS etc. Save a fortune. Limited quantity only.

3100 19 Mb. Disk drive £499.00 PSU unit £165.00
CD1100 controller & BIOS £345.00 PSU extension cable £9.95
Full tech Manual £20.00

Special SUBSYSTEM prices. 1 x 3100 disk + PSU + Controller £799.00
or 2 x 3100 disks + 2 PSU + Controller £1295.00
All prices + VAT and carriage. 90 day guarantee. Data on request.

ALL PRICES PLUS VAT

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec. with manufacturer's markings, fully guaranteed, 50+ £2.95 100+ £5.15.
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ £6.90 200+ £12.30 300+ £19.50

CALLING DEC USERS

Brand new and boxed

RSX 11M 3.2 Documentation kits, fill 3 feet of your bookshelf!! Under half price only £120.00 carr. £6.50 vat on manuals. DEC MSV11-DD 32k x 16 bit RAM £195.00 We are always keen to buy all types of used or surplus DEC equipment.

DISPLAY
-ELECTRONICS-

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies £20.00 Where post or packing not indicated please ADD 60p + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30 We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

32 Biggin Way, Upper Norwood, London SE19 3XF
Telephone 01-679 4414 Telex 27924



ELECTRIC SHOCK

2 WAYS TO RECOVERY

ACT AT ONCE – DELAY IS FATAL

ELECTRIC SHOCK ACT AT ONCE – DELAY IS FATAL

make sure it is safe to approach

If the casualty is in contact with the source of the shock break the contact by switching off the current, removing the plug or

switching the main fuse of this or any possible 'stand on dry insulating material' rubber-soled boots, insulating gloves.

Open books and try to push or pull the casualty clear of the contact using similar insulating material (such as blankets or a sheet) or a long pole. Do not touch him with bare hands.

if the casualty is breathing

Place casualty in the recovery position and call medical aid.

if the casualty is NOT breathing

Get someone to call medical aid while you start artificial respiration—speed is essential

1. Check casualty is not blocked. Remove spectacles and dentures. Insertion into open the casualty's mouth.
2. Place head well back with one hand and pinch the nose with the other.
3. Take a deep breath. Pinch casualty's nostrils together with your fingers. Seal your lips around the mouth and blow air steadily into the nostrils. Watch his chest rise.
4. Remove mouth and pinch nostrils. 5. Repeat and continue inflations at a normal rate of 12 breathings per minute. If the casualty is breathing place him immediately in the recovery position.

IF AFTER FOUR INFLATIONS casualty does not respond to artificial respiration

Check casualty pulse (press tip of your hand and pupil of eye if the pulse is absent the casualty is dead and the only chance of saving him is to start heart beating. Once the casualty is dead, start thumb on the lower part of the breastbone, slightly to the left, with a steady rhythm.

external heart compression

Place the heel of your hand on the upper part of the breastbone slightly to the left of the other hand. With your interlocked fingers, press down on the lower half of the breastbone. Do this 10 times, one per second and then give the casualty two inflations.

Check the pulse again. If it is present continue with inflations until casualty breathes on his own. Then place immediately in the recovery position. If the pulse is absent, continue the compressions. Do not stop the compressions until the casualty has started to breathe.

On recovery continue to watch casualty carefully as breathing may stop. If it does, resume casualty on his back and start artificial respiration again.

Form fields:
 doctor: _____
 phone: _____
 ambulance: _____
 hospital: _____
 nearest first aid: _____
 address: _____

1

2

Display the ELECTRICAL REVIEW shock first aid chart (356x508mm) supplied in thousands to destinations world-wide. Recent deliveries include consignments to companies in Papua New Guinea, Dubai, United Arab Emirates, The Philippines, apart from UK commercial and industrial, educational, Central Government, Local Authorities' orders.

Carry the ELECTRICAL REVIEW pocket-size shock card (92x126mm) designed to help safety and training officers, medical and welfare personnel; all who might find themselves called to save a life. Always pocket your card; there's a useful two-year calendar on the back.

GET IT – READ IT – PRACTISE 1-4
 BE READY TO SAVE A LIFE.
 SOMEONE MIGHT SAVE YOURS.

ACT AT ONCE—DELAY IS FATAL!

To Electrical-Electronic Press
 General Sales Department
 Room 108
 Quadrant House
 Sutton SM2 5AS
 Surrey
 England

Company Registered Number: 151537 (ENGLAND)
 Registered Office: Quadrant House, The Quadrant
 Sutton, Surrey SM2 5AS

Please send copy/copies as indicated

Pocket Card @ 70p each inc VAT
 Paper Chart @ £1.00 each post free
 Card Chart @ £2.00 each post free
 Plastic Chart @ £3.00 each post free

Discounts: 100 + copies 10%
 500 + copies 15%

(Overseas surface and air mail rates supplied on application.)

Appointments

Advertisements accepted up to 12 noon Tuesday, September 6th, for October issue, subject to space available.

DISPLAYED APPOINTMENTS VACANT: £17 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £3.50 per line, minimum £25 (prepayable).
BOX NUMBERS: £5 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS).
PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to BUSINESS PRESS INTERNATIONAL LTD. and crossed.



ecm

ALWAYS AHEAD WITH THE BEST!

£7,000-£20,000

- ★ **Where does your interest lie:** Communications; Computers; Weapons; Radar; Sonar; Data-Comms; Signal Processing; Medical; Telemetry; Simulation; Satcom; Local Area Nets; ATE?
- ★ **Experienced in:** Microprocessor Hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ **There are opportunities in:** Design; Test; Sales and Service for Engineers and Managers.
- ★ **Act now:** Just dial 100 and ask for **FREEPHONE JOBLINE** or send your c.v. to:

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
Freepost, Barkway, Royston, Herts SG8 8BR

(1926)

LINK

SOFTWARE DEVELOPMENT ENGINEER

A programmer is required to join our development team involved with software development of our automated broadcast television products (including processor-controlled broadcast studio colour television cameras). You should be experienced in writing assembly language programs for process control/automation applications using the NSC800 (a CMOS Z80) series of processors or similar. Experience in the use of higher level languages would also be an advantage.

TELEVISION SYSTEMS SALES ASSISTANT

An assistant with a sales engineering background who has the ability to progress into the area of writing and costing proposals and quotations for the design and construction of broadcast television systems (studios and outside broadcast vehicles) is required to join our sales team. You should have a knowledge of television broadcast engineering, a technical writing ability and a financial awareness.

Competitive salaries are offered together with free permanent health insurance, contributory pension scheme and generous relocation assistance where necessary.

Please telephone our Personnel Department on Andover (0264) 61345 for an application form or alternatively, write to us giving us full details of your background and experience.

LINK
ELECTRONICS

Walworth Industrial Estate, Andover, Hampshire, England
Telephone: Andover (0264) 61345

(2216)



RECRUITMENT

We have been successful in filling both senior and junior vacancies from our comprehensive file of applicants who have registered with this Company. We now wish to extend our file to meet future demands and are seeking application for registration mainly from those whose qualifications and experience fall into the following categories:

Management staff with engineering qualifications and experience in Television and Radio broadcasting or related technologies.

Transmitter installation or operations and maintenance engineers and technicians for Broadcasting and Telecommunications services.

Television Studio and Outside Broadcast engineers and technicians.

Graduates with Electronics degree but without material practical experience.

Vacancies occur both for UK based and overseas posts.

If you believe your skills or qualifications meet the above broad requirements please contact:

PERSONNEL & ELECTRONICS LTD.

Triumph House, 1096 Uxbridge Road
Hayes, Middlesex
UB4 8QH, England, UK

Telephone: 01-573 8333. Telex: 934271

(2222)

ELECTRONICS APPOINTMENTS

£6,000 - £16,000

ANALOGUE, RADIO, MICROWAVE
DIGITAL, MICROPROCESSOR, COMPUTER
DATA COMMS, MEDICAL

Design, Test, Sales and Field Service Engineers —
to use our free, confidential service and improve your salary
and career prospects, UK and overseas, contact:



11 Westbourne Grove, London W2. Tel: 01-229 9239 (1935)

LASER-SCAN LABORATORIES LIMITED



Laser-Scan Our range of products includes laser-based displays, plotters and digitisers.

Due to Company expansion we invite applications for:

IN-HOUSE COMMISSIONING ENGINEER

Required to test and align the Company's precision laser plotters and digitisers. A working knowledge of TTL is required, and experience with microprocessors and/or laser optical systems would be an advantage. A minimum qualification of HNC in Electrical and Electronic Engineering or equivalent is required, coupled with at least two years' industrial experience of both digital and analogue circuitry.

To the successful applicant we can offer pleasant working conditions, competitive salary and a non-contributory sickness scheme.

Please apply to:

The Personnel Officer
Laser-Scan Laboratories Limited
Cambridge Science Park
Milton Road
Cambridge CB4 4BH
Telephone: (0223) 69872



(2223)

INNER LONDON EDUCATION AUTHORITY
Learning Resources Branch
Television Centre
Thackeray Road
Battersea SW8 3TB

ENGINEER — ELECTRONIC MAINTENANCE

Salary range: (ST2) £7,035 to £7,974 plus £1,284 London Weighting Allowance.

The ILEA's Television Centre produces a wide range of educational programmes on video and audio cassettes.

The Maintenance section numbers four persons and a vacancy has arisen for an engineer with a sound knowledge of the principles of colour television, and preferably a working experience of maintaining broadcast type TV equipment. Applicants must wish to specialise on the video side (cameras, vision mixers, telecine, etc.), and will receive appropriate training.

An engineering degree, TEC or other equivalent qualifications are desirable.

Application forms from the Education Officer (EO/Estab. 1B), Room 365, The County Hall, London SE1 7PB. Please enclose a stamped and addressed foolscap envelope. Completed forms to be returned by May 4, 1983.

ILEA is an equal opportunities employer.

(2201)

LOGEX ELECTRONICS RECRUITMENT

Specialists in Field & Customer Engineering appointments, all locations and disciplines.

Logex House, Burleigh, Stroud
Gloucestershire GL5 2PW
0453 883264 & 01-290 0267

(24 hours)

TOWNLEY EMPORIUM

Bargains for callers
or send for catalogue

ELECTRICAL, ELECTRONIC & MECHANICAL COMPONENTS

Vast range of surplus test equipment:
Diodes; Thyristors; Resistors;
Terminals; Switches; Relays; Screws;
ICs; Tools.

Harehill Street off Burnley Road,
Todmorden, Lancs OL14 5JY

(2172)

COLOUR TELEVISION

If you have experience in television or test equipment engineering, there could be an interesting and rewarding future for you at Rediffusion Consumer Manufacturing Ltd. We are currently producing an advanced range of colour television receivers at our factories in County Durham and Cleveland and wish to make the following appointments:

PROJECT LEADER — Production Support

A senior engineer with a sound understanding of television systems and receiver circuits is required to lead a team of engineers and technicians responsible for ensuring that engineering standards are maintained during mass production of television receivers.

Responsibilities include investigation of any technical problems encountered in production, component fault assessment and origination of test/quality specifications. Close liaison is required with the design team to ensure that the product conforms to design specification.

PROJECT LEADER — Test Equipment

Effective testing of television receivers plays an important role in ensuring that our very high quality standards are maintained, and we now wish to appoint an experienced engineer of proven ability, to control a team of engineers and technicians responsible for all aspects of production test equipment.

Responsibilities will include the calibration and maintenance of a sophisticated range of test and signal origination equipment, employing both digital and analogue techniques. Although some test gear is designed and constructed locally, close liaison will be required with the design team, based at Chessington, Surrey, both to keep abreast of new development and influence the design of new equipment in the light of production experience.

Both positions are based at our factory in Bishop Auckland, County Durham, which is within easy reach of attractive countryside and has excellent road, rail and air connections. A wide range of good quality housing is available and assistance with relocation expenses will be made available where appropriate.

Attractive salaries will be offered, together with the benefits of a good pension scheme, free life assurance and 22 days' holiday with a choice of leave period.

If you are interested in either of these positions and would like more details, please write to or telephone:

Mr. D. Abbott
Engineering Product Manager
Rediffusion Consumer Manufacturing Ltd.
Fullers Way South
Chessington
Surrey KT9 1HJ
Telephone: 01-397 5411

REDIFFUSION

(2224)



Leeds Western Health Authority THE GENERAL INFIRMARY AT LEEDS Senior Electronics Technician (Grade III or IV)

Applications are invited from persons experienced in electronic maintenance, preferably with imaging and counting equipment, to work in our well-equipped Nuclear Medicine Department. Knowledge of computer systems particularly 8080A microprocessors would be an additional (or alternative) recommendation. The work is interesting, responsible and includes design and development of specialised electronic units. A less experienced person may be considered on the MPT IV Grade.

Minimum qualifications are H.N.C. in electronics or equivalent and N.H.S. experience is desirable.

Salary Scale: MPT III — £6,132 to £7,926 per annum
MPT IV — £5,171 to £6,798 per annum

Application forms and job descriptions are obtainable from The Personnel Officer, Leeds General Infirmary, Great George Street, Leeds LS1 3EX. Telephone (0532) 432799, ext. 3355.

Closing date: August 31, 1983.

(2218)

Television
Broadcast Engineers
BBC Television centre, London.

"Our reputation... excellence!"

Television Recording requires Electronics Engineers to train in Broadcast Engineering, to support an expanding Video Tape and Telecine Operation, which includes complex digital and analogue equipment.

Applicants need not initially possess an in-depth knowledge of Television Engineering, as full training will be given, but previous academic training must be supported by enthusiasm for practical engineering.

After training, applicants will progress to work involving all aspects of Television Recording, including in-depth servicing, acceptance of equipment, design of modifications, and technical investigations.

These challenging posts offer excellent promotional prospects for the self-motivated and committed engineer capable of working at the forefront of today's technology. Salaries range from £8,129 to £9,200 - this includes an allowance for shift working.

A higher salary will be considered in exceptional circumstances. Qualifications required are, a Degree in Engineering, HND, HNC, Full C&G. For further information please write, with details of your academic and work experience, to **Bob Neal, BBC, P.O. Box 2 BL, London W1 2BL.**


Please quote ref: 83.E.4055/WW/178
We are an equal opportunities employer.

BBC
television recording



Appointments

Test & Calibration Engineers

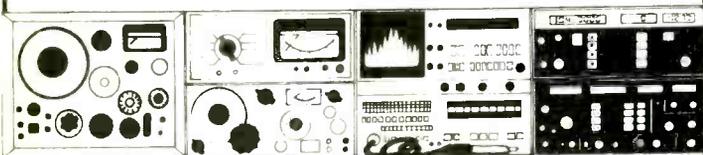

Having introduced an extended new product range, many of which are microprocessor based, Marconi Instruments has once again confirmed itself as Europe's leading manufacturer of sophisticated test and measurement systems. Our products are selling throughout the world and we are naturally developing further new and innovative designs.

A key role in our organisation is that of our Luton based Service Division, where a group of Technicians satisfy a very wide range of customer needs in the repair and calibration of test equipment.

When you join our team you will quickly become individually responsible for work assignments involving many different kinds of propriety products.

Prospects are excellent. The Division is part of a large company with its main Instrument Design/Manufacturing Base at St. Albans, a Microwave Plant at Stevenage and a further substantial Design Manufacturing Group at Donibristle in Scotland. The Company is proud of its policy of promoting men and women from within, as future Salesmen, Managers and Engineers.

Salaries, which are dependent upon experience and ability are excellent and regular overtime is normally available. Progress for competent engineers and technicians can be rapid. Relocation assistance is available in approved cases. Special consideration is given to 'ex-forces' personnel.

Whatever your level of experience we would like to hear from you. Cut out the coupon and send it to John Prodger, Recruitment Manager, Marconi Instruments Limited, FREEPOST, St. Albans AL4 0BR. Tel: (0727) 59292.

Name _____ Age _____

Address _____

Tel. No. _____

Years Experience _____

Present Salary:	£6,000	£7,000	£8,000	Over
	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>
	£7,000	£8,000	£9,000	£9,000

Qualifications _____

Present Job _____

(2143)

marconi instruments



ADVANCED TELECOMMUNICATIONS:

careers with extensive scope at Cheltenham

Join the Government Communications Headquarters, one of the world's foremost centres for R & D and production in voice/data communications ranging from HF to satellite – and their security. Some of GCHQ's facilities are unique and there is substantial emphasis on creative solutions for solving complex communications problems using state-of-the-art techniques including computer/microprocessor applications. Current opportunities are for:

Telecommunication Technical Officers

Two levels of entry providing two salary scales:
£5980-£8180 and £8065-£9085

Minimum qualifications are TEC/SCOTEC in Electronics/Telecommunications or a similar discipline or C & G Part II Telecommunications Technicians Certificate or Part I plus Maths B, Telecommunications Principles B and either Radio Line Transmission B or Computers B or equivalent: ONC in Electrical, Electronics or Telecommunications Engineering or a CIE Part I Pass, or formal approved Service technical training. Additionally, at least four years' (lower level) or seven years' (higher level) appropriate experience is essential in either radio communications or radar, data, computer or similar electronic systems. At the lower entry level first line technical/supervisory control of technicians involves "hands-on" participation and may involve individual work of a highly technical nature. The higher level involves application of technical knowledge and experience to work planning including implementation of medium to large scale projects.

Radio Technicians

£5232-£7450

To provide all aspects of technical support. Promotion prospects are good and linked with active encouragement to acquire further skills and experience. Minimum qualifications are a TEC Certificate in Telecommunications or equivalent plus two or more years' practical experience. Cheltenham, a handsome Regency town, is finely-endowed with cultural, sports and other facilities which are equally available in nearby Gloucester. Close to some of Britain's most magnificent countryside, the area also offers reasonably-priced housing. Relocation assistance may be available.

For further information and your application form, please write to

Recruitment Office
GCHQ Oakley, Priors Road
Cheltenham, Gloucestershire GL52 5AJ
or phone 0242 21491, Ext. 2269.



CAPITAL APPOINTMENTS LTD

THE UK's No. 1 ELECTRONICS AGENCY

If you have HNC/TEC or higher qualifications and are looking for a job in design, test, customer service, technical sales or similar fields:

Telephone now for our free Jobs list
We have vacancies in all areas of the UK
Salaries to £15,000 pa

01-637 5551 or 01-636 9659
(24 hours)

Or if you prefer send a FULL CV to:
CAPITAL APPOINTMENTS LTD
29-30 WINDMILL STREET, LONDON W1P 1HG



(2911)

GRADUATE STATUS ENGINEERS AND SCIENTISTS

COME TO HIGH-TECH COUNTRY

IN COMMUNICATIONS R & D

Hanslope in Buckinghamshire is, we admit, an unlikely backdrop for high technology research and development.

Yet a mere stone's throw away from this delightful rural village the men and women at HM Government Communications Centre are applying the very latest ideas in electronics to the development of sophisticated communications systems and installations, designed to meet special Government needs both at home and overseas.

For graduates and near graduates with real ability and a genuine passion for creative electronics design (the kind of enthusiasm that may already have prompted you to design and build your own communications equipment), this is a superb career environment.

Technically challenging projects cover a wide range of interests including radio (HF to microwave, advanced modulation, propagation studies and micro-circuitry applications); acoustics; magnetics; signal analysis; systems engineering.

The majority of these projects are directed towards specific ends, and we have our own production facility. So, unlike many


other R & D establishments, HMGCC offers you the satisfaction of seeing your work right through from conception to manufacture.

With such a broad spectrum of work and training facilities at your disposal, HMGCC is an ideal environment in which to develop the potential you've gained by studying an electronics-biased course. What's more, we think you'll find the working conditions and location very much to your liking.

Please write to us for further details on the work and the remunerations offered at the Centre. As our careful selection process takes some time, it would be particularly helpful if you could detail your qualifications, your personal fields of interest and practical experience, and describe the type of working environment most suited to your career plans.

Dr. D. Orr, Recruitment Officer,
HMGCC, Hanslope Park, Hanslope,
Buckinghamshire MK19 7BH.

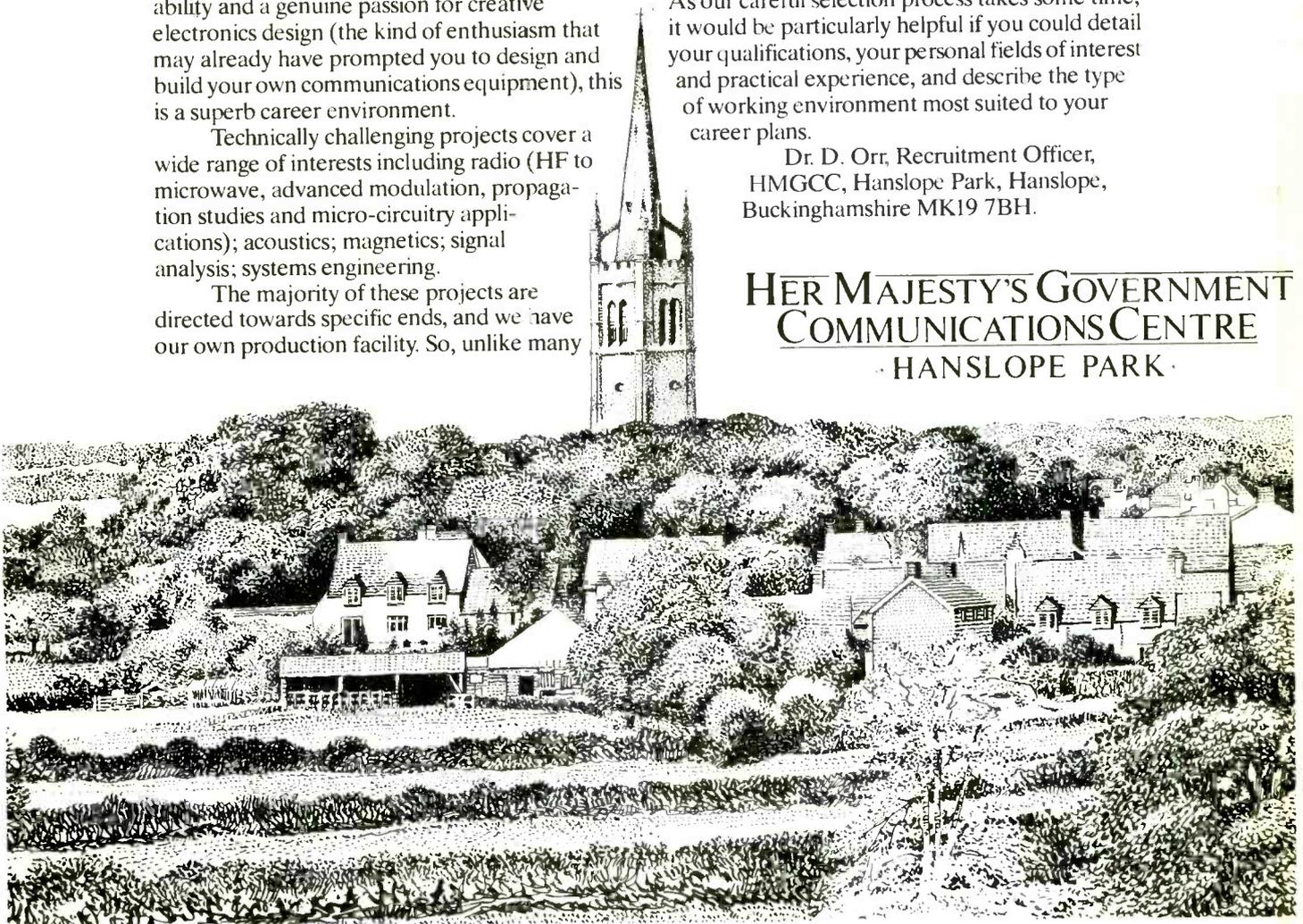**HER MAJESTY'S GOVERNMENT
COMMUNICATIONS CENTRE**
· HANSLOPE PARK ·



Electronics Engineers Aviation Systems Planning

IAL you will find worldwide, wherever there is a need for Aviation, Meteorological, Communications or Medical Services.

The continuing expansion within our Aviation Division enables us to offer further opportunities to career minded electronics engineers. These engineers will be based at our headquarters, near Heathrow Airport, and will undertake the systems planning of ground electronics projects for new and existing commitments. Dealing with these projects will entail an element of overseas travel.

You should be qualified with a degree, HND or HNC and preferably be a corporate member of a recognised professional institution. As well as systems planning your experience should cover

at least one of the following:

- * Radio navigation aids — ILS, VOR, DME.
- * HF, VHF and UHF radio and line communications for civil and military aviation.
- * Primary and/or secondary radar systems for airfield control, terminal and long range applications.
- * Computerised data handling systems for radar display, automatic message switching and meteorological applications.

Salary will be in the range of £8,500 to £11,500 commensurate with experience.

Apply to the Senior Recruitment Officer, IAL, Aeradio House, Hayes Road, Southall, Middlesex, UB2 5NJ. Tel. 01-574 5134. Please quote Ref. K120.



THE HIGH TECHNOLOGY TASK FORCE
 AVIATION SYSTEMS AND SERVICES
 MEDICAL SERVICES
 COMPUTER SYSTEMS AND SERVICES
 COMMUNICATIONS SYSTEMS - WORLDWIDE

(2219)

RADIO ENGINEER : LATIN AMERICA

To work as a technical adviser with a Latin-American organisation for education by radio, with 40 affiliated radio stations in 17 countries.

The engineer will initially be based in Quito, Ecuador, and will later travel to radio stations in other countries. The job consists of planning and running training courses for local technicians in maintenance of mainly small, short- and medium-wave transmitters, aeriels and studios.

Applicants should have radio engineering experience, gained in a broadcasting environment; the post will demand skills in training people with non-technical backgrounds and in planning and improvising equipment. Spanish speakers especially welcome, but language training can be provided.

The post is initially for three years on a basic salary. Because of extensive travel, it is unlikely to suit applicants with families. CIIR will provide orientation and language training, insurance, air fares and various allowances.

For a job description and application form, please send a brief c.v. to CIIR Overseas Programme, 22 Coleman Fields, London N1 7AF, quoting Ref. WW3.

(2212)

BOX NOS.

Box number replies should be addressed to:

Box No.
 c/o Wireless World
 Quadrant House
 The Quadrant
 Sutton, Surrey, SM2 5AS

BORED ?

Then change your job!

1) Video/TV Equipment

Field Service Engineers required with experience of analogue/digital/computer based equipment. £9-£10,000 - Hants

2) Microprocessor-based Control Systems

Commissioning/Service Engineers required. To £8,500 - Sussex

3) Computer Peripherals

Service Engineers to repair complex PCBs for terminals, printers, disc drives, etc. C. £8,000 - Surrey

4) Video/CC TV/Audio Equipment

Installation/Service Engineers needed with experience of audio/video systems. C. £9,000 - Surrey

5) Service Personnel

(RAF, RN, Army)

We have many clients interested in employing ex-service fitters and technicians at sites throughout the UK. Phone for details.

6) £500 per week

We are paying very high rates for contract design and test engineers who have a background in RF, MICROWAVE, DIGITAL, ANALOGUE or SOFTWARE, at sites throughout the UK.

Hundreds of other Electronic and Computer Vacancies to £12,500

Phone or write:

Roger Howard, C.Eng.,
 M.I.E.E., M.I.E.R.E.

CLIVEDEN CONSULTANTS

87 St. Leonard's Road, Windsor, Berks.
 Windsor (07535) 58022 (5 lines)

(1640)

CLIVEDEN

Hammersmith and Fulham Health Authority

CHARING CROSS HOSPITAL

SENIOR CHIEF TECHNICIAN

Salary scale: £9898-£11,395 p.a. inclusive

An appointment exists in this modern teaching hospital, which carries responsibility for the day-to-day administration of the technical staff in the Medical Electronics Department.

The main duties are associated with medical equipment management which includes maintenance, electrical safety testing and evaluation of new equipment. Extensive use is made of a minicomputer for record keeping and work scheduling.

Applicants should have considerable experience of electronic equipment and preferably have experience of running an equipment maintenance section. The successful applicant will probably have a degree, HNC or HND in Electronic Engineering and will be appointed on the Medical Physics Technician I scale.

Application form and job description from the Unit Personnel Dept, Brandenburgh House, 116 Fulham Palace Road, London W6. Tel: 01-748 2040, ext 2992.

Closing date: 14 September, 1983.
 (2225)



Over the past ten years we have become one of the country's foremost leaders in the field of audio pre and power amplifier modules. We now wish to extend the existing range together with launching new and unassociated products. In order to fulfil this expansion programme, our Research and Development Department have the following vacancies:

AUDIO ENGINEER

The successful applicant must have previous experience in the Hi-Fi field and will be required to tackle all aspects of design, development and preproduction of new products (from conception through to launch).

Salary: Negotiable.

R.F. ENGINEER

We require an R.F. Engineer to be involved in a number of new and interesting projects. Suitable applicants are expected to be qualified to degree level and have some relevant experience in the design of low-power R.F. transmission and receiver circuitry from VHF upwards.

Salary: Negotiable.

Apply in first instance with full c.v. to: Mrs. Johnson, Personnel Manageress, ILP Electronics Limited, Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.

(2213)

PHONE
 YOUR CLASSIFIEDS TO
 IAN FAUX ON
 01-661 3033

Test Engineers and Technicians -Wembley, Middlesex

Racal-BCC are members of the highly successful Racal Electronics Group and are world leaders in the design and manufacture of tactical radio communications equipment. We require a number of test technicians and test engineers to fill a variety of grades within the Test Department on both the day and night shift. The department is responsible for the manual and automatic testing and

fault finding of the Company's equipments at various stages of manufacture.

Applicants should be qualified to HNC/HTC level and have experience of radio communications equipment.

We offer excellent conditions of service including good basic pay and all the benefits you would expect from an internationally successful company.



Please apply in writing to:
Mr. A. Charman,
The Personnel Officer,
Racal-BCC, South Way,
Wembley, Middlesex.

Racal-BCC

RACAL

World leaders in electronics

(2217)

drake

Philip Drake Electronics Ltd is a growing, successful company that has established itself as a leading supplier of studio communications equipment, programme quality sound distribution modules and special "one off" designs to the Broadcast Industry.

Our continuing expansion has led to a requirement for bigger premises and we are moving from London to Welwyn Garden City in the autumn of this year. We are looking for suitable people to fill the following positions which have become vacant or are being created to handle our increasing business.

As well as attractive salaries, the Company offers a pension scheme and BUPA membership and the new premises being constructed at Welwyn Garden City will provide a pleasant working environment when completed.

SALES MANAGER

A manager with proven sales experience in the broadcast field and/or sales management experience of professional capital products is required. An engineering background is desirable for handling quotations and customer's enquiries.

The manager is responsible for the efficient running of the sales department including control of staffing, preparation and monitoring of department budgets, monitoring of quotation and invoice procedures and direct involvement with customer visits, preparation of quotations, and checking of quotation output from the department.

The manager will also be involved with exhibitions, and sales literature in collaboration with the marketing manager. Applicants must possess a clean driving licence.

SALES ENGINEERS

The Sales Department requires extra staff to cope with the increasing amount of work. The department is involved in defining customers' requirements, preparing quotations, order acknowledgements, invoices, securing sales and briefing projects engineers on new orders. Experienced staff handle all aspects of the work but we would consider applicants with only quotation experience or sales experience who are able to progress to fulfilling the complete task. An electronic engineering qualification would be an advantage.

WIREMEN

We require wiremen/women able to interpret circuit diagrams and wiring schedules and with a minimum of construction detail to build and wire control panels, racks and bays neatly and quickly to a high standard. Good references are essential but those wishing to work under contract need not apply.

PROJECTS ENGINEER

An additional engineer is required to join our projects team. The department deals with system design of talkback and intercom equipment, including software updates of standard microprocessor controlled systems, one-off system designs to customers' requirements, and modifications to customers' audio and control equipment.

The work involves liaison with customer engineers, detailed system design, one-off circuit design, preparation of production and handbook documentation and support for manufacturing and test departments.

Applicants should have a recognised electronic engineering qualification and two years' experience of system/project engineering of professional equipment. Previous experience of systems involving software control would be an advantage but not essential.

TEST ENGINEERS

We are looking for suitably qualified test engineers with probably four to five years' experience in testing analogue (preferably audio) circuits, who will be involved in varied testing, from small batch produced modules to complete communication systems, and who are able and willing to adapt to digital technology as this is introduced to the Company.

PRODUCTION MANAGER

A person with a good background in production is required to manage our wiring shop and to organise the production of metalwork, printed circuit boards and assembly work using subcontractors. The person will also be expected to oversee the introduction of printed circuit assembly in our factory utilising suitable assembly aids including flow soldering equipment.

TRACER/JUNIOR DRAUGHTSMAN

A tracer/junior draughtsman is required to assist engineers with system designs. The work involves close liaison with engineers and production staff and production of metalwork, circuit and wiring drawings for both manufacturing and customer documentation. The ideal applicant would be self-motivated and capable of adding finer details to the work passed on by the engineer. The work is interesting and challenging and provides scope for advancement as experience is gained.

TEST DEPARTMENT MANAGER

A suitably qualified person with a successful record in testing both analogue and digital equipment is invited to take on the full responsibility of running this department. As well as scheduling and controlling the work of a small team of test engineers, the successful applicant will be required to design test methods and jigs, maintain test records and investigate the introduction of ATE to the department.

AUDIO ENGINEERS

We have vacancies for experienced audio engineers to join our Development Department. Candidates should have a relevant degree and will probably have worked in a design environment. The person will be responsible for all aspects of development from initial concept to production, and will therefore become involved in a variety of tasks. An ability to produce innovative but practical designs with minimum supervision is essential.

All posts are open to men and women. Successful applicants may be asked to work at our London premises until we move to Welwyn Garden City at the end of September, but this is not an essential requirement.

Applications in writing and including an up-to-date CV should be addressed to The Personnel Officer, Philip Drake Electronics Ltd., 23 Redan Place, London W2 4SA or phone Jill Humphreys on 01-221 1476 for an application form. Please quote ref: JH5

drake

(2226)

Appointments

Premier international electronics companies – very secure and expanding in London and the south of England – require professional senior staff (including departmental heads). Relocation allowance up to £3,000.

ELECTRONIC ENGINEERS

Electronic engineers required with degree – H.N.C. – tech. cert. – O.N.C. Almost any background required but software and hardware experience will bring salary of absolute minimum of £6,500 p.a. and could be up to £11,000 p.a.

ELECTRONIC DESIGN/DEVELOPMENT

Engineers required with experience of circuit or component design or development for microwave equipment or digital logic or computer peripherals or electronic packaging or film technology or telecommunications. Also above for updating in modern techniques. Salaries up to £15,000.

SOFTWARE PROGRAMMERS & ENGINEERS

Engineers or mathematicians required for development of commissioning and design proving programmes from assistant to team leader level. Salaries up to £12,000 p.a.

Please contact by telephone, or letter, to discuss companies and possibilities. Watford 49456 anytime.

(2146)

GORE MANAGEMENT SERVICES LTD

SELECTION & TRAINING CONSULTANTS
218 St Albans Road, Watford, Herts.
Tel: Watford 49456

TELECOMMUNICATIONS/ SEMI-CONDUCTOR

Advanced Engineering Applications to £14K + Car + Profit Share Home Counties

The progress of the electronic revolution is now heavily dependent on the interfacing of real world analog signals to digital processing. The complexities of current and future LSI circuitry demands highly sophisticated computer controlled AUTOMATIC TEST EQUIPMENT in all phases of design and manufacture.

Our Client, an established world leader in LSI Test Systems has created exciting career opportunities for 2 talented Engineers to contribute to their success in taking responsibility for the complete application support of an interesting and varied client base.

You will ideally

- Be currently employed in the Telecommunication or Semi-Conductor industries.
- Be performing a Design/Testing or Applications role.
- Be experienced with Digital Signal Processing, Digital/Analog LSI circuits and/or Testing techniques.

A high degree of customer contact providing consultancy advice on future applications and problem solving demands good presentation, communication and organizational abilities.

The benefits include 3 months product training in the U.K. and U.S.A.; a full relocation package where necessary; company car with petrol expenses; company profit share and share purchase plan; 23 days holiday; family BUPA and Life Assurance.

For an initial confidential discussion please telephone Bob Rae or write to him in strict confidence to: –

ARCHIBOLD RAE CONSULTANTS LIMITED.
(High Technology Search and Selection)
7, London Road, Newbury, Berkshire.
Tel: Newbury (0635) 33445.

(2240)

BRIGHTON POLYTECHNIC Learning Resources VIDEO RECORDING & STUDIO ENGINEER £9,060-£10,539

Urgently required to join an experienced and enthusiastic team making educational training and distance learning video and audio programmes. The standard is high (mastering on 1" C-Format) and the variety wide (studio, mobile and V.T. editing).

Further details and application forms from the Deputy Head of Personnel, Brighton Polytechnic, Moulscroomb, Brighton BN2 4AT. Tel: Brighton 693655 Ext. 2536. Closing date, 16th September.

(2229)

UNIVERSITY COLLEGE CARDIFF
Department of Physiology

ASSISTANT EXPERIMENTAL OFFICER/EXPERIMENTAL OFFICER

The department, which has an active neuroscience-based research programme, requires a person with design experience to work in collaboration with the academic staff in the development and maintenance of equipment for research laboratories. Degree in electronics an advantage. This post offers a challenging opportunity for those interested in developing the latest electronic technology in a biomedical environment.

Salary range: OR IB £6,310-£9,875/£10,250-£11,615 p.a. Duties to commence as soon as possible.

Applications (two copies), together with the names and addresses of two referees, should be forwarded to the Vice-Principal (Administration) and Registrar, University College, P.O. Box 78, Cardiff CF1 1XL from whom further particulars may be obtained. Closing date 14th September, 1983. Ref: 2660.

(2232)

BUSINESS OPPORTUNITIES

FOR SALE

Complete
Tube Rebuilding Plant
including automated ovens
Training available

All enquiries Box No. 2237

FIELD SERVICE ENGINEER

LKB Instruments Limited, the UK subsidiary of a major international scientific instrument company, require an additional Field Service Engineer for their Customer Service Department.

Applicants should have a sound knowledge of digital and analogue electronics, preferably with some field experience in the scientific industry.

The work entails the repair and maintenance of instruments situated mainly in Hospitals and University Laboratories. Preference will be given to applicants living between Glasgow and Edinburgh.

Conditions of employment are excellent and in addition to a good basic salary and company car, the company have a profit sharing scheme, BUPA participation and four weeks' annual holiday.

Contact Mrs D. Duff for application forms



LKB INSTRUMENTS LIMITED
232 Addington Road
Selsdon, South Croydon
Surrey CR2 8YD

Tel: 01-651 5313

(2233)

*The Royal Marsden Hospital
Fulham Road, London, S.W.3*

Medical Physics Technician IV

required to work in the Physics and Radiotherapy departments. The successful applicant will form part of a team maintaining and servicing an interesting variety of radiotherapy equipment. The department has three Cobalt treatment machines, 150kV and 300 kV X-ray units, a Philips 10MV linear accelerator and a simulator. Current developments include the installation of a Philips 5MV linear accelerator and a caesium Selectron unit.

Applicants should possess two A levels or equivalent in appropriate scientific subjects and have three years' relevant technical experience.

Salary on scale £6,168 to £7,795 p.a.

Application forms and job descriptions available from the Personnel Department (Tel. No. 01-352 8171, extension 446-447). (2211)

LINEAR ACCELERATORS FIELD SERVICE ENGINEER

T.E.M. Instruments Ltd. require an electronics engineer with some mechanical knowledge and experience in installing and servicing clinical linear accelerators.

The Engineer will also be expected to work on T.E.M. simulators and cobalt units. Training will be provided.

The company offers a good basic salary, paid overtime, a company car, expenses and pension scheme.

Applications and C.V. in writing to the service manager

T.E.M. INSTRUMENTS LTD.
Gatwick Road, Crawley
West Sussex RH10 2RG

(2241)

Video Engineer Dorking

We have an immediate vacancy for a video engineer to work under the supervision of the Television Technical Supervisor at our Video Unit in Dorking. Applicants should have experience in the operation and maintenance of a wide range of colour television equipment, including broadcast cameras and recorders, and qualifications should include ONC or equivalent. A clean driving licence is essential.

Commencing remuneration will be in the region of £8,400, together with a non-contributory pension scheme, and the usual fringe benefits associated with a major clearing Bank. The successful candidate will be an important member of a small team working in a progressive and stimulating environment.

Please apply in writing, giving details of age, education, technical qualifications and practical experience, to:-

J. M. White, Esq.
Manager, Group Video,
Midland Bank plc.,
Vidcom House,
138 South Street,
Dorking, Surrey
RH4 2EU.



Midland Bank (2234)

HUNTINGDON HEALTH AUTHORITY

The new Hinchingsbrooke Hospital, situated in Huntingdon is currently being commissioned and will open for inpatients during the Autumn. The new Bio-Medical Equipment Support Unit requires the following staff:

Technician-in-Charge (MPT I)

To be responsible for the day-to-day control of this unit, which provides the full range of Technical Service Support for Anaesthetics, Electro-Medical and associated equipment.

Medical Physics Technician (MPT II)

For service support for Anaesthetics, Oxygen Therapy and providing first line instruments - mechanical support for a wide range of equipment.

Salary scales: MPT I - £8,901-£10,398 per annum. MPT II - £7,386-£9,212 per annum.

Application forms and job descriptions from District Personnel Officer, District Headquarters, Primrose Lane Hospital, Primrose Lane, Huntingdon, Cambs PE18 6SE. Tel. 0480 50571 ext. 32.

Closing date for applications 5 September 1983.

(2236)

ARTICLES FOR SALE

BRIDGES, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236.

WAVEGUIDE, Flanges and Dishes. All standard sizes and alloys (new material only) from stock. Special sizes to order. Call Earth Stations, 01-228 7876, 22 Howie Street, London SW11 4AR. (2099)

LAMPS AND CABLE. Large amount of lamps and cable for sale - all types and sizes, domestic and industrial. Telephone MIRAGE LIGHTING on HITCHIN (0462) 733388 between 10am-7pm. (1809)

Analogue integrated circuit design on a single chip. Phone Four-D Limited on 0279-29246. 2159

MARINE FIELD/BRANCH/SERVICE/INSTALLATION ELECTRONIC ENGINEER required. Must be familiar with communication, telex, radar, autopilot, gyro, SAT-NAV equipment, etc. and have practical experience. Should be based in or near London. Apply in writing to Ms B. A. Barnard, Telesonic Marine Ltd, 60/62 Brunswick Centre, Marchmont Street, London WC1. (2235)

ENCAPSULATING EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regunning metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC.

LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.

ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE

TELEPHONE: 445 0749/445 2713

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, North Finchley, London, N.12

(5 minutes from Tally Ho Corner)

(1613)

24 COLUMN PRINTER ONLY £69 EACH (Inclusive)

Standard 4-inch 3U mounting; inverted 4 double sized print; single 9V AC or 5V DC power supply; standard electronics interface or serial data; extends only 40mm behind panel.

For further details contact:
Benwick Electronics
9 Doddington Road, Benwick
nr March, Cambs, PE15 0UX
Telephone: Benwick (035477) 471

THE SCIENTIFIC WIRE COMPANY

811 Forest Rd, London, E17. Tel. 01-531 0574

SWG	ENAMELLED COPPER WIRE			
	1lb	8oz	4oz	2oz
8 to 34	£3.83	£2.09	£1.10	£0.68
35 to 39	£3.82	£2.31	£1.27	£0.83
40 to 43	£6.00	£3.20	£2.25	£1.61
44 to 47	£8.67	£5.80	£3.49	£2.75
48	£15.96	£9.58	£6.38	£3.69

14 to 30	SILVER PLATED COPPER WIRE			
	£9.09	£5.20	£2.93	£1.97
14 to 30	£3.97	£2.41	£1.39	£0.94

Fluxcore Solder	TINNED COPPER WIRE			
	£5.90	£3.25	£1.82	£0.94
Fluxcore Solder	£3.97	£2.41	£1.39	£0.94

Prices include P.P. and VAT. Orders under £2 add 20p. S.a.e. for list of copper and resistance wire. Dealer enquiries welcome (9063)



1/4w 1% Metal Film pack of 10. 0-30p
1/2w 5% Carbon pack of 10. 0-20p
1/4w 5% Carbon pack of 10. 0-10p
400mw Diodes 50v-1000v
pack of 5. 0-35p
please add 30p. p+p + 15% vat

other components always available

Brook House, Cranbrook Rd,
Hawkhurst, Kent. 05805 3816 (2220)

EDWARDS HI-VAC ROTARY PUMP & DIFFUSION PUMP £138

Single to 3-phase converter and idler/stabiliser motor £150. Portable Arc welder, blower cooled, special for thin sections £35. 25 Micron filter/separators £10. Centrifuge £49. Rotary burette £20. Pye 200,000 Megohmmeter £45. Zenity phase-shift transformer £49. Sullivan Decade Mica Capacitor total 1uF £45. Sullivan Mirror Galvanometer £35. Intertechnique 4-channel digital recorder £75. Weston Electrodynamicometer £25. Peekel micro-strain gauge apparatus £59. Spemby Thermocouple Thermometer Cr/Al, Fe/Con, Cu/Con, mV, etc. £35. Industrial Microscope £98. Tacussel PRT 20-2 £75. Crompton Parkinson KW Meter £39, etc.

040 376236

(2016)

LINSLEY HOOD DESIGNS

75Watt and 100W amps
Audio Signal Generators

75Watt amp p.c.b. £2.30
100Watt Mosfet p.c.b. £4.00

p&p 50p

S.A.E. for leaflets

TELERADIO ELECTRONICS
325 Fore Street, London N9 0PE

(1762)

EX WD Radio equipment and test equipment. Over 500 sets in stock from £8. Send 50p for illustrated catalogue (including £1 voucher). Weirhead Ltd. 129 St. Albans Road, Watford, Herts. Tel: Watford (0923) 49456. (1974)

FORTY-FIVE HEWLETT PACKARD 5080-9747 8k by 16 bit Memory Boards for sale. Each board contains 34 tms 4030 ram ICs plus many support components. Untested. £5 each, or offer for the lot. Contact J. Mathews. Tel: Windsor 69595. (2228)

RACAL COMMUNICATION RECEIVERS

500kc/s to 30mc/s in 30 bands 1mc/s wide. RA17 MK11 £100, RA17E £150, RA17E £225. New metal locked cases for above £25 each. All receivers are air tested and calibrated in our workshop. Supplied with manual and dust cover, in fair used condition. RACAL SYNTHESISERS (Decade frequency generator) MA350B Solid state for use with MA75 - RA17 - RA217 - RA1217 ETC. £100 to £150. MA250 1.6mc/s to 31.6mc/s £100 to £150. MA250G PRECISION FREQUENCY STANDARD 5mc/s, 1mc/s 100kHz £100 to £150. EDDYSTONE RECEIVER TYPE EC364/7K Solid state, single channel, SSB, mains or battery powered, 1.8 to 27.5mc/s and 400, 535kHz £100 with manual. REDIFON SSB RECEIVER TYPE RA99 Solid state, 10 fixed channels, range 1.5 to 30mc/s and 25kHz to 525kHz, power mains or battery, complete with ISB adaptor ARU10A, £100 with manual. REDIFON TT11 AUDIO TELEPRINTER CONVERTOR Solid state, tested with circuit £25. CREED TYPE 75 TELEPRINTER 50 and 75 bauds for use with above converter £25.

OSCILLOSCOPES

COSDOR COU150 35mc/s, twin beam, solid state £195 with manual. TEKTRONIX 422 Solid state, portable with internal battery pack, 15mc/s, dual trace £350. CT436 DUAL BEAM Oscilloscope, 6mc/s £75. TEKTRONIX 6A7A 100mc/s, dual trace, solid state £350 with manual. MAR-CDNI TF995 SIGNAL GENERATORS From 2mc/s or 1.5mc/s to 220mc/s. AM-FM. AZM £100, AJ £100, AS £150, BS £250 with manuals. TF2005R Two tone signal source audio £150. TF2606 DIFFERENTIAL OC VOLT METER 0 to 1100 volts £100. TF2002 AM SIGNAL GENERATOR 10kc/s to 72mc/s £400. TF2002AS FM and AM signal generator, 10kc/s to 72mc/s - £600. TF2127B DIGITAL SYNCHRONIZER For above £350. TF1066B 6 FM-AM SIGNAL GENERATOR 10mc/s to 470mc/s £300. TF1245 CIRCUIT MAGNIFICATION METER and TF1246 Oscillator £200. H.P. SIGNAL GENERATOR 620A 7 to 11 gigs £100. H.P. SIGNAL GENERATOR TERMINAL with joystick £1200. TEKTRONIX 4601 Hard copy unit for use with above £450. Both units for £1550. RACAL DIGITAL COUNTERS, TYPE 801M 125mc/s £50. RACAL 836 COUNTER 35mc/s £50.

VAT AND CARRIAGE ON ABOVE ITEMS EXTRA. All items are bought direct from H.M. Government, being surplus equipment. Price is ex works. SAE for all enquiries. Phone for appointment for demonstration of any item. JOHN'S RADIO, WHITEHALL WORKS, 84 WHITEHALL ROAD EAST, BIRKENSHAW, BRADFORD BD11 2ER. TEL: (0274) 684007 (848)

POSITIVE PRE-COATED BOARDS

with plastic protection colours
Any quantity

Single-sided board 5p per sq. in.
Double-sided board 8p per sq. in.
Printed circuits also manufactured

MAYLAND PCB, Maylandsea
Chelmsford, Essex CM3 6AB
Telephone: (0621) 741560 (2231)

VALVES, PROJECTOR Lamps, 6000 types, list 75p, world wide export. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Phone (024 366) 2023. (1991)

OPERATIONAL AMPLIFIER EXPERIMENTAL MANUAL

by G. B. Clayton £3.50

DIGITAL ELECTRONIC
CIRCUITS & SYSTEMS £5.50

by N. M. Morris
ELECTRONIC MUSIC
CIRCUITS £15.00

by B. Klein
THE CATHODE-RAY
OSCILLOSCOPE AND ITS USE £5.50

by G. N. Patchett
VIDEOTAPE RECORDING £14.50

by J. F. Robinson
DOMESTIC VIDEO CASSETTE
RECORDERS £15.00

A SERVICING GUIDE £15.00

by S. Beaching
MICRO COOKBOOK VOL 1:
FUNDAMENTALS £13.50

by D. Lancaster
AN INTRODUCTION TO
MICROCOMPUTERS £10.50

VOL 1: BASIC CONCEPTS £10.50

by A. Osborne
WORLD RADIO TV
HANDBOOK £12.00

by J. Frost
1983 THE RADIO
AMATEUR'S H/B £10.00

by A.R.R.L. £10.00

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

Please allow 14 days for reply or delivery (2023)

SERVICES

CIRCOLEC

THE COMPLETE ELECTRONIC SERVICE

Artwork, Circuit Design, PCB Assembly, Test & Repair Service, Q.A. Consultancy, Prototypes, Final Assembly. Full PCB Flow Soldering Service.

Quality workmanship by professionals at economic prices.

Please telephone 01-646 5686 for advice or further details.

TAMWORTH MANOR

302-310 COMMONSIDE EAST, MITCHAM (1391)

FOR THE BEST PCB SERVICE AVAILABLE

★ Circuit Design & Development
Digital and Analogue

★ Artwork Layout
Work of the highest standard by experienced draughtsmen. No minimum charge.

★ Board Manufacture
Prototype to semi-production, excellent rates. 24-hour prototype service from filmwork.

★ Wiring & Assembly
PCB assembly, wiring and cable forming by qualified staff.

★ Test
Full test facilities available.

One or all services available, no order too small. Please telephone Chelmsford (0245) 357935, or write to HCR Electronics, The Industrial Unit, Parker Road, Chelmsford (1169)



Williams P.C.B. Artworks FAST TURNROUND

Cost effective specialist layout
and master artwork

WILLIAMS ARTWORK
GRAYS LANE MORETON-IN-MARSH, GLOS.
Telephone 3386 840121 - to 9 p.m. (1971)

TURN YOUR SURPLUS Capacitors, transistors, etc. into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. (9509)

SMALL BATCH PCBs, produced from your artwork. also DIALS, PANELS, LABELS. Camera work undertaken. FAST TURNAROUND. Details: Winston Promotions, 9 Hatton Place, London EC1N 8RU. Tel. 01-405 4127/0960. (9797)

BATCH PRODUCTION PCB Assembly and Wiring to drawings or samples production runs or prototype. C.M.J. Electronics, Unit 8, 16 Union Mill Street, Horseley Fields, Wolverhampton WV1 3DN. Tel. (0902) 871563. (2214)

PCBS & PANEL LABELS to your requirements. Design - Prototypes - Production. G. N. Sless Custom Products, 78 Derry Grove, Thruscombe, Rotherham, Yorks SG3 0TP. Telephone (0709) 89525. (1892)

WIRELESS WORLD SEPTEMBER 1983



Private enquiries, send 13p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY 01-942 0334 & 2988

(8493)

G3BXI 50ft MAST

Telescopic, tiltover, ground-post, assembly manual, £250
Ready for collection

Eric Dowdeswell, G4AR
Ashtead, Surrey

Tel: 72515 or 01-661 3604 (2238)

Crotech Oscilloscopes Nationwide availability local to You

London & Home Counties

Audio Electronics	London W2	01-724-3564
Carston Electronics	London N1	01-267-5311
Kentwood Electronics	Reading	0734-698040
Precision Instrument Laboratories	London SE15	01-639-4461

Wales & West

Glevum Instruments	Gloucester	0452-31620
--------------------	------------	------------

East Anglia
Electronic & Computer
Workshop
Maplin Electronics
Ambit International

Chelmsford	0245-62149
Rayleigh	0702-552911
Brentwood	0277-230909

Midlands & North

Northern Instruments	Leeds	0532-791054
Universal Instruments	Leire (Leics)	0455-202391
Electronic Measurement Services	Manchester	061-273-4653
Radio Telephone Service	Derby	0332-41235

Scotland

RMR Measurements	Cumbernauld	02367-28170
------------------	-------------	-------------



Crotech Instruments Limited

5 Nimrod Way · Elgar Road · Reading · Berkshire · RG2 0EB
Telephone: (0734) 866945 Telex: 847073 POWLIN G

WW - 032 FOR FURTHER DETAILS

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 93-103

PAGE		PAGE	PAGE
Aero Electronics (AEL) Ltd	86	Farnell Instruments Ltd	Cover ii
Amateur Radio Retailers Association	4	Fieldtech Heathrow Ltd	20, 75
Ambit International Ltd	80	Fylde Electronic Laboratories Ltd	3
Anders Electronics Ltd	17	GP Industrial Electronics	Cover iii, Cover iv
Armon Electronics Ltd	78	Greatch Electronics Ltd	12
Aspen Electronics Ltd	12	Griftronic Emission Ltd	78
Audio Electronics (Cubegate Ltd)	13	Harris Electronics (London) Ltd	7
Bamber, B. Electronics	89	Harrison Bros Electrical Distributors	9
Black Star Ltd	2	Hart Electronic Kits Ltd	86
Broadfields & Mayco Disposals	75	Hemmings Electronics and Microcomputers	19
Cambridge Kits	12	House of Instruments	81
Circuit Services	17	ILP Electronics Ltd	7, 10, 11
Clef Products (Electronics) Ltd	18	Integrex Ltd	88
Control Universal Ltd	78	Keithley Instruments Ltd	19
Cricklewood Electronics Ltd	87	Langrex Supplies Ltd	16
Crimson Elektrik Stoke	15	Levell Electronics Ltd	88
Crotech Instruments Ltd	104	Macdonald & Co (Publishers) Ltd	84
Display Electronics Ltd	91	Microwave Modules Ltd	5, 17
Easibind	6	Midwich Computer Co Ltd	9
Eddystone Radio Ltd	20	Monolith Electronics Co Ltd	15
Electrical Review Shock Cards	92	Nova Products (APB) Ltd	2
Electronic Brokers Ltd	3, 5	Opus Supplies	14
Electronic Equipment	84	Orion Scientific Products Ltd	78
Electrovalue Ltd	80	Pantechnic	84
EMS Manufacturing	81	PM Components	76, 77
Essex Electronics Centre	13	Practical Wireless	18
		P&R Computer Shop	2
		Racom Ltd	86
		Radford Laboratory Instruments	18
		Radiocode Clocks Ltd	17
		Radio Component Specialists	79
		Reprints	86
		Research Communications Ltd	2
		Royal Air Force Association (Wings Appeal)	18, 84
		RST Valves	16
		Sandwell Plant Ltd	7
		Sarel Electric Ltd	84
		Scopex Instruments	89
		Skyleader	76
		Solent Electronic Service Ltd	84
		South Midlands Communications Ltd	9
		Special Products Distributors Ltd	3
		Stewart of Reading	6
		Surrey Electronics Ltd	75
		Technomatic Ltd	82, 83
		Thandar Electronics Ltd	85
		Thanet Electronics Ltd	80
		Thorn EMI Instruments	8
		Thurlby Electronics Ltd	75
		Timbase Ltd	76
		TO Supplies (Export) Ltd	6
		Valradio Ltd	5
		Vigilant Communications Ltd	12
		Wireless World Circards	90

OVERSEAS ADVERTISEMENT AGENTS

France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Ms Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget.
Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106.
Telephone: (03) 585 0581.

United States of America: Ray Barnes, Business Press International Ltd, 205 East 42nd Street, New York, NY 10017 -
Telephone (212) 867-2080 - Telex: 238327.

Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone (312) 63074.
Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 -
Telex: 18-1059.


Jack Mantel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone (216) 621 1919.
Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone (404) 237 7432.
Mike Loughlin, Business Press International, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.

Canada: Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
* Also subscription agents.

Printed in Great Britain by QB Ltd, Sheepen Place, Colchester, for the proprietors, Business Press International Ltd, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.
© Business Press International Ltd 1983. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Services Ltd; Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd; William Dawson & Son (SA) Ltd. UNITED STATES: Eastern News Distribution Inc., 14th Floor, 111 Eighth Avenue, New York, NY 10011.

EP8000 EPROM EMULATOR PROGRAMMER

NEW
PRODUCT

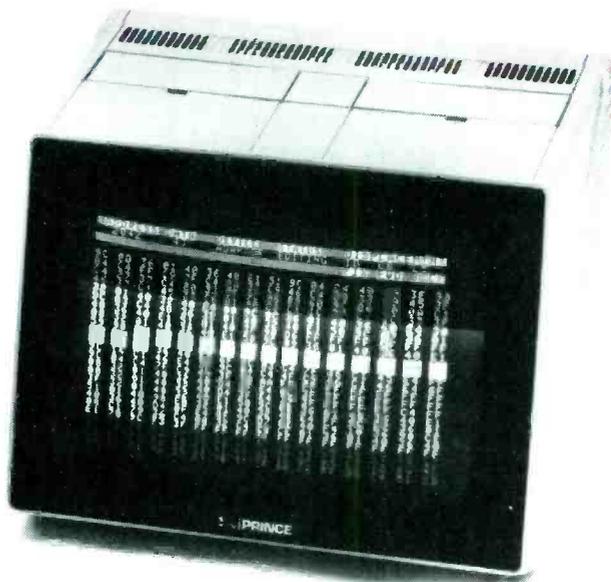

The new microprocessor controlled EP8000 Emulator Programmer will program and emulate all EPROMs up to 8k x 8 sizes, and can be extended to program other devices such as 16k x 8 EPROMs, Bipolar PROMs, single chip microprocessors with external modules.

Personality cards and hardware changes are not required as the machine configures itself for the different devices.

The EP4000 with 4k x 8 static RAM is still available with EPROM programming and emulation capacity up to 4k x 8 sizes.

● EP8000 8k x 8 Emulator Programmer – £695 + £12 delivery ● BSC8 Buffered emulation cable – £49 ● SA27128 Programming adaptor – £69 ● SA25128 Programming adaptor – £69 ● EP4000 4k x 8 Emulator Programmer – £545 + £12 de-

FEATURES

- Software personality programming/emulation of all EPROMs up to 8k x 8 bytes including 2704, 2708, 2716(3), 2508, 2758A, 2758B, 2516, 2716, 2532, 2732, 2732A, 68732-0, 68732-1, 68766, 68764, 2564, 2764. Programs 25128, 27128 with adaptors.
- No personality cards/characterisers required.
- Use as stand alone programmer, slave programmer, or EPROM development system.
- Checks for misplaced and reversed insertion, and shorts on data lines.
- Memory mapped video output allows full use of powerful editing facilities.
- Built-in LED display for field use.
- Powerful editing facilities include: Block/Byte move, insert, delete, match, highlight, etc.
- Comprehensive input/output – RS232C serial port, parallel port, cassette, printer O/P, DMA.
- Extra 1k x 8 scratchpad RAM for block moving.

livery ● BSC4 Buffered emulation cable – £39 ● BP4 (TEXAS) Bipolar PROM Module – £190 ● Prinz video monitor – £99 ● UV141 EPROM Eraser with timer – £78 ● GP100A 80 column printer – £225 ● GR1 Centronics interface – £65

VAT should be added to all prices

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

P8000 — THE PRODUCTION PROGRAMMER THAT HANDLES ALL NMOS EPROMS



**NEW
PRODUCT**

- Checks, Programs, Compares up to 8 devices simultaneously
- Handles all NMOS EPROMS up to projected 128K designs with no personality modules or characterisers — See list
- Easy to use, menu driven operation for blankcheck, program, verify, illegal bit check, checksum, self-test
- Constant display of device type, mode and fault codings
- Individual socket LED indicators for EPROM status
- Comprehensive EPROM integrity checks — Illegal bit check, data and address shorts, constant power line monitoring
- Full safeguard protection on all sockets
- Automatic machine self-test routine
- RS232C interface supplied as standard
- Powered down sockets
- Cost effective price — £695 + VAT
- Available from stock

Write or phone for more details

2704
2708
2716(3)
2508
2758A
2758B
2516
2716
48016
2532
2732
2732A
68732-0
68732-1
68766
68764
2764
2564
MK2764
25128
27128

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN