

ELECTRONICS & Wireless World

May 1985 85p

Enlarging timer

Bench power supplies

Altimeter for microlights

Printer buffer



Australia	AS	3.30	Italy	L	4200
Denmark	DKr.	38.00	Spain	Pts.	370.00
Germany	DM	7.00	Switzerland	SFr.	8.00
Greece	Dra.	24.00	Singapore	MS	7.00
Holland	DFl.	9.00	U.S.A.	\$	4.00

FARNELL 1kW AUTORANGING POWER SUPPLIES

Compact, lightweight and efficient switch mode power supplies

For bench or rack mounting in manual or systems applications

Fast remote programming speed

Autoranging output

Constant voltage, constant current

Operating modes:

- Local or bus control
- Remote programming
- Remote sensing
- Auto parallel
- Auto series
- Auto tracking

Ten turn voltage and current controls

Digital display of voltage, current, over voltage setting and status flags

Bar graph indication of voltage/current capacity

Front panel adjustable over voltage limit

Front panel output enable switch

Current monitoring output

◀ GPIB ▶ option provides:

- Bus control of voltage and current
- Bus measurement of voltage and current
- Clear LED indication of bus control, listen, talk, SRQ

The Programmable AP Series



Get all the details from the colour brochure. Send for your copy now to:



Farnell

FARNELL INSTRUMENTS LIMITED • WETHERBY • WEST YORKSHIRE LS22 4DH • ENGLAND • TEL. (0937) 61961 • TELEX 557294 FARIST G

CIRCLE 1 FOR FURTHER INFORMATION

Two Great Ideas From A.B.I.



NUMBER 1

- ★ OUR UNIQUE DIGITAL IC TESTER WILL TEST OVER 1000 DEVICES FROM TTL, CMOS, MEMORY AND INTERFACE FAMILIES.
- ★ SIMPLE KEYPAD OPERATION MEANS NO NO COMPLEX PROGRAMMING OR SETTING UP.
- ★ "CHIP-SEARCH" FEATURE ALLOWS IDENTIFICATION OF UNKNOWN, UNMARKED OR HOUSE CODED DEVICES.
- ★ PRICES FROM £573.00.

The A.B.I. Digital IC Tester

**SEE US ON
STAND 446 AT THE
ALL ELECTRONICS
SHOW, OLYMPIA
APRIL 30,
MAY 1,2 FOR
THE LAUNCH
OF THIS NEW
PRODUCT**

NUMBER 2

- ★ 16 CHANNELS, 10 MHZ.
- ★ EXTERNAL OR INTERNAL CLOCK WITH TWO QUALIFIER INPUTS.
- ★ 16 BIT TRUE/FALSE LEVEL/EDGE TRIGGER PATTERN SELECTION.
- ★ VARIABLE TRIGGER POSITION.
- ★ STATE (HEXADECIMAL) AND TIMING DISPLAY MODES.
- ★ PRICE, COMPLETE WITH ALL PROBES AND CLIPS – £439.00.

The A.B.I. 16 Channel Logic Analyser

**A.B.I. ELECTRONICS LTD.,
UNIT 21,
ALDHAM INDUSTRIAL ESTATE,
WOMBWELL,
BARNSELY,
SOUTH YORKSHIRE S73 8HA**

**TELEPHONE:
(0226) 751639**

**TELEX:
547376 CEAG G (FOR A.B.I.)**

CIRCLE 72 FOR FURTHER DETAILS.

ELECTRONICS & Wireless World

over 70 years in independent electronics publishing

May 1985

Volume 91 number 1591

FEATURES

21

Printer buffer

by M. Catherwood
General-purpose computer board can be programmed to hold text for printing so that your microcomputer can be freed for other tasks.

27

Channel code and disc format

by J.R. Watkinson
This installment in our Compact Disc series is the first of two covering eight-to-fourteen modulation, eye patterns, sub-codes and error correction.

31

The post-war stride into aerospace

by R.E. Young
Third in an eight-part series that sets out to probe the hidden strengths of Britain's 'total engineering power.'

37

Electronic altimeter

by Frank Ogden
Design uses pressure transducer to act as vertical speed indicator as well as altimeter.

43

Automatic enlarger timer

by J.L. Linsley Hood
Time-consuming use of contact strips is avoided by sensing reflected light from bromide surface.

47

The new logic symbols

by Ian Kampel
Practical aspects of implementing new international standard for logic symbols.
Third and final article gives practical.

59

Look after your sealed nickel-cadmium cells

by Rod Cooper

A rigorous discussion of failure modes with suggestions for avoidance tactics, in two parts.

63

Sampled-data servos — a new analysis

by D.M. Taub
Prior to computing servo performance Dr Taub considers the reverse of the sampling process: conversion from a sampled-data signal to a continuous signal.

67

DC supplies from ac sources

by K.L. Smith
Constructing a stabilized power supply

73

Power supplies

An introduction to bench-type units, with tips for the first-time buyer and a tabulation of what's available.

REGULARS

6

News commentary

A standard for lams?
Alice through the cash nexus
Automatic route planning uses CD
ITEC for the blind
In brief...

13

Communications commentary

17

Feedback

Logic symbols
Campaign for real a.m.
Liquid crystals
DC supplies
Basic physics

24

Events

Round-up of lectures, colloquia, and conferences during May

53

Circuit ideas

Shaft encoder interface
Divide-by-n clock circuit
6800 peripherals with Z80
One-in-n way latch

83

New products

GPIO for Apricot
Low-cost logic analysers
8088 trainer
Bug hunter



Power supplies

Our brief introduction to supply technology is followed by information on a wide range of current bench supplies.

Printer buffer

By taking characters from a microcomputer at high speed and sending them to a printer at its leisure, this buffer reduces waiting time from minutes to seconds. It has parallel and serial ports and holds enough text for around twenty A4 sheets.

by Mike Catherwood



Mike Catherwood is lecturer from North East University in 1980 and an Honorary Degree in Electrical and Electronic Engineering, and has since been working with microprocessors. He is currently Systems Engineer, Engineering Section Manager, East Yorkshire. He is currently working on a small team of people who are developing a new industrial and systems controller. Mike has written his own book on 'Microprocessors' and has also written a book on 'Microprocessors in the Home'.

Avoiding failure of sealed nickel-cadmium cells

Despite using the same basic materials, the life expectancy of sealed nickel-cadmium cells is in stark contrast to that of sealed nickel-cadmium cells in vented type, which have been known to give in excess of 20 years of service life. Premature failure is often a complete mystery to the user. Cooper throws light on the many failure modes, proposes avoidance tactics and suggests experimental cures.

by Rod Cooper

Front cover shows John Linsley Hood's automatic enlarger timer, featured on page 45. Cover design by Phil Brooker; photography by Kenneth Crook.

NEXT MONTH

David Stonebanks shows how to improve performance of cassette recorders with the BBC micro and details an alternative method.

Design for a video camera and computer interface stores eight picture elements from each scan line at a time, reducing the time for storing a picture by a factor of eight.

High-performance helical antenna covers the whole 70cm amateur band though it can be readily adapted for other bands. Using easy-to-obtain parts, it forgives minor inaccuracies and gives true circular polarization.

Circuit ideas include automatic inverter switch-on, easy-to-read hexadecimal display, and over-current trip circuit.

Editor
PHILIP DARRINGTON
01-661 3128

Deputy Editor
GEOFFREY SHORTER, B.Sc.
01-661 8639

Technical Editor
MARTIN ECCLES
01-661 8638

Projects Editor
RICHARD LAMBLEY
01-661 3039 OR 8637

News Editor
DAVID SCOBIE
01-661 8632

Drawing Office Manager
ROGER GOODMAN
01-661 8690

Technical Illustrator
BETTY PALMER

Advertisement Manager
BOB NIBBS, A.C.I.I.
01-661 3130

MICHAEL DOWNING
01-661 8640

ASHLEY WALLIS
01-661 8641

Northern Sales
HARRY AIKEN
061-872 8861

Midland Sales
BASIL MCGOWAN
021-356 4838

Classified Manager
BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production
BRIAN BANNISTER
(Make-up and copy)
01-661 8648

Publishing Director
DAVID MONTGOMERY
01-661 3241

International Agents and the Advertisers Index appear at the back of this issue.

Current issue price 85p, back issues (if available) £1.06, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1, Tel. 01-928 3567. Available on microfilm — please contact editor.

By post, current issue £1.30, back issues (if available) £1.40, order and payments to EEP Sundry Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Tel.: 01-661 3378.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.
Telephones: Editorial 01-661 3614, Advertising 01-661 3130.
Telex: 892084 BISPRSG (EIP)
Facsimile: 01-661 2071 (Groups II & III)
Beeline (300 baud): 01-661 8978 (Type EWW to start, NNNN to end).
Subscription rates: 1 year £15 UK and £19 outside UK.
Student rates: 1 year £10 UK and £12.70 outside UK.
Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3248.
Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone: 0444 59188. Please notify a change of address.
USA: \$49.40 surface mail, \$102.60 airmail. Business Press International (USA), Subscriptions Office, 205 E. 42nd Street, NY 10017.
USA mailing agents: Expeditors of the Printed World Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd class postage paid at New York.
© Business Press International Ltd 1985. ISSN 0043 6062.

BBC Micro Computer System BBC Computer & Econet Referral Centre BBC Computers:

Model B: £299 (a) B+DFS: £346 (a)
Model B+Econet: £335 (a) B+Econet+DFS £399 (a)
ACORN 10 Mbyte Hard Disc £1300 (a)
ACORN 2nd Processors: 6502: £175 (a) Z80: £352 (a)
TORCH UNICORN: Z80 Card: £275 (a) Z80 Disc Pack: £650 (a)
UNICOMM Communications Package: £159 (b)
20 Mbyte Hard Disc+400K Floppy: £1950 (a)

We stock the full range of ACORN hardware and firmware and a very wide range of other peripherals and firmware for the BBC. For detailed specifications and pricing please send for our leaflet.

PRINTERS

EPSON: RX80T £210 (a); RX80FT £220 (a); RX100 £345 (a);
FX80 £315 (a); FX100 £430 (a); KAGA TAXAN: KP810 £255 (a);
KP910 £359 (a) BROTHER: HR15 £340 (a); JUKI 6100 £340 (a).
GRAPHICS PLOTTER WORKSTATION Complete £490 (a)
Basic Plotter £270 (a); HI-Plotter £399 (a)

ACCESSORIES

EPSON Serial Interface: 8143 £28 (b); 8148 with 2K buffer £57 (b).
EPSON Paper Roll Holder £17 (b); FX80 Tractor Attach £37 (b); RX/FX80 Dust Cover £4.50 (d)
EPSON Ribbons: MX/RX/FX80 £5.00; MX/RX/FX100 £10 (d).
JUKI: Serial Interface £65 (c); Tractor Attach, £99 (a); Sheet Feeder £182 (a); Ribbon £2.50 (a)
BROTHER HR15: Sheet Feeder £199; Ribbons — Carbonor Nylon £4.50; Multistrike £5.50 (d);
2000 Sheets Fanfold with extra fine perf. 9.5in. — £13.50; 14.5in. £18.50 (b).
BBC Parallel Lead £8; Serial Lead £7 (d).

BT Approved Modems

MIRACLE WS2000:
The ultimate world standard modem covering all common BELL and CCITT standards up to 1200 Baud. Allows communication with virtually any computer system in the world. The optional AUTO DIAL and AUTO ANSWER boards enhance the considerable facilities already provided on the modem. Mains powered. £129 (c) Auto Dial Board/Auto Answer Board £30 (d) each (awaiting BABT approval).
Software lead £4.50
TELEMOD 2:
Complies with CCITT V23 1200/75 Duplex and 1200/1200 half Duplex standards that allow communications with VIEWDATA services like PRESTEL, MICRONET etc. as well as user to user communications. Mains powered. £62 (b) BUZZBOX:
This pocket sized modem complies with V21 300/300 Baud and provides an ideal solution for communications between users, with main frame computers and bulletin boards at a very economic cost. Battery or mains operated. £52 (c) Mains Adaptor £8 (d) BBC to Modem data lead £7

SOFTY II

This low cost intelligent eeprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface.
Softy II £195.00(b)
Adaptor for 2764/2564 £25.00

ATTENTION

All prices in this double page advertisement are subject to change without notice.

ALL PRICES EXCLUDE VAT
Please add carriage 50p unless indicated as follows:
(a) £8 (b) £2.50 (c) £1.50 (d) £1.00

ACORN IEEE INTERFACE

A full implementation of the IEEE-488 standard, providing computer control of compatible scientific & technical equipment, at a lower price than other systems. Typical applications are in experimental work in academic and industrial laboratories. The interface can support a network of up to 14 other compatible devices, and would typically link several items of test equipment allowing them to run with the optimum of efficiency. The IEEE Filing System ROM is supplied £282.

INDUSTRIAL PROGRAMMER

EP8000.
This CPU controlled Emulator Programmer is a powerful tool for both Eeprom programming and development work. EP8000 can emulate and program all eeproms up to 8Kx8 bytes, can be used as stand alone unit for editing and duplicating EPROMS, as a slave programmer or as an eeprom emulator £695(a)

I.D. CONNECTORS

No of ways	(Speedblock Type)			Edge Conn.
	Header Plug	Receptacle	Edge Conn.	
10	90p	85p	120p	
20	145p	125p	195p	
26	175p	150p	240p	
34	200p	160p	320p	
40	220p	190p	340p	
50	235p	200p	390p	

D CONNECTORS

	No of Ways			
	9	15	25	37
MALE:				
Ang Pins	120	180	230	350
Solder	60	85	125	170
IDC	175	275	325	—
FEMALE:				
St Pin	100	140	210	380
Ang Pins	160	210	275	440
Solder	90	130	195	290
IDC	195	325	375	—
St Hood	90	95	100	120
Screw	130	150	175	—
Lock				

TEXTPOOL ZIF

SOCKETS	24-pin £5.75
	28-pin £8.00
	40-pin £9.75

DISC DRIVES

These drives, fitted with high quality JAPANESE mechanisms are supplied in attractive steel cases painted in BBC colour. The drives are fully Shuggart A4000 compatible. All versions of drives are offered with or without integral power supplies. Power supplies for dual drives are of switch mode type and generously rated. All drives come complete with data & power cables, manual and BBC formatting disc.

Single Drives:
1X100K 40T SS: TS100 £85 (b); PS100 with psu £125 (b)
1X400K 80/40T DS: TS400 £125 (b); PS400 with psu £149 (b)
Dual Drives
Stacked Version:
2X100K 40T SS: TD200 £175 (a); PD200 with psu £200 (a)
2X400K 80/40 DS: TD800 £275 (a); PD800 with psu £300 (a)
Plinth Version:
2X100K 40T SS: TD200P £195 (a); PD200P with psu £220 (a)
2X400K 80T DS: TD800P £295 (a); PD800P with psu £315 (a)

Authorised Distributor Data Recording Products



Industry Standard floppy discs with a lifetime guarantee Discs in packs of 10
40 Track SS DD £15 (c) 40 Track DS DD £18 (c)
80 Track SS DD £22 (c) 80 Track DS DD £24 (c)

DRIVE ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 28 disposable cleaning discs ensures continued optimum performance of the drives. £14.50 (c)

Single Disc Cable £6 (d) Dual Disc Cable £8.50 (d)
10 Disc Library Case £1.80 (d) 30 Disc Storage Box £6 (c)
30/40 Disc Lockable Box £14 (c) 100 Disc Lockable Box £19 (c)

MONITORS

MICROVITEC 14in. & 20in RGB
1431 Std Res £165 (a); 1431 Ap Std Res PAL/Audio £205 (a);
1451 Med Res £240 (a); 1441 Hi Res £389 (a);
2030CS Std Res £380 (a); 2040CS Hi Res £685 (a)
Plinth for 14in. Monitors £8.50.
Microvitec Monitors with TTL/Linear Inputs also available.

KAGA TAXAN 12in. RGB

Vision II Hi Res £225 (a); Vision III Super Hi Res £325 (a)
Green Screens; KAGA 12G £99 (a); SANYO DM811 112CX £90 (a);
Swivel Stand for Kaga Green £21 (c)
BBC Leads: KAGA RGB £5 Microvitec £3.50; Monochrome £3.50 (d)
SANYO CD 3125 NB 14in. RGB Std Res £169 (a)

UV ERASERS

UV1T Eraser with built-in timer and mains indicator.
Built-in safety interlock to avoid accidental exposure to the harmful UV rays.
It can handle up to 5 eeproms at a time with an average erasing time of about 20 mins. £59 + £2 p&p.
UV1 as above but without the timer. £47 + £2 p&p.
For Industrial Users, we offer UV140 & UV141 erasers with handling capacity of 14 eeproms. UV141 has a built in timer. Both offer full built in safety features
UV140 £61, UV141 £79, p&p £2.50.

PRINTER BUFFER

This printer shaver/buffer provides a simple way to upgrade a multiple computer system by providing greater utilisation of available resources. The buffer offers a storage of 64K. Data from three computers can be loaded into the buffer which will continue accepting data until it is full. The buffer will automatically switch from one computer to next as soon as that computer has dumped all its data. The computer then is available for other uses. LED bargraph indicates memory usage. Simple push button control provides. REPEAT, PAUSE and RESET functions. Integral power supply. £245 (a)
Cable set £30

CONNECTOR SYSTEMS

EDGE CONNECTORS

2 x 6-way (commodore)	0.1" 0.156	—	300p
2 x 10-way	—	150p	—
2 x 12-way (vic 20)	—	350p	—
2 x 18-way	—	140p	—
2 x 23-way (ZX81)	—	175p	220p
2 x 25-way	—	225p	220p
2 x 28-way (Spectrum)	—	200p	—
2 x 36-way	—	250p	—
1 x 43-way	—	260p	—
2 x 22-way	—	190p	—
2 x 43-way	—	395p	—
1 x 77-way	—	400p	500p
2 x 50-way (S100conn)	—	600p	—

EURO CONNECTORS

DIN 41612			
2 x 32 way St Pin	230p	275p	
2 x 32 way Ang Pin	275p	320p	
3 x 32 way St Pin	260p	300p	
3 x 32 way Ang Pin	375p	400p	
IDC Skt A + B	425p		
IDC Skt A + C	425p		

For 2 x 32 way please specify spacing (A + B, A + C).

AMPHENOL CONNECTORS

36 way plug Centronics (solder) 500p (IDC) 475p
36 way skt Centronics (solder) 550p (IDC) 500p
24 way plug IEEE (solder) 475p (IDC) 475p
24 way skt IEEE (solder) 500p (IDC) 500p
PCB Mtg Skt Ang Pin
24 way 700p 36 way 750p

GENERATOR CHANGERS

25 way D type
Male to Male £10
Male to Female £10
Female to Female £10

RS 232 JUMPERS

(25 way D)
24 Single end Male £5.00
24 Single end Female £5.25
24 Female Female £10.00
24 Male Male £9.50
24 Male Female £9.50

DIL SWITCHES

4-way 90p 6-way 105p
8-way 120p 10-way 150p

TELEPHONE CONNECTORS

4-way plug 110p
6-way plug 180p
6-way rt ang skt 160p
Flexible cable
4-way 50p/m
6-way 72p/m

RIBBON CABLE

(grey/metre)
10-way 40p 34-way 160p
16-way 60p 40-way 180p
20-way 85p 50-way 200p
26-way 120p 64-way 280p

DIL HEADERS

14 pin	Solder	IDC
16 pin	40p	100p
18 pin	50p	110p
20 pin	60p	—
24 pin	75p	—
24 pin	100p	150p
28 pin	200p	—
40 pin	200p	225p

MISC CONNS

21 pin Scart Connector 200p
8 pin Video Connector 200p

Alice through the cash nexus

Money is extremely useful as a measure of market value in the exchange of goods and services but becomes tyrannical when used to exert power over people. The present UK government has raised the power of money to a new height, both in their technical use of monetarist economics and in the way they seem to attribute an almost mystical essence to that rationale of human greed known as market forces.

Two recent proposals illustrate the fact that almost anything can be sold. In the past men have traded their wives, their children and their honour. Now, in the field of radio communication we are facing the prospect of two new commodities being brought out of the grocer's store-cupboard to be added to the list of things available over the counter. One is a natural resource, the

electromagnetic spectrum; the other a mass-medium, public service broadcasting.

Recent debates on financing the BBC have made it quite clear that a good many politicians are willing to abandon the central principle of public service broadcasting. They are saying it would make good sense for the BBC to obtain at least some of its income by taking advertising.

Most of the discussion around this possibility seems only to have considered matters of expediency. It has largely ignored a central point about public service broadcasting. If we agree that sound and television broadcasting in the UK has reached a level of proficiency in all departments (news, entertainment, arts, education etc.) that makes it a really valuable contributor to our culture, then we should do it the honour of being ready to

pay for a substantial part of it directly — like books, music, theatre, films — either through licence fees or equivalent methods.

Commercial broadcasting, though capable of producing excellent programmes, is vitiated by its dual function. It cannot escape the fact that advertisers are only interested in it as a medium for selling. And unquestionably this pressure distorts its general character. Ask Michael Grade, for example, the new Controller of BBC 1, who used to work in commercial television.

As for the electromagnetic spectrum, the Government has commissioned a firm of management consultants to do a feasibility study of pricing the spectrum. They have made no policy decision yet, but want a technical and economic analysis of what would be the effects of pricing if used as a means of

assigning frequencies when demand exceeds supply.

The mere fact that the Government is even considering such a measure must be thoroughly condemned, on two counts. Both are matters of principle. First, the e-m spectrum is a free natural resource, not a property owned by anybody, even the state, and is therefore not available for sale. To commandeer this resource would be an offensive and dictatorial action, not worthy of a government which is always prating about freedom.

Secondly, the expedient of leaving the distribution of spectrum space to the mechanism of market forces is a cop-out. It avoids the responsibility of having to make difficult political decisions on the relative social worth of different claims for frequencies. One cannot respect a government which even entertains the notion that technical expediency could be a substitute for political responsibility.

British lan agreement

A number of British computer manufacturers have agreed on a standard for local area networks and many others seem likely to follow suit. This follows a feasibility study commissioned by the British Microcomputer Manufacturing Group in conjunction with the DTI and in consultation with the BSI.

Concerned about the existence of a great number of micro network designs in the market, the BMMG were afraid that the lack of common standards and the resulting confusion of incompatible systems would discourage potential users and undermine their own credibility. Another danger was the possibility of one major manufacturer (IBM) producing a design which would dominate the market to the disadvantage of both users and other manufacturers. A year ago they set out a programme to identify, design, specify and encourage the adoption of a local area network standard that would be accepted by UK manufacturers and users, and

promoted as a British and International Standard.

The report was undertaken by Dr Chris Shelton, a member of BMMG, acting as consultant and involved interviewing all the manufacturing members of BMMG as well as a number of users to identify their needs. He needed to define a 'local area network' and define its functional parameters and their compatibility with the Open System Interconnection (OSI) protocol standard of the ISO.

The report, which took ten months in preparation, has now been published. The recommendations are presented in an ordered sequence for implementation. The main point is the adoption of a low-cost scheme that would lead to the final goal of a full OSI environment. The implementation of each phase "creates the opportunity to advance to the next."

Phase one is concerned with the hardware and is the easiest part of the scheme to implement. Existing l.a.n.s were

varied chiefly because there was no standard when their development started and off the shelf systems were too expensive. One system Arcnet was preferred by many because of its high degree of integration; just two i.cs and a hybrid that includes medium access control (m.a.c.) firmware. However the report rejects all existing l.a.n.s because of the high licence fees associated with proprietary designs; the components may not be multi-sourced; may not be readily applied to different microprocessor bus systems; the proprietary interest may preclude the adoption of a system as a standard and the originator may not be prepared to publish sufficient detail to enable the l.a.n. to be specified as a standard.

The hardware recommendations derived from a study of existing systems and the needs of users are: compatible speed options of 250, 500, 1000, and 2000Kb/s; operation over a distance of 1km. To be connected through low-cost 75Ω coaxial cable. Connectors should be BNC (or DIN for the slowest speed); interconnection should be bus based though this could be arranged in a star; no

repeaters or active elements in the cable which is to be isolated through transformers. RS422 signal level. The signal can be modulated using m.f.m. or Manchester to take advantage of new l.s.i. devices such as the AMD 7960. Various options are presented for the implementation of the interface hardware.

The cheapest, at £10-worth of semiconductors consists of an h.d.l.c. device within the clock, modem and driver receiver circuits. This puts the l.a.n. with the budget of the low-cost microcomputers but the software responses of such devices may limit the line speed to 250Kb/s. For a silicon price of about £25, it would be possible to offload the l.a.n. support onto a co-processor and the l.a.n. could operate at up to 1Mb/s. For £10 more, a direct memory access chip could be added and the performance could be extended to 2Mb/s. At the conclusion of phase 1 manufacturers would have plug-compatible hardware. The report recommends the adoption of these hardware standards or find an existing system, such as V-Net or Strathnet, neither of which are adequately documented, which are potentially available for

unrestricted use.

Phase two is the adoption of an interim software standard so that a useful product can be achieved as soon as possible. The report suggests that the Digital Research DR-Net which will communicate with concurrent DOS is suitable because of its wide use, this incorporates a m.a.c. layer, though for the low-cost micros the m.a.c. layer could be implemented through their own schemes. It is hoped that at the conclusion of this phase different manufacturers' equipment will operate together as a multi-user computer.

Phase three recommends that DR-Net be replaced by OSI protocol to enable different operating systems to be used. Dr Shelton admits that the remaining three phases are more tentative and should be taken as suggestions. They are:

4 — To extend the system to a number of other operating systems to ensure its widest use, while also providing the widest scope for software developments to adhere to the standards. 5 — To organize, within this compatible environment, a gateway for connecting this standard of l.a.n. to other standards that may exist, and a gateway to the package switched network. 6 — To cover the longer term of ensuring that application software is developed which can work under this l.a.n. standard.

The BMMG has accepted the report wholeheartedly and at least ten manufacturers have agreed to implement its recommendations. It is thought that with such a kernel many other manufacturers will join the bandwagon to make it a de facto British standard and ultimately a world standard.

Cable news

Geoffrey Pattie, the IT Minister was full of praise for Swindon Cable at a recent visit.

Swindon Cable is the first cable operator to offer new services on a wideband system and they have just scored another first with the introduction of a French tv channel, TVS, to their choice of programmes.

"There have of course been setbacks but this system has demonstrated that they can be overcome. I believe that the cable industry can make a very positive contribution to the prosperity of the country. Cable means investment in new technology and new jobs. It will give this country an advanced broadband infrastructure offering not only entertainment but also new interactive services for businesses and domestic customers.

"We have always taken the view that cable is an industry which should be privately financed but that the Government still has an active

role to play in the future of the industry. We have created the right legal framework and the Cable Authority has announced the first five areas for which it is seeking new applications."

Swindon Cable is a wholly owned subsidiary of Thorn EMI and was one of the eleven initial pilot projects. The five new areas under consideration are Bolton, Cheltenham and Gloucester, West Surrey, and Wandsworth and Tower Hamlets, both in London.

● BT has announced that it has clinched a deal that will allow the direct reception of the American cable tv channel, Cable News Network. The channel will be available to British broadcasting companies from September. Cable news network will be beamed from the headquarters of Turner Broadcasting Systems, in Atlanta to an Intelsat V satellite which is also used to distribute cable tv channels to networks within the UK. British Telecom International also hope to be able to distribute the network to other European countries.



A telephone designed for use in the third world. It is solar powered and communicates by radio, with battery back-up. The equipment can also act as a relay to act as a local link so that remote villages can communicate with each other. Designed by Plessey Radio Systems.

Electronic co-pilot for cars

An electronic system is being developed to provide cars with automatic route planning it knows the position of the car and can specify it at any moment, and can also provide a number of details about the environment or the destination of the journey. The Carin (car information and navigation) project is the brainchild of the Geldrop Project Centre of Philips Research Laboratories. It is planned that the system is coupled to dashboard functions and a speech synthesiser to inform the driver of any problems, such as low petrol or oil, battery faults or high engine temperature. The system could also be linked to traffic warnings received over the car radio and thus avoid areas of heavy congestion, or road works.

At the heart of the computerized system is a modified compact disc player which could not only play compact discs but also read road information stored on

discs, for example a complete road map of the country, street maps of a town etc. A compact disc is a read-only memory with a capacity of about 5Gb/it. The CD system was modified to extend its error correction so that the chance of an error on an undamaged disc was better than 1 in 10¹⁸. If the capacity is increased to the equivalent of a playing time of 66 minutes, then the capacity of the disc excluding any redundant information required by the error correcting algorithm, is 600Mbytes. As an example of the capacity a 1:15000 coloured map of the area around Eindhoven and Geldorp in Holland (where the research is being carried out) would require a memory of about 375Mbits, or 8% of the capacity of the disc. However by a system of identifying and coding intersections in a road by node points and angles, adding the road name information, a road map of the same area would only require 1.5Mbits, or 0.03%

ELECTRONIC KITS . . .

for beginners and experienced kit-builders

Velleman electronic kits have gained respect for their high quality and the varied range which covers many applications in the vast field of electronics. All kits are designed and developed using the latest technology, giving them appeal, not only to the hobbyist and enthusiast but also to the experienced engineer.

. . . and remember, we have a 'rescue service' for instances where enthusiasm exceeds ability!

THE VELLEMAN KIT RANGE

KIT No.	DESCRIPTION	PRICE £ (INCL. VAT)
K607	2W LF AMPLIFIER	6.20
K610	VU-LED MONO	10.40
K611	7W LF-AMPLIFIER	5.40
K612	DIMMER (SUPPRESSED VERSION)	6.00
K613	DIMMER DEPARASITE	9.60
K1682	MICRO PROCESSOR UNIVERSAL TIMER	47.50
B1682H	WOODEN HOUSING FOR UP TIMER	26.10
K1771	FM OSCILLATOR	6.20
K1798	STEREO VU-LED	18.95
K1803	PRE-AMPLIFIER UNIVERSAL MONO	3.95
K1804	60 WATT LF AMPLIFIER	18.00
K1823	1A POWER SUPPLY WITH LM317	6.95
K1861	POWER SUPPLY FOR 60 WATT STEREO	18.65
K1874	RUNNING LIGHT (4 CHANNEL)	17.95
K2032	LOW COST DIGITAL PANELMETER	17.95
K2543	ELECTRONIC TRANSISTOR IGNITION	9.95
K2545	UNIVERSAL CRYSTAL 50HZ TIMEBASE	14.15
K2547	4-CHANNEL INFRA-RED TRANSMITTER	19.90
K2548	4-CHANNEL INFRA-RED RECEIVER	26.55
K2549	INFRA-RED DETECTOR TRANSMITTER (ALARM)	13.55
K2550	INFRA-RED DETECTOR RECEIVER (ALARM)	15.50
K2551	CENTRAL ALARM UNIT	19.15
K2553	STEREO DECODER WITH 19KC FILTER	12.30
K2554	FM TUNER	22.95
K2557	DIGITAL PRECISION THERMOMETER	28.50
K2565	TAPE/SLIDE SYNCHRONIZER	9.20
K2567	20 CM DISPLAY ANODE	21.15
K2568	20 CM DISPLAY CATHODE	24.15
K2569	3-TONE CHIME	8.50
K2570	POWER SUPPLY 5-14V DC 1A	6.95
K2572	STEREO PRE-AMPLI	6.90
K2573	STEREO RIAA PRE-AMPLI	7.80
K2574	UP DOWN COUNTER (4 DIGITS)	49.50
K2575	UP DOORBELL	15.65
K2576	40 WATT AMPLIFIER	12.95
K2577	UNIVERSAL AC MOTOR CONTROL	11.15
K2579	UNIVERSAL START/STOP TIMER	8.25
K2580	POWER SWITCH/DIMMER	10.30
K2581	DC CONTROLLED STEREO TONE CONTROL	15.90
K2582	STEREO AUDIO INPUT SELECTOR	12.50
K2584	DIGITAL PRECISION TIMER	61.00
K2585	CODE-LOCK (40 x 6 DIGITS NUMBERS)	52.00
K2587	240W AUDIO POWER AMP (POWER SUPPLY INCL)	168.00
K2588	3 CHANNEL SOUND TO LIGHT WITH PREAMPLIFIER	22.50
K2590	LIGHT COMPUTER	28.50
K2591	PROGRAMMABLE CONTROLLER MODULE	59.50
K2592	20 WATT LF AMPLIFIER KIT	10.15
K2594	ZERO CROSS PROGRAMMABLE TIMER	11.50
K2595	PRECISION TIMER MODULE K2595	49.00
K2598	CAR BOOSTER 15-30 WATT	14.95
K2599	SCREEN WIPER ROBOT	9.05
K2600	2A DIMMER	6.25
K2601	STROBOSCOPE	11.10
K2602	4 CHANNEL RUNNING LIGHT WITH MODULATOR	24.40

KIT No.	DESCRIPTION	PRICE £ (INCL. VAT)
K2604	KOJAK SIRENE	7.50
K2606	LED AUDIO POWER METER	12.70
K2607	THERMOMETER ADAPTOR	9.50
K2620	GIANT VU METER	27.90
K2622	AM/FM ACRIAL AMPLIFIER	7.85
K2623	LABO POWER SUPPLY 0-24V/3A	29.10
K2625	DIGITAL RPM METER	23.45
K2615	INTERFACE MOTHERBOARD SPECTRUM	26.40
K2616	INTERFACE MOTHERBOARD ZX81	27.15
K2628	INTERFACE MOTHERBOARD COM-64	39.25
K2609	OC OUTPUT BOARD INTERFACE FOR HOME-COMPUTER	18.65
K2610	A/D CONVERTER INTERFACE FOR HOME-COMPUTER	26.95
K2611	OPTO INPUT BOARD INTERFACE FOR HOME-COMPUTER	19.90
K2614	ZX81-SPECTRUM CENTRONICS INTERFACE	29.95
K2618	D/A CONVERTER INTERFACE FOR HOME-COMPUTER	24.80
K2629	REAL TIME CLOCK INTERFACE FOR HOME-COMPUTER	31.30
K2630	SUPPORT CASSETTE FOR INTERFACE SYSTEM SPECTRUM	4.70
K2633	RELAY CARD	11.55
K2634	QUAD TRIAC SWITCH CARD	12.35
K2635	8 TO 1 ANALOG MULTIPLEXER INTERFACE	20.95


VELLEMAN INTERFACE SYSTEM — BUILT AND TESTED		
M2615	INTERFACE MOTHERBOARD SPECTRUM — MOUNTED	48.30
MM2616	INTERFACE MOTHERBOARD ZX81 — MOUNTED	48.90
M2628	INTERFACE MOTHERBOARD COM-64 — MOUNTED	60.65
M2609	OC OUTPUT BOARD INTER. FOR HOME-COMP. — MOUNTED	22.65
M2610	A/D CONVERTER INTERF. FOR HOME-COMP. — MOUNTED	31.70
M2611	OPTO INPUT BOARD INTERF. FOR HOME-COMP. — MOUNTED	30.40
M2614	ZX81-SPECTRUM CENTRONICS INTERFACE — MOUNTED	34.55
M2618	D/A CONVERTER INTERF. FOR HOME-COMP. — MOUNTED	27.90
M2629S	REAL TIME CLOCK INTERF. (SPECTRUM) — MOUNTED	44.30
M2629U	REAL TIME CLOCK INTERF. (UNIVERSAL) — MOUNTED	44.30
M2633	RELAY CARD — MOUNTED	16.85
M2634	QUAD TRIAC SWITCH CARD — MOUNTED	17.55
M2635	8 TO 1 ANALOG MULTIPLEXER INTERF. — MOUNTED	28.90

LISTS OF STOCKISTS

AVON:	L.F. Hanney 77 Lower Bristol Road, Bath. Tel: 0225 24811
BERKS:	Loving Bros. 76 King's Road, Reading. Tel: 0734 55449
BLACKPOOL:	Etson Electronics 15B Lower Green, Poulton-le-Fylde. Tel: 0253 885107
DEVON:	S & R Brewster 86-88 Union Street, Plymouth. Tel: 0752 665011
CHESHIRE:	Douglas Components 90 Wellington Street, Stockport. Tel: 061 480 8971
ESSEX:	R. Jones Electronics 267 Rectory Road, Grays. Tel: 0375 33158
HERTS:	Hemmings Electronics 16 Brand Street, Hitchin. Tel: 0462 33031
LANCS:	Kennedy Electronics 3 Sudell Close, Blackburn. Tel: 0254 56917
	Kennedy Electronics 43 Cannon Street, Preston.
LIVERPOOL:	Progressive Radio 93 Dale Street, Liverpool. Tel: 051 236 0982
LONDON:	Bradley Marshall 325 Edgware Road, London W2. Tel: 01 723 4242
	Bonex Limited 102 Churchfield Road, Acton W3. Tel: 01 992 7748
	Servio Radio 156/158 Merton Road, Wimbledon SW9. Tel: 01 622 2757
MANCHESTER:	Spectron Electronics 7 Oldfield Road, Salford. Tel: 061 834 4583
NORTHANTS:	M.W. Associates 10 Crown Street, Kettering NN16 8QE. Tel: 0536 520359
WILTS:	Camlab Electronics 27 Faringdon Road, Swindon. Tel: 0793 34917
SCOTLAND:	Marshall's Electronics 86 West Regent Street, Glasgow G2. Tel: 041 332 4133
IRELAND:	Baxol Tele Exports Ballinacash, Post Rathdrum, Co. Wicklow. Tel: 0404 6278
	Frank Mozer 5 Angel Corner Parade, Edmonton N18. Tel: 01 807 2784
	TK Electronics 11-13 Boston Road, W7. Tel: 01 567 8910
MIDDLESEX:	LB Electronics 11 Hercies Road, Hillingdon. Tel: 0895 55399
YORKSHIRE:	Harrogate Electronic Services 24 Regent Parade, Harrogate. Tel: 0423 64353

SEND FOR NEW FULL COLOUR SHEET DETAILING COMPLETE RANGE available free from:

VELLEMAN UK. Ltd

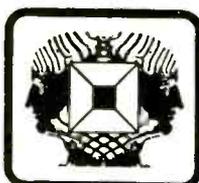

P.O. Box 30, St. Leonards-on-Sea,
East Sussex TN37 7NL, England.
Telephone: (0424) 753246

Please send me your details of Velleman electronic kits:

Name

Address

of the disc capacity.

The system also needs to know where the car is. The first solution is the inclusion of an electronic compass linked to the odometer that will use the car's computer to correct any errors caused by magnetic disturbance such as other vehicles and the massive ironwork in reinforced concrete. Error correction can be carried out by constant reference to the map held in memory. A longer-term solution is the possibility of satellite navigation using the Navstar global positioning system. The 18 American satellites will provide signals that enable a ground receiver to locate itself to within 10m, including height, and provide the time, accurate to that of an atomic clock.

The system requires a video screen, but from the safety point of view it is deemed to be important that the screen can only be consulted when the car is standing still. A typical journey could have the driver insert the disc for the local area, indicate the cars present position and the destination. The computer will store the information and the disc player can then be used for playing music. The system will guide the driver through the speech module. In future the necessary keyboard may be replaced by a touch screen.

Philips emphasize that the system is not a dream of the future but that all the technology already exists and a practical system will be available quite soon.



The elements, CD player, dashboard data, electronic compass and computer, that go together to make the Carin route information system, under development by Philips.

Fears about tape levy

BREMA, the Radio and Electronic Manufacturers Association, has deplored the Government's support for some sort of levy on blank video and audio tapes as expressed in the Green Paper (Cmd 9445). The Green Paper accepts that the proposals will involve some element of rough justice but it is unable to think of any realistic alternative.

The Association is particularly worried because the levy implies that at some future date it could be extended to recording equipment and to any future recording medium that may be developed. Any such levy would be discriminatory

as it could not apply to the millions of pieces of recording equipment already in use. The Association is further apprehensive that once the idea of a levy is accepted, then future Governments could increase the levy over the years, just like any other tax. The one redeeming feature they see in the paper is that it admits that the levy could not be used to compensate for lost revenue by copyright holders.

Finally the Association voiced its fears that once having paid a levy, users could feel licensed to copy freely and that this could lead to more piracy, rather than less.

geometry gates, and using ion implantation techniques, the range will include standard products as well as custom and semi-custom designs. Full production of Gbit/s logic circuits is to start later in the year. Typical of the range is variable modules prescaler and a 4bit synchronous counter, both of which can operate at 900MHz.

- BBC External Services is to install a massive computer which will act as a news source of reports picked up by the monitoring service at Caversham. It needs to have a

storage capacity of about 28bn characters to hold the teleprinter material emanating from international new agencies and monitoring units abroad. It will have 174 v.d.u. input stations and be connected to 100 printers. Monitors will be able to key their transcripts straight into the computer. Journalist who prepare the External Service's news file and daily summary will be able to draw directly on this information and feed their own stories into the system. Bids for contracts to install the computer have been invited from 40 computer companies.

In brief

- The UK f.m. Group (western) of the RSGB has put its thirteenth amateur radio repeater station on the air. In contrast to the other repeaters, this one is a data and r.t.t.y. unit. It operates on the 432MHz band on Channel RB12 from Winter Hill, near Bolton, Lancs. Slant aerial polarization is used. Operation is on 50baud Murray code but ASCII operation at 1200baud is to be implemented. With RSGB approval, the Group hope to attach a 'mailbox' service to allow radio amateurs to leave messages for each other; similar to the telephone bulletin boards.

- BT is to make and sell a 16-bit microcomputer. An agreement has been signed with Bleasdale Computers to produce the Bleasdale 68000 Unix computer. The computers are to be assembled at BT's own plant in Birmingham. Intended chiefly for BT's own use, the computer is also to be marketed outside the company. Unix is an 'open' operating system developed at Bell Labs, and offers multi-user, multi-tasking facilities.

- STC Components are now making development quantities of a range of GaAs i.c.s. Employing one-micron

Anti-piracy law

The Government has expressed its support for William Powell's Private Member's Bill to extend the copyright laws to include computer programs. John Butcher, Secretary for Industry, said: "The Government is anxious that this important measure should become law as soon as possible to help the UK

software industry combat the growing threat of software piracy." It is hoped that penalties imposed by the act will deter software pirates as successfully as the reduction of the level of video piracy since similar Bills were passed in 1982 and 83.

Transputer on the way

Inmos are now producing their super microprocessor, the Transputer in test quantities and hope to have evaluation samples available for customers by the middle of the year. Volume production of the fast 64K static ram and of the 256K dynamic ram is also expected during the year. Static rams

manufactured in Colorado Springs, California and dynamic rams from Newport, Gwent are now being produced in millions and the company, after many years of Government investment is now making a profit. It was sold to Thorn-EMI last September.



Tina 6502

A new advanced microprocessor control system that features:-

- Colour graphics
- Enhanced memory facilities
- Advanced user-friendly software
- On-board features include:-
 - Power supplies
 - RS232 interface
 - IEEE interface
 - CENTRONICS interface
 - EPROM Programmer
 - Switched faults



Marc Z80

Based on a powerful Z80 CPU this new single board microcomputer teaching system features:-

- 56K RAM/EPROM facilities
- On-board switched faults
- CP/M loading facility
- On-board software includes:-
 - Monitor, Machine code display and Modify, Z80 ASSEMBLER/ DISASSEMBLER, Light-pen routines, program de-bugging routines

To find out more about these and other items in the complete LJ range send for our new 1985 catalogue

L J Electronics Ltd

Francis Way, Bowthorpe Industrial Estate, Norwich NR5 9JA.

Telephone: (0603) 748001.
Telex: 975504.



CIRCLE 82 FOR FURTHER DETAILS.

pantechnic

- design manufacture and supply

**POWER AMPLIFIERS
HIGH POWER ASSEMBLIES
CONTROL CIRCUITRY**

- for application in

**INDUSTRY
PUBLIC ADDRESS
HI-FI**


- available

**OFF THE SHELF
CUSTOMISED
C A D DESIGNED**

tel. 01.361.8715 132 High Road
telex 266 873 New Southgate
PANTEC G LONDON N11 1PG.

CIRCLE 85 FOR FURTHER DETAILS.

SATELLITE TV RECEIVING EQUIPMENT

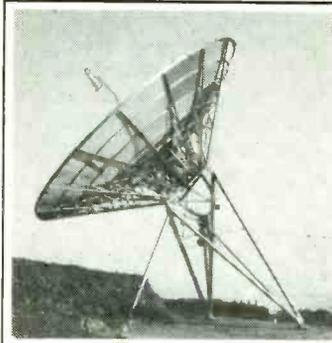

1.9M, 2.5M and 5M Dishes. Receivers, Downconverters, Low Noise Amplifiers, Feed Horns available. Complete systems installed anywhere in the world. A full report on reception feasibilities at any location is available — price £25.00. Please state Longitude and Latitude.


For further details contact

HARRISON ELECTRONICS

22 MILTON ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 7JX Tel: (0702) 332338

Toroidal Transformers

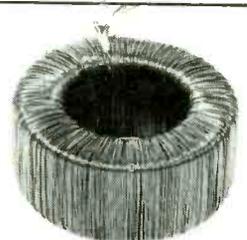as manufacturers we are able to offer a range of quality Toroidal Transformers at highly competitive prices and fast delivery.



Mail Order Price List

15VA 6.92 30VA 7.18 50VA 8.86 80VA 9.92 120VA 10.59 160VA 12.10 225VA 13.69 300VA 14.77 500VA 19.20 625VA 22.09 750VA 26.17 1KVA 38.82 1.2KVA 44.06
price includes p+p & vat.

Available from stock in the following voltages:—6-0-6 9-0-9 12-0-12 15-0-15 18-0-18 22-0-22 25-0-25 30-0-30 35-0-35 40-0-40 45-0-45 50-0-50 110 220 240(max. 10 amp). Primary 240 volt.

Quantity Prices and delivery on request
(we also manufacture conventional E1 type transformers)



Airlink Transformers.

Unit 6, The Maltings, Station Road, Sawbridgeworth, Herts. Tel: 0279-724425.

CIRCLE 89 FOR FURTHER DETAILS.

ELECTRONICS & WIRELESS WORLD MAY 1985

TURN YOUR BBC MICRO INTO A PROFESSIONAL MICROPROCESSOR DEVELOPMENT SYSTEM

THE OPERATING SYSTEM

- FLEX—The Professional Operating System
- Versatile, Flexible & Powerful, the ideal operating system for industrial control
- Provides the power, sophistication and ease of development, previously only offered by larger, more expensive systems

THE HARDWARE


- 6809 Advanced 16 Bit Processor
- Choice of Industrial Interfaces for Target Applications:
 - High Resolution Colour Graphics
 - Industrial input/output boards
 - IEEE communications
 - and many more

THE TOOLS

- PL9 — A fast, efficient control language
- CMS FORTH Interpreter & Compiler
- Cross Assemblers for most 8 bit & 16 bit micro's
- "C", BCPL, PASCAL

THE SUPPORT

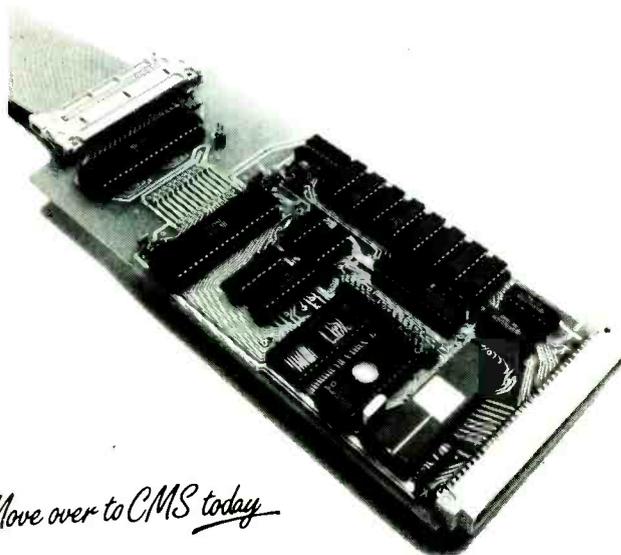- Top rate after sales technical support
- Systems / Hardware Design



Move over to CMS today

CMS	44a Hobson Street Cambridge CB1 1NL (0223) 324141	Cambridge Microprocessor Systems Limited

CIRCLE 7 FOR FURTHER DETAILS.

R. WITHERS COMMUNICATIONS



If you have not heard of (R. Withers Communications) we are main distributors or agents for the following, Yaesu, Icom, Kenwood, M. Modules, Jaybeam, Toevna, Revco Antennas, Clearstone, Mutek, Drae, F.D.K. Tonna, Welz, Zycomm, Neve Radiotelephones.

We are also stockist (British Telecom Approved) of a wide range of cordless telephones and telephone systems. We are also agents for hundreds of other radio communications equipment known the world over, we also manufacture our own range of VHF—UHF beam antennas which are also used by leading broadcast companies for wireless mic applications. We supply a large range of power transistors & modules to the trade. These we import ourselves directly from Japan. Listed below are just some of the many services we offer.

- ★ Supply & repair of all amateur & business radio equipment
- ★ Complete check of your transiever on a spectrum analyser (with comprehensive report) for the all in price of £12.50 subject to an appointment being made
- ★ Supply & complete installations of business radio systems including competitive maintenance contracts, local authorities included
- ★ Supply of 10 metre converted radios LCL, DNT, ICOM
- ★ Only supplier of modified Revco RS 2000 50-520 MHz continuous coverage scanning receiver modified by (R. Withers Comms)
- ★ Probably the largest seller of second hand radio equipment in the country because of our commission sale agreement (3 month warranty) plus equipment facility
- ★ The fastest growing retail & wholesale company in the British Isles. Send for details of any of the equipment or services we offer whether you are in the profession of just an interested party an s.a.e. will speed up your enquiry
- ★ For all your communication needs give R.W.C. a try we promise you will not be disappointed.
- ★ The largest selection of radio allied services offered under one roof, with no expense spared on test equipment and qualified staff...

**584 Hagley Road West, Oldbury, Warley
B68 0BS (Quinton, Birmingham)
Tel: 021-421 8201/2 (24 hr answerphone)**

Overseas customers welcome. We speak German & Japanese.
Import/Export no problem. Please telephone during working hours.

OR TELEX 334303 TXAGWM-G

CIRCLE 84 FOR FURTHER DETAILS.

AUDIO DISTRIBUTION CONSOLE MODEL RTM4-100

The following distribution facilities are provided.

1. Single channel radio distribution from integral variable AM/FM tuner.
2. Single channel cassette tape distribution from integral cassette player.
3. Four channel mixed speech distribution from any standard 200 ohm impedance microphones.

Note that the output of all facilities can be mixed if required and that bass and treble control is provided on the mixed output.

RECORD FACILITY

The integral cassette tape recorder can be used to record the mixed output of the four microphone channels and the radio distribution channel.

CONSOLE

DIMENSIONS: 465mm High x 435mm wide x 330mm deep approximately
POWER SUPPLY: 200/250 Volts A.C. 50 Hz.
AMPLIFIER: 100 Watts RMS
100 Volt line output

PRICE £556 inc VAT and Delivery (Mainland only)

Ultrasonic Burglar Alarm

Portable — wooden finish with internal alarm — easily installed — mains/battery option. Provision for window contacts — pressure mat. External horn and bell unit. Sample units £39.00 + £2.00 pp (£47.13 inc. VAT each), 5 units £35.00 + £2.00 pp £42.55 inc. VAT each, 10 units £33.00 + £2.00 pp £40.25 inc. VAT each.

External Horn

Sample unit £7.50 + £2.00 pp £10.93 inc. VAT each, 5 units £6.75 + £1.50 pp £9.49 inc VAT each, 10 units £6.37 + £1.50 pp £9.05 inc. VAT each.

Burgess E61

Sub-miniature microswitch with common NO-NC contacts. Rated at 5 amps on 125-250V AC. Internal heavy duty contact gold plated for long life. £15. For 100 + VAT, £67.50 for 500 + VAT, £125 for 1,000 + VAT. £550 for 5,000 + VAT. Sample 10 sent for £2.00 + 50p pp (£2.88 inc VAT).

TERMS C.W.O. export enquiries welcome. We find it impossible to advertise all we stock. Please telephone, write or telex for further enquiries. Personal callers always welcome.


ELECTRONIC EQUIPMENT Co.

SPRINGFIELD HOUSE,
TYSSEN STREET,
LONDON E.8. 2ND
TEL NO. 01-249 5217
TLX: 8953906 EECO G

CIRCLE 73 FOR FURTHER DETAILS.

AMPLIFIERS

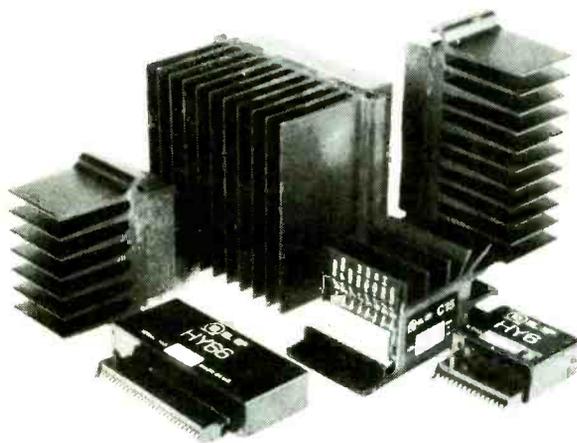WHY ILP? Years of experience in audio, unique designs, world wide sales and outlets, reliable delivery and friendly service.....



PREAMPLIFIER MODULES

All modules are supplied with in line connectors but require potentiometers, switches etc. If used with our power amps they are powered from the appropriate Power Supply.

Type	Application	Functions	Price
HY6	Mono Pre Amp	Full Hi Fi facilities	£7.95
HY66	Stereo Pre-Amp	Full Hi Fi facilities	£14.95
HY73	Guitar Pre-Amp	Two Guitars plus Microphone	£15.95
HY78	Stereo Pre-Amp	As HY66 less tone controls	£14.45

MOUNTING BOARDS: For ease of construction we recommend the B6 for HY6 £0.95 B66 for HY66-78 £1.45.

BIPOLAR MODULES

Ideal for Hi Fi, Full load line protection integral Heatsink, slew rate 15v/μs

Distortion less than 0.01%

Type	Output Power Watts (rms)	Load Impedance Ω	Price	Type	Output Power Watts (rms)	Load Impedance Ω	Price
HY30	15	4-8	£8.45	HY244	120	4	£26.95
HY60	30	4-8	£9.95	HY248	120	8	£26.95
HY6060	30 + 30	4-8	£19.45	HY364	180	4	£39.95
HY124	60	4	£20.95	HY368	180	8	£39.95
HY128	60	8	£20.95				

MOSFET MODULES

Ideal for Disco's, public address and applications with complex loads (line transformers etc.). Integral Heatsink slew rate 20v/μs distortion less than 0.01%

Type	Output Power Watts (rms)	Load Impedance Ω	Price	Type	Output Power Watts (rms)	Load Impedance Ω	Price
MOS128	60	4-8	£30.45	MOS364	180	4	£45.95
MOS248	120	4-8	£39.95				


POWER SUPPLY UNITS

Type	For Use With	Price	Type	For Use With	Price
PSU212	1 or 2 HY30	£11.95	PSU542	1 HY248	£17.95
PSU412	1 or 2 HY60, 1 HY6060, 1 HY124	£13.95	PSU552	1 MOS248	£19.95
PSU422	1 HY128	£15.95	PSU712	2 HY244	£21.95
PSU432	1 MOS128	£16.95	PSU722	2 HY248	£22.95
PSU432	2 HY128, 1 HY244	£17.45	PSU732	1 HY364	£22.95
PSU522	2 HY124	£17.45	PSU742	1 HY368	£24.45
PSU532	2 MOS128	£17.95	PSU752	2 MOS248, 1 MOS368	£24.45

All the above are for 240v operation.

FOR FREE DATA PACK PLEASE WRITE TO OUR SALES DEPT.

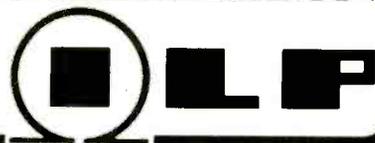Post to: ILP Electronics Ltd., Dept. 6
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 454778 Telex: 965780



CIRCLE 68 FOR FURTHER DETAILS.

BAKER LOUDSPEAKERS

MODEL	INCHES	OHMS	WATTS	TYPE	PRICE
Disca/Group	10	8-16	50	/PA	£18
Midrange	10	8	100	MID	£25
Major	12	4-8-16	30	HI-FI	£16
Superb	12	8-16	30	HI-FI	£26
Woofer	12	8	80	HI-FI	£25
Auditorium	15	8-16	60	Bass	£37
Disca/Group	12	4-8-16	45	PA	£16
Disca/Group	12	4-8-16	75	PA	£20
Disca/Group	12	8-16	100	PA	£26
Disca/Group	15	8-16	100	PA	£35

PA. 150 Watt MICROPHONE VOCAL and GROUP AMPLIFIER £129

4 channel mixing, 8 inputs, dual impedance, 50K-600 ohm, volume, treble, bass. Presence controls on each channel. Master volume control, echo, send return socket. Slave sockets. Post £3.

150 Watt MIXER AMPLIFIER 4 Inputs £99

Discotheque, Vocal, Public Address. Speaker outlets for 4, 8 or 16 ohms. Four inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing control. 240V A.C. Post £2.

100 Volt Line Model, 150 watt £114. MONO SLAVE. 150 watt £80.

Baker Stereo Slave 150 + 150 watt per channel (300 watt Mono) Heavy Duty Model £125. Post £4.

BAKER MOBILE PA AMPLIFIER. All transistor, 60 watt RMS, 12v DC & 240v AC, 4 inputs 50k Aux + 2 mics + 1 phono loudspeaker. Output 4-8-15 ohms + 100 volt line. £89 Post £2

PA systems — amplifier, mike + two speakers

Mobile 60w, 240v AC + battery 12v £199 carr. £20

MkII 150w, 240v AC, complete £249 carr. £20

150 WATT DISCO twin deck system £360 carr. £30

120 WATT DISCO + twin speakers £300 carr. £30

Console only, £145, 120 watt, £199, carr. £10

PA CABINET SPEAKERS. 4 or 8 or 16 ohm 75 watt 20x15x9in. £54. 90 watt 32x15x11in. £73. 150 watt £82. Carr. £10 Black vinyl covered with handles.

RCS SOUND LIGHT. Ready Built Deluxe 4 Channel 4,000 watt with chaser — speed + programme controls £69. Post £2. **New Model MkII** with special 16 programmes: 4 channel 4,000 watt £89. Post £2.

DELUXE STEREO DISCO MIXER/EQUALISER as above but L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phono/line, mike/line. Recording Output £124.

PROJECT CASES Black vinyl top and sides
6x4x1m £3.60 8x5x2in £4. 11x6x5 £9. 9x5x2in £4.80 11x6x3 £5.50 13x8x4 £11.

ALUMINIUM BOXES. 4x4x1 £1.20; 4x2x2 £1.20; 3x2x1 £1.20; 6x4x2 £1.90; 7x5x2 £2.90; 8x6x3 £3; 10x7x3 £3.60; 12x5x3 £3.60; 12x8x3 £4.30; 9x4x4 £3; 6x4x3 £2.20; 4x4x2 £1.60.

"STOP PRESS"

H+H 1000w mono, 500w stereo quality amplifiers. S500D, reconditioned, guaranteed £275, p.p. £5

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD
CROYDON, SURREY, U.K.

ACCESS TEL 01-684 1665 VISA
Same Day Despatch. Closed Wed.
Lists 34p

CIRCLE 77 FOR FURTHER DETAILS.

DON'T GO DOWN WITH YOUR SCOPE! It never was designed to float



The Waugh Instruments Isolation Amplifier enables you to keep your scope earthed and still make measurements up to 1500V from earth, this together with over 100dB rejection at 50Hz means that you can now observe small signals superimposed on 350V sine waves so often encountered in switch mode power supplies, thyristor and triac firing circuits. For details of this and other oscilloscopes accessories contact: - **Peter Waugh at Waugh Instruments, Otter House, Weston Underwood, Olney, Bucks MK46 5JS (0234) 712445.**

CIRCLE 58 FOR FURTHER DETAILS.

SSB LINEARITY

At least one idea that could reduce some of the spurious emissions that tend to be increased by broadband systems is the work that has been going on for several years at Bath University on the application of cartesian (polar) feedback. V. Petrovic described a 100-watt p.e.p. transmitter with cartesian-loop phasing-type s.s.b. generation having third-order intermodulation products some 67dB below the tones of a two-tone test, with image sidebands suppressed by 68dB.

A coordinated presentation of five papers from the US Naval Research Laboratory described a new wide-band h.f. system with frequency-hopping capability being developed for the US Navy and resulting in studies similar to those that led some 15 years ago to the development of the ICS-3 system for the Royal Navy. The Americans, however, plan to use v.mos field effect devices for power amplification, with negative feedback and feedforward linearizing techniques. In all complex shipborne installations the major problem is the proximity of several transmitters and receivers. NRL are developing fast-tuned narrow-band filters for both antenna couplers and for preselection filters for receiver protection, together with the use of adaptive interference cancellation by phasing techniques. They are also developing new broadband h.f. antennas for ship installations.

It was interesting to note that some professional systems designers are at last recognizing that conventional receiver a.g.c. systems designed for analogue s.s.b. voice signals tend to degrade performance on morse and narrow-band data transmission, due to the finite attack time which means that the instantaneous dynamic range of a receiver is significantly less than the claimed 140dB or so available when the a.g.c. range is added. There is also the problem that the a.g.c. bandwidth may be considerably greater than that of a narrowband transmission, particularly where a receiver depends on audio filtering for r.t.t.y. or data reception. The problem arose when "hang

a.g.c." systems were introduced and the ability to switch out the a.g.c. circuits dropped from most h.f. communication receivers.

HF RESURGENT?

A three-day international conference at Savoy Place "HF communications systems and techniques" underlined the resurgence of interest in the application of advanced technology to h.f. Less happily it emphasised that this interest, although spilling over into university and commercial research projects, is primarily centred on Defence communications. For these the trend is firmly towards fast frequency hopping at rates between several hundred and several thousand per second yet capable of providing secure digital speech and data at rates of about 2400bits/second. For other users such technology, unfortunately, offers the prospect of ever increasing spectrum pollution.

The current sunspot-minimum is already leading, particularly after dark in Europe, to excessive overcrowding of h.f. with some users employing spectrum analysers to seek out the few relatively clear channels and then to occupy these whether or not registered with the International Frequency Registration Board. At the conference a number of papers were presented on built-in systems of real-time channel-evaluation which could formalise this type of operation.

Of the 235 delegates from almost 20 countries the vast majority were connected with, funded by or manufacturing for Defence with few from traditional h.f. user organizations such as British Telecom and Cable & Wireless. In the often lively discussion periods it was left to J. Clarke of British Airways and radio amateurs to question the effect of the spread-spectrum techniques on frequencies still required for civilian communications.

Frequency-hopping on h.f. poses state-of-the-art challenges to designers if the problems of multipath, fast switched antenna couplers and digital synthesizers are to be overcome.

ENERGY-SAVING ON U.H.F. TV

For the past decade the major klystron and transmitter manufacturers have been striving to out-do each other in reducing the appalling waste of power in high-power u.h.f. television transmitters. Pulsers, variable couplers, depressed collectors, annular gridded cathode techniques have all been developed with the aim of improving the conversion efficiency of klystron amplifiers that conventionally require constant power, set by the peak sync pulses. Even when referenced to peak sync, conversion efficiency has often been only of the order of 20-25 per cent. When defined in relation to the vision waveform, efficiency drops to just a few per cent. About half a megawatt of electricity is consumed for the 110kW transmitters commonly used in the USA and some broadcasters have complained that electric power costs them more than off-peak programming.

A promising development is the Varian "klystrode" that combines the efficiency of a tetrode with gain and long-life of a klystron and will be capable of true Class B operation — but there will first need to be a new generation of transmitters for this device.

Meanwhile klystron manufacturers are continuing their development of techniques that enable u.h.f. klystrons to match the efficiency of v.h.f. tetrodes. Marconi, with their new American associates Comark, are claiming to have achieved at WITE-TV, Channel 28, Columbus, Ohio a klystron beam efficiency of no less than 77 per cent, with an Amperex (Philips/Valvo) YK1265 klystron vision amplifier, a Comark high energy CTM-20 pulser and the new Marconi B7500 modulator unit.

DIGITAL TRANSCEIVERS

The opening address at the h.f. conference was given by Dr Ulrich Rohde who for many years was the representative of Rohde & Schwarz in the USA but is now a consultant to RCA Government Communications Division and part of a design

team seeking advanced technological solutions for US military communication. He emphasised that "in order to meet communication goals for 1984 and beyond, modern h.f. equipment has to be adaptive, frequency agile and capable of supporting secure, digital voice communication, operating on a point-to-point, and a networked basis as well". His keynote paper explored solutions aimed at an all-digital h.f. transceiver for which there is currently an American defence requirement. For voice encryption, the Americans have chosen linear predictive coding, a technique not unlike that used in children's "speaking toys" and capable of compressing 3kHz analogue speech into an encrypted 2.4Kb/s data stream. He also surveyed work on direct digital synthesizers, PIN-diode switched antenna couplers and digital processing in receivers using linear equalization techniques with a time-gated feedback equalizer to minimise multipath problems.

D.T. Anderson of Rockwell-Collins described the new hybrid analogue/digital receiver type HF2050 (see *Communications Commentary*, October 1984) now being delivered — as the first production h.f. receiver to use digital signal processing — to Canada. In this the signal is digitized at the 2nd i.f. of 3MHz.

But as B.M. Sosin of Marconi pointed out, digitization at signal frequency, as required for an all-digital receiver, throughout the entire range of 2 to 30MHz and for a signal dynamic range of 140dB would require something like 23-bit "words" at a sampling rate of over 60MHz, resulting in bit rates still well beyond device capability.

TWTs FOR DBS

The still unproven reliability of 220-watt travelling wave tubes and amplifiers for high-power direct broadcasting from satellite is one of the factors that are contributing to the uncertainty that still surrounds the early implementation of operational services. The French are still hoping to have a four-channel satellite in operation next year, possibly with two channels leased to the



The Archer Z80 SBC

The **SDS ARCHER** — The Z80 based single board computer chosen by professionals and OEM users.

- ★ High quality double sided plated through PCB
- ★ 4 Byte-wide memory sockets — upto 64k
- ★ Power-fail and watchdog timer circuits
- ★ 2 Serial ports with full flow control
- ★ 4 Parallel ports with handshaking
- ★ Bus expansion connector
- ★ CMOS battery back-up
- ★ Counter-timer chip
- ★ 4 MHz. Z80A

OPTIONS:

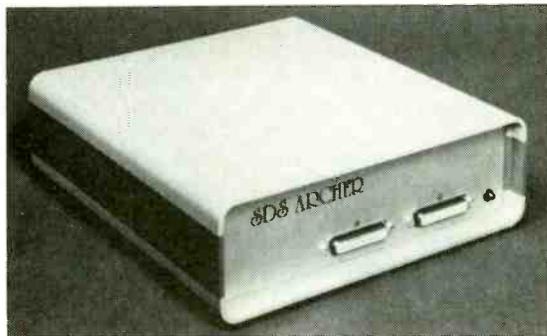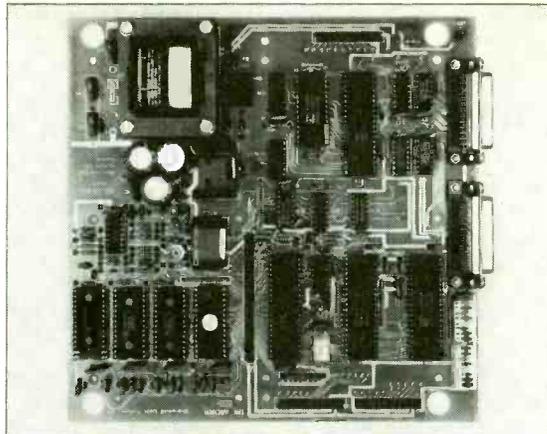- ★ SDS BASIC with ROMable autostarting user code
- ★ The powerful 8k byte SDS DEBUG MONITOR
- ★ On board 120 / 240 volt MAINS POWER SUPPLY
- ★ Attractive INSTRUMENT CASE — see photo.
- ★ 64k / 128k byte DYNAMIC RAM card ★ NEW ★
- ★ 4 socket RAM — ROM EXPANSION card ★ NEW ★
- ★ DISC INTERFACE card ★ NEW ★



Sherwood Data Systems Ltd


Sherwood House, The Avenue, Farnham Common, Slough SL2 3JX. Tel. 02814-5067

CIRCLE 75 FOR FURTHER DETAILS.



NEWRAD INSTRUMENT CASES LTD
Unit 19, Industrial Estate, Gore Road
New Milton, Hants BH25 6SJ
Tel: New Milton 0425 621195

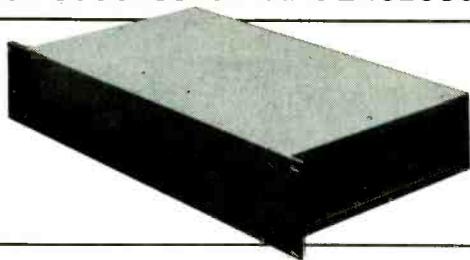**WE HAVE INCREASED THE RANGE
OF OUR SUCCESSFUL NM40 ENCLOSURES**



Beautifully made 19 inch Rack Mounting enclosures complete with heavy gauge chassis and top and bottom covers. Front, Side and Rear panels are aluminium and flat for easy machining. These panels are located with heavy duty aluminium extrusions. Front and Rear panels are satin anodised. Covers are finished in cream.

HEIGHT	DEPTH	PRICE
2U	150	£16.50
2U	250	18.60
2U	300	18.50
3U	150	18.00
3U	250	20.00
3U	300	22.00
4U	150	20.30
4U	250	24.50
4U	300	27.40
6U	150	25.00
6U	250	29.00
6U	300	35.00

PRICES ARE EXCLUSIVE OF VAT. P & P £3.00

CIRCLE 9 FOR FURTHER DETAILS.



AEL AT SPEED

TO BE CRYSTAL CLEAR

Tel. 029-34-5353 Telex 87116 Aero G
MOD approved CAA approved

CIRCLE 64 FOR FURTHER DETAILS.

LOGICAL EPROM PROGRAMMERS & ERASERS

PROMPRO 8 — £775

Powerful commands, easy communications.

64/128/256k buffer.

Emulation, keypad option.

Programs all EPROMS & MPU's

Choose from stand alone, intelligent RS232 units.

Compatible with any computer/terminal.

ERASERS
FROM £88.00

EPROM PROGRAMMERS
FROM
£395.00
(ex VAT)

BIPOLAR & PAL
— CALL!



byTRON

BYTRON LTD.,
High Street, Kirmington,
S. Humberside, DN39 6YZ

Tel. 0652 688626
Telex 527339

CIRCLE 63 FOR FURTHER DETAILS.

ELECTRONICS & WIRELESS WORLD MAY 1985

commercial broadcasting services of Luxembourg. Telefunken also have a high-power Ku-band (12GHz) TWT in an advanced stage of development but not yet tested in orbit. A TWT amplifier capable of 240W of c.w. output with an efficiency of over 40 per cent is being developed by Hughes Aircraft with a target life of seven years and with focussing by temperature-compensated samarium-cobalt magnets. Meanwhile RCA Laboratories are developing solid-state Ku-band active arrays using large numbers of GaAs f.e.t. devices with individual phase shifters which could be used to change the radiation pattern of a d.b.s. satellite in orbit.

But several of the d.b.s. systems registered with the FCC are finding it increasingly difficult to attract investors and few expect earlier implementation of high-power satellites. One American consultant has suggested: "The would-be d.b.s. operators should be blaming themselves, not Wall Street, for their difficulties. Most have been technology-orientated. The easiest part of the d.b.s. puzzle is to put a satellite up there and to put a signal across the USA. The toughest part is to market the service nationally, and to maintain your customers over a period of time."

WIDE C-MAC

In the UK, IBA engineers have been privately demonstrating on closed-circuit an experimental system capable of providing high-definition, wide-screen pictures (up to 5:3 aspect ratio and a subjective definition of almost 1000 lines) when the receiver contains digital processing memory. The system is fully compatible with the standard C-MAC/packet system but with extra time allocated for wide screen pictures from the sound/data and frame flyback periods. The system also allows the 4:3 aspect ratio picture to be panned anywhere within the wider 5:3 picture. The still-experimental equipment is currently being re-jigged into a prototype demonstration unit when it is hoped that public demonstrations will be given. No problems are expected in

putting enhanced C-MAC through a single 27MHz satellite channel.

Amateur Radio

EARS OR MODEMS?

With the spread of personal computers, a rapidly increasing number of amateurs are using various forms of electronic r.t.t.y., data transmission, including "packet radio", automatic request for repetition (ARQ) in the Amtor system, and high speed automatic morse etc.

In implementing any systems involving automatic reception, the greater vulnerability of such systems, compared with the human operator, to interference, multipath and fading becomes a major problem. The mechanical teleprinter, developed for line communication, was never intended to cope with adverse channel conditions and led to the use of space, frequency and polarization diversity systems. In the absence of diversity, it has long been recognized that two-tone and multitone systems are capable of better performance than f.s.k. but advantage has seldom been taken of this by amateurs on h.f. Parallel multi-tone systems such as Piccolo, with inherent signal integration, can produce clean copy at very low signal strengths but demand more complex modems, a very high degree of frequency stability and greater bandwidth than either manual morse or narrow-shift f.s.k. For all these reasons, manual morse has remained the optimum system under adverse conditions not only for amateurs but also in the maritime services.

At the recent h.f. conference, Peter Chapman of the Admiralty Research Establishment (formerly ASWE) described laboratory and field trials of a low-speed modem with inherent frequency and time diversity designed to provide reliable communication under the most adverse conditions. The objective is a fall-back system

capable of performing better than morse and eventually to eliminate the cost of morse-operator training in the Royal Navy.

Throughput of traffic is at the slow rate of 10 bits/second (10 baud) although the signalling rate is around 100 bits/second. The modem transmits ten discrete audio tones in a 3kHz s.s.b. channel, one set of five representing "mark" and the second interleaved set for "space". The tones in each set are sequentially transmitted for 10 milliseconds each, with 10 millisecond gaps so that each symbol is transmitted five times during a 100 millisecond period. It thus differs radically from the parallel multitones of Piccolo.

Propagation trials last September between ARE Portsdown and Wick in the north of Scotland used 25-watts p.e.p. and ran throughout 24-hour periods on two frequencies about 4.88MHz. The frequencies were repeated interchanged between morse and the new modem.

While the results undoubtedly suggest that the modem can outperform morse, at least some of the delegates, who included a significant number of licensed amateurs, felt the scales had been heavily weighted against morse. For example, it was recorded on tape, then brought to the laboratory for transcription by the operators, giving them no chance of adjusting selectivity, notch filter, audio beat tone etc., all of which could have significantly improved the copy, and allowed them to take full advantage of the remarkable characteristics of the human ear.

A truly narrowband c.w. receiver, preferably without a.g.c. and bandwidth adjustable down to under 100Hz and controllable front-end gain etc., with an operator at the controls and preferably the ability to change transmission frequency even by a modest amount would have produced very different results.

The low-cost, low-complexity and reliability of a "kiss" morse system under adverse and emergency conditions should encourage the Royal Navy and other organizations to think very carefully before finally phasing out morse telegraphists in favour of keyboard-only

operators.

But perhaps it is a sign of the times to prefer the inanimate to the animate. Electronic "petsters" — stuffed, furry creatures with built-in microcomputers — are being marketed in the USA "to replace biological animals as pets and companions" by Axlon Inc. Simulated moods — from contentment to anguish, from a lazy response to bouncing enthusiasm, are software controlled by a 4-bit microprocessor with 4K bytes of memory. How soon before they begin to automate the owners?

FROM ALL QUARTERS

The number of new amateur radio licences issued in 1984 in the USA dropped by over 10 per cent compared with 1983. 30 per cent fewer amateurs upgraded their licences and about a quarter of licences are currently not renewing, according to *Ham Radio*. For the first time in 10 years the year finished with a net loss in licence totals.

British Telecom "Ambassador" telephones and some of the other electronic models are proving a source of interference on the 144MHz band, showing a tendency to radiate wideband hash-like signals. Among the increasing number of domestic appliances showing susceptibility to strong local r.f. signals are domestic burglar alarms and smoke detectors.

The UK F.M. Group (Western) recently brought into operation its thirteenth repeater, GB3MT, at the IBA Winter Hill site (mounted on a Granada Television OB link platform) near Bolton, Lancashire. This 432MHz band, slant-polarized (45°), RB12 repeater is for r.t.t.y. and data and the first of its type in the North West. Initially only 50-baud five-unit Murray code is suitable but it is hoped to add ASCII operation at 1200-baud shortly, and approval is being sought to add an "electronic mailbox" for store and collection operation. Membership details of UKFMG(W) from Mr A. Baker, G4NYP, 26 Brooklands Drive, Goostrey, Crewe, Cheshire.

Pat Hawker, G3VA.

EDR editor for DEC — £350



- * Keypad editor similar to KED and EDT
- * Uses no host time or memory when editing
- * Fast Response
- * Edits PDP-11, LSI-11 and VAX files

Why burden your overworked DEC computer with the task of editing files? You can now use the new EDR front end processor from Andelos Systems to do your editing — for a mere £350. The EDR unit sits behind your VT100 (or compatible) terminal, initially in transparent mode allowing direct communication with the host. When you activate the editor, the file is loaded into the EDR unit, and you can quickly and easily edit, while the host is free to serve other users. Being a dedicated unit, response is very fast. On exit the file is returned to the host, and saved to disk, while the EDR processor returns to transparent mode. A unique feature allows you to return to edit mode, using the file still held in local memory.

Andelos Systems

(0635) 201150

Solina, Bucklebury Alley, Cold Ash, Newbury, Berkshire RG16 9NN
DEC, PDP-11, LSI-11, KED, EDT, BT100 are trademarks of Digital Equipment
EDR, ENDELLOS are trademarks of Andelos Systems


CIRCLE 93 FOR FURTHER DETAILS.

PINEAPPLE SOFTWARE

Programs for the BBC model 'B' with disc drive with
FREE updating service on all software

DIAGRAM

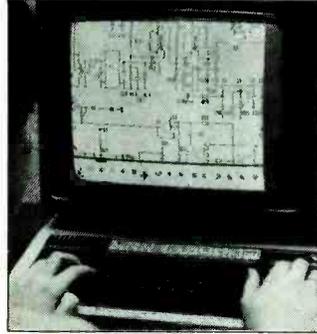• A program which allows you to store very large diagrams — up to 39 mode 0 screens — and view or edit them by SCROLLING the computer screen around over any part of the diagram



FEATURES

- Draw diagrams, schematics, plans etc. in any aspect ratio, e.g. 10:3, 2:12 screens.
- Access any part of the diagram rapidly by entering an index name, e.g. TR6, R5 etc., to display a specific section of the diagram, and then scroll around to any other part of the diagram using the cursor keys.
- Up to 128 icons may be predefined for each diagram, e.g. Transistors, resistor etc., in full mode 0 definition, up to 32 pixels horizontally by 24 vertically.
- Hard copy printouts in varying print sizes up to 9 mode 0 screens on an A4 size sheet, compatible with most dot matrix printers.
- Many other features including, selectable display colours, comprehensive line drawing facilities, TAB settings, etc.
- Disc contains sample diagrams and two versions of the program, one of which will work from a 16k sideways RAM.
- Comprehensive instruction manual.

£25

including P & P

Supplied only on disc - 40T/80T compatible


All orders sent by return of post.

**PINEAPPLE SOFTWARE, 39 Brownlea Gdns.
Seven Kings, Ilford, Essex IG3 9NL**

CIRCLE 91 FOR FURTHER DETAILS.

FYLDE

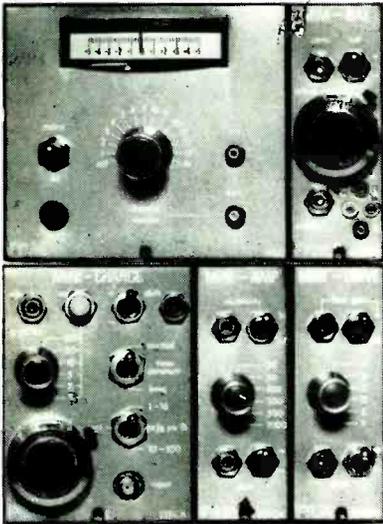TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules — mains or dc option single cases and up to 17 modules in standard 19" crates small size — low weight — realistic prices.

FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

CIRCLE 59 FOR FURTHER DETAILS.

OSCILLOSCOPES

GOULD OS4000 DIGITAL STORAGE Dual Trace	£650
GOULD OS3300B. Dual Trace 50MHZ Delay Sweep	£400
TELEQUIPMENT D83 Dual Trace 50MHZ Delay Sweep	£400
PHILIPS PM3370 Dual Trace 150MHZ Delay Sweep	£375
COSSOR CDU150 Dual Trace 35MHZ Delay Sweep	£200
S.E. LABS SM111 Dual Trace 18MHZ AC or external DC operation	£175
EX-MINISTRY CT436 Dual Beam 6MHZ	£75

SIGNAL GENERATORS

HEWLETT PACKARD 620A 7 — 11 GHZ	£350
HEWLETT PACKARD 618B 3.8 — 7.6 GHZ	£350
MARCONI TF1060/2 450 — 1250MHZ	£150
MARCONI TF2008 AM/FM 10KHZ — 510MHZ	£1,200
MARCONI TF1066B/1. AM/FM 10 — 470MHZ	£300
MARCONI TF995A/2. AM/FM 1.5 — 220 MHZ	£200
MARCONI TF144H/4 10KHZ — 72MHZ	£65

MULTIMETERS

PHILIPS DMM 2517. 4 digit. Autoranging etc.	£95
Complete with Batteries, Leads (Un-used) P&P	£5
AVO 8 Mk5. Complete with Batteries, leads & carrying case. P&P £7.	£90
AVO TEST SET No 1. (Very similar to AVO 8X)	£80
Complete with Batteries, leads & carrying case. P&P £7	
AVO MULTIMINOR. Complete with Batteries, leads & carrying case. P&P £3	£22.50
MARCONI TF2600 VALVE VOLTMETER 12 ranges 1mV — 300V FSD.	£75
* KINGSHILL STABILISED PSU Model 500. 0 — 60V, 0 — 0.5Amps. Current Limiting. Metered. P&P £7	£40
* VARIAC 5 AMP. Input 240V. Output 0 — 265V. Cased. P&P £7	£20
* CROYDON RESISTANCE BOX — MANAGIN. 0.1 — 1111 Ohms (4 decade) Un-used. P&P £7	£25

All above Instruments in Working Order and Supplied with Manual (* — No Manual)

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605. Dual Trace 60MHZ Delay Sweep. Component Tester	£15
HAMEG OSCILLOSCOPE 203.5. Dual Trace 20MHZ Component Tester	£264
BLACK STAR FREQUENCY COUNTERS. P&P £4	
Meteor 100 — 100 MHZ	£99
Meteor 600 — 600 MHZ	£126
Meteor 1000 — 1GHZ	£175
BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle 0.1HZ — 500KHZ. P&P £4	£110
HUNG CHANG DMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4	£33.50
MULTIMETER type U4324. 33 ranges. Complete with batteries and leads. P&P £4	£16
OSCILLOSCOPES PROBES. Switched X1, X10. P&P £2	£11

TANDON 5 1/4" FLOPPY DISC DRIVES 1/2 HEIGHT

Single Sided Double Density	£75
Double Sided Double Density	£100
Brand New. Complete with information p&p	£5

STEPPER MOTORS

Type 1. 200 Steps 4 Phase (5 wire) 12/24V 25oz inch. 2 1/2" dia	£15
Type 2. 6/12 Steps 3 Phase 12/24V. 1 1/2" dia	£2 ea 5 for
£7.50	
Type 3. 24 Steps 4 wire 5V 3.3A 0-250rpm 0-200PPS 2 1/2" dia	£10 ea
Type 4. 200 Steps 120V (3 wire) 25oz inch. 2 1/2" dia	£4
P&P and VAT extra	

This IS A VERY SMALL SAMPLE OF STOCK, SAE Or Telephone for LISTS
Please check availability before ordering.
Carriage all units £10
VAT to be added to Total of Goods & Carriage

STEWART OF READING



110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: 0734 68041

Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

CIRCLE 87 FOR FURTHER DETAILS.

ELECTRONICS & WIRELESS WORLD MAY 1985

LIQUID CRYSTALS

I would like to draw your readers' attention to a discovery made in 1964 that liquid crystals mentioned in a number of your articles are not related to the liquid phase at all. These useful materials are anisotropic organic molecules which form a special phase of crystallites just below the freezing point of the liquid phase. Their correct description should be fluid crystals or fluid crystallites. The term liquid is entirely misleading; the term crystal or crystallite is correct and it shows that the properties of these materials are closely associated with the more familiar crystallites of the solid phase, especially when close to the melting point. It is well known that many solids are very plastic near the melting point and the fluid crystallites used in electronic displays exhibit these properties of fluidity and crystallinity which are not found in the liquid phase. This misleading term of liquid crystals should be replaced by the correct term FLUID CRYSTALS.

W.P. Holland
British Nuclear Fuels Ltd
Sellafield
Cumbria

LOGIC SYMBOLS

I awaited with interest your informative article dealing with new logic symbols. It eventually confirmed my worst misgivings.

For years the government has tried to foist B.S. (British Silly) symbols upon the industry with a delightful lack of success except upon those unfortunate enough to be working on government contracts, where it was made a condition of contract. One is tempted to be alarmed however, when normally rational people such as the Americans endorse such symbols as the ones reported in the article. The author states that international agreement has been reached, consultations have been held, etc. Whoever asks the opinion of the average engineer? There is far too much government time and money spent on these committees who are clearly out of touch with real life, and seek to impose new methods regardless of

consequence.

There is a growing madness to symbolize everything today, even when a plain English identifier is much clearer, and frequently takes less space. An excellent example being any modern car. Try looking for a switch marked "heater", and I guarantee failure. You may however find drawings of palm trees, wavy lines, a perspiring brow, or whatever silly idea came into the designer's head at the time!

Your author states that there is no point in "sticking one's head in the sand". I quite agree. We must resist this nonsense NOW!

L. Hayward
Wareham
Dorset

MOBILE RADIO

I pity the communications of your nationalized power industries who will be forced to work on Band 3 (your issue Dec. 1984)

Also noticeable in your article on mobile radio systems is the lack of mention on 'Trunking' or the use of higher frequencies for public utilities.

Poor old 'Blighty', always behind the times.

P. Hirschmaun
Haifa
Israel

CAMPAIGN FOR REAL A.M.

The article about the heated rear window car aerial (*E&WW* Feb. 1985) covered the questions of sensitivity and directivity in some detail but did not mention the inevitable degradation of the strong signal performance of receivers resulting from the use of untuned r.f. amplifiers.

It would be a pity if the widespread use of demister aerials became one more nail in the coffin of l.f./m.f. broadcasting, but it seems that each new development leads to lower quality l.f./m.f. reception.

Even the unity gain voltage follower used in the demister aerial is likely to cause significant degradation when used with a good quality receiver near powerful m.f. transmitters. Regrettably however few good quality m.f./

l.f. car receivers exist.

The replacement of valves by semiconductors in r.f., mixer, i.f. and especially detector stages has done much to increase distortion and generate spurious whistles.

Developments in linear i.c.s have resulted in considerable improvements, particularly in a.m. detectors but another new development — varicap diode tuning on m.f./l.f. — has definitely been a retrograde step in areas where l.f./m.f. signals are strong.

I have heard one expensive frequency synthesized car radio/cassette player which uses an untuned buffer amplifier on m.f./l.f. between its aerial input and its first varicap diode-tuned circuit and which produces severe distortion on m.f. BBC Radios 1, 2, and 3 within a 15km radius of the Brookmans Park transmitters. This only goes to show that microprocessor controlled wizardry with 18 preset stations (6 on l.f.!) is no substitute for good r.f. design!

On most commercially produced receivers, m.f./l.f. is something of a token gesture with excessive harmonic distortion and an audio bandwidth of 2kHz or so. This leads to the mistaken belief among many listeners that the resulting poor sound quality is an inherent limitation of m.f./l.f. broadcasting, and exaggerates the advantages of v.h.f. M.f./l.f. still has a place, particularly in vehicles and particularly in Britain where certain programmes are not available on v.h.f.

This sad state of affairs prompted me to construct an m.f./l.f. car receiver which did not suffer from the shortcomings of commercially available models in the strong signal area where I live. The design which uses a Mullard TDA1072 a.m. receiver i.c. with permeability tuning and ceramic i.f. filter gives remarkably good sound quality but suffers from one annoying spurious response which is confined to the Barnet area. When receiving BBC Radio 1 on 1089kHz from Brookmans Park, the signal from IBA Capital Radio on 1548kHz from Saffron Green near Barnet causes a 459kHz beat frequency to be generated within the i.c. With either a 455

or 465kHz i.f. this results in an annoying whistle. Beat notes are also audible on weak stations at the l.f. end of the m.f. band. Within the receiver the problem appears to be due to the lack of provision for an r.f. tuned circuit between the r.f. amplifier and mixer stages of the TDA1072, but it is a pity that frequency planning has led to two closely sited m.f. transmitters with a frequency difference of 459kHz.

To sum up, the requirements for an m.f./l.f. car receiver with good handling of strong signals appear to be as follows:

- Permeability, not varicap tuning.
- R.f. amplifier with tuned input and output and NO untuned pre-amplifier stage.
- Good dynamic range in r.f., mixer and i.f. stages coupled with wide a.g.c. range and good detector linearity.

Unfortunately no such receiver appears to exist commercially, presumably because the majority of listeners do not live close to powerful m.f. transmitters or because they believe whistles which CHANGE their pitch when tuning to be an inherent limitation of m.f./l.f. broadcasting, which they are not.

Have any other readers in South Herts found a solution?
D.M. Lauder
Barnet
Hertfordshire

THE CATT ANOMALY

I feel I must assert that I really exist. I was in no position to protest when my parents devised my ridiculous name.

Now, following Ouida Dogg, who turned up again in January, we find Weaver-Mowes joining the act in February. This latest joker purports to be supporting me strongly.

The storm-troopers for the Establishment are happy to be identified, but dissidents tend to feel they need some camouflage. It's short-sighted, because, looking through back numbers, I find that the mean-free-path of the Establishment running-dogs is frighteningly short.

Referring to the W-M letter in February, p.77, I think the most convincing approach to

the "Catt anomaly" (*WW* Sept. 84, p.48) is to concentrate on the electric *charge* on the bottom wire. *W-M* discusses an associated anomaly; the problem of how the electric *current* can come up to scratch. I want people to be forced to face up to the more glaring problem of *charge*. I suggest that the problem of *current* be termed the "Mouse anomaly".

When referring to the problem more generally, one would call it the "Catt and Mouse anomaly". In Feb 85 you published a letter from G. Berzins which demonstrates a failure of comprehension which may be widespread, and so merits discussion. He thinks it is possible for the energy in a TEM wave guided by two conductors, to be transferred by some mechanism within the dielectric. This notion leads to a *reductio ad absurdum*.

Consider a parallel plate characteristic line of characteristic impedance 10 ohms. A TEM step of amplitude 100 volts is travelling down between the conductors. Power is being transferred at the rate of 1,000 watts. According to Theories N or H, electric current and electric charge exist in/on the two conductors.

Now consider a similar parallel plate transmission line lying immediately beneath the lower conductor. Again, it has a characteristic impedance of 10 ohms and a TEM step of 100 volts is travelling down between the conductors. Electric current and charge exist in/on the two conductors. The current and charge in the new upper conductor is exactly equal and opposite to that in the lower conductor of the original transmission line, immediately above it. Now all theories will claim that the activity in each of the four conductors is similar. If this activity is the mechanism for energy transfer, then total energy transfer, 2,000 watts, is made up from four contributions.

Now supposing the middle two conductors are very close together, and they become closer. Still we have four contributions to the energy transfer. Now reduce the middle two conductors to wafer thin, and then remove them. (During this process, the activity in top and bottom conductors will not change). Hey, presto! Current and

charge in the two middle conductors cancel to zero, and the same activity in the surviving top and bottom conductors, previously responsible for the transfer of only 1,000 watts, now transfers 2,000 watts!

Ivor Catt
St Albans
Hertfordshire

D.C. SUPPLIES

Having read Dr K.L. Smith's article on D.C. Supplies from *AC Sources* (Oct. 1984 p.63), it would appear that some very important omissions have been made.

There seems to be an implicit assumption that there is a direct, linear relationship between d.c. load current and secondary winding current and the losses which arise therefrom.

Surely, if d.c. supplies are being considered, then these supplies would embody output filtering (unless the end object is, say, a very crude battery charger). That being the case, then the effects of the output filter must be considered in the design calculations for the transformer. This is particularly so in relation to the magnitude of the conduction angle of the rectifiers and the resulting size of the peak current flowing in the rectifier/secondary winding. It is the size of this peak current (very much larger than the mean current) which dictates the cross-sectional area of the wire to be employed for the winding and the consequent losses.

It is my experience that, unless this consideration is 'built' into the design and then worked backwards toward the primary winding requirements, then a poor design is inevitable. A.M. Wheeler
West Mersea
Essex

BASIC PHYSICS

A connecting thread seems to join this month's (January 1985) correspondence items under the headings "Displacement Current", "Roots of Relativity", "Energy Transfer", and "Electric Charge from a Radio Wave"; they all present arguments over the uncertainties of the fundamental principles of physics.

I wonder, is it possible that

some of our doubts arise because of over-eagerness at the outset to seize upon the first plausible explanation we happen upon, just as a panic-stricken shipwreck victim grasps at anything? Indeed our gratification in being able to grasp an idea seems to cause us to clutch it as if drowning would result from losing it!

Perhaps I may be allowed to offer a couple of remarks on specific points; first, from Chris Parton; "there is a law of physics to the effect that the velocity of light is the same for all observers, and I believe that the conclusion of Michelson's and Morley's celebrated experiment. . . that the velocity of the propagating medium. . . does not affect the observed velocity of light." This assertion by Chris Parton seems to have many fearful souls desperately hanging on to it, yet can we say that the second postulate of relativity theory, which was casually "promoted" to this status from that of a conjecture by Albert Einstein in his apparently little-read paper (ref.1), can be further elevated to a law, to stand with, for example, the Laws of Motion as announced with unqualified assurance by Isaac Newton? Chris Parton "believes" the conclusion generally held for the ether-drift experiment; others could just as well believe a contrary or alternative conclusion can be drawn, for it is not difficult to discern the inherent weaknesses in the experiment's design (ref.3), Michelson's interferometer, for one instance, was rigidly spaced from the emitter used, which means that if every emitter is absolutely immobile in its dedicated ethereal medium for dispersal of its individual radiation, then the obtained results are simply accounted for. It is true the Einstein discounted this possibility, but he gave no grounds for his judgement; does no-one consider he would have removed one cause for doubt had he done so?

And second, in his letter A.J. Clayton took great pains with his detailed discussion of the "imaginary experiment" with which Einstein endowed his "Popular Exposition" (ref.2.), featuring a train hit by synchronized lightning-strikes. Speaking for myself however, I think it would have been quite

sufficient for him to simply draw our attention to Einstein's failure to allocate the radiation from the electrostatic discharges to a medium, which would have a status of motion with respect to all the other elements of the model — train, track, electric fields, etc. If the radiation were not to be propagated in accordance with the regulating characteristics of a medium, either substantial or ethereal, then how was the energy to be transferred — possibly in association with a material displacement in accordance with the Laws of Motion? Since Einstein left us with this problem, the explanatory value of his treatise is in some doubt. Incidentally, there are other serious problems elsewhere within this book, which was intended for the "layman's" edification!

All such concepts as displacement current, electric and magnetic force fields, energy transportation across a vacuum, ethereal media, time with properties of substance — and all such terms of an all-embracing theoretical schema — are ideally inter-related in a mode which reflects precisely action in the physical universe; so when a disturbing lack of correspondence becomes obvious, it is surely the result of human ineptitude? To what extent to our knowledge then to be advanced by ingenuous attempts at the obscuration of our misinterpretations?

The late Prof. Herbert Dingle suggested in "Science at the Crossroads", that Einstein created his much-admired theories to cover the defects of another theory, that of Clerk Maxwell; these in turn may well be covering other misconceptions (vide Ivor Catt in the pages of this journal).

It seems possible that modern physics is based on a schema which was put together without proper circumspection, just about the turn of the century, when instruments were penetrating facets of phenomena which revealed embarrassing shortcomings in the accepted wisdom; this at the very time when public attention was turning to science for guidance in a rapidly developing world of technological innovation. Perhaps "panic" would be too strong a word to introduce here, but now as the "dust of

the old cosmology" begins to settle, should we not be attempting to gain a deeper, wider perspective over the universe?

C.B.V. Francksen
Farnborough
Hampshire

References

1. "On the Electrodynamics of Moving Bodies", Albert Einstein, *Annalen der Physik* 17, 1905. (Translation available in "The Principle of Relativity", Dover Publications Inc., 1952).
2. "Relativity, the Special and the General Theory, A Popular Exposition", Albert Einstein, Methuen & Co., London, 1920.
3. "Michelson Morley Experiment", R.S. Shankland, Case Institute of Technology, Cleveland, Ohio, 1963.

RELATIVITY

Had A.H. Winterflood¹ read my letter² on the M.M. experiment, and understood it like Osinga³, he would have found no need for his proposed measurement for it was done in 1887. Science does accept the M.M. experiment which enshrines the additive theory doesn't it?

If he can prove that this experiment does not rely on the additive theory then we should be told about it for science will be turned on its head. My earlier letter should also relieve Theocharis's mental indigestion!⁴

Alex Jones
Swanage
Dorset

References

1. Letters Feb. 1985.
2. Jones, Letters April 1984.
3. Osinga, Letters July 1984.
4. Theocharis, Letters Feb. 1985.

Simultaneity refers to events having the same time but not necessarily the same place: if they also happen to have the same place, such a 'double event', at a single point in space-time, would be recorded as such by all observers, whatever their position and velocity (rest assured, Mr Marquis). But when two events are separated in space or time, the measurement of that separation depends on the velocity of the observer; no one observer can be 'right', not even the one that is 'at rest', for how can one be at rest with

an event that has only one place and one time? The confusion over this point has been further confused by Dr Scott-Murray's change of concepts in mid-stream, even though his diagrams are excellent examples of explanatory geometry. The trouble with his argument is that it is not clear whether *he* means simultaneity by $\Delta t=0$ or by $t_A=t_B$. This leads to my second point. Figs 2 and 3 purport to show the same sequence of events as observed by M and M' respectively, given that *c* is invariant. But they *cannot* show the same experiment because the delay between either observer's receipt of the two flashes is zero in one diagram and non-zero in the other.

The only *conformal* transformation from M to M' is shown by Fig. 5, where the events, and the invariance of *c*, are preserved, at the cost of a distortion of space-time that is perfectly 'real' to each observer.

Scott-Murray suggests that it would be easier to accept Fig. 4 and assume a ballistic theory of light, presumably explaining the negative result of the M-M experiment by postulating (with Messrs Winterflood, Aspden et al) that photons adjust to *c* only near an observer, having approached from a moving source with a dispersion of velocities. Such a dispersion would easily have been spotted from observing rotating systems like distant galaxies and binary stars. The transformation shown in Fig. 5 (or 6) is the only one that fits the facts — until some new facts turn up.

R.V. Harvey
Grasmere
Cumbria

With reference to the article "Einstein's Trains" by W.A. Scott Murray in Feedback column of *Wireless World*, February 85 issue, I have the following observation to make.

Einstein had taken pains to establish the 'relativity of simultaneity' by showing that events which are simultaneous to the observer in one frame are not simultaneous to another observer in another frame, and hence time is relative. However, even in the same reference frame, events which appear as simultaneous to one observer, need not appear as

simultaneous to another observer situated at a different point closer to one of the places from where light originates. For instance, in the example discussed by Einstein, if an observer is situated closer to A between A & M, he is bound to observe the lightning at A earlier than the lightning at B. Thus what appears to be simultaneous to the observer at M does not appear as simultaneous to another observer even in the same frame. Thus it is not at all necessary to establish the relativity of simultaneity by introducing another observer M' in a running train. As time is constant in a particular reference frame, the fact that an event appearing as simultaneous to one observer is not simultaneous to another observer in the same frame does not establish the relativity of time.

Time is a universal phenomenon and the relativity of time is abhorrent to the common sense, as rightly pointed out by W.A. Scott Murray in his articles in the 'Heretics Guide' series. The Michelson-Morley experiment, which was the forerunner for these mind-boggling theories of space contraction and time contraction, had only established the non-existence of an ether medium for the propagation of light, as the velocity of light was found to be the same in all directions as observed on earth. It should be possible for physicists to establish that it is not necessary to accept length contraction and time contraction in order to explain the observed constancy of the velocity of light. As light is a form of energy and is not matter, a moving light source cannot add its velocity to that of light. The Newtonian laws of addition of velocities apply only to objects of matter having mass and cannot apply to light which is a form of energy always in motion and not having a definite mass.

K. Ganesh
Director, Transmission Project
Madras
India

I thoroughly enjoyed Dr Murray's series "Heretic's Guide to Modern Physics" (*WW* Jun 82 to Jun 83); challenge and provocation are, I believe, important to the evolution of

Scientific Theory. I was disappointed, however, to read Dr Murray's later article "The Roots of Relativity" (May 84), since his good intentions were spoiled by a flaw in his reasoning. Although this error was pointed out by A.J. Clayton (Feedback Jan 85). I therefore feel moved to comment myself.

In "Einstein's Trains", Dr Murray deduces from a consideration of the Second Postulate that "... the situation observed by M' in his own coordinates must be as shown in Fig. 3. where the two flashes arrive at the same instant. . ." But WHY? The Second Postulate implies only that the light approaching M' from both flashes must be *c* in his own frame of reference, as shown correctly in the diagram. What logic does Dr Murray use to show in addition that flashes A and B both occur at time $t'=0$? The very purpose of the 'trains experiment' was to illustrate that one's intuitive notion of simultaneity is inconsistent with the consequences of the Second Postulate. Just because Dr Murray makes an intuitive assumption about simultaneity, it does not follow that Einstein's 'trains experiment' is inconsistent with his Second Postulate.

The view from M is that while the light from the two flashes is propagating through space, M' will edge a little closer to B and a little farther from A. M will DEDUCE therefore that the flash from B will be received by M' before the flash from A, arguing purely from a consideration of the path lengths involved, and without making any presumption about the velocity of light relative to M'. Now by applying the logic of causality, we argue that M' must agree, at least qualitatively, that the flash from B is seen before that from A. The situation is not therefore as shown in Dr Murray's Fig. 3.

Life would indeed be much simpler if we had transformations which did not involve square-roots, but what is wrong with challenging our pedestrian notions of space and time, and developing a theory which is really provocative. I feel Einstein may already have done so.
G.P. Clark
Castle Donington
Derbyshire

VISIT OR
PHONE
OPEN 6 DAYS
A WEEK
ALL STOCKS
ON DISPLAY

HENRY'S AUDIO ELECTRONICS



Equipment • Communications • Computers • Components

INSTRUMENTS STOCKED

SCOPES (UK C/P £6.50)

*HAMEG	
HM203/5 Dual 20MHZ	£264.00
HM204 Dual 20MHZ	£365.00
HM605 Dual 60MHZ	£515.00
*CROTECH	
3030 15MHZ Portable	£179.00
3035 15MHZ Bench	£198.00
3132 Dual 20MHZ	£297.00
(*HAMEG/CROTECH INCLUDE COMPONENT TESTERS)	
HITACHI	
V212 Dual 20MHZ	£329.00
V222 Dual 20MHZ	£395.00
V223 Dual 20MHZ	£450.00
V423 Dual 40MHZ	£650.00
V650 Dual 60MHZ	£880.00
*with probes	

THANDAR

SC110A 10MHZ battery/mains	£175.00
----------------------------	---------

SCOPE PROBES

X1-X10	£10.00
--------	--------

GENERATORS (UK C/P £1.00)

(F) Function (P) Pulse (A) Audio (R) RF	
500 0.1HZ-500KHZ (F)	£110.00
TG101 0.02HZ-200KHZ (F)	£110.00
TG102 0.2HZ-2MHZ (F)	£160.00
TG501 0.005HZ-5MHZ (F)	£295.00
TG105 5HZ-5MHZ (P)	£105.00
TG502 As TG 501 + SWEEP (F)	£495.00
TG503 As TG501 + PULSE (F) (P)	£495.00
AC202A 20HZ-200KHZ (A)	£95.00
LA027 10HZ-1MHZ (A)	£115.00
SG402 100HZ-30MHZ (R)	£77.00
LSG17 100HZ-150MHZ (R)	£115.00
AG203 10HZ-1MHZ (A)	£149.00

POWER SUPPLIES (UK C/P £2.00)

* Twin meter • Single meter (switched) + Digital	
+241 0/30v 0/1AMP	£33.00
+242 0/30v 0/3AMP	£52.13
+154 5/15v 0/4AMP	£43.43
*230N 0/30v 0/1AMP	£97.74
*330N 0/30v 0/3AMP	£178.90
*2302 0/30v 0/2AMP + 5v 1A AND PULSE GEN	£230.00
+ PL310 0/30v 1AMP	£118.00
+ PL320 0/30v 2AMP	£145.00
+ PL154 0/15v 4AMP	£149.00

COUNTERS (UK C/P £1.00)

+ LED + LCD A# 8 digit	
+ 100 100MHZ	£99.00
+ 600 600MHZ	£126.00
+ 1000 1000MHZ	£175.00
+ TF600 600MHZ	£132.50
+ TF200 200MHZ	£175.00

TV EQUIPMENT (UK C/P £1.00)

TC40 VHF/UHF F/S meter	£208.00
LTC910A Tube Tester	£199.00
MC321 PAL(UK) Colour gen.	£252.00
MC328 PAL(B) Colour gen.	£252.00
LHM80A 40Kv meter	£30.00

STOCK SELECTION

(*UK C/P 65p *UK C/P £1.50)	
•LP1 10MHZ Logic Probe	£24.95
•DP70 30MHZ Logic Probe	£25.00
•DP71 50MHZ Logic Probe	£52.00
•ST300 AC Clamp Meter	£30.87
•YF501 Elec. Ins. Tester	£59.13
•DM6013 Digital Cap Meter	£60.43
•KDM6 200MHZ TR DIP Meter	£48.70
*LCR740 LCR Bridge	£230.00
*OM358 Scope Multiplexer	£169.00
•HZ65 Scope Comp. Tester	£24.00
•TC1 Transistor Tester	£24.30
•CM200 Bench Dig. Cap. Tester	£89.00

HAND DMM'S 3 1/2 digit (UK C/P 65p)

(R) Rotary (PB) Push-Button • With case	
3500 10A AC/DC (R)	£36.75
3510 Plus Hfe & Buzzer (R)	£40.45
ME540 10A AC/DC Auto/Man (R)	£41.50
3100 Pentype	£39.75
•KD615 10A DC Hfe Tester (R)	£34.75
6010 10A AC/DC (PB)	£37.83
7030 10A AC/DC 0.1% (PB)	£46.91
•KD55C 10A AC/DC (R)	£38.70
•DM3350 10A AC/DC Auto (R)	£43.44
•KDS28T Miniature with Hfe test	£29.52

PLUS BENCH DMM'S IN STOCK THURBY • THANDAR • SOAR • METRIX • ANALOGUE MULTIMETERS • LARGE RANGE IN STOCK

SOFTWARE

(Please state format required and machine)

MDIS Intelligent Disassembler for all CP/m based	£50.00
IVC HI-RES Provides Pseudo high resolution graphics	£15.00
DISKPN (VG3) Low cost word processor for multiboard based overlays for diskpen	£50.00
MAXIFILE	£20.00
SPOOLER	£15.00
HENRY'S CP/m UTILITIES	£15.00
41 Programs	
ALL DISC Variable disc format for GEMINI/NASCOM CP/m's	£150.00
PREZTEL 2 Interface Galaxy or Nascom to Modem for use with BT Prestel service	£26.04

ASC11 KEYBOARDS

69S D5 Compact 64 Key + 5 function keys. Hall effect keyboard with reprogrammable (2716) ASC11 output decoder EPROM. Steel key frame for good rigidity. Negative going strobe. Requires + 5 volt + 12 volt supplies. (UK C/P £1.00)	£21.70
---	--------

2070 COMPACT 58 KEY KEYBOARD

Contactless capacitive high reliability keys. Full 12B ASC11 codes. Steel key frame for positive rigidity. 1mS strobe, single + 5 volt supply. Repeat key, control and caps. lock. (UK C/P £1.00)	£28.26
---	--------

COMPUTER POWER SUPPLY

Switched mode. Stabilised. Self protecting S/C protected, etc. 220/240V AC + 5V 3.3A + 12V 2.4A. 40% cycle - 5V 0.5A - 12V 0.5A. Suitable Apple replacement (UK C/P £1.50)	£50.00
--	--------

ITT 2020 CABINET

Professional computer case with keyboard cutout. 18" x 15.5" x 4.5" (front slopes). Ideal for single board computers like the Nascom or Gemini Multi-board (3 cards, etc). Very heavy gauge (2.5") plastic with metal base. Attractive silver grey finish. (UK C/P £1.78)	£19.95
---	--------

MODEM CARDS/COUPLER

Brand new. Tested, answer and originate 300 BAUD uncased acoustic modem card by famous manufacturer. RS232 Input/output, power supply + / - 12V at 180mA. Requires 2 magnetic earpieces. 2 switches. 2 LEDs and connectors to complete. Data supplied. Card only	£26.04
Card and remainder of small components	£29.09
Telephone Direct Line coupler type LTU11 MKII. Suitable for direct coupling PRESTEL adaptors and the above acoustic modems. Integral line select and autodial relays requiring TTL inputs data supply.	£13.00
1200 BAUD receive 75 BAUD send direct coupled modem, or PRESTEL. Requires + 5V supply with TTL inputs for data. Line select and autodial. LTU 11 direct coupler required. See above. Data supplied. PRESTEL modem card.	£13.00

COMPUTER FANS

(UK C/P 60p each. £1.00 per pair)	
4% 220/230V AC Brand new	£6.52
4% 220/240V AC Ex-units	£4.78
4% 110/115V AC Ex-units	£4.35

CASSETTE MECHANISMS

Fitted counter. Motor. Stereo record and erase heads. Autostop, solenoid. Brand new available 6V DC or 12V DC (state which). (UK C/P 65p)	£5.17
ALSO miniature stereo cassette replay mechanism 12v. 105 x 100 x 40mm. (UK C/P 65p)	£4.78

LARGE STOCKS OF COMPONENTS FOR UK AND EXPORT. ENQUIRIES INVITED

INSTRUMENTS CATALOGUE

(Large 25p sae) Free to Companies/Colleges, etc. (Upon written request).

SUPPLIERS OF ELECTRONICS FOR EVERY PURPOSE (Official Orders Welcome (subject to confirmation))

ORDER BY POST OR PHONE

301 Edgware Road, London W2
Test Equipment, Audio,
Communications 01-724 3564

404 Edgware Road, London W2
Computers 01-402 6822
Equipment 01-724 0323
Components 01-723 1008

ASK HENRY'S FIRST

ALL PRICES EXCLUDE VAT

Up to £1000 instant credit Available through Lombard Tricity Finance

CALL IN AND SEE FOR YOURSELF

CIRCLE 22 FOR FURTHER DETAILS.

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns	1.25	1.15	1.10
4164 150ns Not Texas	2.65	2.45	2.35
2114 200ns Low Power	1.75	1.60	1.55
2016 150ns Like 6116	3.65	3.35	3.10
6116 200ns Low power	7.75	Call	Call
6264 150ns Low power	14.85	13.75	13.20
2716 450ns 5 volt	3.85	3.45	3.30
2732 450ns Intel type	4.75	4.25	4.10
2732A 350ns	5.25	4.69	4.50
2532 450ns Texas type	3.85	3.45	3.30
2764 300ns Suit BBC	5.40	5.00	4.80
27128 300ns Suit BBC	10.50	9.50	8.65

Low profile IC sockets: Pins 814 16 18 20 24 28 40
Pence 12 13 14 16 18 24 27 38

Available now — The ROAM BOARD for the BBC Micro. Reads Roms via a Low Insertion Force Socket and saves their contents as files, then reloads a file into its sideways Ram as required. Full details on request.

74LS series TTL, wide stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.

Please add 50p post & packing to orders under £15 and VAT to total. Access orders by 'phone or mail welcome. Non-Military Government & Educational orders welcome., £15 minimum.

HAPPY MEMORIES (WW),
Newchurch, Kington,
Herefordshire HR5 3QR.
Tel: (054 422) 618

CIRCLE 25 FOR FURTHER DETAILS.

VIDEO TERMINAL BOARD

★ 80 characters × 24 lines ★

Requires ASCII encoded keyboard and monitor to make fully configurable intelligent terminal. Uses 6802 micro and 6845 controller. Program and character generator (7 × 9 matrix with descenders) in two 2716 EPROMs. Full scrolling at 9600 baud with 8 switch selectable rates. RS232 interface.

Bare board with 2 EPROMS and program listing — £48 plus VAT. Assembled and tested — £118 Send for details or CWO to:

A M Electronics
Wood Farm, Leiston, Suffolk IP16 4HT
Tel: 0728 831131

CIRCLE 45 FOR FURTHER DETAILS.

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

R. Henson Ltd.
21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner
Telephone 01 445 2713/0749

CIRCLE 43 FOR FURTHER DETAILS.

Printer buffer

By taking characters from a microcomputer at high speed and sending them to a printer at its leisure, this buffer reduces waiting time from minutes to seconds. It has parallel and serial ports and holds enough text for around twenty A4 sheets.

An annoying quirk of single-user computers which do not boast multi-tasking operation is that when communicating with slow peripherals, their through-put drops to that of the peripheral. Waiting for such a computer to finish working with a typical low-cost printer can seem like an eternity.

The printer buffer alleviates this problem by appearing to the host computer as a high-speed printer. It stores data from the computer in its memory (dynamic ram) as quickly as possible which reduces the waiting time from possibly several minutes to seconds. It then proceeds to send the stored information to the printer at normal speed.

Features

The buffer is built around the Motorola MC6803 eight-bit microprocessor which contains an enhanced 6800 processor with 128 bytes of ram, a 16-bit timer, a serial-communications interface (s.c.i.) and i/o lines. This processor is a rom-less version of the high-density n-mos M6801 family.

Storage capacity of up to 64 432 bytes — the equivalent of approximately twenty A4 pages — is provided by 64K-byte dynamic rams (d-rams). Centronics parallel interfaces and a serial interface using XON/XOFF protocols are used to allow parallel-to-parallel, parallel-to-serial, serial-to-parallel and serial-to-serial data transfers. Only one serial interface has been included, to simplify the design and keep costs low, so concurrent transmission and reception is only possible with the first three modes.

Since the serial port is configured as a terminal, it may be

necessary to exchange the receive and transmit lines in either the printer or printer cable to allow the buffer to operate correctly in serial-to-serial and parallel-to-serial modes. The serial-interface data rate may be switched between 300 and 9600 baud (using S_1) but is the same for transmit and receive lines. It is possible to switch the data rate during serial-to-serial transfers so that data may be loaded from the computer at one rate and unloaded to the printer at another. Computer and printer interfaces can therefore operate at different rates.

Buffer-ready and error leds indicate when the buffer has space available and that a serial communication fault has occurred. An abort key is also included to allow one to prematurely terminate printing in an orderly fashion. The Centronics interface PRIME signal is used to clear the buffer within the printer during an abort sequence.

The software is interrupt driven with separate input, out-

put and memory-refresh tasks. These will appear concurrent, i.e., printing will commence before data input is complete. Furthermore, subsequent files may be sent to the buffer before the current buffer content has been sent out.

Being general purpose, the design could be used as the basis of a variety of microcomputer applications. The address is easily changed and more i/o, eeprom space, etc., could be added. The M6803 processor operates in mode three in this application so its internal ram is not available. However, the 6803 can be made to operate in mode two for applications requiring standby ram, see Motorola MC6801 Reference Manual/MC6801RM(AD2).

Interfaces

Centronics interfaces are handled by an MC6821 peripheral interface adapter (p.i.a.). Use is made of the 6821 automatic handshaking features to generate host acknowledgment, ACK, and printer data strobe, DS, pulses. A BUSY signal is produced at port one, line four (P14) of the 6803 to

by Mike Catherwood



Mike Catherwood graduated from Heriot Watt University in 1980 with an Honours Degree in electrical and electronic engineering, and has since been working with Motorola in East Kilbride. He is currently Systems Engineering Section Manager for single-chip microcontroller products and guides a small team of engineers giving technical advice to potential and existing customers. Mike loves music, hill walking, badminton, good food and real ale — although not always in that order, he points out.

Fig. 1. 6821 Centronics handshake timing applies to both printer output and computer input. Timing with this type of interface is rarely critical.

Fig. 2. In the serial interface, each character sent consists of one start bit, eight data bits and one stop bit. Data rates are determined by a programmable timer within the 6803 microprocessor.

Specification

Two Centronics parallel ports and one serial Modes

Parallel-to-parallel

Parallel-to-serial

Serial-to-serial

Serial-to-parallel

Serial RS232 port

Transmit/receive using

XON/XOFF protocols

300 or 9600 baud

One start, one stop and

eight data bits

Parallel Centronics interfaces

Eight-bit parallel

DS/ACK handshaking

Busy and prime lines

supported

64K-byte circular buffer



6803 microprocessor/6821

p.i.a.

Abort and multiply copy

functions

Error and busy indicators

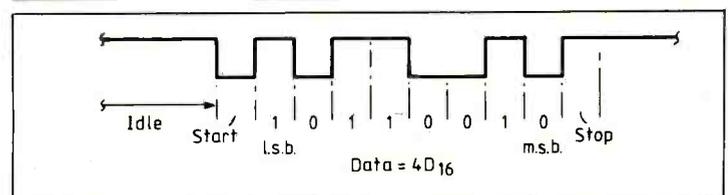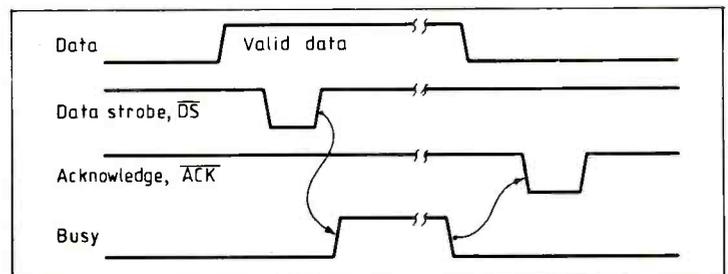

PRINTER BUFFER

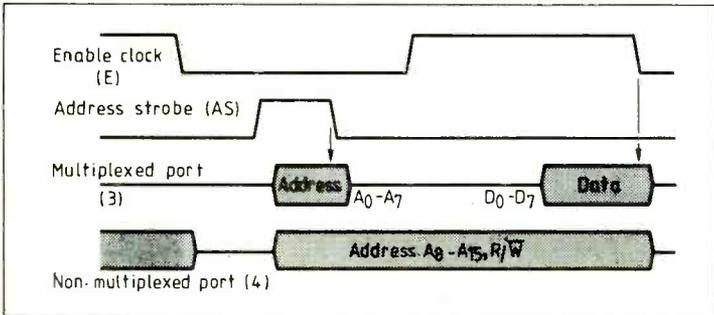


Fig. 3. Multiplexed data/address signal timings for the 6803 microprocessor. Lines are usually multiplexed in this way to make the most of pins on the i.c. package.

Fig. 4. Circuit of the 64K-byte printer buffer (r.h. page). Multiple copies of the buffer content may be made by keeping one's finger on the abort button. When using parallel-to-serial mode, data is actually available on the parallel output port, but the handshake timing may not be used.

Using a microprocessor with built-in serial data facilities and a parallel interface adapter with handshaking, this 64K-byte printer buffer operates with any Centronics or RS232 compatible computer and printer. Software handshaking (XON/XOFF protocol) is used on the serial port.

indicate to the host computer that the buffer is full. Some computers may not use this line. A PRIME line is also provided (P15) to reset the printer.

Figure 1 shows the 6821 handshake timing. Once set up, the data is transferred by pulsing the data strobe signal DS. Data must remain stable while DS is low. There are also associated set-up and hold times to be considered, but timing with this type of interface is rarely critical. Data transfer is acknowledged by the receiver some time later by pulsing the ACK line; some interfaces define a time-out period for this. The interface is now ready for further transfers.

If you intend using very long cables then the p.i.a. lines should be buffered using line drivers. Unbuffered, the 6821 will drive up to around 2m of ribbon cable. It is wise to interleave ground with the signals to remove any coupling effects.

The serial interface uses the full-duplex s.c.i. within the 6803, which operates using a

standard mark/space (n.r.z.) form. It can also support a bi-phase mode of communication, although not in this application. Each character sent consists of one start bit, eight data bits and one stop bit, Fig. 2, and uses the on-chip programmable timer as a data-rate generator. The buffer operates at either 300 or 9600 baud but data rates of between 150 and 76 800 baud are possible using different crystal frequencies and software-selectable prescaler values.

To generate common data rates, a bus frequency of 1.225MHz is necessary (equivalent to a 4.91MHz crystal) which requires the use of a 1.25MHz bus version of the MC6803. Consequently a 1.5MHz MC68A21 is also theoretically required, although it is unlikely that a standard 1MHz part will not do the job if you have one available. If the serial interface is not required, you can use a 4MHz crystal and the slightly cheaper 1MHz bus version of the 6803. The RS232 interface buffer could then also be omitted.

Use of XON/XOFF protocol on the serial port removes the need for any active handshaking lines. It would be relatively easy to add an asynchronous communication interface adapter like the MC6850 to the system to provide an additional serial interface with hardware handshake facility if required.


The XON/XOFF protocol uses

Ascii codes DC1 and DC3 to provide the transmitting device with receiver buffer empty/full status. When the receiver buffer is within a predetermined number of characters of being full (64 characters in this design) the receiver sends Ascii code DC3 to the transmitting system, indicating that transmission should stop fairly soon (XOFF). After a while, the buffer will empty and when sufficient space becomes available (256 characters in this case), the receiver sends Ascii character DC1 to the transmitting system, indicating that it may resume transmission (XON).

Hardware

All members of the 6801 family have a multiplexed address/data bus when in their expanded mode, Fig. 3. Address lines A₀-A₇ are multiplexed with data lines D₀-D₇ on port three. An address-strobe pulse occurs during the low phase of enable signal E. The address is only guaranteed to be valid on port three during the falling edge of AS, at which time it is frozen by an LS373 latch i.c., Fig. 4. Address lines A₈-A₁₅ produced by port four are not multiplexed and are valid throughout most of the enable cycle.

During the E-clock high phase, port three either presents data for writing or expects to see data for reading. Read/write line R/W should only be lowered during the positive E phase to prevent

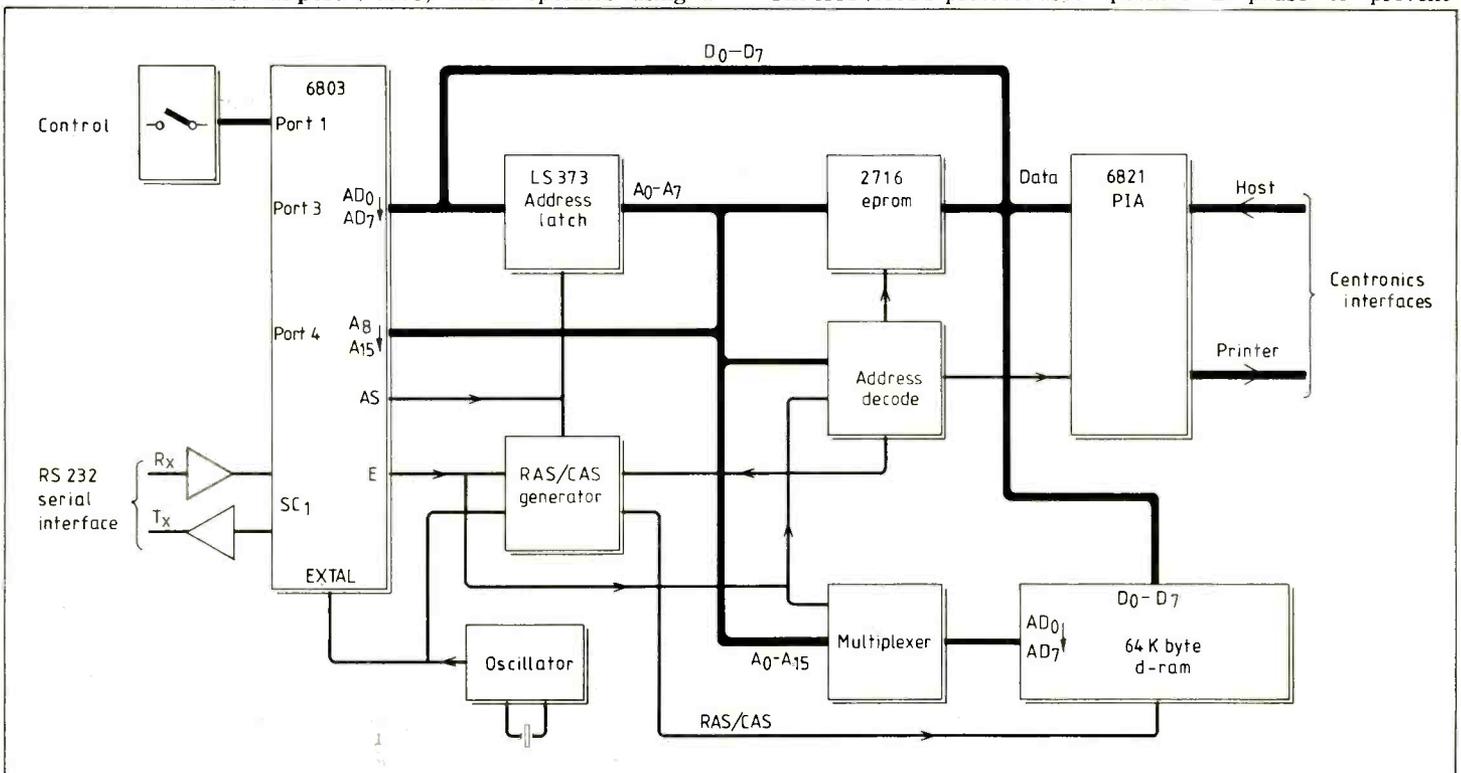

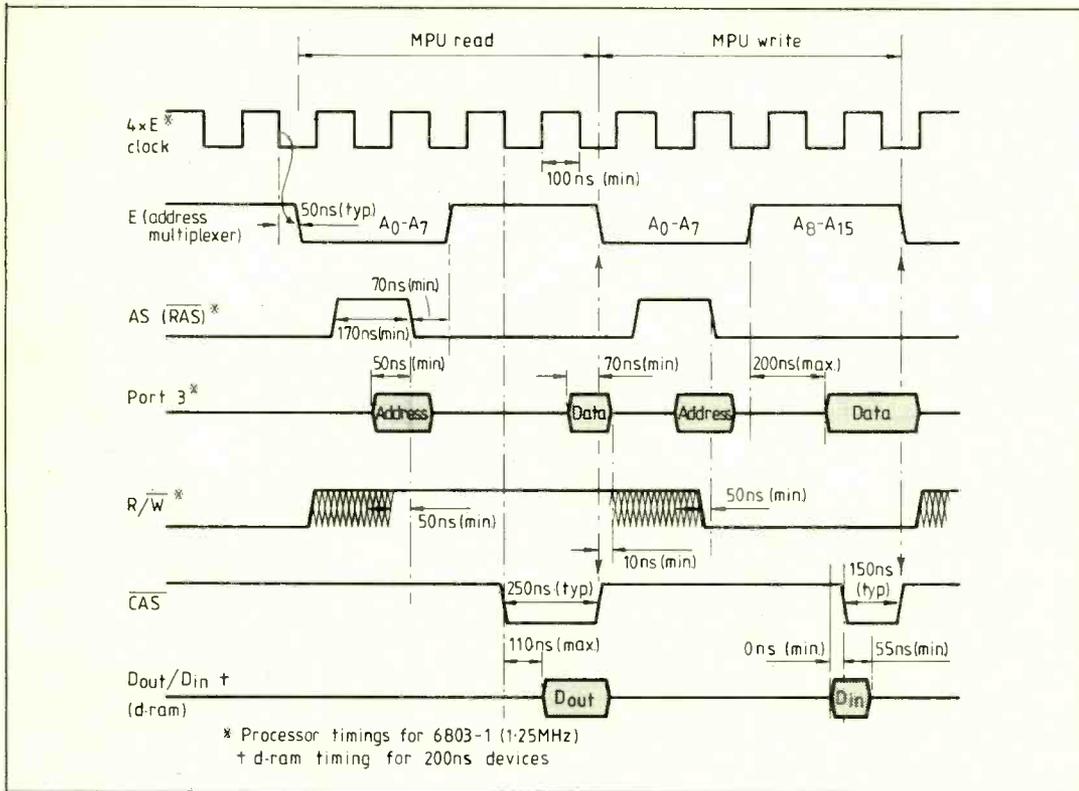


Fig. 5. Printer buffer timing required for dynamic rams.

An address must be multiplexed into the rams in two halves on eight lines. Half of the address is latched by the row-address strobe, RAS, and the second half by the column-address strobe, CAS.

erroneous writing. Data is read by the processor during the E-signal falling edge. As with all multiplexed bus systems, care must be taken to ensure that all device output buffers are disabled during the E-signal low phase, otherwise bus contention will result. Having obtained essentially separate address and data buses, connection of the 2716 eprom and 6821 p.i.a. is easy.

Memory decoding is arranged to keep as much of the 64K-byte address space as possible free for buffer ram while using a minimum of i.cs. As the software is less than 1K-byte long, only half of the 2716 is used; address line A₁₀ is tied low.

Most systems using dynamic ram have d-ram controllers to generate timing signals and to refresh the memory independently. These controllers tend to be costly and as their performance is not essential in this application I chose to use a software refresh technique (described later). As a bonus, the hardware required to implement this is minimal.

To reduce the number of pins used, 64K-bit dynamic rams multiplex address lines A₀₋₇ with lines A₈₋₁₅ using two signals called row-address strobe, RAS, and column address strobe, CAS, Fig. 5. Referring to Fig. 4, the address bus is multiplexed with the E signal using two LS157 quad two-to-one-line multiplexers. The timing of AS allows it to

be used directly as RAS during the low E-signal phase.

Generating CAS is a little more difficult. When the ram is accessed the RAMEN signal is clocked through two D-type latches by the microprocessor input clock. The E signal is derived from the processor clock and is one quarter of its frequency. The D-type devices are however held clear during the E-signal low phase (CAS is held high). In order to meet data set-up times for the processor and d-rams, CAS is also conditioned by the R/W signal. Hence, CAS will only fall if RAMEN is true and the latches have been clocked twice during the high E phase for a write and once for a read.

Propagation delay through the 6803 internal dividers has not been characterized as it is intended that the device is used with its on-chip oscillator, i.e. with a crystal connected between pins one and two. Using the internal oscillator makes the relationship between pins three (EXTAL) and 40 (E) of little consequence. For an injected clock, however, values are typically less than 50ns over the standard temperature range of 0 to 70°C, which is well within the specification for this design using 200ns rams even though it almost unforgivably violates worst-case design practice!

Software, construction and operation will be discussed in a subsequent article.

EVENTS

April 30 to May 2
British Electronic Week. incorporating the All-Electronics Show, Fibre Optics & Electronic Product Design. Olympia, London.

Your Generation, IEE Faraday Lecture. Dominion Theatre, London.

Tickets free on receipt of ann s.a.e. by the Farada Officer, IEE, Station House, Nightingale Road, Hitchin, Herts. SG5 1RJ.

May 1
Personal and Domestic Robots IEE colloquium at the IEE Savoy Place. London WC2R 0BL. Tel: 01-240 1871 Ext. 269

May 2
NDT in undergraduate engineering. IEE discussion meeting. Phone as above

May 3
Image restoration and two-dimensional filtering. IEE colloquium. As above

May 6 to 9
Radar 85. International IEEE/IEE conference in Washington, D.C. Details from Radar 85, 1331 Pennsylvania Avenue NW, Washington DC 20004, USA.

May 7
Fault-tolerant microprocessor control systems. IEE Lecture. Telephone as above. The human contribution to technology: IEE Lecture in Edinburgh. As above.

May 8
Vision modelling. IEE colloquium. As above.

The UK 5000 project. IC design made easy. IEE lecture. As above.

May 13
Software, does it enhance accuracy? IEE discussion meeting. As above.

May 15
Applications of CAD packages to the design of control systems: IEE colloquium. As above.

GTO devices and their applications. IEE colloquium. As above.

May 16
Microwave acoustics and acousto-optics. IEE colloquium. As above.

Intelligent knowledge based systems and Alvey. IEE lecture in Oxford. As above.

May 17
Optical mass data storage. IEE colloquium. As above.

May 20
Applications of MAC to cable. IEE lecture. As above.

May 21 to 23
Sensor 85. Transducer exhibition and conference, Karlsruhe Exhibition Centre, FRG. Network Events Ltd., Tel. 0280 815226.

Silk-screened plated-through p.c.bs for the buffer, currently being manufactured, will cost £14 including vat and UK or overseas postage from Combe Martin Electronics, King Street, Combe Martin, North Devon EX34 0AD. A complete kit of parts, excluding p.c.b. and case, is available from Technomatic Ltd, see advertisers' index.

Hi-Tech components

HI-TECH COMPONENTS, GILRAY ROAD, DISS, NORFOLK. TEL: 0379 4131

6502 FAMILY		8086 FAMILY	
6502	3.50	8086	19.50
6502A	4.95	8088-2	22.50
6520	2.25	8216	1.75
6520A	2.45	8237A-5	23.50
6522	3.25	8251A	6.00
6522A	4.45	8253-5	7.50
6532	5.00	8255A-5	5.50
6532A	5.95	8259A	6.60
6551	5.25	8272	35.00
		8284A	9.50
		80C86	46.65
		80C88	46.65
		82C52	15.68
		82C54	19.04
		82C55A212	9.88
		82C59A	15.22
		82C82	6.26
		82C84A	8.94
		82C88	16.80

6800 FAMILY	
6800	2.50
6802	3.50
6803C	8.40
6809E	6.25
6809P	6.25
6810	1.70
6821	1.70
6840	3.70
6845	7.50
6850	1.70
6862	3.70
6875	8.00
68800	4.30
68809	11.00
68810	1.88
68821	3.70
68840	6.00
68850	2.00
68854	8.75

Z80 FAMILY

Z80ACPU	2.50
Z80ACT	2.50
Z80ADMA7	9.5
Z80API0	2.50
Z80ASIO-0.6.20	
Z80ASIO-1.7.95	
Z80ASIO-2.7.95	
Z80BCPU	5.95
Z80BCTC	5.95
Z80BP10	5.95
Z80BSIO-019.95	
Z80BSIO-119.95	
Z80BSIO-219.95	
Z80SIO-0	6.00
Z80SIO-1	6.00
Z80SIO-2	6.00

MEMORIES — EPROM

2532-300ns	4.95
2532-450ns	3.95
2564-300ns	6.95
2708-450ns	3.95
2716-450ns	3.50
2716-3 RAIL	7.95
2732-350ns	4.95
2732-450ns	4.45
2764-200ns	7.95
2764-250ns	5.15
2764-300ns	4.75
27C64-250ns	10.95
27C64-300ns	10.45
27128-250ns	19.00
27128-300ns	16.00

MEMORIES RAM

4116-150ns	1.30
4116-200ns	1.20
4164-150ns	4.00
4416-200ns	4.70
4532-200ns	2.45
4564-150ns	4.45
8118-100ns	1.95
81256-150ns	25.00
8416-200ns	6.00
8416-LP-200ns	6.40
8417-200ns	6.00
8417-LP-200ns	6.40

MEMORIES — RAM

Z80 POWER ZKXB CMOS	
MK48202B-150ns	32.00
MK48202B-200ns	24.00
MK48202B-250ns	23.00

BIPOLAR PROMS

TBP185030N	1.54
TBP185A030	1.38
TBP24510N	2.06
TBP24541N	6.68
TBP24581N	5.50
TBP245A10N	1.40
TBP245A41N	4.40
TBP28L22N	3.10
TBP28LA22N	4.14
TBP28S166N	19.00
TBP28S42N	4.50
TBP28S46N	4.50
TBP28S86N	5.00
TBP28SA42N	4.50
TBP28SA46N	4.50
TBP28SA86N	8.62
AM27513PVCI	3.74
AM27519PC	1.92
AM27519DC	15.00
AM27525DC	15.00
AM27529DC	6.46
AM27535DC	22.00

MEMORIES E2 PROM

X2804AP-300ns	14.95
X2804AP-350ns	13.45
X2804AP-450ns	12.75
X2816AP-300ns	29.95
X2816AP-350ns	25.00
X2816AP-450ns	22.50



0379 4131

TERMS OF BUSINESS

- * All prices exclude V.A.T. and carriage. Please add carriage to order total before adding V.A.T.
- * Carriage charges extra on all orders as follows: Components £0.75 Disc drives £4.50
- * Strictly cash with order or credit card (Access or VISA) only
- * Delivery is normally from stock but please allow up to 28 days.
- * Any query or complaint regarding an order should be made in writing within 7 days of receipt of the order. No telephone queries will be entertained

- * Goods incorrectly ordered cannot be accepted for replacement without our prior agreement. Due to high processing costs, a minimum of 15% handling charge may be levied on any returns or cancelled orders.
- * We will issue a full immediate refund, if requested, for out of stock items.
- * All items carry full manufacturers warranty.
- * A V.A.T. receipt will be supplied with all orders
- * Prices quoted are correct at the time of going to press but we reserve the right to effect changes without prior notice

LINEAR/INT. DEV.

4702	8.90
HCI-55564-5 (Speech Synthesis)	10.66
AM7910DC	34.88
AM7911DC	34.88
25L S2518PC	3.60
25L S2521PC	3.28
25L S2538PC	2.72
25L S2539PC	2.72
26L S31PC	2.62
26L S32PC	2.62
6402	6.40
75107BN	0.69
75110AN	0.86
75150P	0.86
75154N	1.05
75159	2.30
75160AN	2.60
75161AN	2.82
75162AN	4.08
75172NG	1.96
75173N	1.44
75174	2.82
75175	1.96
75182	0.50
75183	0.50
75188	0.86
75189	0.86
754518P	0.22
754528P	0.29
754538P	0.22
754548P	0.88
75468N	0.31
75491N	0.41
75492N	3.50
AY-3-1015	9.70
AY-3-1270	4.50
AY-3-8910	8.84
AY-5-3600	4.50
DPB304	0.99
L203	3.80
LF398	0.30
LM301AN	0.94
LM308AN	0.56
LM311N	0.60
LM317MT	0.80
LM317T	1.06
LM319N	1.90
LM324N	0.40
LM3337T	1.20
LM3339	0.48
LM339N	0.38
LM348N	0.64
LM350T	3.12
LM358N	0.60
LM3900	0.68
LM393N	0.48
LM725CN	2.90
741CP	0.16
LM747CN	0.60
LM748CN	0.30
MC1413P	0.80
MC1416	0.80
MC14411	10.10
MC14412	14.20
MC1458BPI	0.35
MC1495L	6.30
MC1496P	0.70
MC1723P	0.40
MC3242A	6.30
MC3302P	0.48
MC3340P	2.36
MC3357P	1.90
MC3423PL	0.81
MC3441AP	2.90
MC3446AP	2.90
MC3447P	4.30
MC3448A	3.99
MC3470P	6.44
MC3480	7.76
MC3487	1.80
NE555P	0.35
NE556PC	0.42
RO32513-L	9.40
RO32513-U	9.40
TL010-CP	0.44
TL061-CLP	0.28
TL062-CP	0.47

FAIRCHILD FAST

74F00PC	0.60
74F04PC	0.60
74F08PC	0.65
74F109PC	0.65
74F11PC	0.52
74F138PC	0.52
74F138PC	1.26
74F139PC	1.26
74F151	1.26
74F153	1.26
74F157	1.30
74F158	1.17
74F161	2.34
74F164	1.68
74F175	1.82
74F181	3.90
74F189	5.10
74F190	3.20
74F194	1.68
74F20PC	0.52
74F240	3.16
74F241	2.42
74F243	2.80
74F244	2.96
74F245	6.08
74F251	1.26
74F253	1.26
74F257	1.26
74F258	1.34
74F280	1.74
74F283	1.74
74F32PC	0.52
74F352	1.26
74F353	1.26
74F373	3.16
74F374	3.16
74F379	1.83
74F381	6.62
74F382	4.22
74F398	3.16
74F399	2.70
74F521	2.76
74F533	3.16
74F534	3.16
74F537	6.02
74F538	4.38
74F539	4.38
74F64PC	0.52
74F74PC	0.58
74F86PC	0.77

F.D. CONTROLLERS

FD1771P	30.00
FD1791	15.50
FD1791-02	11.00
FD1793	18.40
FD1793-02	11.00
FD1795	25.00
FD1797	21.00
FD2143	14.00
WD1691	14.00
WD2143	12.00

DATA CONVERTERS

ZN425E-8	3.76
ZN425I-8	8.00
ZN426E-8	1.90
ZN427E-8	6.68
ZN427I-8	12.50
ZN428E-8	5.10
ZN428I-8	9.70
ZN429E-8	1.60
ZN432CJ-10	20.79
ZN432E-10	13.00
ZN433CJ-10	25.00
ZN434	0.98
ZN435	4.38
ZN436E	1.26
ZN440	55.00
ZN441	46.80
ZN447	7.80
ZN448E	6.66
ZN448J	12.48
ZN449	2.72
ZN4134J	22.50
ZN4234E	9.40

VOLTAGE REF.

ZN404	0.50
ZN423	0.98
ZN458	0.92
ZN458A	0.92
ZN458B	1.12
ZNREF-025	1.90
ZNREF-040	1.90
ZNREF-050	1.90
ZNREF-062	1.90
ZNREF-102	3.05

UHF MODULATORS

UM1111	2.95
UM-1233	3.45

VOLTAGE REG.

7805	0.45
7812	0.45
7815	0.45
78H05SC	0.81
78H12ASC	8.95
78H16ASC	9.95
78L05	0.30
78L12	0.30
78L15	0.30
78S40DM	7.50
78S40PC	3.00
7905	0.45
7912	0.45
7915	0.45
LM309K	0.95
LM317K	2.45
LM323K	4.95
LM338K	4.50

TTL

74LS00	0.20
74LS01	0.22
74LS02	0.20
74LS03	0.20
74LS04	0.20
74LS05	0.22
74LS08	0.22
74LS09	0.22
74LS10	0.20
74LS109	0.27
74LS11	0.17
74LS112	0.54
74LS113	0.27
74LS114	0.44
74LS12	0.25
74LS122	0.42
74LS123	0.70
74LS124	2.30
74LS125	0.49
74LS126	0.29
74LS13	0.17
74LS132	0.60
74LS136	0.44
74LS138	0.55
74LS139	0.55
74LS132N	1.28
74LS137N	1.81
74LS138N	1.20
74LS139N	0.78
74LS151N	1.16
74LS153N	0.90
74LS157N	1.02
74LS158N	1.02
74LS160N	0.90
74LS161N	0.90
74LS162N	1.51
74LS163N	1.51
74LS164N	0.95
74LS165N	2.24
74LS167N	1.35
74LS168	0.80
74LS169	1.10
74LS166	1.41
74LS165	0.61
74LS166	1.40
74LS167	1.00
74LS174	0.70
74LS175	0.96
74LS176	0.96
74LS177	0.96
74LS178	0.96
74LS179	0.96
74LS180	0.96
74LS181	0.96
74LS182	0.96
74LS183	0.96
74LS184	0.96
74LS185	0.96
74LS186	0.96
74LS187	0.96
74LS188	0.96
74LS189	0.96
74LS190	0.96
74LS191	0.96
74LS192	0.96
74LS193	1.10
74LS194	0.28
74LS195	0.28


CMOS 4000 Series

4001	0.56
4002	0.42
4003	0.23
4004	0.40
4005	0.16
4006	0.74
4007	0.52
4008	0.34
4009	0.93
4010	2.40
4011	1.40
4012	1.95
4013	0.39
4014	1.16
4015	0.78
4016	0.25
4017	

Oryx

connect with quality

The Oryx name means a range of soldering tools and accessories designed to meet any modern requirement. Our comprehensive range includes lightweight, cordless rechargeable soldering irons, the famous "Super" and "Viking" standard designs and lightweight and temperature - controlled models. All with a wide selection of tip designs and sizes. The unique Portasol butane gas soldering iron completes the range. Oryx also supply the largest range of SR desoldering tools, including the new anti-static pump, power supply units, safety stands and solder pots.

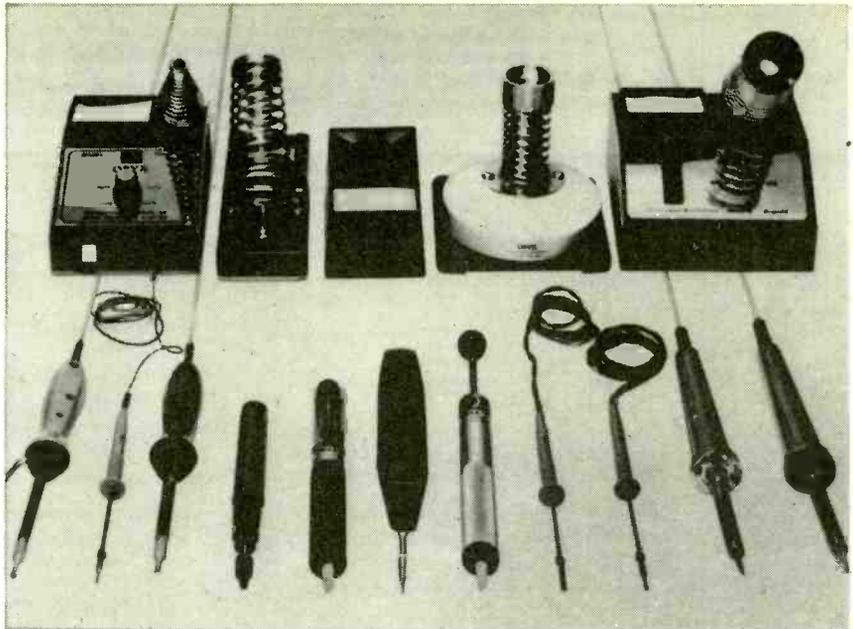

Oryx - advanced design at an ordinary price

GREENWOOD ELECTRONICS DISTRIBUTORS

Toolrange 0734 22245 Reading, S.T.C. Electronic Services 0279 26777 Harlow, Verospeed 0703 641111 Eastleigh, Electroplan 0763 41171 Royston, Engineering and Electronic Supplies 0639 54162 Wales, Cobbies 01-699 2282 London, Buck & Hickman U.K. Anglia Components 0945 63281 Cambridge, E.I.C. Ltd. 0727 36311 St. Albans, Willowvale Electronics 0734 860158 Reading, Longs 09328 61241 Surrey.

Please telephone or write for further information to:

Greenwood Electronics Portman Road, Reading, Berkshire, RG3 1NE
Tel: Reading 0734 595844. Telex: 848659

CIRCLE 54 FOR FURTHER DETAILS.

FREQUENCY COUNTERS

HIGH PERFORMANCE
HIGH RELIABILITY
LOW COST


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz - 1.2GHz
- ★ Sensitivity <50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100	(100MHz)	£116.72
METEOR 600	(600MHz)	£147.77
METEOR 1000	(1GHz)	£204.12

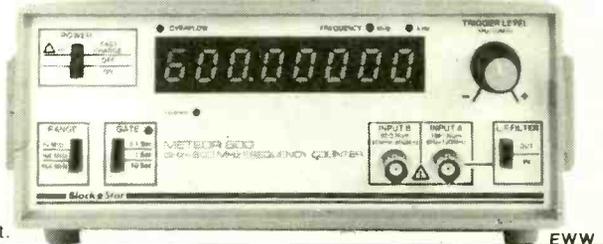NOW AVAILABLE WITH
T.C.X.O. OPTION
Illustrated colour brochure
with technical specification
and prices available on request.




Designed and
manufactured
in Britain

Black★Star

BLACK STAR LTD, Dept WW, 4 Stephenson Road, St Ives,
Huntingdon, Cambs PE17 4WJ, England.
Tel: (0480) 62440 Telex: 32339

CIRCLE 39 FOR FURTHER DETAILS.

Z80A MICRO-CONTROLLERS

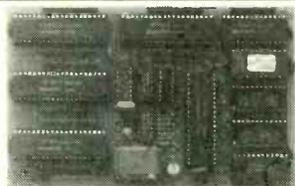

- 4MHz Z80A CPU
- 4K EPROM - 2K supplied with MCV2.0
- 4K Battery backed RAM - 2K supplied
- 4 x Z80A PIO's (64 I/O lines)
- Z80A CTC
- Standard 100mm x 160mm Eurocard
- Cost effective prices (£94.04-10 off)
includes all connectors, manual etc.

Designed to meet the power and flexibility of today's stand - alone micro-controllers, the GNC CUB makes full use of the powerful Z80 family IC's. Micro-controllers are available with up to 64K RAM, 8K EPROM, RS232 etc. Manuals include circuit diagrams and assembly language listings. No ULA's, PAL's or other funnies. Write, phone or circle to find out more about our powerful range of Z80A micro-controllers and multi - tasking software.

PRICES

CUB (built & tested)	£103.44
Bare board	£20.00
Manual (free with CUB/board)	£3.50

Please add £1.00 for P&P plus V.A.T.

GNC ELECTRONICS
Little Lodge, Hopton Road,
Theltham, Diss, Norfolk. IP22 1JN.
Tel: Diss (0379) 898313.

CIRCLE 47 FOR FURTHER DETAILS.

RUGBY TIME?

MSF CLOCK is EXACT

- 8 DIGIT display of Date, Hours, Minutes and Seconds.
- SELF SETTING at switch-on, never gains or loses, automatic GMT/BST and leap year, and leap seconds.
- EXPANDABLE to Years, Months, Weekday and Milliseconds and use as a STOPCLOCK to show an event time.
- COMPUTER or ALARM output also, parallel BCD (including Week-day) and audio to record and show time on playback.
- DECODES Rugby 60KHz atomic time signals, superhet receiver (available separately), built-in antenna, 1000Km range.
- LOW COST, fun-to-build kit only £79-70 (ready-made to order) includes ALL parts, 5x8x15 cm case, pcb, by-return postage and list of other kits, GET THE TIME RIGHT.

CAMBRIDGE KITS

45(WS) Old School Lane, Milton, Cambridge, Tel 860150.

Channel code and disc format — 1

By J.R. Watkinson

Eight-to-fourteen modulation, eye patterns, subcodes, flags and error correction.

The channel code used in the Compact Disc has to operate within a number of constraints. ○ First, the d.c. content of the code should be as small as possible for several reasons. Disc run-out and contamination cause low frequency noise in the replay signal which can be filtered out if there is no information content at those frequencies. The code d.c. content will also appear as noise in the tracking and focus servo systems. Finally, a d.c.-free code simplifies the design of the data separator.

○ The efficiency of the code, which is the relationship of bit rate to channel bandwidth, should be high as this has a major influence on the playing time. High-density run-length-limited codes are usually selected by balancing the maximum run length against d.c. content. Fortunately the jitter of a non-contact rigid medium such as CD is relatively low, permitting the use of a long maximum-run length¹.

○ The CD system depends heavily on error correction and a channel code that uses symbols of the same size as those in the error correction will reduce the possibility of error propagation².

○ The bit rate is lower than those used in computer discs, thus no simplification is necessary to achieve the necessary operating speed. A complex encoding process is acceptable because relatively few encoders are necessary.

The March and April articles 'Principles of Optical Storage', parts 1 & 2) showed that there is a cut-off frequency due to the n.a. of the optical system. All recorded frequencies must be below this cut-off by a sensible margin to allow for disc warp and focus errors. This determines the minimum time between transitions. It is fundamental to the

channel code that the period between successive transitions is an integral multiple of one-third the minimum period. The basic time period T is one cycle of 4.3218MHz or 231.4ns. Fig. 1 shows that the minimum wavelength allowable is 6T and that this corresponds to 720kHz. The minimum period between transitions is 3T, but it can also be 4T, 5T etc. To retain a reasonable clock content, the maximum period between transitions (the run-length limit) is 11T, corresponding to a frequency of 196kHz. There are consequently time periods used in all CD recording.

The basic clock period is three times smaller than the minimum transition spacing, so the resolution of the medium has apparently been increased by a factor of three. This gain cannot be fully realised because some data patterns cannot be recorded if the 3T spacing rule is to be obeyed. Data to be recorded must be converted to a form which accepts the restriction.

The basic period T is assembled into symbols of 14T length. Examining all the possible combinations of a 14T symbol (2¹⁴), there are 267 patterns where the run length is neither less than 3T nor more than 11T. From these, 256 patterns are selected to uniquely determine all possible combinations of an eight-bit data symbol. Fig. 2 shows some actual patterns and some invalid patterns for comparison. This conversion process gave rise to the name of e.f.m. (eight-to-

fourteen modulation) for the CD channel code.

To prevent violation of the rules by certain 14T patterns following others, and to control the d.c. content of the code, three packing periods are placed between each symbol. Each eight-bit data symbol therefore requires 17T to be recorded. This coding is 8/17 efficient, and when multiplied by the resolution improvement of three times, yields the actual efficiency

$$\frac{3 \times 8}{17} \times 100\% = 141\%.$$



Although the highest frequency in the channel code is 720kHz, or 1.44 million transitions per second, the bit rate is

$$4.3218 \times \frac{8}{17} \text{ Mbit/s} = 2.0 \text{ Mbit/s}$$

This series is outlined in an introductory article which appeared in January's issue. The second article in the series, entitled 'Principles of optical storage', is in two parts and appeared in the March and April issues. A second part of this present article will be provided next month.

Fig. 2. Part of the code block for E.F.M. code showing examples of various run lengths from 3T to 11T.

Fig. 1. Limit frequencies of CD channel code: master clock frequency of 4.3218MHz, T=231.4ns (a), highest recorded frequency with transition 3T apart, frequency 720kHz (b), and lowest recorded frequency with transitions 11T apart, frequency 196kHz, (c).

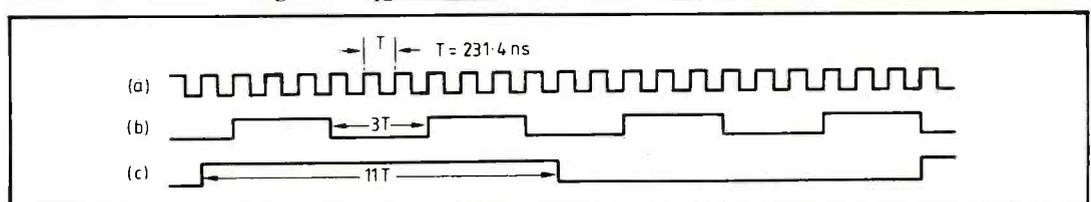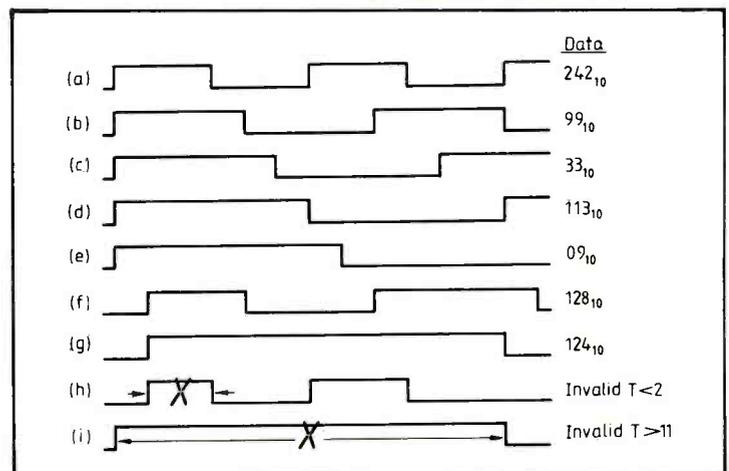

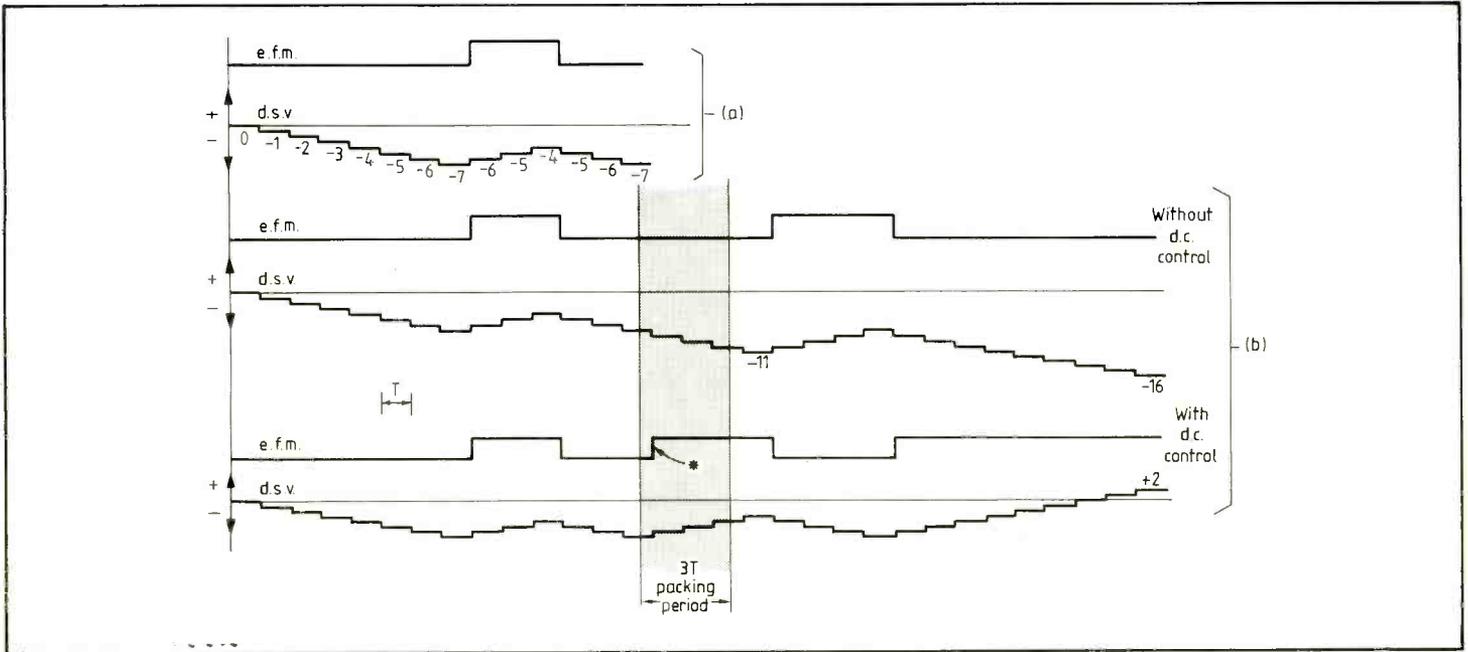


Fig. 3. Digital sum value example calculated from e.f.m. waveform (a). Two successive 14T symbols without d.c. control (upper) give d.s.v. of -16, (b). Additional transition (*) results in d.s.v. of +2.

Fig. 4. Characteristic eye pattern of e.f.m. observed by oscilloscope. The only information of interest is the time when the signal crosses zero. Notice reduction in amplitude of the higher frequency components.

Fig. 5. One CD data block begins with a unique sync. pattern and one subcode byte followed by 24 audio bytes and eight redundancy bytes. Each byte requires 14T in e.f.m., with 3T packing.

The choice of packing bits for d.c. control is determined as follows. The digital sum value (d.s.v.) of the channel patterns is derived as shown in Fig. 3(a). If the channel code is true during a T period, one is added to the d.s.v., if the code is false, one is subtracted. Clearly if the channel code is to be d.c.-free, the average d.s.v. must be zero. In Fig. 3(b), two successive 14T symbols are shown, both of which have a positive d.s.v. By adding a transition in the packing period, the second symbol is inverted, and the overall d.s.v. is reduced³. As the only parameter of interest is the time (3-11T) between transitions, this inversion has no effect on the data.

The interference read-out process causes the reflected light to

increase and decrease about some average value, which superposes a d.c. level on the readout signal, in addition to a component at the rotational frequency of the disc (3.3 to 9.5Hz) and harmonics thereof. Because the code is d.c.-free, a simple coupling capacitor can be used to remove these effects.

If a typical read-out signal is observed on an oscilloscope that triggers on a positive zero-crossing, the next zero-crossing could be 3T, 4T etc later, as shown in Fig. 4. The 'scope superposes all of these waveforms to give the characteristic eye pattern of CD.

Notice that the amplitude of 3T, 4T and 5T period signals is less than the others because they are closer to the optical cut-off frequency (see March and April articles).

The quality of the optics and focus servo can be assessed by comparing the 3T amplitude with maximum amplitude.

The first step in data separation is to locate the zero crossing in the waveform and to produce a transition in a binary signal at these points. Since the code is d.c.-free, the threshold or slicing level can be obtained by integrating the signal itself. This recreates the channel code. Every read-out transition is used to phase-lock a data separator clock of period T. The clock is used to establish the number of T periods between transitions and thus recreate the 14T symbols. These are converted back to data bytes using either a rom or gate array. The truth table, known as the code book, has been optimized to

permit decoding with minimum logic⁴.


Like most r.l.l. codes, e.f.m. requires a preamble to synchronize the phase-locked loop before data can be read. This unique preamble consists of three transitions separated by 11T.

Each of the data blocks shown in Fig. 5 consists of 33 symbols of 17T each, following the preamble, making a total of 588T or 136 μ s. Each symbol represents eight data bits: the first symbol in each data block is used for subcode, the remaining 32 bytes represent 24 audio bytes and 8 bytes of redundancy for the error correction system.

The subcode byte forms part of a subcode block that is built up a byte at a time from 98 successive data blocks. The start of a subcode block is denoted by the presence of S_0 and S_1 synchronizing patterns in the first symbol positions of two successive data blocks. These are two of the (267-256) patterns which are not in the code book and can be uniquely identified. The presence of these two sync. patterns reduces the size of the subcode block to 96 bytes. A future article of the series is devoted to subcode.

REFERENCES

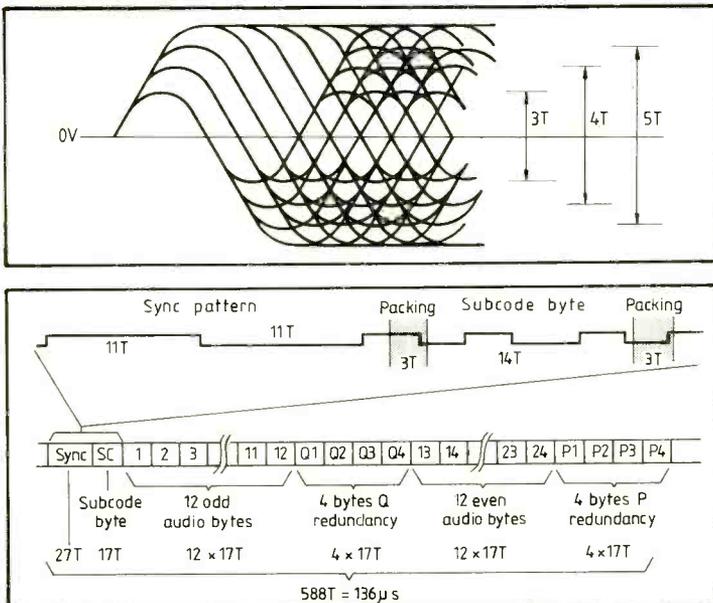
1. Channel codings for digital audio recordings, Toshi T. Doi. *J. Audio Eng. Soc.* April 1983.
2. 4. EFM — The modulation method for the Compact Disc digital Audio System., Hiroshi Ogawa and Kees A. Schouhamer Immink. AES convention, N.Y. June 1982.
3. Optimization of low frequency properties of eight-to-fourteen modulation, Kees A. Schouhamer Immink and Ulrich Gross. IERE Conference on Video and Data Recording, Southampton, April 1982.



TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

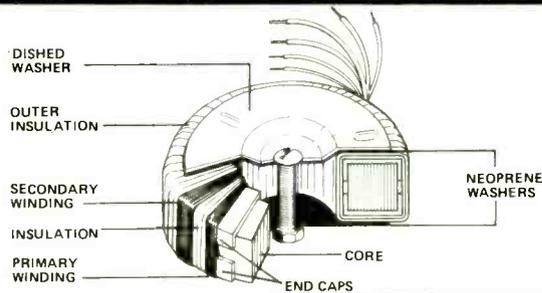Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 14 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm 0.35Kg Regulation 19%			50 VA 80 x 35mm 0.9Kg Regulation 13%			120 VA 90 x 40mm 1.2Kg Regulation 11%			225 VA 110 x 45mm 2.2Kg Regulation 7%			500 VA 140 x 60mm 4Kg Regulation 4%		
SERIES SECONDARY			2x010 6-6 4 16			4x010 6-6 6 10.00			6x012 12-12 9 38			8x016 25-25 10 00		
No	Volts	RMS Current	2x011 9-9 2 77	2x012 12-12 2 08	2x013 15-15 1 66	4x011 9-9 6 66	4x012 12-12 5 00	4x013 15-15 4 00	6x013 15-15 7 50	6x014 18-18 6 25	6x015 22-22 5 11	8x017 30-30 8 33	8x018 35-35 7 14	
0x010	6-6	1 25	2x014 18-18 1 38	2x015 22-22 1 13	2x016 25-25 1 80	4x014 18-18 3 33	4x015 22-22 2 72	4x016 25-25 2 40	6x016 25-25 4 50	6x017 30-30 3 75	6x018 35-35 3 21	8x025 45-45 5 55	8x033 50-50 5 00	
0x011	9-9	0 83	2x017 30-30 0 83	2x018 35-35 0 83	2x019 40-40 0 83	4x018 35-35 1 71	4x019 40-40 1 71	4x020 45-45 1 71	6x026 40-40 2 81	6x027 45-45 2 50	6x028 50-50 2 25	8x042 55-55 4 54	8x048 110 4 54	
0x012	12-12	0 63	2x020 220 0 22	2x021 240 0 20	2x022 240 0 20	4x028 110 1 09	4x029 220 0 54	4x030 240 0 50	6x029 220 1 02	6x030 240 0 93	6x033 50-50 2 25	8x029 220 2 27	8x030 240 2 08	
0x013	15-15	0 50	80 VA 90 x 35mm 1Kg Regulation 12%			160 VA 110 x 40mm 1.8Kg Regulation 8%			300 VA 110 x 50mm 2.6Kg Regulation 6%			625 VA 140 x 75mm 5Kg Regulation 4%		
0x014	18-18	0 42	3x010 6-6 6 64	3x011 9-9 4 44	3x012 12-12 3 33	5x011 9-9 8 89	5x012 12-12 6 66	5x013 15-15 5 33	7x013 15-15 10 00	7x014 18-18 8 33	7x015 22-22 6 82	9x017 30-30 10 41	9x018 35-35 8 92	
0x015	22-22	0 34	3x013 15-15 2 66	3x014 18-18 2 22	3x015 22-22 1 81	5x014 18-18 4 44	5x015 22-22 3 63	5x016 25-25 3 20	7x016 25-25 6 00	7x017 30-30 5 00	7x018 35-35 4 28	9x025 45-45 6 94	9x033 50-50 6 25	
0x016	25-25	0 30	3x016 25-25 1 60	3x017 30-30 1 33	3x018 35-35 1 10	5x017 30-30 2 66	5x018 35-35 2 28	5x019 40-40 2 00	7x026 40-40 3 75	7x027 45-45 3 33	7x028 50-50 3 00	9x042 55-55 5 68	9x026 110 5 68	
0x017	30-30	0 25	3x019 110 0 72	3x020 110 0 72	3x021 110 0 72	5x028 110 1 45	5x029 220 0 72	5x030 240 0 66	7x029 220 1 36	7x030 240 1 25	7x033 50-50 3 00	9x029 220 2 84	9x030 240 2 60	
(encased in ABS plastic)			3x022 220 0 36			3x023 240 0 33								

Why a Toroid?

- * Smaller size & weight to meet modern 'slimline' requirements.
- * Low electrically induced noise demanded by compact equipment.
- * High efficiency enabling conservative rating whilst maintaining size advantages.
- * Lower operating temperature.

Why ILP?

- * Ex stock delivery for standard 240V range
- * Fast prototype service available
- * 3 weeks despatch for special orders
- * 2 year no quibble guarantee
- * No price penalty for call-off order

Prices including P & P and VAT

VA	Size	£	VA	Size	£
15	0	7.06	160	5	12.17
30	1	7.67	225	6	13.75
50	2	8.90	300	7	14.97
80	3	10.06	500	8	19.60
120	4	10.65	625	9	22.30

For 110V primary insert "0" in place of "X" in type number
 For 220V primary (Europe) insert "1" in place of "X" in type number.
 For 240V primary (UK) insert "2" in place of "X" in type number.
IMPORTANT Regulation — All voltages quoted are FULL LOAD.
 Please add regulation figure to secondary voltage to obtain off load voltage.

Mail Order — Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

Trade — We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 3
 Graham Bell House, Roper Close,
 Canterbury, Kent. CT2 7EP
 Tel: (0227)454778 Telex: 965780



ELECTRONICS LTD.

CIRCLE 31 FOR FURTHER DETAILS.

BRAND NEW ELECTRONIC COMPONENTS



QUALITY .25W CARBON FILM RESISTORS

Qty	1-9K	10-24K	25-49K	50-99K	100K+
Price	4-25	3-95	3-70	3-45	3-25

Price per 1000. Sold in multiples of 1000.
 Small quantity prices available.

LEAD-FORMING SERVICE AVAILABLE

Save assembly time and money with pre-formed leads.
 Size setting £2-00 plus £1-50 per 1000.


Write or Phone for full Details
HARRISON ELECTRONICS

22 MILTON ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 7JX Tel: (0702) 332338

ELECTRONIC POWER UNITS FOR XENON ARC AND MERCURY ARC LAMPS

UNITS AVAILABLE FOR LAMPS RANGING FROM 75 TO 6500 WATTS.

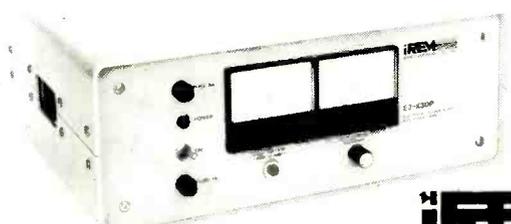Lamp housings and lens systems manufactured as standard off the shelf models or to specific design.



K. T. Manners Design Ltd.


P.O. Box 936, London, W4 4NW Telephone: 01-994 7155. Telex: 28604

CIRCLE 88 FOR FURTHER DETAILS.

ELECTRONICS & WIRELESS WORLD MAY 1985

CARACAL

SINE WAVE INVERTERS 200 to 1000 VA

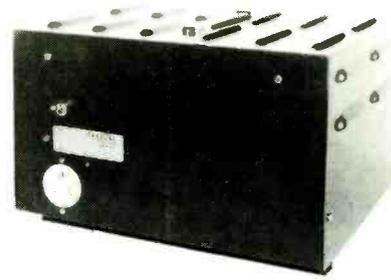

CARACAL'S new range of pulse width modulated inverters are now even better than ever compared to older tuned-type inverters — with even higher efficiency, lower standby current and lower weight than before.

CARACAL inverters have been in use around the world for many years wherever a reliable and stable source of backup or standby AC power is needed for computers, communications, instrumentation, and for mobile, field or marine applications.

ASK ABOUT OUR CUSTOM/OEM SERVICE — THE U.K.'s BEST INVERTERS TO SUIT YOUR DESIGN — FROM 50 TO 1000 VA

CARACAL POWER PRODUCTS LTD.
 42-44 SHORTMEAD ST., BIGGLESWADE, BEDS.
 Tel: 0767 — 260997

LANGREX SUPPLIES LTD

RST Climax House, Fallsbrook Rd., Streatham, London SW16 6ED RST
Tel: 01-677 2424 Telex: 946708

SEMICONDUCTORS

AA119 0.10	ASZ27 0.90	BC173 0.11	BD132 0.48	BF257 0.27	GEX541 1.50	OA2207 1.50	OC205 2.75	ZTX504 0.21	2N1671 5.00	2N3819 0.30
AA130 0.17	ASZ15 1.20	BC177 0.28	BD136 0.40	BF258 0.28	GJ3M 1.50	OC126 2.50	OC206 2.75	ZTX531 0.24	2N1893 0.32	2N3820 0.39
AA130 0.17	ASZ16 1.10	BC178 0.28	BD137 0.40	BF259 0.34	GM0378A 1.50	OC210 3.00	OC207 2.50	ZTX550 0.25	2N2147 4.00	2N3823 0.60
AA131 0.15	ASZ17 1.00	BC179 0.28	BD138 0.48	BF336 0.33	KS100A 0.45	OC222 2.50	OC211 2.00	IN914 0.05	2N2148 3.75	2N3866 1.00
AA132 0.15	ASZ20 2.30	BC182 0.11	BD139 0.48	BF337 0.36	MJE370 0.73	OC224 2.50	OC212 2.00	IN916 0.09	2N2219 0.32	2N3904 0.17
AA137 0.55	ASZ21 2.50	BC183 0.11	BD140 0.50	BF338 0.33	MJE371 0.71	OC225 1.00	R2009 2.25	IN4002 0.06	2N2220 0.20	2N3906 0.17
AC125 0.25	BA145 0.13	BC212 0.11	BD141 0.50	BF520 2.00	MJE520 0.47	OC226 1.50	R2010B 2.00	IN4003 0.06	2N2221 0.20	2N4058 0.20
AC126 0.25	BA148 0.15	BC213 0.11	BD142 2.00	BF521 0.20	MJE521 0.73	OC228 2.00	TIC44 0.27	IN4004 0.07	2N2222 0.20	2N4059 0.20
AC127 0.25	BA155 0.11	BC237 0.11	BD181 1.20	BF598 0.20	MJE2955 1.30	OC229 2.00	TIC262D 1.20	IN4005 0.09	2N2223 4.25	2N4060 0.16
AC128 0.30	BA156 0.10	BC238 0.11	BD183 0.80	BF710 0.97	MJE3055 1.10	OC235 1.50	TIP29A 0.48	IN4006 0.11	2N2268 0.25	2N4061 0.16
AC141 0.28	BA157 0.11	BC239 0.11	BD2137 0.54	BFW11 0.96	MPF102 0.35	OC236 1.50	TIP30A 0.45	IN4009 0.07	2N2484 0.25	2N4124 0.16
AC141K 0.35	BA158 0.10	BC258 0.11	BDX10 0.91	BFX85 0.30	MPF103 0.35	OC240 0.90	TIP31A 0.33	IN4148 0.04	2N2646 0.50	2N4126 0.16
AC142 0.28	BA159 0.10	BC259 0.11	BDX12 2.00	BFX87 0.30	MPF105 0.35	OC243 1.50	TIP32A 0.36	IN5400 0.13	2N2904 0.32	2N4286 0.15
AC142K 0.35	BA160 0.06	BC303 0.34	BDX20 1.50	BFX88 0.30	MPSA06 0.26	OC244 0.85	TIP33A 0.54	IN5401 0.13	2N2905 0.32	2N4288 0.18
AC176 0.30	BA161 0.06	BC307 0.11	BDY60 3.75	BFX90 0.30	MPSA06 0.26	OC245 0.65	TIP34A 0.67	IS44 0.04	2N2906 0.32	2N4289 0.18
AC187 0.28	BC107 0.16	BC308 0.11	BF115 0.75	BFY51 0.25	MPSU01 0.53	OC271 0.55	TIP41A 0.48	IS920 0.06	2N2907 0.21	2N4400 0.11
AC188 0.28	BC108 0.16	BC327 0.12	BF152 0.16	BFY52 0.25	MPSU06 0.65	OC272 1.00	TIP42A 0.42	IS921 0.09	2N2924 0.26	2N4401 0.11
AC189 1.30	BC109 0.16	BC328 0.12	BF153 0.16	BFY64 0.30	MPSU56 0.69	OC273 1.00	TIP2955 0.70	2G301 1.00	2N2925 0.22	2N4402 0.11
AC191 1.10	BC110 0.15	BC338 0.12	BF154 0.17	BFY90 0.95	NE555 0.45	OC274 0.70	TIP3055 0.56	2G302 1.00	2N2926 0.15	2N5457 0.32
AC192 1.10	BC115 0.18	BCY30 1.25	BF159 0.17	BSX19 0.27	NK7401 3.50	OC275 0.65	ZS140 0.25	2G306 1.00	2N3053 0.26	2N5458 0.32
ACY21 1.15	BC116 0.19	BCY31 1.50	BF160 0.17	BSX20 0.27	NK7402 3.50	OC276 1.00	ZS170 0.21	2N404 0.30	2N3052 0.11	2N5459 0.32
AD149 0.75	BC117 0.23	BCY32 1.50	BF167 0.24	BSX21 0.29	OA5 1.20	OC277 1.00	ZS178 0.23	2N404A 0.32	2N3055 0.65	2S017 12.00
AD161 0.35	BC118 0.18	BCY33 1.40	BF173 0.30	BT106 1.20	OA5 1.20	OC281 0.65	ZS271 0.21	2N4067 0.32	2N3440 0.70	2S019 12.00
AD162 0.35	BC119 0.18	BCY34 1.40	BF178 0.35	BTY79/400R 0.35	OA7 0.55	OC282 1.90	ZS278 0.12	2N4068 0.32	2N3441 0.85	2S024 35.00
ADZ11 12.50	BC120 0.15	BCY35 1.30	BF179 0.35	BU205 2.00	OA7 0.55	OC283 1.00	ZTX107 0.57	2N4069 0.12	2N3442 1.25	2S025 35.00
ADZ12 12.50	BC125 0.15	BCY40 2.80	BF180 0.30	BU206 1.50	OA7 0.12	OC284 3.00	ZTX108 0.12	2N4070 0.25	2N3614 2.20	2S026 35.00
AF106 0.35	BC137 0.19	BCY43 0.30	BF181 0.28	BU208 2.00	OA7 0.12	OC285 1.75	ZTX109 0.12	2N4071 0.25	2N3702 0.11	2S027 35.00
AF114 3.50	BC147 0.12	BCY44 0.30	BF182 0.30	BY100 0.40	OA8 0.17	OC286 2.00	ZTX110 0.14	2N4072 0.25	2N3703 0.11	2S028 35.00
AF115 3.50	BC148 0.12	BCY45 0.19	BF183 0.28	BY126 0.13	OA8 0.17	OC287 1.00	ZTX111 0.14	2N4073 0.18	2N3704 0.11	2S029 35.00
AF116 3.50	BC149 0.13	BCY71 0.18	BF184 0.28	BY127 0.14	OA9 0.08	OC288 1.00	ZTX112 0.18	2N4074 0.20	2N3705 0.11	2S030 35.00
AF117 3.50	BC157 0.11	BCY72 0.17	BF185 0.30	BZK61 0.17	OA9 0.08	OC289 1.00	ZTX113 0.18	2N4075 0.20	2N3706 0.11	2S031 35.00
AF139 0.33	BC158 0.13	BCZ11 1.75	BF186 0.12	BZV88 0.10	OA9 0.08	OC290 1.50	ZTX114 0.18	2N4076 0.20	2N3707 0.11	2S032 35.00
AF186 1.00	BC159 0.13	BD115 0.42	BF196 0.13	CRS140 0.60	OA202 0.15	OC291 3.75	ZTX115 0.18	2N4077 0.20	2N3708 0.11	2S033 35.00
AF239 0.39	BC167 0.11	BD121 1.70	BF197 0.14	CRS140 0.60	OA211 1.50	OC292 2.75	ZTX116 0.18	2N4078 0.20	2N3709 0.11	2S034 35.00
AFZ11 4.00	BC170 0.11	BD124 2.00	BF200 0.40	CRS340 0.75	OA220 1.50	OC293 2.75	ZTX117 0.18	2N4079 0.20	2N3710 0.11	2S035 35.00
AFZ12 4.00	BC171 0.11	BD124 2.00	BF204 0.65	CRS340 0.75	OA220 1.50	OC294 2.75	ZTX118 0.18	2N4080 0.20	2N3711 0.10	2S036 35.00
ASZ26 1.40	BC172 0.11	BD131 0.44	BF244 0.35p	GEX66 3.00	OA220 1.50	OC295 2.75	ZTX119 0.18	2N4081 0.20	2N3712 0.10	2S037 35.00

VALVES

A1834 9.00	E130L 18.50	EF86 3.50	GXU1 15.35	OD3 2.50	OY3-AS 63.24	UF41 2.00	4-250A 80.00	6CG7 2.50	12AX7 1.75	5642 9.00
A2087 13.50	E180C 10.50	EF89 2.50	GXU2 30.00	OC6 3.50	OV3-1 64.00	UF42 2.10	4-400A 80.00	6CG16 1.50	12AY7A 4.00	5644 3.00
A2134 17.50	E186F 11.50	EP91 2.95	GXU3 25.40	OC8 2.50	OV4-250 10.14	UF43 1.75	4B3 2.00	6CL6 3.75	12BA4 3.50	5651 4.45
A2293 16.00	E188CC 8.91	EP94 2.50	GXU4 44.50	OC8 2.50	OV4-400 76.20	UF85 1.75	4C35 120.00	6CW4 8.00	12BA6 2.50	5670 4.50
A2426 27.50	E280F 22.51	EP95 5.99	GXU5 20.00	OC9 2.50	OY5-500 190.00	UF89 2.00	4CX250B 45.00	6D2 1.50	12BE6 2.50	5675 28.00
A2521 25.00	E282C 12.00	EP98 2.00	GXU6 20.00	OC9 2.50	QY5-3000A 350.00	UL41 5.00	4CX350A 120.00	6D6K 3.00	12BH7 2.75	5687 6.00
A2900 15.00	E288CC 17.50	EF183 2.00	GZ32 4.00	OC9 2.50	QZ06-20 32.70	UL84 1.75	4X150A 60.00	6DQ6B 4.75	12BY7 3.00	5696 4.50
A3343 45.00	EAS2 125.00	EF184 2.00	GZ33 4.75	OC9 2.50	RG2-250 32.68	UM80 2.00	4X150D 56.00	6EA8 3.00	12C1 2.00	5718 7.50
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250 32.68	UR7 3.00	4X150E 56.00	6E88 3.00	12E11T 28.00	5725 5.50
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250A 32.68	UR8 2.25	4X150F 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250B 32.68	UR8 2.25	4X150G 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250C 32.68	UR8 2.25	4X150H 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250D 32.68	UR8 2.25	4X150I 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250E 32.68	UR8 2.25	4X150J 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250F 32.68	UR8 2.25	4X150K 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250G 32.68	UR8 2.25	4X150L 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250H 32.68	UR8 2.25	4X150M 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250I 32.68	UR8 2.25	4X150N 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250J 32.68	UR8 2.25	4X150O 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250K 32.68	UR8 2.25	4X150P 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250L 32.68	UR8 2.25	4X150Q 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250M 32.68	UR8 2.25	4X150R 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250N 32.68	UR8 2.25	4X150S 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250O 32.68	UR8 2.25	4X150T 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250P 32.68	UR8 2.25	4X150U 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250Q 32.68	UR8 2.25	4X150V 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250R 32.68	UR8 2.25	4X150W 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250S 32.68	UR8 2.25	4X150X 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250T 32.68	UR8 2.25	4X150Y 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250U 32.68	UR8 2.25	4X150Z 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00	GZ37 4.75	OC9 2.50	RG3-250V 32.68	UR8 2.25	4X150AA 56.00	6E96 2.25	12E14 65.00	5726 11.37
A3343 45.00	EAS2 125.00	EF184 2.00</								

The post-war stride into aerospace.

by R.E. Young,
B.Sc. (Eng.)
F.I.E.E.,
M.R.Ae.s.

R.E. Young continues the story of British electronic invention. The notorious delays and overspending which beset industry are not the whole picture

During the movement of the aircraft industry from 'ordinary' aeroplanes into the new world of rockets and supersonic travel, the role of British electronics changed from being a supplier of the proverbial 'Black Boxes' to that of an equal partner with extensive technical responsibilities varying from instrumentation to project coordination.

Both industries already had what was probably unequalled experience of dealing with fresh areas of technology. During the greater part of World War II, and during the period immediately after it, the aircraft industry handled intensive power-plant development, and especially the jet engine. In the electronics connection, they had encountered various forms of airborne radar such as AI (Air-Interception) and the (largely) radar-based navigational aids. Over the same period, radar had over-shadowed all other electronics developments; and the R & D effort alone had been on a scale which had not been seen in the country before, with the possible exception of nuclear research. In parenthesis it may be added that it has been stated that at this time, the British radio industry — essentially based on radar — reached a "war figure exceeding £100,000,000 annually"¹. Allowing a conservative factor of 10, the modern equivalent becomes £1 billion a year, which by any standards, and especially for a 'light' industry, represents an outstanding total.

Early aerospace/electronics projects

In the introduction to this series it was pointed out that " — since the

late 1950s, a significant number of technological projects — have not reached their target" and that "In extreme cases they have been abandoned; in others the project time scale has become so extended and the overall cost so high that the further development, which it would have been uneconomic to have carried out, has been completely blocked".

This statement, based on the performance of the United Kingdom as a whole, is pessimistic in that a large proportion of British aerospace projects *did* reach their target; but often — it must be admitted — after delays and consequent increase in costs which were several orders higher than the original 'worst-case' predictions.

The late 1950s are particularly significant for these aerospace projects because, by this time, the publication of details of programme delays and 'huge' increases in R & D expenditure had given rise to a great deal of critical comment. This was, of course, added to the general criticism which, as noted in the introduction, was being directed against the alleged failure of the British to keep up — in terms of *successful* development — with modern technology.


Part of this criticism, which has been maintained until the present day, concerned itself with the scale of the resources that had been made available for the individual projects. The general conclusion reached was that these resources — both human and material — had been totally inadequate; and that, in any case, the scale of effort required for this new technological world in which


aerospace and electronics were involved had not even been glimpsed.

Like all such generalised statements, it contained an element of truth in seizing on this 'world' being new; but it did not get anywhere near analysing the root cause of the trouble — the almost interminable delays which individually could stop progress on the project as a whole, until they had been cleared. Thus, on the face of it, this was a matter of insufficient resources.

Clearly it is not possible even to survey briefly all the ways in which such delays could, and did,

1. The 'Flutter Dart' research rocket

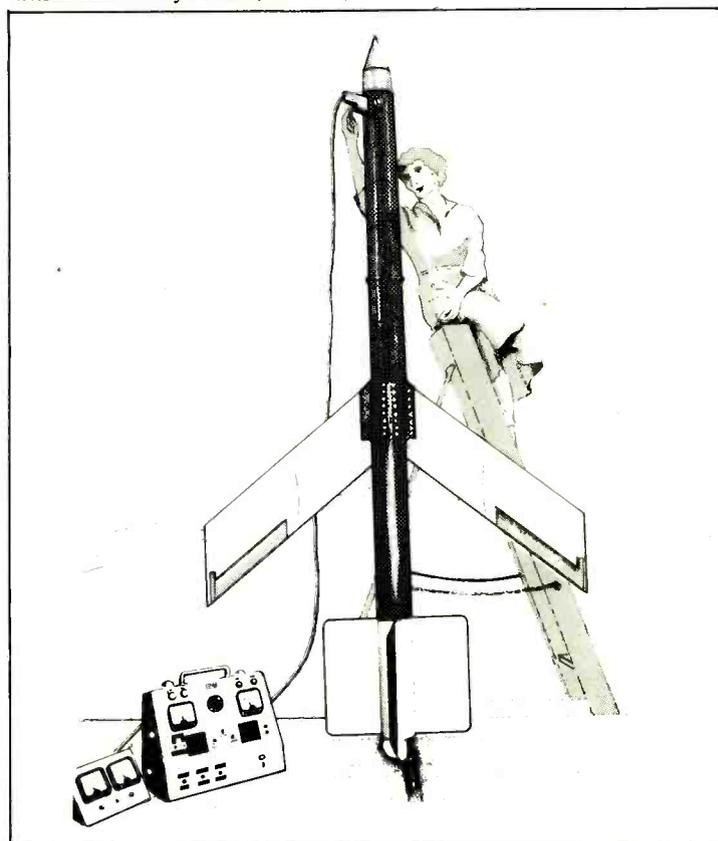

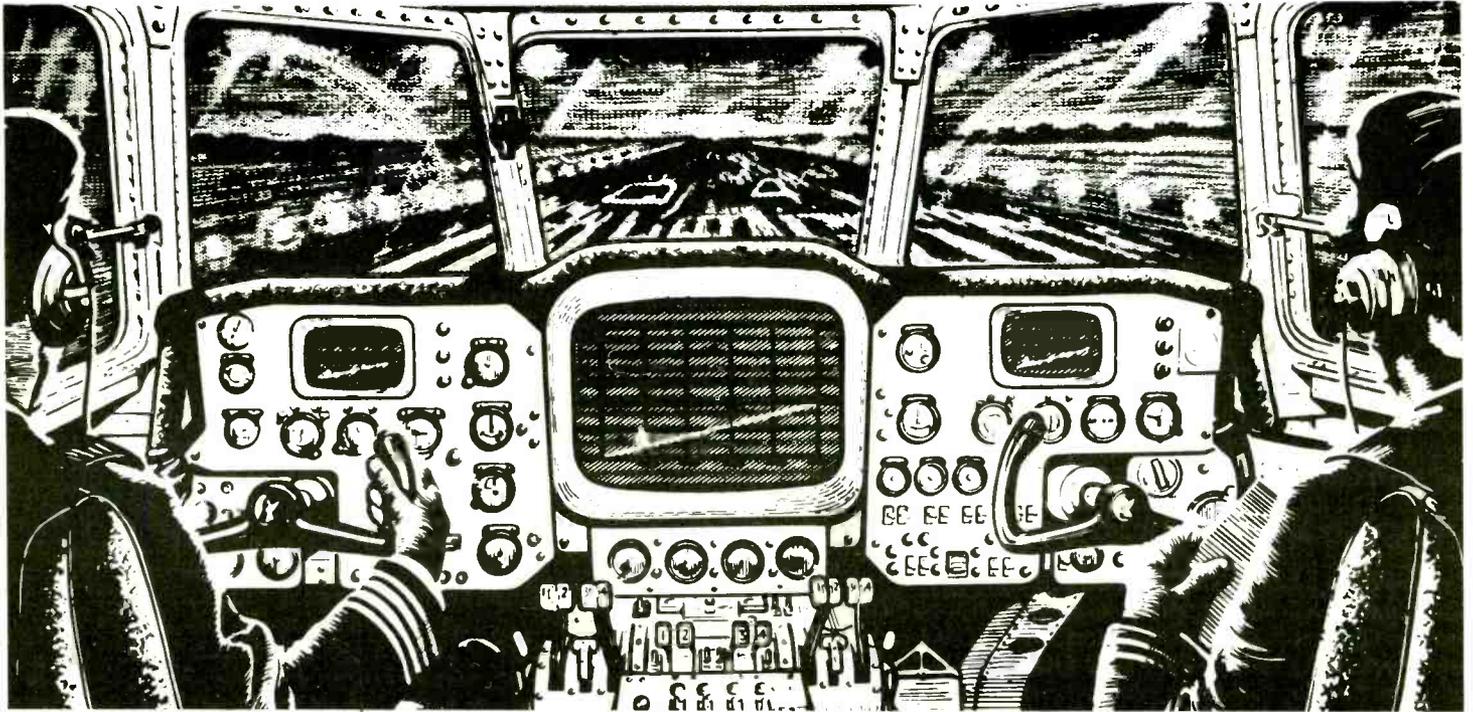

2. Final descent on to the runway with 'derived-information' landing system in use.

arise with so many *interacting* — mutually dependent — factors combining to obscure completely the real sources of technical failure.

Nevertheless, not only were such intractable — frequently intermittent — 'fault clearance' problems tackled much more quickly than is usually realised; but new techniques and basic principles of attack were evolved which broke new ground for a much wider field than 'aerospace/electronics'. The latter can be illustrated by looking at the concept of data marshalling which has been taken into a number of fields exemplified by 'Crisis Control'² with its original background lying in aerospace instrumentation and aircraft testing. Further instances of this spread into other fields will be given in this series.

Data marshalling, with its definition as 'the separation, streaming and systematic presentation, of "masses of data"', has been chosen in this instance to bring out one of the far-reaching and fundamental problems of aerospace development: to obtain measurement (including 'binary' state) information which can be relied on, and then to interpret it correctly.

Flight trials — dual problem

'Trials' uncertainty and hence delay have two main causes. The first is associated with the success of actual flight trials where the testing and proving of the

aero-space systems is obviously utterly dependent upon the 'goodness' of the derived information. There is no need to stress the virtually insurmountable difficulty of identifying (at best) trouble in, say, the main rocket control system when the telemetry (instrumentation) equipment is suspect. It will also be realised that, with unmanned vehicles in particular, there is always an element of doubt when the data coming from an isolated (inaccessible) source cannot be verified. Means for reducing these uncertainties to an acceptable minimum — particularly 'independent check' techniques² — are discussed later in this article, where an example will be given of how full advantage was taken of 'having an aircraft available' to investigate and develop telemetry systems, using tv techniques.

The second aspect — associated with interpretation in its widest sense — is concerned with:

(a) the mode of presentation of measurement information so that it is unambiguous and can be read out with the minimum of error; and

(b) the direct data marshalling function of separating out information vital to a specific section of an investigation from an accumulation of data which is so varied in form and so large in amount that it saturates conventional methods of extraction. By the very nature of trials work, these difficulties are particularly great during the early stages of

the project; and where the design of the elements in the various systems is far from being finalised.

When these main-system uncertainties are compounded by additional possibilities of error in the instrumentation chain, it is clear that — as noted in connection with 'setting to work' in the first article — the process of reaching a satisfactory solution is extremely lengthy. In turn this means almost invariably that the main project is held up until a final *overall* solution has been arrived at and found acceptable. From talks with engineers in several countries, it can be said that they find it almost inevitable that "at least one crisis" will appear in an R & D programme; and that their main difficulty was to extract the data they needed from the near-infinite amount available to them, if they were to avoid 'shut-down' scale delays. Although extensive theoretical investigation and simulation work had been carried out throughout design and prototype manufacture, both the main and the instrumentation systems were untried in terms of being 'put together' for flight trials and some 'unknowns' were almost certain to be encountered. Also, this was a new world, certainly as far as detailed engineering practice was concerned.

Thus it says much for the teams themselves and their powers of adaptability that they were able to take advantage of earlier experience and 'know-how' and apply them successfully in this new world. This flexibility in

approach was shown to the full in the way in which equipment, e.g. a specific telemetry installation, was, in effect, developed during use and the fresh unknowns thus introduced, were anticipated.

Reducing uncertainties — key divisions

Environmental testing. One of the outstanding features of aerospace development has been the growth of environmental testing, first for individual components, then for, say, a control or telemetry system assembly, and finally for whole rockets or satellites. The range of 'environments' that were simulated grew correspondingly, beginning with variable-frequency vibration, steady acceleration forces (by centrifuge methods), and, — found imperative for telemetry installations, — high values of shock. These various 'mechanical' conditions were then supplemented by three main kinds of climatic - environmental — chamber in which controlled temperature, air pressure and humidity testing could be carried out; in addition, these tests could be made on a long term or cyclic basis³⁴.

It may be noted that the wind tunnel may be regarded as the earliest form of environmental chamber, but also as providing mechanical-type testing by virtue of the air flow; while one of the largest electronic firms in the UK carried out prolonged vibration tests on radio sets, as mechanical assemblies, well before World War II, by means of an oscillating platform on which the sets were mounted.

Research rocket — the 'Flutter Dart'. It will be appreciated that the cost of setting up a complex wind tunnel testing programme — especially to include supersonic flow — is extremely large; and, in practical terms, can become prohibitive when a number of entirely new testing techniques have to be evolved. Thus if, as with the 'Flutter Dart', a relatively cheap rocket can be equipped with suitable electronically (telemetry) based instrumentation to give the required research information, then testing under 'real' conditions becomes possible; and the need for complex simulation and large-scale facilities generally is eliminated.

Briefly, the Flutter Dart⁵ was a five-inch (13cm dia.) solid-fuel

rocket with special attachment points enabling wings (and control surfaces) of various configurations to be fitted for testing under accepted flight trials procedures. As the name implies, the rocket and its instrumentation were designed to yield research information on aerodynamic 'flutter' of different wing forms at airspeeds going through the transonic barrier to supersonic values. Flutter, 'divergence' and control surface characteristics were obtained from sampled information telemetered over a time division system with up to 24 channels available. Data sources included accelerometers, strain gauges and a specially designed transducer giving aileron movement, crucial for the flutter measurements.

That this special transducer was developed and built in-house is a telling illustration of how the joint team operated, with — in this case — electronics providing instrumentation required by aerodynamics; and of how, it will be realised, close liaison was maintained throughout between all members of the design and development manufacturing groups. The adaptability shown and the coordination achieved both within the organisation and outside will be brought into the next article.

'Independent check' television development. For this work⁶ associated with aerospace telemetry, the primary research task was to take advantage of being able to monitor and control the operation of airborne telemetry-type equipment which normally would be 'inaccessible to human agency'. Also, at the same time as information was being gathered on the specific communication (sender-plus-receiver) channel, it was possible to obtain data on individual telemetry components and sub-systems inserted in the main installation and this included evaluation of television not only as an instrumentation technique in itself, but

also as an independent check method for 'difficult' remote measurements. The importance of this last aspect is, if anything, greater now than it was at the time, especially for the emergency conditions of crisis control^{2,4}, while the wideband information capacity which was provided means that the results obtained have equal relevance today.

Amongst other practical points, flying-spot scanning was employed for the airborne camera chain. This enabled a compact and low-cost assembly to be designed where no external source of illumination was required for the conventional dial instruments being viewed. It should be noted that the data transmitted from them was, in essence, in digital form; while once the data had been, in effect, 'encoded' (brought into video form), no further degradation in its accuracy could take place⁴.

Landing systems for 'zero — zero' operation. In 1967 it was possible to write that "Stemming from the original work of the Blind Landing Experimental Unit (B.L.E.U.) of the Royal Aircraft Establishment, and developed under their aegis, the Autoland system has now over 20,000 aircraft landings to its credit".


This quotation, taken from a *Wireless World* article⁷, stands on its own as a statement of the success of the development of this automatic landing system. The development programme itself was also a model of its kind with full interchange obviously maintained between the operational side and the system designers, and, in turn, between them and the development teams.

The blind-landing system was based on 'leader-cable' azimuth guidance, and final 'flare-out' descent to the runway under radio altimeter control; in 1967 this general principle was being retained with further development effort largely being given to improvement rather than to

Articles in this series

- British invention, innovation and electronics (March)
- Radar and television — interchange and spin-off (April)
- The post war stride into aerospace (May)
- R & D management and economics
- 'Big system automation and telemetry
- Vehicle instrumentation
- Human communications
- The future

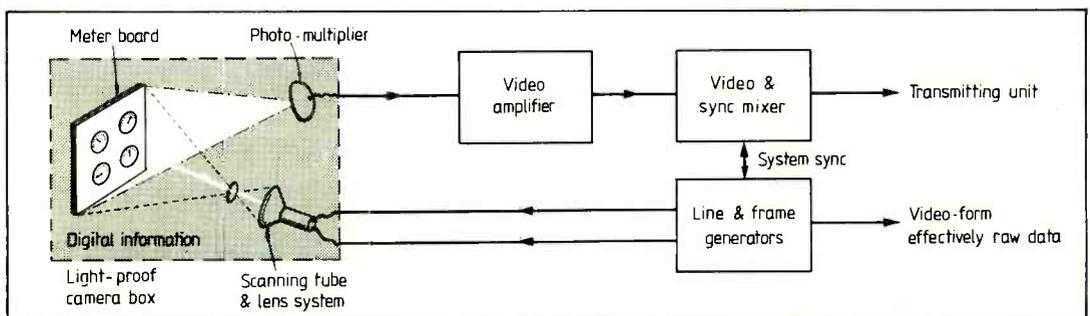3. 'Flying-Spot' tv telemetering — schematic.



change of principle. These improvements were, of course, of a major character, especially with regard to replacement of the leader-cable by radio methods.

As indicated in the *WW* article, the problems with leader-cable were essentially those of physical installation, particularly with regard to the need to extend azimuth guidance — and hence the leader cables — to at least a mile beyond the approach end of the runway. In practical terms, this problem becomes insuperable where the runway is built close to the sea or even, in some cases, when access cannot be gained to areas surrounding the airport. In fairness it must be pointed out that radio guidance can suffer from reflections from buildings and imperfections of the site; and the discussion of these aspects was taken further in the 'state of the art' sections of the *Wireless World* article.

Finally, the role of the pilot as a 'systems manager' will be reviewed in the light of suggestions put forward at the end of the 1950s. Some details of these suggestions were given in the article, largely without comment; but they take on a new significance in relation to e.g. control under emergency conditions and to accurate 'at-a-glance' presentation of information. With regard to the article itself, it may be added that it had attracted considerable interest not only in the UK but also internationally, giving, as it did, a comparatively wide picture of British achievement during the pre-1970 period.

Reverting to the question of the suggestions introduced above, they were concerned with

presenting to the pilot *instantaneous* information (as far as possible without ambiguity) of this position relative to the runway and the path of his descent to it.

Two basic systems were put forward⁶. The first employed a primary radar in the nose of the aircraft which, with television-type scanning of passive reflector runway markers, gave a picture to the pilot corresponding to what he would see with ordinary runway lighting and clear weather conditions. One of the main advantages of this system is that it is virtually independent of ground installations — particularly telling in remote areas where maintenance of complex equipment may be difficult.

The second scheme — a 'derived-information' system — was somewhat different in that it presented ground-derived (radar) guidance intelligence to the pilot in two ways. For the vertical plane, the display of a pulse height-finding radar — as used in GCA (Ground-Controlled Approach) — was sent to the pilot over a television-capacity radio link; and without delay or transfer errors being introduced.

Azimuth guidance was transmitted to the aircraft in audible "dot-dash" or similar form, being derived either from a static radiated twin-beam pattern or a microwave radar system strobing in azimuth^{7,8}.

The conduct of the research design studies lying behind these two schemes will be examined in the next article in the context of R & D management. An anecdotal illustration of the interchange that took place is afforded by the

remark of the test pilot who, on seeing the GCA type height display shown, said that he liked the speed and 'clarity' of the system, but that he "did not think that he would like to see himself side-ways on".

This was one of the pieces of evidence which pointed — as one would expect — to the greater acceptability of the primary radar system; although it must be noted that the derived information scheme would enable a monitoring GCA controller to keep in touch with the descent, and to intervene in an emergency with speech superimposed on the 'dot-dash' channel.

These considerations lead to the crux of the pilot's role in automatic landing — the assumption of control in an emergency. The fundamental point at issue is the degree to which the pilot should "surrender his direct authority" during an automatic landing in anticipation of a low-probability emergency⁷.

As treated in the next article, this question can clearly be approached in several ways; but in the present context it does appear from the more recent parallel work on crisis control that the primary radar system, in particular, would provide an 'instantaneous' and accurate independent check on the automatic-landing process. This means that the guidance control data supplied to the pilot should be in such a form that time is not required for analysis and interpretation, so that he can act without delay — due to distraction — in an emergency.

References

1. Rowe, A.P.: *One Story of Radar*. The University Press, Cambridge, 1948
2. Young, R.E.: *Crisis Control*, *Wireless World*, June and July 1982
3. Charlish, G.: 'Making sure the product will always work', *Financial Times*, London, Friday March 6, 1964, p. 15.
4. Young, R.E.: *Control in Hazardous Environments*, Peter Peregrinus Ltd., Stevenage, England, 1982
5. Poole, S., Potton, A., and Titley, C.O.: 'Analogue Telemetry Equipment and Systems — Pt. 2', *Electron. Eng.*, London, Vol. 33, No. 396, February 1961.
6. Young, R.E.: 'Analogue Telemetry Equipment and Systems — Pt. 1', *Electron. Eng.*, London, Vol. 33, No. 395, January 1961.
7. Young, R.E.: 'Automatic Landing in Airline Service', *Wireless World*, November 1967.
8. Young, R.E.: 'Aircraft Landing Techniques... and the Future', *Electron. Eng.* London, Vol. 33, No. 402, August 1961.

BOOKS

Creative Animation and Graphics on the BBC Micro by Mike James: Collins, 212 pages, soft covers, £7.95, ISBN 0 00 383007 1. Covers animation, sprites, two-dimensional technical graphics (though not graphs and charts), three-dimensional graphics and painting. Examples are in BBC Basic. Many useful tips.

Colour and Mono Television: volume 2, display tubes, timebases, synchronising and power supply circuits, by K.J. Bohlman. Dickson Price Publishers Ltd., 235 pages, soft covers, £8.95, ISBN 0 85380 155 X. Textbook for tv receiver technicians. Many of the circuit

examples relate to older sets, perhaps inevitably: there is little enough to see inside the latest ones. For those who collect spellings of 'Schmitt' (as in trigger), there is a novel one here. Schmitt. Volume 1 deals with the tuner, i.f., video and audio stages; volume 3, to follow, will describe colour decoders and digital circuitry.

The Commodore 64 Roms Revealed by Nick Hampshire with Richard Franklin and Carl Graham: Collins, 215 pages, £8.95, ISBN 0 00 383087 X. The bulk of the book consists of a reconstructed source-code listing of the Commodore roms, with extensive explanatory notes.

Other chapters describe memory usage and list main entry points. Essential for the serious programmer.

Commodore 64 Wargaming by Owen Bishop and Audrey Bishop: Collins, 252 pages, soft covers, £8.95, ISBN 0 00 383010 1. Programming techniques and listings for war games in a variety of settings from ancient times to the distant future, and how to adapt and extend them.

CP/M Techniques by Ken Barbier: Prentice-Hall International, 224 pages, soft covers, £19.35, ISBN 0 13 187857 3 (PBK). For the programmer with some knowledge

of assembly language. Covers programming techniques, i/o, tricks with discs (both floppy and hard) and customizing your Bios. Good clear explanations.

The Dandy Dipole by Daniel Bostick (WA2ZYR) and Donald Shatraw: Unadilla/Microwave Filter Company Inc. (6743 Kinne Street, East Syracuse, NY13057, U.S.A.), 24 A4 pages, soft covers, \$3.95. Good practical guide for the radio amateur, although rather expensive. Discusses layout, matching, s.w.r., baluns and traps for dipoles from 1.8 to 28MHz, with tables, illustrations and technical details of Unadilla products.

SUPER HY-LIGHT STROBE KIT

Designed for Disco, theatrical uses, etc.

Approx. 16 joules. Adjustable speed. Price £45 + £2 p&p (Total inc. VAT £54.05). Case and reflector price £15 + £2 p&p (total inc. VAT £19.55). Footscap SAE for further details including Hy-Light and Industrial Strobe Kits.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £10.44 (£12.00 inc. VAT)
 2ft 20 watt £7.44 (£8.75 inc. VAT)
 18in 15 watt £5.00 (£5.75 p&p (£6.61 inc. VAT)
 13in 10 watt £4.00 (£4.75 p&p (£5.46 inc. VAT)
 12in 8 watt £3.60 (£4.20 p&p (£4.71 inc. VAT)
 9in 6 watt £3.00 (£3.60 p&p (£4.02 inc. VAT)
 6in 4 watt £3.00 (£3.60 p&p (£4.02 inc. VAT)
230V AC Ballast Kit for either 6in, 9in or 12in tubes £5.50 p&p 55p (£6.96 inc. VAT)
 For 13in & 18in. Tubes £6 p&p 75p (£7.76 inc. VAT)
 For 12V DC op. 12in & 13in. tubes only £5.50 p&p 75p (£7.18 inc. VAT)
175 WATT SELF-BALLASTED BLACK LIGHT MERCURY BULBS.
 Available for either B.C. or E.S. fitting, price £10.80 + p&p £1.25 (total inc. VAT £12.05)
400W UV LAMP & BALLAST complete - £48.80 + £3.50 (£50.15 inc. VAT)
400W UV LAMP only. £20.00 + p&p £2.50 (£25.88 inc. VAT).



ROBOT ENTHUSIASTS

The following two Motors are ideally suited for experimenters in this field.

1. ESCAP precision Swiss-made ironless rotor. 6V DC geared Motor with 70:1 gearbox. 6V DC - 16 r.p.m. 3V - 8 r.p.m. amazing power, no load current, only 10 ma. approx. Size 4" x 2 1/2" cm. Ex. equipment, tested and guaranteed. **ONLY £4.50 + 50p p&p (total inc. VAT £5.75)**

2. 12/24V D.C. Reversible Precision built motor manufactured by Escap - will operate from 24V down to 2V DC - Current consumption negligible. A range of speeds between 2 to 36 r.p.m. obtainable. Approx. half manufacturers price. **£15.00 p&p £2.00 - total inclusive of VAT £19.55.**

MICRO-SWITCH

Button type 10amp c/o contacts. **£6.90** for 10 post paid. inc. VAT.

VORTEX BLOWER & SUCTION UNIT

Powerful multi-stage dynamically balanced totally enclosed rotors. 1 1/2in. inlet and outlet. 110V AC. £22.00. Switchable transformer for 240V AC. **£8.00 p&p £3.00 - total £34.50 inc. VAT.**

VB4 CENTRIFUGAL BLOWER

240V AC powerful 1/50 hp. 0.23A motor. **£18.00 + £2.00 p&p - total inc. VAT £23.00, N.M.S.**

12/24V DC CENTRIFUGAL BLOWER

0.4A producing 30 cu.ft. **£7.50 + £1.00 p&p - total inc. VAT £9.78, N.M.S.**

COOLING or EXTRACTOR FAN

Quiet smooth running. Size 4 3/4 x 4 3/4 x 1 1/2. Supplied for 240V AC operation. Price **£4.75 + £1 p&p - total inc. VAT £6.62, N.M.S.**

HEAVY DUTY SOLENOID

mt. by Magnetic Devices 230V. A.C. intermittent operation. Approx. 20lb pull at 1.25 in. Ex.-equip. Tested. **£10.00 + £1.50 p&p (total inc. VAT £13.23).**



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230, 240V a.c. 50/60 OUTPUT 0-260V.
 200V/1A Max. **£18.50**
 0.5KVA 2 1/2A Max. **£21.00**
 1KVA 5A Max. **£29.00**
 2KVA 10A Max. **£41.00**
 3KVA 15A Max. **£56.00**
 5KVA 25A Max. **£99.00**
 10KVA 50A Max. **£181.00**
 15KVA 75A Max. **£275.00**



3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual input 200-240V or 380-415V. Star connected.
 3KVA 5amp per phase max. **£113.40** All V.V.T.s plus carriage and VAT
 6KVA 10amp per phase max. **£170.10**
 10KVA 16amp per phase max. **£345.45**
 Comprehensive range of TRANSFORMERS L.T. ISOLATION & AUTO (110-240V) Either cased with American socket and mains lead or open frame type available for immediate delivery. Leaflet on request.

12V D.C. BILGE PUMPS

400 G.P.H. 15ft. head, 3amp. **£8.00 + £1.00 p&p (£10.35 inc. VAT)**

700 G.P.H. 10ft. head, 3.5amp. **£11.50 + £1.50 p&p (£14.95 inc. VAT)**

1750 G.P.H. 15ft. head, 9amp. **£15.00 + £1.75 p&p (£19.26 inc. VAT)**

SINGLE DIAPHRAGM COMPRESSOR NMS

Max. 20PSI. One CFM approx. 240 volts A.C. **£18 + £2 p&p (£23 inc. VAT)**

EPROM ERASURE KIT

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case to include 12, 8 watt 2537 Angst. Tube. Ballast unit, pair of bi-pin leads, Neon indicator, safety microswitch, on/off switch and circuit.

LESS CASE Price **£13.60 + 75p p&p (Total inc. VAT £16.50)**
Warning: Tube used in this circuit is highly dangerous to the eyes. Unit must be fitted in suitable case.

SOLID STATE E.H.T. UNIT

input 230V A.C. Approx. 15kV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec. 30 sec. to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, e.g. supplying neon or argon tubes etc. **£6.50 + 90p p&p (Total inc. VAT £8.50) N.M.S.**

FROM STOCK AT PRICES THAT DEFY COMPETITION

AC GEARED MOTORS
 DC MOTORS SMALL
 MICROSWITCHES
 RELAYS
 REED SWITCHES
 SOLENOIDS A.C. or D.C.
 PROGRAMME TIMERS

C.F. BLOWERS
 AC CAPACITORS
 STROBE KITS
 FLASHTUBES
 CONTACTORS
 SYNCHRONOUS MOTORS

WIDE RANGE OF XENON TUBES
 WRITE/PHONE IN YOUR ENQUIRIES

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB. Tel: 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10

Ample parking space
 Showroom open
 Monday-Friday



Personal callers only. Open Saturdays
 9 Little Newport Street
 London WC2H 7JJ
 Tel: 01-437 0576

CIRCLE 52 FOR FURTHER DETAILS.

TDS900 FORTH COMPUTER

Build the TDS 900 into your products, program it with a VDU and your forecasts become fact.

NOW FROM £99

- ☆ Single board computer. 12k RAM and 8k ROM (expandable).
- ☆ All C-MOS for lower power. FORTH language. Compiled and fast. On-board screen-editor, compiler and debug facilities.
- ☆ Easy connection with serial and parallel channels, A/D, D/A converters, triacs, printers, keyboards and displays.



Triangle Digital Services Limited
 100a Wood St., Walthamstow, London E17, England
 Telephone: 01-520 0442 Telex: 262284 (Ref. 775)

Agents in USA, France, Switzerland, Netherlands, S. Africa, Australia

CIRCLE 57 FOR FURTHER DETAILS.

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, heavy duty brush assembly, continuously rated
25 WATT 5/10/25/50/100/150/250/300/500/1kΩ
 1.5kΩ £4.25 + 30p p&p. (£5.23 incl. VAT)
50 WATT 25/50/100/150/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ
 100 WATT 175/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ
 £10.25 + 75p p&p (£12.65 incl. VAT)
Black Silver Skrimed Knob calibrated in Nos 1.9, 1.11 2in dia. brass bush. Ideal for above Rheostats 30p ea. - VAT



INSULATED TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work constant speed clutch. Size L 8in. W 4in. H 6in. weight 6lb
500V 300 megohms **£49 p&p £2 (£58.65 incl. VAT)**
1000V 1000MΩ **£55 + p&p £2 (£65.55 incl. VAT)** SAE for leaflet

L.T. TRANSFORMERS

"Special Offer" 0.63V/0.63V at 10 Amp 112V 0.10 Amp or 6V at 20 Amp) Price **£9.00 p&p £2.00 - inclusive of VAT £12.65 N.M.S.**

GEARED MOTORS

5 rpm 240V AC mt. by Carter **£6.05** £1 p&p (£8.11 inc. VAT) N.M.S.
 20 rpm 115V AC Synchronous, torque approx. 80lb in **£20.00 - £4 p&p (Total inc. VAT £27.60) N.M.S.**

TRANSFORMER 240V operation. **£9.15 + £2.00 p&p (Total inc. VAT £12.82)**

28 rpm Torque 20lb in reversible 180th h.p. 110V AC. Price **£9.50 + p&p £1.80 (Total inc. VAT £12.99)**

Suitable **TRANSFORMER** for 230-240V AC operation. Price **£5.20 + p&p £1.40 (Total inc. VAT £7.58) N.M.S.**

38.8 rpm GEARED MOTORS Torque 35lb in. reversible 115V AC inc. start capacity. Price: **£11.55 + p&p £2.00 (Total inc. VAT £15.58), N.M.S.**

Suitable **TRANSFORMER 230V AC** operation. Price **£5.20 - 50p p&p (£5.56 incl. VAT)**

CROWN 37 rpm 2000lb in approx. 110V AC, reversible geared motor. Price **£35 p&p £1.50 (£36.50 inc. VAT) N.M.S.**

Suitable **TRANSFORMER** for above **£10 p&p £1.50 (£12.22 inc. VAT)**

57 rpm 240V 1/22 hp continuously rated REVERSIBLE 50lb in. mount by Wynstronets. New Ideal for garage doors, curtains etc. **ONLY £12.00 - £2.00 p&p (incl. VAT £16.10), inclusive capacitor**

71 rpm Torque 10lb in reversible 170th h.p. 110V AC motor. Price **£9.50 - £1.80 p&p (Total inc. VAT £12.99)**

Suitable **TRANSFORMER** for 230-240V AC operation. Price **£5.20 + p&p £1.40 (Total inc. VAT £7.58) N.M.S.**

24V DC 200 rpm 10lb in mt. by Carter. Ex-equip. tested. **£8.00 - £1.50 p&p (Total inc. VAT £10.93)**

230/240V AC SYNCHRONOUS, 2 rpm, 6 rpm, 6 rev per day. Any type **£4.80 - 50p p&p (Total inc. VAT £6.10)**

CHECK METER

230/240 AC 40 amp. fully reconditioned **£7.50 - £1.75 p&p (Total inc. VAT £10.64)**

SANGAMO WESTON TIME SWITCH

Type S251 200/250 A.C. 2 on/2off every 24 hours. 20 amps contacts with override switch. Diameter 4" x 3". Price **£9.50 + £1.50 p&p (£12.65 inc. VAT & p&p)**. Also available with solar dia R&T. Other types available from stock.

N.M.S. New Manufacturers Surplus
 R&T Reconditioned and tested
 Goods normally despatched within 7 days

ROBOTS

For Education, Training and Industry



NEPTUNE I
Kit from **£1250**



NEPTUNE II
Kit from **£1725**



MENTOR
Kit from **£345**

NEPTUNE I 6 axes; 8 bit control system, 2.5Kg capacity, 1120mm reach

NEPTUNE II 7 axes; 12 bit control system, 2.5Kg capacity, 1120mm reach

MENTOR DC servo desktop robot; 8 bit control system, 300gm capacity, 420mm reach

Robots programmed from keyboard or hand-held simulator (model robot)

Robots may also be taught by 'lead by the nose' method

Extensive software is supplied free with each robot.

Leads available for connection to BBC, ZX Spectrum, Apple IIe, Commodore 64 and VIC 20.

Most other micros are also easily usable with these robots.

Robots also available ready built.

Please phone for brochure: 0264 50093.
West Portway Industrial Estate, Andover SP10 3WV.
 A private and independent company giving prompt, personal service.

CIRCLE 14 FOR FURTHER DETAILS.

New Forth Microcard system



The Essex Forth Microcard measures only 10cm x 8cm but it is equipped to take on ambitious control tasks using the powerful FORTH Programming Language.

You can use the Essex Forth Microcard to turn a BBC B computer into a flexible workstation during program development but from then on the Microcard stands on its own.

The Essex Module Driver directly interfaces between mains level input/output signals and the Forth Microcard to provide safe and easy power control.

- R65F12 Processor with on chip Kernel
- Interactive Extended Fig FORTH Programming and 6502 Macro Assembler with FR1 Development ROM
- 40 Input/Output Lines and two programmable timers
- RS232 Interface and Autostart Operation
- BBC Compatible Development Tools

SEND TODAY FOR OUR INFORMATION PACKAGE ON THIS REVOLUTIONARY SYSTEM

* Special Pricing Introductory Price
 ■ FORTH MICROCARD £119
 ■ I/O MODULE DRIVER £78
 ■ FORTHWRITER DISK £48
 SUBSTANTIAL DISCOUNTS FOR LARGER QUANTITIES

Essex Electronic
 UNIVERSITY OF ESSEX
 COLCHESTER
 CO4 3JQ

CIRCLE 55 FOR FURTHER DETAILS.

USED TEST EQUIPMENT & COMPUTER PRODUCTS

- ★ Fully guaranteed
- ★ Performance to original specification
- ★ Wide range of instruments & computer products

From

CARSTON

01 943 4477

Ring for latest stock information



99, Waldegrave Road, Teddington, Middlesex TW11 8LL.
ELECTRONICS LTD. Telephone 01-943 4477. Telex 23920 (Euhire)
 Used test equipment and computer specialist

CIRCLE 69 FOR FURTHER DETAILS.

ELECTRONICS C.A.D. "ANALYSER"

PERFORMANCE ANALYSIS of LINEAR CIRCUITS using the BBC MODEL B AND SINCLAIR SPECTRUM 48K MICRO'S

Simulates Resistors, Capacitors, Inductors, Transformers, Bipolar and Field effect Transistors, and Operational Amplifiers in any circuit configuration.

Performs FREQUENCY RESPONSE ANALYSIS on Circuits with up to 30 Nodes and 100 Components, for Phase and Gain/Loss, Input Impedance and Output Impedance.

Ideal for the analysis of ACTIVE and PASSIVE FILTERS, AUDIO, WIDEBAND and R.F. AMPLIFIERS, LINEAR INTEGRATED CIRCUITS etc., etc.

"ANALYSER" can greatly reduce or even eliminate the need to breadboard new designs.

USED BY INDUSTRIAL AND UNIVERSITY R&D DEPARTMENTS WORLD WIDE.

VERY EASY TO USE. PRICES FROM £20 ACCESS OR AMERICAN EXPRESS WELCOME...

For further details write or phone NUMBER ONE SYSTEMS

DEPARTMENT WA
 9A CROWN STREET, ST IVES
 HUNTINGDON
 CAMBS. LK. PE17 4EB
 TEL: 0480 61778 TELEX: 32339

CIRCLE 20 FOR FURTHER DETAILS.



Audio Measuring Instruments, Audio Amplifiers, Loudspeakers and Loudspeaker Components for the professional and enthusiast

RADFORD AUDIO LTD.
 10 BEACH ROAD
 WESTON-S-MARE, AVON BS23 1AU
 TEL. 0934 416033

CIRCLE 42 FOR FURTHER DETAILS.

Electronic altimeter

This low-cost instrument also indicates the rate of climb or descent. Groundlings can use it as a barometer.



by Frank Ogden

The author's version is fitted with straps for fixing to the pilot's knee. To the right of the altimeter display is the variometer, which is sensitive enough to reach almost to full-scale deflection in the lifts at Quadrant House. The black insulating tape is for vibration-proofing.

Proper aircraft instruments are hideously expensive because they have guaranteed accuracy over a wide range of environmental conditions. I fly a micro-light aircraft and find little need for instruments which read way beyond the performance limits of the machine. The design outlined here is a combined altimeter and variometer (vertical speed indicator) which provides accurate and reliable readings to transition altitude (3000ft).

Naturally I have optimised the design to my own requirements, but selection of other resistor values would allow the circuit to be used as a weather barometer — there is enough long term stability — or as a straight altimeter reading to 20 000ft and beyond. It would be more difficult to incorporate a vario function on

the extended height scale, though.

The design is a true aneroid barometer. The pressure transducer, an MPX 100 manufactured by Motorola, was intended as a cheap and cheerful unit to measure the vacuum in an induction tract for automotive fuel injection systems. Designed to read over the range 0 to 15p.s.i., it comprises a silicon strain-gauge configured as a Wheatstone bridge with an in-built vacuum chamber under the silicon die. Variations in air pressure cause flexing of the gauge resistors. This leads to a voltage change across the bridge of roughly 1mV/1000ft (30mbar).

IC₁ is a chopper-stabilised op-amp connected in the differential mode with a gain of about 50. Thus the output at the


test point (pin 10) would show a 1V positive change for an increase in height of 20 000ft.

Anyone who wishes to make a large-range altimeter should note this. A digital voltmeter module with a scaled f.s.d. of 1V (reading 1999) connected to this point would make a very effective digital altimeter with a resolution of 10ft. Note however, that liquid crystal displays tend to fade at the low temperatures associated with this altitude.

IC₂ provides further voltage gain, about 20 times with the resistor values shown, and also acts as a buffer for IC₁. This is important because the current output of the 7650 chopper amplifier is very limited. The voltage change at pin 6 of IC₂ is about

The pressure transducer can be ordered through Motorola distributors, including Hawke Electronics (45 Hamworth Road, Sunbury on Thames, Middlesex), who list it at £11.50 plus v.a.t. An equivalent device is the Sensym SPX100A, stocked by Farnell Electronic Components (Canal Road, Leeds LS12 2TU) at £20.35 plus v.a.t.

ELECTRONIC ALTIMETER

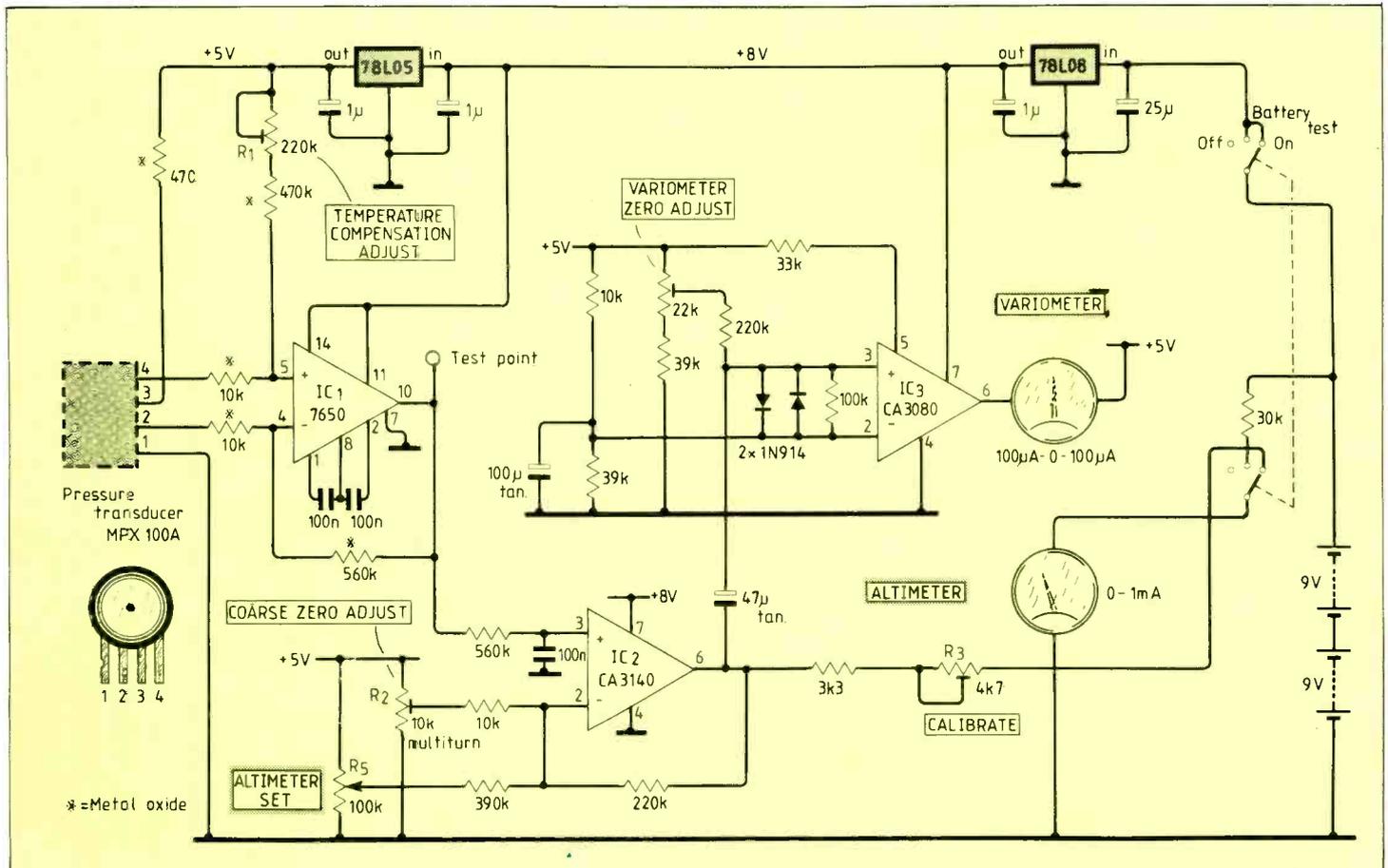

Pressure transducer is a low-cost device intended for the motor industry. Temperature compensation is achieved by the 7650 chopping op-amp and a Wheatstone bridge circuit.

1V/1000ft, which is available to drive a meter movement for altitude indication. The resistor and preset associated with the meter movement are for altimeter calibration purposes. The original design used a 1mA instrument; other movements could be used provided that a suitable scaling resistor chain is provided.

The main reason for wanting a large voltage change with height is that the vario circuit can then be very simple. IC₃ is a transconductance op-amp (voltage in, current out) connected directly to a centre-zero meter movement.

A low-leakage tantalum bead capacitor couples the voltage changes at pin 6 of IC₂ to the input of IC₃. This translates any changing voltage into a static output current proportional to the rate of change of the voltage and deflects the centre zero meter, giving an accurate indication of rate of climb or descent.

As shown, the circuit is sensitive enough to produce deflection by just running up or down a flight of stairs. In keeping with the requirements of hang gliders and microlights, it is much more sensitive than standard aircraft variometers. Maximum output current from IC₃ is controlled by the single programming resistor attached to pin 5.

Power is provided by a couple of PP3 batteries: total current drain is about 18mA. The cascaded voltage regulator chain ensures that the 5V supply which powers the transducer and other components is of extreme stability over the life of the batteries. The circuit will operate down to a combined battery voltage of

about 11V.

My original was built on Veroboard and housed in a small ABS box. Layout is uncritical but care should be taken to avoid voltage gradients around the front-end components. Leakage through the board around the input pins to IC₁ can cause 'noise' to affect the vario. A good soaking with Damp Start or other proprietary water-repellent silicone compound is a good idea. Guard bands around the input circuitry may also be useful. The keener constructor — not me — would want to make a proper p.c.b. using glass epoxy material, finally passivating with some sort of conformal coating.

Setting up the circuit is a little bit involved because most of the adjustments are interactive. Preset R₁ controls temperature compensation. R₂ provides coarse adjustment of output voltage. R₃, instrument calibration, should initially be set to its minimum value.

The most pressing design problem with any electronic altimeter circuit is the removal of temperature drift. The silicon strain-gauge resistors in the transducer possess an extremely large temperature coefficient. The Wheatstone bridge connec-

Continued on page 41



The altimeter was designed for low cost flying such as microlighting. Here the author prepares to get airborne in a 40hp Striker, G-MJPJ.

The new logic symbols — 3

This third and final part considers the practical aspects of implementing the standard.

Part 1 of this series gave a preview of a complex symbol in Fig. 8. This figure will now be explained in detail, and for convenience, is repeated as Fig. 27. It depicts what amounts to three separate logic functions in one symbol, and this is achieved by embedding common control boxes, as may be seen. This is, in fact, the 74690 device. An outer multiplexer (MUX) block has embedded within it a 4-bit register; the register block has embedded within it a 4-bit synchronous counter.

For the moment let us leave aside why one should want to condense all these functions into one symbol and instead consider the meaning of the symbol, for in so doing, we shall also see how the same logic functions may be represented at different levels by means of the new logic symbols.

The easiest way to explain the logic symbol shown in Fig. 27 is to show a simplified lower-level representation of the same logic functions in Fig. 28. Here may be seen the three primary logic functions, and suddenly the whole thing becomes much more simple.

The following explanation of the device's function is applicable to either figure since identical labels have been employed. The counter/divider is a decade counter (signified by the '10' after the 'CTRDIV' portion of the general qualifying symbol. The input on pin 13 selects mode (high for count or low for load). Pin 1 is an active-low counter-clear, and the ripple-carry output on pin 19 goes high at a count of 9 (CT=9), subject to Anding with input ENT. Parallel loading is performed at the A, B, C, D inputs when pin 13 is low (Mode 1), in response to a clock pulse at pin 2. Pin 2 has an alternative function signified by

that portion of the label to the right of the solidi: the counter is clocked by a pulse at pin 2 provided that pin 13 is high (Mode 2) and both enables (G3 and G4) are high. The '+' sign signifies an 'up' counter.

The 4-bit D-type register is used to staticise the output from the counter when clocked by a positive-going pulse applied to pin 9. This register may be independently cleared by a low on pin 8.

The output multiplexer selects either the output from the register if the select input on pin 11 is high (dependency label 21 true), or the output from the counter if the same pin is low (dependency label 21 false). Three-state outputs (signified by the inverted triangle on the four outputs) is enabled by a low on pin 12 (EN dependency labelled 23).

The above is readily followed with respect to Fig. 28, and if this is firstly understood, the explanation of the symbol in Fig. 27 follows by comparison. Note that Fig. 27 divides the three separate functions into what amounts to three vertical columns, and the inputs to each segment of the common control blocks correspond to those taken to the different common control blocks in Fig. 28. Because of the need to take an output from the inner (CTRDIV10) common control block (to pin 19) it has been necessary to introduce interconnection dependency in Fig. 27 (Z22). Particular note should also be taken of the two horizontal sections of the upper element of the array portion of the symbol; this enables the two alternative inputs to the multiplexer to be shown with their respective dependency labels; as explained previously, it is implied that the same rules apply for the lower

elements in the array (i.e. all bits feed a register and an output multiplexer).

Getting the level right

I would now like to consider the practical aspects of different levels of representation. The foregoing example has clearly demonstrated two important points about the new logic symbology:

- (a) the form is dependent upon the originator;
- (b) the level of representation is variable for complex functions.

I believe that the level of representation should be selected with the purpose in mind. If the simplest representation for understanding the logic function is required, then this must be a merit judgement. If the most compact form of representation is required (say on a compact circuit diagram) then a complex condensed symbol may be used.

Let us consider the two alternatives shown in Figs 27 and 28. The device manufacturer may choose to use the complex symbol given in Fig. 27 because it takes less space on his data sheet. To the newcomer to the symbology it is more difficult to understand this than the expanded version given in Fig. 28, but with regular use and familiarity, it is perfectly adequate. The device manufacturer could also legitimately argue that this complex symbol is an alternative to the simple and uninformative rectangle which would have been used prior to the new symbology, and that as such, it is a great improvement, since the full logic functions are represented (for those who can understand it).

On the other hand, if the purpose is to explain the purpose of the device to someone not

by Ian Kampel,
M.I.E.R.E.

Further reading

IEC Publication 617:12, Graphical Symbols for Diagrams: Binary Logic Elements. (This is the international standard which has resulted from discussion by all participating countries, and this forms the basis for all complying national standards). International Electrotechnical Commission, 1 Rue de Varembe, Geneva, Switzerland. British Standard 3939: Section 21,

Graphical Symbols for Electrical Power Telecommunications and Electronics Diagrams: Binary Logic Elements. (This is the relevant British Standard. At the time of writing, Issue 3 is expected to be published in the Spring of 1985, and should be identical in detail to the IEC publication mentioned above). British Standards Institution, British Standards House, 2 Park Street, London W1A 2BS. (Telephone: 01-629 9000)


A Practical Introduction to the New Logic Symbols by Ian Kampel. (Butterworth Scientific Ltd).

Acknowledgements


The author is greatly indebted to the following: D.B.J. Hicks of the British Standards Institution, C.J. Stanford and L. van Rooij, General Secretary and Deputy General Secretary of the International Electrotechnical Commission, for their invaluable assistance in the research work for my book, N. Warnock-Smith of Butterworth Scientific Ltd., for his kind co-operation in the use of illustrations from my book for this article, and J. Molyneaux, who penned the excellent illustrations.

LOGIC SYMBOLS


27

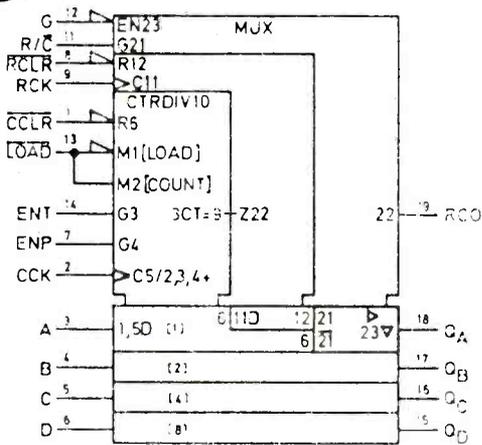


28

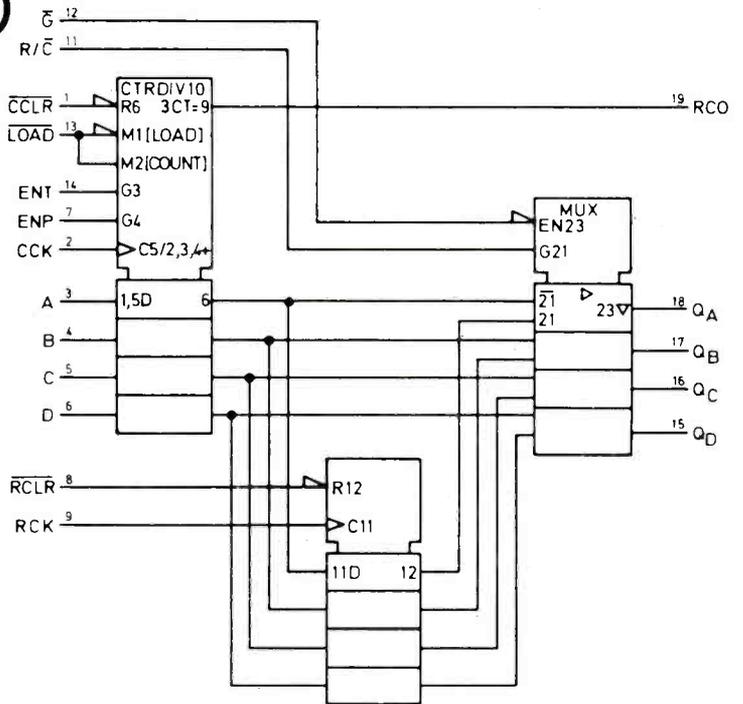


29

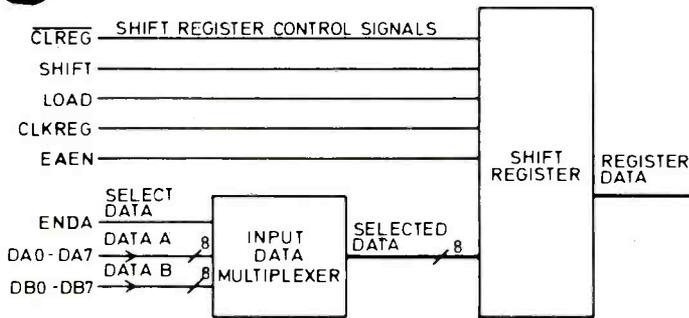

30

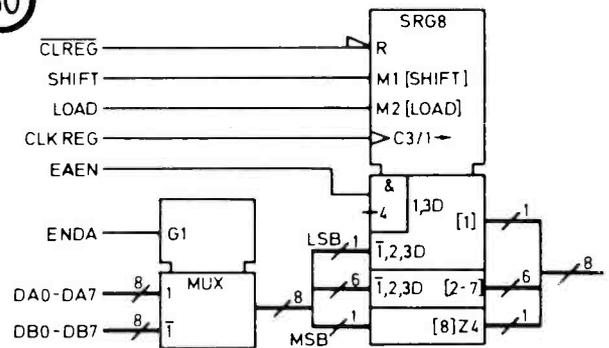

31

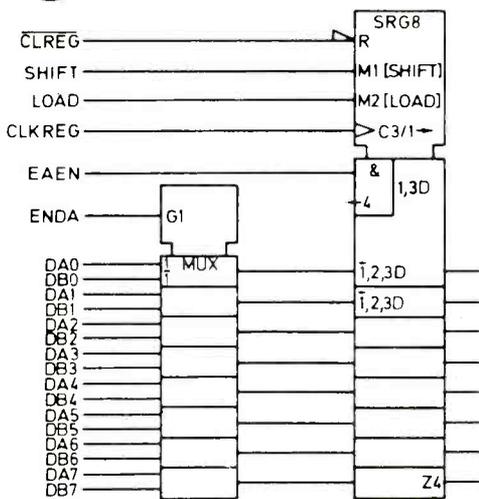

32

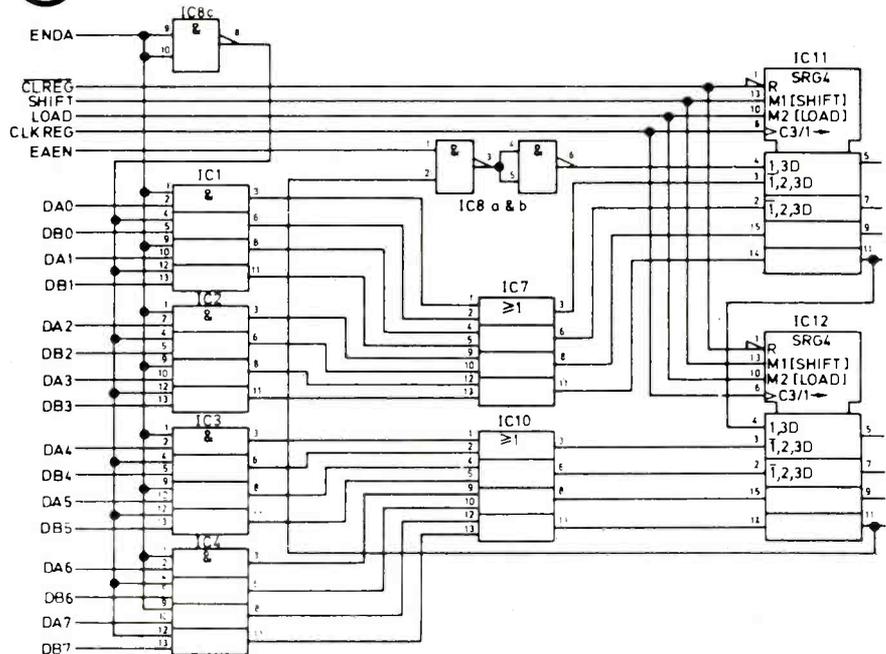


Fig. 27 Example of a more complex symbol - a 4-bit synchronous counter with output registers and multiplexed 3-state outputs (74690)

Fig. 28 Simplified representation of Fig. 27.

Fig. 29. Block diagram showing all the interface signals for a circuit.

Fig. 30. Pure logic diagram of Fig. 29.

Fig. 31. Logic diagram version of Fig. 30.

Fig. 32. Circuit diagram version of Fig. 31.

expected to understand such a complex symbol as that shown in Fig. 27, then undoubtedly the version shown in Fig. 28 should be used.

During the transitional period when old and new symbols will exist side by side (as they presently do in a single Texas Instruments data book), I think that manufacturers should provide both versions for a complex device such as that considered here. The compact form can then be used accurately by engineers on logic circuit diagrams, yet the simpler equivalent version is available in the data sheet to aid understanding (for them and the end-user). As time passes, the simpler circuits could gradually be phased out.

Beware of academics

The new logic symbology is a sitting target for those academically-minded persons who might get a kick out of purposely creating over-complex symbols. If the new logic symbols are to be a success, let no one take this particular path, for it will bring forth wrath! *Understanding is the thing*, especially over the next few years when so many are required to learn so much so quickly.

Practical implementation in design groups

I shall finish this series with an example of how the new logic symbology might be used to good advantage in a design group where system engineers, equipment engineers and board designers have to work hand-in-hand. To do this I have taken a portion of a more complex example given in my book on this subject (see Chapter 18 of the book).

Figure 29 shows part of a design requirement at the level that a system designer may wish to consider matters. He wants to multiplex two 8-bit parallel data streams (DATA A and DATA B) and apply the output to a shift register (true, this is too simple for a system but a simple example is necessary — this represents a small portion of a much larger design requirement). The block diagram is how he might initially present the requirement. Figure 30, on the other hand, is a representation of the same thing as he can now present the requirement employing the new logic symbols. Where the block diagram

left certain aspects in an ambiguous form (e.g. the polarity of the SELECT DATA, SHIFT, LOAD, and enable signals, not to mention the form of clock and direction of shift), the pure logic diagram makes everything clear. It also enables him to show the requirement for an end-around capability controlled by the EAEN input; the block diagram requires many words to make all this clear, whereas the logic diagram using the new symbols specifies *everything*.

Where the pure logic diagram given in Fig. 30 depicts the logic functions in the simplest manner without specific reference to methods of physical implementation, an equipment engineer might turn this into a more detailed *logic diagram* as shown in Fig. 31. This shows the detail of *all* logical relationships but does not, in this case, show the point-to-point wiring. It provides sufficient detail, however, for him to place a specific design requirement for a board designer to follow.

The design engineer receiving the logic diagram shown in Fig. 31 might then produce a *circuit diagram* such as that shown in Fig. 32. (This might be far from an optimum implementation of the design requirement, but does serve to show how a logic diagram and a circuit diagram can greatly differ in form). We can see here that for reasons best known to himself, he prefers to use two 4-bit shift registers than a single 8-bit shift register, and perhaps for economic, supply, or a host of other practical reasons, he prefers to build his own multiplexer with And or Or gates than use multiplexer devices.

Improved clarity

The rather pathetic design implementation shown in Fig. 32 is really chosen to illustrate one of the tremendous advantages of the new logic symbology. Let us now consider the problem in reverse, and assume that we are stuck with this circuit diagram and wish to clearly represent this in a handbook. Figure 31 does just that, in a much simpler form, yet still provides all the necessary information about overall functions including all input and output lines; all that is missing is implementation detail. Figure 30, on the other hand, provides an even simpler representation of the overall function if individual

lines need not be shown. Now whilst words may be added to complement either the logic diagram or the pure logic diagram to explain it more simply, *they cannot convey any extra information about logic function*.

Conclusion

These final examples show the great features of the new logic symbology. *It is both concise and precise*. Amazingly, this statement holds true no matter what the level of representation chosen.

This article can only scratch the surface of the new symbology, and as you will have seen, this is far from a standard for drawing office personnel — it is for *engineers*.

Electronic altimeter

from page 38

tion cancels much of the temperature drift, but the bridge is essentially unbalanced towards the high end of the pressure range.

The full drift voltage with temperature is developed as a large common-mode variation on the input to the differential amplifier. The basic 7650 chop-amp has an exceptional common mode rejection ratio. This is artificially reduced by unbalancing the input circuit through adjustment of R_1 , the temperature compensation trimmer, in a direction which cancels any change in the differential voltage across the transducer with temperature. The standing voltage on pins 2 and 4 of the transducer is about 1V: this changes with temperature at the rate of (roughly) 1mV/K.

Having checked that the standing current of the assembled unit is in the region 15 to 20mA, connect a voltmeter to the test point on IC_1 . This should read in the region of 0.5 to 2.5V with R_1 at mid-setting. Adjust R_2 such that the output voltage of IC_2 (pin 6) is around 2V. Warm the transducer gently with a hair-dryer and note the direction of any change in output voltage from IC_2 . Adjust R_1 , noting the direction of adjustment. This will alter the standing output voltage from IC_2 . Readjust R_2 to bring the output voltage back to 2V.

Allow the transducer to cool back to room temperature. Warm (gently!) the transducer once more and note if temperature drift is increased, reduced,

reversed or eliminated. Repeat the process until any sensitivity to temperature is eliminated. Make sure that the voltage on the IC_1 test point (pin 10) does not go outside the range 0.5 to 2.5V.

With temperature stabilization achieved, calibrate the instrument using R_3 . This is best done by comparing readings with that of a certified instrument. Set R_3 to mid position. Set R_3 to minimum. Adjust R_2 such that the readings on both instruments are the same at ground or airfield level. If the airfield has an altitude of above 100ft, readjust both instruments such that both ground level readings are just under this figure.


Fly both instruments up to 1500ft or more. The electronic instrument should considerably over-read. Note the reading of both instruments accurately.

On the ground once more, use R_2 to reproduce the meter deflection achieved at the known altitude. Back off R_3 so that the instrument now reads the same as the certified instrument did at that altitude. Re-adjust R_2 to bring instrument within the normal adjustment range of R_5 , the 'altimeter set' control. Finally, carry out a flight check of the instrument against the certified altimeter.

R_4 zeroes the vario. If a less sensitive rate of climb/descent indicator is required, simply reduce the value of the capacitor connected between IC_2 , pin 6 and IC_3 . Happy flying.


Not only in height is the range of Clark Masts wide but also in the field of application. Every model, mechanical or air-operated, has been created in response to customer requirement and proved in service; for over 25 years.

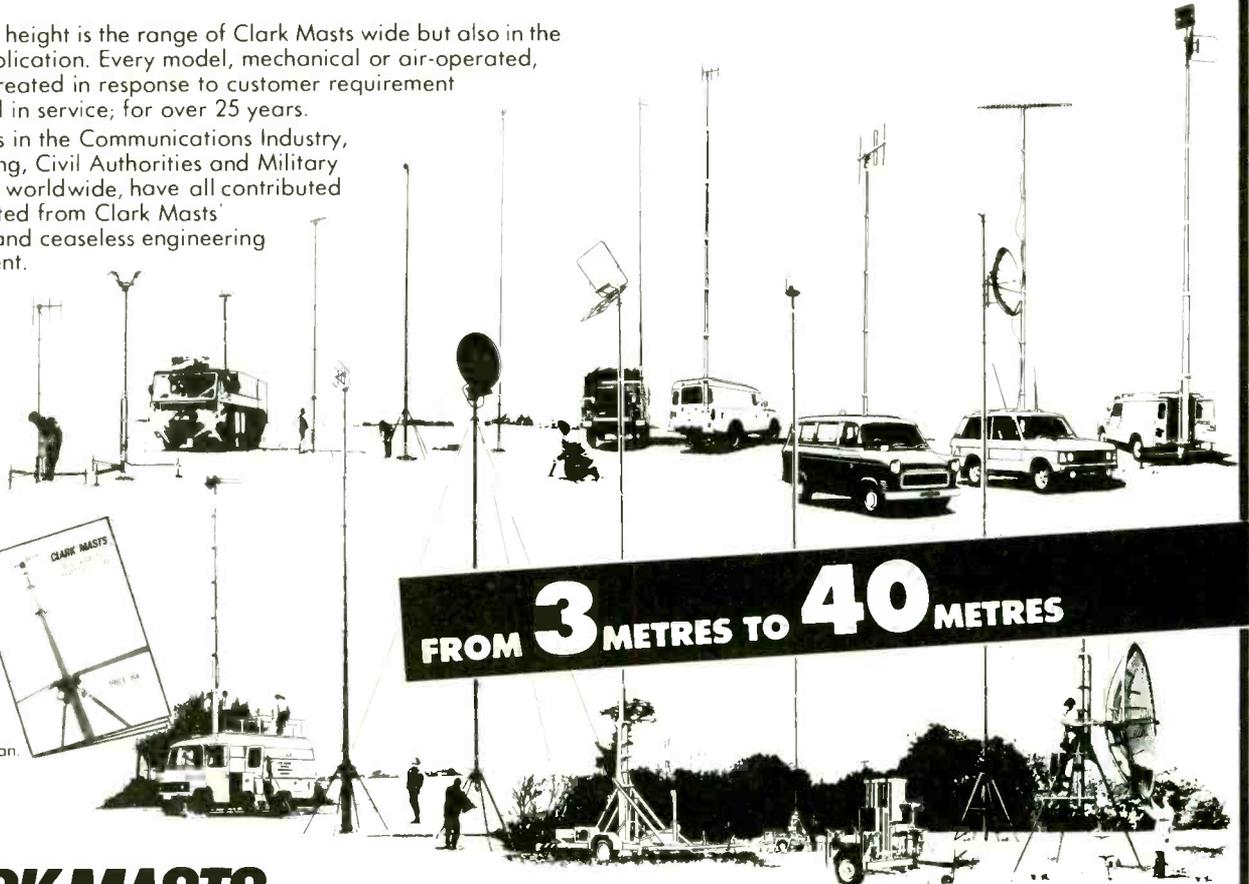Major users in the Communications Industry, Broadcasting, Civil Authorities and Military Commands worldwide, have all contributed and benefited from Clark Masts' reliability and ceaseless engineering improvement.



FROM 3 METRES TO 40 METRES

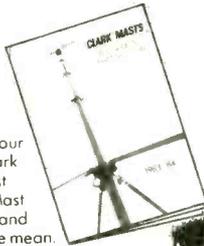Write for your copy of Clark Masts' "Fast Guide to Mast Selection" and see what we mean.



CLARK MASTS

UK CLARK MASTS Ltd. (WV), Binstead, Isle of Wight, England. Tel. (0983) 63691 Telex. 86686.

EUROPE GENK TECHNICAL PRODUCTS N.V. (WV), Woudstraat 21, 3600 Genk, Belgium. Tel. 011/38.08.31 Telex. 39354.

CIRCLE 32 FOR FURTHER DETAILS.


LOOK AHEAD!

WITH MONOLITH MAGNETIC TAPE HEADS VIDEO HEAD REPLACEMENT KIT

DOES YOUR VCR GIVE WASHED OUT NOISY PICTURES - IT'S PROBABLY IN NEED OF A NEW HEAD - FAST FROM OUR EX-STOCK DELIVERIES.

SAVE £££s ON REPAIR CHARGES.

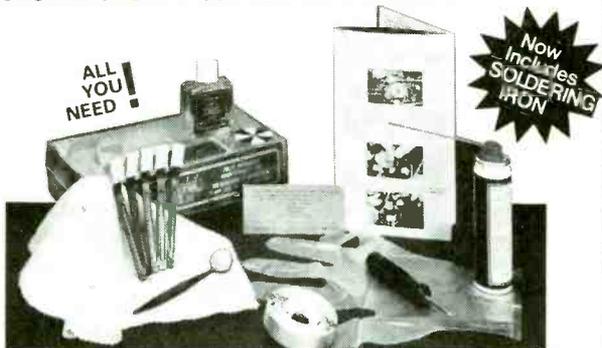OUR UNIVERSAL REPLACEMENT VIDEO HEADS FIT ALL MODELS OF VHS OR BETAMAX VCRs. FOLLOWING OUR REPLACEMENT GUIDE AND WITH A PRACTICAL ABILITY, YOU CAN DO THE WHOLE JOB IN YOUR OWN HOME WITH OUR HEAD REPLACEMENT KIT.



KIT CONTAINS - NEW VIDEO HEAD, 5 CLEANING TOOLS, HEAD CLEANING FLUID, CAN OF AIR BLAST, INSPECTION MIRROR, ANTI-STATIC CLOTH, VHS/BETAMAX MAINTENANCE MANUAL, CROSS HEAD SCREWDRIVER, HANDLING GLOVES, MOTOR SPEED DISC, SERVICE LABEL, HEAD REPLACEMENT GUIDE.

VHS KITS £63.25, BETAMAX KIT £75.25. Prices include P&P and VAT
HOW TO ORDER: PLEASE STATE CLEARLY THE MAKE AND MODEL OF YOUR RECORDER. THERE ARE TWO VERSIONS OF THE VHS HEAD AND YOUR ORDER CAN BE PROCESSED FASTER IF YOU CHECK THE SIZE OF THE CENTRE HOLE OF THE HEAD WHICH WILL BE EITHER 5mm OR 15mm DIAMETER.

CATALOGUE: For our full Catalogue of Replacement Video and Audio Cassette/Reel to Reel Heads, Motors, Mechanisms, etc. Please forward 50p P&P.

THE MONOLITH ELECTRONICS CO. LTD.
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone: Crewkerne (0460) 74321
Telex: 46306 MONLTH G



CIRCLE 61 FOR FURTHER DETAILS.

FOR QUALITY COMPONENTS
BY MAIL ORDER

ELECTROVALUE

FREE
44 PAGE
PRICED AND
ILLUSTRATED
CATALOGUE
ON REQUEST

FREE POSTAGE
GOOD DISCOUNTS
GOOD SERVICE
THOUSANDS OF
STOCK ITEMS
PHONE YOUR ORDER
ACCESS OR
BARCLAYCARD

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham,
Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475
North Branch, 680 Burnage Lane, Manchester M19 1NA
Phone 061 432 4945
Please mention this publication when replying

CIRCLE 37 FOR FURTHER DETAILS.

Now! Tek quality and expert advice are just a free phone call away...



Our National Order Desk line gets you fast delivery of the industry's leading value/performance portables... and technical advice from experts!

The 60MHz 2213A, 2215A and the 100MHz 2235 and 2236 offer unprecedented reliability and affordability, plus the industry's first 3 year warranty on labour and parts, CRT included.

All 2200 series scopes have the bandwidth for digital circuits and sensitivity for low signal analogue measurement. The sweep speeds for fast logic families, and delayed sweep for fast, accurate timing measurement. The top of the range 2236 combines a counter/timer/DMM with the scope to provide fast, easy measurements for voltage, resistance and temperature.



These UK manufactured 'scopes are obtainable through the National Order Desk. Call us to order or obtain literature, or to talk to our expert on 'scope applications.

...talk to Pete

Dial 100 and ask for
Freefone Tek-scope

Tektronix UK Ltd
Fourth Avenue, Globe Park,
Marlow, Bucks SL7 1YD
Tel: (06284) 6000
Telex: 847277 & 847378

The Company reserves the right to modify designs, specifications and change prices without notice.

CIRCLE 29 FOR FURTHER DETAILS.

Tektronix
COMMITTED TO EXCELLENCE

Gould... Innovation and Quality in Oscilloscopes

ELECTRONICS APPLICATIONS

TRANSDUCER APPLICATIONS

Dual-Purpose Storage...

The Gould 1421 Digital Storage Oscilloscope (DSO).


A Dual-Purpose DSO for Electronics and Transducer applications. Compare the benefits of the low-cost 1421 and its suitability for two diverse application areas, with the performance of our competitors. The 1421 has a storage bandwidth up to 20MHz - in single and dual-channel modes.

Take a look at the heavyweight performance details of this compact, lightweight DSO:

- No trace degradation with time.
- Storage of pre-trigger information.
- 2MHz 8-bit ADC for transient capture.
- 20MHz repetitive signal storage.
- 1k store per channel.
- x10 post-storage expansion.
- Pen recorder output.
- Single channel trace hold for waveform comparison.
- Conventional 'scope operation up to 20MHz.

And all the usual benefits of a Gould Digital Storage 'Scope.

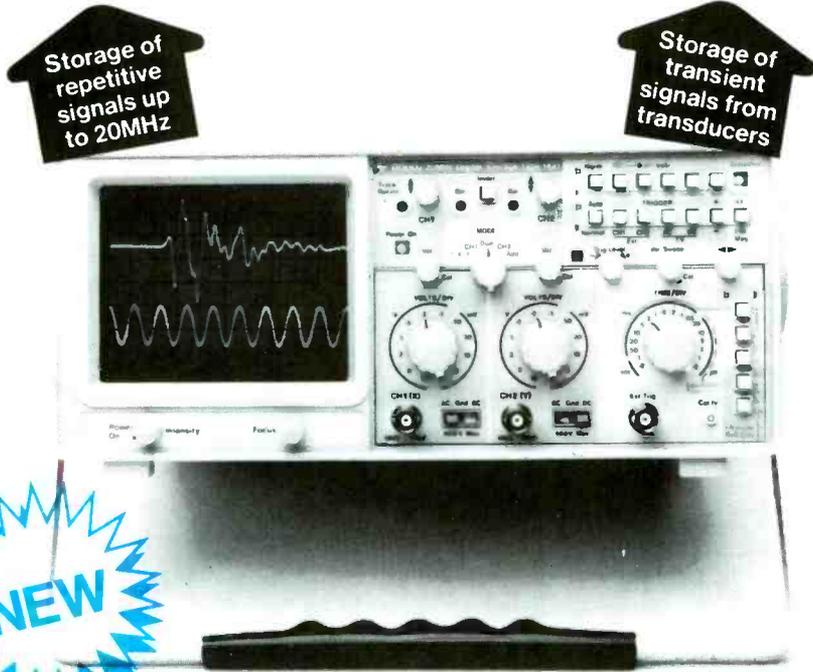Ask for more details now from Gould Instruments Ltd., Roebuck Road, Hainault, Ilford, Essex IG6 3UE. Telephone: 01-500 1000. Telex 263785.



BRITISH MADE
TWO YEAR WARRANTY



CIRCLE 56 FOR FURTHER DETAILS.

CRICKLEWOOD ELECTRONICS LTD

It's no secret...

That there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED
40 Cricklewood Broadway, London NW2 3ET
Tel: 01-450 0995/01-452 0161
Telex: 91 4977

CIRCLE 8 FOR FURTHER DETAILS.


GET TUNED TO TELEVISION

The technology of television won't stand still: satellites, videotex, cable, video, equipment interfacing, high-definition. Follow developments month by month in this unique magazine for all interested in the technology of domestic TV and video.

May issue's main features are:

- Video Fader Unit Clean fades, colour capable, cheap and easy to build.
- Teletext Intrusions Modifications for teletext interference.
- Tomorrow's Sets Chips that give new signal processing possibilities.

May issue out now

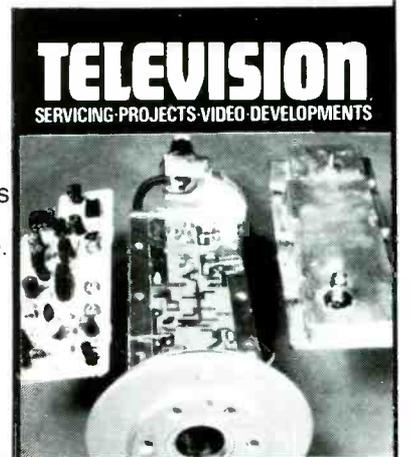

Automatic enlarger timer



by J.L. Linsley Hood

This instrument is intended as a labour saving device in the photographic darkroom in the preparation of enlargements on bromide or similar (black and white) printing paper.

In conventional photographic practice, it is necessary to determine the required exposure of the paper to compensate for variations in the density of the negative, the light output of the enlarger, the aperture of the enlarging lens, and the activity of the print developer, and this is normally done by making a series of test strips having graded exposures, so that the most satisfactory exposure can be determined subsequently by inspection.


The only snag with this practice is that it is time consuming, and if a large number of prints is to be made from negatives having differing optical densities, a large part of the darkroom time may be occupied in making test strips for each negative.

Techniques which have been evolved for minimising this

wasted time, determining the required exposure by optical or photoelectric techniques, have relied in general upon the use of some device which could be moved into the region of the projected image so that the enlarger exposure timer could be set, prior to the exposure, to give an appropriate exposure duration. My own thoughts, however, had turned to the possibility of a system which measured the light scattered back from the surface of the printing paper so that the printing exposure could be controlled 'in real time', as contemporary phraseology would have it.

This has the advantage of being much quicker in use, since all that is necessary, when the negative is in place and correctly focussed, is to place a piece of printing

Fig. 1. Layout of reflex automatic photoelectric enlarger timer system

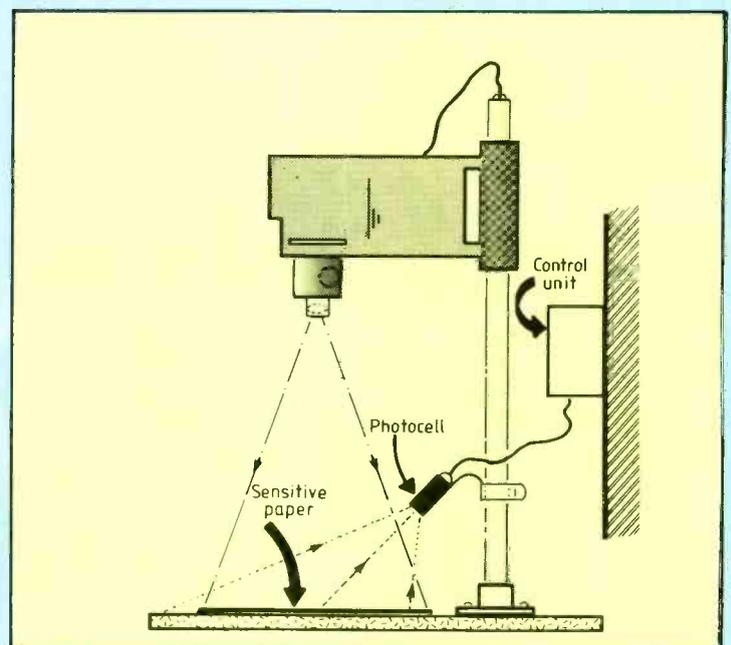

DARKROOM TIMER

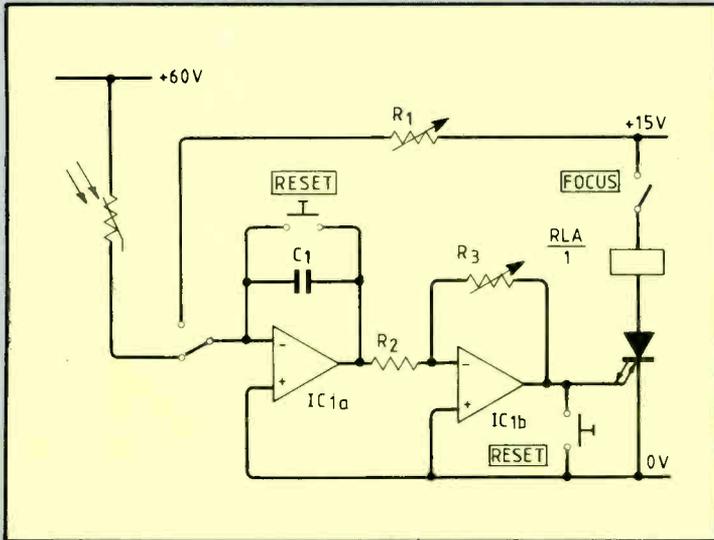


Fig. 2. Basic circuit of timer

paper in the correct situation, and press the 'on' button. The enlarger then switches on for a suitable period, and when the photoelectric sensor judges that an adequate exposure has been given, switches the lamp off again.

Fig. 3. Complete circuit of enlarger timer

I have had such a system in use in my own darkroom for very many years, since I tend to use a 35mm camera as a photographic diary,

and I like to print the majority of the resultant negatives to somewhat larger than contact print size. My earliest model used a photomultiplier tube/lens assembly, but this was delicate and prone to damage, and I have, in consequence, revised and updated the system over a period of many years to take advantage of improvements in electronic and photocell technology.

Although a similar system could be evolved for colour printing, there are additional problems there, associated with the colour sensitivity of the photocell in use, and I have not sought to confront these, since my own interests lie mainly in the field of monochrome photography.


Practical problems

The use of any reflected-light photoelectric system obviously leads to the possibility of exposure errors due to variations in the amount of light reflected from the surface of the bromide paper sheet, in the general layout shown in Fig.1, depending on whether the paper is glossy or

mat in surface finish. However, provided that one is consistent in the use of a particular paper type in the making of a series of prints, differences of this kind are merely reflected in apparent differences in paper sensitivity — which will, in any case, probably vary from one batch of paper to another.

A more basic snag, assuming that the photocell viewing system has been chosen so that it 'sees' the whole of the desired printing area, is that the system operates by averaging the print to a notional 'grey' tone.

While this averaging effect, in determining the exposure which is required by the sensitive paper, works surprisingly well with the majority of 'normal' subjects, where the amount of dark tone is balanced by a similar quantity of lighter area, there are, clearly, occasions when the expected appearance of the picture will be light — such as where the bulk of the picture area is occupied by sky, or other light-toned objects. There will also be occasions when the overall tone of the picture will be very dark,

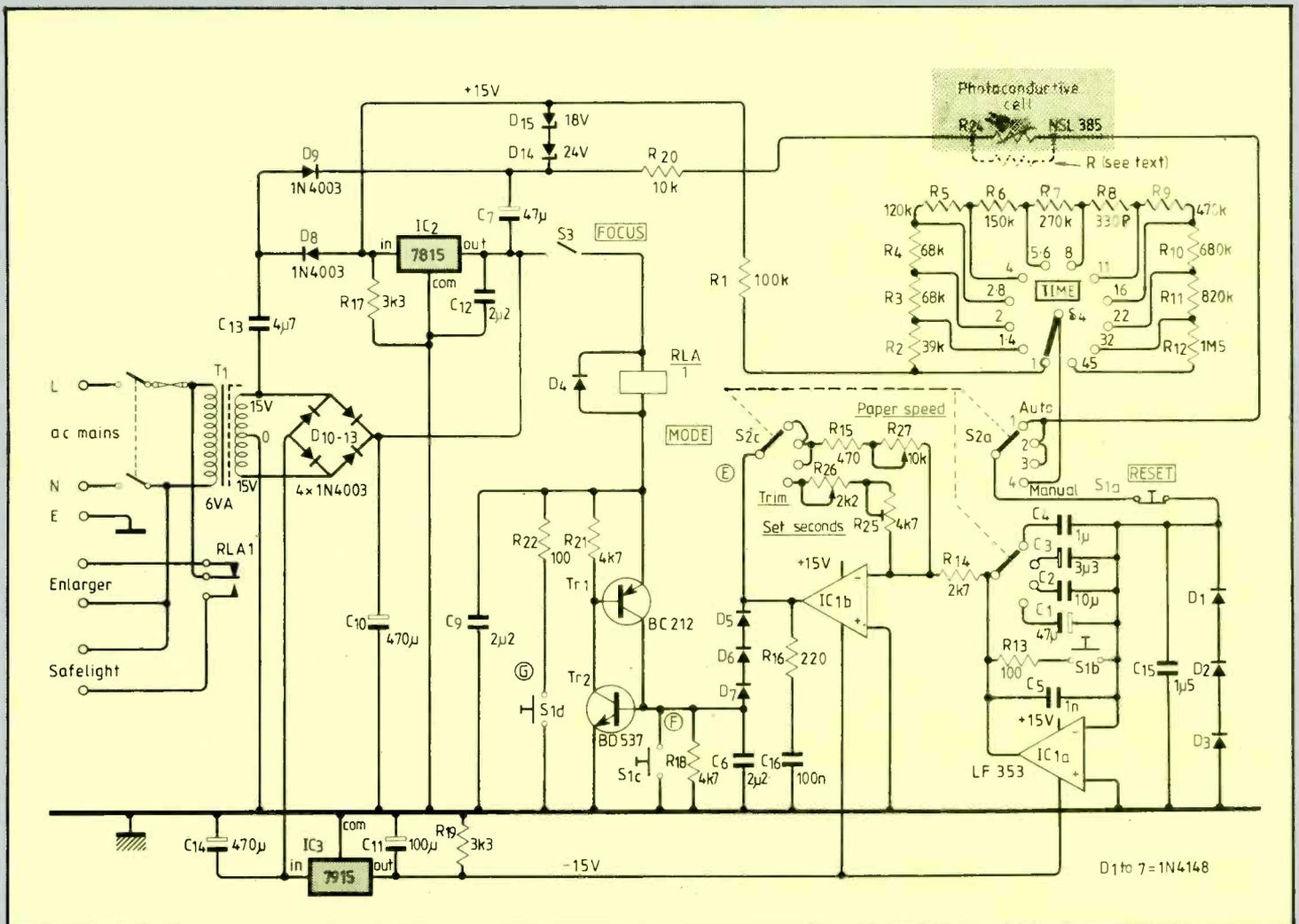

and again the exposure determining system cannot be expected to give an exposure which will produce this effect.

It is therefore necessary to build into the circuitry some control, at the disposal of the user, which will allow him to decide whether he wishes an overall light, or overall dark result. Fortunately, most enlarging papers allow some measure of latitude in printing exposure, which can be compensated for by adjustment to the developing time of the print, where complete development is usually assessed visually, so complete precision in exposure is not normally imperative. Experience suggests that with printing papers of normal contrast an exposure error of $\pm 30\%$, relative to an ideally correct exposure is tolerable.

In the contemporary version of this instrument, a cadmium selenide photocell is employed, as R_{24} in Fig. 1, housed in a simple tubular holder, which permits a field of view of about 30° , mounted on a bracket on the enlarger column below the enlarger lens. It should be remembered in this context, though, that although it is desirable for the photocell to 'see' the whole of the required exposure area, in order properly to average the subject matter, this metering function also requires the photocell to sit at a constant distance from the printing area.

So, while it is convenient, in practice, for the photocell to move up or down with the enlarger head, if one is making different sizes of prints, in this case it is necessary to recalibrate for each working size. If, on the other hand, it is merely desired to make a similar sized print with the head in another position, thereby giving differing effective enlargements, it is desirable that the photocell should remain in the same position relative to the sensitive paper, when the instrument calibration will remain constant.

To avoid difficulties due to ambient light during the exposure of the paper, the switching circuit in the timer is arranged to switch off the darkroom safelight during the time that the enlarger light is switched on, though if the enlarger is situated in a position where the safelight does not shine very strongly on the enlarger easel, this provision may be omitted.

The effectiveness of the system may be judged from the observation that a series of

prints, with the enlarger head in a constant position, and with the enlarger lens head in a constant position, and with the enlarger lens aperture adjusted between $f/2.8 - f/16$, (an exposure range of 64:1), could be made which were identical in density and contrast, merely by allowing the timer to adjust the exposure duration in response to the light reflected to the photocell.

Since there are occasions when a manual timing facility would be

Circuit design

The basic circuit is shown, in very simplified form in Fig. 2. In this, a capacitor (C_1) is charged through either a variable resistor (R_1) to give a manually set time exposure, or through a photocell to give an automatically determined one. The positive-going voltage change, through IC_{1a} and IC_{1b} is used to trigger a resettable thyristor and actuate the switching relay $RLA1$, which is normally energised in the 'lamp off' condition. A switch in series with the relay allows the enlarger lamp to be switched on for the purposes of inspection of the negative or for focussing.

Because the possible range of illumination levels of the photocell is low, since it is only actuated by light scattered back from the surface of the sensitive paper, and this itself may be relatively dimly lit, it is necessary to use a very sensitive cell. Cadmium selenide photoconductive cells, such as those manufactured by Silonex (formerly 'NSL'), offer an adequate low-level light sensitivity, coupled with an adequate speed of response at these levels to permit a timely cut off of enlarger illumination.

Unfortunately, the penalty paid is that the total current flow through the photo-conductive cell is relatively low, even at moderately high voltages applied to the cell, so the timing circuit must operate at a fairly high impedance. This requirement is easily satisfied by the use of fet input op-amps and polycarbonate timing capacitors.

The desired linearity of the RC charging circuit is attained, even with a simple variable resistor, such as R_1 in Fig. 2, by using $IC_{1(a)}$ as an active integrator. In this configuration, although the potential across the capacitor continues to increase, as it charges, the actual potential drop across the photocell or R_1 remains constant, leading to a linear charging

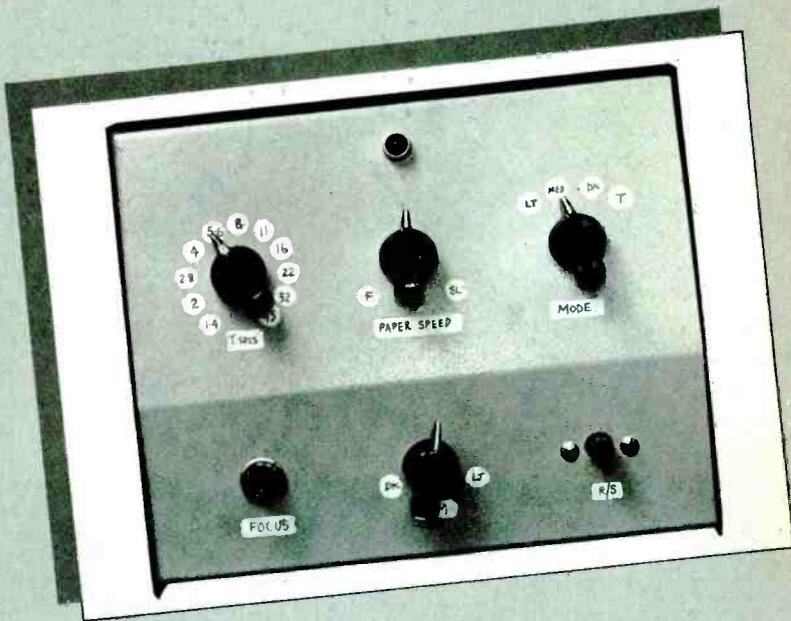


Fig. 4. Author's prototype unit, which can be mounted on a wall. Leads connect to sockets below panel.

rate.

The 'gain' of the system; in the sense of the magnitude of the voltage required to be developed across C_1 before the thyristor is triggered; is set by the ratio of $R_3:R_2$, a value which is determined by the user, and the system is 'reset' following a timing cycle by switches which discharge C_1 , and return the thyristor to its formerly non-conducting state.

Many photographic timer systems, devised by electronic engineers for the use of photographers, go to considerable lengths to ensure that the precision of the timing cycle is as high as present circuit technology allows. While I would not wish to decry this attempt, it is apparent that accuracy in timing is usually both more costly to achieve, and more elaborate in its method, than that necessary in a less precise system, and if one is thinking of the cost to oneself, in time and money, of such an exercise, the question inevitably arises as to whether it is really worth all the effort.

I make this point as a photographer, since it is very clear to me that changes, of only a few volts, in the supply voltage to the enlarger lamp, or of a few degrees in the temperature of the developer bath, or of the oxidation of the developer solution, or of the quantity of accumulated bromides in the solution as a consequence of its repeated use, from one print to another, or even of the duration of the print development, can all bring about variations in the print density which greatly exceed those likely to arise through inaccuracies in the timing circuit.

With this reservation in mind, I

DARKROOM TIMER

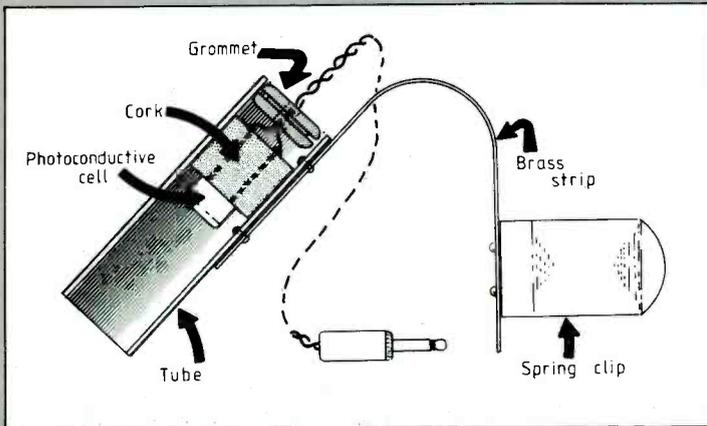


Fig. 5. Tubular holder for photosensitive cell giving a 30 degree viewing angle. Terry clip fixes to enlarger column.

have chosen to employ a circuit which is adequate for the purpose in hand, and with no greater complexity or cost than is demanded by its specification, and I have shown the final circuit employed in Fig. 3.

This follows the circuit layout shown in Fig. 3, but with a few additional adjustments being provided. In order to obtain a reasonable operational stability, I have derived a $\pm 15V$ stabilised power supply from the mains by the use of a pair of 15V i.c. stabilisers, IC₂ and IC₃, while a simple voltage doubler circuit, driving a pair of Zener diodes (D₈, D₉, D₁₄ and D₁₅) generates the higher-voltage, very low-current supply for the photo-conductive cell.

'Subject control' (light, normal or dark) and 'Auto/Manual Timing' is controlled by the input switch S_{2a,b,c}, of which the first positions effect only the automatic (photocell controlled) circuit operation. I have chosen the timing capacitors in these positions to give exposures in the range 1:3.3:10, as offering, in practice, a reasonable approximation to the average print density of a high-key, normal, or low-key presentation.

In the manual timing position of this switch, a chain of resistors, connected across the poles of switch S₄, (R₂-R₁₂), provide a sequence of timing durations in the ratio 1:1.4:2, etc., which offers the practical convenience that each step will allow a comparable, and useful increment in print density, and a two-step movement, up or down, will double or halve the given exposure.

A preset control, R₂₅, allows the timing period to be adjusted

Very low light level linearity in the photoconductive cell response may be assisted if a resistor, in the range 150-300 Megohms, is connected in parallel with the cell. A low level of residual ambient light — from a remote safelight, or from the enlarger lamphouse — may achieve the same result.

to the correct seconds value, with the 'Trim' pot. R₂₆ set in the middle of its travel. In the other limb of switch S_{2c}, R₂₇ gives a 'Paper Speed' control. I will discuss the functions of these controls later, when I describe its method of use.

The diode chain D₁-D₃ prevents the input voltage applied to the input of IC_{1a} from becoming too positive when the timing cycle continues beyond the normal time of completion, and the diode chain D₅-D₇ sets a 2V nominal trip level for the 'resettable thyristor' Tr₁, Tr₂ returned to its non-conducting state by S1_c.

A minor snag which arises when transistors are coupled, in the manner shown, to simulate thyristor action, is that, because of the high current gains and high transition frequencies of the devices which must be used, the transistor pair is very sensitive to inadvertent triggering by short duration, fortuitously arising voltage spikes at either its input or its output connections.

The capacitors C₆, C₉ and C₁₂, which should be non-polar types, are included to avoid this possibility. Resistors R₁₇ and R₁₉ are included to discharge the supply line capacitors following switch off. The photocell R₂₄ normally performs this function for the +57V line and R₂₀ limits the possible current flow through R₂₄ and D₁-D₃ under strong illumination conditions.

As mentioned earlier, the darkroom safelight is switched off during the time that the enlarger lamp is 'on'. This function is accomplished by the relay RLA1.

The whole unit is mounted in a small sloping panel earthed metal box, fixed to the darkroom wall, close to the enlarger, to prevent actuation of the switches causing undesired enlarger vibration, and is shown in Fig. 4.

Method of use

Over the years I have experimented with various photocell housings, and have ended up with the very simple layout shown in Fig. 5. This is held on the enlarger column with a 'Terry' clip — since it is very light, strong fixing is unnecessary — so that it can be positioned as I have sketched in Fig. 1 and receive light from the desired printing area.

Stray light around the edges of the negative, which would give misleading results, is masked off at the negative stage — this is, in

any case, good photographic practice if the worker wishes to preserve the highest degree of brilliance and 'sparkle' in his prints.

Setting up the 'manual timing' chain to give time intervals reasonably close to the specified values should not be too difficult if one chooses a time duration position of, say, 16 or 22 seconds, and then adjusts R₂₅ to give the best fit. The 'Trim' control, which should be positioned in the centre of its travel for this purpose, is then used, in practice, if, for example, a print exposure duration of 8 seconds is thought to give slightly too light a result, and 11 seconds is thought to be over-generous in exposure.

The use of the 'Automatic' function, may, however, call for a little more experimentation, since the light falling on the photocell is very dependent on the geometrical layout of the enlarger easel and photocell mounting. Ideally, a 'normal' type of print, which will, again depend on the photographers typical subject preference, should be rendered to its best advantage with S₂ in the position which gives C₃ as the timing capacitor, and with the 'Paper Speed' control in the middle of its travel for a normal paper/developer combination. This will then allow some scope for compensation for print variables in normal use.

If it is found that C₂ or C₄ give better 'normal print' results, with the photocell assembly employed, the values of C₂, C₃ and C₄ can be modified in the light of these experimental results. It should be remembered that papers do vary quite a bit in effective speed, from one to another, with modern 'resin-coated' bromide papers being the fastest, fibre-based chlorobromides being the slowest, and with variable contrast papers (relying on light filtration for change in contrast) lying somewhere between these extremes.

It is also useful to remember that papers will have a higher effective speed in a 'PQ' than in an 'MQ' developer, and with a warm developer, as compared with a colder one, and with developer which is fresh, as the beginning of the print session, as compared with the rather more tired solution of an hour or two later, so too hasty a judgment of component value modifications for C₂-C₄ or R₂₇ should not be made.

If it wasn't Philips you might think it was a trick

With a price-tag of just £286*, Philips new high-performance dual-trace PM 3206 oscilloscope won't make your money do a disappearing act.

But its remarkable specification might make you think it had been pulled from a magician's hat.

In fact, the only trick Philips has up its sleeve is the ability to conjure up modern design and production techniques to keep costs down without compromising quality.

The formula of features for the 15 MHz PM 3206 includes:

- Easy-to-use, reliable triggering, even on complex waveforms
- Wide sensitivity range 5mV-20V
- Bright CRT with excellent display
- Robust construction, tested to withstand the harshest environments

Circle the magic number today and we'll send you further details.



Authorized distributors:
Electronic Brokers (01-267 7070)
Philips Service (01-686 0505)

Philips Test and Measuring
Pye Unicam Ltd
York Street Cambridge CB1 2PX
Tel (0223) 358866 Telex 817331

The new PM 3206 - it's magic!

OS14

* Price excludes VAT and is correct at time of going to press.




Test & Measuring Instruments

PHILIPS

CIRCLE 26 FOR FURTHER DETAILS.

XIX^{IN} VME BACKPLANES SET THE STANDARD

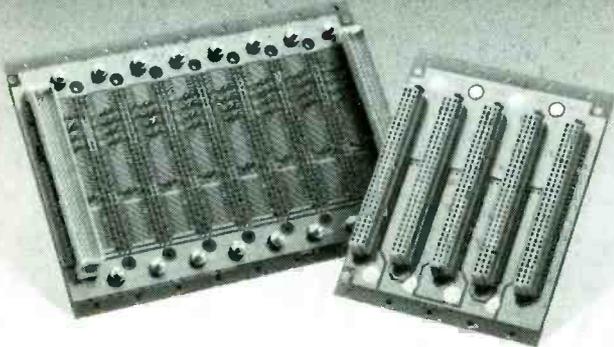

XIX^{IN} VME Backplanes from Sarel are available to meet two functions. The XJI Backpanel is the main VME Bus, the XJ2 is the I/O Expansion Bus.

- The 6 layer XJI VME Bus is designed and manufactured to conform with the highest VME and IEEE Specifications.
- Plug-in method of termination allows designers freedom to integrate VME with the P896 and P1000 IEEE standards.
- Full width use of 19" sub-rack means no loss of card positions, allowing a full 21 slots and the system can be made to conform to standard European architecture.
- The XJ2 3 layer I/O Expansion Bus has been designed to allow a controlled characteristic impedance of approximately 100 ohms unterminated.
- Both backplanes available in standard slot capacities, 4, 5, 7, 9 and 21.

Please send me details of how XIX^{IN} VME Backplanes set the standard.

Name _____

Company _____

Position _____

Address _____

Telephone _____



Sarel Limited

Cosgrove Way, Luton, Beds.
Telephone: Luton 20121

The infinite choice!

CIRCLE 12 FOR FURTHER DETAILS.



Here is the complete range of ICOM marine radio-telephone equipment, from left to right: the M700 HF SSB transceiver offers long-range capability at a sensible price. The M5 VHF hand-portable, quick channel access with its push-button keyboard. M12 and M2 VHF hand-portables, 12 and 56 channels respectively using knobs or thumb-wheels. Finally the M80 VHF radio-telephone, a wide range of options are available for this and all other ICOM marine radios.

ICOM radios are versatile, rugged, water-resistant and most important of all – reliable.


More detailed information is readily available from your local ICOM dealer or direct from Thanet Electronics Ltd.

Thanet Electronics Ltd

Suppliers of Radio Communication Equipment to the Ministry of Defence.
143 Reculver Road, Herne Bay, Kent, England. Tel: (0227) 363859/363850

CIRCLE 48 FOR FURTHER DETAILS.

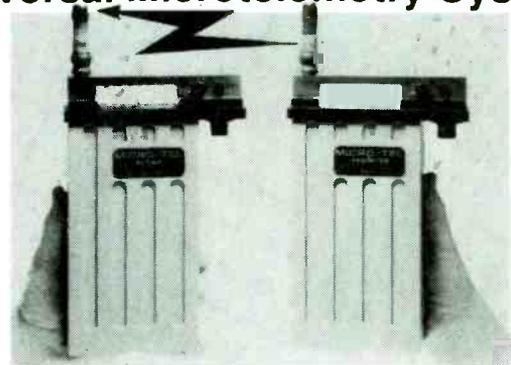MICRO-TEL Universal Microtelemetry System



Micro-tel is a system of integrated UHF radio/modems ruggedly constructed and suitable for a wide range of 'line of sight' data communications applications.

Features:

- UHF Home Office type approved radio (MPT 1309)
- 5 Radio Channels
- 1200 BAUD Modem/Demodem
- 12 Volts/250 m Amps Power
- RS232 Data Input/Output
- Small size 145 x 210 x 60 mm

Micro-tel offers a simple and reliable solution for:

- Building to building computer comms
- Instrument to computer data links
- Industrial systems data links


Dealer and OEM enquiries welcome.

MIDL

MEASUREMENT DEVICES LIMITED

Silverburn Crescent, Bridge of Don Industrial Estate, Aberdeen,
AB2 8EW Telephone: (0224) 824141 Telex: 739506 (MDLAB)

CIRCLE 15 FOR FURTHER DETAILS.

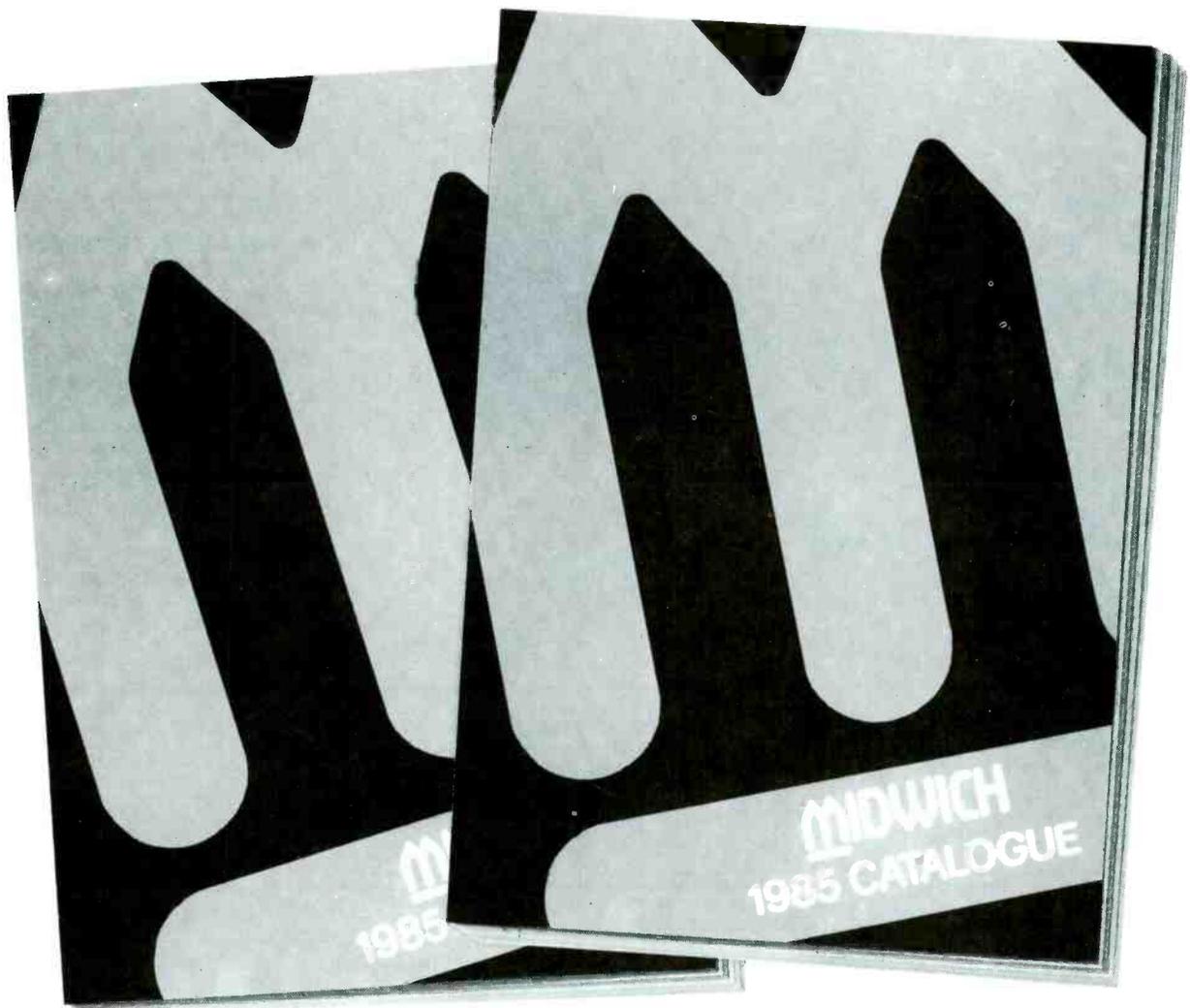

IT WON'T COST YOU A PENNY.

**BEING WITHOUT ONE COULD
COST YOU DEARLY.**

The 1985 Midwich catalogue is now available, absolutely free.

It's the most comprehensive catalogue yet, containing many of the latest and very best computer components on the market, at highly competitive Midwich prices and a service that is second to none.

Which means it will provide your organisation with a vital source of information including numerous

technical specifications and pin-out diagrams.

Fill in the coupon and send for your copy today.

You'll soon discover why no organisation can afford to be without one.

Reply to Dept EWW6 Midwich Computer Company Limited
Gilray Road, Diss, Norfolk IP22 3EU

Name

Organisation/Company

Position

Address

Postcode

Tel. No.

MIDWICH
COMPUTER COMPANY LIMITED

CIRCLE 28 FOR FURTHER DETAILS.

RADIOCODE CLOCKS LTD

SPECIALISTS IN ATOMIC TIME, FREQUENCY AND SYNCHRONISATION EQUIPMENT



NEW PRODUCTS

- **MINIATURE RUBIDIUM OSCILLATOR MODULE**
Lower power, fast warm up, optional output frequencies, programmable frequency offsets.
- **RUBIDIUM FREQUENCY STANDARD**
High performance, compact and rugged instrument. 2U rack or 1/4 ATR case options.
- **INTELLIGENT OFF-AIR FREQUENCY STANDARDS**
Microcomputer controlled instruments, directly traceable to N.P.L., precision ovened local oscillator, comprehensive monitoring and status information, real time synchronisation.
- **LOW COST MSF FREQUENCY STANDARD**
Instant operation, directly traceable to N.P.L., self-contained portable unit, no scheduled frequency changes, 24 hr transmission, real time synchronisation

- Off-air frequency standards
- Intelligent time systems
- Caesium/Rubidium based clocks & oscillators
- Master/slave systems

- Time code generators/readers
- Record/replay systems
- Intelligent display systems
- Precision ovened oscillators
- Time/frequency distribution systems

Radiocode Clocks Ltd*

Unit 19, Parkengue, Kernick Road Industrial Estate, Penryn, Falmouth, Cornwall. Tel: Falmouth (0326) 76007


(*A Circuit Services Associate Co.)

CIRCLE 33 FOR FURTHER DETAILS.

Parthia
Beckhampton,
Nr. Marlborough,
Wilts.

Tel. Avebury (067 23) 219

MARTIN ASSOCIATES sales

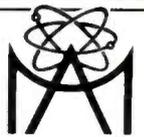

ANALYSERS			
Airmec	248A	Wave Analyser 5-300MHz	£50.00
Airmec	853	Wave Analyser 30kHz-30MHz	£70.00
Solartron	1250	Frequency response Analyser 10uHz-65kHz i/p 1uV-300V RS232C/IEEE 1yr Old	£4950.00
BRIDGES			
Marconi	TF868B	Universal LCR Bridge 1%	£150.00
Marconi	TF 2700	Universal LCR Bridge 1% Battery powered.	£225.00
GENERATORS			
Philips	PM 5770	Pulse Generator 1Hz-100MHz o/p 10V into 50 ohms	£200.00
Tektronix	148	Television Insertion Test Generator	£3500.00
OSCILLOSCOPES			
Coscor	CDU 150	Dual Trace DC-30MHz 10mV/div	£150.00
Solartron	A 100	Dual Trace DC-100MHz 10mV/div	£250.00

USED ELECTRONIC EQUIPMENT

METERS			
H-P	3406A	R.F. Voltmeter 10kHz-1.2GHz Sample Holding	£995.00
Keithley	135	4 digit handheld DMM Almost New	£145.00
Marconi	TF 2604	Electronic Voltmeter 20Hz-1.5GHz	£160.00
MISCELLANEOUS			
Disa	55D05	Digital Constant Temperature Anemometer for fluid measurement etc.	£120.00
Coulter	550/551	Digital Air Contamination Monitor & Probe for determining dirt particles in environment	£250.00
Laminar	Laminarflo	Clean Air Workbench to keep work area dust free.	£200.00


MICROPROCESSOR & COMPUTING			
Elan	E2	EPROM Programmer 1 copy socket 1 yr Old	£625.00
Elan	E9	EPROM Programmer & Editing 8 Sockets 1 yr Old	£995.00
DEC	RK05-AB	Digital Disk Cleaner for Disk Cartridges	£125.00
DEC	Pr/s 01	Tape Reader	£125.00
Fluke	9010A/001	Microprocessor Trouble Shooter c/w 8065 & Z80 Pods New RS232	£4895.00
Dranetz	626	Universal Mains Disturbance Analyser c/w P 6001-01 & PA6003 Plug Ins 8 months Old	£6200.00
Racal Dana	488	GIPB Analyser RS232 6 months Old	£525.00
Shaffner	NSG 200 E	Line Interference Simulator c/w 223A High energy Module 6 months Old	£2200.00
H-P	7470A/002	Two Pen Graphic Recorder IEEE 1 Months Use	£495.00

THE ABOVE IS A SAMPLE OF OUR STOCK SEND S.A.E. FOR CURRENT LIST ALL ITEMS SUBJECT TO AVAILABILITY, CARRIAGE & V.A.T.

CIRCLE 18 FOR FURTHER DETAILS.

MICRO ENGRAVER

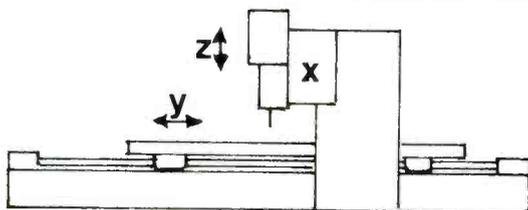MICROPROCESSOR-CONTROLLED ENGRAVING MACHINE



STEPPING MOTOR XYZ MACHINE. Complete with microprocessor controller and software programmed to engrave alphabet and numbers. Also features easy operator programmable XYZ sequence to engrave, drill or cut out special shapes and logos. XY axis travel 400/400mm. Z 50mm with 90watt spindle drive motor. Qwerty touch-keyboard, liquid crystal display. Machine supplied complete and ready to manufacture labels. PRICE £3,500 (VAT extra)

J.A.F. GRAPHICS
70 Leek Road, Congleton, Cheshire CW12 3HU - 0260 275127

CIRCLE 10 FOR FURTHER DETAILS



MITSUBISHI

MGF-1402
MGF-1403
MGF-1412
MGF-1801

GaAs FETs


FROM STOCK

Aspen Electronics Limited

UK representative for Mitsubishi Electric

2/3 Kildare Close, Eastcote, Ruislip
Middlesex HA4 9UR


Tel: 01-868 1188 Tlx: 8812727

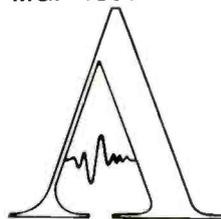

CIRCLE 6 FOR FURTHER DETAILS.

ELECTRONICS & WIRELESS WORLD MAY 1985

One-in-n-way latch

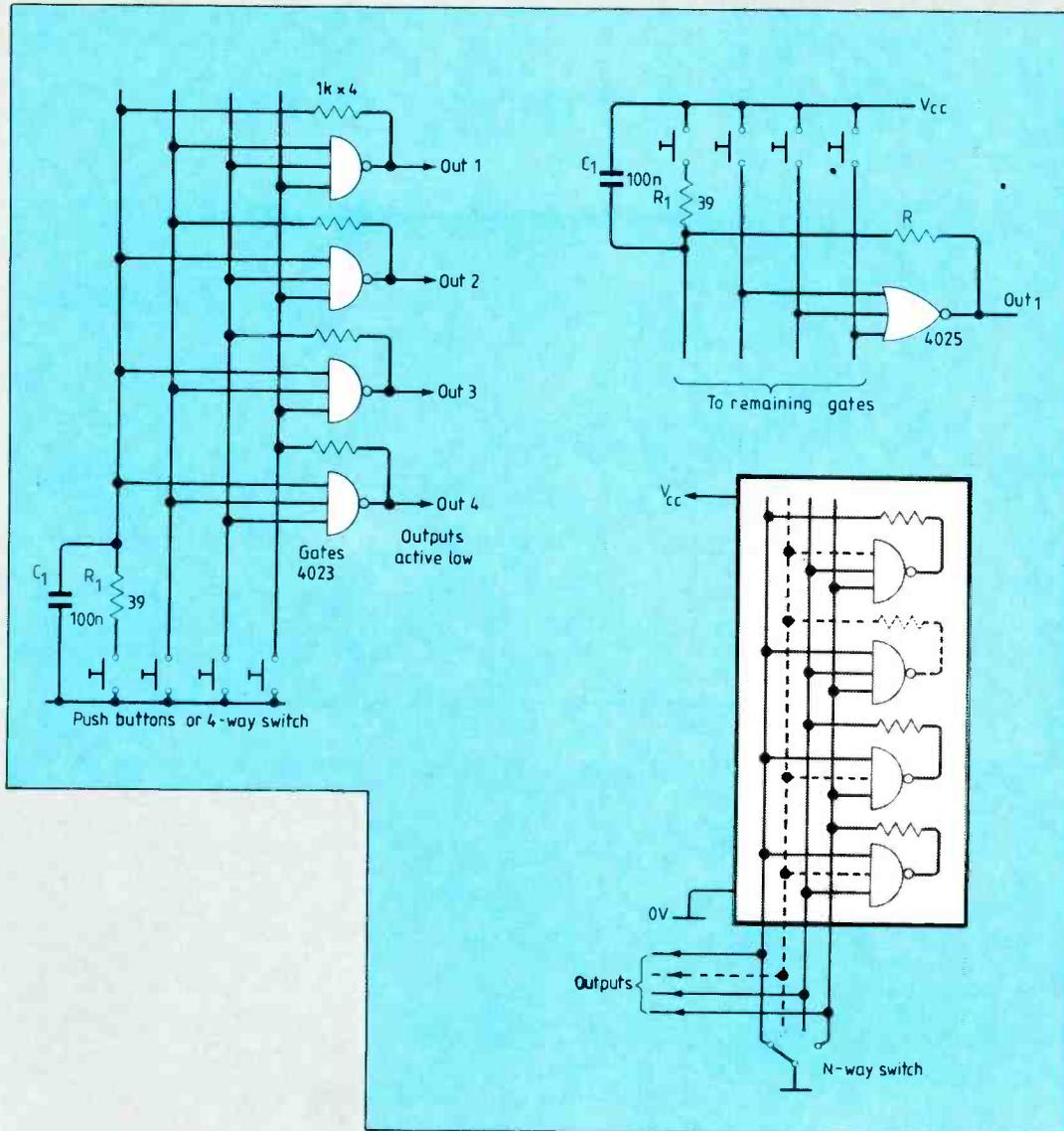

Contact debounce, a predetermined power-up setting and simplicity are features of this one-in-n-way push-button latch. When any button is pressed, its corresponding button line is taken low, forcing all others high. Only one line can be low at a time.

Resistors are included to prevent shorting of the gate outputs and an optional RC element makes sure that the first line is selected at power up. Further gates and button lines may be added following the same principle, i.e., each gate must have inputs connected to every button line except its own.

A Nor-gate version with active-high output is shown in the second diagram. The circuit seems suitable for monolithic implementation since the inputs and outputs can share the same pin if necessary as shown in the third diagram. Using this method, a 14-pin dil package could provide latching and debounce for a 12-way switch. Power-up setting would be achieved as in the first diagram using an external RC element.

Louis D. Thomas
Comdial Comms Systems
Pentwyn
Cardiff


Resistance-indicating continuity tester

Continuity testers giving simple on/off indications have always been useful for circuit checking. There are many occasions though when a continuity indicator will give a short-circuit indication despite a significant

resistance between its terminals. This instrument gives an audible indication of residual resistance of the nominal short circuit and its open-circuit probe voltage is only 10mV.

Two TL062 i.c.s form a simple oscillator whose input frequency is determined by the small input voltage fed to it by the 3140 through 100kΩ resistor.

Input to the 3140

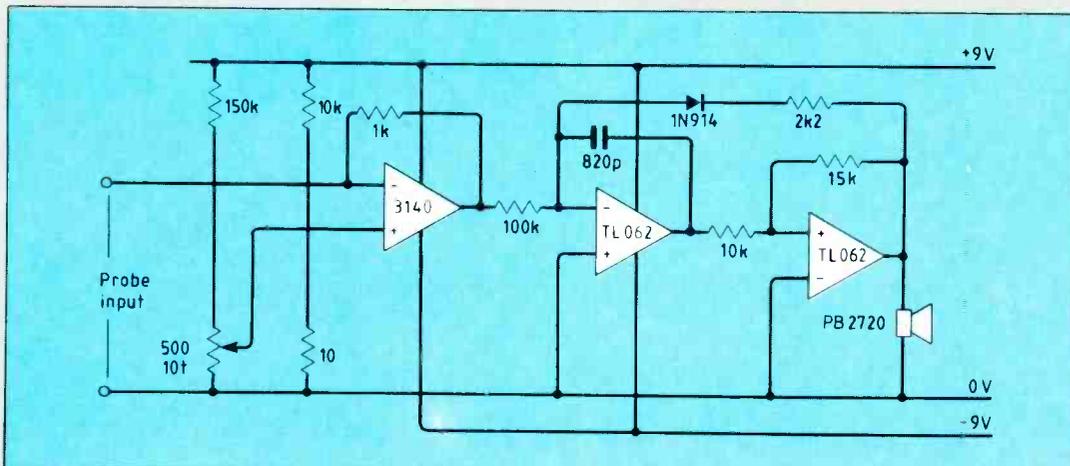

comes through a resistive bridge.

When the probes are open circuit, the bridge is in balance (set by a 500Ω, ten-turn potentiometer) and no output occurs. When the probes are shorted, the bridge becomes totally unbalanced and there is a high-pitched sound from the piezoelectric buzzer. Any small resistance between the probes moves the bridge toward its balanced condition and reduces the pitch of the note.


Residual resistance ranges other than 10Ω are produced by changing the 10Ω resistor. We found that using two resistors of 1 and 10Ω and selecting them by a switch is most useful.

T. Lavin and R.T. Irish
Royal Military College of Science
Swindon
Wiltshire

Shaft encoder interface

This is an interface between an optical incremental shaft encoder and a counter, designed as a finite-state machine. Although finite-state machines have been used for a number of years to implement sequential logic functions, the cost and complexity of designs using standard logic gates and bistable i.cs has restricted their range of applications. However, availability of read-only memory (rom) at reasonable cost makes the state machine an attractive solution to sequential logic design.

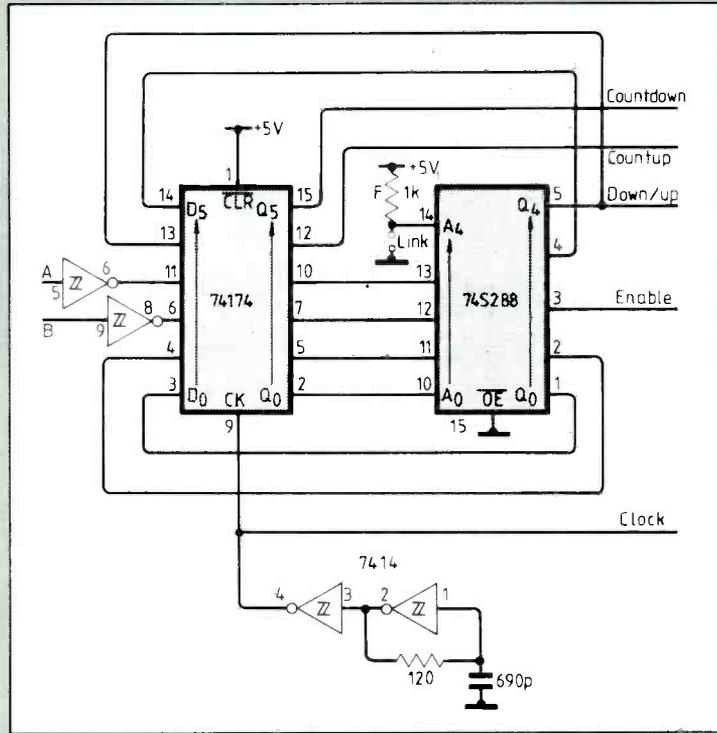This interface drives 74190/191-type synchronous counters and asynchronous 74192/193 types. It uses a 74S288 32-byte prom programmed with the data shown later. Five outputs are provided: COUNTUP and COUNTDOWN, which may be used with 192/193 counters, and ENABLE and UP/DOWN for use with 190/191 counters. Outputs for asynchronous



counters are taken through latches since the rom outputs are strictly speaking only valid on the clock edge.

For 190/191 counters, the clock input must be connected

to the system clock. The two outputs from the shaft encoder (must be t.t.l. compatible) are connected to the A and B inputs of the interface. A further input, F, allows the circuit to

Data for shaft encoder prom.

Address	Data
00-07	1C 10 1C 1C 09 1D 1D 1D
08-0F	1F 1F 1F 1F 1E 1E 1E 1E
10-17	1C 10 1C 08 09 1D 11 1D
18-20	13 1F 0B 1F 1E 0A 1E 12

respond to either a single edge of one input (F low) or to both edges of both inputs (F high), giving approximately four times greater resolution.

In certain applications, it may be important to have each count representing exactly the same amount of shaft rotation and this will not be achieved if counting is performed on every edge since the output edges will not be evenly spaced. The system clock runs at roughly 5MHz, which allows the interface to operate correctly with a 1000-line shaft encoder rotating at up to 150 000rev/min. The design is easily modified for use with eproms, but the speed advantage is then lost.

M.H.S. Winder
Dept of Engineering
University of Reading

Divide-by-clock circuit

Besides being relatively simple, this circuit has the advantage that it does not require changing of passive components when the division ratio is altered.

In the phase-locked loop circuit, a clock-controlled voltage-to-frequency converter, VFC100, is used instead of the internal voltage-controlled oscillator. Due to this converter, input frequency in the lock state is

$$f_{in} = V_d f_{cl} / 20V_{cc}$$

where f_{cl} is the applied clock frequency. The internal v.c.o. is connected to the output of the system so that the output frequency, f_{out} , yields



$$f_{out} = V_d / R_1 C_1 V_{cc}$$

Eliminating the ratio V_d / V_{cc} from both expressions gives

$$f_{out} = 20f_{in} / R_1 C_1 f_{cl} = \text{const} \times f_{in} / f_{cl}$$

Output frequency may be set to a required value by the choice of clock frequency only.

Kamil Kraus
Rokycany
Czechoslovakia

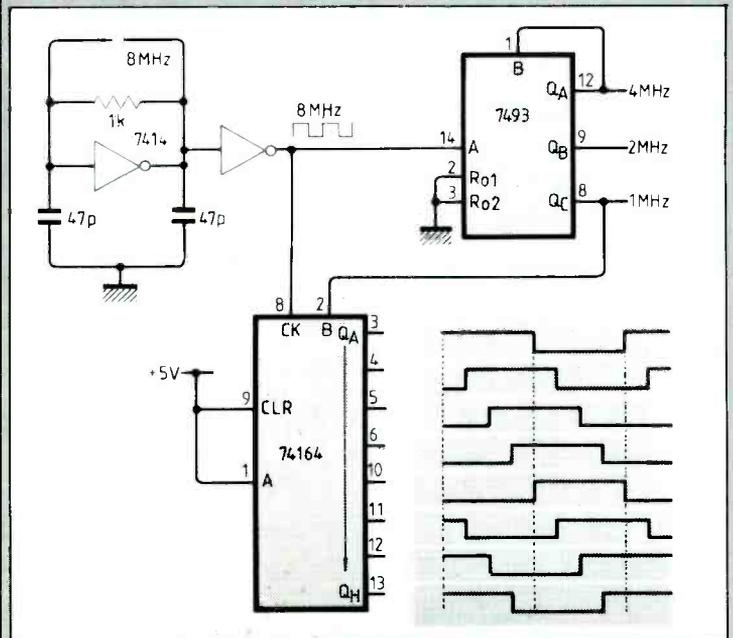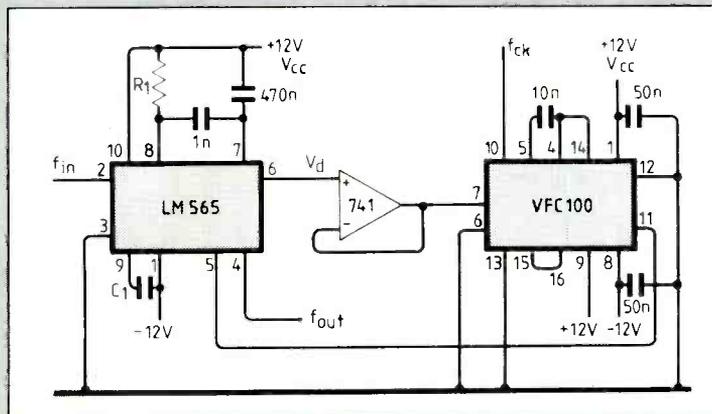

Eight-phase clock

Eight 1MHz square waves, each separated by $\pi/4$ radians in phase, are useful for running eight processors in parallel.

The 7493 is a negative-edge triggered counter arranged to divide by eight. The 74164 shift register, being positive-edge

triggered, shifts the 1MHz output half way between changes of the counter to avoid uncertainties in the output condition on each negative transition of the 8MHz clock. Square waves of up to 32MHz could be produced by a different clock circuit.

G.A. Hardy
Nottingham

Running 68xx peripherals with Z80


While expanding my Z80 computer system I had to interface a disc drive using an MC6843 controller since I could not find a device directly compatible with the Z80 at the time. The resulting circuit could

be useful for connecting other 68-series peripherals to the Z80.

The only thing that prevents direct connection between the Z80 and 6843 is the latter device's enable input. This signal is essential for correct operation, especially its negative edge which latches data into the chip. When the Z80 fetches a memory or i/o instruction, both D-type

bistable i.c.s are set by the Z80 clock positive edge. The next clock positive edge resets the first bistable circuit and enables reset of the second on the clock negative edge. Output of the second bistable i.c. is the required enable signal.

M. Darko
Zagreb
Yugoslavia

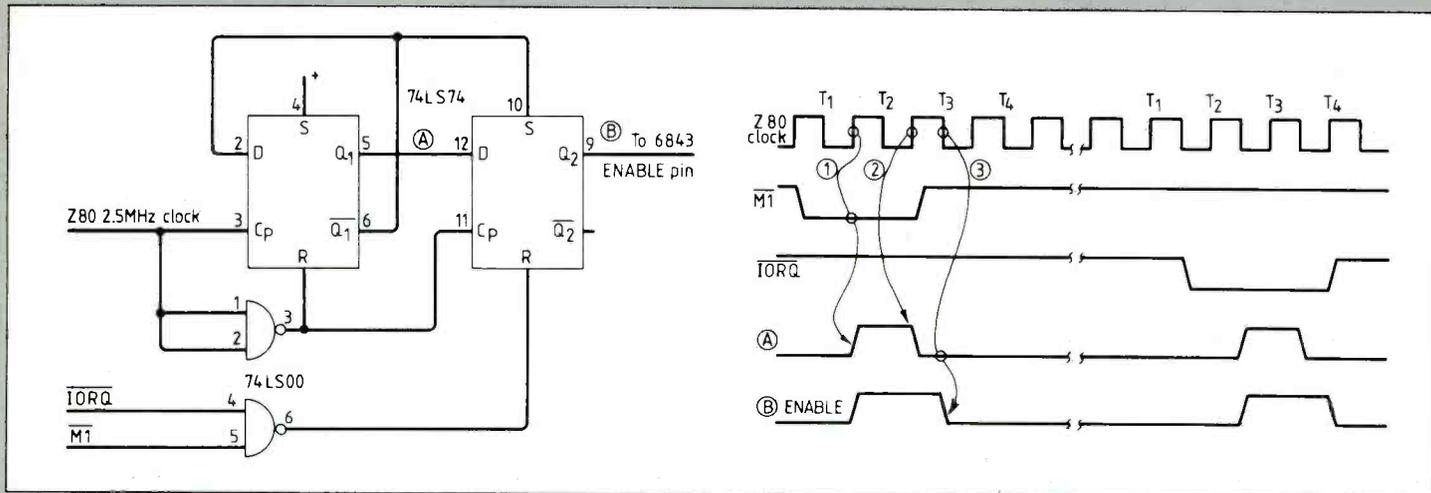

Marker processor for sweep measurements

I have been using this circuit in a network analyser for up to 100MHz. It produces clear rectangular marks, which can be summed to the detector or log amplifier output and fed to the Y channel of the display device.

One half of IC₂ is taking samples at the mark rate from the incoming t.t.l.-level sweep signal. Looked at in the frequency domain only the lower sideband of the mixing frequency and the nearest marking oscillator harmonic exist at the 74S74 output. Unlike with conventional mixers, the reference input does not have to be an impulse train. A t.t.l. input signal will suffice because the 74S74 is an edge-triggered bistable D-type device.

Retriggerable monostable circuit IC₃ (a 74LS122 may be used) serves as a digital low-pass filter, delivering output pulses only while its pulse width remains shorter than the cycle time of the incoming beat.


Circuit IC_{1a} is a peak detector, IC_{1b} is a unity-gain buffer and the circuit around IC_{1c} translates the detected amplitude into current.

An essential feature of a good mark system is that the mark width on the screen does not depend on the frequency band

swept. This is accomplished by making current to the LS123 pulse width determining circuit a linear function of the amplitude of the sawtooth voltage deviating the v.c.o. Hence the low-pass cut-off frequency is made a linear function of sweep bandwidth.

The mark width regulating circuit has proved effective with sweep bandwidths ranging from 100 to 1MHz. Faster logic i.c.s should allow use of higher frequencies.

Jouni Verronen
Oulu
Finland

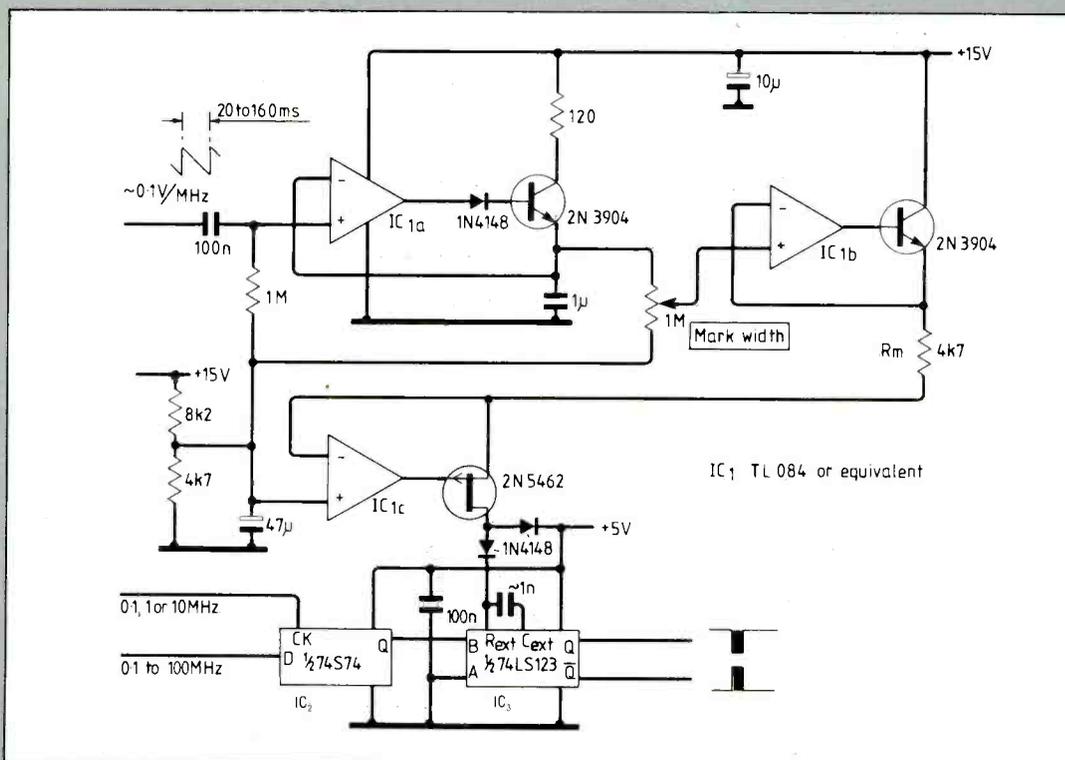

DATA MAN ORIGINALS...

GANG-OF-EIGHT is our FAST EPROM PROGRAMMER which handles CMOS or NMOS EPROMS from 2716 to 27256 (25XX too) using FAST or NORMAL programming methods. FAST programming 27128's takes 2 minutes, NORMAL programming takes 14. All possible levels of Vpp are covered including 25, 21 and 12.5 volts. G8 has an LCD which tells you what you're doing — or doing wrong. BLANK CHECK, VERIFY and CHECKSUM facilities are included. Good value. **£395**
GANG-OF-EIGHT-PLUS is now available. PLUS what? Well, PLUS an RS232 INTERFACE which lets you download in INTELHEX, MOTOROLA S, TEKHEX, ASCII, SIMPLE HEX etc. Oh, yes, PLUS 50 quid too, but you might think it's worth it **£445**



EMULATOR/ EDITORS



SOFTY 2, our intelligent EPROM PROGRAMMER/EMULATOR, plugs into a TV, shows you memory and lets you TEXT-EDIT in HEX (INSERT, DELETE, SHIFT BLOCKS without overwriting or rewriting etc). It also calculates ADDRESS-OFFSETS in hex, UPLOADS and DOWNLOADS in SERIAL and PARALLEL, saves programs on TAPE, and PROGRAMS, COPIES and EMULATES EPROMS 2716, 2732 and 2532. Great DEVELOPMENT TOOL for PIGGY-BACK SINGLE-CHIPPERS and other small microsystems. TV lead, ROMULATOR-cable with 24 pin DIL Plug and power supply included, ready to plug-in and use **£195**
2764 and 27128 ADAPTOR lets SOFTY 2 handle larger EPROMS for **£25.00**

Z80 DEVELOPMENT TOOLS

MENTA is a Z80 development system designed by DATAMAN for the SCHOOLS COUNCIL. MENTA has a built in ASSEMBLER and TV hex display: it lets you enter program in hex or mnemonics and execute them FULL SPEED or A STEP AT A TIME. All the REGISTERS and the STACK are displayed on-screen and you can SEE MEMORY CONTENTS CHANGING as instructions are executed. MENTA is a microsystem with 24 bits I/O — it can be used as a controller for ROBOTS and intelligent machines. MENTA appears in GCE syllabusses; a TEACHER'S GUIDE, PUPIL READER and WORKSHEETS are available — also CONTRCL MODULES — UNIVERSAL I/O, A to D, D to A, MOTOR and VARIABLE SWITCHED INPUT for less than £20 each. A MENTA with TV flylead and power-supply costs **£99**

MICRODOCTOR is for DIAGNOSIS, finding troubles in microsystems. You just plug into the micro-processor socket, READ and WRITE to the MEMORY and I/O. MD does CHECKSUMS, RAMTESTS on memory, checks for SHORTS on the bus, and prints memory in HEX or ASCII. You can also DISASSEMBLE and print the SOURCECODE in Z80, 6502, 6800 or 8085 mnemonics. When your SCOPE or MULTIMETER can't find the problem — consult the MD. When you order say which processor or ask about multiprocessor MD **£295**



CONNECTIVITY TESTERS



I.C.T. (Intelligent Connectivity Tester) is the project name for a 40 pin dual-in-line CUSTOM-CHIP developed by DATAMAN. The chip is called the MT72017 and it will appear soon in BARE-BOARD TESTERS, IDC CABLE TESTERS and LOOM ASSEMBLY EQUIPMENT all over the world. An EVALUATION-SYSTEM/CONTROLLER for the MT72017 is available on a EUROCARD and you can BUILD YOUR OWN custom connection-pattern tester for **£295**
 The controller has full documentation, source-code, circuit diagram, parts-list and a description of operation. Each MT72017 tests 26 points and a single controller will handle hundreds of 'em — thousands of test-points.
 MT72017 chip prices: **£12.50** (1 to 99) **£11.25** (100-999) **£10.25** (1000 up). We do not sell samples of the MT72017 without a controller.

LOGIC ANALYSER TA2080 by THANDAR with SPECIAL MODS by DATAMAN which gives RS232 interface and prints TIMING and STATE diagrams — and DISASSEMBLES Z80, 6502, 6800 code on the screen or printer. THANDAR TA2080 **£1950** DATAMAN RETROFIT **£295**

LOGIC ANALYSERS

CP/M COMPUTERS

OLIVETTI INTERFACES

EPSON AND NEC COMPUTERS QX10, HX20 and PX8, PC8800. ALL COMPUTERS are sold with a free bundle of useful software written by DATAMAN.


OLIVETTI TYPEWRITER INTERFACES designed by DATAMAN for ET121 and 221 — cheaper than a DAISYWHEEL printer RS232, HPIB (IEEE) and PARALLEL including fitting. **£195**

EPROM ERASERS from. **£39.00**

If you need more data send for a FREE LIT-PACK and an ORDER FORM or, better still, JUST BUY THE PRODUCT AND EXAMINE IT — you may return any item within 14 days for A FULL REFUND (we deduct only postal charges). Add £2.50 for carriage to orders below £100. ADD VAT TO ALL UK ORDERS. Terms: cheque with order. Dealers who mean business welcome. Goods normally in stock — TODAY DESPATCH IS POSSIBLE — please phone us **DATAMAN DESIGNS, LOMBARD HOUSE, DORCHESTER, DORSET DT1 1RX. TELEX: 418442. PHONE (0305) 68066.**

CIRCLE 30 FOR FURTHER DETAILS.

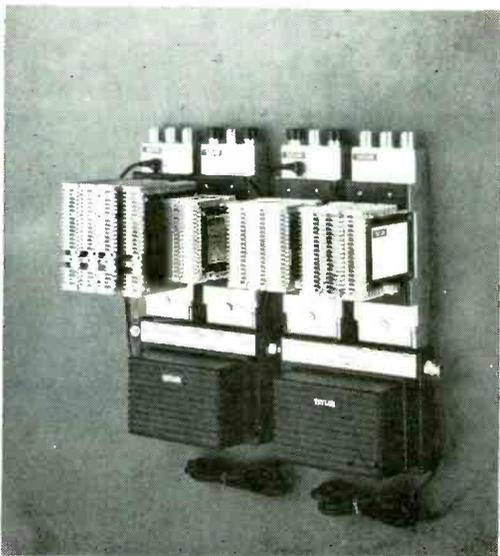CABLE T.V. HEAD END AND REPEATER AMPLIFIERS



CHANNEL CONVERTERS

TCUU UHF-UHF Single channel converter. Gain adjustable +2dB-16dB. Maximum output +26dBmV. Crystal controlled oscillator. Power requirement 14V 25mA. (Quote Channels required).
TCUV As TCUU except UHF to VHF converter. (Quote Channels required).
TCVU As TCUU except VHF to UHF converter. (Quote Channels required).

SINGLE CHANNEL AUTOMATIC GAIN CONTROL AMPLIFIERS

TAG4863 Gain 48dB, maximum output 63dBmV. Regulator + or - 8dB. Power requirement 14V 210mA.
TAG4063 Gain 40dB, maximum output 64dBmV. Regulator + or - 16dB. Power requirement 14V 210mA.

SINGLE CHANNEL AMPLIFIERS

TSS4663 Gain 28-46dB adjustable. Maximum output 63dBmV. Power requirement 14V 170mA.
TSS3062 Gain 12-30dB adjustable. Maximum output 62dBmV. Power requirement 14V 26mA.

DRIVER AMPLIFIERS

TS1030FM FM driver amplifier. 10dB Gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1030B3 Band III driver amplifier. 10dB gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1030UHF UHF driver amplifier. 10dB gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1040S Single channel UHF driver amplifier. 10dB gain. Maximum output 40dBmV. Power requirement 14V 10mA. (Quote channel required).

DISTRIBUTION AMPLIFIERS

TE2042 Domestic distribution amplifier. 1 input, 1 output. Gain 20dB. Maximum output 42dBmV.
TE1638 Domestic distribution amplifier. 1 input, 2 outputs. Gain 16dB. Maximum output: 2 at 38dBmV.
TS2046 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 46dBmV.
TS2846 40-860MHz. Gain 28dB UHF, 22dB VHF. Maximum output 46dBmV.
TS2845 Separate UHF/UHF inputs. Gain 28dB UHF, 22dB VHF. Maximum output 46dBmV.
TS2054 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 54dBmV.
TS2060 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 60dBmV.
TS5565 Gain 55dB UHF, 55dB VHF, 42dB FM. Maximum output 65dBmV.

REPEATER AMPLIFIERS

TSC3660 Repeater. Gain 16-36dB UHF, 10-30dB VHF. Maximum output 60dBmV.
TSC3665 Repeater. Gain 16-36dB UHF, 10-30dB VHF. Maximum output 65dBmV.
TSC3060 Repeater. Gain 10-30dB VHF. Maximum output 60dBmV.

QUALITY AT LOW COST


TAYLOR BROS (OLDHAM) LTD

LEE STREET, OLDHAM - TEL. 061-652 3221 - TELEX 669911

CIRCLE 34 FOR FURTHER DETAILS.

AFFORDABLE ACCURACY

QUALITY MULTIMETERS FROM ARMON

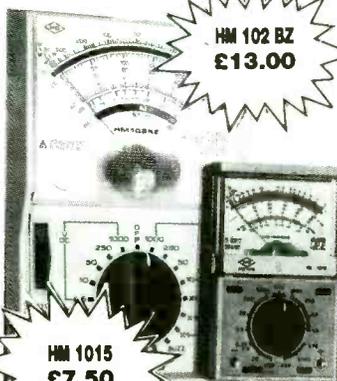

HM 102 BZ
£13.00


ANALOGUE

HM-102BZ
10ADC Range, 20KΩ/VDC. Buzzer, Battery Test Scale..... £13.00
 19 measuring ranges
HM-102R
Low end voltage & current ranges. Jack for Audio o/p Voltages..... £11.00
 20 measuring ranges
HM-1015
Rugged. Pocket sized meter, for general purpose use..... £7.50
 16 measuring ranges
 Battery, Test Leads and Manual included with each model.

HM 1015
£7.50

DIGITAL

HC-6010 0.5% Accuracy Standard Model..... £33.50
HC-5010T 0.125% Accuracy, TR Test Facility..... £39.50
 All models have full functions and ranges and feature:
 3 1/2 digit 0.5" LED display
 Low battery indication
 Auto zero & Auto polarity
 ABS Plastic Casing & Tilt Stand
 DC AC 10amp Range
 Overload Protection on all ranges
 Battery, Spare Fuse, Test Leads and Manual

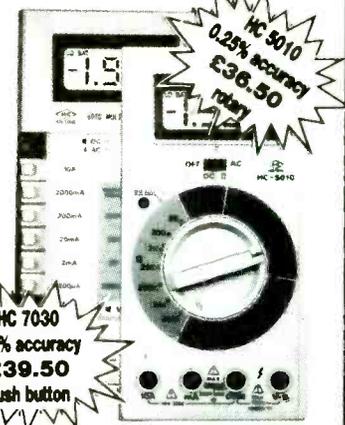

HC 5010
0.25% accuracy
£36.50

HC 7030
0.1% accuracy
£39.50
push button

FULL DETAILS ON APPLICATION FROM:-

ARMON ELECTRONICS LTD

DEPT A HERON HOUSE, 109 WEMBLEY HILL ROAD, WEMBLEY, MIDDLESEX HA9 6AQ
 TELEPHONE 01-902 4321 TELEX 923985


PLEASE ADD 15% to your order for VAT. P&P Free of charge. Payment by cheque with order
 Offer applicable to mainland UK only

Trade enquiries invited

Please allow 28 days for delivery

CIRCLE 40 FOR FURTHER DETAILS.

METER PROBLEMS?

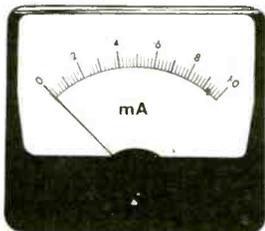

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full information from:

HARRIS ELECTRONICS (London)

138 GRAY'S INN ROAD, W.C.1 Phone: 01-837 7937
 Telex: 892301 HARTRO G

CIRCLE 44 FOR FURTHER DETAILS.

ADVANCED ACTIVE AERIAL



**APRS
STAND
163**

The aerial consists of an outdoor head unit with a control and power unit and offers exceptional intermodulation performance. SOIP +90dBm, TOIP +55dBm. For the first time this permits full use of an active system around the 1f and mf broadcast bands where products found are only radiated from transmitter sites. The system is developed from broadcast monitoring arrangements we have had in continuous use for ten years.

- General purpose professional reception 4kHz - 30MHz
- -10dB gain, field strength in volts/metre to 50 Ohms
- Preselector and attenuators allow full dynamic range to be realised on practical receivers and spectrum analysers
- Noise -150dBm in 1Hz. Clipping 16 volts/metre.

SURREY ELECTRONICS LTD., The Forge, Lucks Green, Cranleigh, Surrey GU6 7BG. Tel 0483 275997



Your product ?

One superb product deserves another.

You know your product is the best you can make but today's electronic products are crammed full of components any one of which could damage your reputation.

In the wound magnetics world, more and more electronics manufacturers are turning to Weyrad because they find the expertise, quality and reliability they need.

They also find the flexibility in manufacture, the pricing they want and the dedication they need to help them make a better product. And they find a company determined to keep its lead in the market.

Weyrad have been in the business of high technology wound mechanics for over 30 years and now with massive resources have a fully equipped factory and an experienced staff of designers and engineers capable of making the



smallest to the largest components; capable of making simple windings or the most complex; capable of designing and manufacturing custom assemblies including voltage generation and power modules.

Weyrad's products are found in TVs and audio equipment with household names. In aircraft, ships and fighting vehicles. In industrial and commercial machinery around the world. In telecommunications equipment and in the automotive industry.

Weyrad were Britain's first wound electronics company to win the coveted standard BSI BS 5750 for its quality control, which gives Weyrad customers unrivalled assurance of manufacturing standards. But then, when you make an outstanding product, it's important to make sure it stays the best, isn't it?

For more details of how Weyrad can help you improve your products contact our Marketing Department.



Weyrad

H I G H · T E C H · W O U N D M A G N E T I C S

Contact the Marketing Dept., Weyrad (Electronics) Ltd., Lynch Lane, Weymouth, Dorset. Telephone: (0305) 783801



CIRCLE 67 FOR FURTHER DETAILS.

TEST INSTRUMENTS

A wide range of high performance instruments that put professional test capability on your bench.

COUNTERS — TF600 5Hz to 600MHz TF200 10Hz to 200MHz TF040 10Hz to 40MHz PFM200A 20Hz to 200MHz (hand-held model) TP600 prescales to 600MHz TP1000 prescales to 1000MHz

MULTIMETERS — TM351 0.1% 3½ digit LCD TM356 0.25% 3½ digit LCD TM355 0.25% 3½ digit LED TM354 0.75% 3½ digit LCD (hand-held model) TM451 0.03% 4½ digit LCD with autoranging and sample hold TM452 0.05% 4½ digit LCD with built-in frequency counter (hand-held model)

OSCILLOSCOPE — SC110A 10MHz, 10mV sensitivity, 40mm CRT with 6mm graticule divisions

THERMOMETERS TH301 -50°C to +750°C, 1° resolution, TH302 -40°C to +1100°C and -40°F to +2000°F, 0.1° and 1° resolution. Both accept any type K thermocouple

GENERATORS — TG101 0.02Hz to 200kHz Function Generator TG102 0.2Hz to 2MHz Function Generator TG105 5Hz to 5MHz Pulse Generator TG501 0.005Hz to 5MHz Function Generator TG502 0.005Hz to 5MHz Sweep Function Generator TG503 0.005Hz to 5MHz Pulse Function Generator

LOGIC ANALYSERS — TA2080 8 channel 20MHz TA2160 16 channel 20MHz

ACCESSORIES — Bench rack test leads carrying cases, mains adaptors probes, thermocouple probes, microprocessor disassembly options

For further information contact

Thandar Electronics Ltd, London Road, St Ives, Huntingdon, Cambs PE17 4JH
Telephone (0480) 64646 Telex 32250

 **thandar**
ELECTRONICS LIMITED
CIRCLE 13 FOR FURTHER DETAILS.



Richardson Electronics (Europe) Ltd.



We are the leading suppliers of R.F. Power Transistors and Electronic Tubes for the communications and industrial markets. With our parent company we represent all the major manufacturers and from our nine million pounds worth of stock we can supply virtually any form of tube or R.F. Transistor of American manufacture or its European equivalent. We can normally dispatch your requirements on a same day service.

Send for further information to

Dean Road, Outer Circle Road Industrial Estate Lincoln, England LN2 4DV
Tel: 0522-42631 Telex: 56175 REEL UK

CIRCLE 17 FOR FURTHER DETAILS.


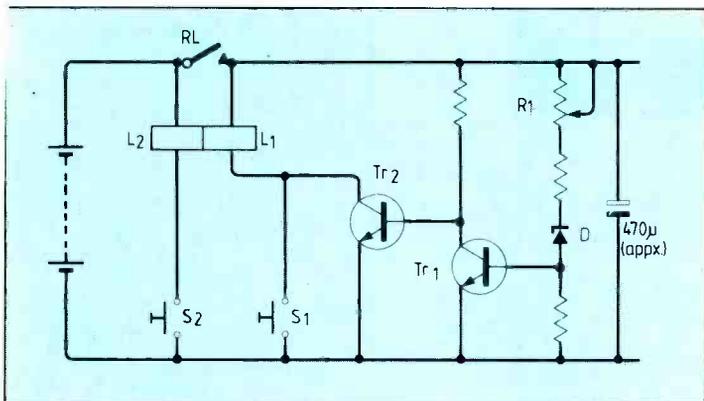


Fig. 2. Low-voltage cut-out circuit is turned on by pressing push-button PB₂. Relay closes, but Tr₁ clamps base of Tr₂ and holds off the coil L₁ of the relay. If voltage falls below that set by pre-set pot R₁ and zener, Tr₁ releases Tr₂, the turn-off coil L₁ opens the relay and the load and circuit are switched off. Alternatively, the load may be turned off by pressing push-button PB₁.

Fig. 3. Reverse-charge damage illustrated in Fig. 1 can be ameliorated but not eliminated completely by adding reverse-biased Schottky diodes to a battery. This type of protection is not needed if cells are discharged singly, using either a dc/dc converter to step the voltage up to a usable level, or low-voltage components which work from 1.25V like those suggested.

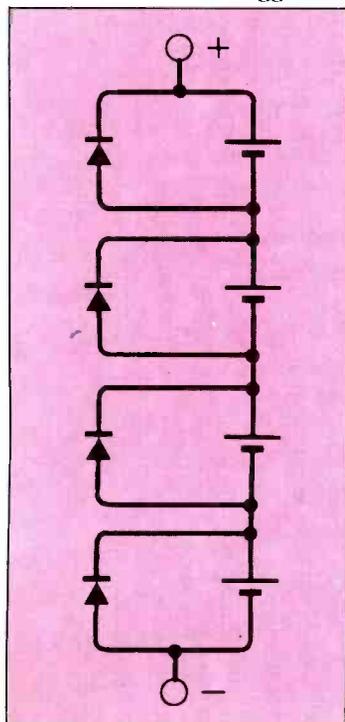

cell the water of reaction is a large part of what little electrolyte is present.

It follows that removal of what to the uninitiated may seem to be very small amounts of water from the cell results in a large reduction in cell capacity. The ways in which water can be removed are discussed in failure modes 1 and 2.


The material separating the plates is usually either nylon or polypropylene, both of which have good resistance to potassium hydroxide solution used as electrolyte, while the outer case is generally nickel-plated steel. These materials are involved in failure mechanisms of their own, as shown in part 2.

Failure mode 1: loss of electrolyte water due to reverse charging

When cells are connected together to form a battery, there is bound to be a cell of lesser capacity than the rest; it is impossible in manufacture to produce cells of exactly equal capacity, even if they are all of one type. In any case even if a good balance was possible, unbalance is likely after a period of operation for reasons which are detailed later.

If such a battery is discharged fully, the cell or cells of slightly less capacity than their neighbours will be discharged first and then driven in reverse until the rest of the battery is also exhausted. This causes permanent damage to sealed cells. The following explanation refers to the discharge graph of Fig. 1.

 Readers will be familiar with the upper part of the curve, the one most often published by makers to show their cell characteristics. It is the lower part of the curve which is of interest here. When current is passed in the wrong direction, oxygen is evolved at the cadmium electrode which oxidizes any remaining cadmium to the discharged state:



This reaction takes place during phase A. At the nickel electrode, hydrogen is evolved as gas, increasing the internal cell pressure. Eventually, the cadmium available for oxidation runs out and phase B is entered, where oxygen is evolved as well as hydrogen. The pressure in the cell rises rapidly and in due course the pressure-release valve will open to vent gases to atmosphere. During phases A and B it is the water of the electrolyte that is consumed. With a conventional vented cell this is of no great importance because of the large excess of water, but in a sealed cell there is no great amount of water and the water of reaction is encroached upon quite early on during the reverse charging process. A permanent reduction in cell capacity results.

Moreover, this process is a vicious circle — it is the cell that has been reverse charged which will be the prime candidate for more reverse charging next time the battery is discharged, because its capacity will have been marginally further reduced in relation to the other cells in the battery. The end result is often a battery of, say, six good cells and one completely dead cell. With encapsulated batteries like the PP3 and PP9 types this is disastrous because the whole battery has to be scrapped, there being no really practicable way of dismantling and reassembling the battery to service the dead cell. In any case, putting a new cell into a partly-used battery is asking for more trouble for the very reasons under discussion.

Avoidance tactics

Clearly it is possible to prevent reverse charging by stopping short of 100% discharge. Unfortunately there are difficulties. Deciding where to halt is one. It is not feasible to monitor the remaining capacity in individual cells, so the usual method is to monitor the total battery and operate a cut-out at, say, 1 volt per cell. Thus a seven-cell battery of nominal 8.75V would be halted at 7V. Such a voltage-sensing unit cannot distinguish between a battery of six healthy cells at 1.25V each and one completely dead cell being reverse charged at -0.4V; and is of limited value. One could raise the threshold of the cut-out to 1.1 or

1.2V but this means discarding a significant part of the battery capacity. But the technique is worth considering if capacity is not all that important to the application.

This problem with voltage-sensing increases with the number of cells in the battery and cut-outs of this kind are most effective with just two to five cells. Neither are cut-outs universally applicable; it is no consolation to know that the battery in your NiCd-powered handlamp is being protected against reverse charge if the cut-out abruptly plunges you into pitch dark, nor if your radio transmitter stops working half-way up a mountainside. These are cases where half a loaf is better than no bread!

Of course, extra features could be built-in, such as a pre-cut-out alarm or a manual override, but human nature being what it is, the last-mentioned would be self-defeating and both would increase the size, complexity and cost of the cut-out, all these things being at a premium in portable battery powered equipment. Some voltage sensors introduce a small voltage drop in the circuit which may be unacceptable. This need not be so if a latching relay is used as the cut-out switch. Such a relay uses no power in the on or off-state and introduces virtually no voltage drop for all practical purposes. I have used the circuit shown in Fig. 2.

Prevention diodes. This method of avoiding damage from reverse-charging consists of a reverse-biased diode connected across each cell in a battery, Fig. 3. If a current attempts to pass in the wrong direction through any given cell it is provided with an alternative path through the diode. Referring to Fig. 1, such diodes would have to exhibit a V_f lower than that of phase A to avoid electrolyte decomposition at the rated current of the load. At a load current of, say, 0.5 amp, V_f would have to lie in the region of 0.3 to 0.4V. This is a tall order for most diodes.

Schottky diodes can present a practical proposition, although they are on the expensive side. A graph of V_f versus current is shown in Fig. 4 for a 1 amp wire-ended Schottky but this is only a typical graph and I have found it necessary to select for low V_f from a batch of devices to get the best results. Care is also required in selecting the type of device because they are primarily

intended for use in s.m.p.s. and low V_f types tend to have high leakage currents, low leakage types tend to have high V_f . Leakage current is obviously important as it must be kept small in relation to the internal self-discharge of the cell. For a standard D-cell this self-discharge current may be of the order of several hundred μA so the $10\mu\text{A}$ of this particular diode at 20°C can be disregarded.

Having experimented with deliberate reverse charging, I found diodes to be most effective at higher currents. For example a C-cell reverse-charged at 0.5 amp can have this current reduced by a factor of between 5 to 10 with a Schottky diode but only by a factor of two at 100mA. So although it is not a perfect method it does help to delay cell destruction.

The difficulty with this technique lies in its practical implementation. Where batteries are made up using cylindrical cells in the strapped-together arrangement, the diodes may be inserted in the gaps between cells. In the type of battery where the cells are connected end-on in a common plastics sleeve it may be necessary to slit the sleeve to make the connection, weakening the assembly in the process. In either case the presence of soldered joints where there is the possibility of electrolyte leakage may be unacceptable for some applications. With encapsulated batteries like the PP3 and PP9 it is well-nigh impossible to incorporate these diodes. However, it is very easy to do so where the battery consists of cells housed in individual holders, so it is worthwhile paying some attention to the battery compartment when considering reverse-charge protection with diodes.

Avoid batteries

By far the best method of avoiding reverse-charge failure is not to use batteries at all! One way of doing this is to use a single cell in conjunction with a d.c./d.c. converter to step the voltage up to a reasonable level where most of the present generation of semiconductor devices operate. Clearly such a system has no reverse-charge failure mechanism, and so does away with voltage cut-outs and protection diodes. Needless to say, the reliability of the NiCd power source is greatly improved.

Taking a closer look at this technique reveals several other important benefits of both technical and economic nature. Firstly, there is only one set of rubber seals to go wrong with a single-cell system, whereas there are many sets of seals on a battery, so the probability of electrolyte leakage — which will be shown later as a failure mode — is very much reduced. Secondly, single cells of equivalent capacity tend to be more physically robust than strings of interconnected small cells. This is important in hand-carried equipment or in vehicle-mounted applications which can be subjected to very rough treatment, like being dropped! Thirdly, by standardizing on one type of cell and using a range of converters giving appropriate working voltages for different pieces of equipment, it is possible to reduce the inventory of battery types. This could be of interest if you have several items of equipment and are faced with stocking a miscellany of batteries. Also, it follows that recharging requirements are much simplified. Lastly, a single-cell system can work out to be cheaper in the long run, stemming from the fact that the cost per watt-hour for a single cell is less than for a battery of equivalent capacity. For example, a PP9 of 10.4Wh costs £12 but a super-F cell of 12.5Wh costs only £9. Allowing for converter losses, these two systems give about the same amount of useful energy, but the single cell costs 25% less. Of course, the initial cost of the converter must be taken into account, but since a well designed device is likely to outlive several NiCd cells the real cost spread over a period of time will be small in comparison.

The lower cost of single cells makes the carrying of a spare cell with portable equipment a more attractive proposition than for batteries — £24 in the above for a PP9 and spare, only £18 for a super-F and spare. Also, if you are unlucky in having a recharging accident, a random or premature failure due to one of the modes under examination, it is not then such a hard financial blow to replace a single cell. The same argument applies when the time comes to replace the NiCd power source due to old age.

Against these benefits must be set the inefficiency of conversion from such a low starting voltage as 1.25V. The voltage drop

across typical switching transistors and diodes is not so much less than this figure, so it is notoriously difficult to design a converter with a respectable efficiency specification. However, it can be done using special techniques. The Texas Instruments TL496 is a switching regulator i.c. which can be used as the basis for such a converter, Fig.5. Although it is more efficient operated from two cells, when it can give 80mA and 8.6V and about 55% efficiency, it can also operate from a single cell to give 40mA at about 7V. The inductance should have a value of it 40 to $50\mu\text{H}$ and as low a d.c. resistance as possible — less than 0.15Ω . Achieving this is not difficult considering the comprehensive data now provided by the ferrite manufacturers. An RM5 or RM6 core is satisfactory. Working frequency is about 10kHz. Some designers may consider it a disadvantage to have to provide their own wound component for L, not being an off-the-shelf item. For those wishing to avoid coil-winding, the Verkon V9-a provides a solution as it is self-contained dc/dc converter, providing nominal 9V d.c. output at currents up to 80mA. The V9-a is specifically designed to operate from a single NiCd or other low-impedance cell, is small enough to be p.c.b.- mounted, and has a quoted conversion efficiency of around 75%.

Another way of avoiding batteries is to design circuitry so that operation from one cell is possible. There are several suitable c-mos op-amps on the market which can work perfectly well from 1.25V, such as TLC251, ICL7611, ICL7622 and also audio amps like LD502. Although very useful for certain applications, the limitations are severe — e.g. driving relays, meters, leds is difficult. Nevertheless too many circuits for portable instruments are designed for 6 or 9V operation when they could work from a

single cell equally well, simply through lack of imagination on the part of the designer.

Continued Next Month


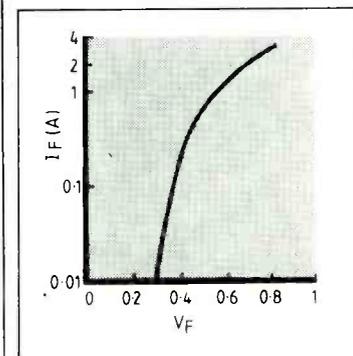


Fig. 4. Graph of I_F versus V_F for wire-ended Schottky rated at 1 amp.

Sources of components

Texas switching regulator i.c. TL496. Quarndon Electronics Ltd, Slack Lane, Derby.
Osmor latching relay CLA-5. Electrovalue, St. Judes Road, Egham, Surrey.
Verkon V9-ad.c./d.c. converter and wire-ended 1A Schottky diodes. J. Biles Engineering, 120 Castle Lane, Solihull, West Midlands.

Fig. 5. Circuit to step up 1.25V to about 7V at 40mA using the TL496 as a step-up dc/dc converter. See text for inductor details.

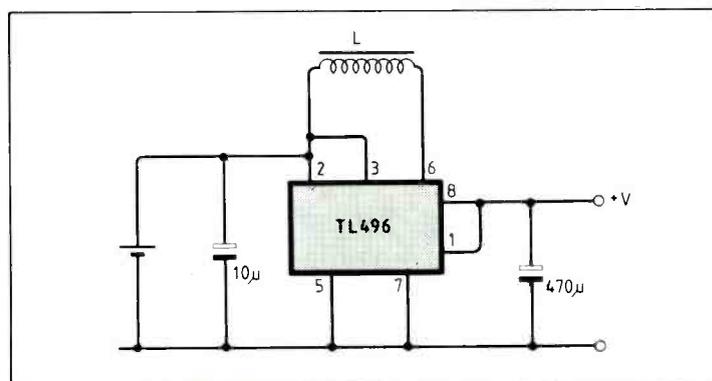

CIRCUIT MODELLER for CP/M & MS DOS

by Harcourt Systems

An engineering package for CP/M* and MS DOS* microcomputers to carry out accurate, fast designs of linear circuits.

CIRCUIT MODELLER can find voltage gain, phase shift, Z_{in} and Z_{out} for most linear electrical and electronic circuits. The limits of capacity are set by the microcomputer RAM, which must be at least 60 KBytes. This gives a capacity of 32 nodes, 101 resistors, 101 capacitors, 101 inductors, 31 mutual inductors, 31 simple operational amplifiers and 31 controlled sources.

Features include:

ADD & EDIT to construct and alter circuit
LOAD & SAVE to save and recover circuit from disk
GAIN to display gain and phase
ZIN to display input and output impedances
BW to find centre frequency and $-3dB$ Av points of circuit
SEARCH to find frequency corresponding to given gain
PRINT to print synopsis of circuit diagram sufficient for its precise reproduction.

Operating Speed

CIRCUIT MODELLER is an all-compiled package with seven overlays in which the inner two loops of pivotal condensation are written in Z80 assembler. This means that whereas microcomputer CAD is usually slow, **CIRCUIT MODELLER** can solve a four hybrid-pi amplifier in a few seconds.

Graphics

PLOT is an extension to **CIRCUIT MODELLER** enabling an ordinary 132 column printer to plot both dB gain and phase angle against frequency for the circuit. A log/log plot is obtained with automatic axis scaling.

Themselves designers of high performance electronic equipment, Seasim Controls have recognised the importance of **CIRCUIT MODELLER** which they are making available in association with Harcourt Systems.

Prices: CP/M 80 version - £160 + p&p + VAT,
 MS DOS & PC DOS versions - £214 + p&p + VAT. Order, or send for more details from **SEASIM CONTROLS LIMITED**


The Paddocks, Frith Lane, Mill Hill, London NW7 1PS

Telephone: (01) 346 9271 - Telex: 21189


*CP/M is a trademark of Digital Research

*MS DOS is a trade mark of Microsoft

**AVAILABLE IN
 SIX WEEKS
 TRANSIENT
 ANALYSIS MODELLER**

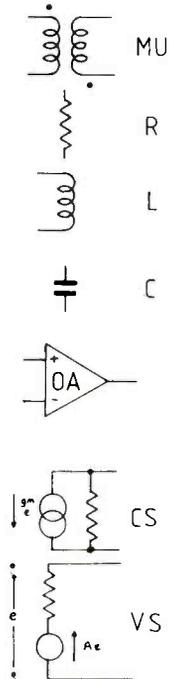

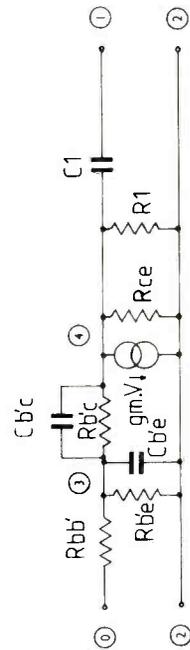**AVAILABLE IN
 SIX WEEKS
 TRANSIENT
 ANALYSIS MODELLER**



CIRCLE 16 FOR FURTHER DETAILS.

HAMEG MORE THAN JUST ONE STEP UP

HM208 £1200.

Dual Trace, Digital Storage 2mV - 20 V/cm
 20 MHz Bandwidth Algebraic Add, Invert
 X - Y, Component Tester 4 x 1k Stores,
 20 MHz Clock, Roll, Refresh, Pre-trigger.

HM605 £515.

Dual Trace 1mV - 20 V/cm
 60 MHz Bandwidth Algebraic Add, Invert
 X - Y; Single Shot Delay Sweep,
 Var Hold-off Component Tester, 14kV CRT

HM204-2 £365.

Dual Trace 1mV - 20 V/cm
 20 MHz Bandwidth Algebraic Add, Invert
 X - Y; Single Shot Delay Sweep,
 Var Hold-off Component Tester

HM203-5 £264.

Dual Trace 2mV - 20 V/cm
 20 MHz Bandwidth Algebraic Add, Invert
 X - Y Component Tester


2 Year Warranty

HAMEG

FOR THOSE WHO COMPARE

74-78 Collingdon St. Luton, Beds, LU1 1RX

Tel: (0582) 413174 Telex 825484

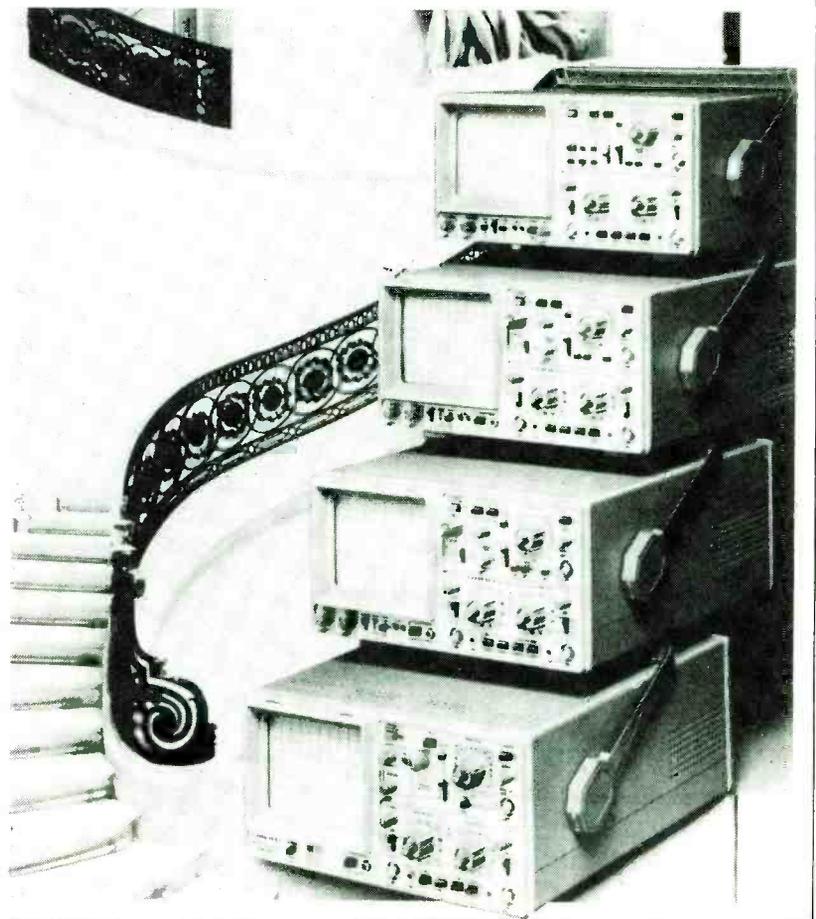

CIRCLE 35 FOR FURTHER DETAILS.

Sampled-data servos — a new analysis

by D.M. Taub
M.Sc., Ph.D.

Prior to computing servo performance Dr Taub considers the reverse of sampling: conversion from a sampled-data signal to a continuous signal

When the error signal in a servo loop is of sampled-data form, then at some point before it can be used to drive the plant it has to be converted back to continuous form. The point at which this conversion takes place depends on the type of compensator used. In the case of a compensator designed to work with sampled-data signals e.g. one using digital*, charge-coupled device or

switched-capacitor techniques, it is done at the compensator output, whereas with compensators designed to work with continuous signals it is done in two stages, a sampled-data stage followed by a continuous-signal stage, in which case conversion is carried out at the interface between the two.

The circuit which carries out the conversion is generally known as a 'hold' circuit, and various types exist. In the simplest and most widely used type, the output between one sample and

the next is held constant at a value proportional to the weight of the sample most recently received. Typical input and output signals are shown in Fig. 15 (a) and (b). In mathematical terms one can say that the output between one sampling instant and the next is described by a polynomial equation of zero order; hence the circuit is known as a 'zero-order hold' circuit.

In a more complicated arrangement the output immediately after the sampling instant is proportional to the weight of sample just received, but it then changes at a uniform rate proportional to the difference between that sam-

Fig. 15. Input and output signals of zero-order hold circuits: the hold circuit converts a sampled-data signal back to a continuous signal. Input at (a), output of zero-order hold (b), and output of first-order hold (c).

Fig. 16. Response of a hold circuit to a unit-impulse input.



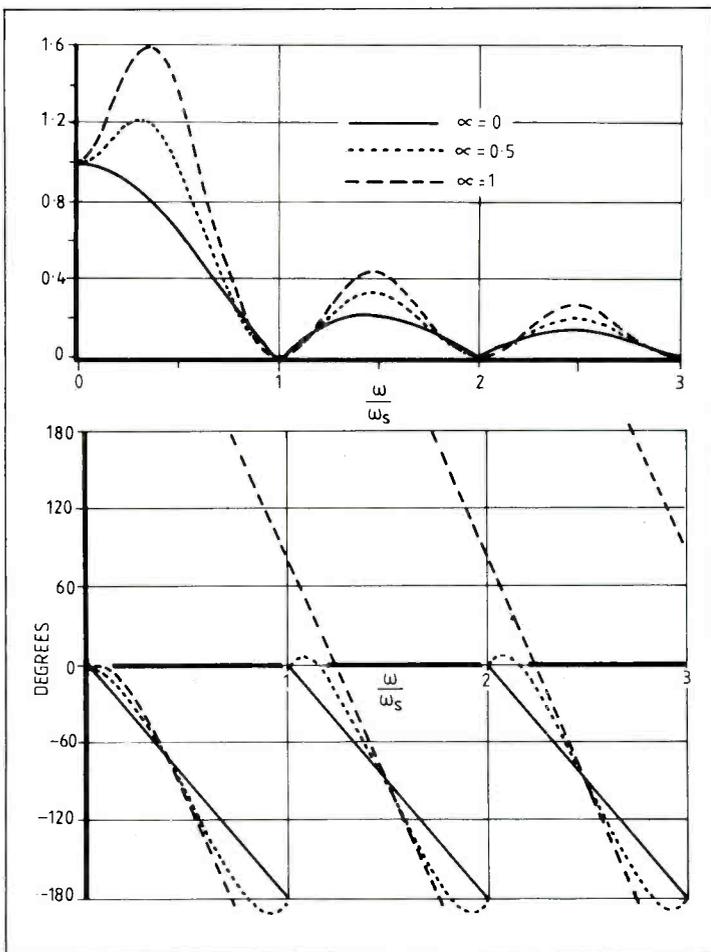


Fig. 17. Gain characteristics of various hold circuits, amplitude above, phase below.

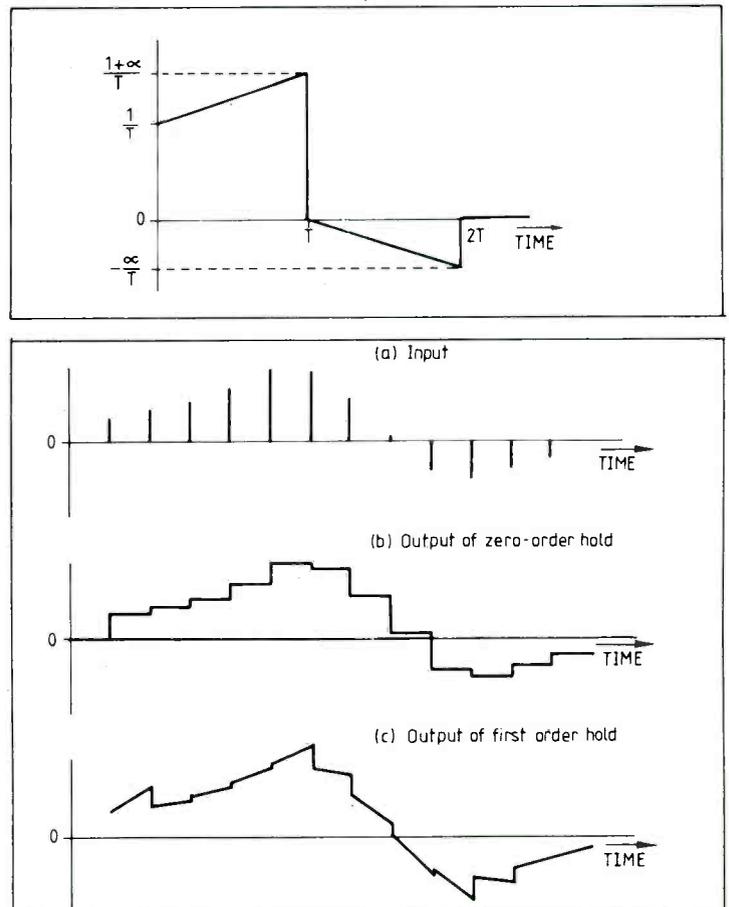

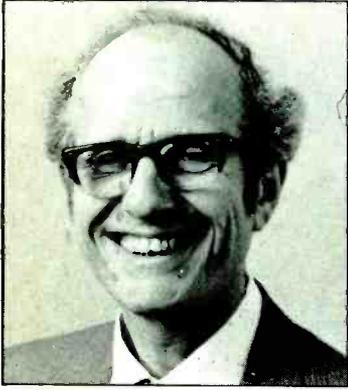

Since 1950, Matthew Taub has been continuously engaged in development work on digital electronics. After five years with Ericsson Telephones Ltd (now part of the Plessey Group), where he worked on electronic switching in telephone exchanges, he went to Leo Computers Ltd (now part of ICL), contributing to the development of the mercury delay-line store and input/output section of the LEO 2 computer. He joined IBM UK Laboratories Ltd in 1957 and is now a Senior Technical Staff member. Areas of work at IBM included magnetic core logic circuits, computer architecture, read-only and magnetic disc techniques, and circuits for c.r.t. displays. During the past two years he's been active on the working group developing Futurebus multiprocessor systems.

He has 22 publications in journals, a further 26 in the IBM Technical Disclosure Bulletin, and is named as inventor or co-inventor on 27 patents. The published work earned him a PhD degree from Cambridge University in 1982. Previously he'd studied electrical engineering at University College, Nottingham, gaining the B.Sc (Eng) degree in 1945, and after a short period with Ferranti went on to carry out research into noise phenomena in electron tubes at the Cambridge University Engineering Laboratory, for which he received the M.Sc. degree.

ple and its predecessor. The input signal of Fig.15(a) then produces an output as shown in Fig. 15(c). In this case the output the output between sampling instants is described by a first-order equation, giving this circuit the name of 'first-order hold'.

The zero-order hold can be regarded as a limiting case of the first-order hold, in which the constant of proportionality governing the rate of change of output is zero. Higher-order hold circuits are possible, but are not important in practice.

Gain characteristics of hold circuits

The gain of zero and first-order circuits can be covered in a single analysis. To produce the output described above, the response $a(t)$ to a unit impulse at the input (i.e. a sample of unit value) must be as shown in Fig. 16. The factor of $1/T$ in the amplitude is necessary for consistency with the sampling process assumed in the (April issue): a continuous signal of unit value gives rise to samples of weight T , which on reconversion to a continuous signal, produces unit value again. Positive values of α represent the first-order case, and $\alpha = 0$ the zero-order case.*

The gain characteristic is found by taking the Laplace transform of $a(t)$, as follows (see ref.5, section 3.4).

$$\begin{aligned}
 H_1(s) &= \int_0^{\infty} a(t) e^{-st} dt \\
 &= \frac{1}{T} \int_0^T \left(1 + \frac{\alpha t}{T}\right) e^{-st} dt + \\
 &\quad + \alpha \int_T^{\infty} \left(1 - \frac{t-T}{T}\right) e^{-st} dt \\
 &= \frac{1 - e^{-Ts}}{Ts} \left\{ 1 + \right. \\
 &\quad \left. + \alpha \left[\frac{1 - e^{-Ts}}{Ts} - e^{-Ts} \right] \right\} \dots 3.1
 \end{aligned}$$

The gain at real frequencies is found by setting $s = j\omega$, which gives

$$\begin{aligned}
 H_1(j\omega) &= \frac{1 - e^{-jT\omega}}{jT\omega} \left\{ 1 + \right. \\
 &\quad \left. + \alpha \left[\frac{1 - e^{-jT\omega}}{jT\omega} - e^{-jT\omega} \right] \right\} \dots 3.2
 \end{aligned}$$

* Textbooks generally restrict the term 'first-order hold' to the case where $\alpha = 1$, and Kuo (ref.6) describes circuits in which $0 < \alpha < 1$ as 'fractional-order', but this is a misnomer.

List of principal symbols

A, B, C, D	points in the servo loop at which signals are continuous functions of time (Fig. 21)	T	sampling interval
A(s) to D(s)	signals at points A, B, C and D respectively as functions of complex frequency	t	time
a(t) to d(t)	— ditto — as functions of time	U, V, X, Y	points in the servo loop carrying sampled-data signals (Fig. 21)
f_s	sampling frequency	U(z) to Y(z)	z-transforms of signals at U, V, X and Y
H	gain; subscripts indicate points between which the gain applies	u(n) to y(n)	sample values at U, V, X and Y
j	$\sqrt{-1}$	z	e^{Ts}
K	multiplication constant in expressions where gain is expressed in terms of poles and zeros	α	hold-circuit proportionality constant
k	integer	β_k	coefficient of z^k in numerator polynomial of $H_{VX}(z)$
L	$H_{XV}(j\omega) \sum_{k=0}^m \xi_k e^{jkT\omega}$	γ_k	coefficient of z^k in denominator polynomial of $H_{VX}(z)$
m	integer; also highest power in general polynomial expressions	$\delta(t)$	Dirac function
M	highest power of z in numerator and denominator polynomials of $H_{UV}(z)$	$\Delta\tau$	time delay between A and B (Fig. 21)
n	sample number	ζ_k	coefficient of z^k in numerator polynomial of $H_{UV}(z)$
p(t)	sampling waveform	η_k	coefficient of z^k in denominator polynomial of $H_{UV}(z)$
s	complex frequency	$\lambda_1, \lambda_2, \dots$	zeros of $H_{XD}(s)$
		μ_1, μ_2, \dots	poles of $H_{XD}(s)$
		ν_k	coefficient of z^k in numerator polynomial of $H_{XV}(z)$
		ξ_k	coefficient of z^k in denominator polynomial of $H_{XV}(z)$
		ψ_1, ψ_2, \dots	poles of $H_{XV}(z)$
		ω	angular frequency
		ϕ	phase angle

The modulus and phase angle of this function are plotted in Fig. 17.

In the zero-order case where $\alpha = 0$ this last equation reduces to

$$H_0(j\omega) = \frac{1 - e^{-jT\omega}}{jT\omega}$$

and using equations 2.1 and $T = 2\pi/\omega_s$ this becomes

$$H_0(j\omega) = e^{-j\frac{\omega}{\omega_s} \pi} \frac{\sin \frac{\omega}{\omega_s} \pi}{\frac{\omega}{\omega_s} \pi} \dots 3.3$$

APPENDIX

Effect of using unit impulses in sampling waveform

To keep the mathematical expression as simple as possible, it has been assumed in the main text and in the programs, that the sampling waveform consists of impulses of weight T (part 2), and that on conversion back from a sampled-data signal to a continuous signal, the output immediately following a sample of weight T has unit value. In practically all the published literature, however, sampling is assumed to be done with unit-weight impulses. Therefore to relate the material presented here to other publications, the principal equations for unit-weight sampling pulses are given. The equations are numbered as in the main body of the

text but with the prefix U to indicate unit-weight impulses.

Gain of first-order hold circuit:

$$\begin{aligned}
 H_1(s) &= \frac{1 - e^{-Ts}}{s} \left\{ 1 + \right. \\
 &\quad \left. + \alpha \left[\frac{1 - e^{-Ts}}{Ts} - e^{-Ts} \right] \right\} \dots U3.1
 \end{aligned}$$


Gain of zero-order hold circuit:

$$H_0(s) = e^{-j\frac{\omega}{\omega_s} \pi} T \frac{\sin \frac{\omega}{\omega_s} \pi}{\frac{\omega}{\omega_s} \pi} \dots U3.3$$

REFERENCES

- J.J. Distefano, A.R. Stubberud and I.J. Williams. 'Feedback and Control Systems' (Schaum's Outline Series, McGraw-Hill, New York, 1976).
- M. Healey. 'Principles of automatic control'. (Hodder and Stoughton, London, 1975).
- M.K. Haynes. 'Magnetic recording techniques for buried servos'. *IEEE Transactions on Magnetics*. Vol. MAG 17, 1981 pp 2730-4.
- N.H. Hansen. 'Head-positioning system using buried servo'. *ibid* pp 2735-8.
- P.A. Lynn. 'Introduction to the analysis and processing of signals' (Macmillan, London, 1973).
- B.C. Kuo. 'Analysis and synthesis of sampled-data control systems' (Prentice-Hall, Englewood Cliffs, NJ, 1963)
- A.M. Tropper. 'Matrix theory for electrical engineering students' (Harrap, London, 1962).
- S. Goldman. 'Transformation calculus and electrical transients', (Prentice-Hall, New York, 1949).
- D.M. Taub. 'Programs for computing sampled-data servo performance'. IBM Technical Report no.12.199, (IBM United Kingdom Laboratories, Hursley, May 1982).

D.c. supplies from a.c. sources — 4

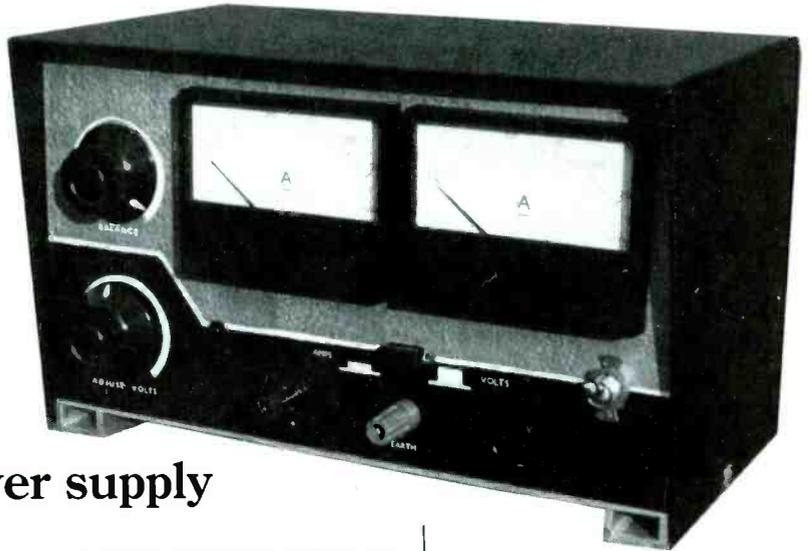

Constructing a stabilized power supply

An important step in studying a topic is when the experimenter puts theory into practice. And as lab. or bench type power supply designs seem to be unendingly popular, here is another, which can supply some 80 watts at 13.8V.

There is a "chicken and egg" situation in such designs as that shown in block form in Fig. 1. For example, what transformer rating (in VA) is required, when we do not yet know the r.m.s. secondary currents? These currents through the rectifiers are known and these depend on the source resistance R_s . R_s will only become known when the size, and therefore wire gauge and turns on the transformer windings, are known. . . !

'From experience' (an expression nearly as famous as 'it can be shown') an R_s of about one ohm is common for such power levels as used here.

$$R_L \text{ will be } \frac{21 \text{ volts}}{6 \text{ amps}} = 3.5\Omega$$

on full load. Therefore τ_c will be about 5.6ms from Fig. 3 (part 3). Equation 11 (part 3) then yields $I_{rms} = 6.3A$ for one half, therefore the total r.m.s. current is $\sqrt{2} \times 6.3 = 9$ amps. This, together with the total r.m.s. voltage of 40V across the secondary gives a required rating for the transformer amounting to 360 VA. (Equation 10 would give this directly, because from the transformer's point of view, it is feeding a bridge rectifier).

Now the d.c. power in the load plus dissipative pass elements is $40V \times 6A = 240$ watts. Therefore the transformer utilisation factor is $360/240 = 1.5$, meaning that it has to be about one and a half times bigger than you'd

think. The iron in the transformer used for the practical design had a centre limb area of 2.9 square inches, so that it can handle $(2.9 \times 6.9)^2 = 395VA$, which is comfortably within the requirements.

You would expect the peak voltage (no load) across the smoothing capacitors with a 20 volt half winding secondary to be $20 \times 1.414 = 28$ volts. With $R_s \sim 1$ ohm we would lose about 6 volts at full load, so the mean d.c. level at the input to the series regulators would be $\sim 22V$. Then we have the peak ripple voltage to consider. Using equation 12 (part 3)

$$\hat{V}_r = \frac{6(10 - 5.6) \times 10^{-3}}{2 \times 10^{-2}} = 1.32 \text{ volts}$$

This shows that the troughs in the supply to the regulators will reach a low of $22 - 1.32 = 20$ volts, say. Therefore with the 20-0-20 r.m.s. transformer we will not be able to reach the full $\pm 20V$ output on full load of 6A. Hence the 'spec.' judiciously says 'reduced load at the top end'.

The completed unit yielded transformer secondary voltages of 20.3V and rectified d.c. voltages on the smoothing capacitors of 27.3V with no output load current drawn. When 6A was taken, the capacitor voltages dropped to 21.2V and the peak ripple voltage was measured as 1.25 volts.

There are many integrated blocks from the i.c. designers that give excellent performance, including thermal shut down and current limiting. The three-terminal adjustable type, such as the 317, are particularly versatile. The 317 is already dated, but is still very popular.

The design shown in Fig. 2

uses it to control the positive supply, together with shunt booster transistors to up the current to 5-6 amps. The common 2N3055 is used for this. In effect, the 2N3047 plus the 2N3055 act as one much larger p.n.p. device — but is overall cheaper for the power handling capability. The 'current division' resistors (1ohm and 0.25ohm) at the input share out the current to the 317/2N3055 in the ratio 1:4. The 317 limits at just over an amp, so the whole control leg limits at approx 5 to 6 amps if the output is short circuited.

The single variable resistor (4.7k) on the 'var' terminal of the 317 can reduce the output to 1.4 volts minimum. To reduce the output to zero requires a bias of -1.4 volts on its tail end. This -1.4 volts is obtained across the two forward biased silicon diodes as shown in Fig. 2. The 6A diode gives one junction drop to compensate for the base-emitter drop in the 2N3047, and is generously rated. The other components around the 317 comply with the maker's recommendations (1).

Once the positive line is stabilised, it can be used as a reference level for the negative line. Any change in this line's output voltage is divided down and tapped off the wiper of the 1k 'balance' potentiometer, amplified, inverted by the operational amplifier and (with lots of current gain) fed back via the compound emitter follower to 'cancel' most of the original change.

By the time we have 6 amps going through the 2N3055s, the h_{FE} is reducing. This point was offered as criticism to E.J. Hatch with his very high demand on the 2N3055. I agree with this and the result is an increasing demand on the driver transistor, the 2N3054

by K.L. Smith
Ph.D.*

* University of Kent at Canterbury

POWER BACKED PRODUCTS



Choose our DC to DC converters, encapsulated AC to DC or open card power supplies and you'll get more than just the product.

The hidden ingredients packed into every unit are decades of design, manufacturing and applications knowledge, backed by the financial strength and stability of Computer Products Inc; five plants throughout the world, design and manufacturing right here in Europe, with total commitment to new technology, computer aided design and automatic test equipment.

All this plus guaranteed technical specifications and a full TWO YEARS warranty which underwrites our quality confidence.

Distributed by Amplicon from extensive stocks means you get fast delivery backed by a team of professional sales and service engineers, all trained at the factory to know our products and help you apply them.

So pick Packaged Power, go for more value, back the White Horse.

15 WATT TRIPLE OUTPUT DC TO DC CONVERTERS

ES series offer better regulated power from a smaller package than any other triple output DC/DC converters on the market today. Featuring a wide 2:1 input range and efficiency as high as 82% achieved by simplified MOSFET circuitry with 100KHz switching regulation.

Nine models available with isolated, regulated, low noise outputs of 5V/±12V, 5V/±15V or 12V/±5V.

Six sided copper shielding provides EMI/RFI suppression and over voltage protection and 500V DC isolation are standard.

COMPUTER PRODUCTS
POWER PRODUCTS LIMITED
CIRCLE 4 FOR FURTHER DETAILS.

AMPLICON

Amplicon Electronics Limited Richmond Road Brighton East Sussex BN2 3RL UK
Tel. Brighton (0273) 608331 Telex: 877470 AMPCON G.

FIELD ELECTRIC LTD

3 SHENLEY RD, BOREHAMWOOD, HERTS.
TELEPHONE 01-953-6009

☑/OFFICIAL ORDERS/OVERSEAS ENQUIRIES WELCOME
OPEN 6 DAY'S A WEEK 9.00am/5.00pm THUR. 9.00am/1.00pm

ALL TRANSFORMERS 250 PRIMARIES		
LAMBDA 9-0-9V	60AMP	£25.00
C LYONS 250V	10AMP ISOLATING	46.00
12-0-12V	80AMP	30.00
WODEN 11V	80AMP	35.00
WODEN 7.6V	120AMP	40.00
WODEN 27V	30AMP	25.00
WODEN 60-0-60V	60AMP ISOLATING	115.00
GOODYEAR 115V	50AMP ISOLATING	115.00
PLEASE RING FOR C/P		


ALL P.S.U. 200-250 V.A.C. INPUTS		
SWITCH MODE P.S.U. C/P 2.00 UNLESS STATED		
3.5V 10AMP D.C.		£12.50
ADVANCE 5V 20AMP D.C.		18.50
5V 30AMP DC		19.95
5V 40AMP D.C.		40.00
5V 60AMP D.C.		20.00
FARNELL 6V 5AMP D.C. 145x87x32 M/M		20.00
FARNELL 5V 20AMP D.C.		20.00
6V 40AMP D.C.		40.00
FARNELL 24V 5AMP		35.00
FARNELL 12V 10AMP		35.00
FARNELL FAN COOLED MULTI-RAIL SWITCH MODE		
+15V AT 15AMP - 5V AT 1AMP + 12V AT 4AMP - 12V AT 1AMP		28.00
GOULD MULTI-RAIL SWITCH MODE NEW		
5V 40AMP - 12V 4AMP + 15V 11AMP C/P 6.00		75.00
GOULD NEW & BOXED 6V 40AMP		60.00
GOULD PMA47 12V 3AMP DC LINEAR		16.95
COUTANT 0-7V 7AMP D.C. LINEAR NEW & BOXED		19.95
COUTANT ESM LINEAR MULTI-RAIL		
5V 13AMP D.C. ±12V 1.5AMP OR ±15V 1.5AMP		
12V OR 24V 2AMP UNREGULATED COMPLETE BOOK CIRCUIT DIA. NEW		40.00
BOXED C/P 6.00		
VOLTEX LINEAR MULTI-RAIL + 12V 600M/A + 5V 1AMP D.C.		11.25
P.C. SUPPLY + 5V 1AMP D.C. TOROIDAL T/X REGULATED		6.95

WE ALSO BUY EQUIPMENT SURPLUS TO REQUIREMENT.

SEND LIST OR PHONE

ALL PRICES INC VAT 15% UNLESS STATED

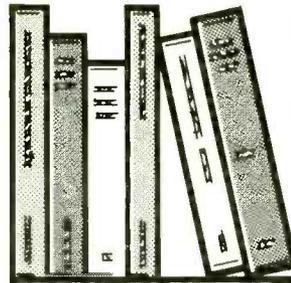
COLOUR MONITORS
RGB INPUT 230 V.A.C.
19" SCREEN
MEDIUM RESOLUTION
£55.00 INC. VAT
RING FOR DETAILS



RSGB BOOKS

AMATEUR RADIO CALL BOOK

1985 EDITION

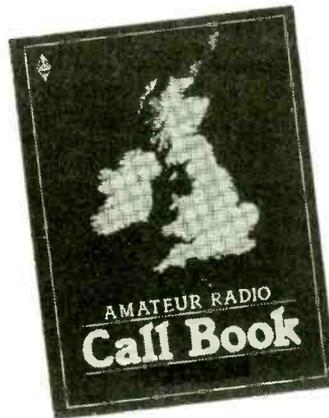

The latest version of this best-seller from the RSGB.

An up-to-date and comprehensive guide to all UK and Eire call signs — and all in one book.

There are more than 53,000 callsigns listed in this expanded edition, and more efficient production techniques have allowed us to keep the cover price to a very acceptable level. The Call Book includes lists of RSGB affiliated societies, groups, and special callsigns, plus the latest RSGB repeaters list.

Most addresses given are the locations of the stations, thereby giving the VHF/UHF enthusiast an easy reference for beam directions. The Call Book first appeared at the NEC Exhibition, and is now readily available."

NOW IN STOCK: Amateur Radio Software

"Written especially for the RSGB, this extremely useful new book will have immediate appeal to all amateurs who want to make use of their home computers. There are many programs, listings and full instructions on how to make the best of both worlds.

Author Dr John Morris G4ANB says there is hardly an activity in amateur radio where a computer cannot be used. Many subjects covered include vhf contests, scoring, component values, propagation predictions, where to point your antenna for moonbounce or satellite working, cw, and much more besides! How to write your own programs, and use the software to its best advantage is what this book is all about."

OTHER RSGB PUBLICATIONS

Radio Amateurs' Examination Manual	£3.46.
1985 World Radio TV Handbook	£poa.
VHF/UHF Manual	£9.52.
Microwave Newsletter Technical Collection	£6.15.
A Guide to Amateur Radio	£3.52.
Morse Code for Radio Amateurs	£1.48.
How to pass the RAE	£3.08.
Test Equipment for the Radio Amateur	£5.77.
Microwave Newsletter Technical Collection	£6.15.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby, including listeners. The Society publishes a range of books, log books and maps for the radio amateur. A large selection of other radio and electronics books are also stocked, a full list is available on request. Contact the membership services section for more information about amateur radio, the RSGB and its publications. All publications sold by the RSGB are available at discounted prices to members.



RSGB Publications

Cranborne Road, Potters Bar,
Hertfordshire EN6 3JW

CIRCLE 70 FOR FURTHER DETAILS.

ELECTRONICS & Wireless World

Any Production Queries
Please phone
Brian Bannister on
01-661 8648
or Jackie Perry on
01-661 8649

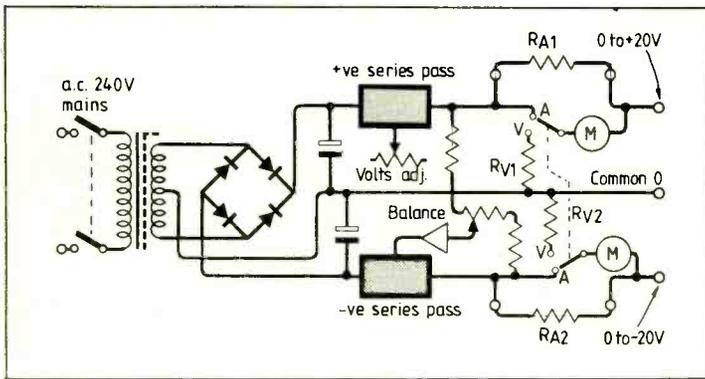


Fig. 1. The diagram shows how positive and negative lines can be obtained from a centre tapped transformer secondary in conjunction with a bridge rectifier. The negative line is referenced to the stabilised positive supply.

Simple volt-amp meter switching to monitor the output is illustrated.

here. If the h_{FE} drops to ~ 10 (as it might with $I_c \sim 10A$) — then the poor old 2N3054 could be called on to deliver more than an amp! (Therefore this could be the device to fail first). The circuit will manage 6A fairly well, as the h_{FE} for the 2N3055 is still well over 20 and the base drive therefore $\sim 300mA$. The 2N3054 can supply this and its own h_{FE} should be ~ 70 . Therefore the base drive from the BC177 collector is required to be about 4mA — well within the capability. Finally there is no difficulty driving the BC177 from the 741.

One other point is that we fall into the habit of saying 'an on silicon junction drops about 0.7 volts'. This is not necessarily true for the power devices used here. For example, the V_{be} given for a

2N3055 at $I_c = 6A$ is 1.7 volts. The 2N3054 might very well drop a further 0.9 volts at $\sim 300mA$. Finally there is the $V_{ce(sat)}$ for the BC177, which is about 0.6 volts. There is one more junction drop at 6 amps — that across the resistor labelled 'R' on Fig. 2. At 6 amps, 'R' is chosen to drop just one small signal silicon 'on' voltage to turn on the BC109 current limited transistor. Therefore the minimum voltage differential from source to output terminal must be, $1.7 + 0.9 + 0.6 + 0.7 \sim 4$ volts at 6 amps. The differential available in the practical design operating at 13.8 volts output is $21.2 - 13.8 = 7.4$ volts. Which, on the above argument, is sufficient.

When the current limit transistor turns on, current is shunted away from the base of the 2N3054. The output voltage rapidly collapses and the op-amp rapidly saturates. The current remains at 6A. However, all the available supply voltage is across the 2N3055, whose resistance has been raised, and maximum dissipation is occurring in it. In fact the thermal lag will safeguard the devices for a time, but the dissipation is actually greater than $P_{c(max)}$ for them, so prolonged shorting would probably result in failure. . .

Power dissipation and heat sinking


As I stated in article 1, the series regulator is a dissipator of surplus power and plenty of heat will be generated. The 2N3055 can dissipate 117 watts absolute maximum, but the mounting base temperature T_{mb} , for this must be $25^\circ C$. In practice, the mounting base temperature will be greater and power derating must be applied. The derating must reduce the dissipation to zero at a junction temperature T_j of $200^\circ C$. This is the absolute maximum junction temperature allowable.

In order to remove the heat from the base-collector junction, it has to flow through the thermal resistance of the path, junction to mounting base. The IEC 148 symbol convention for this is $R_{th j-mb}$, which is rather heavy on subscript use, but descriptive. . .

The mounting base (which is in effect, the case) then warms up. Further heat removal must be arranged from the mounting base to the heat sink. This has a resistance, $R_{th mb-h}$. Finally, the heat sink must dissipate the heat arriving, into the ambient surroundings. This resistance is written $R_{th h-amb}$.

Thus the total thermal resistance from the junction to ambient is,

Fig. 2. the practical circuit shows all the design points discussed in the text.

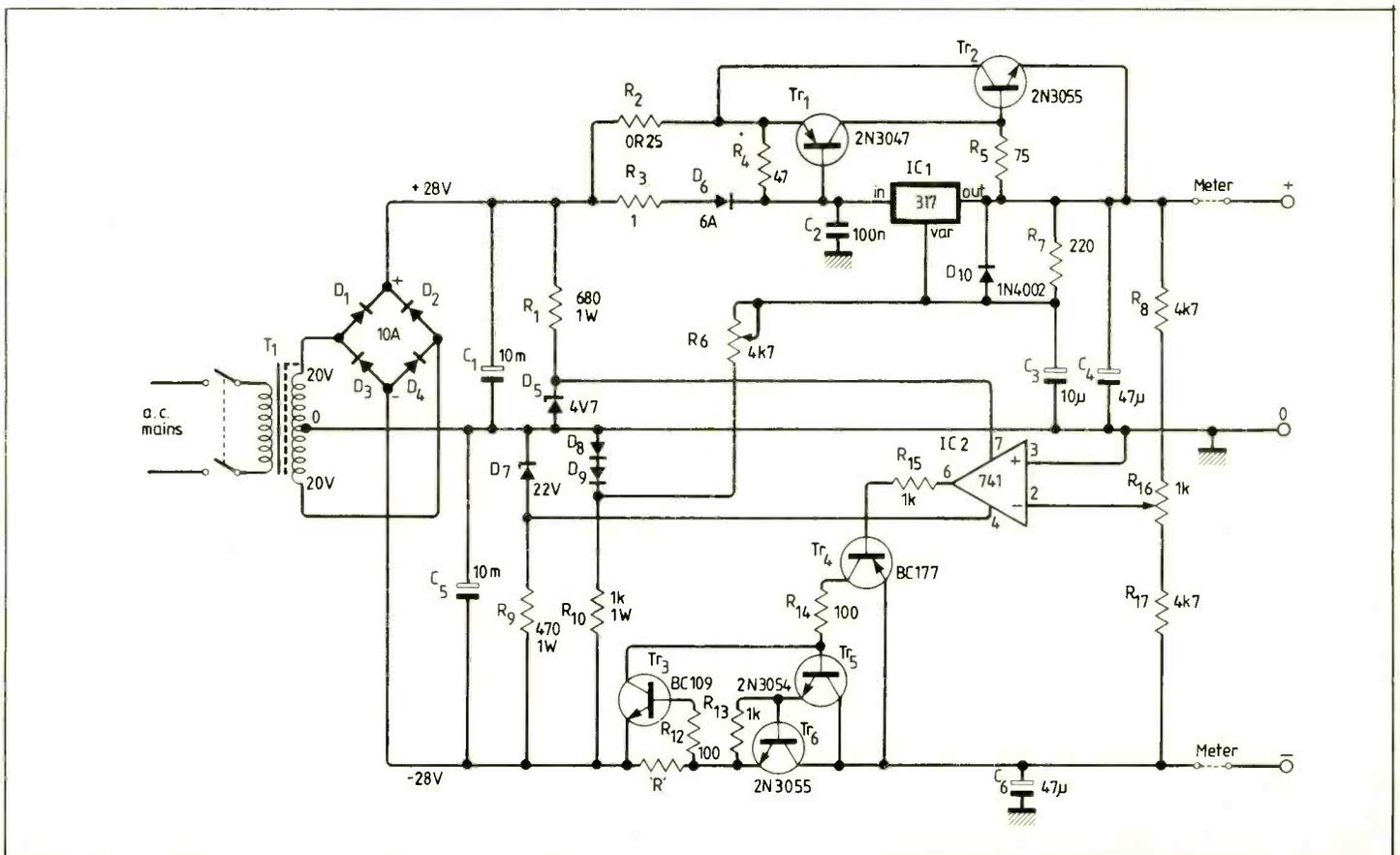

$$R_{th\ j-amb} = R_{th\ j-mb} + R_{th\ mb-h} + R_{th\ h-amb}$$

The direct heat loss from the mounting base to the surroundings has been ignored in my argument, so has the (much smaller) contribution to the heat production by the dissipation at emitter-base junction-

The TO3 package 2N3055 has an $R_{th\ j-mb}$ of 1.5°C per watt. If a mica washer with thermal grease is used between it and the heat-sink, then an $R_{th\ mb-h}$ of 0.5°C per watt should be obtained. It only remains to establish a value of $R_{th\ h-a}$ for a suitable heatsink to be chosen, by an argument like the following.

If you remember your basic physics, then a TO3 case on a mica washer and heat sink is simply a Lee's disc situation, except that the shape is far from a disc. If P_{tot} is the power dissipated by the 2N3055, then the temperature of the mounting base, the junction and the thermal resistance is related by

$$R_{th\ j-mb} = \frac{T_j - T_{mb}}{P_{tot}}$$

Similarly the flow of heat to the ambient surroundings is given by

$$R_{th\ j-mb} + R_{th\ mb-h} + R_{th\ h-amb} = \frac{T_j - T_{amb}}{P_{tot}}$$

Therefore as all the numbers are known except $R_{th\ h-amb}$, this can be calculated. As an example, if the present power supply is intended to operate continuously at 13.8 volts at 6 amps output (although in a communications system there will be an "on/off" diversity factor), then the 2N3055 on that side must dissipate $(21.3 - 13.8) \times 6 = 45$ watts. Therefore

$$R_{th\ h-amb} = \frac{200 - 20}{45} - 2 = 2^\circ\text{C per watt}$$

I chose a 110mm length of extrusion 30D. The thermal resistance of this sink is 1.3°C per watt at 45 watts dissipation. Therefore the T_{mb} and T_j values reached at a T_{amb} of 20°C are 100°C and 168°C respectively. On a 6A at 13.8V soak test, the case of the 'negative' 2N3055 reached ~ 90°C.

The above calculation does show up the fact that the heat dissipation is not sufficient for sustained short-circuit conditions — or a continuous maximum current drain at low output voltages (less than 8 volts. . .). A larger heat

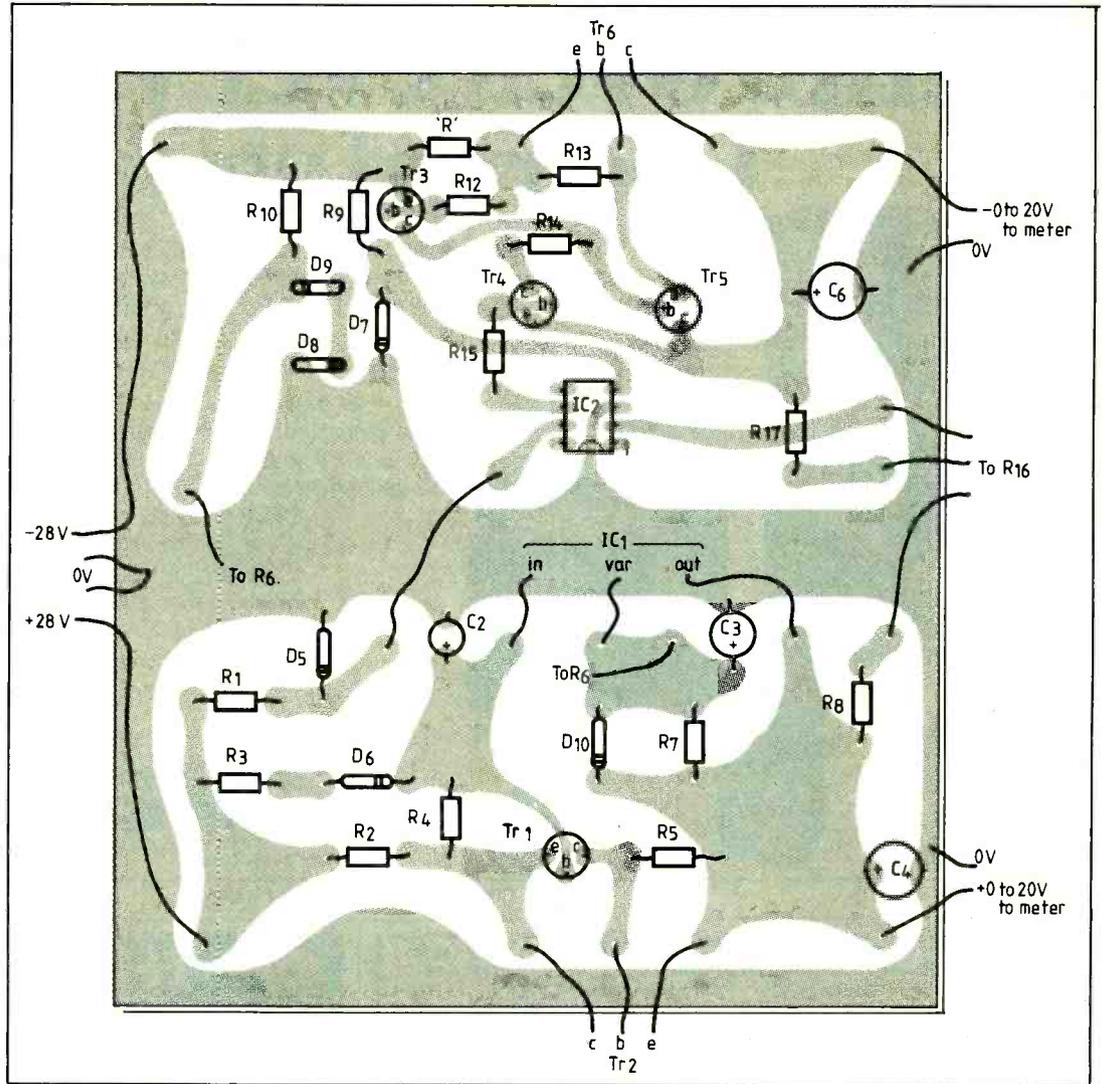


Fig. 3. The printed circuit design is shown at (a), with component layout at (b).

sink would alleviate these limitations.

Construction

The circuit details and printed-circuit layout are shown in Fig. 2 and Fig. 3 (a) and (b). Each heat sink has the dimensions mentioned above. In my unit, simple voltmeter and ammeter switching was incorporated to indicate the output quantities, (see Fig. 1).


Performance

Figure 4 shows the results obtained under load for the two outputs. The ranges over which good stability is obtained is clearly seen. The limitations predicted for the high output (20V) shows up. The negative line regulation (given a constant positive line) is


$$\begin{aligned} \text{Load regulation} &= \frac{\Delta V_o}{V_o \Delta I_o} \times 100 \\ &= \frac{13.86 - 13.79}{13.8 \times 6} \\ &= 0.08\% \end{aligned}$$

This is better than the positive side, which is 0.57%. For the test "to extremum" the current limit resistor 'R' was shorted.

Fig. 4. The test results on the bench are shown here. The sharp drop-off in the positive output shows the capability of the 317 chip.

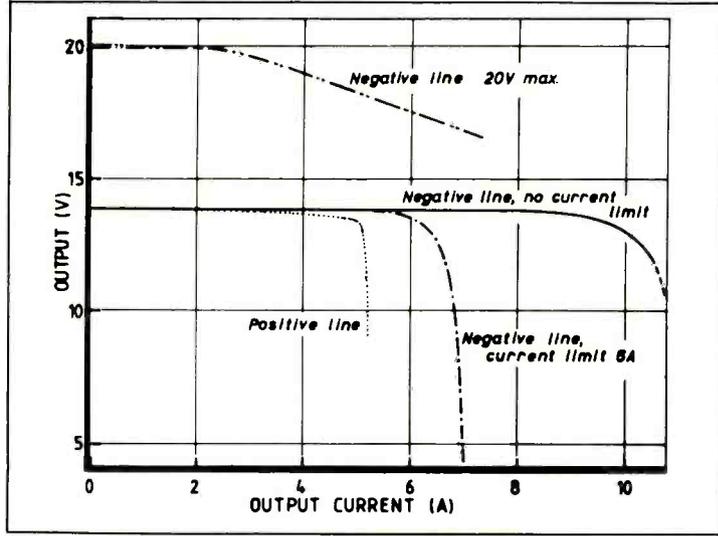

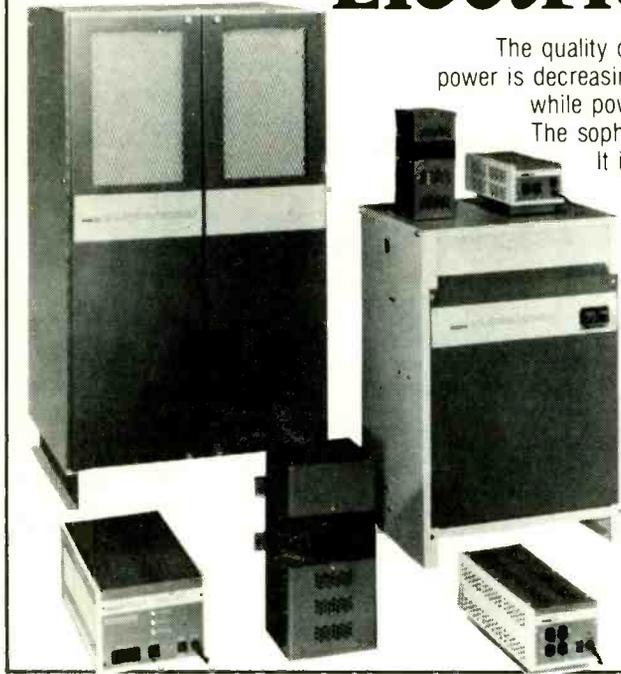Electronic technology improves every year. Electrical power does not.



The quality of electronic equipment is increasing every year, but the quality of electrical power is decreasing. Computer technology is continuously experiencing a high rate of growth while power utilities in the U.S. are already failing to meet peak demands for power. The sophistication of electronic equipment requires clean power to operate smoothly. It is the user's responsibility to protect his equipment against these problems.

Sola power protectors are the simplest, most effective and economical way to eliminate these problems by cleaning and stabilizing your power just before you use it. The Minicomputer Regulator provides ultra-isolation and regulates voltage for small microprocessor based systems such as CRT terminals and POS systems. CVS, a sinusoidal constant voltage transformer, blocks out brownouts, transients and voltage spikes for instrumentation applications. Solatron/ Acuvolt conditions power and regulates voltage for large computers and industrial equipment. All these products are UL listed.

Guard today's technology against yesterday's electricity with Sola power protectors.



The Power Protectors

CIRCLE 11 FOR FURTHER DETAILS.

TRANSFORMERS EX-STOCK				INVERTERS 12/24V DC-240V AC			
MAINS ISOLATORS Pri/Sec 120V x 2 (60-1000VA Tap Secs)				100W £65.15			
VA	Price	P&P		250W £172.70			
20	6.11	1.70		500W £196.19			
40	9.96	1.89		1000W £396.72			
100	11.63	2.10		2000W £779.90			
200	16.47	2.36		4000W £1160.00			
250	19.92	2.77		CONSTANT VOLTAGE TRANSFORMERS 1% Spike-free stable mains			
350	24.64	2.84		250VA £172.40			
500	30.64	3.10		500VA £196.69			
1000	55.65	4.70		1KW £338.40			
1500	71.79	5.95		2KW £594.50			
2000	86.38	6.35		3KW £840.00			
3000	121.12	OA		4KW £1266.00			
400/440 to 200/240V CT				5KW £1531.00			
VA	Price	P&P		6KW £1743.00			
60	9.98	1.90		7.5KVA £2073.00			
100	11.88	2.10		10KVA £3347.00			
200	16.47	2.36		AVOS & MEGGERS			
250	19.92	2.52		8Mk6 (latest) £138.70			
350	24.64	2.84		DA211 LCD £68.40			
500	30.69	3.10		DA2000 LCD £72.80			
1000	55.65	4.20		DA117 AUTO £157.00			
2000	86.38	5.50		Megger Gen £116.40			
3000	121.14	OA		Batt Megger £85.50			
6000	240.19	OA		TT169 Transistor Tester £61.30			
60/30V or 30-0-30V				7.5KVA £2073.00			
Pri 2x120V. 2x30V Tap				10KVA £3347.00			
Secs. Volts available				AVOS & MEGGERS			
6, 8, 10, 12, 16, 18,				8Mk6 (latest) £138.70			
20, 24, 30, 36, 40, 48, 60,				DA211 LCD £68.40			
24-0-24 or 30-0-30V.				DA2000 LCD £72.80			
60V	30V	Price	P&P	DA117 AUTO £157.00			
0.5	1	4.34	1.47	Megger Gen £116.40			
1	2	5.28	1.50	Batt Megger £85.50			
2	4	9.12	1.94	TT169 Transistor Tester £61.30			
3	6	10.36	1.96	P&P £2 VAT 15%			
4	8	14.80	2.22	WW MODEM PROJECT			
6	12	18.91	2.30	Transformers T1, T2			
8	16	26.75	2.86	£6.90 pair inc VAT, P&P			
10	20	31.43	3.20	METAL OXIDE 1/2W			
12	24	37.99	3.36	5% RESISTORS £10/100			
30/15V or 15-0-15V				12, 20, 33, 47, 75, 390, 430,			
2x15V Tap Secs. Volts				510Ω, 560, 1k, 1k1, 1k3,			
available 5, 7, 8, 10, 13,				1k6, 1k8, 2k, 3k, 3k9, 15k,			
20-0-20 or 25-0-25V				16k, 24k, 27k, 39k, 56k,			
30V	15V	Price	P&P	82k, 100k, 110k, 120k,			
0.5	1	3.35	1.36	130k, 150k, 200k, 220k,			
1	2	4.64	1.48	270k, 300k. P&P 20p.			
2	4	7.34	1.69	BRIDGE RECTIFIERS			
3	6	8.50	1.45	1A 400V 32			
4	8	10.15	1.99	2A 200V 45			
5	10	12.55	2.10	3A 100V £2.60			
6	12	14.20	2.30	50A 100V £3.20			
8	16	19.00	2.36	12.5A 500V £3.40			
10	20	21.92	2.46				
12	24	24.36	2.63				
15	30	27.96	3.20				
20	40	37.42	5.14				
AUTOS							
105, 115, 220, 230, 240V							
For step-up or down							
VA	Price	P&P					
20	5.08	1.49					
150	7.31	1.69					
250	8.96	1.78					
500	13.96	2.34					
1000	23.84	2.90					
1500	29.58	3.35					
2000	44.34	4.20					
3000	75.22	5.10					
5000	113.11	OA					
CASED AUTOS 240V cable							
I/P 115V USA skt outlets							
VA	Price	P&P					
20	7.57	1.59					
50	9.81	1.69					
150	12.70	1.99					
250	15.47	2.78					
500	25.38	2.90					
1000	35.43	3.97					
2000	63.49	4.76					
3000	91.14	OA					
EDUCATIONAL METERS							
Front finger screw							
Terminals 78x98mm							
0-10A DC - £3.98							
0-30V DC - £3.98							
50 p&p							
PLEASE ADD 15% VAT TO ALL ITEMS AFTER P&P							
MINIATURES							
Sec V	Amp	Price	P&P				
3-0-3V	0.2	3.26	.96				
6x2	1Ax2	3.12	1.30				
0-0-9	0.1	2.72	.96				
9x2	0.33x2	2.53	.96				
8-9x2	.5x2	3.53	1.30				
8-9x2	1Ax2	4.48	2.31				
15x2	.2x2	2.53	.96				
12-0-12	.05	3.11	.96				
20x2	.15x2	3.55	1.30				
20x2	.15x2	3.55	1.30				
15-20x2	9A	4.34	1.70				
15-27x2	5	5.88	1.70				
15-27x2	1A	7.66	5.50				
0-CTx15V	5	2.66	.96				
0-CT-15V	4A	7.28	1.08				

CIRCLE 41 FOR FURTHER DETAILS.

OFF THE SHELF POWER FROM DANNELL




Laboratory PSU 2302

- Dual PSU 2 x 30V/240V AC
- Built in pulse generator
- Fixed voltage/Current supply 5V/1A



Photomultiplier PSU DM4

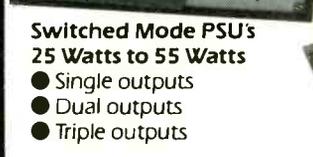- Highly stable voltage to 3kV
- Very low ripple and noise
- Remote control input



Switched Mode PSU's
25 Watts to 55 Watts

- Single outputs
- Dual outputs
- Triple outputs



Dannell Electronics Limited

For Comprehensive Data Pack & Price List Circle 23

Another Quality Product from Dannell

SALES DESK ☎ 0376 47415

Dannell Electronics Limited
 Unit 27, Business Centre, Hay Lane, Braintree, Essex CM7 6ST
 Telephone: Braintree (0376) 47415 Telex: 995801 GLO TLX-G-D14

CIRCLE 23 FOR FURTHER DETAILS.



Power supplies

Our brief introduction to supply technology is followed by information on a wide range of current bench supplies.

On hearing the words power supply, one immediately forms an image of a box containing a mains transformer, bridge cell and capacitor. After all, the majority of instruments and appliances still use this well-worked formula albeit with a few enhancements like a three-terminal regulator i.c. — the conventional linear power supply.

But a power supply need not necessarily supply d.c. More importantly, other techniques for converting mains power have progressed significantly in recent years because of the need for smaller units and higher efficiency. These efficient power supplies vary considerably in design, but they all use power switching of one kind or another. Despite what some designers might say to obscure the issue, being regulated by switching circuits they are all switch-regulated supplies.

The two basic types of switch-

ing regulator are primary switching types, in which mains voltage to the primary winding of a transformer is switched, and secondary types which switch output from a transformer secondary winding. Unlike linear regulators, which are essentially power dividers, a switching circuit designed as a power converter can give an output voltage which is higher than its input voltage.

Primary switch-regulated supplies are smaller and more efficient than secondary types, mainly because they only need a small high-frequency isolating transformer. Their drawbacks are the need for high-voltage medium-frequency switching power transistors and the fact that a large part of the circuit is at mains potential. Regulation is obtained by feeding back output voltage to the mains switching circuit so mains isolation is required between the transfor-

mer primary and secondary and in the feedback circuit.

Switching regulators are not a new concept, but they have not been common until recently. Component prices have had something to do with this but the components concerned are now widely available and reasonably priced. Good switching regulators require fast power transistors and diodes, high-quality smoothing inductors and high-frequency capacitors. The main reason for the switching regulator's slow appearance is probably complexity. A reliable, electrically quiet switch-regulator is difficult to design.

Television sets have had switching regulators in them for some years now. Our tv-repair expert calls them 'the service engineer's nightmare', which helps to confirm their complexity. They took over from a most inefficient power source — a potential divider — and power

consumption in large colour tv sets has quartered. Obviously using semiconductors instead of valves has allowed this power reduction, but comparing like with like, a potential divider supplying 12V at 1A in a modern set would waste more power than one supplying 200V at 1A in an older valve tv. Efficiencies of around 90% are possible using switching regulators.

There are applications though where switching regulators will not be seen for a few years yet. High-fidelity power amplifiers are possibly the best argument for linear power supplies. A switching regulator here would cause switching noise directly in the amplifier, it could cause r.f. noise problems, and its regulation would be worse than that of a linear supply because of the amplifier's widely varying current demand, especially during music transients.

Linear supplies have a wide dynamic range and their inefficiency is not so much of a problem with modern push-pull power amplifiers. They are also more able to withstand abuse than switching regulators and there are numerous ways of protecting linear supplies against short circuits.

When a switching regulator starts up, extremely high currents must be switched by the

★★ NI-CAD BARGAINS ★★

Ex-equipment but little-used, re-chargeable Nickel-cadmium batteries at fraction of L.P.
DEAC Type 1000DK 6 Cell Button-stack (7.2V) Measures 2½x2" Diam. Capacity 1AH. Price each £3 - inc vat (pp 25p)
DEAC Type 600DK 3 Cell Button-stack (3.6V) Measures 1½x1" Diam. Capacity 600mAh. Price each £1.50 inc vat (pp 25p)



★★ STEPPER MOTORS ★★

Brand new stock of 'ASTROSYN' Type 20PM-A055 stepper motors. 28V DC. 24 steps per rev. 15 oz-in torque @ 100PPS. Body length 2½" diameter 2", shaft ¼" diam x 4¼" spirally threaded. Weight 16oz. Price each £11.50 (p&p 50p). Connections supplied. INC. VAT

PANTEC 'BANANA' MULTI-METERS

We are agents for the Pantec range of instruments including the famous 'BANANA' meter illustrated. FULL ONE YEAR GUARANTEE. LOWEST U.K. PRICE only £25 inc VAT & carriage. Brief spec as follows 20kOhm/v. DC. 10kOhm/v. AC. Resistance x1, x100, x1000ohm. 5 range DC/V. 3 range AC/V. DC Current to 2.5A. Send s.a.e. for full specifications.



DATRON Model 1051 DIGITAL VM



1051 Multi-function digital voltmeter (DC) with Options fitted for AC Volts and Resistance. Total list is over £2200. Little used condition. £750.

★★ CROSS-HATCH GENERATORS ★★

LABGEAR COLOURMATCH CM6004PG
UHF television pattern generators giving cross-hatch, dot and gray scale patterns. Fully tested and guaranteed. NOW JUST £20 inc VAT & p&p

LABGEAR COLOURMATCH CM6010RG Gated Rainbow colour pattern generators. Cross-hatch/dot & gated rainbow (RGB) colour bar patterns. £65 inc


UNADHM E0684 PAL Colour-bar & pattern gen. £275+

KORTING 82512 PAL/NTSC Colour & pattern gen. 275+

Mail Order customers please add £2.50 postage each item.



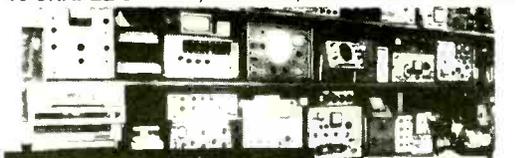RALFE · ELECTRONICS
10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753



'OSCILLOSCOPES'

TEKTRONIX 454 Dual-trace 150MHz sweep delay £650
TEKTRONIX 453 Dual-trace 50MHz sweep-delay £500
TELEQUIPMENT D75 Dual-trace 50MHz Delay £400
TELEQUIPMENT D63 15MHz Dual & Differential. £300
TELEQUIPMENT DM63 as above + STORAGE £500
SONY/TEK 335 35MHz Dual-trace portable £1K
HEWLETT-PACKARD 1707A Dual-trace 75MHz £700
HEWLETT-PACKARD 141A 20MHz Storage £350

1000 WATT AUDIO AMPLIFIERS

H & H PROFESSIONAL AUDIO POWER AMPLIFIER MODEL S500-D available ex-stock in superb, little-used condition at vastly reduced price. Specification includes Dual-Channel 500-500W. THD 0.005% IMD 0.02%. Output impedance 2.5-16ohms. Frequency response: ±1db 10Hz-20KHz. (NB: For industrial applications these amps can be configured to DC response). Forced air cooled dissipators for reliability and cool operation. Size 19" Rack mount x 3.5" Ht. PRICE JUST £275 inc vat & handbook. Carriage + £5. (NB: List price over £700.)

★ 125W MAINS INVERTERS ★

12V DC Battery Input to 230V AC. Output @ 125 watts crystal-controlled 50Hz time-base oscillator, fully enclosed in blue-steel cases with integral 13A socket. Dimensions approx. 4x6x10" BRAND NEW £60 inc VAT & Carriage.

MAINS CONDITIONS

Small quantities available of the following constant-voltage transformers at surplus prices.
ADVANCE MT140A 230V 150W £20 + vat (pp £2)
GOULD ECVN' 220V 250W £45 + vat (pp £3)
GOULD TCVN' 220V 1500W £95 + vat (pp £5)
CETRONIC REGUVOLT' 220V 3KW £350 + vat (pp £10)

MARCONI TEST EQUIPMENT

Fully re-conditioned test equipment, 90-day guaranteed.
TF9956/5 AM/FM SIGNAL GENERATOR 0.2-220MHz £500
TF1245 Q-METER WITH OSCILLATORS 1246 & 7 £1
TF2002 AM/FM SIGNAL GENERATOR 01-72MHz £550
TF893A AUDIO POWER METERS TO 10W £85
TF2905 SINE SQUARED PULSE & BAR GENERATOR £250
TF2604 ELECTRONIC VOLTMETER £150

EDDYSTONE Communications receivers
770R/1 Covering 19-165MHz &
770U/2 Covering 150-500MHz

COMPANIES PLEASE NOTE that we would be very pleased to receive your invitation to tender for your surplus or redundant equipment. Contracts offered for factory contents removals on regular basis

★ COMPUTER PERIPHERALS ★

1.6MB 8" FLOPPY DISC DRIVES — New Stock

BRAND NEW At a surplus price. Fully Shugart compatible 'MFC CORPORATION' Model M-700 DOUBLE-SIDED industry standard 8" floppy disc drives. Double-density, up to 1.5MBytes. Power requirements ±5V and +24V @ 1.1A. 240V AC 50Hz. LOWEST PRICE EVER. £160 — INC. VAT. CARRIAGE & HANDBOOK.

ORE 4000A DRIVES

Data Recording Equipment Model 4000A 5 + 5 MB Top-loading disc drives in stock. Brand new including full technical manual. Few remaining £250 each + VAT. SHUGART 8" Flexible disc drives model SA800. Condition as new £150 + VAT (Including postage and handbook copy).

★ MULTI-RAIL LINEAR PSU's ★

Recent stock of brand new COUTANT ESM-Series Power Supplies at surplus prices. Model ESM15.2 giving regulated, stabilised DC outputs 5V @ 15A and ±12V to ±15V @ 1.5A each and an un-stabilised 24V @ 2A. 240V AC input. Measures 5-8x11". Fully enclosed. In original cartons with handbooks. £45 each + VAT (+ carriage £5)

COUTANT LINE SUPPLIES:
MODEL ASA2000. 5V. 20A. £35
MODEL ASC300. 24V. 2A. £20
(inc vat. pp £4 & £2 respectively)

★ SWITCH-MODE POWER SUPPLIES ★

Fully tested and guaranteed PSU's now at LOWEST EVER PRICES. Manufactured by FARNELL, GOULD/ADVANCE.
5V @ 10amps £18
5V @ 20amps £20
19V @ 15amps £35
12V 16A (110V in.) £20
5V @ 60amps £35
12V @ 15amps £40
HEWLETT-PACKARD 5V DC @ 100A. Brand new. £125.

All prices now include VAT, packing and posting.

★ CENTRIFUGAL BLOWERS ★

TORIN Type U62B1. 230V Cap/Start (supplied), very powerful (200W, 3000 rpm) centrifugal fans for large rack cooling or enclosure extractive applications. Overall dimensions 20x12 cms, outlet 6x4 cms. BRAND NEW. Surplus stock. £15 each inc. VAT, p&p £1.50.

★ INSTRUMENT COOLING FANS ★

All fans available ex-stock and GUARANTEED
230V 10W 5-Blade 3½x3½" NEW £7
115V 13W 5-Blade 3½x3½" NEW £6
115V 4½x4½" 5-Blade NEW £6
115V 7W 4½" 3-Blade WHISPER £5
230V 40W Papst 350M/Hr. Ex-equip. £13

All prices include VAT (pp - 50p)

CIRCLE 49 FOR FURTHER DETAILS.

Valradio

AC-DC Power Supplies
Input 200-250V. 50Hz or 100-120V 60Hz to order.
Output 1.0-30V. 25A. D.C. Output 2:0-70V. 10A. A.C. Output 3:0-250V 4A. AC.

ALL CONTINUOUSLY VARIABLE
Other units are also available with outputs of:
0-60V 12A 0-120V 6A 0-240V 3A
Fixed output models, 12, 24 or 50V

AC-AC Frequency Changers
For changing 60Hz AC mains to 50Hz or 50Hz mains to 60Hz. Input 100-127V or 200-250V, 50 to 400Hz, Single Phase. Output 100-127V or 200-250V, Single Phase. Six different models are available; 60, 120, 200, 300, 500 or 1000VA. Also special fixed/variable frequency models available.

DC-DC Converters
Isolate DC input from DC output. To provide DC output levels different than that of DC input

VALRADIO POWER LIMITED
AK INTERNATIONAL BUILDING, LAWRENCE ESTATE,
GREEN LANE, HOUNSLOW, MIDDX TW4 6DU.
ENGLAND. Tel: 01-570 5622
TACKLING POWER SUPPLY PROBLEMS SINCE 1937

CIRCLE 24 FOR FURTHER DETAILS.

First Castle Power

1ST FOR PRICE FOR QUALITY FOR SERVICE

MAINS ADAPTORS
POWER SUPPLIES — LINEAR/SWITCHMODE
DC/DC CONVERTERS — BATTERY CHARGERS

Manby Electronics Ltd, a subsidiary of FIRST CASTLE ELECTRONICS PLC, specialise in the design and production of a wide range of power supplies. From simple plug in Mains Adaptors to complex multi-output Switch Mode types

RING (050782) 8031
TELEX 56268
for a 24 HOUR quotation
(slightly longer for unusual designs)

7 DAY SAMPLE SERVICE FREE OF CHARGE

MANBY ELECTRONICS LTD.
MANBY PARK,
LOUTH, LINGS,
TEL (0507 82) 8031 **TELEX 56268**

CIRCLE 66 FOR FURTHER DETAILS.

POWER SUPPLIES

Further reading

Regulated Power Supplies by Irving M. Gottlieb, Sams, £18.50. The third edition of this book contains information about switching and linear supplies and includes plenty of applications ideas.

power device until the output filter capacitor is charged. At switch on, input to the switching circuit climbs from zero and the pass transistor can cope with charging the output capacitor (some switching regulators have a 'soft-start' circuit which allows the capacitor to charge slowly at switch on). If the output is shorted however and the pass transistor survives, it will almost surely fail when the short is removed as the power circuit has to charge the output capacitor from zero with a fully-on input voltage. Any protection circuit included must be very fast as the switching rate of most supplies is between 20 and 40kHz.

Linear regulated power supplies are also more practical in applications requiring variable voltage and current, such as a low-voltage bench power supply. Switch-regulators, although tolerant of input fluctuations, do not lend themselves to variable output. Efficiency in a switch-regulated supply can fall rapidly when the load falls outside design parameters or when one circuit is used to give different output voltages.

So far only linear and switching power supplies have been mentioned. An often overlooked form of power supply (possibly because of its price) is the ferrite-resonant transformer, which has been around for 50 years. It offers around 1% regulation, between 80 and 90% efficiency, inherent short-circuit protection and transient filtering, and an almost square-wave output which requires little smoothing when rectified. The so-called constant-voltage transformer makes for a low component-count supply and lends itself to computer power applications because of its rejection of mains faults.

Basically, this type of transformer has a secondary or tertiary winding (or combination of the two) which, in conjunction with a

Characteristics of bench power supplies available on the UK market.

MAKE	TYPE	D/PV	D/PI	RIPPLE	R-LOAD%	R-LINE%	D/P R	FL	CL	CV	CC	V	I	C	PRICE	REMARKS	
Bang & Olufsen	SN16A	30	1	100µV	0.05	0.15	0.005	*	*	*	*	*	*	*		overload protected	
		30	1	100µV	0.05	0.15	0.005	*	*	*	*	*	*	*		"	
		5	3	50µV	0.15		0.003	*	*	*	*	*	*	*		"	
	SN17	30	2	<100µV	0.015	0.01	0.002	*	*	*	*	*	*	*		"	
	SN18	60	1	<100µV	0.015	0.01	0.002	*	*	*	*	*	*	*		"	
Beha	NG303	30	3	<10%	<2	<1	0.005	*	*	*	*	*	*	digital		Dvm may be used separately	
	NG306			Double version of above													
Bertan	214	1000	15mA	15mV	0.005	0.001		*					*			Programmable	
	215	3000	5mA	15mV	0.005	0.001		*					*			"	
	205A-01R	1000	30mA	10mV	0.005	0.001		*					*			"	
	205A-50PN	50000	0.3mA	2V	0.005	0.001		*					*			Programmed. Analogue, binary or GPIB	
Coutant	LC60	30	2	2mV	<0.05	<0.01	0.01	*	*	*	*	*	digital	145		Dvm can be used externally	
	LCT60			1mA	<1mA	<0.01	>30k								290		Outputs track
				Dual version of LC60													
Daren	DPM4	3000	6mA	<10mV	0.01	0.001							*			Remote control. For photomultipliers.	
Elcanic	212	25	3	5mV	0.01	0.01							*			A.c. outputs 4-24V at 5A	
	215	25	5	5mV	0.01	0.01							*			"	
	301	25	10	5mV	0.01	0.01							*			"	
	2302	30	2	1mV	0.01	0.01							*			A.c. o/ps. 1Hz t.t.l. pulse gen	
		30	2														
		5(fixed)	1														
	300	25	10											*			
	500	0.1											*				
	6a.c																
	12a.c.																
Delta	SM3540	35	40	10mV	5mV	5mV	<0.05	*	*	*	*	*	*			Soft start. Remote sensing. OV protected. Programmable.	
	SM6020	60	10	10mV	5mV	5mV	0.01	*	*	*	*	*	*			Soft start. Remote sense. Programmed by 0-5V.	
		30	20	50mA	70mA	70mA											
	or																
	EK30-10	30	10	1mV	10mV	1mV		*	*	*	*	*	*			Programmable. Protected.	
					5mA	10mA	3mA										
	E015-2	15	2	0.1	2mV	1mV	0.1	*	*	*	*	*	*				
	E030-1	30	1	0.1	4mV	2mV	0.1	*	*	*	*	*	*				
	E0303	30	3	0.1	4mV	2mV	0.1	*	*	*	*	*	*				
	E060-0.6	60	0.6	0.1	8mV	4mV	0.1	*	*	*	*	*	*				
E0300-0.1	300	0.1	0.5mV	20mV	10mV	0.01	*	*	*	*	*	*					
E018-0.60	+/-18	+/-0.6	0.1mV	5mV	5mV	0.1	*	*	*	*	*	*				For op-amps. Tracked.	
Electronic Measurements	HCC7.5-30	7.5	30	100mV	0.1	0.1		*	*	*	*	*	*			Soft start. Programmable. S.c.r.	
	HCR300-0.9300		0.9	650mV				*	*	*	*	*	*				
Farnell	E30/1	30	0.5	<1mV	<0.03%	<0.02%	0.04	*					*	89		Switch-selected V range.	
		or															
		15	1														Overload protected
	E30/2	30	1											102			
		or															
		15	1														
	ET30/2	30	1											191		Dual outputs	
		30	1														
		or															
		15	2														
		15	2														
	L50/05	50	0.5	<1mV	<0.01%+2mV		0.1		*	*	*	*	*	121			
					Other models to:												
	L12/10C	12	10	"	"	"	"		*	*	*	*	*	260		Crowbar protected.	
	O30/2	30	2	<2mV	<0.01%+2mV		0.002		*	*digital				145		Digital meter usable externally	
				0.01%+1mA													
D30-2T	30	2						*	*digital				281		Dual unit		
	30	2															
D30-4	30	4						*	*digital				265				
D100-1	100	1						*	*digital				260				
TOPS 1	4-6	1	<2mV	0.1%+5mV	.05%+2mV	<0.05		*					104		Overload protected. No meters-cal. pots.		
	12-17	0.2															
	12-17	0.2			0.05%+2mV												
TOPS 2	4-6	5						*					176		"		
	12-17	1															
	12-17	1															
TOPS 3	4-6	4	<2mV	0.02%+5mV	.05%+2mV			*	digital				219		Digital metering. Over-voltage protection.		
	5-17	1															
	5-17	1															

POWER SUPPLIES

MAKE	TYPE	O/PV	O/P1	RIPPLE	R-LOAD%	R-LINE%	D/P R	FL	CL	CV	CC	V	I	C	PRICE	REMARKS
	TSV 70	70	5	<1mV	0.01%+1mV	.01%+1mV	.05	*	*	*	*	*	*	*	530	Switch-selected output.
		or														
	E350	350	0.2	<5mV	<0.5%	<0.1%		*	*	*	*	*	*	*	333	Remote sensing. Overload protected.
HEWLETT PACKARD	Much too large a range to accommodate here. From 30W to several kW. Single and multiple outputs. simple bench types and complex, programmable instruments. Small part of range as follows															
	6214B	10	0.1	200µV	4mV	4mV	.005	*	*	*	*	*	*	*		6200 & 6209 autoseries, auto-parallel, autotracking, programmable.
					500µA	750µA										Single, dual range
	6200B	20	1.5	"	4mV	4mV	.02	*	*	*	*	*	*	*		
		or			250µA	250µA										
	6216B	25	0.4	"	4mV/.5mA	4mV/.5mA	.02	*	*	*	*	*	*	*		
	6206B	30	1	"	4mV	4mV	.04	*	*	*	*	*	*	*		
		or														
	6218B	50	0.2	"	4mV	4mV/500µA	.04	*	*	*	*	*	*	*		Single, dual range output
	6212B	100	0.1	"	8mV	"	.08	*	*	*	*	*	*	*		
	6209B	320	0.1	1mV	2mV	2mV/200µA	.02	*	*	*	*	*	*	*		
	6205C	20	0.6	200µV	4mV	4mV	.025	*	*	*	*	*	*	*		Programmable, autotracked
		or														
		40	0.3													
		and														
		20	0.6													
		or														
	6234A	25	0.2	200µV	1mV	1mV		*	*	*	*	*	*	*		
		25	0.2													
Hunting Hivolt	Series 650	1-10k	0.025	<0.05%	<0.05%	<0.02%		*	*	*	*	*	*	*	1789	Switched mode, high voltage to remote control, monitor.
	6 models	to													2025	
		5-50k	0.005												8590	External high voltage to discs.
	Series 4000	50k	0.08	<0.05%	1%	0.02%		*	*	*	*	*	*	*	11661	
		to														
		150k	0.024													
	Series 2000	2.5-25k	0.08	<0.02%	0.05%	0.02%									4467	Separate h.v. system to
		to													8824	
		20-200k	0.01													
Keithley	Several programmable current and voltage sources, plus:															
	247	3k	0.006	3.5mV	0.005%	0.001%		*	*	*	*	*	*	*		Overload protected.
Kepeco	Very large range of instruments--summarized only															
	BOP50-2M	+/-50	+/-2	1mV	0.001%	0.0005%	0.0005	*	*	*	*	*	*	*		6PIB programmable. 4-quadrant volts/current stabilized
	12 models	to			0.5mA	0.002%	50k									
	BOP1004M	+/-100	+/-4	"	"	"	"	*	*	*	*	*	*	*		
	MPS620M	6	5	0.1mV	0.01%	0.01%		*	*	*	*	*	*	*		Remote sensing.
		20	1	"	"	0.05%		*	*	*	*	*	*	*		20V outputs track.
		20	1	"	"	"		*	*	*	*	*	*	*		
Kikusui	PADL/LP	8	20	0.5mV	.005%+1mV	.005%+1mV		*	*	*	*	*	*	*	634	Overload protected.
	48 models	to														Remote programming.
	PAD1k-0.2	1k	0.2	0.5mV	.002%+5mV	.002%+5mV		*	*	*	*	*	*	*	1865	Series or parallel.
				0.05mA	0.1mA	0.1mA										
	PAE35-10	35	10	0.2mV	1mV	1mV		*	*	*	*	*	*	*	875	Programming speed up to 35V/µs
				1mA	2mA	0.5mA										
	3 models	to														
	PAE35-30	35	30	0.4mV	1mV	2mV		*	*	*	*	*	*	*	1575	
				5mA	3mA	1mA										
	PAC7-10	7	10	0.5mV	0.03%	.005%+1mV		*	*	*	*	*	*	*	428	
	8 models	to														to
	PAC110-1	110	1	"	"	"		*	*	*	*	*	*	*	400	
	PABB-2.5	8	2.5	0.5mV	.02%+2mV	.02%+2mV		*	*	*	*	*	*	*	143	Simple bench supplies.
	17 models	to														to
	PAB350-0.2	350	0.2	"	"	"		*	*	*	*	*	*	*	184	
	PDM1B-2.5	+1B	2.5	0.5mV	.005%+2mV	.005%+1mV		*	*	*	*	*	*	*		Dual tracking, +and- can be set
	-1B															
	5 models	to														
	7034	+60	0.5	0.5mV	3mV	3mV		*	*	*	*	*	*	*		
		-60														
Lambda	LA-200-V	16.5	4	60mV	20mV	20mV		*	*	*	*	*	*	*	149	T.t.l. on/off. Protected.
	LA-300-V	16.5	7	"	"	"		*	*	*	*	*	*	*	173	
	LA-250-V	32.5	2	"	"	"		*	*	*	*	*	*	*	149	
	LA-350-V	32.5	3.5	"	"	"		*	*	*	*	*	*	*	173	
	LB 701	7.5	270	15mV	.1%+10mV	.5%+6mV		*	*	*	*	*	*	*	4450	Programmable. Rack or bench
				<1/VZ	1Z+10mA	1Z+6mA										

capacitor, acts as a tank circuit. The core is separated magnetically into two sections by a magnetic shunt; the section with the tank circuit is resonant at the mains frequency and saturates, but the primary section does not. Energy is transferred between the two sections proportionally with input level and output load to provide constant voltage. The resonator is not strictly an LC one as it involves magnetism in the core, hence the term ferroresonance.

Glossary

Automatic recovery. Some supplies need resetting after being overloaded. One which returns to normal output when the overload is removed has automatic recovery.

Bipolar supply. Usually used to describe a supply whose output can travel from positive to negative and vice-versa, rather than one with separate positive and negative outputs or one with transistor drivers.

Bridge circuit. This term not only used to describe a diode configuration in a rectifier circuit but also a bridge driver circuit in switch-regulated supplies.

Brown-out. This is an input voltage level at which the supply still functions, but not necessarily within its specification. Derived from the American term for the practice of dropping mains voltage to reduce demand.

Common-mode output. Current through an impedance connected between the ground terminal to which the supply output is returned and a separate ground terminal.


Complementary tracking. Some supplies may be connected together so that the output of one tracks the output of the other.

Converter. In some applications, a d.c. supply higher than the one available is required. Rather than use a separate power supply, a d.c.-to-d.c. converter is used to step up voltage from the existing supply.

Crowbar protection. For expensive circuits sensitive to overvoltage, such as found in a computer, crowbar protection is often used to sense an overvoltage condition and drag down the supply using a shunt element like a thyristor to blow the fuse. It is a cheap means of protection for situations where overvoltages might occur. If overvoltage will occur, a less terminal means of shutdown is preferred.

Current mode. Some supplies have linear and adjustable current limiting and are designed to run indefinitely with the current limiting on. As load increases, voltage drops proportionally while the current-limit point is exceeded. This mode has numerous applications like zener-diode, led and diode testing, and can even be used to estimate the size of a large capacitor. Such a supply can also be used as a constant-current load for experimentation.

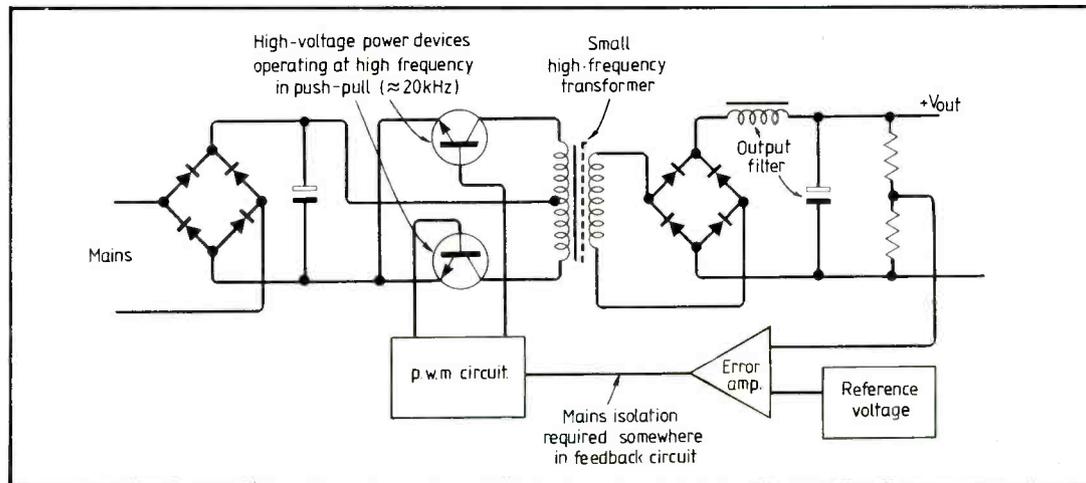Primary-type switching regulator using p.w.m. and push-pull driving transistors. Being high-frequency components, the mains transformer and filtering elements are much smaller than usual. This type of regulator is highly efficient but mains isolation is required both in the transformer and feedback loop. Some primary switching regulators use a single-ended drive stage.



CVT, constant-voltage transformer, see text.

Digital control. Many supplies are now capable of being controlled digitally either by a dedicated controller or by a computer through say a GPIB interface or a slower RS232 serial link. Digital control is used in automatic testing, process control and in laboratories. Much of the power-control circuit may be digital, even though the supply may act in the same way as a conventional linear one. In this case analogue-to-digital and digital-to-analogue converters are used. **Dual tracking supply.** A supply with interdependent positive and negative output voltages.

EMI. Electromagnetic interference is generated by switching supplies. Without adequate screening and filtering, this can affect surrounding circuits, the mains supply and the power supply output.

Ferroresonance (see text)

Foldback limiting. Protection circuit which actively reduces current supply as overload increases. This avoids overheating the supply and damaging any circuit connected to it during overload, but unless the supply has a separate linear current regulator, it cannot be used in constant-current applications.

GPIB (IEEE488, IEC625-1, HPIB, etc.). More and more supplies designed for computer control are becoming available. GPIB — for general-purpose interface bus — is a widely used standard means of connecting instruments to a computer and most manufacturers use it. Its drawbacks are that it is quite expensive to implement and that the standard does not define how the control software should be written (see our March issue).

Inverter. An apparatus for converting d.c. into a.c. Often used for providing mains voltage from a car battery either in remote areas or locally for battery back-up. Unlike the uninterruptible power source, an inverter does not necessarily switch in automatically, and even if it does, at least a few mains cycles will be lost.

Line regulation. Expression of a supply's tolerance to input-voltage fluctuation. Assuming constant load conditions, line regulation is the output-voltage maximum deviation measured while varying the load from

MAKE	TYPE	D/PV	D/PI	RIPPLE	R-LOAD%	R-LINE%	D/P R	FL	CL	CV	CC	V	I	C	PRICE	REMARKS
															4600	
	LES	7.5	57	10mV	.02%+2mV	.02%+2mV		*	*	*	digital				1175	Remote sense. Switched mode.
					0.5%	.5%+50mA									1500	
	LK	20	7.2	500µV	0.15%	0.15%		*	*	*	*	*	*		980	Programmable
					10mA	10mA									2740	
															2740	
	LP	20	17	500µV	0.1%+1mV			*	*	*	*	*	*		745	Single, dual and triple. Programmable
		20	17												to	
		250		0.13	0.2%										840	
		250		0.13	5mA											
		10	18												395	
		to													to	
		250	72												685	
	LA	10	18		0.05%+0.5mV			*	*	*	digital				505	Programmable. Single and dual.
		to													to	LA 10 Auto series/parallel.
		250	0.072		2.5mA	1mA									570	
		10	12.6												770	
		to													to	
		120	1.5												885	
		20	1.36												850	
		20	1.36												to	
		250	0.1												940	
		250	0.1													
	LT	7	135	10µV	.02%+2mV	.02%+2mV									1725	Programmable. Switched mode.
		to			or	or									to	
		60	19.3	15µV	0.3%	0.3%		*	*	*	digital				1825	
		7	270												3360	
		to													to	
		60	45												3420	
Linstead	S 10	30	2	<300µV		<0.01%	<0.005	*	*						* 306	Remote sensing.
		30	2													
	S 14	5	1	<5mV		<0.3%		*							67	
Philips	PE1535	40	0.5	<1.5mV	<40mV	<0.05%	0.02	*	*	*	*	*	*		* 137	Remote programming and sense.
				<1mA	<4mA	<2.5mA										
	PE1536	20	2	<1mV	<10mA	<0.01%	*	*	*	*	*	*	*		* 239	
				<2mA	<3mA	<0.05%										
	PE1537	40	1	<1mV	<15mV	<0.01%	*	*	*	*	*	*	*		* 239	
				<1mA	<3mA	<0.05%										
	PE1538	75	0.5	<1mV	<25mV	<0.01%	*	*	*	*	*	*	*			
				<1mA	<3mA	<0.05%										
	PE1539	20	6	<1mV	<12mV	<0.01%	*	*	*	*	*	*	*		373	
				<2mA	<4mA	<0.05%										
	PE1540	40	3	<1mV	<18mV	<0.01%	*	*	*	*	*	*	*		373	
				<1mA	<4mA	<0.05%										
	PE1541	75	1.6	<1mV	<30mV	<0.01%	*	*	*	*	*	*	*		373	
				<1mA	<4mA	<0.05%										
	PE1542	7	3	<0.5mV	<7.5mV	<0.05%	*	*	*	*	*	*	*		411	
				<1.5mA	<4mA	<0.5%										
		20	1	<1mV	<20mV	<0.05%	*	*	*	*	*	*	*			
		20	1	<0.5mA	<4mA	<0.5%										

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

RECHARGEABLE BATTERIES

Dry Fit Maintenance FREE by Sonnenschein.
A300 07191315 12v 3 AH same as RS 591-770 NEW £13.95 A300 07191202 6-0-6 1.8 AH same as RS 591-382 EX EQUIP £4.99 Miniature PCB mount 3.6v 100 Mah as RS 591-477 NEW £1.00 SAFT VR2C 12v 'C' size NICADS in 18 cell equipment pack. Good condition - easily split to single cells £10.50 + pp £1.90

EX-STOCK INTEGRATED CIRCUITS

2732 ex equip £3.25. 27128 - 250ns NEW £12.00.
6116-200 £4.50. 6116-250 £3.95.
6264LP-150 £22.00. 4164-200 £3.50. 4864-150 £4.00.
4116-300. £1.20. 2114 £1.75. 6800 £2.50. 6821 £1.00.
68A09 £8.00. 68B09 £10.00. 68B09E £14.50.
D8085AH-2 £12.00. D8086 £20.00. Z80A £2.99.

HOT LINE DATA BASE

DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base
1000's of stock items and one off bargains.
ON LINE NOW - 300 baud, full duplex CCITT tones. 8 bit word. no parity
01-679 1888

MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference
SD5A As recommended by ZX81 news letter matchbox size up to 1000 watt load **£5.95**
L2127 compact completely cased unit with 3 pin fitted socket Up to 750 watts **£9.99**

Anderson Jacobson

AJ510 VIDEO DISPLAY TERMINAL



Made by one of the USA's largest peripheral manufacturers the AJ510 Professional VDU terminal has too many features to include in space available - just a few are:
internal Z80 cpu control, very readable 15" non glare green screen, 24 lines by 80 characters, 128 ASCII character set with lower case and graphics, standard RS232 interface, Cursor addressing, numeric key pad etc. Supplied in good TESTED second hand condition with full manual **£225.00 + carr £10.00.** Data sheet on request.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 90X90 Dim. 92 x 92 x 25 mm Miniature 240 v equipment fan complete with finger guard. **£9.95.**
GOLDB JB-3AR Dim 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £8.95**
BUHLER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost **£32.00. OUR PRICE ONLY £12.95** complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans **£1.60**

BUDGET RANGE VIDEO MONITORS

At a price YOU can afford, our range of EX EQUIPMENT video monitors defy competition!! All are for 240v working with standard composite video input. Units are pre tested and set for up to 80 col use on BBC micro. Even where MINOR screen burns MAY exist - normal data displays are unaffected.

1000's SOLD TO DATE

12" KGM 320-321, high bandwidth input, will display up to 132 columns x 25 lines. Housed in attractive fully enclosed brushed alloy case. B/W only **£32.95**
24" KGM large screen black & white monitor fully enclosed in light alloy case. Ideal schools, shops, clubs etc. **ONLY £55.00** Carriage £10.00

A Major company's over production problems, and a special BULK PURCHASE enable TWO outstanding offers.



COLOUR MONITOR SPECIALS

'SYSTEM ALPHA' 14" Multi Input Monitor.

Made in the UK by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future monitor requirements. Two types of video input, RGB and PAL Composite Video, allow direct connection to most makes of micro computers and VCR's. An internal speaker and audio amplifier may be connected to your system's output or direct to a VCR machine, giving superior colour and sound quality. Many other features include PIL tube, Matching BBC case colour. Major controls on front panel, Separate Contrast and Brightness - even in RGB mode, Two types of audio input, Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc. etc.

This must be ONE OF THE YEAR'S BEST BUYS!!

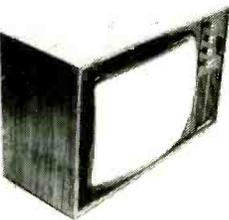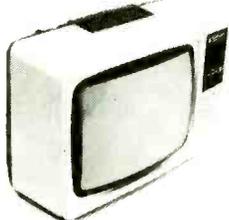Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. SUPPLIED BELOW ACTUAL COST - ONLY **£149.00 + Carr.**



DECCA RGB 80-100 Monitor.

Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only **£99.00**, a price for a colour monitor as yet unheard of!! Our own interface, safety modification and special 16" high definition PIL tube, combine with the tried and tested DECCA 80/100 series chassis to give 80 column definition and picture quality found only on monitors costing 3 TIMES OUR PRICE. In fact, WE GUARANTEE you will be delighted with this product, the quality for the price has to be seen to be believed. Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features include internal audio amp and speaker, Modular construction, auto degaussing 34 H x 24 D, 90 day guarantee. Supplied in EXCELLENT condition, **ONLY £99.00 + Carr.** Also available UN-MODIFIED but complete with MOD DATA. Only **£75.00**. Carriage and Insurance on monitors **£10.00**

DATA MODEMS

Join the communications revolution with our super range of DATA MODEMS with prices and types to suit all applications and budgets!!

Most modems are EX BRITISH TELECOM and are made to the highest standard for continuous use and reliability. RS232 interfaces are standard to all our modems, so will connect to ANY micro etc. with an RS232 serial interface.

DATTEL 2B see SPECIAL OFFER centre of this ad

MODEM 13A. 300 baud. Compact unit only 2" high and same size as telephone base Standard CCITT tones. CALL mode only. Tested with data. **ONLY £45.00 + PP £4.50**

MODEM 20-1. 75-1200 baud. Compact unit for use as subscriber end to PRESTEL, MICRONET or TELECOM GOLD. Tested with data. **£39.95 + PP £6.50**

MODEM 20-2. same as 20-1 but 1200-75 baud **£99.00**

TRANSDATA 307A. 300 baud acoustic coupler. Brand new with RS232 interface. **ONLY £49.95**

DACOM DSL2123 Multi Standard Modem, switchable CCITT or USA BELL 103 standard. V21 300-300. V23 75-1200. V23 1200-75 or 1200-1200 half duplex.

Auto answer via MODEM or CPU. CALL or ANSWER modes plus LED status indication. Dim 2.5" x 8.5" x 9". BRAND NEW fully guaranteed **ONLY £268.00 + PP £4.50**

DATTEL 2412 Made by SE LABS for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol. Many features include Auto answer, 2 or 4 wire working etc. etc. COST OVER **£800. OUR PRICE £185.00**

DATTEL 4800. RACAL MPS4800 high speed good condition **£285.00 CARR £10.00**

SPECIAL 300 BAUD MODEM OFFER

Another GIGANTIC purchase of these EX BRITISH TELECOM, BRAND NEW or little used 2B data modems allows US to make the FINAL REDUCTION, and for YOU to join the exciting world of data communications at an UNHEARD OF PRICE OF ONLY **£29.95**. Made to the highest POST OFFICE APPROVED spec at a cost of hundreds of pounds each, the 2B has all the standard requirements for data base, business or hobby communications. All this and more!!

● 300 baud full duplex
● Full remote control
● CCITT tone standards
● Supplied with full data
● Modular construction
● Direct isolated connection



- CALL, ANSWER and AUTO modes
- Standard RS232 serial interface
- Built in test switching
- 240v Mains operation
- 1 year full guarantee
- Just 2 wires to comms line

Order now - while stocks last. Carriage and Ins. **£10.00**

SAVE £250 SUPER PRINTER SCOOP



BRAND NEW CENTRONICS 739-2
The 'Do Everything Printer' at a price that will NEVER be repeated. Standard CENTRONICS parallel interface for direct connection to BBC, ORIC, DRAGON etc. Superb print quality with full pin addressable graphics and 4 type fonts plus HIGH DEFINITION internal PROPORTIONAL SPACED MODE for WORD PROCESSOR applications 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available ONLY from DISPLAY ELECTRONICS at the ridiculous price of **£179.00 + VAT** Complete with full manual etc. Limited quantity - Hurry while stocks last.
Options: Interface cable (specify) for BBC, ORIC, DRAGON or CENTRONICS 36 way plug **£12.50**. Spare ribbon **£3.50** each BBC graphics screen dump utility program **£8.60**. Carriage and Ins. **£10.00 + VAT**

HUNDREDS OF PRINTERS

EX STOCK FROM **£49.00**. Call Sales Office for Details.

1 only large CALCOMP 1036 AO 3 pen drum plotter and offline 915 magtape controller. Good working order. **ADD VAT TO ALL PRICES £2500.00.**

EX STOCK

DEC CORNER

PDP 1140 System comprising of CPU, 124K memory + MMU 16 line RS232 interface, RP02 40 MB hard disk drive, TU10 9 track 800 BPI Mag tape drive, dual rack system, VT52 VDU etc. etc. Tested and running **£3750.00**

BA11-MB 3.5" Box, PSU, LTC **£385.00**

DH11-AD 16 x RS232 DMA interface **£2100.00**

DLV11-J 4 x EIA interface **£310.00**

DLV11-E Serial. Modem support **£200.00**

DUP11 Sych. Serial data i/o **£650.00**

DQ200 Dialog - multi RK controller **£495.00**

D211-B 8 line RS232 mux board **£650.00**

KDF11-B M8189 PDP 1123+ **£1100.00**

LA36 Decwriter EIA or 20 ma loop **£270.00**

LAX34-AL LA34 tractor feed **£85.00**

MS11-JP Unibus 32 kb Ram **£80.00**

MS11-LB Unibus 128 kb Ram **£450.00**

MS11-LD Unibus 256 kb Ram **£850.00**

MSC4804 Obus (Equip MSV11-L) 256 kb **£499.00**

PDP11/05 Cpu, Ram, i/o, etc. **£450.00**

PDP11/40 Cpu, 124k MMU **£1850.00**

RT11 ver. 3B documentation kit **£70.00**

RK05-J 2.5 Mb disk drives **£650.00**

KL8JA PDP 8 async i/o **£175.00**

M8E PDP 8 Bootstrap option **£75.00**

VT50 VDU and Keyboard - current loop **£175.00**

VT52 VDU with RS232 interface **£250.00**

1000's of EX STOCK spares for DEC PDP8, PDP8A, PDP11 systems & peripherals. Call for details. All types of Computer equipment and spares wanted for PROMPT CASH PAYMENT.

DISPLAY ELECTRONICS

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum BONA FIDE account orders from Government Depts., Schools, Universities and established companies **£20.00**. Where post and packing not indicated please ADD **£1.00 + VAT**. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

32 Biggin Way, Upper Norwood, London SE19 3XF

Telephone 01-679 4414 Telex 894502 Data 01-679 1888



ERS — PRINTERS — PRINTERS — PRINTERS PRINTERS — PRINTERS — PRINTERS — PRI

SUPER DEAL? NO — SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter

BRAND NEW AT ONLY £499 + VAT

Made to the very highest spec the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUME command compatibility and full control via CPM Wordstar etc.

Many other features include bi-directional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with up to 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information. Optional extras: RS232 data cable £10.00. Tech manual £7.50. Tractor feed £140.00. Spare daisy wheel £3.00. Carriage & Ins. (UK Mainland) £10.00.



PROFESSIONAL KEYBOARD OFFER

An advantageous purchase of brand new surplus allows a great QWERTY, full travel, chassis keyboard offer at fractions of their original costs. ALPHAMERIC 7204/60 full ASCII 60 key, upper, lower + control key, parallel TTL output plus strobe. Dim 12" x 8" +5 & -12 DC. £39.50. DEC LA34 Uncoded keyboard with 67 quality, GOLD, normally open switches on standard X, Y matrix. Complete with 3 LED indicators & i/o cable - ideal micro conversions etc. pcb DIM 15" x 4.5" £24.95 Carriage on keyboards £3.00.

66% DISCOUNT

ELECTRONIC COMPONENTS EQUIPMENT


Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.s, Transistors, Relays, Caps, P.C.B.s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the 'BARGAIN/PARCEL OF A LIFETIME'. Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.

2.5kls £4.25 + pp £1.25
10kls £10.25 + pp £2.25

5kls £5.90 + £1.80
20 kls £17.50 + £4.75



GE MODEL 30

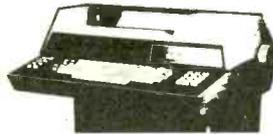

A large purchase of these stand alone terminal units offers an EXTREMELY LOW PRICE for a professional printer for direct connection to your micro. The printer has a standard RS232 serial interface with switchable rates of 110, 200 and 300 baud. Upper and lower case characters are printed by a matrix head with character widths up to 132 columns. Unit accepts standard fan fold sprocket fed paper from 4" to 9.5". Many other features such as numeric keypad, electronic keyboard, auto motor on/off and FREE floor stand. Supplied in good S/H working condition - complete with manual ONLY £95.00 CARRIAGE & INS. £10.00

GE TERMIPRINTER



A massive purchase of these desk top printer-terminals enables us to offer you these quality 30 cps printers at a SUPER LOW PRICE against their original cost of over £1000. Unit comprises of full QWERTY, electronic keyboard and printer mech with print face similar to correspondence quality typewriter. Variable forms tractor unit enables full width - up to 13.5" 120 column paper, upper - lower case, standard RS232 serial interface, internal vertical and horizontal tab settings, standard ribbon adjustable baud rates, quiet operation plus many other features. Supplied complete with manual. Guaranteed working £130.00 or untested £85.00, optional floor stand £12.50 Carr & Ins £10.00.

EXTEL PRINTERS

EX NEWS SERVICE compact, quality built 50 column matrix printer, type AE11. Unit operates on 5 BIT BAUDOT code from current loop, RS232 or TTL serial interfaces. May be connected direct to micro, or comms receiver via simple filter network to enable printing of most world wide NEWS, TELEX and RTTY services. Supplied in tested second hand condition with 50 and 75 baud xtls, data sheet and large paper roll. ONLY £49.95. Dimensions 15" D x 5" H x 10" W CARR £6.00 Spare paper rolls £4.50 each

TELETYPE ASR33 I/O TERMINALS



FROM £195 + CAR + VAT Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

20,000 FEET OF ELECTRONIC AND COMPUTER GOODIES ENGLAND'S LARGEST SURPLUS STORE - SEEING IS BELIEVING!!

D.C. POWER SUPPLY SPECIALS

Experimentors PSU Ex-GPO. All silicon electronics. Outputs give +5v @ 2 amps +12v @ 800 ma -12v @ 800 ma +24v @ 350 ma and 5v floating @ 50 ma. Dim 160 x 120 x 350 mm. All outputs are fully regulated and short circuit proof. Supplied in NEW or little used condition. Complete with circuit.

ONLY £15.50 + £2.50 pp
FARNELL 5 Volt 40 amps. Type number G6-40A. This miniature switching PSU measures only 160mm wide 175mm deep and 90mm high, yet delivers a massive 40 amps!! Fully regulated and smoothed with over voltage protection etc. 120 or 240 volts AC input. Supplied BRAND NEW and boxed with circuit at a fraction of the current list price. ONLY £130.00 + £3.00 carr & ins.
LAMBDA LMCC 5V BRAND NEW 240v AC input with 5 volts DC at 3 to 10 amps fully regulated output. Completely enclosed unit measures only 9" x 4" x 5" £29.99

LAMDA LMCC5V 110v AC input with 5 volts DC at 8 to 10 amps fully regulated output. Slightly smoke damaged, hence ONLY £10.95
PERIPHERAL SYSTEM SUPPLY. Runs almost any system. Fully cased unit supplied in a brand new or little used condition. Outputs give 5v @ 11 amps "+" 15-17v @ 8 amps "-" 15-17v @ 8 amps and "+" 24v @ 4 amps. All outputs are crowbar protected and the 5 volt output is fully regulated. Fan cooled. Supplied tested with circuit. £55.00 + £8.50 carr.

1000's of other POWER SUPPLIES EX STOCK - CALL SALES OFFICE FOR DETAILS

DUAL DISK DRIVE/ WINCHESTER CASES

Very smart, fully enclosed case unit custom made to accept two full height 5 1/4" floppy disk drives or two 5 1/4" winchesters such as the RHODIME RO200 or TANDEM series etc. An internal switched mode PSU supplies all the required voltages to enable you to plug in your drives and go!!

Other features include mains filter, internal cables with standard drive connectors, space for internal PCB, standard fan cut out and mounting, air filter. Overall dimensions 28 cm W x 30 cm D x 19 cm H ONLY £55.00 + £6.00 CARR.

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s tracs diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings fully guaranteed. 50 + £2.95 100 + £3.15

TTL 74 Series A gigantic purchase of an 'across the board' range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100 + £6.90 200 + £12.30 300 + £19.50

NORTH STAR HORIZON

Pro S100 system with dual 5" floppy drives, software, manuals etc. £850.00 Call sales office for details

ULTRA COMPACT 300 BAUD ACOUSTIC MODEM — COUPLER

A Major manufacturer's over production and a bulk buy special enables us to offer this BRAND NEW TRANSDATA 307A ultra compact, BT APPROVED, 300 baud full duplex acoustic modem at a fraction of manufacturer's list price. The unit operates on the standard CCITT V21 frequencies with RS232 interface via 25 way 'D' skt.


Combine the adjustable cup system, which fits almost any phone with the benefit of "No jacks or phone cables" and a light weight of only 1.2 Kg and you have a truly portable modem!! Supplied complete with data, 90 day guarantee and ready to use.

ONLY £49.95 + £3.00 pp



PROFESSIONAL 6 FOOT 19" RACK CABINETS

LARGE 19" equipment cabinet. Totally enclosed with locking front and rear doors. An internal sub frame 63" high is pre drilled for standard 19" equipment etc. Other features include internal 12" cooling fan, two-tone blue and gray finish with alloy trims. Mounted on 4 heavy duty castors, mains panel etc. And at a current cost from IMHOFS of over £500 A snap at ONLY £125. Supplied in NEW or little used condition. Carriage £22.00. Ext. Dim 72.5" h x 23.5" w x 26" d

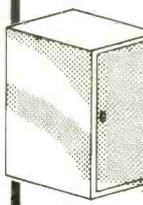

LOGICAL KEYBOARD

Heavy duty unit in attractive satin alloy case. 55 full travel keys are laid out in a logical format of:



Making a very useful keyboard, ideal for persons unfamiliar with or confused by the standard QWERTY layout. All keys generate the equivalent ASCII outputs and various control codes shown in data. A 7 bit latched parallel TTL output with strobe enables direct connection to any similar micro port etc. Many other features such as internal 240v to 5v PSU, MAINS ON/OFF switch. Supplied in NEW or little used condition with data. ONLY £25.95 Post and packing £4.50

1000's of other EX STOCK items including POWER SUPPLIES, RACKS, RELAYS, TRANSFORMERS, TEST EQUIPMENT, CABLE, CONNECTORS, HARDWARE, MODEMS, TELEPHONES, VARIACS, VDU'S, PRINTERS, POWER SUPPLIES, OPTICS, KEYBOARDS etc. etc. Give us a call for your spare part requirements. Stock changes almost daily.

Don't forget, ALL TYPES and QUANTITIES of electronic surplus purchased for CASH

CIRCLE 76 FOR FURTHER DETAILS.

HART
WORLD

**LINSLEY-HOOD
300 SERIES AMPLIFIERS**



35 Watt Complete Kit, MosFet O/P £79.50
45 Watt Complete Kit, MosFet O/P £83.50
Reprints of Original Articles from 'Hi-Fi News' £1 no VAT.

**LINSLEY-HOOD 100-WATT MOSFET
POWER AMPLIFIER**

The very latest amplifier design, published in 'Wireless World' by the renowned John Linsley-Hood. This may now be taken as the standard by which the rest are judged! Our kit, approved by the designer, has massive heat sinks and power supply and includes all components needed to build. Case size 412mm wide, 254mm deep and 145mm high. Automatic switched speaker protection is included as standard. Cost of all parts is over £120. Our complete stereo kit price £105.50.

**LINSLEY-HOOD CASSETTE RECORDER
CIRCUITS**

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions. Complete Stereo Record/Play Kit £25.26
VU Meters to suit £2.30 each
Reprints of original Articles 75p. No VAT.

STUART TAPE RECORDER CIRCUITS


Complete Studio quality record/Play electronics to bring that old valve machine back to life. Full details in our REPRINT £1.30 (No VAT).

PW WINTON STEREO AMP

Super HiFi Mosfet Amplifier Kit giving 50 Watts per channel at .014% distortion, housed in attractive wood veneered cabinet. Full Kit is normally £109. SPECIAL OFFER, NOW ONLY £89. Reprint of descriptive articles 85p (No VAT)

**DGS001 2-MOTOR,
SOLENOID CONTROLLED
CASSETTE DRIVE**

Fully solenoid controlled cassette mechanism suitable for Hi-Fi or digital use. With a logic control board the deck can be operated by lightweight touch controls or output from a micro. Ideal for applications under automatic control such as telephone answering machines, data loggers, automatic background music systems, remote control recorders and microcomputer program and data storage. Two motors and three solenoids control all functions including search in fast forward and rewind.
Standard fittings include reed switch for auto off, 3 digit counter, stereo R/P and erase Head.
Overall size 176mm X 130mm X 75mm.
DGS001 Cassette Mechanism. £37.25 Quantity prices on request.
INF140 Full technical specification and drawings £1.

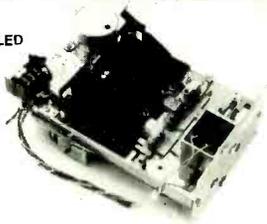

**HIGH QUALITY REPLACEMENT
CASSETTE HEADS**



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £5.11
HM90 High Beta Permalloy Head. A hard-wearing, higher performance head with metal capability £8.06
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £9.91
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £3.73
Please consult our list for technical data on these and other Special Purpose Heads.
MA481 Latest version Double Mono (2/2) Record/Play Head. Replaces R484 £8.90
SM166 Standard Mounting 2/2 Erase head. Compatible with above or HQ551 4 Track head £5.90
H524 Standard Erase Head. Semi double gap, high efficiency £1.50
H561 Metal Tape Erase Head. Full double gap £4.90

**HART TRIPLE-PURPOSE TEST
CASSETTE TC1**

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback £4.54.
Curved Pole Type for inaccessible heads £4.85

Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.
Please add part cost of post, packing and insurance as follows:

INLAND Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50
OVERSEAS Please send sufficient to cover Surface or Air Post as required.

AM VARICAP DIODE BARGAIN Super wide range SMV2012 varicap diodes in matched sets to eliminate tracking errors! Matched pair only 25p. Matched 4 only 60p.

SET OF 4 COILS to use with above to make long, medium and short wave AM tuner. Normally 30p each. OUR PRICE FOR THE SET ONLY 55p

INF10 Application circuit using coils and matched pair of SMV2012 varicaps. 35p
168A I/F Transformer 30p
CFU455F2 I/F Filter 50p
Suitable PC Board £1.50
Push Button PC Mounting Wavechange Switch £1.60

COMPLETE STEREO TUNER MODULE

Three band LW/MW/FM Stereo Tuner fully assembled on PCB 165 x 85mm. Supplied with Ferrite rod aerial and band switch fully wired. Facility provided to drive tuning meter and stereo LED. Only needs 12v DC supply. FM sensitivity. 2.5uV. Price only £7.99 inc. VAT and post.

STEREO 10W POWER AMPLIFIER MODULE

Ready built and tested music centre power amplifier module complete and ready to use. Mains input 220/240v with power to spare for tune and tape deck. Size 190 X 110 X 65mm. ONLY £8.90 plus Vat and Post.

AUTOMATIC 10-CASSETTE AUTO PLAYERS

Suitable for background music systems. Lenco type PAC10 plays each cassette forward and backwards before changing to the next. Any cassette may be rejected at the touch of a button. Mains powered. Wood finish case with perspex top cover. Play through any high quality stereo amplifier system. Orally over £500 each! Our price for ex-demonstration models only £230. One only Brand New £310.

Personal callers are always very welcome but please note that we are closed all day Saturday

**24hr SALES LINE
(0691) 652894**

**ALL PRICES EXCLUDE VAT
UNLESS STATED**

HART
HART ELECTRONIC KITS LTD
PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 3AF

**E.M.S. POWER
SYSTEMS**



Solve all your Power Problems by contacting E.M.S.

E.M.S. specialise in systems to eliminate your power problems.

Products range from 35VA switched square wave Power Packs to 1KVA fully uninterruptible sine wave systems.

E.M.S. also manufacture chargers which range up to 60 amps.

For further details please contact:

E.M.S. Manufacturing Limited
Chairborough Road
High Wycombe
Bucks
Tel: (0494) 448484

CIRCLE 36 FOR FURTHER DETAILS.

**LYONS INSTRUMENTS LIMITED
WARE ROAD, HODDESDEN,
HERTS EN11 9DX**

Attention is drawn to the Guildline Digital Platinum Resistance Thermometer the cost of this £1780 and not £2760 as previously, wrongly, stated in Electronics & Wireless World, March '85 issue.

Lynwood GD1 VDUs: Intelligent Green micro controlled, RS232, printer port, 101 key k/b. Full Video enhancements. ONLY £149 + £15 P&P (S/H)
Burrheads MT686/7/TD710: Intelligent Green 12" VDU with 3 micros and 64K store. RS232. Programmable... Only £199 new or £149 S/H + £15 P&P
Open Chassis Video Monitors from above VDUs £40+7.00 p&p



Multirail Switching PSUs from above 5v 4A 12v +24v £25 + £1.50
Data General 6012 VDU's very attractive display working RS232 with integral 73 key k/b either dumb terminal mode or page buffered. Only £120.00 + £15.00 p&p



Centronics 306 Line printers: Professional fast (120 cps), superb quality 80 column printer. Parallel i/f. ONLY £99 + £15.00 P&P
Osborne Executive Portable CP/M system with oodles of software. Twin floppy drives £900 + £15 p&p
Diablo 630 Daisywheel printer. OEM i/f. NEW £599 + £15 P&P
Calcomp 565 Drum Plotter, 10thou steps. ONLY £450 + £10 P&P

BECKENHAM PERIPHERALS LTD

Callers welcome by appointment

01-466 5582
34 Rodway Road, Bromley
Kent BR1 3JL

We also buy redundant peripherals

CIRCLE 46 FOR FURTHER DETAILS.

ELECTRONICS & WIRELESS WORLD MAY 1985

POWER SUPPLIES

maximum to minimum. It is expressed as a percentage.

Operating area. Supplies with wide output-voltage ranges can often supply more current at higher voltages because dissipation in the linear regulating circuit is lowest. Rather than giving a fixed rating of, say 0-30V at 5A, some manufacturers provide an operating area graph of current versus voltage.

Regulation, see load/line regulation.

Remote sensing. Specifications for power supplies don't take into account the leads connecting the supply to the load. With long leads and high currents, voltage drop can be significant and output impedance of the supply increases. Remote sensing is used to minimize these effects. Normally, voltage is sensed at the supply output terminals and fed back to the control amplifier which provides regulation. Remote sensing involves taking the voltage sensing lines out directly to the load.

Resolution. Smallest voltage or current increment which an adjustable supply can repeatedly be set to.

Response time. When subjected to a step or transient load, a supply takes time to respond. It is likely that response times in current and voltage modes will be different.

Ripple rejection. In a regulating circuit, ripple rejection is the ratio of r.m.s. input ripple voltage to r.m.s. output ripple voltage.

Shunt regulation. A shunt regulator, a good example of which is a zener diode, stabilizes voltage by acting as a load whose impedance rises rapidly as voltage falls below a certain level and vice-versa. With no load, a shunt regulator draws high current, and with full load draws very little current. Unless load is constant, shunt regulators are inefficient. Their advantage is that they are unaffected by output short-circuits.

Suppressor. This term is used for any device used to filter out unwanted noise or transients. These include LC mains filters, metal-oxide voltage dependent resistors, which can be found over the mains input or d.c. output, high-speed silicon suppressors, which are like a zener diode but able to withstand extremely high currents in short bursts, and simple capacitor suppressors, which may be found almost anywhere in a supply circuit.

Settling effect. When load on a supply changes, it takes time for the supply to reach thermal equilibrium. This is the settling effect.

Transient response. Like power amplifiers, power supplies take time to respond to transient load variations. A supply's transient response is difficult to quantify and is probably best expressed in an oscillograph. Some manufacturers express transient response in terms of time taken for output voltage to recover to within a certain tolerance for a given step load change.

Zero-crossing switch. Some supplies only allow the mains to switch on at the voltage zero crossing point.

MAKE	TYPE	O/PV	O/PI	RIPPLE	R-LOAD%	R-LINE%	O/P R	FL	CL	CV	CC	V	I	C	PRICE	REMARKS	
Powerbox	2000	4-6	3	10mV	10mV	2mV	0.004	*	*	*	*	*	*	*			
		40	1.25	3mV	0.05%	0.05%											
	3000	4-6	3														
		40	1.25	As 2000 but with 20V output													
	3535	+/-11-16	1		0.1%	0.2%	0.02	*	*								11-16V outputs track.
		4-6	3		25mV	2mV											
	3525	4-6	3	3mV	0.25%	0.15%	0.002	*									25V outputs track.
		25	1	3mV	0.25%	0.05%	0.003										
	SB15-20 to SB2501.25	15	20	50mV	0.05	0.05	<0.001						*	*			Switched mode.
		1.25	250	1.25	*	*	*	*					*	*			*
Powerline	LAB501	30	1	1mV	0.05%	0.05%	<0.015	*	*	*	*	*	*	*		Programmable. Analogue or digital	
				500µA	0.5%	0.5%	3-70k										
	Models with common characteristics:																
	LAB502	30	2					*	*	*	*	*	*	*			
	LAB505	30	5					*	*	*	*	*	*	*			
	LAB515	15	10					*	*	*	*	*	*	*			
	LAB510	30	10					*	*	*	*	*	*	*			
	LAB702	70	2					*	*	*	*	*	*	*			
	LAB521	30	1						*	*			*	*			
	LAB522	30	2						*	*			*	*			
	LAB532	30	2						*	*			*	*			
	IC	20	0.5	12-15	0.5				*	*			*	*			
12-15				0.5					*	*			*	*			
20		0.5	4.5-5.5	5					*	*			*	*			
			4.5-5.5	5													
LAB520		30	20					*	*	*	*	*	*				
LAB530	30	30					*	*	*	*	*	*					
Racal-Dana	9231	31	1.1	<1mV	<0.01%	<0.01%	0.005	*	*					digital		Remote sensing. Protected.	
				Dual 9231													
	K unit	5	3.5	Can be combined with other units													
				9232	31	2.2											
	9232Q	Dual 9232															
	Radford	N14	6000	3mA	0.05%	High source Z	2.2M	*					*	*		130	E.h.t. supply
12a.c.					3A	unstab.											
LAB59		25	8					*							100	Muffield instrument. variable	
				300	0.1	unstab.											
N59		25	8	25a.c.	8				*						90	Muffield instrument. Step variable	
	6.3a.c.			3													
N59C	25	10	12a.c.	6				*						130	Continuous		
			25a.c.	8													
Takasago	GP07-10	7	10	<500µV	<0.005%	<0.005%		*	*	*	*	*	*				
				Models from above to 1000V at 0.5A (GP01000-05) with common characteristics. Must be ordered with 220V input if needed													
Thurlby	PL310	30	1	<1mV	<0.01%	<0.01%	<0.005	*	*	*	*	*	*	digital		Remote sensing	
				PL320	30	2	*	*	*	*	*	*	*	*			
				PL154	15	4	*	*	*	*	*	*	*	*	*		Outputs can be combined in series or parallel
PL3206P	30	2	Range of dual and triple units based on above														
			GP1B controlled. Based on PL320														
Time Electronics	9810	33	1	<2mV	0.05%	0.05%	0.005	*	*			*	*	595	GP1B remote and local		
				9809	66	1.1	<2mV	0.05%	0.05%	0.005	*	*			*	*	825
or +/-33																	
Weir	4000-30-1	30	1	2mV	0.05%	0.01%	<0.01	*	*	*	*	*	*	digital	115		
				1mA	1mA	0.1%	>30k										
4000-30-2	30	2					*	*	*	*	*	*	*	digital	150		
			Twinpack versions of these available, including mixed types														

DEWSBURY

ELECTRONICS



POCOMTOR AFR 2000 RTTY ALL MODE



SPECIAL FEATURES:

- Fully automatic recognizing of ARO, FEC Collective and FEC Selective (SITOR/AMTOR)
- Fully automatic searching and synchronizing in Baudot mode according to Baud rate and phase, indication of baud rate and phase
- Manual preselecting of all Baudot and ASCII speeds
- Optimum microprocessor controlled signal reception with 16'000 (sixteen thousand) samples per second and steady re-phasing on forward and backward run of signal

- Special narrow band quadrature discriminator for all used LF shifts from 50 to 1000Hz
- Simple and quick tuning with 16 line LED bar indication
- Extremely simple operating
- Current-saving 8 bit C-Mos microprocessor
- Development and manufactured in Switzerland

FEATURES AND APPLICATION:

The POCOMTOR AFR-2000 RTTY ALL MODE DECODER allows the simple and easy writing of the usual teletype codes as BAUDOT, ASCII (including 200 baud press service), ARO, FEC-Collective, FEC-Selective (SITOR/AMTOR) and the FEC procedure used for secret services, which differs from the usual CCIR recommendation 476 2. The POCOMTOR AFR-2000 is a complete teletype decoder with built-in new quadrature discriminator for automatic adapting and processing of the normal shift offsets of 50Hz to 1000Hz. The POCOMTOR AFR-2000 is the first RTTY reception device on the consumer area that fully automatically determines the received baud rate and synchronizes thereon, without being necessary as yet usual to test the baud rates and phase (Normal/Reverse) in question in a troublesome way. It is now only required to call up the automatic routine and after a short time for the signal reception of about 10 to 15 seconds the synchronization is reached and the text can be written.

In the mode ARQ/FEC, i.e. during synchronous character transfer (without start and stop bit) the built-in intelligence finds out by itself whether it is an ARQ or FEC signal, whereby it is additionally differentiated between FEC-Collective and FEC-Selective. To balance signal phase moves there is a steady adaption of the microprocessor controlled sampling, as to pre-running characters and to after-running characters.

The technology of the POCOMTOR AFR-2000 RTTY ALL MODE DECODER corresponds to the highest requirements. Its extraordinary prize/performance ratio will not be reached in near future on the easy way. Choosing the POCOMTOR AFR-2000 you take the most modern receiving device on the market. Its for that you receive more and have to tune less. It has never been thus easy to receive radio teletype.

Dewsbury Electronics offer a full range of Trio Equipment always in stock.

We are also stockists of DAIWA-WELTZ-DAVTREND-TASCO TELEREADERS-MICROWAVE MODULES
ICS AMTOR-AEA PRODUCTS-DRAE-BNOS



Dewsbury Electronics, 176 Lower High Street, Stourbridge, West Midlands.
Telephone: Stourbridge (0384) 390063 / 371228. Open Monday thru Saturday.
Instant H.P. subject to status, Access, Barclaycard and real money.



CIRCLE 53 FOR FURTHER DETAILS.



1 CHANNEL VHF WALKIE TALKIE 250mW/9V KIT No 626

Specification

RECEIVER

Sensitivity: 0,25uV
First IF: 10,7Mhz
Second IF: 455khz
Crystals used: carrier: 3
- 10,7=crystal frequency.

Audio out: 300mW

Power consumpt.: 15mA

(sq. open).

TRANSMITTER

RF out: 250mW (can be

increased to 1W)

Crystals used: osc.frequency

X2=carrier.

Power cons.: 48mA(300mW).

32R speaker used also as


micro.

Description

A lightweight, small handle talkie with main advantage its VERY LOW consumption. . .

A typical 9v battery will last for several hours. Can be used between 140 to 165Mhz just changing crystals or trimming a few coils. P.c. board dimentions: 80x55mm.

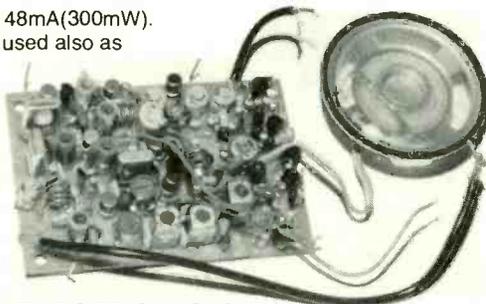All transisters used are bipolar for low cons. Also, two special IC's, the one in flat pack version for limited space.



C & A ELECTRONIC O.E.
PO Box 25070 Athens 10026
GREECE Tel: 5242867. Tlx: 210798 CAGR

CIRCLE 65 FOR FURTHER DETAILS.

Versatower:

A range of telescopic towers in static and mobile models from 7.5 to 36 metres with tilt-over facility enabling all maintenance to be at ground level.

Designed in accordance with CP3 Chapter V; part 2; 1972 for a minimum wind speed of 140 kph in conditions of maximum exposure and specified by professionals world-wide where hostile environments demand the ultimate in design, quality and reliability.

Suitable for mounting equipment in the fields of:

Communications

Security surveillance - CCTV

Meteorology

Environmental monitoring

Geographical survey

Defence range-finding

Marine and aero navigation


Floodlighting

Airport approach lighting

Further details available on request.



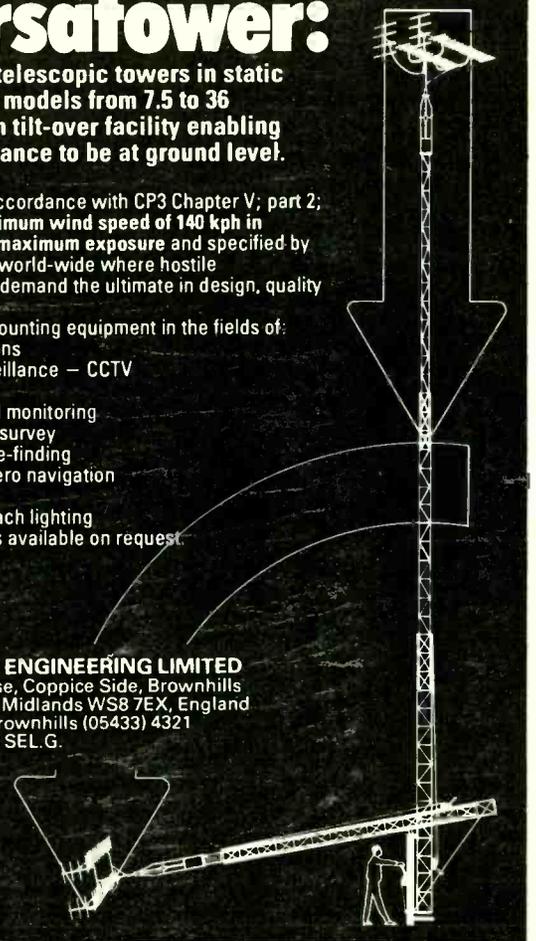
STRUMECH ENGINEERING LIMITED
Portland House, Coppice Side, Brownhills
Walsall, West Midlands WS8 7EX, England
Telephone: Brownhills (05433) 4321
Telex: 335243 SEL G.



CIRCLE 38 FOR FURTHER DETAILS.

E.h.t. multiplier

A new design for high-voltage multiplier provides an e.h.t. supply up to 30kV for c.r.t.s from an input voltage of between 5 and 5kV. The unit uses single-cell silicon diodes and is claimed to provide improved regulation when compared with split diode systems. They will operate over a wide temperature range and are rated for continuous operation at an ambient temperature of 55°C. It is housed in a flame-retardant plastic case with epoxy resin seals and is approved to BS415. Edicron Ltd., 1 Wesley Avenue, London NW10 7BZ. EWW213

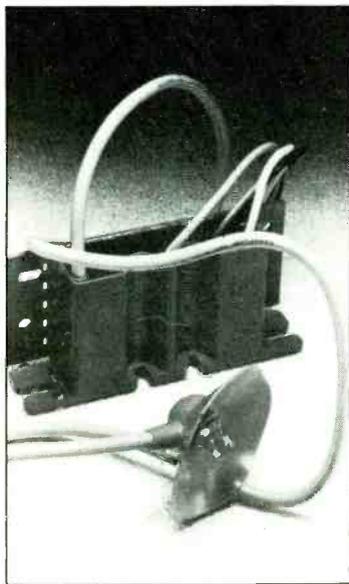


Low-cost wire stripper

At a price claimed to about a third of any comparable tool, the TC1017 is a self-adjusting wire stripper and cutter suitable for most types of wire of diameters from 0.5 to 5mm. The tool operates in one continuous action by gripping the wire and then cutting and removing the insulation by the sliding action of the blades. A pressure adjustment is provided for wires with particularly tough

or soft insulation but in practice there is little need to use this.

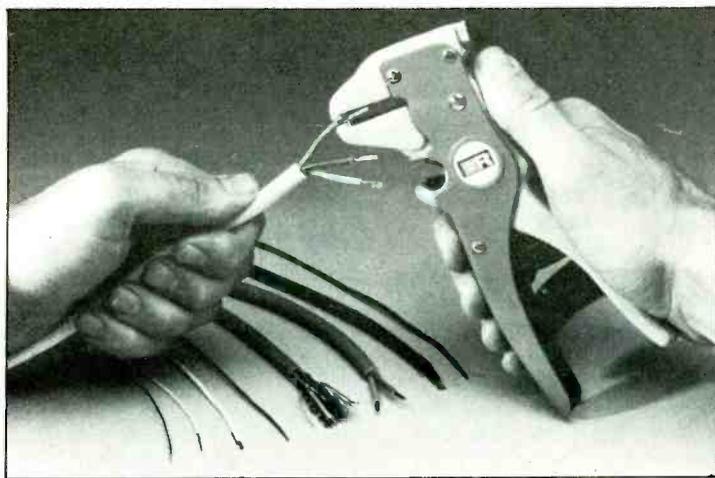Incorporated into the tool is a pair of cutting blades so that cables may be cut to length and trimmed before stripping. Graduations along the jaw of the stripper enable measured lengths to be stripped. Trade price £4.30 from B&R Electrical Products Ltd., Temple Fields, Harlow, Essex CM20 2BG. EWW219



Static locator

A pocket sized static electricity locator is designed and made in the UK. The EVL9 has three ranges; 1kV, 5 and 25kV and uses leds to indicate the presence and polarity of static. A simple conversion table is provided to calculate the field


strength. The battery powered instrument may be used in such static-sensitive environments as computer rooms, electronic component assembly areas, hospitals, laboratories etc. It costs £109.75 inclusive from Technotrend Ltd., The Town House, High Street, Chobham, Surrey GU24 8AF. EWW218



Camera for screen graphics

Computer graphics displays as well as tv images can be easily and quickly reproduced with the Datacam 35 colour recording camera. It uses 35mm Polachrome film and an Autoprocessor can be used to produce and mount slides without the need for any darkroom facilities, or they can be processed normally. Another

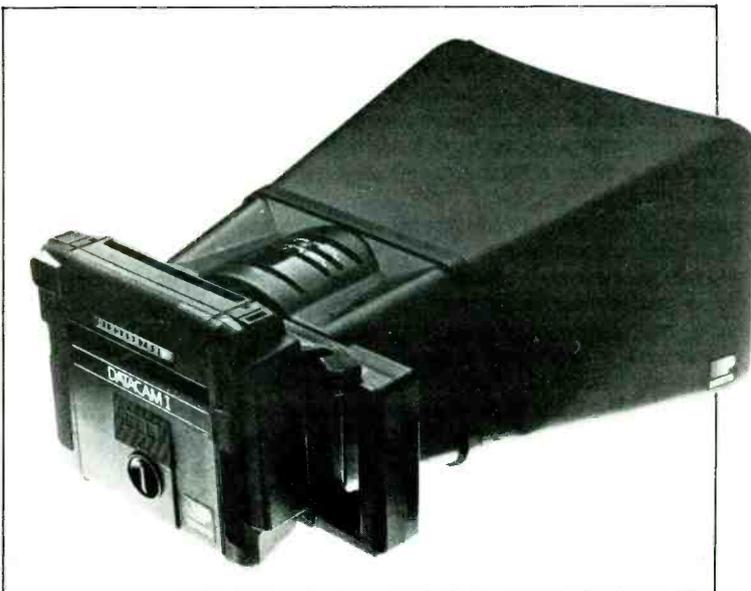camera, the Datacam 1, produces 3 by 4in colour prints instantly by using Kodamatic Trimprint colour film. Two versions are available of each camera suitable for use with a 12 to 13in screen or a 19 to 21in. Dicoll Data Systems Ltd., Bond Close, Kingsland Estate, Basingstoke, Hants RG24 0QB. EWW222



Lowest-cost modem

The cheapest multi-standard modem yet is the Demon, which for a v.a.t.-exclusive price of £49.95 gives access to dial-up databases on both the 300 baud and viewdata standards. And a front-panel push-button allows selection of the corresponding American modes.

Most other controls, however, are implemented in software to avoid the cost of switches. At present the Demon, which was first announced last autumn as the Unicom modem, is available only in a version for the BBC Micro. The software is supplied in eeprom at an extra £20. The data connection to the computer is via the serial port, which doubles as a control line: mode selection is carried out by keying the RTS line.

The software offers a number of attractive facilities: Prestel telesoftware downloading, user-to-user file transfer with the so-called CP/M protocol, auto-dialling, auto-answer and auto-scanning mode selection. One feature of its design is that all functions are controlled by means of 'star' commands. Users can incorporate these in their own software to make do-it-yourself computer bulletin boards.



But a drawback of the software control is that there is no quick way of discovering the status of the modem. And the user cannot check whether a call has succeeded, since the unit has no telephone extension socket. Another problem is that although the rom is said to use 'legal' system calls only, it seems to conflict with certain other packages — for example, Addcomm and the Computer Concepts graphics extension rom.


Versions of the Demon are planned for several other computers, including the Amstrad CPC464, Apple II, ZX Spectrum and Commodore 64. The Demon Modem has not yet received BABT approval.

Demon Electronics Ltd., 182 Royal College Street, London NW1 9NN.
EWW210

GPIB for Apricot

A plug-in card together with a disc library of driver subroutines provides a full implementation of the IEEE-488 interface bus for the ACT Apricot personal computer. The card enables users of the computer to program and access data from such sources as automatic test stations, test and measurement equipment and signal interfaces such as Microlink. The software allows the IEE-port to be used from

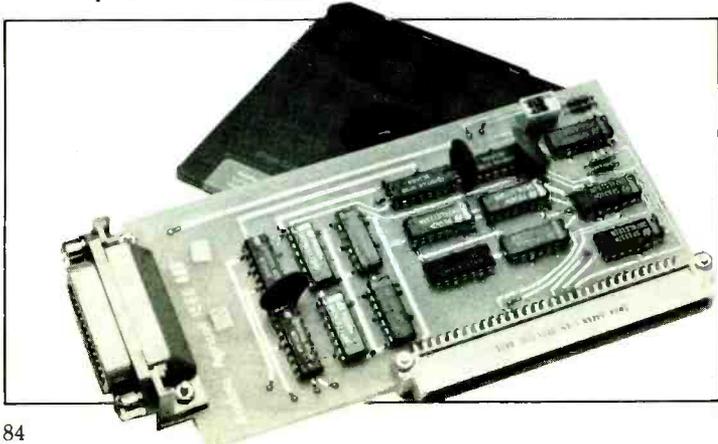Microsoft controller functions, which include: secondary addressing, parallel data transfer in eight bits, serial and parallel polling, status tests from software, remote line control and data transfer at 20Kb/s. The p.c.b. plugs directly into the backplane of the computer or may be connected through a lead if required. Electroplan Ltd., PO Box 19, Orchard Road, Royston Herts SG8 5HH. EWW205



Terminal software for Spectrum

A cassette program, Spacenet, will allow Sinclair Spectrum owners to use their VTX5000 Prestel modems with ASCII services such as Bulletin boards and commercial databases which are not accessed through Prestel. The modem speed is still fixed at 1200/75 but most databases and an increasing number of bulletin boards are providing services at this data rate. Once connected to a service all control characters can be sent for editing or cancelling various functions. Program transfer is possible in both directions using

Xmodem principles. Copies of the screen can be saved and reloaded into the computer as can any software received by the system. Local echo is provided as an option.

Another program, Specterm, provides similar functions and allows all known Spectrum RS232 interfaces to be used with a modem and will communicate even with Spectrum-incompatible computers. The software manufacturer tells us that BBC, Tandy and CP/M computers, amongst others, have been used to store Spectrum data. Each program cost £5.95 from Stephen Adams, 1 Leswin Road, London N16 7NL.
EWW207

Comal for the BBC

Latest in a flurry of recent language releases from Acornsoft is a version of Comal for the BBC Micro. Comal, which has been described as a half-way house between Basic and Pascal, is widely used in educational computing in Scandinavia (where it originated) and the Netherlands. It has also won official approval in Scotland and the Irish republic as the recommended language for secondary schools.

Comal is an interpreted language. For the beginner it is as easy to pick up at the keyboard as Basic, yet it does not share that language's tendency to engender untidy programming habits.

On paper, a Comal listing looks much like its Basic equivalent: most of the keywords are the same (though the tokens used for program storage differ), there are the same variable types and the program lines are numbered.

Comal's practical advantage lies in its powerful control structures. For example, in addition to the Repeat-Until loop (which is executed at least once) it has the useful While-do loop, which is not executed at all if on entry the exit conditions are already met. For decision-making, Comal has Case-when for use where the course to be taken depends on the value of a variable: a neat alternative to complicated If-then statements.

String-handling is made exceptionally easy by the sub-

string specifier, a simple yet strikingly effective device which by-passes the cumbersome Left\$, Mid\$ and Right\$. Filing commands are comprehensive, yet plainer in their meanings than their Basic counterparts.

Each program line entered at the keyboard is checked for syntax errors by the editor, which echoes any faulty line with the error marked. When the program is listed, loops and other features are indented automatically to emphasise the structure, making the flow of control easy to follow.

Keywords are displayed in upper case letters, variables and procedure names in lower case, and the editor inserts certain formal details of syntax where they have been omitted.

Execution speed is a little slower than BBC Basic — by about 15% according to Acorn — though that still makes it faster than most other eight-bit Basics. However, Comal's special features make it possible to write compact code which is also much simpler to de-bug.

Acornsoft's Comal conforms to the Comal-80 standard published in 1982. It includes many extensions specific to the Electron and BBC Micro such as sound and graphics commands, which have the same syntax as their BBC Basic equivalents. The language is supplied in a 16K rom for £49.85 including v.a.t., together with a clear and well-written 440-page manual, also available separately at £10. Acornsoft Ltd., Betjeman House, 104 Hills Road, Cambridge CB2 1LQ. EWW211

AUDIO · VIDEO · DATA

A superb range of innovative loading
and duplicating technology
· Worldwide ·



the leaders

Tape Automation Ltd, Unit 2, River Way, Harlow, Essex CM20 2DN.
Telephone (0279) 442946, Telex 265871 MONREF G quoting Ref: 84: AUL001.


EUROPE · USA · JAPAN · UK · INDIA

CIRCLE 21 FOR FURTHER DETAILS.


New from **ORYX-PORTASOL** Portable Gas Soldering Iron

ORYX – market leaders in soldering irons and accessories introduce the revolutionary PORTASOL. This new approach to catalytic soldering iron technology is truly

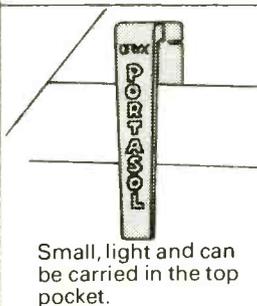
pocket portable (173 mm) and independent of any external energy source. PORTASOL is powered by ordinary cigarette fuel and one filling lasts for 60 minutes continuous use.



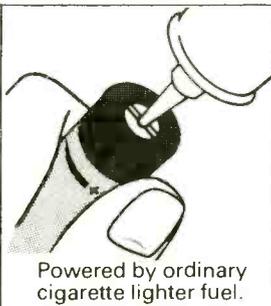
Small, light and can be carried in the top pocket.



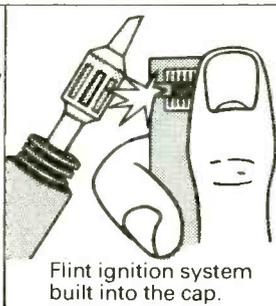
Powered by ordinary cigarette lighter fuel.



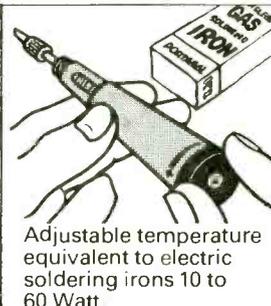Flint ignition system built into the cap.



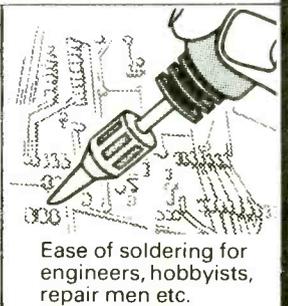Adjustable temperature equivalent to electric soldering irons 10 to 60 Watt.



Ease of soldering for engineers, hobbyists, repair men etc.

- ★ Portasol makes an ideal and handy present.
- ★ Immediately available for use anytime anywhere.
- ★ Portasol meets all safety standards.
- ★ No problem with statics.
- ★ Adjustable temperature for sensitive components.

ONLY
£17.25
INCLUDING VAT, P&P

ORDER WITH THIS COUPON TODAY

To: Greenwood Electronics, Portman Rd, Reading Berks RG3 1NE.
Please send.....(qty.) PORTASOL at £17.25. I enclose cheque/P.O./cash for £..... or debit my Barclaycard no.Access no. Expiry date

NAME

ADDRESS

Please send technical leaflet. Tick Allow 14 days for delivery.

EWW 5

CIRCLE 51 FOR FURTHER DETAILS.

NEW PRODUCTS

Low-cost logic analyser

Claimed to be by far the best in price to performance ratio, the Thurlby LA-160 at £395 offers 16 data channels, expandable to 32, and a 2000-word acquisition memory. The state domain display shows the data in any of five formats: binary, octal, decimal, hex or mixed. A full 16-channel timing display is available by connection to any conventional oscilloscope. The maximum clock rate is 10MHz for the LA-160A or 20MHz for the LA-160B.

Comprehensive trigger facilities include 230bit trigger width, the ability to set the trigger word in any display format, selectable trigger hold-off and a trigger arm input with variable delay. Data can be captured synchronously or asynchronously using the clock of the circuit under test or an internal clock with 16 selectable frequencies. Two clock qualifiers enable data to be captured selectively, e.g. on the read cycle of a processor bus.

The instrument is microprocessor controlled through a front-panel keyboard with all the set-up information being stored in permanent memory. A non-volatile reference memory is also included. This can be loaded from the acquisition memory and allows reference data to be stored for comparison. Extensive software facilities include word search, block memory compare, word-by-word comparison and stop on equality or non-equality acquisition modes. A built-in RS232 interface enables the




contents of the acquisition memory to be dumped to a computer and printed. Options include high impedance input modules, expansion units, an IEEE488 bus analysis connector and a direct printer interface. The LA-160 is truly portable, weighing less than 1.8kg.

Thurlby believe that its low cost makes it suitable for each engineer to be allocated one, rather than the usual queue to use the lab's only instrument. The low cost also makes it available to educational establishments and service departments who hitherto have been unable to afford a logic analyser. Thurlby Electronics Ltd., New Road, St. Ives, Huntingdon, PE17 4BG. EWW215

Glass-less relay

The changeover contacts on the SDS RS family of reed relays can switch 240V, 1A and up to 40VA. The relay does not use the conventional glass envelope for the reed element, but instead uses the coil body which is encapsulated inside the relay housing. The coils are polarized and 160mW of power is sufficient to achieve high contact pressure.

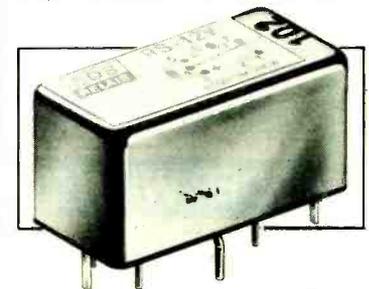Polarizing also enables latching relays with one or two coils to be produced in a package only 20 by 10 by 10.2mm. For use in telecommunications, telemetry, instrumentation and control systems. They are sealed and magnetically screened. SDS Relais Ltd., 17 Poters Lane, Kiln Farm, Milton Keynes MK11 3HF. EWW221



THURLBY LA160

CLOCK= EXT CLOCK POLARITY= POSITIVE TRIGGER BIN= XXXX XXXX 0011 0010 HEX= XX32
 CLOCK ENABLES= 11 TRIGGER ENABLES= 1101 TRIGGER ARM= 1
 ARM DELAY= ON TRIG HOLD-OFF= OFF



LOGIC= NEGATIVE MEMORY= AQU

LOC	DATA																LOC	BINARY	HEX	ASCII
	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	D15	D0		
-21																	-21	0000 0001 0001 1101	0110	..
-20																	-20	0000 0010 0001 1110	021E	..
-19																	-19	0000 0011 0001 1111	031F	..
-18																	-18	0000 0100 0010 0000	0420	..
-17																	-17	0000 0101 0010 0001	0521	..
-16																	-16	0000 0110 0010 0010	0622	..
-15																	-15	0000 0111 0010 0011	0723	..
-14																	-14	0000 1000 0010 0100	0824	..
-13																	-13	0000 1001 0010 0101	0925	..
-12																	-12	0000 1010 0010 0110	0A26	..
-11																	-11	0000 1011 0010 0111	0B27	..
-10																	-10	0000 1100 0010 1000	0C28	..
-9																	-9	0000 1101 0010 1001	0D29	..
-8																	-8	0000 1110 0010 1010	0E2A	..
-7																	-7	0000 1111 0010 1011	0F2B	..
-6																	-6	0001 0000 0010 1100	102C	..
-5																	-5	0001 0001 0010 1101	112D	..
-4																	-4	0001 0010 0010 1110	122E	..
-3																	-3	0001 0011 0010 1111	132F	..
-2																	-2	0001 0100 0011 0000	1430	..
-1																	-1	0001 0101 0011 0001	1531	..
0																	0	0001 0110 0011 0010	1632	..
1																	1	0001 0111 0011 0011	1733	..
2																	2	0001 1000 0011 0100	1834	..
3																	CURS	0001 1001 0011 0101	1935	..
4																	4	0001 1010 0011 0110	1A36	..
5																	5	0001 1011 0011 0111	1B37	..
6																	6	0001 1100 0011 1000	1C38	..
7																	7	0001 1101 0011 1001	1D39	..
8																	8	0001 1110 0011 1010	1E3A	..
9																	9	0001 1111 0011 1011	1F3B	..
10																	10	0010 0000 0011 1100	203C	..
11																	11	0010 0001 0011 1101	213D	..
12																	12	0010 0010 0011 1110	223E	..
13																	13	0010 0011 0011 1111	233F	..
14																	14	0010 0100 0100 0000	2440	..
15																	15	0010 0101 0100 0001	2541	..
16																	16	0010 0110 0100 0010	2642	..
17																	17	0010 0111 0100 0011	2743	..
18																	18	0010 1000 0100 0100	2844	..
19																	19	0010 1001 0100 0101	2945	..
20																	20	0010 1010 0100 0110	2A46	..
21																	21	0010 1011 0100 0111	2B47	..
22																	22	0010 1100 0100 1000	2C48	..
23																	23	0010 1101 0100 1001	2D49	..
24																	24	0010 1110 0100 1010	2E4A	..
25																	25	0010 1111 0100 1011	2F4B	..
26																	26	0011 0000 0100 1100	304C	..
27																	27	0011 0001 0100 1101	314D	..
28																	28	0011 0010 0100 1110	324E	..
29																	29	0011 0011 0100 1111	334F	..

Bug hunter

A device for detecting and locating clandestine radio microphones is the Ranger surveillance receiver. It improves over earlier systems by being able to operate in the presence of strong local radio signals, it can detect power line bugs without being connected to the power line, it can locate a

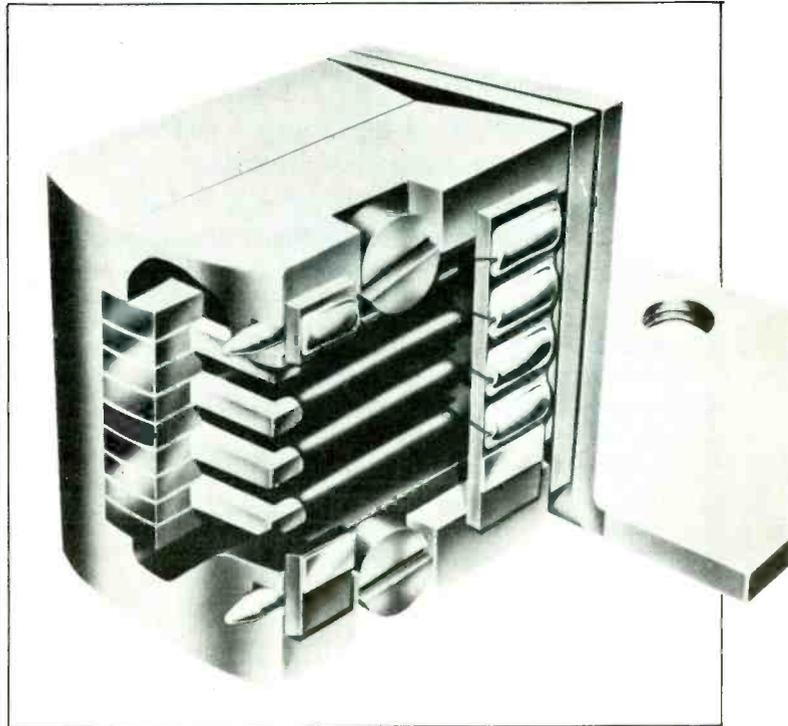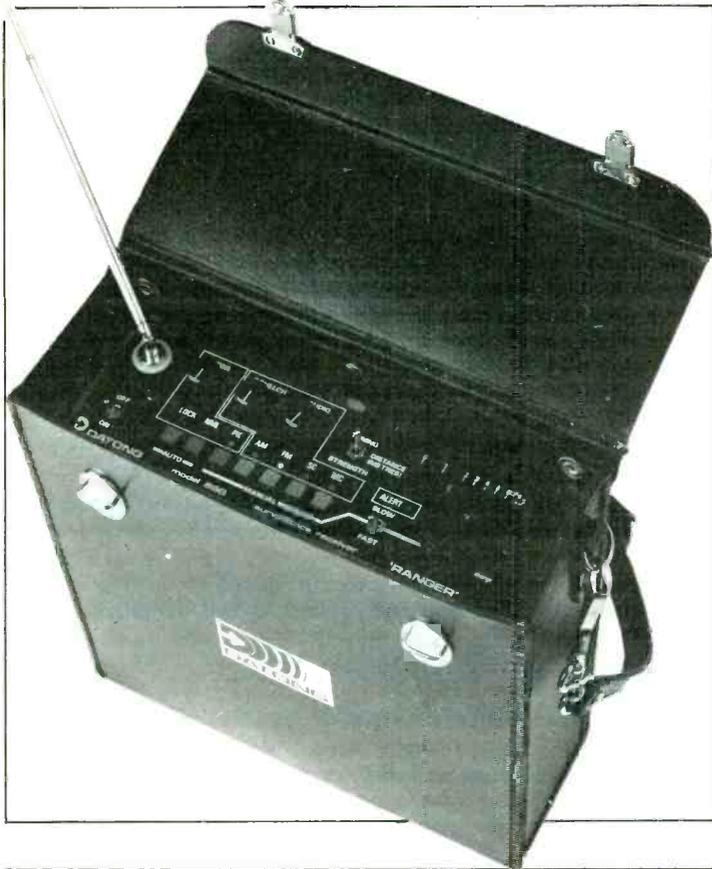bug to within a few centimetres and needs no specialist operator skills. An average room can be 'swept' in about two minutes and the sweep covers a frequency range from v.l.f. to several GHz. It also checks all likely modulation methods. The device is portable and operates from rechargeable batteries. Datong Electronics Ltd., Spence Mills Lane, Bramley, Leeds LS13 3HE. EWW217




Nine-channel tape head

Designed for high speed data storage on 0.25in tape, the D99RW01 has nine channels designed for eight-bit words and a parity bit. The manufacturers point out that this method eliminated the need to buffer incoming signals before writing to the tape in serial format for subsequent reconversion to parallel on read output. There are also audio applications with the use of NAB audio cartridges

and could be used, for example for the 'jingles' in popular radio. The volume production version has a head gap of 100microns, a nominal inductance of 2.7mH providing an output of up to 4mV with a tape speed of 15ips and a data rate of 3200Hz. Other versions can be built to meet customer specification. Monolith Electronics Ltd., 5 Church Street, Crewkerne, Somerset TA18 7HR. EWW223

Tantalum capacitors

Of particular use in timing circuits where high stability, high reliability and low dissipation are important, the Mepco Electra range of metal cased solid tantalum capacitors is available. The 40SS range can also be used in decoupling, blocking, bypass and filtering applications. They are manufactured using porous sintered tantalum anodes with tantalum oxide dielectric. They feature very low d.c. leakage. Voltage ranges are from 6 to 100V in preferred capacitance values from 0.1 to 330µF, at 10% tolerance. Greenwood Electronics, Portman Road, Reading, Berks RG3 1NE. EWW216

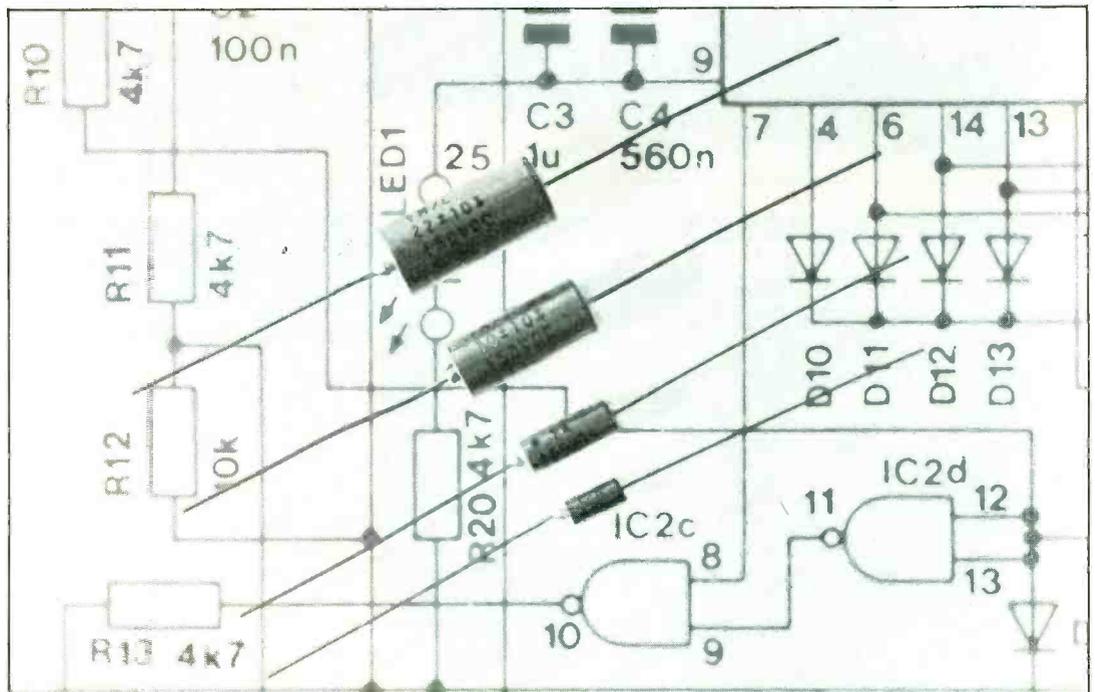

A low-cost professional Logic Analyser the new Thurlby LA-160

from £395 +vat

- 16 data channels, expandable up to 32
- 2,000 word data acquisition memory
- Non-volatile reference memory
- Powerful search and compare facilities
- Clock rates up to 20MHz
- Data state and logic timing displays
- Binary, octal, decimal or hex formats
- Hard-copy data print-out option

An essential instrument for today's electronics


An oscilloscope and logic probe are not enough to unravel the complexities of today's electronic equipment. A logic analyser is now the essential tool for digital electronics work both hardware and software. With prices measured in £1,000s, however, many engineers have been denied the use of one. Until now!

Innovative design and high volume production using the latest component technology provide the

Thurlby LA-160 with performance exceeding many high-cost analysers but at a price measured in £100s.

The LA-160 enables digital information to be precisely recorded and then examined in detail either as a data state display or as a logic timing diagram (via the user's own oscilloscope).

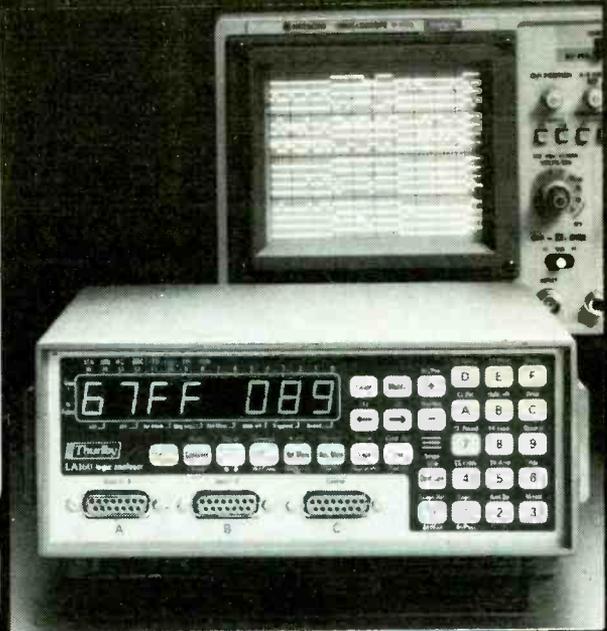Contact us now for a full colour technical data sheet.



Thurlby Electronics Ltd., New Rd.
St.Ives, Huntingdon, Cambs. PE17 4BG
Tel: (0480) 63570 Tlx: 32475

CIRCLE 79 FOR FURTHER DETAILS.

The world's most advanced low-cost bench multimeter!

Thurlby 1905a £325 + VAT



A complete high performance bench DMM

● 5½ digits; 0.015% acc; 1 µV, 1mΩ, 1nA.

● Full ac and current functions as standard

A sophisticated computing and logging DMM

● Linear scaling with offset; null/relative

● Percentage deviation; running average

● dBV, dBm general logarithmic calculations

● Limits comparison; min and max storage

● 100 reading timed data logging

● RS232 and IEEE-488 interface options

Thurlby Electronics Ltd
New Road, St.Ives, Cambs. PE17 4BG
Tel: (0480) 63570




CIRCLE 80 FOR FURTHER DETAILS.

Digital storage oscilloscopes

from Hitachi

more speed, more memory, more features

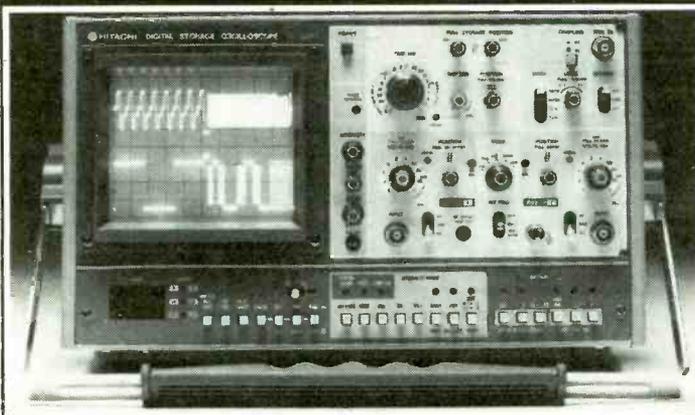

The new Hitachi VC-6041 combines a 40MHz A-D converter with 8K words of acquisition memory to provide ultra high resolution capture of high speed transient events.

A wealth of state-of-the-art features includes signal averaging, roll mode, variable pre-trigger, post storage expansion to X100, digital voltage and time readout, pen recorder output, and a GPIB data option.

If your application is a little less demanding choose the VC-6015, it's the easiest to use digital storage 'scope around. It has dual channel storage at 1MHz clock rate, 2K word memory, variable pre-trigger, X10 post storage magnification and a full pen recorder output, yet it costs only £1,450.

We hold the complete Hitachi 'scope range in stock for immediate availability. Ring us now to get full specifications and prices or to arrange a demonstration on (0480) 63570.

Thurlby-Reltech Instruments, 46 High Street, Solihull, W. Midlands, B91 3TB


CIRCLE 81 FOR FURTHER DETAILS.

SOME IDEAS NEVER SELL... but our new innovations do!

Crotech 'scopes are chosen for use throughout the electronics industry and in education for their reliability and ease of use.

... and they're affordable too!!

LIKE THE 3132 DUAL TRACE 'SCOPE

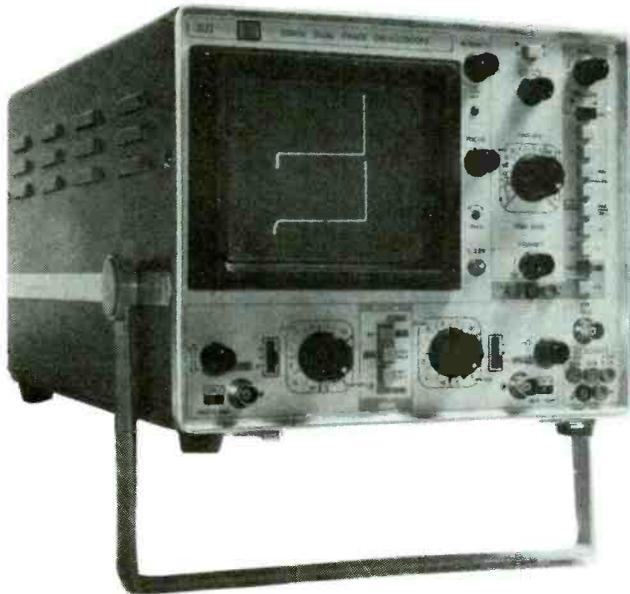

The innovations...

- * Component Comparator
 - * Triple Output DC Source
- plus...
- * 20MHz Bandwidth
 - * 2mV/div Sensitivity
 - * 40ns/div Timebase
 - * TV Frame and Line Trigger
 - * Add and Subtract
 - * X - Y mode
- ... and very affordable


For free details call:

Crotech Instruments Limited

2 Stephenson Road, St. Ives, Huntingdon, Cambs. PE17 4WJ
Telephone: (0480) 301818

CIRCLE 50 FOR FURTHER DETAILS.

FROM THE INNOVATORS

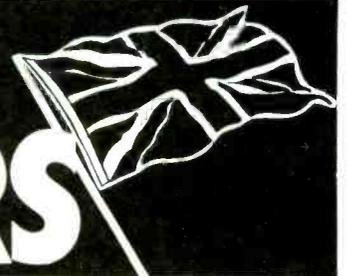

A SELECTION
FROM OUR
EXTENSIVE
RANGE

UK Designed and Manufactured Power Supplies

HIGH EFFICIENCY, SWITCH MODE.

RUGGED, HIGH PERFORMANCE LINEARS.

45 Watts 4 Outputs	176 x 108 x 42mm	1 off £66.50
60 Watts 4 Outputs	197 x 108 x 52mm	1 off £74.85
120 Watts 5 Outputs (standard)	Eurocard Size	1 off £110.00

(OVP, EMI Filter, Case, Power Fail options available)

15-35 Watts	Industry Standard Chassis	1 off £29.72
30-75 Watts	Industry Standard Chassis	1 off £51.38
50-120 Watts	Industry Standard Chassis	1 off £76.38

(Dual and Triple Outputs also available)

GREENDALE ELECTRONICS LIMITED

CIRCLE 90 FOR FURTHER DETAILS.

Green Lane,
Dronfield,
Sheffield S18 6LL
Tel: (0246) 417661



A member of the
Crystalline Group

BULGIN Power Supplies

The Bulgin Power Supplies range includes both fully designed customised and standard products; including units for BT applications, all available at competitive prices for OEM quantities.

Encapsulated EPS range. Twelve Models, P.C.B. or chassis mounting various input/output voltages.

Low Cost Switched Mode QSM range. Dual input voltage various output combinations from 30 to 130W and up to 300W.

DC-DC Converters, DC range. P.C.B. mounting, six types, various input/output combinations up to 5W.

Open Frame Linear OFL range. For 3 1/2" and 5 1/4" disc drive and general applications.

Eurocard Linear ECPS range. User selectable input/variable output. Conform to DIN mechanical standards.

Eurocard Switched Mode ESM range. Conform to DIN mechanical standards, dual input voltage/multiple outputs. Available for base mounting as TSM range.

Uninterruptible Power Supplies, UPS range. Three models rated 120vA, 250vA or 500vA giving hold-up time of up to 20 minutes at full load when the mains fail.

Full technical literature on request to the

Power Conversion Division,
A. F. Bulgin & Co. PLC, Bypass Road, Barking, Essex IG11 0AZ
Telephone: 01-594 5588 Telex: 897255



CIRCLE 94 FOR FURTHER DETAILS.

COMPONENT PACKS

All Brand New except where marked
Price: £1 per pack
Order 12 you get one extra FREE
Please add £1 post if order under £20

- | | |
|---|--|
| 1 - 5 13 amp ring main junction boxes | 35 - 4 battery operated model motors |
| 2 - 5 13 amp ring main spur boxes | 36 - 2 air spaced 2 gang tuning condensers |
| 3 - 25 13 amp fuses for ring mains | 37 - 2 solid dielectric 2 gang tuning condensers |
| 4 - 5 surface mounting switches | 38 - 10 compression trimmers |
| 5 - 3 flush switches intermediate type | 39 - 1 Long & medium wave tuner kit |
| 6 - 5 in flex line switches | 40 - 4 x 465 KC IF transformers |
| 7 - 4 in flex line switches with neons | 41 - 8 rocker switches 10a mains SPST |
| 8 - 2 80 watt brass cased elements | 42 - 6 rocker switches 10a mains SPDT |
| 9 - 2 mains transformers with 6v 1a secondaries | 43 - 5 rocker switches 10a SPDT |
| 10 - 2 mains transformers with 12v 1a secondaries | 44 - 1 rocker switches 10a SPDT |
| 11 - 1 extension speaker cabinet for 6" speaker | 45 - 1 24 hour time switch mains operated |
| 12 - 5 octal bases for relays or valves | 46 - 1 6 hour clockwork time switch |
| 13 - 12 glass reed switches | 47 - 2 2 lever switches 4 pole changeover up and ditto down |
| 14 - 4 OCP 70 photo transistors | 48 - 2 6v operated reed switch relays |
| 15 - 25 assorted germanium transistors OC45 etc | 49 - 10 neon valves - make good night lights |
| 16 - 4 tape heads, 2 record, 2 erase | 50 - 2 x 12v DC or 24v AC 4CO relays |
| 17 - 2 ultra sonic transmitters and 2 ditto receivers | 51 - 1 x 12v 2C D very sensitive relay |
| 18 - 2 15000 mfd computer capacitors | 52 - 1 x 12v 4C D relay |
| 19 - 2 i.d.r. similar DRP *2 | 53 - 2 mains operated relays 3 x 8a changeovers (second hand) |
| 20 - 5 diff micro switches | 54 - 10 rows of 32 gold plated IC sockets (total 320 sockets) |
| 21 - 2 mains interference suppressors | 55 - 1 locking mechanism (with 2 keys) |
| 22 - 2 25 watt crossover units | 56 - 1 miniature Uniselector with circuit for electric jigsaw puzzle |
| 23 - 1 40 watt 3 way crossover unit | 57 - 5 dolls house switches |
| 24 - 250 screws and self tappers | 58 - 2 telephone handsets |
| 25 - 1 of each water switches - 6p 2 way, 4p 3 way, 2p 6 way, 1p 12 way | 59 - 2 flat solenoids - to make current transformer etc |
| 26 - 2 tape deck counters | 60 - 5 ferrite rods 4" x 5" - 16" dia |
| 27 - 1 6 digit counter 12v | 61 - 5 ferrite slab aerials LW & MW |
| 28 - 1 6 digit counter mains voltage | 62 - 4 200Ω ear pieces |
| 29 - 1 BOAC in flight stereo unit (s.h.) | 63 - 1 Mullard Thyristor Trigger module |
| 30 - 2 NICAD battery chargers | 64 - 10 assorted knobs; spindles |
| 31 - 1 key switch with key | 65 - 5 diff thermostats |
| 32 - 2 humidity switches | |
| 33 - 2 aerosol cans of ICI Dry Lubricant | |
| 34 - 96 x 1 metre length colour-coded wires | |

Most items available in quantity at good discounts. Access & Barclay cards welcome

N.B. ELECTRONIC SUPPLIES
34 America Lane, Haywards Heath, Sussex RH16 3QU
(24hr phone ordering 0444 454563)

CIRCLE 60 FOR FURTHER DETAILS.

SALE BY AUCTION

Tuesday 30th April 1985

Test equipment including:-

TEK 308 data analyser, leader function and signal generators HV probes, video head checkers, oscilloscope calibrator. FM stereo generator (all new). Fluke 3010 logic tester marconi signal generators, power meters, voltmeters. HP spectrum analyser TEK 491 spectrum analysers ICE DMMS bryans and HP recorders.

Computer equipment including:-

53 Anderson Jacobson printers, 80 DEC terminals VT100, VT101, VT102, VT131, VT125 VT180, DEC LA 34 and 100 printers 7 rainbow 100A + P.C.s. Modems, Texas, Motorola and Intel development systems. Wayne-Kerr Datum Artworker CAD PCB Design System Honeywell 101 28 track tape recorder. MAD-1 256K computer systems with floppies and hard disk 110 in all. Altos 20MB and 40MB computers. HP printers, displays etc. 15 Tally printers. 25 Mellordata terminals. 12 Diablo printers. Zilog 8000 computer system. Olympia scriptwriter. Qume terminals. Superbrain and Osbourne computers. TEK 4662, 4112A, 4112B, 4661 and 4114B. Accoustic couplers. 9 Westward 3219 terminals (new). Professional 350 computer. 43 Newbury data terminals. Altos 8000, 286-10, 5-5, 5-15 computers. Phoenix 12" monitors. DEC RX-180 dual disk drive (new) Tallgrass 20+20 and 12MG. 89 IBM 3178 C10 and C80 terminals (all new). 9 TI terminals (new). Anadex printers. 2 Alcatel paternoster automatic assembly machines. General and surplus components and equipment. I.C.s etc.etc.

Suitable entries still accepted.

Catalogues from the auctioneers below price £1.50 inc. viewing one week prior and on morning of sale 8am-5pm


Industrial Auctions Limited
Bromyard Road Industrial Estate
Ledbury
Herefordshire
HR8 1LG
Telephone 0531 5456 Telex 35686

NEW PRODUCTS

Precision inductors

A range of high stability, high Q, precision inductors has been produced by Oxley. They feature an alumina former on to which is fused a thick, high-conductivity silver alloy. The terminations are silver plated copper and are bonded with a high melting point solder which will not melt when normal assembly. With values from 0.045 to 1.83 μ H and a standard

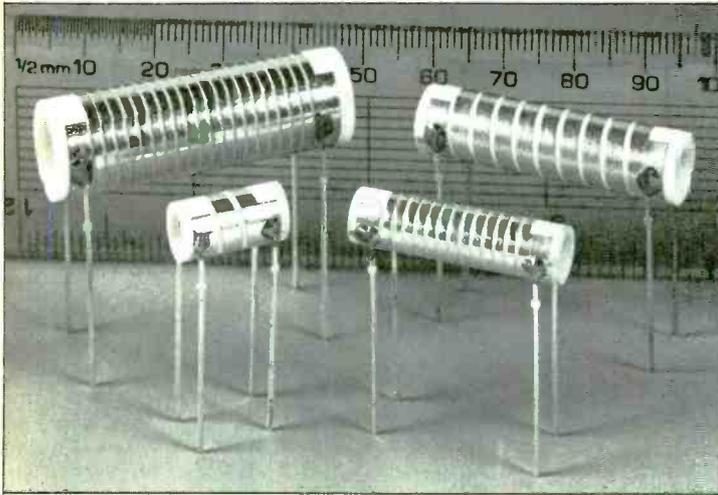
tolerance of $\pm 5\%$, the inductors may be used as reference standards in instrumentation, to reform clock pulses in high-speed digital communications, precision LC oscillators and many other tank circuit applications where long-term stability is required. Oxley Developments Co. Ltd., Priory Park, Ulverston, Cumbria LA12 9QG. EWW214



Toroidals to order

Adding to their existing facilities for transformer prototyping, MS Components can now offer a similar service for toroidal transformers. Using Micro-controlled winding technology, prototype toroids can now be delivered in seven to ten days from the receipt of an order. Primary/secondary combinations are possible

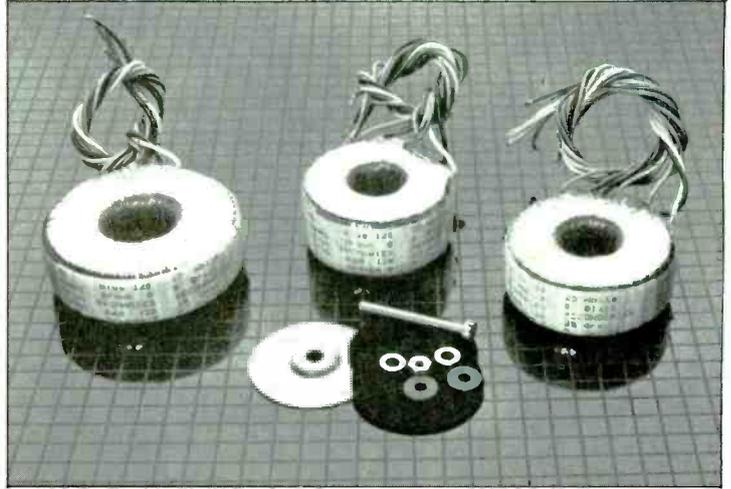
between 15 and 500VA with an output tolerance of $\pm 3\%$ at rated load. Mounting kits are included in the price quoted at the time of ordering. The transformers have a maximum operating temperature of 105°C and are flash tested to 4.5kV. MS Components Ltd, Waring Street, London SE27 9LH. EWW226



Upgraded tracker ball

The RB2 computer input tracker ball is now available with improved speed and temperature specification. Known as the RB2/CAD controller, it is available as a standard model, with enhanced specifications or it can be 'customized' with various options for quantity users. The standard tracker ball comes in a case with three user-definable

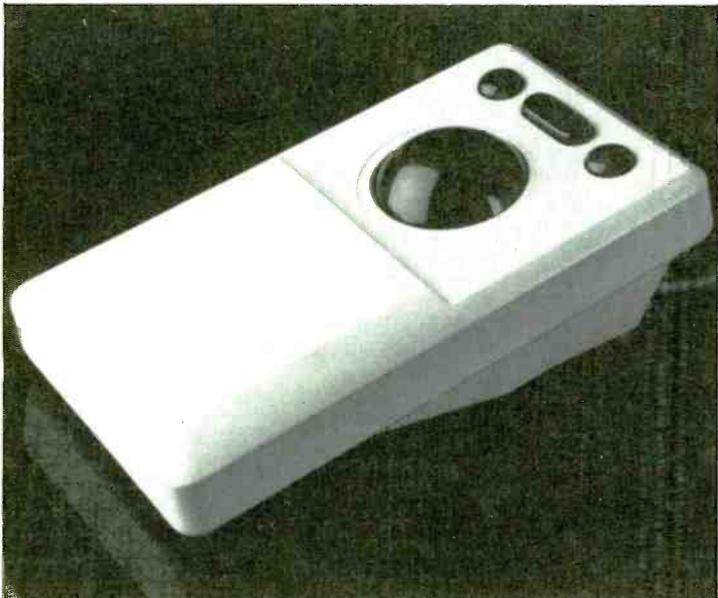function keys making it ideal for positional control applications such as c.a.d. word processing, robotics, graphics etc. A version is available with a standard RS232C interface communications module. The one-off price for the RB2/CAD from Marconi starts at about £70. MEDL Power Division, Carholme Road, Lincoln LN1 1SG. EWW227



Battery charger for u.p.s.

A modular battery charger for use with uninterruptible power supplies has been developed by Avel-Lindberg. Working with systems that have a nominal supply of 24V, the charger can supply an inverter with a low-ripple d.c. and the necessary float charging current for the batteries to a maximum of 40A. Phase-control thyristor circuitry can control the float voltage to a preset level, and boost the voltage and output current limit modes of operation. The boost charge facility may be used with vented lead-acid batteries but should be disconnected if

sealed batteries are in use. Mains input voltage may be selected and the charger can cope with a 10% voltage variation on the mains. The unit is designed to comply with various r.f.i. and safety standards; the output is short and open-circuit protected, and will operate over a wide ambient temperature range. Matching inverters, static switches and alarm/status inductors are available to complete a u.p.s. system. Avel-Lindberg Ltd., South Ockendon, Essex RM15 5TD. EWW208





PHONE
0474 813225
3 LINES

P. M. COMPONENTS LTD
SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
966371
PM COMP

INTEGRATED CIRCUITS

AN124	2.50	MC1327	0.95
AN2140	2.50	MC1327Q	0.95
AN240P	2.80	MC1349P	1.20
AN612	2.15	MC1351P	1.50
AN7140	3.50	MC1357	2.35
AN7145	3.50	MC1358	2.35
AN7150	2.95	MC1358	1.58
BA521	3.35	MC1495	3.00
CA1352E	1.75	MC1496	1.25
CA3086	0.46	MC145106P	9.95
CA3123E	1.50	MC1723	0.50
ETT610	2.50	SAA1025	7.25
HA1377	3.50	ML231B	1.75
HA1156W	1.50	ML232B	2.50
HA1339A	2.95	MSM5807	6.75
HA1551	2.95	PLL02A	5.75
LA1230	1.15	SAA500A	3.50
LA4031P	1.95	SN7502N	2.75
LA4102	2.95	SN7503N	3.50
LA4140	2.95	SN76110N	8.50
LA4400	4.15	SN76115N	1.25
LA4420	1.95	SN76131N	1.30
LA4422	2.50	SN7626DN	2.95
LA4430	2.50	SN76533N	1.65
LA4461	3.95	SN76544N	2.65
LC7120	3.25	SN76570N	1.50
LC7130	3.50	SN76650N	1.15
LC7131	5.50		
LM324N	0.45		
LM3808N	1.50		
LM3801A	1.75		
LM3831	2.95		
LM3900N	3.50		
M51513L	2.30		
M51512L	2.95		
M51521L	1.50		
MB3712	2.00		
MC1307P	1.50		
MC1310P	1.50		

SN76660N	0.80	TBA5200	1.10
STK014	7.95	TBA5300	1.10
STK043	5.95	TBA5300	1.10
STK415	7.95	TBA5400	1.25
STK433	5.95	TBA5400	1.35
STK435	7.95	TBA5500	1.95
STK437	7.95	TBA5600	1.45
STK439	7.95	TBA5600C	1.45
STK461	11.50	TBA5700	1.00
TA7061AP	3.95	TBA641A122.50	2.50
TA7100P	1.65	TBA651R	2.50
TA7120P	1.65	TBA720A	2.45
TA7130P	1.50	TBA750Q	2.85
TA7176AP	2.95	TBA800	0.89
TA7203	2.95	TBA810AS	1.65
TA7204P	2.15	TBA810P	1.65
TA7205AP	1.15	TBA820M	0.75
TA7222AP	1.80	TBA820Q	1.45
TA7227P	4.25	TBA890	2.50
TA7310P	1.80	TBA907/2X2.35	1.50
TA7313AP	2.95	TBA990	1.49
TA7321P	2.25	TCA270	1.10
TA7609P	3.95	TCA270S0	1.10
TA7611AP	2.95	TCA501	3.50
TA7618	6.85	TCA940	1.65
TAA320A	1.95	TDA440	2.20
TAA350A	1.95	TDA1001	1.95
TAA550	0.35	TDA1004A	4.15
TAA570	1.95	TDA1006A	2.50
TAA661B	1.20	TDA1035	2.15
TA700	1.70	TDA1037	1.95
TBA120AS/B/C	1.00	TDA1170	1.95
SA/SB/T/U	1.00	TDA1190	2.15
TBA395	1.50	TDA12700	3.95
TBA396	0.75	TDA1327	1.70
TBA440N	2.55	TDA1327	1.70
TBA480Q	1.25	TDA2020	2.95
TBA510	2.50	TDA2030	2.80
TBA510Q	2.50	TDA2522	1.95
TBA520	1.10	TDA2523	2.95

NEW BRANDED CATHODE RAY TUBES
PLEASE ALLOW ADDITIONAL £3 PER TUBE FOR CARRIAGE.

A1865/20	65.00	F31-10GM	65.00	M50-120GV	65.00
AW3611	25.00	F31-10GR	65.00	M50-120LC	65.00
CME822GW	19.00	F31-10L	65.00	M61-120LC	75.00
CME142GH	45.00	F31-12L	65.00	M61-120W	75.00
CME142BW	39.00	F31-12CL	65.00	S6AB	45.00
CME1523GA	39.00	F31-13GR	65.00	SE4/D/P7	45.00
CME1523W	39.00	F31-13LD	65.00	SE42BP31AL	55.00
CME1431GH	39.00	F31-13LG	65.00	SE42BP31AL	55.00
CME1431W	39.00	F31-13LL	160.00	SE5FP31	55.00
CME202GH	45.00	F41-141L	160.00	T937	65.00
CME2024W	45.00	F41-142LC	185.00	T948N	65.00
CME2325W	45.00	M7-120W	19.00	T948H	65.00
CME3126GH	45.00	M14-100GM	45.00	V3191	59.00
CME3128GH	45.00	M14-100L	45.00	V4150LC	55.00
CME3128W	45.00	M17-151GVR	175.00	V4254B	65.00
CME3132GH	45.00	M17-151GR	175.00	V4274GH	65.00
CME3155W	45.00	M19-100W	55.00	V4283W	65.00
CRE1400	29.00	M19-100Y	45.00	V5002LD	65.00
CV429	85.00	M19-101GR	55.00	V5004GR	59.00
CV1456	19.00	M19-103W	55.00	V5004LD	59.00
CV2185	15.00	M23-110GH	55.00	V5001GH	65.00
CV2191	19.00	M23-111W	55.00	V6006GH	65.00
CV2193	15.00	M23-111GH	55.00	V6007DP31	59.00
CV2519	85.00	M23-111LD	55.00	V6007GW	65.00
CV5320	85.00	M23-112GM	55.00	V6008GW	59.00
CVX389	55.00	M23-112GV	55.00	V6008W	65.00
D9-110GH	39.50	M23-112W	55.00	V6009W	59.00
D9-120	45.00	M23-112KA	55.00	V6048CLA	59.00
D10-210GH	45.00	M23-112LD	55.00	V6048F	65.00
D10-210GH68B	65.00	M23-112W	55.00	V6048J	49.00
D10-210GH72	65.00	M24-120GM	59.00	V6052GH	65.00
D10-230GH	35.00	M24-120GR	59.00	V6052GR	65.00
D10-230GM/90	25.00	M24-120LC	59.00	V6064BLA	65.00
D13-30GH	49.50	M24-120W	59.00	V6064B31	55.00
D13-33GM	49.00	M24-121CL	59.00	V6064CLA	55.00
D13-47GH/26	55.00	M24-121WA	59.00	V6069GH	55.00
D13-51GL/26	85.00	M28-12GH	55.00	V6070P31	49.00
D13-51GM/26	85.00	M28-13L	55.00	V7016A	65.00
D13-45GH/01	45.00	M28-13LC	59.00	V7030	59.00
D13-47GH/26	55.00	M28-13GR	49.00	V7031GH	59.00
D13-550GH	65.00	M28-131GR	55.00	V7031/67A	59.00
D13-600GM	59.00	M28-132GM	55.00	V7035A	49.00
D13-610GM	59.00	M28-133GH	55.00	V7037GH	65.00
D13-611GH	59.00	M31-100GH	55.00	V8004GR	55.00
D13-630GH	59.00	M31-101GH	55.00	V8080GH	65.00
D14-120GH08	65.00	M31-182GR	53.00	V8101A	65.00
D14-150GH	75.00	M31-182GV	53.00	2BP1	9.00
D14-150GM	75.00	M31-183W	55.00	3BP1	13.50
D14-172GH/84	55.00	M31-184W	65.00	4EP1	30.00
D14-172GR	55.00	M31-184GH	65.00	3W1P	18.50
D14-173GH	55.00	M31-184P31	65.00	3W1P08M	55.00
D14-173GM	55.00	M31-185GH/VR	65.00	5BP1F	30.00
D14-173GR	55.00	M31-186W	65.00	5BP1F	30.00
D14-181GH/62	55.00	M31-190GR	59.00	5HP31	30.00
D14-181GH/98	65.00	M31-190LA	55.00	5CP1	30.00
D14-181GJ	55.00	M31-190W	55.00	6EP1S	39.00
D14-181GM	53.00	M31-191GH	59.00	13BP1	13.50
D14-182GM/98	85.00	M31-191GR	59.00	13BP4	25.00
D14-200BE	89.00	M31-191W	59.00	32D/1085	65.00
D14-200GM/50	85.00	M31-192W	59.00	88D/89B/89D/89L	15.00
D14-200GM	75.00	M31-195GH	59.00	1273	39.00
D14-210GH	75.00	M31-195GM	59.00	1844	45.00
D14-210GH/50	110.00	M31-210GH	59.00	9442E1	80.00
D14-320GH	85.00	M31-220W	59.00	954470GA	75.00
D14-320GH/82	85.00	M31-270G	65.00	95449GM	75.00
D14-340GH/KM	45.00	M31-271P31	65.00	7709631	75.00
D16-100GH	65.00	M31-271W	65.00		
D16-100GH/65	65.00	M36-12W	75.00		
D16-100GH/79	69.00	M36-141LA	75.00		
D16-100GH/79A	75.00	M36-141L	75.00		
D16-100GH/87	65.00	M36-141W	75.00		
D16-100GH/87A	65.00	M36-170LG	75.00		
D16-100GH/87B	65.00	M38-100GR	65.00		
D16-100GH/87C	65.00	M38-101GH	65.00		
D16-100GH/87D	65.00	M38-103GR	65.00		
D16-100GH/87E	65.00	M38-120WA	65.00		
D16-100GH/87F	65.00	M38-121GR	65.00		
D16-100GH/87G	65.00	M38-121GHR	65.00		
D16-100GH/87H	65.00	M38-121LA	65.00		
D16-100GH/87I	65.00	M38-121WA	65.00		
D16-100GH/87J	65.00	M38-122GW	65.00		
D16-100GH/87K	65.00	M38-141LA	65.00		
D16-100GH/87L	65.00	M38-142GR	65.00		
D16-100GH/87M	65.00	M38-142LA	65.00		
D16-100GH/87N	65.00	M38-340P31	65.00		
D16-100GH/87O	65.00	M38-341GR	65.00		
D16-100GH/87P	65.00	M38-341P31	65.00		
D16-100GH/87Q	65.00	M38-344P39	65.00		
D16-100GH/87R	65.00	M43-12GM/01	65.00		
D16-100GH/87S	65.00	M43-12LG/01	65.00		
D16-100GH/87T	65.00	M44-120LC	65.00		
D16-100GH/87U	65.00	M47-25GR/22	65.00		
D16-100GH/87V	65.00	M50-120GH	65.00		
D16-100GH/87W	65.00	M50-120GR	65.00		

SEMICONDUCTORS

AA12	0.25	RC174	0.09
AC126	0.45	BC174A	0.09
AC127	0.20	BC177	0.15
AC128	0.28	BC178	0.15
AC128K	0.32	BC182	0.10
AC141	0.28	BC182LB	0.10
AC141K	0.34	BC183	0.10
AC142K	0.30	BC183L	0.09
AC176	0.22	BC244LB	0.09
AC176K	0.31	BC204	0.10
AC187	0.25	BC207B	0.13
AC187K	0.28	BC208B	0.13
AC188	0.25	BC212	0.09
AC188K	0.37	BC212L	0.09
AD142	0.79	BC212LA	0.09
AD143	0.82	BC213	0.09
AD149	0.70	BC213L	0.09
AD161	0.39	BC214	0.09
AD162	0.39	BC214L	0.09
AD161/2	0.50	BC219	0.09
AF106	0.50	BC238	0.09
AF114	1.95	BC238	0.09
AF121	0.60	BC239	0.12
AF124	0.65	BC251A	0.12
AF125	0.35	BC252A	0.15
AF126	0.32	BC258	0.25
AF127	0.67	BC258A	0.39
AF139	0.40	BC284	0.30
AF150	0.60	BC300	0.30
AF178	1.95	BC301	0.30
AF239	0.42	BC303	0.26
AU106	4.50	BC307B	0.15
AU110	3.50	BC327	0.10
AU110	5.00	BC328	0.10
BC107A	0.11	BC337	0.10
BC107B	0.11	BC338	0.10
BC108	0.10	BC347A	0.13
BC108A	0.11	BC347B	0.13
BC108B	0.12	BC478	0.20
BC109	0.10	BC527	0.20
BC109B	0.12	BC547	0.10
BC109C	0.12	BC548	0.10
BC114	0.11	BC549A	0.10
BC116A	0.15	BC597	0.11
BC117	0.19	BC557	0.08
BC119	0.24	BC557B	0.08
BC125	0.25	BC558	0.10
BC139	0.20	BCY33A	1.60
BC140	0.31	BD115	0.30
BC141	0.25		
BC142	0.21	BD124P	0.59
BC143	0.24	BD131	0.42
BC147A	0.12	BD132	0.42
BC147B	0.12	BD133	0.40

PHONE
0474 813225
3 LINES

P. M. COMPONENTS LTD
SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
966371
PM COMP



A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 18.50	EBF80 0.65	EL822 12.95	M8223 4.50	QS1202 3.95	UL84 0.85	3AT2 3.35	6B8C 1.00	6J8H 2.50	12SJ7 0.80	833A 60.00
A1834 7.50	EBF83 0.85	EM1 9.00	M8225 3.50	QS1203 4.15	UJ5 3.50	3B2 3.00	6B8D 1.50	6J8J 2.50	12SN7GT 1.85	866A 4.50
A1896 11.50	EBF85 0.95	EM4 9.00	ME1401 29.50	QS1206 1.05	UJ7 8.00	3B4 7.00	6B8E 2.50	6J8K 4.95	12S7 2.50	872A 27.50
A2087 11.50	EBF85 0.95	EM80 9.00	ME1402 29.50	QS1207 0.90	UJ8 9.00	3B7 4.50	6B8F 1.60	6K8Y/G 3.00	12SQ7GT 3.20	873 60.00
A2134 14.95	EBF89 0.70	EM81 9.00	ME1501 14.00	QS1208 0.90	UY1 3.50	3B24 24.00	6B8G 3.00	6K8Z 3.20	13D3 3.20	884 5.50
A2293 6.50	EBF93 0.95	EM84 1.65	MH4 3.50	QS1208 0.90	UY85 0.70	3B26 24.00	6B8G6G 3.00	6K8Z 3.20	13D7 3.20	930 9.95
A2599 37.50	EBL1 2.50	EM85 3.95	MH4 3.50	QS1209 3.15	V235A/1K 250.00	3B28 12.00	6B8H 1.95	6K8M 2.50	13D9 3.20	931A 13.95
A2792 27.50	EBL21 2.50	EM87 2.50	MHL06 4.00	QS1210 1.50	V238A/1K 295.00	3B26 15.00	6B8H 1.95	6K8T 2.95	13D7 2.50	954 1.00
A2900 11.50	EC0 2.75	EN32 15.00	ML4 4.50	QS1211 1.50	V240C/2K 225.00	3C24 1.00	6B8J 1.20	6L1 2.50	13DR7 2.95	956 1.00
A3042 24.00	EC70 1.75	EN9 1.10	MS4B 5.50	QS1212 3.20	V246A/2K 295.00	3C3 19.00	6B8K7A 1.95	6L15 3.15	13E1 115.100	1299A 0.80
A3283 24.00	EC80 9.50	EN92 4.50	MU14 1.50	QS1215 2.00	V240C/2K 225.00	3C34 1.00	6B8L 1.50	6L19 1.95	13E7 1.50	1619 2.50
AC/HL/DD 4.00	EC81 7.95	ESU150 14.95	MZ1-100 125.00	QS1218 5.10	V241C/1K 195.00	3C35 1.00	6B8M 0.58	6L21 2.50	13E7 1.50	1625 3.00
AC/THI 4.00	EC86 1.00	ESU872 25.00	N37 12.50	QS1218 5.10	V246A/2K 295.00	3C36 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AC122 59.75	EC88 1.10	EV51 0.80	N78 3.85	QS1219 3.15	V246A/2K 295.00	3C37 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AH221 39.00	EC90 1.10	EV51 0.80	OA2 2.85	QS1219 3.15	V246A/2K 295.00	3C38 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AH238 39.00	EC91 5.50	EV83 1.50	OA2 2.85	QS1219 3.15	V246A/2K 295.00	3C39 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AL60 6.00	EC92 1.75	EV84 5.95	OA2 2.85	QS1219 3.15	V246A/2K 295.00	3C40 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AN1 14.00	EC93 1.50	EV86/87 0.50	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C41 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C42 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C43 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C44 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C45 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C46 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C47 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C48 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C49 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C50 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C51 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C52 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C53 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C54 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C55 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C56 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C57 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C58 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C59 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C60 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C61 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C62 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C63 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C64 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C65 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C66 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C67 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C68 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C69 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C70 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C71 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C72 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C73 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C74 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C75 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C76 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C77 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C78 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C79 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C80 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C81 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C82 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C83 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C84 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C85 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C86 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C87 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C88 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C89 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C90 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C91 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00	3C92 1.00	6B8N 1.85	6L22 0.50	13E7 1.50	1626 3.00
AR12 4.00	EC95 7.00	EV88 0.55	OB2 0.85	QS1219 3.15	V246A/2K 295.00</					

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply

**AUDIO FREQUENCY
TRANSFORMERS OF EVERY TYPE
YOU NAME IT! WE MAKE IT!
OUR RANGE INCLUDES**

Microphone transformers (all types), Microphone Splitter/Combiner transformers, Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.

We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E. E. C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.

E. A. Sowter Ltd.

Manufacturers and Designers

E. A. SOWTER LTD. (Established 1941) : Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
P.O. Box 36, Ipswich, IP1 2EL, England
Phone: 0473 52794 and 0473 219390
Telex 987703G Sowter

CIRCLE 86 FOR FURTHER DETAILS.

ELECTRONICS & Wireless World

EDITORIAL FEATURES 1985

ISSUE DATE	PUBLICATION DATE	FEATURE
July, 1985	June, 21st	VDU's
Sept. 1985	Aug. 16th	Communication Receivers

**For more details regarding
advertising
Contact Bob Nibbs
01-661 3130**

It's easy
to complain
about
advertisements.
But which
ones?

Every week millions of advertisements appear in print on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints.

If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code.

Then, if an advertisement bothers you, you'll be justified in bothering us.

The Advertising Standards Authority. ✓
**If an advertisement is wrong,
we're here to put it right.**

ASA Ltd, Dept 2 Brook House, Torrington Place,
London WC1E 7HN

This space is donated in the interests of high standards of advertising.

Appointments

Advertisements
accepted up to 12
noon April 29th for
June issue

DISPLAYED APPOINTMENTS VACANT: £19 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £4.00 per line, minimum £25 (prepayable).
BOX NUMBERS: £5 extra. (Replies should be addressed to the Box Number in the
advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 4AS).
PHONE: IAN FAUX, 01 661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to BUSINESSPRESS INTERNATIONAL LTD. and crossed.



ECM

THE BEST APPROACH

£7,000-£30,000 + CAR

- ★ **Where does your interest lie:** Graphics; CAD; Robotics; Simulation; Image and Signal Processing; Medical; Automation; Avionics; Acoustics; Weapons; Comms; Radar; Opto and Laser?
- ★ **Experienced in:** VLSI; Microprocessor Hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ **There are hundreds of opportunities in:** Design; Test; Sales and Service for Engineers and Managers
- ★ **For free professional guidance:** Call: 0638 742244 (till 8pm most evenings) or write (no stamp needed) to

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
FREEPOST, The Maltings, Burwell, Cambridge. CB5 8BR.

(1926)

MEDICAL RESEARCH COUNCIL INSTITUTE OF HEARING RESEARCH SOUTHAMPTON CLINICAL OUTSTATION

RESEARCH OFFICER IN ELECTRONICS (RO/SRO)

A vacancy exists for a research officer with experience in electronics at IHR Southampton. The post will be based at the Institute of Sound and Vibration Research at the University, but will also relate to the other half of the team's activities, at the Royal South Hants Hospital.

The research is on clinically applicable aspects of hearing and deafness, advanced testing techniques, and the use of signal averaging equipment by computer for which a very high level of technical support is required. The appointee will be required, with minimal supervision to design and construct new equipment involving transducers and interfaces. There will also be a little general technical support for the research team including calibration, repair and servicing work. A general electronics background is needed and a knowledge of Z80 CP/M systems and of digital interface techniques would be advantageous. For further information about the post please contact Dr. A.R.D. Thornton (Tel: 0703 37946).

The appointment will be made on the Research Officer grade (£6483-8492) or Senior Research Officer grade (£8574-10,938). The MRC has a pension scheme and generous leave allowances.

(2566)

CALIBRATION/ SERVICE ENGINEERS

c £8,250 + Overtime + July Review

Bradley Electronics is one of the leading organisations in the electronics industry. We provide a range of advanced electronic equipment and engineering services to MoD, Industry and the Health Care market.

Our Repair and Calibration laboratory, the largest of its type in the UK, provides a comprehensive service for commercial and military organisations, with its full facilities for maintaining and calibrating all types of electronic equipment.

Opportunities exist for Engineers to work with a wide variety of equipment, including Multimeters, Oscilloscopes, Navigation Systems and Electronic Counter Measure Systems. Ability to trace, diagnose and rectify faults in these complex equipments is essential. Education to a minimum of C&G/TEC or equivalent is required, together with considerable practical knowledge and experience in electronic testing, servicing of radar, and telecommunications equipment. Experience of this nature gained in the Services will be of particular value.

The Company is located close to the underground, bus routes and the North Circular Road/M1. The salary and conditions package available is consistent with the Company's membership of a large, successful Group with considerable resources.

For full details please call our Personnel Manager, Roger Loughney, on 01-450 7811. Or write to him at Bradley Electronics Limited, Electral House, Neasden Lane, London NW10 1RR.

Bradley Electronics

(2560)

Appointments

CUT THIS OUT!

Clip this advert and you can stop hunting for your next appointment. We have a wide selection of the best appointments in Digital, Analogue, RF, Microwave, Micro-processor, Computer, Data Comms and Medical Electronics and we're here to serve *your* interests.

Call us now for posts in Design, Test, Sales or Field Service, at all levels from £6,000-£16,000.



Engineering & Technical Recruitment
11 Westbourne Grove, London W2. Tel: 01-229 9239. (1935)

Philip Drake Electronics is a successful and growing company that has now established itself as the leading U.K. supplier of studio communications equipment and programme quality sound distribution modules to the Broadcasting industry.

An increasing workload has lead to a requirement for the following personnel:

PROJECT AND TEST ENGINEERS

Project and test engineers are required to work in the Systems Engineering Group which primarily deals with the custom design, manufacture and test of studio talkback and intercom systems.

Project Engineers should have a suitable engineering qualification and at least two years experience of system/project engineering with professional analogue equipment. The work includes detailed system design, liaison with customers, and technical support for production and test.

Test Engineers should have analogue experience but have the ability to adapt to digital technology. The job entails test custom built equipment from prototype circuit boards to complete studio systems and providing after sales service and support. The post is one which provides excellent opportunities for advancement within the systems group.

TECHNICIAN/JUNIOR ENGINEER

An opportunity exists for a Technician/Junior Engineer to join our product development team. The successful candidate will be involved in all aspects of design from concept to production. He/she will work primarily with analogue circuits although there will be involvement with digital circuits. An ability to work with minimum supervision is essential and it is expected that the successful candidate will be qualified to TEC or degree level although ability is more important. Experience of the professional audio industry would be an advantage.

SOFTWARE ENGINEER

We are currently looking for two suitably qualified software engineers to strengthen our development team. The successful candidates would be required to write software in PASCAL and ASSEMBLER for the MC68000 family and must be able to work on their own initiative with minimal supervision. The ability to communicate ideas clearly is essential.

In addition to attractive salaries, the company offers a non-contributory pension scheme, BUPA membership and a pleasant working environment in newly constructed premises in Welwyn Garden City.

If any of the above positions appeal to you please apply in writing including your current CV or phone Jenni McCoy on Welwyn Garden City (0707) 333886 for an application form.

Philip Drake Electronics Ltd.,
37 Broadwater Road,
Welwyn Garden City,
Herts AL7 3AX.

(2565)

CAPITAL APPOINTMENTS LTD

THE UK'S No. 1 ELECTRONICS AGENCY

If you have HNC/TEC or higher qualifications and are looking for a job in design, test, customer service, technical sales or similar fields:

Telephone now for our free jobs list
We have vacancies in all areas of the UK
Salaries to £15,000 pa

01 808 3050
(24 hours)

CAPITAL APPOINTMENTS LTD
76 WILLOUGHBY LANE, LONDON N17 0SF

(291)

CRANLEIGH SCHOOL

An independent HMC board school of 580 pupils requires a teacher of ELECTRONICS and PHYSICS for September 1985.

The successful candidate who should have a degree in Physics or Engineering will join thriving Departments offering courses in both subjects to A Level. There are excellent opportunities for project work. All help will be given to candidates from industry.

Accommodation available. Salary above Burnham scale, and other benefits.

Applications, with full c.v. and names of two referees, to The Headmaster, Cranleigh School, Cranleigh, — Surrey GU6 8QQ.

(2561)

Don't Forget! for your classified adverts
ring

Ian Faux 01 661 3033

ELECTRONICS ENGINEERS

The future of underwater acoustic design is in West London



At Dowty Electronics Communications Division we are determined to advance our position among the leaders in underwater acoustic design. We see ourselves as making a major contribution to creative engineering through our insistence on the highest standards and by providing the best facilities.

Now we are looking for like-minded electronics engineers - professionals who insist on standards of excellence beyond the accepted and who are continually striving to improve on their own best.

If these attitudes appeal to you and you like working in small specialised teams evolving the future of underwater acoustic design, we have vacancies at all levels for professionals with at least 2 years' experience in one or more of these disciplines:

DIGITAL DESIGN

- signal processing for sonar related systems.
- signal decoding and interface systems.

ANALOGUE DESIGN

- radio frequency applications.
- low frequency audio circuits, filters, hybrids
- low frequency high power audio amplifiers

- audio multiplexing circuits

SYSTEMS DESIGN

- sonar systems, underwater data links

SOFTWARE DESIGN

- development of mathematical models of sonar and underwater systems

TRANSDUCER DESIGN

- underwater transducer design fabrication and measurements

Check where your future lies


Why not discuss informally the opportunities with our design teams. At our well-equipped West London headquarters Prospects for electronic engineers have never been better and you can expect a highly competitive salary and benefits.

For full discussion, please contact Gavin Rendal, on 01-578 0081 during office hours up until 6.00 pm. Alternatively, write to him with full CV, quoting reference #5/01 to Dowty Electronics Limited, Communications Division, 419 Bridport Road, Green'crd, Middlesex UB6 8UA.

Electronics



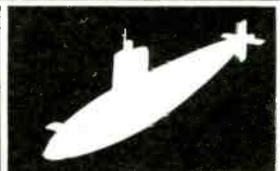**LINKING EVERY
SPHERE BY CREATIVE
ENGINEERING**



(2556)

Appointments

Telecommunications Engineering Technicians


Openings in Servicing and Maintenance Up to £8,873

Our business is to install and maintain the communications equipment used by the Police and Fire Brigades in England and Wales – some of the latest you will find in operation anywhere.

We have a number of vacancies at our Service Centres in various parts of the country, for Telecommunications Engineering Technicians with practical skills in locating and diagnosing faults in a wide range of equipment from computer-based data transmission to FM and AM radio systems.

The work provides excellent opportunities for extending your technical expertise, with specialised courses and training to keep you up to date on developments and new equipment. There are also opportunities for day release to gain higher qualifications.

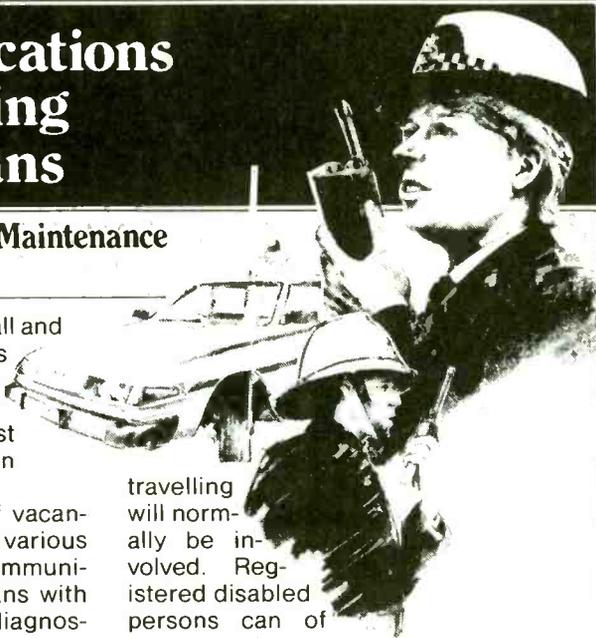Applicants, male or female, must be qualified to at least City & Guilds Intermediate Telecommunications standard and possess a current driving licence. Some



travelling will normally be involved. Registered disabled persons can of course apply.

The Home Office is an equal opportunities employer.

Salary will be on a scale £6501 to £8873 a year with generous leave allowance and pension scheme.

Good prospects for promotion.

If you are interested in working with us, please write for further details and an application form, quoting reference WW/3 to: Miss M Andrews, Home Office, Directorate of Telecommunications, Horseferry House, Dean Ryle Street, London SW1P 2AW.



Home Office

Directorate of Telecommunications

(2557)

BORED ?

Then change your job!

- 1) **TEST CALIBRATION ENGINEERS**
To work on a variety of micro based instruments and A.T.E. Windsor £12,000+
- 2) **REMOTE CAMERA EQUIPMENT**
Test engineers to work on high speed digital systems to £10,000. Surrey.
- 3) **TECHNICIAN ENGINEER**
For maintenance of VAX pdp11 and flight simulation systems. Middx. To £11,000.
- 4) **DATA PROCESSING EQUIPMENT**
Customer service engineer to work on PDP8 and PDP11's, printers and graphics displays. £12,000 + car. Berks/Bucks.
- 5) **MARINE SERVICE ENGINEER**
To maintain a variety of marine communications and navigation systems. Surrey. To £10,000.
- 6) **DEVELOPMENT/TEST ENGINEER**
To design and support a variety of medical systems. £10,000. Berks/Middx.

Hundreds of other Electronic and Computer vacancies to £12,500

Phone or write:
Roger Howard, C.Eng., M.I.E.E., M.I.E.R.E.
CLIVEDEN CONSULTANTS
92 The Broadway, Bracknell, Berkshire
Tel: 0344 489489 (1640)

CLIVEDEN

DESIGN AND DEVELOPMENT ENGINEER

Experienced engineer required to join small electronics company involved in design and manufacture of telecomms products for BT and other PeT authorities.

Applicants should have experience in line equalisation equipment, filters, SMPS and automatic testing using microprocessor techniques.

Qualifications to degree or HNC with suitable experience. Attractive salary + usual benefits to right person.

Application to include current c.v. to: Kenton Research Ltd. Europe Trading Estate, Erith, Kent DA8 1QL. Telephone: (032 24) 419 33

(2519)

ELECTRONICS TECHNICIAN

The electronics and computer services department of Inco's refinery in North West London is concerned with the construction and installation of process control equipment and the maintenance of bought in hardware.

A vacancy now exists for a suitably qualified person with demonstrable practical and logical ability to assist with the work of the department.

Starting salary will be based on qualifications and experience. £8000 — £9000. Other benefits include non-contributory pension and life cover scheme. Subsidised canteen, sports and social club, car park, 23 days holiday.

Please write or telephone for an application form to: D.J. Booker, Personnel Officer, Inco Europe Ltd., Bashley Road, London NW10 6SN. Tel: (965) 6031

(2567)

INCO
INCO EUROPE LIMITED

The Publishers take all reasonable care to ensure that classified advertisements are genuine, but readers must satisfy themselves that they will be obtaining what they require before entering into transactions, particularly if they involve large sums of money. (2519)

SCOTTISH OFFICE DIRECTORATE OF TELECOMMUNICATIONS WIRELESS TECHNICIAN (£6,501 — £8,873) (CURRENTLY UNDER REVIEW)

Applications are invited for 2 posts of Wireless Technician in the Central Services Department of the Scottish Office. The posts are based in East Kilbride and Edinburgh.

Candidates must have a sound theoretical and practical knowledge of radio communications systems both fixed and mobile, in the frequency range H F to 2 GHz. They must also be able to use test equipment and simple machine tools. A sound basic knowledge of digital techniques would be an advantage. They should have a minimum of 3 years appropriate experience and should hold an ordinary National Certificate in Electronic or Electrical Engineering or a City and Guilds of London Institute Certificate in an appropriate subject or a qualification of higher or equivalent standard. Some assistance may be given with re-location expenses.

A valid UK driving licence is essential.

Application forms and further information are obtainable from Scottish Office, Personnel Division, Room 110, 16 Waterloo Place, Edinburgh EH1 3DN (Quote Ref PM PTS) 1/4/85 (031-556 8400, Ext. 4317 or 5028).

Closing date for receipt of completed application forms is 10 May, 1985.

THE CIVIL SERVICE IS AN EQUAL OPPORTUNITY EMPLOYER. (2572)

**HAMPSTEAD HEALTH
AUTHORITY
ROYAL FREE HOSPITAL
MEDICAL PHYSICS
DEPARTMENT
ELECTRONICS
TECHNICIAN**

Salary: Grade II - £8802 - £10711
or Grade III £7492 - £9367

A Senior Technician is required to join a team looking after a wide range of sophisticated medical equipment at this modern hospital near Hampstead Heath.

The post offers an excellent opportunity to gain experience on equipment such as linear accelerators and computer controlled radiotherapy machines etc. A good knowledge of electronics is essential and an HNC full Tech or equivalent qualification and 3 years experience is needed for the Grade III post.

Experience with the above equipment is not necessary as training will be given.

For job description and application form please contact the Personnel Department, Royal Free Hospital, Hampstead, London NW3. Telephone 01 794 0500 ext 4286

Closing date: 10 May 1985

(2559)

Electronics Engineer

An Electronics Engineer is required by a small but expanding company manufacturing equipment for the Security Industry. An engineer with practical ability and both analogue and digital experience is required for development of new products, improving existing products, design and building of test equipment occasional assistance with testing and general technical assistance to the management.

Applicants should have some years experience and possess HNC/HND minimum qualification. Applicants should write, enclosing full C.V. to:

Mr. D.G. Wills,
Aro Dynamics Westmorland Road,
Kingsbury, London NW9 9RR
(2564)

**MAINTENANCE
ENGINEER**

Required by busy London Studio complex. Digital and Analogue tape machines + state of the art consuls. We need someone bright, practical and hardworking who responds well to pressure in a creative environment. If you can keep your head when all about you are losing theirs, write to: Box. No. 2571

c/o Electronics and Wireless
World,
Quadrant House,
The Quadrant, Sutton, Surrey.
SM2 5AS
(2571)

TECHNOLOGY TRAINING

Fundamental to future success in advanced electronics

GEC Avionics is one of the world's most innovative and successful designers of airborne and surface-based electronic and radar systems.

Top quality training is fundamental to future success in our competitive industry. We have already invested in a modern technology training centre for technicians, technician engineers, apprentices and graduates and are now investing in the following high-calibre personnel.

Technology Training Officer

Your task is to develop new course material for specialised fields. Responsibilities include overall planning; programming; course development; day-to-day control of the centre; and some lecturing.

You must have electronics lecturing/training experience in a similar centre, College of Further Education or armed forces training establishment.

Apprentice Instructor

Over 100 apprentices undergo instruction in the application of tools and techniques at the centre. Your task is to help plan and implement 1st year Craft and Technician training programmes, recommending the most effective means of developing apprentices' Craft and Electronics skills to TEC standards.

Time-served and with an HNC or equivalent, you must be energetic, resourceful and communicative. Lecturing experience is preferred, but training will be provided.

We offer exceptional working conditions, an attractive salary and comprehensive benefits including relocation assistance if appropriate.

GEC AVIONICS

For further details please telephone or send your CV to Malcolm Howard, Assistant Personnel Manager, GEC Avionics Limited, FREEPOST, Elstree Way, Borehamwood, Hertfordshire WD6 1BR. Telephone 01-906 6230. Alternatively telephone our 24-hour answering service on 01-207 3455. Please quote reference GA/85-007.

(2563)

CAPACITY AVAILABLE

FREE P.T.H. PROTOTYPE of the finest quality with EVERY P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited, 34, High St., Halstead, Essex. Tel. (0787) 477408/474554. (2126)

VALVES, PROJECTOR Lamps, 6000 types, list 75p, world wide export. Cox radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Phone (0243) 672023 (1991)

SERVICES

Williams P.C.B. Artwork, 49 Westbourne,
Mossybourne, Evesham, Worcs. WR11 5PT.
(2537)

QUICK TURNROUND FOR PCB REPAIRS

Let Jacrow check-and-repair your boards on ATE, quickly and accurately, UK and overseas. Phone 01-680 9191 for full details, without obligation. Jacrow Systems Services, 29/31 Lower Coombe Street, Croydon, Surrey CR9 1LX. Quote ref: EW585 (2471)

Computers
in engineering and broadcasting

PROGRAMS FOR PROGRAMMES

BBC Bush House, London

Bush House is the broadcasting centre of BBC External Services. From 50 studios we broadcast radio programmes in 36 languages, 24 hours a day. Its facilities represent some of the most advanced broadcasting technology currently available.

To support our operations, we make extensive use of computers. Our Electronic Distribution System, comprising a digital processor and over 200 peripheral terminals, is used to collect, edit and distribute the text of News and Current Affairs programmes. The Control Room uses a processor controlled switching system to route programmes to transmitters, throughout the world, via lines and satellites. The Test Room utilises sophisticated Test equipment and micro-computers for the acceptance, modification and repair of the wide range of advanced broadcast equipment used in Bush House studios.

Our increasing involvement with leading-edge technology means we require more Engineers to operate, maintain and develop our electronic systems, both hardware and software, in both EDS and Test Areas.

Qualified to degree level in Electronics or equivalent, you must have good knowledge of electronics, analogue and digital techniques, an understanding of processor concepts and knowledge of programming at assembler level. Normal hearing and colour vision are essential.

Salaries are currently under review – additional allowances are paid for shift work, nights and weekend working together with a London Weighting Allowance.

Applicants with a bias towards digital electronics to work in the EDS area, or those with practical test experience with an interest in professional audio equipment, should write, clearly indicating their preference to:

The Engineering Recruitment Officer, BBC, P.O. Box 2BL, London W1A 2BL, quoting ref: 85.E.4019.

BBC

We are an equal opportunities employer.

(2569)

WANTED

- * MICROCOMPUTERS
- * PERIPHERALS
- * INSTRUMENTATION

For fastest, best CASH offer, phone,
COMPUTER APPRECIATION
Oxford (0865) 55163
Telex 838750

(2492)

STEWART OF READING
110 WYKHAM ROAD
READING RG6 1PL
TEL NO: 0734 68041

**TOP PRICES PAID FOR
ALL TYPES OF SURPLUS
TEST EQUIPMENT,
COMPUTER EQUIPMENT,
COMPONENTS etc.**
ANY QUANTITY.

(2616)

**When replying to classified
advertisements, readers are
recommended to take steps
to protect their interests
before sending money**

(2519)

**SMALL SELECTION ONLY LISTED
RING US FOR YOUR
REQUIREMENTS WHICH MAY BE
IN STOCK**



Portable Battery or Mains Oscilloscope. SE Laboratories 111 Oscilloscope — Solid State — General purpose — Bandwidth DC to 18/20MC/S at 20MV/CM — Dual Channel — Rise time 19NS — Calibrated Sweep — Calibrator — Display 10CMx8CMs — Power AC — 95 Volts to 100-190 Volts to 260 or 24 Volt DC battery — Size: W 25.5 CM — H 25.5 CM — H 25.5 CM — 56CMs Deep — WT 11.4 KGS — Carrying handle — Tested in fair condition with operating instructions £120.00.



Latest Bulk Government Release — Cossor Oscilloscope CDU150 (CT531/3) £150 only. Solid state general purpose bandwidth DC to 35MHz at 5MV/CM — Dual Channel — High brightness display (8x10cm) Full delayed time base with gated mode — Risetime 10NS — Illuminated graticule — Beam finder — Calibrator 1KHz squarewave — Power 100 — 120V/200V — 250 volts AC — Size W 26CM — 41CM deep — WT 12.5 K.G. carrying handle — colour blue — protection cover front containing polarized viewer and camera adaptor plate — probe (1) — Mains lead. Tested in Fair condition with operating instructions — £150.00.


Communication Receivers: Racal 500KC/S to 30MC/S in 30 bands 1MC/SWIDE — RA17 MK11 £125. RA17L £150. RA17E £200. New Metal Louvred Cases for above £25. All receivers are air tested and calibrated in our workshop — supplied with dust cover — operation instructions — circuit — in fair used condition. Racal Synthesisers (Decade frequency generators) MA3508 Solid State for use with — MA79 — RA217 — RA1218 Etc £100 to £150. MA250 — 1.6MC/S to 31.6 MC/S £100. MA1350 for use with RA17 receiver £100. MA259G Precision frequency standard 5MC/S — 1MC/S — 100KHz £100 to £150. Panoramic Adaptor RA66 £150. RA137 and RA37 £40 to £75 LF converters 10 to 90KC/S. RA216 Independent SSB unit £50 RA98 SSB-ISM Converter £50. RA121 SSB converter £75. EC96/47K Solid state — single channel — SSB — mains or battery — 1.6 to 27.5 MC/S and 400 to 535KHz £100 with manual Plessey PR155G Solid State 60KC/S — 30MC/S £400. Creed 75 Teleprinters — Fitted tape punch and gearbox for 50 and 75 bauds — 110Volts AC supply — in original transport tray sealed in polythene — like new £15EA. Redifon TT11 Audio Teleprinter converter receiver solid state — supply 110 or 240AC — Made for use with above teleprinter enabling print-out of messages received from audio input of communication receiver £15 with circuit tested. Redifon TT10 Converter as above but includes transmit facilities £20. Oscilloscopes — stocks always changing Tektronix 465 — 100MC/S £750. FM Recorder Sanghmd Sabre 111 14 channels £350. Transtel Matrix printers — AF11R — 5 level Baudot Code — up to 300 Bauds — for print out on plain teleprinter paper £50 to £100. Transtel AH11R — As above but also 8 level ASC11 (CCITT No 2 and CCITT No 5) Like new £100. Army field telephone sets. Type F — L and J — Large quantity in stock £5 to £15 depending on type and quantity P.O.R. Don 10 Telephone Cable — half mile canvas containers £20. Night viewing infra-red AFV periscopes — Twin Eyepiece — 24 volt dc supply £100ea. Original cost to government over £11,000ea. Static inverters — 12 or 24 volt input — 240 volt AC sine wave output — various wattages P.O.R. XY Plotters and pen recorders various — P.O.R. Ferrograph series 7 Tape recorders mono £100. stereo £150. Signal Generators various — TF995/A3 £60. TF801D/8s — 10MC/S to 485MC/S £90 TF144H/A4 £90. TF1060/2 £60. HP606A — £90 £140 HP608 £50 HP614A £100 HP616B £100 HP620A £100. Marconi TF1064B/S £100 TF791 Deviation meter £100. TF833A Power meter £50 Aerial mast assembly 30ft high complete with 16ft whip aerial to mount on top — guyropes — insulators — Base and Spikes etc. in heavy duty carrying bag — new £30. Racal frequency counter Type 836 £50 Tektronix plugs-ins — 1A1 £50. 1A2 £40. 1A4 £100 ME50. All items are bought direct from H.M. Government being surplus equipment. Price is Ex works. S.A.E. for enquiries. Phone for appointment for demonstration of any items. Also availability or price change. V.A.T. and carriage extra.

**EXPORT TRADE AND QUANTITY
DISCOUNTS GIVEN**
JOHNS RADIO (0274) 684007
WHITEHALL WORKS,
84 WHITEHALL ROAD,
EAST BIRKENSHAW, BRADFORD
BD11 2ER

WANTED. REDUNDANT TEST EQUIPMENT — RECEIVING AND TRANSMITTING EQUIPMENT — VALVES — PLUGS — SOCKETS SYNCHROS ETC.

(2743)

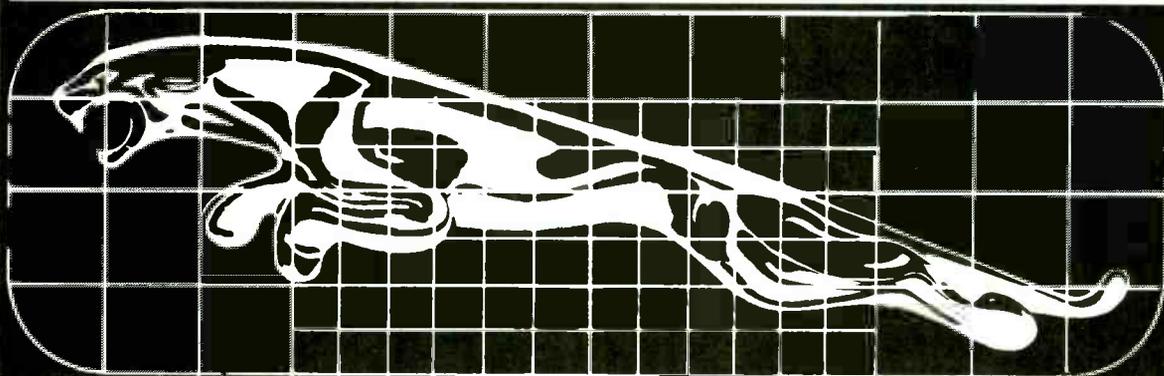CREATIVE ENGINEERS EXPERIENCED IN ELECTRONICS OR INSTRUMENTATION?



—THEN MAKE THE JAGUAR CONNECTION...

... to do so you'll need to be amongst the best in your field but if you are you'll be joining a team of dedicated professionals who are totally committed to keeping the name Jaguar at the forefront of advanced automotive engineering excellence.

ELECTRONICS DESIGN AND DEVELOPMENT ENGINEERS

The design and development of electrical components and full systems is a challenging brief. It demands a high level of self motivation to meet project deadlines through inspired project management within the company and by close liaison with component suppliers.

A degree in electronics is therefore essential as is considerable electronic/electrical engineering experience preferably gained in an automotive environment.

INSTRUMENTATION ENGINEERS

The perfection of Jaguar Cars requires sophisticated measurement techniques both on experimental test rigs and in devising dynamic vehicle tests.

This is where your challenge begins.

To meet it you'll need to be capable of preparing transducers, processing circuits and recording equipment or a background in software for control applications.

Proven technical ability in the instrumentation/electronics field is therefore essential as is a high level of self motivation.

Salaries are negotiable and could be up to £11,000 inclusive of bonus and the benefit package is as you would expect from a major employer.

Make the Jaguar connection now by writing in confidence with full C.V. to:


Mark Hails,
Officer, Organisation and Personnel Planning,
Jaguar Cars Limited,
Browns Lane,
Allesley,
Coventry CV5 9DR

We are an equal opportunity employer.



ARTICLES FOR SALE

DRIOTWICH STANDARD FREQUENCY RECEIVER

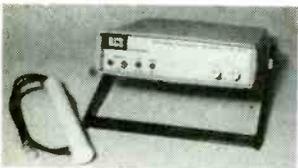

Outputs, 1MHz, 10MHz
Phase locked crystal oscillator. Complete with ferrite rod aerial, usable throughout U.K. Now available in updated version.
£185.00
R.C.S. Electronics, Wolsey Road, Ashford, Middx. Phone 53661. (2656)

Quartz Crystal Units
ACCURATE
RELIABLE

Private enquiries, send 13p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY 01-942 0334 & 2968 (8493)

FM BROADCAST EQUIPMENT

A special range of high quality transmitters, power amplifiers, stereo encoders, UHF repeater links, compressors, antennas etc.

Built to high specifications at an economic price. VHF/UHF data and telemetry systems (MPT 1309) available ex-stock.

Full catalogue available.

Cyberscan International, 3 Eastcote View, Pinner, Middx HA5 1AT.
01-866 3300

(2542)

CAPACITY AVAILABLE

FOR THE BEST PCB SERVICE AVAILABLE

*Circuit Design & Development
Digital and Analogue

*Artwork Layout
PCB artwork layout and mechanical detailing. P.O. approved standard.

*Board Manufacture
Prototype to semi-production, excellent rates.

*Wiring & Assembly
PCB assembly, wiring and cable forming. Flow soldering facilities available.

*Test
Full test facilities available.

One or all services available.
Please telephone Chelmsford (0245) 357335, or write to HCR Electronics, The Industrial Unit, Parker Road, Chelmsford. (30mins from Liverpool Street St.)



(1169)

Appointments

DESIGN/ DEVELOPMENT OPPORTUNITIES

Cambridgeshire

Cathodeon Crystals Ltd (a member of the CEI Group) is a leading Manufacturer of precision components for the Telecommunications industry.

The Company is currently involved in a number of new projects and is seeking to expand it's Development department as part of it's planned growth.

Filter Designer

We are looking for an ambitious Electronics Engineer to work on the development of high performance Crystal Filters. We are interested in hearing from persons with practical experience of Filter design who have the drive and ability to see the projects through to the production stage. Those without previous Filter design experience would be considered as trainee engineers provided they have the appropriate skills.

Graduate Engineer

Instrument Development

A Design and Development Engineer is required to be responsible for the development of a range of high precision X-ray measurement machines from conception to production stage.

The post is of a multidisciplinary nature and is likely to appeal to those who have an interest in, or experience of, equipment design, precision machines, software development, electronics. Specific experience in these disciplines is less important than an analytical approach to problem solving and the ability to work to strict deadlines. Ideally candidates should be a graduate in a scientific discipline.

Being part of a major Group the company is able to offer a range of employment conditions normally associated with a large employer.

Salary will be commensurate with the importance of this position. Relocation assistance is available where appropriate.

If you are interested in either position, please contact Christina Moon, Personnel Manager, Cathodeon Crystals Ltd, Linton, Cambridge, CB1 6JU. Tel (0223) 891501.

(2568)



**CATHODEON
CRYSTALS**

WANTED

CIRCOLEC THE COMPLETE ELECTRONIC SERVICE

Artwork, Circuit Design, PCB Assembly, Test & Repair Service, Q.A. Consultancy, Prototypes, Final Assembly. Full PCB Flow Soldering Service.

Quality workmanship by professionals at economic prices. Please telephone 01-646 5686 for advice or further details.

**TAMWORTH MANOR
302-310 COMMONSIDE EAST, MITCHAM**

(1391)

WANTED

SURPLUS

We offer good prices for test equipment, components, redundant computers, PCB's connectors. Immediate settlement.

TIMEBASE

94 Alfriston Gardens
Sholing, Southampton SO2 8FU
Telephone: (0703) 431 323

(1832)

E C COMPONENTS

We buy large and small parcels of surplus I/C, transistors, capacitors and related electronic stock. Immediate settlement.

Tel: 01-208 0766
Telex: 8814998

(2491)

WANTED

All types of surplus electronic components and equipment. We specialise in factory clearance.

**SGS Electronics,
The Vineyard, Bowley Lane,
Boddendam, Herefordshire
HR1 3LF. Tel (056) 884 532**

(2541)

WANTED SURPLUS ELECTRONIC COMPONENTS AND EQUIPMENT

We also welcome the opportunity to quote for complete factory clearance

**B. BAMBER ELECTRONICS
5 STATION ROAD, LITTLEPORT, CAMBS.
Phone: Ely (0353) 860185**

(2483)

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO

**86 Bishopgate Street
Leeds LS1 4BB
0532 435649**

(9956)

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC.

LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.

ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE
TELEPHONE: 445 0749/445 2713

R. HENSON LTD.

21 Lodge Lane, North Finchley, London, N.12

(5 minutes from Tally Ho Corner)

(1613)

SERVISCOPE

EAST STREET, FARNHAM, SURREY.

TEL: 0252 722666

CONTACT: G.P. SKINNER

A SELECTION OF TELEVISION AND ELECTRONIC COMPONENTS FOR DISPOSAL

68 PF Ceramic Cap
470 PF Pulse Ceramic 12K
PYE 731/728 - Mains Switch
TEC - 8000/8500 Therm Cut Out
GEC - 1040/Therm Cut Out
IN4002
BC308B
BD137
BC307
BAX 13
TAA661
PHIL 210 - Brightness Knob
PHIL 210 - Volume Knob
TEC 1500 - Brill/on-off Knob

TEC 1500 Earth Strip UHG Tuner
PHIL G8 Focus Control
PHIL G8 UHG Tuner
VRRistor - E299/DC/p348
TEC 1400 Mains Dropper
PHIL 210 Frame Out Put Transformer
PHIL G8 AFC Assembly
PHIL G8 - Vision Selectivity Assembly
PHIL G8 - Vision Gain Assembly
PHIL G8 - Sound Selectivity Assembly
PCF80
PL36
EF184

CATHODE RAY TUBES COLOUR

A51 - 110X/A51 - 220X A67 - 120X A56 - 120X

ALL AT KNOCK DOWN PRICES

- FOR A DETAILED LIST PLEASE APPLY TO

0252-722666

(2533)

COMPUTER APPRECIATION

16 Walton Street, Oxford OX1 2HQ

Tel: Oxford (0865) 55163 Telex: 838750

IBM PERSONAL COMPUTER Model XT, with single floppy & 10MB Winchester AS NEW £2,700.00
 UNITRON Model 2200 microcomputer. APPLE II/e & CP/M compatible machine with 6502 & Z80 processors, 64kbyte memory, detached keyboard with numeric pad and floppy disc interface. BRAND NEW & BOXED £350.00
 COMPAQ PLUS IBM PC COMPATIBLE portable computer with 10MB hard disk, single floppy disc, 640k bytes, graphics, comprehensive software etc. AS NEW £2,900.00
 ROCKWELL AIM 65/40 single board 6502 development system with display, keyboard, power supply and cassette recorder £525.00
 PHILIPS P2000 SYSTEM comprising, 48K Z80 processor with integral tape drive, twin 5 1/4" floppy disc drives, HONEYWELL Model L32 120cps matrix printer. Runs CP/m £850.00
 OLYMPIA BOSS MICROCOMPUTER, small Z80 based business system with 80 col. screen, 64k byte memory, twin 5 1/4" floppy disc drives, HONEYWELL Model L32 120cps matrix printer. Runs CP/M £550.00
 MANNESMANN/TALLY Model M80MC matrix printer. With microprocessor control, 200cps bidirectional PRINTING WITH U/L case, self test. Compact but heavy duty machine. BRAND NEW & BOXED £125.00
 CENTRONICS Model 730-2 matrix printer £95.00
 CENTRONICS Model 702 matrix printer, 132 col. 165cps, bidirectional printing with self test. In good ex-demo condition £225.00
 DEC boxes & power supplies. Various models available (BA11MF, SB11AA, BA11LX) all with 22 bit addressing or easily modified & various optional processors etc. P.O.A.

ITT Model 350 TELEFAX Facsimile transmitter/receiver. Microprocessor controlled (8085) CCITT Group 2 machine for transmitting documents over an ordinary phone line. BRAND NEW AND BOXED £350.00
 TEKTRONIX Model 4601 hard copy unit for 400 series graphics terminals £95.00
 TEKTRONIX Model 611 graphics storage display. For use with any DAC computer output. £150.00
 FACIT Model 4020 high speed paper tape reader. Parallel TTL interface £225.00
 FACIT Model 4070 PAPER TAPE PUNCH. BRAND NEW £350.00
 CALCOMP Model 563 AO drum plotter 0.1mm step size £650.00
 CALCOMP Model 763 AO plotter. As above, but high speed P.O.A.
 CALCOMP Model 1036 AO graph plotter. High speed 3 colour plotter with Type 915 magnetic tape unit for optional off-line use, & selectable for 7/9 track, 800/1600 b.p.i. etc. P.O.A.
 C.I.L. Model 6000, 2 pen AO high speed graph plotter P.O.A.
 HEWLETT-PACKARD Model 75C portable computer £350.00
 HEWLETT-PACKARD Model 85 desk top computer with integral graphics display, printer & tape drive. Includes printer interface (82949A), ROM drawer (82936A), 16K expansion (82903A) & I/O ROM (15003) £850.00
 GOULD-BRYANS Model 50000 graph plotter. 380mm x 280mm plotting area with 0.1mm resolution and vector plotting speed of 35cm/s. With intelligent controller providing 112 character set at 4 orientations RS 232 interface. NEW £985.00
 HEWLETT-PACKARD Model 41C calculator with printer £125.00
 GENERAL DATACOMM (IAL) Model LDM-1 private line modem £150.00
 GENERAL DATACOM Model TDM 1240 4 line statistical multiplexer as used with above modem. 280 controlled. Manufactured 1981 £150.00
 SONY U-matic video recorder with stereo sound £150.00
 DEC LSI-11/23 processor with MMU £500.00

Please note: VAT & CARRIAGE extra on all items * Visitors by appointment, please * Technical manuals are available from us for many items stocked.

CIRCLE 83 FOR FURTHER DETAILS.

ELECTRONICS & Wireless world

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 95 - 103

	PAGE		PAGE		PAGE
ABI Electronics Ltd	1	Electronics & Wireless World Production	69	Pantechnic	10
Advertising Standard Authority	94	E & WW Editorial Features List	94	Pinapple Software	16
AEL Crystals	14	Farnell Instruments	Inside front cover	PM Components	92/93
AF Bulgyn	80	Field Electronics	69	Pye Unicam	49
Airlink Transformers	10	Fylde Electronics Laboratories	16	Radio Code Clocks	52
AM Electronics	20	GNC Design	26	Ralfe Electronics	74
Amplicon Electronics Ltd	68	Gould Instruments	44	Radford Electronics	36
Andelos Systems	16	Greendale Electric	89	Radio Components Specialists	12
Armon Products Ltd	58	Greenwood Electronics	26, 85	Radio Society of Great Britain	69
Aspen Electronics	52	Hameg Ltd	64	Richardson Electronics	60
Barrie Electronics Ltd	72	Happy Memories	20	R. Withers Communications	11
Beckenham Peripherals	80	Harris Electronics	58	R. Henson	20
Black Star Ltd	26	Harrison Bros	10, 29	Sarel Electric Ltd	50
Bytron Ltd	14	Hart Electronics	80	Seasim Controls	64
Bulgyn	90	Henrys/Audio Electronics	20	Service Trading Co Ltd	35
CA Electronics	82	Hi Tech Electronics	25	Sherwood Data Systems	14
Cambridge Kits	26	ILP Electronics	12/29	Solar Banner (European) Ltd	72
Cambridge Microprocessor Systems	11	Industrial Auctions	90	Stewart of Reading	16
Carston Electronics	36	JAF Graphics	52	Strumech Engineering	82
Caracal Power Products	29	J. Bull (Electrical) Ltd	90	Surrey Electronics	58
Computer Appreciation	104	KT Manner's	29	Tape Automation Ltd	85
Clark Masts	42	Langrex Supplies	30	Taylor Bros (Oldham)	58
Conquin Software	Inside back cover	LJ Electronics	10	Technomatic Ltd	4/5
Cricklewood Electronics	44	Lyons Instruments	80	Tektronix	43
Crotech Instruments	89	Manby Electronics	74	Television	44
Cybernetic Applications	35	Martin Associates (Electronics)	52	Thandar Electronics	60
Dannell Electronics Ltd	72	Measurement Devices Ltd	50	Thanet Electronics Ltd	50
Dataman Design	57	Midwich	51	Thurlby Electronics	88
Dewsbury Electronics	82	Monolith Electronics	42	Triangle Digital Services	35
Display Electronics	78/79	Newrad Instrument Cases	14	Valradio Ltd	74
EA Sowter Ltd	94	Number Ones System's	36	Vellerman (UK) Ltd	8
Electronic Equipment Co.	11	Jack Mantel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 4415 - Telephone (216) 621 1919.		W. Waugh Instruments	12
Electrovalue Ltd	42	Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.		Waurad Electronics	59
EMS Manufactures	80	Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone (404) 237 7432.			
Essex Electronic Centre	36	Mike Loughlin Business Press International, 15055, memorial Ste 119, Houston, Texas - Telephone (713) 783 8673.			
European Electronic Systems	Back cover	Canada: Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.			
		*Also subscription agents			

OVERSEAS ADVERTISEMENT AGENTS

France and Belgium: Pierre Mussard, 18 - 20 Place de la Madeleine, Paris 75008.

Hungary: Ms Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan. Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku 106. Telephone: (03) 585 0581.

United States of America: Jay Feinnan, Business Press International Ltd, 205 East 42nd Street, New York, NY 10017 - Telephone (212) 867-2080 - Telex: 23827. Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone (312) 63074. Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Jack Mantel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 4415 - Telephone (216) 621 1919. Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301. Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone (404) 237 7432. Mike Loughlin Business Press International, 15055, memorial Ste 119, Houston, Texas - Telephone (713) 783 8673. Canada: Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269. *Also subscription agents

CIRCUIT BOARD DESIGN WITHOUT THE TEDIUM

smARTWORK lets the design engineer create and revise printed-circuit-board artwork on the IBM PC or compatibles.

Forget tape. Forget ruling. Forget waiting for a technician, draftsman, or the CAD department to get to your project. smARTWORK software turns your IBM PC or compatible into a professional, high quality drafting tool. It gives you complete control over your circuit-board-design — from start to finish.

What makes smARTWORK so smart is that it understands electrical connections. Conductor spacing is always correct, lines do not become too narrow, and connecting lines do not intersect other conductors. smARTWORK can automatically find and draw the shortest route between two conductors. Or you can specify the route.



smARTWORK is the only lowcost printed-circuit-board artwork editor with all these important advantages:

- Complete interactive control over placement and routing
- Quick correction and revision
- Production-quality 2× artwork from pen-and-ink plotter
- Prototype-quality 2× artwork from dot-matrix printer
- Easy to learn and operate, yet capable of sophisticated layouts
- Single-sided and double-sided printed-circuit boards up to 10×16 inches
- Multicolour or black and white display
- 32 user selectable colour combinations; coincident points may be displayed in contrasting colours
- Can use optional Microsoft Mouse as pointing device

System Requirements

- IBM PC, XT or compatible with 192K RAM, 2 disk drives and DOS 2.0
- IBM Colour/Graphics Adapter with RGB monitor or B & W monitor
- Epson MX-80/MX-100 or FX-80/FX-100 dot-matrix printer
- Houston Instruments DMP-41 pen-and-ink plotter (optional)
- Microsoft Mouse (optional)

The Smart Buy

At £895 (+VAT) smARTWORK is exceptional value, particularly when compared to conventional engineering workstation costs.

Write to the address below or use the enquiry card for more information on smARTWORK. Or call Richard Lambert on 0524 381423 to arrange a FREE demonstration or to discuss your requirements.

Starter kit comprising of: SAM 2001 PC, monochrome monitor, FX-100 dot matrix printer, DOS-2.0, smARTWORK, 1 Year on-site maintenance and much more..... £3995.00

Starter kit plus 10M hard disk drive..... £4995.00

Colour monitor..... £395.00

Microsoft Mouse..... £149.00

Pen and ink plotters from..... £1795.00

smARTWORK..... £895.00

smARTWORK Demo disk....£10.00

10% Discount on all Orders processed and paid for before 28th February 1985.

Note: All prices exclude VAT and are subject to change without notice.

Terms: Strictly CASH WITH ORDER.

Conguin Software, 20 Morecambe Road, Lancaster LA1 5JA
Phone: 0524 381423 CIRCLE 2 FOR FURTHER INFORMATION


Spot On!

Time has been our business since 1974.
Precision has been our aim.
We have experience in display,
code generation, off air time,
off air frequency and
frequency standards.
Single units to the largest system.

Our time is at your disposal.



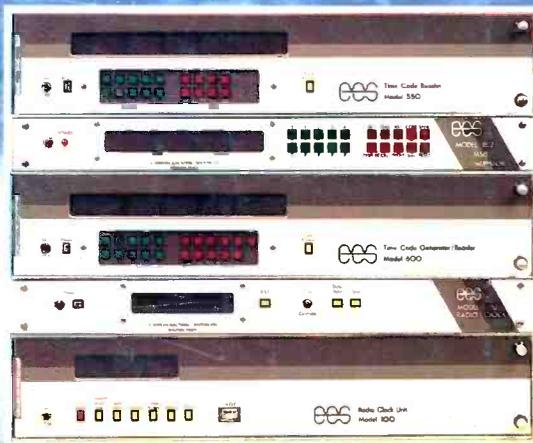**European Electronic
Systems Limited,**
Woodham Mortimer Place,
Maldon, Essex. CM9 6SW.
Telephone: 024541-5911.
Telex: 995917



Time Code Reader.

MSF Rugby Simulator.

Tape Search System.

Radio Clock (5 mSec)

Radio Clock (500 μ Sec)

Made in England.

CIRCLE 3 FOR FURTHER INFORMATION