

# Wireless Weekly

and the Wireless Constructor.

Vol. 4.  
No. 13.

## CONTENTS

5XX at Work.


Garden Aerials.

A Useful Grid Bias Unit.

Novel Detector.

A Carborundum Crystal Receiver.

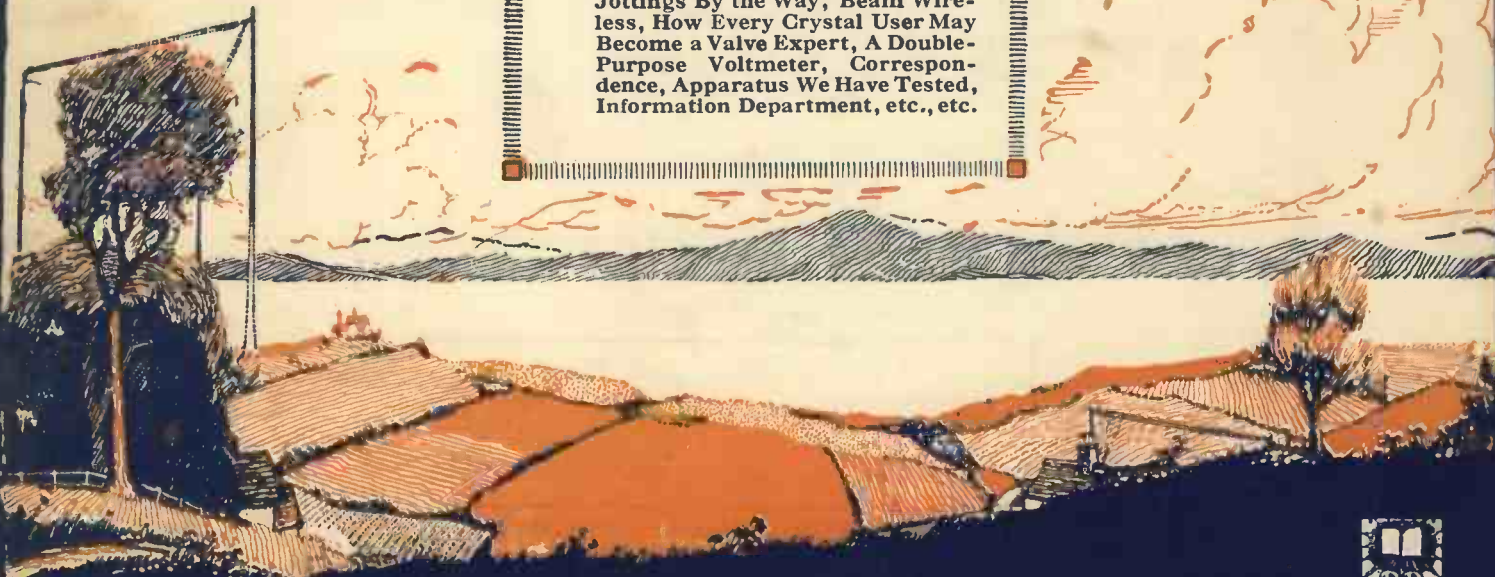Valve Notes, Random Technicalities, Jottings By the Way, Beam Wireless, How Every Crystal User May Become a Valve Expert, A Double-Purpose Voltmeter, Correspondence, Apparatus We Have Tested, Information Department, etc., etc.



## H.F. Transformers Explained



## Every step fully explained—

**E**VEN if a man has never built a Set before—if he has never had the opportunity of examining one closely—if he knows absolutely nothing about Wireless—if he has no friends to advise him—he could still select a suitable design from among those described in **"Wireless Sets for Home Constructors,"** and get splendid results from the very beginning.

The complete beginner—if he lived near a Broadcasting station—would probably build one of the Crystal Sets. Even if he wished to start with a Valve Receiver right away, without going through a probationary period

on a Crystal Set, he would find the 2-Valve Broadcast Receiver a wonderfully simple and efficient instrument, costing but little for material. The more advanced experimenter, on the other hand, will appreciate the many exclusive and original features which are incorporated in the 4-Valve Universal Receiver—its sensitiveness and its power.


In any case, we would emphasise that the reader will find every step fully described and explained in the clearest and most interesting manner.

### SHOWS HOW TO BUILD:

Simple Crystal Receivers.      A three-valve Regenerative Receiver.  
An inductively-coupled Crystal Set.      A single-valve Reflex Receiver.  
A two-valve Low Frequency Amplifier.      A three-valve Broadcast Receiver.  
A two-valve Broadcast Receiver.      A four-valve Universal Receiver.

Together with information as to the testing and operation of Receiving Sets

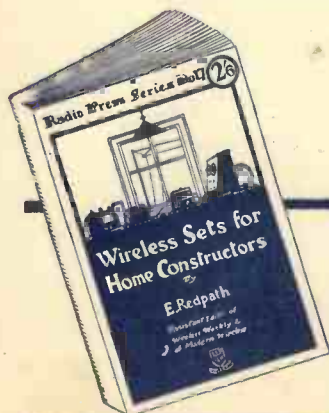Published by Radio  
Press Ltd., Devereux  
Court, Strand, W.C.2.  
Post free 2/8.



## Wireless Sets for Home Constructors By E. Redpath.

2/6

Radio Press  
Series No 17.





# Wireless Weekly

Vol. 4, No. 13  
July 30, 1921

## CONTENTS

	Page
Editorial .. .. .	398
Garden Aerials .. .. .	399
Jottings By The Way .. .. .	401
Beam Wireless .. .. .	403
Valve Notes .. .. .	406
5XX at Work .. .. .	408
Practical Back-of-Panel Wiring Charts .. .. .	411
Utilising Valves to Best Advantage .. .. .	412
Random Technicalities .. .. .	414
A Novel Crystal Detector .. .. .	415
High-Frequency Transformers .. .. .	416
A Double Purpose Voltmeter .. .. .	419
How Every Crystal User May Become a Valve Expert .. .. .	420
Time Signals .. .. .	423
Correspondence .. .. .	424
Apparatus We Have Tested .. .. .	427
Information Department .. .. .	429

Editor: JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.

Assistant Editors: { P. W. HARRIS.  
E. REDPATH.

### Radio Press, Ltd.

Publishers of Authoritative Wireless Literature.  
**DEVEREUX COURT, STRAND, W.C.2.**  
Tel.—Central 3763.

Advertisement Managers: SCHEFF PUBLICITY ORGANISATION,  
LTD., 125, Pall Mall, London, S.W.1  
Tel.—Regent 2064.

Scientific Adviser:  
Prof. G. W. O. HOWE,  
D.Sc., M.I.E.E.

Advisory Editors:  
Prof. R. WHIDDINGTON,  
M.A., D.Sc.  
Prof. C. L. FORTESCUE,  
M.A., M.I.E.E.

Staff Editors:  
E. H. CHAPMAN, M.A., D.Sc.  
A. D. COWPER, M.Sc.  
G. P. KENDALL, B.Sc.  
R. W. HALLOWS, M.A.  
S. G. RATTEE, Member I.R.E.



All correspondence relating to contributions is to be addressed to the Editor of "Wireless Weekly."

Nothing contained herein is to be regarded as permission or encouragement to infringe any patent rights.



## Imperial Wireless and the "Beam"

In our Editorial for July 9 we referred to Senatore Marconi's latest work with directional wireless in developing the system which has now received the popular title of "the wireless beam." Fully realising the importance of the great inventor's work we have been publishing in the last few issues a complete report of the Paper given by the well known inventor before the Royal Society of Arts, so that by this time our readers will be able to judge for themselves the full purport of the Paper. It is of some interest to note in passing that *Wireless Weekly* is the only radio journal to reproduce this Paper in full.

### The Rugby Station

In the Editorial referred to we stated that it was probable that the Post Office would complete their present plans for the Rugby station while carefully watching any developments on the shorter waves, and we are glad to see that this policy has been adopted by the Government. Instead of abandoning, as was suggested in some quarters, the work on the Rugby station, the giant installation which, when completed, will be the greatest in the world, the Government have wisely decided to push forward with the present work whilst co-operating with the Marconi Company in trials of the new "beam" system. In a few days' time, perhaps even before these lines appear in print, an agreement will be submitted to the House of Commons for their approval, whereby the Marconi Company will erect, as contractors, a "beam" station in England adapted for communication with Canada, and capable of extension so as to provide for "beam" communication with South Africa, Australia, and India.

According to the provisional arrangement, the station is to be completed within twenty-six weeks of the time when the site is made available for the Company, and it is conditional that the contract for the installation shall only be accepted and paid for by the Government if it fulfils certain important guarantees.

### The Question of Cost

In giving further details, the Postmaster-General stated that the Marconi Company were erecting a station for the Government at cost price, plus 10 per cent. contractor's profits, the maximum to be £58,000. Should additional units be

required for Australia or South Africa additional units would cost a maximum of £36,000. Thus, in a short time the British Government should possess a well equipped high-power station of great range at Rugby, together with a station of the new system for comparison with the older method. This certainly seems to be the common-sense way of dealing with the problem.

### The Dominions and the "Beam"

So far as the Dominions are concerned, they apparently do not all see eye to eye with the Home Government. In a statement before the Australian Parliament, Mr. Bruce said that the Government intended to proceed with the erection of a "beam" station at once. The British Government had advised the construction of both a "beam" and a high-power station of the older type, as the "beam" system can only maintain communication with Australia for seven hours daily. The Federal Government, which was unable to accept those views, was influenced to some extent by what was considered to be the shortness of vision shown by British experts in the past. Owing to the great development of the "beam" system, Mr. Bruce said it was probable that if a high-power station were now adopted it would, when completed, be obsolete.

It will thus be seen that the Australian Government intends, in the language of the racecourse, to "put all its money on one horse" by abandoning the idea of erecting a high-power station on lines already proved capable of satisfactory work during a large part of the day, and confining themselves to the "beam." They are therefore likely to find themselves in a position of considerable difficulty if, after more prolonged tests, the "beam" system should fail to live up to its promise. At the same time, the British Government, by having both high-power and "beam" stations available, will be in a much sounder position.

### A Gratifying Feature

One aspect of affairs is most gratifying to all who are interested in the progress of the art. We refer to the fact that the Government and the Marconi Company seem at last to be working in accord. We hope that we have seen the last of unpleasant bickerings in this direction, which have done much to hinder progress in the past.



# Garden Aerials

By E. H. CHAPMAN, M.A., D.Sc., Staff Editor.

*In view of the warm weather many readers may wish to enjoy the experience of wireless reception in the open air. The following article describes the best methods of arranging temporary aerials for this purpose.*

**E**VEN in the worst of British summers there are occasions when the listener-in feels tempted to take a receiving set out into his garden and spend a lazy hour listening to the music of one or other of the broadcasting stations. Of course, such a thing can be accomplished by the use of long telephone leads taken from the set in the house, but, with such an expedient, difficulties in tuning may arise. Besides that, there is not the same charm about it as having the set within easy reach of a comfortable deck-chair.

Fortunately, British broadcasting is now so efficiently carried

that, a good earth connection can be quickly made with an ordinary garden fork. In most of the experiments under consideration, the earth connection consisted of a garden fork driven as far in the ground as possible. The

4 ft. above the ground. Fairly good results were obtained on the telephones from 2LO with this aerial. Raising the wire so that one end was about 9 ft. above the ground, the other end still being 4 ft. above the ground,

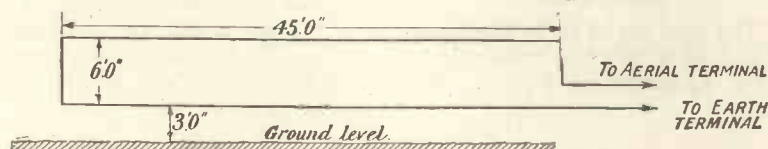


Fig 2.—Illustrating a type of aerial which was tried, the relative heights and lengths being given.

metal on the handle of the fork was first scraped clean and rubbed with a file for three or four inches. Then the bared end of a length of bell-wire was laid on the clean patch of metal and several turns of the insulated wire were wrapped round the fork handle over the bared wire. After these several turns had been wound as tightly as possible over the fork handle, the insulated wire was twisted with the free end of the bared wire in order to

increase signal strength a little, and 2LO was audible on the loud-speaker up to distances of a yard or two.

## Another Aerial

The next aerial to be tried consisted of 15 ft. of bell-wire with a 3-gallon watering can attached to the end of it. With the watering-can fastened at a height of 11 ft. up an elderberry tree, music from 2LO received on a small loud-speaker could be

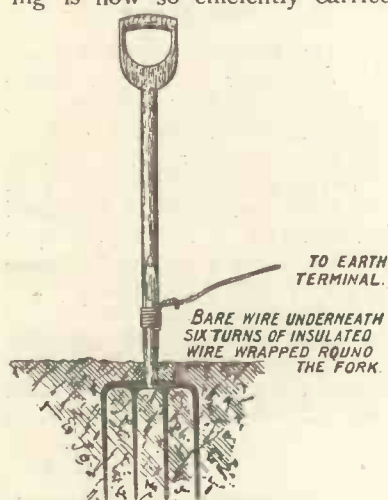


Fig. 1.—A quick and convenient method of making a temporary earth connection.

out that it is possible to get good results from a temporary aerial and a temporary earth connection such as may be installed in a garden in a very few minutes.

## Some Recent Experiments

I have recently made a few experiments with small aerials in a garden and the results obtained are worth setting down as an indication as to what can be done in this way.

## Earth Connections

First of all, there is very little difficulty in making a good earth connection in a garden. Often enough, there is a convenient water-point handy, but failing

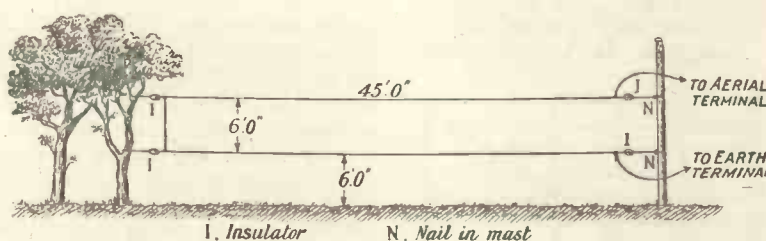


Fig 3.—A form of garden aerial which can be recommended.

keep the wire in position. Fig. 1 illustrates the way in which the fork was used as an "earth."

## Testing the Earth Connection

Before putting up an aerial, the efficiency of the fork as an earth was tried. Using a two-valve set and the earth connection alone, no aerial at all being used, 2LO 15 miles away was distinctly audible in the telephones.

## The First Aerial

The first aerial tried consisted of about 12 ft. of bell-wire placed

heard from 5 to 10 yds. away. The addition of another 15 ft. of wire to the aerial, making 30 ft. in all, increased signal strength appreciably, even though the 3-gallon can was placed only 7 ft. above the ground, being hung over the top of an open window frame. With this aerial, a fox trot from 2LO was heard a good 15 yds. away from the loud-speaker. When the 3-gallon watering can was removed from the end of the aerial wire, there was only a small diminution of signal strength.

## Further Trials

The next aerial tried consisted of 100 ft. of bell-wire fastened at one end to a pear tree and at the other to the house. The wire was only about 7 ft. above the ground and at the middle of its course the wire passed under a large elderberry tree. Signal strength with this aerial was better than had been obtained with the other aerials tried, but the loud-speaker was unable to compete with a noisy lawn-mower a couple of gardens away.

## Best Results

The next aerial to be tried consisted of a vertical rectangle of wire, as shown in Fig. 2. The

height of the top horizontal wire was 9 ft. above the ground, the height of the bottom horizontal wire, 3 ft. above the ground. As will be seen from the diagram, no earth was used. The wire used in making this aerial was, as before, No. 18 bell-wire. Results with this aerial were so good that a second aerial of the same shape was made of No. 24 enamelled wire and placed a yard higher than the last aerial. Small insulators tied to a tree were used to support the wire at one end, and at the other end the wire was twisted round nails driven in an aerial mast, a thin piece of rubber tubing being placed over each nail before the wire was twisted

round it. Fig. 3 is a sketch illustrating this aerial.

## Stations Received

The type of aerial shown in Fig. 3 is one to be recommended for use in a garden. It can be quickly put up with the aid of a small ladder or a pair of steps, and the results obtainable with such an aerial are remarkably good. With the aerial illustrated in Fig. 3, the writer obtained splendid loud-speaker strength from 2LO 15 miles away. In addition, Birmingham, over 100 miles away, was received at excellent telephone strength. Moreover, tuning with this aerial was noticeably sharp.

## Fixed Condenser Capacities

THOUGH it is not possible to arrive at an accurate measurement of the capacity of a fixed condenser unless a capacity bridge is available, one can nevertheless obtain a pretty good idea by making use of the rough-and-ready test to be described. The only essential is a variable condenser whose maximum capacity is known. Cheap condensers are sold as ".0003  $\mu\text{F}$ ," ".001  $\mu\text{F}$ ," and so on, but no guarantee is usually given

which gives a regular increase from minimum to maximum as the knob is rotated. There is, as a matter of fact, a slight irregularity in increase at the very bottom of the scale, but for all practical purposes a good condenser with a well-centred spindle and absolutely straight plates will give a regular increase. The chart shown in Fig. 1 may be used for the average .0005  $\mu\text{F}$ , and a similar one can be made in a few minutes to suit any other value. It will be noticed that a small allowance is made for the minimum capacity of the condenser which will never be zero. This charge enables the approximate capacity at any given setting to be read off in a moment.

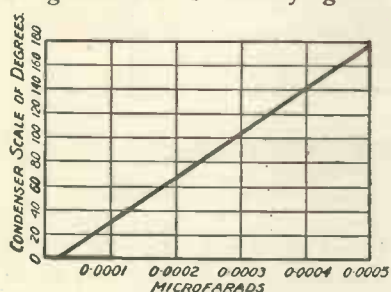


Fig. 1.—Curve showing relation of capacity of .0005 condenser to scale of degrees.

with them and they are very seldom up to the stated figure.

## Guaranteed Capacity

If, however, one purchases a variable condenser from a good maker a guarantee will come with it that its capacity is as stated. This condenser should be of the square law rotary vane type;

## Wiring Up

Now wire up the variable condenser and the fixed condenser which it is desired to test in the way shown in Fig. 2. It is not necessary to use a D.P.C.O. switch, though it saves time to do so. Throw the fixed condenser into circuit first of all and plug in different A.T.I.'s or work the slider of a single layer inductance until you hit upon a signal which is as sharply tuned in as possible. Suppose that the condenser under test is stated to have a capacity of .0003  $\mu\text{F}$ , then

the .0005  $\mu\text{F}$  variable condenser should give the same tuning when set at about 105 degrees.

## Indications

If you find that you have to set this condenser at a higher reading, then the fixed condenser is above its stated capacity. If, on the other hand, a lower setting is required, then the capacity of the fixed condenser is less than it should be. The approximate amount of the error can be ascertained by noting the variable condenser readings and seeing by means of the chart the capacities which they indicate. Thus if to obtain the same tuning we must set the variable condenser at

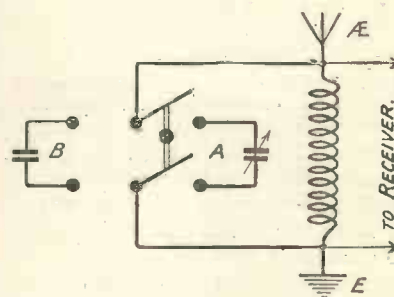


Fig. 2.—The method of connecting the switch for comparison of condenser capacities.

nearly 140 degrees, then the capacity of the fixed one is about .0004. In the same way a variable condenser reading of 60 degrees means that the real capacity of the fixed condenser is about .00018  $\mu\text{F}$ .

R. W. H.



**GOOP-WAYFARER No. 761****Synopsis of Previous Chapters**

Professor Goop and Wireless Wayfarer, the discoverers of a new circuit of stupendous possibilities are engaged in describing in detail the results of their labours for the benefit of all really serious experimenters. So far entirely original methods of insulating the aerial, of making the tuning inductance, of concocting the condenser and of attaching leads have been described. If you want to be at least eighteen months ahead of the fashion in wireless

**BEGIN THIS GREAT NEW SERIAL NOW!****The Telephone Receiver**

It is not perhaps usual to deal with the telephone receivers when only the ATI, the ATC and certain leads have been wired in the circuit. But this is not a usual circuit. No harm can be done by providing the telephones at this stage. They should be worn day and night by the constructor for a week or so in order that his ears may be properly flattened before he brings them into serious use, and that all superfluous hairs immediately above his ears may have been plucked out before the actual process of "broadcasting" on a grand scale begins.

**Making Receivers Comfortable**

You may discover when you first don the headbands that your head is adorned with peculiar bumps. Should this happen the best thing is to take your seat in the armchair wearing the phones, and to get a friend to hammer the bands gently but firmly until they are shaped to the contours of your cranium. It might be as well prior to this operation to consult a phrenologist. It would be sad, for example, supposing you had the bump of electrical genius highly

developed, to have it flattened out in this way. Many a promising career has been ruined by failure to attend to little matters of this kind.


**A New Headgear**

Personally I have always disliked metal bands, for though my head is of a noble, intellectual type, which head harness of any good make fits to perfection, I have a thin patch on the top, and in cold weather the feel of a steel band sends cold shivers all down my spine. I have therefore adopted for my own use an entirely original type of gear. Look at the pictures. Compare the look of agony on the face of the fellow caught in the grip of

top with one sweeping stroke. As scythecraft is not much practised in our larger towns, I may say that the city dweller who has neither lathe nor scythe at his disposal will be able to make quite a good job of it with a tin opener. The receivers are then detached from their bands. Little slits are made in the brim quite close to the crown immediately above the ears. The thingamejigs of the receivers are next pushed through the slits and attached to the crown by means of paper fasteners. The use of drawing pins for this purpose is not recommended.

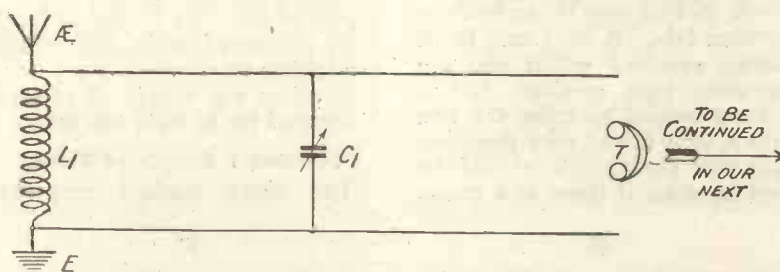**Method of Use**

The use of the Brimbolophone calls for a little self-restraint on



Goop-Wayfarer circuit No. 761 as described up to date. The method of obtaining the telephone receivers is detailed in this instalment.

a pair of ordinary rat-traps with the contentment, the beatitude, the *joie de vivre* of his opposite number who is revelling in the comfort of the Wayfarer Brimbolophone. The apparatus gets its name from the fact that it is made from the brim of a discarded bowler hat. The hat should be placed first of all in the lathe, and its crown neatly turned off. Should you not have a lathe, it is best to engage the services of a skilled scythewielder. You then sit upon the ground with the hat firmly upon your head whilst he mows off the


the part of those who have been brought up with the manners of a perfect gentleman. My friend Poddleby had a sad accident when he first donned the Brimbolophone. He was sitting before his wireless table, wearing, of course, both the apparatus and the pleasant expression which it brings, when the door opened and Mrs. Poddleby entered, ushering in Selina Snaggsby, who was dying to hear some wireless. Naturally Poddleby leapt to his feet, and, without thinking what he was doing, swept off his Brimbolophone in

polite salutation. One of his receivers caught the visitor a shrewd blow in the left eye, and, owing to the sudden jerk upon the phone-cords, large portions of his set were torn up by the roots. Be very careful, therefore, when you are wearing the instrument not to mistake it for a hat. Should you find that you are unable to restrain your natural politeness, it would be as well to fix it on with sticking-plaster as a precaution. It is important that the Brimbolophone when not in use should always be hung on a peg screwed on to the edge of the table, and never laid flat. Gubbworthy, another convert to this latest fashion in wireless millinery, neglected this precaution, and was astonished on returning from a long week-end to discover a family of seven kittens established in his Brimbolophone. Pay due attention to these small points, and the Brimbolophone will bring a new joy into your life.
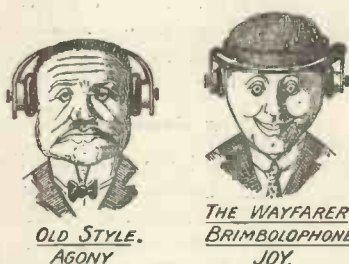
## Acquiring the Receiver

I promised the week before last to tell you how to obtain a telephone receiver for threepence. Since I wrote the Postmaster-General has, I believe, reduced his charges for the use of call boxes, so that now it can be done for even less. A little care is, of course, required whilst you are capturing your receiver, and it is most unwise to leave the box with a long tail of wire dangling from your pocket. Nor should the deed be done if there is a queue

of people waiting outside to use the box after you. Not only is this method of obtaining a receiver inexpensive, but it may also provide the obtainer with a holiday and an entire change of scene for fourteen days or more at no expense whatever. Personally I favour a safer and even cheaper method of providing oneself with headphones. I have never bought a pair yet, but I have always at least one excellent set in use. My method is to go round to Poddleby and borrow a pair from him. If he forgets about them, well and



Abolish discomfort by wearing this fashionable type of receiver.

good, but should he be mean enough to come at some future date and demand their return I hand them back with a haughty stare and a few cold words of thanks. Then I toddle round to Snaggsby and obtain the loan of a pair of his. As I have at least forty wireless friends, and others are taking up wireless every day, I calculate my supply of phones is assured for at least ten years.

## Obtaining a Supply of Valves

The same method may be

employed for keeping up a stock of valves. In this case it is as well to purchase a milliammeter, which need not necessarily be in working order. You can then offer to take valve curves for any of your friends, and tubes of all kinds from peanuts to power valves will positively rain down upon you from all quarters. Some of these people will, of course, come round and demand to see the curves. In this case you can always copy those published by makers (with slight variations) on to a sheet of graph paper. You then give back the valve, saying that it is a pretty priceless dud, certainly not worth the trouble of carrying home. It is ten to one that your victim will bow before your superior knowledge—the possession of the milliammeter gives one a wonderful amount of prestige—and that he will request you to throw the thing into your dustbin in order to save him trouble. With the exercise of a little ingenuity it is really possible to avoid having to purchase anything at all in the way of wireless gear. It is just the knowledge of these things which marks out the expert from the beginner. Next week I will show you how to provide yourself with as many high-tension batteries as you want at absolutely no cost at all with the help of an entirely new method which involves neither borrowing nor the other thing.


WIRELESS WAYFARER

A VERY neat double detector, which is a most useful pattern for the experimenter to have, can be made in the way shown in the diagram. On a small panel two detectors are mounted which may be either of the same type or of quite different patterns. One contact of each is connected to one of the two terminals on the panel, whilst the other is taken to one of the contacts of a 2-stud selector switch from whose arm a lead runs to the other terminal. It will be seen that either detector can be thrown into action by simply turning the switch across to the appropriate stud.

With such a contrivance
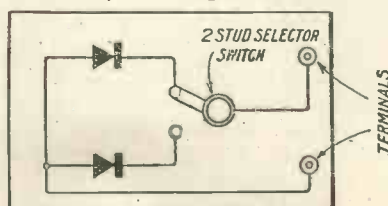
## A USEFUL DOUBLE DETECTOR

crystals can be tested against one another in the easiest possible way. This double detector may also be used for general receiving purposes, it being a distinct ad-



By means of the arrangement shown, crystals may easily be compared.

vantage to have two crystals, either of which can be used at will should one of them get out of adjustment, or should it seem to have lost its original sensitivity. Another use for this double detector is as follows: Wire the detectors so that the cup of one and the catwhisker of the other are connected to the common terminal, joining the other contacts to the studs of the selector switch. Now place a piece of the same crystal in each, and the device enables you to see at once in which way current should pass, for it can be reversed by the simple process of turning the switch from side to side.

R. W. H.



# Beam Wireless

By **SENATORE  
GUGLIELMO MARCONI,**  
G.C.V.O., LL.D., D. Sc.

Continued from page 378.  
Vol 4, No. 12.

**T**HESE experiments with Australia were continued during the month of May, consistently good results being obtained at two receiving stations situated in the vicinity of Sydney.

It seems obvious, if we consider the position and altitude of the sun, that during the morning period the waves travelled from England to Australia starting in a westerly direction, across the Atlantic and Pacific Oceans, along the longest route, which is approximately 12,219 nautical miles, whilst during the evening period they travelled in an easterly direction over Europe and Asia, along the shortest route, which is about 9,381 nautical miles.

In Canada, at Montreal, reception was found to be possible for 16 hours out of the 24.

These results were so encouraging that I was tempted to try a wireless telephony test to Australia.

With rather experimental arrangements at Poldhu, intelligible speech was transmitted for the first time in history from England to Sydney on Friday, May 30, of this year.

## Oil-Cooled Valves

For the telephony test to Australia, oil-cooled valves were employed for the main valve and for modulating valves. The wavelength was 92 metres and an independent drive was employed for controlling the main valves. The total power supplied to the valves was approximately 28 kw. divided up as follows: 18 to the main valves, 8 to the modulating valves and 2 to the drive valves. No reflector was employed.



*Mr. Leon Deloy (8AB) whose success has done much to popularise 100-metre work amongst amateurs.*

A continuous development of the short-wave transmitter has been taking place at Poldhu. To utilise considerable power, required the study and development of circuits for paralleling valves satisfactorily, and the design of special valves to maintain the wavelength steady has necessitated the application and development of an independent drive. These problems have been solved satisfactorily and the production of commercial transmitters dealing with powers up to the order of 50 kw. now presents no difficulties. (Slides were shown here of the interior and exterior of the small experimental station at Poldhu.)

It was gratifying to all concerned that the experiment succeeded the very first time it was tried, Mr. C. S. Franklin being in charge of the transmitting apparatus at Poldhu and Mr. Ernest T. Fisk (with whom I have never discussed technical matters in my life) of the receivers at Sydney.

It is also interesting to observe that these extreme distances

were obtained without the use of any reflector at either end.

The results obtained between England and Australia easily constitute a record for ratio of distance to wavelength, for Sydney, by the shortest route, is approximately 189,000 wavelengths from Poldhu.

In my opinion, it appears to have been proved conclusively that adequately designed reflectors, even if of comparatively moderate size, will enormously increase the effective strength of the signals.

This cannot but augment the efficiency of communication, besides increasing the number of hours during which it will be possible to work with very distant countries.

## Use of Reflectors

Moreover, the use of receiving reflectors will be of the greatest advantage to practical working, because whilst magnifying the strength of the received waves they reduce all interference whether caused by atmospheric electricity or other stations, un-

less, of course, the direction from which the interference may be coming happens to coincide exactly with that of the corresponding station.

The energy magnification, due to the concentration of the energy by the directional effect, has been carefully calculated by Mr. Franklin, and tests carried out at Poldhu have fully confirmed his figures.

The slide shows comparative polar diagrams of the field in all directions from three separate transmitters. The red circle is a polar curve of a plain non-directional aerial. The green curve shows the polar curve of a two-wavelength aperture reflector. The black curve shows the polar curve of an 8-wave aperture reflector, such as we propose to use for practical purposes.

(A slide was here shown.)

The case which was tried experimentally at Poldhu was an aerial and reflector  $\frac{1}{2}$ -wave high 3 waves wide, the aerial being fed at four points with a cable feeder system. The horizontal polar magnification figure of about 30 was found.

## General Laws

Mr. Franklin believes there are some general laws regarding these aerials which may be stated as follows:—

(1) The ratio of the loss by radiation to the loss by ohmic resistance, and therefore the efficiency, remains constant for all sizes of the aerial at the same frequency. This efficiency figure is very high, and can easily be of the order of 80 per cent.

(2) The natural decrement of the aerial is very high, and remains constant whatever the extension, as the ratio of the inductance to the resistance of the aerial remains the same.

(3) The greatest magnification for a given area, and therefore for a given cost, is obtained by having equal areas of reflector or aerial at the transmitter and receiver. Thus an aerial of 20 square wavelengths at transmitter and receiver gives a magnification of 200, but if divided into two aerials at transmitter and receiver, each of 10 square wavelengths, gives a magnification of 10,000.

(4) For a given area of aerial at the transmitter and receiver,

the magnification goes up as the fourth power of the wave frequency used. Thus, assuming aerials 1 kilometre wide and 100 metres high at transmitter and receiver, these would each be 10 square wavelengths for 100-metre wave, and would give a combined magnification of 10,000. For half this wavelength (50 metres) each aerial would be 40 square wavelengths, and would give a combined magnification of 160,000.

## Energy Capacity of Aerials

Up to what ranges this fourth power law can be effective in compensating for the greater attenuation of the shorter wave has yet to be ascertained.

The energy capacity of these

should not be one hundred times as great as the speed attainable with a frequency of 30,000, which represents the frequency of a wavelength of the order of those which it is proposed to use for the Imperial stations. Of course, this is not taking into account the mechanical difficulties.

## Further Tests

Between the 12th and the 14th of June (both inclusive) of this year, some further important tests were carried out between Poldhu and a small receiving station at Buenos Aires in the Argentine, the distance between the two points being 5,820 nautical miles (10,780 kilometres).

For this radio-telegraphic test



Mr. Dan Godfrey, Jr., conducting the augmented wireless orchestra at the London Studio.

aerials is enormous, and they could never conceivably be worked to their limit. It would be quite possible practically to superimpose several waves and thus several services on the same aerial.

It should not be lost sight of that very high speeds of working appear to be possible only if short waves are employed, whilst speeds of the same order are quite unattainable with the long waves now in general use for long-distance radio communication.

I might, in other words, state that there exists no theoretical reason why with a frequency of 3,000,000, such as is the frequency of oscillation of a 100-metre wave, the speed

the wavelength was 92 metres and the power to main valves was 21 kw. This gave a radiation of 17 kw. The parabolic reflector was employed to concentrate the energy towards South America, and gave a strength of field in that direction which would otherwise have required a radiation of approximately 300 kw. from the aerial without reflector to produce the same effect.

Although many of the arrangements employed were far from perfect, very strong signals were received for over ten hours each day at Buenos Aires.

Messages were sent by the Argentine Minister of Agriculture, Dr. Le Breton, who happened to be in London, to the



Minister of War, General Justo, in the Argentine, and every message transmitted was correctly received in one transmission.

At the conclusion of the tests we received a communication from the Argentine Committee, representing the wireless interests in the Argentine, who are conducting the wireless telegraph services through their super-power station with Europe and the United States of America, to the effect that the signals from Poldhu transmitted by this new system were received at Buenos Aires with such regularity and extraordinary strength as to permit a service being conducted at any speed, and expressing the opinion that the Argentine station should be immediately equipped with the new system which, they are confident, will handle more than double the traffic in six hours than they are now able to handle in twenty hours with their present super-power station. Excellent results were also obtained at Rio in Brazil.

#### A Prophecy

All these results, many of which have greatly exceeded my expectations, convince me that by means of this system economical and efficient low-power stations can be established which will

□

maintain direct high speed services with the most distant parts of the globe during a considerable number of fixed hours per day.

I am further of the opinion that by means of these comparatively small stations a greater number of words per 24 hours could be transmitted between England, India and her distant Dominions than would be possible by means of the previously planned powerful and expensive stations.

#### Comparative Privacy

Another particular advantage of this system should not be overlooked. As distant stations situated only within a certain angle or sector of the beam are enabled to receive, this condition brings about a comparative privacy or secrecy of communication unobtainable with any other system of radio communication, and this may prove to be of the greatest value in war time, besides considerably increasing the number of stations it will be possible to work, by reducing the possibilities of mutual interference between them.

The comparative economy in capital cost of these stations, the small amount of electrical power which need be employed, together with the capability of

□

working at very high speeds, should make it possible to bring about a substantial reduction in telegraphic rates. The importance of this to the Empire must be obvious.

I wish to take this opportunity of expressing my high appreciation to Mr. C. S. Franklin for all the valuable work he has carried out in order to make this system a practical success, and also to Mr. G. A. Mathieu for his practical and theoretical assistance.

I also wish to thank Mr. Ernest T. Fisk, the Managing Director of the Amalgamated Wireless (Australasia), Ltd., Mr. H. H. Beverage, Research Engineer of the Radio Corporation of America, Mr. J. H. Thompson, Chief Engineer of the Marconi Wireless Telegraph Company of Canada, Ltd., Commander J. Lloyd Hirst, Marconi's Wireless Telegraph Company, Ltd. Representative on the Commercial International Committee in the Argentine, and Mr. P. Eisler, Manager of the Commercial Radio International Committee in Brazil, for their most valuable co-operation in arranging at very short notice to successfully receive in their respective countries the signals transmitted from Poldhu.

(Finish)

□

## The Harkness Circuit and Some Claims.

**W**E have received a number of inquiries regarding the so-called "Harkness" circuit, for which great claim has been made in the American press. Reports regarding this circuit have been published in the lay press of this country, together with the claim that it is easily capable of covering the range of 1,000 miles or more, and to be incapable of oscillation or interference.

The actual circuit, however, has little in it to justify such claims. Incidentally it should be stated that the receiving conditions in America are on the average greatly superior to those in this country, which possibly accounts for the extraordinary claims frequently made for quite

ordinary circuits. The present circuit consists of a single valve receiver with aperiodic aerial tuning and a high-frequency transformer in the anode circuit. The high-frequency currents in the secondary of this circuit are rectified by a crystal and fed back through a low-frequency transformer to the grid circuit of the first valve in the normal way.

It will thus be seen that there is nothing essentially novel in the circuit. The method of coupling the aerial to the closed circuit is of the type already described in these pages, in which a single layer coil on a suitable former has wound over it a smaller number of turns constituting the aerial circuit. An identical arrangement is used in the anode

circuit of the valve, the smaller number of turns forming the primary winding and the larger the secondary. No direct reaction is provided for.

It will thus be seen that the arrangements closely resembles many of the reflex receivers previously described in these pages, and its range cannot be expected to be any greater. Any claims made that the set will not energise the aerial should be accepted with the greatest reserve, for in a loose-coupled set with a tuned circuit directly or indirectly connected to the plate, the inter-electrode capacity of the valve may be quite sufficient to feed back enough energy to create oscillations, although, of course, the damping introduced by the crystal is a stabilising factor. Stability in circuits such as this is usually obtained by sacrificing sensitivity, for obviously if the set cannot be brought near the oscillating point, the maximum amplification is not obtainable.



### A New Method of Feeding Back the Low-Frequency Currents in a Reflex Circuit.

**T**HE method which I have developed for feeding back the low-frequency currents in a reflex circuit, and which has become standard with most experimenters, sometimes has raised against it the objection

low-frequency currents through a choke coil to the grid of the valve, the aerial circuit being also connected across the grid and filament of the valve, a stopping condenser being employed.

This latter parallel method is not, of course, as straightforward and simple as the method which connects the transformer in the

low-frequency A.C. is practically eliminated, and is certainly eliminated in so far as the aerial picks up the parasitic currents.

#### Details of Circuit

Fig. 1 shows the method. It will be seen that in this circuit the aerial is connected to earth through an inductance coil  $L_1$ . The main tuning circuit is  $L_2$   $C_2$ , acting, of course, in conjunction with the aerial capacity. A fixed condenser  $C_1$ , having a capacity of, say, .0003  $\mu$ F, is connected in the position shown, while a condenser  $C_3$  of .001  $\mu$ F capacity is connected across the secondary  $T_2$  of the feed-back low-frequency transformer  $T_1$   $T_2$ . A high-frequency transformer  $L_3$   $L_4$  is included in the anode circuit of the valve and a crystal detector is used for rectification purposes. The low-frequency potentials established across  $T_2$  are communicated to the grid of the valve through the inductance  $L_2$ , while the condenser  $C_1$  pre-

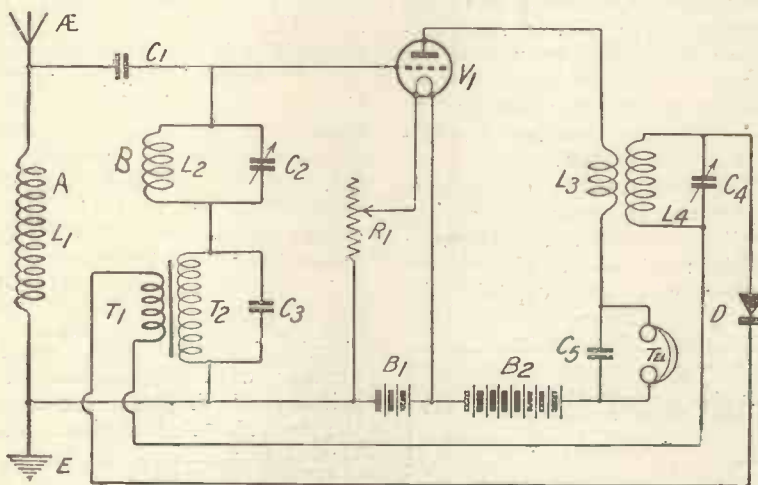


Fig. 1.—A circuit for eliminating A.C. hum.

that the aerial sometimes picks up A.C. current from electric light mains, etc., and these currents traverse the secondary of the transformer connected in the aerial circuit, thereby producing potential differences across this circuit which are communicated to the grid of the valve, and consequently produce a hum in the telephones or loud-speaker.

Experience shows that this effect is rarely experienced, especially when constant aerial tuning is employed, but where severe trouble occurs the only alternative method has been the parallel input arrangement used on a number of commercial sets. Readers will recall that this method consists in feeding the

aerial circuit, and some trouble is sometimes experienced due to the resonating of the choke coil.

I have now developed a method which possesses all the merits of the series input arrangement, while at the same time all chance of picking up

vents the current from being short-circuited through  $L_1$ .

This circuit may be operated in two ways; either the inductance  $L_1$  may be made of very high value, in which it is regarded purely as a short-circuit for low-frequency currents picked up by

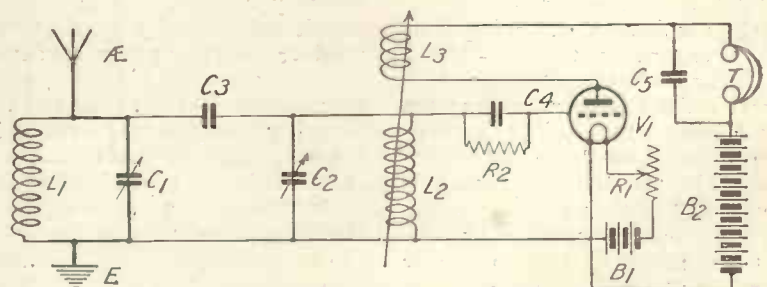


Fig. 2.—A circuit which is not quite what it appears to be.



the aerial from electric light mains, or the inductance  $L_1$  may be made an integral part of the main oscillating circuit. If  $L_1$  is used as a choke coil some of the disadvantages of the parallel input method will be experienced. The coil  $L_1$ , under these circumstances, will have negligible impedance to low-frequency currents and negligible resistance. Any low-frequency currents picked up by the aerial will consequently not produce any noticeable potential differences across  $L_1$  which could be communicated to the grid of a valve. On the other hand, the coil  $L_1$  would choke back high-frequency currents which would traverse  $C_1$ , the circuit  $L_2 C_2$ , the condenser  $C_3$ , and so to earth.

I much prefer, however, to make the coil  $L_1$  an integral part

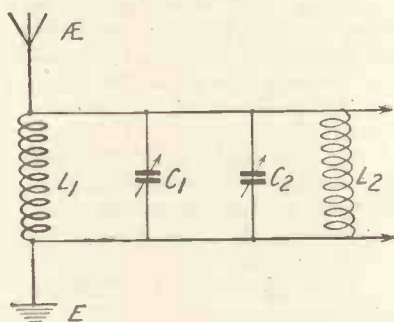


Fig. 3.—A circuit which acts similarly to that of Fig. 2.

of the main oscillation circuit, and in these circumstances the aerial,  $C_1$ ,  $L_2$ ,  $C_2$ ,  $C_3$ ,  $L_1$  and the earth form one single oscillating circuit, the wavelength of which may be altered by altering any of the inductances or capacities.

This raises a very interesting point which I have not seen raised before, and experimenting with the Fig. 2 circuit really brought the matter home to me. This circuit, at first sight, appears to be simply a tuned aerial circuit coupled to a tuned grid circuit  $L_2 C_2$ , reaction being introduced from the anode circuit of the valve into the circuit  $L_2 C_2$ .

It would, in most cases, be thought that the condenser  $C_3$  simply served as a coupling condenser between the two tuned circuits, and that all the merits of inductive coupling would be obtained. I have tried various sizes of the condenser  $C_3$  down

to  $.0001 \mu\text{F}$ , and in all cases I found that the two circuits  $L_1 C_1$  and  $L_2 C_2$  acted together to produce what was virtually a single circuit. There was certainly no increase in selectivity, and any change in the condenser  $C_1$  so as to detune the aerial circuit could be compensated for by making a suitable change on the condenser  $C_2$ . If, for example,  $C_1$  were increased, signals would disappear, but could be brought back again by reducing  $C_2$ . The whole circuit acts very similarly to the arrangement of Fig. 3, which, of course, may be simplified into the arrangement of Fig. 4, which is the simplest of aerial tuning arrangements.

#### Size of Coils

Fig. 3, of course, is not intended to indicate a circuit equivalent to Fig. 2, but nevertheless the effects are very similar. For example, an increase of  $C_1$  may be compensated for by a decrease of  $C_2$ , and the inductances  $L_1$  and  $L_2$  are, in Fig. 2, considerably larger than they would be if they were not acting in parallel with each other. Since they act in parallel, of course, the net inductance is smaller, and consequently larger coils are required than would otherwise be the case.

#### A Useful Example

A useful circuit embodying this method of feed-back is illustrated in Fig. 5, and it will be seen that a constant aerial tuning condenser  $C_1$  is provided. The coil  $L_1$  may be shunted by a variable condenser or not, but since

the variable condenser does not make any difference, except as a duplicate method of tuning, it is omitted. In the Fig. 5 circuit a tuned anode circuit  $L_3 C_4$  is provided, the crystal detector  $D$  and the primary  $T_1$  of the step-up transformer  $T_1 T_2$  being con-

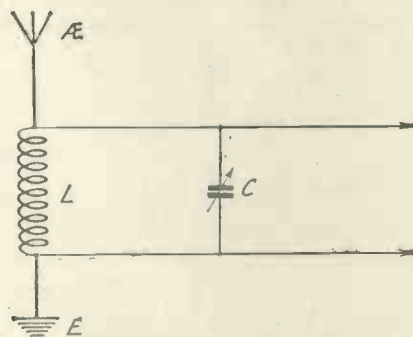


Fig. 4.—Simplified form of Fig. 3.

nected across this circuit. The variable condenser  $C_2$  governs the wavelength. The coils  $L_1$  and  $L_2$  may conveniently be of the same size, and for the reception of stations on the waveband 300 to 500 metres it will usually be found that the following values will serve.

The condenser  $C_1$ , of course, has a capacity of  $.0001 \mu\text{F}$ , while  $L_1$  is a No. 75 Lissen coil, for example. The condenser  $C_3$  may have a capacity of  $.0003 \mu\text{F}$ , while  $C_2$  has a maximum capacity of  $.0005 \mu\text{F}$ . The inductance  $L_2$  is another No. 75 plug-in coil, while  $C_5$  has a capacity of  $.001 \mu\text{F}$ . The anode inductance  $L_3$  is a No. 50 plug-in coil for wavelengths up to 420 metres, and above this wave-

(Continued in col. 3, page 423.)

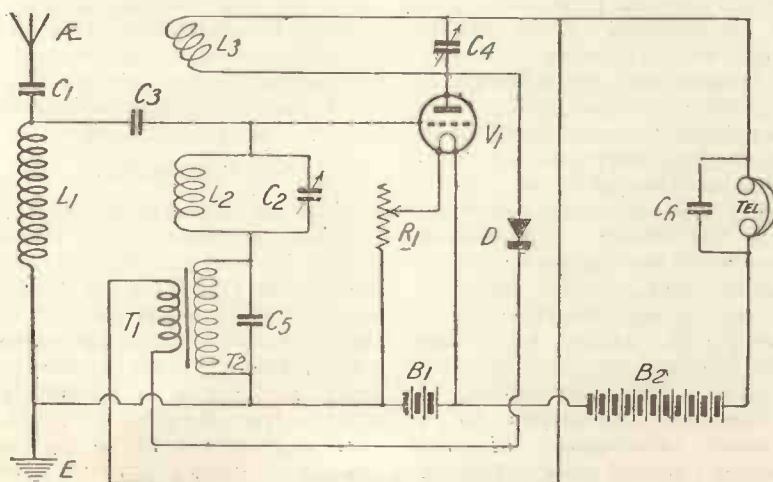


Fig. 5.—A useful circuit with constant aerial tuning embodying the feed-back system of Fig. 1.



*Dame Clara Butt at the microphone.*

UPON the occasion of the recent recital given by Dame Clara Butt from the new high-power broadcasting station, the transmitter and studio were for the first time thrown open to Press inspection by the courtesy of the British Broadcasting Company. I had, in consequence, the privilege of inspecting the whole station from microphone to aerial, and I think my feelings may best be compared to those of Sinbad in the Valley of Jewels; here before me was fascinating experimental work of all sorts going on, and it seemed that almost unlimited interesting information was to be had for the asking, yet I had only one head in which to carry it away. Before attempting to reduce my impressions to a coherent description of the station, I should perhaps explain that the present arrangement of 5XX is a purely experimental

one, and does not in any way represent the final form of the station. Even its location should not be assumed to be the present one, since it is possible that it will be moved from Chelmsford to some other similar position outside London when once the preliminary experiments are over, and permission has been obtained from the Postmaster-General to erect the permanent station.

#### The Transmitter

Since the station is regarded as entirely temporary, the transmitter is laid out without any attempt to reproduce the sound engineering qualities of one of the permanent stations, the whole aim of the engineers in charge being at present to produce a plant which will enable the necessary experiments to be carried out with the minimum of expense. So experimental is the installation, indeed, that certain

## 5XX AT WORK

A VISIT TO THE  
HIGH-POWER  
EXPERIMENTAL  
STATION OF THE  
BRITISH BROADCASTING  
COMPANY.

of the main feed switches are arranged upon a temporary switchboard attached to a pillar, and from the handles of the switches cords are led through pulleys to a handrail, beside which an attendant is constantly standing, with his hand ever ready to jerk the switches open by means of the cords should any mishap occur in the transmitting plant itself. The cords are necessary, of course, in view of the fact that with the very high voltage input heavy arcing is liable to take place on these switches, which would be liable to cause injury to anyone opening them by hand. Incidentally, this arrangement led to a somewhat amusing episode, which occurred during my visit to the station. This was responsible for the momentary break in a transmission which listeners may have noticed.

#### A Startling Incident

During the mild confusion brought about by the influx of the Press representatives to the shed containing the transmitter, one of the photographers entered, and set up his camera in a distant corner. Presently he ignited his magnesium powder with somewhat startling effect, since the spectators had not noticed his arrival, and consequently were quite unprepared for the sudden small explosion and blinding flash of light, accompanied by the sound of small fragments scattering across the floor, which signified that he had exposed his plate. The engineer at the switchboard was similarly unprepared, and the flash of the magnesium powder was followed practically instantaneously by the clatter of the switches as he jerked at his



*Intimate details of the working of the new station are given below by "Wireless Weekly" special representative, who visited the station recently.*


cord. He realised almost instantly, of course, that he was the victim of an unintentional practical joke, and swiftly closed the switches again, so that the break was only short.

#### The Studio

The studio itself, which is, of course, only of a makeshift nature, is situated in the main buildings of the Marconi's Wireless Telegraph Company's works, in what I took to be the board room. An inner wall of hanging felt has been erected in this room, the floor and ceiling being similarly covered. There is thus a space, perhaps five feet wide, left all round the felt wall, but inside the main wall of the apartment. The microphone is of the now familiar type devised by Captain Round, and first used at 2LO. It is mounted in the usual soft rubber saddle and supported upon a movable tripod. It was

placed for the recital in one corner of the inner enclosure, and the grand piano occupied a position near the middle of the opposite side. The singer was placed at a considerable distance from the microphone itself.

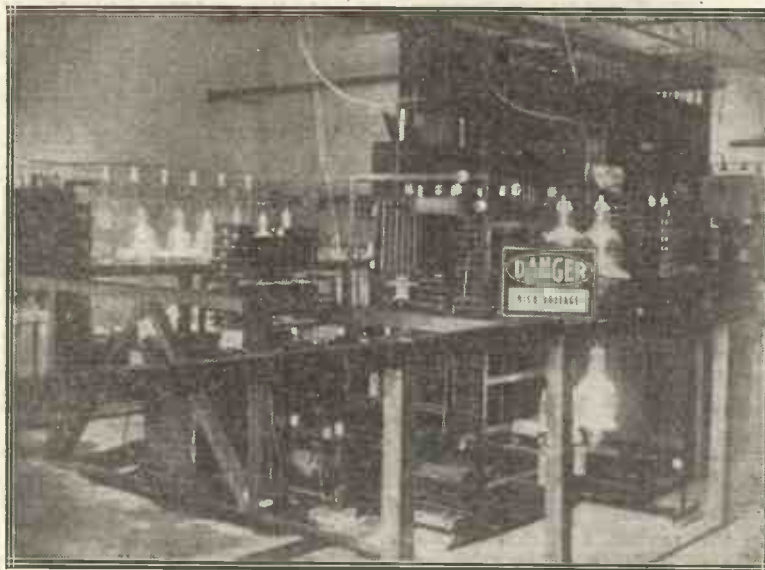The leads from the microphone are taken out into a small passage outside the board room to one of the portable speech amplifiers commonly used for the broadcasting of operas and plays. The first check on the quality of the speech currents takes place on this amplifier, and controls are provided for adjusting the relative prominence of high and low notes.




*In the foreground is the drive oscillator (bearing the word danger). The main bank of rectifying valves and the closed circuit condensers are visible in the background.*
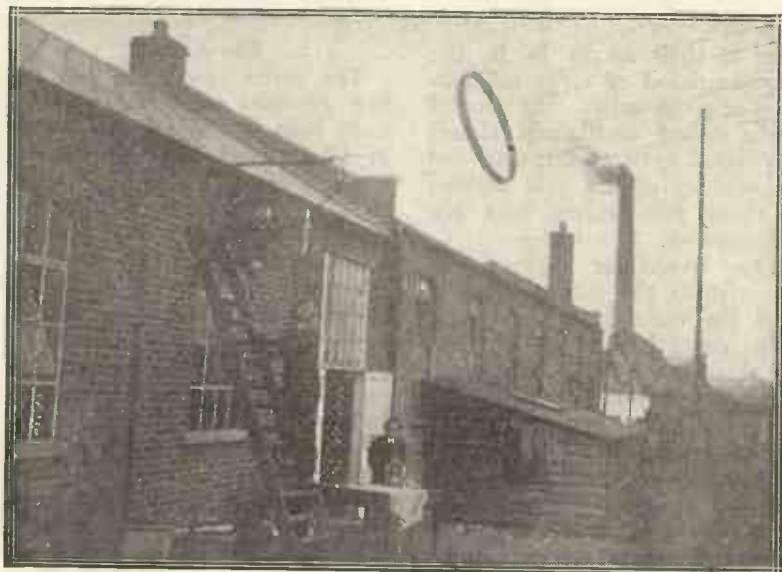
#### The Control Room

The output from the speech amplifier adjacent to the studio is taken to a hut at a distance of about 100 yards from the main building, where the usual control room has been established. Here the output is subjected to further amplification to bring it up to the required strength for application to the modulator valves, and the main checking of the quality of the speech currents is done. The principal impressions of the visitor here are of rows of power-amplifying valves, apparently being worked in parallel, most of them with their anodes glowing with a cheerful red heat. A loud-speaker is provided here which can be fed either with the speech currents which are being handled by the amplifiers, or by a frame aerial receiving set in an adjacent room, which enables actual comparison to be made of the quality of the speech currents applied to the transmitting set, and of the actual transmitted signals. This loud-speaker was arranged with its trumpet near one of the windows of the hut, and the majority of the visitors heard the recital with its aid.

In the control room also is located the telephone for communication between the studio and the control room, the control room and the transmitting room, and the control room and Savoy Hill.



*The cage lead-in at 5XX, showing the lead-in insulator.*

## The Transmitter

The whole of the transmitting plant is contained in one large shed, from alternating current generator to aerial tuning inductance. One's first impression on entering the shed is of the roar of revolving machinery, the blinding glare of banks of enormous valves, and the splashing and trickling of water. This latter is discovered upon investigation to proceed from the cooling system of the main oscillator and modulator valves, which are of the recently developed water-cooled type.

The main power supply for the transmitter is a converter consisting of a motor running direct from the mains, and driving an alternator generating current of 300 cycles per second. The output from this alternator is then fed through a step-up transformer, and supplied to a bank of 12 rectifying valves. The output from these valves after being suitably "smoothed" appears as a direct current of 9,000 volts, which forms the main high-tension supply.

## The Circuit

The circuit is precisely the same as that employed at 2LO—that is to say, a master oscillator system is employed, in which a small local oscillating circuit is used, to generate high-frequency oscillations of the desired frequency, which are then amplified by a further bank of valves, and applied either directly or through a loose-coupled arrangement to the aerial circuit. The "drive oscillator," as it is called, consists of two rectifying valves, supplying the current for two large transmitting valves of a type known as the M.T.7A., whose filaments are supplied with 24-volt current, and which give an output of approximately 3.5 amperes of high-frequency current to the main amplifying valves. The 4 valves required for the drive circuit are mounted upon one panel, with the necessary controls, the usual standard inductance with ball reaction coil being employed. The condenser is of the air dielectric type, and the total power in the drive circuit can be taken as 6 kilowatts.

The output from the drive is taken to the two magnifier


valves, which are of the water-cooled type. These two valves together then increase the high-frequency energy to between 15 and 16 kilowatts, transferring it to a closed oscillatory circuit, whose condenser consists of a great bank of plates separated by air. This bank is decidedly reminiscent of the huge one which was employed at the old spark station at Clifden, Ireland, for trans-Atlantic work, and consists of nearly 30 plates approximately 8 feet by 5 feet, spaced about 1 foot apart, and hung beneath the roof of the shed.

The filament voltage of the magnifier valves is in the neighbourhood of 40 volts, and the

given to show the relative strength of modulation of different types of transmission, the following examples being some of the most striking.

Nature of Transmission.	Relative Strength.
Speech.	12
Music.	20
Savoy Bands.	25
Big Ben.	30

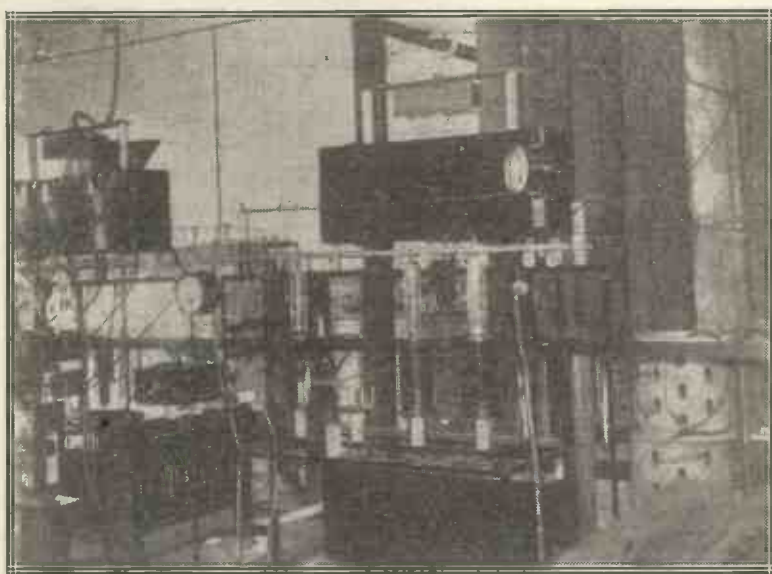The main aerial tuning inductance is composed of stranded cable, which appeared to be about  $\frac{3}{4}$  in. thick, and the reading of the aerial ammeter was in the neighbourhood of 40 amperes, the actual power at the time being 16 kilowatts. A direct earth is used.



The large water-cooled valves are used as magnifiers and as modulators

input to their anode is in the neighbourhood of 1,700 milliamperes at 9,000 volts. The current in the closed oscillatory circuit was stated to be 25 amperes, and the reading of the grid current of these two valves was 200 milliamperes.


The modulator valves, to whose grids the output currents from the main speech amplifier in the control room are applied, are three more Marconi-Osram water-cooled valves, whose filaments are supplied with 48-volt current. The anode current of these valves is again 1,700 milliamperes at 9,000 volts, and a most enormous negative bias is applied to their grids. Some most interesting figures were

## The Aerial

The aerial is carried on the two 450-foot steel masts which have been in use for some time at Chelmsford, and consists of a single cage of the "L" type, its natural wavelength being between 1,300 and 1,400 metres. The actual length of the horizontal span is considerably less than the distance between the masts, and consequently the down lead can be kept well away from the mast at one end, with a view to reducing absorption effects in the mast itself. The down lead is also of cage formation, and comes down to a leading-in insulator made of porcelain of truly impressive dimensions.

G. P. K.



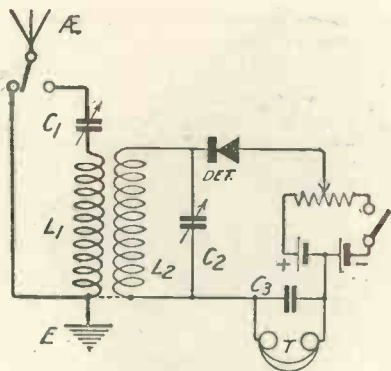

The Circuit.


**T**HIS is a simple crystal receiver employing a loose-coupler, vario-coupler, or basket coils. B is a single pole, double throw switch for earthing the aerial direct when the receiver is not in use. The variable condenser C has a capacity of  $0.001 \mu\text{F}$ , and is connected in series with the aerial tuning inductance P. The secondary coil S is tuned by the variable condenser D, whose capacity is  $0.0005 \mu\text{F}$ . H is the carborundum detector and F the usual potentiometer of about 400 ohms resistance. The single pole, single throw switch I is optional, but if not used, the batteries added externally to the set should be disconnected when the receiver is not being used. Its purpose, of course, is to switch off the current which would otherwise flow through the potentiometer unnecessarily. Across the telephone terminals T is connected the condenser J of  $0.001 \mu\text{F}$ , and this may be conveniently fixed as shown.

As regards the external bat-

teries, two dry cells may be connected in series, a negative terminal of one being joined to a positive terminal of the other, the remaining two terminals being connected to the minus and plus terminals on the set. From the point where the two

and S. The simplest method is to couple the two coils closely to commence with, and tune first on C, and then on D, the coil coupling being varied when interference is experienced.

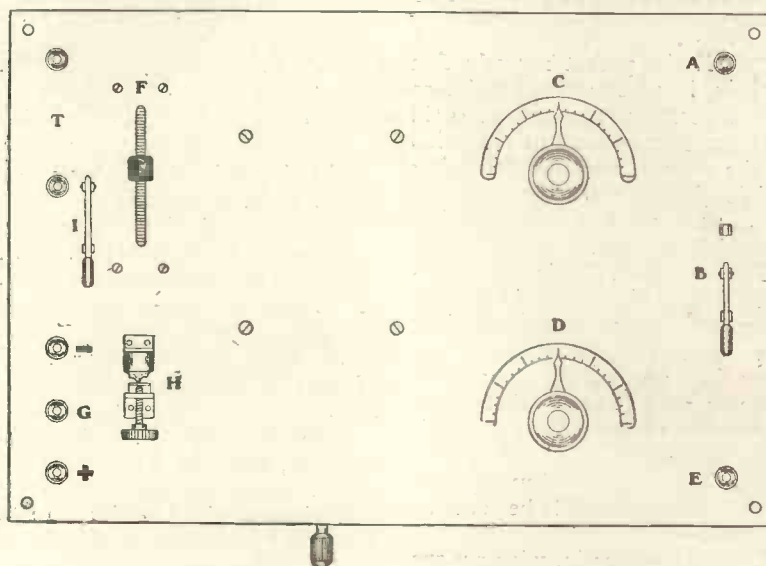To adjust the detector correctly first place the potentiometer



The lay-out of the Panel.

cells are joined a tapping is taken and connected to terminal G.


Tuning is carried out by adjustment of the variable condensers C and D, and by variation of the coupling between P

meter slider in the centre and apply more pressure to the crystal than is usual with the ordinary detector. Having received signals, vary the potentiometer slider for loudest results. A little experimenting is advisable.

Slightly better results are sometimes obtained by making a permanent connection between the earth terminal and the variable condenser D, as illustrated by a dotted line on the wiring chart.
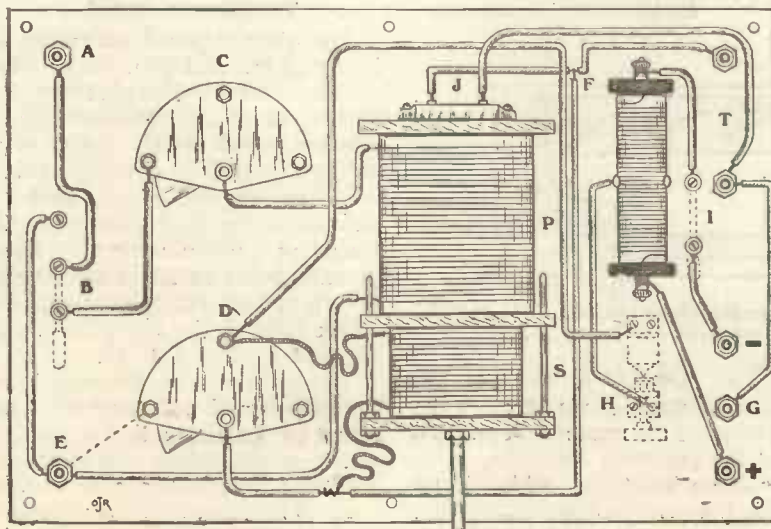
#### PERSONAL

We are given to understand that Mr. W. H. Lynas, of Messrs. Alfred Graham & Co., sailed from this country for New York on July 26, and we have been asked to point out that readers wishing to communicate with him after that date should address their correspondence to the Company.



Practical wiring diagram.

# Utilising ... Valves .... to Best ... Advantage

HOW TO MAKE A  
USEFUL GRID BIAS  
UNIT.

FOR the purest reproduction in low-frequency amplifiers a certain amount of grid bias must be applied to the grids of the valves, and the following article gives constructional details of a neat method of obtaining variable grid bias.

The compact little unit described may be applied to any set using low-frequency amplification, and since the connections and operation are simple, the constructor need have no theoretical knowledge of the subject to use it with success.

The box is made of wood  $\frac{3}{8}$  in. thick, which should be cut as follows:—

From a piece  $2\frac{1}{4}$  in. wide cut the two end pieces each  $4\frac{1}{4}$  in. long,

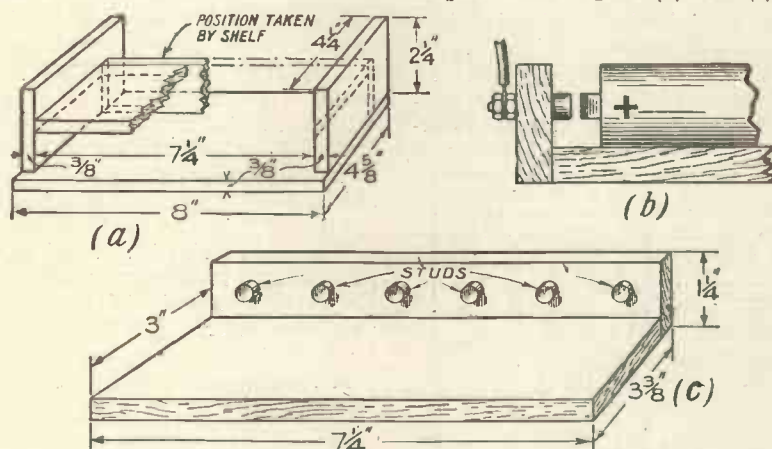


Fig. 2.—Details of the containing box, showing the positions of the studs, and the method of making contact with the batteries.

and from the same width cut two pieces 8 in. and  $7\frac{1}{4}$  in. long respectively. These two latter are the sides, the longer being fixed later to one of the end pieces by means of a small hinge so that the interior will be easily accessible.

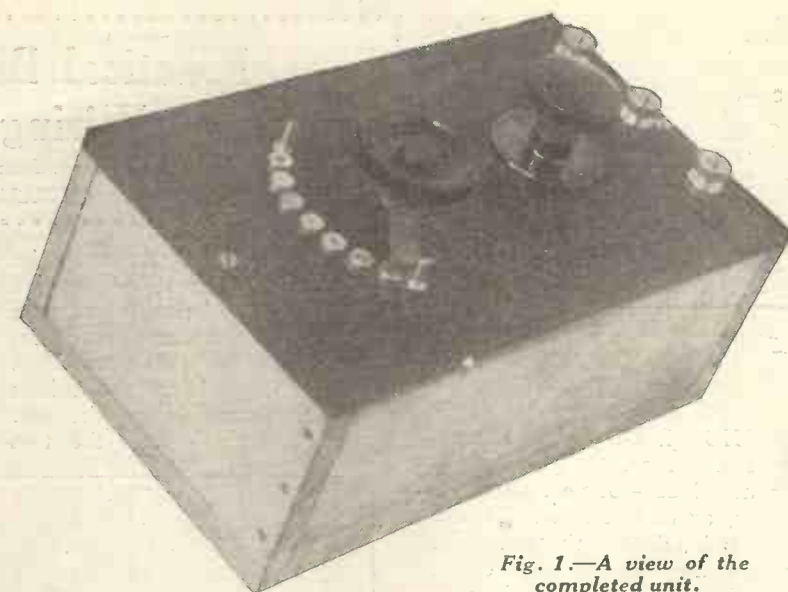


Fig. 1.—A view of the completed unit.

The base is 8 in. long and  $4\frac{5}{8}$  in. wide.

The two end pieces are now fixed to the base as in Fig. 2 (a), by means of small screws or nails. It should be noted that these end pieces are flush with one side of the base, thus leaving a space of  $\frac{3}{8}$ ths of an inch on the other side.

Two pieces of  $7\frac{1}{4}$  ins. long are now cut, one 3 in. wide, the other  $1\frac{1}{4}$  in. wide. These two pieces are joined at right angles, so that the wider piece has the thickness of the other piece added to its length, as in Fig. 2 (b) and (c).

tive, on the wide piece, and with their terminal strips touching the smaller piece.

The six studs are now fixed in position so that each stud makes contact with a different terminal strip of one of the batteries. It will generally be found advisable to snip off a small portion of each negative terminal (the longer strip, if not marked otherwise) in order to ensure good contact between terminal strip and stud, and to prevent possible short-circuiting.

The ledge is now fixed between the ends of the box in the position indicated in Fig. 2 (a),  $\frac{7}{8}$ ths of an inch above the base, and with the studs in the lower section. This section is now complete except for the insertion of the flashlamp batteries.

## The Ebonite Panel

The ebonite panel measures 8 in. by  $4\frac{5}{8}$  in., and  $\frac{1}{4}$  in. thick. As will be seen by the photograph, Fig. 1, there are two controls; a selector switch which varies the voltage used from 0 to  $13\frac{1}{2}$  volts in steps of  $4\frac{1}{2}$  volts, and a potentiometer, in this case one of Burndept manufacture. This potentiometer varies in extremely minute stages, the voltage applied to the grid of the valve from the filament heating battery.

The positions on the panel for the switch and potentiometer are found by drawing a line down the centre of the panel, and marking points at  $2\frac{1}{2}$  in. and 5 in. from one end. The former is the position for the potentiometer, and the

## Contact Studs

Six contact studs are to be inserted in the smaller piece. To find the positions for these, three flashlamp batteries, which comprise the grid biasing battery, are laid side by side, negative to posi-



latter is that of the selector switch. This latter should be placed temporarily in position, the arm pointing to the nearer end of the panel. The arm is now depressed until it touches the panel, and is then moved round to about 2 in. from the centre line, then back again to a similar distance

fixed condenser of .0003  $\mu$ F capacity is connected, as shown, in order to by-pass any high-frequency currents which may be flowing in the circuit.

#### Dead Studs

It will be noticed that the second, fourth and sixth studs of

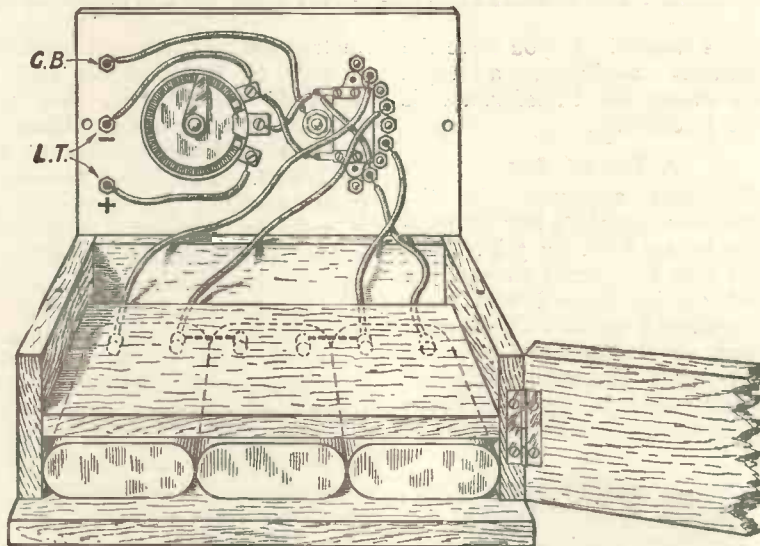


Fig. 3.—The internal wiring of the unit, showing connections to the batteries. Note the dead studs of the selector switch.

on the other side, using enough pressure to leave a mark on the panel. This procedure for finding the positions for the studs is advisable rather than following definite measurements, as the arms of different makes of switches vary in length. Seven studs of 5/16th in. diameter are to be inserted with their centres 3/8th of an inch apart, and these distances are marked off along the line made by the switch arm, the

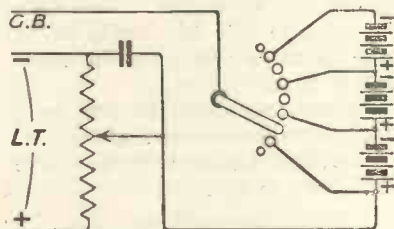


Fig. 4.—A circuit diagram showing how to wire the unit.

centre stud occupying the point where this line crosses the centre line of the panel. The potentiometer, which must be of the rotary type, is easily assembled, and there remains but the wiring up of the components. This is easily accomplished by referring to Fig. 3, or Fig. 4, in which the connections are clearly seen. A

the selector switch are left dead. This is necessary, as short-circuiting of parts of the battery would take place as the arm moves if each stud were connected to the battery.

Joints may be soldered or made by means of lock-nuts, according to the ability of the constructor, the former method, of course, being preferable.

#### Fitting the Panel into the Box

The panel may now be screwed to the box providing the potentiometer spindle does not press on the shelf. If this occurs a hole large enough to take the spindle without friction is bored in the shelf. With the panel in position, the sides, which have until now been omitted in order to facilitate securing the wires to the battery studs, are fixed in position, the longer one, as mentioned before, being fastened by means of a hinge.

#### Securing the Batteries

Since flashlamp batteries vary somewhat in size it may be necessary to insert some cardboard strips, which have been soaked in paraffin wax, behind the batteries, so that they will be pressed

tightly against their studs when the hinged side is closed.

The instrument is now mechanically complete, the polishing or varnishing being left to the reader's taste.

Fig. 5 is a circuit diagram of the grid bias unit in use with a low-frequency amplifier. When more than one stage of low-frequency amplification is used, the unit will effectively apply negative potential to the grids of two or even three valves, providing that these are of the same type.

#### Alteration to Existing Amplifier

Only one alteration to the amplifier is necessary, and this is the breaking of the connection between one side of the transformer secondary winding and the valve filament. This transformer lead is connected to the terminal G.B. of the grid bias unit, preferably, by means of a terminal which should be mounted on the amplifier for this purpose. The terminals L.T.— and L.T.+ are merely connected to the corresponding terminals on the filament battery or on the set.

A considerably higher anode voltage must be applied to the valves when using grid bias.

Assuming that a 6-volt accumulator is used in conjunction with a bright emitter valve, as in Fig. 5, with 4 volts across its filament,

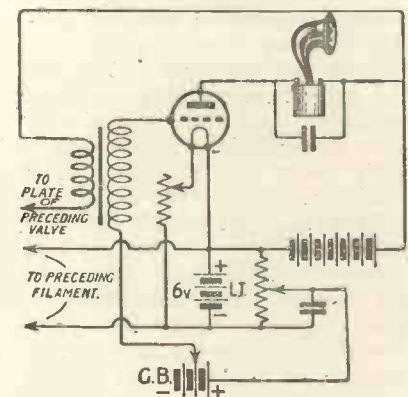


Fig. 5.—A diagram showing how the unit is connected up to an existing amplifier.

and with the rheostat in the negative lead, the negative terminal of the accumulator will have a negative potential of 2 volts with respect to the filament. Thus with the switch cutting out all the batteries in the unit and with the potentiometer slider as its extreme negative end, the grid has

(Continued in Col. 3, Page 419)

# Random Technicalities

By PERCY W. HARRIS, Assistant Editor.

*Some notes of interest to both the home-constructor and the experimenter.*

THE "D coil" receiver, which was described in *Wireless Weekly* recently, appears to have interesting possibilities. Some readers may wonder whether, in a coil wound to have so little external field, the total inductance may be comparable with a coil of the same diameter wound in ordinary solenoid form. For the purpose of finding to just what wavelength such a coil will tune, I wound a specimen from the data given by the inventor. If you will refer to the article you will see that it consists of ten turns for one winding and forty for the other on a 3 in. former. The ten turns of the smaller coil and ten of the larger are wound simultaneously, the four ends of the coils being brought out to suitable terminals.

## Practical Tests

Using the ten turns as an aperiodic aerial coil and the forty as the secondary winding of a crystal receiver (a variable condenser being shunted across the coil in the usual way) I tested the coil on an ordinary aerial to find what would be the minimum and the maximum wavelength with .0003  $\mu$ F condenser. The minimum turned out to be 180 metres and the maximum 450 metres. With a .0005  $\mu$ F it was possible to include 600 metres in the range. The inductance is thus slightly larger than one would obtain with the same number of turns wound in the conventional way upon an ordinary former of the same diameter.

## Transformer Data

It is surprising how few experimenters trouble to base the opinions they so freely express upon a sound foundation of measurement. Take, for example, the question of inter-valve L.F. transformers. How many experimenters trouble to make an accurate comparison between the

various makes? If you have the apparatus available, a rapid comparison of transformers is most interesting.

## A Testing Box

My own apparatus for the purpose consists of a box measuring 9 in. by 6 in. by 5 in. deep, fitted with an ebonite panel. This panel carries three knobs, each controlling a switch. The central switch is a four-pole two-way type, while the other two are the two-pole two-way type. There are, in all, fourteen terminals on



*The experimental D Coil.*

the panel, a row of eight along the back, two on the left, two on the right, and two in front. The row at the back is marked "IP, OP, IS and OS" in duplicate. The pair of terminals on the left are connected to the receiver. Those on the right are for connection to a valve panel. The pair of terminals in the front belong to a grid biasing battery, so that the valve used may be suitably adjusted on its curve.

The central switch changes the receiver from one transformer to the other, all four connections being altered at once. The switches on the left and right serve as reversing switches for IP and OP and IS and OS respectively. For operation the

instrument is connected up with a pair of transformers (one a standard transformer, the capabilities of which are well known), and the other the transformer to be tested. The input terminals of the test box are connected to a suitable receiver. The two output terminals are joined to a single-valve panel and, of course, the necessary grid bias applied by means of the terminals provided. A station is then tuned in, accurate adjustment of filament and plate voltages being made on the valve panel. A turn of the knob in the centre then removes the first transformer and substitutes the second, while a turn of the left- or right-hand knob soon establishes which way the transformer works better (IS or OS to grid and IP or OP to plate).

## Single Stage Work

If you intend to use only one stage of transformer coupled note magnification on a crystal receiver, you will probably not find a great deal of difference in the various makes of transformers. If, however, you desire to use two stages you will find there is a great difference. It is here that the cheap and shoddy transformer shows up so badly. One may seem quite fair by itself, but a pair of them will give the most irritating distortion.

When transformers are used with valve detectors a change of valve often makes a considerable difference in quality.

## An Important Difference

The average crystal has a fairly low impedance, and may work very well indeed with a transformer, the primary of which has far too low an impedance for the average valve. To get the very best results the impedances of valve and transformer should be matched, which means, of course, that all valves will not work equally well with the same transformer.



## A Novel Crystal Detector

ONE of the chief drawbacks of most crystal detectors is that they are too easily set out of adjustment by a slight knock or other cause, and many of them require a good deal of adjustment before a sensitive point is found. Carborundum in contact with a steel plate is perhaps the least troublesome of ordinary crystal detectors, but

firmly on the point of the crystal, as shown.

The stem of the cup may be held in the vice while the plug is held in place with the left hand, and the filling done by pouring the melted wax from a small tin held in the right hand. The wax must be allowed to set firmly before removing the plug. Fig. 3 (b) shows the completed crystal cup. On removing the plug a small cavity will be left with the crystal point exposed at the bottom.

In assembling the detector, the cup is first of all inserted in one end of the ebonite tube and the pin inserted to hold it in position. The brass cap and terminal are then fitted. The tube is then held vertically and the wax cavity filled with mercury. The rubber ring is next put in place and the copper contact piece inserted.

The rubber ring should be of sufficient thickness to necessitate a little pressure being exerted on the copper contact before its fixing-pin can be inserted. This will ensure that the cavity containing the mercury will be leak-proof.

The pin having been inserted,

the brass cap and terminal are fitted and the detector is complete and ready for use.

It may be remarked that it is advisable to test the crystal itself for sensitivity with an ordinary steel contact before mounting in the detector described.

It is, of course, necessary to use a battery and potentiometer

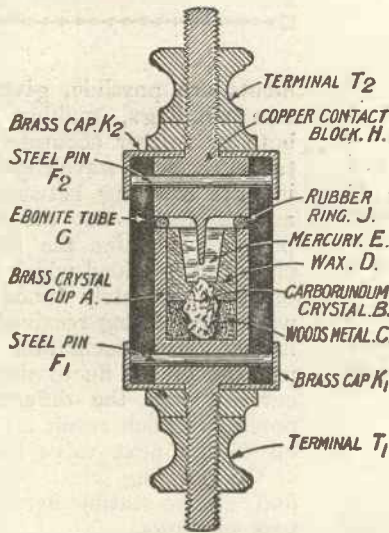


Fig. 1.—A sectional view of the detector, showing the construction. even this type has its disadvantages. If the crystal point is allowed to scrape on the plate it is likely to be spoilt, and in its usual form the crystal and contact plate are exposed to the atmosphere and dust.

The detector about to be described was devised to overcome these defects, and it gives very good results.

Its main features are a carborundum crystal in contact with mercury enclosed in an air-tight space.

The mounting of the crystal in the cup calls for special attention. The crystal is first fixed in position with a little Wood's metal in the usual way, as shown in Fig. 3 (a). It is then necessary to cover the crystal and the inside of the cup with insulating material, leaving only the point of the crystal exposed for making contact with the mercury. This is accomplished by filling the cup with wax, while holding a tapered soft metal plug

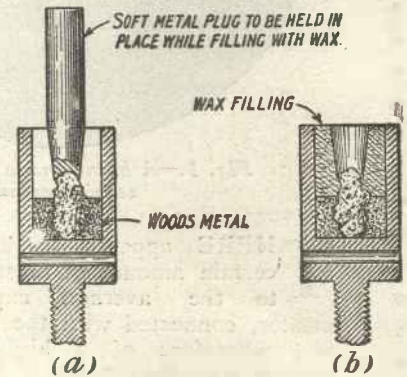


Fig. 3.—The crystal cup, showing method of fixing the crystal.

in conjunction with carborundum detectors to secure maximum sensitivity.

T. A. LEDWARD.

### ERRATUM.

We are asked to point out that in the advertisement columns of our last issue, the address of Messrs. W. Molback was wrongly given, the correct address being 24, High Holborn, W.C.1.

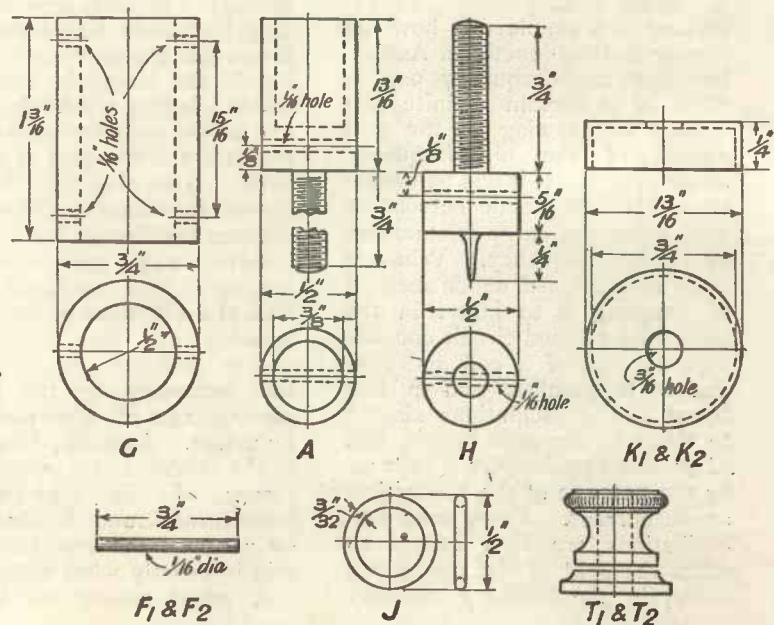


Fig. 2.—A detailed diagram showing the construction of the necessary parts.

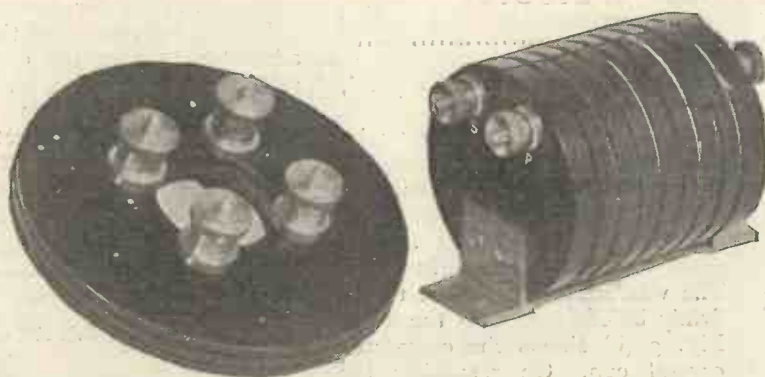


Fig. 1.—A home-made transformer of the disc type, and a semi-aperiodic "barrel" transformer.

THERE appears to be a certain amount of mystery, to the average experimenter, connected with the why and wherefore of a high-frequency transformer, but I hope to show in the course of these notes that it is a perfectly straightforward piece of apparatus, whose elementary theory is quite easily understood. True, there are mysteries connected with its behaviour, but they are not such as to affect the ordinary user.

#### The Tuned Anode Method

To anyone who understands the working of the tuned anode method of high-frequency amplification the transformer system will present little difficulty, and it should first, perhaps, be explained in a simple way how the former method functions. Assuming that high-frequency oscillations of a certain definite frequency are flowing in the grid circuit of the high-frequency amplifying valve, it will be understood that the anode current of that valve will carry fluctuations of similar frequency. What is done in the tuned anode method of coupling is to insert in the plate lead a tuned circuit consisting, usually, of a coil and condenser in parallel, and in this tuned circuit oscillations similar to those in the grid circuit, but of greater amplitude, are built up by the passage of the fluctuating anode current. These amplified oscillations are then caused to affect the grid of the succeeding valve, in the ordinary manner.

The grid of the next valve is actually connected through a small condenser to the plate end of the tuned anode circuit, in order to prevent the high positive potential of the anode battery upsetting its functioning. Since a grid condenser must be used in this way, it follows that a grid-leak must also be employed, usually, to maintain the grid at a suitable working potential.

#### Action of a transformer

In its essentials, the high-frequency transformer functions in a very similar manner, the main difference relating to the method of handing the energy on from the anode circuit of the first valve to the grid of the next. Instead of making a direct connection through a suitable condenser, the high-frequency transformer performs this transference by including in the magnetic field of the anode winding a secondary winding whose ends are connected to the grid and filament of the next valve. Assuming that the transformer functions in the ordinary manner familiar in the case of a low-frequency transformer, the magnetic field produced by the flow of oscillations in the primary winding will then cause alternating voltages to appear in the secondary by the familiar phenomenon of electro-magnetic induction. Actually, this is one of the controversial points in the theory of the high-frequency transformer, and it should not be assumed too confidently that this is exactly what happens.

A great variety of arrange-

## High-Frequency

By G. P. KENDALL

In view of the increasing popularity of the high-frequency transformer, the following are some of the types and use of these instruments.

ments are possible, given these two windings, making one or both or neither accurately tuned to the received wavelength, varying the coupling between them, and so forth, but the essential principle remains the same. A circuit is provided which is more or less accurately tuned to the wavelength being received, which is set into oscillation by the passage of the fluctuating anode current, and the differences of potential which result are passed on to the next valve by virtue of the coupling (electro-magnetic and electro-static) between the two windings.

#### Types of High-Frequency Transformers

There are three main types of high-frequency transformer at present in use, and since they have somewhat different characteristics and hence applications, it is desirable for the experimenter to understand in a general way how they work and

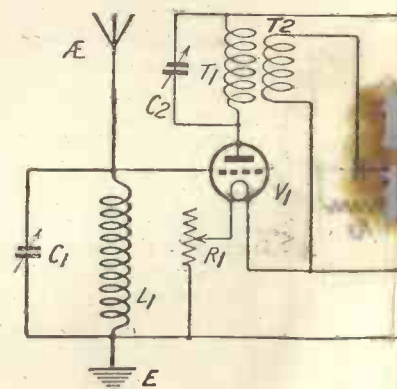


Fig. 3.—A 2-valve circuit with a transformer.



# ency . . . Transformers

L., B.Sc. Staff Editor.

popularity of the high-frequency  
type, which explains the action  
will be of considerable interest.

how they differ from one another. The tuned type is the one which is now most commonly seen, and this is the simplest from the theoretical point of view. In one form not often used, but nevertheless capable of giving good results, the "transformer" can consist simply of two ordinary plug-in coils, tuned by two variable condensers, mounted upon a two-coil holder and more or less closely coupled together. This arrangement, of course, is exactly the same as that which is known as a loose-coupled tuner in which the coils are respectively the aerial and secondary circuit inductances. The two circuits must be tuned to resonance with the desired frequency, and the energy is handed from one to the other mainly by virtue of the magnetic coupling between them. When this arrangement is used as a transformer one of the coils is connected in the anode circuit of the high-frequency amplifying valve, and the other

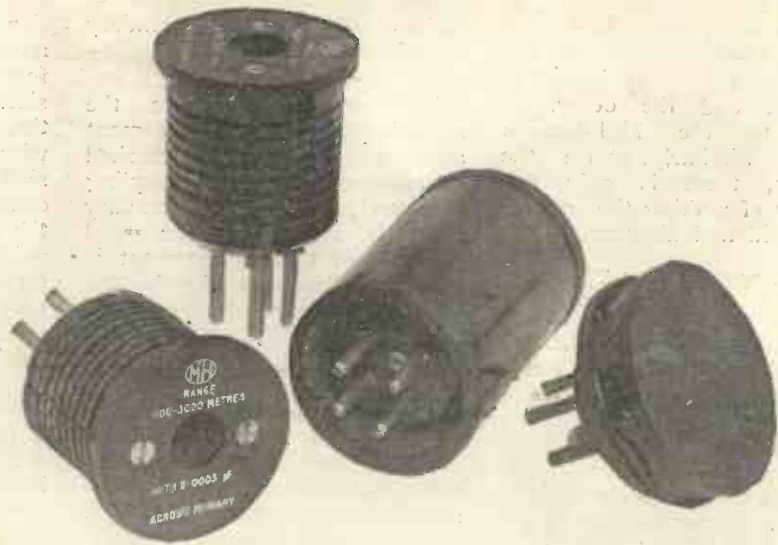


Fig. 2.—Various types of tuned transformers with plug-in mountings.


is connected to the grid and filament of the following valve. The general effect of varying the coupling is practically the same as in the case of the loose-coupled aerial and secondary circuit tuner, that is to say, that the closer the coupling the stronger the signals up to a certain point, and the weaker the coupling the greater the selectivity, with diminished signal strength.

## Later Improvements

It will soon be found by the user of such an arrangement as this that tuning is somewhat difficult, and the whole device rather cumbersome. If experiments are made towards its simplification, it will be found that if the coils are placed exceedingly close together to secure the maximum possible coupling, the tuning condenser across one of the windings, say, the secondary, can be entirely dispensed with, with only a very slight diminution in signal strength. Two circuits which are exceedingly closely coupled, it is well known, can be tuned by means of only one variable condenser, and advantage is taken of this fact in the majority of present-day tuned high-frequency transformers. The two windings are commonly placed in narrow slots in an ebonite former,

the actual winding being carried out in a more or less haphazard manner, the result forming what is known as a slab winding. Since exceedingly close coupling between primary and secondary appears in many cases to give improved results, one of the earliest successful tuned high-frequency transformer receivers employed transformers in which the two windings were run into the slot simultaneously, so that the two wires actually lay more or less side by side throughout the winding. Good results were obtained in this way, but the practical difficulties were considerable, since the insulation of these very fine wires is by no means robust, and leakages here meant short circuiting the high-tension battery.

A modification which was adopted to overcome this trouble is to wind on first the primary winding, then a few turns of silk to completely cover the wire, and then over this the secondary. Such transformers function quite well, but they have the practical drawback from the point of view of the experimenter that of all the various ways of connecting them up there is only one which gives proper results, and a number of others which give only poor results, so that it is sometimes exceedingly confusing to decide whether a given trans-

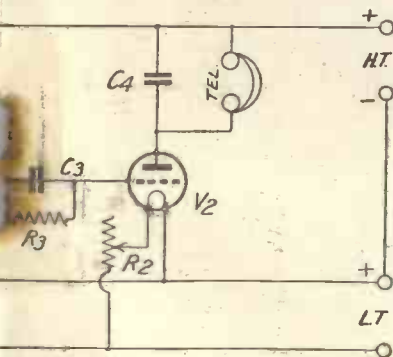

"tuned primary" transformer.

former is really doing its best. It is usually found that only one of the two windings can be employed as the primary, and that it is most essential that the correct end should be joined to the plate, and the other, of course, to the high-tension positive. Similarly, with the secondary, there is only one right way of making the connection to grid and filament.

#### The Separate Slot Type

The matter becomes very much simpler when the two windings are placed in separate slots side by side, with a narrow space of ebonite between them. When this is done, one winding can be adopted as the primary, quite arbitrarily, and it merely remains to reverse the connections to the two ends of this winding or alternatively of the secondary to obtain correct results. In the majority of cases this arrangement is now adopted, and in at least two well-known makes a number of slots are employed connected up alternately in series, primary and secondary, and it appears that the slight loosening of coupling which results is not really disadvantageous. Indeed, a deliberate further loosening is done in some cases by cutting the slots for the primary a little deeper than those for the secondary. It is difficult to see what advantage this can be without separate tuning of the windings, but the transformers in question certainly perform very well.

#### Tuning Arrangements

With any of these types it is possible to tune either primary or secondary, and there is little to choose between these two possibilities. The majority of those now upon the market are intended to function with a condenser across the primary, and their turn numbers are calculated accordingly. Nevertheless, the tuned secondary has some advantages, the principal one being a slight increase in the stability of the receiver when two or more stages are employed. When the secondary is tuned it is duly set into oscillation, of course, by the passage of the fluctuating anode current through the primary, and it would appear that there is a little less back-transference of

energy through the valve in this case. This appears to be the reason for the slight gain in stability with the tuned secondary transformer.

#### Loose Coupling

The only case where the secondary tuning arrangement appears to possess marked advantages is where the coupling between primary and secondary is made variable, and a good example of this arrangement is that known as the Grebe C.R.13. In a good form of this circuit two plug-in coils are used for primary and secondary, two No. 75's being suitable for broadcast wavelengths. A variable condenser of  $.0003 \mu F$  can be connected across the secondary coil, and the two should be mounted upon a two-coil holder.

line of experiment for anyone possessing the means to carry out the fairly simple constructional work involved. A lathe is most desirable for the making of formers of various sorts and sizes, and given this appliance there is no reason why anyone with a certain amount of patience should not make some useful contribution to our knowledge of the subject. As a good starting-point for experiment, a transformer should be made capable of giving results equal to those of the best types now in use, and this can be done by either turning or obtaining ready turned an ebonite bobbin  $2\frac{1}{2}$  in. in diameter,  $\frac{1}{4}$  in. thick, and with two slots  $\frac{1}{8}$  in. wide and  $\frac{1}{4}$  in. deep turned in its edge. These slots can be spaced apart about  $1/16$ th in.,

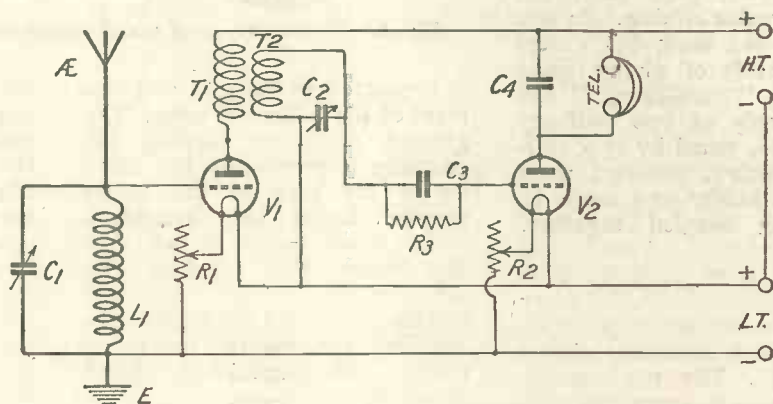


Fig. 4.—The connections of a "tuned secondary" H.F. transformer.

There appears to be definitely a best position for the primary coil with respect to the secondary, and a little care should be taken in adjusting the coupling. The principal advantage of this circuit appears to be that very little energy is transferred back through the inter-electrode capacity of the high-frequency valve to its own grid circuit, consequently there is no need to damp down the amplification obtained to prevent self-oscillation. In the case of two stages of high-frequency amplification this method can be employed, and is capable of giving wonderfully good results in fairly skilled hands, but, of course, there are a large number of variable factors:

#### Construction

The construction of high-frequency transformers of the tuned type provides a most interesting

that is to say, the dividing wall between them should be  $1/16$ th in. thick, and about 80 turns of No. 40 s.s.c. wire in each will be found correct with a variable condenser of  $.0003 \mu F$  across the primary for wavelengths of 300 to 500 metres. Since rapid comparison is essential in working with high-frequency transformers, as indeed it is in the majority of wireless experiments, it is desirable to adopt the convenient convention of mounting the transformer with four valve pins in its centre, to plug into an ordinary valve socket. Transformers of all sorts are thus interchangeable, so long as the same scheme of connections is adhered to, and one can always instantly compare any new developments which one may produce with the standard. Also, of course, rapid changes of wavelength become possible.

(To be continued)



## A Double Purpose Voltmeter

**M**OST of us use a voltmeter either for testing the condition of the filament battery or for discovering the E.M.F. most suitable for the filaments of various types of valves; but comparatively few people ever bother to measure the amount of grid-biasing voltage applied to their low-frequency valves, being content to use flashlamp batteries for the purpose and to reckon them always at 1.5 volts per cell. This is unsatisfactory, for two reasons: in the first place, voltage falls off when the battery has been in use for some time, even though the current drawn from it is of tiny proportions, and secondly, no account is taken of the voltage drop through the filament rheostat. A simple method of using a voltmeter which is not mounted on the set for measuring both grid and filament potentials is shown in Fig. 1. Leads from the filament busbars are brought to one pair of terminals, whilst to another pair are taken leads running from the negative leg of the filament and from the I.S. of the transformer secondary. With some voltmeters it does not

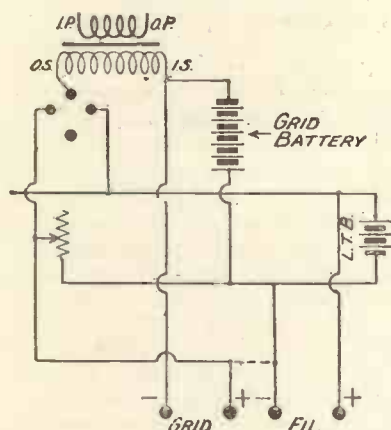


Fig. 1.—The internal wiring necessary when a voltmeter is used outside the set.

matter in which direction current is passed through them, as they have a central zero mark, but other instruments have terminals marked plus and minus and read only if current flows in the right direction. If terminals are arranged and marked, as shown in the drawing,

readings can be obtained in a moment of either grid or low-tension potentials. The low-tension reading in this case will show the E.M.F. of the accumulator. If it is desired to be able to read the voltage applied across the filament of the valve, then the negative-filament terminal should be connected (as dotted) to the negative leg of the valve instead of to the busbar lead.

Where the voltmeter is mounted on the set a rather more elaborate arrangement will be necessary.

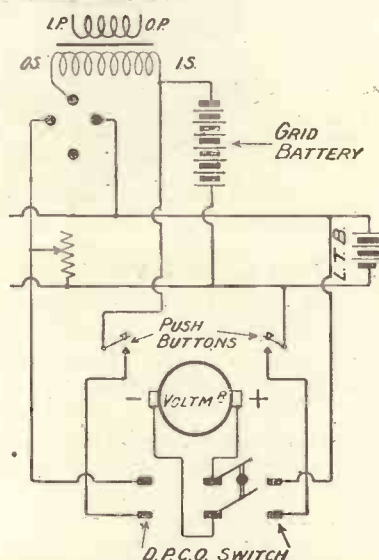


Fig. 2.—Showing how to wire up when the voltmeter is mounted upon the panel of the set.

Fig. 2 shows how this can be done quite neatly. Two small push-buttons are mounted one on either side of the voltmeter, and either above or below it is placed a double-pole change-over switch of the midget type. When the switch is brought over towards the right, pressure upon the right-hand push-button will cause the instrument to record the E.M.F. of the low-tension battery. By throwing the switch over to the left the other push-button can be used to obtain the grid voltage reading. Here again the low-tension voltage reading will be that of the accumulator. If it is desired to obtain the filament reading the right-hand push-button must be wired into the lead from the nega-

tive leg of the valve as previously indicated, by disconnecting the push-button from the negative lead to the accumulator, and connecting it to the negative leg of the valve filament.

R. W. H.

## Utilising Valves to Best Advantage

Continued from page 413.

a negative potential of 2 volts with respect to the filament. This voltage can be changed to 4 volts + by rotating the potentiometer knob until the slider is at the other end of the resistance. Only the negative part of this variation is of any use, however, but by switching in one flashlamp battery by placing the switch arm on the third stud, a variation between  $6\frac{1}{2}$  volts— and  $\frac{1}{2}$  volt— is obtainable. With the arm on the fifth stud, the variation is from 11 volts— to 5 volts— and by switching over to the last stud variation between  $15\frac{1}{2}$ — and  $9\frac{1}{2}$  volts— may be obtained, this being for use only with very high anode potential.

The particular voltages given apply only when the valve is used under the conditions mentioned; but regardless of the voltage allowed across the filament, providing a 6-volt accumulator is used, any voltage between zero and  $13\frac{1}{2}$ — may be applied to the grid of the valve in the manner described.

Should a 4-volt filament heating battery be used or one of lower voltage in conjunction with dull emitter valves, a continuous variation of the grid potential will not be obtainable. The lower the voltage of the filament battery, the greater will be the gaps between the variations. This is owing to the fact that the difference of potential across the gaps is equal to the voltage across any two consecutive tappings of the biasing unit ( $4\frac{1}{2}$  volts) minus the voltage of the filament battery. Thus to avoid these gaps it will be seen that the filament battery should have a voltage of not less than  $4\frac{1}{2}$  volts. Using a 4-volt battery, however, the gaps which are of only  $\frac{1}{2}$  a volt, may be easily compensated for by adjustment of the anode potential.

## How Every Crystal User may become a Valve Expert

By E. REDPATH,  
Assistant Editor.

*Continuing from last week's instalment, the present article explains how reaction may be employed and gives constructional details of a complete receiving set embodying the principles dealt with so far.*

### Introducing Reaction

**B**Y slightly modifying the arrangement described in the last article, as indicated in the circuit diagram, Fig. 3, it is possible to make use of the principle of reaction. Referring to Fig. 3, it will be seen that, in addition to the aerial tuning inductance  $L_1$ , and the original anode-tuning inductance  $L_2$  (part of an original crystal receiving set), a further inductance,  $L_3$ , has been introduced in the anode circuit of the valve.

As it is necessary that  $L_3$  should be variably coupled with the aerial tuning inductance  $L_1$ , a very convenient method would be to remove the single fixed coilholder from the baseboard of the apparatus illustrated in the previous article, and substitute a two-coil holder provided with the usual ebonite knob or lever, by means of which the angle between the coils may be varied. In this case, the coil  $L_3$  may conveniently consist of a No. 35 or No. 50 plug-in coil.

A pictorial representation of the suggested arrangement is given in Fig. 4, and the action involved is as follows:—

The high-frequency pulses of anode current, which, in the oscillatory circuit  $L_2, C_2$ , build up to fairly powerful oscillations, are now made to traverse the coil  $L_3$ . If this coil is coupled to the aerial tuning inductance  $L_1$  in the correct direction as regards their respective windings,

the effect will be to strengthen the oscillations in the aerial circuit, thus causing increased changes in grid potential, and consequently more powerful anode pulses with oscillations of greater amplitude set up in the circuit  $L_2, C_2$ , and louder signals in the telephones  $T$ .

If the coupling between the coils  $L_3$  and  $L_1$  is increased unduly, by bringing them too close together, the strengthening effect will be such as to cause the whole system to become unstable and to actually generate oscillations.

### A Precautionary Rule

This point must be most carefully watched, as the radiation of energy from the aerial, which occurs when the set is oscillating, is certain to cause interference with adjacent receiving stations.

It is thought that it may be taken for granted that no reader will wish to interfere with any neighbouring receiving station by using reaction in a manner not only contrary to the terms of his licence, but which must of necessity impair the clarity of his own reception.

A safe plan is to make a rule never to increase the reaction

coupling sufficiently to cause the received speech, music, etc., to lose its natural quality and tone.

### A Complete Receiver

The photograph, Fig. 1, shows a receiving set complete with valve and plug-in coils. Fig. 2 is another photograph of the same set with the coils and valve removed to show more clearly the arrangements of the various components.

In this one set are embodied the various principles explained in the beginning of this present and preceding articles. The valve functions as a high-frequency amplifier and incoming signals, after undergoing one stage of high-frequency amplification, are rectified by a crystal detector.

By this arrangement, signals which would be quite unable to actuate the crystal detector direct, may be made to give clearly audible signals in one or two pairs of telephone receivers, a result which could not possibly be obtained by using one or even more valves as low-frequency amplifiers following a crystal set.

### The Results Obtainable

With the set as illustrated, used in conjunction with a good outdoor aerial, perfectly clear speech was received from several

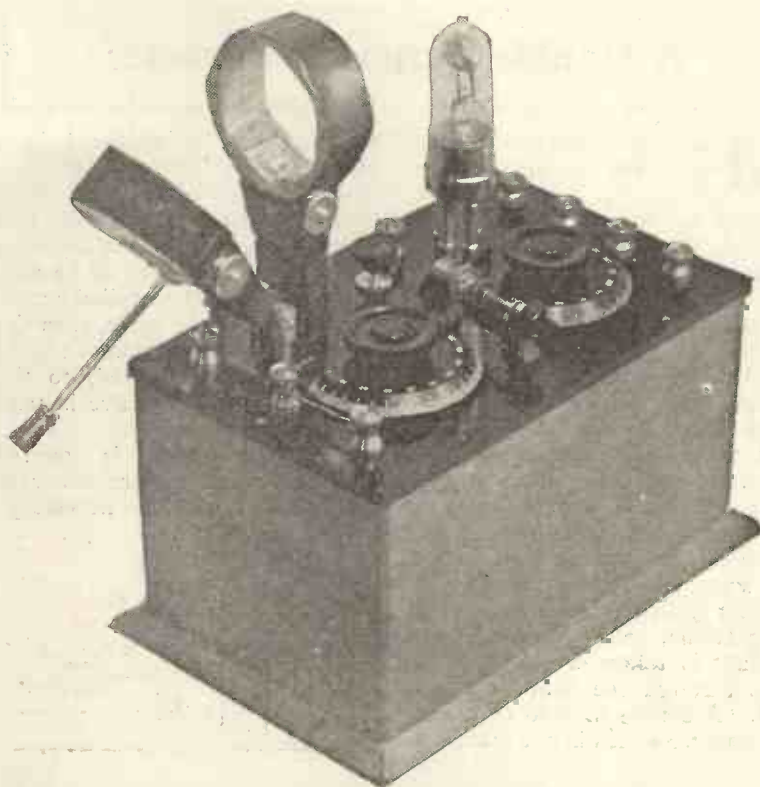


Fig. 1.—A photograph of the complete receiver described in this article.



of the British broadcasting stations, also from Chelmsford, Radiola, Paris, Brussels, the Hague and Amsterdam, suitable coils being used, of course, in the case of the long-wave stations.

Speech and music transmitted

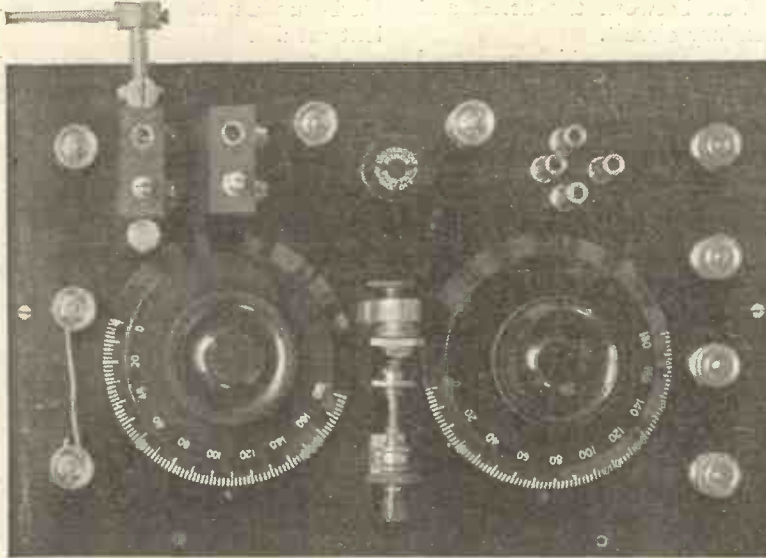


Fig. 2.—A close-up view of the top of the panel, with coils and valve removed, to show the layout of the parts.

by the local broadcasting station, some 15 miles distant, were received with considerable strength and with particular clarity and purity of tone. At such a distance from the transmitting station it was these latter points which proved more noticeable than mere loudness.

The set also proved extremely selective, and, although there are only three variable controls, careful adjustment of these is necessary in order to obtain the best results. This matter will be referred to again presently.

#### Circuit Arrangements

Fig. 5 is a theoretical circuit diagram of the receiving set, and careful reference to the diagram in conjunction with the following explanation will enable the action to be understood.

On the left of the set are three terminals, A<sub>1</sub>, A<sub>2</sub> and E (Fig. 5). With the aerial lead connected to the terminal A<sub>2</sub> and the terminal E earthed, the variable condenser C<sub>1</sub> is in series between the aerial itself and the aerial tuning inductance L<sub>1</sub>. This is the best arrangement for the reception of short waves, the inductance L<sub>1</sub> consisting of a 50-turn plug-in coil.

With the aerial lead connected to the terminal A<sub>1</sub>, and terminals

A<sub>2</sub> and E connected together by means of the short-circuiting link shown (or a piece of bare copper wire), the condenser C<sub>1</sub> is in parallel across the inductance L<sub>1</sub> which, for the British broadcasting wavelengths, may be a 35-

turn or a 50-turn coil. For the Hague and Amsterdam a 100-turn coil will be necessary, a 150-turn coil for Chelmsford and Radiola, and a 250-turn coil for Eiffel Tower.

The sizes of the coils depend to some extent upon the dimensions of the aerial to which the set is connected, but, provided that the variable condenser C<sub>1</sub> has a maximum capacity of 0.001  $\mu$ F, the sizes quoted will be found satisfactory.

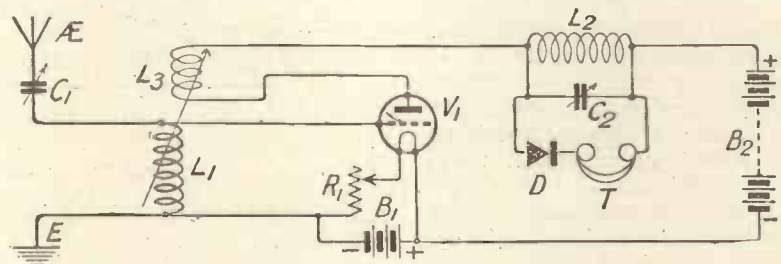


Fig. 3.—A circuit similar to that given in Fig. 3 of our last issue, but with a two-coil holder to enable reaction effects to be obtained.

#### Capacity of Variable Condenser

In connection with any receiving set, it should be borne in mind that when using a variable condenser in series in an aerial circuit, its value should not be reduced below about 0.0002  $\mu$ F and preferably should vary between 0.0003 and 0.001  $\mu$ F.

When using a variable condenser in parallel across an aerial tuning inductance, it should be the object of the operator to have as large a value of inductance and as small a value of parallel capacity as possible.

Referring again to the theoretical circuit diagram, Fig. 5, it will be seen that the aerial end of the tuning inductance L<sub>1</sub> is connected direct to the grid of the valve, whilst the earth end of the same coil is connected to the negative side of the filament. When the aerial circuit, therefore, is tuned to the same frequency as the incoming signals, potential differences are set up between the ends of the coil L<sub>1</sub> and are applied to the grid and filament of the valve. The positive side of the high-tension battery B<sub>2</sub> is connected to the anode of the valve, via the inductance L<sub>2</sub>, whilst the negative side of the battery is, of course, connected to the filament of the valve.

The varying grid potential, due to the incoming signals, causes the electron flow from filament to anode (equivalent, of course, to current flow from the high-tension battery to the anode) to vary at the same frequency. In parallel across the inductance L<sub>2</sub>, however, there is the variable condenser C<sub>2</sub>, and, if the latter is adjusted so that the oscillatory circuit L<sub>2</sub> C<sub>2</sub> is tuned to the same frequency as the aerial circuit, the high-frequency pulses of current from the high-tension battery cause oscillations of considerable amplitude to be built up in the closed oscillatory circuit.

The action is, in fact, somewhat similar to the development of large swings or oscillations of a heavy pendulum by the application of small but correctly-timed impulses.

#### Rectification

The amplified oscillations in the closed circuit L<sub>2</sub> C<sub>2</sub> are then

rectified by the crystal detector D and made audible in the telephone receivers T, both of which are connected across the variable condenser C<sub>2</sub>.

The anode inductance L<sub>2</sub>, which should consist of a coil at least one size (50 turns) larger than the aerial coil L<sub>1</sub>, is variably coupled to the latter, and, provided that their respective windings are in the correct sense, some of the energy of the amplified oscillations will be re-transferred to the aerial circuit, so

gives out unexpectedly. At the same time it indicates that it is a comparatively simple matter to add a high-frequency amplifying valve to an existing inductively coupled crystal receiver, the valve itself acting as a kind of amplifying link between the aerial and secondary circuit.

A photograph which appeared with the first article of this series, illustrated one of the ex-Government Mark III\* receivers with a high-frequency amplifying valve added in this manner.

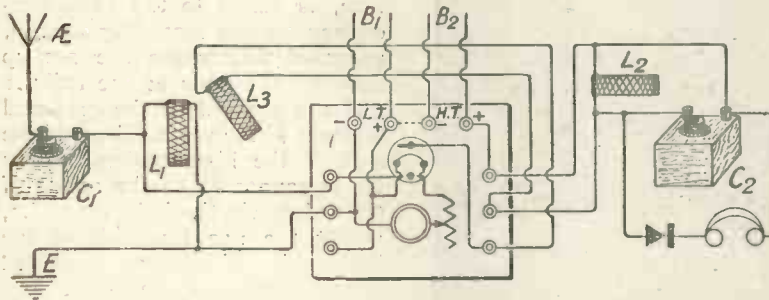


Fig. 4.—A pictorial representation of Fig. 3. The coil L<sub>2</sub>, condenser C<sub>2</sub>, crystal detector and telephones being those of any crystal receiving set.

strengthening the oscillations applied to the grid and filament of the valve. This is known as a reaction or regenerative effect, and, as already pointed out, an unnecessarily tight coupling between the coils L<sub>2</sub> and L<sub>1</sub> (that is to say, bringing the coils too close together) will not only completely spoil the effect, but will be practically certain to cause interference to adjacent receiving stations.

#### As a Crystal Receiver

Suppose the valve, rheostat, filament lighting battery B<sub>1</sub> and high-tension battery B<sub>2</sub> to be omitted from the diagram, Fig. 5. There remains an ordinary inductively coupled crystal receiver with aerial circuit tuned by the series-parallel condenser C<sub>1</sub>, the closed oscillatory or secondary circuit L<sub>2</sub> C<sub>2</sub>, inductively and variable coupled to the aerial circuit, and the detector D with telephones T connected, as usual, across the secondary condenser.

With the set illustrated in the photograph, Fig. 1, it is only necessary to turn out the valve and disconnect the high-tension battery to enable it to be used as a selective crystal receiver. This will be found very useful on occasions when the accumulator

#### Components Required

The following are the components as fitted in the actual set illustrated. It is to be understood, however, that any reliable make of components may be employed. Similarly, it is not

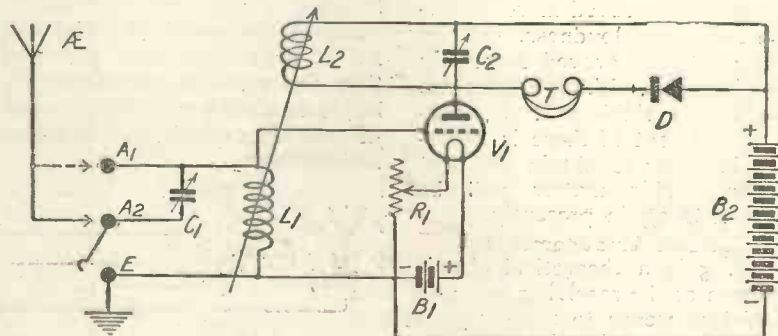


Fig. 5.—The circuit used in the receiver.

essential that the containing box and ebonite panel should be of exactly the dimensions specified, and, provided that all connections are correctly made, the results obtained should prove quite satisfactory:—

- Nine terminals.
- Four valve legs and nuts.
- One filament rheostat (Lissenstat).
- One 2-coil holder.
- Two variable condensers, one 0.001  $\mu$ F, and one 0.0005  $\mu$ F (Jackson Bros.).

One crystal detector. (That fitted to the original set is an ex-Government "Perikon" detector.) Practically any type of detector will do, but, for stability, one of the firm contact type is preferred to one of the cat-whisker type. Carborundum-steel gives excellent results.

(Further constructional details will be given next week.)

#### Handy Pliers

ONE of the most ingenious kinds of pliers that the writer has struck is a pattern made in America. These are so arranged that however wide open or close together the jaws may be they are always parallel with one another. With ordinary pliers the jaws are, of course, at an angle to one another, which means that they can never obtain a very secure grip upon a round object. The parallel jaw pliers are delightful to work with, for once they have a grip they never slip. The writer uses a small pair of gas pliers of this kind for wireless work and finds them a great help. Nuts can be tightened with them without any risk of their slipping and burring the edges,

and they are of the utmost value in a whole host of other ways. These pliers are very little more costly than those of the ordinary type, and any constructor who visits a tool shop should certainly ask to see them.

Another tool which is exceedingly handy is a pair of nut pliers of small size. These are so arranged that they do not slip when a nut is gripped with them, and they are exceedingly useful for getting at small nuts in out-of-the-way corners. R. W. H.



# Time Signals

## SOME INTERESTING CORRESPONDENCE

*The following letters, which have passed between Radio Press, Ltd. and the British Broadcasting Company, Ltd., will doubtless prove of interest to our readers.*

The British Broadcasting  
Co., Ltd.,  
2, Savoy Hill,  
Victoria Embankment,  
London, W.C.2.

July 16, 1924.

DEAR SIRs,—We believe that your time signal broadcasting system is one of the most useful features of your service, but we think that its value would be greatly enhanced if a time signal could be sent out at 8 a.m. and at 12 noon. The present times are not by any means always convenient, and the "10 o'clock time signal" is often sent later.

The proposed 8 o'clock time signal would be extremely useful for those going to business, and what is more, those who are regulating clocks and watches would not have to wait 24 hours, as at present, in most cases.

Trusting you will give these suggestions careful consideration.—We remain, yours faithfully,

RADIO PRESS, LTD.,  
JOHN SCOTT TAGGART,  
Chairman and Managing  
Director.

Messrs. Radio Press, Ltd.,  
Devereux Court,  
Strand, W.C.2.

July 18, 1924.

DEAR SIRs,—Many thanks for your letter of the 16th inst. regarding our time signals, which we have read with interest.

From your allusion to the possibility of having to wait twenty-four hours for our time signal, it appears that you are not fully aware of the number of times daily when either Big Ben or Greenwich, or both are broadcast. For your information we would mention that the Greenwich signal is given daily at 4 p.m. and 10 p.m., subject, of course, to there being nothing in course of transmission which does not interfere. Big Ben is broadcast at 1 p.m. on Tuesdays, Thursdays and Fridays and daily at 6 p.m. and 7 p.m. On Sundays Big Ben is given at 3 p.m. and 5 p.m.

We think that you will probably agree that with all these time signals being broadcast most of our hearers have already sufficient opportunities for synchronising their watches or clocks.—Yours faithfully,

C. H. LEWIS,  
Organiser of Programmes.  
The British Broadcasting  
Co., Ltd.

The British Broadcasting  
Co., Ltd.,  
2, Savoy Hill,  
Victoria Embankment,  
London, W.C.2.

July 21, 1924.

DEAR SIRs,—We thank you for your letter of July 18, but regret to say that we still consider the time signal transmission inadequate for the purposes we mentioned.

The transmission of Big Ben, while interesting and perhaps sufficiently accurate for some, is not accurate enough for the correct checking of watches and clocks.

The Greenwich time signal is the only one which may be said to be sufficiently accurate for this purpose, and this signal, as you state, is given at 4 p.m. and 10 p.m. In the first place, the time between 4 p.m. and 10 p.m. is rather short for adequate checking, and, secondly, the great proportion of those who wish to check their watches would be at business at 4 p.m., and consequently the signal would be of no assistance to them.

We cannot help but feel that, in view of these remarks, a time signal transmission at 8 a.m. from Greenwich and one at, say, 1.30 p.m., would be desirable.

We particularly think that the 8 a.m. time signal should be sent to enable many of your listeners to check their watches and clocks before going to business in the morning.—Yours faithfully,

RADIO PRESS, LTD.,  
JOHN SCOTT TAGGART,  
Chairman and Managing  
Director.

P.S.—With your permission we would like to publish this correspondence in view of the interest taken in the transmission of accurate time signals throughout the country.

J. Scott-Taggart, Esq.,  
F.Inst.P., A.M.I.E.E.,  
Radio Press, Ltd.,  
Devereux Court,  
Strand, W.C.2.

July 23, 1924.

DEAR SIR,—We are in receipt of your letter of the 21st inst., and note that you still consider our time signals inadequate for those who wish to check accurately their clocks and watches.

We have been considering for some time the question of revising our present arrangements in regard

thereto, and we are happy to inform you that, in future, the following time signals will be relayed from Greenwich and Big Ben:—

Greenwich daily at 1 p.m., 4 p.m. and 10 p.m.

Big Ben daily at 6 p.m., 7 p.m., and at the end of the evening programme if this finishes within five minutes before any 1-hour.

We note your suggestion with regard to the 8 a.m. time signal from Greenwich, but we do not consider this is necessary at the present time.

We shall be happy for you to publish this correspondence if you so desire.—Yours faithfully,

For the BRITISH BROADCASTING  
Co., LTD.,  
C. H. LEWIS,  
Organiser of Programmes.  
The British Broadcasting  
Co., Ltd.

### VALVE NOTES

(Continued from Page 407.)

length, although a No. 50 will do, the best size is probably No. 75. The condenser C4 may conveniently be a .0005  $\mu$ F variable condenser, or one of .0003  $\mu$ F capacity. The telephone condenser C6 has a capacity of .002  $\mu$ F.

Experiments may be carried out by cutting out C1, and the experimenter will be interested in trying the effect of coupling L3 to L1, instead of to L2.

### BINDING CASES

Binding cases and indexes for Vol. III are available, and binding can be done for those readers who desire it. Back numbers should reach us during the last week of each month, and binding is done during the first week of the following month.

Prices: Cases only, cloth 2s. 6d. (post 4d.), half leather 4s. 6d. (post 4d.); binding and supplying case and index 4s. 6d. (post 1s.) and 7s. 6d. (post 1s.) respectively.



# Correspondence

## A ONE-VALVE REFLEX CIRCUIT

SIR,—It may not be known to many home constructors what interesting results can be obtained by the use of a single-valve reflex circuit with a loose-coupled aerial.


The set is easy to construct, comparatively inexpensive, and, above all, harmless to one's neighbours (which cannot be said of the straightforward one-valve set with reaction, especially in the hands of a beginner), since the well-known property of the reflex valve of rapidly changing from H.F. to L.F. oscillation (and vice-versa), will compel the unfortunate culprit to loosen the reaction.

The addition of the three-coil holder does away with probably the chief objection to a reflex circuit, namely, the coarseness of tuning, with the result that a really good variable condenser with vernier (such as the Sterling "straight line" condenser) is essential for tuning.

It will be seen from the diagram that the usual "tune-stand-by" switching has been simplified and the DPDT has been replaced by a SPDT switch; but, what is more important from the financial point of view, the same condenser with

clips, but the writer has not found this essential, and prefers to resort to home-made basket coils for the

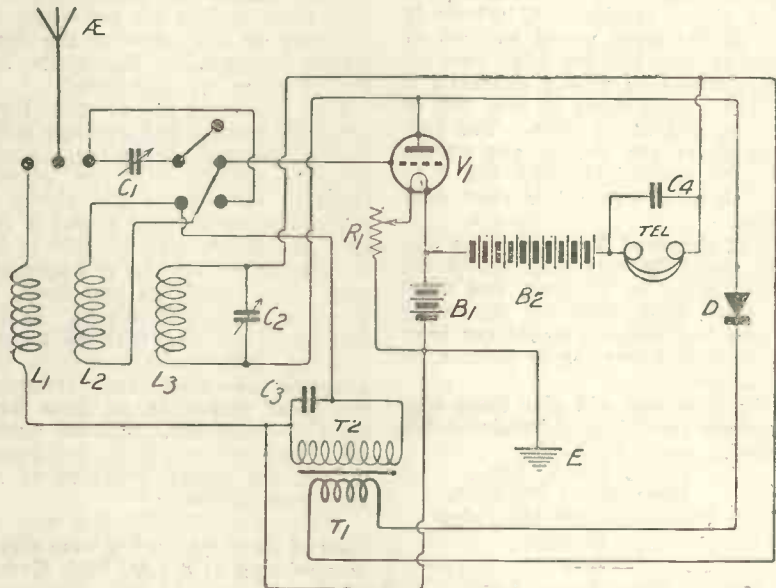factory, which only too often is not the case with the ebonite at present on the market. Two small tumbler




*A diagram of the circuit, showing improvements made by our correspondent.*


necessary rough tuning of the primary.

With regard to components and cost, the panel is 9 in. x 12 in., and

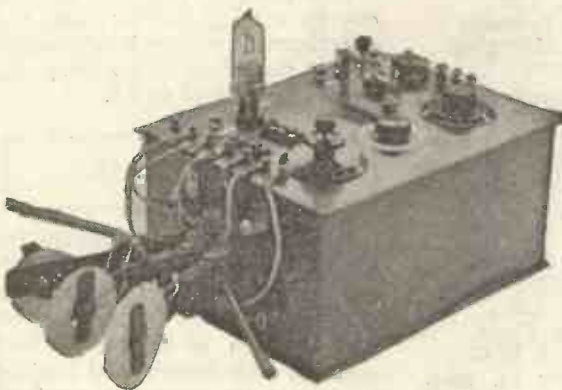switches for H.T. and L.T. were fitted on the panel; these, while adding somewhat to the appearance of the set, cannot be regarded as



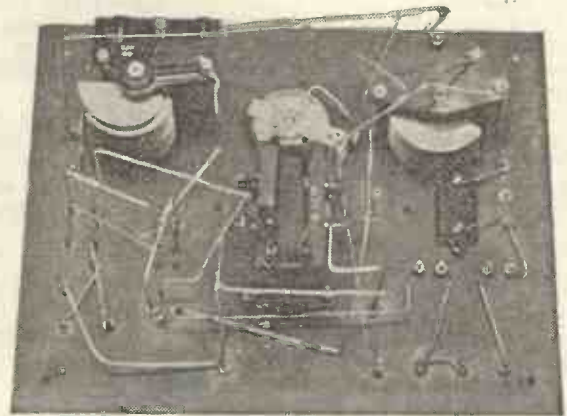*A photograph of Mr. Naunton's receiver.*



*A view of the wiring of the one-valve reflex receiver.*

vernier is used both for "tune" and "stand-by" positions. A cheap variable condenser, should the user so desire, can easily be put across the primary coil by slipping its leads into the Ilgranic coil-holder spring

made of 3-16th in. thick ebonite with two supporting legs. This, although rather too thin, was used because it was already in the possession of the writer, and has been tested electrically and found satis-

at all essential. Several transformers were tried, and it was found that the better makes (Marconi, R.I., Sterling, etc.) were practically equal (perhaps the 1:3 is a little better than the 1:5 in a reflex cir-



cuit), whereas with the cheaper brands there was considerable howling when the valve was fully turned on. With regard to the crystal rectification, it is essential to have some mechanical contrivance for adjusting the pressure of the cat's whisker, because under certain conditions of reception, too much pressure is as harmful as too little. Hertzite, with a small spring of Resistin wire (or any nickel alloy) was found very satisfactory. Lastly, we come to what is the most important component, namely, the valve. When a valve is being used for some single purpose in a non-reflex circuit there is usually little to distinguish one make from another; this, however, is far from true when used in reflex circuits. The writer has tested several valves, British and foreign, on this set, and there is no doubt that the outstanding valve is the Cossor (PI). This assertion is made for no other reason than giving credit where it is due. The Cossor was found to work best on this set with 6v. L.T. and 66v. H.T., although good results were obtained with 4v. L.T. The total cost of the parts (including the mahogany cabinet) was about eight pounds.

When wiring the panel care should be taken to keep the plate and grid circuits as well separated as possible.

Another precaution which amply repays the trouble is to test the valve-holder (and ebonite through which the valve sockets pass) on the megger. The writer knows of a reflex set which was a constant source of worry to the owner until the leaky composition holder was replaced. It will be found, however, that whatever precautions are taken, the valve will always rectify to a certain extent when the circuit is not acting dually—a state of affairs brought about when the anode tuning is unsatisfactory.

#### A PECULIAR EFFECT

The reaction effects with a dual circuit differ in some respects from those obtained with an ordinary one-valve circuit, notably in the fact that when listening to a near-by station reaction has practically no effect upon signal strength, whether this is due to high-frequency saturation or not the writer is at present unable to say.

The results obtained with the set are excellent, and at times approach the performance of a three-valve set, the writer wishes to emphasise the words "at times" because, in his opinion, therein lies the difference in results obtained with this set and the more powerful, straightforward circuits. Most of the British broadcasting stations, including Aberdeen and Bournemouth, and the School

of Posts and Telegraphs (Paris) have been heard with the set, but, unlike working with, say, a three-valve tuned anode reaction set, it is impossible to tune-in any given station at will, for example, the announcer's voice at Aberdeen may be quite clear on one evening and impossible to hear at all on the next. Within about ten miles, depending upon the district, of a broadcasting station, the set will operate a small loud-speaker, although to obtain really satisfactory volume the addition of an L.F. panel is essential.

#### FREAK RESULTS

Freak receptions have been obtained; thus, on one occasion, Glasgow was clearly audible on the loud-speaker (at Manchester). Used on the outskirts of Manchester, it has been possible to listen to other stations while that station has been transmitting, but here again the results vary. On occasions the loose coupling can be opened sufficiently to eliminate the Manchester station entirely; on other occasions a slight metallic distortion is noticeable (this distortion disappears when Manchester shuts down), while again, at times, the near-by station can only be eliminated sufficiently to make the distant station readable. On such occasions loosening the coupling still further entirely eliminates the distant sta-



# SIEMENS TELEPHONE HEAD SETS.

- § Unrivalled for sensitiveness and quality.
- § Headband attached to receivers by ball and socket joint, ensuring comfort to the user.
- § Terminals totally enclosed.
- § Earpieces provided with a groove to minimise condensation of moisture.

**PRICES:**

120 ohms ..	£1 2 6		2000 ohms ..	£1 4 0		4000 ohms ..	£1 5 0
-------------	--------	--	--------------	--------	--	--------------	--------

*Also manufacturers of*

LOUD SPEAKERS,	LIGHTNING PROTECTORS,	SWITCHES,	JACKS AND PLUGS,
CORD TABS,	WIRELESS RECEIVING SETS,	BATTERIES,	EBONITE, etc.

**Obtainable from all dealers.**

tion. Lastly, there are evenings during which the writer is unable, while Manchester is transmitting, to obtain any other station.

In conclusion, the writer thinks there is little doubt that the ST74 circuit with three-coil holder is the cheapest and most convenient set for the beginner to practice tuning experiments with the minimum of annoyance to his neighbours.

—Yours faithfully,

W. J. S. NAUNTON,  
M.A. (Camb.), M.Sc. (Lond.)  
Manchester.

set employing a universal loose-coupled aerial tuner may be of interest.

Owing to my being out all day, and the fact that my people at home desired to have facilities for listening either to 5XX or 2LO as they might wish, without having to change coils, or undertake any tuning operations, I first tried connecting two receiving sets in parallel across aerial and earth. This was satisfactory up to a point, but not sufficiently stable to leave for an inexperienced operator to manage.


To proceed—insert a coil of 150 or 200 turns in the primary aerial socket L<sub>1</sub>, and one of, say, 75 or 100 turns in the reaction socket L<sub>3</sub>, place stand-by-tune switch in "stand-by" position and tune in 5XX. When this is satisfactorily accomplished place a coil of 35 or 50 turns in the secondary aerial socket L<sub>2</sub>, tightly couple the primary and secondary coils, place stand-by-tune switch in the "tune" position, and tune in 2LO, using reaction if necessary.

If any mutual interference is encountered, ascertain whether or not the secondary aerial circuit is earthed. If it is, break this connection, as it is important that this secondary circuit should be isolated. If the interference is still experienced, loosen the coupling between the primary and secondary aerial coils and retune. It will be noticed that the tuning of the closed circuit is very sharp.

When these tuning operations have been accomplished 5XX will be received on "stand-by," and 2LO on "tune." The principle underlying this arrangement is that of the now well-known acceptor wave-trap, which absorbs the usually unwanted frequencies, but in this case the desired ones.—Yours faithfully,

S. E. LLOYD.

Goodmayes.

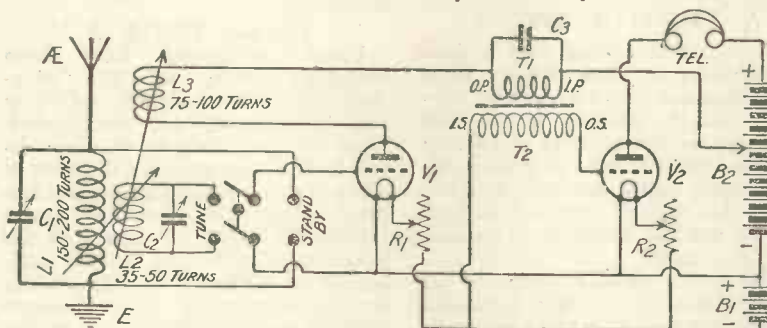


A circuit diagram showing the tuning arrangements for listening to either 5XX or 2LO, as used by Mr. Lloyd.
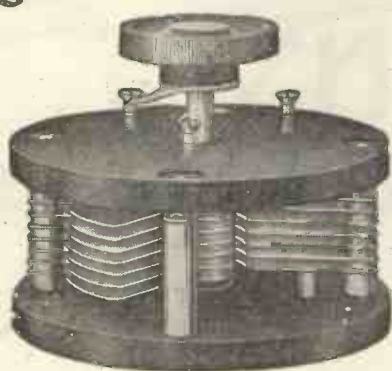
## RECEIVING 5XX

SIR,—The following report of some experiments with a two-valve (Rectifier and 1 L.F.) experimental

The following arrangement, however, will be found quite satisfactory, and is now in daily use at my receiving station.



We also manufacture:—  
Vernier Condensers, Dual Condensers,  
Dust-Proof Condensers for use on table.  
Built up on the same lines as the above  
Standard Condensers.



## Silvertown Variable Condensers.

These condensers are strongly constructed and the greatest care is taken in the adjustment of the various parts.

Capacities 0.0001, 0.0002, 0.0005, and 0.001 mfd. Moving vanes are shaped to give low minimum capacity. Fitted with a stop to allow of a movement of 180 degrees only. Any of the stock sizes can be supplied with dial and knob, instead of knob and pointer, at extra cost.

Prices 7/6, 8/6, 11/6, & 15/- each.

MAKERS: The Silvertown Company, 106, Cannon Street, London, E.C.4. WORKS: Silvertown, E.16.

# Silvertown

## WIRELESS ACCESSORIES

Quality guaranteed by over 50 years' electrical manufacturing experience.





Conducted by A. D. COWPER, M.Sc., Staff Editor.

### An Automatic Crystal Detector

The "Utility" Crystal Detector, submitted by Messrs. Wilkins and Wright, Ltd., is an ingenious device in which the searching for sensitive spots is made mechanically, instead of requiring the customary process of hand-setting.

The mechanism is enclosed in a metal case  $2\frac{1}{2}$  in. long by  $1\frac{1}{2}$  in. diameter, adapted for mounting behind a panel in the usual one-hole-fixing style. The lid of this case, which is fixed, carries the small terminal screws; a spindle and knob outside the panel actuates the device. The crystal, of the galena type, is mounted

in a small spring cup on a vertical axis inside the case.

Rotating the controlling knob performs three operations: turns the crystal-cup slowly; advances the latter by a cam action to and from the exploring cat's whisker; and moves the cat's whisker by an irregular eccentric action over the face of the crystal. The combination of these motions effectively explores the whole exposed face of the crystal in time, provided that the parts are properly adjusted at the start.

It was found necessary to make small adjustments in the sample submitted before the action was satisfactory—a matter

of no great difficulty. The particular portion of crystal found therein was also of indifferent quality; it was replaced by a reliable piece, and then very satisfactory results were obtained. On an average, one good setting was found for every complete revolution of the knob, with the apparatus closed up. The rectifying efficiency of such good settings was found, by measurements, to be on a par with the optimum results obtained by careful hand-setting with the usual open type of detector.

Provided that the crystal is inserted (not a very easy matter) and the instrument adjusted by

## RADIO INQUIRIES

### How We Can Help You

You may be in difficulties and want information on some technical point, or you may be wondering how to improve your set, but—

Whatever it is you want to know, just write us fully, stating your requirements and the exact circumstances of the case, and you will receive in return the advice of an expert, giving the information you desire.

For each answer please enclose P.O. for 2/6 to cover expense, and if you require complicated diagrams or calculations, send 4/6.


We endeavour to answer all queries same day as received, but as each one is given individual attention this is not always possible.

### RADIO INQUIRIES,

51, Imperial Buildings, Oxford Road,  
MANCHESTER.

*Please write distinctly.*

### BRITISH OUR TYPE A II CONDENSER.

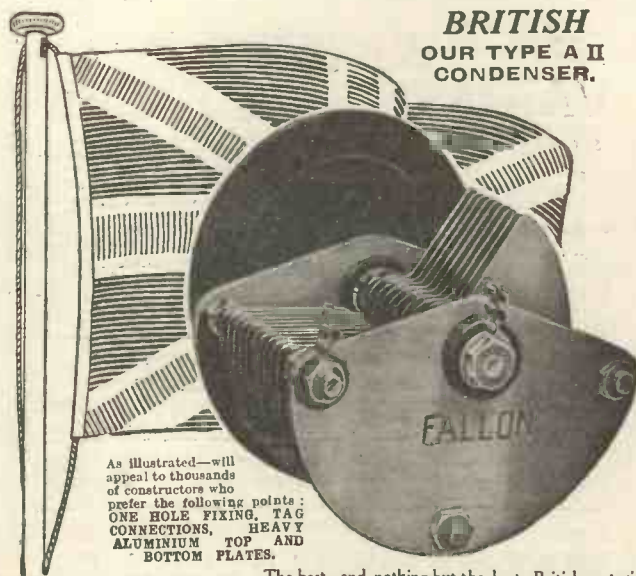

As illustrated—will appeal to thousands of constructors who prefer the following points: ONE HOLE FIXING, TAG CONNECTIONS, HEAVY ALUMINIUM TOP AND BOTTOM PLATES.

Write direct for Trade Terms:

**FALLON**  
CONDENSER Co., Ltd.

The Condenser People.  
Phone: Tottenham 1932.

WHITE RIBBON WORKS,  
BROAD LANE, N.15.

(All correspondence to ABOVE address).

NEW CITY DEPOT:  
143, Farringdon Rd., E.C.1.  
MANCHESTER DEPOT:  
19, Bridge St., Deansgate.  
SCOTTISH DEPOT:  
120, Wellington St., Glasgow.

The best, and nothing but the best, British material and workmanship are put into this FALLON CONDENSER. Metal-to-metal adjustable bearings. Stout, well-cut aluminium vanes. Complete in every respect and exactly as illustrated.

	Plates	Price
.001	57	8/-
.0005	29	6/-
.0003	19	5/6
.00025	15	5/-
.0002	13	4/6
Vernier	5	4/-
Vernier	3	3/6

For those who prefer it we still supply our ORIGINAL A II Model, which is exactly the same as above, except that instead of having aluminium ends it has composition ends, and is supplied with our special feature, the Aluminium Screening Disc, which Disc is also supplied with the model illustrated.

competent hands, this device can be termed "fool-proof" in operation, good settings being obtained by quite blind and casual rotation of the exposed knob; and as such will offer obvious advantages in broadcast crystal receivers for family use.

## Radio Construction Tools

Messrs. Thos. R. Ellin (Foot-print Works), Ltd., have submitted for inspection and trial a set of small tools of a type suitable for home-constructional work.

An extension hacksaw frame, taking blades from 8 in. to 12 in. in length, and of sturdy construction, has pegs to carry the blade in two alternative positions at right angles, without removing the adjusting screw—a convenience at times when working into a difficult corner of a panel. On trial it was found rigid in use and handy to adjust.

An 8-ounce soldering iron, with bit adjustable to any angle, proved extremely convenient in use to get at awkward connections behind a boxed-up panel; it is of a useful weight for small

radio work, and the special type of hollow perforated handle was found to keep comfortably cool.

A 4-ounce pin hammer appeared just the right size for small cabinet work; it has a polished ball at the other end of the head, which is useful for small rivetting.

Seven-inch japanned tinsnips were convenient for cutting off wire-ends and trimming condenser plates, etc. The 7-in. all-bright snips, with spring handle and leather loops for holding closed when put away in the tool-chest, appealed particularly to the writer, as an exceedingly handy tool in general radio work.

The 5-in. round-nose electricians' pliers were convenient for making terminal loops, etc., had sharp-cutting edges, and also a small pipe-grip type of rounded toothed jaws, which proved excellent for holding and turning obstinate bolts and nuts of small size.

A tiny, narrow-jawed, adjustable spanner, opening, however, to about  $\frac{3}{4}$  in. maximum, proved invaluable for handling those No. 2 B.A. nuts on condenser spindles

and the like which defy ordinary spanners.

The quality of these tools was obviously of the highest order, as might be expected from a maker whose trade-mark is familiar to all engineers. The tools included in this selection can be recommended as likely to give every satisfaction to the amateur constructor.

## Valve-Windows

A neat and at the same time an economical finish can be given to an American type of multi-valve cabinet receiver by the valve-window or peep-hole fitting recently marketed by Messrs. Grafton Electric Co.

Samples submitted showed a nickel-plated ring  $1\frac{1}{4}$  in. outside diameter, with a back-ring of similar size for the rear of the panel, and provided with three small screws and nuts for fixing. A small circle of fine wire-gauze is placed in position behind the front ring.

Actual trial showed that these windows were easy to fit, and gave a very pleasing and finished appearance to the receiver at a minimum of trouble.

## WATMEL VARIABLE GRID LEAK

5 to 5 Megohms,  
2/6.  
50,000 to 100,000  
Ohms, 3/6.  
Other Resistances  
to suit any circuit.

ARE THE BEST  
FOR THE  
FOLLOWING  
REASONS:

Continuously  
Variable.



Patent  
206098

Silent in operation.  
Constant in any  
temperature. Dust  
and damp proof.  
Each tested and  
guaranteed. Neat  
and well made.  
Send P.C. for des-  
criptive folder.

SEE THE TRADE MARK  
ON EVERY GRID LEAK.



BEWARE OF  
IMITATIONS.

Coil Former for Winding Inductance Coils

For full details see "Apparatus Tested," June 1924,  
"Wireless Weekly."

4/6

NOTE NEW ADDRESS:

**WATMEL WIRELESS Co.**

332a, Goswell Road, London, E.C.1.

'Phone: CLERKENWELL 7990.



Established  
26 Years.

**REPAIRS** TO HEADPHONES  
TO LOUD SPEAKERS  
TO COILS

REWOUND to any RESISTANCE & MADE EQUAL to NEW.  
PRICE QUOTED ON RECEIPT OF INSTRUMENTS.

PROMPT DELIVERY.

**The VARLEY MAGNET COMPANY**

'Phone: Woolwich 888.

WOOLWICH, S.E.18.

Your New Coils for  
**THE NEW HIGH POWER B.B.C. STATION**  
must be **Robust** and **Efficient**—let them be

## "Tangent" Tuning Coils

They possess these qualities:—

On strong cylindrical frames with coils air-spaced,  
you can handle with impunity, and there is nothing  
more efficient for either crystal or valve sets.

Note  
Reduced  
Prices



With Aerial Circuit '001 Condenser in parallel use COIL No. 100	With Secondary Circuit '0005 Condenser in parallel use COIL No. 200	With Anode Circuit '0003 Condenser in parallel use COIL No. 200	With Reaction on Aerial use COIL No. 100
PRICE 6/-	PRICE 7/-	PRICE 7/-	PRICE 5/-

Also for H.F. Amplification use The "Discol" H.F. Transformer,  
for New High Power Station use No. 250—Price 5/6 each.

**GENT & CO., LTD.**  
"Faraday Works,"  
**LEICESTER.**



# Information Department



SUPPLIED BY RADIO PRESS SERVICE DEPT., LTD.

**J. McL. (LEITH)** asks: Is the efficiency of a set appreciably increased by using separately insulated stranded wires for tuning coils?

Since high-frequency currents travel entirely upon the surface of a conductor, and not through its substance, theoretically all conductors should have their surface area increased as much as possible by constructing them of a large number of fine separately-insulated strands. The resulting reduction in high-frequency resistance should undoubtedly prove of considerable benefit in all wireless circuits carrying high-frequency oscillation. A practical difficulty occurs, however, in the use of conductors consisting of a large number of very fine wires (such as "Litzendraht"), and special care must be taken to make proper connection to every strand, as considerable losses occur if even one strand remains unconnected,

and therefore it is doubtful whether the amateur constructor should attempt to use it. It is further argued that the dielectric losses in the insulating material between the strands may become serious on the shorter waves.

**H. J. C. (BARROW-IN-FURNESS)** asks whether there is any objection to making the extension handles of variable condensers of metal?

This does not seem to be a very desirable practice, since one of the objects of a long handle to the knob of the condenser is to reduce capacity troubles from the hand of the operator, and if the handle is made of metal it may simply form an extension of the condenser itself. To obtain the greatest benefit from an extension handle it should undoubtedly be made of some insulating material, and it should be as rigid as possible.

## A SUBSTANTIAL PRICE REDUCTION IGRANIC H. TYPE VARIOMETER. 150-600 metres

As from 1st August you may purchase the


### IGRANIC H-type VARIOMETER

for two-thirds of its previous price.

Reduced from 15/- to

# 10/-

All Dealers stock them.

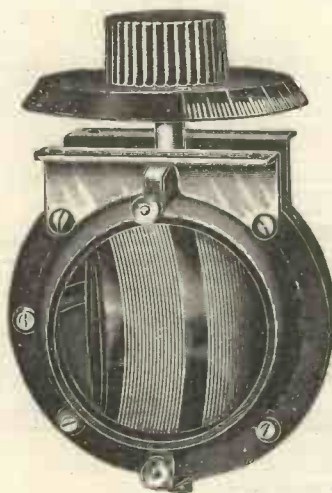

AN IGRANIC VARIOMETER PROVIDES THE SIMPLEST METHOD OF TUNING.

Stator and rotor are of moulded ebonite, possessing high insulating qualities and great strength. The stator is wound internally and the rotor externally with high conductivity copper wire, ensuring maximum efficiency and a large inductance ratio. This variometer is supplied complete with knob, dial and fixing brackets which may be affixed in four separate positions enabling the variometer to be mounted with ease in any desired position.

WRITE FOR LIST Y32.

149 Queen Victoria St.  
LONDON.

Works:  
Elstow Rd., BEDFORD.



Manchester—30, Cross Street.  
Birmingham—73/4, Exchange Buildings.  
Glasgow—50, Wellington Street.  
Cardiff—Western Mail Chambers.  
Bradford—18, Woodview Terrace,  
Manningham.  
Newcastle—90, Pilgrim Street.

**T. S. W. (KIDDERMINSTER)** states that he wishes to make a piece of ebonite tube of a size which he cannot obtain from any dealer, and asks for our advice as to its production from a thin sheet.

The first essential is some kind of former upon which to mould the ebonite, and a jam jar will be very suitable, in view of the fact that the tube has only to be 4 in. in length. Try and find one of the right diameter, and then obtain a piece of ebonite sheet  $\frac{1}{8}$ -in. thick, and measuring 4 in. in one direction and such a size in the other that it will pass round the former and give a small overlap. The sheet should then be softened by immersing for some little time in boiling water, and then taken out and quickly bent round the former and tied in position with tape quite tightly. Upon cooling it will be found that it retains the shape which has been impressed upon it, and the overlapping edge can be bevelled off by means of a file.

**U. S. M. (TINTAGEL)** inquires whether it is advantageous to use copper foil instead of the more usually recommended tin foil for fixed condensers.

Electrically there is little to be said upon the matter, but practically the copper foil is much to be preferred, since it is so very much easier to handle and also soldering is made very much easier. Tin foil, it will be remembered, is very apt to burn when one attempts to solder it.

**F. H. (SOUTHEND)** asks whether there is any practical limit to the size of a loud-speaker horn?

It would seem that within quite wide limits the larger the loud-speaker horn the better the reproduction that is obtained, provided that the signals are of sufficient strength and the reproducing mechanism attached to the horn is of adequate size. For use out of doors loud-speaker horns have been constructed in America with lengths up to 18 feet, and it is reported that they have given remarkably good reproduction. So large a horn, of course, involves quite an elaborate wooden structure.

**A. B. L. (LIVERPOOL)** experiences a good deal of difficulty in obtaining a critical setting of his reaction coupling, and asks whether we can suggest any modifications in his circuit to improve matters?

The trouble which our correspondent appears to be experiencing is that known as overlap, which should be removed rather by modifications of the conditions under which the valve is working than by actual alterations to the circuit. Vary the plate voltage and filament current over quite wide limits, try a different value of grid leak, and if necessary try a different valve as a rectifier. When you have secured correct values for all these factors, it should be quite possible to set the reaction to the threshold of oscillation without any tendency to flop over into actual self-oscillation.



**RECORD YOUR  
RADIO SIGNALS**

WITH A

**WESTON MOVING COIL  
RELAY**

as fully described by Mr. Percy W. Harris in last week's "Wireless Weekly." A limited number of perfectly new and unused No. 30 Weston moving coil Relays, available at 17/6 each while stock lasts. Remember each instrument is brand new ex Government stores and originally cost about £9. Will operate on a current of 50 micro amperes.

**PRICE  
17/6**


ECONOMIC LTD.  
ELECTRIC

Head Office: 10, FITZROY  
SQUARE, LONDON, W.1.

Showrooms:  
303, EUSTON RD. N.W.1

**CAM-OPERATED VERNIER  
COIL HOLDER.**

*Quality*  
RADIO

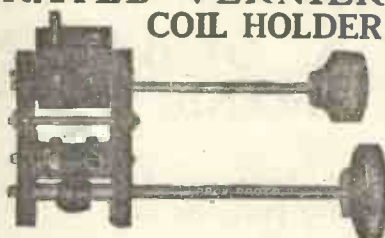


The usual fixed socket has a very slow movement giving a metric adjustment in both directions through 10°. This is effected by a cam operated by a separate knob.

Price, 2-way (only) 9/-, on base 1/- extra. Post 3d.

With Reaction Reverse and Short-Circuiting Switch, 12/6. If your dealer has not got them we will send post free if you mention his name and address.

**GOSWELL ENGINEERING CO., LTD.**  
12a, Pentonville Road, London, N.1.  
Liberal Trade Terms. Phone: North 3051.

# VALVES repaired Quick



Send your "burnt-out" valves to a proper valve manufacturer's for repair. You will get them back same as new—and perfectly "hard" i.e., with thorough vacuum.

We guarantee our repaired valves:

- (1) Not to consume more current;
- (2) To have same amplification;
- (3) To have same radiation.


If cap is broken new nickel-plated cap supplied FREE.

If glass is broken—new glass supplied free but in no case can new grids or plates be supplied.

Our files are packed with testimonials from users who regularly receive American Broadcasting on our repaired valves.

We cannot be equalled for good work, low price and QUICKNESS.

**RADIONS, LTD., Bollington, nr. Macclesfield.**



**GOOD  
TRADE  
TERMS**

We make the new Radion Low Consumption Valve, price 10s. Uses only a third of usual current.



# LISSENIUM

## How to tell good parts—

**W**HEN signals roar in from stations only one hundred miles away, it is more difficult to tell the difference between good parts and bad parts. But when stations are being tuned in many hundreds, perhaps thousands, of miles away, then you can tell your good parts ARE good parts. Then, too, it is that every fraction of applied energy takes effect—IF THE PARTS ARE RIGHT.


**T**HOSE who use **LISSEN PARTS** sooner or later all realize how continually improving results seem to keep pace with one's better understanding. Though initially quite easy to use, **LISSEN** Parts have been designed and made so that for even the most skilful experimenter there is wide enough scope in a receiver built with **ALL LISSEN** Parts to make the receiver for ever a fascinating thing.

**PARTS WITH HIDDEN POWER—LISSEN PARTS**
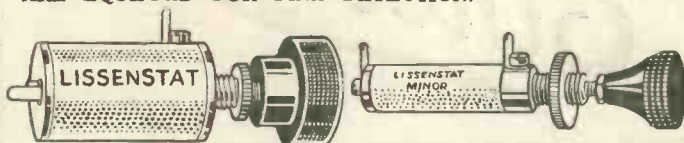
## The Key to fine detection—

**T**HE key to a large safe often strikes one as appearing wholly inadequate for the massive door—yet how easily it turns in the lock.

**LISSENSTAT** control, so guileless in its outward appearance, opens the way to fine detection just as easily. Critical electronic flow follows every fractional turn of its noiseless control. Silently it works—and well. Stations that have before been difficult to get, stations that have been impossible to get—now they come in distinctly and with great certainty. It is now known that receivers which are fitted with **LISSENSTAT** or **LISSENSTAT MINOR** ARE EQUIPPED FOR FINE DETECTION.



**LISSENSTAT** Gives the most acute tuning possible **7/6**

You can get more out of your valves by using unique filament control.

**LISSENSTAT MINOR**

Is replacing many thousands of discarded and inefficient rheostats. Provides such a high degree of **LISSENSTAT** control at a popular price **3/6**

## Have you got an unreliable Grid Leak?

**I**F so, it is impossible for you to properly regulate the charge that should accumulate on the grid. You should preferably fit the **LISSEN** Variable Grid Leak—you know then that you have a control which will give correct grid potential for every valve or circuit you choose to employ. **LISSEN ONE HOLE FIXING, OF COURSE, POSITIVE STOPS BOTH WAYS. 2/6**




**A STABILIZING RESISTANCE. LISSEN** Variable Anode Resistance, 20,000 to 250,000 ohms. Same outward appearance as the **LISSEN** Variable Grid Leak ... **2/6**

**LISSEN LIMITED** 30-32, Woodger Rd., Goldhawk Rd., Shepherd's Bush, London. W.12.  
Parts with hidden power—**LISSEN** Parts
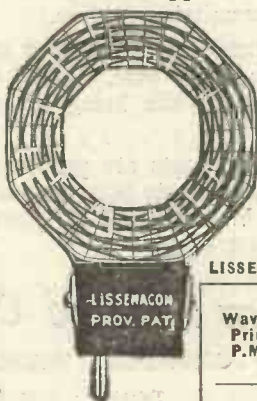
## The function of an inductance—

**T**HE two chief functions of an inductance in radio frequency circuits are, firstly, to give the largest possible E.M.F. across its terminals for any frequency within its range, and, secondly, to transfer this energy by means of its magnetic field to another inductance in another circuit.

**A** COIL that has a strong magnetic field may not necessarily be the coil which builds the highest E.M.F. across its terminals. Particularly is it difficult to combine these two desirable objects in compact coils. A great fault with many coils is that electrical efficiency is sacrificed to considerations of size, outward appearance, and attractiveness to the eye.



**T**HE shape of the coil, the absence of a solid former, the gauge of the wire, the well designed air spacing, these are some things which make **LISSENAGON** coils so efficient electrically, and the shape of the coils also, which brings the inductance down to a compact size, while the whole voltage across each coil is distributed evenly, so that when current is passing through it, the resultant magnetic field is an extremely strong one, while the E.M.F. also is very high.

**HOLD A LISSENAGON COIL UP TO THE LIGHT**

**LISSENAGON TUNING CHART. Note the Intermediate Coils, 30, 40, and 60**

TABLE I. Wavelength range when used as Primary Coils with Standard P.M.G. Aerial and .001 mfd. condenser in parallel.			TABLE II. Wavelength range when used as Secondary Coils with .001 mfd. condenser in parallel.		
No. of Coil.	Minimum Wave- length.	Maximum Wave- length.	Minimum Wave- length.	Maximum Wave- length.	PRICE.
25	185	350	100	325	4/10
30	235	440	130	425	4/10
35	285	530	160	490	4/10
40	360	675	200	635	4/10
50	480	850	250	800	5/-
60	500	950	295	900	5/4
75	600	1,300	360	1,100	5/4
100	820	1,700	500	1,550	6/0
150	965	2,300	700	2,150	7/7
200	1,885	3,200	925	3,000	8/5
250	2,300	3,800	1,100	3,600	8/9
300	2,500	4,600	1,400	4,300	9/2

## Tone so Pure—

every instrument of an orchestra can be identified.

Judge an audio frequency transformer—

FIRSTLY, in terms of tone purity.

SECONDLY, in terms of volume.

With **LISSEN** Transformers TONE

QUALITY HAS ALWAYS COME

FIRST.

**LISSEN** Transformers are so designed that they build up a whisper of sound to a great degree of loudness with absolute purity of tone—each of the three types is tested for purity first right through the whole range of audible frequencies—then tested for volume.

**SUPERLATIVE AMPLIFICATION.** If you contemplate buying an expensive transformer, be sure there is none to equal the **LISSEN** T1—use it always behind the detector valve and throughout when superlative amplification is desired. ALWAYS FOR **30/-**

**FOR REFLEX CIRCUITS.** Under all conditions, the **LISSEN** T2 Transformer is one which will give pure and powerful amplification in these circuits ... **25/-**

**A POPULAR TRANSFORMER.** Money cannot buy better transformer value than the **LISSEN** T3. Because of its skilfully balanced design, this transformer actually compares with many other transformers sold at nearly twice the price **16/6**

**FIT EITHER TYPE OF LISSEN TRANSFORMER—and make sure**

## Don't Use Mixed Parts—

Use **LISSEN** Transformers for purity and volume.

Use **LISSENAGON COILS** for sharp tuning, for strong tuning.

Use **LISSEN** Radio Frequency Parts for extending range.

Use **LISSENCEPTOR** for eliminating interference.


Use **LISSEN** TUNER for covering a wide wavelength with one control.

Use **LISSEN** MICA Variable Condenser for fine tuning.

Use **LISSEN** VERNIER CONDENSER for fine tuning, especially in H.F. circuits.

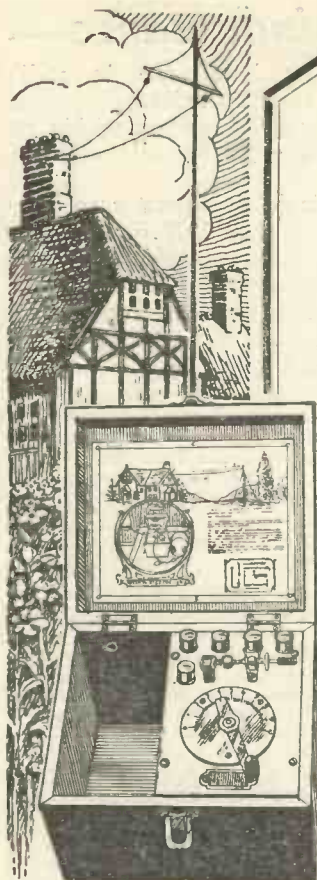USE A **LISSEN** PART WHEREVER YOU CAN—and your receiver will give results you could never get with mixed parts





## Western Electric CRYSTAL SET

A really efficient crystal set which, with a good aerial and earth, will give satisfactory reception up to a distance of thirty miles from a transmitting station.

The set is tuned by means of a specially designed variometer, and is ideal for those who, having no electrical knowledge, require a set which, while being simple to operate, will yield good results.

All component parts are permanently connected and mounted in a polished mahogany box, and each set is supplied complete with one pair of Western Electric 4,000 ohms Headphones, and leather head-pad.

**Western Electric Company Limited,**

CONNAUGHT HOUSE, ALDWYCH, W.C.2.

Telephone: CENTRAL, 7345 (9 lines).

Branches: BIRMINGHAM, LEEDS, GLASGOW, NEWCASTLE, CARDIFF, MANCHESTER, SOUTHAMPTON, LIVERPOOL, and DUBLIN.



Notice the gracefully shaped neck and flair of the Ethovox.

Ethovox Loud Speaker either 120 ohms (No. 203), or 2000 ohms (No. 204).

£5

*Renowned for sound and perfect tone*

**Ethovox**  
REGD

**M**AKE the best of a good set by using a good loud speaker. The Ethovox Loud Speaker gives perfect reproduction of all musical and vocal notes. If reception is good, the Ethovox will reproduce every sound with all its original delicacy and volume. This perfect Loud Speaker is famous for its clarity and true tone and it is very popular. The instrument is gracefully shaped and is coloured a warm mahogany shade. It blends harmoniously with its surroundings, both optically and aurally! The nearest Burndeft Agent will let you hear the Ethovox in operation—what you hear will convince you that it is indeed a perfected Loud Speaker.

**BURNDEFT**  
**WIRELESS APPARATUS**

Burndeft, Ltd., Aldine House, Bedford Street, Strand, W.C.2.

Visit our Stand at the British Empire Exhibition, in the Palace of Engineering, Avenue 13, Bay 13.

*It will pay you always to watch WIRELESS WEEKLY Advertisements.*



You get it  
**BETTER**

on

*Stella*

## LOUDSPEAKERS & PHONES

### STELLA PHONES.

Tested and Guaranteed to give perfect reproduction without distortion. Light and comfortable to wear. Equal to phones costing much more.

4,000 OHMS Stamped B.B.C. .. Per Pair **17/6**

### WEMBLEY PHONES.

These have the same diaphragm as the Stella and give the same faultless reproduction. They are lighter and are made that only the ear-pieces, and not the headband, touch the head at the sides.

4,000 OHMS, Stamped B.B.C. .. Per Pair **14/6**


### BIG STELLA LOUD SPEAKER.

For every Loud Speaker used in the home, in public hall or out-doors, Big Stella gives clearest and most perfect results at a price which will prove to you the folly of purchasing the costly instruments now on the market.

BIG STELLA carr. paid **70/-**
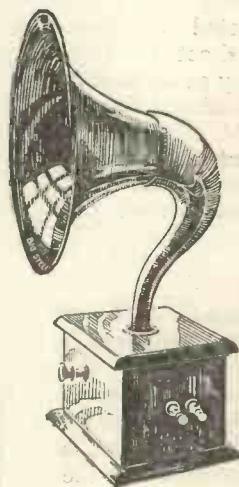
### LITTLE STELLA.

A smaller model giving equally wonderful reception carr. paid **35/-**



As Exhibited at Wembley. Avenue 11. Bays 8 & 9.

Buy at Wembley, or from any good Wireless Dealer. Substitutes are inferior—do not accept. If unobtainable write direct to

**STELLA WORKS,**  
31-37, Wybert Street, LONDON, N.W.1.


Telephone: Museum 8390.

## CHARGING PANEL for DIRECT CURRENT

The polished wood panel measures 15 by 9 in., is well insulated at back, and is fitted with 6 good quality Terminals (2 in-put and 4 out-put), best quality Volt and Ampere Meters reading 1-12 volts, 1-10 amps., 4 Lamp Holders, 2 Fuse Boxes (one on each main), and Double-pole Switch. Suitable for any D.C. supply voltage, the charging rate being determined by the lamps used (the voltage of the latter should be the same as the supply).

No. 15104. Price 50/-

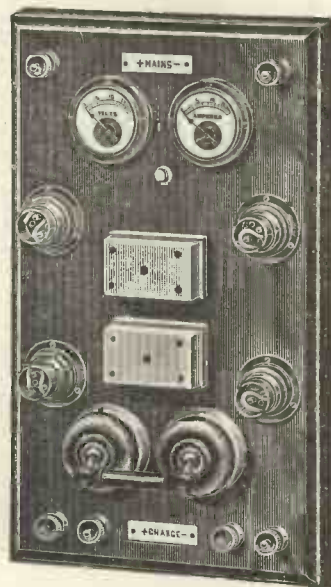Kindly order from your dealer. We cannot supply direct.



**Brown Brothers**

Allied Companies: Thomson & Brown Brothers, Ltd. Brown Brothers (Ireland) Ltd.

Wholesale Only. Head Offices and Warehouses: GREAT EASTERN ST., LONDON, E.C.2. 118, George St., Edinburgh, and Branches.

## Capacity Ratio 150 to 1


PANEL  
MOUNTING  
TYPE

But that is not all. By fitting Bowyer-Lowe Square Law Condensers to your sets you will make them easier to tune, more selective and will greatly improve the purity and volume of all your signals.

These condensers have the lowest losses of any yet made. They are supplied in all usual capacities, in standard, vernier and double types. With each one calibration charts are given so that in a moment you can find the exact setting of your set for all wavelengths.

Mr. Percy Harris says all condensers for tuning purposes should be of the Square Law type.

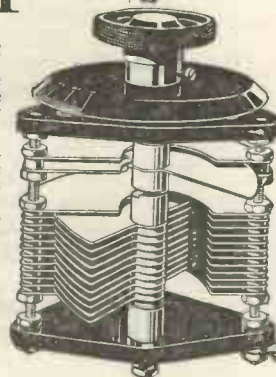Write NOW for full particulars and price list.



## BOWYER-LOWE SQUARE LAW CONDENSERS

Good dealers stock them. If you cannot obtain them locally order direct mentioning your dealer's name.


BOWYER-LOWE CO., Ltd. Letchworth.

\*0003 M.F. Standard 16/-

\*0003 M.F. with Vernier 19/-

\*0005 M.F. Standard 17/-

\*0005 M.F. with Vernier 20/-

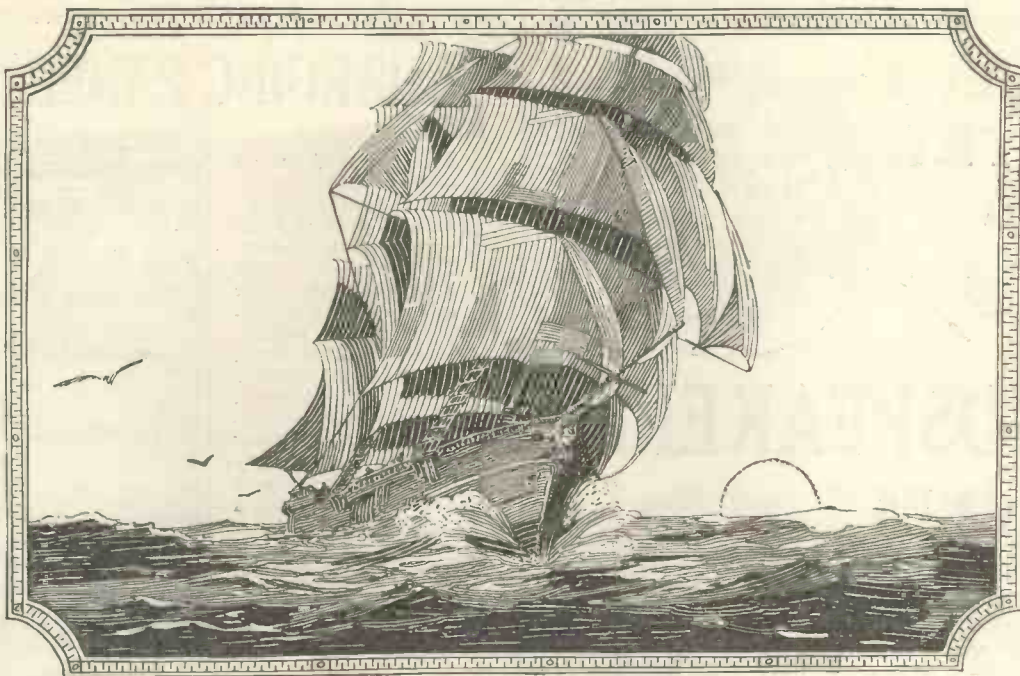

## Voyages of Discovery

TO the new user of a Cossor P.2 Valve (designed specially for long distance reception), every occasion gives an opportunity for discovering new Stations.

While previously the Receiving Set was probably limited to two or three hundred miles, now practically every Continental high-power Broadcasting Station is brought within its range.

Why this marked superiority? The reason lies in the actual design of the Cossor Valve—so different to all others.

Amplification and rectification is dependent upon the efficient

use of the electron stream given off by the heated filament. These electrons shoot off at a tremendous velocity at all angles. In a Valve with a tubular Anode, and long, straight filament, a large proportion of the stream escapes from the ends of the tube, only to be wasted against the sides of the glass.

Remember that the only electrons that are used are those which reach either the Grid or the Anode. In the Cossor this means practically all of them, because its filament, arched like a bridge, is almost totally enclosed by the hood-shaped Grid and Anode.

**Q** This Advertisement explains why the P.2 Valve has achieved such remarkable results in high frequency amplification—easily the most exacting branch of Radio.

**Prices:**

P.1. For Detector and I.F. amplification	12/6
P.2. (With red top) for H.F. amplification	12/6



# Cossor

A.C. COSSOR, Ltd., Highbury Grove, London, N.5.

## Valves


It will pay you always to watch WIRELESS WEEKLY Advertisements.



# HULLO EVERYBODY!!

## RAYMOND'S VARIABLE CONDENSERS

### NEW MODEL.

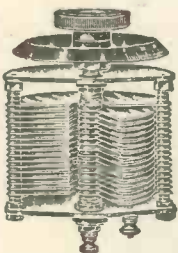

INCLUDING KNOB.

Nat. Phys. Lab. Certificate for Guaranteed Capacity.

Cap.	Height without Price. connections.	
•001 ..	6/11 ..	3 1/2 in.
•00075 ..	5/11 ..	2 3/8 in.
•0005 ..	4/11 ..	2 in.
•0003 ..	4/6 ..	1 1/2 in.
•0002 ..	4/- ..	1 1/8 in.
•0001 ..	3/6 ..	1 in.
•00005 (vernier) 2/6		

EBONITE DIAL 8d. extra.


POST 6d. SET.

ALL PARTS NICKELLED. One hole fixing. Narrowest spacing. Aluminium end plates. Accurate Capacity. Rigid Construction. Low Loss. Electrically and Mechanically Perfect. Many unsolicited Testimonials.

NEW MODEL with 3 Plate Vernier at bottom. Specification as ordinary, but the Vernier allows absolutely the finest tuning possible. Very sharp and defined. They do not need varied long and technical words to recommend them. Satisfied users are the best recommendation. Assembled for panel mounting, and for a limited period. I will include FREE an EBONITE DIAL to retail customers only.

POST 6d. PER SET PLEASE.

Height	Cap.	Price
4 in. ...	•001 ...	8/11
2 1/2 in. ...	•0005 ...	6/11
2 1/4 in. ...	•0003 ...	6/8

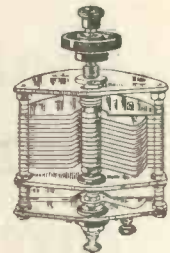

Complete with 2 Knobs and Dial.

### POST FREE COLUMNS (except where marked).

Gauze Valve Windows ..	7d.
Double 'Phone Cords, 72in.	1/11
Porcelain S.P.D.T. Switch	1/11
Ditto, D.P.D.T. Switch ..	2/6
Battery Clips .. doz.	10d.
Ebonite Valve Holders ..	1/-
Variometer 250/650 ..	2/6
Lead-in Wire .. 10 yds.	1/6
Twin Flex .. 12yds.	1/11
2 colour Flex .. 6yds.	1/3
100 ft. 7/22 Aerial Wire with four insulators ..	3/9
Nugraving Titles ..	7d.
Chatterton's Compound ..	8d.
"R.I." Choke Coil ..	10/-
Watmel Var. Grid Leak ..	2/6
Watmel Anode Resistance ..	3/6
Nickel Panel Switches, D.P.D.T. ..	1/5
Ditto, S.P.D.T. ..	1/2
W.O. Pillar, large ..	1/3
'Phone 4 B.A. ..	1/1
'Phone 2 B.A. ..	6 for
Med. Pillar 4 B.A. ..	10d.
Valve Sockets, plain ..	1d.
Ditto, with Shoulder ..	1/1
(Above with Nut and Washer.)	
Single Coil Plug on Stand ..	1/3
Ditto Swivel movement ..	1/6
Plug and Socket 6 pairs ..	10d.
Screw Spade Terminals doz.	10d.
Pin Screw Terminals doz.	10d.
Empire Tape 1 in. 12 yds.	9d.
Insulating Sleeve 6 yds.	2/-
Ebonite Coil Plugs 2 for	1/6
Best quality ditto ..	2 for 1/10
Ebonite Knobs 1 1/2 in. 2 B.A.	6d.
Moulded Knobs 1 1/2 in. 2 for 8d.	
Knobs 1 in. 4 B.A. 2 for 8d.	
Ditto 1 in. 2 B.A. 2 for 8d.	
H.F. Transformers Plug-in type 250/700 ..	3/11
Ebonite ex handles 6 in.	9d.
Ebon. Bushes 2 or 4 B.A. doz. 1/-	
D.C.C., I.R.C. Bell Wire 10 yds.	1/-
Tinned Copper, square 16 gauge, 18 ft.	1/6
Spearpoint Whisker ..	4d.
Gold Whisker ..	4d.
Set of five, one gold ..	6d.
100,000 ohm Fixed ..	1/6

### BASKET COILS.

Chelmsford (Tandco) ..	2/-
Tandco 1,300/1,750 metres 1/8 (All Tandco in Stock)	
Waxless set of 5 200/2,000 1/11	
Waxed set of 6 200/3,600 1/11	
Special Duplex Coil fitted on adaptor for Chelmsford 2 1/11 (For Variometer 650 metres) Post 4d. each.	

LISSEN—	
Variable Grid Leak 2/6	
Anode Resistance 2/6	
Lissen Minor .. 3/6	
Lissenstat. .. 7/6	
Do. Universal .. 10/6	
2-way Switch .. 2/9	
Series Parallel .. 3/9	
T1 Transformers 30/-	
T2 25/-; T3 16/6	
Lissen Coils and all parts stocked.	
IGRANIC—	
Coils: 25, 5/-; 35, 5/-; 50, 5/2; 75, 5/6; 100, 7/-; 150, 7/10; 200, 8/8; 250, 9/-; 300, 9/5; 400, 10/3; 500, 10/6	
50 ohm Rheostat .. 7/-	
Potentiometer .. 7/6	
Vernier Rheostat .. 7/6	
30 ohm Rheostat .. 7/-	

DUBILIER CONDENSERS.	
Type 600A ..	
•001, •002, •003, •004, •005, •006 Fixed 3/-	
•0001, •0002, •0003, •0004, •0005 .. 2/6	
Type 577, •01 .. 7/6	
Grid Leaks each 2/6	
Anode Resistance 50,000, 80,000 or 100,000, on stand complete .. 5/6	

GOSWELL ENGINEERING CO.—	
Patent Valve Holder .. 1/6	
Cam operated Vernier, Two-way Coil Stand, Vernier 9/-	

VALVES.	
Cosser P.I. P.2 .. 12/6	
Mullard Ora .. 12/6	
Ediswan .. 12/6	
Marconi R. and R.5 .. 12/6	
A.R.D.E. Ediswan .. 21/-	
D.E.R. .. 21/-	
D.E.3 .. 30/-	
All Valves stocked Post 6d. each.	

N. & K. HEADPHONES GENUINE STAMPED	
4,000 ohms .. 12/9	
6,000 ohms .. 13/3	
Genuine N. & K. Post 6d. pair.	

EBONITE 1/2 in. cut to Size at 1d. sq. in. Stock sizes.	
6 x 6 .. 1/6	
7 x 5 .. 1/6	
8 x 6 .. 2/-	
9 x 6 .. 2/3	
10 x 8 .. 3/4	
12 x 9 .. 4/6	
12 x 12 .. 6/-	

### ACCUMULATORS. BEST MAKES. UNDER MY OWN LABEL.

4 v. 40 .. 17/6	
4 v. 60 .. 19/6	
4 v. 80 .. 23/6	
6 v. 60 .. 28/-	
6 v. 80 .. 35/-	



Ebonite Valve Holder, cut from solid rod, hand-turned, 8 nuts and washers .. 1/3

### HEADPHONES.

Sterling, 4,000 ohms. .. 25/-	
Brown, "F" type 25/-	
Brown, "A" type 62/-	
B.T.H. .. 25/-	
Siemens .. 25/-	
Gecophone .. 25/-	
Western Electric .. 25/-	
Brunet, 4000 .. 17/6	
Single Brunet, 4,000 8/6	
8,000 Brunet (for Crystal Sets only) 19/11	
Brunet De Luxe 18/11	
Lightweight "K" 10/9	
Dr. Nesper adjustable .. 13/6	
Ericsson (E.V.) 12/6	
Post 6d. pair.	

### WEST END DEPOT FOR

Polar; Jackson Bros.; R. I.; Burndey; Goswell Eng. Co.; Grafton Electric; Silvertown; Igranic; Lissen; Radio Press Envelopes; Dubilier; Edison Bell; Woodhall Goods, etc.

### VARIOMETERS.

Ebonite 200/650 4/6	
Ebonite Ball Rotor 7/6	
Impregnated Board 3/6	

### EBONITE COIL STANDS.

2-way, ex handles 4/6	
3-way, ex handles 5/6	
2-way, good value 3/9	
3-way, good value 4/11	
Also at 4/3, 4/6, 5/11	
2-way for Basket Coils .. 5/11	
Universal .. 5/11	
3-way, 1/6 each extra	
Francis .. 12/6	
2-way .. 17/6	
3-way .. 17/6	
Cam Vernier .. 8/6 & 9/6	

### L.F. TRANSFORMERS.

Radio Instruments 25/-	
Igranic, Shrouded 21/-	
Powquip, Shrouded 18/-	
Forno, Shrouded 18/-	
General Radio .. 14/11	
Brunet, Shrouded 11/9	
Forno, Open .. 12/6	
Powquip, 2-1 or 4-1 .. 14/6	
Raymond .. 10/-	
Eureka Concert Grand .. 30/-	
Ditto, 2nd Stage 22/6	
Silvertown .. 21/-	
Woodhall .. 23/9	

### EDISON BELL FIXED CONDENSERS.

•0001 to •0005 .. 1/3	
•0002 to •006 .. 2/-	
•001 .. 1/3	
2000 Detector .. 5/9	
Raymond—Fixed .. 10d.	
•001 to •0003 .. 1/-	
•002 to •004 .. 1/3	
•006 .. 1/3	
•01, •02 .. 1/6	
•05 .. 3/6	
T.C.C. 1 mfd. .. 4/-	
T.C.C. 2 mfd. .. 4/6	
Post 3d. each.	

### CALLER'S COLUMN. NO POST ORDERS.

Wound Coils (1600) .. 1/6	Valve Holders, Ebonite 8d.
Tapped Coils (1600) .. 1/6	Basket Coil Adapters 8d.
Filament Dials .. 2/6	Ditto, extra quality 1/3
Ebonite 4 1/2 in. with knob .. 5d.	Plugs and Clips .. 6d.
Copper Foll. foot .. 2d.	Shaped Coil Plugs .. 8d.
Washers, 2 and 4 B.A. .. 1d.	Edison Bell .. 1/-
Nuts, 2 B.A., 2 doz. 3d.	Ebonite Coil Plugs .. 4d.
Nuts, 4, 5, 6 B.A. 3d.	Ditto, extra quality 6d., 7d., 8d.
Filostat (D.E. or R. Valves) .. 1/9	72 in. 'Phone Cords 1/5
Microstat (D.E. or R. Valves) .. 2/6	Panel Switches, nickel S.P.D.T. .. 10d.
Allen Var. grid leak 1/6	Ditto, D.P.D.T. .. 1/4
Ditto Anode Res. .. 1/6	Switch Arm (best) with 12 studs, nuts and washers .. 10d.
Good Fixed Condensers .. 8d.	Studs, complete, doz. 4d.
Dutch Valves, Tubular .. 4/9	Pointers .. 2 a 1d.
Dutch "R" type .. 6/6	100,000 ohm res. and clips .. 1/3
Phillips "R" .. 6/6	Unit Coil Plug .. 1/1
French Metal .. 6/6	Nugraving Titles .. 7d.
Porcelain Switches, S.P.D.T. .. 1/3	Myers Valves .. 12/6
Ditto, D.P.D.T. Switches, 1/11	Adhesive Tape, roll 3d.
Insulated Pliers, pair .. 1/-	30v. H.T. Batt. .. 4/6
Screwed Rod, 2 B.A., foot .. 2d.	60v. H.T. Batt. .. 7/6
Ditto, 4 B.A., foot .. 2d.	H.F. Transformers 250/700 .. 3/6
Boxes 8 x 6 x 5 deep .. 14/6	Single Phones, 120 ohms. 5/-
Knobs, 1 1/2 in. 2 B.A. 3d.	Ditto 4,000 .. 7/-
Best quality ditto .. 2d.	Button Brass .. 3/9
1 in. 2 B.A. .. 2d.	Button Aluminium .. 4/9
1 1/2 in. 4 B.A. .. 2d.	Stand for Phone .. 2/3
Real Ebonite Dials .. 1/1	Coil-Stands, 2-way 2/6
Set of Spanners, etc. 2/2	Ditto, ext. handles .. 3/3
Best Grid Leak and Condenser .. 1/3	Ditto, 3-way .. 4/9
Grid Leaks, 2 meg. .. 1/1	Electron Aerial, 100ft. 1/4
East-Fix Crystal cups 1d.	Copper Aerial, 100ft. 1/10
Vario. Crystal Sets 7/11	Extra Heavy, 100ft. 2/3
Ebonite Variometer 3/11	Egg Insulators .. 1d.
TERMINALS.	Rubber Lead-in, 10yds. 1/3
(With Nut and Washer.)	English 4.5 Batteries 4d.
Large W.O. or Pillar .. 1d.	Clips .. 2 a 1d.
Medium phone .. 1d.	Sieving 4d., 3 yds. 10d.
Phone 2 B.A. .. 1d.	16 g. Sq. Tinned .. 6d.
Small Pillar, 4 for 3d.	Copper, 18 ft. .. 6d.
Pin screw terms, 2 for 1d.	Twin Flex, 4 yds. 6d.
Spade Screw terms, 4 for 3d.	Burndey Detector 5/-
Spade Tags .. 5 a 1d.	Variometers, 250/650 1/6
Valve Sockets 2 for 1d.	Raymond Transformer 9/11
Valve Pins .. 3 a 1d.	Mic-Met Detector .. 6/-
Stop pins .. 4 a 1d.	Many good ones 10d. & 1/2
Plug and socket pair 1d.	Nickel or Brass, best 1/6
Spade Tags 4 for 1d.	(All above glass enclosed.)
Brass Plug and Socket, pair 1d.	Hertzite .. 8d.
Wander Plugs, pair 2d.	Stingalite .. 1/- & 9d.
	Gecosite 1/3 Neutron 1/6
	Whiskers, silver or gold 2d.
	Spearpoint .. 2d.
	Universal Rheostats 1/3
	Ormond Rheostat .. 1/9

Right Opposite  
**DALY'S**  
Gallery Door

**K. RAYMOND**  
27, LISLE STREET, W.C.2


'Phone: Gerrard 4637.


No responsibility accepted on post orders unless cheques and postal orders are crossed and made payable to K. Raymond. Moneys sent must be registered.

HOURS OF  
BUSINESS:

Daily 9 to 7.45  
Sundays 10 a.m. to 1 p.m.

It will pay you always to watch WIRELESS WEEKLY Advertisements.

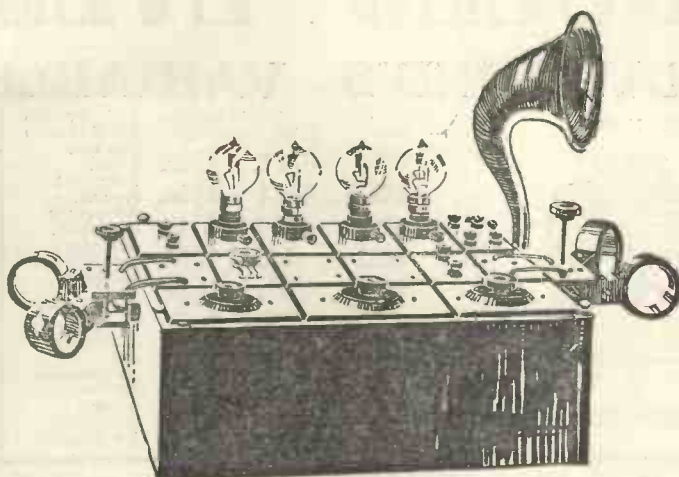Get the book  
that tells you  
how to build  
this set   
by:—



# POLAR-BLOK

## ELASTIC SET CONSTRUCTION

For 2/-, the POLAR-BLOK Book gives you double the interest and treble the efficiency in your wireless endeavours, besides saving you untold expense in blind experiment.

With this book you are fully able to build your own wireless installation to any desired circuit QUICKLY, SIMPLY, and in a WORKMANLIKE WAY.

You need no special engineering knowledge nor skill, and no tools beyond a pair of pliers and a screwdriver. You can start in a modest way—say by building a POLAR-BLOK CRYSTAL SET—and keep adding and experimenting according to the Polar-Blok Book until you have a MULTI-VALVE SET that will give you everything in wireless, like the one illustrated above.

*At each stage of your work your set is always a Complete and Finished piece of apparatus, neat and rigid, until you wish to add the next valve and extend.*

You cannot fail to build a set which will give you better results than a ready-made receiver costing much more.

Send P.O. for 2/- to-day for the POLAR-BLOK BOOK and begin NOW to build your winter entertainment.



34-35, Norfolk Street, Strand, London, W.C.

POLAR STOCKISTS THROUGHOUT THE COUNTRY.

Get the Polar Wireless Catalogue — 6d. POST FREE.

### WIRELESS OPERATORS WANTED

There are now Vacancies on our Seagoing Staff for Junior Wireless Operators trained on our apparatus. Youths of good education, preferably between 17 and 25 years of age, wishing to enter the Wireless Profession should communicate with the Managing Director, London Radio College, 82-83, High Street, Brentford, Middlesex, who will be pleased to furnish particulars of the training course necessary to qualify for our service.




**CHELMSFORD B.B.C. STATION**

To obtain the best results from the new B.B.C. Station at Chelmsford you must use the world-famous "Permanite" Crystal (Regd. No. 438341), now supplied in two sizes:—  
The 1/6 size, which is easily broken into two or three pieces for keeping in reserve, and the Handy size that fits the Crystal Cup. Both complete with Cat's Whiskers. Per Box

**1/6**


# PAY an EARLY VISIT to GAMAGES

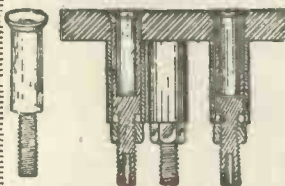**VALVE HOLDERS**

The latest type for Flush Mounting. Reduced height makes for compactness, reduced capacity and reduced solid dielectric efficiency. Soldering Hole for reliable and neat connection. Flush for protection of valve. Easy to mount and cheaper than valve holders. Brass finish, Post 14d.

**1/-**  
per set of 4**COIL SOCKETS**

for holding.  
Burndept or  
Honeycomb  
Coils.

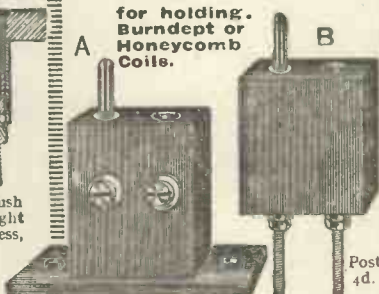


Post 4d.

Nicely made and finished in best ebonite. As illustration for Panel Mounting. Very useful for Home-made Coils. Order yours right away, the value will amaze you. Post orders are guaranteed satisfaction or money refunded in full. A Type as B Type as sketch, Price **1/6** sketch, Each **1/-**
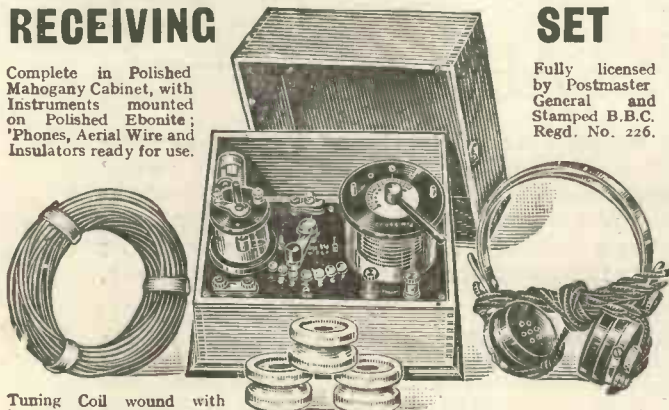
# GAMAGE CRYSTAL BROADCAST RECEIVING SET

Complete in Polished Mahogany Cabinet, with Instruments mounted on Polished Ebonite; Phones, Aerial Wire and Insulators ready for use.



Fully licensed  
by Postmaster  
General and  
Stamped B.B.C.  
Regd. No. 226.


Tuning Coil wound with best quality wire and tapped in seven places. The Crystal Detector, designed to prevent dust from deteriorating the sensitivity of the crystal, contains our famous "Permanite" Crystal, which has given such excellent results. A Fixed Condenser is incorporated, while terminals are fitted for extra induction. High-grade, sensitive Headphones are supplied. The task of finding a sensitive spot on the crystal is minimised by means of a buzzer. Will receive telephony for 25 miles and signals from Spark Stations using a wave-length of 300-500 metres for 150 to 200 miles.

**£3: 16: 6****WIRELESS ON EASY TERMS!**

GAMAGES have now extended their easy payment system to Wireless, and you may now secure on payment of first deposit, Approved Wireless Apparatus from £5 upwards, balance being payable in 6 or 12 monthly instalments. Write for details to Wireless Dept.

**A.W.GAMAGE Ltd., HOLBORN, LONDON, E.C.1**  
**BENEFINKS, CHEAPSIDE, LONDON, E.C.2.**

It will pay you always to watch WIRELESS WEEKLY Advertisements.

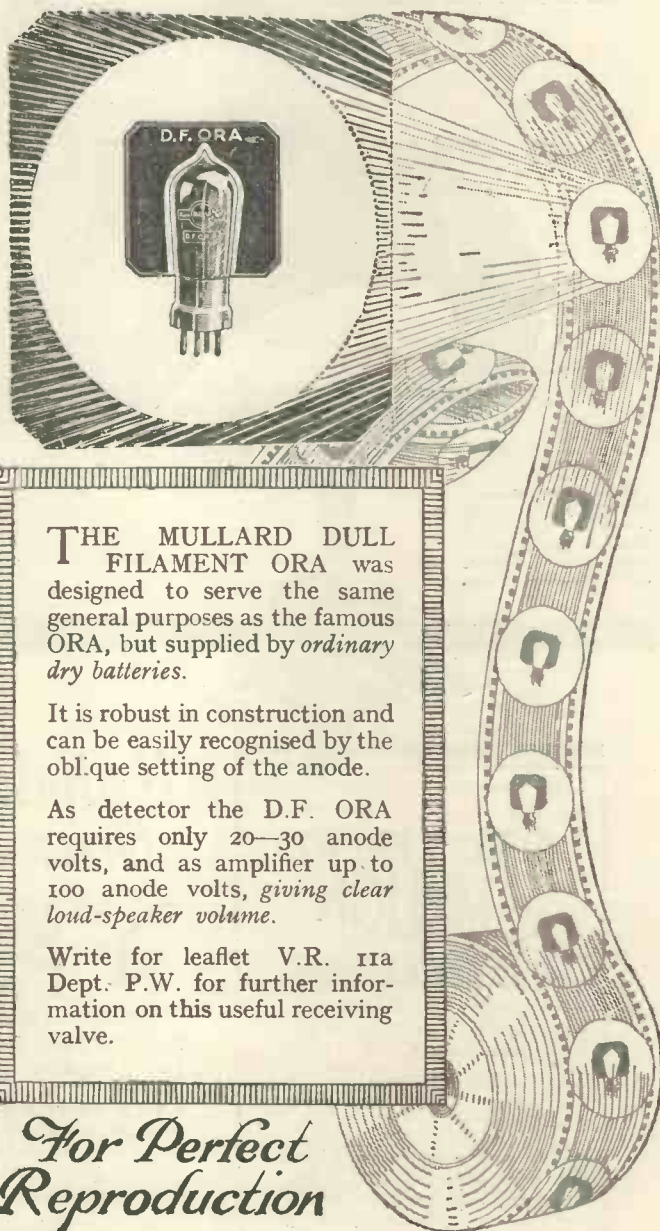**A Valve for Every Wireless Circuit****D.F. ORA.**

THE MULLARD DULL FILAMENT ORA was designed to serve the same general purposes as the famous ORA, but supplied by ordinary dry batteries.

It is robust in construction and can be easily recognised by the oblique setting of the anode.

As detector the D.F. ORA requires only 20-30 anode volts, and as amplifier up to 100 anode volts, giving clear loud-speaker volume.

Write for leaflet V.R. 11A Dept. P.W. for further information on this useful receiving valve.

*For Perfect  
Reproduction*

# Mullard

## THE MASTER VALVE

Advertisement of—The Mullard Radio Valve Co., Ltd. (P.W.), Nightingale Works, Nightingale Lane, Balham, S.W.12.

British Empire Exhibition.  
Palace of Engineering—Avenue 14—Bay 13.

(162.)

# The STRAD<sup>66</sup> of LOUD SPEAKERS<sup>99</sup>

Illustration shows  
Swan Neck Model  
AR 15 - £6-0-0  
Write for leaflet WD 3  
giving full particulars  
of all Amplion models.



Antonio Stradivari passed on to mankind instruments of amazing purity and richness of tone. His violins are with us still, but his secret he carried to the grave.

## Exclusive AMPLION Features

The wooden horn is a specialty of Amplion loud speakers and ensures a rich and mellow tone.

The sound conduit is rubber insulated, therefore non-resonant.

The Amplion is the only loud speaker with a floating diaphragm, another reason for its pure tonal value, thus an Amplion affords

**BETTER RADIO  
REPRODUCTION**

BRITISH  
EMPIRE  
EXHIBITION 1924

See Our Exhibit  
AVENUE 11  
BAYS 11-13  
PALACE OF  
ENGINEERING

## A product of the House of GRAHAM

**Y**OU may not have a Stradivarius violin, but you can have the "Strad" of loud speakers. Thirty years' experience and research enable the House of Graham to provide you with the Amplion of to-day, the instrument that gives a faithful rendering of every note in the harmonic scale. With full volume, clarity and rich mellow tone, the Amplion speaks to the world.

Every instrument has the backing of a service organisation at once unique in its conception and application. If your Amplion does not give better radio reproduction let the House of Graham know. Don't be satisfied with "good enough" when the best is in every instrument. The House of Graham makes no charge for service.

Obtainable from all Wireless Dealers of repute.

The  
World's  
Standard

# AMPLION

Wireless  
Loud  
Speakers

Showrooms:  
25-6, Savile Row,  
W.1, and  
82, High Street,  
Clapham, S.W.4.

**ALFRED GRAHAM & CO.**  
(E. A. GRAHAM)

St. Andrew's Works,  
Crofton Park, London, S.E.4.


Telephone:  
Sydenham 2820-1-2

Telegrams:  
"Navalhada, Catgreen,  
London."

*It will pay you always to watch WIRELESS WEEKLY Advertisements.*



## VOTE *for* PENTON

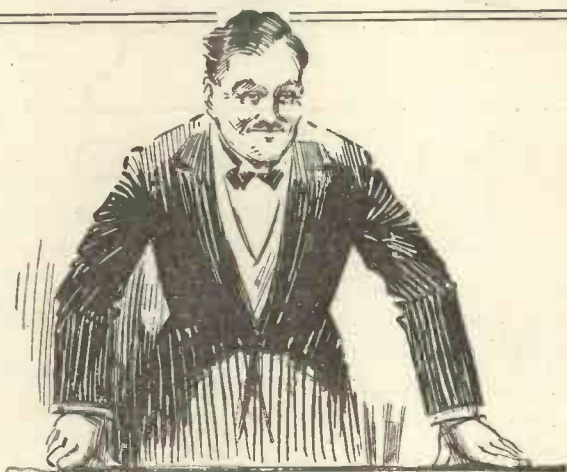

### *Mr. E. Conomy opens the Campaign*

LADIES AND GENTLEMEN—

In asking you to elect the "Penton" Low-Consumption Valve as a member of your sets, I do so on the plea that no member will stand for a bigger or more important percentage of your personal interests. You want decreased cost of listening—well, here it is. You want no more distortion, but peace and tranquillity combined with perfect reception. You have them all if you elect

### PENTON LOW CONSUMPTION VALVES

I put it to you that sooner or later you will learn that to pay more than 15/- for valves is to pay more than the most perfect valve is worth. Why pay it?—and again, why pay for needless current used by more wasteful members than Penton Low-Consumption Valves? Penton stands for the total abolition of all such unnecessary taxes on your wireless entertainments.

*For saving's sake elect*

## PENTON LOW - CONSUMPTION VALVES


PENTON LOW-CONSUMPTION VALVE, PRICE 15/- Postage 9d. Type H.E.4 for 6-volt accumulators. Plate voltage 40. Filament current .15 amp. Filament volts 5.

From all good Wireless Dealers.

List of Stockists on request from

**PENTON ENGINEERING CO.,  
15, Cromer St., London, W.C.1**

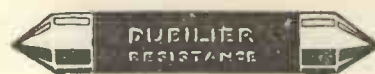Telephone: Museum 4681. Telegrams: Erpentobal Kincross.  
F.A.C.



*Grid Leak.*

### *Point-duty.*

The small grid leak which you use in your set is on "point-duty" and must exercise an efficient control over the electrons. If it is of too high a resistance, congestion will occur and the grid will become choked. If it has not sufficient resistance the grid will never attain a working voltage. Actually its resistance should lie between half a million and five million ohms (.5—5 megohms), though between fairly wide limits the exact resistance is not highly important.

It is, however, most important for the leak to remain CONSTANT in action, since if it becomes erratic or overheated the charges on the grid will be badly controlled and poor reception will result.

Long experiment in our laboratories has enabled us to produce grid leaks which are both constant and silent in use.

They are made in resistances of .5, 1, 2, 3, 4 and 5 megohms and the price in all cases is

## 2/6


*The Dubilier Condenser Co. (1921), Ltd.  
Ducon Works, Goldhawk Rd., London, W.12*

# DUBILIER

CONDENSER CO. (1921) LTD

E.P.S. 60.

# ROMANCE

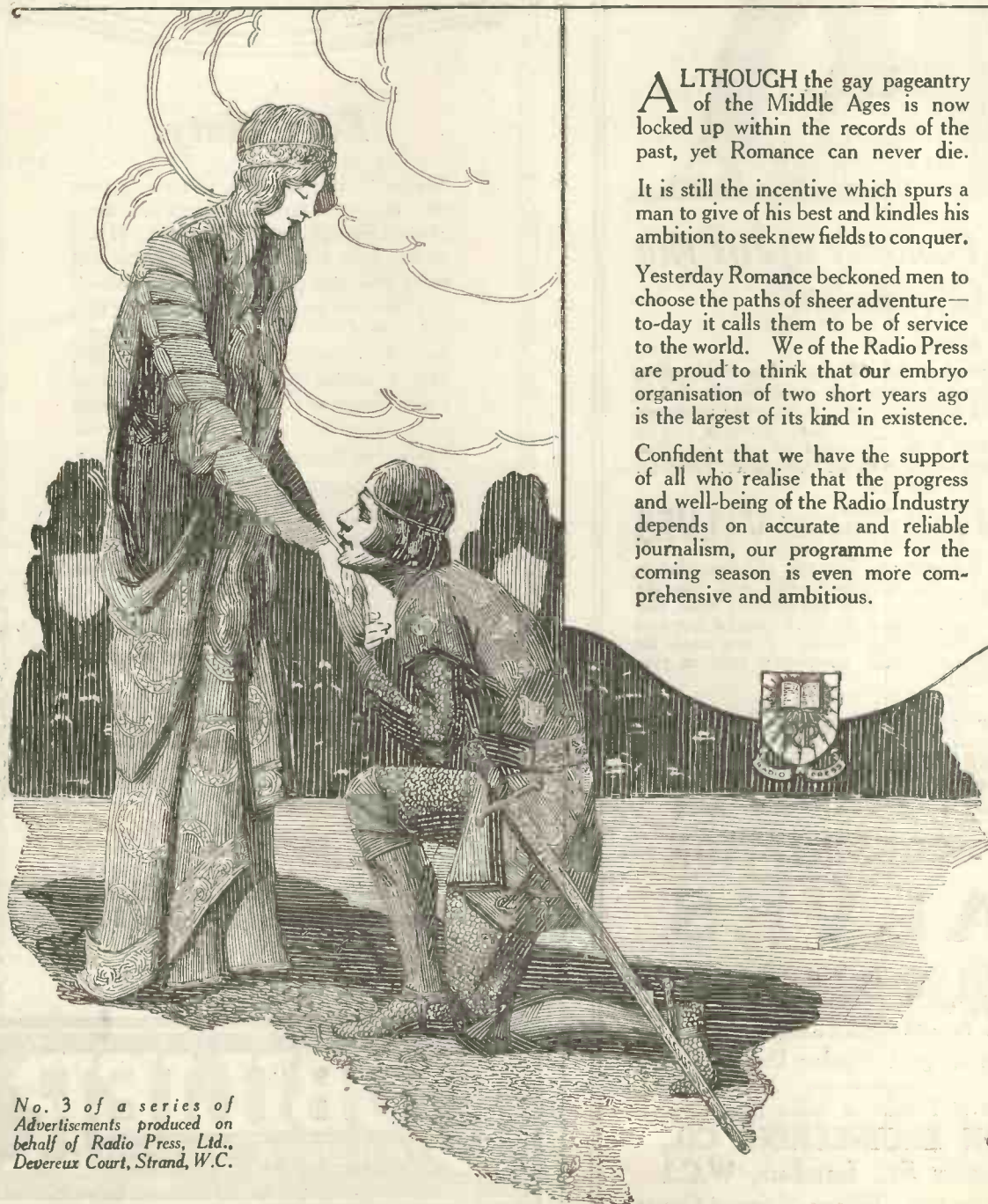

**A**LTHOUGH the gay pageantry of the Middle Ages is now locked up within the records of the past, yet Romance can never die.

It is still the incentive which spurs a man to give of his best and kindles his ambition to seek new fields to conquer.

Yesterday Romance beckoned men to choose the paths of sheer adventure—to-day it calls them to be of service to the world. We of the Radio Press are proud to think that our embryo organisation of two short years ago is the largest of its kind in existence.

Confident that we have the support of all who realise that the progress and well-being of the Radio Industry depends on accurate and reliable journalism, our programme for the coming season is even more comprehensive and ambitious.

No. 3 of a series of  
Advertisements produced on  
behalf of Radio Press, Ltd.,  
Devereux Court, Strand, W.C.

Gilbert Ad. 1189



## Wireless Weekly Small Advertisements

**STUDENTS**, successfully completing our 12 months' course on Wireless, are definitely guaranteed a position within one month of completion. Salary £150 to £500 per annum. (No Postal Tuition.) Prospectus free.—Wireless College, Bournemouth.

**HEADPHONE REPAIRS**.—Rewound, remagnetised, readjusted. Lowest prices quoted on receipt of telephones. Delivery three days. Est. 26 years.—Varley Magnet Co., London, S.E.18.

**TELEPHONE RECEIVERS** and Loud Speakers Rewound, 2,000 ohms, 3/6.—A. Roberts & Co., 42, Bedford Hill, Balham, S.W.12.

**MARCONI L.S.5 valves**, 2 at 30/- each, one U.3, 2 electrode, some Cossor and Ediswan R 7/-. Mic-Met and Hertzite, 4/-. Brown F 4,000, new, 17/6, Brown A 8,000, 30/-. Six 2 M.F. Mansbridge, 1/6 each. Two Igranit potentiometers, 4/- each. Moving coil volt and ammeter, 30/- each. Bonnard, 10, Kent Gardens, Ealing.

### WHOLESALE ONLY.

**WIRELESS DEALERS.** Our New 68-page Trade List of Radio parts now ready showing Trade and Retail prices. It is yours for the asking.

#### COMPLETE SETS, ACCESSORIES & COMPONENT PARTS

We were one of the very first Wholesale Factors of "Wireless," and our New Catalogue is the very latest thing in Wireless. Large Radio List issued.

**STAGGERING PRICES. HUGE STOCKS.**  
BUY FROM AN ESTABLISHED HOUSE.  
**IMPORTANT—Trade Only Supplied.**

**HOBDAY BROS., LTD.** (DEPT. B.) 21, 23, 25 & 27 GT. EASTERN ST., LONDON, E.C.2  
'Phone—CLERKENWELL, 2800 (6 lines)

### EL-BE UTILITIES The "MIKROTUNE"


Makes Tuning Simple & Certain.

Reversible Coil-holder. **12/6**  
Adds 50% value to any set.

Coils under minutest control. A PERFECT VARIOMETER.

Send us the name of your Dealer and we will arrange a demonstration for you.

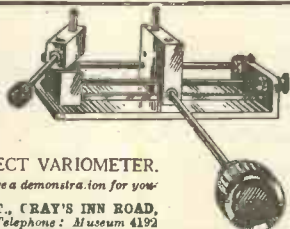**LEIGH BROS.** 37, SIDMOUTH ST., CRAY'S INN ROAD, LONDON W.C.1. Telephone: Museum 4192



### CABINETS YOU WANT

PICKETT'S Cabinets—they're good value, from 1/6 each, highly polished. Cabinet Works, Albion Rd., Bexley Heath, S.E. Write for Lists W.L.

### EBONITE

Sheet rod and tubing in all sizes kept in stock and cut to any required size while you wait, or sent by post on receipt of cash.

**WE CAN TURN ANYTHING IN EBONITE.**

**BURGE, WARREN & RIDGLEY, LTD.,**

91/92, GREAT SAFFRON HILL, LONDON, E.C.1. 'Phone: Holborn 50

**FINEST WORK & PROMPTITUDE.**  
INCOMPARABLE  
WHITE  
FILLING.

**HAND AND MACHINE  
ENGRAVING  
ON ANY MATERIAL.**

'Phone  
Central 1137.  
**CLIFFT & COCKLE**  
51, Arcade Chambers, St. Mary's Gate,  
MANCHESTER.

**Radio Press Information Dept.**  
**2/6 QUERY COUPON 2/6**

WIRELESS WEEKLY. Vol. 4. No. 13. July 30, 1924.  
This coupon must be accompanied by a postal order of 2/6 for each question, and a stamped addressed envelope.)

## The Peto Panel Service

—an entirely new departure in Radio

**BECAUSE** we realise that an experimenter's chief difficulty in building up a good Set lies in the preparation of the Panel and the construction of the cabinet we are inaugurating the *Peto Panel Service*.

### Types A and B.

Every Receiving Set described in future issues of MODERN WIRELESS and WIRELESS WEEKLY will be available in two forms. Type A will be the Set identical in every respect with the author's specification using the actual components illustrated in the article. Type B will be the pattern revised by Peto-Scott Co. Ltd., using their own guaranteed components and standardised cabinets. Both of these types will be available as finished instruments or in sets of parts for home construction. Naturally type B, while sacrificing nothing of the efficiency, will often mean a saving in cost of at least 25% in the initial outlay.

### Guaranteed Ebonite.

Remember that every panel is of the highest grade Post Office Ebonite, fully guaranteed against leakage. Both sides are matted, and it is cut to size, drilled, tapped, and engraved. There is nothing for the experimenter to do except assemble the components on the panel and wire according to instructions.

### Service Department free to users.

If, after completion, the Instrument does not work correctly it may be returned to us for testing—should the fault be traced to a component purchased from us it will be immediately replaced and the Instrument put in working order without charge. Should the fault, on the other hand, be due to incorrect wiring the Instrument will be put in working order at a nominal charge.

### List of Sets available.

Decide now which of these Sets you will build and get full particulars and prices from us without delay:

The Transatlantic V

The Puriflex

The S.T. 100

The 3-Valve Dual

The Omni Receiver

The All Concert de luxe



The S.T. 100 (3-valve).

### Improved H.F. Transformers.

Specially designed for selectivity and low high-frequency losses. Tunes very sharply with a variable condenser of .0002 mfd. Primary and secondary wound in a number of separate grooves. Air core. Standard 4-pin fitting. Manufactured from pure ebonite, hand turned and polished.

Prices: 300 to 600 metres ... **6/6**

Chelmsford & Radiola Wavelengths **7/-**

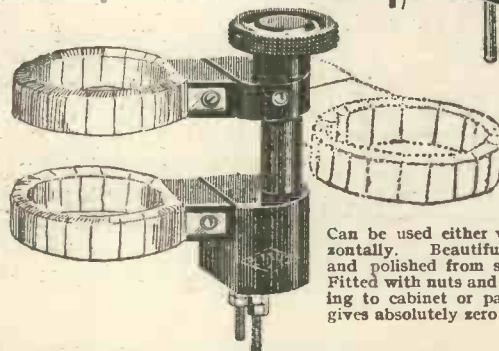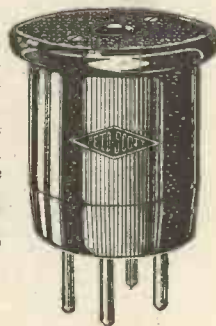

**Rotary  
Coil  
Holder.**

Can be used either vertically or horizontally. Beautifully hand turned and polished from solid ebonite rod. Fitted with nuts and bolts for clamping to cabinet or panel. A half turn gives absolutely zero coupling.


Price **7/6**

**PETO - SCOTT CO. LTD.,**

Registered Offices: **77, CITY ROAD, E.O.** (For all Mail Orders).

Branches: London: 62, High Holborn, W.C.1, and 230, Wood Street, Walthamstow. Cardiff: 94, Queen Street. Liverpool: 4, Manchester Street. Plymouth: Near Derry's Clock. G.A. 1163

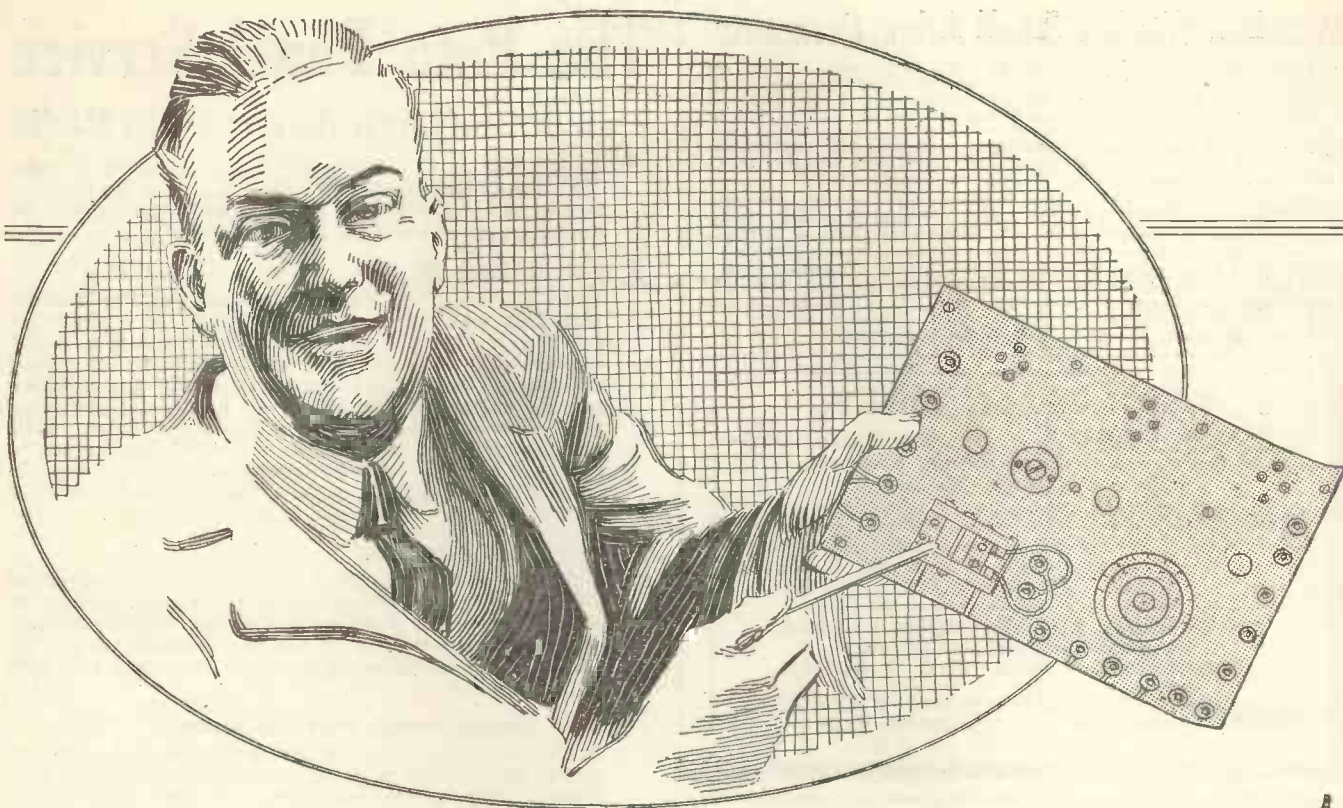*It will pay you always to watch WIRELESS WEEKLY Advertisements.*



Why! it's as plain as a pikestaff!

### Panel Card

#### No. 1

Giving full instructions for building a 3-Valve Set by means of a full size Card-board Model. This Receiver has a range of 500 miles under favourable circumstances, and will operate a Loud Speaker from the nearest B.B.C. Station up to 30 miles away. Cost of complete components as specification is £5 12s. 6d.

**1/-**

Sold by all Booksellers and Newsagents and published only by **RADIO PRESS LTD.**, Devereux Court, Strand, W.C.2.

AT last we have arrived at the very easiest method of demonstrating to a man how to build a Receiving Set. Our idea is this:—almost every Wireless Set consists of merely an ebonite panel and a cabinet—the latter being just a convenient method of supporting and protecting the underneath side of the panel. The panel itself is the only important part of the Set and therefore in this System we are issuing a series of full size panel cards of different types of Receiving Sets, cut to the exact size of the panel and containing a photograph of the top of the panel on one side and on the other side its wiring diagram. Nothing could be simpler. On

this full-size cardboard model it is easy to follow through every connection in the wiring, and to duplicate the Receiving Set with complete accuracy.

Included in every envelope are complete descriptive details of the Receiving Set together with a theoretical circuit diagram and a complete specification of components required.

Finally, full instructions are given for operating the Set and obtaining the best results.

This Radio Press Panel System is going to be one of the finest methods ever conceived for teaching the complete novice how to build a first-class Receiving Set without wasting time and money on early failures.

## RADIO PRESS PANEL CARD SYSTEM



USE THIS FORM AND SAFEGUARD YOURSELF !

" WIRELESS WEEKLY "  
AND  
" MODERN WIRELESS "

ORDER FORM

Provided this form is used when ordering goods or making enquiries, Radio Press Limited, Proprietors of "WIRELESS WEEKLY" "MODERN WIRELESS" and their series of handbooks, etc., guarantee to use, within their discretion, every endeavour to see that complete satisfaction is obtained. In no single case have Radio Press Limited failed to obtain satisfaction for the reader.

.....  
.....  
.....  
Date.....

Dear Sirs,

CUT HERE.

The Management of Radio Press Limited respectfully request that immediate and careful attention will be given to this communication.

*It will pay you always to watch WIRELESS WEEKLY Advertisements.*



STEPPING STONES



TO SUCCESS



**S**UCCESS in Radio is certainly dependent upon gradual and logical progress. The man who sets out to build an intricate and elaborate Receiving Set without first taking the trouble to learn some of the more elementary principles of Wireless, is very much like the man who is in such a hurry to reach the other side of the stream, that he omits to take due advantage of the stepping stones provided.

Radio—like every other hobby—wants understanding, and the easiest and most economical way of acquiring knowledge is to make systematic use of the Radio Press "stepping-stones" given below.


	Price		Price
1 Wireless for All ... ..	9d.	14 12 Tested Wireless Sets ... ..	2/6
By John Scott-Taggart, F.Inst.P.		By Percy W. Harris.	
2 Simplified Wireless ... ..	1/-	15 More Practical Valve Circuits ...	3/6
By John Scott-Taggart, F.Inst.P.		By John Scott-Taggart, F.Inst.P.	
3 How to Make your own Broadcast Receiver By John Scott-Taggart, F.Inst.P.	1/6	16 Home-Built Wireless Components ...	2/6
4 How to Erect Your Wireless Aerial ...	1/-	17 Wireless Sets for Home Constructors	2/6
By B. Muttell, A.M.I.E.E.		By E. Redpath.	
5 The Construction of Wireless Receiving Apparatus ... ..	1/6	18 Tuning Coils and How to Wind Them	1/6
By P. D. Iyers.		By G. P. Kendall.	
6 The Construction of Crystal Receivers... By Alan L. M. Douglas	1/6		
7 How to Make a "Unit" Wireless Receiver ... ..	2/6		
By E. Redpath.			
8 Pictorial Wireless Circuits ... ..	1/6		
By Oswald J. Rankin.			
9 Wireless Valves Simply Explained ...	2/6		
By John Scott-Taggart, F.Inst.P.			
10 Practical Wireless Valve Circuits ...	2/6		
By John Scott-Taggart, F.Inst.P.			
12 Radio Valves and How to Use Them... By John Scott-Taggart, F.Inst.P.	2/6		
13 500 Wireless Questions Answered ...	2/6		
By G. P. Kendall & E. Redpath.			
<b>RADIO PRESS PANEL CARDS.</b>		<b>RADIO PRESS ENVELOPES.</b>	
No. 1 How to make the W.I. receiver ... 1/-		No. 1. How to Build an S.T. 100 Receiver	1/6
By Herbert K. Simpson		By John Scott-Taggart, F.Inst.P.	
		No. 2. How to Build a 4-Valve Receiver	2/6
		By Percy W. Harris.	
		No. 3. How to Build a "Simplicity" 3-Valve Set ... ..	2/6
		By G. P. Kendall, B.Sc.	
		No. 4. How to Build the All-Concert de Luxe Receiver ... ..	2/6
		By Percy W. Harris.	
		<b>SIMPLEX WIRING CHARTS.</b>	
		No. 1. For 2-Valve Set ... ..	1/-
		No. 2. For 3-Valve Set ... ..	1/-
		No. 3. For 4-Valve Set ... ..	1/-

From all Booksellers, or post paid 2d. per book or 3d. per envelope extra direct from Publishers.

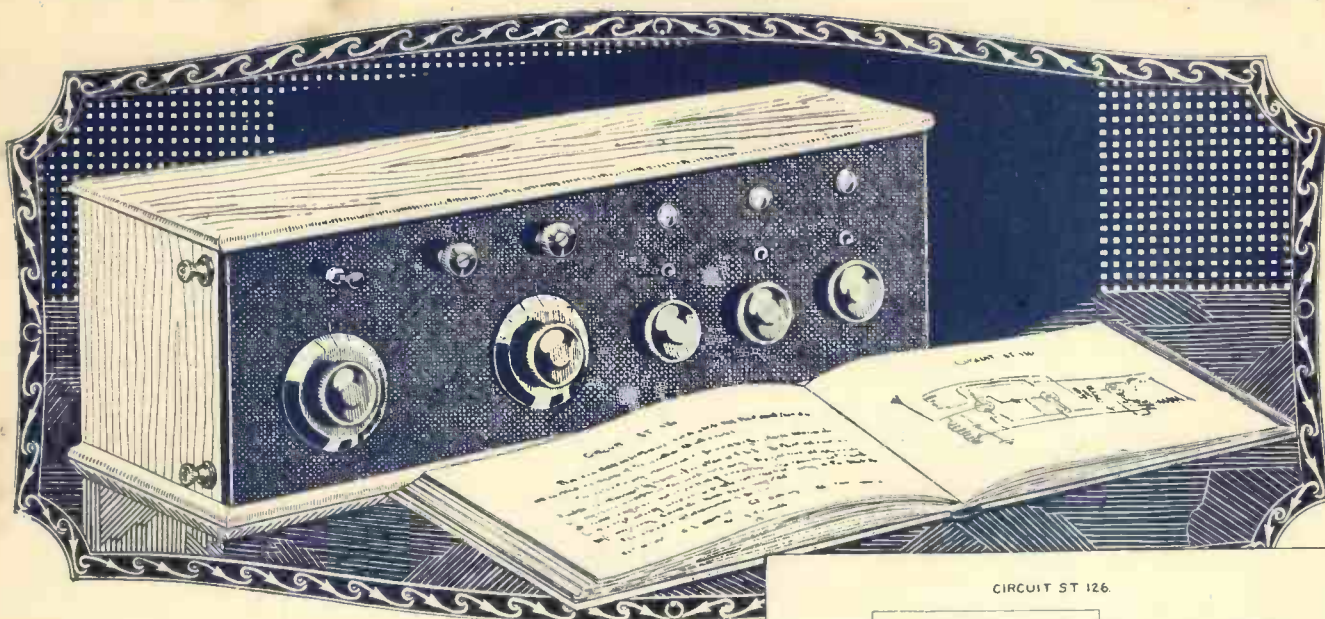
**RADIO PRESS Ltd. — the Largest Wireless Publishers in the World — Devereux Ct., Strand, W.C.2**

*It will pay you always to watch WIRELESS WEEKLY Advertisements.*





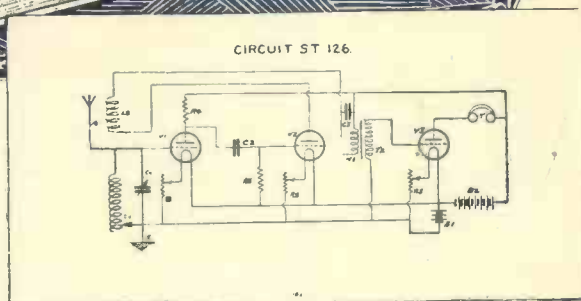Yes! you, too, need  
this fascinating Book  
of Circuits.



**A**LL the difference between success and failure in building a home-made Set lies in the correct values of the components and their arrangement.

Anyone who possesses a little wireless knowledge and who has built up a Set before will be able to pick up a copy of **MORE PRACTICAL VALVE CIRCUITS**,

*By John Scott-Taggart, F.Inst.P.*

and build any type of Set according to his own ideas and incorporating any of the scores of circuits described in it without further assistance.

These clear diagrams are so accurate and the descriptions given are so complete, that to a man who already knows something about Wireless, the Book is almost as good as a huge constructional Book showing how

to build dozens of different types of Instruments

For instance, opposite every Circuit is a full description of it—its advantages and disadvantages, how it should be used, the values of the fixed condensers and resistances, and so on. All this information is given because every Circuit is a practical one, and not a paper one. You can be confident that it will do all that is claimed for it.


This Book contains a very large number of circuits, including all the recent reflex circuits, together with such special Circuits as the Reinartz and the Flewelling. It is beautifully printed on good quality paper and bound in full cloth—a real reference Book, in fact. Get a copy from your Bookseller to-day, or direct for 3/8 post free.

RADIO PRESS Ltd., Devereux Court, Strand, W.C.2.

# More Practical Valve Circuits

*By John Scott-Taggart, F.Inst.P., A.M.I.E.E.*

**3/6**  
in  
full cloth

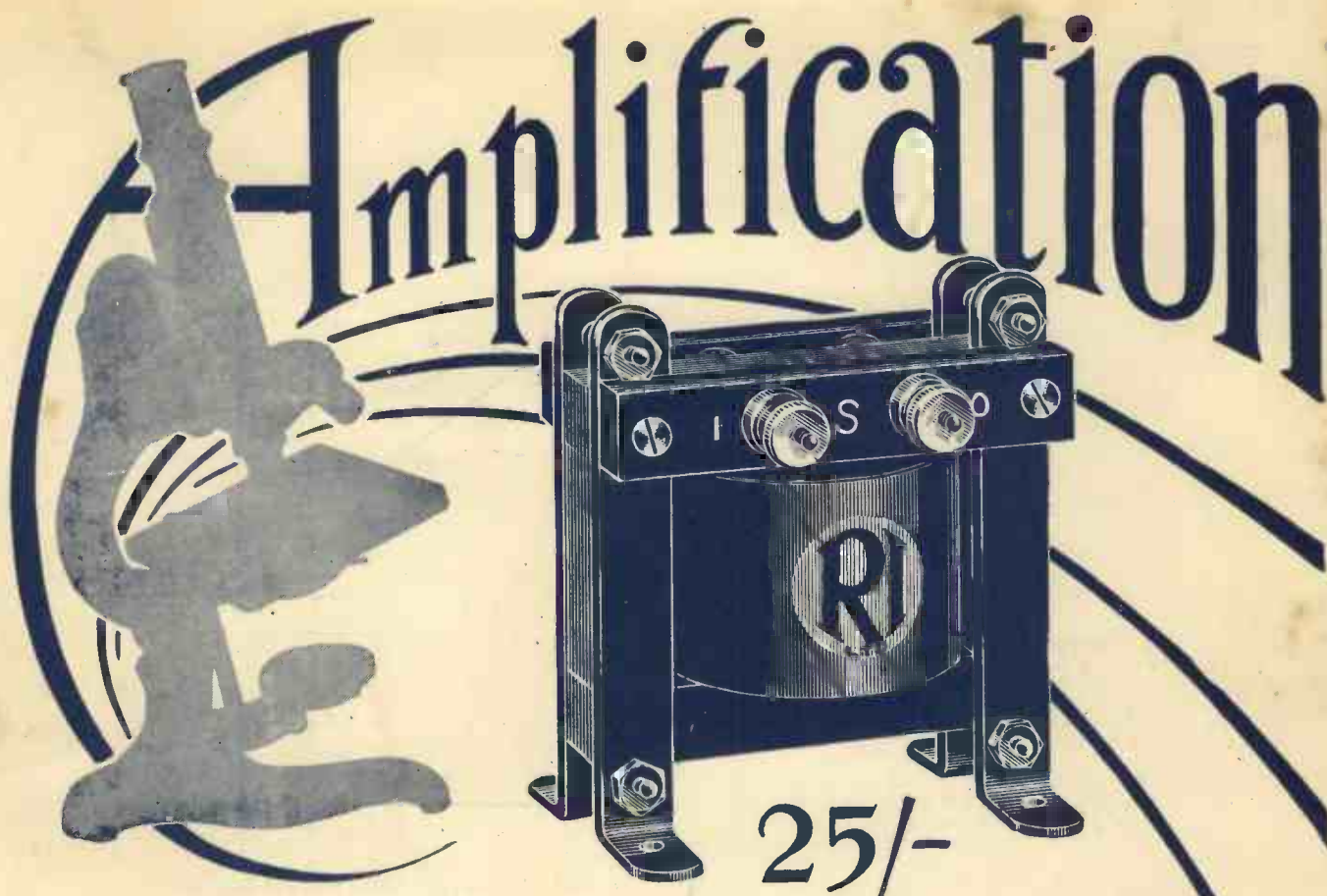

ANY ratio of transformation can be obtained with ease provided simple proportions in winding are adhered to, but all the wire in the world and inappropriate tests, applied to the same, will not produce good amplification.

To maintain steady and clear amplification over a wide range of frequency is a problem that can best be solved by a firm with years of research experience behind it. The best test of a transformer is—Will it do its job better than any other on the market? *The use of tests that do not show the capabilities of the instrument and are not in any way connected with the purpose for which it was designed is no indication of real transformer value.* The surest test is your own experience—failing that, take the experience of the greatest number of transformer users you know. The result will be R.I. every time. The absolute superiority of R.I. is world standard knowledge and you will agree.

*Send for illustrated catalogue T2 free on application.*

## RADIO INSTRUMENTS LTD.

Managing Director : J. JOSEPH, M.I.E.E.

Chief Designer : W. A. APPLETON, M.B.E., M.I.R.E. (late Admiralty Technical Research Officer).

*Works, Offices and Showrooms :*

**12, Hyde Street, New Oxford St., W.C.1.**

Telephone : Regent 6214-6215-6216.

Telegrams : "Instradio, London."

Printed for the Proprietors, RADIO PRESS, LTD., Devereux Court, Strand, W.C.2. by THE AVENUE PRESS (L. Upcott Gill & Son, Ltd.), 55-57, Drury Lane, London, W.C.2. Published on Wednesday of each week at 3, Bolt Court, Fleet Street, London, E.C.4. Address for Subscriptions and Editorial Communications :—Devereux Court, Strand, London, W.C.2. Advertisement Managers :—THE SCHEFF PUBLICITY ORGANISATION, LTD., 125, Pall Mall, London, S.W.1. Registered as a newspaper and for transmission by Canadian Magazine Post. Subscription rates :—32/6 per annum, 16/3 for six months, post free. Sole Agents for Australasia :—GORDON & GOTCH, (Australasia), LTD. For Canada :—IMPERIAL NEWS, LTD. For South Africa :—CENTRAL NEWS AGENCY, LTD. For Japan :—SALE & FRAZER, LTD.