W TO EVALUATE TAPE RECORDER SPECS

ar Electronics

WORLD'S LARGEST- SELLING ELECTRONICS MAGAZINE

Features:

Clandestine Shortwave **Broadcasts**

How to Light Up with Modern "LEDs"

Digital Electronics Course, Part I

Construction Projects:

Low-Cost Background **Music Adapter**

Versatile Nickel-Cadmium Battery Charger

Test Reports:

Heathkit AR-2020

4-Channel Receiver

Design Acoustics D6 Speaker System

Dynascan Cobra CAM-89


CB Transceiver


Data Precision

Digital Multimeters

EXCLUSIVE!

An Flectronic Salt Meter Family

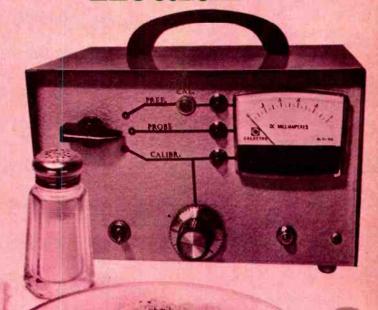

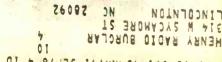

> 94435 16ANNSS 1ED BOLIEC



t of each is up to us

professional 10½-inch tape reels. Its unique combination of bias and equalization switching controls give 12 different settings to optimize the performance of any tape on the market.

The RT-1050's 3-motor transport system is activated electronically by full logic, solid state circuitry, triggered by feather touch pushbutton controls. Its transport is completely jam- and spill-proof, permitting you to switch from Fast Forward to Fast Rewind, bypassing the Stop button.

The RT-1050 was specifically

designed for easy operation with a wide combination of professional features like extended linearity VU meters with adjustable sensitivity, mic/line mixing, pushbutton speed selection and reel tension adjustment buttons. There's also an exclusively designed pause control and independent control of left and right recording tracks.

The same 2-track recording system studios use for better signal-to-noise ratios and higher dynamic range is incorporated into the RT-1050. Yet it can be easily converted to 4-track use with an

optional plug-in head assembly. Everythir considered it's the most versatile open-reel deck you can buy. Professionals prefer it for its studio-quality performance Everyone appreciates its completely simple operation.

Pioneer open-reel and cassette deck are built with the same outstanding quality, precision and performance of all Pioneer stereo components. That's why, whichever you choose, you know it's completely professional and indisputably the finest value ever in a studio-quality tape deck.



Giving you the bes

High fidelity is important to us at Pioneer. It's all we do and it's all we care about. We are excited that cassette tape decks have reached a level of performance that meet the highest standards. We are excited because we know that it means more enjoyment for you from your high fidelity system. We also know that you can now get more versatility and more value out of your high fidelity system than ever before.

The great advances in cassette technology have had impact on the reel-to-reel tape deck concept as well. We believe that the era of the small, inexpensive 7-inch reel tape deck is past. Neither its convenience nor its performance make it a good value compared to the new cassette technology. And it is now possible for Pioneer to offer you a professional studio-quality 101/2-inch reel deck at prices that compare favorably with what you might expect from old fashioned 7-inch reel units. In our udgment the old ideas must move aside or the new ideas. And Pioneer has some very intelligent new ideas in tape for you.

The convenience of cassette. The performance of open-reel.

The stereo cassette deck has become a "must" in complete high fidelity systems. Because of its convenience, price and performance, it has virtually replaced the once popular 7-inch open-reel deck. As Julian D. Hirsch, prominent audio reviewer put it, "The best cassette machines compare favorably with a good open-reel recorder in listening quality." Pioneer proves it with four top-performing models.



Stacks compatibly with other components.

Our new CT-7171, with built-in Dolby, is a deck with a difference. It's designed with all controls up front so you can stack other components on or under it. Even the illuminated cassette compartment is front loading, for easy access and visibility.

Performance features stack up, too. Bias and equalization switches provide optimum recording and playback for every type of cassette tape made. You'll produce distortion-free recordings consistently with two oversized, illuminated VU meters plus an instantacting peak level indicator light. And for those unpredictable program source peaks, there's a selectable Level Limiter circuit. It's similar to the type used in professional recording studios to prevent "clipping" distortion.

Finding a desired program point in a recorded cassette is simple with our new CT-7171. A memory rewind switch,

working together with the 3-digit tape counter, plus an exclusive Skip button, lets you monitor audibly at accelerated speed to make precision cueling a breeze.

Automatic tape-end stop, dual concentric level controls, separate mlc/line inputs, pause control, in addition to many other features, make the CT-7171 the recording studio that fits on a shelf.

Whether you choose the sophistication of the CT-7171 or Pioneer's CT-5151, CT-4141A or CT-3131A, which share many of its features, you're assured optimum performance and maximum value. One tradition that never changes at Pioneer.

Open-reel. A professional recording studio in your home.

Professionalism comes with all three studio-quality open-reel models. The RT-1020L (7½, 3¾ ips) is unequalled in 4-track units. With three motors and three heads, it has virtually every professional feature you'd want. Yet it's extremely simple to use. In addition to stereo record/playback, it also highlights 4-channel playback. The complete extent of its capabilities becomes apparent only after you've worked with it. Then you'll recognize the magnitude of Pioneer's accomplishment.

Our RT-1050 is a 2-track, 2-speed (15, 7½ ips) 3-head deck which, like all our open-reel models, can handle



12 Bias & Equalization settings optimize performance.




Whether you use a cassette or open reel deck is up to you.



Model	RT-1050	RT-1020H	RT-1020L
Maximum Reel Size	101/2"	101/2"	101/2"
Speeds	15 & 71/2 ips	15 & 71/2 ips	71/2 & 33/4 ips
Number of Tracks	2 (4 optiona)	4	4
Wow & Flutter (at high speed)	0:36%	0.06%	0.10%
Frequency Response (±3dB)	30Hz-22MHz	30Hz-22kHz	40 Hz-20kHz
Tape Blas Selection	3 position	3 position	3 position
S/N Ratio	57dB	55d8	55dB
Equalizer Selection	4-Position	2-Position	2-2osition
Mic/Line Mixing	yes .	yes	yes
LED Peak Indicator	7es	no	no
Memory Recording	/es	yes	yes
VU Meter Scale Selection	/es	no	no
4-Channel Playback	no	yes	yes
Motors	3	3	3
Price	¢60005	\$649.95	\$349.95

Model	CT-7171	CT-5151	CT-4141A	CT-3131A*
Dolby Noise Reduction	yes	yes	yes	no
Tape Selection		Bias & Equal.		Equalization
Auto. Tape Stop	yes	yes	yes	yes
Memory Rewind	yes	yes	no	no
Pause Control	yes	yes	yes	yes
Freq. Response*	30-16,000 Hz	30-16,000 Hz	30-15,000 Hz	30-15,000 Hz (*Chrome Tape)
Peak Indicator	yes	yes	no	no
Level limiter	yes	yes	no	no
Skip cueing	yes	yes	yes	no
Signal/Noise (Dolby)	58 dB	58 dB	58 dB	_
S/N (Less Dolby)	48 dB	48 dB	48 dB	47 dB
Tape Heads	Ferrite	Ferrite	Permalloy	Permalloy
Motor Type	DC Servo	DC Servo	DC Servo	DC Servo
Wow & Flutter (WRMS)	0.10%	0.12%	0.13%	0.13%
Price	\$369.95	\$269.95	\$239.95	\$179.95

*not shown

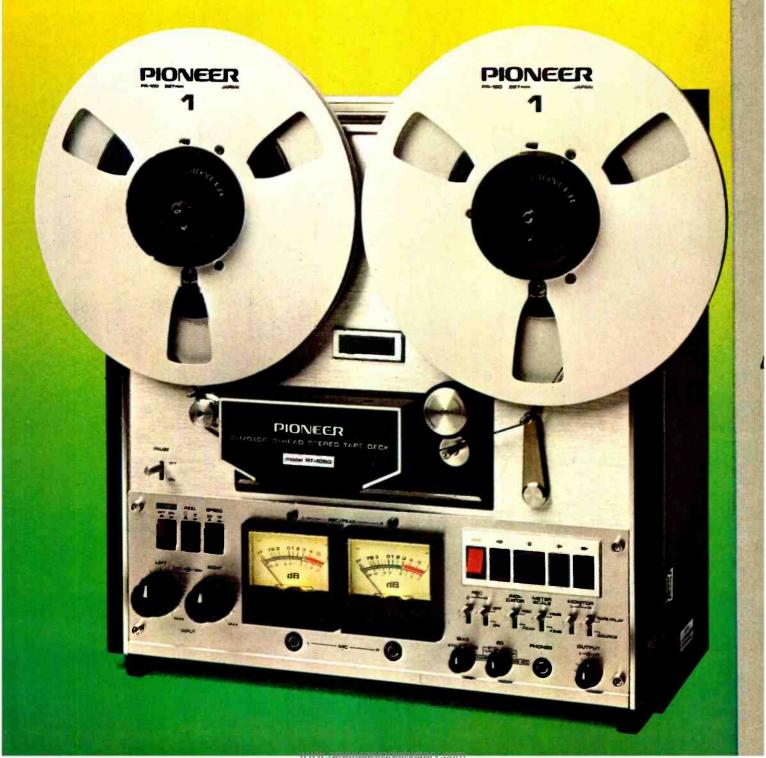













In response to the needs of the recording and broadcast industries, Stanton creates the <u>new</u> calibration standardthe 68I TRIPLE-E....

A definite need arose.

The recording industry has been cutting discs with higher accuracy to achieve greater definition and sound quality.

Naturally, the engineers turned to Stanton for a cartridge of excellence to serve as a primary calibration standard in recording system check-outs.

The result is a *new* calibration standard, the Stanton 681 TRIPLE-E. Ferhaps, with this cartridge, the outer limits of excellence in stereo sound reproduction has been reached.

The Stanton 681 TRIPLE E offers improved tracking at all frequencies. It achieves perfectly flat

frequency response to beyond 20 Kc. It features a dramatically reduced tip mass. Actually, its new nude diamond is an ultra miniaturized stone with only ½ the mass of its predecessor. And the stylus assembly possesses even greater durability than had been previously thought possible to achieve.

The Stanton 681 TRIPLE-E features a new design of both cartridge body and stylus: it has been created for those for whom the best is none too good.

Each 681 TRIPLE-E is guaranteed to meet its specifications within exacting limits, and each one boasts the most meaningful warranty possible: an individual calibration test result is packed with each unit.



For further information write Stanton Magnetics, Inc., Terminal Drive, Plainview, N.Y. 11803.

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

WORLD C. F. H. C. L. C.	
FEATURE ARTICLES	
A NEW WAVE OF TEST INSTRUMENTS	38
HOW TO EVALUATE TAPE RECORDER SPECSJulian D. Hirsch	46
SELECTING AN ELECTRONIC MUSIC SYNTHESIZER	50
DX'ING CLANDESTINE SHORTWAVE STATIONS	53
BASIC LOGIC COURSE	56
LIGHT UP YOUR CIRCUITS WITH LED'S	58
ELECTRONIC GERIATRICS	96
CONSTRUCTION STORIES	
AN ELECTRONIC SALT METER FOR FAMILY HEALTH	33
A PAIR OF USEFUL TEST IDEAS CHECK & SELECT PUT'S	37 37
SCA ADAPTER REVEALS HIDDEN MUSIC AND NEWS ON YOUR FM RECEIVERSFrank P. Karkota, Jr.	43
INDOOR 20-METER HAM ANTENNA	52
BUILD A POLARITY-SENSING CONTINUITY TESTER	
BUILD A VERSATILE NICKEL-CADMIUM BATTERY CHARGER	68
COLUMNS	
STEREO SCENE	22
CB SCENE Len Buckwalter Mayday, Pan, Security	
SOLID STATELou Garner Experimenting with light emitting diodes	
AMATEUR RADIO Herbert S. Brier Getting started in amateur radio	
TEST SCENE	
HOBBY SCENE Editorial Staff	101
PRODUCT TEST REPORTS	
HEATHKIT MODEL AR-2020 4-CHANNEL RECEIVER DESIGN ACOUSTICS MODEL D-6 SPEAKER SYSTEM	76
DYNASCAN COBRA CAM 89 CB TRANSCEIVER	78
DEPARTMENTS	
EDITORIAL	
LETTERS	. 6
NEW PRODUCTS	. 16
NEWS HIGHLIGHTS	. 26
TIPS & TECHNIQUES	. 0

POPULAR ELECTRONICS, October 1974, Volume 6, Number 4 Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S., Possessions and Canada, \$6,98, all other countries, \$8.98. Second class Postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada and for payment of postage in cash. Subscription service and Forms 3579, P.O. Box 2774. Boulder, CO 80302. POPULAR ELECTRONICS Including ELECTRONICS WORLD, Trade Mark Registered, Indexed in the Reader's Guide to Periodical Literature. Copyright © 1974 by ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved.

Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review.
Forms 3579 and all subscription correspondence should be addressed to POPULAR ELECTRONICS. Circulation Dept., P. O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address. Include your old address, as well as new—enclosing, if possible, an address label from a recent issue.
Editorial contributions must be accompanied by return postage and will be handled with reasonable care, however publisher assumes no responsibility for return or safety of art work, photographs, models, or manuscripts.

manuscripts

ELECTRONICS LIBRARY

Popular Electronics

EDGAR W. HOPPER

Publisher

ARTHUR P. SALSBERG

Editorial Director

LESLIE SOLOMON

Technical Editor

JOHN R. RIGGS

Managing Editor

EDWARD I. BUXBAUM

Art Director

ALEXANDER W. BURAWA

Associate Editor

JOHN McVEIGH

Assistant Editor

ANDRE DUZANT

Technical Illustrator

ELLEN S. FINKELSTEIN

Editorial Assistant

LEN BUCKWALTER LOU GARNER JULIAN D. HIRSCH RALPH HODGES WALTER G. JUNG MILTON S. SNITZER

Contributing Editors

JOSEPH E. HALLORAN

Advertising Director

JOHN J. CORTON Advertising Sales

LINDA BLUM
Advertising Service Manager

PEGI MCENEANEY

Executive Assistant

STANLEY NEUFELD

Associate Publisher

FURMAN H. HEBB Group VP, Electronics & Photo

ZIFF-DAVIS PUBLISHING COMPANY Popular Electronics Editorial and Executive Offices

Editorial and Executive Offices
One Park Avenue New York, New York 10016
212-725-3500
William Ziff, President

William Ziff, President
W. Bradford Briggs, Executive Vice President
Hershel B. Sarbin, Senior Vice President,
Secretary, and Treasurer

Philip Sine, Senior Vice President
Phillip T. Heffernan, Vice President, Marketing
Frank Pomerantz, Vice President, Creative Services
Arthur W. Butzow, Vice President, Production
Edward D. Muhlfeld, Vice President, Aviation
and Automotive Divisions

George Morrissey, Vice President Sydney H. Rogers, Vice President Sidney Holtz, Vice President Lawrence Sporn, Vice President, Circulation Edgar W. Hopper, Vice President, Electronics Div.

Midwestern Office
The Pattis Group, 4761 West Touhy Ave.,
Lincolnwood, Illinois 60644, 312 679-1100
GERALD E. WOLFE, GEORGE B. MANNION
DAVID ALLEN

Western Office 9025 Wilshire Boulevard, Beverly Hills, CA 90211 213 273-8050; BRadshaw 2-1161 Western Advertising Manager, BUD DEAN

Japan: James Yagi Oji Palace Aoyama; 6-25, Minami Aoyama 6 Chome, Minato-Ku, Tokyo 407-1930/6821









The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



TWENTY YEARS AGO...

Color TV emerged from the laboratories... Citizens Radio Service included only one frequency (465 MHz) for low-power, party-line use... The first stereo tape recorders appeared... The acoustic suspension speaker was developed... A magazine called POPULAR ELECTRONICS was started.

The year was 1954. And the first issue of POPULAR ELECTRONICS (October 1954) was sold out at newstands to an electronics-hungry public. Devoted to how-to-do-it, how-to-use-it, how-it-works and why-it-works, the magazine quickly captured a large, loyal readership.

The lead article in that first issue was "Build Your Own Bike Radio"—a four-tube, point-to-point wired AM radio that barely fit across the straight part of a bike's handle bars. It was written by Lou Garner, our *Solid State* columnist. Other 1954 features covered subjects such as how to build a coil-winding jig, a 4-watt power amplifier (mono, of course), and the beginning of a series called "So You Want to be a Ham."

As the years passed, POPULAR ELECTRONICS served as an information center for active electronics enthusiasts, introducing them to the latest technologies: homemade pc boards in 1956, video tape recording in 1957, FM multiplexing in 1959, the laser in 1961, hi-fi laboratory checks in 1962, and a transistorized auto ignition system project in 1963. In 1966, a major article on integrated circuits predicted that these devices would make possible a new generation of products for home and industry.

Then, in 1968, POPULAR ELECTRONICS embarked on a series of "firsts"—exciting, advanced-technology projects to occupy the hands and minds of readers. For example, in 1968, the first digital readout construction project was introduced by POPULAR ELECTRONICS. This was followed by the first laser communications system in 1969. (That one was shown at the Smithsonian Institution, by the way.) In these pages, readers saw the first digital multimeter project in 1970, the first build-it-yourself calculator in 1971, the first alpha brain-wave project in 1973, and the first digital wristwatch kit in 1974. Continuing this stimulating tradition, next month we will introduce a moderately priced laser video communication link—that's video transmission and reception without strung wires and with no license requirement!

It has certainly been a revolutionary two decades for POPULAR ELECTRONICS. There's much more to come as new generations of electronic devices and thrilling applications are developed in the unfolding years. You'll be sure to read about them here.

art Salsberg

Another introductory offer to new members of the ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB



404/445 ELECTRONIC CIRCUITS MANUAL

by J. Markus Pub. price, \$22.00 Club price, \$15.75

637/458
DESIGNING
WITH TTL
INTEGRATED
CIRCUITS

by Texas Instruments Inc.

Pub. price, \$19.50 Club price, \$13.50

404/437 SOURCEBOOK OF ELECTRONIC CIRCUITS

by J. Markus Pub. price, \$21.50 Club price, \$17.50

389/756
SEMICONDUCTORS
MEMORY
DESIGN AND
APPLICATION

by Texas Instruments Inc. Pub. price, \$18.50 Club price, \$13.75

491/364 THE DESIGN OF DIGITAL SYSTEMS

by J. B. Peatman Pub. price, \$16.50 Club price, \$11.75



286/515
INTEGRATED
CIRCUITS:
A Basic Course
for Engineers
and Technicians
by R. G. Hibberd

Pub. price, \$10.25 Club price, \$8.45

MOS/LSI DESIGN AND APPLICATION

by Carr & Mize Pub. price, \$18.50 Club price, \$13.50



HANDBOOK

PHYSES

388/458 Magnetic Recording

C. E. Lowman
Pub. price, \$14 50
Club price, \$9.75



by T. G. Hicks Pub. price, \$19.50 Club price, \$14.25



Pub. price, \$37.45 Club price, \$14.95



of these great professional books for \$ 100

VALUES FROM \$8.45 to \$37.45

Special \$1.00 bonus book comes to you with your first club selection



by J. G. Graeme Pub. pricε, \$14.00 Club pricε, \$10.50

353/387
MINICOMPUTERS FOR
ENGINEERS &
SCIENTISTS

by G. Kern Pub. price, \$17.75 Club price, \$10.50



649/170 OPERATIONAL AMPLIFIERS

by Tobey, Graeme & Huelsman Pub. price, \$15.00 Club price, \$11.50

209/731 STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 10/e

by Fink and Carroll Pub. price, \$34.85 Club price, \$24.95

Save time and money by joining the Electronics and Control Engineers' Book Club

Here is a professional club designed specifically to meet your day-to-day engineering needs by providing practical books in your field on a regular basis at below publisher prices.

How the Club operates: Basic to the Club's service is its publication, the *Electronics and Control Engineers' Book Club Bulletin*, which brings you news of books in your field. Sent to members without cost, it announces and describes in detail the Club's featured book of the month as well as alternate selections which are available at special members' prices.

When you want to examine the Club's feature of the month, you do nothing. The book will be mailed to you as a regular part of your Club service. If you prefer one of the alternate selections—or if you want no book at all for that month—you notify the Club by returning the convenient card enclosed with each Ralletin

As a Club member, you agree only to the purchase of four books over a two-year period. Considering the many books published annually in your field, there will surely be at least four that you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

MAIL THIS COUPON TODAY

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

582 Princeton Road, Hightstown, New Jersey 08520

Please enroll me as a member of the Electronics and Control Engineers' Book Club and send me the two books indicated below. I am to receive the higher priced of the two for just \$1, and my first selection at the special Club price. Actual postage, plus 25t handling charge will be added (sales tax, also, if applicable). These books are to be shipped on approval, and I may return them both without cost or further obligation. If I decide to keep the books, I agree to purchase as few as four additional books (including this first selection) during the next two years at special Club prices (guaranteed 15% discount, often more).

Write Code No. of bonus book here	Write Code No. of first selection here
Name	
Address	
City	
State	Zip
	E33265

CIRCLE NO. 16 ON READERS SERVICE CARD

www.americananadiohistory.com



QUALITY STEREO EQUIPMENT AT LOWEST PRICES.

YOUR REQUEST FOR QUOTA-TION RETURNED SAME DAY.

FACTORY SEALED CARTONS-GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:

A.D.C.

KLH

A.R. DYNACO SHURE KOSS

SONY


FISHER

AND MORE THAN 50 OTHERS BUY THE MODERN WAY BY MAIL-FROM



Department 217S 12 East Delaware Chicago, Illinois 60611 312-664-0020

CIRCLE NO. 20 ON READERS SERVICE CARD

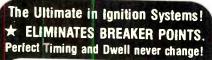

* Eliminates Tune-ups. Never wears out or needs any Maintenance.



The Most Advanced "OPTO-ELECTRIC SYSTEM"

 The Allison Breakerless System eliminates the Points and Condenser, replacing them with an Opto-Electronic And Condenser, replacing ment with an opto-crectionic Trigger, using a Light-Emitting Diode and Phototransistor. Also completely eliminates wiper-arm "friction" wear. The only "TRUE" Electronic Ignition ... that you can install for under \$100. Gives 40-times more Timing Accuracy than ANY system using mechanical Breaker-Points! Unlimited RPM. Smoother running .(No timing fluctuation as with Magnetic-units). Unaffected by Temperature, Moisture, or Vibration! All Solid-State Components. Easier Starting under any condition! Increased Horsepower. Sparkplugs last longer. Perfect timing increases engine Efficiency and Gas Mileage up to 30%

Quick and Easy Installation! Tested and Proven reliability.

Only \$4995 • SATISFACTION GUARANTEED! Complete.
 ● 1-YEAR FACTORY WARRANTY.

(State Make, Year, Engine Size). (Calif. Res. add Tax).

 CONVERT YOUR "C-D" UNIT TO BREAKERLESS! "TRIGGER-UNIT" DNLY \$34.95

Send Postcard for FREE BROCHURE Today.

ALLISON AUTOMOTIVE CO. P.O. Box 881-P, TEMPLE CITY, CAL. 91780

CIRCLE NO. 2 ON READERS SERVICE CARD



THE LONG AND THE SHORT OF TONEARMS

Ralph Hodges's clear, thorough article on "Matching Tonearms And Cartridges" (Stereo Scene, July 1974) goes a long way toward providing an understanding of the factors involved in improving the reproduction of ripply and warped records. On the subject of tonearm length, however, it should be pointed out that, as stated, a shorter arm will contribute more warp wow than will a longer one (all else being equal)-particularly if the pivot allowing vertical motion is the same distance above the record in both arms. If the pivot is in the plane of the record, the warp wow contributed by the arm's geometry is minimized.

> JACK REED Chicago, III.

FOR A GOOD CAUSE

I am attempting to build up a library of POPULAR ELECTRONICS for our newly formed Lynbrook Amateur Radio & Electrical Hobbyist Club. If any readers feel generous and would like to donate past issues of PE (and other magazines) to our club, please drop me a note at the address below, and we will gladly pay postage. We can use all types of magazines devoted to hobby electronics, communications, etc.

> ROBERT HUMMEL Director/Radio Club 30 Durland Rd. Lynbrook, N.Y. 11563

Any interested readers are asked to write directly to Mr. Hummel.

SEES NO NEED FOR TWO COUNTERS

I agree with Paul Michael ("Portable Time Base for Digital Clocks," July, 1974) that the 555 makes an excellent source of 60-Hz pulses for driving a digital clock when an ac line signal is not available. However, I see no need for the two 7490 decade counters shown. There is no reason why the 555 itself cannot be operated at 60-Hz, thus eliminating the extra circuitry. A high-quality 1-µF capacitor can be used for C1, and the output can be taken from pin 3 of the 555. A high-quality tantalum, Mylar, or metallized paper capacitor is more stable than the average 0.01-µF ceramic disc capacitor.

HAROLD J. TURNER, JR. Senior Technical Editor National Radio Institute Washington, D.C.

IN REBUTTAL

In response to Kenneth B. Rothman, KBY-0535 ("Letters," July 1974), there are groups across the country working with the FCC on a continuing basis in an effort to clean up the air. We of the "Quit Skip QSL Club" have chapters in 12 states cooperating with the local FCC Offices. In fact, in three states, our members who are qualified to do so are given the TVI complaints to investigate. This relieves the FCC of much work and does a great deal toward improving public acceptance of us CB'ers. We do not pretend to be a "police force," but each State Chapter has assigned monitors gathering information on infractions of Part 95.

> GEORGE CAPPS, QS1MO National Director Quit Skip QSL Club Rte. 2, Box 174 Rolla, MO 65401

CAN'T PEAK WITH Q MULTIPLIER

After assembling the Q Multiplier (April 1974), I checked it out with an oscilloscope to assure myself that it was operating properly. I installed it in my Hallicrafters SX62A receiver. It operates fine on NULL, but on PEAK, I lose everything. When I pull the plug on the Q Multiplier, the receiver works properly again. In an attempt to get the multiplier working properly with my receiver, I have attempted to adjust the receiver's i-f transformers-to no avail. How can I get my Q Multiplier to work in the PEAK mode?

> OWEN P. BURKLOW Scottsdale, Ariz.

The Author replies: "It appears that your SX-62A already has a pretty good i-f. From the description of your problem, it is pretty definite that the Q of the i-f transformer is such that it is pulling the Q Multiplier out of oscillation as you tune to the center of the i-f passband.

"There are several solutions I can recommend: (1) Reduce the value of C1 to 50 to 180 pF, using the largest value that will keep the multiplier in smooth oscillation. (2) Decrease the value of C6 to 500 to 800 pF. This will increase oscillator feedback, but it will change the frequency (readjust L1 as necessary) and will result in some reduction in the height and depth of the peak and null. (3) Increase the value of R2 to 15,000 ohms, which has basically the same effect as solution 2."

A CLEARER UNDERSTANDING OF DECIBELS

"Understanding Decibels" in the April 1974 issue was very good. However, some clarification is desirable. The second sentence would be more accurate if the word "bel" were used in place of "decibel." The "deci" prefix is used to denote a quantity that is one tenth that of a bel, thus simplifying how we write power levels. Mr. Ward's formulas take this into consideration. (Note: The word "bel" was designated by an international committee for


POPULAR ELECTRONICS

countries using common logarithms. For those countries using the natural, or naperian, logarithms, the words "neper" and "decineper" were formulated. The latter differ somewhat from "bels" and "decibels.")

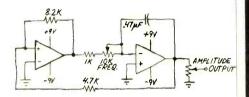A. L. AYERS Appleton, Wisc.

AN EASIER WAY TO DO IT

The triangle-wave generator shown in the Test Equipment Scene (May 1974) was doing things the hard way. My circuit is much simpler. It uses less than half the



parts, but it doesn't sacrifice performance. It also features better linearity, which is important for test purposes. And the circuit is drift-free, eliminating the need for relatively expensive output capacitors. I have designed the circuit to be frequency-variable without the need to readjust the output level to maintain a constant amplitude.

WOLFGANG RUPPRECHT Munich, Germany

COMMENTS ON THE "NEW LOOK"

... The new big size is great.

CHARLES L. KELSY Mayville, N.Y.

... I think it's in great taste. Especially, enjoyed your article "How to Set Up a Home TV Service Shop."

BOB J. LATHIM Dwight, III.

... These latest changes have helped to further increase its effectiveness.

GEORGE E. PARKER Englewood Cliffs, N.J.

... Keep the new size and the metrics and you have a permanent subscriber.

ARTHUR YASUI Palo Alto, Calif.

DON'T SUPPLY KEYBOARDS INDIVIDUALLY

Our company was accidentally listed in Don Lancaster's article in your July 1974 issue ("How to Select EM Keyboards & Controllers") as a supplier of AGO keyboards. While we do manufacture keyboard controllers for our modular synthesizer systems, we cannot economically handle individual keyboard manuals. We'd like to extend our apologies to those people to whom we have not replied in this regard.

DAVE ROSSUM Eµ Systems Santa Clara, Calif.

Now that the AT 12S with genuine Shibata stylus is here... all other stereo cartridges over \$50 are obsolete!

Better performance from existing stereo records, and ideal operation of any CD-4 discrete playback system is yours when you select an audio-technica

audio-technica four channel cartridge.

Now four models including the new AT12S at only \$49.95 suggested retail. All with audio-technica

genuine Shibata tips that permit response to 45,000 Hz and above, while minimizing record wear and offer ng superb tracking. Write today for free literature and list of audio-technica dealers nearest you.

AUDIC-TECHNICA U.S., INC. Dept. 104P, 33 Shiawassee Avenue, Fairlawn, Ohio 44313 CIRCLE NO. 6 ON READERS SERVICE CARD



Ever wonder why no other TV/Audio home study school puts its prices in its ads?

Maybe it's because they can't match this value!

No other school gives you complete TV/Audio service training with a big screen 25" diagonal color set and all the electronic instruments you need for under \$1000. Or gives you a choice of five ways to learn, starting

You pay less because NRI passes its savings on to its students.

NRI pays no salesmen. We buy no outside "hobby kits" for our experiments or training kits. NRI designs its own instruments and TV sets... to give you great performance plus real training that you can put to practical use. The result is lower tuition rates and exclusive extras, like including a console TV cabinet (a \$140 extra from other schools).

Nearly 1 million students have come to NRI for home training.

Home study isn't a sideline with NRI. We've been its innovating leader for 60 years. Nearly one million students have enrolled in our many career courses. NRI is one of the few home study schools with a full-time staff of engineers, authors and editors to help you with any problem. NRI graduates will tell you: you can pay more, but you can't buy better training.

as low as \$312... with convenient, inexpensive time payment plans. (Check the difference in interest rates alone!) NRI quotes its prices because we believe you get the top educational value from NRI.

15 Electronic courses available... including digital computer training and complete communications.

Send for the free NRI electronics catalog and check out the full spectrum of courses available, including Color TV, FCC Licensing, Complete Communications Electronics, Computer Electronics, Marine and Aircraft Electronics, Mobile Communications, etc.



Mail the card for your Free NRI catalog. No salesman will call.

AVAILABLE UNDER GI BILL

Check the GI Bill Box on the card for information.




NRI SCHOOLS

McGraw-Hill Continuing Education Center 3939 Wisconsin Avenue, Washington, D.C. 20016

good with 7 kits ... \$312

Or low monthly terms


A basic TV/Audio Servicing Course including 7 training kits for your experiments. You build your own solid-state radio, solid-state volt-ohmmeter, and experimental electronics lab. Includes 65 bite-size lessons (16 on color TV), 15 special reference texts with hundreds of servicing short cuts, tips on setting up your own business, etc. This completely up-to-date course covers black & white and color TV, FM multiplex receivers, public address systems, antennas, radios, tube, transistor and solid-state circuits.

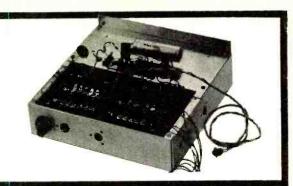

better ...with 11 kits and B/W TV...\$425

Or low monthly terms

A complete course in B&W and Color TV Servicing, including 65 lessons (16 on color TV), 15 special reference texts and 11 training kits. Kits you build include your own solid-state radio, solid-state volt-ohmmeter, experimental electronics lab, plus a 12" diagonal solid-state black & white portable TV...to build and use. At each assembly stage, you learn the theory and the application of that theory in the trouble-shooting of typical solid-state TV sets.

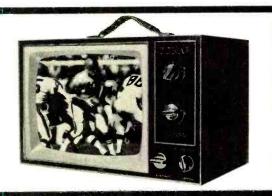

better yet with 12 kits and 19" diag. Color TV...\$695

Or low monthly terms

The same basic 65 lessons and reference texts as before, plus kits and experiments to build a superb solid-state 19" diagonal color TV receiver...complete with rich woodgrain cabinet, and engineered specifically for training by NRI's own engineers and instructors. This handsome set was designed from the chassis up to give you a thorough understanding of circuitry and professional trouble-shooting techniques. You build your own solid-state radio, solid-state volt-ohmmeter, and experimental electronics lab.



best ... with 14 kits and 25" diagonal Color TV...\$995

The ultimate home training in Color TV/Audio servicing with 65 bite-sized lessons, 15 reference texts, and 14 training kits...including kits to build a 25" diagonal Color TV, complete with handsome woodgrain console cabinet; a wide band, solid-state, triggered sweep, service type 5" oscilloscope; TV pattern generator; digital multimeter, solid-state radio, and experimental electronics lab.

This Master course combines theory with practice in fascinating laboratory units. Unlike "hobby kits", the NRI color TV was designed with exclusive "discovery" stages for experimentation and learning. Building the set will give you the confidence and ability to service any color TV set on the market. And you'll have a magnificent set for years of trouble free performance.



Plus Advanced Pro Color...\$535 Or low monthly terms

An advanced Color TV Servicing Course for experienced technicians. 18 color lessons, 5 new "Shop Manuals", and the NRI 19" diagonal solid-state Color TV set are included.

OCTOBER 1974



New Products

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Reader Service Card inside the back cover or write to the manufacturer at the address given.


CONTINENTAL SPECIALTIES BREADBOARD

Continental Specialties Corp. is now marketing the new Proto Board-203, a breadboarding system that consists of special connector-matrix sockets capable of accommodating up to 24 14-pin DIP IC's and a built-in 5-volt, 1-ampere power supply. The power supply is regulated and has protection against short circuits. The Proto Board contains three QT-59S DIP-type sockets, four QT-59B bus-strip sockets. and one QT-47B bus-strip socket. Circuits are breadboarded by plugging component leads and prepared hookup wire into the connector matrix, eliminating the need for soldering. The unit measures 934 in. by 61/2 in. by $2\frac{3}{4}$ in. $(23.5 \times 16.5 \times 7 \text{ cm})$ and weighs 5 lb (2.3 kg). It retails for \$75.

CIRCLE NO. 69 ON READER SERVICE CARD

YAMAHA STEREO FM RECEIVER

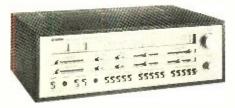The Model CR1000 stereo FM receiver is the top of Yamaha's line. The FM tuner section features a MOSFET front end, an IC i-f amplifier with a seven-stage differential amplifier and six ceramic filters, and a mul-



tiplex demodulator with negative feedback. The preamplifier section includes a microphone amplifier for mixing, two tape record/monitor circuits with dubbing capability, tone controls, and a loudness control. The amplifier section is rated at 75 watts continuous rms power per channel into 8 ohms, rated at less than 0.1 percent IM and THD and 10-100,000 Hz (+0, -1 dB) frequency response. Yamaha's Auto-Touch Tuning system automatically defeats the afc during tuning. The retail price of the receiver is \$850.

CIRCLE NO, 70 ON READER SERVICE CARD

UNGAR DOUBLE-INSULATED SOLDERING IRON

The new double-insulated DI line, from Ungar, features a heater and handle with two-conductor cord set and safety plug.

The entire system is double-insulated to meet the latest safety standards. Four rugged stainless-steel heaters and three heat ranges provide flexibility for different soldering jobs. The handle is molded of durable plastic and incorporates a cool finger grip for operator comfort. The No. 555 double-insulated two-conductor handle accepts thread-in No. 300 series heaters. A 45-watt integral heater with built-in iron-plated chisel tip for heavy duty applications is also available.

CIRCLE NO. 71 ON READER SERVICE CARD KENWOOD STEREO RECEIVER

Direct-coupled, complementary-symmetry output circuits, a power transformer with heat sinks, and a dual protection circuit are three of the features of Kenwood's new Model KR-5400 stereo receiver. The amplifier section is rated at 35 watts rms per channel into 8 ohms, with both THD and ID



values of 0.5%. A front-panel selector switch controls up to three pairs of speaker systems (any two of which can be switched in at a given time) and silences the speakers for headphone listening. The FM tuner sensitivity is 1.9 μV (IHF); capture ratio is 1.5 dB (IHF). The stereo decoder employs an IC phase-locked loop to reduce beat interference and intermodulation distortion. Special input and output terminals are provided for any 4-channel decoder or adapter, as is a special FM DET OUT for future discrete broadcasts. Retail price is \$279.95.

CIRCLE NO. 72 ON READER SERVICE CARD ANTENNA SPECIALISTS MOBILE ANTENNA

A new three-way antenna has been announced by the Antenna Specialists Company. They say that the Model M-267 antenna is designed to offer significantly improved mobile performance over previcus combination CB/AM/FM designs. Featured is a new coupler to reduce insertion losses. and deterioration of AM and FM broadcast reception. The coupler allows use of the single antenna system for both broadcast receiver and CB transceiver without switching or adjustments. On transmit, the antenna system has low VSWR and is designed for cool operation with a power rating safety factor of 20. The single-length, non-telescoping whip unscrews from its waterproof mount for low overhangs, garages, and car washes. Retail price is \$35.60

CIRCLE NO. 73 ON READER SERVICE CARD BOSE 4-CHANNEL PREAMPLIFIER

The Bose Model 4401 is described as an ultra-quiet preamplifier that offers com-

plete 4-channel discrete and matrix capabilities. Signals from all current program sources, both stereo and quadraphonic, can be processed by the preamp. Circuitry for the SQ decoder and the CD-4 demodulator is contained on easily-installed plug-in modules. The preamp features full tape recorder flexibility, with the tone controls and high- and low-cut filters in the circuit to process the signal prior to recording. There are also provisions for using an external equalizer system with the preamp. Specifications include: output impedance 600 ohms; rated output, 2 V rms min; frequency response, 20 Hz to 20 kHz ±0.2 dB; harmonic or IM distortion, less than 0.2 %; hum and noise, -80 dB min. Dimensions are 6" high by 13 1/8" deep. The basic preamp is \$499.00; SQ decoder module, \$74.95; enclosure, \$34.95.

CIRCLE NO. 74 ON READER SERVICE CARD ACOUSTIC RESEARCH SPEAKER SYSTEM


The new π /one from Acoustic Research is a three-way acoustic-suspension speaker system that features a control panel located on the front panel. The control panel has a "woofer environmental control" that can be set to insure proper spectral balance regardless of the location of the speaker, room acoustics, or personal preference. The 0π position provides acoustical balance in a corner setting; 2π is for speakers against a wall; and 4π is for a free-standing position. The control panel also contains a three-level (0, -3, and -6)dB) set equalizer for both the midrange and tweeter drivers. With the midrange and tweeter switches set to 0 dB, brilliance and presence are said to be achieved with a uniformly flat response. The π/one employs a 12" woofer, 1 1/2" dome midrange. and a 34" dome tweeter. Impedance of the system is 8 ohms, and recommended amplifier power is 25 watts rms. Each system weighs 55 lb and measures 14" by 25" by

CIRCLE NO. 75 ON READER SERVICE CARD SIMPSON DIGITAL MULTIMETER

A new digital multimeter, the Model 360 from Simpson Electric, is designed and engineered for a proad spectrum of testing and measuring applications. Handy and



POPULAR ELECTRONICS

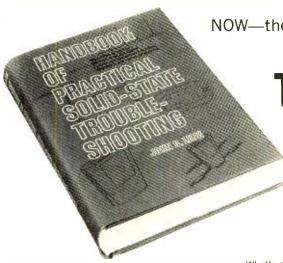

The Handbook of Practical Solid-State Troubleshooting

—yours for just \$2.59!

And you'll also receive a RISK-FREE trial Membership in The Electronics Book Service. (No obligation ever to buy ANY minimum number of books.)

Now you can tackle malfunctioning solid-state circuits and equipment with new speed, ease and accuracy! A broad promise—but one you're sure to agree with when you see the hundreds of techniques available to you in John D. Lenk's HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING.

This book, now selling actively at \$13.95, is one you should own. It is also typical of the kind of practical books offered to members of the *Electronics Book Service*. And you may have a copy for a token price of \$2.59, as a means of introducing you—on a no-obligation basis—to a trial membership in the *Electronics Book Service*.

Covering a complete cross-section of solidstate circuits and equipment including Basic Circuits, Home Entertainment, Laboratory and Industrial Instruments and Digital Equipment and Systems, this conveniently indexed book gives you shortcut techniques for:

- Finding out how to deal with any specific problem area—determining primary symptoms of poor performance
- Discovering the right way of tracking down and isolating the problem to a particular circuit in trouble
- Localizing the trouble right down to the functional circuit unit itself

With the instant help of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING, you'll rapidly become adept at servicing even the most complex solid-state circuits and components! And without ever relying on time-consuming trial and error!

Through simple explanations and detailed illustrations, all the troubleshooting techniques in this book are made easy for you. And they cover just about every malfunction you might encounter in solid-state electronics. For instance, in the big section on troubleshooting TV receivers, you'll find techniques for quickly locating the source of such problems as:

No Sound and No Picture Raster . . . No Sound, No Picture Raster, and Transformer Buzzing . . . Distorted Sound and No Picture Raster . . . Picture Pulling and Excessive Vertical Height . . Dark Screen . . . Picture Overscan . . . Narrow Picture . . . Foldback or Foldover . . . Nonlinear Horizontal Display . . . and over 40 more possible malfunctions in any circuit!

What's more—to contribute to your speed and proficiency—more than 180 illustrations clearly show you the tests and troubleshooting procedures for:

- In-and Out-Curcuit Transistors
- Amplifiers, Inverters and Phase Splitters
- Video Amplifier Circuits
- Diodes
- Delays
- · Pulse Delay, Time and Width
- Sound IF and Audio Circuits
- Multivibrators
- Gate Circuits
- RF Tuners and AGC Circuits
- Basic Power Supplies

The depth and breadth of coverage you'll find in HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING is unmatched anywhere—and its clearly outlined techniques will give you new speed, ease and accuracy in troubleshooting all kinds of solid-state circuits and equipment!

A point of significance to you: the Electronic Book Service has NO minimum purchase requirements, as most book clubs do. Once you have paid \$2.59 for your copy of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING, you need purchase no further selections.

So act now. Just mail the coupon below to get your copy of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING for just \$2.59—and to receive all the benefits of membership in the *Electronics Book Service* on a RISK-FREE trial basis. *Send the coupon right now!*

What membership in the ELECTRONICS BOOK SERVICE means to you

- 1. When you enroll as a member, you will receive at a token price (plus postage and handling with tax where applicable) the introductory selection described elsewhere in this offer.
- 2. Thereafter you will receive approximately once a month (but no more than 13 times per year), a free bulletin describing the forthcoming selection. If you want the selection, no further action is required . . . it will be shipped to you automatically. If you don't want it, just return the card that accompanies the bulletin.
- 3. You have 10 days to decide whether you want the selection or not. Return the card so we receive it no later than the date specified. If you don't have 10 days to answer and receive an unwanted selection, return it at our expense.
- **4.** Any selection you decide to buy will be billed to you at the exclusive member's price, which saves you at least 15% off the publisher's regular list price.

(Your regular bulletin also describes a number of alternate selections, also available to you at the special member's prices.)

5. There is no obligation to purchase any minimum number of selections. Your only obligation is the token price you pay for your introductory selection. You may purchase as many or as few as you wish, and you will be under no pressure to buy any more. And you may resign at any time without obligation, once you have paid for your introductory selection.

ELECTRONICS	BOOK	SERVICE
Done CCE1 M1/0)		

Dept. 6651-M1(8) Englewood Cliffs, New Jersey 07632

Please enroll me in Electronics Book Service on a risk-free trial basis. I am to receive all announcements, free of charge, and will be entitled to full privileges as a Member without obligation to buy any specific number of club selections. As my first selection under this trial membership, send me the HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING for only \$2.59.

Name			
Address			
City	State	Zip	

rugged enough for field use, it is claimed to have the accuracy and flexibility required of a good general-purpose laboratory instrument. The 31/2-digit non-blinking LED display is 0.33-in. high. Polarity selection (both + and - on the display) is automatic, as is overrange indication. A special analog indicator just below the display is useful for scanning nulls and peaks. The DMM features 29 ac, dc (voltage and current), and resistance ranges, including a low-power ohms function. The Model 360 operates on rechargeable batteries or ac line power. A wide range of accessories is available, including carrying case and a variety of r-f. high-voltage, and other special probes.

CIRCLE NO. 76 ON READER SERVICE CARD BIC AUTOMATIC PROGRAMMED TURNTABLE


The Model 980 is one of two belt-driven "programmed" 33- and 45-rpm turntables marketed by British Industries Co. It uses a low-speed synchronous motor with 5-Hz fundamental vibration frequency. It is also



the only automatic turntable with a record-changing capability using a solidstate electronic frequency module to adjust speed and featuring a ± 3-percent pitch range. A built-in Programmer can be set to repeat a single record up to six times before automatic shut-off and is also used for automatically playing up to six different records. Shut-off is manually programmed, rather than sensed by the automatic spindle, eliminating one of the major causes of changer malfunction. Critical styles pressure and anti-skating adjustments are performed by tandem controls which can be operated separately or simultaneously. Other features include: a "feather-touch" cycling button, rubber shock mounts that minimize feedback problems, adjustablerate ascent and descent cueing, etc. Retail price is \$199.95. A walnut wood or black molded base and a hinged dust cover are available.

CIRCLE NO. 77 ON READER SERVICE CARD METAL CIRCUIT SYSTEMS PC MATERIALS

A new nonconducting metal sheet for printed circuitry has been developed by Metal Circuit Systems. To make pc boards, a design is drawn or scribed directly on the surface of the pc material, rendering a working board. Because pressure is all that is required, there is a substantial saving in time, labor, and materials. Without using a new board, circuits can be erased for making new designs. A more economical ver-

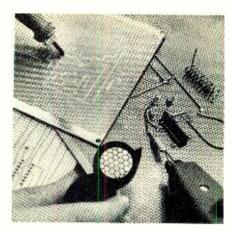

sion for direct wiring purposes, rather than printed circuitry, is also available. Since the metal sheet is nonconducting, components and wiring can be spot soldered at random, independent from adjacent areas of the board.

CIRCLE NO. 78 ON READER SERVICE CARD

OUAL CASSETTE DECK

Long known as a manufacturer of quality automatic record players, Dual is now in the cassette deck business with the introduction of the Model 901. Automatic reverse, continuous playback, bi-directional recording, and automatic bias switching for pre-coded standard and chromiumdioxide tape formulations are provided. A built-in oscillator permits the Dolby noise reduction system to be calibrated for any tape formulation. The deck's recording level meters are said to be designed with the ballistics of broadcast-quality VU meters so that the pointers give precise indications of the recording level. Others features include a continuous-pole/ synchronous motor, precision belt-driven system, intermode switching without the use of the stop switch, and alc. Response is 20 Hz to 14 kHz ± 1.5 dB. Wow and flutter are 0.09% Wrms. Retail price is \$4.50.

CIRCLE NO. 79 ON READER SERVICE CARD

DYNACO HIGH-POWER STEREO AMPLIFIER

You can get 200 watts rms/channel or 600 watts rms in mono, both into 8-ohm loads. from Dynaco's new Stereo 400 power amplifier. To protect both the amplifier and driven speaker systems, Dynaco has incorporated into the amplifier several safety features. The Dynaguard TM, an exclusive dynamic power limiting circuit, provides speaker protection in direct proportion to the damage potential of the signal. A delay circuit eliminates turn-on thumps, and relay protection is provided against as little as 0.5 volt dc at the output. Volt-amp limiting protects the output stages against reactive and low-impedance loads, and separate thermal sensors are used for each channel. Basic amplifier can be equipped with a forced-air cooling fan and an optional dB-output metering system. The Stereo 400 is available in both kit and factory-wired forms.

CIRCLE NO. 80 ON READER SERVICE CARD


eed our log.




Your communications "stakes" are on the table, when you need CB 2-way radio. Play it safe with any one of the experience-proven veterans from PACE—the largest selection of handheld CB transceivers in the industry. All are guaranteed and all have PACE's U.S. Factory Service Program. See your PACE Dealer soon or write for new full product line catalog.

((P)) PACE COMMUNICATIONS

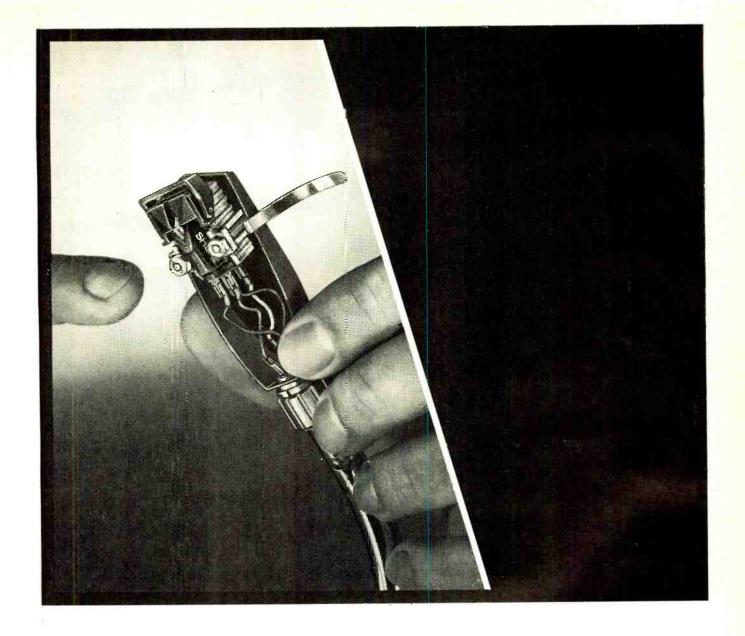Division of Pathcom Inc., 24049 S. Frampton Ave., Harbor City, Calif. 90710 EXPORT: 2200 Shames Drive, Westbury, New York 11590. Available in Canada. CIRCLE NO. 28 ON READERS SERVICE CARD



The heart of hi-fi.

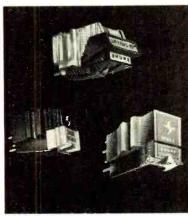

Beauty is truth, truth beauty. The fact is that all too few music lovers realize that while certain high fidelity components can be less than best, there is one component that cannot endure a sacrifice in quality: the cartridge. Because the hi-fi cartridge functions as the source of sound (the point at which the recording is linked with the balance of the hi-fi system), its role is absolutely critical. Just as the camera can be no better than its lens, the finest hi-fi system in the world cannot compensate for an inferior cartridge. Suggestion: For a startling insight into the role of the cartridge in the overall hi-fi system, and a breathtaking re-creation of your favorite recording, see your nearby Shure cartridge dealer. He'll introduce you to the Shure cartridge that is correct for your system and your checkbook. Or, next best, send for our brochure:

Shure Brothers Inc.

222 Hartrey Ave., Evanston, III. 60204 In Canada: A. C. Simmonds & Sons Limited

SHURE


OCTOBER 1974

CIRCLE NO. 35 ON READERS SERVICE CARD

free

The "NEW LOOK" **1975**

LAFAYETTE
Radio Electronics
CATALOG

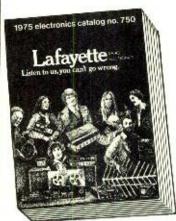

The ONLY Nationally Distributed Full-line Catalog with a Major Showing of the Newest NAME-BRAND electronics products for 1975.

FREE SEND TODAY

SAVE on exclusive Lafayette Products plus MAJOR BRANDS

Stereo and 4-Channel Systems - Tape Equipment - Car Stereo - CB and Ham Gear - Police/Public Service Receivers - Antennas - Cameras - TV - PA and Test Equipment - Musical Instruments and Amplifiers - Books - Electronic Ca

Lafayette
Listen to us, you

can't go wrong.

Dept. 35104

Dept. 35104
Lafayette Radio Electronics
111 Jericho Tpke., Syosset, L.I., N.Y. 11791
Send me your FREE 1975 Catalog
Name Apt
Street
City State
Zip
Send a 1975 Catalog to my friend
Name Apt
Street
City State
Zip

CIRCLE NO. 24 ON READERS SERVICE CARD



New Literature

BROOKSTONE "HARD-TO-FIND" TOOLS CATALOG

The Brookstone Co. has just published its second 1974 catalog of hard-to-find tools (and other things). This 60-page catalog features 76 new products in addition to the thousands of other very useful items listed in previous editions. The listings include unusual craftsmen's hand tools and small power tools, as well as a wide array of devices, especially applicable to the electronics field. Address: Brookstone Co., Brookstone Bldg., Peterborough, NH 03458.

DYNASCAN "COBRA" CB BROCHURE

Highlighted in the four-color "COBRA" brochure from Dynascan are eight CB transceivers. Four AM models (three mobiles and one base) and four SSB/AM models (two mobiles and two bases) are described, and individual features are detailed. Address: Dynascan Corp., 1801 W. Belle Plaine Ave., Chicago, IL 60613.

BSR SOUND PRODUCTS BROCHURE

Brochure No. MD 11179 from BSR describes nine record players, a "Quasi-Quad" 4-channel synthesizer, two cartridge tape players, and two graphic equalizers. This colorful brochure contains a table of turntable features, brief descriptions of all products listed, and a glossary of BSR turntable features. Address: BSR (USA) Ltd., Blauvelt, NY 10913.

CEI TIME PRODUCTS CATALOG

Listed and described in Caringella Electronics' new time products catalog are four all-electronic digital clocks and a standard time receiver. The clocks range from a 1-digit desk model to a 1-digit wall model to a 6-digit crystal-oscillator-driven model, ending with a giant 6-digit crystal-controlled model featuring 3½" (8.9-cm) numerals. The receiver tunes WWV on 5, 10, and 15 MHz. Prices are given for both assembled and kit-form units. Address: Caringella Electronics, Inc., P.O. Box 327, Upland, CA 91786.

RCA ELECTRONICS INSTRUMENTS CATALOG

RCA's Electronic Instruments Catalog No. 1 lists and describes a wide range of test gear for servicing, industrial maintenance, laboratories, schools, and safety tests. The catalog is broken down into instrument types and includes multimeters, safety

measurement devices, dc power supplies, R/C substitution box, oscilloscopes, color and signal generators, etc. Along with the instrument descriptions, the 24-page catalog also provides brief descriptions of accessories. Prices are given for all items listed. Address: RCA Electronic Instruments, 415 South Fifth St., Harrison, NJ 07029.

SOLITRON SEMICONDUCTORS

A new condensed catalog covers Solitron's Florida division's complete line of power transistors, hybrids and diodes. The 56-page book, printed in two colors, provides a quick reference guide to the company's discrete power devices, hybrid power regulators and Schottky diodes. Package illustrations and dimension drawings are also given for reference. Address: Solitron Devices, Inc., 1177 Blue Heron Blvd., Riviera Beach, Fla. 33404.

AMPHENOL CONNECTOR CATALOG

A 52-page general catalog (No. GL-4) that describes the company's broad lines of r-f, coaxial, and microphone connectors and tube/relay sockets and plugs is available from Amphenol. The catalog fully describes and illustrates all listings. It features a comprehensive page-referencing index to all components described. Altogether, three separate indexes are provided to help users quickly locate required components. Also included is a glossary of often-used connector terms. Address: Amphenol Sales Div., Bunker Ramo Corp., 2875 S. 25 Ave., Broadview, IL 60153.

GC ELECTRONICS PROJECTS BOOK

Thirteen easily assembled electronic projects are featured in the new Fascinating Electronic Projects book (No. FR-174) available from GC Electronics. The book contains schematics, instructions on how to build such devices as an emergency lamp flasher, metal locator, rechargeable lantern, lie detector, etc. Most of the projects are battery operated, have solid-state design, and can be built for less than \$10. The book also contains an introduction that offers valuable construction tips for electronic project construction. For a copy of book No. FR-174, send \$1.25 to:GC Electronics, Div. of Hydrometals, Inc., 400 S. Wyman, Rockford, IL 61101.

INTERSIL TRANSISTOR REFERENCE GUIDE


Intersil has just published a comprehensive 24-page guide to bipolar transistors and FET's. Called the "Intersil Bipolar and Field Effect Transistor Cross Reference Guide," the publication lists 1162 industry part numbers in alphanumeric order, with 2N and 3N numbers, followed by the house numbers of all major suppliers. For each part listed, there is a description of the transistor and a brief indication of its typical application. Address:Intersil, Inc., 10900 N. Tantau Ave., Cupertino, CA 95014.

POPULAR ELECTRONICS

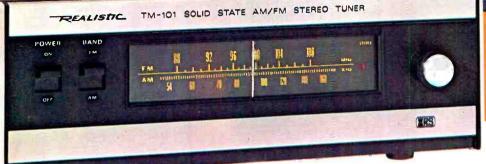there's only one thing cheap about these new Realistic stereo components...the







5095

FREE New 1975 Radio Shack Catalog

OVER 2000 PRODUCTS EXCLUSIVES ON EVERY PAGE BEAUTIFUL FULL COLOR

Stereo • Quadraphonic • Phonographs
TV Antennas • Radios • Citizens Band
Kits • Recorders • Tape • Tools
Auto Tune-Up • Electronic Parts
Test Instruments • More!

164 pages of the finest in home and hobby electronics. Respected names like Realistic, Micronta, Archer, Science Fair—and they're available only at Radio Shack stores and dealers nationwide! See what's really new in electronics by sending for this exciting catalog.



SEND FOR YOURS TODAY! FILL OUT COUPON BELOW

-	
1975 Catalog	Mail to Radio Shack, P. O. Box 1052, 433 Ft. Worth, Texas 76101. (Please print.)
Name	Apt. No
Street	
City	
State	ZIP

Realistic SA-101 Stereo Amplifier. Inside the handsome walnut-grain wood case is an ITL/OTL amplifier with plenty of power for compact speakers. It's versatile too, with inputs for a magnetic or ceramic phono, tuner and tape. And there are separate volume, balance and tone controls, a speaker in/out switch, and a stereo headphone jack for private listening. U.L. listed. #31-1983.

Realistic TM-101 Stereo Tuner. Our lowest priced tuner, but it pulls in FM stereo and AM the way you like it. You'll hear more stations and less noise thanks to three-ganged FM tuning, ceramic filter, advanced multiplex IC and external FM antenna terminals. Other features include a slide-rule dial, stereo beacon and walnut-grain wood case. It's a perfect "system mate" for the SA-101. U.L. listed. There's only one place you can find it . . . Radio Shack! #31-1984.

Save \$34.80 on a Complete System





Master Charge or Bank Americard at participating stores. Radio Shaek

A TANDY CORPORATION COMPANY

OVER 3000 STORES • 50 STATES • 8 COUNTRIES


Retail prices may vary at individual stores

Sylvania goes



one better.

We give you two TVs instead of one.

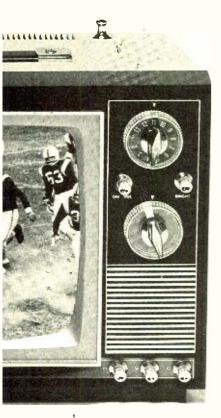

With Sylvania's Master TV Career Program you get not just one but *two* TV sets to build. Color *and* Black & White. Both Solid State.

With all Sylvania Career Programs you get our exclusive Autotext method of instruction, a modern, step-by-step approach to learning, which gets you through the basics of electronics quickly and easily.

An optional Cassette System, a technique that adds an extra dimension to learning. It's almost like having an instructor right in your own home. As you play the tapes, he'll guide you through your lessons, explaining as you read, going over schematics and reinforcing everything you learn!

Plus a choice of Programs that can lead to any number of career goals. In TV, communications, automation, digital and solid-state electronics. And in fields you haven't even dreamed of.

Plus specialized advanced training and carefully-engineered Project Kits for that "hands-on" training you need to make it in the world of electronics.

Throughout your training, Sylvania makes that extra effort to go one better.

Send the card or mail in coupon today for our FREE Catalog. And go with Sylvania.

SYLVANIA Technical Schools Home Study Division694-410-0 Sylvania Technical Systems, Inc. 909 Third Avenue New York, N.Y. 10022

Please send meFREE illustrated career catalog. I understand that I am underno obligation.

Name _____

Address _____

City_____

State Zip ____

Age_____ Veterans: Check here □

GIE SYLVANIA

Cabinet optional.



Stereo Scene

By Ralph Hodges

PROMISES FOR 1975

HE June Consumer Electronics Show is now well established as the principal showcase for the high-fidelity industry and its annual introductions of new products. It is a trade-only show, functioning primarily to allow dealers to select their lines of merchandise for the fall season. But the press is also invited to attend, which it does in droves, since most of the big audio stories for the coming six months are there in one form or another—often as advance prototypes

on display in the exhibition booths, or sometimes just as twinkles in the eyes of product managers who are usually not too reluctant to talk about future plans.

The greatest drawback of the show is its sheer size, which puts mental and physical endurance to a severe test. I'm never confident, after leaving, that I was able to see all I should have, and the subsequent weeks usually prove me right. But in any case, the following is a selective compendium of what I

did see this year that might, in my estimation, be of mild or passionate interest to readers of this column. Apologies in advance to those readers (and manufacturers) who feel their interests have been slighted, should that be the case.

Logic. Last year, when a host of manufacturers introduced four-channel receivers with built-in CD-4, SQ, and QS (or RM, as it is frequently labeled) facilities, there were grumbles about the lack of sophistication in the SQ and QS matrix circuits, which tended to be quite rudimentary. So it remained to be seen what steps, if any, would be taken this year to elevate the status of the matrix decoders.

Good news. In the interim, SQ IC's with logic became available from several sources, and hence Fisher and Kenwood both appeared at the show with CD-4/SQ full-logic receivers. Lafayette, Pilot, and Sherwood also offer models with full-logic SQ, but without CD-4. Marantz, meanwhile, have retained the pocket on their receivers' undersides into which an optional decoder module—full-logic SQ or QS with Vario-Matrix are offered at the present time—can be plugged.

SQ full logic currently exists in two forms: wave-matching with front-back and wave-matching with variable blend. Wave-matching and front-back are both gain-riding systems, channels into which leakage information has crept (and which are not carrying important information of their own at the moment) are attenuated by the logic action. Variable-blend works by logic-controlled mixing of channels in which leakage signals are mutually out of phase, thereby achieving electrical cancellation. (The channels' proper information is not out of phase, and thus is not reduced.) Also of interest: the SQ IC packages incorporate voltage-controlled amplifiers. This means that a single potentiometer can serve as a master volume control for all four channels. Since the potentiometer does not handle any audio, the arrangement is ideal for remote-control applications—a feature on which Fisher has already capitalized.

Frequency Synthesizing. For some years the Heath Model 1510 has been the only frequency-synthesizing FM tuner on the market. Those who favor the principle (providing virtually flawless tuning accuracy) will be glad



THE EASIEST MONEY YOU'LL EVER MAKE...BELIEVE IT OR NOT! IT'S TRUE

"I MADE \$35,000 IN JUST 1 DAY AT HOME IN BED WITH THE FLU

By simply putting my successful money method in action I'm making thousands of dollars every week whether I work or not...

I WILL QUICKLY TEACH ANY MAN OR WOMAN MY PROVEN "EASY MONEY SECRET" OF STARTING FROM SCRATCH AND MAKING A FORTUNE PRACTICALLY OVERNIGHT!

OFFICIAL PROOF OF RESULTS CERTIFIED NOTORIZED AND DOCUMENTED **LEGAL SWORN AFFIDAVIT:**

TO WHOM IT MAY CONCERN.

As the Accountant for Unique Ideas, Inc., Mr. Ernie Tucker, Pres., I attest to the fact that he earned Thirty Five Thousand Dollars in a single day and presently averages in the thousands every week

Personally I've always found him to be both a Successful and Honest Man I Certify that all of these statements are true

Certified Public Accountant's Name Available upon Request Notary Public

Bank Reference: Chelsea National Bank

825 Seventh Ave. New York, N.Y. 10019

ACRES VIDEO COMPA

Harry Shalita Dec. 3

1973



AN HONEST NO NONSENSE WAY TO RICHES IT ACTUALLY WORKS FOR YOU

No equipment to buy or lease, no hustling your friends to buy junk merchandise and no books or correspondence course required.

DEFINITELY NOT A CON GAME, FRANCHISE, INVESTMENT SCHEME OR GIMMICK

YOU DON'T NEED MONEY TO MAKE MONEY

Obviously you were not born rich so what? 85% of the men and women who are rich today started with very little money and had only average education, so why not be honest with yourself and stop using lame excuses, stand up and fact that the only real difference between you and thousands rich Americans is that they discovered the right moves to make and you did not!

YOU GET RICH MAKING "THE RIGHT MOVES"

I've proven this to be true despite the fact that I was born poor and barely squeaked through high school. I still made a fortune in just a short period by making the right moves and I'll show you exactly how I did it.

But why am I so anxious to reveal to you my secret money making method? Surely there's more to it than because I enjoy helping others share in the rich good life as I have but frankly I expect to profit at least two hundred thousand dollars, maybe more, from the publishing of these ads in nationally famous magazines and newspapers.

STOP WASTING PRECIOUS YEARS

I should know, I wasted more good years than I care to remember, before I finally discovered the secret of making money, I stayed up to my neck in debt, bounced around from one eight hour dead end job to another. Just working, waiting and wishing for a great fortune to fall in my lap. I got married, became a proud father at a young age. I worked in a toy factory for a short time and peddled cosmetics from door to door. but everything I tried my hands at failed because I didn't know the right moves make. This only happened to me twelve years ago. No doubt there are millions who are suffering this agonizing torment now

REVEALING: THE RICH MAN'S SECRET MONEY MAKING METHOD It's true that most rich persons keep

their money making secrets to themselves, seldom sharing it with others, but fortunately I met several unusually fair minded rich men who were so impressed with my ambition to get rich that they agreed to teach me the secret money making techniques that their many years of making millions had taught them, providing I would virtually work for them at least one year. I eagerly jumped at the opportunity to gain this valuable knowledge and said yes to their generous proposition. So for one year I listened and watched very closely, until financial wizards made thousands of dollars every single day. I'll always be most grateful to these men for teaching me their fast and easy money making secrets. It didn't even matter that I was practically pennyless when I first put these methods into action

SUDDENLY IT STARTED MAKING MONEY FOR ME

At first it was unbelievable ... I paid off all my bills and my wealth continued to multiply. Huge sums of cash poured in so fast that I was forced to employ a full time bookkeeper and retain a corporation attorney, accountant and tax expert to help manage my prosperous financial affairs.

We had investments, property, stocks, money in the bank and can afford most anything we want. My family and I enjoyed our wealth and success. We were very proud of our accomplishments and it was our secret of making the right easy moves that made it all happen.

THIS IS YOUR CHANCE DON'T BLOW IT

It's a better chance than I had. If you're really serious I'm willing to share my secret. Surely I can afford to give it to you free of charge, but I won't, why should I give you something for nothing? Instead I'm going to ask you to send me ten dollars for sharing my secret. What's more, I want you to know that I intend to make a fair profit

the information I mail you, why not? If I can show you how to make more money than you ever made in your life why should you care if I make a profit? Remember what I'm giving you for only ten dollars cost me 12 years to master. Even more important you get certified and documented proof beyond the slightest doubt that my method can make a fortune, this is why I can offer you the strongest legally binding guarantee possible!! A guarantee so incredible that you'll probably think it sounds too good to be true.

UNUSUAL \$1000 GUARANTEE

This is a legal and binding guarantee from me to you. The information I'll send you can actually put thousands of dollars in your pocket. But this is my pledge to you, after just 10 days if you don't agree my secret method is worth at least \$1000.00 in cash to you (one hundred times the ten dollars you pay) send it back and I'll rush a full refund, including your 8¢ postage. You take absolutely no-risk -not even the price of a stamp.

-pacaeseseseseseseseseseseseseses **GET READY TO GET RICH**

Every single day my method can bring you more cash. You'll never again need to borrow, budget or ask anyone for credit. You'll be proudly independent. You can enjoy those luxuries you've always dreamed about, but never could afford. Sound impossible? But it's not, you only need a serious belief in my proven method, very small capital and enough ambition to give it a try. Remember "nothing ventured nothing gained" and there's absolutely no way you can lose.

JOIN THOUSANDS WHO ENJOY THE RICH GOOD LIFE:

made 2 thousand dollars the first month using your money making method. I'm glad I took a chance." Sincerely, Ed K., N.Y. You can easily learn what I taught him and now his money worries are over, so why not take advantage of this rewarding opportunity. Any news of good fortune travels fast, already thousands of just average men and women have benefited from my concept, you will too. But I will not promise you'll make as much money as fast as I have, yet, it's possible you'll make a lot more even faster

YOU CAN LIVE HIGH ON THE HOG AND DO LESS WORK ...

I'll show you how to stop breaking your back to make ends meet and start using your head to get easy riches. If you're seriously fed up with being treated like a hard working stiff while others enjoy the rich good life, then don't pass up this opportunity—you risk absolutely nothing-not even the price of a stamp.

MAKE THE RIGHT MOVE NOW

RUSH ORDER COUPON Ernie Tucker, Pres Unique Ideas, Inc. Dept. PE-O 1674 Broadway New York, N.Y. 10019

Yes count me in on your \$1000 guarantee offer. I enclose \$10. Rush your proven easy money method. I understand that it has been officially certified, notorized and documented. If I don't agree it can actually put \$1000 or more in my pocket within 10 days can return it for a full refund, including my 10¢ postage. There is no risk on my part.

Name	
Address	
City	
01.1.	Zin

CIRCLE NO. 39 ON READERS SERVICE CARD

to learn of two new products in the running: the Kenwood 700-T and the Scott T33S. The Scott unit is a redesign of a model offered some years back. It retains the digital readout and the coded card system the Heath tuner also employs. Kenwood, on the other hand, feels the consumer will be more comfortable with a conventional tuning dial. It is precisely calibrated, however, and it is actually twice as long as it appears, since throwing a switch displays the frequencies of either the lower or upper half of the FM band on the dial face.

Yamaha, incidentally, has introduced what is called the lowest distortion FM tuner in the world. For stereo reception, typical rated distortion is well below 0.1 per cent. It's next to impossible to find an FM signal generator that can match such a figure.

Signal Processors. The term "preamplifier" is becoming inadequate to describe the latest generation of control equipment, whose functions often go considerably beyond providing adjustable gain with low noise and distortion. Infinity's new preamp, still a prototype, has a correlator-type single-pass noise reduction system at present. It may be offered with unique suppressor for record noise (scratches, etc.), employing an audio delay line. A new equalizer shown by Technics, also a prototype, operates in twelve bands. with each band continuously variable in "Q" (essentially, effective bandwidth) and center frequency. SAE's Mark 1XB preamplifier incorporates a seven-band equalizer. And a number of companies have come up with some interesting preamplifier controls, such as front-panels switches that alter the input characteristics of the magnetic-phono sections.

A new Dynaco product is always an event. The PAT-5 preamplifier, besides featuring redesigned phono and tone-control sections, has been especially designed for use with superpower amplifiers, and employs heavy-duty power and speaker switches. Four-channel preamplifiers are still relatively rare, but Bose now offers one (Model 4401) with built-in full-logic SQ, and BGW will shortly have a four-channel unit with comprehensive switching and equalization facilities. Marantz's Model 3800 stereo preamp has built-in Dolby B noise reduction circuits.

Power Amplifiers. Amplifiers delivering more than 100 watts per channel are becoming pretty commonplace now. The focus of attention has therefore turned to new types of amplifiers, with the FET designs developed by Sony and Yamaha looming large in this category. FET's are inherently lower in certain types of distortion than bipolar transistors, and the new power FET's seem to offer some advantages in terms of reliability as well. Great claims are being made for the audible superiority of FET output devices by the companies involved, and it will be interesting to see how these pan out. Rated power outputs are 80 watts per channel for the Sony unit (Model TA-8650 integrated stereo amplifier) and 150 watts per channel for the Yamaha CM-5000X power amp.

Infinity is on the point of bringing out a Class D "switching" power amplifier. The most obviously advantageous features of Class D operation (employing digital techniques with a duty cycle of, in this case, 500 kHz) is less heat buildup, and the possibility of using a high-frequency power supply stepped up considerably from the rate of the 60-Hz power line. This results in a very compact amplifier—17 x 11 x 3 inches—capable of 250 watts per channel.

Speaker Systems. The numbers of speaker systems on the market at any given moment always exceed the space available to describe them, so I have to be very selective here. First I'd like to mention the Dahlquist DQ-10. which made its initial appearance at the show this year. The DQ-10 closely resembles the Quad electrostatic speaker, and in this instance imitation is a very sincere form of flattery. Although the DQ-10 employs all dynamic drivers, the electrostatic is its acoustic model. Paramount in the design considerations is the reduction of wavelength-associated diffraction effects from enclosure surfaces and edges, and the elimination of timedelay effects between its five drivers. I mention this because these are "hot" issues among speaker designers today. For anyone looking for a speaker in the close-to-\$400 price bracket this one is worth a listen.

Rectilinear has two new models, the 5 and 7, which are said to be highly efficient. The new Technics speakers, comprising four models, also made their first and very gratifying appearance at the show. Other systems that I

was not able to hear but heard about are: the JBL L65 "Jubal," with a new wide-dispersion compression tweeter; the latest in Altec's Stonehenge series, the Model III, employing a single coaxial driver; the Leslie Model DVX-580, a design with dipole radiation characteristics that can be aimed at any part of the listening room; and the Philips Motional-Feedback speakers. The Philips feedback loop, involving only the woofer, uses a motionsensing transducer near the woofer voice coil. The output of the transducer is routed back to the input of the power amplifier (built into the speaker cabinet) where it is employed as a conventional negative-feedback signal to "condition" the audio signal to the woofer's characteristics.

The unique Heil woofer, discussed in some detail in the June installment of this column, will reportedly be ready in the early autumn. It is, if anything, even smaller than I reported then, and it will certainly have some impact on future speaker-system design if it proves successful.

The Acoustic Research people have developed new versions of their venerable dome midrange and tweeter drivers. Reportedly these are capable of significantly more acoustic output. The first product in which they'll be available—the AR π /one—has calibrated level controls meant to suit various room placements.

Record Players. BIC, which nominally stands for British Industries Corp., has introduced a line of impressive American-made automatic multiple-play turntables—the only changers in the hi-fi component field using belt drive.

Otherwise, most of the action in record players is in the area of single-play units, which are becoming increasingly popular. Dual now offers the Model 601, a belt-drive version of the direct-drive 701. Technics has several new models, all of them direct-drive, and Pioneer has added three single-play units, with the direct-drive Model PL-71 leading the list

Turntables employing magnetic suspensions have been few, far between, and not particularly well-received. This year, Stanton and Teac are offering such units, the Teac being direct driven and the Stanton featuring belt drive. I think it can be safely assumed that the troubles afflicting earlier magnetic-suspension designs

have been corrected in these newer products.

There appears to be a trend in Europe towards automation—as exemplified by the Philips GA-209 and B&O 4002. Both of these single-play turntables attempt to come as close as possible to single-pushbutton operation. The Philips machine has three motors to perform the chores of cueing, tone-arm cycling, and platter drive. The B&O 4002, with a remarkably sophisticated straight-line-tracking tonearm, has more features and automatic safeguards than can be listed here, and is probably, for the present, the most elaborate record player now available.

Tape Decks. If you have become jaded with ordinary four-channel tape decks featuring track synchronization, 15-ips operation, 101/2-inch reels, and flawless solenoid-actuated controls, the Teac A-7340 is the next frontier. In this model the transport and electronics are entirely separate, the latter having been turned into an elaborate eight-channels-in, fourchannnels-out mixer with balanced microphone inputs, external processor loops, and peak-indicating LED's for low, middle and high frequencies augmenting the four VU meters. Dokorder's Model 1140 is not quite so flexible, but it does feature an easyto-use system for bias adjustment. Tandberg's Model 10X, with three tape speeds, is, I believe, the first machine with the 15-ips tape speed and 101/2-inch reels to offer Dolby B-Type noise reduction.


Developments in the cassette format surge forward, as always. The most far-reaching innovation of the year is likely to be the double-layer tapes from 3M (Scotch) and Sony. Generically termed "Ferri-Chrome" tapes (two oxide layers, the bottom being ferric oxide, the top chromium dioxide), they appear to provide significant advantages in terms of sensitivity and overload headroom. Machines optimized for their use are just beginning to appear, but since compatibility with FeCr tape is merely a matter of bias and equalization adjustment, no alteration of cassetteequipment design will have to be involved.

As for cassette equipment, it looks as though the difficult technology of three-head cassette-deck design (with separate heads for erase, record, and playback, to permit off-the-tape

monitoring) is finally being coped with, if the Sony TC-177SD and Dokorder MK-60 are any indication. Reports have it that the Sony is a very viable three-head design. On the other hand, Nakamichi Research, which pioneered three-head cassette decks, has introduced a pair of two-head units, the Model 500, and its portable equivalent, the Model 550. The Nakamichi machines share two important features: unusually high headroom before high-frequency tape saturation (rated approximately 4 dB above other machines at 10,000 Hz); and recording-level meters (peakreading) with a range of 45 dB. This latter would enable the user to actually observe the basic noise level of the program source while recording, inmost cases.

Whether you consider them merely a styling exercise or a genuine boon for convenience of installation, frontloading cassette decks are beginning to appear thick and fast. In addition to the handsome Pioneer Model CT-F7171, introduced shortly before the show, there are similar decks from Concord, Sony, and Technics. Several of these units incorporate solenoid transport controls; while the ones that don't have that feature, do have switch mechanisms with ample mechanical advantage to provide light-touch operation. In general, these products have panel dimensions matching those of other electronic components in their respective manufacturer's line. Complete control access from the front facilitates stacking the decks with amplifiers and tuner, or even flush-mounting them in equipment cabinets.

In passing, I should make some mention of the rapid developments taking place in the eight-track tape field. Why any serious recordist should want to work with eight-track is beyond me, but if he does, he now has Dolbyized machines from AKAI and 3M (Wollensak), as well as an ANRSequipped model from JVC. The latest offering for the quadraphonic enthusiast is the Model ARS-858 fourchannel recorder from Technics. But most important of all, new tapes are becoming available for eight-track recording, the first of which is the Scotch "Classic" cartridge. If eighttrack is ever to rise to the stature of cassettes, it's likely that new tape types, along with other tape refinements, are going to have to lead the

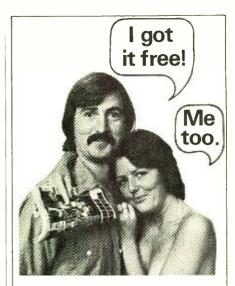

I, Dick Blake, sent off to the Warehouse Sound Co. and quickly received a full-color catalog of stereo components and complete music systems. I testify that they carry every major brand and offer super discounts! Furthermore, if you'll include \$1 for postage, those great people will also send either one of the following: their new 64-page catalog of professional products for musicians, or the 1975 edition of the Music Machine Almanac, which is a 185-page institutional guide to stereo equipment, complete with photos, prices, and specifications for over 40 brands! Sells on the newsstands for 1.95 - soit's a good deal. Do it today!

> WAREHOUSE SOUND CO. BOX S SAN LUIS OBISPO CA. 93405 (805) 543-2330

WARE	HOU	ise
SOU	ND	Co.

Railroad Square, Box S San Luis Obispo, CA. 93405
(805) 543-2330
name
address
city/state
zip
Also enclosed is \$1.00 for: (check one)
Professional Products Catalog

1975 Music Machine Almanac

116HIGHTS

New ASCII Standards Proposed

The National Bureau of Standards has proposed new standards for graphic representation of the control characters of ASCII, and for code extension techniques in 7 or 8 bits. The control character proposal adopts the voluntary industry standard developed by the American National Standard Institute and specific graphical representation for the 34 control characters of ASCII.

The second proposal provides for extensions through the use of the coding structure. Additional control codes and graphic character codes may be defined, and thence used in a 7- or 8-bit environment. It is expected that, as a result of this standard, additional sets of character codes will be defined for extended Roman characters, mathematical symbols, Greek and Cyrillic characters, and control characters needed for visual displays and automatic typesetting.

The NBS, as proposed, would then serve as the registry for additional code assignments and will publish these as a basic reference. Copies of the proposed standards are available from the Office of ADP Standards Management, NBS, Washington, DC 20234

Noise-Reduction Discs and Tapes

The release by Klavier of a solo recital of selections from French romanticists by harpist Susan McDonald marks the arrival of dbx-encoded discs. According to Klavier, surface noise is virtually eliminated on discs using the dbx process, with approximately 35-dB reduction in tape and background noise, as well as improved transient and dynamic response. The encoded discs are priced at \$7.00. For more information, contact Klavier Records, 5652 Willowcrest Ave., North Hollywood, CA 91601.

The Advent Corporation announced the release of the first Dolby-encoded recordings on chromium-dioxide tape in the U. S. Called Process CR/70TM, the recorded cassettes feature music from the Nonesuch and Connoisseur Society catalogs and original recordings produced by Advent. It is claimed that the design of the tape housing prevents jamming, permitting use of thinner-base C-90 and C-120 tape. Advent reports that each Process CR/70 cassette is individually sampled to insure that all recorded cassettes are of uniform quality. Prices range from \$4.95 to \$7.95 per cassette.

First Solar-Powered Digital Watch

The use of solar power cells and LSI CMOS

technology has resulted in a new digital watch called Synchronar, made by Ragen Precision Industries. Silicon solar cells constantly charge the watch's storage cells, drawing power from sunlight, ambient light, or an ordinary light bulb. An average daily exposure of 10 to 15 minutes of sunlight is all that the watch is said to require.

LED's are used to display time, date, and month. The display is mounted on the edge of the watch case facing the wearer, and the two solar cells are set into the face. The display adjusts its brightness to the prevailing light. The Ragen Synchronar is priced at \$500.

Four-Channel FM Tests Underway

Station K-101, San Francisco, is conducting a test program of various schemes for discrete 4-channel FM broadcasting. The National Quadraphonic Radio Commission, in making the test, is using five proposed methods for discrete transmission. The program, from midnight to 6 a.m., will run through October.

Audio manufacturers such as JVC, RCA, Fisher, Marantz, and Panasonic are participating; and the FCC has a group of engineers observing the tests. Results will provide information for formulating a national standard for discrete four-channel transmissions.

In another test, a group of CATV companies and a cable FM equipment manufacturer, in cooperation with Santa Clara University and Panasonic, are transmitting discrete four-channel FM programs over CATV/FM lines in the San Jose and Santa Clara areas. On the university's FM radio channels of 91.1 and 89.1 MHz, over the lines of CATEL and TelePrompter, will use the CD-4 system and the prototype Dorren discrete four-channel FM generator. It is hoped that the tests will lead to discrete CD-4 transmissions on cable FM lines.

Price Reductions on CMOS IC's

Price reductions averaging 15 percent on plastic, commercial ceramic and chip versions of standard CMOS integrated circuits have been announced by RCA Solid State Division. These price reductions apply across the standard CD4000A product line. Price reductions of 20 percent are being applied to popular medium-scale integration types, with a 10 percent reduction on gates and some other MSI types. The world-wide market for CMOS is expected to more than double this year, probably exceeding \$130 million.


re test equipment

...with power for the professional...with economy for the hobbyist! Fresh, from the laboratories of Continental Specialties, whose QT Sockets and Proto-Boards have taken the electronics market by storm...

here are exciting NEW ideas to make your circuit design and testing faster, safer, easier and less expensive!

NOW...PROTO POWER!

New Proto Board 203 with built-in regulated short-proof 5V, 1AMP power supply. Ready-to-use. Just plug-in and start building! 2 extra floating 5-way binding posts for external signals. Completely self-contained with power switch indicator lamp and power fuse. 24-14 pin DIP capacity. All metal construction.... no chipping or cracking like plastic cases. Two-tone gold/black pleasing. quality case makes PB203

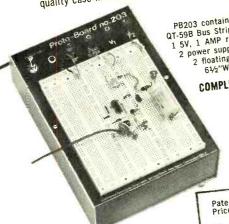

PB203 contains: 3 QT-59S Sockets; 4 QT-59B Bus Strips; 1 QT-47B Bus Strip; 1 St. 1 AMP regulated power supply; by, 1 Ame regulated power supply; 2 power supply 5-way binding posts; 2 floating binding posts; 934"L x 61/2"W x 23/4"H. Weight: 5 lbs.

COMPLETE

ORDER TODAY!

Patents Pending • Made in U.S.A. Prices subject to change

Build and test circuits as fast as you can think without soldering or patch cords with NEW

Breadboard Assemblies

Here are four versatile new Continental Specialties' Proto Boards, made from convenient combinations of QT Sockets and Bus Strips, that let you make all circuit and power interconnections with common solid #22 wire, while power distribution busses make wiring a snap. Aluminum base plates offer solid work surfaces and perfect ground plane, Rubber feet prevent scratching. Each Proto Board features one or more 5-way binding posts to tie into system or power supply ground. And all are compatible with digital and linear ICs, in T05s, DIP packs and discrete components. Each is assembled and ready-to-use.



Proto Board 103. 2,250 solderless tie points. (4) 5-way binding posts.

5.8"

24-14 pin DIP capacity. 9" x 6".

Here's a low cost, big 10 IC capacity breadboard kit with all the quality of QT Sockets and the best of the Proto-Board series ... complete down to the last nut, bolt and screw. Includes 2 QT-35S Sockets; 1 QT-35B Bus Strip; 2 5-way binding posts; 4 rubber feet; screws, nuts, bolts; and easy assembly instructions.

COMPLETE KIT ...

ORDER YOURS TODAY!


NEW! PROTO-CLIP for power-on, hands-off signal tracing. Eliminates shorting leads ... and costs under \$ 5

Bring IC leads up from pc board for fast signal tracing and troubleshooting. Inject signals. Wire unused circuits into boards. Scope probes and test leads lock onto Dynagrip (see circle) inset for hands-off testing. New plastic construction eliminates springs, pivots. Non-corrosive nickel/silver contacts for simultaneous low resistance connections. Narrow throat for high density pc boards.



Proto Board 102. Compact, 12-14 pin DIP capacity. 7", 41/2". 3995

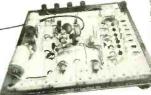Proto Board 101. Compact. Inexpensive. 10-14 pin DIP capacity. 2995 5.8" long x 4.5" wide. long x 4.5" wide.



Proto Board 104. Huge. 3,060 solderless tie points. (4) 5-way binding posts. 32-14 pin DIP capacity. 94/2" long x 8" wide. 7995

14-pin Proto-Clip

. \$4.50 each

\$4.75 each

16-pin Proto-Clip

Available off-the-shelf at your local distributor or order directly from Available of the specialties. Phone charges accepted for BankAmericard, Master Charge, American Express. Write for Free catalog. Dealer inquiries invited. Continental Specialties Corporation



325 East St., Box 1942, New Haven, CT 06509

Telephone: (203) 624-3103


Available thru Len Finkler, Ltd. CANADA: Ontario

OCTOBER 1974

Metric-to-English SLIDE RULE. Convert lengths, area, weight, volume instantly. Yours FREE with a minimum \$5.00 order!


learn by doing!

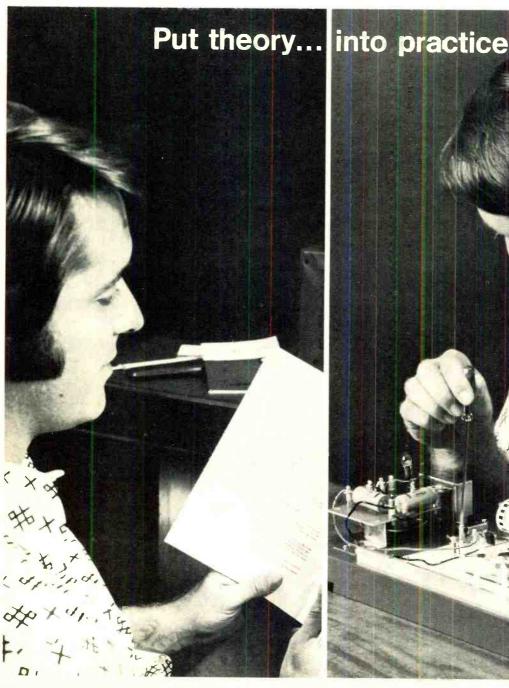Perform more than 200 exciting experiments with CIE's fascinating ELECTRONICS LABORATORY PROGRAM!






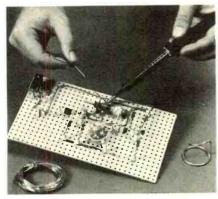
You get your own 161-piece electronics laboratory... with authentic electronic components used by industry!



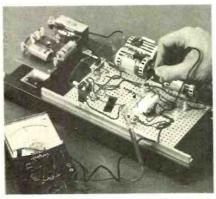You learn how to construct circuits and connect them with a soldering iron, which is part of your CIE laboratory equipment. This "hands on" experience is extremely valuable in applying what you learn.



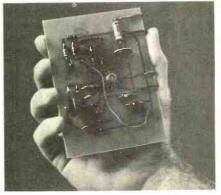Testing and troubleshooting are an important part of your learning experience. Included in your laboratory is a precision "multimeter" to diagnose electrical and electronic troubles quickly and accurately.



Modern space-age components like this IC (integrated circuit) are professional quality and can be used again and again in many of your projects. Lesson by lesson, piece by piece your knowledge grows!

Prepare now for a high income career in Electronics...the Science of the Seventies.

Electronic miracles are changing today's world with breathtaking speed.

And with this growth in electronics technology has come a brand new need...a demand for thousands of electronics technicians, trained in theory and practice to build the products, operate them and service them during the Seventies.

Don't just wait for something to "happen" in your present job. Get ready now for a career you'll really enjoy with a good income and plenty of opportunity for advancement.

Experience with experiments is your best teacher

"Hands on" experience helps to reinforce basic theory. When you learn by doing, you discover the "how" as well as the "why." You'll find out for yourself the right way as well as the wrong way to use electronic components. How to construct your own circuits, to discover trouble spots and learn how to fix them. And with CIE's special Auto-Programmed® Lessons, you learn faster and easier than you'd believe possible.

CIE's fascinating course, Electronics Technology with Laboratory, teaches you Electronics by making it work before your eyes. And you do it yourself, with your own hands.

Importance of FCC License and our Money-Back Warranty

Many important jobs require an FCC License and you must pass a Government licensing exam to get one.

But, a recent survey of 787 CIE graduates reveals that better than 9 out of 10 CIE grads passed the FCC License exam.

That's why we can offer this famous Money-Back Warranty: when

OCTOBER 1974

you complete our Laboratory Course, which provides FCC License preparation, you'll be able to pass your FCC exam or be entitled to a full refund of all tuition paid. This warranty is valid during the completion time allowed for your course.

You get your FCC License - or your money back!

You'll have high paying job opportunities

Electronics is still young and growing. In nearly every one of the new exciting fields of the Seventies you find electronics skills and knowledge are in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications. With a CIE Diploma and an FCC License you can choose the career field you want . . . work for a big corporation, a small company or even go into business for yourself.


Here's how two outstanding CIE students carved out new careers: After his CIE training, Edward J. Dulaney, President of D & A Manu-

facturing, Inc., Scottsbluff, Nebraska, moved from TV repairman to lab technician to radio station chief engineer to manufacturer of electronic equipment with annual sales of more than \$500,000. Ed Dulaney says, "While studying with CIE, I learned the electronics theories that made my present business possible."

Marvin Hutchens, Woodbridge, Virginia, says: "I was surprised at the relevancy of the CIE course to actual working conditions. I'm now servicing two-way radio systems in the Greater Washington area. My earnings have increased \$3,000. I bought a new home for my family and I feel more financially secure than ever before."


Send now for 2 FREE BOOKS

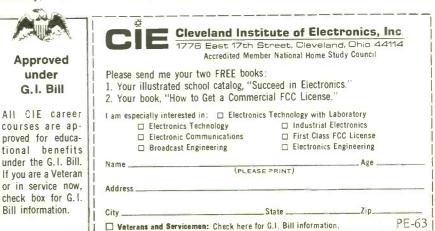Mail the reply card or coupon for our school catalog *plus* a special book on how to get your FCC License. For your convenience, we will try to have a representative call. If coupon is missing, write: Cleveland Institute of Electronics, Inc., 1776 E. 17th St., Cleveland, Ohio 44114. Do it now!



The new Mallory CA3 Intrusion Alarm.

Reliable.

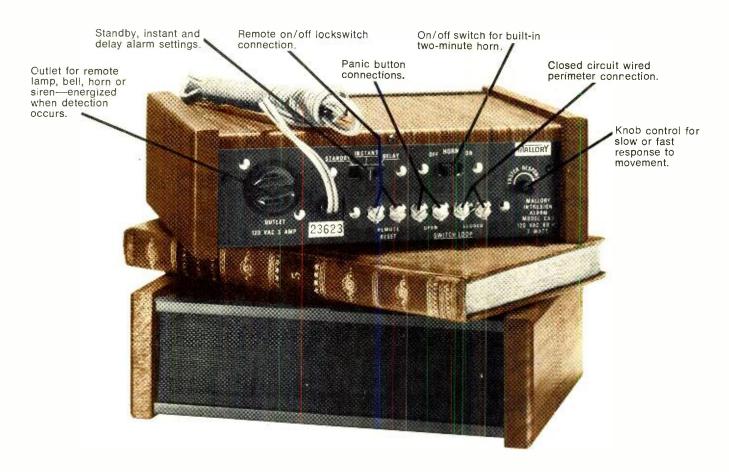

(And inconspicuous.)

This area-and-perimeter device creates and transmits an ultrasonic wavelength field for detection up to a distance of 20 feet. And because of its modern design and walnut-grain finish, the CA3 is attractive and inconspicuous enough to pass as a radio or stereo tuner.

Virtually any movement by an intruder (or a break in the perimeter circuit) activates the built-in horn and the remote outlet for two minutes. An automatic reset handles the possibility of a new or renewed intrusion. And special CA3 circuitry guards against false alarms from line transients and insects. A variety of companion indoor or outdoor accessory devices is available.

The Mallory CA3 Ultrasonic Intrusion Alarm. From the manufacturer of the most complete line of do-it-yourself security products. Another sound reason to see your Mallory distributor today.



MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC. Box 1284, Indianapolis, Indiana 46206; Telephone: 317-261-1501

Batteries • Capacitors • Controls • Security Products • DURATAPE' • Resistors • Semiconductors • SOWALERT' • Switches • Timing Devices and Motors

DURACELL* DURATAPE® and SONALERT® are registered trademarks of P. R. Mallory & Co. Inc.

ommon table salt, like water, is an essential ingredient to all animal life on earth — including man. Recently, however, research has revealed that diets high in sodium, one of the elements in salt, may be a leading cause of hypertension. Also, the reduction of dietary sodium intakes has become an important treatment in the management of congestive heart disease. (For more information on the clinical and physiological roles of salt in human nutrition, see the box on the third page of this article.)

With salt being linked to medical problems, it is no wonder that many of us have become concerned with the benefits of low-salt diets. Unfortunately, progress in salt metering has long been held back by the high cost of ac-type conductance meters required for testing foods. (Dc-type ohmmeters are useless for this application.) While commercial ac salt meters cost \$1000 or more, less than \$30 will buy the components for you to build your own. The salt meter described in these pages will permit you to rapidly sample the salt content in baby foods, canned and raw foodstuffs, and drinking water. Simply immerse the probe tip into the food sample, and observe the meter pointer's deflection.

The salt meter's design takes advantage of the fact that salt-enriched foods conduct electrical current. The higher the salt content, the greater the current flow. Pure salt-free water has a specific conductance (the reciprocal of resistance, or 1/R) of 0.05 µmhos, or a resistance of 20 megohms. Its low conductivity results from a deficiency of ions. Our saltmeter, on the other hand, expresses conductivity in terms of currents ranging from 0 to 1.0 mA, affording the greatest possible convenience for the average user.

About The Circuit. The salt meter (see Fig. 1) is a true ac-type conductance meter. It is based on an acenergized bridge circuit, which consists of R2, R3, and R5. External test probe PL1 is switched (via S2B) across R3. Dipping the probe into a food sample places a given parallel resistance across R3 which, in effect, unbalances the bridge and causes current to flow through the 20,000-ohm primary winding of T2. This current is inductively coupled into the secondary circuit of T2 where it is rectified and fed to meter M1. Note that no do appears in the circuit.

OCTOBER 1974

Popular Electronics

OCTOBER 1974

CONSTRUCTION

BY L. GEORGE LAWRENCE

An Electronic Salt Meter For Family Health

With this low-cost device, you can check food for salt content, an important consideration for weight and hypertension



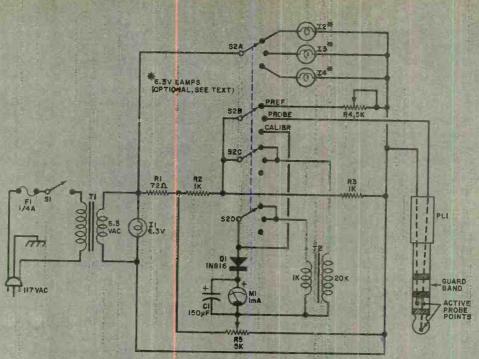


Fig. 1. The circuit of the salt meter is a true ac-type conductance arrangement. The bridge circuit is unbalanced by resistance across probe.

PARTS LIST

C1-150-µF, 50-volt electrolytic capacitor

D1-1N816 diode

F1-1/4-ampere fuse

I1-I4—6.3-volt lamp (I2-I4) optional—see text)

M1-0-1-mA meter movement (Calectro No. D1-912 or similar)

PL1—Four-conductor, 14-in. phone plug (Calectro No. F2-833 or similar)

R1-72-ohm, 1-watt resistor

R2,R3—1000-ohm, 1-wat: 5% resistor
R4—5000-ohm, linear-taper potentiometer
with screwdriver-adjust shaft

R5-5000-ohm, linear-taper potentiometer

S1—Spst switch

S2—Four-circuit, 3-position rotary switch (RCA No. 56584 or similar)

T1-6.3-volt, 1-ampere filament transformer (Lafayette Radio No. 33P80946 or similar)

T2—20,000-ohm primary, 1000-chm secondary miniature driver transformer (Calectro No. D1-719)

Misc.—Suitable chassis; control knobs (2; 3 if building reference standard); 5-percent resistors (see Fig. 2 for values) and 44-in phone jack (for reference standard); probe cable; three-conductor power cord; fuse holder; machine hardware; hookup wire solder; etc.

Switch S2 has three positions: PREF, PROBE, and CALIBR (meter null). Each position is equipped with an indicator lamp (I2 to I4) that identifies the position to which the switch is set. These lamps are optional. Omitting them will not affect the instrument's performance and will allow you to use a simpler switch for S2.

In the PREF position of S2, tastepreference potentiometer R4 is adjusted to a low-salt value of, say, 0.73 as indicated on the meter. However, before R4 is adjusted, S2 must first be put into the CALIBR position and R5 set for a meter reading of 0.1 mA.


In the PROBE position, external test probe *PL1* is in the circuit. (Note that this probe is a standard ¼-in., four-conductor phone plug. Only the tip and second conductor are active.) Inserting the probe into a food sample causes a current to flow, its magnitude

dependent upon the salinity of the food, and resistance drop across R3. This resistance drop, resulting from the flow of current, causes the meter's pointer to swing up-scale to give a measure of saltiness. (For typical readout values, see the table on the opposite page.)

In the CALIBR (meter null) position, the ac bridge can be balanced by adjusting calibration control R5. Balancing is achieved by adjusting R5 until the meter's pointer rests at the zero index of the scale. To ready the instrument for taste preference calibration and probe readings, adjust R5 for a 0.1-mA meter reading. Now, if the test probe's active contacts are shorted to each other, the meter will read precisely 1.0 mA.

The saltmeter is also capable of indicating probe contamination. If *PL1* is not wiped perfectly clean after each

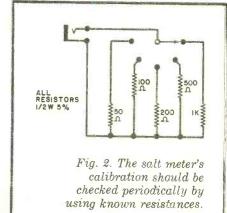sample test, an error will be indicated by the meter pointer's up-scale swing. To investigate probe contamination or internal leakage due to extensive use,



set S2 to CALIBR and R5 for a meter pointer null indication. Then switch to the PROBE position. If the meter's pointer remains at the zero index, no contamination or leakage exists.

The salt meter should be periodically checked against a calibration reference of known resistance. Such a reference can be made from a rotary switch, 5-percent tolerance resistors, and a phone jack that properly mates with the four-conductor phone plug used for *PL1* as shown in Fig. 2. The jack and potentiometer can be housed in an external box, or room can be made for mounting them on the front panel of the instrument case where the reference will be always handy.

Now, by plugging the salt meter's test probe into the reference circuit's jack, you can obtain an error-free analog meter reading. Consult the table for reference values.

Construction. The salt meter's simple circuit lends itself nicely to

FOOD SAMPLE READINGS

Food Sample	Meter Reading (mA)	DC Resistance (ohms)	Test Resistance (ohms)
Fresh tap water*	0.17	5000-13,000	1000
Fruit dessert with			
tapioca	0.64	3400	220
Plums	0.64	3400	220
Coffee with cream*	0.68	4000-8500	185
Bananas	0.73	3200	155
Custard Pudding	0.77	7500	132
Vegetables with			
ham	0.80	6500	110
Vegetables with			
lamb	0.81	4000	105
Beef stew	0.88	6100	67

^{*}All food samples, except those indicated by an asterisk, are baby foods in glass jars. Readings obtained with 0.1-mA calibration setting and test probe inserted in food above guard band; dc resistance taken with standard dc-type ohmmeter connected only to probe.

CLINICAL AND PHYSIOLOGICAL ROLES OF SALT IN HUMAN NUTRITION

It is important for all of us to understand both the clinical and physiological roles salt plays in human nutrition. Major importance resides in the quantities of sodium that can be consumed without harm.

Therapeutically, low-salt diets were employed as early as 1901 for patients with edematous heart disease. Later, this form of treatment was extended to people suffering from congestive heart failure, renal diseases, hypertension, cirrhosis of the liver, toxemias of pregnancy, and Meniere's disease. In tests, when eating salt-restricted foods, one-fourth to one-third of hypertensive patients responded with a reduction in blood pressure.

There is good evidence that an adult's daily ingestion of 250 to 375 mg of sodium-chloride salt causes no harm. This is all the human body requires to maintain good health. Even so, the daily intake ranges from 10 g for Americans to 27 g for many people in certain areas of Japan. Diabetic children have been observed to have an intense craving for salt — as much as 60 to 90 g/day — which triggers a powerful hypertensive effect.

High salt intake can become a critical issue where infants are concerned. Unable to speak, the infant is totally subordinated to the food preferences of the mother, who salts things "just right" for her own tastes — not baby's true health needs. A special problem begins when the infant is between one and three months old, the age most American infants are fed supplementary commercial foods (baby food) comprised of strained vegetables, meats, and fruits. Even to many fruits, salt is added prior to canning.

The sodium concentration in strained fruits is fairly low, typically 0.6 to 2 mg/100 g of food substance. However, in the case of strained meats, sodium contents may range from 293 mg to 510 mg/100 g of food weight. Vegetable samples have an average sodium content of about 358 mg/100 g of food weight.

The seriousness of the above numbers becomes clear when we examine a 5-month-old infant weighing 6 to 8 kg and who consumes at least 100 g of commercial baby food per day. In addition to an average of 305 mg of sodium ingested, the infant will drink about 1.1 liter of cow's milk, which can have as much as 2.14 g of sodium per liter. The only statement likely to be printed on a carton is that the contents are pasteurized and that vitamin D has been added.

Adding all his food sources together, baby is bound to consume about 2.3 g of sodium chloride daily. This is equivalent to 23 g/day for a 68-kg (150-lb.) adult. It is certainly dangerously high for a small child. Here, researchers are concerned about the possibility that such abnormally high intake of sodium chloride in infancy might play an important part in hypertension in adulthood.

In research work conducted under the auspices of the Atomic Energy Commission, the lifetimes of laboratory rats were drastically shortened when the rats were fed nothing but baby foods. Three out of seven of the rats developed hypertension and died.

Clerarly, some form of salt metering is of vital importance to any family interested in good dietary control.

straightforward point-to-point wiring in a suitably large chassis case. Most of the work is involved in machining the front panel to accept the meter movement, controls, and lamps. (Do not forget to allow room for the calibration standard's switch and jack if you intend to mount them on the front panel.) In the prototype, *PL1*'s cable exited the salt meter through a grommet-lined hole in the rear panel; if you wish, the cable can exit a grommet-lined hole in the front panel.

Mounted on the rear panel should be the holder for F1, and the three-conductor line cord should exit through a grommet-lined hole or be held in place with a plastic strain relief. The two transformers mount to the floor of the chassis. Then all resistors, the diode, and the capacitor install directly between the appropriate lugs of the controls, meter, etc., as shown in Fig. 1.

In Use. One of the ac salt meter's outstanding features is its ability to speedily sample baby foods. Conduct all tests at room temperature.

In practice, a taste preference reading is set prior to actual food tests. Assume this reading to correspond to a very mildly salted food item, such as bananas, or 0.73 on the meter scale. Now, with the salt meter switched to PROBE, a similarly mildly salted food item should yield an equally low reading. The taste-preference calibration allows an electronically unskilled person to recognize safety levels without having to figure out complex electrical relationships.

Some food items will surprise you. One sample jar of beef-stew baby food yielded a reading of 0.92 — much too salty for an infant. Fresh water, supposedly pure, turned out to be highly conductive, indicating high ion activity due to pollution.

The approximate percentage of sodium chloride (salt) in foods can be determined by weight. For a test, prepare mashed potatoes from fresh potatoes. Add 500 mg of salt to 99.5 g of mashed potatoes and measure the conductivity of the mixture. Then add another 500 mg of salt and again measure the conductivity; note how far up-scale the meter's pointer deflects beyond your first test reading

Most prepared foods contain such conductive substances as acids and food coloring in addition to salt. However, salt tends to be the dominant conductive agent.

BUILD AN

AC Power Line Monitor

Don't risk losses due to power outages

BY GARY McCLELLAN

N THESE times of fuel shortages and increasing electric power demands, power outages have become common occurrences. At the very least, an outage can be a nuisance. The outage becomes serious when it lasts several hours and you have a freezer full of food. To play it safe, you should equip your home with an ac line monitor that will alert you in the event of an outage so that you can take corrective measures.

An ac power line monitor need not be expensive. The one shown schematically below will cost about \$8 for all new parts. Once assembled, it will monitor your power line on a continuous 24-hour basis, remaining passive until an outage occurs. Then when power is interrupted, a loud buzzer sounds and a panel light comes on. The panel lamp serves as an alert system for those times when power is interrupted and you are away from home. Even if power is restored before you return home, the lamp remains on until the system is manually reset.

The circuit consists of three basic parts. Its power supply is comprised of *T1*, *D1*, *C1*, and *R1*. This is followed by controlling relay *K1*. Finally, there is a dual alarm system, with the buzzer independently powered by *B1* providing an audible alarm and *I1* providing a visual alarm in the event power was interrupted and restored.

In operation, the incoming ac is rectified by *D1* and dropped to about 75 volts by *R1*. Capacitor *C1* filters the rectified ac to prevent relay chatter

and provides about 5 seconds of delay after power goes off, thus preventing false alarms.


When the line cord is first plugged into an ac receptacle, *K1* does not immediately energize. Instead, *I1* lights up. For *K1* to energize, *S1* must be momentarily depressed to bypass the *I1* circuit. Once *S1* is depressed and returned to its operating position, *K1* will remain energized for as long as ac power is supplied to the circuit.

Now, if power is interrupted for longer than 5 seconds, *K1* deenergizes, making its upper contacts. This completes the B1/buzzer circuit and sounds the audible alarm. The buzzer will continue to sound until *S1* is set to RESET or the battery runs down.

In the event that power is restored, I1 comes on and remains on until S1 is set to its RESET position, at which time the relay pulls in and I1 extinguishes.

There is nothing critical about assembling the alarm system. If you build it into a metal utility box, make certain that no ac portion of the circuit contacts the box itself.

Periodically check out the condition of *B1* to make sure it is capable of sounding the buzzer. To do this, simply unplug and reinsert the line cord in an ac outlet. If the buzzer does not sound or puts out a weak buzz, replace the battery. If you wish, you can substitute a nickel-cadmium battery for *B1* and periodically recharge it. This way you will not have to worry about running out of batteries on a weekend.

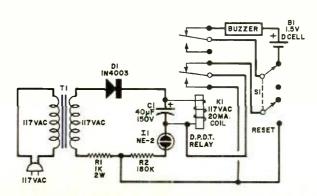

A PAIR OF USEFUL TEST IDEAS

Check & Select PUT's


Use VOM as Dwell-Angle Indicator

BY RALPH TENNY

BY JAMES CAMERON

F you have some programmable unijunction transistors (PUT's) whose condition you are not quite sure of, you will want to build this simple test circuit. It will quickly sort good PUT's from bad ones. With a PUT plugged into the socket and the power turned on, the potentiometer is slowly adjusted from maximum to minimum. If the PUT is good, the speaker will emit a series of clicks or pops over some portion of the potentiometer's range.

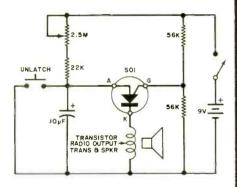You can also sort PUT's into grades and determine the correct anode re-



The PUT will oscillate at certain input currents.

sistor for reliable operation. To do this, use a dial plate and indicator knob to record the resistance of the potentiometer. With the PUT oscillating, a high resistance setting indicates the lowest allowable value of input current, while the lowest resistance setting indicates the maximum input current. To use that particular PUT in a circuit, the anode resistor must be within the indicated resistance range. If the resistance is too high, the PUT will not turn on; with too low a resistance the input will cause the PUT to latch in. To unlatch the circuit, the power must be removed or the capacitor must be discharged (using the switch shown).

PUT's that operate with a wide range of permissible input current can be used in variable oscillators, while those with a narrow range can be used in less demanding circuits where the anode resistor can be tailored for the application.

ITH ONLY two or three extra components, you can use the dc-voltage function of your multimeter to set the dwell angle in the distributor system of your car. The theory behind this is that, if a square wave is measured with a dc voltmeter, the potential indicated depends on the amount of time the voltage is at its peak versus its 0-level time. A square wave with a 10-volt peak and 50-percent duty cycle (on time) would measure 5 volts. Increase the duty cycle to 75 percent, and a 7.5-volt reading would be obtained.

The dwell angle in an ignition system corresponds to the closed versus the open time of the points. The voltage "seen" by the dc voltmeter is then proportional to the dwell angle. In an ignition system, the peak potential is that delivered by the battery. This voltage varies when the engine is being cranked and is therefore not suitable as a reference. To obtain a stable reference (or peak) voltage, a simple zener-diode arrangement can be used as shown in the schematic.

In practice, best accuracy is obtained when the zener diode's voltage is near the full-scale index of the meter's scale. Since most cars now employ a 12-volt system, and most multimeters have a 10-volt scale, a zener diode with an 11-volt rating is most convenient to use.

With an 11-volt zener diode and power limited to 100 mW, the zener current should be less than 10 mA (100 mW/11 V). If a 12-volt battery and an 11-volt zener diode are used, the drop across the current-limiting resistor is 1


volt. Hence, if 10 mA flows through the resistor, the resistor's value should be 100 ohms. This is not a critical value; you can use any ¼-watt resistor of a value within the 75- to 150-ohm range.

The potentiometer in the circuit eliminates the need for making calculations on paper. (Select a pot with a 1000- to 5000-ohm resistance.)


To use the zener-diode circuit with a voltmeter, disconnect the distributor points from the coil and disconnect the capacitor from across the points to eliminate any charge/discharge time-constant effects. The zener-diode circuit then connects to the ignition system as shown in the schematic. Now, open the points and measure the voltage. If the meter's pointer does not swing to exactly the 10-volt mark on the scale, adjust the potentiometer for a 10-volt reading.

To take a dwell-angle measurement, crank the engine and observe the voltmeter's pointer swing. Your reading indicates the percentage of the time the points are open. What you want to know is the dwell angle, or the amount of time the points are closed. Hence, you must subtract the meter reading from 10 and multiply the result by 10 to obtain the dwell angle in percentage. For example, if you obtain a reading of 4.8, subtract this figure from 10 to obtain 5.2. Then when you multiply the result by 10, the dwell is 52 percent.

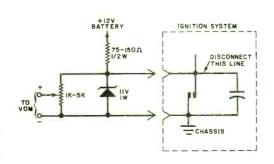It is a good idea to check the battery voltage while cranking the engine. The zener voltage must be lower than the battery voltage or an error will be introduced into the measurement.



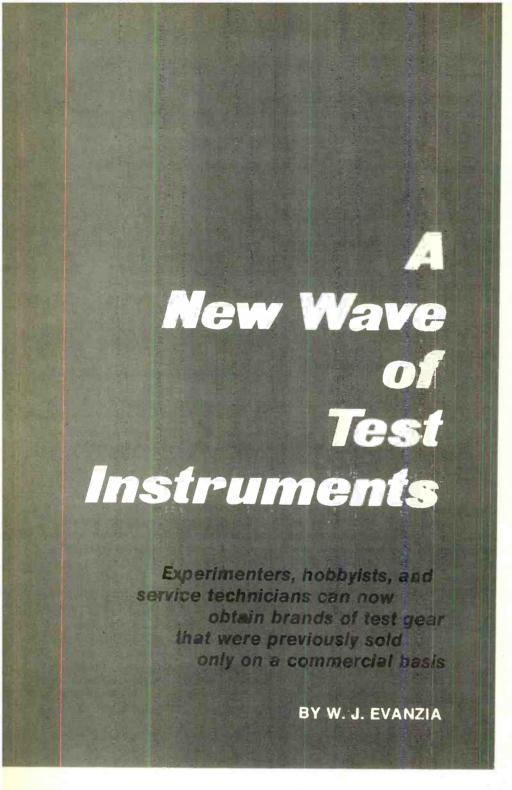Zener diode provides a reference to measure voltage across points and determine dwell angle



A LARGE number of test-equipment manufacturers specialize in supplying electronics technicians and hobbyists with test and measuring instruments. In contrast, OEM (original equipment manufacturing) instrument companies concentrated their production efforts to meet commercial needs—"defense" industries, device manufacturers, laboratories, etc.

But times have changed. Now, some of these OEM companies recognize

that electronics enthusiasts are accustomed to spending substantial amounts of money for good-quality instruments and that the numbers of such potential customers run into the thousands. The result is that a few OEM companies have diverted some of their energies to reaching this "consumer" market with reasonably priced test instruments.

Currently, the most common test instrument offered is the digital multimeter, or DMM. But other instru-

ments—such as oscilloscopes, frequency counters, and signal and function generators—are making their appearances. The manufacturers involved include some of the "biggest" names in the industry. Here is a roundup of what they are offering to the "consumer" market.

A Choice of DMM's. Data Precision is offering a pair of DMM's. Serious experimenters looking for a good bench and field DMM will find the Model 245 battery-powered multimeter to be a very convenient and versatile multi-tester. Priced at \$295, it offers a very high degree of testing accuracy in a truly miniature package. If you want a bench-only DMM, the 3½-digit Model 134 is available for only \$189

Because low-power complementary n and p MOSFET's are used with a liquid crystal display in the Model 2000 Danameter, *Dana Laboratories'* DMM requires less power than any other multimeter on the market. A single 9-volt battery will operate the DMM for about a year.

Although the 3½-digit Danameter is less precise than the Data Precision Model 245, it is also considerably less expensive at its retail price of \$195. And the Danameter is built to take the rough-and-tumble environment of a TV service shop and tool caddy.

The Danameter can measure ac and dc voltages to 1000 V full-scale with a l-mV resolution, direct current over a range of 20µA to 2 A, and resistance to 200 megohms.

The Ballantine Model 3/24 DMM sells for \$195. It has a full, three-function measuring capability with 24 ranges and features a 3½-digit display and battery operation. Ac and dc voltages are each provides with four measurement ranges, while alternating and direct currents are each allotted five measurement ranges. Six ranges are set aside for resistance measurements. Accuracy on the dc voltage ranges is typically 0.2 per cent, ±1 digit, and on the direct-current ranges 0.5 percent, ±1 digit.

Three options are available as power sources for the Model 3/24: an adapter for storage battery or external dc supply; an ac power supply adapter; and a rechargeable battery supply.

The John Fluke entry into the low-cost DMM market is the Model 8000A, priced at \$299. It offers numerous options to increase the instrument's




Hewlett-Packard 1221A Oscilloscope



Data Precision 134 DMM



Data Technology 21 DMM

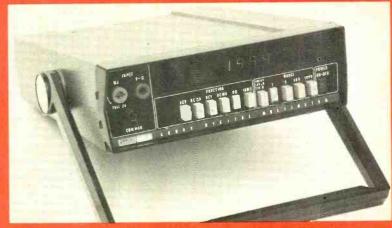


Fluke 8000A DMM



Ballantine 1010A Oscilloscope



Dana Laboratories 2000 Danameter DMM

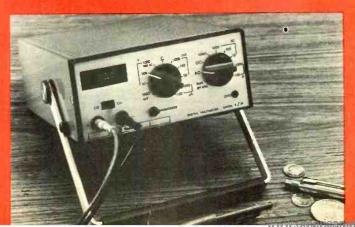

Ballantine 3/24 DMM



Hewlett-Packard 790A DMM

basic flexibility. Among them are a rechargeable battery pack, 100-kHz to 500-MHz r-f probe, high-voltage probe, BCD output, 2-A to 200-A clamp-on ac adapter, etc.

The Model 8000A has 26 ranges, including one that measures down to 1 μ V on ac and dc, down to 100 nA on ac and dc, and down to 100 milliohms. The display consists of a $3\frac{1}{2}$ -decade cluster.

Data Technology offers no less than three low-cost DMM's. The miniature Model 21 (it is about the size of a hand-held calculator) sells for \$269, including a battery charger and carrying case. It features a 3½-digit display and ac and dc voltage and resistance measuring capabilities. It also measures capacitance (not electrolytic values). No current-measuring capability is featured.

The Model 20, selling for \$269, is basically the same as the Model 21 in features and functions, including the capacitance-measuring capability. However, it is a bench-type instrument, designed to be operated from line power. Featuring four decades of display and current-measuring capability on both ac and dc, but no capacitance-measuring capability, the \$329 Data Technology Model 30 rounds out the company's low-cost DMM line. This model offers a choice of either line or battery powering and features automatic polarity sensing and display on the dc voltage and current functions. (The Models 20 and 21 also feature automatic-polarity capability on their dc voltage ranges.)

United Systems Corp., a subsidiary of Monsanto, offers two DMM's retailing at less than \$300, plus a rather unique third that sells for \$395 (it features a direct-readout decibel-measuring function). The Digitec Model 2110 sells for \$219. It employs a 3½-digit display and measures up to 1000 V dc, 500 V ac, and 20 megohms. It does not measure current. A choice of power options—standard ac or rechargeable battery—is available.

Providing current-measuring capability on ac and dc, the Digitec Model 2120 sells for \$295. Also a 3½-decade instrument, it features auto-polarity on the dc voltage and current ranges. It measures to 1000 V dc, 750 V ac, and 20 megohms.

The \$395 Digitec Model 2180 is the only DMM in this report to offer decibel-measuring capability. Except for this, the Model 2180 is identical in

features and functions to the Model 2120.

Hewlett-Packard's Model 970A miniature DMM has a highly unconventional package design. The instrument weighs only 7 ounces and resembles a small flashlight with a probe sticking out the top (with interchangeable tips available). The 3½-decade miniature LED readout can be flipped over so that it appears rightside-up no matter in what orientation the user has the instrument.

The Model 970A is basically a field-service troubleshooter's instrument. It features automatic ranging, autopolarity, and automatic zeroing. It can measure dc and ac (optionally up to 500 MHz) voltages and resistance. (An optional ammeter adapter is available.) Voltages to 500 V on both ac and dc and resistance to 10 megohms can be measured with the DMM. Decimal point location is automatic. The instrument comes with a sun shield, carrying case, battery charger, and instruction booklet.

Keithley Instruments' Model 168 DMM, selling for \$299, is a fullfunction instrument, capable of measuring dc and ac voltages and currents and resistance. It has a 3½-digit LED display, autoranging, choice of line or battery operation, and LED function indicators. A choice of high or low ohms test voltages is available. In the high ohms function, the test potential is 1 V, while on low ohms, it is 100 mV (which eliminates pn junction conduction when running resistance tests in circuits containing transistors and diodes).

Low-Cost Oscilloscopes. Until the advent of digital electronics, most general-purpose oscilloscopes were adequate for the great majority of tasks they had to perform. Digital circuitry changed all that, as many of us have discovered when tracing pulses through a system with a scope limited to a 5-MHz bandwidth and risetime measured in the slow microseconds. In the early days of digital electronics, an adequate scope for digital work cost upwards of \$1000. Now, reasonably priced scopes for this use are available.

Tektronix, one of the most famous names in laboratory-type scopes, selling has a lower-cost line of scopes that includes the Telequipment Model D61 for \$475. It has a bandwidth of dc to 10 MHz at the -3-dB points and a

risetime of a mere 35 ns (that's nanoseconds!). Vertical deflection is variable from 10 mV to 5 V/cm in nine calibrated steps, while horizontal deflection is variable between 500 ns to 500 ms/cm in 19 calibrated steps. Input impedance is 1 megohm, shunted by 35 pF.

The dual-trace, single-beam scope has alternate and chopped modes, triggered sweep with automatic and normal trigger modes, X-Y capability, and a vector mode. Also featured is a X5 magnifier.

You get more bandwidth (dc to 15 MHz) and greater sensitivity (2 mV) with *Hewlett-Packard's* Model 1220A and Model 1221A oscilloscopes. The \$595 Model 1221A features a single trace, while the \$695 Model 1220A is a single-beam, dual-trace instrument.

In the dc mode, bandwidth is dc to 15 MHz, while in ac it is limited to 2 Hz on the lower end. The specified risetime is about 23 ns. Input impedance is approximately 1 megohm, shunted by 30 pF. Maximum input signal level is ±400 V dc plus peak ac. The time-base sweep ranges from 0.1 μs to 0.5 s/cm. A X10 magnifier permits detailed examination of the displayed waveform. The scopes are triggered internally from approximately 10 Hz to 15 MHz on signals causing 1 cm or more vertical deflection. The external trigger operates over the same range on signals with amplitudes of 0.1 V peak-to-peak or greater. As with the Telequipment Model D61, both H-P scopes can be triggered by the TV field line, a feature particularly useful in TV servicing. And the three scopes operate in the X-Y mode to provide a means of making phase- and sweepfrequency measurements in tests of TV tuners and i-f strips.

Rounding out our report on scopes is the *Ballantine Labs*. Model 1010A, a dual-trace, single-beam instrument retailing for \$595. This scope has a bandwidth of dc to 10 MHz at the -3-dB points from a 50-ohm source. The input impedance is 1 megohm, shunted by 28 pF. Featured are both alternate and chopped modes and a X10 trace magnifier.

Frequency Counters. Among the first test instruments to "go digital" was the frequency counter. These instruments proved to be invaluable to anyone who had to know the precise frequencies of such diverse signals as a digital-proportion R/C pulse train, transmitter's r-f carrier wave, and the



Fluke 1941A Digital Counter



Hewlett-Packard 5281A and 5382A Frequency Counters



Tektronix Telequipmen D61 Oscilloscope



Rallantine 5225 A Frequency Counter



Wavetek 30 Sweep Generator

clock rate of a time base. Now several OEM companies are supplying the consumer market with a variety of counters at relatively low prices.

Hewlett-Packard has two counters. The Model 5381A, retailing for \$249, has a frequency range of 10 Hz to 80 MHz. A 1-MHz internal crystal time base in this counter provides less than 0.3 ppm/month aging and ±10 ppm temperature compensation from 0° C to 40° C. Input sensitivity is 25 mV at 30 Hz to 20 MHz, and 50 mV from 30Hz up to the upper frequency limit of the counter. Input impedance is 1 megohm, shunted by a capacitance of 50 pF.

A three-position (X1, X10, X100) switch determines the input signal levels. On the X1 range, up to 5 V rms can be accommodated over the entire frequency range. From dc to 40 Hz, up to 200 V (dc plus peak ac) is permitted, and from 40 Hz to 100 kHz, 250 V rms can be applied without damage to the instrument. Gate times are manually selectable, providing resolutions of 10 Hz at 0.1-s, 1 Hz at 1-s, and 0.1 Hz at 10-s gate timing.

For even more precise counting, Hewlett-Packard sells the Model 5382A frequency counter for \$450. It offers an optional temperaturecompensated oscillator that meets FCC requirements for professional communication equipment. In addition, it has a specified top end range of 225 MHz and features temperature compensation of ±2 ppm from 0° to 40° C as well as greater sensitivity. Both H-P frequency counters can operate on an external precision time base through a built-in rear-panel connector. Input levels at these connectors from 250 mV to 25 V can be accommodated. The 80-MHz Model 5381A has a seven-decade display, while the 220-MHz Model 5382A has an eightdecade display.

Ballantine Labs.' Model 5725A 90-MHz frequency counter sells for \$325. It features frequency-counting, totalizing, and ratio capabilities. In the count mode, it is a straight frequency counter. Switching to the totalize mode, the instrument continuously counts the events (pulses) applied at the input. Separate pushbutton switches are provided for stopping and starting (or continuing) the events count and for resetting the display and logic to zero.

In the ratio mode, any signal from 5 Hz to 90 MHz applied to the front-panel input is compared to another

FOR MORE INFORMATION-

Some of the OEM companies mentioned in this article plan to sell directly to the consumer, others only through authorized representatives.

For purchasing information and detailed specifications on the instruments discussed in these pages, write to the companies at the following addresses:

Ballantine Labs., P.O. Box 97, Boonton, NJ 07005

Dana Labs., Inc., 2401 Campus Dr., Irvine, CA 92664

Data Precision Corp., Audubon Rd., Wakefield, MA 01880

Data Technology Corp., 2700 S. Fairview St., Santa Ana, CA 92704

John Fluke Mfg. Co., Inc., P.O. Box 7428, Seattle, WA 98113

Hewlett-Packard Co., 1501 Page Mill Rd., Palo Alto, CA 94304

Keithley Instruments, 2877 Aurora Rd., Cleveland, OH 44139

Systron-Donner, Datapulse Div., 10150 W. Jefferson Blvd., Culver City, CA 90230

Tektronix, Inc., Telequipment Div., P.O. Box 500, Beaverton, OR 97005

United Systems Corp., Div. of Monsanto, 918 Woodley Rd., Dayton, OH 45403

Wavetek, 9045 Balboa Ave., San Diego, CA 92123.

signal of from 10 kHz to 2 MHz applied to a rear-panel input. The display indicates the ratio between the two signals.

Fluke's general-purpose Model 1941A laboratory frequency counter that sells for \$299 has a 5-Hz to 40-MHz range, 40-mV sensitivity, and gate times of 1 ms to 1 s in decade steps (plus a 600-ms time). Resolution is 1 Hz at 1 s, decreasing to 1000 Hz at 1 ms gate times. An LED overflow indicator comes on when the six-digit display is exceeded.

The counter utilizes a highly stable 10-MHz crystal-controlled oscillator as a time-base reference. An external 10-MHz signal can be substituted for the internal time-base signal. The time base provides an aging rate of 6×10^{-7} parts/day. Temperature dependence is 10 $^{-6}$ parts over a range of 20° C to 30° C, or 5×10^{-6} parts from 0° C to 40° C.

The Model 1941A provides a totalize mode. By using external switching, the number of events occurring per minute, hour, day, week, month, or any other desired period can be counted and displayed. A BCD output and an offset input are available as options.

Unique Generators. Wavetek's Model 30 could be called "every man's sweep generator" because it has a price tag that belies its performance capabilities. Retailing for only \$149, it has a unique combination of features. It is, first and foremost, a basic sine/square-wave signal generator with a frequency range of 2 Hz to 200 kHz in three 1000:1 ranges.

Adding to the instrument's versatility are linear and logarithmic functions with fixed sweep times of 2.5 s for driving the horizontal amplifier of a scope, 250 ms for general-purpose use, and 25 ms for driving an X-Y recorder. External capacitors can be added to increase the sweep time.

The log sweep function is particularly useful in audio work for aligning tape recorder heads, making equalization tests, etc.

A high-level sine-wave output that is variable up to 1 V rms open circuit from a 600-ohm source has a specified distortion of less than 2 percent from 2 Hz to 20 kHz. Available also is a 50-percent duty cycle square-wave pulse output with nominal 0-V to 0.5-V and 3-V to 5-V TTL levels.

The rear panel of the Model 30 con-

tains a 0.8-V peak-to-peak triangle-wave output, a low-level sine-wave output, a sync pulse output, a sweep ramp output, and a generator-controlled voltage output.

The Model 30 generator employs conventional 9-volt batteries as a power supply, making it completely independent of line power. For an additional \$25, you can get an optional rechargeable battery pack and recharger unit.


For \$445, you can buy a combination frequency counter/function generator in the Model 304A from Monsanto's United Systems Corp. This rather unique instrument provides sine, square, and offset square waves over a frequency range of 10 Hz to 1 MHz in its generator function. Distortion on the sine function is specified at 0.1 percent typical. Settability and resolution over the generator's range is 0.1 Hz. Three 20-dB steps of attenuation are provided. Operated as a frequency counter, the Model 304A has a frequency range out to 15 MHz.

Systron-Donner's Datapulse Division offers a wide-range function generator in their Model 400. This \$450 generator provides sine, square, and triangle waveforms. It has a frequency range of 0.02 Hz to 2 MHz in six decade range steps.

The Outlook. It is obvious from the foregoing that today's technician and serious experimenter have available to them a wide variety of test instruments from a host of brand-name manufacturers. The OEM entry into the technician/consumer market widens the scope even farther, bringing to the average shop a prestige heretofore reserved for space-agency research and development, and military and government test facilities.

Hobbyists and experimenters must shop carefully, of course—assessing needs and analyzing available equipment. With options and accessories, some low-cost instruments may wind up more than the budget allows.

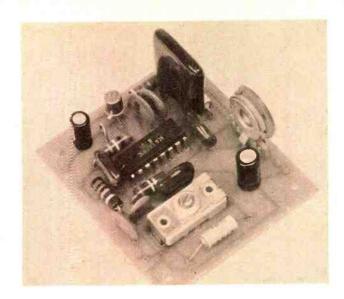The OEM incursion into the market is still very new and, as a result, only superficial at present. We predict that over the next few years, other companies will join the ranks of those OEM companies already doing business on the consumer market. We further predict that the move will bring a greater diversity in test and measurement capabilities.



BY FRANK P. KARKOTA, JR.


SCA ADAPTER REVEALS HIDDEN MUSIC AND NEWS ON YOUR FM RECEIVERS

N AN EFFORT to utilize more fully the radio spectrum, the Federal Communications Commission some time ago authorized FM radio stations to use special subcarriers to broadcast additional program material. This was covered in the FCC's Subsidiary Communications Authori-

zation — hence the letters SCA, applied to the process in general. The most common use of SCA is in the transmission of background music; but other broadcasts include detailed weather forecasting, special time signals, and other material designed and intended for special-interest

groups, doctor's offices, stores, factories, and other public places.

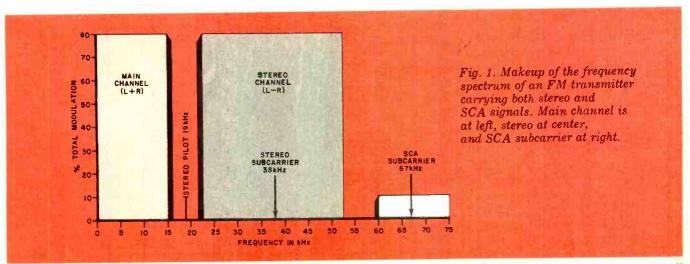Broadcasters who use SCA generally make their profits by leasing the special receivers required to detect the subcarriers. However, the SCA adapter described here will enable the owner of almost any conventional FM



receiver to listen to these broadcasts. (A word of caution: it is illegal to use SCA broadcasts for commercial purposes without written permission from the broadcaster.) Using a single IC, this low-cost SCA adapter can derive its operating power from the receiver with which it is used. In many cases, the adapter can be built directly into the cabinet with the receiver. A small pc board and simple alignment procedures make the project easy to construct and use.

How SCA is Handled. In mono FM broadcasting, the main channel transmits only audio frequencies up to $15 \, \text{kHz}$, and the transmitter/modulator is designed for this range only. For all stereo FM broadcasting, the transmitter/modulator is designed to pass not only the $15 \, \text{kHz}$ main (L + R) channel, but also a $19 \, \text{kHz}$ stereo pilot

carrier and an amplitude-modulated 38-kHz subcarrier that contains the stereo (L - R) information. For an FM station to transmit also the SCA information, it must be able to accommodate the SCA channel as a narrowband (7-kHz deviation) subcarrier centered at 67 kHz. The audio-modulation frequency spectrum for an FM transmitter carrying both stereo and SCA is shown in Fig. 1.

To extract the SCA material from this composite signal requires the equivalent of two receivers — one to demodulate the composite from the FM transmission and the other to recover only the SCA from the detected composite signal. A conventional FM receiver performs the first operation, and the output of its detector forms the input signal for the second "receiver." Essentially, the latter is in the form of a narrow-band FM receiver

tuned to 67 kHz. The audio output of this SCA adapter is used to drive an external amplifier and speaker.

How It Works. The schematic of the adapter is shown in Fig. 2. The IC is a new unit which contains a complete FM strip on a single chip. Although designed to work at the conventional 10.7-MHz i-f, this IC works well at 67 kHz for SCA.

The demodulated composite signal is applied to control potentiometer *R1*, which acts as a squelch (to be explained later). The relatively low value of *C1* provides a high-pass filter to reject the main channel and most of the stereo subcarrier. Capacitor *C2* and inductor *L1* form a tuned circuit that helps to reject noise above and below 67 kHz. Capacitors *C3* and *C4* are used as bypasses to allow one side of the tuned circuit (*C2-L1*) to remain at signal ground while current from pin 3 biases the i-f amplifiers connected to pin 1.

The internal i-f amplifiers also provide the limiting that eliminates any amplitude variations that might be present on the input signal. This also improves the rejection of the stereo subcarrier since the stereo information appears as amplitude noise.

The limited and amplified signal then enters the internal quadrature detector where capacitor C7 and the tuned circuit formed by L2, C8, and C9 form the required phase-shift network for tuning the detector. Resistor R5 connected across the tuned circuit determines the bandwidth of the detector. The detected signal then drives a squelch-controlled audio preamplifier (also on the chip) and a set of level detectors in each i-f amplifier that provides a dc output proportional to the log of the input signal. This dc voltage is applied through R2 to the base of Q1, while C5 removes any 67-kHz component that might be included. When a predetermined signal level appears at the input to the i-f arnplifiers, the base current of Q1 causes it to saturate. Resistor R3 forms the load for Q1. When Q1 saturates, the low emitter-to-collector voltage cannot squelch the internal audio system. When the signal level drops below the predetermined level, Q1 is cut off; and its output signal (at pin 5) is sufficient to operate the internal audio squelch.

The recovered audio output (pin 6) is de-emphasized by R4 and C10 while C11 blocks the dc component from the audio output.

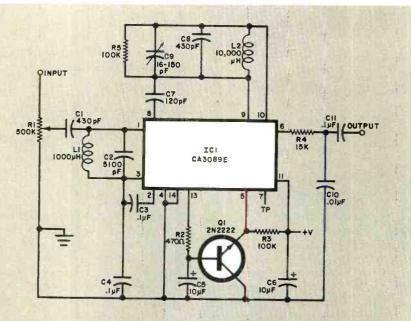


Fig. 2. Single IC contains a complete i-f system, a quadrature FM detector and an audio amplifier.

PARTS LIST

C1, C8—430-pF, 5%, silver-mica capacitor C2—5100-pF, 5% silver-mica capacitor C3, C4, C11—0.1-µF, 10-volt disc capacitor C4, C6—10µF electrolytic capacitor C7—120-pF, 5% silver-mica capacitor C9—16-150-pF trimmer capacitor (Arco 424 or similar) C10—0.01µF disc capacitor IC1—CA3089E L1—1000-µH, 5% inductor (Nytronic WEE-1000 or similar) L2—10,000-µH, 10% inductor (Nytronic

WEE-10,000 or similar)

Q1—2N2222


R1-500,000-ohm trimmer potentiometer (CTS X-201 or similar)

R2-470-ohm, ½-watt resistor

R3, R5—100,000-ohm. ½-watt resistor R4—15,000-ohm, ½-watt resistor

Misc.—Power supply, interconnecting shielded cables, pc board, optional mounting hardware, etc.

Note—The following are available from Communications Poly Services, 46 Groton Rd., Westford. MA 01886: etched and drilled pc board at \$2.10; complete kit of parts at \$11.95, both postpaid. Massachusetts residents, please add 3% state sales tax.

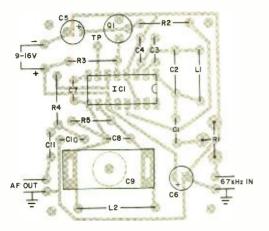

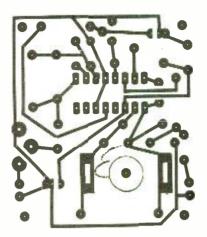


Fig. 3. Actual-size foil pattern and (far left) component installation. Observe polarities on electrolytics.

Construction. Although there are no r-f signals present, the high gain of the IC makes parts placement in the circuit somewhat critical. A pc board is therefore recommended (Fig. 3). When the tuning capacitor, C9, is installed, the side of the capacitor having the top plate should be closest to capacitor C6. Observe the notch code on IC1 and the polarities of the two electrolytic capacitors.

The test point is simply a small loop of bare wire, soldered into the board at the point (TP) shown in Fig. 3.

The demultiplexer requires between 9 and 16 volts dc at 20 to 30 mA. If it is not available from the conventional receiver, a small supply can be built using the circuit shown in Fig. 4.

Alignment. Use shielded cable to connect the adapter input to the FM receiver. If you are lucky, the FM stereo receiver will have a phono jack marked "detector out," "composite out," "output to MPX adapter," "output to stereo adapter," or some variation of these. If the receiver does not have this jack, or if it is a mono receiver, a connection must be made to the FM detector before the deemphasis network. Make the connection as shown in Fig. 5. Connect the output of the SCA adapter to the ex-

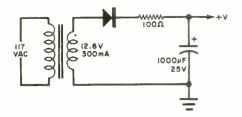


Fig. 4. This power supply can be built if not available elsewhere.

ternal audio amplifier and speaker.

Before applying power, temporarily connect a short circuit between the emitter and collector of Q1. Adjust variable capacitor C9 for half mesh, and set potentiometer R1 fully clockwise (rotor at input end).

Connect a dc voltmeter from the test point to the side of C9 closest to C6. Turn on the FM receiver and apply power to the SCA adapter. When the FM receiver is tuned across the band, noise and distorted main-channel programming will be heard on those stations not carrying SCA. When a station carrying SCA is tuned, this material will be heard. Adjust C9 for zero volts on the dc voltmeter. If a dc voltmeter is not available, adjust C9 for best results.

Remove the temporary short across Q1. If the audio output drops away when this is done, the SCA adapter is receiving too little signal. Check the connection to the FM receiver to make sure it is properly made.

The internal squelch circuit is used to quiet the SCA adapter between music selections in the event that the station making the SCA broadcasts turns off the subcarrier between selections. In this case, adjust potentiometer *R1* to silence the noise between selections.

The ultimate quality of the demultiplexed SCA signal is largely a function of the FM receiver. It is important to have a strong signal, as free of multipath as possible. It should be noted that the signal level required for noise quieting increases as the bandwidth of the received signal increases. It is for this reason that a stronger signal (compared to a mono transmission) is required for adequate reception of stereo broadcasts; and an even


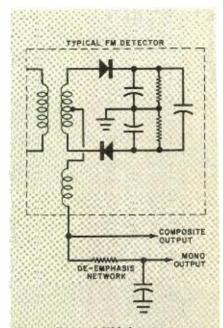


Fig. 5. Typical FM detector showing where the composite output can be taken out.

stronger signal is required when an SCA subcarrier is added. Note, also, that any distortion (such as phase) present in the FM receiver will appear in the demultiplexed signal as crosstalk.

Modifications. There have been rumors of a proposal to reallocate the FM subcarriers to accommodate four-channel sound. If this comes about, or if you hear of any frequency other than 67 kHz being used for the SCA subcarrier, the SCA adapter described here can easily be modified for the new frequency by changing the value of two capacitors. For C2, the value is $10^9/(4\pi^2f^2)$; and for C8, use $10^8/(4\pi^2f^2)$ —70; where C is in picofarads and f is in kilohertz.

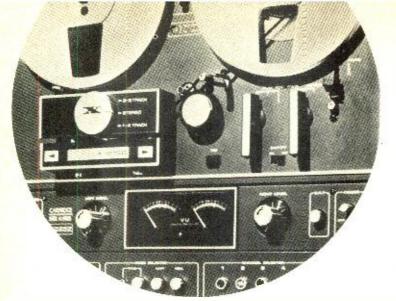

HOW TO EVALUATE TAPE RECORDER SPECS

BY JULIAN D. HIRSCH Hirsch-Houck Laboratories

T ECHNICAL terms and figures cited in test reports and manufacturers' literature on tape recorders may confuse some prospective buyers. Presented here are the major ones used to judge a tape recorder's performance, with explanations and observations to clarify their true meanings. Though test conditions are rarely specified by manufacturers, we will detail those used in our Hirsch-Houck Laboratories evaluations given in the Product Test Reports in Popular Electronics.

Frequency Response. One of the first specifications one looks for in evaluating a tape recorder is its frequency response. As a minimum, a frequency-response specification should include the range limits, variation over the specified range, and tape speed (for example, 40-20,000Hz ±3 dB at 7½ ips). The frequency response also depends on the tape used, but with most open-reel recorders, this is not very critical.

Most tape recorders cannot achieve their rated frequency response at maximum recording level, especially at the lower tape speeds. This is due to saturation of the magnetic coating on the tape at the higher frequencies that are boosted by the recording equalization and appear as a roll-off of high-frequency response. As a result, it is customary to measure frequency response at a lower level (not more than -10 to -15 dB).

Recorders differ considerably in their susceptibility to high-frequency tape saturation. The recording equalization, a key factor, is rarely (if ever) specified and cannot be measured from outside the machine. The easiest way to judge a recorder's high-frequency "head-room" is to measure its frequency response at 0 dB and at a lower level (such as -20 dB.) The smaller the difference in high-frequency response between the two measurements, the better the recorder in this respect.

In the Hirsch-Houck Labs tests that appear in this magazine, we record at -20 dB, using a sweeping oscillator and play back into a chart recorder that is synchronized to the frequency sweep. Similar results, with less resolution, can be obtained by recording spot frequencies and reading the playback levels on a meter.


Cassette recorders present special problems. The high-frequency recording equalization is greater than that used in open-reel machines, and the test level should not exceed -20 dB. One manufacturer even recommends a $-30\,dB$ level for testing his recorder. For best results in any tape recorder, the recording bias should be matched to the tape characteristics. This is absolutely vital with cassette recorders. Not only must the bias be set for the type of tape, it must also be set for the specific brand. (With reference to the latter, bias set for chromium-dioxide tape from one manufacturer need not

be reset for another manufacturer's tape since there is so little difference among brands of CrO₂ tapes.)

A frequency-response rating of "40-20,000 Hz ± 3 dB" means that the output can vary a total of 6 dB from maximum to minimum within the specified frequency range, in this case, 40-20,000 Hz. Without an actual response curve (rarely supplied by the manufacturer but included in most equipment test reports), one cannot assume that two recorders with identical ratings will sound alike. One recorder may have a rising response at the high end and sound "bright." Another, still within the ±3-dB rating, could have a falling high-frequency response and sound subdued or even dull. Between the extremes, there are an infinite number of response variations that can be defined only graphically. If the variations were small, such as ± 1 dB, the ratings could be compared with greater validity. But most recorder manufacturers use a broader tolerance to encompass the wider range of variations found within an extended range of frequencies.

Another aspect of recorder frequency response that is not always specified separately is *playback* response. This parameter indicates the accuracy of a recorder's playback equalization and its suitability for playing commercially recorded tapes or tapes made on another recorder. Playback response is measured with a standard test tape, which usually has a

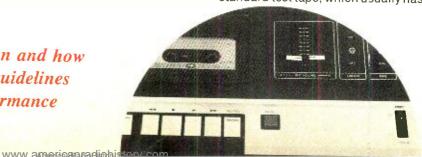What the specs mean and how they're determined provide guidelines to product performance



relatively limited range compared to the coverage of most of today's recorders. Typically, these are 50-15,000 Hz at 7½ ips, 50-7500 Hz at 3¾ ips, and 31.5-10,000 Hz for cassettes.

Distortion. Tape recorder distortions are difficult to summarize in a single specification because they vary widely with level, frequency, and the nature of the test signals. At middle frequencies (such as 1000 Hz), the total harmonic distortion (THD) is easy to measure. At frequencies exceeding one-half to one-third of the recorder's maximum response frequency, the harmonic levels in the playback will be reduced or eliminated by the deck's inherently limited response so that THD cannot be used to measure nonlinearity at the higher audio frequencies where it is most serious. Two-tone intermodulation (IM) distortion measurements are needed for this, but there is no universal standard for such tests at present.

The THD ratings published for tape recorders (such as "less than 1 percent") can be assumed, in the absence of other information, to be measured with a 1000-Hz signal recorded at an indicated level of 0 dB on the recorder's meters. This is the procedure followed at Hirsch-Houck Labs, and we believe it to be typical of industry practice. Since distortion is also affected by tape speed, it should be specified at each operating speed.

As with many other tape recorder specifications, distortion can also be affected by the type of tape used. Fortunately, in the case of open-reel recorders, the differences are minor within any one classification of tape. Most manufacturers do not specify the tapes used in their own tests, but our test reports do. In the case of the cassette recorder, the tape is a critical

factor and *must* be known for any interpretation of the ratings.

Signal-To-Noise Ratio. The dynamic range of a tape recorder is limited by the maximum level that can be recorded and played back with an acceptable distortion and by the residual noise level in the playback output. The ratio of these two levels is known as the "signal-to-noise" (or S/N) ratio and is expressed in decibels (dB). Strictly speaking, it is the signal plus noise-to-noise, or (S+N)/N, ratio, but in this case, the difference is minor.

Usually, a single figure like "55 dB" is given as the S/N rating. Implicit in such a rating is a specific—but often unstated—distortion level at maximum signal input. A THD of 3 percent is generally used as a reference for S/N rating of home tape recorders.


As with all hi-fi components, the distortion of a tape recorder increases as the program level increases, especially near the recorder's maximum capability. However, one cannot assume that 3-percent THD will coincide with a any ''0-dB''—or other maximum-recording level on the deck's meters. As a rule, the reference distortion will be reached with an input of +3 to +6 dB, allowing some recording "headroom" for brief peaks that might not register on the meters. In the case of cassette recorders, the headroom is usually not more than 2 or 3 dB at middle frequencies (and sometimes considerably less) and reduces greatly at higher frequencies due to the greater recording equalization necessary to achieve a wide frequency response.

The audible noise level in the playback output consists mostly of hiss or wideband random noise. There will usually be some low-frequency noise (such as power-line hum) as well. But this is much less audible due to the characteristics of human hearing. An unweighted noise measurement responds equally to hum and hiss and may give an unduly pessimistic result in terms of the subjective character of the noise. Hence, it is customary to "weight" the noise measurement to discriminate against the less-audible low and high frequencies. Sometimes the weighting curve is specified-such as "ANSI A"-but often it is not. As with flutter, S/N ratings can only be compared when they are based on the same reference distortion and noise-weighting characteris-


Crosstalk And Separation. These are two different manifestations of the same effect—leakage of a signal from one track of the tape to another. This leakage is largely a function of head design, but it can also occur in the wiring to the heads and in the recorder's electronics.

Crosstalk and channel separation are usually specified at a middle frequency, such as 1000 Hz, although they vary with frequency. Crosstalk is the more serious from a listening standpoint. It is a transfer of signal from one pair of tracks to the other. When playing the tape in the forward direction, the second pair of tracks is being played backwards, and the crosstalk will be in the form of noise or garbled sounds with no relationship to the desired program.

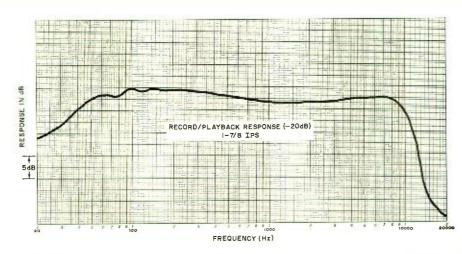When the leakage occurs between the two stereo channels in the same direction of tape travel, its only effect is to slightly dilute the audible separation of the program. Since any tape recorder is likely to have much better channel separation than the program being recorded actually requires, this "problem" is trivial. Typical specifica-



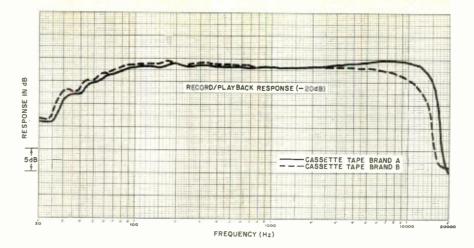Response of a high-quality open-reel recorder at 1 7/8 ips. This is good for an open-reel recorder at this speed. Cassette recorder at same speed would be as good, if not better. Curves show difference in over-all frequency response for two types of cassette tape (with same bias setting).



tions for a high-quality recorder might be: crosstalk more than 60 dB at 1 kHz; separation more than 50 dB at 1000 Hz.

Wow And Flutter. These are the audible effects of frequency modulation of the program material caused by uneven tape motion across the heads. When the speed fluctuation occurs at a low rate (less than 10 Hz), the characteristic "wow" sound can be heard. This is especially apparent on tones of extended duration, such as the organ and the decay of piano notes. Faster rates, up to 200 Hz or more, are heard as "flutter"—a slight muddying of the sound and, in extreme cases, a "gargling" quality.

Wow and flutter measurements are frequently combined in a single flutter rating, expressed as a percentage of frequency modulation. For example, a 0.2-percent flutter will cause a 1000-Hz tone to vary between 998 and 1002 Hz. Higher and lower frequencies will be affected proportionately. The audibility of flutter depends on several factors, including: magnitude, rate, and program material (duration and frequency range of tones).

The human ear is most sensitive to

flutter affecting frequencies in the vicinity of 3000 Hz, which is why a 3150-Hz frequency is now generally used for flutter measurements. Standard test tapes are recorded with a 3150-Hz tone that has very low intrinsic flutter, typically less than 0.02 percent. The tape is played on the recorder and its output is measured with a flutter meter, a device that is essentially a calibrated FM receiver that is fixed-tuned to 3150 Hz and contains a meter that indicates the percentage of frequency modulation.


Unweighted rms flutter measurements respond equally to flutter rates over a wide range (such as 0.5 to 10 Hz for wow, 10 to 200 Hz for flutter, or 0.5 to 200 Hz for a combined measurement). Since the most audibly objectionable flutter rates occur between 1 and 10 Hz, current IEEE standards call for a weighted peak flutter measurement, emphasizing the frequency range and reducing the contribution of higher and lower frequencies to the final measurement. Some recorder manufacturers use a similar weighting curve applied to rms rather than peak measurements. These are usually identified as "Wrms" flutter measurements.

Weighted readings are always less than unweighted readings, usually by 20 to 30 percent. A peak measurement will always be greater than an rms measurement. A comparison among published flutter ratings for different recorders is valid only if the same technique is used in all cases.


Cassette recorders are tested in the same manner, except that presently available test cassettes have a residual flutter level between 0.1 and 0.2 percent, which is more than that claimed for the latest recorder designs. To test cassette decks, a standard test tone is recorded and played back into the flutter meter. Some flutter is introduced when recording and some during playback, adding to or cancelling each other at different times. By taking several readings and averaging the results, it is possible to establish an approximate flutter rating.

In multispeed recorders, flutter is usually less at the higher speeds. Bidirectional recorders may exhibit slight differences in flutter when running in forward and reverse directions due to variations in the tapetensioning and guidance system. As a rule, these effects are minor.

In most cases, a flutter level of 0.1

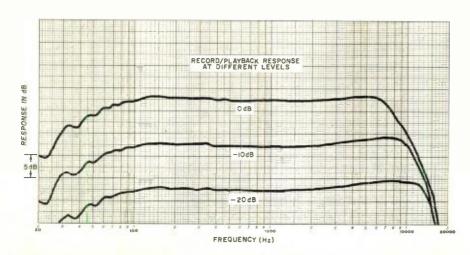

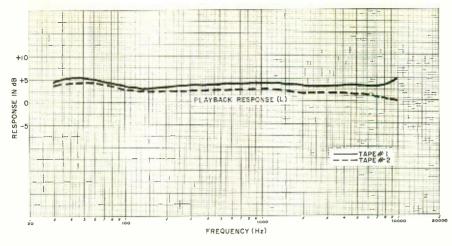Effects of recording level on frequency response of a cassette recorder. Testing level is usually -20 dB.



The playback response of a cassette recorder using two different samples of the same test tape.

percent or less will not be audible. Most of the better open-reel recorders and a few cassette decks can meet this requirement. Typical good cassette recorders have 0.15 to 0.25 percent flutter, while low-priced open-reel decks fall into the same range. With some types of music, this can be audible; but, in general, it would be apparent only to a critical listener. Flutter levels exceeding 0.3 percent are not consistent with high-fidelity reproduction.

Miscellaneous. There are a number of tape recorder characteristics that are never mentioned in published specifications. Most of them are probably of little interest to the average user, who can generally obtain the information from the manufacturer. But a few items that might be meaningful to the home recordist deserve mention.

Meter Characteristics. The level meters of many recorders are labelled as being "VU," usually incorrectly. The VU stands for volume unit, and the characteristics of a VU meter are detailed in an IEEE/ANSI specification. These include a frequency response within ± 0.5 dB from 25 Hz to 16,000 Hz

and a 0-VU reading corresponding to 1mW at a specified impedance (usually 600 ohms). When a signal that will result in a 0-VU reading is applied, the meter pointer should swing to 99 percent of that reading in 0.3 second, with an overshoot of 1 to 15 percent, and should return to rest in approximately the same time when the signal is removed.

Typical home-recorder meters rarely have the ballistic characteristics of a VU meter and are more correctly labelled as "dB meters" (assuming that their dB calibrations are correct, which is not always the case). In our recorder tests, we apply toneburst signals to check the response of the meters. Some meters overshoot considerably, but most are too slow and indicate considerably less than a true VU meter on transient signals.


It is important to know the general response characteristics of a recorder's meters to be able to allow sufficient reserve range for brief program peaks. Most meters, including true VU meters, are average-responding devices and will not indicate the peak level of the signal. Some recorders have peak-reading meters that are able to respond in a few milli-

seconds. In some units, the meters indicate the outputs of the recording amplifiers, thereby including the effect of the equalization and reducing the likelihood of over-recording a signal containing strong high-frequency content.

Microphone Input Dynamic Range. The noise level of a good open-reel recorder, or a cassette recorder equipped with Dolby noise reduction circuitry, is negligible for most practical purposes. When taping from records or FM tuners, the noise in the input signal will usually exceed that introduced by the recorder.

A notable exception is the case in which microphones are used for "live" recording. Assuming that ambient background noise is low and that precautions have been taken to eliminate hum pickup, the noise (hiss) in the recorder's microphone preamplifiers will often be unpleasantly audible, especially when operating near maximum gain. Although no recorder manufacturer known to us specifies the noise contribution of his microphone amplifiers, our lab tests include a check of the increase in noise at maximum and at lower microphone gain settings.

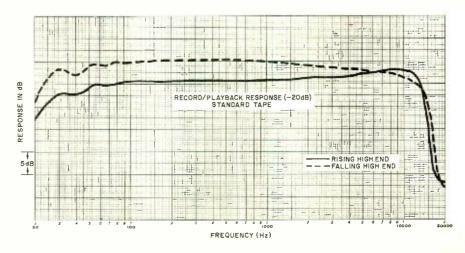Response curves for two recorders with almost identical specs. However, recorder with solid-curve response has a rising high end and would sound brighter than recorder with dashed curve, which has droop at the high end.






HE design of most commercial synthesizers is based on the original RCA and Moog systems — a series of keyboard-controlled vco's and vcf's interconnected through patch cords, matrix switches, relays, or stop-like fixed presets. The majority have only one- or two-note-at-a-time capability, although the latest designs are beginning to go truly polyphonic.

At present, synthesizers fall into several broadly defined categories: studio models, live-performance models, economy build-it-yourself kits, and individual modules.

Studio Models. Synthesizers for recording studios are the most expensive, featuring as much in performance and variations as can possibly be offered. However, they are not really suitable for live performances. Typical of the synthesizers in the studio category are several custom Moog units (see box on page 51 for manufacturer and supplier addresses), the Synthi 100 from Electronic Music Studios, and the ARP 2500 from ARP Instruments.

Live-performance synthesizers are usually offered through music stores for retail prices ranging from a low of about \$900 to a high of \$3000 or more. Currently popular versions are the ARP Odyssey and Soloist, the Minimcog, and EMSA's Electrocomp 101 (made by Electronic Music Labs., Inc.), and the lonic Performer

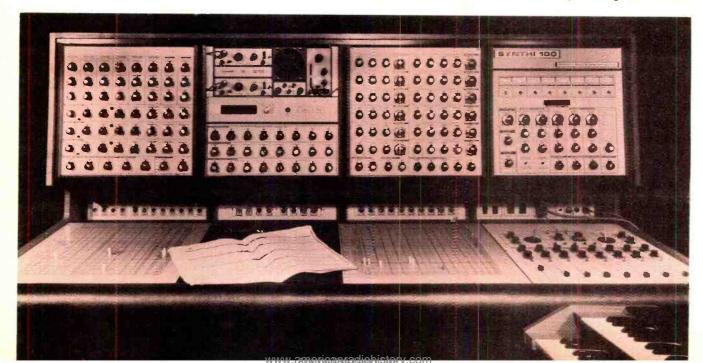Prices for these synthesizers are somewhat high, but they are comparable to what you would have to pay for other quality musical instruments, and much less than for most electronic organs. At present, the prices are high because the synthesizers are sold and serviced by retail music stores, because much engineering cost must be



MORE EM BOOKS

Organ Building, R.L. Eby. This is a complete handbook on electronic organ and synthesizer parts and pipe-organ materials. It costs \$3 from Newport Organs, 486 Production Place, Newport Beach, CA 92660.

Musical Acoustics, C.A. Culver. Discussed in this book are the basics of all musical instruments, timbre, tone production, harmonic structures, etc. The book was published by McGraw-Hill Book Co. in 1956.

Music, Physics, And Engineering, H.F. Olsen. An updated version of the out-of-print *Musical Engineering*; it includes material on much of the original RCA synthesizer experiments. The book was published by Dover Publications in 1967.


Psychology of Music, C.E. Seashore. Published by McGraw-Hill Book Co. in 1938; you may have to hunt through the shelves of a large library to find a copy of this book. In it you will find discussions on instruments, their tonal structures, and how music is interpreted.

SYNTHESIZER MANUFACTURERS

The following is a list of addresses of the manufacturers and suppliers of commercial synthesizer products mentioned in the text:

ARP Instruments, 320 Needham St., Newton, MA 02164
Electronic Music Laboratories, Inc., Box H, Vernon, CT 06066
Electronic Music Studios, 460 West St., Amherst, MA 02164
Εμ Systems, 3455 Homestead Rd. #59, Santa Clara, CA 95051
Ionic Industries, 128 James St., Morristown, NJ 07960
Moog Music, Inc., Box 131, Williamsville, NY 14221
PAIA Electronics, Box 14359, Oklahoma City, OK 73114
Southwest Technical Products Corp., 219 West Rhapsody, San Antonio, TX 78216

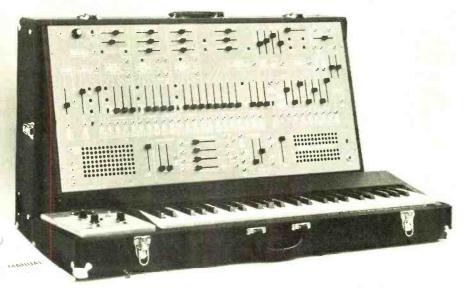Total Technology, Box 828, Belmont, CA 94002



ARP Instruments Model 2600 (above) costs about \$2800

The EMSA Synthi 100 (opposite) is complete professional studio model (\$20,000 up).

amortized over a relatively few units, and because, when these instruments were designed, components and techniques were far more expensive and complex than they are with today's IC's

If you question that last statement, consider that you can get four analog switches that double as sample/hold devices in the RCA CD4016 for only \$1.50. Just \$2.50 will buy a three-waveform vco with extreme stability in the Intersil 8038. Motorola's MC14049 gives you a hex analog switch that doubles as a hex vca for only \$2, and their MC1408 8-bit D/A converter sells for \$5. RCA's CD4046, another \$5 IC, can be used to make a phase-locked loop tracker. In addition, the price of the 741 operational amplifier IC, the mainstay of all EM, now sells for less than 50c.

Another frequently overlooked cost factor is that the switches, patches, controls, etc. used in synthesizers are expensive items in the quantities required for EM systems. And don't forget that the cabinet is another high-expense item.

Once the newer IC's are put to use in synthesizers and all-digital tone generation schemes are prevalent, we can reasonably expect prices to drop drastically. But even if the prices remain the same, there should be considerably more in the way of performance from the instruments.

Basic Models. The third synthesizer category is the bare-bones kit type. PAIA Electronics, with their Model 2720 that sells for \$200, is a good example of such a system. The least expensive synthesizer (actually a composer) you can buy is the *Psychtone* from Southwest Technical Products Corp. It sells for \$53.

The fourth route to synthesizers is the use of modules to build up a custom system that does exactly what you want. Two leaders in this field are E μ Systems (their catalog is \$5, which is refundable with your first order) and Total Technology.

Buying Hints. This seems to be the overall picture as we see it. If you are interested in the commercial gear, try to arrange a live demonstration so you can compare several different makes and models. Better yet, try to rent a synthesizer or use it on a lease/purchase basis to make certain that it meets your specific needs. In short, if possible, try before you buy.

INDOOR 20-METER HAM ANTENNA

BY ROLAND J. MCMAHAN

Author pulls in overseas contacts easily with 6-ft. home-brew antenna

MATEUR RADIO contacts from the west of North America to Europe are not unusual on 15 and 20 meters. But when they are made using a 6-ft (1.83-m) long coil of wire sitting on a desk as an antenna, that's something new and different. With just such an antenna, this author was able to contact Northern Ireland, France, and Costa Rica in a few short minutes—which is a little out of the ordinary.

Such an indoor ham antenna will be of great value to apartment dwellers and travellers who do not have the space in which to erect a more elaborate antenna. Add to this the fact that the antenna has a minimum of TVI and a high signal-to-noise ratio. It can be fabricated at a minimum of cost

How to Make the Antenna. To fabricate the indoor antenna, wind 22 turns of #14 stranded wire around the outside of a 2-in. (5.08-cm) innerdiameter plastic pipe. (You can get the pipe at most hardware stores.) The pipe should be 6 ft (1.83 m) long. The preferred type of pipe to buy has holes through it and is used in septic-tank drain-line applications. You can use the holes to tie or hold the ends of the coil.

Other than winding the 22 turns of wire, there are two rules that must be observed when making the antenna: (1) The top turn must form a closed loop and be soldered to assure good electrical conductivity and mechanical strength. (2) When connected to the ground or counterpoise system, the antenna must resonate on the 20-meter band.

The second rule is the only difficult part of the fabrication process because not all ground systems are the same. In this step, you will have to use a dip oscillator to find the resonant frequency.

If you try to use this 20-meter antenna on 15 meters as well, you will find that the response is too sharp for this. However, you can tap the coil five turns up from the bottom to obtain 15-meter operation. Slide the first five turns together so that they are closely wound before completing the 20-meter antenna. The remaining turns can be randomly wound, some

as much as 8 or 10 in. (20.3 or 25.4 cm) apart.

To adjust the antenna to 20 meters, you might try sliding the top four turns close together, about 10 in. (25.4 cm) from the top. Sliding the turns down lowers the resonant frequency, as does close winding. Your own adjustments will depend on your ground system and the local capacity of the ground.


Final Steps. When the resonant frequency appears to be at about 14.2 MHz, you are ready to connect the ground and antenna to your station. Use an SWR meter at the antenna connection. The ground connects to the coax fitting at the transmitter side of the SWR meter.

Check the SWR on 20 meters, using low power. If it is 1.2:1 or lower, the antenna is ready to put into service. If not, check the SWR at the lowest and highest ends of the band; a lower reading on the high end means the resonant frequency is too high, and vice versa. Slide turns until you obtain a reading that is very low at 14.2 MHz. Tape some turns to prevent them from slipping.

When you use the antenna on receive, do not be surprised at how much quieter the band appears to be as static is greatly reduced by the very high Q of the antenna. Signals may also appear to be much stronger than you are used to, and the receiver's antenna tuning control may be more effective than it was with other antennas.

This is a quarter-wave, current-fed, low-impedance antenna system. It works best on the 50-ohm output of a transmitter. If you decide to hoist the antenna to the top of an outside pole, use ac line ("zip") cord or coaxial cable as the transmission line. Con-

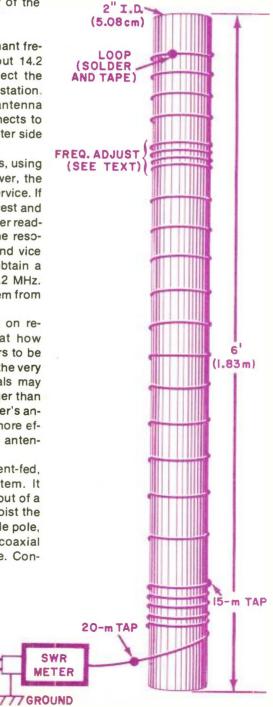nect the ground side of the transmission line to the metal pole, and use some ground radials, making each radial long enough to total 17 ft. (5.17m) when added to the length of the pole. Resonance is all-important; so, work with the antenna until it is properly resonant.



HE SECRET ambition of a great many shortwave listeners is to single-handedly uncover a piece of international intrigue. The radio waves themselves offer enormous opportunities to do just that. For example, beginning with a single piece of unusual transmission during the Cuban

DX'ING THE

with anti-Castro slogans and fictitious orders to those same fictitious guerillas. Then, in October 1961, Radio Libertad commenced transmissions on that very same frequency (while at almost the same time Radio Swan became Radio Americas and the Defense Intelligence Agency was created

CLANDESTINE SHORTWAVE STATIONS

missile crisis, when Radio Americas switched ID's with VOA sites (including the historic one at Brentwood, now of ITT SW facsimile fame), we determined that it was primarily a military, rather than a CIA, operation. We further learned that it was capable of transmitting from secret locations other than its publicized Swan Island site. Now these conclusions have been confirmed by none other than E. Howard Hunt of Watergate fame.

Of course, Radio Swan has faded into the past (the same can't be said for Hunt and his Bay of Pigs book, Give Us This Day), but many other clandestine broadcast operations are still in business. Any one of these clandestine operations can prove to be the Radio Swan of this decade. All you have to know is where and when to listen for sudden changes in signal strength, schedules, and format.

Radio Free Russia. Although it has never received the publicity enjoyed by the CIA's Radio Free Europe and Radio Liberty, Radio Free Russia could become one of the most important operations of the 1970's, now that the CIA's clandestine broadcast role has been substantially reduced. Operated by the right-wing National Alliance of Russian Solidarists (or NTS in Russian), Radio Free Russia began with a low-powered portable transmitter in West Germany, A decade later, it was claimed that the same transmitter was still being used, but shortly after the Cuban missile crisis, a major expansion got under way.

Starting about the latter part of 1962, Radio Free Russia's programs were aired over transmitters belonging to the Taiwan government -Broadcasting Corporation of China—and those belonging to Radio Caribe in the Dominican Republic with Radio-TV (now merged

Tune in on international intrigue

BY C. M. STANBURY II

Dominicana). But it was an off-spring of Radio Swan-Radio Libertad-that became the most effective outlet for

According to Hunt's book, the original Bay of Pigs blueprint consisted of three parts. First, a Cuban expeditionary force would establish a beach head and "government-in-arms." Second, Radio Swan, transmitting from Swan Island "and elsewhere." would broadcast appeals for help on behalf of the government-in-arms. Finally, with these widely heard Radio Swan broadcasts as justification, there would be massive Pentagon intervention. Someone, apparently the newly elected President John F. Kennedy, cancelled all but the first part of the plan. When that failed, Hunt tells us that he and the Chief of Propaganda Operations "issued one communique. . . It denied there had been an invasion, downplaying the assault as a resupply effort to guerillas in the Escambray." What Hunt doesn't tell us is that at 2300 EST the next night (April 20, 1961), "Radio Escambray Libre" appeared on 7000 kHz as an entity completely separate from


The French Connection. The easiest way to QSL Radio Libertad was always to log them while carrying Radio Free Russia's programs and send your report to NTS at their French address, 125 bis rue Blomet, Paris 15. Before Radio Libertad faded from the scene in 1968, the same year Radio Americas went silent, NTS was verifying all Radio Libertad transmissions from a Venezuelan address.

Meanwhile, until early in 1974, Radio Free Russia's Bavarian transmitter site was heard from time to time in North America prior to 1500 EST sign-off on heavily jammed frequencies varying between 11,400 kHz and 6350 kHz. Now, these two transmitters have also gone silent. Apparently, the government of West Germany has cancelled their transmitting privileges in the interest of detente with Moscow. This raises a question for the SWL that could turn out to be as historically important as the truth about Radio Swan/Americas: Where and in what form will NTS reappear?


The North American SW Association provides a possible clue. They report one "Radio Omega," a religious organization that formerly shared the NTS West German transmitters. broadcasting over Radio Monte Carlo. Although nominally a commercial station RMC is controlled through a complex corporate structure by the French government. RMC has two SWBC frequencies of its own-6035 kHz and 7135 kHz-and feeds programs to an MW relay on the island of Cyprus in the Mediterranean via various SW point-to-point channels. It leases a pair of 100-kW SWBC transmitters to the evangelical Trans World Radio, whose schedule also includes programs in Russian.



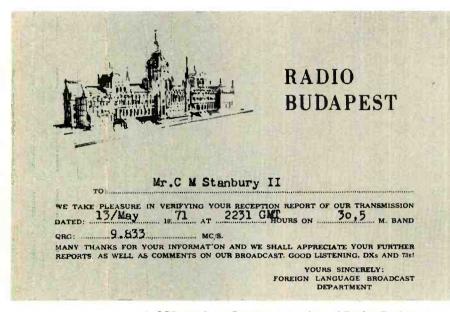Map from a pamphlet advertising Radio Free Russia transmissions over R. Caribe in the Dominican Republic.



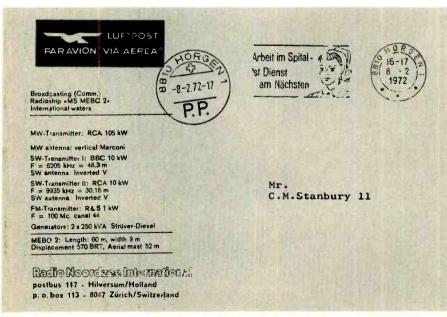A QSL card confirming reception of Radio Budapest while it was carrying R. Espana Independiente transmissions.



Radio Northsea International QSL card.

In And Around Venezuela. Radio Caribe in the Dominican Republic began its career as Radio Liberacion de Venezuela, an operation that culminated in the attempted assasination of the then Venezuelan President. Romulo Betancourt. It is also certain that one of the sites used for NTS's Radio Libertad was in or near Venezuela, although for a time they probably also used a non-Venezuelan location. Today, the most widely heard clandestine station in the Americas operates from a location in or near Venezuela. Radio Euzkadi, beaming Spanish- and Basque-language broadcasts to Spain in the late afternoons (EST), transmits on frequencies varying from 13,250 kHz to 12,070 kHz.

As in the case with NTS, Radio Euzkadi's key address is in France: B.P. 59, Poste Centrale, 75790-Paris, Cadex-16. But this is where the similarity between the two broadcasters appears to end. Unlike the rightist NTS. Radio Euzkadi can best be described as "liberal left" but is, nevertheless, in direct competition with the Marxist Radio Espana Independiente.

Interchangeable ID's. With so much competition on the SW frequencies nowadays, including deliberate jamming, high power has become increasingly more essential for successful clandestine operations. Except when used as a cover like Swan Island, the days of the exotically isolated, low-power site used exclusively for a single clandestine purpose (for example, the NTS base in the Bavarian forest) are passing away. Thus, Radio Espana Independiente used transmitters owned by Radio Bucharest on, for example, 12,140 kHz until sign-off at 1810 EST. The same transmitters are also used for Radio Portugal Livre (12,005 kHz between 1820 and 1850 EST), although Radio Bucharest denies involvement in clandestine activities. Similarly, Radio Peyk-e-Iran (Radio Courier of Iran) uses at least one transmitter belonging to Radio Sofia between the hours of 0930 and 1310 EST on 11,695 kHz.

Just as Radio Swan, Radio Americas, and Radio Libertad were either intended to or did in fact operate from more than one transmitter site, so do the Communist clandestine stations. In the mid-1960's Radio Espana Independiente was noted sharing a transmitter with one of the Soviet home services and in 1971 used one of Radio Budapest's transmitters for a short time. Peyk-e-Iran has an outlet on 11,415 kHz that, unlike the more readily heard 11,695-kHz channel, may emanate from a Soviet location in central Asia.

Because big-league clandestine operations have access to a multitude of high-power transmitters at a variety of locations, they can greatly expand their coverage whenever the action heats up. Such an expansion, especially when it occurs suddenly, is precisely what the SWL should be listening for. It indicates covert major-power involvement in the crisis and, therefore, history in the making.

White, Black, and Grey. There are three classifications into which the intelligence community officially divides clandestine broadcast stations. A black operation is one in which there is a major element of deception. It now appears that as soon as *Radio Swan* came on the air in May 1960, a CIA agent leaked word to the DX community that it was officially classified as "black," and this is what originally started the debate among radio clubs as to the real nature of the station.

The only thing clandestine about a white station is that its broadcasts are illegal in the country to which they are beamed. Of course, if a station transmits from the country to which it is beamed, then the transmitter site is also kept secret—for reasons of security rather than deception. Nearly all the clandestine stations in the Near East and Africa are white operations.

In other parts of the world, the majority of clandestine operations are various shades of grey. Radio Bucharest denies airing Radio Portugal Livre transmissions, but RPL does not hide its eastern Europe support. As long as Radio Free Europe and Radio Liberty hid their CIA funding, they were grey. The Bonn government's own Voice of Germany officially leases time from Radio Trans Europe in Portugal, along with Radio Canada International and various religious organizations, but according to informed sources, V of G actually owns RTE.

Medium-Wave Operations. The standard AM broadcast band has often played parts in clandestine operations. Hence, it shouldn't be overlooked by the serious SWL. For example, this author's observations of VOA's missile crisis station on Dry Tor-

CLANDESTINE & CLANDESTINE-RELATED STATIONS FOR THE BEGINNER

Frequency (kHz)	Station Identification	Remarks
6035	R. Monte Carlo	Listen for new or expanded Russian programs
6205	R. Northsea International	May have left air or changed ID
6240	R. Libertacao	Until 1800 EST sign-off
7135 9505	R. Monte Carlo Radio-TV Dominicana	Same as RMC above Includes facilities of former R. Caribe/ Free Russia/Liberacion de Venezuela
9615	R. Canada Inter- national, relayed by R. Trans Europe (Sines, Portugal)	2245-2300 EST in Russian; site reported to be secretly owned by W. German government
11,415	R. Peyk-e-Iran	1310 EST sign-off; site unknown
11,695	R. Peyk-e-Iran	1310 EST sign-off; uses R. Sofia transmitter
12,005	R. Portugal Livre	1820-1850 EST; uses R. Bucharest transmitter
12,070*	R. Euzkadi	1430-1500, 1530-1600, 1630-1700 (all EST)
12,140	R. Espana Independiente	Until 1810 EST sign-off; uses R. Bucharest transmitter
13,250*	R. Euzkadi	Same as R. Euzkadi above

^{*} Frequency varies.

Note: For EDT add one hour to times given under "Remarks."


tugas eventually established that, for security reasons, the ID's of those SWBC stations feeding it programs had been arranged to provide confusion

During the 1960's, Cuba's Radio Progreso network, including its 50-kW transmitter operated on 690 kHz, aired the English-language Radio Free Dixie with the then-fugitive Robert Williams as principal commentator. In recent years, however, most of the clandestine MW activity has been from international waters and apparently nothing but white operations. This includes a number of transmitters off the European coast and Carl McIntyre's Radio Free America, which operated briefly off Cape May, New Jersey, last fall.


Any of the white operations could be hiding a black operation like *Radio Swan*. Some of these white stations already have complex international

connections. The owners of Radio Northsea International, for example, originally financed the station (6205 kHz) by selling electronic equipment to Biafra. As RNI explained it in an exclusive statement to this author: "Our mission took place on the request of the Swiss Red Cross and the Caritas, both welfare institutions, as their major problem existed in the communications media. . . There was no direct telephone, telegraphic, telex, or any other communication link to Biafra, only over Nigeria. Therefore, Mr. Bollier and Mr. Meister installed a wireless communication link with a transmitting and receiving station in Biafra."

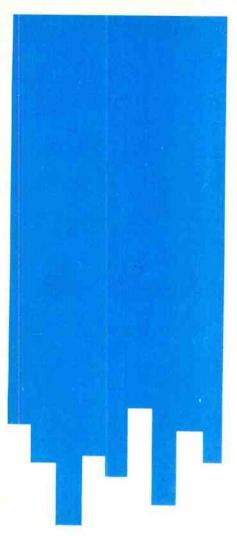With most of the stations like RNI operating in European international waters about to be forced off the air by Dutch anti-pirate legislation, one must wonder where some of these broadcasting ships are likely to wind up.



BASIC DIGITAL LOGIC COURSE

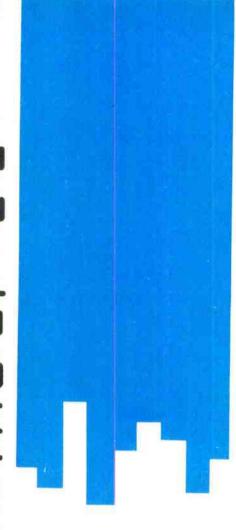

THE emergence of experimental digital IC projects has been so rapid that many people tend to get lost amid strange-sounding names like "quad 2-input positive NAND gate" and "BCD to 7-segment decoder/driver." Such terms describe the building blocks of digital electronics. To provide an introduction to logic for beginners and refresher information for more advanced experimenters, here is the beginning of a Digital Logic Course series.

This first instalment describes number systems and provides important background information for the next two instalments.

Number Systems. Early man was forced to count with small pebbles or knots on a string when he wanted to inventory his possessions. As time went on, and perhaps because he found it convenient to count with his fingers, man eventually devised a number system with ten digits. This provided a far more convenient and versatile counting system since, for

example, the number 16 could be represented with merely two digits rather than 16 pebbles or knots.

NUMBER SYSTEMS

The comparatively recent development of electronic digital computers has revived interest in number systems based on something besides the decimal. A system based on two digits is of particular importance in electronic digital computers. The reason for this is that an electronic circuit can be made to occupy only one of two states: on or off (saturated or cut off). Of equal significance is that any form of logic statement can be reduced to contain only true and false assertions.

Since electronic circuits required to implement true and false logic statements are very simple, a computer can be designed based on a two-digit number system, in which one digit corresponds to "true" and the other to "false". The two-digit, or base-two, number system is called the binary system and its digits, called bits (for binary digits), are 1 and 0.

BY FORREST M. MIMS

The Binary System. The easiest way to understand the binary system is to learn to count in binary fashion. One basic rule governs counting in any number system: record successive digits for each count until the count exceeds the total number of available digits; then start a second column to the left of the first and resume counting.

Since the binary system has only two digits, counting is very easy. You can prove this to yourself by counting to the equivalent of the decimal number 10 in binary. The binary of decimal 0 is 0. The binary of 1 is 1. Here the similarity ends. To express 2 in binary, you must start a new column since both binary, bits have been used in the first column. Hence, the binary of 2 is 10 (read one-zero-not ten). Three is expressed as 11 (one-one) in binary, which uses up both binary bits for the first two columns. So, a new column must be started for binary 4, which becomes 100, while 5, 6, and 7 become 101, 110, and 111. With 8, represented by the binary 1000, we must once again start a new column.

Binary Arithmetic. By learning how to count in binary, we have also derived three basic rules for addition: $(1) \ 0 + 0 = 0$; $(2) \ 0 + 1 = 1$; and $(3) \ 1 + 1 = 10 \ (1 + 1 = 0$, carry 1). These rules can be used to add any two binary numbers. For example, let us add 12 and 9 in binary:

Start with the right-hand column and add the *least* significant digit. Then continue adding each successive column, working from right to left, finishing up with the *most* significant bit:

Note in the above example that the addition of the two most significant bits yielded a 0 with a 1 carry. A carry can also occur within the addition as in: 1011 + 1101 = 11000.

Converting Binary to Decimal.

Binary numbers are fundamentally easy to work with. But how do you convert a string of 1's and 0's to easily recognized decimal numbers? The process is simple, using a technique known as "expansion." Each digit column of a decimal number corresponds to a power of the base-10 to which it must be raised. Let us use the number 846 as an example:

A binary number can be expanded in the same way and converted into a decimal number. For example, let us expand (10111)2. The subscript denotes the base of the number system—in this case, 2 or "binary"—and helps in preventing confusion. The expansion is as follows:

Since the position of each digit in a binary number determines the power of 2 invoked, it is easy to convert binary to decimal simply by assigning the decimal equivalent to each column. A 0 in a column means that the column's power-of-2 decimal equivalent is *not* invoked. Therefore, the decimal equivalents of all columns containing a 1 are added to find the total decimal equivalent. Let us convert 10011 to decimal:

Manual binary arithmetic involving numbers containing more than three or four bits is both tedious and cumbersome when you are accustomed to counting in a decimal system. But an electronic computer can perform thousands of lengthy binary additions in fractions of a second. This ability is vital to the success of digital computers and calculators, since all arithmetic operations can be performed by addition or its variations. Subtraction is the inverse of addition, while multiplication is simply repeated additions and division is the inverse of multiplication.

These facts about addition are important because they mean that even the most complicated arithmetic operations can be solved by addition. In practice, manual arithmetic rarely invokes this process. After all, you would find it inconvenient to multiply 641 by 197 if you had to write 197 times the number 641 and add the columns. But an electronic computer does the equivalent of this in only a few milliseconds.

The Octal System. Sometimes binary numbers are condensed into other number systems to further simplify computer processing. Since the binary system has only two digits, it does not take long to accumulate a string of seemingly endless 1's and 0's. A decimal number with only two digits, for example, requires five binary bits. A six-digit decimal number requires 19 bits.

Complicated binary numbers can be simplified by dividing them into groups of three or four bits and encoding the results in other number systems. Since the binary numbers for the decimal dig-

its 0 through 7 form groups of no more than three binary digits each, a long binary number can be reduced to a third of its length by converting it to a base-8, or octal, number system.

You can use a table of octal numbers and their binary equivalents to convert a long binary number such as 11101100001101 into octal. First, divide the number into groups of three bits each, beginning with the least significant bit:

11 101 100 001 101.

Then assign the octal equivalent to each three-bit group, using the octal-

Decimal	Binary	Octal
0	0	0
1	1	1
	10	1 2 3
2 3	11	3
4	100	4
5	101	5
6	110	6
7	111	7
8	1000	10
9	1001	11
10	1010	12
11	1011	13
12	1100	14
13	1101	15
14	1110	16
15	1111	17
16	10000	20
17	10001	21
18	10010	22
19	10011	23
20	10100	24

to-binary equivalents given in the table:

Hence, $(11101100001101)_2$ equals $(35,415)_8$. It is obvious that the latter number is easier to process than the former

Sometimes the base-16 (hexadecimal) number system is used to further simplify long binary numbers. The hexadecimal technique requires that the binary number be subdivided into groups of four bits each, again starting with the least significant digit. The result is a hexadecimal number that is only a fourth the length of the original binary number.

Next month, we will discuss logic concepts and circuits and demonstrate how logic circuits can be combined to make a binary adder.

SOLID-STATE PERSPECTIVE

How light-emitting diodes work and some tips on where to use them

BY WALTER G. JUNG Contributing Editor

N JUST a few short years, the lightemitting diode (LED) has found its way into innumerable circuits and devices as a "state" indicator. Not too long ago, there was only one type of LED (red); but today there is such a wide variety from which to choose that selection can become confusing.



Fig. 1. Schematic symbol for LED is standard diode with arrows for light output.

To correct this, let's take a look at what a LED is, how it works, what electrical and optical characteristics are available, and how to make the best use of them.

What Is a LED? A LED is a pnjunction semiconductor device specifically designed to emit light when forward biased. This light can be one of several colors—red, amber yellow, or green—or it may be infrared and thus invisible. The schematic symbol for a LED is shown in Fig. 1. It is similar to the symbol for a conventional diode except that the arrows are added to indicate light emission.

Electrically, a LED is similar to a conventional diode in that it has a relatively low forward voltage threshold. Once this threshold is exceeded, the junction has a low impedance and conducts current readily. This current must be limited by an external circuit, usually a resistor.

The amount of light emitted by the LED is proportional to the forward current over a broad range, thus it is easily controlled, either linearly or by pulsing. The LED is extremely fast in its light output response after the application of forward current. Typically, the rise and fall times are measured in

nanoseconds. Because of this fast response, LED's make excellent highspeed switched sources of light for

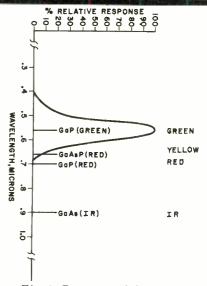


Fig. 2. Response of the human eye to various types of LED light emissions.

use in multiplexing, strobing, and optical communications systems.

LED's are small in size compared to conventional incandescent lamps; and, in fact, a LED actually consists of a tiny "chip" a few thousandths of an inch across mounted in a relatively large plastic package. As you might expect, a LED is also very light in weight.

Because of their low operating voltage and low current drive requirements, LED's consume very little power—about 30 mW (20 mA at 1.6 V being typical). Consequently, LED's generate little heat. A side benefit of the low power requirement permits interfacing LED's with most digital and linear IC's or low-power transistor stages.

A LED does not "use itself up," and has little wearout mechanism, so very long life can be expected. Some manufacturers predict 100,000 hours or more, which amounts to over 11 years of continuous use. On a practical basis, once wired in and operated within specified ratings, a LED should last forever.


Characteristics. It was once said that LED's came in three colors—red, redder, and reddest; but recent advances in semiconductor technology have changed the picture greatly. The early red LED's were made of gallium-arsenide phosphide (GaAsP) compounds. These are still the most inexpensive types available. Gallium phosphide (GaP) is now used to produce green, yellow, and red LED's.


The relative sensitivity of the human eye to the standard LED emission wavelengths is shown in Fig. 2. Note that the eye is most sensitive in the green area with the peak at 0.56 microns. The GaP red emission is at 0.69 microns, while GaAsP red is at 0.66 microns.


The light output of a LED tends to be monochromatic—of a single color (wavelength). The light output of LED's is usually specified in candelas, a measure of intensity; though sometimes it is specified in foot-lamberts, a measure of intensity per unit area.

Interpreting Data Sheets. To use a LED properly, you must have some understanding of the data sheets. A few illustrations from typical data sheets are shown in Fig. 3.

The simple curve in Fig. 3A shows that LED light output increases linearly with forward current up to 50

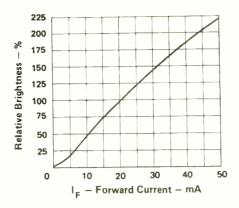

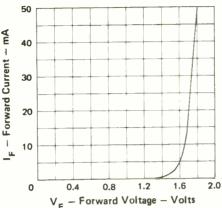

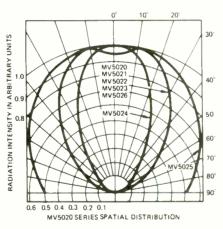

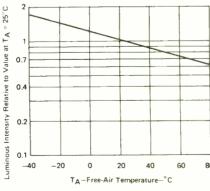


Fig. 3. Brightness (A) and voltage (B) vs current for Fairchild 100 units. (C) Intensity for various lenses (Monsanto MV5020). (D) Intensity vs temperature for TI type TIL209A.

mA, which, incidentally, is a typical continuous maximum current for plastic-packaged devices. Figure 3B is a current/voltage characteristic, showing the "knee" where conduction starts (in this case, at about 1.65 V, which is typical for a GaAsP diode). A GaP diode has a higher knee voltage (2 to 3V), but the curve's general shape is similar. Note that the diode current increases rapidly above the knee, which is why current limiting must be used to prevent damage to the diode.

The lensing arrangement of the diode package makes a big difference in how bright the LED appears off axis. As shown in Fig. 3C, the light can be formed into a narrow beam (as for the MV5024) or it can be wider (as for the MV5025). The beam-width used depends on the application. For example, a narrow-beam LED is correct for an optical communicator, but it is not good for a panel lamp since it will not catch the eye off to one side.

Even with a constant-current drive, temperature plays a role in the light output of a LED, as shown in Fig. 3D. However, for most hobby applications, this is not an important consideration unless a high-temperature environment is contemplated.

As a general rule, the LED should always be operated within recommended values. Maximum current can be exceeded on a peak basis as long as the average current is within specifications. The reverse voltage applied should be watched—3 volts is the usual maximum. A clamping diode can be used to prevent voltages that are too high.

Package Styles. Although LED's are manufactured in a wide variety of packages, only a few of the configurations have become favorites.

One of the most popular packages is the T-1 3/4, a 1/4"-diameter, high-dome, epoxy-encapsulated style. The Monsanto MV5020 series is typical of this type. It is intended for front panel or pc board mounting, and is available with a clear lens (MV5020), a diffused lens (MV5021), a plain red lens (MV5022). or a diffused red lens (MV5023). An uncolored, clear lens produces a point source of light, while a clear diffused lens softens the effect. A red lens aids contrast if the ambient light is high. A diffused red lens spreads the beam and widens the angle of visibility, often desirable features.

These LED's are shipped in a plastic clip for insertion in a panel. The leads

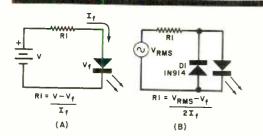


Fig. 4. Calculation of series current-limiting resistor for dc shown at (A); for ac, shown at (B).

are square and can either be soldered or wire-wrapped. The cathode lead is identified by the flat side on the plastic base, though in some cases the cathode is identified by a shorter lead. Green and yellow LED's that complement the MV5020 red series and have the same packaging are the MV5222 and MV5322, respectively.

The Fairchild FLV 100/101/102/108 series of "button" LED's are in small plastic packages similar to the TO-106 outline, but with only two leads. The respective part numbers correspond to a point source (FLV 100), diffused wide angle (FLV 101), red diffused area source (FLV 102), and an uncolored version (FLV 108) of the FLV 102. All of these packages benefit from the contrast enhancement provided by a black case. Although these units are best suited to pc board mounting, a plastic panel-mounting clip is available.

Another useful type of LED is the Texas Instruments TIL209/TIL209A, a red LED is a miniature 1/6"-diameter T-1 lamp size. It has a diffused red lens and is visible over a wide angle. The TIL209 has round leads, while the 209A has square leads. A companion green LED (TIL211) is also a diffused source. TI is currently working on yellow LED's, which should be available soon.

Hewlett-Packard has a series of red LED's which have a built-in current-limiting resistor. This eliminates the need for an external limiting circuit. Two models that operate from a 5-volt supply (can be driven by TTL) are the 5082-4860, a red diffused unit in T-1 ¾ size, and the 5982-4468, a clear diffused unit in T-1 size. The 5087-4860 can be panel-mounted and has wrap leads.

Litronix has also incorporated a current limiter in a LED package to operate over a wide variety of supply voltages. These devices come in T-1 3/4 and T-1 sizes. They have red diffused lenses. The RLC-200 is usable at voltages up to 12.5 V maximum, while the RLC-210 works up to 16 volts.

Driving LED's. A LED can be driven by either an ac or dc source, requiring a current-limiting resistor in either case. The two basic driving circuits are shown in Fig. 4 The equations show how to determine the value of the limiting resistor.

In Fig. 4A, the positive of the voltage source is connected to the LED's anode, so a forward current, I_r , flows. The current depends on V, the LED forward voltage drop (V_r), and the value of RI. The forward voltage drop varies between 1.6 and 3 volts. depending on the type of LED and can be determined from the published data sheets. As an example, assume that the LED requires 20 mA, has a V_r of 1.6, and the voltage source is 5 V. Then RI = (5-1.6)/0.02 = 170 ohms. (180 ohms would the nearest standard value.) Check the required wattage of

REFERENCES ON LED'S

Book:

Light Emitting Diodes. Farrest Mims, Howard W, Sams Co., Inc., 4300 W. 62 St., Indianapolis, IN 46268.

Manufacturers' Literature:

"Optoelectronics Handbook," Fairchild

"Application Notes," Monsanto

"Optoelectronics at Work," Motorpla-

"The Opticelectronics Data Book!" Texas Instruments

"Application Notes," Hewlett-Packard

Manufacturers' Addresses

Chicago Miniature Lamps, 4433 N. Ravenswood, Chicago, IL 60607

Dialight, 60 Stewart Ave., Brooklyr, NY 11201 Fairchild Microwave & Optoelectronic Div., 464 Ellis St., Mountain View, CA 94040

General Electric Co., E. Nela Park, Cleveland, OH 44101

Hewlett-Packard Co., 620 Page Mill Rd., Palo A to, CA 94304

Litronix, 19000 Homestead Rd., Cupertino, CA 95014

Monsanto, 10131 Bubb Rd., Cupertino, CA 95014 Motorola Semiconductor Products, 5005 E. McDawell Rd., Phoenix, AZ 85036

National Semiconductor, 2900 Semiconductor Dr., Santa Clara, CA 95051

Opcoa, 330 Talmadge Rd., Edison, NJ 08817 Texas Instruments, Dalias, TX 75222 Xciton Corp., 5 Hemiock St., Latham, NY 12110

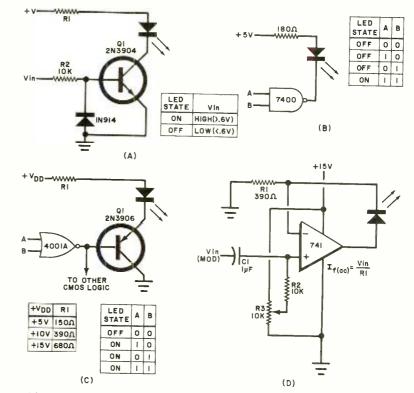


Fig. 5. (A) Saturated transistor drive and truth table.
(B) and (C) are TTL and CMOS drives. (D) uses linear modulator.

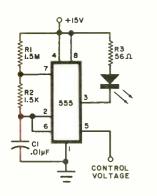


Fig. 6. Using a 555 IC to pulse-modulate LED.

the resistor since it will dissipate most of the source voltage.

In the ac circuit in Fig. 4B, the voltage source is $V_{\rm rms}$, a sine wave. If the peak reverse voltage applied to the LED is over 3 V, the protective clamping diode, D1, is used. Any small-signal or rectifier diode can be used for D1. Since the LED rectifies the ac,

Low-power logic such as CMOS cannot drive LED's directly so a buffer such as a CD4049 or CD4050 must be used, but current is limited. A solution is to use an emitter-follower buffer as shown in Fig. 5C. A beta of 100 for Q1 will reduce the drive current required to 200 µA, which is compatible with the 4000A series of CMOS. The circuit in Fig. 5C is an example of OR logic since the LED is lit for a logic one on either A or B. Limiting resistor R1 should be selected to match the supply voltage. An npn transistor could also be used for Q1 by connecting the collector to the supply with the LED and R1 in the emitter circuit. A basic asset of CMOS is its very high noise immunity, so a slightly reduced output swing from the gate in Fig. 5C is not a real detriment as far as driving other CMOS inputs is concerned. There are no fanout restrictions.

So far, we have discussed only onoff types of LED drives. A linear driver is shown in Fig. 5D. An op amp is used to make the LED current precisely

Fig. 7. Sensitive polarity indicator using op amp and two LED's of different colors.

only half of the total current contributes to useful light output. To maintain a brightness equal to that obtainable with dc, the value of the limiting resistor is cut in half—thus the 2 in the denominator of the equation.

Some practical drive circuits are shown in Fig. 5. An npn switching transistor is used in Fig. 5A. A high level on the input line switches Q1 into saturation, supplying current to the LED. Current-limiting resistor R1 is chosen as shown in Fig. 4A. The value of the supply voltage (+V) can be anything up to the $V_{\rm ceo}$ rating of Q1.

One of the most important uses for the LED is as a logic status indicator in digital circuits. Since TTL logic can sink up to at least 16 mA, it mates easily with a LED as shown the example in Fig. 5B. This is an AND gate so that the LED is on only when both A and B are high. Keep in mind that the current flows through the LED when the gate output is low. This, in effect, subtracts from the fanout of the stage if it is coupled to another logic stage. If the fanout is required, use a TTL buffer to drive the LED alone.

proportional to the input modulation signal. Potentiometer *R3* determines the dc bias current in the LED since the voltage at the rotor of *R3* also appears across *R1*. If *R3* is centered, *R1* "sees" 7.5 volts and the current through the LED is 20 mA. The audio signal, through *C1*, modulates the dc bias signal to control the LED current proportionally. This circuit could be used as the transmitter end of light-beam communicator. It is simple, inexpensive and easy to set up; and none of the components is critical.

Some Applications. A pulser that is useful for on-off modulation of visible or IR LED's is shown in Fig. 6. A 555 timer IC is used as an astable oscillator which provides a 10-µs pulsed output every 10 ms (a 100-Hz rate). The circuit can be frequency modulated by applying an audio signal to pin 5. Resistor R3 sets the peak LED current to about 200 mA; and, since the duty cycle is only 0.001, the LED is not overloaded.

Using a narrow-beam IR LED (such as the Motorola MLE60) in this circuit and a silicon detector at the receiver,

an invisible light-beam communication link can be constructed.

A sensitive polarity (or null) indicator is shown in Fig. 7. The circuit uses an op amp to achieve a very low input-voltage threshold. Since the input signal is applied to the op amp noninverting input (+), the op amp output is positive when the input is positive and negative when the input is negative. A positive input lights the green LED, and a negative signal lights the red LED. The LED's can be separate devices, or a dual unit such as the Monsanto MV5491 (red/green) LED can be used.

The input threshold is the offset of the op amp used. For a 741, it is ± 6 mV or less. There are no loading effects since the input draws very little current. If the added sensitivity is not needed, the op amp can be omitted and the LED's driven directly through R2. This is a useful option if the source impedance is low.

The circuit shown in Fig. 8 uses two high-gain comparators to determine whether a critical voltage is between two limits. In the circuit shown, the limits are +4 and +6 volts. The two comparators are wired as OR gates, so that the LED is energized if either comparator output is low. This would occur if $V_{\rm in}$ were less than +4 V or more than +6 V. Using this general idea, different reference voltages can be used to monitor almost any voltage level.

Conclusion. Of course, we have not covered all of the possible uses for the various types of LED's. Hopefully, some ideas have been generated. Others can be obtained from the references given in the accompanying box.

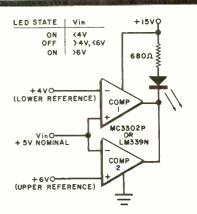


Fig. 8. Window comparator turns LED on when input exceeds predetermined limits.

The TV of the future is here... in the Heathkit Digital-Design GR-2000 TV





At ELEMENTARY ELECTRONICS. they said: "The fact is, today's Heathkit GR-2000 is the color TV the rest of the industry will be making tomorrow...

there is no other TV available at any price which incorporates what Heath has built into their latest color TV."

The **FAMILY HANDYMAN** reviewer put it this way: "The picture quality of the GR-2000 is flawless, natural tints, excellent definition, and pictures are steady as a rock. It's better than any this writer has ever seen."

POPULAR SCIENCE pointed out "more linear IC's, improved vertical sweep, regulators that prevent power supply shorts, and an industry first: the permanently tuned I.F. filter."

The **RADIO-ELECTRONICS** editors said the Heathkit Digital TV has "features that are not to be found in any other production color TV being sold in the U.S.:

"On-screen electronic digital channel readout...numbers appear each time you switch channels or touch the RE-CALL button...On-screen electronic digital clock...an optional low cost feature...will display in 12- or 24-hour format...Silent all-electronic tuning. It's done with uhf and vhf varactor diode tuners...Touch-to-tune, reprogrammable, digital channel selection...up to 16 channels, uhf or vhf...in whatever order you wish...there's no need to ever tune to an unused channel. LC IF amplifier with fixed ten-section LC IF bandpass filter in the IF strip...eliminates the need for critically adjusted traps for eliminating adjacent-channel and in-channel

carrier beats. No IF alignment is needed ever. *Touch volume controls...* when the remote control is used... touch switches raise or lower the volume in small steps,"

POPULAR ELECTRONICS took a look at the 25-in. (diagonal) picture and said it "can only be described as superb. The Black (Negative) Matrix CRT, the tuner and IF strip, and the video amplifier provide a picture equal to that of many studio monitors..."

Furthermore, the Heathkit GR-2000 is an easier kit-form TV to build. **POPULAR ELECTRONICS** pointed out that "Each semiconductor has its own socket and there are 12 factory-fabricated interconnecting cables...The complete color adjustments can be performed in less than an hour."

To sum up, **POPULAR ELECTRONICS** concluded its study by stating, "In our view, the color TV of the future is here—and Heath's GR-2000 is it!"

Why not see what the experts have seen? The Heathkit Digital Design Color TV—without question the most remarkable TV available today.

Mail order price for chassis and tube, \$669.95. Remote Control, \$89.95 mail

order. Clock, \$29.95 mail order. Cabinets start at \$154.95 (Retail prices slightly higher.)





TOMORROW'S PRODUCTS are in kit-form todaywith Heathkit electronics



(A) New Heathkit Digital Electronic Alarm Clock. Like no other clock you've ever owned...with features as new as tomorrow! Wakes you with an electronic "beep" and shuts off at a touch—no fumbing for knobs or switches. And if the power goes off, you still get to work on time—the clock has its own emergency battery supply. Other features are a 24-hour alarm cycle with AM indicator light to aid in setting; 7-minute repeatable snooze cycle; 12 or 24-hour time format; automatic brightness control. Kit GC-1092A, 82.95*. Shipping weight, 5 lbs.

(B) New Heathkit Digital Electronic Calendar/Clock. In this unique timepiece, we swapped the alarm feature for the date-and held the same low kit price featured in its alarm clock twin. Reads out the time in hours, minutes & seconds, with big orange digits. Plus, it gives you the month and day, either automatically for 2 seconds out of every 10, or anytime at the touch of an electronically activated control. It also features 12 or 24-hour time format, automatic brightness control, and built-in fail-safe reserve battery supply. Kit GC-1092D, 82.95*. Shipping weight, 5 lbs.

(C) New Heathkit Exhaust Gas Analyzer. A timely kit for the week-end mechanic and the professional alike. Checks exhaust gas of cars for pollution level and measures air/fuel mixture to help you tune for top economy.

Also a great training aid in automotive mechanics classes for demonstrating results of proper anti-pollution system adjustments. Easy to assemble, simple to use. Kit Cl-1080, 59.95*. Shipping weight 6 lbs.


(D) New Heathkit Tune-up Meter. Successor to the popular Heathkit ID-29—now with new, extended 0-20 VDC range. Checks dwell on 4-cycle, 3, 4, 6 & 8 cylinder engines with conventional ignition. Two rpm ranges. Reads voltage from 0-20 VDC. Use on 6 or 12V systems, either ground. No batteries required. Kit CM-1073, 29.95*. Shipping weight, 5 lbs.

HEATHKIT ELECTRONIC CENTERS — Units of Schlumberger Products Corporation. Retail prices slightly higher.

Retail prices slightly higher.


ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA:: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY:: Louisville; LA:: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS:: Boston (Wellesley); MICH:: Detroit; MINN.: Minneapolis (Hopkins); MO:: St. Louis; NEB:: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho, L.I., Rochester, White Plains; OHID: Cincinnati (Woodlawn), Cleveland, Columbus; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; WASH:: Seattle; WIS.: Milwaukee.

	HEATHKIT	FREE 1975	HEAT	TH
		HEATHKIT CATALOG 350 easy-to-build kits in all	Schlum	berger
1	一个 一	price ranges. Send for your free	copy today!	
	न	Heath Company Dept. 10-10 Benton Harbor, Michigan 49022		
	☐ Please se	nd my free 1975 Heathkit Catalog. is \$, plus shipping.		
	_	nd model(s)		
	Name			
	Address			
ŀ	City	State	Zip	
		cifications subject to change without rices; F.O.B. factory	notice.	CL-534

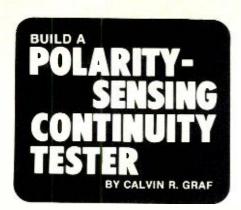

COMPACT polarity-sensing continuity tester can prove a very useful tool on any workbench. With it, you can check for short circuits, open circuits, continuity, and the polarity and condition of rectifier and light-emitting diode and transistor junctions. It can even be used to check most capacitors and any purely resistive component rated at up to 20,000 ohms.

The tester's circuit (see schematic) is very simple, consisting of a 6.3-volt transformer, two LED's, and a And if neither LED comes on, the decurrent-limiting resistor that is common to both LED's. Owing to the fact that test current comes from the stepped-down 60-Hz ac line, only one LED will come on for each alternation. The forward conduction of one LED protects the other LED from reversecurrent conduction during alternating cycles of the ac voltage.

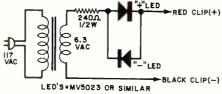


When a unidirectional device (diode or transistor) is tested, current flows in only one direction. Hence, only one LED lights. (Note: If one LED comes on at full brilliance and the other glows very faintly, the device under test can be considered good.) If both LED's come on, the device is shorted.

vice under test is open.

Transistors can be safely tested with this device because of the low current drawn. Less than 5 mA of current produces a bright LED glow, while as little as 200 µA of current can be observed as a faint glow.

The circuit is designed so that, when the red alligator clip is connected to the anode of a diode (or p side of a transistor junction) and the black clip is connected to the cathode of the diode (or n side of the junction), the "+" LED will light. Reversed connections do not require that the leads be transposed; simply observe which of the LED's lights and check the alligator clip hookup.

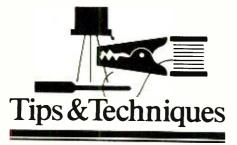Continuity for resistance can be observed by the brilliance at which the LED's glow. The brighter the glow, the lower the resistance, and vice versa. Also, capacitances greater than about $0.05~\mu\text{F}$ will cause a faint glow of both LED's (demonstrating that the capacitor is good at 60 Hz).



SWITCH OFF SOLDERING IRON TO PREVENT INDUCED-VOLTAGE DAMAGE TO MOSFET'S

Damage resulting from induced voltages during soldering is the biggest problem the experimenter and technician must face when dealing with MOS devices. One way to contend with the problem is to install in the line cord of your soldering iron a switch that will break the ac power circuit on demand. Now, just before you solder a MOS connection, switch off the iron's power and solder away. The tip will remain hot long enough to complete quite a number of solder connections. As the tip cools off, power will have to be restored to the heating element. But do not switch on the power until the iron is a couple of feet away from the MOS device.

-Michael W. Zachary

STRANDED WIRE AND BRAIDED SHIELD FACILITATE EASY SOLDER REMOVAL

The next time you prepare a length of coaxial cable and have some braided shield left over (or if you have a short length of cable that does not seem worth saving), do not throw it away. The porous braided shield makes an excellent solder removal aid during desoldering operations. Just place the braid over the soldered connection and press the tip of your soldering iron or gun against the braid over the connection. As the braid heats up, it will draw off most of the solder. In a pinch, when you have no braid handy, you can also use stranded wire. Simply strip away about 2 in. of insulation and lay the exposed conductors over the connection and heat. Capillary action will again draw off most of the solder.

-Ron Samchuk, VE4SR

MOLEX SOCKET TERMINALS MAKE MINIATURE JUMPER CABLES

It is often desirable to make fast connections to single terminals of IC's or closely-spaced wire-wrap posts. Jumper cables made from conventional alligator clips are too bulky for such applications. But you can assemble miniature cables that will fill the bill from lengths of stranded wire and Molex Soldercon® socket terminals (available from a number of surplus parts outlets). Simply solder the wires to the terminals and tightly shrink a short length of heat-shrinkable tubing over the connector. Care must be exercised to prevent solder from flowing into the connector proper. This can be obviated by pushing a flat toothpick into the clip end of the connector before soldering.

-B.F. Rordorf

DOWEL AND LONG NOSE PLIERS MAKE QUICK SUBSTITUTE FOR SPANNER WRENCH

On occasion, you might have to install or remove a spanner nut. Lacking the proper

wrench, you first instinct is to grab your long-nose pliers and set to work. While using the wrong tool for the job is not recommended, on rare occasions you can make do with a substitute if you are careful. If you must work on a spanner nut with long nose pliers, clamp between their jaws a hardwood dowel and grip tightly. Set the jaws into the spanner nut's slots and carefully apply tightening or loosening torque. If you are careful, no damage should result. Forgetting to use the dowel will likely produce marred and gouged results as the jaws slip out of the slots while you are attempting to apply grip and torque pressure.

-John T. Bailey

MASKING TAPE SIMPLIFIES KIT AND PROJECT BUILDING

When assembling an electronic kit or project, keeping track of the components that go into assembly can be difficult even if you use muffin tins and other such devices for holding the components after separation. Double-sided masking tape can be an enormous help in alleviating the situation. Just run parallel strips of the tape on a sheet of cardboard, spacing the strips so that components can be easily accommodated without interfering with each other, and press the components into the tape. You can arrange the components by category: resistors, disc and other small capacitors, diodes, transistors, etc. Now, as you need the component, you can locate it at a glance. When you are all through, if the tape's mastic is still usable, cover the cardboard with waxed paper and it can be used again.

-Mark Austin

C-M	OS
4000AE	\$.60
4001AE	.60
4002AE	.65
4004AE	5.90
4006AE	3.90
4007AE	.70
4008AE	3.60
4009AE	1.00
4010AE	1.30
4011AE	.65
4012AE	.65
4013AE	1.50
4014AE	4.10
4015AE	4.10
4016AE	1.25
4017AE	3.90
4018AE	3.20
4019AE	1.35
4020AE	4.20
4021AE	3.80
4022AE	3.20
4023AE	.65
4024AE	2.30
4025AE	.65
4026AE	9.90
4027AE	1.95
4028AE	3.20
4029AE	5.80
4030AE	1.30
4035AE	3.80
4037AE	4.00
4040AE 4041AE	3.35
4041AE	3.30
4042AE	3.35
4043AE	3.35
4048AE	1.50
4049AE	1.40
4050AE	1.40
4051AE	3.60
4056AE	3.50
4060AE	5.17
4069AE	.90
4076AE	4.30
TOTOME	4.00



Here's a highly versatile lab instrument at a fraction of the cost of conventional unit. Kit includes two XR205 IC's, data & applications, PC board (etched & drilled, ready for assembly) and detailed instructions.

Waveform Generator Kit XR205K Only \$28.00

DM8820N	4.00	9602	2.00
DM8820AN	6.50	9614	3.00
DM8830N	4.50	9615	3.00
DM8831N	5.00	9616	4.50
DM8832N	5.00	9617	3.00
9600	1.30	9620	3.50
9601	1.30	9621	3.00

HYBRID POWERAMPLIFIERS

Power SI-1010Y SI-1025E	10W 25W	1HF 25W 65W	Price \$ 6.40 18.00
SI-1050E	50W	120W	25.40

7475N 7476N

Voltage Regulators

1 4 4 4 0 0 1 1	CEEO
LM100H	\$5.50
LM104H	6.50
LM105H	5.10
LM105F	8.50
LM109H	9.50
LM109K	6.30
LM200H	3.80
LM204H	4.70
LM205H	3.00
LM209H	3.50
LM209K	3.70
LM300H	.90
LM300N	1.40
LM304H	1.40
LM305H	1.10
LM305AH	1.40
LM305N	1.20
LM309H	1.75
LM309K	1.95
LM335	2.30
LM336	2.40
LM 337	2.40

LIVIZUSTI	3.30
LM209K	3.70
LM300H	.90
LM300N	1.40
LM304H	1.40
LM305H	1.10
LM305AH	1.40
LM305N	1.20
LM309H	1.75
LM309K	1.95
LM335	2.30
LM336	2.40
LM337	2.40
LM340-05K	2.60
LM340-06K	2.60
LM340-08K	2.60
LM340-12K	2.60
LM340-15K	2.60
LM340-18K	2.60
LM340-24K	2.60
LM723H	1.30
LM723D	3.90
LM723CH	.80
LM723CN	.75
L129	1.50
L130	1.50
L131	1.50



with liquid crystal display with liquid crystal display. Beautiful, reliable & accurate. \$149.00 plus \$2.50 for shipping & handling. (California residents add 6% sales tax.)

Memories

	71163
P1101A	\$7.00
P1101A1	8.50
P1402A	8.50
P2102	16.00
P3101	5.50
P3101A	5.50
MM6560N	5.00
MM6561N	5.00
DM8599N	5.00
93403	5.00

LED's 125"dia.

.120			
209	Red	\$.25	
209	Yellow	.35	
209	Green	.35	

.160 dia.

		-
216 216 216	Red Yellow Green	.25 .30 .30

.200 dia.

220	Red	.25
220	Yellow	.30
220	Green	.30

Displays

SLA1	Red	2.25
SLA11	Green	4.25
SLA21		4.25
SLA2	±1 Red	2.25
SLA12	±1 Green	2.25
SLA22		2.25
SLA3	Red	7.50
SLA4	Red	7.50

Optoisolator

_	#-	 	~.	 	-
мст	2			1	.4

Linear ICs

LM301A LM301AM LM301AN LM302H LM302N LM306H LM307H LM308H LM308AH LM311H LM311H LM318H LM318H LM555CM LM709CN	TO-5 Mini-dip Dip TO-5 Dip TO-5 TO-5 Mini-dip TO-5 TO-5 TO-5 TO-5 TO-5 Mini-dip TO-5	\$.90 .75 1.10 .95 1.40 2.80 .90 1.20 5.00 1.40 1.70 2.50 .95 45
LM710CH LM710CN LM725CH LM733CH LM733CN LM741CH LM741CM LM747CH LM747CN LM748CN LM3046CN LM3054CN	TO-5 Dip TO-5 TO-5 Dip TO-5 Mini-dip TO-5 Dip Dip Dip Dip	.60 .75 5.00 1.50 1.50 .45 .44 1.90 .90 .40 .95

Phase Locked Loops

LM567CM Mini-dip 2.00

IC sockets

8 pin	DIL	.22
14 pin	DIL	.26
16 pin	DIL	.29
24 pin	DIL	.75
28 pin	DIL	1.10
36 pin	DIL	1.70
40 pin	DIL	1.90

Teflon

3 pin	TQ-5	.55		
4 pin	TQ-5	.65		
6 pin	TO-5	.90		
8 pin	TO-5	1.10		
40	TOE	1 40		

Shift Registers

1402A	\$ 8.50
1403A	6.00
1404A	6.00
1405A	4.50
1406	6.00
1407	6.00
1506	3.00
1507	3.00
2505K	4.00
2512K	5.50
2524V	4.00
2525V	5.50
2807	4.00
2808	5.50
TMS3114	8.20
MM 5055N	
MM5056F	
MM5057N	5.00

Schottky TTL

	\$.80
SN74S02N	.80
SN74S03N	.80
SN74S04N	.80
SN74S08N	.80
SN74S10N	.80
SN74S11N	.80
SN74S20N	.80
SN74S30N	.80
SN74S32N	.80
SN74S40N	.80
SN74S41N	.80
SN74S64N	.80
SN74S74N	1.30
SN74S85N	6.10
SN74S86N	2.90
SN74S112N	2.50
SN74S113N SN74S133N	1.50
SN74S133N SN74S138N	4.50
SN74S139N	4.20
SN74S140N	1.00
SN74S151N	3.30
SN74S153N	3.30
SN74S154N	3.40
SN74S157N	3.00
SN74S158N	3.00
SN74S160N	6.60
SN74S161N	6.60
SN74S174N	4.75
SN74S175N	5.00
SN74S181N	12.50 5.10
SN74S189N SN74S194N	4.40
SN74S195N	4.40
SN74S251N	4.20
SN74S253N	4.20
SN74S275N	3.20
SN74S258N	3.70
SN74S260N	.90 5.70
SN74S280N	
SN74S289N	5.00
93510	6.80
93S16	6.80
93S21	3.50
93522	3.20
93548	3.70

HIGH SPEED TTL

SN74H00N	\$.35
SN74H01N	.50
SN74H04N	.37
SN74H05N	.37
SN74H08N	.45
SN74H10N	.45
SN74H11N	.45
SN74H15N	.37
SN74H20N	.40
SN74H40N	.37
SN74H74N	.70

You deserve PREMIUM QUALITY COMPONENTS

When you order from us, that is what you receive! We've been buying and selling top quality components for nearly ten years. Our annual volume exceeds \$3 million. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies.

Now you can take advantage of our component buying skills and power. Select from a broad range of advanced devices. Enjoy competitive and often amazingly low prices. Depend on shipment in 48 hours or less and rely on our guarantee of complete satisfaction — ANCRONA CORPORATION.

74150N 1.15 74151N .90 74152N 2.20

74153N

7400N	\$.20	1
7401N	.28	4
7402N	.24	
7403N	.24	
7404N	.26	
7405N	.30	
7406N	.43	
7407N 7408N	.50	
7409N	.25	
7410N	.25	
7411N	.30	
7412N	.50	
7413N	.80	
7414N	2.80	
7416N	.48	
7417N	.65	
7420N	.26	
7421N	.50	
7423N	.50	
7425N	.50	
7426N 7427N	.50	
7427N	.50	
7430N	.24	
7432N	.30	
7433N	.60	
7437N	.50	
7438N	.50	
7439N	1.00	
7440N	.24	
7441AN	1.15	
7442N	1.00	
7445N	1.15	
7447N 7448N	1.30	
7450N	.24	
7451N	.30	
7453N	.25	
7454N	.25	
7460N	.25	
7470N	.30	
7472N	40	

7480N	.65	74154N	1.65
7481N	1.20	74155N	1.50
7482N	1.00	74156N	1.50
7483N	1.00	74157N	1.25
7484N	3.00	74158N	1.55
7485N	2.50	74160N	1.90
7486N	.50	74161N	1.60
7489N	3.00	74162N	2.00
7490N	.80	74163N	1.60
7491N	1.30	74164N	1.90
7492N	.85	74165N	1.90
7493N	.85	74166N	2.00
7493AN	.85	74170N	2.50
7494N	1.30	74173N	1.80
7495N	1.00	74174N	1.50
7495AN	1.50	74175N	1.90
7496N	1.10	74176N	1.70
7497N	1.50	74177N	1.70
74100N	1.60	74180N	2.50
74105N	.55	74181N	3.90
74107N	.50	74182N	1.20
74108N	.90	74184N	2.90
74109N	.90	74185N	2.30
74110N	.70	74190N	2.90
74111N	.90	74191N	2.90
74114N	.90	74192N	1.50
74115N	.90	74193N	1.40
74118N	.90	74194N	1.90
74119N	.80	74195N	1.00
74121N	.60	74196N	2.40
74122N	.90	74197N	2.40
74123N	.95	74198N	2.60
74125N 74126N	1.40	74199N	4.50
74128N	1.20	74200N	5.00
74128N	2.00	74221N	1.70
74132N	.90	74251N	
74136N	1.90	74278N	2.90
74141N	1.80	74279N	.90
74147N	2.90	74293N 74298N	2.50
7/11/19/1	3.50	/4298IN	2.50

SN74L02N SN74L03N SN74L04N SN74L10N SN74L20N SN74L42N SN74L47N SN74L47N	.35 .40 .40 .35 .40 1.60 1.60
SN74L73N	.75
SN74L74N	.90
SN74L90N	1.60
SN74L93N	1.75
SN74L95N	1.60
93L00 93L01 93L08 93L08 93L10 93L11 93L12 93L14 93L16 93L18 93L21 93L22 93L24 93L24 93L38 93L34 93L34 93L36 93L40 93L41 93L60	1.50 1.60 1.80 2.80 4.20 1.70 3.50 1.50 1.80 2.80 3.70 4.00 4.20 6.50 6.50 3.00 2.70


LOW POWER TTL

MIN. ORDER \$10.00



SEND CHECK OR MONEY ORDER (NO. C.O.D.) TO

P. O. Box 2208P, Culver City, CA. 90230

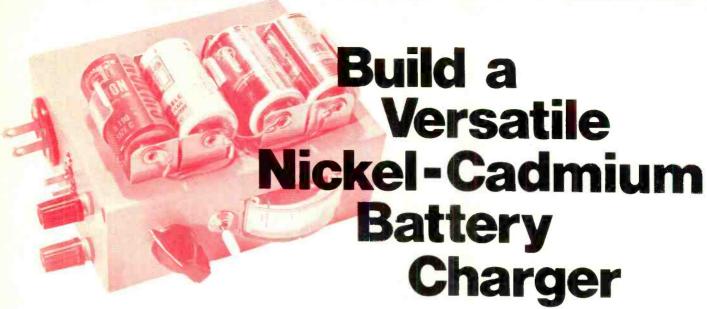

Provides variety of charging rates and operates from ac line or 12-V dc source

N THESE DAYS of portable devices powered by nickel-cadmium batteries, recharging devices are becoming increasingly important. Unfortunately, most chargers are designed for a specific application. For example, a charger for a calculator may not satisfactorily charge the batteries in a portable tape recor-

der. Similarly, you can't expect to charge the batteries in a walkie-talkie with a charger designed for a photographic speedlight. Here's a general-purpose battery charger you can build for under \$15 that will accommodate popular AA-, C-, and D-size nickel-cadmium cells. With this unit, you won't need a separate charger for

each piece of equipment containing batteries.

The battery charger, shown schematically in Fig. 1, overcomes the single-application design by providing a variety of charging rates. To make it as versatile as possible, the power source for the charger can be the ac line through *PL1* or any 12-volt dc source (including a car battery) through *PL2*. It can charge from 1 to 4 C cells at once with the cells either installed in battery clips on the charger or connected to the charger through an external cord.

Values of current-limiting resistors *R1* through *R4* were selected to keep the charging current through the cells low enough so that damaging overcharging would not occur. Switch selection, via *S2*, automatically switches in the proper series resistance to match the number of cells connected to the charger circuit. Meter *M1* provides a means of monitoring the charging current so that you always know the charge current is within cell ratings.

A 12-volt filament transformer, *T1*, and diode, *D1*, permit the charger to operate from a 117-volt ac line source. To operate the charger from a 12-volt dc source, *S1* must be in its alternate position, placing the *R6/PL2* circuit in the system and removing the *PL1/T1/D1* circuit. Resistor *R6* is in the circuit to insure that the same charging current is delivered in the dc mode as in the ac mode.

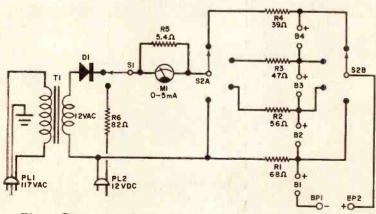


Fig. 1. Charger can be used for one to four C cells with cells in clips or connected to binding posts.

PARTS LIST

B1-B4—D-cell battery holders
BP1, BP2—Five-way binding post (one black, one red)
D1—200-PIV, 200 mA silicon diode
M1—0-5-mA meter movement
PL1—Ac plug with line cord, or use chassis-mounting plug
PL2—Polarized dc plug (automotive or other), or use chassis-mounting plug
R1—68-ohm, 1-watt resistor

R2-56-ohm, 1-watt resistor

R5—5.4-ohm, ½-watt resistor
R6—82-ohm, 1-watt resistor
S1—Dpst switch
S2—2-pole, 4-position rotary switch
T1—12-volt, ½-ampere filament transformer
Misc.—Chassis box; hookup wire; hardware;
rubber grommet or plastic strain reliefs (2)
for line and dc power cords; solder; etc.

R3-47-ohm, 1/2-watt resistor

R4-39-ohm, 1/2-watt resistor

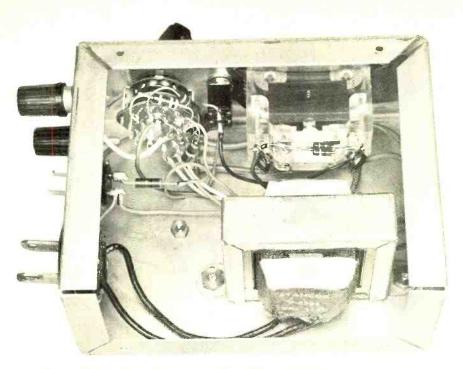


Fig. 2. Photo shows inner assembly of the prototype. All parts are installed by point-to-point wiring so it is not necessary to use circuit board.

The values of *R1* through *R4* were selected to yield slightly less than 100 mA of charging current. When *S2* puts *R1* in the circuit, charging current is delivered to only the *B1* battery con-

tacts. Switching through R2, R3, and R4 successively adds the remaining battery contacts so that up to four batteries can be recharged simultaneously. Note, however, that the circuit is

"live" only if the proper number of batteries are installed for any given switch position. For example, if S2 were in the R4 position, four batteries must be in the charger; any lesser number would leave an open circuit.

If you examine the schematic, you will note binding posts *BP1* and *BP2*. These connectors are a convenience feature that allows batteries of different physical configurations to be recharged with the aid of test leads. Select black and red binding posts for *BP1* and *BP2*, respectively.

The only other component in the circuit is *R5*. This resistor serves as a current shunt for *M1*. It permits the meter, a 0-5-mA movement, to accommodate a 0-120-mA current range.

Building the battery charger is a simple and straightforward project. As shown in Fig. 2 and the lead photo, no printed circuit or perforated phenolic board is required during assembly. All parts are installed by point-to-point wiring.

In use, the battery charger, operating at a 1/10 C charging rate, will fully charge a depleted nickel-cadmium battery in about 14 to 16 hours. For only partially discharged cells, the recharging time will be shorter.

We're too British to boast.

So here's what the experts say about us.



Rather than appear immodest, we'll let the experts who write for the audio publications tell you about an automatic turntable we're quite proud of—our 8100X Transcription Series model.

High Fidelity magazine says:

"The new cam system in the 810QX is credited with providing smoother and quieter operation than in past models. Average flutter was very low at 0.05%; total audible rumble by the CBS-ARLL method was —52db. The arm has negligible friction laterally and vertically, and requires a 0.3 gram stylus force for automatic trip. Taking it all together-performance, features, styling—the BSR 810QX moves into ranking place among the best automatics we know of."

Stereo Review magazine says:

"The BSR 810QX has an unusually complete array of operating controls and adjustments, yet is simple to use. The wow and flutter were very low—respectively 0.03 and 0.045% at 33½ rpm and 0.05 and 0.04% at 45 rpm. The BSR 810QX, undeniably a well-constructed and attractively styled record player, was also a very easy one to operate. The controls had a smooth, positive feel and action."

This is a modest way to tell you how good our 810QX Transcription Series turntable really is. We would be pleased to send you detailed specifications. Just drop us a note.

McDONALD

BSR (USA)Ltd.,Blauvelt,N.Y.10913

CIRCLE NO. 7 ON READERS SERVICE CARD



HEATHKIT MODEL AR-2020 4-CHANNEL RECEIVER (A Hirsch-Houck Labs Report)

Low-cost quadraphonic kit



THE Model AR-2020 is the Heath Company's new low-priced 4-channel hi-fi receiver. It contains AM and stereo FM tuners, an SQ matrix decoder, and four amplifier channels rated at 15 watts each continuous output power into 8-ohm loads. The receiver is designed to accept external 4-channel programs from up to three different discrete high-level sources and has inputs for 2-channel stereo AUX and magnetic PHONO cartridge. Tape recording outputs are provided for use with a 2- or a 4-channel tape deck.

The receiver measures 20 in. (50.8 cm) wide by 14 in. (35.7 cm) deep by 5 in. (12.7 cm) high. Its weight is 24 pounds (10.9 kg). The retail price of the Model AR-2020 receiver kit is \$249.95, which includes decorative wood end panels.

General Description. The front panel of the receiver features a "blackout" dial window, behind which the logging scales illuminate in soft green when power is turned on. The legend STEREO appears in red when a stereo FM broadcast is received. (There is no tuning meter.)

Pushbutton switches are provided for selecting the input source (AUX 4, AUX 2, TAPE 4, PHONO, FM, or AM) and selecting the operating mode (4 CH

discrete, STEREO, MATRIX, or MONO) and for turning on and off the power and energizing the speaker outputs. In the STEREO mode, the same program appears at the front and rear outputs on each side of the 4-channel listening setup, while in MONO, an input to any of the channels appears in all four channels simultaneously. Front- and rearchannel stereo headphone jacks are provided for private listening.

Four controls permit individual channel level adjustments to be made, while a single master volume control operates on all channels simultaneously. Separate bass and treble controls are provided for the front and rear channels, each operating simul-


taneously on the left and right channels over which it exercises control.


The receiver has facilities for 300-ohm and 75-ohm external FM antennas. A pivoted AM ferrite-rod antenna is featured, but no connectors are provided for using an external AM antenna.


Laboratory Measurements. As with most Heathkit receivers, the Model AR-2020 is meant to be aligned and adjusted without the need for external test instruments, using the STEREO indicator lamp in lieu of a multimeter. Our test unit appeared to perform satisfactorily after following the alignment procedure without instruments detailed in the kit's assembly manual. We then followed the instrument alignment procedure on the tuner before proceeding to perform our laboratory measurements.

In our tests, the FM tuner had an IHF usable sensitivity of 2.5 μ V in mono, with an excellent limiting curve that yielded a 50-dB S/N ratio with only a 2.9- μ V signal input. In stereo, the usable sensitivity was 5.0 μ V, and a 55- μ V signal was needed for a 50-dB S/N ratio. The receiver does not employ interstation noise muting or automatic stereo/mono switching on FM. The STEREO light and multiplex decoder are functional for all inputs exceeding about 2 μ V.

The FM distortion was 0.5 percent in mono and 0.66 percent in stereo. The ultimate noise quieting was 63 dB in mono and 57 dB in stereo. Other FM performance parameters, all of which were good for a low-priced receiver, include a 1.9-dB capture ratio, 47-dB AM rejection, and 71-dB pilot carrier suppression. We were unable to measure the alternate-channel selectivity and image rejection owing to the presence of the non-defeatable afc. In

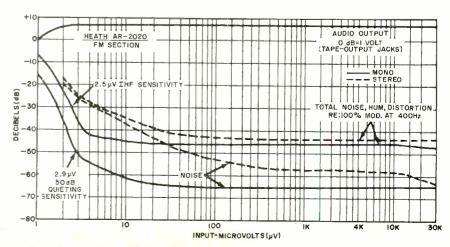


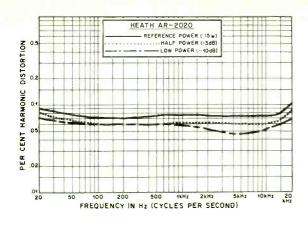

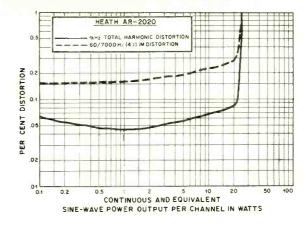

spite of the lack of muting, the interstation noise was not objectionable, and tuning for low distortion was not critical.

The stereo FM frequency response was ±1 dB from 30 Hz to 15,000 Hz. Channel separation was better than 22.5 dB over that range and exceeded 35 dB through the middle-frequency range. The AM tuner sound was like most we have heard—acceptable though far from high-fidelity in its frequency response. The lack of an external AM antenna terminal prevented us from making AM frequency-response measurements.

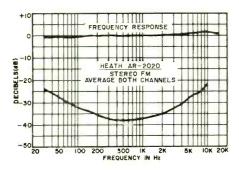

The audio section of the receiver was excellent, easily surpassing its ratings. With all four channels driven simultaneously into 8-ohm loads at

1000 Hz, the output waveform clipped at about 22 watts/channel. The THD was less than 0.1 percent (typically about 0.07 percent) from 0.1 watt up to about 21 watts, and IM distortion increased smoothly from 0.16 percent at 0.1 watt to 0.3 percent at 20 watts.

Unlike most receivers, the distortion in the AR-2020 was almost unaffected by frequency or power output over a wide range. From 1.5 watts to 15 watts, and from 20 Hz to 20,000 Hz, the distortion was typically between 0.06 and 0.08 percent. It never exceeded 0.1 percent.

The tone controls use feedback cir-

TIGER "B" — BASIC POWER

Now available, our latest version of the amplifier that started it all; the faithful old "Universal Tiger". We have put him in a fancy new chassis and added our famous complementary differential input circuit, but this is still the rugged, low distortion, economical amplifier that thousands of you out there love so well. With a power output of 75 Watt into an 8.0 Ohm load, or 90 Watt into 4.0 Ohms the "Tiger B" is the ideal BASIC amplifier for all types of applications; from HiFi systems to public address work, to instrument amplifiers; you name it. With its tremendous frequency response, -1.0 dB at 1.0 Hz and 100KHz and super low distortion of .05% IM at rated output, Tiger "B" is ideal for almost any application using an audio amplifier.

Nothing but the best components and first quality fibreglass circuit boards are used in this kit. The chassis is bronze anodized and the perforated metal cover is standard.

For those who insist on "guilding the lilly" we have an accessory kit to add an output meter, input level control, overheat indicator lamp, front panel power switch, etc.

Circle our reader service number for your free copy of our latest catalog.





Southwest Technical Products Corp. 219 W. Rhapsody, Dept. RE San Antonio, Texas 78216

The better the the better you

COMPU-TRAINER TUBE & TRANSISTOR and lessons. Compare DIGITAL MULTIMETER tuition 12:01:36

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. Equipment you'll build and keep. Our courses include equipment like the 5" solid-state oscilloscope, transistor and tube-tester, vector monitor scope, 74 sq. in. B&W TV, and solid state stereo AM-FM receiver. The unique NTS Digital GR-2000 color TV with first ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock,) and big 315 sq. in. ultra rectangular screen. This is just a sampling of the kind of

ELECTRO - LAB

NTS DIGITAL GR-2000 SOLID STATE TROUBLESHOOTER COLOR TV WITH 315 SQ. IN. PICTURE VOM AND VARACTOR DIGITAL TUNING

better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

equipment



POWER SUPPLY

www.americanadiohistory.com

Compare our training; compare our tuition. We employ no middlemen because we need no salesmen. We believe you have the right to make your own decisions based on the facts, and you'll find these all spelled out in our catalog mailing. Lessons, kits, and experiments are described in full color. Most liberal refund policy and cancellation privileges - it's all in writing. And our low tuition is another big advantage. No frills, no commissions to pay. This means lower tuition for you. You receive solid training value. NTS puts more into your training, so you get more out of it. Make your own decision. Mail the card, or write if card is missing. There's no obligation, ever, and no salesman will call.

Approved for Veteran Training. Get facts on new 2-vear extension.

NATIONAL (TECHNICAL) SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905 Resident & Home Study Schools 4000 South Figueroa St., Los Angeles, Calif. 90037 cuitry, with a sliding bass turnover frequency and a rather considerable range of ± 17 dB in the bass and ± 15 dB in the treble ranges. The RIAA equalization was very accurate, within ± 1 dB from 30 Hz to 15,000 Hz. With the channel level controls set to their midrange positions (-11.5 dB), 10 watts output required a 0.48-volt input (AUX) or 5.8-mV input (PHONO). The corresponding S/N measurements, referred to 10 watts output, were 86 dB and 76 dB—both exceptionally good.

Phono overlcad, in spite of the relatively low phono preamplifier gain, occurred with only 38 mV of input signal when the internal PHONO ADJ sensitivity controls were set according to instructions for maximum gain. As Heath points out, reducing these control settings can allow phono inputs of many volts to be accommodated without distortion, but the relatively low gain is further reduced when this is done.

The relatively limited dynamic range of the receiver makes it advisable to avoid the use of cartridges with unusually high output levels. Fortunately, the receiver's low noise level makes it practical to operate the volume and level controls at higher-than-normal settings without excessive hiss, minimizing the possibility of overload distortion.

The IC matrix decoder is a second potential source of distortion; it overloads at phono inputs of 25 mV with the recommended internal control settings. We suggest reducing the matrix gain somewhat, at least to the point where the dynamic range matches that of the phono preamplifier.

Assembling the Kit. Ten circuit board assemblies are employed in the AR-2020 kit. Seven of them plug into an eighth "master" board. The remaining two, for the tuner and volume/tone controls, mount separately from the other boards. The plug-in assemblies save a lot of time, as does the familiar Heath prefabricated cable harness for interconnecting the various parts and subassemblies and the fact that most of the controls and switches mount directly on the tone board.

Carefully following the step-by-step assembly procedure in the kit's manual makes building the kit practically mistake-proof. A determined new-comer to kit building could probably assemble the receiver with good results on his first try.

Working carefully, the kit took us about 26 hours to assemble.

User Comment. The AR-2020 re-

ceiver makes effective use of current IC technology. It uses a single IC for the entire FM i-f amplifier, another for the limiter/quadrature detector, and a third for the multiplex demodulator. The audio section is more conventional, employing just one IC for the phono preamplifiers of both input channels and another for the matrix decoder. (Although it is not stated anywhere, the IC is for the standard SQ matrix.)

The FM tuner delivers excellent performance. It has been some time since we have seen a quality FM tuner without a tuning meter and interstation muting. Fortunately, the AR-2020's afc system makes tuning easy. In its power capability and general quality of the audio section, the AR-2020 outclasses most other low-priced 4-channel receivers.

We were surprised at the receiver's lack of tape monitoring facilities. It has 4-channel recording outputs and inputs, but both cannot be used simultaneously for listening to a tape while making a recording.

As the test results reveal, the AR-2020 is a good receiver, honestly and conservatively rated. For someone who enjoys kit building, the AR-2020 certainly provides the most receiver for the money.

CIRCLE NO. 5 ON READER SERVICE CARD

DESIGN ACOUSTICS MODEL D-6 SPEAKER SYSTEM (A Hirsch-Houck Labs Report)

Seven-driver, three-way system



Speaker system from Design Acoustics appears to be quite conventional. Its walnut-finish wood cabinet measures 24½ in. by 16½ in. by 13¾

in. (62.23 cm \times 41.91 cm \times 34.93 cm) and weighs about 30 lb (13.6 kg). This is about as conventional as the D-6 gets.

Within the modernistic cabinet, seven drivers are employed in a three-way system. A 10-in. (25.4-cm) woofer is mounted on the rear panel of the enclosure, along with its damped ducted port. A 5-in. (12.7-cm) midrange driver faces forward. Rounding out the speaker complement are five 21/2-in. (6.35-cm) tweeters, one facing forward and the remaining four mounted on the bevelled edges around the perimeter of the front panel. The speaker arrangement in the D-6 is designed to yield a 180° dispersion in both the horizontal and vertical planes to provide a hemispherical listening area coverage.


The crossover frequencies in the speaker system are located at 800 Hz and 2000 Hz. A pair of switches on the rear of the enclosure permit the lis-

tener to select between an anechoic flat response or to reduce the levels of the woofer and/or tweeter by about 3 dB to permit compensating for room acoustics and speaker location.

This speaker system can be positioned either horizontally or vertically almost anywhere in a listening room. The only requirement is that the rear panel, on which the woofer is mounted, must be at least 2 in. (5.1 cm) from the wall. The impedance of the system is nominally 8 ohms. An amplifier of at least 20 watts (minimum) is recommended for driving the system.

The retail price of the D-6 speaker system is \$249 for the walnut-finished version or \$299 for the rosewood-finished enclosure. Optional 2¼-in. (5.72-cm) bases for using the speaker system in a floor-standing location are \$15 per pair.

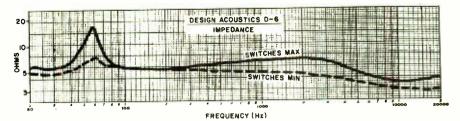Laboratory Measurements. When POPULAR ELECTRONICS



we measured the frequency response of the D-6 speaker system in a normal "live" room with the tweeter and woofer switches set high, the result was quite smooth. The response rose slowly with increase in frequency so that the output at the highest frequencies was about 5dB to 8 dB higher than the bass and midrange levels. Setting the tweeter level switch to its attenuator position reduced the output by about 5 dB at frequencies beyond 2000 Hz to provide an overall frequency response that was exceptionally flat — within ±2 dB from 45 Hz to 15.000 Hz.

The low-frequency output was measured both in front of the woofer and at the port opening. The "crossover" between the woofer and the port radiation occurred at 55 Hz. The overall bass response, a combination of the radiation from the woofer and the port, was excellent — within ±2.5 dB over a frequency range of 43 Hz to 600 Hz. It was ±1 dB from 50 to 600 Hz. The low-frequency (woofer) switch reduced the output by about 3 dB at frequencies below 800 Hz in the attenuate position.

We measured the bass distortion with our microphone directly in front of the woofer. Consequently, our figures do not reflect the low-distortion distribution of the port at frequencies below 55 Hz. Even so, the distortion measured less than 3 percent down to 50 Hz, reaching 5 percent at 40 Hz and, ultimately, 10 percent at 35 Hz. The results were essentialy the same whether we used a constant 10-watt drive or a constant acoustic output of

90 dB sound-pressure level (SPL) measured at a distance of 1 meter from the speaker. A measurement that could include the outputs of both the port and woofer would most likely have shown even lower distortion.

The tone-burst response was uniformly good. With both level switches set to maximum (anechoic flat), the impedance of the speaker system was 5 to 8 ohms at most frequencies up to about 5000 Hz. It fell to 4 ohms in the 10.000-Hz to 20.000-Hz range and increased to 16 ohms at the 58-Hz bass resonance. With both switches set to their attentuation positions, the 58-Hz peak was reduced to 7 ohms, and the system impedance was lowered at most other frequencies, falling as low as 3.5 ohms at frequencies beyond 10,000 Hz. Hence, we deem it inadvisable to use a D-6 speaker system in parallel with another speaker system on the same channel. This might result in too low an impedance for many amplifier outputs to accommodate.

User Comment. In our simulated-versus-live recorded listening test, the D-6 speaker system was 100-percent perfect at any point in our listening room! (For this test, the controls were in the anechoic flat positions.) This is the only speaker system in our experience to achieve this status. Not only were the highs "on the nose," but the important midrange portion of the audio band was reproduced with no coloration that we could detect by ear or by measurement. The bass range was clean and solid and so well-matched to the sound of the other

drivers that there was no hint of transition from the angled forward-facing tweeters to the rear-facing woofer.

For our listening tests, the speaker systems were located a few feet from the nearet wall. Placement closer to a wall or in a corner would boost the bass response, which was impressively powerful in our listening tests. (Presumably, this is why Design Acoustics has provided a switch with which to attenuate the lows, if necessary, to preserve balance.) The D-6 was fairly efficient, requiring ony about 1 watt of drive power to generate a 90-dB SPL measured at a 3-ft (91.44-cm) distance from the speaker system.

Omnidirectional speaker systems (or quasi-omnidirectional hemispherical radiating systems like the D-6) are usually tolerant of any location placement in a listening room. But they are perhaps more responsive than conventional speaker systems to the absorption characteristics of the room. For example, our listening/test room is moderately "live" and has a hard floor so that even the downward-angled tweeter contributed significantly to the total output energy of the system. It is conceivable that a heavily carpeted floor coud absorb much of the output from the lowest tweeter, but since at maximum this would amount to only about 20 percent of the total high-frequency output of the system, the loss would go unnoticed.

In short, the Model D-6 easily ranks among the finest speaker systems we have heard. It is not easy to describe its sound character without resorting to such overworked — but communicative — adjectives as "open," "airy," "neutral," "uncolored," and the like. These and many others surely apply to the D-6. After listening to this speaker system for a while, the colorations heard from many other systems stand out like a sore thumb.

CIRCLE NO. 65 ON READER SERVICE CARD

DYNASCAN COBRA CAM 89 CB TRANSCEIVER

Console-style base station with PA feature



THE Dynascan Corp. Cobra CAM 89 is a somewhat different kind of AM base-station CB transceiver as a result of its console-like design and greater number of controls than is usually the norm. Except for the channel selector, the controls are located in a row across the front panel's lower half that slopes away at about a 30° angle. These controls are for microphone gain (DYNAMIKE), VOLUME and

power on/off, Squelch, Tone, rf Gain, and Delta Tune.

The transceiver also features two toggle switches. One turns on and off the automatic noise limiter (anl), while the other switches the system to either CB or PA operating mode. External speaker jacks are provided for PA operation and the receiver.

Operation on all 23 channels is facilitated by a crystal frequency synthesizer and a large channel selector switch. Two meters are provided. One meter indicates relative output power on transmit and signal strength on receive. The pointer of the other meter swings up-scale with the speech signal and indicates when 100-percent modulation has been reached.

The Dynascan Corp. Cobra CAM 89 CB base-station transceiver retails for \$240.

The Receiver. Double conversion to 11,275-kHz and 455-kHz i-f's is used in the receiver with a ceramic filter for selectivity. The sensitivity measured $0.5 \mu V$ for 10 dB (S + N)/N with 30 percent modulation at 1000 Hz. Adjacent-channel rejection was a minimum of 45 dB, and overall bandpass, with the tone control set at its midpoint was 450 to 3500 Hz. Image rejection was 56 dB. The squelch threshold range was 0.3 to 10,000 µV, while the agc provided a 7-dB a-f output change with a 20-dB, or 1- to 10-μV, r-f input change. The output change was 4 dB with a 60-dB (10- to 10,000-μV) input change. An S9 reading was obtained with a 1000-µV input signal.

The extremely good effectiveness of the automatic noise limiter (anl) could

readily be heard simply by switching it on and off in the presence of impulse noise. With the anl on, the overall a-f volume dropped 8 dB with r-f signals near 1 μ V and 4 dB with signals above 10 μ V.

Advancing the tone control attenuates the response at the high-frequency end of the receiver's a-frange, while slightly increasing the low-frequency response. This allows the user to tailor the voice quality to his liking. At maximum high-frequency attenuation, the overall level of the voice output drops somewhat.

The r-f gain-control setup is unusual. Instead of varying the circuit gain at an amplifier stage, a diode-type attenuator varies the signal level to the antenna input of the r-f amplifier.

For PA service, a class B, a-f output stage provided 4 watts of output power with 7 percent distortion at the start of clipping, using a 1000-Hz test signal and an 8-ohm speaker load. Depending on the control setting, 3 to 4 watts of output power was obtainable on receive with a 1-µV input signal. We also observed that low audio frequency distortion was considerably less than is usually the case.

A conventional frequency-synthesis system employs several nominal 23.5-and 14.9-MHz crystals in conjunction with conversion crystals cut to 11.730 MHz on receive and 11.275 MHz on transmit.

The Transmitter. The transmitting setup is a customary one, with the carrier supplied by a frequency-synthesis system and passed through a spurious-response filter. The carrier

then goes to two r-f stages and the power-output amplifier, which has the usual output-matching network with a TVI filter. The power-output amplifier is collector-modulated by the receiver's audio output amplifier.

With 100-percent modulation, 3.5 watts of carrier output was measured, exhibiting only 2.5 percent distortion at 1000 Hz. By raising the speech input, or microphone gain, 6 dB above that required for 100-percent modulation, the positive peaks continued to rise. This resulted in an upward carrier shift and 10 percent distortion with the positive-peak level equivalent to what would normally be needed for a 4-watt carrier output. At the same time, the negative peaks crossed over, causing the adjacent-channel splatter, with a test tone, to be down nominally 40 cB. On the other hand, with voice modulation and the microphone gain control set for the correct modulation level (as indicated by the panel meter), the splatter can be held to better than 60 dB down

The transmitter's meter scale is calibrated to indicate 100-percent modulation with a steady tone. However, due to the damping characteristics of the meter movement, proper 100-percent modulation with voice is indicated by an average swing to near the center of the scale. Too much microphone gain and continually kicking the meter's pointer to the 100percent point results in over-modulation and undesirable splatter. The overall frequency response was 350 to 2850 Hz at the 6-dB points, while frequency tolerance held to within 350 Hz.

CIRCLE NO. 66 ON READER SERVICE CARD

DATA PRECISION MODELS 134 AND 245 DIGITAL MULTIMETERS

Bench and portable models challenge analog instruments



GOING digital is the "in" thing these days in multimeter design. More and more manufacturers are switching to easily read and interpreted digital displays, abandoning the traditional analog meter movement with its crowded scales and wide room for error both in electrical characteristics and the user's interpretation. The Data Precision Model 134 digital multimeter, retailing for \$189, is an excellent example of the type of instrument that offers the most by going digital.

The Model 134 DMM features a ½-in. (1.27-cm) high 3½-decade display. The bright orange gas-discharge display employs a seven-segment format that is easy to read over a wide viewing angle and from a long distance. The numeral segments cleanly abut at the

corners to produce digits without the breaks common to some other types of seven-segment display systems.

With a + sign implied, the DMM displays a - sign when negative voltages are being measured. Couple this with the instrument's automatic polarity sensing system, and you can well understand how convenient the Model 134 can be when measuring voltages and currents of different polarities.

Functions. The Model 134 DMM is designed to measure dc and ac voltages, direct and alternating current, and resistance. Two rotary switches dominate its front panel to the right of

the display window. One switch is for function selection, while the other sets the range. The only other accessible control is a ZERO potentiometer; this is used for setting the display to zero when the instrument is switched to the resistance function.

Four ranges, going from 1 to 1500 volts full-scale, are provided for the dc voltage measurements. Resolution is 1 mV on the 1-V range. Accuracy is a very good 0.2 percent full-scale, ±0.2 percent of reading, except on the 1000-V range where the figures are 0.5 percent full-scale, ±0.5 percent of reading.

Four ranges, going from 1 to 1000 V full-scale, are also provided for measuring ac voltages. The useful frequency range for measuring ac voltages is 50 Hz to 1000 Hz, but the DMM will measure voltages at frequencies up to about 5000 Hz at slightly reduced accuracy. The basic accuracy on the ac ranges is 0.7 percent full-scale, ±1 percent (±2 percent on the 1000-V range) of the reading. Input impedance is 10 megohms, shunted by 60 pF.

Current in both the ac and the dc modes can be measured in four ranges from 1 mA to 1 A full-scale, with 1 μA as the least significant digit. Under measurement conditions, the nominal voltage drop across the DMM is 100 mV, and current-reading accuracy is 0.5 percent full-scale, \pm 0.8 percent of reading.

For resistance measurements, six decade ranges (from RX0.1 to RX10M, using the kilohm position of the function switch) provide readings of 199.9 ohms to 19.99 megohms full-scale. The least significant digit is 0.1 ohm. Test current is 10 mA on the lowest range, reducing to 1µA on the 1-megohm range. (Test current on the 10-meghom range is 100 mA.) The maximum open-circuit voltage is 15 V, and accuracy is 0.5 percent full-scale.

The DMM is fully overloadprotected on all ac and dc voltage ranges to 1500 V. On the resistance ranges, overload protection is to 250 V, while on the current ranges, protection is to 3 A.

This bench-size instrument measures 81/8 in. deep by 71/8 in. wide by 31/2 in, high (22.5 x 18.1 x 8.89 cm). It weighs 41/4 lb (about 2 kg).

Test Results. We tested the Data Precision Model 134 DMM against our voltage and resistance standards and found it to perform well within its rated specifications. In the actual-use test,

We've put it all together: great looks, accurate reproduction, phenomenal dispersion, and a reasonable price.



Design Acoustics: our name might tell you something. From the beginning, our objectives have been to design truly different speaker systems-systems which achieve accurate reproduction as a result of uniquely flat power response and wide dispersion.

Take the unconventional D-12, for example, It houses nine high-frequency drivers producing uniform dispersion over the entire listening area. The smooth midrange is there, as is the clean, solid bass. Hirsch-Houck Laboratories writes: "Without a doubt, the Design Acoustics D-12 is one of the finest-sounding home speaker systems we have ever encountered.

For those preferring a more conventional look, we offer the D-6-which is anything but conventional. At heart, the D-6 is a direct descendant of the D-12, housing seven drivers strategically placed to attain the same flat energy response with wide dispersion.

You can hear the whole story at better sound stores. Laboratory test reports available on request.



Design Acoustics, Inc., 2909B Oregon Court, Torrance, California 90503 · (213) 320-4981 CIRCLE NO. 13 ON READERS SERVICE CARD

Milniosh catalog DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



FM/FM STEREO - AM TUNER AND PREAMPLIFIER



	McIntosh Laboratory, Inc. East Side Station P.O. Box 96 Binghamton, N.Y. 13904 Dept. PE
1	NAME
	ADDRESS

If you are in a hurry for your catalog please send the coupon to McIntosh. For non rush service send the Reader Service Card to the magazine.


CIRCLE NO. 25 ON READERS SERVICE CARD

the DMM underwent steady use for several hours a day over a period of seven weeks. At the end of that time, we retested the instrument to discover whether or not it had drifted out-ofspec.; it hadn't.

More out of curiosity than for any other reason, we took a look inside the DMM to see what Data Precision, formerly an OEM-only company, was offering for the money. We were pleasantly surprised to see only high-quality materials and workmanship employed throughout, including a complicated printed-circuit switching arrangement. For the \$189 list price, we expect so see the Model 134 DMM replacing many traditional analog instruments in professional test facilities and on home workshop benches.

Another Data Precision DMM.

While we were testing the Model 134, Data Precision sent us their Model 245 DMM (\$295). This battery-powered multimeter is one of the most compact we have ever seen (second only to Hewlett-Packard's Model 97OA DMM to our knowledge). It measures only 5½ in. wide by 3½ in. deep by 1¾ in. high (14 x 8.9 x 4.45 cm) and weighs 1.3 lb (0.59 kg). In spite of its very compact size, this new DMM features 4½ decades of $^{5}/_{16}$ -in. (8.25 mm) seven-

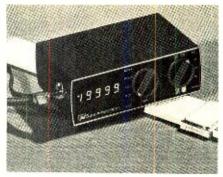

segment gas-discharge readouts and full range/function capabilities.

Four ranges each are available for alternating-current, direct-current, ac-voltage, and dc-voltage measurements. Five ranges are set aside for resistance measurements. For both ac and dc voltage, measurement capability is provided for 1.9999 to 1000 V full-scale. The current ranges go from 1.999 mA to 1.999 A full-scale. And for resistance measurements, the ranges go from 1999 ohms to 19.999 megohms full-scale.

On the dc-voltage ranges, input resistance is 1000 megohms on the 1-V range and 10 megohms on all other ranges. In ac, input impedance is 1 megohm, shunted by 60 pF. The frequency response in the ac-voltage function is 30 Hz to 50,000 Hz. When measuring current, the voltage drop is 100 mV. Finally, test curent in the re-

sistance function is 1.8 mA on the low range, dropping to 0.35 μA on the 10-megohm range.

While the Model 245 DMM will prove very useful on a service bench, it really shines as a field-service instrument. Its built-in rechargeable battery supply makes the multimeter completely independent of line power. The cells will deliver up to six hours of operating time with a full charge. Recharging from the ac power line with a recharger/ac power supply (provided with the DMM) from no charge to full charge can be accomplished overnight.


For bench use, Data Precision has not sacrificed one important nicety. Built into the bottom of the multimeter's case is a small tilt leg. Flipped down, it tilts the front upward at a comfortable viewing angle.

One interesting thing about the Model 245 is that each instrument comes with its own final-acceptance booklet in which the test technician signs his name to verify that certain tests and calibration have been performed. Some of the things he signs for are a 12-in. (30.5-cm) drop test, a 1000-V test of the 1-V range, application of 117 V at 60 Hz to the ohmmeter section of the instrument, and an eight-hour burn-in at 45° C.

CIRCLE NO. 67 ON READER SERVICE CARD

MALLORY MODEL CA3 ULTRASONIC ALARM

Twenty-foot range, no-wiring system

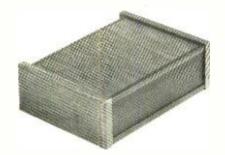

THERE are many ways to keep an electronic "eye" on doors, windows, and other entrances into a factory, store, or home. Most "security" systems employ some form of direct wiring between a number of sensors scattered around the area to be kept under surveillance and a main control unit. For those people who do not wish to go through the mess and bother of wiring up a system, there are ultrasonic alarms that have sensor, electronics package, and sounder or other trip indicator all in one package.

In essence, an ultrasonic security system "floods" the area to be kept under surveillance with a high-frequency sound that is beyond the range of human hearing. Any motion within the secure area disturbs the ultrasonic sound pattern. The system senses the disturbance and triggers on, energizing a horn, a buzzer or bell, or a light. A good example of an all-in-one ultrasonic alarm system is the Model CA3 from Mallory. It retails for \$139.95.

The alarm provides coverage at up to 20 ft (6.1m) away in a conical pattern measuring about 90° wide in front of the built-in transducer. All operating controls for the system are located on the rear apron. There is a HORN ON/OFF switch and a STANDBY/INSTANT/DELAY switch, as well as a response speed control. In addition to the controls, the rear apron accommodates a 120-volt ac, 3-ampere outlet into which a bell, buzzer, siren, lamp, or other signalling

device can be plugged. Finally, there are six screw-type lugs, arranged in three pairs for: REMOTE RESET and OPEN and CLOSED SWITCH LOOPS.


In the three-position switch's STANDBY position, the system is on but cannot be tripped. In INSTANT, the alarm immediately trips upon detection of an intruder, while in DELAY, a 30-second alarm delay permits the user to exit the premises before the alarm arms.

The alarm device can be either the system's built-in horn or any device rated at up to 300 watts plugged into the rear-apron outlet. Once the alarm trips, it remains energized for about 2 minutes, after which it shuts off and automatically rearms itself. The variable-response control allows the response to movement to be set fast or slow.

The screw-type lugs permit the use of some optional devices with the basic alarm system. A pair of wires

terminated in a normally-open pushbutton switch can be connected to the REMOTE RESET terminals to permit the alarm to be reset from a location outside the protected area. Panic switches, thermostat devices, mat switches, etc., can be connected to the OPEN LOOP contacts to provide a variety of services. And normally closed devices-like magnetic window and door switches-can be connected to the CLOSED LOOP contacts to provide perimeter protection.

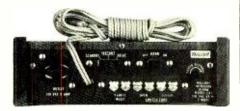The model CA3 ultrasonic alarm reguires only 3 watts of power for its circuitry, plus whatever extra power is demanded by the devices plugged into the rear-apron outlet.



User Comment. We tested the Model CA3 alarm in various environments. In our shop, we verified that the range was indeed about 20 ft. However, we also noted that this could be extended by a good percentage if the alarm is used in a hard-walled area, probably as a result of the ultrasonic energy bouncing between the hard walls in the hallway in which the test was performed. The sensitivity control permitted us to adjust the system to respond to only a slight intrusion.


As with all ultrasonic detection systems, this one affected some animals—specifically, cats and dogs. But we can also report that this system did not affect our remote-controlled TV receiver as some others have done in the past.

We also tried using the system as a light turn-on device, plugging an ordinary lamp into the socket on its rear panel. When we entered our darkened home, the alarm tripped (with the internal horn disabled for this application) and turned on the lamp to light our way. With the alarm system powering the lamp for its usual 2 minutes, we had plenty of time to find the wall switch without tripping over furniture.

The housing of the alarm itself is attractively styled, with wood-grain vinyl-clad metal top and bottom panels and real wood end pieces. The front panel is a dark anodized fine mesh metal. In short, it will blend well into any furniture setting.

CIRCLE NO. 68 ON READER SERVICE CARD OCTOBER 1974

THE ULTIMATE PLIFIER FROM SAE

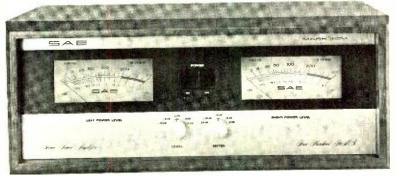

To find out what makes the Mark IIICM the finest amplifier ever made, send today for your free copy of "The Ultimate Amplifier."

SAE, Inc. **Electronics Division** P.O. Box 60271 Terminal Annex Los Angeles, California 90060 Please send my free copy of "The Ultimate Amplifier. NAME ADDRESS STATE PF-1074

CIRCLE NO. 33 ON READERS SERVICE CARD

The New **Electronics** Book

Sophisticated Electronics For Fun

By Joe R. Urschel


A totally new step by step guide to the "how to" of modern electronics, with 190 illustrations in this big 8 1/2" X 11" book.

Now, whether you're a novice or an expert you can benefit from this fact filled, easy to read book. Plus how to use TTL logic, in a non-academic approach to analog and digital electronics.

Special Bonus

Complete tried and proved plans to build . two electronic slot machines. electronic clock with chimes • juke box with no moving parts • computer game. Available in the Chicago area at Kroch's & Brentano's bookstores.

Order Today	
KROCH'S & BRENTANO'S 29 Please send mecopies of Sophisticate completely satisfied. I may return the book(s	d Electronics For Fun, \$6.95 each If not
Name	
Address	
City/State/Zip	
☐ Charge my K & B account	Payment in amount of \$enclosed
Charge my Master Charge or Bank Americard Illinois residents add 5% tax. Free delivery in Chicago an handling charge. Sorry. no C.O.D.'s.	Expiration date d suburbs. Elsewhere add 40° per book mailing &

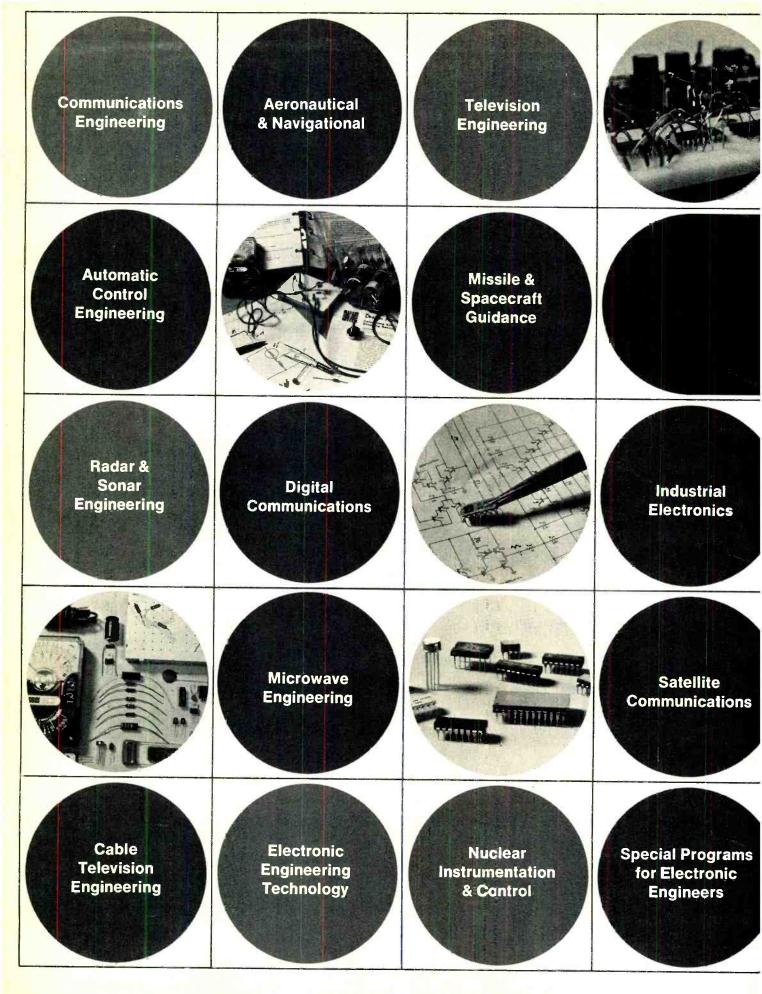


Computer Engineering

ADVANCED ELECTRONICS CAREER TRAINING AT HOME

If you are too busy to go to college to learn advanced electronics, CREI brings college level training to you. CREI programs give you practical engineering training that you can apply in your work to move ahead to higher paying jobs. And CREI lets you specialize in exactly the area of electronics you want. You have a choice, depending on your qualifications, of 18 different programs.

Not only are CREI programs college-level but arrangements are available for you to earn college credit applicable to advanced degrees.

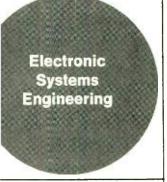Only CREI offers you a choice of 18 programs in advanced electronics



Nuclear Engineering Technology

Special Programs for Non Electronic Engineers For over 45 years CREI programs have been recognized by leading technical organizations as effective home study training in advanced electronics.

NEW OPTIONAL LAB PROGRAM



CREI now offers a supplementary ELECTRONIC DESIGN LABORATORY PROGRAM to make learning advanced electronics easier and to give you actual experience to use in your work. Only CREI offers this complete college type laboratory program. You learn to actually design electronic circuits. At the same time you get extensive experience in tests and measurements, breadboarding, prototype

building and other areas important to your career.

Qualifications to Enroll. To qualify for enrollment in a CREI program, you must be a high school graduate (or equivalent). You should also be working in electronics or have previous training in this field.

Send for FREE book. If you are qualified, send for CREI's newly published book describing your career opportunities in advanced electronics. This full color book is filled with facts about career opportunities for you.



Accredited Member, National Home Study Council

CREI, Dept. E1210-E 3939 Wisconsin Avenue Washington, D. C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name		Age
Address		
City	State	ZIP
If you have previous	training in electroni	cs, check here 🗌
Employed by		
Type of Present Work		

Veterans and servicemen, check here for G. I. Bill information 🗌

CRCI

CAPITOL RADIO ENGINEERING INSTITUTE

A Division of McGraw-Hill Continuing Education Co. 3939 Wisconsin Avenue, Washington, D. C. 20016

Planning to mov

Let us know 8 weeks in advance so that you won't miss a single issue of POPULAR ELECTRONICS.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription, It helps us serve you promptly Write to: P.O. Box 2774, Boulder, CO 80302, giv-

ing the following information:

Change address only.

Extend subscription.
Enter new subscription. 1 year \$6.98 Payment enclosed (1 extra BONUS issue)

Bill me later -AFFIX LABEL ---0887 no label handy, print OLD address here. zip print print please have 1 00 address

Add'I postage: \$2 per year outside U.S., its poss. & Can.





3 Scene

By Len Buckwalter

MAYDAY—PAN—SECURIT

CCORDING to regulations, don. i have an emergency unless know the exact meaning of these to a terms: Mayday, Pan and Secuitor They're of French origin and descaled the exact degree of distress.

- Mayday means immediate dates of loss of life or property.
- Pan says danger with no mediate threat.
- Security is a warning about safety So if your boat capsizes, the car at plodes or you're lost in the woods. you may be saved by a French Legionesia who happens to be an expert in seconnational communications law.

This bit of nonsense was promoted when I received a large plastic sens imprinted on both sides with and all 1000 words of radiotelephone careating procedures. Designed 🐽 🚌 posted in full view, it prescribes official way to summon help. The page lisher slanted it to the boatman, 200 also suggests a CB'er might beaute from his condensed version of the Geneva Convention on telecomregor, cations. It may make an excellent conversation piece for admiralty lawsers. but is hardly what you need in real 16.

In a tight situation, a CB radio can summon police, Coast Guard, fire department, doctor, ambulance or almost anyone else to the rescue. And a speedy call, say the rescuers, is cree as because the toll of death and injuly is closely tied to the time that passes botween the radio call and when help arrives. That time can be extremisely brief if you pick up the mike and elemmon help moments after the accideal. And there's the rub! You might be to e victim and be unable to pressible magic button, utter "Mayday" (c: whatever appropriate term) to scramble rescuers to your aid.

Meanwhile, a wife, husband, preteen child, your maiden aunt, boss or other passenger may have survived

e injury. Maybe ∴ ∈ak on the CB rig ion can appear g to the unin-Mates has about aird, with 61 dif-Services 1981, with 1988, is hardly the The Secretarian series and that a CB ver if only one 's how to use it is take on oil is at what you can nsider, first, to call for nanning the

terms men-🦠 💆 visely allows sed to attract s immediate ty. The Comane body of CB advisibly substituting to eat of the usual orchibleud | www.cleanumissiontime, flequences and that it is you may call An is enquestion in . . raency commember on some of your can get on the er end choutain. ou believe will arty jar. o. Hr. . . . ckler for rules, though, and was a sall "Mayday," consider vital to the merm will be undelsioned Remonst hat happened or the Treach Co Ses flares were less shall if a little cherg struck—and age ray open made s on a nearby so p- -but as or sould Plain language that ocean't states your predicament, geogrephing co. Joh les exact as possible) and the while the elp you need, is probabilities because finique on CB. Even come professionals use the informer approach to fall listening on the corast upon the hight and hearworld a confidenced operator, Har Scotter Sammoned help from a coccount to marely said: "Will an, reche, was be answer this

Royale jet sink to that problem of gov. to 2000 to 1000 meone knows radio in an

emergency. It is folly to venture into some situations without one or more passengers knowing how to call for help, whether aboard a boat at night, during limited visibility or while cruising beyond sight of land. Certain driving conditions also multiply the risk, like crossing a desert or a desolate, unpopulated part of the country. If you go camping, CB also reduces the danger following an accident in an isolated region.

In most cases, a simple demonstration to a non-CB'er of how to work the radio should be enough insurance. Be sure to clinch the lesson by having the student actually take the mike and, without assistance, correctly set up the dials and switches for the call. Another successful system I've tried, where nontechnical people must operate electronic equipment, is a simple placard fastened on or near the equipment. For a CB set, it can be as uncomplicated as:

- (1) Turn VOLUME up
- (2) Turn squelch clock. Alex
- (3) Turn CHANNEL SELT ATT TO
- (4) Press button on Michael and while talking

The foregoing should a stronger so that it's appropriate course. Point out whe tions are located and be obvious to anyon

Has anyone been - ... by term foresight? I recall a session of mass Doris Day, in an old took over the control of the sector and, following instructions: flew the mighty plan house horsy but safe, landing. The story of a room ray real-life pilot died at the modern of oils small airplane with to a rition in their

There are many wa Which one is the rig





aboard-none of whom could fly. Tragedy was averted when the dead pilot's wife grabbed the controls and was talked down to a non-lethal crash by someone on the ground. Like Doris, the woman was no pilot, but knew how to work the radio.

CB Telphone? "I have need to talk over my mobile CB rig through a HANDBOOK touch-tone phone system," writes a reader from Tuscon, Arizona. At some time, we all have that need. What greater electronic luxury could there be than using a mobile CB rig on land or water to make a conventional telephone call, with no phone patch or other intermediary. Just tap some pushbuttons on the rig to dial the desired number, then wait for the ring at the other end of the circuit. It would link your CB set to any telephone in the world. What are the chances of getting such an accessory?

Hams are already using the system on the 2-meter band. Called "autopatch," it's done with a simple encoder attached to the transceiver. It creates a pair of audio tones for each digit (or other dialing function) and modulates them onto the carrier. At the receiver end, a decoder processes the signals for feeding the telephone line. In operation, the autopatch sysem is remarkably like speaking over a egular phone.

But CB'ers will probably have to vait many moons before they can njoy the benefits of an autopatch. Its purpose in ham radio is direct access to the telephone dialing system sole-

for emergency or other special communications. It is not authorized tor personal use. For example, a ham cack on a paralyzed freeway may not dial home and say, "Hold the hamberger, dear, I'll be late for dinner."

Another barrier to the CB autopatch a purely technical. It calls for much to me-brewing and interconnection of equipment—which is a ham's province, but a CB'er's pitfall. The possibildy of commercially built autopatch for ೦೬ is also remote because it would be contrary to FCC law for CB to compete with an existing system that is already aconsed to provide mobile telephone stravice (e.g., Ma Bell). Unless some->>> can prove that direct phone aceres for CB would be in the public rest, there is little chance it would taget with approval. So the convensee of phoning from a car is still restricted to hams and those block-VIP limousines.



they come through LOND AND CLEAR in the all-new 1975 COMMUNICATIONS

Here is everything you want to know need to know 4 about Citizens' Band, Amateur Radio Shortwave Listening.



DON'T TURN A DIAL. In fact don't even buy a dial or anything else anti you've checked out the 1975/Communications Handbook. Whatever your tacher specialty - whether you're an old hand or just getting started this vital "how to guide will help you get greater value, greater enjoyment out of every minute you spend with your equipment

The all-new 1975 COMMUNICATIONS HANDBOOK is scheduled to go on sale nationally November 21, 1974.

YOU CAN RESERVE YOUR COPY NOW AT THE SPECIAL PRE-PUBLICATION PRICE OF ONLY \$1.00 POSTPAID.

Regular newsstand price is \$1.25, mail order \$1.60

So to make sure you come through "Loud and Clear" in 1975,

RESERVE YOUR COPY NOW AND SAVE WITH THIS SPECIAL PRE-PUBLICATION
OFFER AVAILABLE TO READERS OF
POPULAR ELECTRONICS MAGAZINE ONLY.

PRE-PUBLICATION RESERVATION FORM


Communications Handbook Ziff-Davis Service Division 595 Broadway

New York, New York 10012

Enclosed is \$1. Please reserve my copy of the 1975 Communications Handbook at the special pre-publication price to be mailed to me on or before November 21, 1974,

Print Name	
Address	
City	
State	Zip
PAYMENT MUST BE	ENCLOSED WITH ORDER

PE-1074

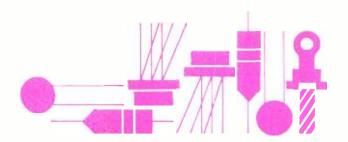

Solid State

EXPERIMENTING WITH LIGHT EMITTING DIODES

ED'S—light emitting diodes—are being used in everincreasing numbers by hobbyists and experimenters as well as by original equipment manufacturers. Physically small, lightweight, available in several colors, rugged, easily installed, efficient, and with a virtually unlimited service life, they are ideal visual indicators.

As pilot lamps, LED's are rapidly displacing incandescent bulbs despite a somewhat higher initial unit price. The difference in device cost is deceptive, however, at least as far as original installations are concerned. Where an incandescent bulb is used as a pilot, one must provide a socket, mounting bracket and, usually, a colored lens or jewel and suitable mounting. In contrast, a LED can be wired directly and permanently in place and, generally, has its own integral lens. When the *total* installed cost is considered, then, a LED may prove less expensive, in many cases, than an incandescent lamp, while offering the advantages of low power drain and long life.

Probably, simple pilot installations account for the majority of present LED applications. If you feel that LED's can be used *only* in such applications, however, you may be in for a surprise.

Put on your thinking cap and consider their unique electrical characteristics: they are basically diodes, their power requirements are nominal, and they are tolerant of a broad range of currents. A typical low-cost unit is capable of supplying a useful light output with currents as low as 10 mA, while accepting maximum currents of up to 50 mA without damage. These characteristics permit LED's to be used in a variety of valuable, interesting, and practical projects, both individually and in conjunction with other solid-state devices. Several of many possible LED applications are illustrated schematically in Figs. 1 through 3.

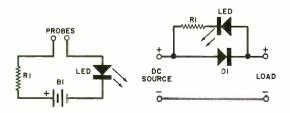


Fig. 1. Circuit (A), left, is continuity checker; (B), right, polarity reversal alarm.

The simple continuity checker circuit illustrated in Fig. 1A can be assembled at minimum cost in a single evening. A standard probe body, a small metal box, or even a large plastic vial can be used for housing the project. The battery

may be two or more penlight cells or even a 9-volt transistor battery, while *R1*, a half-watt resistor, has a value chosen to limit the short-circuit current to between half and three-quarters of the LED's maximum rating. Typically, a 1.6 volt, 50-mA LED, used with a 9-volt battery, would require a 240- to 330-ohm resistor.

In operation, the instrument is used just as one would use an ohmmeter for checking the dc continuity of circuit wiring, terminal connections, switch contacts, and even components, such as coils, transformers, loudspeakers and relays. The LED lights if there is a continuous dc path between any two terminals to which the test leads are applied.

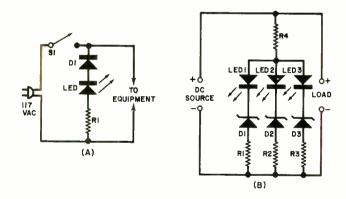


Fig. 2. Two useful applications: (A) Line pilot for ac; (B) voltage monitor for dc.

Unlike many inexpensive commercial continuity checkers, this unit will provide a positive indication even if the circuit's resistance is moderately high. An experimental model assembled using a 9-volt battery and a bargain-package LED provided a useful output with test resistances of up to 3000 ohms.

A useful variation of the polarity reversal protection circuit discussed in our August column is shown in Fig. 1B. Here, the protective diode is shunted by a LED in series with current-limiting resistor R1. With correct dc polarity applied, diode D1 acts as a virtual short, supplying power to the equipment (load). If the supply polarity is reversed accidentally, D1 acts as an open circuit, preventing equipment damage, while a small reverse leakage current, limited by R1, flows through the LED, illuminating this device and signalling the operator.

This circuit may be assembled in an external case attached between the equipment's supply terminals and the

dc power source or, if preferred, built into the protected equipment.

Despite their low voltage ratings and dc power requirements, LED's can be used as ac line pilots and low-level night lights (in place of neon bulbs). Simply add a small rectifier diode (*D1*) and a current-limiting resistor (*R1*), as illustrated in Fig. 2A. Generally, *D1* would be a 200-volt silicon rectifier, the LED a 1.6-volt, 50-mA (max) type, and *R1* a 10,000-ohm, 2-watt resistor.

You can use the inexpensive voltage monitor circuit given in Fig. 2B with any type of equipment in which do supply voltages are critical. Typical examples are small aircraft radio gear, precision test instruments, and some types of medical electronic equipment. Standard LED's are used in conjunction with zener diodes *D1* to *D3* and current-limiting resistors *R1* through *R4*. The zener values are chosen for the minimum, optimum and maximum voltages which can be tolerated by the equipment, taking into account the voltage drops across the LED's and the series resistors.

Assuming that D1 is chosen for the low-voltage limit, D2 for the optimum voltage, and D3 for the maximum voltage, the three LED's will light in a varying pattern to identify supply voltage conditions. With optimum voltage applied, LED1 and LED2 are illuminated. If all three are dark, the supply voltage is either too low or absent, while if only LED1 lights, the voltage is above the minimum, but below the optimum value. Finally, should all three light, the voltage is at or above the high limit.

With suitable circuit component values, the LED voltage monitor is capable of maintaining a constant check on do supply voltages to within a half-volt, or better, in practical installations.

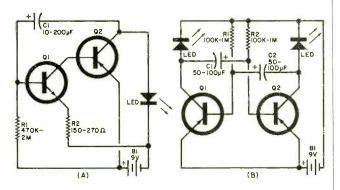


Fig. 3. LED flasher circuits: (A) relaxation oscillator; (B) alternate blinker.

Unlike incandescent lamps, which have a characteristic thermal time lag, LED's can be flashed at rates of less than 1 Hz to many kHz, permitting their use in visual timers or metronomes, toys, opto-couplers, alarms, and similar projects. Any of several techniques may be used to provide an attention-getting repetitive flash. The simplest employ a single special-purpose device, such as a UJT, PUT or MISER. However, quite acceptable resuits can be obtained using low-cost general-purpose transistors, as found in bargain assortments. Two practical circuits are illustrated in Fig. 3.

The complementary relaxation oscillator shown in Fig. 3A features direct-coupled npn(Q1) and pnp(Q2) transistors, with the LED serving as the output load. Capacitor C1 provides the feedback necessary to start and maintain oscillation. The circuit's repetition rate (frequency) de-

BE CHOOSEY

YOU CAN AFFORD TO WITH EICO

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. If you prefer, you can "Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Burglar-Fire Alarm Systems and name of nearest EICO distributor, check reader service card



CIRCLE NO. 14 ON READERS SERVICE CARD





1975 catalog

244 PAGE RADIO, TV & ELECTRONICS CATALOG!

Your buying guide for Everything in Electronics... Stereo, H-Fi, TV's, Radios, Tape Recorders, CB, Kits, Tools, Books, and Electronic Parts.

WRITE
FOR
YOUR
FREE
COPY
NOW!

burstein - applebee

DEPT. PE 3199 MERCIER ST.
KANSAS CITY, MO. 64111

NAME ______
ADDRESS _____
STATE _____ ZIP _____

OCTOBER 1974

pends on the transistors' characteristics, on the component values, and on the supply voltage. If desired, the npn and pnp devices may be interchanged, provided all other dc polarities (C1, LED, and B1) are reversed.

You can use this circuit as a simple flasher or as a visual timer or metronome, by making one of the frequency determining components variable (such as *R1*).

While the exact component values will vary with the transistors' characteristics and the supply voltage, good starting values for circuits using small general-purpose transistors are shown at Fig. 3A. Generally, the larger the feedback capacitor(C1) and the base bias resistor(R1), the lower the flashing rate, and vice versa.

An alternate flashing action is provided by the collector-coupled multivibrator circuit given in Fig. 3B. This is an especially good circuit for use in toys, with the LED's serving, say, as the flashing eyes of a clown or similar character. Although pnp devices are shown, npn types may be used simply by reversing all dc polarities. With a given pair of transistors and a fixed supply voltage, the circuit's repetition rate is determined by the values chosen for C1, R1, C2 and R2. The greater the R-C time constant, the lower the flashing rate.

The circuits described are but a small sampling of those which can be developed using LED's. All were benchtested using inexpensive 1.6-volt, 50 mA red devices.

Perhaps the most interesting of the new LED devices is the RLC-200 series introduced recently by Litronix, Inc. (19000 Homestead Road, Vallco Park, Cupertino, CA 95014). These devices feature an internal current-regulator IC, permitting their use with 4.5 to 16 volts, without an external current limiting resistor.

Reader's Circuit. The "Wail/Whoop" siren generator circuit given in Fig. 4 offers interesting possibilities whether or not you operate an emergency vehicle. If you're a student, you might consider its use as part of a Science Fair project. If you're part of a rock group or involved in amateur theatricals, it could prove useful for special sound effects. It should make a fine alarm source for an intrusion or burglar detection system. And even if you're not involved in any of these, it's worth tackling.

Submitted by reader Max W. Hauser (1712 Francisco St., Berkeley, CA 94703), the generator features a pair of readily available IC's and is designed for operation on a standard 12-volt dc power source. Max writes that he designed and built the system a little over a year ago.

In operation, a voltage-controlled oscillator, IC2, serves as the basic signal source. Its mode of operation is established by selector switch S2, while its instantaneous fre-

quency is determined by the voltage applied to its control terminal (pin 5).

With S2 in the WAIL position, IC2's frequency is controlled by a ramp voltage developed by a network consisting of R10, C4, and C11. As S1 is depressed and released, C4 charges and discharges, changing the control voltage applied to IC2 and causing a corresponding change in frequency, first rising, then dropping in pitch.

When S2 is switched to its whoop position, IC2 is controlled by a low-frequency sine wave developed by op amp IC1A, connected as a modified Wien bridge oscillator (C1, R4, C2 and R7). The frequency determining feedback bridge develops a signal of about 5 Hz, establishing the cyclic whoop rate.

The characteristic triangular output of *IC2* is shaped into an approximate sine wave by a second op amp, *IC1B*, serving as a nonlinear buffer amplifier. Feedback diodes *D3* and *D4*, in conjunction with shunt resistor *R17*, determine the final output waveform

Max has specified standard components in his design. If preferred, individual type 741 op amps may be used for IC1A and IC1B in place of the 558. All diodes are general purpose types. Except for C1 and C2, which should be either Mylar or polystyrene types and the 15-volt electrolytics, all other capacitors may be either low-voltage ceramic or conventional paper units. Switch S1 is a momentary contact, NO, spst pushbutton switch, and S2 is a spdt toggle, slide or rotary switch.

Parts layout and lead dress should not be overly critical as long as good wiring practice is observed and all signal-carrying leads are kept short and direct. Either a suitable etched circuit board, perf board, or point-to-point wiring techniques may be used for duplicating the design. After assembly, checking and preliminary test, *R17*'s value may be changed for an optimum sine-wave output signal. Max indicates that this is the only critical component in his circuit, and suggests that some builders may prefer to substitute a 100,000-ohm trimmer potentiometer for the 56,000-ohm fixed value unit to insure ease of final adjustment.

According to Max, the "Wail/Whoop" generator delivers an output signal of approximate 1 volt, p-p. This is adequate to drive any standard audio amplifier/loudspeaker system. If preferred, of course, a separate power amplifier may be provided just for the generator. In his tests, Max found that a 1-watt commercial modular amplifier supplied an output level quite satisfactory for his applications.

Device/Product News. Every now and again, yours truly is taken to task by an irate reader or manufacturer (not to

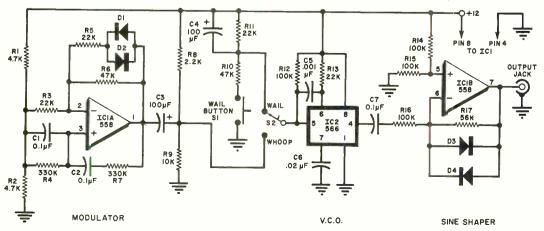


Fig. 4. Wail/Whoop generator circuit uses just two IC's Output is about 1 V.

mention our Editorial Director) for failing to mention a specific new device. Unfortunately, so many new solidstate devices, products and related components are introduced in any given month that it would be impossible to cover them all in the space available, even if the column were doubled in length and devoted entirely to brief discussions of new products. Quite often, a new device of spectacular interest must be omitted simply because it is too costly for average use (would you believe over \$300.00 for a single IC?), too complex to describe adequately in a few paragraphs, or is offered only to OEM's (original equipment manufacturers) who purchase in large quantities. My goal, generally, is to offer a representative sampling of new products covering as broad a range as is feasible to insure touching upon (nearly) everyone's special interests. Our featured selections this month, for example, include both discrete and IC devices suitable for linear and digital applications.

From Texas Instruments, Inc. (P.O. Box 5012, M/S 308, Dallas, Texas, 75222), comes news of four new silicon power transistors and several interesting new IC's.

Offered in two series, TI's new power transistors are npn devices. Designated the TIP63, TIP64 Series, and the TIP65, TIP66 Series, these new units are available in TO-66 and TO-3 plastic packages respectively.

Featuring $V_{\rm reo}$ breakdown voltages ranging from 300 to 350 volts and a continuous power dissipation of 20 watts at 25°C case temperature, the TIP63 and TIP64 series are high-voltage, medium-power units designed for both industrial and consumer applications. The TIP65 and TIP66 Series are horizontal TV deflection transistors designed for line-operated CRT deflection circuits; the units feature 1200- and 1400-volt C-E off-state voltage ratings, 1.5-ampere rated collector current, and fast switching with a typical fall time of 0.7 μ s at 1 ampere.

Designated types SN76701, SN76702, SN76710, and SN76711, TI's new IC's are designed for varactor tuned TV applications. All four units are supplied in 16-pin plastic DIP's. The SN76711 is a logic control circuit for 16-channel systems, the SN76710 a similar device for 14-channel applications. Types SN76701 and SN76702 are analog voltage switches. In practice, one SN76701, one SN76711, and three SN76702 devices, used together, could form a complete 16-channel TV electronic tuning system.

Suggesting that it is suitable for use in oscillators, switching regulators, series regulators, converters, and inverters, RCA (Solid State Division, Box 3200, Somerville, NJ 08876) has announced a new epitaxial-base npn silicon transistor designed especially for use in high-current, high-speed switching circuits. Identified as type 2N6500, the unit is rated for a $V_{\rm ceo}$ of 120 volts and a continuous collector current of 4 amperes, with a total saturated switching time of less than 1 μs . It is supplied in a TO-66 package.

If you're working with digital designs, there's good news this month from your friends at Motorola, Inc., Semiconductor Products Division (P.O. Box 20924, Phoenix, AZ 85036). Not only have the boys from Phoenix introduced three new MECL 10,000 IC's, but they've announced substantial price cuts on many of the standard items in the line, with some reductions ranging up to 45 percent. The new MECL 10,000 devices include the MC10153L quad latch (negative clock), the MC10178L binary counter, and the MC10212L high-speed dual 2-NOR/1-OR gate. All three devices are supplied in 16-pin ceramic DIP's.



EVERYTHING YOU WANTED TO KNOW ABOUT CD IGNITION SYSTEMS BUT DIDN'T KNOW WHOM TO ASK.

Send for FREE Tiger booklet (20 pages) which answers all your questions.

Name		
Address		
City		
State	Zip	

CLIP OUT THIS AD AND SEND TO-

TRI-STAR CORP.
P. O. Box 1727 Dept. E
Grand Junction, Colo. 81501
CIRCLE NO. 38 ON READERS SERVICE CARD

It takes more learn about

Bell & Howell Schools introduces three fascinating learn-at-home programs featuring some of the finest equipment available as your "teachers." Choose the program you prefer—then mail card for free details today!

Experience is the best teacher, without a doubt. And when it comes to learning electronics, we feel it's hands-on experience with state-of-the-art equipment that counts the most. That's why with Bell & Howell Schools'learn-at-home programs you work with some of the most up-to-date equipment. Equipment that's being used today—and will be used tomorrow. So the skills and knowledge you acquire will be useful for years to come.

Of course, with all our learn-at-home programs you'll have plenty of lab manuals and basic principles to work with. And you'll also get exciting "teachers" to help make electronics come alive...

Lab Starter Kit gives you hands-on experience with the very first lesson.

We get you started with the basics in an exciting way! At the very beginning you get a fully-assembled volt-ohm meter as well as design panels, modular connectors, experimental parts and battery. So you don't just read about electronics principles, you actually see them at work!

You build your own Electro-Lab* electronics training system.

Whatever program you choose, you get your own home laboratory including oscilloscope, digital multimeter and design console to give you actual experience in wiring, soldering, assembling, testing, trouble-shooting and circuit analyzing.

 Learn new skills in the field of Home Entertainment Electronics including building the new generation color TV.

What better or more exciting way to learn digital electronics! Once you have the basics under your belt and get into color theory and service, you'll build a 25" diagonal color TV and probe into the digital technology behind digital channel numbers that flash on the screen... a digital clock that flashes the time to the second and an automatic channel selector.

As you put the set together, you'll discover how advanced integrated circuitry works, how to trouble-shoot it and much more. Upon completion of the program you'll have gained the specialized occupational skills to service color TV's plus the principles that you can apply to repair a variety of home electronic equipment. And you'll have the foundation to understand and work with new product applications as they're developed, too!

II. Use professional communications equipment as you delve into Communication Electronics .

Here's how to pick up skills in the vital field of two-way radio, widely used in public safety. marine, industrial and transportation areas. Bell & Howell Schools Communication Electronics Program can help prepare you for the FCC licensing exam, right through to 1st class radiotelephone operator. And teach you skills in two-way radio, radar or commercial broadcasting.

broadcasting.

For a refundable deposit, you get to use the special two-way radio equipment lab featuring an FM transceiver, frequency meter, and modulation meter. All regular, first-rate commercial grade test equipment.

than books to electronics.





Electronic Geriatrics

By John T. Frye, W9EGV, KHD4167

ARNEY, returning from lunch, held the door of the service shop open for a frail, stooped man making a shuffling exit. The latter thanked him with a tired smile and then turned around creakily in the doorway to say in the cracked voice of age, "Do the best you can, Mac. I'll expect no miracles. That little set's pretty old—but then so am I!" The old man's lips were still curled in a sardonic smile as he turned around and left.

"It must be tough, getting old," Barney mused as he plugged in his soldering iron.

"Yep," Mac agreed, starting to remove the back of the small portable TV set the last customer had brought in. "Age takes its toll of both men and electronic gear. Did you ever stop to think that you and I are, in a way, in the electronic geriatrics field?"

"Come again?"

"Geriatrics is that branch of medicine dealing with the problems and diseases of old age and aging people. Here in the shop we're concerned with the problems and component failures that occur in aging electronic equipment. Much of our work, like that of the doctor, is concerned with diagnosis; and, like him, we employ a wide variety of techniques to pinpoint the cause of the symptoms our 'patients' display."

Black Boxes and Surgery. "Both the doctor and the technician often employ the 'black-box' approach. The doctor introduces various drugs and dyes into his patient and then traces their course through the body with X-ray or other means and measures the quantity and quality of these substances showing up at the various body outputs. From this, he deduces the level of functioning of various body organs. We do the same thing and call it 'signal injection' and 'signal tracing.' If we cannot pinpoint the difficulty with this black-box method, both of us resort to exploratory surgery.

"Yes, every day you and I perform surgery—some minor and some radical—there on the bench. The surgeon removes obstructing gallstones, kidney stones, emboli, and intestinal masses. We seek out and correct open circuits that block current flow. Doctors give a transfusion of whole blood to anemic patients. We give an electron transfusion by replacing a depleted battery. The doctor is likely to give a 'shot' of cortisone into a sore and inflamed joint. We give a 'shot' of contact cleaner from an aerosol can to smooth out an erratic control or tuner. We, too, perform 'transplants' that are sometimes rejected. Any technician who has substituted for an unobtainable exact duplicate power transformer and has seen the replacement start to smoke and has smelled the unmistakable odor of scorched insulation and shellac knows exactly what I mean."

"Yeah," Barney interrupted, getting into the metaphori-

cal spirit, "and don't forget our patients also need proper nutrition and exercise. Try feeding 60-hertz equipment on 25 hertz, and you've got electronic dyspepsia no Alka-Seltzer will cure; or let a hi-fi or TV set sit around idle in a damp basement for a few months, and it is ready for a trip here to our hospital."

Factors Hastening Aging. "Several factors hasten the aging process of electronic equipment," Mac said. "You've just mentioned dampness which, accompanied by dust, invites arcs in high-voltage circuits, arcs that soon form a carbonized path to bleed away current and overload high-voltage rectifiers and flyback transformers and lead to the breakdown of these components. Heat is another aging element. It melts the seals on capacitors, allowing moisture to enter and cause these units to have a high dc leakage. Heat raises the ambient temperature of transformers, resistors, transistors, IC's, and other components above their rated temperature and contributes to their premature failure. Heat also has a bad effect on many pc boards, rendering them brittle and causing them to warp and crack and break the printed conductors etched in them.

"Incidentally," he said, tossing a plastic slide rule over to Barney, "here's a *Circuit & Conductor Calculator* put out by the G.T. Schjeldahl (pronounced 'Shell Doll') Company of Northfield, Minnesota. With it you can calculate the temperature rise above 20° C. ambient for various currents through an etched conductor of a given thickness and a given width. You can also determine the ohms/1000 ft for a conductor of that width and thickness. Schjeldahl, a major manufacturer of flexible printed circuits such as those used under the dashboards of modern cars, is giving these calculators away free, as long as they last, to people who write for them on company letterheads. Hey, why are you grinning like a Chessie cat?"

"I was just thinking you hadn't mentioned the thing that ages electronic equipment faster than anything else I know; namely, kids! How many times do we get TV sets or hi-fi's in here in which the little monsters have run pencils through both speaker grilles and cones? How many times have we fished pennies, bobby pins, bubble gum, and crayons out from under stuck turntables? We both know how hard kids are on TV tuners and tonearms. They spin the former like a roulette wheel and wrestle with the latter when it is trying to go through its change cycle. I'm trying to forget the TV sets that come in with the knobs broken off or lost, the transistor radios that have been dropped into the bathtub or the ocean, and the tape recorders that have had Cokes spilled through their innards. Some of the things kids do to abuse electronic equipment is enough to make a strong man cry."

"Spoken like a confirmed bachelor!" Mac said, smiling. "However, I've got to admit I've noticed a tremendous difference in how long radios, TV sets, hi-fi's, and tape recorders last in different households; and the homes in which electronic equipment seems to need a minimum of service are invariably those in which there are no children or ones in which the parents have the small-fry under firm control. But let's change to a more pleasant subject. Suppose we try to write a prescription for long life of electronic gear."

Prescription for Long Life. "Operate the equipment from a proper power source. When operating on ac, that

means making sure both the frequency and the voltage are as specified. When operating on dc, that means making sure you use the proper batteries *properly installed*. And when the equipment is not going to be used for a while, get those batteries out of there, no matter how 'leak-proof' they are claimed to be. What we see here in the shop reveals the danger of placing too much blind faith in that claim.

"Protect the equipment from temperature extremes. That means not leaving it on the dash or on the deck behind the rear seat of a closed car sitting in the sun, not locating it near a heat register or radiator or above a cookstove or oven, not failing to see it has ample ventilation when operating, and not placing it directly in the recurrent blasts of cold air from an adjacent air conditioner. Rapid temperature cycling is possibly even harder on electronic equipment than is a sustained elevation of temperature.

"Treat electronic apparatus gently. Just because the impact-resistant case of your transistor radio does not break when you drop it doesn't mean the radio has not suffered 'internal injuries.' Such a jar often breaks the speaker loose from its moorings or the tuning capacitor loose from the pc board. The board itself may be cracked by the violent flexing resulting from the jar. In this case, the bright edges of the conductor fracture may maintain current flow across the break for a few weeks until those edges become oxidized; then the radio 'just quits playing for no reason at all.' Finally, don't let children abuse electronic equipment. Teach them to change TV channels gently, to let the automatic record changer do its thing without interference, and to shut the equipment off when they are not paying attention to it.'"

"Leaving the TV set down for a week or so when it conks out may get the point across to the rambunctious kids," Barney suggested. "Let 'em miss a few episodes of Bat Man."

"Now let's not get carried away," Mac demurred. "After all, we have to make a living, and the Supreme Court has handed down decisions against cruel and inhuman punishment. There's one more thing: if you want to keep your TV set or hi-fi from having a 'stroke,' it's still an excellent idea to pull the line plugs during a thunderstorm. A nearby bolt can induce a surge of voltage into the power lines that can leap across the open on-off switch contacts and do all kinds of havoc before you hear the thunder clap."

"We are extending the potential life of electronic equipment, though," Barney pointed out. "Using solid state cuts

down on the damaging heat such equipment produces internally. Transistors and IC's, properly protected from overloads and transients, have a very long life—so long, in fact, that it has never been measured accurately. Solid-state components are much more resistant to mechanical damage than are tubes. And you, with your long gray beard, know much better than I the improvements that have extended the life of other electronic components."

"Thanks a bunch for that 'long gray beard' crack," Mac replied. "You're right, though, in that no Johnnie-comelately in electronics can fully appreciate the accuracy and reliability engineered into modern resistors, capacitors, coils, and transformers. I still remember those triplesection 8 µf wet electrolytic capacitors the size of a large fruit can that, after the little black nipple of an expansion seal had rotted, spilled electrolyte all over your bench every time you turned the chassis on edge. The first 'dry' electrolytics were not much better. The essential electrolytic moisture readily evaporated from the square or rectangular paraffin-coated cardboard cases and left the capacitors really dry—and useless. Heat quickly melted the sealing wax from the ends of cardboard cases of paper tubular capacitors and let in the moisture. To get away from this, some manufacturers potted paper units in tar and placed them in metal cases riveted or bolted to the chassis. For a period we had metal-cased paper capacitors and cardboard cased electrolytics!

"Resistors were not nearly so accurate, reliable, and compact as the ones we have today. Carbon units were all about two inches long and 3/16" in diameter, with no insulation. With age, they made great excursions in resistance. The only way you could get stability in resistance was to go to wirewound units. Candohm made metal-encased, wirewound bleeder resistors that were riveted to the chassis to provide heat-sinking. This was better in theory than in practice, in my experience. After a radio containing these resistors was out a couple of years or so, most of the sections of the bleeder resistor were bridged with individual wirewound units."

"I'd like to throw in just one more thing," Barney said. "Shoot."

"I've always heard that a doctor who treats himself has a fool for a doctor and a fool for a patient. That goes, doubled in spades, for the fellow who tries to repair modern complicated electronic circuitry without the necessary knowledge and equipment. Nothing can shorten the life of a color TV set faster than some heavy-handed homebrew servicing."

Coming Next Month—

Build a Laser TV System

A Career as a Tech Rep

The 1975 Color TV Sets

Multimeter Range Extender Project

and more





By Herber S. Brier, W9EGQ

GETTING STARTED IN AMATEUR RADIO

Y INTERNATIONAL agreement, Amateur Radio is a noncommercial radiocommunications service used by over 600,000 licensed persons around the world (over 250,000 in the United States). They are interested in radio techniques, intercommunications, and technical investigations from strictly a personal viewpoint and without pecuniary interest. Amateurs (otherwise known as hams) operate their own radio stations on over a dozen bands of frequencies in the radio spectrum from 1700 kHz into the gigahertz region. International amateur communications must be in plain language and are limited to technical remarks relating to tests or to personal information too unimportant to be sent by commercial facilities. Communications on behalf of third parties are strictly forbidden.

These restrictions may be modified by agreements between individual governments, however. The United States, for example, has agreements with Canada, Israel, Jordan, Liberia, and virtually all South and Central American countries to permit their amateurs to handle unimportant third-party essages and emergency traffic relating directly to the safety of life and property. The third-party messages are often in the form of "phone patches," which are conversations carried on interconnecting telephone lines and the radio equipment. In addition, the United States and about 43 other countries have reciprocally agreed to allow amateurs to operate in each other's territories.

In the United States, the Federal Communications Commission issues amateur licenses in five classes. The lowest class is the 2-year, nonrenewable Novice license, which requires passing a 5-wpm code test and a written examination on elementary radio theory and regulations. It authorizes code operation with a 75-watt transmitter in segments of the 3.5-, 7-, 21-, and 28 MHz amateur bands. The highest class is the 5-year, renewable Extra

license which requires a 20-wpm code test and a very comprehensive written test. All citizens and resident aliens who have filed their intention to become citizens are eligible to apply for the license. The Novice license is issued by mail and is free of charge; but all other amateur licenses are issued for a \$9.00 fee (which may go to \$10.00 soon).

Rather than review here the mechanical steps necessary to apply for a license, we suggest that you obtain a copy of *The Radio Amateur's License Manual*, which is \$1.00 from the American Radio Relay League, Inc. (ARRL), Newington, CT 06111. It may also be bought in many stores that sell amateur equipment. The Manual contains the complete text of the FCC regulations, complete instructions for applying for any class of license, and study guides to preparing for the required examinations.

Other publications valuable to the prospective amateur are How to Become a Radio Amateur (\$1.00 from ARRL); The Radio Amateur's Handbook, (\$4.50 from ARRL); and Radio Handbook, 19th edition, by William I. Orr, W6SAI, which is \$14.95 and can be obtained from Radio Publications, Inc., Box 149, Wilton, CT 06897, or from most equipment dealers.

Except for specifying the technical standards that signals must meet and the frequencies for each class, the FCC regulations require only that U.S. amateur transmissions must not be commercial, secret, profane, or cause unnecessary interference to other stations or services. Also, emergency communications relating directly to safety of life and property have priority over all other communications.

On the Air. Most amateurs start their careers with a Novice license so that they can get "on the air" with a minimum of effort and expense and enjoy their hobby while studying for a higher class. Some, however, who are particularly allergic to the code, prefer to

try for a Technician class license. This, like the Novice license, is available by mail and requires passing a 5-wpm code test. However, it has a written examination of the same scope at the General class and authorizes all amateur privileges on the amateur frequencies above 50.1 MHz, except between 144 and 145 MHz.

On the other hand, many Novices soon discover that code or CW operation has a peculiar fascination of its own. They also have so much fun working each other, exchanging QSL (confirmation) cards, ragchewing, and making new friends that they frequently neglect to study for a new license until their Novice ticket is about to expire. Surprisingly, there is not as much difference between what interests the amateur newcomer and the higher class (license-wise) oldtimer as you might think. Of course, the latter may have acquired a little more operating skill and more equipment, but most of them are still interested in ragchewing about every subject under the sun-and DX chasing.

At first glance, the above evaluation of the interests of the average amateur seems to dispute their reputation as being leaders in pushing back the frontiers of electronics. Not at all! We still have the same numbers of dedicated experimenters that we always had. They are transmitting and receiving slow-scan TV picture in the low-frequency phone bands, launching communications satellites that extend the range of low-power vhf stations to other continents, and carrying out other activities that will influence communications in the future.

No-Code 220-MHz Phone. As long as amateur operator licenses have been issued in the United States, a proficiency in Morse code had been a prerequisite. Although international

King Hussein (WJ1) of Jordan is a famous amateur radio operator.



regulations have waived the code requirement for operation above 144 MHz for decades, the FCC has strongly resisted any suggestions that the U.S. join other countries in issuing code-free, amateur vhf licenses. However, in an all-day meeting last May between officials of the Amateur and Citizens Radio bureau or the FCC and the ARRL, the FCC revealed that it is considering the establishment of a new 220-MHz "Communicator" class license, with a written examination covering elementary phone theory and amateur regulations, but no code test!

There are already 43 petitions to modify the amateur licensing structure on file with the Commission; and they will have to be considered when it holds formal hearings on the matter. So don't look for a no-code license to appear tomorrow. Government processes just don't move that fast. Incidentally, one of the other petitions on file advocates the reduction of the General class code speed requirement to 10 wpm, as it was in 1931.

New Logging and Call-Letter Rules Effective July 10, the FCC revised section 97.103 of the amateur regulations. Logs of fixed and portable amateur stations are now required to show only locations and dates of any operations, signatures of visiting control operators, and copies of third-party traffic. Mobile stations do not have to log contacts, but repeater-station logging requirements have not been modified. In announcing the more liberal logging rules, the FCC pointed out that, although it is no longer a legal requirement, a detailed station log is valuable in the event a station is accused of some rule violation.

In Docket 20092, the FCC has proposed that, by paying the \$25.00 special call-letter fee, any Extra class operator may request any currently unassigned set of call letters, including a "2-letter" call, in his area-but only one "2-letter" call to a customer, even if he has more than one amateur stations. In the same docket, special in-memoriam call letters (for example, a special call letter assigned to a club in honor of a deceased member) will be eliminated. Interested parties have until Oct. 9 to file comments on docket 20092 (16 copies) and until Oct. 24 to file replies.

Coming events. Two of U.S. am-0CT0BER 1974 ateurs' biggest annual contests will occur in a few weeks: the CQ World-Wide DX Contest and the ARRL Sweepstakes. The rules summarized below are sufficient for casual participation, but we suggest you request the complete rules and score sheets from the sponsors if you intend to enter into serious competition. Include a legalsize, stamped (20¢), self-addressed return envelop with your request. The World-Wide DX Contest will run from 0000 GMT, Saturday, to 2400 GMT, Sunday; by phone on Oct. 25 and 26, and CW, Nov. 22 and 23. Use any amateur bands to work as many DX stations and zones as possible, exchanging signal reports and zone number with each station worked. (A zone map is included with the rules and entry forms.) Each station may be worked only once per band. Total score is computed by multiplying the total number of contacts (points) by the total of zones and countries worked. Enquiries and entries should be sent to: CQ WW DX Contest, 14 Vanderventer Ave., Port Washington, N.Y. 11050.

The ARRL Sweepstakes will take place from 1500 GMT, Saturday, to 0300 GMT, Monday, for CW on Nov. 2-4 and for phone on Nov. 16-18. Exchange "message preambles" with each station worked: contact number; precedence (A, if power under 200 watts; B, if over 200 watts); call letters; check (last two digits of year licensed); place (ARRL section). Each station may be worked only once per band. Total score is the number of contact points multiplied by number of ARRL sections worked. A section map is included with the SS package; and they are also listed in the front of each issue of QST magazine. Suggested frequencies: 3.55-3.65, 7.05-7.1, 14.05-14.1, 21.05-21.1, 28.05-28.1 and 3.85-3.95, 7.225-7.275, 14.25-14.3, 21.3-21.4, 28.6-28.8 MHz. Novices must remain in Novice bands. The address is Sweepstakes, ARRL, Newington, CT 06111.

The ARRL 160-meter contest will probably be held December 6-8; the 10-meter contest on Dec. 14-15. Then comes CQ's 160-meter contest on Jan. 25-26, 1975, though we have not received official notice of these.

Signoff. The is the first of a new series of quarterly feature columns on Amateur Radio in POPULAR ELECTRONICS. Your comments will be most welcome.

Superb communication for any outdoorsman!



Lightweight and longer range. Weighs only 30 ounces. That's very little extra weight in your pack.

The separate speaker and mike give you maximum transmit range. Choose the power you need—5 watt or 2 watt. And. flexibility with up to 3 channels. Suggested retail price: Only \$86.95.

Spectacular with new Royce battery pack — guaranteed for one full year!

An optional accessory. But, one that will pay off many times over. New 12.5 volt battery can be re-charged over 750 times. Powers the Model 1-406 and any Royce highpower unit for a full 8 to 10 hours! Suggested retail price, including charger, only \$35.45. But, if your conventiona walkie-talkie conks out after 3 hours, when you're lost in the woods, you'll think it was worth \$100! The world's first—from Royce, of course. So good we guarantee it for 1 year.





By Leslie Solomon

A DMM TURNED FREQUENCY COUNTER

IGITAL multimeters (DMM's) are finding their way on to an ever-increasing number of test benches as more and more electronics servicemen and hobbyists come to appreciate the advantages of the unambiguous digital readout. Another digital test instrument that is equally useful on the test bench is the frequency counter. Unfortunately, you don't see as many of these around since, if an economic factor is involved, most people will choose a DMM first.

At this point, we would like to introduce you to a circuit that, when added to the front end of your DMM, will turn it into a frequency counter. It won't have all of the advantages of a good commercial frequency counter; but in building and using it, you will learn a lot about analog and digital processing.

In building the circuit shown, we used components that we had on hand or that are readily available from surplus dealers. Essentially, the input op amp squares up the signal and drives a monostable multivibrator. When the multivibrator is triggered, the constant-amplitude, fixed-width output pulses are summed in an op amp rectifier that produces a dc output proportional to the frequency of the input.

A 709 was used as the input squarer simply because we had it on hand. A 741 could be used, but its upper frequency is limited. The front-end circuit of a frequency counter (FET and Schmitt trigger) could be used instead of the 709. Actually all that is needed is a decent input impedance and the capability of squaring up the input to whatever frequency is desired.

The width of the output pulse of the 74121 multivibrator is determined by a selectable time constant. For example, when measuring low audio frequencies, you can start with a $0.1-\mu F$ capacitor and a 5000-ohm potentiometer. As you go up in frequency,

drop the value of the capacitor in decade steps but use the same value of potentiometer. Incidentally, the circuit shown was used to cover the audio range from a few Hz to about 100 kHz. The values can be changed to reach almost any other frequency within reason.

The 741 output op amp is an integrator that accumulates the pulses and delivers a dc voltage proportional to the number of pulses received. This is then measured on the 2-volt dc range of the DMM.


Setting up the circuit is simple. Short the 709 input to ground and adjust the zero-set potentiometer (on the 741 input) until the DMM indicates zero. It will be possible to adjust this control from some small negative voltage, through zero, to some small positive voltage. Once set, this control does not have to be adjusted for any other range, except for some slight drift in the 741 circuit with time.

Using 0.1 μ F as the timing capacitor, set the input frequency to 1 kHz. Then adjust the calibrate potentiometer associated with that capacitor until the meter indicates 0.100 (assuming the DMM has a $3\frac{1}{2}$ -digit capability). Now as the input frequency is varied, the DMM will display the frequency, except for the decimal point.

Keep in mind that this is not a construction project, but is meant only to introduce you to frequency counting at low cost. A conventional dc voltmeter can be used as the output indicator; and, in conjunction with a decent audio generator, the meter scale can be calibrated for frequency. Once you discover how useful it is to be able to measure frequencies, you will wonder how you can get along without this piece of test equipment. (Incidentally, now that you know how to make a frequency-to-dc converter, give some thought to making a dc-to-frequency converter so that you could use a frequency counter as a dc voltmeter.)

LCD Readouts. Liquid-crystal displays (in wristwatches, DMM's, etc.) are of two types: those that appear as non-mirrors on a mirror background and field-effect displays that appear as dark elements on a light background. Unfortunately, neither of these can be seen in the dark—although there have been some suggestions that tiny incandescent lamps could be used. On the other hand, the LED display is good in the dark but gets "washed out" in daylight.

Recently, we had the pleasure of seeing a new type of display. It is a tritium-powered backlighted fieldeffect liquid crystal that appears as conventional dark digits on a light background in daylight, but is backlighted with a soft green glow (due to the tritium) in the dark. Developed by D. Gene O'Quinn, this soft green glow is not the result of afterglow due to exposure to bright light (as with watch dials) but comes from the tritium itself. The amount of radioactivity is very slight, and should power the readout for many years. The most likely first use will be in wristwatches with other applications to follow.

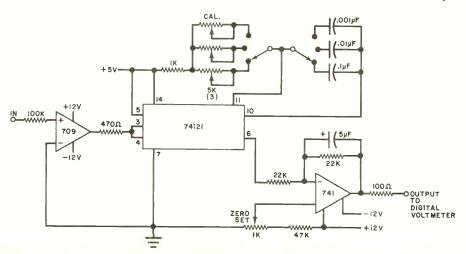



Where to get Parts

In answer to many letters, here are some addresses of suppliers of semiconductors (and other components). The hobby enthusiast should have a collection of their catalogs for locating parts for projects.

First, the larger mail order houses, some of whom also have retail stores in large cities: GC Electronics (Calectro), 400 S. Wyman St., Rockford, IL 61101; Radio Shack, 2617 W. 7th St., Fort Worth, TX 75107; Allied Electronics Corp., 2400 W. Washington Blvd., Chicago, II 60612; Burnstein-Applebee, Dept. PE, 3199 Mercier St., Kansas City, MO 64111; Lafayette Radio Electronics, P. O. Box 10, Dept. 35014, Syosset, NY 11791; Olson Elec-

tronics, Dept. IQ, 260 S. Forge St., Akron, OH 44327.

Others, perhaps not as large but excellent sources of semiconductors, where you may find hard-to-get IC's and other special items, are: Solid State Systems, Inc., P. O. Box 617, Columbia, MO 65201; Altai Electronics, P. O. Box 28592, Dallas, TX 75228; Poly Paks, F. O. Box 942E, Lynnfield, MA 01940; Solid State Sales, P. O. Box 74A Somerville, MA 02143; Tracy Design Corp., 15870 Schaefer, Detroit, MI 48227; Digi-Key, P. O. Box 126, Thief River, MN 56701; Delta Electronics Co., P. O. Box 1, Lynn, MA 01903; Babylon Electronics, P. O. Box J, Carmichael, CA 95608.

Simple Color Organ Circuit


Q. Although you have published many circuits for color organs in the past, I never built one because they were either too complicated or I didn't need one at the moment. Now, I thought I would like to try experimenting with the idea. What simple, basic circuit could I start with to build a color organ?


A. A basic (reduced to the minimum) color organ circuit is shown here. The reversed transformer takes the speaker output from an audio system and drives the SCR's. Gain is adjusted by the potentiometers. You can try various filters in the gate lead of each SCR or just vary the value of the resistor in series with the potentiometer arm. Be sure to use an isolating transformer for safety. Select the lamps and the transformer to match the rating of the SCR's.

Checking Transistor Beta

Q. I know there are many transistor checkers around, but what I am looking for is a cheap way to determine beta. Is there a really simple way?

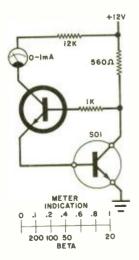A. Try this circuit for npn transistors. When you plug an unknown transistor into the socket (SO1), the circuit will automatically stabilize its collector current at 20 mA. Read the value of beta on the meter using the conversion scaling. For pnp's, be sure to use a pnp to source the current, and use -12 volts for $V_{\rm CC}$. Almost any transistor can be used as the current source.



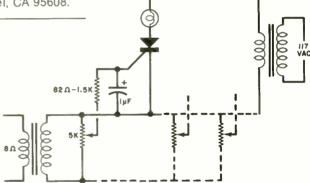



Now...the most enjoyable, do-it-yourself project of your life—a Schober Electronic Organ!

You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ



You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystalclear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models, with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores.

ment actually superior to most you see in stores. Join the thousands of Schober Organ builderowners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives—first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!

Please se	Corp. Street, New York, and me Schober Oplease find \$1.00 Schober Organ m	N. Y. 10023 Organ Catalog for 12-inch L.P.
NAME		
ADDRESS		
CITY	STATE	ZIP
CIRCLE NO. 3	4 ON READERS	SERVICE CARD





THE NEW WORLD OF ELECTRONIC MUSIC

by Walter Sear

Explained in this book are the fundamentals of acoustics, electricity, magnetism, sound recording, electronic sound generators, filters and amplifiers as a background for a practical description of electronic music, and the equipment that is used in creating the "new" music. This book is a broad outline guide for the music student, musician, and serious music listener with an interest in both electronically and acoustically generated music. The book is non-electronic in nature, but it contains much useful information on the electronic music medium for electronics hobbyists who want o get started in a new area of experimentation.

Published by Alfred Publishers, 75 Channel Dr., Port Washington, NY 11050. Soft cover, 131 pages. \$4.95.

BASIC PRINCIPLES OF DIGITAL COMPUTERS

By Vester Robinson This book is devoted to developing an understanding of the basic principles upon which computers and other digital equipment are based. It starts with a broad view of the whole computer field and then goes on to individual topics, such as mathematics, circuits, logic, and functional components. Finally, it assembles these topics to form a whole system, analyzes the system in some detail, and develops the principles of programming. Not only are binary, octal, decimal, and hexadecimal systems explained, but conversions among them are also illustrated. Each chapter ends with review exercises, answers for which are given at the back of the book.

Published by Reston Publishing Co., Inc., P.O. Box 547, Reston, VA 22090, Hard cover. 422 pages. \$13.95.

LINEAR CIRCUITS FOR ELECTRONICS TECHNOLOGY

by Gary M. Miller

Practical up-to-date material on the electronic circuits used in communication systems includes power supplies, all types of amplifiers, oscillators, and new IC's. The use of complicated equivalent circuits is minimized in the discussions; instead, practical approximations allow complex amplifiers to be fully understood while

yielding accurate results. Power supplies are covered early in the book so that the reader can better understand their effects on the circuits subsequently studied. A survey of communication systems is also included. The math level prerequisite does not include calculus.

Published by Prentice-Hall, Inc., Englewood Cliffs, NJ 07632. Hard cover. 332 pages. \$13.95

TRANSISTOR CIRCUIT APPROXIMATIONS, Second Edition

by Dr. A.P. Malvino

This is a revision of an already successful textbook that covers the fundamentals of transistor circuit analysis. Featuring an "ideal transistor" approach, the text utilizes approximations of the most significant aspects of transistor action. Four new chapters—dealing with FET's, special diodes, latching devices, and optoelectronic devices—have been added to this new edition. More problems appear at the end of each chapter as well. The book is suited for students in community colleges, 4-year colleges, technical institutes, and industrial training programs. Algebra and basic electricity are the prerequisites.

Published by McGraw-Hill Book Co., 1221 Avenue of the Americas, New York, NY 10020. Hard cover, 512 pages. \$10.95.

HANDBOOK OF IC CIRCUIT PROJECTS

by Jim Ashe
This new book tells how to use those lowcost IC's you have been reading about in
practical, simple projects that were once
too complicated or expensive to be of general appeal. The book presents 33 projects
in eight broad categories. The categories
cover a wide range of interests: hobby electronics, hi-fi, automotive, SWL'ing,
amateur radio, science and electronics,
and linear and digital testing. The book
leads off with an introduction to the IC and
ends with three appendices that cover the
device and IC's used in the projects, IC literature for the amateur, and IC suppliers.

Published by Tab Books, Blue Ridge Summit, PA 17214, 224 pages, \$7.95 hard cover; \$4.95 soft cover.

BEYOND SHORTWAVE

This new booklet from the Worldwide TV-FM DX Association (WTFDA) is an introduction to the world of DX'ing above 30 MHz. It starts off with propagation basics, then proceeds to separate chapters devoted to TV, FM, uhf, and vhf radio. The text is illustrated and includes information on such topics as meteor scatter reception, choosing DX equipment, photographing TV-DX, improving FM reception, and listening to "private" uhf and vhf communications.

Published by WTDFA, P.O. Box 163, Deerfield IL 60015. Soft cover. 32 pages. \$1.00.

ELECTRONICS MARKET PLACE

NON-DISPLAY CLASSIFIED: COMMERCIAL RATE: For firms or individuals offering commercial products or services, \$1.60 per word (including name and address). Minimum order \$16.00. Payment must accompany copy except when ads are placed by accredited advertising agencies. Frequency discount; 5% for 6 months; 10% for 12 months paid in advance. READER RATE: For individuals with a personal item to buy or sell, \$1.00 per word (including name and address.) No minimum! Payment must accompany copy. DISPLAY CLASSIFIED: 1" by 1 column (2-1/4" wide), \$200.00. 2" by 1 column, \$400.00. 3" by 1 column, \$600.00. Advertiser to supply cuts. For frequency rates, please inquire.

GENERAL INFORMATION: First word in all ads set in bold caps at no extra charge. All copy subject to publisher's approval. All advertisers using Post Office Boxes in their addresses MUST supply publisher with permanent address and telephone number before ad can be run. Advertisements will not be published which advertise or promote the use of devices for the surreptitious interception of communications. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st. Send order and remittance to POPULAR ELECTRONICS, One Park Avenue, New York, New York 10016, Attention: Hal Cymes.

FOR SALE

FREE! bargain catalog. Fiber optics LED's, transistors diodes, rectifiers, SCR's, triacs parts, Poly Paks, Box 942 Lynnfield, Mass 01940

GOVERNMENT Surplus Receivers Transmitters. Snooperscopes, Radios, Parts, Picture Catalog 25 cents Meshna, Nahant, Mass 01908.

LOWEST Prices Electronic Parts. Confidential Catalog Free KNAPP 3174 8th Ave S.W., Largo, Fla 33540

ELECTRONIC PARTS, semiconductors, kits, FREE FLYER Large catalog \$1.00 deposit. BIGELOW ELECTRONICS Bluffton, Ohio 45817

PADIO - T V Tubes - 36 cents each Send for free catalog Cornell, 4213 University, San Diego, Calif 92105

AMATEUR SCIENTISTS. Electronics Experimenters Science Fair Students Construction plans-Complete including drawings, schematics, parts list with prices and Robot Man -Psychedelic shows -Emotion/Lie Detector - Touch Tone Dial Quadraphonic Adapter - Transistorized Ignition Burglar Alarm - Sound Meter over 60 items. Send 25 cents coin (no stamps) for complete catalog. Technical Writers Group, Box 5994, University Station, Raleigh, N.C. 27607


METERS-Surplus, new, used, panel or portable. Send for list Hanchett Box 5577, Riverside, CA 92507

WE SELL CONSTRUCTION PLANS. TELEPHONE Answering Machine, Speakerphone, Carphone, Phonevision, Auto Dialer, Touch Button Dialer, Central Dial System, TELEVISION \$35.00 Color Converter, Video Tape Recorder \$25.00 Camera. HOBBYIST. Electron Microscope, 96 Hour Tape Music System, Ultrasonic Dishwasher, Radar-Oven, Plans \$4.95 each, NEW ITEM: \$75. Electronic Pocket Calculator, \$7.50. COURSES: Telephone Engineering \$39.50 Detective Electronics \$22.50. Integrated Circuit Engineering, \$49.50. NEW SUPER HOBBY CATALOG plus year's subscription to Electronic New Letter AIRMAILED \$1.00. Don Britton Enterprises. 6200 Wilshire Blvd., Los Angeles, Calif. 90048.

JAPAN HONG KONG DIRECTORY. World products information, \$1.00 today. World Trade Inquiries, Hillyard Washington 99207

SCOPES, meters, test equipment, military and industrial surplus Send 25 cents for Bargain Bulletin . Lawrence Instruments, P.O. Box 744, Sunbury, Pa. 17801.

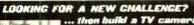WAVEFORM GENERATOR KIT 8038 Function Generator IC Producing Sine, Square, Triangular Waveforms, \$10.95 PPD: 8038 IC, \$6.75 each PPD PHOTOLUME CORPORATION, 118 East 28th Street, New York, NY 10016





ATV Research DANOTA CITY, NESR. 68731

DIGITAL FLECTRONICS Complete schematics, parts Discrete Component Digital Clock lists, theories \$3.00 - Sound Sensitive Switch, \$1.50. Increase technical competence, hobby skills - Complete Course in Digital Electronics is highly effective, \$10.00. Free literature. DYNASIGN, Box 60A7, Wayland, Mass. 01778

MECHANICAL, ELECTRONIC devices catalog 10 cents Greatest Values - Lowest Prices. Fertik's, 5249 "D Philadelphia, Pa. 19120.

SOUND SYNTHESIZER KITS-Surf \$12.95, Wind \$12.95. Wind Chimes \$17.95, Electronic Songbird \$6.95, Musical Accessories, many more. Catalog free. PAIA Electronics. Box J14359, Oklahoma City, OK 73114

FREE CATALOG. Parts, circuit boards for POPULAR ELECTRONICS projects. PAIA Electronics, Box C14359. Oklahoma City, OK 73114.

COMPLETE CONSTRUCTION PLANS-TELEPHONE: Answering Device, Automatic Dialer, "Black Boxes" Diverter, Call Limiter, Conference Bridge, Central Dial Exchange, Melodic Ringing, Recorder-Actuator, Remote Control Schematics, Speakerphone, Telelink Burglar Alarm, Voice Scrambler, \$3.00 each, ELECTRONIC Biofeedback Conditioner, Horticulture Stimulator Multifrequency Encoder Network (Speeds telephone calling 100% 1). S5.00 each. DODECAHEDRON Speaker Enclosure \$7.50 Photographic Pinhole Camera \$2.00, ONE YEAR SUBSCRIPTION. Telephone-Electronics Newsline \$3.00 COURSES: Telecommunications. Electronic Protective Systems, F. E. T. Theory and Application, \$24.95 each. Catalog of plans 50 cents All of the construction plans above. \$19.95 TELETRONICS COMPANY OF AMERICA, P.O. Box 3486. Los Angeles, California 90028.

DISCOUNT PRICES

B & K, SENCORE, LEADER and RCA Test Equipment RAYTHEON, ICC/MULLARD Tubes TELEMATIC Test Jigs

Free Catalog FORDHAM RADIO SUPPLY CO., INC. 558 Morris Ave. • Bronx, N.Y. 10451

1/2 INCH VIDEO TAPE \$7.25 per hour on 7" reel. Free information. Oregon Magnetics. Box 13374. Portland. Oregon 97213



AUTHENTIC, INSTRUMENTED, FLYING ROCKETS for casual or serious experimenters. Over 80 scale original, multi-stage or ready-to-fly models. Solid-propellant engines for safe, electric launch system liftoffs up to 2,500 feet. Measure altitude, temp. inversions, more. Real telemetry, electronic tracking, aerial still and movie photography with super-miniaturized equipment. New, detailed tech manual and full-color catalog. 25 cents from ESTES INDUSTRIES Dept. 18B, Penrose, Colo. 81240.

ELECTRONIC Parts wholesale, Catalog 10 cents, Donlyn Electronics, P.O. Box 15421, Phoenix, Arizona 85060.

For faster service

USE ZIP CODE

> on mail

COMPUTER / DATA INPUT KEYBOARD



Honeywell 8 bit biary coded board.56 keys, alphanumeric and computer symbols.. Built in TTL decoder, 13½"x5¾"

STOCK NO.F5119

\$47.50 ea.

2/90.00

Many request for a transformer capable of power ing a 250 watt amplfier, have promted us to locate this beauty. Good for up to 450 watts continuous service. 64 volts ct, @ 6 A., 18 volts ct @ 8 A., 32 volts @ 6 A. and 400 volts @ .150 A. STOCK NO.F9905 11.95 ea. 2/22.00 5/50.00



31/2 DIGIT LIQUID CRYSTAL DISPLAY



This is the Liquid Crystal Display specified in the Jan. POPULAR ELECTRONICS article, "Build This Digital Wrist Watch" Comes complete with socket, and data Comes complete w..... plus reprint of above article. \$19.75 STOCK NO:F5192

DIGIVAC 7 SEGMENT FLUORSCENT READOUT

Tung-Soi DT1704B, 9 pin, electrically similar to G.E. Y4075 Blue-green color. We supply 9 pin socket. 1.2 volts Fil., 25 to 50 volts anode. Makes all digits and 14 letters. STOCK NO.J 5140, with data. \$2.65 ea. 2/5.00, 6/14.00

MINIMUM ORDER \$5.00. Include postage, excess refunded. New edition of our catalog now available



BOX 1, LYNN MASSACHUSETTS 01903

Phone (617) 388-4705

BURGLAR-FIRE alarm supplies and information. Free catalog. Protecto Alarm Sales, Box 357-G, Birch Run, Michigan 48415

FREE CATALOG. IC's, Puts, Transducers, Thermocouples, Led's, Transistors, Circuit Boards, parts, Chanev's, Box 15431, Lakewood, Colo. 80215.

WE SELL MONEY MAKING CONSTRUCTION MANUALS!—Reclaim refined GOLD and SILVER for CONSTRUCTION EXCELLENT full time or part time money!-Color Catalog 25 cents-Airmailed 50 cents. Creative Products, Dept. PE-1074, 8415 Lofland, Houston, Texas 77055.

BUGGED??? New locator finds them fast. Write, Clifton, 11500-L N.W. 7th Avenue, Miami, Florida 33168.

TELEPHONE "BUGGED"? Countermeasures Brochure \$1.00, Negeye, Drawer 547, Pennsboro, W. VA 26415.

HEAR POLICE/FIRE Dispatchers! Catalog shows exclusive directories of "confidentia" channels, receivers. Send 10 cent stamp, Communications, Box 56-PE, Commack, N.Y. 11725

YOU WILL SAVE BIG MONEY! Surplus, Clearouts, Bankruptcy, Inventory, Deals, Catalog \$1 (redeemable), ETCOA Electronics, Box 741, Montreal, H3C 2V2, U.S.

Minimum Order \$3.00

106

IN 414814/\$1.00

Terms: FOB Cambridge Mass. Send check or Money Order Include Postage.

P.O. BOX 74A

CRYSTALS, Scanners, \$3.88, include make and frequency G Enterprises, P.O. Box 461PC, Clearfield, UT 84105.

LOW NOISE RESISTORS-carbon film. Brand new as low as 2-1/4 cents each. Components Center-PE Box 134, N.Y. N.Y. 10038.

FREE CATALOG. Kits, Components, audio equipment. Electronic Supply Pacs, Box 175, Floral Park N.Y. 11001.



IC Manual-Latest Edition-1500 types types/diagram number, \$3.95. 32—function digital computer kit-IC, transistors, instructions, \$14.00. IC applications manual-numerous circuits-Analog/Digital, \$3.95. Electronics, P.O. Box 127. Hopedale, Mass. 01747

ELECTROENCEPHALOPHONE: Brainwave monitor Professional biofeedback intruments. J&J, 8102-E, Bainbridge, WA 98110.

HOBBYISTS-For all your electronic parts requirements at low prices, send for free flyer to: Dartek Electronics, Dept. P. Box 2460. Dartmouth, Nova Scotia, Canada, U.S. In-

LIQUID crystal digital wristwatch display. Includes instructions for building your own. Identical display used in high priced wristwatches. Could also be used in projects requiring 3-1/2-digit display, \$8.95 each, Limited quantity, Tricounty Winslow, Box 5885, Grand Central Station, New York, N.Y. 10017.

CALCULATOR OWNERS: Use Your +-x+ calculator to compute square roots, trigonometric functions, logarithms, and more! Quickly, Accurately, Easily! Send today for the First and Best Calculator Manual . now in use throughstill only \$2.00 Postpaid with Unconout the world ditional Money-Back Guarantee! Mallmann Optics and Electronics, Dept. 20A, 836 South 113. West Allis, Wisconsin 53214

ELECTRONICS Catalog and Diodes: 25 cents (redeemable). BDJ, 33 Howard, Orangeburg, New York 10962

LED digital clock kit. Parts tested complete with case. Lowest price anywhere \$34.85. LEDtronics, Box 357, Neosho, Mo. 64850.

200 MHZ Counter, Drilled Boards. Instructions \$28.50. Free Flyer. Davis Electronics, 6 W. Oakwood, Buffalo. N.Y.

FREE 1975 Electronics Catalog. McCord Electronics, Box 276-N. Sylvania, Ohio 43560.

BUBBLE ETCHER. Etches 6"x8" board in half time. Acrylic construction. Complete photo process instructions. Requires inexpensive aguarium pump. \$12.00. ETCHER, Box 25066, Northgate Station, Seattle, WA 98125

COMPUTE roots trigonometric functions, exponentials, logarithms and more with highest precision on four function calculators. Manual \$1.85. Transmission Lines, Inc., Box 292, Ipswich, MA 01938.

AUTORANGING DMM, deluxe VOM's, logic probes and more. Lowest prices. Free catalog. Electro Industries, 4201 Irving Park, Chicago, Illinois 60641.

ELECTRONIC surplus components for the ham. experimenter. Catalog 10 cents. SASCO Electronics, 1009 King St., Alexandria, VA 22314.

ARE YOU PREPARED? 10,000 cubic foot, pull ring ignited emergency smoke grenades are now available! 3 for \$7.50, 9 for \$20.00. Postpaid. Pacific Aero Supply, Box 601, Malibu, Calif. 90265

DIGITAL/ANALOG PLANS for Home and Lab!!! Send for free 16-page ideas catalog featuring the EXPERIMENTER'S COMPUTER SYSTEM, practical plans, tutorials, etc. M.P. Publishing Co., Box 378-P, Belmont, Massachusetts 02178.

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans. \$2.00. Sanders, Dept. A-33, Box 92102, Houston, Texas 77010.

CONSTRUCTION PLANS: Laser ... \$2.00. Rocket Tracking Transmitter...\$2.00. Space Monitor-Missile Tracker \$2.00, Free Catalog, Electro-Research, P.O. Box 20285, Ferndale, Michigan 48220.

CD IGNITIONS, VHF/UHF monitors, crystals, CB radios, Southland, Box 3591-B, Baytown, Texas 77520.

CMOS Experiments, 20 unusual circuits and useful instruments which can be built from single CMOS digital I.C. Booklet-\$5.00. RJ Electronics, Box 191, Lexington, MI 48450

TELEPHONE TAPPED??? CAR FOLLOWED??? Countermeasure Equipment OFFICE BUGGED??? Catalog \$1.00. Security, Box 671, Westwood, New Jersey

CAPACITORS, AC Oil. Wide variety, whole lot liquidation sale, KSE, 15 Turner, New Bedford, MA 02740.

WHILE THEY LAST!!! CALCULATOR & CLOCK CHIPS by NATIONAL SEMICONDUCTOR

MM5311N 4.75 6-Digit 28-Pin MM5725N 3.50 MM5312N 4.75 4-Digit 24-Pin MM5736N 3.25 MM5314N 4.75 6-Digit 28-Pin MM5738N 3.00 MM5314N 4.25 6-Digit 24-Pin MM5738N 3.00 MM5315N 6.55 4-Digit 40-Pin, Alarm Spec sheets free with order. Send check or money order to C & C Specialists P.O. 80x 7847, Stanford, Ce. 94301

MM5725N 3.50 8-Digit Calculator MM5736N 3.25 6-Digit Calculator MM5738N 3.00 8-Digit Calculator MM5739N 2.95 8-Digit Calculator

ELECTRICAL and ELECTROMAGNETIC Phenomena in the Brain and Human Thinking, 17 p. \$2.50-Short Exposition of Brain's Functioning and Problems. Z.J. Daszewski / own Research Lab., 361 Garretson Ave., Perth Amboy, N.J. 08861.

PYROTECHNICAL chemicals, casings, tools, supplies. fuse. Price List 50 cents. Westech, Logan, Utah 84321.

PRACTICAL Applications of Digital IC's. 100's of tips, circuits, projects, on TTL. 443pp \$19.95. Money Back Guarantee, GEA, P.O. Box 285, Northfield, Ohio 44067.

iquiries.	\$5.95. Electronics, P.O. Box 127, Hopedale, Mass.	01747.	
SLA-37 segment LED readouts .77" numbers. 45 Ma/seg., red or yellow \$5.50 MINIATURE TRIM POTS	TRANSISTOR SPECIALS C/MÖS (DIODE CLAMPED 2N256 PNP GE TO-3 \$.50 2N4004 PNP GE TO-5 4/\$1.00 74C 10 \$.50 2N11378 PNP GE TO-3 \$.95 2N1016A NPN Si TO-82 \$ 1.95 74C 165 \$.50 82 \$.74C 165 83 \$.74C 165	.75 .65	
5K, 10K, 20K, 25K, 50K, 100K, \$.75 3/\$2.00	2N1137B PNP GE T0-3 \$.95 74C 157 \$2 2N1016A NPN Si T0-82 \$.1.95 74C 165 \$3 2N2226 NPN Si T0-82 \$2.50 CD 4001 \$4 MPS3393 NPN Si T0-92 4/\$1.00 CD 4002 \$2 2N3866 NPN Si T0-5 \$.75 CD 4009 \$.65 .65 1.50	
MULTI-TURN TRIM POTS Similar to Bourns 3010 style 3/16" × 5%" × 1¼" 50, 100, 500, 2000, 5000, 10,000 ohms. \$1.50 ea. 3/\$4.00	2N1016A NPN Si TO-82	3.65 3.65 1.60 1.50 2.25 3.65	
PRINTED CIRCUIT BOARD 41/2"×61/2" single sided fiber	2N3638 PNP Si TO-5	1.35 3.65	
glass board, 1/16" thick, unetched \$.40 ea. 5/\$1.75	20V 4.7UF TANT. 5/\$1 LED READOUT \$3.25 20V 4.7UF TANT. 5/\$1 MAN-3 LED PRV 2A 12V 10UF ELECT. 5/\$1 READOUTS \$1,75 200 .95	6A 1.25	
NIXIE TUBES Similar to Raytheon 8650		1.75	
tubes, with socket & data sheet \$2.25 3/\$6.00	1103 1024 bit RAM	.50 LD	
DIODE ARRAYS ARE USED TO READ SEVEN LEVEL TAPE, 100 ma SPACING	8223 - PROGRAMMABLE S316 ALARM CLOCK S12.	50 =	
VERIPAX PC 30ARD This board is a 1/16" single sided paper epoxy board. 4½" x6½" (standard veripax). DRILLED and ETCHED which	193K-0 keyboard manig 5-9.	2513 64 75 CHARACTER GEN \$11.50 2516 64 6 8 STATIC CHARACTER GEN \$11.50 SANKEN AUDIO POWER AMPS SI 1010 Y 10 WATTS \$ 7 95 SI 1025 E 25 WATTS \$18.88 SI 1050 E 50 WATTS \$29.95	
DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with busses for power supply connections. Is also eiched for 22	TTL IC SERIES 74.00—.50 7474—.48 7400—.21 7475—.80 7401—.21 7476—.47 7401—.21 7476—.47	.\$.50 .\$.50 \$1.00	
pin connector \$5.25	7402— 21 7480— 65 7403— 21 7483—1.10 7404— 23 7485—1.50 7405— 22 7486— 48 7406— 43 7499—3.00 7407— 50 7490— 83 7408— 24 7491—1.30 7410— 21 7492— 85 7410— 21 7492— 85	\$1.65 .\$.65 \$1.75 \$1.25 .\$.41 .\$.41	
10 WATT ZENERS 3.9, 4.7 OR 5.6 V	7411 30 7493 85 IM 308 OPER AMP. HERENDIM. LOW POWER S 7412 45 7495 99 301°748 · HI PER OP. Amp. 7413 85 7496 95 536—EET INPUT OPER AMP. \$ 7416 45 74107 50 537—PRECISION OP. AMP. \$ 7417 45 74121 55 IM 3900—OUAD OP. AMP.	\$1.15 .S.41 \$2.90 \$2.50 \$ 63	
Silicon Power Rectifiers PRV 1A 3A 12A 50A 100 .06 .11 .30 .80 200 .07 .16 .35 1.15 400 .09 .20 .50 1.40 600 .11 .25 .70 1.80 800 .15 .35 .90 2.20 000 .20 .45 1.10 2.60	7404 23 7485 1.50 7406 43 7489 3.00 7407 50 7490 83 7408 24 7491 1.30 7410 21 7492 85 7411 30 7493 85 7412 45 7495 99 7413 85 7496 95 7416 45 74107 50 7417 45 74121 55 7417 45 74121 55 7417 45 74121 55 7412 30 74125 1.40 7426 30 74125 1.40 7427 55 74150 1.15 7430 30 74125 1.40 7427 55 74150 1.50 7438 50 74157 1.25 7438 50 74157 1.25 7438 50 74157 1.25 7430 24 74151 95 7432 30 74154 1.65 7438 50 74157 1.25 7440 1.10 74165 2.35 7441 1.00 74165 2.35 7445 1.10 74173 1.80 7446 1.25 74177 1.80 1 382 DUAL AUDIO PERAMP 1 382 DUAL AUDIO PERAMP 1 382 DUAL AUDIO PERAMP 1 383 STEREO PERAMP 1 370 AGG SQUELCH AMP 1 382 DUAL AUDIO PREAMP 1 384 DUAL AUDIO PREAMP 1 385 DA	\$2.20 \$2.95 \$2.95 \$2.95 \$2.95 \$2.95 \$3.95 \$1.15 \$1.20 \$1.20	
REGULATED MODULAR POWER SUPPLIES +-15VDC AT 100 ma, 115VAC INPUT	7448—1.25 74192—1 50 7450— .24 74193—1.45 7451— .30 74195—1.00 7472— .40 75491—1.10 13407—5 12.15 18 or 24 VOLT TO	\$1.50	
151 41 40	7473 48 220 PUS REG		

SOLID STATE SALES

Similar to 8038C IC Voltage con

trolled oscillator, as featured in Oct. 73 P.E. they have sine, square and triangular outputs good to IMHz. Two of them can be used to

Send 20c for our catalog featuring Transistors and Rectifiers; 325 Elm St., Cambridge, Mass

make an FM generator...\$5.95

RELIABLE

EAST COAST SEMICONDUCTOR

PRODUCTS

SCR'S

1.5A 6A .40 .50

200 used to 400 1.10 1.60 2.60 5.95 600 1.70 2.30 3.00

TRIACS

ALPHA THETA BRAINWAVE biofeedback instruments. Analog instruments from \$125, digital processing systems from \$225. BioScan. Box 14168-E, Houston, Texas 77021

SURPRISE! Build inexpensively, the most Unusual Test Instruments. Futuristic Gadgets using Numerical Readouts! Catalogue Free! GBS, Box 100A, Green Bank West Virginia 24944

ELECTRONIC ORGAN KITS. KEYBOARDS and many components Independent and divider tone generators. All diode keying. I.C. circuitry. Supplement your Artisan Organ. 35 cents for catalog. DEVTRONIX ORGAN PRODUCTS. Dept. C. 5872 Amapola Dr. San Jose Calif. 95129.

ELECTRONIC IGNITION Capacitor transistor, pointless Auburn sparkplugs Information 10 cents Anderson Engineering, Epsom. N H 03234

LASER DIODE, 6W GaAs \$10.25, Liquid Xtal 3.1.2 digit. 4 \$9.75.8038 VCO \$5.95, 1101 \$1.95, INTEL 1103 \$3.00, 8223 ROM \$4.95, CATALOG 10 cents, ELECTRONIC DISCOUNT SALES, 138 N 81st St., Mesa, Arizona 85207

WHOLESALE Scanners. CB, Crystals. Directories. SSB/AM, Catalog 25 cents G—Enterprises. Box 461P. Clearfield. Utah 84105

PRACTICAL Applications of Digital IC s 100 s of tips, circuits, projects, on TTL 443 pp \$19.95 Money Back Guarantee, GEA, P.O. Box 285, Northfield, Ohio 44067

PLANS AND KITS

TRIGGER SWEEP GENERATOR—improve your low cost scope by adding solid state trigger sweep. Complete kit. \$20.00 PPD Information Free. PHOTOLUME CORPORATION, PO Box 139, New York, N.Y. 10016

"CRYSTAL Set Handbook"—50 cents. Catalog 25 cents Refundable. Laboratories. 1477-L. Garden Grove. Calif 92642.

COMPUTERS you can build one, large or small Construction manual \$3.00 Digitronics, 667 East 1700 South, Orem. Utah 84057

AUTOMATIC TELEPHONE RECORDER SWITCH (includes audio patch) Complete construction manual \$2.00. TELTEC, Box 16103, Memphis, Tenn. 38116.

SAVE GAS Professionally maintain your car. Use ignition analyzer adapter with your oscilloscope. Complete instructions and diagnostic manual \$5.00. Assembled unit \$19.95. JJ Industries. Box 62. Stamford. Conn. 06904.

PLANS, heat, power from 20,000 watt windmill or solar panels \$9.00 each. DanRan, Box D, Reno, Nevada 89506.



HIGH FIDELITY

DIAMOND NEEDLES and Stereo Cartridges at Discount prices for Shure. Pickering, Stanton, Empire. Grado and ADC Send for free catalog, LYLE CARTRIDGES. Dept P. Box 69, Kensington Station, Brooklyn, New York 11218.

KITS¹ LOUDSPEAKERS, CABINETS, AMPLIFIER, Featuring genuine walnut, heavy gauge chassis, top quality components and engineering at factory sawings Pride and performance combined. Ruxton, Dept P1, PO Box 30312, Santa Barbara, CA 93105

WANTED

QUICKSILVER, Platinum, Silver, Gold, Ores Analyzed Free Circular Mercury Terminal, Norwood, Mass 02062 HAMMERLUND model HQ-180AC, 1970 Write Simpson 2417 So Wilcox, Monterey Park, CA 91754

TUBES

RADIO & T V Tubes—36 cents each Send for free Catalog Cornell, 4213 University, San Diego, Calif 92105 RECEIVING & INDUSTRIAL TUBES, TRANSISTORS All Brands Biggest Discounts Technicians. Hobbyists Experimenters — Request FREE Giant Catalog and SAVE' ZALYTRON, 469 Jericho Turnpike, Mineola, N Y 11501 TUEs receiving, factory boxed, low prices, free price list Transleteronic, Inc., 1306 40th Street, Brooklyn N Y 11218A, Telephone 212-633-2800

"TUBES ANTIQUE Send your want list PO Box 5570 Compton, Calif 90224

TUBES "Oldies". latest. Lists free. Steinmetz, 7519 Maplewood, Hammond, Indiana 46324

TUBES 60% OFF LIST PRICE. McCord Electronics. Box 276-T. Sylvania. Ohio 43560.

CASH PAID FOR OBSOLETE RECEIVING TUBES WE300B. WE300A. WE350B. WE252A. WE274A/B. WE284D. RCA45 RCA50. Small and large quantities, and movie theatre equipment, amplifier WE86A. WE59A. WE30A. WE91A B, pick-up WE9A. WE10A. etc. Contact M Takabe. 303 Fifth Ave. N Y C 10016. Tel (212) 679-1970

MOVIE FILMS

8MM-SUPER 8-16MM MOVIES' Biggest Selection' Lowest Prices' Free Catalog' Cinema Eight, Box PE, Chester Connecticut 06412

ELECTRICAL SUPPLIES & EQUIPMENT

PLATING Equipment. Portable Platers. Supplies and 'Know-How Build your own tanks for nickel, chrome, etc Easy-to-install PVC liners Rectifier components all sizes. Schematics, parts lists, formulas, operating instructions for all plating Guaranteed to save you 25°c-75°c. Some good units for sale Write for details Platers Service Company, 1511-PE Esperanza, Los Angeles, Calif 90023.

TAPE AND RECORDERS

RENT 4-Track open reel tapes—all major labels—3,000 different—free brochure Stereo-Parti, 55 St. James Drive. Santa Rosa, Ca. 95401.

1930-1962 Radio Programs. Reels. \$1.00 Hour! Cassettes. \$2.00 Hour! Mammoth Catalog, \$1.25. AM Treasures. Box 192F, Babylon, N.Y. 11702.

CASSETTE L	.A	E	BEL	S	
Plain white cassette labels. Norelco cassette cleaners.	paper	m	ailer bixes	hold No	relca
type plastic box, famous brand cassettes "Like new	10 1/2	2	metal or fi	beiglass	reels
Send for open reel and cassette discount catalog	- 1	-9	10-99	100	1000
Cassette Labels (Multiples of 10)			02	015	01
Norelco Cassette Cleaner		65	60	55	50
Cassette Paper Mailer Boxes		03	025	022	
Scotch Cassette SC90HE, Buy 2 get ONE FREE	2	72	2 55	2 44	2 39
10-1/2" Fiberglass Reels, Used		50	50	40	35
80 1/2" Metal, NAB Hole Used	1	00	1.00	90	80
Plus Postage by Weight and Zone			Minimum	Order,	\$5 00
SAXITONE TAPE SALES			OLUMBIA I		

GOVERNMENT SURPLUS

GOVERNMENT Surplus. How and Where to Buy in Your Area. Send \$2.00. Surplus Information, Headquarters Bldg... Box 30177-PE, Washington, D.C. 20014.

ELECTRONIC Equipment and Parts. Big 36 page Free Catalog. Send for your copy today! Fair Radio Sales. Box 1105-P. Lima. Ohio 45802.

MANUALS for Govt Surplus radios, test sets, scopes List 50 cents (coin). Books, 7218 Roanne Drive, Washington, D.C. 20021.

PERSONALS

MAKE FRIENDS WORLDWIDE through international correspondence. Illustrated brochure free. Hermes. Berlin 11. Germany.

INVENTIONS WANTED

CASH-ROYALTIES for patented unpatented inventions Global Marketing Service. 2354-P Telegraph. Oakland. California 94612

INVENTORS Protect your ideas! Free "Recommended Procedure" Washington Inventors Service, 422T Washington Building, Washington, D.C. 20005.

PATENT Searches including Maximum speed, full airmail report and closest patent copies. Quality searches expertly administered with complete secrecy guaranteed. Free Invention Protection form and "Patent Information." Write Dept. 910. Washington Patent Office Search Bureau. Benjamin Franklin Substation. P.O. Box 7167, Washington. D.C. 20044.

YOUR INVENTION—IDEA PRODUCT—WANTED NOW Your invention properly developed, searched and prepared for outright sale or cash/royalty. U.S and overseas manufacturers are in touch with us looking for new products to market Your invention may be patented or unpatented. Our staff includes Graduate Engineer and Patent Engineers who are ready to develope and market your invention. The Gilbert Adams Organization. Dept. 20K-1, 80 Wall Street, New York N.Y 10005.

LEDS

TTI

MV5024 Red To-18 High Dome @ 2V 5 for \$1.00 MV50 Red Emitting 10-40 MA @ 2V 6 for \$1.00 MAN 3 type Seven-Segment Readout-\$1.45ea 3 or more\$1.00ea MAN 4 type Seven-Segment Dip \$-\$2.25ea 3 or more\$2.00ea

		- 1	II.				_
<u> </u>						, смо	_
7400	\$.23		\$.27	74157		CD4001	S .60
7401	.23	7454	.40	74160	1.65	CD4002	.60
7402	.23	7459	.25	74161	1.65	CD4009	1.40
7403	.23	7460	.25	74163	2.50	CD4010	.60
7404	.25	7470	.45	74164	2.50	CD4011	.60
7405	.24	7472	.41	74165	2.50	CD4012	.60
7406	.50	7473	.47	74166	1.75	CD4013	1.50
7407	.50	7474	.47	74170	3.00	CD4016	1.40
7408	.25	7475	.90	74173	1.75	CD4023	.60
7409	.25	7476	.47	74174	1.85	CD4025	.60
7410	.23	7480	.50	74175	1.85	CD4027	1.25
7411	.30	7482	1.75	74176	.85	CD4030	.60
7413	.89	7483	1.15	74177	.85	74C00	.65
7416	.45	7485	1.10	74180	1.05	74C04	.70
7417	.45	7486	.47	74181	3.75	74C20	.65
7418	.25	7488	4.00	74182	1.00	74C173	2.60
7420	.23	7489	3.00	74 184	2.30	8000 S	eries
7421 7423	.27	7490 7491	.89 1.15	74185 74187	2.30	8090	\$.35
7425	.32	7491	.95	74190	1.50	8091	.55
7425	.31	7493	.95	74191	1.50	8092	.55
7427	.32	7494	.97	74192	1.50	8093	.55
7429	.40	7495	.95	74193	1.50	8094	.55
7430	.33	7496	.95	74194	1.50	8095	.55
7432	.26	74100	1.50	74195	1.05	8096	.55
7437	.45	74107	.47	74196	1.25	8097	,55
7438	.50	74121	.55	74197	1.05	8098	.55
7439	.50	74122	.47	74198	2.25	8121	.90
7440	.23	74123	1.05	74199	2.75	8123	1.60
7441	1.10	74125	.60	74200	7.00	8130	2.25
7442	1.05	74126	.80			8200	2.70
7443	1.10	74141	1.15	AL:	50	8210	3.25
7444	1.15	74145	1.15	AVAIL	ARIF	8220	1.60
7445	1.10	74150	.95	74H Se		8223	5.00
7446	1.25	74151	1.20	745 Se		8280	.75
7447	1.25	74153	1.50		ries tries	8288	.90
7448	1.25	74154	1.25	Many C		8836	.60
7450		74155 74156	1.30	8000 S		8837	1.50
7451	.27	/4156	1.30	1 0000 31	ciica	8880	1.35
20%	Direct	nt for 10	n Dincor	Combine	d _ Ab	7400 9	ariar

20% Discount for 100 Pieces Combined - Above 7400 Series

OCTOBER \$PECIAL\$ OCTOBER

ı			
ı	7400-7401-7403	GATES5 fo	
ı	7404-7410-7420	GATES5 fo	
ı	MC836P-MC846P	DTL4 fo	
ı	MC862P-MC863P	DTL4 fo	
ı	IN4148 Silicon Signal	Switching Diade 15 fo	r \$1.00ea
ı	Tis 97-Tis 98 NPN	Transistur ——————— 10 fo	r \$1.00ea
ı	LM301H/LM301N	AMP 3 fo	r \$1.00ea
ı	LM741CH/LM741CN	OP AMP 3 fo	
ı	LM380N	2 Watt Audio AMP	\$1.25ea
ı	LM3900N	Quad AMP DIP	S .55ea
ı	LM311H/LM311N	Comparators	\$1.00ea
ı	LM309K	5V 1 AMP	\$1.25ea
ı	NESSS _ NESSS _ N	ES67 PHASE LOCK LOOPS	\$2 Office

LINEAR

	LM300 LM301H/N	Pos. V Reg To 5 Improved Op Amp	\$.85
	LM302H	Voltage Follower	.85
	LM304H	Negative Voltage Regulator	1.10
	LM305H	Positive Voltage Regulator	1.00
1	LM307H/N	Op Amp (Super 741)	.40
	LM308H/N	Micro Power Op Amp	1.15
	LM309K	5 Volt Regulator / Amp	1.70
1	LM310H	Improved Volt, Follwer Op Amp	1.35
	LM311H/N	Hi-performance Volt, Comp.	1,15
1	LM319H	Hi-Speed Dual Comp.	1.55
ı	LM320K-5V-15	/ - Ta 3 Neg. Regulator	1.75
	LM324N	Quad 741 Op Amp	1.90
ì	LM339	Quad Comparator	2.35
ł		V-15V-24 Positive Valt Regulator	2.00
	LM370N	A 6 C - Squelch Amp.	1.55
	LM373N	AM/FM \$\$ B Strip	3.30
	LM350N	Dual Feripheral Driver	1.00
	LM351N	Dual Feripheral Driver (75453)	.65
	LM380N	2 Watt Audio Power Amp	1.50
	LM703H	RF/IF Amp	.45
	LM733H	Video Amp	1,00
	LM5558V	Dual Op Amp	1.00
	LM741H/N LM747H/N	Comp. Op Amp	.40
		Dual Compen. Op Amp	
	LM748N LM1458N	Freq. Adj. 741	.40
	LM1456N	Dual Comp. Op Amp T.VFM Sound System	.65
	LM3900N	Quad Amp	.75
	LM555N	Timer	1.00
	LM565-LM566-		2.50ea
	LM75451	Dual Peripheral Driver	.49
ł	LM75452	Dual Peripheral Driver	.49
	LM75453	Dual (LM351)	.65
	Satisfac	tion Guaranteed. All Items 100% Tested	

Satisfaction Guaranteed. All Items 100% Tested \$5.00 Min. Order — 1st Class Mail — No Extra Charge California Residents — Add 6% Sales Tax Wholesale Out ets — Write for Special Discounts Write for FREE Catalog — Oata Sheets .20 & each



P. O. Box 822 - Belmont, Ca. 94002

PHONE ORDERS WELCOME

(415) 592-8097
CIRCLE NO. 22 ON READERS SERVICE CARD

380-381 382 560 566 566 567 703 709 710 711 723 741 1 50 1 00 2 50 2 50 2 50 40 30 30 30 60 40 80 .75 1.00 1.50 .75 .70 .80 747 748 1303 1304 1305 1307 1458 3065 3075 128 70 132 3.00 141 150 144 1550 145 125 151 1 00 153 1.00 153 1.00 153 1.00 154 1.00 157 1.00 157 1.00 157 1.00 157 1.00 157 1.00 157 1.00 151 1.50 151 1.50 48 50 61 61 65 63 64 64 65 66 60 66 66 66 66 67 67 71 67 71 67 71 H72 73 H73 L73 74 H74 L74 F75 F76 H76 B3 83 85 L86 S B8 B8 B8 163 164 1166 105 105 105 105 173 174 173 174 175 177 177 180 181 182 948 949 967 968 961 962 963 9094 9097 9099 9230 9233 9235 9236 9236 937 944 945 Of bit RAM 256 bit blooker Fleid PROM 66 bit RAM To Sorte 256 bit RAM To Sorte 66 bit RAM 1024 bit state RAM

CIRCLE NO. 40 ON READERS SERVICE CARD

KE 10(N)% DISCOUNT ON ORDER OF OVER 10 S.

\$.43

.75 .47 1.11 .44 2.75

.76 1.29 .79 .79 .89 .89

.57

.69 .79 1.23 1.15 1.09

.89 1.29 1.59 1.39 1.59 1.89 1.65 1.65

.99

3.65 .89 1.59 1.39

.99 2.19

7475 7476 7483

7490

7492

74150 74151

74153

74154

74198

74199

301

340T

381

555

3900

\$.19

.19 .22 .29 .39 .25 .25 .19 .39 .39 .39 .39 .39 .29 .45 .39 .109 .99 .99 .99 .99

.24 .27 .39 .19 .39

.36

7401 7402

7400

7420

7440

7447 7448

7450

7454

7460 7464 7465

FREE PAMPHLET: "Tips on Safeguarding Your Invention. Write: United States Inventors Service Company, 708-T Carry Building, Washington, D.C. 20005.

FILE your own patent application. Complete information and materials. Write: Inventor's Guide, 468-R. Goodspeed Road, Virginia Beach, Virginia 23451

...Manufacturers Need

If you have an idea for a new product, or a way to make an old product better, contact us, "the idea people." We'll develop your idea, introduce it to industry, negotiate for cash sale or licensing.

Send for our FREE "Invention Kit." It has a special "Invention Record Form," an important

New Products

brochure, "Your Invention — Its Development, Pro-tection & Marketing," and a Directory of 500 Corporations Seeking New Products. You'll learn how ideas become a reality!

INTERNATIONAL ELECTRONICS UNLIMITED

mDIF

mDIP mDIP TO-3

mOIP DIP

DIP

DIP

DIF mDIP DIP

DIP

mDIP DIP DIP OIP

mDIP

mDIP mDIP

DIP

DIP mDIP mDIP

mDIP

DIP DIP

DIP

TO-220

.35 1.10 1.65

1.05

1.29

1 95

.89

1.79 .79 .99 2.75 2.65 .29

.35 .79

69

.65 .65 5.95 .39 .39 .39

LINEAR CIRCUITS

Hi perf. op amp

Op amp Micro-pwr op amp 5V reg 1A Hi perf. V comp

Hi-speed dual comp

Quad op amp Quad comp Pos V reg (5V, 6V, 8V 12V, 15V, 18V, 24V) 2w audio amp

Lo noise dual preamo

Prec. V reg
Timer
Phase locked loop
Phase locked loop
Op amp
Volt reg.

Volt reg.
Comp. op amp
Dual 741
Freq adj 741
Dual Comp op amp
Quad amp
Prec. timer
Function gen.
Dual prl. driver
Dual prl. driver
Dual prl. driver
Dual grl. driver

Quad seg driver

5001 LSI 40 pin DIP 4 funct

DATA SUPPLIED ON REQUEST WITH ORDER. ADD \$.50 PER DATA FOR ITEMS PRICED UNDER \$1.00

CALCULATOR & CLOCK CHIPS w/data

5001 LSI 40 pin DIP 4 funct S 5002 LSI Same as 5001 exx batt pwr 5005 LSI 28 pin DIP 4 funct w/mem MM 5311 28 pin BCD 6 dig mux MM 5312 24 pin 1 pps BCD 4 dig mux MM 5313 28 pin 1 pps BCD 6 dig mux MM 5313 28 pin 6 dig mux MM 5314 24 pin 6 dig mux

75492 Hex dig. drive

(408) 659-4773

.6w audio amp

RAYMOND LEE ORGANIZATION

230 Park Avenue, New York, N.Y. 10017 I'd like to find out how to take action on my idea. Send Free "Invention Kit No. A-112"

Please Print Cit State CANCISCO LOS ANGELES TORONTO VANCOUVER DENVER CHICAGO

INVENTORS! FREE BROCHURE LISTING CORPORATIONS which may be interested in your invention. Many well-known manufacturers have engaged us to locate new products. For Free brochure and information regarding the promotion of your invention. contact: Gilbert Adams Organization, Dept. 20K, 80 Wall Street New York, New York 10005.

INVENTORS! Don't sell or license your invention until you receive our offer, Eagle Development Company, Dept. P. 10, 82 Wall Street, New York City 10005

LOGIC PROBE KIT

- Ten nano/sec capability Checks TTL & DTL logic
- Dual slope memory Internal 5V regulator

POWER SUPPLY SPLITTER KIT

MEMORIES

1101 1103	256 bit RAM MOS 1024 bit RAM MOS	\$1.75 4.95 3.95
5260 7489 8223	1024 bit RAM low power 64 bit RAM TTL Programmable ROM	2.75 4.95

LED'S AND OPTO ISOLATORS

IVIV TUB	Hed 10 18	⇒ .∠5 e
MV50	Axial leads	.20
MV5020	Jumbo visible red	.33
ME4	Infra red diff. dome	.60
MAN1	Red 7 seg270"	2.50
MAN2	Red alpha num .32"	4.95
MAN3A	Red 7 seg127"	.79
MAN3M	Red 7 seg127" claw	1.15
MAN4	Red 7 seg190"	2.15
MAN5	Green 7 seg270"	2.95
MAN7	Red 7 seg270"	1.35
MAN8	Yellow 7 seg270"	3.95
MAN66	60" high dir. view	4.65
DL707	Red 7 seg3"	2.15
MCD2	Opto-iso diodes	1.09
MCT2	Opto-iso transistor	.69

4000 SERIES RCA-EQUIV

DATA SUPPLIED ON REQUEST WITH ORDER. AOD \$.50 PEP DATA FOR ITEMS PRICED UNDER \$1.00

CD4001	S .55	CD4017	2.95
CD4009	.85	CD4019	1.35
CD4010	.85	CD4022	2.75
CD4011	.55	CD4023	.55
CD4012	.55	CD4025	.55
CD4013	1.20	CD4027	1.35
CD4016	1.25	CD4035	2.85

ON ORDERS OVER \$25.00 DEDUCT 10%

8.95 8.45

6.95 7.95

All items are new, unused surplus parts — tested functional. Satisfaction is guaranteed. Shipment will be made via first class mail — postage paid — in U.S., Ganada and Mexico within three days from receipt of order. Minimum order — \$5.00. California residents add sales tax

INTERNATIONAL ELECTRONICS UNLIMITED P.O. BOX 1708 MONTEREY, CALIF. 93940 USA

CIRCLE NO. 21 ON READERS SERVICE CARD

INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING at home att makes including transistor. Experimental kit—trouble-shooting. Accredited NHSC, Free Booklet, NILES BRYANT SCHOOL, 3631 Stockton, Dept. A, Sacramento, Calif. 95820

LEARN WHILE ASLEEP, Hypnotize! Strange catalog free. Auto-suggestion, Box 24-ZD, Olympia, Washington 98501 DEGREE IN ELECTRONICS through correspondence. Free catalog. Grantham. 2000 Stoner Avenue. Los Angeles. California 90025.

INTENSIVE 5 week course for Broadcast Engineers. F.C.C. First Class license. Radic Engineering Incorporated, 52 S. Palm Ave., Sarasota, Florida 33577

SHORTCUTS To Success! Highly Effective. Profitable Short Courses (75 Choices). Study At Home. Diploma Awarded. Our 29th Year. Free Literture. CIEE-D, Box 20345, Jackson, Miss. 39209.

DIGITAL:THEORY,DESIGN ,

LOGIC NEWSLETTER ©

SAMPLE COPY \$ 1.00 LOGIC NEWSLETTER POB 252 WALDWICK, N.J. 07463

DEGREE Program in Electronics Engineering. Our 29th Year! Free literature. Cook's Institute, Dept. 13, Box 20345. Jackson, Miss. 39209



SCORE high on F.C.C Exams Over 300 questions and answers. Covers 3rd, 2nd, 1st and even Radar, Third and Second Test, \$14.50; First Class Test, \$15.00, All tests. \$26.50 R.E.I., Inc., Box 806, Sarasota, Fla. 33577

SELE-STUDY OR RADIO REPAIR COURSE THERE'S MONEY TO BE MADE REPAIRING CB RADIOS. This easyto-learn course can prepare you for a career in electronics enabling you to earn as much as \$16.00 an hour in your spare time. For more information write: CB Radio Repair Course, Dept. PE-10, 531 N. Ann Arbor, Oklahoma City, Okla. 73127.

LEARN design techniques. Electronics Monthly Newsletter. Digital. linear construction projects, design theory and procedures. Sample copy \$1.00. Valley West. Box 2119-B. Sunnyvale. Catifornia 94087.

FCC LICENSE through tape recorded lessons. Also Radar Endorsement, Radio License Training, 1060D Duncan, Manhattan Beach, Calif. 90266

C.E.T. Practice Exams. Associate and Journeyman level \$10.00. Options \$5.00. P.O. Box 30103. Lincoln. Nebraska 68503.

DESIGN Transistor Circuits Using Only Arithmetic! BJT UJT, FET \$3. Stewart, 601 Chestnut, Union, N.J. 07083.

MUSICAL INSTRUMENTS

30% DISCOUNT name brand musical instruments. Free Catalog, Freeport Music, 455N, Route 110, Melville, N.Y

WHOLESALE! Professional Guitars. PA Systems. Altec Speakers, 240W RMS Amplifiers, Free Catalog, Carvin. Escondido, Calif. 92028.

30% + DISCOUNT. Name Brand Musical Instruments. Free Catalog. Continental Music. Dept. H. P.O. Box 3001 Garden City, New York 11530.

MAGAZINES

MAGAZINE SUBSCRIPTIONS at lowest prices available anywhere, Magazine House, Box 390E, Millwood, N.Y.

EMPLOYMENT OPPORTUNITIES

ELECTRONICS/AVIONICS EMPLOYMENT OPPORTUN-ITIES. Report on jobs now open. Details FREE. Aviation Employment Information Service, Box 4240E, Northport, New York 11768

8-TRACK PROFESSIONAL TAPE TRANSPORT

Same type unit found in the most expensive home tape players. It's a complete 8-track player system with BUILT-IN PREAMP—just plug into any stereo amplifier (see some of our low-priced units). Excellent replacement unit, or you can design your own high-quality stereo tape system. It's the type you insert a cartridge to turn-on deck, then enjoy up to 80 minutes of non-stop, non-repeat stereo. Remove cartridge and player "shuts off" automatically. Built-in output controls in preump. Peatures: 4 PROGRAM INDICATOR LIGHTS. automatic or manual program change, plays your car tapes at home. WOW-FREE precision fancooled motor, which operates off 1157uc. Requires external 12Vdc supply, for the electronics. With diagrams. WATT STEREO

AUDIO AMP



□ Only

\$19.95

8-Watt Stereo Amplifier, 8-Track Tape Transport

and hook-ups both.

20-WATT STEREO AM-FM-MULTIPLEX 20-watt Solid State Amplifier!
 All Solid State, Printed Circuitry WITH GLASS
 Side Rule Dia!
 All Purpose, All Family System! ESCUTCHEON

* Silde Rule Dial
* All Purpose, All Family System!

The most unusual HI-FI stereo buy of 1974. A unit that has so many unique and different functions, makes it the finest system of its kind at the usual Poly Pak economy price and property of the finest system of its kind at the usual Pyrak economy prices are panel. Another external panel of player in the finest provided and provided the property of provisions are panel. Another external panel of provided the property of provided the property of provided the provided that the provided the provided that the provide


60-WATT AM-FM-MULTIPLEX Same as above except amplifier heavy-duty stereo 60 watt unit. \$59.95


□\$59.95

2 for \$19.95

The factory "snipped" most of the cables to this compact 8 watt stereo unit with aluminum escutcheon plate. It's easy to use because we have all the cables' marked ready to use. With power supply. 115 vac. 3 controls, LEPT and RIGHT VOLUME controls for two speakers for balancing and center TONE control. With knobs. 7 x 3½ x 3½. Hookup spee sheets. 7. SEGMENT I FO Readoute

				Culti	16463	10
(AI	I "LEC	" TYI	PES)	MAN-1		The state of
Type MAN-1 MAN-3 MAN-4	Char. .27 .12 .19	Each \$3.75 1.49 2.50	Special 3 for \$9. 3 for \$3. 3 for \$6.	MILIT	Par Service	SLA
REFLE	CTIVE	BAR	TYPES	MA	MAN-3	150
SLA-1**	.33	2.10 4.95	3 for \$5. 3 for \$13	- di	4 SLA-3	coa, equal to

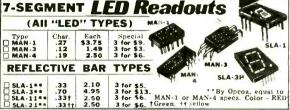

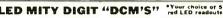

Scientific Devices "Digital Counting Modules" outperform any other DCM on the market today. More features than ever before! Not gaseous, not incandescents, not mixie but the modern LED. Choose from such famous manufacturers as Monsanto's MAN-1, MAN-4, Litronics 707 and 704, Opcoa's SLA-1 (the last 4 having character highst of 0.33 at no extra charge). Each kit includes 3x2" p.c board with fingers for a FREE edge connector, side-mounting dip socket, LED readout of your choice, resistors, 3 IC's, and Molex connectors MAN-4. 19h. Monsanto (this ELIMINATES SOLDENING YOUR IC's) and 5124. 133 h. Opcoa" Pin-for-pin MAN-1. "Pin-for-pin MAN-4 elec characteristics."



SANKEN HYBRID

| Since | Since

CLOCK CHIPS as Low as ON A "DIP" \$7.77 BLUE RIBBON MMS311 6-digit 28-Pin \$7.77 MMS312 4-digit 24-Pin 7.77 MMS313 6-digit 28-Pin 7.77 MMS314 6-digit 24-Pin 7.77 MMS316 4-digit 40-Pin, Alarm WITH DATA SHEETS

BRAND NEW LOWEST PRICES
GENERAL ELECTRIC 3-WATT \$2.50
AUDIO AMP
3 FOR 3-0.0 \$2.50
Pelivers 3.5 watts continuous. 10 watts peak. With
eat sinks: micro-mini size: 3/x/3/x/2/3 to 30V supily. High sensitivity. 8 to 16 ohm.

INCLUDE Years of Business INTEGRITY

Policy

20-Years of Money-Back **GUARANTEES** LOWEST PRICES:

48-HR. SERVICE

6-8-12 DIGIT Your Choice \$16.95 Calculator Basics

BASIC KIT #1 — includes case, all-function flex Key Keyboard, Cal Tech CT5002 calculator chip, 9-digit Antex LED display with built-on individual magnifiers.

BASIC KIT #2 — same as Basic #1 except calculator chip is National 8-digit MM5725.

BASIC KIT #3 — same as Basic #1 except calculator chip is National 6-digit MM5736 and 75492.

12 DIGIT BASIC #4 — Key parts include: CT5001 chip, 4-3 digit readouts, factory etched PC board, case, carrying case, 2-resistor networks, decimal switch. Wild Rover Keyboard with ON-OFT switch diagrams. Sale \$24.95

12° DIGIT BASIC "MEMORY" KIT #5 — Key parts for 4-memory calculator. Case with "slight touch keyboard", CT5005 memory chip, 6 MAN 3's, ON-OFF switch, book, (*extend key allows 12 digits), pc boards), \$19.95

WRIST WATCH

*3-1/2 digit. 7 segment *Only 1-1/16 x 11/16 x 1/4"

*Only 1-1/16 x 11/16 x 1/4"

See POPULAR ELECTRONICS (Jan. 1974) for building your own electronic digital wristwatch using the Liquid Crystal Display (LCD) as its basic. Easy to see, 3½ digit display, requires less than 1/1000 of power as LED'S. Visibility na ceases with ambient light. Difficult reading of LED'S of light. Pulsates SECONDS in center of display, NO NEED OF TRANSISTOR RESISTOR interface, as LED'S, thus smaller package. Chip contains holder, tiny connecting terminals, and "slide-in-place chrome spring face pite". Size of display in holder: 1/1/16 x 11/16 x 1/4". Operating freq. 32 hertz. 45-microwatts of power. Operating freq. 32 hertz. 46-microwatts of power. Operating freq. 32 hertz. 46-microwatts of power. Operating freq. 32 hertz. 48-microwatts of power operating freq. 32 hertz.



NATIONAL Buy any 3 — Take 10%
LINEAR OP AMPS (A) TO-5, Dip
LM-300 POS V.R. (super 723) TO-5 \$.81
LM-301 Hi-performance op amp (A) 39 LM-302 Voltage follower TO-5 81
LM-302 Voltage follower TO-5
LM-304 Neg. volt. Reg. TO-5 1.15
LM-305 Pos. Voltage Reg. TO-595
LM-307 Super 741 op amp (A)
LM-308 Hi-Q fet type op amp TO-5 1.09
LM-309H 5V Volt-Regulator TO-5 1.05
LM-309K 5V VoltReg. 1 Amp TO-3 1.65
LM-310 Voltage-Follower TO-5 1.25
LM-311 Hi-perf. Volt. Comp. (A) 1.09
I M 210 Dear Mt Court DID

	Ħ	LM-308 Hi-Q fet type op amp TO-5 1	.33
	ŏ	LM-309H 5V Volt-Regulator TO 5	0.5
		LM-309K 5V VoltReg. 1 Amp TO-3 1 LM-310 Voltage-Follower TO-5 1	65
	Ō.	LM-310 Voltage-Follower TO-5	25
	$\overline{\Box}$	LM-311 Hi-perf. Volt. Comp. (A) 1	09
	Ē	LM-318 Prec. HI-Speed DIP	96
	8	LM-319 HI-speed Duat Comp. DIP 1	50
	ř	LM.320 MINUS 5 12 or 24V V D TO 2 1	-0
	Ħ	LM-322 Prec. Timer	75
	Ħ	LM-324 Quad (4-741's in DIP) 2	19
	ã	LM-322 Prec. Timer 1 LM-324 Quad (4-741's in DIP) 2 LM-339 Quad Comparator. DIP 1	.75
	Ħ		
		15, 18. 24V 2	95
1	П	LM-350 Dual Peripheral Driver DIP	69
1	ŭ	LM-370 AGC Squeich op amp, TO-5 1	50
		LM-371 R-F. I-F on amp	25
	ř	LM-371 R-F, I-F, op amp	50
	H	LM-374 AM-FM SS IVAD TO-5 3	50
	Ħ	LM-376 Pos. V. Reg	65
	嵩	LM-376 Pos. V. Reg	69
	Ħ	LM-380 600mW LM-380, mini DIP 1	69
	Ħ	LM-380 600mW LM-380, mini DIP 1 LM-381 Low noise dual pre amp DIP 1 LM-382 Low noise dual pre amp DIP 1	.69
	Ħ	LM-382 Low noise dual pre amp DIP 1	.89
	Ħ.	LM-703 RF-IF amp. TO-5	.59
		LM-703 RF-IF amp, TO-5	.51
	ñ	LM-709 Operational amplifier (A)	.36
	ă	LM-710 Differential amplifier (A)	.45
	Ĭ	LM-711 Dual Differential Amp (A)	
	ñ	LM-723 Voltage Regulator (A)	.69
	ñ	LM-72S Instrument Op Amp	.69
	8	LM-733 Differential Video	.75
		LM-741 Freq. Comp. 709 (A) LM-741CV Mini DIP 741C	.41
	$\overline{\Box}$	LM-741CV Mini DIP 741C	.41
	$\overline{\Box}$	LM-747 Dual 741 (A)	.89
		LM-748 Freq. adjustable 741C (A)	.41
		LM-1303 Stereo pre amp DIP	-91
	Ò	LM-1304 FM Stereo Multiplexer 1	.25
		LM-1304 FM Stereo Multiplexer 1 LM-1307 FM Multi. Stereo Dem. DIP	.91
		LM-1458 Dual 741's mini DiPs. TO-5	.63
		LM-1496 Modulator, Demodulator 1 LM-3028 Differential RF/IF amp	.00
	Ü	LM-3028 Differential RF/IF amp 1	.50
		LM-3900 Quad "current mirror" amp	.95
		LM-4250C Programable op amp 2	.50
	Ц	LM-75451 Dual peripheral driver LM-75453 Dual peripheral driver	.44
	Ц	LM-75453 Dual peripheral driver	.44
	Ë	LM- 75491 Quad seg. driver, LED (DIP) 1	-65
	Ō	LM-75492 Hex digit driver, 250ma, DIP 1	.85
100	-		-

4000	tereet, parts may be missing.					
SCRS!	TRIACS!	PRV	Sale			
QUAL	PRACS!	D 50	\$.75			
SAME	PRICE /o		1.25			
	LE!	400	1.98			
10-Amp F Tab Plast		☐ 500 ☐ 600	2.25 2.50			

LINEAR PACTORY VACTORY WARRED **FACTORY OF TACTORY VALUE OF TACTORY OF TACTORY OF TACTORY VALUE OF TACTORY
RC4195 Dual 15V Tracking V.R 2.50
[] RC-2556 Dual 555's
☐ TVR-2000 Super 723. T0-5 1,00
(A) TO-5 or DIP BUY ANY 3 - TAKE 10%
35 WATT AUDIO - \$3.98

.63 .00

AMPLIFIER BASIC

For Class AB use. Basic includes: Signetic 540-30 transistor high power driver T0-5 IC: with a pair of complimentary 35-wat plastic transistors, i.e. 2N5296 npn and 2N6109 pnp. With schematics, printed circuit and parts board layouts.

CHIPS" CT5005 "CALCULATOR

12-Digits, 40 Pin 9-Volt version of 5001 12-Digits, 28-Pin with 3-function memory. MM5725 8-Digits, 4-Funct. LED 6-Digits. 28-Pin. 9V 6.95 3 for \$18. 4.95 3 for \$12. BUY 10 15-

Inflation-Fighting ECONOMY IC PRICES

Nyw Nyw	.24 .24 .24 .27	SN77430 SN77432 SN7437 SN74438 SN7441 SN7441 SN7444 SN7444 SN7446 SN7445 SN7450 SN7450	.24 .45 .49 .24 1.19 1.09 1.25 1.19 1.39 1.39 1.45 .28 .28 .26 .39 .39 .49 .55	SN7472 SN7473 SN7473 SN7475 SN7476 SN7476 SN7481 SN7482 SN7483 SN7485 S	.99 .99 1.05 .99 .99 1.55 1.25	SN74140 SN74141 SN74145 SN74148 SN74150 SN74150 SN74153 SN74153 SN74154 SN74155	2.50	5N74163 5N74164 5N74165 5N74166 5N74174 5N74175 5N74177 5N74177 5N74181 5N74181 5N74182 5N74187 5N74183 5N74183	3 1.75 4 2.85 5 2.85 6 1.85 8 1.85 8 1.25 9 1.25 9 1.25 1.
---	--------------------------	---	---	---	--	---	------	--	--

only \$14.95 IC'S FOR EXPERIMENTERS LIQUID CRYSTAL DISPLAY

Money Back	Guarantee! F.	actory Marked! \$1 00	ı
SN7404. SN7404. SN7413. SN7441. SN7442. SN7445. SN7446. SN7446. SN7448. SN7448. SN7472.	20 for \$1. 20 for \$1. 5 for \$1. 10 for \$1.	actory Marked \$1.00 SN7407 S for \$1. SN74107 10 for \$1. SN74107 10 for \$1. SN74123 10 for \$1. SN74123 10 for \$1. SN74154 5 for \$1. SN74181 5 for \$1. SN74189 5 for \$1. SN74189 5 for \$1. SN74193 5 for \$1.	
SN7473.	10 for \$1.	Includes factory-good, rejects & defects, who	



INTEGRATED CIRCUIT SOCKETS

| 14-Pin, DIP | 5.45 | 14-Pin, DIP | 14-Pin, DIP | 14-Pin, DIP | 15-Pin | 1

Terms: add postage Rated: net 30 Phone Orders: Wakefield, Mass. (617) 245-3829 Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

20c CATALOG ON Fiber Optics, 'ICs', Semi's, Parts
MINIMUM ORDER — \$4.00
POLY PAKS P.O. BOX 942E, LYNNFIELD, MASS. 01940 Orders over \$1 Worth Free Merchandise

7448 — \$.85 7450 — \$.17

7453 - \$.17

quality units.

anteed.

\$1.50 ea

Varo -

New \$.95

Miniature 5VDC Relay

200 OHM Coil, SPDT, 1 x 1/2 in.

mounting TO-3 Case Transistors.

supply. 2000 MFD 30 WVDC — \$.59

4000 MFD 20 WVDC — \$.79

Guardian Heavy Duty Type

MC724P-77c MC725P-77c

MC726P-770

All IC's 100% Guar-

Reg. \$.90 ea. Our Price: 4 for \$1

TO-3 tested and guaranteed units.

Prime 1st

Motorola Voltage Variable Caps

New - MV2112 - Nominal cap. is 56PF

Varies over a range of 3 to 1 from 2 to 30 VDC.

Motorola 3 AMP 600 PIV Rectifiers 1N 4723

Metal "Bullet" case, Factory New, Regular

Our Price: 3 for \$1

LM309K

National, 5VDC IC 1 AMP Voltage Regulator,

\$.99 ea.

FULL WAVE BRIDGE

NEW - \$1.49

MOTOROLA TO-3 MOUNTING KITS

#MK-20. has all hardware including socket for

4 FOR \$1

MALLORY FILTER CAPS

Miniature Twist Lock. Perfect for small power

115 VAC SOLENOID

\$1.49

MC778P-89c

MC786P-77c

MC789P-77c

MOTOROLA RTLIC'S

MC790P-89c

MC792P-77c MC793P-77c

MC9722P-890

- VS647 - 2 Amp 600 PIV - Brand

ALTAJ ELECTRONIC BARGAINS

Bargain Flyer \$.10 free with order

PRIME TTL DIP IC'S PRICES CUT!	7472 — \$.35 7473 — \$.35 74H73 — \$.40
7400 — \$.16	7474 - \$.38
74S00 — \$.49	7475 - \$.69
7402 — \$.16	7476 - \$.44
7403 — \$.16	7483 - \$.88
7404 — \$.16	7486 - \$.39
74S04 — \$.49	7490 - \$.79
7405 — \$.19	7491 - \$.89
7406 — \$.25	7492 - \$.89
7408 — \$.16	7493 - \$.89
7409 — \$.19	7495 - \$.69
7410 — \$.16	7496 - \$.69
7413 — \$.49	74107 - \$.44
7416 — \$.39	74109 - \$.49
7417 — \$.29	74121 — \$.38
7420 — \$.16	74123 - \$.75
7427 — \$.22	74145 — \$.69
7430 — \$.16	74150 — \$.79
7432 — \$.22	74151 — \$.75
7437 — \$.44	74153 — \$.95
7438 — \$.44	74154 — \$.95
7439 — \$.59	74157 — \$1.19
7442 - \$.69	74161 — \$1.19
7445 — \$.69	74164 — \$1.29

LED LAMP SALE!

Jumbo Red - Like MV5024 - 8 for \$1 Jumbo Green — Like MV5222 — 5 for \$1 Mini-Red — Like MV50 — But Better — 10 for

All Our LED Lamps are factory new and guaranteed

Core Memory Special

4K x 16 — Original Cost Over \$400 each Brand New by Ampex. Units were mfg. in 1973 and are ultra fast, state of the art memories, Imagine 65, 536 bits of core in a plane only 10 x 10 in. square. These will store 4096 16 bit words, with drawings. Best Memory Buy in USA!

Special - \$39.95 Ea.

PC Board Special #2

New Boards designed for telecommunication eqmt. Board contains: 9-47 MFD 50V Electrolytics. 14-IN4004 Rectifiers, 10-IN914 Diodes, 3-2N3567 Trans., 8 Asst. TI Plastic Transistors, 1-SDA345 Fairchild Plastic Power Transistor (4 AMPS NPN), 2 RCA 2N5416 (1 AMP 200V. PNP), 2-RCA 40321 (700 MA 300V NPN) The 2N5416 and 40321 have slip-on heat sinks. Board also has 1 each RCA 40319 and 40314 which is a 5 watt complimentary pair, plus many other resistors and caps. Quantity limited. Sold on a "first come" basis.

Special \$2.95 Ea.



74175 — \$1.89 74180 — \$.89

74181 — \$3.50

74182 - \$.89

74192 - \$1.25

74193 - \$1.25

74197 - \$1 25

74200 - \$5.50

JUMBO LED READOUT

.65 inch character size. Twice the size of regular readouts. Brand New Litronix DL747. Outperforms SLA-3, easy to read, Draws only 20MA per segment. Perfect for giant digital clocks \$3.50 ea

FAIRCHILD AUDIO AMPIC

#VA-716 TO-99 Metal Can. 250 MW, Low Distortion Good General Purpose Audio AMP. New - With specs.

\$.59 EA

MINIATURE ELECTROLYTICS — UPRIGHT STYLE 10 MFD 25V — \$.08 50 MFD 16V — \$.12 100 MFD 16V - \$.16 500MFD16V - \$.28

DISC Caps -- Have 1/2 in. Leads for PC Boards .01 MFD 50V - \$.03 .05 MFD 25V - \$.05 1 MFD 25V -- \$.07

This Month's Specials

Man3-7 Segment LED Readout for pocket calculators \$.49 Nixie Tubes - New B5853-S1, 0-9 w/Decimal pt.

\$.89 2N3232 - NPN Silicon Power. TO-3. Like 2N3055

\$.39 2N2712 - TO-92 Plastic NPN Silicon. HFE 75-225

8 for \$1 16 Pin IC Sockets - New, Wire Wrap Style, 4 for \$1

TTL IC GRAB BAG

We got in a big new lot untested. Most are marked with 7400 series numbers, may even include some linears, our sample test shows many are useable. Mix of 200 Pcs. - \$3.95

3 DIGIT LED READOUTS

Perfect for pocket calculators. Has 3 digits same size as MAN-3 inone 12 pin dip only 5ma per segment. Properly multiplexed. 100% Prime Units. Like Litronix DL-33. Best Price in U.S.A.!

\$1.49 each (3 digits)

ALTAJ ELECTRONICS

P. O. BOX 38544 DALLAS, TEXAS 75238

TERMS:

Send Check or Money Order, No C.O.D. Add 10% to help cover postage and handling. Texas residents add 5% Tax

LED Readouts With Internal Logic

Brand new. These are getting hard to find MC719P-77c MC770P-89c MC790

TI #TIL306. Factory Fresh, Brand New. Has a 7490, 7475, 7447. and a MAN-1 Type Readout, ALL IN ONE 16 PIN DIP. Regularly \$22.00 ea.

Special - \$6.95 Ea.

CIRCLE NO. 3 ON READERS SERVICE CARD

BUSINESS OPPORTUNITIES

MADE \$40,000,00 Year by Mailorder! Helped others make money! Free Proof. Torrey, Box 318-NN, Ypsilanti, Michigan 48197.

FREE CATALOGS. Repair air conditioning, refrigeration. Tools, supplies, full instructions, Doolin, 2016 Canton Dallas, Texas 75201.

MAILORDER MILLIONAIRE helps beginners make \$500 weekly. Free report reveals secret plan! Executive (1K10). 333 North Michigan. Chicago 60601.


PIANO TUNING LEARNED QUICKLY AT HOME! Tremendous field! Musical knowledge unnecessary. Gl approved. Information free. Empire School, Box 450327. Miami 33145.

FREE Secret Book "2042 Unique Proven Enterprises. Fabulous "Little Knowns." Work home! Haylings-BH. Carlsbad, California 92008.

\$200.00 DAILY In Your Mailbox! Your opportunity to do what mail-order experts do. Free details. Associates. Box 136-J. Holland, Michigan 49423.

\$49.95 Telephone Answering Machine! Your cost \$33.50! Details: Palomar, Box 17384EB. Jacksonville, Florida 32216

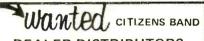\$178.00 WEEKLY Work one hour daily Free brochure FAS, Box 13703-A. San Antonio TX, 78213.



DEALER-DISTRIBUTORS

Send this Ad to:

PAL ELECTRONICS CO. P. O. Box 778 • Westminster, Ca. 92683

EARN \$15,000 annually plus. Full year trial plan Import-Mailorder business. Postcard brings details: Northeast Imports, Box 121PE10, Fremont, N.H. 03044

Make BIG Profits In YOUR OWN ONE-MAN **ELECTRONIC FACTORY!**

Start home, spare time. A postcard with your name & address, will bring you Free Illustrated Literature about this unusual opportunity! Write TODAY!

BARTA-DJ, Box 248, Walnut Creek, Calif. 94597

START SMALL, highly profitable electronic production in your basement, Investment, knowledge unnecessary, Free illustrated literature. Barta-CJ. Box 248, Walnut Creek. California 94597.

TELEPHONE conference caller. Retail \$69.95. Free wholesale details: C&S Electronics. 16 Filmore Place. Freeport, N.Y. 11520.

HOW TO SELL BOOKS BY MAIL. FREE INFORMATION McCord, Box 276-D, SYLVANIA, OHIO 43560.

\$1,000 MONTH Mailorder, Send Stamp, Fiddes, Box 1242F Glen Burnie, MD 21061

EMPLOYMENT INFORMATION

AUSTRALIA NEEDS YOU! Jobs. Transportation Opportunity Book. Rents. salaries, giant employees list, taxes, schools, farming, social life, \$1.00, John Price, 312-P Wainani Way, Honolulu, Hawaii 96815

TREASURE FINDERS

FAMILY FUNL OUTDOOR ADVENTURE! Find valuable coins and treasure with world famous metal detectors. Free illustrated booklet. Detectron. Dept. PE, Box 243, San Gabriel, Calif. 91778.

TREASURE FINDER locates buried gold, silver, coins, treasures, 5 powerful models, \$19.95 up. Instant financing available. Free catalog. Dealer inquiries invited. Reico. Dept. A-33. Box 10839. Houston. Texas 77018.

REAL ESTATE

FALL CATALOG! 272 pages! Over 2,500 top values in FARMS, RANCHES, RECREATIONAL LANDS. BUSINESSES, TOWN and COUNTRY HOMES in 40 states coast to coast! Over 4,100 PHOTOS! UNITED FARM AGENCY, 612-EP West 47th St., Kansas City, MO 64112.

Popular Electronics sports action films

OCTOBER 1974

ADVERTISERS INDEX

SER	EADER VICE NO.	ADVERTISER	PAGE NUMBER
1 2 3 4	Allison Automoti Alpha Electronic Altaj Electronics Ancrona Corp	ve Co	
6 7	BSR (USA) Ltd Bell & Howell So	U.S., Inc	.92, 93, 94, 9
8 9 10	Cleveland Institu Clifford's Hi-Fi	dio Engineering Institute ute of Electronics Wholesalers	.28, 29, 30, 3
11 12 13	Delta Products, Design Acoustic	s Co	THIRD COVE
14 15 16 17	Edmund Scienti Electronic and (fic Corp Control Engineers' Book Cl Service	11 ub
18 19		Sound Company, Inc., The	
5	Heath Company	·	.62, 63, 64, 6
20 21		ectronics Unlimited	
22	James Electroni	cs	
23	Kroch's & Brent	ano's	
24	Lafayette Radio	Electronics	
25 26 27	MITS, Inc Mallory Distribu NRI Schools	atory, Inc tor Products Company	
28 30		cations	
31 32	Radio Shack . Royce Electronic	cs Corporation	
33 34 35 36 37 29	Schober Organ Shure Brothers Solid State Sale Southwest Tech	Corp., The	
41 38		nasonic	
39	U.S.Pioneer Ele Unique Ideas,	ctronics Corp	ECOND COVER,
		ınd	

SHOW TIME Enjoy your sports favorites in sound or silent, Standard 8 or Super 8 color or 8&W films. Order the latest Columbia, Castle, or Sportlite Film Catalogs for the latest listings and price changes -25 cents each (coins or stamps, please) SPORTL(TE, Elect-10 Dept., P.O. Box 24-500. Speedway. Indiana 46224

RECORDS

OLDIES, 45rpm Free Catalog Corny's Record Shop, Box 335TP, Mason, Ohio 45040.

RUBBER STAMPS

RUBBER address stamps. Free catalog, 45 type styles Jackson's, Box 443G, Franklin Park, III, 60131

BOOKS

FREE catalog aviation/electronic/space books. Aero Publishers, 329PE Aviation Road, Fallbrook, California 92028

FREE book prophet Elijah coming before Christ, Wonderful bible evidence. Megiddo Mission. Dept. 64, 481 Thurston Rd., Rochester, NY 14619.

BOOKS-thousands titles, bargains, Catalog Free Cassiano, 92-27 New York Blvd., Jamaica, New York 11433

UNUSUAL BOOKS! Catalogue Free! International Imports Box 7789PE. Atlanta. Georgia 30309.

LEARN RADIO ANNOUNCING! Books, Magazines: Deejay Box 1355-C. Sioux Falls. South Dakota 57101

POPULAR ELECTRONICS INDEXES. Detailed and complete subject indexes now available to both 1972 and 1973 magazines. Hundreds of subject references to help you quickly find that special project, article, or product test. 1972 and 1973 editions \$1.00 each. INDEX. box 2228. Falls Church, Va. 22042.

DO-IT-YOURSELF

TELEPHONES UNLIMITED, equipment, supplies, Catalog 50 cents. Box 1654E, Costa Mesa, Calif. 92626.

PLASTICS

CASTOLITE pours like water, hardens like glass without heat. Crystal clear, colors, Embed flowers, seashells, mementos, anything. Make fine gifts. Form flexible molds over any pattern, size. Reproduce your own designs in plastics, candlewax. metal, plaster. cement. Send 50 cents for profitable manual catalog. CASTOLITE, Dept. 74L/PE. Woodstock, III, 60098

HYPNOTISM

SLEEP learning. Hypnotic method, 92% effective, Details free. ASR Foundation, Box 7566EG. Fort Lauderdale Florida 33304.

Ruidoso New Mexico 88345 self-hypnosis recer FREE Hilphotism. Self-Hypnosis. Sleep Learning Catalog!

self-hypnosis record releases fantastic mental ant results! Free trial. Write: Forum (AA10). 333 Vichigan, Chicago 60601

MISCELLANEOUS

WINEMAKERS: Free illustrated catalog yeasts, equipment. Semplex, Box 12276P, Minneapolis, Minn. 55412.

SAVE! INSTALL CARPET professionally. Booklet \$3.95. Satisfaction Guaranteed, Surprise Bonus, Carpet Club of America, 511, Kenilworth, Utah 84529.



Spectacular sound! Stereo testing! Background music and sound effects! Special Interest Records available exclusively from Ziff-Davis Send for your free Record Catalog -Ziff-Davis Publishing Co., Dept 23, One Park Ave. New York, N.Y. 10016

FREE IC With Every \$10 Order*

- REDUCE YOUR PROJECT COSTS
- MONEY BACK GUARANTEE
- 24-HOLIR SHIPMENT
- ALL TESTED AND GUARANTEED

. TRANSISTORS

NPN:	
2N3563 TYPE RF Amp & OSC to 1 GHz (pl. 2N918)	6/\$1.00
2N3565 TYPE Gen. Purpose High Gain (TO 106)	6/\$1.00
2N3567 TYPE High Current Amplifier/Sw 500mA	3/\$1.00
2N3691 TYPE GP Amp to 25mA and 50 MHz	6/\$1.00
2N3866 TYPE RF Pwr Amp 1-2 W @ 100-600 MHz	\$1.50
2N3903 TYPE GP Amp & Sw to 100mA and 30 MHz	6/\$1.00
2N3904 TYPE GP Amp & Sw to 100mA (TO-92)	5/\$1.00
2N3919 TYPE RF Pwr Amp 3-5 W @ 3-30 MHz	\$3.00
2N4274 TYPE Ultra-High Speed Switch 12ns	4/\$1.00
MPS6515 TYPE High-Gain Amplifier hee 250	3/\$1.00
Assort. NPN GP TYPES, 2N3565, 2N3641, etc. (15)	\$2.00
PNP:	
2N3638 TYPE Gen. Purpose Amp & Switch	4/\$1.00
2N4249 TYPE Low-Noise Audio Amp 1µA to 50mA	4/\$1.00

	FET's:	
	N-CHANNEL (LOW-NOISE):	
	2N4416 TYPE RF Amplifier to 450 MHz (TO-72)	2/\$1.00
	2N5486 TYPE RF Amp to 450 MHz (plastic 2N4416)	3/\$1.00
	2N5163 TYPE Gen. Purpose Amp & Sw (TO 106)	3/\$1.00
	2N4091 TYPE RF Amp & Switch (TO-106)	3/\$1.00
	E100 TYPE Low-Cost Audio Amplifier	4/\$1.00
	ITE4868 TYPE Ultra Low Noise Audio Amp.	2/\$1.00
	TIS74 TYPE High-Speed Switch 40s2	3/\$1.00
	Assort. RF & GP FET's, 2N5163, 2N5486, etc. (8)	\$2.00
	P-CHANNEL .	
	2N4360 TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
	E175 TYPE High-Speed Switch 125sz	3/\$1.00
	M104 TYPE MOS FET (Diode protected) 0.3 pF	\$3.00
	LINEAR IC's:	
	309K Voltage Regulator 5V @ 1A (TO-3)	\$1.90
	380 2-5 Watt Audio Amplifier 34dB (DIP)	\$1.50
	555X Timer 1µs-1 hr, Dif. pinout from 555 (DIP)	\$.90
	709 Popular DP AMP (DIP/TO-5)	\$.39
	723 Voltage Regulator 3-30 V @ 1-250mA (DIP/TO-5)	\$.75
	739 Qual Low - Noise Audio Preamp/OP AMP (DIP)	\$1.00
	741 Freq. Compensated DP AMP (DIP/TD-5/MINIDIP)	\$.45
	2556 Dual 555 Timer 1 usec to 1 hour (DIP)	\$1.55
	LM305 Positive Voltage Regulator (TO-5)	\$1.25
	MC1458 Dual 741 DP AMP (MINI-DIP)	\$.95
	Assorted Linears-741/709/723, etc. (4)	\$2.00
,	DIODES:	

F7 VARACTOR 1-3 W Output @ 100-500 MHz, 5-30 pF *MAIL NOW! With every order of \$10 or more, postmarked prior to 11/30/74, FREE 739 or 749 Low-Noise Dual OP AMP included—\$1 VALUE.

1N914 TYPE Gen. Purpose 100V/10mA 1N3600 TYPE Hi Speed SW 75V/200mA

1N3893 TYPE RECTIFIER Stud Mount 400 V/12 A

1N759 ZENER 10 Volt 400mW 1N968 ZENER 15 Volt 400mW 1N968 ZENER 20 Volt 400mW 05 VARACTOR 5-50 W Output @ 30-250 MHz, 7-70 pF

1N4608 TYPE GP & SW 80V/400mA

1N749 ZENER 4.3 Volt 400mW 1N753 ZENER 6.2 Volt 400mW

1N755 ZENER 7.5 Volt 400mW 1N757 ZENER 9.1 Volt 490mW

ORDER TODAY—All items subject to prior sale and prices subject to change without notice. DATA SHEETS included with all items. WRITE FOR FREE CATALOG offering hundreds of semi-conductors not listed here. Send 10% stamp.

TERMS: All orders prepaid. We pay postage. \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax.



Tel. (415) 851-0455

CIRCLE NO. 1 ON READERS SERVICE CARD

SPECIAL interest records available, produced by the editors of the world's leading special interest magazines. Send for free catalog. Record Catalog CL, Ziff-Davis Publishing Co., One Park Avenue, New York, N.Y. 10016.



Here's the Magazine that unsnarls the facts. Complete directories and buying guides compare products feature by feature, cost by cost—Open-Reel, Cassette and 8-Track Tape Machines • 4-Channel Components—decoders; headphones; microphones; raw tape; accessories and more. Plus special features and articles—by the authorities—to keep you up-to-date.

1974 Fdition—#11 1974 Edition-#11

Order by number from
Ziff-Davis Service Division,
595 Broadway, N. Y., N.Y. 10012.
Enclose an additional 35c per copy
for postage and handling. Outside
USA all magazines are \$2.50 per

BACK ISSUES AVAILABLE: copy, postpaid.

1973 Summer-#13 1973 Winter-#78 \$1.50 each

PAYMENT MUST BE ENCLOSED WITH ORDER

10/\$1.00 6/\$1.00

6/\$1.00

2/\$1.00

3/\$1.00 4/\$1.00

4/\$1.00 4/\$1.00

4/\$1.00 4/\$1.00

4/\$1.00

\$1.00

LIVE IN THE WORLD OF TOMORROW...TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in ecological and physical science items — plus 4,500 finds for fun, study or profit ... for every member of the family.



A BETTER LIFE STARTS HERE

LIE DETECTOR TYPE METER

Amazing Emotion Meter reveals hidden likes, dislikes. Easy to use; sensitive, accurate. Measures changes in body resistance caused by changes in emotional state. Needle movement indicates emotional response (not whether favorable or unfavorable). Effectiveness depends on questions asked and interpretation. Unique 10-oz.



set ideal for entertainment and education — parties, science projects, psychological experiments. Requires 9V transistor battery (not included). Instructions

No. 42,1974AV (2% x 4 x 1¾")\$19.95 Ppd.

LOW-COST ULTRASONIC CLEANER

Full pint capacity at price of old 1/3 pt mcdel. For home, industry! Makes grimy, small delicate parts & objects sparkle — from diamonds to dentures, electronic items to coins & combs. Fully transistorized metal & stainless steel cabinet (6 x 4 x 4") with built-in tank has frequency control, item platform. Incls. cleaning powder, mfrs. 1-yr guar. 110-120v AC.



Stock No. 71,003AV

NEW! KIRLIAN PHOTOGRAPHY KIT!

Experiment in the fascinating new field of "Kirlian electrophotography—images obtained on film without camera or lens by direct recording of electric charge transmitted by animate & inanimate objects. Each "aura" differs—animate aura said to change corresponding to physical changes. Kit incls. portable darkroom, double transformer isolated from power source; instrs.



Stock No. 71.938AV .

"HIGH VOLTAGE PHOTOGRAPHY" by H.S. Dakin No. 9129AV. (60-PG. PAPERBACK BOOK)

GET A CHARGE FROM THE SUN!

Our 12V Solar Battery Charger allows direct conversion of light-to-electricity. Compact panel put on a boat can automatically charge its 12V battery over entire daylight period. Use anywhere for a trickle charge. Big value, it comprises 30 ½V silicon solar cells in series widnigde. series w/diode.



No. 71,971AV (AB, 30 W-HRS./WK.) 9 x 18" HI CURRENT MODEL (6W, 12V, 500 mA) No. 72,010AV (AB. 150 W-HRS./WK.) 6 x 6" LO VOLTAGE MODEL (1.5V, 38W, 250 mA)\$89.95 Ppd\$420.00 Pnd. ...\$49.95 Ppd



12v WIND-POWERED GENERATOR

Cheapest continous source of electricity available! Attach to 12v truck batt. (not incl) and get free electricity from the wind. Needs only 7 mph wind — 15 amps output in 23 mph wind; double the watt-hour output of ordinary radio chargers. Perfect remote area and alternate energy prevents over hardingation. Price includes packing & shipping.

prevents overcharging/action. Price includes packing & shipping.

No. 19,189AV (10"-145 lb.).....\$475.00 Ppd.



ON-TIME BIOFEEDBACK MONITOR

New—measures & records % of tng. time spent producing alpha/theta! Electronic scoring device to observe exact degree of progress in alpha-theta prod'n. for greater relaxation, concentration. Deluxe sensitive instrument gives realiable audio & visual feedback of alpha/theta brainwaves.

α visual reedback of alpha/theta brainwaves. Tracking time (0-20 min.) of alpha or theta rhythm generated is switch-controlled. Other innovative features incl. artifact inhibitor (no muscle interference). 12 lb.

.



3-CHANNEL COLOR ORGAN KIT

Easy to build low-cost kit needs no technical knowledge. Completed unit has 3 bands of audio frequencies to modulate 3 independent strings of colored lamps (i.e. "lows"-reds, "middles", greens, "highs" blues. Just connect hi-fi, radio, power lamp etc. & plug ea. lamp string into controlled individ SCR circuits; isolation transformer; custom plastic housing, instr.

Stock No. 41,831AV\$18.95 Ppd



ASTRONOMICAL MIRROR KITS

Grind your own mirror for powerful telescopes. Kit contains fine annealed pyrex mirror blank, tool, abrasives, diagonal mirror, and eyepiece lenses. Instruments you build range in value from \$75.00 to build to fellers. to hundreds of dollars.

Stock No. 70,003AV 41/4" diam. 3/4" thick	.\$13.75 Ppd.
Stock No. 70,004AV 6" diam. 1" thick	.\$19.75 Ppd.
Stock No. 70,005AV 8" diam 13%" thick	
Stock No. 70,006AV 10" diam. 13/4" thick (30 lbs.)	
Stock No. 70,007AV 121/2" diam. 21/4"thick (46 lbs.)	.\$98.50 F08



3" ASTRONOMICAL REFLECTING TELESCOPE

See stars, moon, planets close-up!
3u to 90X. Famous Mt. Palomar Type.
Aluminized & overcoated 3" diameter
f/10 primary mirror, ventilated cell. Fork type
equatorial mount. Durable PVC tube. Includes 1" F.L. 30X Ramsden, Barlow
lens to triple power, 3X finder
telescopes, hardwood tripod. FREE: "STAR CHART", "HOW TO USE" book.

Stock No. 85,240AV	. \$49.95 Pnd
DELUXE 3" REFLECTOR TELESCOPE #80,162AV	. \$79.95 Ppd
4¼" REFLECTOR (45X to 135X) #85,105AV	. \$149.50 FOE
6" RBFLECTOR (48X to 360X) #85,187AV	.\$249.50 FOE



MAIL COUPON FOR

164 PAGES . MORE THAN 4500 UNUSUAL BARGAINS

pictely new Catalog. Packed with huge selection of telescopes, micropes, binoculars, magnets, magnifiers, prisms, photo components logy and Unique Lighting items, parts, kits, accessories — many 1-lo-get surplus bargains, 100's of charts, illustrations. For hobby experimenters, schools, industry.

EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N. J. 08007 Please rush Free Giant Catalog "AV"

Name	
Address	



PLEASE SEND **GIANT FREE** CATALOG "AV"

30 DAY MONEY-BACK GUARANTEE

-		
ľ	١	K
	и.	

COMPLETE & MAIL WITH CHECK OR M.O. FOMUND SCIENTIFIC CO. 300 Educary Building Barrington N. L. 08007

Many	Stock No.	Description	Price Each	Total
_				
-				
	Add Handling Chg.: \$1	.00, Orders Under \$5.00, 50¢	, Orders Over \$5.00	
Lenck	ose Chack Comoney	order for \$	TOTAL \$	
	230 Claren Children	0.001 101 4		

STATE_

CIRCLE NO. 15 ON READERS SERVICE CARD

ADDRESS

CITY

MARK TEN B, THE GAS SAVING, PLUG SAVING, TUNE-UP SAVING, ELECTRONIC IGNITION FROM DELTA. NOW AS LOW AS \$49.95.

Years of testing and use by race car drivers in all categories have proven Delta's Mark Ten B the most advanced ignition system

on the market today.

Prove it to yourself. Give you car vroooom!
With a Mark Ten B Capac tive Discharge Ignition System under the hood of your car great things will happen...like reducing costly tune-ups by as much as 75%. Further, you get better all-weather starts, quicker acceleration and better mileage.

Many operational problems caused by emission control devices, poor manifolding or improper fuel mixtures disappear. Delta's Mark Ten B even improves the performance of brand-new factory installed electronic ignitions (Chrysler and Ford). Factory systems merely eliminate points and condenser, but the Delta Mark Ten B combines the advantages of capacitive discharge with solid state

PELITA PRODUCTS INC.

PELITA PRODUCTS INC.

BUILD BUIL

kt form. Or, if you prefer, get the complete ready-to-install unit. Either way, you can install it yourself in minutes with no rewiring, even over Chrysler and Ford systems.

Mail the coupon today and discover how to enjoy happy motoring with Delta's Mark Ten B. The do-it-yourse fer's dream that really pays off.



bled @ \$64.95 ppd	☐ Ship ppd. ☐ Ship C.O.D. Please send: Mark Ten B assem- Mark Ten B Kit @ \$49.95 ppd. (12 volt negative ground only) Stan- \$49.95 ppd 6 Volt: Neg. Ground Only 12 Volt: Specify
Pos. Ground (12 Volt Positive or Negative G	Neg. Ground Standard Mark Ten Deltakit ^a @ \$34.95 ppd.
Car Year	. Make
Name	
Address	
City/State	7in

CIRCLE NO. 12 ON READERS SERVICE CARD

The Specification Guarantee*. Perhaps someday everyone will have it.

40Hz - 12kHz (+2/-4dB) (+2/-3dB)

40Hz - 13kHz (+2/-4dB) (+2/-3dB)

50dB or better

58dB or better

Within ±1.5%

You're looking at the new Technics 600 Series, two of the finest cassette decks we've ever made. But equally important, they're also our first

Frequency Response: Normal Tape Position

CrO, Tape Position

S/N Ratio (Weighted, Signal level 250 pWb/mm) Without Dolby

THD (0 VU at 1 kHz)

Speed Accuracy

With Dolby (Above 5 kHz)

examples of "the Specification Guarantee." The only kind of a specification we feel is worth serious consideration.

That's because "the Specification Guarantee" isn't merely a collection of overly impressive numbers achieved under ideal conditions. It's five meaningful perform-

ance specifications that every Technics RS-676US and RS-610US cassette deck, including yours, is guaranteed to meet or surpass*. And if by some unlikely chance it doesn't, we will make sure it does. After all, that's what we feel a guarantee is all about.

But the guarantee isn't the only impressive thing about these specs. The numbers are equally impressive. Even when you compare

them with the "unguaranteed" performance figures you usually see. Yet our figures are conservative, understated. Figures that your

unit is likely to surpass rather than just meet. And that makes them even more impressive.

The RS-676US. The RS-610US. And "the Specification Guarantee."

The concept is simple. The execution is precise. The performance is outstanding. The name is Technics.

50Hz - 10kHz ±3dB 50Hz - 12Hz ±3dB 49dB or better

"Specification Guarantee will be bonored for a period of ninety days from the date of original purchase. Void if the product is damaged, altered, or abused following original sale, or if repaired by other than authorized Panasonic personnel, or if the product is not purchased and retained within the U.S.A. or Puerto Rico. Test procedures are available in detailed description on request from Technics by Panasonic, 200 Park Avenue, New York, N.Y. 10017. Specification Guarantee is in addition to the usual parts and labor warranty.

57dB or better

2.3% or better

Within ±2.0%

200 PARK AVE., NEW YORK, N.Y. 10017. FOR YOUR NEAREST AUTHORIZED TECHNICS DEALER, CALL TOLL FREE 800 447-4700, IN ILLINOIS, 800 322-4400.

Technics by Panasonic

