Tips, guides and reports for people repairing televisions and electronic equipment

# AND HOME ELECTRONICS REPAIR April 2004 £3.20

# **CES Las Vegas report**



# Replacing the Painter chip Vintage radio repairs

**Wireless broadband links** 



Satellite, Audio, Monitor, TV, VCR and DVD faults

# Classic remote controls, so good, it's scary...

**Classic** Europe's leader in remote control design are proud to launch the first handsets of the brand new SYSTEM RC range.

These remotes, suitable for use with Philips recent using the RC2031 (8 level) and the RC2007/RC200 (4 level) handsets have full 4 and 8 level controls plus Led indicators so you know what level you are in. The 8 level handset even has bi-colour Led's.

These SYSTEM RC remotes are available now from your usual Classic distributor at a price that is anything but scary.

For your free look up card giving more information on these handsets together with the 57 other types added to our range visit the Classic website, www.classic-electronics.co.uk and click on 'NEWS', contact your usual Classic distributor, phone us on 01635 278678 or email us at sales@classic-electronics.co.uk



Technical helpline 01635 278678



### 323 Comment

TV – the low-down.

### **324** Teletopics

Digital TV system for mobile phones. Analogue TV switch-off proposal. Pioneer joints Euro HDTV project. BoxClever to be sold off. Top-Up TV. Blue laser breakthrough.

### 326 CES Las Vegas 2004 Manufacturers worldwide use the annual

Manufacturers worldwide use the annual International Consumer Electronics Show to announce or launch major new products and developments. George Cole reports on the highlights of the show.



### 331 Workshop equipment guide

Eugene Trundle takes a look at what's good and what's new in the world of test gear and aids for bench and field servicing. This second part concentrates on some of the more recent technology we have to deal with, some ways of cost saving, aids and tools.

### **345 Service casebook**

Michael Maurice on problems he's encountered in the field and the workshop.

## 346 Introduction to computer networking

In this concluding instalment of his latest series Fawzi Ibrahim describes the Domain Numbering Service.

### 348 Replacing the Painter chip

Philips refers to the main microcontroller IC in the A10E chassis as the Painter. It's a small, surfacemounted 100-pin device that can be the cause of many symptoms. Particular care is required when replacing it. Martin Cole explains how to carry out the repair.



### **350 Vintage repairs**

Pete Roberts describes a couple of 'no-reception' faults with vintage radio equipment, a Radford FM tuner and a Motorola car radio.

### 352 Wireless broadband links

Steve Beeching on the advantages of having a wireless broadband link for internet connection.

### **354 DX and Satellite Reception**

Terrestrial DX and satellite TV reception reports. Broadcast and satellite TV news. A channel-pass filter for Band I. Roger Bunney reports.

### **357** Monitors

Guidance on repairing monitors and related equipment.

### 358 Audio faults

### 359 Test Case 496

### **360 Extended fault reports**

Reports on tricky or complex TV fault conditions that are too long for inclusion in our regular faultfinding section.

### **362 TV fault finding**

365 VCR clinic

### 366 DVD faults

### **368** Letters

Picture and sound quality and an aerial mystery. Burn ups. The Philips LO1 chassis.

### 369 Help wanted

### 370 Web service

Useful websites for TV professionals, technicians and enthusiasts.

### 372 Books to buy

The Television book service, with details of some of the titles you can order.

### 374 What a life!

I had the shop to myself for a while. Some faulty TVs and a dead VCR. Then a visit from the shop steward. Donald Bullock's servicing commentary.

### 376 Satellite notebook

Audio narrative setting. Digital channel update. Recording MPEG-2 signals on a DVD. Ku-band signals from Express 3A at 11°W. Digibox fault reports.

```
379 Next month in Television
```

### Editor

John A. Reddihough TVeditor@highburybiz.com

Deputy Editor Tessa Winford

Production Editor Jane Massey

### **Advertisement Sales**

Luke Baldock 01322 611 289 Fax 01322 616 **3**76

Editorial Assistant Caroline Fisher 01322 611 274

Managing Editor Bill Evett

### Publishing Director Tony Greville

Note that we are unable to answer technical queries over the telephone and cannot provide information on spares other than that giver in our Spares Guide.

### Disclaimer

We work hard to ensure that the information presented in Television is accurate. However, Television's publisher – Highbury Business – will not take responsibility for any injury or loss of eornings that may result from applying information presented in the magazine. It is your responsibility to familiarise yourself with the lows relating to dealing with your customers and suppliers, and with safety practices relating to working with electrical/electronic circuitry – particularly as regards electric shock, fire hazards and explosions.

Next issue, dated May, on sale April 21



# TV - the low-down

V has been a part of most people's daily lives for several generations. It's remarkable the strides that this medium has taken in a relatively short time span, from crude beginnings to its current predominance - to the extent that it now provides front-page stories day after day in the popular press. At the end of the nineteenth century TV was already being written about by some visionaries. The telephone and the telegraph had been invented, also the cathode-ray tube (though in a very simple form), so signals could be transmitted and there was the possibility of remote picture displays. Radio transmission was to follow shortly.

It seems that as early as 1907 Boris Rosing was able to demonstrate TV as a practical system at the St. Petersberg Technical Institute, using a CRT as the display device. In 1908 A.A. Cambell Swinton proposed a system that used electronic means both to produce the video signal and display it. Not much happened till the mid Twenties, when Baird became active in the UK and researchers in the US were developing practical electronic cameras. By the early Thirties there had been several major advances, including in particular RCA's demonstration of a fullyelectronic TV system in 1933, with the transmitter atop the Empire State building. But the Depression has taken hold worldwide, making further advances difficult. Despite this the BBC started its TV service, the first in the world with regular scheduled transmissions, in 1936. In the pre-war period however transmissions were severely limited, and the number of sets that were sold in the UK was only some 10-20,000. It was hardly a mass medium. The US was not to get regular TV services until 1941.

World War II saw major strides in the development of electronics, though not for TV purposes of course. But radar has many similarities, and the work on this helped the development of TV in the immediate post-war era. Since then there has been one development after another. leading to the present situation where high-quality sets are available to all at knock-down prices and you can get your signals, with a wide variety of channels, off-air, via cable or from satellites. Or, for that matter, from tapes and discs. It's the predominant medium that affects everyone's life. But - there always has to be one, doesn't there - what is TV doing for human happiness? Is it a benign or malign influence? It can of course be either, depending on choice of material watched and who is doing the watching. There are overall effects however.

Happiness is not an easy thing to

### What is TV doing for human happiness? Is it a benign or a malign influence?

assess, especially on a mass scale. Nevertheless a certain amount of research has been done. The outcome seems to be that we are no happier now than we were a generation ago despite all the advances that have made life easier, in the developed countries at any rate. In fact it seems that in the US people are slightly less happy than they were in the Fifties. The situation appears to be much the same in the UK.

Various factors can be measured to determine general welfare: for example crime, the number of broken families, and any increase in depression, alcoholism and the use of drugs. These negative factors have become increasingly strong in recent years. What could be the cause? There are probably many, but Professor Richard Layard of the London School of Economics has done some very interesting work that points to TV as being a major negative influence. His conclusions are to be published later this year in a book. It's likely to create quite a stir.

The professor (he is now Lord Layard)

#### COPYRIGHT

© Highbury Business, 2004. All rights reserved. No part of this publication may be reproduced, stored or transmitted in any form or by any means without the written permission of the publishers.

All reasonable precautions are taken by *Television* to ensure that the advice and data published are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

### CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, Television, Highbury Business, Media House, Azalea Drive, Swanley, Kent, BR8 8HU. Editorial correspondence should be addressed to Television, Editorial Department, Highbury Business, Media House, Azalea Drive, Swanley, Kent, BR8 8HU.

#### INDEXES AND BINDERS

Indexes for Vols. 38 to 53 are available at  $\pounds$ 3.50 each from SoftCopy Ltd., who can also supply an fifteen-year consolidated index on computer disc. For further details see page 379.

Binders that hold twelve issues of *Television* are available for £6.50 each from Modern Bookbinders, Pringle Street, Blackburn, BB1 1SA. Telephone: 01254 59 371

Make cheques payable to "Television Binders".

Newstrade Enquires Distributed by COMAG

Telephone: 01895 444055

ISSN 0032-647X

points out that watching TV alters the happiness of society in two ways: it makes people more violent, and it makes them less satisfied with what they have. There has been much investigation into the effect of TV on violence: how, for example, children become more aggressive the more time they spend watching TV. But there seems to have been no such effect back in the Fifties. Why? Because in those days TV mirrored the level of violence in society, whereas today it grossly inflates violence. It also shows much bad behaviour that people come to accept as normal. Then there is the wealth factor - TV presents a world that exaggerates wealth and thus feeds dissatisfaction. In all, TV can cause general unhappiness.

It's difficult, in fact virtually impossible, to see what could be done about the malign influence of TV. We can't ban TV. Even totalitarian regimes can't suppress it in this age of satellite signals (though you may have to hide the dish!). Censorship would hardly be acceptable in today's developed societies. It seems that guidance, to programme makers on what is acceptable, and to viewers on what to watch and how much, is the best that can be done. But it's hard to believe that this will achieve much. There is nevertheless a huge responsibility on all who run this predominant medium.

#### SUBSCRIPTIONS

Highbury Fulfilment Services, Link House, 8 Bartholomew's Walk, Ely, Cambridge CB7 4ZD. Telephone 01353 654 431 Fax 01353 654 400 Email hbc.subs@highbury-wyvern.co.uk Please notify change of address.

#### Subscription rates:

UK 1 year £33.80, 2 years £54.00, 3 years £71.00. Republic of Ireland 1 year £38.95, 2 years £62.00, 3 years £81.85. Mainland Europe 1 year £49.00, 2 years £78.40, 3 years £102.90. Rest of World 1 year £63.50, 2 years £101.00, 3 years £133.00. Cheques should be made payable to Television.

#### **BACK NUMBERS**

If available issues are £4.00 each.



# **TELETOPICS**

# Digital TV system for mobile phones

A European trial involving Nokia, Philips, Vodaphone and Universal Studios of Germany is being run in Berlin to test the feasibility of broadcasting digital terrestrial TV channels to mobile phone handsets. The trial is part of a project called Broadcast Mobile Convergence (BMCO). It uses a new transmission standard known as DVB-H (Digital Video Broadcasting – Handsets). This is based on the DVB-T standard used for conventional DTT services, like Freeview in the UK, the main difference being the transmission of far less data. The chipsets used for reception require about a tenth of the power of those

### Pioneer joins Euro HDTV project

Pioneer has joined the Euro1080 Project, which started transmitting Europe's first HDTV service in January, via Astra at 19·2°E. Resolution of the HDTV transmissions is 1.920 x 1,080 lines. using a 50Hz interlaced format. The service consists of two channels, a Main Channel of live and recorded programmes that are broadcast on a carousel basis daily, and an Event Channel of items such as football matches and concerts. The footprint of the Main Channel covers over thirty European countries, extending from Norway to Greece.

Pioneer markets a range of PureVision HDTV-ready plasma TV sets that feature the company's Pure Drive technology. This provides advanced video signal processing and thus improved display quality whatever the source, including PC signals and compressed formats.

Pioneer has signed a memorandum of understanding to buy NEC's plasma screen business for some £205m. The deal will increase Pioneer's share of the world plasma display market to about 22 per cent. NEC will continue to market NECbranded plasma displays supplied by Pioneer on an OEM basis. Pioneer expects the deal to enable it to increase production fairly quickly and also broaden its range. in STBs and IDTV sets.

DVB-H uses a system called time-slicing: the digital receiver is turned on only when it is receiving a digital signal and is turned off when there is no signal, thus greatly reducing power consumption and extending battery life. To increase efficiency, encoding systems such as MPEG-4 are employed instead of the MPEG-2 system used for conventional DTT broadcasting. DVB-H channels can be transmitted alongside DVB-T services.

The trial. run by the BMCO project, is to run from April 2004 to next September. It involves about fifty people who will use

### Analogue TV switch-off proposal

The Digital Television Group and broadcasters including the BBC. NTL and ITV have proposed a staggered analogue TV switch-off starting in 2007. The government had announced a switch off at some time during the period 2005-2010, as soon as 95 per cent of homes can receive digital transmissions. But the DTG and others consider that greater pressure would be put on the public to convert to DTT by means of a phased switch-off: BBC2 analogue transmissions would be switched off first, followed by BBC1 and Channel 4. leaving only digital transmissions.

The DTG estimates that it would take about five years to complete the analogue switch-off throughout the UK.

### Joint ODD venture

Toshiba and Samsung have announced a new joint venture, known as Toshiba Samsung Storage Technology Corporation. for optical disc drives (ODDs). Operation starts on April 1. The company will integrate business planning and ODD development. procurement and marketing, including CD-ROM and DVD-ROM drives. The headquarters will be in Japan, with a wholly-owned subsidiary in Korea. To start with there will be some 700 employees.

### Labgear bought by Philex

Labgear Ltd., a well-known manufacturer of aerials and receiving equipment such as amplifiers and filters, has been bought by accessories specialist Philex PLC. Labgear has been designing and producing equipment at its Cambridgeshire location for over sixty years. Philex, which was established in 1982, has announced that it intends to develop Labgear's terrestrial and satellite aerial and signal distribution range. modified Nokia 7700 media handsets to receive the DVB-H transmissions. There are plans to run a large-scale trial involving about 1,000 people next year. If the trials are successful, the first DVB-H services could start in 2006.

Samsung launched a mobile phone with a built-in analogue tuner in Korea in June 2003. A month later NEC announced the first working prototype of a mobile phone that can receive DTT transmissions. NEC hopes to launch commercial products in Japan in 2005. Sanyo has also demonstrated a prototype mobile phone with digital TV reception capability.

# BoxClever to be sold off

BoxClever is expected to be sold off to an investment company for some £350m. It was put into receivership late last year by its bankers, and had already made plans to close all its stores. The aim was to create a sustainable business then come out of receivership. This would involve improving the cash balance and reducing the customer termination rate. Endeva, which provides service backup (logistics, call-centre operation and servicing facilities), would remain part of the operation.

BoxClever was established in 2000 from the merger of the Radio Rentals and Granada rental businesses. At the time it had nearly 900 stores with a turnover of some £700m. By November 2001 the number of stores had fallen to 416, with increased use of call-centre facilities to deal with its 2.4m customers. The capacity of the call-centre facility at Bedford was being increased. By last November the number of stores had fallen to 180, with about 1.5m customers, a turnover for the year of £350m and a profit of £160m. There have been further store closures since then. It seems that the company is unable to service the loans its bankers have provided, including £748m from WestLB, a state-owned German bank

The business is being continued on a call-centre (phone and internet) only basis. There are also plans to consolidate all head office and call-centre operations at Bedford.

## **Digital TV report from Ofcom**

The Office of Communications (Ofcom) has issued its first report on the digital TV market. This replaces the ITC Multi-channel TV report and covers the last quarter of 2003. It reveals that by the end of 2003 digital TV penetration was estimated to have reached 50.2 per cent of UK households, an increase from 48 per cent at the end of the previous quarter. Sky's subscribers in the UK and Ireland rose to some 7,208,000 by the end of the year. while the number of Freeview households is estimated to have grown to about 2,996,700. In addition the latest estimates suggest that about 211,000 households use free-to-air digital satellite reception: this figure has fallen following the BBC's

### JVC launches wood-cone speaker



JVC's new micro component DVD audio/video system, Model EX-A1, features a loudspeaker system that uses a wooden cone (see accompanying photograph). The cone has long been a limiting factor in moving-coil loudspeaker design. The aims are stiffness with surround flexibility. In this respect wood is ideal, but has been difficult to use. JVC has solved the problem by using birch that's soaked in Japanese rice wine to enable it to be shaped and moulded without cracking.

### Manufacturing job losses

decision to end encryption and the with-

than 3.2m households now receive free-to-

The total number of cable TV sub-

ble at about 3.2m, of which some 2.3m

into account the number of households

that receive digital TV in more than one

quarter of 2003 15 per cent of Freeview

adaptors were bought by those who already had digital TV reception facilities

of one sort or another.

way. Ofcom estimates that during the last

scribers is estimated to have remained sta-

receive digital services with more switch-

An adjustment has been made to take

drawal of the solus card scheme. More

air digital signals.

ing over.

The manufacture of consumer electrical and electronic goods in the UK seems to be in steady decline. Samsung is to close its plant at Wynyard, Teeside with the loss of over 400 jobs. The plant was opened in 1995 and has been producing flat-screen monitors and microwave ovens. The company says that low international prices have made production in the UK uneconomic. A similar problem has led Matsushita to review the future of the Panasonic plant at Pentwyn near Cardiff, where top-ofthe-range TV sets, STBs and other products are assembled. It's likely that operations will be greatly reduced by the end of the year, with some 600 job losses. The plant was opened in 1997 and currently employs 1,700 people. Some operations, including R and D and laptop PC production, will continue. Others are likely to be transferred to Matsushita's plant at Pilzen in the Czech Republic.

### **Blue laser breakthrough**

There has been much reporting on the rival Blu-ray and HD DVD optical disc formats that could supersede the standard DVD system. They are based on the use of a blue- instead of a red-light laser. There is one big snag at present however: no one has discovered how to make blue lasers cheaply – at present sample blue lasers cost over £500 each.

Twenty or more companies around the world have been trying to use the molecular beam epitaxy (MBE) process used for CD and DVD lasers to produce blue lasers, so far without success. Current blue lasers are made using the much slower and more expensive metal organic chemical vapour deposition process. Researchers working at Sharp's advanced optoelectronics laboratory at Oxford however claim to have achieved a breakthrough in adapting MBE technology for blue laser production. The process involves the evaporation of pure metals on to sapphire in a vacuum at rigidly controlled temperatures, with a whiff of ammonia as a catalyst. Obviously they are not saying more! Sharp is now making every effort to get the process to work on a mass-production scale.

Sharp set up the laboratory at Oxford ten years ago.

### **DAB** news



Some 300,000 DAB radio sets were sold in the UK last year, an increase of 222 per cent. Dixons and Comet are both now selling more DAB than analogue radios. Bush and Philips have recently launched pocket DAB radio models. The Bush PSDAB2003 is expected to sell for about £99 and has the aerial concealed in its headphones. The Philips Model DA1000 (see accompanying photograph) weighs just 100g and also has FM band coverage. A signal-strength indicator is included for manual tuning, and up to twenty DAB and FM stations can be preset. The DA1000 has mains/battery operation: the two rechargeable AA batteries provide ten hours of operation after a charge.

### Top-Up TV

Top-Up TV, the newly-announced pay-TV service designed for digital terrestrial TV, is in dispute with the BBC over the position of its channels in the Freeview electronic programme guide (EPG). The service aims to offer DTT viewers an extra ten channels for a monthly subscription of £7.99. These channels will be UK Gold, Turner Classic Movies (TCM), E4, Boomerang, Cartoon Network, Bloomberg, UK Style, Discovery Channel, Discovery Home and Leisure UK Food.

The service plans to use ex-ITV/ONdigital STBs, as these have a smart-card reader – Top-Up TV estimates that about 400,000 of them are still in circulation. It needs some 250,000 subscribers to break even.

The cispute with the BBC has been referred to the regulator Ofcom. It revolves around Top-Up TV's wish to have its programmes listed alongside the Freeview channels by genre. The BBC however believes that a mixture of free-to-view and pay-TV channels could confuse viewers and would prefer to list the Top-Up TV channels at the bottom of the EPG, next to the digital radio channels.



Manufacturers worldwide use the annual Consumer Electronics Show to announce or launch major new products and developments. This year was noteworthy for increased participation by the IT industry. George Cole reports on the highlights of the show.

The International Consumer Electronics Show (CES) takes place each January in Las Vegas. This year's event attracted the major consumer electronics companies and computer giants such as Microsoft. Intel, Hewlett-Packard and Dell. Companies use CES to announce or launch major new products and developments: this year's event was no exception. It attracted some 129,000 visitors, and there were 2,400 or so exhibitors.

### **TV developments**

No surprises that there were many TV developments on show, including combiproducts. Panasonic was showing combination TV sets with a built-in DVD recorder. Models PV-27DR84 and PV-DR2714 combine flat-screen TVs with a DVD-RAM/R recorder. The sets use Panasonic's PureFlat CRT technology, with 27in. screens, and include a front AV input socket plus audio output and optical



Samsung's 80in. plasma TV with 1,920 x 1,080 resolution, capable of displaying high-definition images.

digital output sockets at the rear. The TV/DVD recorders will also play CD-R/RW, MP3 and WMA discs. Model PV-DR2714 also incorporates a VCR that includes hi-fi audio, VCR Plus and Auto Clock Set, and in addition has a built-in FM radio, an alarm clock with a timer function and Tower Remote Control.

The Philips LCD range includes 17 and 26in, models that use a flash-memory card to enable users to store and play back video, music and images.

At every electronics show the Korean companies Samsung and LG seem to battle it out to show the largest flat-panel displays. This year Samsung had an 80in. plasma TV with 1,920 x 1,080 resolution, capable of displaying high-definition images. The company also showed a prototype 52in. LCD TV set with a contrast ratio of 1,000:1. LG showed a 60in. widescreen plasma integrated HDTV, Model DU-60PY10, which has connections for a PC as well as high-definition component, DVI (Digital Video Interface) and standard AV inputs. The 50in. Model DU-50PZ60 includes picture-in-picture and picture-outside-picture display modes. LG's LCD TV range includes 42, 30, 23 and 17in. models. The 23in. widescreen model RU-23LZ has WXGA resolution (1,280 x 768 pixels) with a contrast ratio of 400:1, built-in stereo speakers and an NTSC tuner. The 17in. model has the same display specification, a built-in DVD player and a PC connection.

LG also showed a 60in. LCD rear-projection HDTV, Model TU-60SZ31, which has a built-in hard disk able to store up to thirteen hours of HDTV material. It has WXGA resolution and an integrated ATSC/digital tuner. Model DU-52SZ60D uses DLP (a digital light processing chip) to produce a 52in. rear-projection display with WXGA resolution and is cable ready. There were also 48 and 42in. rear-projection models, the latter with 3:2 pull-down cinema correction.

Panasonic showed no fewer than six new rear-projection HDTV sets with either 53 or 47in. displays. They all feature Panasonic's P3 (Precision Picture Processing) technology, which includes auto-convergence, a 540p progressive-scan doubler, a new motion-adaptive 3D digital comb filter, an HDMI (High Definition and Multimedia Interface) input with HDCP (High-bandwidth Digital Content Protection), new digital noise reduction and new sharpness and contrast circuits. Model PT-53TW54 has two tuners to provide a picture-in-picture split screen with a freeze mode and 3:2 pull-down. There are four AV inputs, one at the front, three S-video inputs, one in front, and the set provides 60W total audio output via a six-speaker system. There's also a 3D menu system.

Panasonic's new Viera flat-panel range consists of ten high- and enhanced-definition models with screen sizes from 14 to

50in. There are five plasma and five LCD models. The high-definition plasma models have 50, 42 and 37in. screens with a 3,000:1 contrast ratio. They are equipped with an ATSC tuner, an SD memory-card slot and an HDMI input, and can provide picture-in-picture displays. In addition the 50 and 42in. models have a PCMCIA slot. The two enhanced-definition plasma models, with 37 and 42in. screens, have an ATSC tuner, 4 000:1 contrast ratio, an HDMI input, 3:2 pull-down, two-tuner picture-in-picture capability and an SD memory-card slot. There are three LCD models with 14, 17 and 20in. 4:3 screens plus two models with 26 and 32in. widescreen HD (WXGA) displays. All models include a three-line digital comb filter. The HD models include an HDMI input and PCMCIA and SD memory-card slots.

Philips was showcasing its Ambilight technology, which has been developed in conjunction with Philips' research and lighting divisions. It is based on the light that's reflected from the back of the set on to the wall. Sensors determine how much light there is in the room and control the TV output accordingly: in a dark room there will be reduced light output while in a bright room the light output will increase. The Matchline 32, 37 and 42in. LCD FlatTV models and 42 and 50in. plasma FlatTV models incorporate this technology. They are high-definition TVmonitors that feature Philips' PixelPlus 2 technology with Digital Natural Motion and Flat NXT speakers. According to Philips PixelPlus 2 improves the colour reproduction and increases resolution and picture depth by up to thirty per cent. It works with any input signal, including terrestrial, cable and satellite broadcast signals, interlaced- and progressive-scan DVD inputs, DVB/MHP digital TV signals and HD transmissions.

### **CE/IT** convergence

The move from analogue to digital technology in the consumer electronics field has resulted in growing convergence between the IT/computer and CE industries. Little wonder then that IT companies had lots to show at this year's CES. Microsoft already has its software in most PCs, and sees the home PC as an increasingly serious challenger to the domestic TV set. Last year Microsoft launched Windows XP Media Center, a super-set of its Windows XP operating system designed for reproducing music, images and video with a home PC. A Media Center PC can be operated with a remote-control handset as well as a mouse and keyboard. This year Microsoft chairman Bill Gates announced Media Center Extender Technology, which will enable content stored on a PC – such as video, images and music - to be seen and heard almost anywhere in the home regardless of where the PC is located. Microsoft expects its Media Center

Extender Technology to be built into various products including TV sets, games consoles and set-top boxes.

Microsoft and Matsushita/Panasonic also used CES to announce that a raft of companies support their HighMAT (Highperformance Media Access Technology) standard. This is designed to improve interoperability for video, digital images and music between PCs and consumer devices that use storage systems such as CDs and DVDs. Panasonic plans to launch DVD players, DVD recorders, DVD Home Theatre systems and CD players that support the new standard.

Hewlett-Packard, Dell and Gateway showed flat-screen and high-definition TV sets, digital music players and cameras last year. A year after it launched a 42in. plasma TV set, Gateway has become one of the leading flat-screen brands in the US. Hewlett-Packard showed a 42in. plasma TV set and a 30in. LCD model, also a home-cinema projector. The TV sets are to be launched in the US this June. HP plans to introduce what it calls a Home Entertainment Hub, which serves as a central-storage server and access point for video, music and images. Dell had 23 and 30in. LCD sets on display. Both models include component video connections and are HDTV compatible.

'Intel Inside' usually refers to a microprocessor chip used in a PC. The semiconductor giant has now announced plans to produce chips that will provide flat-panel TV displays. It says that its technology will enable high-definition, large-screen TV sets, with clearer pictures than current systems, to be sold for less than the US equivalent of £1,600. The new rear-projection display system, code-named Cayley, is based on LCOS (Liquid Crystal on Silicon) technology. LCOS works by sandwiching a liquid-crystal layer between a glass cover and a highly-reflective, pixelpatterned mirror-like surface which sits on top of a silicon chip that provides digital modulation. Three such chips are required to modulate and reflect pure RGB light beams. Intel claims that its Cayley technology creates an extremely bright display. It plans to start delivering Cayley-based LCOS microdisplay devices during the second half of the year. A number of firms, including Chinese manufactures InFocus, TCL and Skyworth, and Primax PDC in Taiwan, are developing products based on prototype microdisplay devices from Intel.

One of the big differences between a TV set and a PC is that the latter takes some time to boot up, as drivers and files are loaded into the working memory from the hard disk. But InterVideo, a US company, has developed a software system that will turn on in an instant. The InstantON system uses a cut-down version of Linux called LinDVD, which is stored in a memory chip. Within ten seconds of switching on a PC the software is loaded and users The Philips Model HDRW770 is a combined harddisk (80GB) and DVD+RW recorder that includes 5.1channel Dolby Digital audio and a TV Guide Plus EPG.



can access DVDs, TV programmes, MP3 files, photo images and more. LinDVD can also be used for web surfing, email, chat and video conferencing. If InstantON PC users want to access Windows applications such as Word or Excel however they have to use a remote-control handset to switch off LinDVD and reboot in the Windows mode. Sharp plans to launch a portable PC that uses InstantOn technology.

Instantec Philco's NetVision is an internet TV that includes the Windows XP operating system and Windows Media Player. Digital Fidelity showed a hard-disk based hi-fi system that uses Windows XP. The Fujitsu-Siemens Activity 300 set-top box also uses Windows XP.

Apple Computer had a success with the introduction of its iPod mini audio player, which has a 4GB hard drive capable of storing up to 1,000 music tracks. Apple has licensed its iPod technology to Hewlett-Packard, which will be selling players and will also install iTunes music software in its PCs. Apple uses AAC (Advanced Audio Coding) for audio compression.

### **Blue-laser** optical discs

The rival Blu-ray and HD DVD camps were out in force at CES. Blu-ray is a high-definition, blue-laser optical disc format that's backed by most major consumer electronics companies including Sony, Philips, JVC, Panasonic, Pioneer and Sharp. Discs have been developed with a capacity of up to 27GB. PC companies Dell and Hewlett-Packard are now supporting the format, while film company Columbia Tristar plans to launch prerecorded Blu-ray discs in 2005/6. It believes that DVD sales will peak in 2005, after which the film and video industries will need a new format to maintain revenues.

The specification for the Blu-ray disc, called BD-ROM (Blu-ray Disc Read Only Memory), has been agreed. The specification for a write-only disc called BD-R is expected to be agreed this summer.

A Blu-ray rewritable disc (BD-RE) will come later. LG was one of a number of companies that showed Blu-ray hardware at CES: Model LGX8D420 combines a Blu-ray recorder with a hard-disk recorder – it's expected to go on sale in the US this autumn.

But Blu-ray is not an official format

approved by the DVD Forum which, instead, has given its approval to the HD DVD format developed by Toshiba and NEC. The two companies showed a prototype player that can play high-definition DVD discs and also standard DVD discs. The player has a single-lens optical head that integrates red and blue laser diodes, enabling it to read both types of disc. The HD DVD format is currently at version 0.9.

Toshiba maintains that an optical unit of this type provides the functionality, compactness and cost-effectiveness required for consumer HD DVD players, pointing out that it's more economical than a dual-lens head or dual optical heads. Toshiba has also developed an LSI chipset for HD DVD players. It consists of a servo controller, a data signal processor and an ATAPI interface (Attachment Packet Interface) – the latter enables a PC to control an optical disc drive.

A 12cm HD DVD disc can store over two hours of high-definition movie content. The dual-layer, single-sided read only version has a storage capacity of 30GB, while a single-layer, single-sided rewritable version has a 20GB capacity. A dual-layer, single-sided rewritable version with a capacity in excess of 32GB is under development.

Toshiba says that the HD DVD format has been designed to provide maximum compatibility with current DVD standards. It uses the same back-to-back bonding of two 0.6mm thick, 12cm diameter substrates. This enables manufactur-

ers of current DVD discs to use existing production equipment for the new discs. Toshiba also adds that the format is PCfriendly, because the discs don't need a cartridge. It's very impressive technology, but many wonder whether the strength of current Blu-ray support means that HD DVD will fail to achieve general acceptance.

### **DVD** equipment

There was also plenty of standard DVD equipment on show,

including DVD recorders. The Philips Model HDRW770 is a combined hard-disk (80GB) and DVD+RW recorder that includes 5.1-channel Dolby Digital audio and a TV Guide Plus EPG. Sony's DVD recorders cater for both the DVD+RW and DVD-RW formats. The new Sony range includes the entry-level Model RDR-GX300 which features Precision Cinema Progressive. This proprietary technology consists of several elements including a timebase corrector and pre-frame noise reduction and pre-video equaliser systems. Other new features include simultaneous recording and playback in the DVD-RW VR (Video Recording) mode. It is to sell in the US at the equivalent of about £350.

Panasonic's new DVD players all include Windows Media Player compatibility as standard and JPEG playback. They also have progressive-scan output sockets. Model DVD-F86 has a five-disc changer and can play DVD-Audio discs while Model DVD-SA97 also has an HDMI interface (High-Definition Multimedia Interface). The entry-level Model DVD-S27 sells in the US for the equivalent of about £55!

Toshiba's DVD/VCR combi Model SD-V595 also has an HDMI interface – this combines audio and video in a single digital interface for connection to a suitablyequipped TV set or STB. The LG Model LST-341GA has a 120GB hard-disk drive that can store up to 12.5 hours of HDTV programming, 82.5 hours of standard-definition digital programmes or 120 hours of analogue TV programmes.

Storage media

Toshiba showed an 0.85in. hard-disk drive (HDD) that can store up to 4GB of data. The company has already developed a 1.8in. HDD that's used in devices such as palmtop computers, notebook PCs, hand-held GPS units and digital audio players. Although the new drive will be only a

Sony had on show what it calls Location Free TV, a portable broadband LCD television system that can be carried and used virtually anywhere in the home. quarter the size of the 1.8in. one, it will have an initial storage capacity of 2-4GB. Toshiba expects the new drive to be used in a wide range of devices including mobile phones, digital camcorders and external storage units. It will be launched later this year.

Sony has developed Hi-MD (see Teletopics last month), which has five times (1GB) the storage capacity of a standard MiniDisc. Hi-MD technology enables users to record up to 45 hours of music compressed at 48kilobits/sec on one disc, with a transfer speed of up to a hundred times. Hi-MD Walkman recorders use a new codec (coder-decoder) called ATRAC3 plus, which provides music compression at 132, 105, 66, 64 or 48kilobits/sec. Hi-MD recorders can be connected to a PC via a USB cable for high-speed music transfer. When connected to a PC the Hi-MD recorder acts as an external drive, enabling users to transfer data files such as presentations, digital images and spreadsheets to the disc. Microsoft Word documents, PowerPoint presentations and JPEG images can be stored. The USB connection provides power, so there is no drain on the battery when the recorder is being used as a data-storage device. Hi-MD recorders include Models MZ-NH1, MZ-NH600D, MZ-NH900 and MZ-NH800 which includes a remote AM/FM/TV/Weather Band tuner. The discs are due to go on sale in the US this month (April) at the equivalent of about £5 each.

#### Wireless developments

A growing number of homes have wireless data networks that use IEEE 802.11 technology (known as WiFi), and most of these homes have a high-speed broadband internet connection. PC companies are keen to exploit this development with products that enable digital content stored in a PC to be made available around the home. Sony and Philips have been at the forefront of consumerelectronics companies that are also keen to use these technologies in their products.

Sony had on show what it calls Location Free TV, a portable broadband LCD television system that can be carried and used virtually anywhere in the home. It consists of a 12-1in. wireless touch-screen LCD monitor and a base station that incorporates a dualband wireless connection and high-speed Ethernet port for transmitting data. The system provides access to TV, video, web pages, streamed video, email and digital photos with no need for a PC. Sony says that it can also be used to control most majorbrand AV products in the home. Location Free TV is compatible with the IEEE 802 11a/b/g standards (b has a maximum data rate of 11Mbits/sec while the others run at up to 54Mbits/sec). The screen has SVGA resolution (800 x 600) and includes 3D Y/C



Sony's Hi-MD system has five times (1GB) the storage capacity of a standard MiniDisc.

separation circuitry for improved picture quality. Viewers can freeze and save a TV scene by using the monitor's capture button.

Wireless connection to the base station gives access to the web via a dedicated internet browser. By using an on-screen keyboard, users can use email, shop online and watch streamed media such as music videos and internet radio. By using built-in memory or Memory Stick cards, the device can display digital images as well as MPEG-1 files. The Location Free TV can be connected to a printer via the base station's USB port. A printer connected in this way can also accept print commands from a PC. The base station houses an NTSC tuner and a 56k modem, and has an Ethernet port and S-Video, USB and IR ports. The LCD monitor weighs less than 3kg and includes Ethernet and USB ports, a Memory Stick slot, a headphone jack. a keyboard port and an AV input for camcorder connection. Location Free TV is to go on sale later this year.

Sony also announced its wireless DVD Dream system, Model DAV-FR10W, which includes Sony's new DIAT (Digital Infrared Audio Transmission) technology. This transfers digital audio signals without compression, and transmits multichannel digital audio throughout a local area using infrared light as the carrier. It eliminates the need for wires to connect rear speakers. The new system includes a five-disc DVD/CD/SACD changer, and comes with four floor-standing speakers, a centre subwoofer, a six-channel digital amplifier and a tuner unit. It will be available in the US from September, at the equivalent of about £700.

Philips' Streamium Flat TV, Model 23PF99766, uses a WiFi wireless link and a wired Ethernet connection and can display content from a PC or via a broadband internet connection. The 23in. screen has WXGA (1,280 x 768) resolution. It can display streamed video in the MPEG-1 and MPEG-4 formats,

-----

can show JPEG images and play MP3 music files. It will go on sale in Europe this summer – no price details have been released.

Panasonic has adopted an alternative wireless system that operates in conjunction with Power Line Communication (PLC) technology. It provides broadband connectivity to every room in a house via

existing power lines, using adapters about the size of an audiocassette. Each adapter contains a power plug, a LAN connector and an LSI chipset that converts broadband data signals into signals that can travel via a power line. The adapters connect a broadband internet link to the power lines in the house.

Panasonic points out that while existing home networking technologies have their advantages some, like coaxial cable and Ethernet, may require installing new cables. With some wireless LANs it can be difficult to communicate between rooms, and security may be a problem. Panasonic's HD-PLC (high-definition ready high-speed PLC) technology is designed to overcome these problems. It is also resistant to interference from other signals, such as amateur radio. Panasonic has combined OFDM (Orthogonal Frequency Division Multiplexing) with Wavelet compression technology to reduce the noise caused by interference to a fifth of typical levels. Panasonic has also developed a new TDMA (Time **Division Multiple Access) specification** that provides efficient data transfer. By using TDMA technology, Panasonic says that HD-PLC enables devices connected to the adapters to exchange data, such as high-definition video content, PC files and audio data, at speeds up to 190Mbits/sec. Panasonic expects to launch PLC adapters for consumer and office use by the end of the year.





# WORKSHOP EQUIPMENT GUIDE

Eugene Trundle takes a look at what's good and what's new in the world of test gear and aids for bench and field servicing. Part 2 concentrates on some of the more recent technology we have to deal with, some ways of cost saving, aids and tools, and concludes with a 'contacts list' for the various items that have been mentioned.

Part 1 last month covered most of the basic workshop equipment, such as multimeters, oscilloscopes and component testers, also equipment for recep-

tion testing and setting up, safety testing, and equipment specific to TV and VCR needs. We'll kick off this month with soldering and rework equipment.

# AND REWORK

The increasing use of lead-free solder, the proliferation of surface-mounted assemblies and the ever-shrinking size of components, PCBs and modules has necessitated a rethink of soldering operations in the consumer-electronics workshop. The old soldering gun or heavymetal, hand-held job no longer cuts the mustard with the processor-based, submillimetre spaced assemblies we so often encounter in 2004!

But we still have to deal with power circuitry, where most problems arise, and much can be done with a good temperature-controlled soldering iron. They start from as little as £30, with the new N78AR type from Maplin: it's adjustable



The Leister Hot Jet from Welwyn Tools.

over the range 350-480°F, and a threepack of assorted bits is available to go with it. Several good temperatureadjustable irons are available at about the £85 mark. The Antex 660-TC for example is presettable from 65-450°C and can take a wide range of bits in the Antex 1100 range.

You generally have to go to about £200 for digital readout of the tip temperature. The Antex 50W SMT Rework kit is an excellent package that includes a range of bits - some shaped, branding-iron style, to suit various IC packages. I've got one, and it works well for me. Weller digitallycontrolled irons start at just under £200 with Model WSD81, which has a 50-450°C range, 80W capability and automatic tool recognition. Precision Model WSL comes at about the same price, with a lightweight handpiece, fast thermal recovery and a hot-tip change facility. For heavy soldering work there's Model WSD151, a 150W job. Industry rivals JBC and Pace have similar equipment at similar prices throughout the range. The Pace Model ST45-PS90 at £115 has digital readout and SensaTemp control. X-tronic is a new company in this field, with a range of value-for-money soldering irons, stations and tweezers, all available from CPC.

Soldering irons and tweezers are not enough when you regularly work with high-density, surface-mounted processor circuitry, typically in digiboxes and camcorders. For this you need a rework station that deals with all the pins of a complex chip at once. Several rival systems that use different techniques are available. The X-tronic 626 outfit is relatively inexpensive at £700: it uses hot air, with temperature and airflow controls, and comes with a single general-purpose nozzle –





other nozzles are available at prices from £30 to £130 however. Welwyn's Leister Hot Jet S at £260 also blasts out hot air, from a hand-held blower: this company has a range of products for SMD rework. Generally these workstations are priced at over £1.000. The JBC JT7000, which uses hot air and heat-shielding dishes, is £1,250; the Pace MBT2500 system, which uses iron bits and vacuum extraction, comes at £1,350. These are both well-established systems that have been reviewed in past issues of *Television*.

The ERSA rework station, which uses infra-red heating that can cope with the new BGA (ball-grid array) chips as well as conventional surface-mounted devices, is a relative newcomer. Critical-temperature under-board heating is required for BGA ICs. The ERSA IR500A combines this with surface heating, laser-positioning and vacuum device removal. It's an excellent tocl for the professional but is not cheap at £3,950, £4,650 with extras. It received a very favourable review in our October 2003 issue.

You have to be very committed to invest in these sorts of rework stations, and require a repair throughput that will provide a reasonable return on the investment. Not every service GP can justify such expense. But, with care, much can be done using more modest equipment, though some repairs may need to be farmed out – like replacement of the Painter chip in certain Philips TV models. For more on that, see the Help! section later.



PC monitors are generally much more than just a TV shorn of its tuner and fitted with a higher-definition tube, as the reports in our Monitors pages make clear. Their service and repair is largely a specialist business, which has to contend with the difficulty of getting service information and spares, also the economic problems of a market awash with good second-hand monitors and in the process of changeover to flat LCD screens.

Test-pattern generators for use with PC monitors are available from Ozan, which

supplies the Teletest PC at £170. It's a hand-held, battery-operated type that provides colour bars, greyscale, crosshatch and other patterns to VGA and SVGA specifications. There's a home-brewed alternative here, in the form of construction kits – see the DIY section later. We've already mentioned the

special monitor LOPT tester from HR. This is available from SEME at £73, the order code being EQU488.

Computer servicing involves two areas, software and hardware. In the software field Norton has a new version of SystemWorks at about £50. It has four components: a Go Back system to restore normality after a software crash: AntiVirus, a 'policing' system that works in the background continually to detect and eliminate bugs and worms; Utilities, which has the ability to detect and repair problems within the Windows operating system, including hard-drive problems; and CleanSweep, for backing up and restoring files and removing unwanted clutter downloaded from internet sites.

When problems arise in a PC's power supply there's nothing for it but the meter and an oscilloscope. Readers of Television, steeped in this sort of troubleshooting, should be able to cope with faults of this type without too much trouble. Hardware problems elsewhere in a PC can often be dealt with using a softwarebased diagnostic approach. Ultra-X has a range of tools and utilities under the generic name Quicktech. They are designed to track down faults in any IBMcompatible PC that's fitted with a processor from the 386 to the Pentium IV, and use 'friendly' drop-down menus, working when necessary from a self-booting program. There are four packages in the Ultra-X range, ranging in price from £134 through £280 and £311 to the top kit at £940. The latter includes a diagnostic



Above: the ERSA IR500A – the ultimate rework station? Left: A PC used as a virtual oscilloscope. This one is by Grundig. Below: A PC interface for 'virtual' measurement.

card, loopback plugs and other accessories.

Some horrible faults can assail a networked PC's external wiring and links. To deal with these Belkin supplies twisted-pair and coaxial cable testers at £60-£80, while Peak is now making a new type of network cable tester that sells at £100. CPC's product range includes several LAN and Ethernet network testers in hand-held form, ranging from £68 to £308 for the comprehensive Fluke MicroScanner Pro with length measurement and LCD readout.

### SOFTWARE AND PC-BASED DIAGNOSTICS

Problems with other equipment can often be traced, and maybe fixed, using a PC and specialised peripheral equipment. There has been much progress recently in the field of 'virtual' instruments, basically precision A-D converters with software that makes possible the display, mapping, analysis and storage of 'real' quantities like waveforms, voltage and current levels, etc.

The PC Multi Instrument, new from Tecstar, combines the functions of an oscilloscope, a spectrum analyser, RMS voltmeter, transient recorder and waveform generator. These functions can be used individually or in concert with the others. The PC screen display, simulating an oscilloscope screen with quantitative captions, can be expanded to full size for clear readout, and there's a full-colour printout facility. The hardware consists of a USB-linked box which is powered from the PC and has three BNC input sockets: two switched probes are provided. The data-acquisition system has sampling rates of 5, 25 or 50MHz, at £340, £570 and £620 respectively. These primarily govern the bandwidth of the dual-trace oscilloscope function, whose other features are 0·1-80V full height, 256k word memory, comprehensive (including TV) trigger modes, maximum 655ksec/div timebase and 50 times X magnification.

Pico has been in the virtual instrument business for many years and makes a wide range of products, none of which sports knobs, dials or buttons! The simplest, at about £70 and £90 respectively, are





# **D-GEN** A breakthrough in low cost pattern generators, 14 display outputs at 512\*288 resolution, including three full testcards of 4:3 and 16:9 ratios.





The Pico ADC-100 simulates a high-resolution, dual channel oscilloscope plus spectrum analyser and DMM when used with a PC.

Models ADC-40 and ADC-42. They come with operating software on disk and plug into a PC's parallel port.

Model ADC-100, at £215, simulates a high-resolution, dual-channel oscilloscope plus spectrum analyser and multimeter, with 12-bit sampling at 100ksamples/sec. The more sophisticated ADC200/212/216 sell at £290 to £450. At the top of the range there's Model ADC212/100 at £600. with a bandwidth of 50MHz, sampling at 5Gsamples/sec, 12-bit resolution and 1 per cent accuracy: the buffer size is 128k, capturing good signal detail.

Bus-diagnosis and chip-programming software like Sony's Trace system is very useful and time-saving but obviously brand-exclusive. If only there could be a 'universal' system of this type, suitable for all makes and models, with common software and operating protocols! Such a thing would require industry-wide cooperation, perhaps with the backing of Intellect and the IC manufacturers. One day, perhaps...

### DIY KITS

On several occasions in this guide I've mentioned build-it-yourself test equipment as an alternative way of obtaining what you need. Service technicians are certainly well qualified to undertake such projects: the skills, expertise, materials and tools required are all right there to hand! There was a time when self-assembled test gear was available commercially – many will no doubt remember Heathkit. Now the field is mainly confined to simple projects from the likes of Velleman: IR remote-control testers, fixed-tone signal generators and so on – more for the hobbyist than the service technician.

But parts kits for pattern generators have recently become available from CRH Electronics Design. and there have been many excellent constructional articles in past issues of Television: expertly designed, easy to understand and construct, and cheap at first cost. CRH's greatest triumph, for me anyway, is the brilliant D-GEN TV pattern and test-card generator which I reviewed in the February issue: £75 plus maybe four hours' enjoyable work gives you a full-blown, highly-featured instrument! CRH also provides kits for computer monitor testers, and simpler pattern generators, at £30 and £58 respectively. I'm sure that they are as good as the D-GEN I have here

Regarding *Television* magazine projects. the best one I've come across is Alan Willcox's capacitor ESR meter design published in the March and April 1999 issues. We've built two of them in the workshop and they see more use, and save us more time and money, than any other gadget we possess. The June 2003 issue included details of a good and effective PAT tester that can be built for about £50. There have been many others over the years, ranging from LOPT and remotezapper testers to an FM stereo-signal generator. For more details of publication dates and, if required, reprints, refer to the SoftCopy Ltd. Index and Directory panel on page 379 of this issue.

### SECOND-USER EQUIPMENT

Another possibility for cash-strapped service technicians is used equipment, often discarded by government departments and other public-sector or public-funded organisations or, more sadly, being disposed of by businesses that are being disbanded – there have been several for-sale advertisements relating to this in Television over the past couple of years.

I know of three suppliers of surplus test and diagnostic equipment, in many cases little used, at prices way below 'list': you may well have helped to pay for it at initial acquisition, so you should certainly not hesitate to snap it up second-hand!

Anchor Supplies, with premises in Nottingham, has a regularly-changing selection of test equipment and tools. As I write, though the situation may have changed by the time you read this, the company has LCD DMMs at £6.50, ones with a transistor test facility and leads at £10, the Beckman H110 type at £30, and Thandar bench models at £25.

Metrohm PAT testers are going for £60, and Megger 500V insulation testers for £35. Signal generators start at £35, oscilloscopes at £95. Amongst the scopes are the Tektronix modular storage types 7623A and 7623B at £500 and £550 respectively. Switchable  $\times 10/\times 100$  100MHz probes are available at £10, and temperature-controllable soldering irons with digital readout at just £38.



A laptop PC doubling as an oscilloscope

### WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES **DIGITISE YOUR** SLIDES



(using a video capture card)

"Liesgang diaty" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk ..£91.91+ vat = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA. 47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) ... £37.00 + vat = £43.48 30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole. ...£35.00 + vat = £41.13 40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses. £32.00 + vat = £37.60 Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle	£15	97 +	vat =	£18.76
VSL4022F 4mm F1.22 63x47 degrees viewing angle	£17	65 +	vat =	£20.74
VSL6022F 6mm F1.22 42x32 degrees viewing angle	£19	05 +	vat =	£22.38
VSL8020F 8mm F1.22 32x24 degrees viewing angle	£19	90 +	vat ≕	£23.38
Better quality C Mount lenses				

VSL1614F 16mm F1.6 30x24 degrees viewing angle.....

...£26.43 + vat = £31.06 VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle......£77.45 + vat = £91.00 1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat 1000 of 1 value £5.00 + vat

866 battery pack, originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite £7.46+vat = £8.77 easily



Please add 1.66 + vat = £1.95 postage & packing per order

#### JPG ELECTRONICS Shaws Row, Old Road, Chesterfield, S40 2RB Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch Callers welcome 9:30 a.m .to 5:30 p.m. Monday to Saturday



Email: info@digirepairs.co.uk

Why go anynere else for asonic in. 2

SPARES DIRECT

avaards.

PART

enory TELEVISION

3 KW 32802 Lookup C

Order

From phones to cameras, home cinema systems to DVD players, Panasonic brings ideas to life. If you service or repair any of our products, we can make your life easier too, thanks to the new Panasonic Spares Direct website.

Specially developed for smaller companies who only need parts or advice occasionally but still want genuine discounts on guaranteed spare parts, it's now open for business.

Register on the subscription-based site now and for just £24 for a year's access you'll find the most competitive prices, online technical information and repair manuals, special offers and immediate part number identification.

It's fast, it's easy, it's trouble-free and it's the only place you need to visit when you need to service or repair any Panasonic product.

So why call us for spares when you can now visit us 24 hours a day?

Visit www.panasonic-spares-direct.co.uk for more information.



Panasonic CS UK Willoughby Road, Bracknell, Berkshire, RG12 8FP

www.panasonic-spares-direct.co.uk

Stewart of Reading is very fond of oscilloscopes and, at the time of writing, has the Farnell DTV12-14 types, dual-trace with 12MHz bandwidth, at £75 and the Tektronix 2445. a 150MHz, four-channel model, at £425. Another £100 will buy you a Tektronix dual-trace digital storage Model 2232, with a bandwidth of 100MHz. In the bench power supply department the Farnell HPS3010 0-30V, 0-10A type is available at £140, and a 500VA mains-isolating transformer is going for a mere £40. Kenwood wow/flutter meters are for sale at £50, and highquality Fluke true-RMS 4<sup>1</sup>/<sub>2</sub>-digit DMMs for £95 used or £150 in as-new condition.

For audio technicians – and those tracking down the cause of rattles and resonances in TV cabinets! – there's the Farnell sine/squarewave oscillator covering 10Hz-1MHz at a bargain £75. And so on. But stock keeps changing – a check at the company's website is recommended.

Test Equipment Solutions operates at the high end of the second-user market. Bench power units starting at £85 and Philips 120MHz frequency timer/counter Models PM6670 and PM6673, at £350 and £395 respectively, may be of interest to the repair and service engineer. As with the other test-equipment firms mentioned here, TES has a wide and changing range of products on offer. Contact details are in the accompanying panel.

# SERVICE AIDS

The test equipment we've looked at so far will, hopefully, get you a diagnosis. The next step is repair and component replacement. For this you need a range of tools. jigs and 'consumables'. Before a large TV set gets as far as the bench however transport is necessary. This can be done safely, often single-handed, with the Liftmate, a two-wheel trolley with fork-lift or suction cups to support the set and a hand-winch to raise and lower it. The Dixon Telelift is similar. See the contacts panel for agents' phone numbers.

The range of service aids available today is so vast that a whole issue of *Television* could be filled with them. So I'll confine myself here to stuff that's new, things associated with the equipment described above, and others that I think you ought to know about! Chemtronics makes micro-tip applicators – plastic sticks with tiny lint-free buds – for cleaning CD and DVD opticalunit lenses and small, closely-spaced contacts in relays and leaf-switches. They cost £16.50 for fifty. Maplin's new PCB cleaner, code N64AN, at £2 for a 200ml can is another good cleansing agent.

Various service aids are required for soldering activities, and I can endorse Steve

Beeching's recommendation of the ChipQuick SMD removal kit (page 454. June 2003 issue), at a cost no less than is justified. I've found that Multicore 99C is a good type of lead-free solder for use on SM PCBs. It comes in 1.22 and 0.79mm diameters on 250 and 500g reels. Even in these small diameters it contains five cores of flux. There's now an ultra-skinny desoldering braid, with 0.65mm width, in the Servisol Solda-Mop range. for removing solder bridges at IC pins. I find that soldering flux spray dispensers are a bit too liberal for me and do best with a little bottle and brush: AID2067 from SEME contains 6ml in runny-liquid form and costs £4.

Still on the subject of surface-mounted components and their manipulation, Pro'sKit makes some excellent tweezers for use on tiny PCBs. There's a stainless-steel set of four (bent, straight, flat and reverseacting) for £4, and a pair with built-on magnifying glass (on a hinged arm) at about £7. A pair of 80mm tweezers from CPC (code TLO1209) at only £2 also incorporates a magnifying glass, this time a 3.5x one mounted at the back end.

Good illumination with built-in magnification is essential for servicing today's electronic equipment. The price of magnifying bench lamps has come down with the introduction by CPC of a new model, code LAO1331. It has a 22W circular fluorescent lamp, a spring-balanced articulated arm and a 3x dioptre lens – all for £30. In the higher price range CPC stocks a new range of Luxo illuminated magnifier lamps at prices from £110 to a whopping £332 for Model WAVE ESD, the last word in staticdissipative, specially made for the electronics industry, high-tech lamps with two 7W fluorescent light sources.

Kamasa makes a very good little multiangle table vice with a ball-swivel head. It's ideal for holding tuners and other small subassemblies, even PCBs, while they are being worked on. It is not expensive at £8, and does as well for me as similar clamps that cost three times as much or more.

CPC has a large, new range of batteryoperated drills that are suitable for those who mount dishes or terrestrial aerials on walls and chimney stacks. Drilling into brick and concrete calls for a lot of torque, staying power, as light weight as possible and a hammer action. These drills are not cheap, but there's no point in skimping when you do a lot of this work.

Suitable types are the Bosch 24V GBH24V and GBH24VRE at £349 and £299 respectively and the De Walt DW004K at £350. Prices are of course very much less for those who are prepared to drag a mains cable up the ladder.



The Dixon Telelift in action.



### HELP!

Difficult jobs are no less likely to come along because you are not prepared for them! The economics of a smaller workshop mean that it's simply not possible to purchase all the expensive tools and jigs that may be required, especially when they are unlikely to see much use. Although companies such as Test Equipment Solutions rent out their wares at so much a week, this is seldom relevant for the domestic-electronics repair technician. Sony agents are lucky in that they can take advantage of the company's free jig and tool loan scheme to facilitate the repair and alignment of equipment, mainly electro-mechanical, it has made.

That well-known service company MCES of Manchester can help with surface-mounted ICs, for example the troublesome Philips Painter chip. It will fit ICs such as this for a labour charge of £22. which includes return carriage, but responsibility for the diagnosis and selection of the appropriate replacement chip remains. of course. with their customer. Television readers will be aware of the presence of surface-mounted and ball-grid array chips in digiboxes: advertisers in Television can take care of digibox fault-diagnosis and repair, but the plummeting price of Freeview adaptors is, I fear, threatening the viability of all but the simplest repairs.

An SMD-reflow facility at MCES in Manchester

### Who's got the golden probe?

My Golden Probe award this year goes jointly to CRH Electronics Design of Stoke-on-Trent for those magical little self-build, value-for-money pattern generators; and to distributor CPC for the sheer volume and variety of test gear, tools and service aids it can supply.

There were no nominations for the booby prize this time. So my bag of duff components and weeping, smelly electrolytic capacitors will stay here for the present.



CRH Electronic Design, 43 Jonathan Road, Trentham, Stoke-on-Tent, Staffs ST4 8LP.

Website: www.videocomer.co.uk

### LOG OFF

The prices quoted in this guide have been rounded off and do not include VAT or carriage. Prices vary from one supplier/distributor to another.

Those I've quoted are typical, taken from catalogues and advertisements.

### Available from CPC

Available from Maplin

Available from CPC

01727 832 266

0115 986 4902

01304 502 100

ABI

ANTEX

BELKIN

ALBAN ELECTRONICS LTD

**ANCHOR SUPPLIES** 

AVO/MEGGER

BMR	Available from SEME
BOSCH	Available from CPC
BUROSCH	Available from CPC
CALTEK	Available from CPC
CELTEK	Available from CPC and SEME
CHEMTRONICS	Available from CPC and SEME
CHIPQUICK	Available from CPC
COASTAL AERIA	L SUPPLIES 01903 723 726 Sadelta and Perifelec
CPC PLC	08701 202 530
CRH CR 43 Jonat Stoke-on Website: ww	H Electronic Design, han Road, Trentham, h-Tent, Staffs ST4 8LP ww.videocorner.co.uk
DE WALT	Available from CPC
DIGISAT Av	ailable from Myersat 020 8520 7277
<b>DIXON TELELIFT</b>	08700 114 326
ELECTRONICS D	ESIGN SPECIALISTS Available from CPC
ERSA Ava	ailable from Blundell 0247 647 3003
FARNELL ELECTRO	ONIC COMPONENTS 0870 1200 200
FLUKE	Available from
Willow Val	e Electronics, Farnell
GRUNDIG	Available from

# CONTACTS

### HAMEG INSTRUMENTS LTD 01234 856 34

Also available from CPC, SEME and Willow Vale Electronics

IORIZON	020 8281 3777
HR	Available from SEME
NSTEK	Available from CPC and Maplin
BC	Available from Willow Vale Electronics
KASAMA	Available from CPC
KENWOOD	Available from CPC SEME and Vann Draper
ACUNA	Available from Coastal Aerial Supplies
LEDU	Available from CPC and SEME
LEISTER	Available from CPC and Welwyn
LEVELMETER	Available from CPC
LIFTMATE	01778 345 365
LUXO	Available from CPC
MAPLIN ELEC	CTRONICS
	0870 429 6000
MCES	0161 746 8037
MEGGER	Available from CPC and Farnell
METEX	Available from CPC and SEME
MULTICORE	Available from CPC and SEME
NORTON	Available from CPC
OZAN I	REECALL 0500 009 070
PACE	Available from CPC
PEAK	01298 70 012
PERIFELEC	Available from Coastal Aerial Supplies
PICO TECHN	OLOGY LTD 01480 396 395

Available from CPC

5	PRO'SKIT	Available from CPC and Farnell
	PROMAX	Available from Alban Electronics
E	ROBIN	Available from CPC and Maplin
C n	SEAWARD SEME and V	Available from CPC, Willow Vale Electronics
n	SEME LTD	01664 484 000
C	SERVISOL	Available from CPC and SEME
С	STEWART OF	READING
er	JILWART OF	01189 268 041
es	SWIRES RESEA	ARCH
С		01268 417 584
Е	TECSTAR	Available from CPC
С	TEKTRONIX	Available from CPC
'n	TELETEST FI	REECALL 0500 009 070
C	TELEVÉS	01633 875 821
5	TENMA	Available from CPC
C	TEST EQUIPM	IENT SOLUTIONS
0		01753 596 000
	THANDAR/TH	HURLBY
C	and	Available from CPC Willow Vale Electronics
C	ULTRA X	WWW.UXD.COM/ Available from CPC
CIE	VANN DRAPE	R ELECTRONICS 01283 704 706
C	VELLEMAN	Available from CPC and Maplin
C	WELLER	Available from CPC Farnell and SEME
m	WELWYN TO	OL COMPANY LTD 01707 331 111
es	WILLOW VAL	E ELECTRONICS LTD 0870 600 0271
	X-TRONIC	Available from CPC

## Television Repair / Mod Kits

Maxe S Mojel	Kot type	Code	Make S Model	KIT TYPE	GODE	Make 3 Model	kit type	SODE	Makie 3 Model	KUT VYPE	GOUE
	ALBA		GOOD	MANS.	eatinued	เมารย	BISHI	boutined		SAMSUN	g
14521	PSU	ONWAKIT	F16	PSU VIDEO	GOODKIT1	CT25A4STX		MITSKIT1	CI5944	FRAME	. SAMKIT2
1402	PSU	ONWAKIT	10	VIDEO .	GOODKITT	CT25AV1B	IDA 61765 Peli	MITSKITT	C16844	FRAME	SAMKIT2
1455T	PSU	ONWAKIT		RUNNON	G	CT25AV1BS	PSU	MITSKIT3	VIK320	PSU PSU	SAMSUNGKIT
1456T	PSU	ONWAKIT	CUC 2050		MODKIT48	CT25AV1BD	PSU	MITSKIT3	VIK350	PSU.	SAMSUNGKIT
1458T	PSU	. ONWAKIT	CUC 2051	PSU	MODKIT48	CT25AV1BDS	PSU		VI375	PSU.	SAMSUNGKIT
1459T	PSU	ONWAKIT	CUC 2058		MODKIT48	CT28AV1B	PSU	MITSKIT3	VI395	PSU	SAMSUNGKIT
1499Y	STANDBY	MODKIT37	CUC 2059		MODKIT48	CT28AX1BD	PSU .	MITSKIT3	WINNER 1	PSU	SAMSUNGKIT
145LTA	STANDBY	MODKIT37	CUC 2080	PSU	MODKIT48	CT28AV1BDS.	TDA 84785	MITSKIT3		A11110	
2002	PSU	ONWAKIT	CUC 7301/3		GRUNDIGKITT	CT29A51	TDA 81785	MITSKITZ		JULANSP	1
2009B	PSU	ONWAKIT	(BUZ90)	PSU	GRUNDIGKIT2	CT29A6.	TDA 81785	MITSKIT2	51CS03H	PSU.	SHARPKIT1
2052T	PSU .	ONWAKIT	CUC 7301/3			CT29B2	TDA 81785	MITSKIT2	56EW53H	PSU.	SHARPKITT
2152T	. PSU	ONWAKIT	(MJF18004)	PSU	GRUNDIGKIT3	CT29B3	TDA 8178S	MITSKIT2	59CS03H	PSU	SHARPKIT2
2099TX	STANDBY .	MODKIT37				CT29B6.		MITSKIT2	59CS05H	PSU.	SHARPKIT2
BTV17	STANDBY	.MODKIT37		HINAR	7	CT33B3	TDA 8178S	MITSKIT2	59CSD8H	PSU.	SHARPKIT2
CTV501	PSU .	ONWAKIT	HIT14RC	PSU	ONWAKIT	M5 SERIES	PSU	MITSKIT3	59DS03H	PSU	SHARPKIT3
CTV/01	PSU .	ONWAKIT				DA	232 1313232	10	59FW53H	PSU & EW	MODKIT49
CTV840	PSU .	ONWAKIT		JYG		NJ.	ALL LULUULE	70	66CS03H	PSU.	SHARPKIT2
CTV485	PSU	ONWAKIT	AV29SX1EK	FIELD O/P	JVCKIT1	CE25 CHASSIS	PSU	NIKKAIKIT1	66CS05H	PSU.	SHARPKIT2
			AV29SX1EN	FIELD O/P	JVCKIT1		PSU.		66CSD8H	PSU.	SHARPKIT2
	ARAL		AV29SX1EN1	FIELD O/P	JVCKIT1	CZOF4TPAN	F30	NINNAINTT	66EW53H	PSU & DULBY	MODKIT45
CT1417	PSU		AV29SX1PF	FIELD O/P	JVCKIT1	DA	MASOM	2	66EW54H	PSU & DOLBY	MODKIT49
CT2159U	PSU .	ONWAKIT	AV29TSIE1		JVCKIT1	UC561	TDA 8175	PANKITA	66FW54H	PSU & EW	MODKIT49
CT2162UNT	PSU	ONWAKIT	C14E1EK	PSU	ONWAKIT	TX25XD60	VERT OUTPUT	PANKIT2	76FW53H	PSU & DOLBY	MODKIT45
CT2863UNT		ONWAKIT	C21ET1EK	PSU	ONWAKIT	TC28XD60	VERT OUTPUT	PANKIT2	76FW53H		MODKIT49
7.000.0000			CS21M3EK	PSU	ONWAKIT	TX28XD70	VERT OUTPUT.	PANKIT2	76FW54H	PSU & DOLBY	MODKIT45
13	SGATAT	ung				TX29XD70	VERT OUTPUT		76FW54H	PSU & EW	MODKIT49
F SERIES	PSU	MODKIT30		MATSO	7	TX-W26D3	VERT OUTPUT.	PAN <mark>KIT2</mark>	DA-100 CHA	SSIS PSU & EW	MODKIT49
TVC563	STANDBY	MODKIT37	1455	PSU	ONWAKIT					(D) (D) VI VI	
			1496R/T (H3N90	)PSU	MODKIT43	4	PHILIPS		AL	SONY	
(	GOLDSTA	LK	1496R/T (BUZ90	)PSU	MODKIT44	310.10708		.PHILKIT3	SLV715HB	VCR - PSU	MODKIT40
CF25A50F	FRAME	MODKIT36	1498	PSU	ONWAKIT	310 20491		PHILKIT2	SLV///UB	VCR - PSU	MODKI140
CE28A50E	FRAME .	MODKIT35	2086	PSU	ONWAKIT	310.20496		PHILKIT10		52147(0)111.200.2	vr I
CF28C22F	FRAME	MODKIT36	2096R/T (H3N90	)PSU	MODKIT43	310.31994		PHILKITS	25020400	I RIGHIGIA I	J
CF28C28F	FRAME	MODKIT36	2096R/1 (BUZ90	). PSU	MODKIT44	310 32252		PHILKITA	35065920		
CF29C42F	FRAME	MODKIT35	21V1N (BUZ90)	PSU	GPUNDICKIT2	310.32254		PHILKITS	EV70	PSU	THORNKITT
			21V1T(MJF1800	4) PSU	GRUNDIGKIT3	310.32255		PHILKIT7	ICC7 CHASS	IS TDA 8178FS	THOMKIT
C	SOODWAN	13	TVR180R/208	STANDBY	MODKIT37	310 32262			ICC7 CHASS	IS FRAME	THOMKIT3
147TT	PSU	ONWAKIT	TVR185T	STANDBY	MODKIT39	310.62264		PHILKIT1	ICC8 CHASS	IS TDA 8178FS	THOMKIT1
149T	PSU	ONWAKIT				ANUBIS A	SOPS	PHILKIT2	ICC8 CHASS	IS FRAME	THOMKIT3
1430RA	PSU .	ONWAKIT	UXUU	TSUBIS	3は10	CP110 CHASSIS	SOPS .	PHILKIT8	ICC9 CHASS	SIS EAST/WEST	THOMKI14
1430RS	PSU	ONWAKIT	AV1 SERIES	PSU	MITSKIT3	GOOR CHASSIS	SOPS	PHILKIT10	ICC17 CHAS	SIS PSU.	MODKI141
1430RW	PSU	ONWAKIT	CT1M5B	PSU	MITSKIT3	G110 CHASSIS	SOPS	PHILKIT3	R3000	PSU	THOMKIT2
1455TS	PSU	ONWAKIT	CT26M6PT	PSU	MITSKIT3	GR2 1 CHASSIS	SOPS	PHILKIT1	R4000	. PSU	THOMKIT2
2019R	PSU	ONWAKIT	CT21A2STX	TDA 8178S	MITSKITS	GR2.2 CHASSIS	SOPS	PHILKIT1	TX92F CHAS	SIS EAST/WEST	THOMKIT4
2029T	PSU	ONWAKIT	CT21AX1B	PSU	MITSKIT3	D-16 CHASSIS	SOPS	PHILKIT6			
2029TA		ONWAKIT	CT21A3STX	TDA 8178S.	MITSKIT1	HSM VIDEO	SOPS	PHILKIT5			1
COMPACT 11		MODKIT47	CT21AV1BS	PSU	MITSKIT3	JSM VIDEO.	SOPS	PHILKITA			- 1
F16 CHASSIS	FRAME	GOODKIT1	CT25A2STX		MITSKIT1	L SM VIDEO	SOPS	PHILKIT7			
FIO CHASSIS	LINE	GOODKITT	CT25A3STX	TDA 8178S.	MITSKIT1			COLOR FOR LIVER	1		1
( ) ) ( ) ( ) ( ) ( ) ( ) ( ) ( ) ( ) (	000		L								
Orden g	sode prug	e   orde	k code i	Pruge 0	rder cod	e price	ORDER C	ode pl	rice ol	rder sode	Price
GOODKIT	1£ 11	.00 MODK	IT35	£ 9.50 N	ODKIT46	£ 12.00	PHILKIT2		£ 2.50 SA	MKIT2	£ 8.00
GRUNDIG	KIT1£ 10 KIT2 £ 10	50 MODK	T36	£ 5.00 N	ODKIT47	£ 15.50	PHILKIT3		£ 4.00 SA	MSUNGKIT	£ 16.00
GRUNDIG	KIT3£ 10	.50 MODK	T39	£ 8.50 M	ODKIT48	F 13 00	PHILKIT4		£ 4.25 SP	ARPKIT1	£ 11.00
JVCKIT1	£ 11	.00 MODK	T40	£ 6.00 N	IKKAIKIT1	£ 12.00	PHILKIT6		£ 5.50 SH	ARPKIT3	£ 9.00
MITSKIT1	£3	.00 MODK	T41	£ 6.00 0	NWAKIT	£ 12.00	PHILKIT7	••••••	£ 7.60 TH	IOMKIT1	£ 7.00
MITSKIT3	£ 6	.00 MODK	T43	£ 7 00 P	ANKIT1	£ 15.00	PHILKITS	•••••••••••••••••••••••••••••••••••••••	£ 4.25 TH	10MKIT2	£ 12.00
MODKIT30	0£ 10	.00 MODK	T45	£ 4.00 P	HILKIT1	£ 10.00	PHILKIT10	·	£ 8.50 TH	IOMKIT4	£ 4.00
	N a	WY AT	1เลยโรง	77			Ne	M A	1=12 1915	1 12	
		45 01	1						0000	0 50	
P	niips LU1.	TE Chas	ssis PSU	Kepair I	<u> (/t</u>	Ve:	stel 11AM	Cia Cha	ssis PS	U Repair N	Kit 👔
Fits the	following m	odels .				Fits the fr	llowing	ande			
						ins the IC					
							Bush, Go	oodman	, Hitachi	, Ioshiba	
2	8PT4457/05	, 28PW5	407/05,28	PW6006/	05	Model	Is BD2851	S, BD29	51S, BD	2581S, BD32	251S
										,	
	Orde	er Code	: MODKIT	50			Orde	r Code	: MODK	<b>(IT</b> 51	
	Pr	ice : f 1	8.00 + 42	t			Dri	Ce + £ 1	0.00 +	vat	
_				-		L	rn	UCILI	0.00 +	* 61 6	
X	P. Hanse	Umit 18	Poin In Con	າກາອກອາກ	Comira 9	CONTRACTOR	Wanalal	Middles			
				LEVE VENUER	0000000000000	6 Generality	ananona a l	annas anas	Shall a utility		ud 21
Tel:	: (929) 39	990 232	5	• ax : ((0	20) 890	3 5125	Ema	ail : sa	ISS OG	rar data.c	o uk

### **Digital Satellite Accessories**



distributor of electronic components

### 105°c Electrolytic Capacitors

VALUE CODE PRICE PER	VALUE	Code price p	ER	VALU	e cod	e price	PER	VALU	E CODI	PRI	GEPER	VALU	ECODI	PRICE	PER
Pack		P	agk				Pack				Pack				Pack
6.3 Valta	26 N	/กกรลงการการการ	1	R	n Malla	aanodimaa	and land	00	0 1/2 /00	(BALIE)	Manana A	90	(a) Way/khan	a a ta Man	mad
220uF CAP163£0.70	1000uFC	CAP46£3.65	10	100uF	CAP66	F0 85	10	2 2uF	CAP94	F0 51	5	33UE	CAP206	6175	BOOD 6
470uFCAP164£0.80	1500uFC	CAP47£3.90		220uF	CAP67	£1.75	10	3.3uE	CAP95	£0.50	5	47uE	CAP106	£4 35	10
	2200uFC	CAP48£2.00		330uF	CAP68	£2.45	10	4.7uF	CAP96	£0.50	5	100uF	CAP154	£4.50	5
10 Volts	3300uFC	CAP49£2.20	2	470uF	CAP69	£4.35		6.8uF	.CAP187	£0.80		220uF	CAP155	£2.00	2
100uFCAP118£0 45	4700uFC	CAP50£3.65		680uF	CAP70	£4.90		10uF	CAP97 .	£0.95		330uF	CAP206.	£2.50	1
220uF CAP165£1.00	6800uFC	CAP51£3.90	2	1000uF	CAP71 .	£5.25	10	22uF	CAP98 .	£1.05		11			
470uFCAP29£1.20				1500uF	CAP143.	£4.50	5	33uF	CAP99 .	£1.55			360	Volta	
680uFCAP166£1.20 10		35 Vons		2200uF	CAP72	<mark>£3</mark> .25	2	47uF	CAP100.	£1.75	10	1uF	CAP156.	£0.70	10
1000uFCAP119£1.50	1uFC	AP130£0.40	10	3300uF	CAP144.	£3.25		68uF	CAP188.	£1.30		2.2uF	CAP207.	£1.20	10
2200uFCAP120£2.10	3.3uFC	AP131£0.40	10					100uF	CAP101.	£2.10	10	3.3uF	CAP157.	£1.50	10
3300uFCAP167£1.60	4.7uFC	AP132£0.45	10		CĐ	Volta		220uF	CAP102.	£6.00	5	4.7uF	CAP208.	£1.10	5
10.00.01	10uFC	AP52£0.50	10	0.22uF.	CAP145.	£0 45	10	330uF	CAP189.	£3.00.		10uF	CAP158.	£2.25	10
10 VOVA3	22uFC	CAP53£0.45	10	0.33uF.	CAP178.	£0.35	<mark>.</mark> 10	470uF	CAP103.	£6.00		22uF	CAP159.	£3.40	10
220FCAP121£0.35	33uFC	AP54£0.50	5	0.47uF	CAP73 .	<mark>£0.3</mark> 5	10	680uF	CAP190.	£3.00.		33uF	CAP209.	£2.60	5
330FCAP122 £0.35	47uFC	AP55£0.85	10	1uF	CAP74 .	£0.35	10	1000uF	CAP191	£3.00.		47uF	CAP210.	£1.50	2
1470FCAP123£0.3510	680FCi	AP133£0.55	10	1.5uF	CAP179.	£0.35						100uF	CAP211.	£3.00	2
1000FCAP124£0.60	1000FC	AP56£0.85	10	2.2uF	CAP75 .	£0.35	10		160	Volta		330uF	CAP212.	£5.00	1
220 E CAP125 CO 80 40	1500FC	AP57£0.95	5	3.3uF	CAP76 .	£0.50	10	0.47uF.	CAP192.	£0.45.					
2200FCAP125£0.80	22005	AP58£1.45	5	4.70F	CAP77 .	£0.35	10	1uF	CAP193	£0.45.			400	Volks	
470 E CAP31 61 75 10	470 F	AP134£1.60	10	0.8uF	CAP180.	£0.50	10	2.2uF	CAP146.	£0.45.		0.47uF.	CAP213.	£0.60	10
680uE CAP32 £2.10 6	6800E	AP13021.70	10	1005	CAP78 .	£0.50	10	3.30F	CAP194.	£1.00.		1uF	CAP107	£2.15	5
1000uF CAP33 \$2.10 10	1000uFC	AP 39 20.30	10	15UF	CAP79 .			4.7uF	CAP195	£1.00.		2.2uF	CAP108.	£2.25	
1200uF CAP169 £1.50 5	1500uF	AP173 64.00		2205	CAD91	£0.75	10	100F	CAP 147			3.30F	CAP214.	£2.25	5
1500uE_CAP170_£1.505	2200UE C	AP61 \$2.45	2	4705	CAD92	CO 05	10	2205	CAD140			4.7UF	CAP109.	£3.15	5
2200uE CAP34 £5.25 10	3300uF C	AP62 £10.00	6	56uE	CAD191	£1.10	10	17UE	CAD106	£2.30.		100F	CAP110		
3300uF CAP35 £5.00 5	4700uE C	AP136 63.50	2	68uF	CAD83	£1 30		1000E	CAP150.	62.20	5	22UF	CAP111.	£2.50	
4700uF CAP36 £6.10 10		100		100uF	CAPRA	£1 20	10	22005	CAP107	63.00		33UF	CAP215		
6800uFCAP171£4.50		AO Valka		150uF	CAP85	£2 80		470uF	CAP198	£3.04.	1	68UE	CAP216	£3.50	
	2200uFC/	AP174 £1.80	2	220uF	CAP86	£2 80	10	47001			·······	100uF	CAP160	EA 00	2
26 Volta	2200uFC/	AP175 £2.00	1	330uF	CAP87	£4 00	10		200	Valla	I	150uF	CAP217	£3.20	
10uFCAP37£0.45				470uF	CAP88	£5.25	10	22uE	CAP199	£1.60	5	220UE	CAP161	£7.00	2
15uFCAP172£0.45		SO Volta		680uF	CAP89	£5.00	10	100uF	CAP151	£3.25	5	560uF	CAP162	£4.00	1
22uFCAP38£0.45	0.47uFC/	AP176. £0.35	10	1000uF	CAP90	£5.40		220uF	CAP200	£2.50	1				
33uFCAP126£0.40	1uFC/	AP137 £0.35	10	2200uF	.CAP182	£2.20		330uF	CAP201	£2.50	1		<u>A</u> BA	Makka	
47uFCAP39£0.48	2.2uFC/	AP138£0.35	10	4700uF	CAP183.	£4.00						1uE	CAP113	£2.80	5
68uFCAP127£0.55	3.3uFC/	AP139£0.35	10						260	Volta		2.2uF	CAP114	£3.20	5
100uFCAP40£0 70	4.7uFC/	AP140£0.35	10		100	Volta		0.47uF	.CAP202.	£0.60).		3.3uF	.CAP218.	£3.20	5
120uFCAP128£0.8510	6.8uFCA	AP177£0.45	10	0.1uF	CAP184	£0.80	10	1uF	.CAP152.	£0.60.		4.7uF	CAP115.	£4.95	
150uFCAP41£0.95	10uFC	AP63£0.50	10	0.22uF	CAP185.	£0.80	10	2.2uF	.CAP203.	.£1.30.		10uF	.CAP116.	.£5.50	5
220uFCAP42£1.2010	22uFC	AP64£0.70	10	0.33uF	CAP186.	£0.80	10	3.3uF	.CAP104	.£1.75.	10	22uF	CAP117	.£4.15	
330uFCAP43£1.405	33uFC/	AP141£0.85	10	0.47uF .	CAP91 .	£0.50	5	4.7uF	CAP204	£2.00.	10	33uF	CAP219	.£3.00	2
470uFCAP44£1.90	47uFC	AP65£0.85	10	1uF	CAP92 .	£0.85	10	10uF	CAP105	.£2.60	10	47uF	.CAP220	.£2.00	1
680uFCAP45£3.155	68uFCA	AP142£0.90	10	1.5uF	CAP93 .	£0.70	5	22uF	CAP153	£2.30	10	100uF	.CAP221	.£3.00	1
			- 1								_				

## Aerial & Satellite Installation Accessories

	SLx Aprial	Amplifiers		SLx Masthead Amplifiers
Now with built in Dig	gital ByPass Operate	es with Sky™ DigiEye		UHF TV antenna pre amplifier designed for the professional aerial installer
Class leading noise	figure of 4dB or less		-	15dB gain masthead amplifier ideal for majority of domestic installations
6dB signal amplifica	tion on all models		a la la	26dB gain masthead amplifier for longer cable runs (loss of more than 3dB) or if connected to passive splitters
Description	Order Code	Price	0	Requires 12V DC power supply via downlead either via
2 Way - No Bypass	SLX2	£ 8.00 + vat	1	dedicated power supply unit or from a distribution ampli-
2 Way - with Bypass	SLX2B	£ 9.25 + vat		tier with I ne powering
4 Way - No Bypass	SLX4	£ 13.00 + vat	bot	15dB Amp Order Code : 27830R Price : f 4 30 + vat
4 Way - With Bypass	SLX4B	£ 14.00 + vat	regrater	26dB Amp Order Code : 27924B
6 Way - No Bypass	SLX6	£ 18.00 + vat	Integitar	Price : £ 4.50 + vat
6 Way - With Bypass	SLX6B	£ 19.00 + vat	By Pas	SLx Masthead Amp PSU
8 Way - No Bypass	SLX8	£ 18.50 + vat		Order Code : 27832R
8 Way - With Bypass	SLX8B	£ 20.00 + vat		Price : £ 5.00 + vat
				Postage for 2+ £ 5.00 + Vat
Soax Plug	Screw Type	TWISE OD	SL	x Satellite Finder
	8600 PU138	r connectors	Allows the user to find the best a	izimuth / elevation settings for a
	1		satellite dish , resulting in the be	st signal reception / picture and a second
			Compact	design
Under Code : PLG51	Order Code : PLG62	Under Code : PLG101	Backlit me Audible signal si	trength reading
Price : £ 1.25 + vat	Price : £ 1.60 + vat	Price : £ 1.00 + vat	Adjustable le	avel control
Bag of 100	Bag of 100	Bag of 100	Frequency Range	: 950 - 2250Mhz
Price : £ 9.00 + vat	Price: £12.50 + vat	Price : £ 6.00 + vat	Order Code : 2	7860R Price : £ 10.00 + vat
			-	

distributor of electronic components

## Konig Replacement Remote Controls

Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code
AKAL		EERGUSON contin	ued	HITACHIcontin	ued	NOKIA		PHILIPScontinu	ued	SHARP contin	ued	TOSHIBA	continued
CT2582E	IR9700	68LS2	IR9639	C24WS511T	IR9983	3126	IR9157	RC9020	IR9434	RRMCG0662PESA.	IR9487	1480RBW	
CT2585 CT2885	IR9700	A10R A14R	IR9259	C2514 C2546	IR9677	C1	IR9161	RC9050	IR9556	RRMCG0777PESA	IR9487	1480TBT	IR9953
CT2/85E	IR9700	A36R	1R9259	C2546TN C2547TN	IR9677	C2 C3	IR9161	RC9057 . RC9060	IR9710	RRMCG0898CESA.	IR9487	1480TBY	IR9953
RC556	IR9397	B51NX	IR9639	C2556TN	IR9983	C4	IR9161	RC9070	IR9434 IR9710	RRMCG1014BM5A RRMCG1023BM5A	. IR9711	1480TBZ	IR9953
RC85	189700	B59F B59N	IR9639	C2567TN	IR9983	D1	IR9161	0.4400.000	-	RRMCG1031BM5A	IR9788	1510RDT	.IR9962
AMSTRAD	IRASA	B59NX B68F	IR9639	C2567TN2 C2586TN	IR9983 IR9983	D2	IR9161	CX5312W	IR9432	RRMCG1046BM5A	IR9788	155R9B	
SRX510	IR9386	B68NX	IR9639	C2t 59H	IR9142	E2 EM2	IR9161	CX5325W	IR9432 IR9432	RRMCG1048BM5A RRMCG1050BM5A	IR9788	155R9B1 155R9BW	IR9962
AE6001	IR9352	C68NX	IR9639	C2661 .	IR9142	ES5	IR9701	CX534WT	IR9432	RRMCG2799CESA	IR9487	155R9BZ	IR9962
Beolink 100	IR9843	D51ND D59F	IR9639	C2846TN C2847TN	IR9677 IR9677	FS10 FS11	IR9573	RM109	IR9546	SV2044S	IR9487	156R9B	IR9962
		D59N.	IR9639	C2856TN	IR9983	FS4/1	IR9573	SANYO		SV2145G SV2145S	IR9487	156R9BG	
RC51321	IR9398	D78N	IR9639	C2866TN	IR9983	FS5	IR9506	4AA4U1T0092	IR9459	SV2577S	IR9487 IR9487	1720RB	
RC51331 RC61331	IR9398	E51N E59R8.	IR9639	C28W410TN C28W510TN	IR9983	FS9	IR9573	JXCL	IR9530	SV2877S	. IR9487	1732TD	IR9852
		RCU1734	IR9584	CBP1476R CBP1646R	IR9142	FS9	IR9573	JXCR	IR9530 IR9457	SV28//S1	189487	2100RBG	
8669493	IR9188	RCU1785	IR9594	CBP2067	iR9142	IRC2	IR9157	JXGA	IR9139	RM604	IR9974	2100RBT	
1532	IR9503 IR9516	RCU1789 RH880	IR9594	CBP2216 CBP222	IR9142	IRS1	IR9535	JXGT	IR9460	RM607	IR9974	2102RBZ	IR9962
8627 105 463	IR9188	RH885	IR9325	CBP226 CBP260	IR9142	IRS2 IRS3	IR9535 IR9535	JXGW JXGY	IR9460	RM615	IR9511	2132DB.	IR9852
1555-46	IR9516	RHT10	IR9639	CL2156TAN	IR9983	RCN610	(R9752	JXLB	IR9460	RM620 RM625	IR9511	2140RB 2140TB	IR9852
1563-46 IB16	IR9516 IR9504	RHT30 T49F	IR9259	CL2556TAN	IR9983	RCN624	IR9757	RC238	IR9974	RM630	IR9511	2141TB	IR9852
IC16	IR9504	T49N	IR9639	CL2586TAN CL2856TAN	IR9983	SM1	IR9491 IR9491	RC254 RC258	IR9530	RM632	.IR9511	2145DD	IR9852
IL32	IR9503	T51N	IR9639	CL2886TAN	IR9983	DAMASONIC		RC305 RC307	IR9974	RM633. RM634	.IR9511	2150TD	IR9953
IM32 IM55-16	IR950.3 IR9516	159F T59N	IR9639	CL28WTTAN CL28WD2TAN	IR9983	02280227	IR9835	RC308	IR9457	RM635.	IR9511	2152DD.	IR9953
IM63-16	IR9516	T68N	IR9639	CL 32WD2TAN	IR9983	91005926 EUR50100	IR9835 . IR9826	RC317 RC318	IR9457 IR9457	RM641	IR9321	2163DB	IR9953
1P32	IR9503	1752	IR9584	CLE871B	IR9602	EUR51920	IR9835	RC321 RC612	IR9457	RM641A RM650	IR9321	2163DB	
IQ16 IR32	IR9504 IR9504	1758 T789	IR9584	CLE874B	IR9602	IR3592	IR9826	RC625.	IR9457	RM651	IR9336	216R9B2	
TC106	IR9406	T78DPL	IR9639	CLE876 . CLE876C	IR9476	TC1485DR TC14S1R	IR9826	RC628. RC6=2	IR9457	RM654	IR9336	2180TD	IR9953
TC143	IR9406	GOLDSTAR		CLE876D	IR9477	TC150E	IR9562	RC645	IR9974	RM656	IR9448	2181TB	IR9852
TC144 TC190	IR9406 IR9529	105-068 105209B	IR9403 IR9862	CLE902A	IR9477 IR9677	TC1785DRS	IR9826	RC700	IR9139	RM658	IR9321	219R	IR9962
TC192	IR9529	105210A 105-219J	IR9862 IR9854	CLE902B CLE903A	IR9677	TC1785IR TC1785UR	IR9826	RC710	IR9139	RM670	IR9123	219R9B2	IR9962
10194	1113323	105-224V	IR9854	CLE921A	IR9983	TC2185DRS	IR9826	RC711 RC901	IR9460 IR9139	RM671 RM672	IR9123	2522DB	
RC51331	1R9398	105230A	IR9862	CLE922A	IR9482	TC21R1C	IR9826	S02	IR9460	RM673	IR9123	2527DB	
RC61331	IR9398 IR9397	105-230C 38T1	IR9854 IR9854	CLE922B CLR876E	IR9982 IR9477	TC21S1R	IR9834	503	113-00	RM681	IR9442	2535DD	IR9852
DAEWOO		CB20E40X	1R9854	CP 146TA CP2546	IR9677	TCC23PFR TNQ1410	IR9826 IR9826	37AM12S	IR9788	RM682 RM683	IR9442	2545DB	IR9852
DMQ1414	IR9397	CBT4902	IR9403	CP2546TA	IR9677	TNQ8E0421	IR9826	51AM12S	IR9788	RM684	IR9442	2545DD 2550TB .	IR9852 IR9953
DMQ14A 1 DMQ20A 1	IR9840 IR9840	CBT4902E CBT9905	IR9403	CP2500TAN CP2841TA	IR9677	TNQ8E0428	IR9826	54AM12S	IR9788	RM686	IR9442	2552DB	IR9953
DMQ2195	IR9840	V\$068K	IR9862	CP2856TA CP2856TAN	IR9983	TNQ8E0430 TNQ8E0432	IR9826	54CS05SN	IR9788	RM687C	IR9448	2555	IR9953
DMQ2895	IR9840	GRUNDIG	120614	CP2886TAN CP28WD2TAN	. IR9983	TNQ8E0435	. IR9836 IR9836	5V2044 5V2145	IR9487 IR9487	RM689 RM694	IR9441 IR9452	2555DB.	
FERGUSON	N	CUC5200	IR9614	CP32WD2TAN	IR9983	TNQ8E0441	IR9826	70CS03S		RM698	IR9442 IR9448	2557DB 2563DB	IR9953 IR9953
20H3 22B5	IR9594 IR9584	CUC5301 CUC5302	IR9529 IR9529	CP11556 CPT1557	IR9576	TX14S1T	IR9834	72CS05SN	IR9711	RM719	IR9448	2563DD.	
22H3	IR9594	CUC5310 BC212	IR9614 IR9614	CPT1560 CPT1561	IR9576	TX21S1RC TX21S1T	IR9834 IR9834	C1421 C2021	.IR9487	RM817	IR9441	2577DB	IR9953
2422	IR9584	RC300	IR9614	CPT2155	IR9575	TX21S1TC	1R9834 IR9826	CV2121. CV3707	IR9487	RM820 RM826	IR9452	2579DB 2636B	IR9953
2423	IR9584 IR9584	TP590VT	IR9509	CPT2558.	IR9575	TX25A2C	IR9836	CV3709	.IR9487	RM828	IR9452	2835DB	IR9852
2445	IR9584 IR9584	TP600VT TP610	IR9509	CPT2566	IR9575	TX25W2	.IR9836	CV3720	IR9487	RM831	.IR9443	2852DB	IR9953
2453	IR9584	TP621	IR9299	CPT2669 CPT2785	IR9575	TX25W2C TX25W2CI	IR9836	DV1416SN DV1506SN	IR9487	RM832 RM833	IR9451	2855DD	IR9953
2475	IR9584	TP650	IR9509	CPT2870	IR9575	TX28A1D	IR9826	DV1706SN DV21081S	IR9487	RM834 RM836	IR9452 IR9871	2857DB 2857DD .	
26H3 29132	IR9594 IR9584	TP661 TOP	IR9562	CST1435	IR9576	TX28A2CI	IR9836	DV2130EX	IR9487	RM837	IR9451	2863DD	IR9953
36K2 41H3	IR9594 IR9594	TP663	IR9614 IR9529	CST1560 CT2116	IR1576 IR9476	TX28W2 TX28W2C	IR9836	DV25073S	IR9711	RM841	IR9452	2873DB	IR9953
4233	IR9584	TP711	IR9529	CTRM200M	IR9542	TX28XDP1C TX29AD1D	IR9835 IR9835	DV25081S DV25083S	IR9711	RM842 RM883	IR9443 IR9871	2879DB	IR9953
4415	IR9584	TP715	IR9749	JVC	100000	TX29W2CI	IR9836	DV28037S	IR9711	RM886	IR9871	3327DB 3339DB	IR9953
4423	IR9584 IR9584	TP760HIFI	IR9614	AV25TS1EN	. IR#698	TX33A2CI	IR9836	DV28081S	.IR9711	THOMSO	N	3357DB	
51A0 51A2	IR9584 IR9584	TP770 TP771	IR9749 IR9749	AV25VM1EN AV28VM1EN	IR9698	RC5002.	IR9510	DV3750S	IR9788	14GM53	IR9639	-3387DB.	IR9953
51A3	IR9584	TP800	IR9749	AV29SX1EN AV29TS1EN	IReo98	RC5140. RC5154	IR9510 IR9510	DV3760S DV5160S	IR9788 IR9788	14GM56 14M570	IR9639 IR9639	40PW8DB	IR9953
51A5	IR9584	TRC1	IR9715	AV32WZ2EN	IR9698	RC5240	IR9510	DV5403S	IR9711	21M576 21MG51	IR9639	48J6DB	.IR9953
51G2 51G3	IR9594 IR9594	TRC2	IN9715	RC8074	.IR9698	RC5260.	IR9510	DV5465S	IR9711	925TX1 049	IR9508	55PJ6DB	IR9953
51H3	IR9594	2970491	IR9479	RMC530 RMC682	IR9698 IR9698	RC5300 RC5350	IR9510 IR9510	DV5470S DV5935H	IR9711	RCT3000	IR9259	7037DD	IR9953
51J7	IR9594	A518780	IR9142	RMC761	IR9698	RC5410 RC5420	IR9553	DV6301S	IR9711	RCT5000 RCT5020	IR9259 IR9502	7053DD	IR9953
5980	IR9594 IR9584	C1414	IR9476	RMC770	.IR9698	RC5540	IR9510	DV6311S	IR9711	RCT5141S	IR9470	CT9369	IR9962
59B2 59B3	IR9584 IR9584	C2057H C2067	IR9142 IR9142	RMC771	IR9698 IR9698	RC5/01	IR9434 IR9553	DV6332S	IR9711	TOSHIB	6	CT9387	
59B4	IR9584	C2067H	IR9142	RMC793	IR9698	RC5801 RC5901	IR9556	DV6336S	IR9711 IR9711	1400 1400R	IR9962	CT9396	IR9962
59D2	IR9584	C. 146TN	IR9677	CHINGS SOIL		RC5903	IR9556	DV7002S	IR9711	1400RB.	IR9962	CT9414 CT9432	IR9962
59D3 59G2	.IR9584 IR9594	C2147TN	IR9983	FB300	IR9616	RC6404	IR9465	DV7011S	IR9711	1400RBN	IR9962	CT9455	IR9962
59G3	IR9594	C2166TN C2170TN	IR9677	FB50 FB52	IR9514 IR9514	RC6416 RC6512	IR9465 IR9464	DV70245 DV70325	IR9711	1400RB1	IR9962	CT9475	
59H5	IR9594	C LOGTN	IR9983	FB70	IR9514	RC6804	IR9434	DV7036S BRMCG0351CESA	IR9711	1400RDT.	IR9962	CT9480 CT9552	IR9962
59J/ 59LS2	IR9594 IR9639	C2259H	IR9142	FB90	IR9514	RC7141	IR9465	RRMCG0351CESB.	. IR9487	1440RBT	IR9852	CT9626	
6223	IR9584 IR9584	C22+1 C22o7H	IR9142 IR9142	FB91	IR9514	RC7507	IR9464	RRMCG0370CESA	.IR9487	1440TB	IR9852	CT9785	IR9953
66B2	IR9584	C2268H C2273	IR9142	076G047240	R9490	RC7512 RC7535	IR9864	RRMCG0483PESA RRMCG0489CESB	IR9487	1440TBT 1450RB	IR9852	CT9859 CT9867	IR9953
66H3	IR9594	C2273H	IR9142	076L067240	IR9490	RC8201	IR9434	RRMCG0568PESA	IR9487	1450RD	IR9852	CT9868	IR9953
66H5	IR9594 IR9594	C24W11N C24W511TN	IR9983	2092T	IR9490	RC9010	IR9434	RRMCG0618PESA	. IR9487	1480RBT.	IR9953	СТ9949	IR9953
		,			2	0 77			1	F			-
- 1 × 1		קי	<b>j</b> C	98	E	5.50		rev 4	3	BEC	D	-	

![](_page_23_Picture_4.jpeg)

This is just a selection of Konig Remote Controls that we stock. KUNIG

distributor of electronic components

## Transistors / Linear IC's

	Part No	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price
	BU208A	£0 75	IRF5450	£5 00	MJE350	£0.80]	STK4191	00.83	STK5464	63.00	STR371	64.00	TDA2450.3	£10.00]	TDA4665	62.50	TDAR128	62.00
	BU2508DF	00 03	IRF5740	£3 00	MJF		STK4191 X	E14 00	STK5466	£5 00	STR380	£3 50	TDA2460-2	£0 70	TDA4600	£4 75	TDA8138A	.£1 30
	BU2508A	£1 00	IRF5840	£3 00 £0 80	MJF 16206 MJF 18004	E4 50	STK419-130 STK419-140	£15 00	STK5467	£4 00	STR381	£3 90	TDA2501	£3 00	TDA4671	£5 00	TDA8138B	.£2.00
	BU2508AF	£1 10	IRF611	£1 20	MJF18006	£2 00	STK4192	£7 00	STK5471	E9 00	STR384	£3 50	TDA2507	. £4 50	TDA4681	£4 50	TDA8140	£2.00
	BU2508D	£1 30	IRF620	£1 00 £0 75	MJF 18008 MJF 18204	£1 75 £2 50	STK4197 II STK4199 II	£9 50 £10 50	STK5472 STK5473	£3 75 £4 80	STR40090 STR40115	£3 50 £6 00	TDA2510	£4 50	TDA4685	£2 75	TDA8143	£1 60
margener	BU2F08DF	£1 20	IRF634	£1 25	STK0025	£4 20	STK41990	£10 50	STK5474	£5 00	STR4090A	£6 50	TDA2515	£4 50	TDA4687	£5 00	TDA8146	£2 00
Descent         Los         Thread         Case         Thread         Case <th< td=""><td>BU2508DA</td><td>£1 50 £1 70</td><td>IRF640F</td><td>£1 50 £2 00</td><td>STK0039 STK086</td><td>£6 00 £10 00</td><td>STK420 STK4204 II</td><td>£4 00</td><td>STK5476</td><td>£3 50 £4 50</td><td>STR41090</td><td>£3.30</td><td>TDA2520-1</td><td>£9 00</td><td>TDA4700A</td><td>.£7 50</td><td>TDA8153</td><td>£10 00</td></th<>	BU2508DA	£1 50 £1 70	IRF640F	£1 50 £2 00	STK0039 STK086	£6 00 £10 00	STK420 STK4204 II	£4 00	STK5476	£3 50 £4 50	STR41090	£3.30	TDA2520-1	£9 00	TDA4700A	.£7 50	TDA8153	£10 00
	BU2520AX	£1 40	IRF630S	£2 00	STK1039	£4 60	STK4204II	£10 50	STK5478	£2 50	STR4211	£3 15	TDA2522	£12 00	TDA4714C	.£3 50	TDA8170	£2 30
Basesson         Constra         <	BU2520DF BU2520DX	£2 25 £2 00	IRF642 IRF644	£2 00 £2 00	STK1040	£6 40	STK4211 II	£10 00	STK5479	£3 00	STR43111	£9 50	TDA2523	£8.50	TDA4716C	£4 50	TDA8172	£2 00
Bisson         Dial         Dial <thdial< th="">        Dial         <thdial< th=""> <thd< td=""><td>BU2522AX</td><td>£1 50</td><td>IRF650</td><td>£2 00</td><td>STK1050</td><td>£6 50</td><td>STK4221 II</td><td>£12 00</td><td>STK5482</td><td>£2 85</td><td>STR441</td><td>£9 50</td><td>TDA2530</td><td>£3 00</td><td>TDA4725</td><td>£7 50</td><td>TDA8174</td><td>£2 00</td></thd<></thdial<></thdial<>	BU2522AX	£1 50	IRF650	£2 00	STK1050	£6 50	STK4221 II	£12 00	STK5482	£2 85	STR441	£9 50	TDA2530	£3 00	TDA4725	£7 50	TDA8174	£2 00
Barty Con         Barty Con <t< td=""><td>BU2525A BU2525AF</td><td>£3 25 £2 20</td><td>IRF710</td><td>£1 50 £0 85</td><td>STK2025</td><td>£7 00</td><td>STK4231 II</td><td>£10 50</td><td>STK5483</td><td>£4 40 £4 50</td><td>STR44115</td><td>£4 75</td><td>TDA2548</td><td>£2 00</td><td>TDA4780</td><td>£6 00</td><td>TDA8175</td><td>£7 00</td></t<>	BU2525A BU2525AF	£3 25 £2 20	IRF710	£1 50 £0 85	STK2025	£7 00	STK4231 II	£10 50	STK5483	£4 40 £4 50	STR44115	£4 75	TDA2548	£2 00	TDA4780	£6 00	TDA8175	£7 00
Backborg         Ling         Ling <td>BU2525AX</td> <td>£1 90</td> <td>IRF730</td> <td>£1 25</td> <td>STK2028</td> <td>£5 00</td> <td>STK4241</td> <td>£10 50</td> <td>STK5487</td> <td>£5 25</td> <td>STR450A</td> <td>£7 00</td> <td>TDA2549</td> <td>. E4 00</td> <td>TDA4800</td> <td>£5 00</td> <td>TDA8177</td> <td>£3 00</td>	BU2525AX	£1 90	IRF730	£1 25	STK2028	£5 00	STK4241	£10 50	STK5487	£5 25	STR450A	£7 00	TDA2549	. E4 00	TDA4800	£5 00	TDA8177	£3 00
BARDY AL         Constrain         First Prior         Total Prior <t< td=""><td>BU2525DF</td><td>£2 40 £1 75</td><td>IRF740</td><td>£0 90 £3 00</td><td>STK2029 STK2030</td><td>£6 00 £10 00</td><td>STK4241 V STK4272</td><td>£12 50</td><td>STK5488</td><td>£4 80</td><td>STR451</td><td>£8 00</td><td>TDA2560Q</td><td>.£7 00</td><td>TDA4850</td><td>£4 75</td><td>TDA8179S</td><td>£7 50</td></t<>	BU2525DF	£2 40 £1 75	IRF740	£0 90 £3 00	STK2029 STK2030	£6 00 £10 00	STK4241 V STK4272	£12 50	STK5488	£4 80	STR451	£8 00	TDA2560Q	.£7 00	TDA4850	£4 75	TDA8179S	£7 50
Dispect         Corr         Pressure         The second	BU2527AF	£4 00	IRF820	00 03	STK2038	£7 00	STK4273	£5 50	STK561	£4 00	STR4512	E4 00	TDA2574V	£3 50	TDA4852	£3 25	TDA8205	£12 50
Dissist         Case         Protect	BU2527DF	£2 00	IRF830F	£0 65	STK2058 IV	£9 50 £16 00	STK4274 STK4274	£5 00	STK563 STK5632	£4 15 £3 00	STR452 STR453	£4 75 £5.00	TDA2576A	£9 00	TDA4854	£5 00	TDA8212	£3 50
BATTORNA         C.D.         Price         D.D.         Price         D.D.         Price         C.D.         Price         D.D.         D.D.         D.D.	BU2527DX	£2 00	IRF840	E0 85	STK2101	£10 50	STK430	£5 00	STK5720	£4 00	STR454	£13 00	TDA2578A	£7 00	TDA4856	£5 00	TDA8215H	. £3 00
DEPTERAN         CED B         PERSED         CED B	BU2708AF	£2 00	IRF9140	£10 00	STK2139	£5 50 £6 75	STK4301 STK4311	£5 00 £6 50	STK5725 STK5730	£3 50 £3 00	STR455	£5 50 £4 70	TDA2579A	£2 10	TDA4858	£3 50	TDA8217	£2 25
Burgenergy         Constraint         Constraint <thconstraint< th="">          Constraint</thconstraint<>	BU2708AX	£2 00	IRF9230	£4 00	STK2155	00 63	STK433	£4 00	STK583	£4 00	STR457	£6 00	TDA2652	£48 00	TDA4861	£3 50	TDA8304	. £4 CO
Burgers         Geo         Person         C.10         Transfer         C.10         Transfer <td>BU2708DX</td> <td>£2 00</td> <td>IRF9510</td> <td>£1 50 £1 50</td> <td>STK2230 STK3102 II</td> <td>£4 70 £5 30</td> <td>STK4332 STK435</td> <td>£3 65 £3 75</td> <td>STK6316 STK6324B</td> <td>£3 00 £5 00</td> <td>STR470 STR50020</td> <td>£3 00 £3 50</td> <td>TDA2653A</td> <td>£4 50</td> <td>TDA4866</td> <td>£2 75</td> <td>TDA8305</td> <td>£5 00</td>	BU2708DX	£2 00	IRF9510	£1 50 £1 50	STK2230 STK3102 II	£4 70 £5 30	STK4332 STK435	£3 65 £3 75	STK6316 STK6324B	£3 00 £5 00	STR470 STR50020	£3 00 £3 50	TDA2653A	£4 50	TDA4866	£2 75	TDA8305	£5 00
Display         Display <t< td=""><td>BU2720AX</td><td>£2 00</td><td>IRF9520</td><td>£1 50</td><td>STK3106</td><td>£25 00</td><td>STK4352</td><td>£5 00</td><td>STK6327</td><td>£12 00</td><td>STR50092</td><td>£5 50</td><td>TDA2820M</td><td>£1 00</td><td>TDA4918A</td><td>£17 00</td><td>TDA8310</td><td>£6 00</td></t<>	BU2720AX	£2 00	IRF9520	£1 50	STK3106	£25 00	STK4352	£5 00	STK6327	£12 00	STR50092	£5 50	TDA2820M	£1 00	TDA4918A	£17 00	TDA8310	£6 00
Burgerson         District	BU2720DX	£2 00	IRF9530	£125 £200	STK3122 III STK3152 II	£7 25 £9 00	STK436	E4 30	STK6328A STK6431	E4 00 E6 00	STR50103A STR50112A	£2 60 £6 50	TDA2822M	£0 60 £2 00	TDA4930	£5 00	TDA8350Q	.£2 75
Display         Exc.         Person         Exc. <t< td=""><td>BU2722AF</td><td>£3 30</td><td>IRF9540</td><td>£1 75</td><td>STK3156</td><td>£5 00</td><td>STK437</td><td>£6 00</td><td>STK6607</td><td>£4 00</td><td>STR50113</td><td>£5 00</td><td>TDA3301B</td><td>£ 16 00</td><td>TDA4940</td><td>£2 00</td><td>TDA8354Q</td><td>£2 75</td></t<>	BU2722AF	£3 30	IRF9540	£1 75	STK3156	£5 00	STK437	£6 00	STK6607	£4 00	STR50113	£5 00	TDA3301B	£ 16 00	TDA4940	£2 00	TDA8354Q	£2 75
Burgerson         Construction         Transfer         Construction         Transfer         Construction         Transfer         Construction         Transfer         Construction         Transfer         Construction         Constr	BU2725DF	£2 00	IRF9541	£2 00 £0 95	STK350-030 STK392-040	£7 00	STK4372 STK439	£4 90 £5 00	STK6712BIV	£5 50	STR50115	£5 00	TDA3303	£7 00	TDA4941	£2 80	TDA8356	£2 00
Dialogram         Dialogram <thdialogram< th=""> <thdialogram< th=""> <thd< td=""><td>BU2725DF</td><td>£2 00</td><td>IRF9620</td><td>£0 85</td><td>STK401-050</td><td>68 00</td><td>STK4392</td><td>£5 00</td><td>STK6732</td><td>£10.00</td><td>STR50330</td><td>£4 75</td><td>TDA3502</td><td>£3 60</td><td>TDA4950</td><td>£1 00</td><td>TDA8361AN3</td><td>. £8 00</td></thd<></thdialogram<></thdialogram<>	BU2725DF	£2 00	IRF9620	£0 85	STK401-050	68 00	STK4392	£5 00	STK6732	£10.00	STR50330	£4 75	TDA3502	£3 60	TDA4950	£1 00	TDA8361AN3	. £8 00
Builton         Construction         Stready         Construction         Stready         Construction         Thousance         Construction         Construction           Builton         Construction         Stready         Construction	BU2727A	£2 00	IRF9630	£2 00	STK401-080	£9 00	STK441 STK4412	£6 80 £4 50	STK6822 STK6875	£7 50 £6 50	STR51041	£5 00	TDA3504	£3 00	TDA4951	£4 50	TDA8361N3	. £9.00
Dissolution         Dissolution <thdissolution< th=""> <thdissolution< th=""></thdissolution<></thdissolution<>	BU2727AF	£2 00	IRF9640	£2 30	STK401-140	£ 12 00	STK443	£7 00	STK6922	E10 00	STR51424	£7 00	TDA3521	£7 50	TDA5400	00 63.	TDA8362AN3	£7 50
Bubble         Bubble         Construct         Cons	BU508AF	£0 60	IRFBC20	£1 10 £1 20	STK4017 STK4019	£4 00 £4 80	STK4432 STK457	£8 00 £4 70	STK6932 STK6962	£4 50 £2 75	STR53041	£4.00	TDA3560	£6 00	TDA5500	£9 00	TDA8362BN3	£8 50
Biology         Diversity         Diversity <thdiversity< th=""> <thdiversity< th=""> <thdiv< td=""><td>BU508APH</td><td>£0 60</td><td>IRFBC40</td><td>£2 10</td><td>STK402-040</td><td>£7 00</td><td>STK459</td><td>£5 60</td><td>STK6972</td><td>£3 00</td><td>STR5412</td><td>£2 80</td><td>TDA3561A</td><td>£3 00</td><td>TDA5610-2</td><td>£7 50</td><td>TDA8362N4</td><td>£9 00</td></thdiv<></thdiversity<></thdiversity<>	BU508APH	£0 60	IRFBC40	£2 10	STK402-040	£7 00	STK459	£5 60	STK6972	£3 00	STR5412	£2 80	TDA3561A	£3 00	TDA5610-2	£7 50	TDA8362N4	£9 00
Bussep         Other         MPTP202         S11 all         Thread P1         Thread P1 <ththread p1<="" th="">         Thread P1         Thread P1&lt;</ththread>	BU508D	£0 75	IRFD120	£1 00	STK402-070	£7 00	STK460 STK461	£6 60 £6 00	STK6981B	£5 00 £6 00	STR55041	£4 50 £5 50	TDA3562A	£2 60	TDA5620	£4 50	TDA8362N5	£12.00
Builton L. B. 200 Meriland L. 2	BU508DF	£0 85	IRFD9120	£1 20	STK402-071	.27 00	STK463	£9 50	STK6982H	£6 00	STR58041	£2 50	TDA3563A	£4 00	TDA5830-2	£11 00	TDA8366N3	£11 50
Bull 15         64.00         PFIC20         C100         STM220         C100         STM210         C100         STM210 <thc100< th="">         STM210         C100         <t< td=""><td>BUH1015</td><td>£4 25</td><td>IRFF120</td><td>£1 00</td><td>STK402-090 STK4021</td><td>£3 80</td><td>STK465 STK4773</td><td>E8 20</td><td>STK7216 STK7217</td><td>£4 20 £2 50</td><td>STR59041 STR60001</td><td>£3 00 £5 25</td><td>TDA3564</td><td>£3 25 F2 20</td><td>TDA6100Q</td><td>£1 50</td><td>TDA8370</td><td>£11 50</td></t<></thc100<>	BUH1015	£4 25	IRFF120	£1 00	STK402-090 STK4021	£3 80	STK465 STK4773	E8 20	STK7216 STK7217	£4 20 £2 50	STR59041 STR60001	£3 00 £5 25	TDA3564	£3 25 F2 20	TDA6100Q	£1 50	TDA8370	£11 50
Delefield         Delefield         Delefield         Structure         Structure <t< td=""><td>BUH1215</td><td>£4 50</td><td>IRFIBC40</td><td>£1 00</td><td>STK402-100</td><td>00 63</td><td>STK4793</td><td>. £8 00</td><td>STK7225</td><td>£5 00</td><td>STR6008X</td><td>£5 75</td><td>TDA3566</td><td>£2 80</td><td>TDA6103Q</td><td>£2 25</td><td>TDA8374</td><td>£10 00</td></t<>	BUH1215	£4 50	IRFIBC40	£1 00	STK402-100	00 63	STK4793	. £8 00	STK7225	£5 00	STR6008X	£5 75	TDA3566	£2 80	TDA6103Q	£2 25	TDA8374	£10 00
Bulks 17         C 17         Bit Micro Mic	BUH515D	£2 50	IRFP054	£4 00	STK402-100	£9 00	STK4803	£10 00 £8 00	STK7226 STK7233	£17 00 £7 00	STR6020 STR61001	£2 70 £4 75	TDA3566A TDA3567	£3 00 £3 50	TDA6106Q	£1.25	TDA8375A	£12 50
Bury Hol         Edd         STACKED         STACKED         STACKED         LTP         LTP <thltp< th="">         LTP         LTP</thltp<>	BUH517	£2 75	IRFP064	£5 00	STK4024 1	£5 50	STK4833	£8 50	STK7251	£5 00	STR7001	£6 00	TDA3569	£3 00	TDA6108JF	£3 00	TDA8380	£2 00
Bull B0         ET44088         CT 00         STM4088         CF 00         STM4130         E 00         STM2120         E 00         TTAA450         <	BUH715	£4 25	IRFP150	£2 40	STK4025	£4.80	STK4853	£17 00	STK7253 STK730-060	£6 50 £6 50	STR80145 STR81145	£4 75 £3 75	TDA3570 TDA3576B	£3 75	TDA6111Q	£2 25 £5 50	TDA8424	£4 00
Bulkerin         File	BUL 310	£1 25	IRFP240	£3 00	STK4026II	£4 80	STK4863	£7 00	STK730-080	26 00	STR81159	£4 00	TDA3650	£6 75	TDA6160-25	£4 75	TDA8432	£5 50
Burlian, EDS   REP360 EDS   EDS   STK4802   ED 10 STK4869 ED 00 STK736 ED 25 TDA443 ED 5 TTA440 ED 5 TTA440 ED 5 TTA440 ED 5 TTA440 ED 5 TTA444 ED 5 TDA443 ED 5 TTA440 ED 5 TTA444 ED 5 TDA443 ED 5 TDA444 ED 5 T	BUL381D	£1 25	IRFP340	£2 50	STK4028	£5 50	STK488-010	£8 00	STK7308 STK7309	£4 00	STR8124 STR83145	£10 00 £5 00	TDA3651 TDA3651A	£2 00 £3 50	TDA6160-2X	£2 50	TDA8433 .	£6.00
BUTTIAK         EDS P         ImpPresso         12 / 200         TTALESS         <	BUT11A BUT11AF	£0.35	IRFP350	£3 25	STK4032 II	£5 10	STK488-050	00 83	STK7310	£3 20	STR83159	£7 00	TDA3652	£5 00	TDA7056	£2 00	TDA8443	£3 50
BUT12A         DB         IRFP460         CH 400         STK4038         C 800         STK403         C 800 <thstk403< th=""> <thstk403< th="">         C 8</thstk403<></thstk403<>	BUT11AX	£0 50	IRFP450	£2 70	STK4036	£4 70	STK4093	£10 00	STK73405 II STK73410	£5 50 £3 50	TDA1420	£8 00 £12 00	TDA3652TX10 TDA3653B	£8 00 £0 80	TDA7262 TDA7263	£3 25 £3 50	TDA8451 TDA8453	£3 25 £3 50
BUTTAR         ED 09         IFFP9240         C1300         STR4000         IES         STR4000	BUT12 BUT12A	08 03 £0 80	IRFP460	£4 00 £14 50	STK4036V	00 83	STK501	£5 50	STK73410 II	£5 00	TDA1514A	£3 25	TDA3653C	£0 85	TDA7263M	£4 00	TDA8461	£9 50
BUT18         CO 80         IFFPC-00         C1 A0         STK4042         E B00         STK315         E S00	BUT12AF	09 03	IRFP9240	£3 00	STK4040 II	£6 50	STK5314	£4 75	STK7356	£4 25	TDA1540	£5 00	TDA3654Q	£0 80	TDA7265	£5 00	TDA8501	£3 75 £11 00
BUTHAF         C0 65         IFFPC50         F6 00         STR40500         L1 800         TTA3420	BUT18A	E0 80	IRFPC40	£3 00 £4 50	STK4042 II	£8 00	STK5315	£5 00	STK7358	£4 40	TDA1541A	£4 00	TDA3724	£3 00	TDA7266	£5 00	TDA8560Q	£4 25
BUTSAF E.0 06   HFFFE40 E.5 01 STK405.000 F.7 00 STK5325 F.7 30 STK7390 F.7 00 TDA15520 F.3 50 TDA7340 F.4 00 TDA739V F.5 50 TDA6560 F.1 00 BUTAF E.0 10 HFFF50 F.4 50 STK405.000 F.1 5 50 TDA15530 F.4 50 TDA15530 F.4 50 TDA15530 F.4 50 TDA739V F.5 50 TDA6560 F.1 50 BUTAF E.0 10 HFFF50 F.4 50 STK405.000 F.1 50 TDA1550 F.4 50 TDA1550 F.4 50 TDA1550 F.4 50 TDA739V F.4 50 TDA7585 F.4 00 TDA5660 F.1 50 BUTAF E.0 10 HFFF50 F.4 50 STK405.000 F.5 50 TDA1550 F.4 50 TDA1550 F.4 50 TDA1590 F.5 50 TDA4586 F.1 50 TDA5560 F.1 50 BUTAF E.0 10 HFFF50 F.4 50 STK405.100 TTA553 F.1 50 STK405.100 TDA5550 F.1 50 STK405.100 TDA5530 F.1 50 STK405.100 TDA5530 F.1 50 STK405.100 TDA5530 F.1 50 STK405.100 STK433 F.2 50 STK474.00 F.1 50 STK405.100 STK433 F.2 50 STK474.00 F.1 50 TDA1550 F.1 50 TDA4520 F.2 50 TDA4520 F.2 50 TDA4520 F.2 50 TDA550 F.1 50 TDA550 F.1 50 STK407.00 F.0 50 STK433 F.2 50 STK474.00 F.1 50 TDA550	BUT18AF	£0 65	IRFPC60	00 83	STK4050 II	£16 00	STK5324	£3 00	STK73605	£3 75	TDA15461 TDA1547	£10 50	TDA3725	£3 00 £4 00	TDA7269	£5 0 1 £2 75	TDA8561Q TDA8562Q	£5 25 £5 00
BUZ714 E0 75 [HFFPF40 E550 STK405070A E800 STK333 E150 STK7426 E550 TTA1552C E150 TDA757 E500 TDA757 E500 TDA7586 E500 TDA757 E500 TDA758 E500 TDA757 E500 TDA5586 E50 TDA558 E50 TDA5586 E50 TDA558 E50 TDA5586 E50 TDA558 E5	BUT56AF	£0 65 £2 00	IREPE40	£5 50 £4 50	STK405-030	£7 00	STK5325	£370	STK73907	£7 00	TDA1552Q	£3 50	TDA3740	£4 00	TDA7293V	£5 50	TDA8563Q	£4 75
Bu2/TA*         L100         Inter-P30         L4 50         STK4030V         L1500         STK7331         E300         STK7404         E500         TDA7596         E500         TDA85870         E100           BU2/TA*         L100         IRF5840         L125         STK40812         E500         TDA85800         E500         TDA8590         E500         TDA8590         E500         TDA8590         E500         TDA8731         E600         TDA8733         E500         TDA8733         E500         TDA8731         E600         TDA8731         E600         TDA8733         E500         TDA8731         E600         TDA8731 </td <td>BUZ71</td> <td>£0 75</td> <td>IRFPF40</td> <td>£5 50</td> <td>STK405-070A</td> <td>£8 00</td> <td>STK5330</td> <td>£8 50</td> <td>STK73908</td> <td>£5 50</td> <td>TDA1553CQ</td> <td>£3 00</td> <td>TDA3770</td> <td>£7 75</td> <td>TDA7294 V</td> <td>.£4 00</td> <td>TDA8566Q</td> <td>£5 50</td>	BUZ71	£0 75	IRFPF40	£5 50	STK405-070A	£8 00	STK5330	£8 50	STK73908	£5 50	TDA1553CQ	£3 00	TDA3770	£7 75	TDA7294 V	.£4 00	TDA8566Q	£5 50
Bu227AF         E100         IRFSH40         E125         STK4080         E500         STK4206         E500         TDA15560         E125         TDA4200         E500         TDA3506         E500         TDA3506         E500         TDA3506         E500         TDA3506         E500         TDA3507         E500         TDA421         E500         TDA3702         E500         TDA3703         E500         TDA421         E500         TDA3703         E500         TDA3703         E500         TDA421         E500         TDA421         E500         TDA3703         E500         TDA47073         E500         TDA421         E500         TDA421         E500         TDA421         E500         TDA421         E500         TDA421         E500         TDA3703         E500         TDA3703         E500         TDA3704         E600         TDA421         E100         TDA3704         E600         TDA3704         E600         TDA3704         E600         TDA3704	BUZ72A	£1 00	IRFS740	£4 50 £1 75	STK4050V STK405-120	£15 00 £11 00	STK5331 STK5332	£3 00 £1 80	STK7402	£5 60	TDA1554Q	£3 00	TDA3771	£4 60	TDA7296	£5 00	TDA8567Q	£7 00
Du2.7.s.         L1.0s         Dir.2.20         L1.0s         Dir.A.330         C.F.30         TDA4570         E.30         TDA4570         E.60           DU2.7s.         E.10         IRF224         E.75         STK407-00         E.60         STK417         E.60         TDA4521         E.60         TDA3731         E.60         TDA3732         E.60         TDA3732         E.60         TDA3732         E.60         TDA3732         E.60         TDA3733         E.50         TDA4520         ITA350         ITA350 <td>BUZ72AF</td> <td>£1 00</td> <td>IRFS840</td> <td>£1 25</td> <td>STK4060</td> <td>£5 10</td> <td>STK5333</td> <td>£6 50</td> <td>STK7406</td> <td>£6 50</td> <td>TDA1556Q</td> <td>£3 25</td> <td>TDA4400</td> <td>£175</td> <td>TDA7300</td> <td>£5 50</td> <td>TDA8569Q</td> <td></td>	BUZ72AF	£1 00	IRFS840	£1 25	STK4060	£5 10	STK5333	£6 50	STK7406	£6 50	TDA1556Q	£3 25	TDA4400	£175	TDA7300	£5 50	TDA8569Q	
BUZPRA £1101   #F244 E1 60   STK407-070 68 50   STK333 £500   STK410 £1500   TDA15610 £500   TDA422 £200   TDA7318 E500   TDA7308 E700   TDA7308   TDA7	BUZ73AF	£0 60	IRFZ42	£2 75	STK4005	£0 50 £7 00	STK5336	£3 50	STK7406H	£7 50 £6 75	TDA1557Q TDA1558Q	£3 00 £3 00	TDA4420	£1 20 £3 00	TDA7302	£4 50 £8 00	TDA8571J	.29 00
DUZ717B         C 22 00         TDA4213         C 1 30         DTA4131         C 1 30         TDA4129         C 3 00         TDA4313         C 6 50         TDA8100         E 5 50           BUZ80         E 1 36         AU11015         E 2 50         STK4111         E 4 00         STK5340         E 2 30         TDA1596         E 4 00         TDA4313         E 1 50         TDA87441         E 5 50           BUZ80         E 1 00         AU11015         E 2 30         STK4112         E 8 00         STK5342         E 2 45         STK7554         E 4 80         TDA4429         E 4 00         TDA7340         E 8 00         TDA8444         E 1 40 00           BUZ80         E 1 00         AU11012         E 8 00         STK41240         E 1 4 80         STK5342         E 5 00         TDA1670A         E 8 00         TDA8444         E 1 4 00           BUZ80         E 1 00         AU11032         E 8 00         STK41240         E 1 4 80         STK5532         E 1 00         TDA1675A         E 2 50         TDA4480         E 1 00         TDA850         E 8 00         TDA8544         E 1 00           BUZ80         E 1 50         AU1504         E 3 00         STK4131         E 4 80         STK7536         E 0 00         TDA4501	BUZ76A	£1 10	IRFZ44	£1 60	STK407-070	£8 50	STK5337	£5 00	STK7410	£15 00	TDA1561Q	£5 00	TDA4422	£2 00	TDA7312	£4 50	TDA8708	£6 00
BU280A £135 BU280A £200 BU280A £200 BU280A £200 BU280A £200 MU11015 £250 STK:4112 £500 STK:4112 £500 STK:412 £245 STK:7541 £200 BU280A £100 BU280A £100 BU280A £100 BU280A £100 MU11032 £800 STK:412 426 £100 STK:412 426 £100 STK:312 £260 STK:412 426 £100 STK:312 £200 STK:412 426 £100 STK:312 £500 STK:412 426 £100 STK:312 £100 STK:313 £3 £00 STK:7561 £200 STK:7561 £200 STK:7562 £1000 STK:7561 £200 STK:7562 £1000 STK:7561 £200 STK:7561 £200 STK:7562 £1000 STK:7562 £1000 STK:7563 £200 STK:7562 £1000 STK:7562 £1000 STK:7562 £100 STK:7562 £1000 STK:7562 £100 STK:7576 £150 STK:7563 £100 STK:7576 £150 STK:7562 £100 STK:7576 £150 STK:756 £150 STK:758 £1000 STK:757 £1200 STK:756 £150 STK:758 £1000 STK:757 £100 STK:757 £100 STK:757 £100 STK:757 £100 STK:757 £100 STK:757 £100 STK:757 £100 STK:757 £100 STK:757 £100 STK:757 STK:750 £100	BUZ77B	£2 50	IRFZ48	£2 75	STK4101	£5 00	STK5339	£4 00	STK746	£9 00	TDA1582Q	£5 50 £4 25	TDA4427	£3 00	TDA7313 TDA7318	£6 50 £5 50	TDA8709	£7 00 £5 50
Bu283         E2:00         Multions         E3:00         STK:411-230         E1:200         STK:513         E3:00         STK:754         E3:00         TDA16346         E3:00         TDA1635         E3:00         TDA3841         E1:00         TDA3846         E1:00         TDA3846         E1:00         TDA3846         E1:00         TDA3846         E1:00         TDA3846         E1:00         TDA3846         E1:00         TDA3845         E1:00         TDA3856         E1:00	BUZ80 BUZ80AF	£1 35 £2 00	MJ10016	£7 00 £2 50	STK4111 STK4112	£4 00	STK5340	£3 50	STK752	£3 00	TDA1599	£4 00	TDA4431	£1 50	TDA7330A	£7 00	TDA8745	£8 50
Bul2900         L10.00         MJ11032         E8.00         STK411240E         E14.00         STK551A         E7.00         TDA1670A         E2.00         TDA4811         E2.15         TDA7359         E3.00         TDA8842         E14.00           BU2905         E1.000         MJ15003         E2.50         STK4121         E4.40         STK5532         E5.00         STK7563         E2.00         TDA4830         E1.00         TDA7350         E7.00         TDA8844         E14.00           BU2906         E1.60         MJ15015         E2.00         STK4121         E4.00         STK7563         E8.00         TDA16875A         E2.00         TDA4501         E2.80         TDA4502         E4.00         TDA7370V         E3.25         TDA7374V         E3.50         TDA9105         E5.00         TDA1701         E1.40         TDA4504B         E3.00         TDA7374V         E3.25	BUZ83	£2 00	MJ11016	£3 00	STK411-230	£12 00	STK5343	£3 80	STK7561	£6 50	TDA16846	£2 00	TDA4474 TDA4480	£4 00 £6 00	TDA7350	£8 00 £3 00	TDA8840	£10 00
BU2905 £10.00 MU1503 £2.50 STK412.150 £18.50 STK535 £4.00 STK756 £8.00 TDA1754 £2.00 TDA450 £10.00 TDA736 £5.50 TDA9102 £2.60 BU290 £1.50 MU15015 £2.50 STK412 £5.60 STK5351 £4.00 STK7563 £8.60 TDA1853 £2.00 TDA4500 £3.00 TDA7365 £5.50 TDA9102 £2.60 BU290 £1.50 MU15015 £2.50 STK4130 II £7.00 STK5362 £4.00 STK7573 £3.00 TDA18634 £2.00 TDA4500 £3.00 TDA7370 £3.25 TDA9103 £4.75 BU290A £1.80 MU15016 £3.50 STK4130 II £7.00 STK5362 £4.00 STK7576 £1.50 TDA1701 £4.40 TDA4503 £3.25 TDA7372A £4.50 TDA9103 £5.50 BU291A £2.60 MU15023 £4.00 STK4133 II £6.00 STK5371 £3.50 STK766 £5.00 TDA1771 £7.50 TDA4504 £8.00 TDA7375V £5.25 TDA9105 £5.00 BU291A £2.50 MU15023 £4.00 STK4133 II £6.00 STK5371 £3.50 STK777 £4.00 TDA1771 £7.50 TDA4505 £6.50 TDA7376 £1.00 TDA9143 £12.00 TDA9143 £12.00 TDA7375V £5.25 TDA9104 £2.50 STK4766 £5.00 TDA1771 £7.50 TDA4505 £6.50 TDA7376 £1.00 TDA9143 £1.00 TDA9151 £1.100 TDA9151 £1.100 TDA9160 £2.50 TDA4557 £4.00 TDA4557 £4.00 TDA4356 £1.00 TDA9160 £9.50 MUE13007 £1.00 STK4141 II £4.20 STK5331 £3.00 STK78617 £2.400 TDA1847 £2.50 TDA4565 £1.50 TDA736 £1.00 TDA9160 £9.50 MUE13007 £1.00 STK4142 £3.00 STK4352 £5.00 STK7852 £2.50 STK7801 £2.400 TDA1841 £3.00 TDA4565 £4.50 TDA7365 £1.00 TDA9160 £2.50 TDA9160 £2.70 TDA7385 £1.00 TDA9160 £2.70 TDA7385 £1.00 TDA9160 £2.70 TDA7385 £1.00 TDA9160 £2.50 TDA4565 £1.50 TDA7386 £1.00 TDA9160 £2.50 TTA9140 £6.00 TDA4565 £1.50 TDA7386 £1.00 TDA9160 £2.50 TDA9176 £6.50 TDA9176 £6.50 TDA9202 £1.50 TDA9202 £1.50 TDA9202 £1.50 TDA9202 £1.50	BUZ900	£10 00 £15 00	MJ11032 MJ11033	£8 00	STK411-240E	£14 00	STK5352	£5 00	STK7561A	£7 00	TDA1670A	£2 00	TDA4481	£2 15	TDA7359	.£3 00	TDA8842	£14 00
Bu2906         L16 00         M/JS0J4         L3 00         S1K4122         L5 60         STK7563F         L6 50         TDA18633         L2 20         TDA7365         L5 50         TDA9102C         L2 20           BU2904         L1 60         M/IS016         L2 300         STK4130I         L7 00         STK3582         L4 00         STK57573         L3 00         TDA4501         E4 00         TDA7370V         E3 25         TDA7370V         E3 25         TDA9102C         E5 00         TDA9102         E4 00         STK3582         L6 00         TDA7577         L7 00         TDA9102         E5 00         TDA4503         E3 25         TDA7372V         E3 25         TDA9102         E5 00         TDA9102         E4 00         STK4131         E4 80         STK5371         E3 50         STK761         E3 00         TDA1771         E2 00         TDA45048         E8 00         TDA7375V         E5 25         TDA9102         E4 00         TDA9102         E4 00         TDA7374V         E3 50         STK4131         E4 25         STK4131         E4 00         TDA7374V         E3 50         STK770         E4 00         TDA45046         E3 00         TDA7374V         E3 50         TDA7374V         E3 50         TDA7374         E4 50         TDA9141         <	BUZ905	£10 00	MJ15003	£2 50	STK412-150	£18 50	STK5353	£4 00	STK7563	£8 00	TDA1675A	£2 00	TDA4500	£3 00	TDA7362	£4 50	TDA8843	£15 00
BuZ90A         £1.80         Mu15016         £3.60         STK4130II         £7.00         STK5364         £2.50         STK7576         £15.00         TDA/3701         £14.00         TDA/3024         £4.05         TDA/3724         £4.50         TDA/3724	BUZ906 BUZ90	£16 00 £1 50	MJ15004 MJ15015	£3 00 £2 50	STK4122 STK4130 II	£5 60 £7 00	STK5361 STK5362	£3 75 £4 00	STK7563F	£6 50 £3 00	TDA 16833	£2 00	TDA4501	£2 80	TDA7365	£5 50	TDA9102C	£2 50
Bulzgina         L2 60         Minisozz         E4 00         STK433         L2 40         STK537         L2 50         STK760         E5 00         TDA4504B         E8 00         TDA7374V         E3 50         TDA9109         £1 00           BUZ93         £1 50         Mu15023         £4 00         STK4132         £6 00         STK5371         £3 50         STK761         £3 00         TDA45056         £3 00         TDA7375V         £5 25         TDA9141         £6 00         TDA9132         £4 00         TDA7375V         £5 25         TDA9141         £6 00         TDA9143         £4 00           IRF130         £2 25         Mu15024         £1 00         STK4141         £8 00         STK5371         £3 50         STK770         £9 00         TDA45056         £3 00         TDA7378         £1 00         TDA9143         £1 00           IRF140         £5 50         MUE13005         £0 60         STK4141         £4 20         STK5333         £3 75         STK78603         £7 50         TDA4506         £2 00         TDA7384         £1 100         TDA9160         £9 50           IRF240         £4 25         MUE13005         £1 00         STK4141         £4 20         STK53321         £3 65         STK78603 <t< td=""><td>BUZ90A</td><td>£1 80</td><td>MJ15016</td><td>£3 50</td><td>STK4130II</td><td>£7 00</td><td>STK5364</td><td>£2 50</td><td>STK7576</td><td>£15 00</td><td>TDA1701</td><td>£14 00</td><td>TDA4503</td><td>£3 25</td><td>TDA7372A</td><td>£4 50</td><td>TDA9105</td><td>£5 00</td></t<>	BUZ90A	£1 80	MJ15016	£3 50	STK4130II	£7 00	STK5364	£2 50	STK7576	£15 00	TDA1701	£14 00	TDA4503	£3 25	TDA7372A	£4 50	TDA9105	£5 00
BU293       C1 50       MJ15024       C3 00       STK4131 III       C7 00       STK5371       C3 50       STK770       C4 00       TDA4970A       C2 00       TDA4505E       C6 50       TDA7376B       C1 00       TDA4914       C4 00         IRF120       C2 25       MJ15025       C3 00       STK4140 III       C8 00       STK5372       C2 26       STK770       C4 00       TDA197A       C2 00       TDA7376       C1 00       TDA9144       C1 100       TDA9144       C1 100       TDA9160A       C2 00       TDA73781       C1 00       TDA9160A       C9 00       TDA9160A       C2 00       TDA73777       C4 50       TDA9160A       C9 00       TDA9160A       C9	BUZ91A	£2 60	MJ15022 MJ15023	£4 00	STK4131	£4 80 £6 00	STK5364 STK5371	£2 50 £3 50	STK760 STK761	£5 00 £3 00	TDA1770	£7 50 £2 00	TDA4504B	£8 00 £3 00	TDA7374V	£3 50	TDA9109	£10 00
Link         Link <thlink< th="">         Link         Link         <thl< td=""><td>BUZ93 IRF 120</td><td>£1 50</td><td>MJ15024</td><td>£3 00</td><td>STK4133 II</td><td>£7 50</td><td>STK5371</td><td>£3 50</td><td>STK770</td><td>£4 00</td><td>TDA1870A</td><td>£2 00</td><td>TDA4505E</td><td>£6 50</td><td>TDA7376B</td><td>£10 00</td><td>TDA9143</td><td>.£4 00</td></thl<></thlink<>	BUZ93 IRF 120	£1 50	MJ15024	£3 00	STK4133 II	£7 50	STK5371	£3 50	STK770	£4 00	TDA1870A	£2 00	TDA4505E	£6 50	TDA7376B	£10 00	TDA9143	.£4 00
IRF140       £5 50       MJE13005       £0 60       STK4141 V       £6 00       STK5383       £3 00       STK76603       £7 50       TDA1940       £6 00       TDA357       £4 00       TDA3584       £11 00       TDA9162       £9 50         IRF240       £5 50       MJE13007       £1 00       STK4142       £5 30       STK5383       £3 00       STK78617       £2 400       TDA4557       £4 00       TDA7384       £11 00       TDA9162       £11 10         IRF240       £4 25       MJE13007       £1 00       STK4151       £6 60       STK45392       £5 10       STK795       £2 57       TDA2032       £6 50       TDA7396       £11 00       TDA9162       £11 00         IRF250       £3 75       MJE15028       £2 00       STK41512       £6 50       STK5421       £4 50       STK8420       £1 00       TDA3986       £1 00       TDA9170       £7 00         IRF251       £6 50       MJE15028       £2 00       STK4154       £5 50       STK8422       £3 75       STK8250       £1 00       TDA3986       £1 00       TDA9170       £7 00         IRF250       £6 00       STK4154       £5 05       STK8422       £3 75       STK8250       £1 20       TDA4568	IRF130	£4 75	MJE13004	£1 00	STK4140 II STK4141 II	£4 20	STK5372	£2 60 £3 75	STK780	£9 00 £4 80	TDA1872A TDA1908A	£2 75 £2 50	TDA4510 TDA4556	£2 00 £3 70	TDA7377 TDA7381	£4 50 £11 00	TDA9144 TDA9151	£12.00 £11.00
IRF240         £4 25         INDETSOR         £2 00         STK4151         £6 80         STK5392         £5 00         STK795         £2 25         TDA2003         £6 50         STK3736         £1 00         TDA9162         £1 100           IRF250         £3 75         MUE15028         £2 00         STK4151         £6 60         STK5392         £5 00         STK795         £2 25         TDA2003         £6 50         TDA7386         £1 00         TDA9170         £7 00           IRF251         £6 50         STK4152         £6 50         STK5392         £5 00         STK4755         £2 51         TDA2004         £1 50         TDA7393         £1 0.00         TDA9176         £6 50           IRF330         £6 00         MUE15029         £2 00         STK4154         £5 05         STK8250         £1 00         TDA2065         £1 00         TDA7394         £6 60         TDA9177         £8 00           IRF340         £3 25         MUE15030         £2 400         STK4164         £5 05         STK4334         £5 70         STK8280         £1 200         TDA4580         £1 00         TDA7396         £4 50         TDA9210         £4 25           IRF340         £3 25         MUE15030         £1 40         STK414	IRF 140 IRF 230	£5 50	MJE13005	£0.60	STK4141 V	£6 00	STK5383	£3 00	STK78603	£7 50	TDA1940	£6 00	TDA4557	£4 00	TDA7384A	£11 00	TDA9160A	£9 50
IRF250       £375       MUE15028       £200       STK4152       £60       STK5422       £375       STK8050       £16.00       TDA204       £150       TDA4566       £250       TDA7393       £10.00       TDA9176       £650         IRF251       £600       MJE15029       £2.00       STK4154V       £14.00       STK5422       £375       STK8250       £500       TDA2004       £150       TDA4566       £2.50       TDA7393       £10.00       TDA9177       £6.50         IRF330       £6.00       MJE15030       £2.50       STK4164       £6.50       STK8260       £120       TDA2006       £0.70       TDA4580       £10.00       TDA7396       £4.50       TDA9177       £6.50         IRF340       £325       MJE15031       £4.00       STK4164       £5.50       STK8260       £1.80       TDA2006       £7.07       TDA4580       £1.00       TDA7396       £4.50       TDA9302H       £2.25         IRF340       £5.50       STK4164       £5.50       STK4343       £5.70       STR10006       £4.25       TDA2030       £1.60       TDA4600II       £1.60       TDA7439       £4.25       TDA9303       £9.00       TDA9503       £9.00       TDA9503       £9.00       TDA2030 </td <td>IRF240</td> <td>£4 25</td> <td>MJE13009</td> <td>£1 00</td> <td>STK4151</td> <td>£6 80</td> <td>STK5391</td> <td>£5 00</td> <td>STK795</td> <td>£3 25</td> <td>TDA1941</td> <td>£3 00 £0 65</td> <td>TDA4560</td> <td>£2 70 £1 50</td> <td>TDA7385</td> <td>£10 00 £11 00</td> <td>TDA9162</td> <td>£11 00 £7 00</td>	IRF240	£4 25	MJE13009	£1 00	STK4151	£6 80	STK5391	£5 00	STK795	£3 25	TDA1941	£3 00 £0 65	TDA4560	£2 70 £1 50	TDA7385	£10 00 £11 00	TDA9162	£11 00 £7 00
IRF330         E6 00         TDA/394         E6 00         TDA/390         E1 00         TDA/396         E1 00         TDA/396         E1 00         TDA/390         E0 00         TDA/390         E0 00         TDA/390         E0 00         TDA/390         E0 00         TDA/390         E1 00         TDA/390         E0 00         TDA/390         E1 00         TDA/390<	IRF250 IRF251	£3 75 £6 50	MJE15028	£2 00	STK4152	£6 50	STK5421	£4 50	STK8050	£16.00	TDA2004	£1 50	TDA4566	£2 50	TDA7393	£10.00	TDA9176	£6 50
IRF340       E325       MUE f5031       £4.00       STK4181V       £8.00       STK5434       £5.70       STK8280       £18.50       TDA2009       £1.60       TDA4600       £2.00       TDA7331       £7.00       TDA9302H       £2.25         IRF350       £7.50       MUE f6002       £3.00       STK4162       £5.50       STK5436       £5.00       STR1006       £4.50       TDA2020       £1.60       TDA7331       £7.00       TDA9500       £2.55         IRF440       £5.50       MUE f8004       £1.25       STK4164       £1.75       STK5441       £3.05       STR1006       £2.57       TDA2030       £8.00       TDA4601       £1.20       TDA7495       £4.25       TDA59503       £9.00       TDA9501       £9.00       TDA9500       £4.25       TDA9503       £9.00       TDA9500       £4.25       TDA96910H       £9.50       TDA95010H       £9.05       TDA9600       £4.25       TDA9610H       £9.50       TDA9610H       £9.50       TDA9610H       £9.50       TDA9610H       £9.00       TDA9610H       £9.50       TDA9610H	IRF330	£6 00	MJE 15030	£2 50	STK4161	£6 50	STK5431	£5 50	STK8260	£12 00	TDA2005	£1 50 £0 70	TDA4568	£2 25 £10 00	TDA7394	£6 00 £4 50	TDA9177	£8 00 £4 50
IRF 440         £5 50         M.E 18004         £1 25         STK 4164         £1 30         STK 5441         £3 50         STK 11006         £2 57         TDA2030         £0 80         TDA4601         £1 20         TDA4739         £4 50         TDA9500         £7 50           IRF 440         £5 50         M.E 18006         £1 25         STK 5141         £3 50         STK 11006         £2 57         TDA2030         £0 80         TDA4601         £1 20         TDA7495         £4 25         TDA95003         £9 00         TDA4601         £1 20         TDA7495         £4 25         TDA95003         £9 00         TDA4601         £1 00         TDA4601         £1 00         TDA95003         £9 00         TDA4601         £1 00         TDA7500         £1 80         TDA95014         £9 00         TDA95005         £4 00         TDA9600         £4 25         TDA96004         £1 00         TDA96005         £1 20         TDA96005         £1 20         TDA9600         £4 25         TDA9614         £8 00         TDA9600         £4 25         TDA9614         £8 00         TDA9614         £8 00         TDA96141         £8 00         TDA96141 <td>IRF 340 IRF 350</td> <td>£3 25 £7 50</td> <td>MJE 15031</td> <td>£4 00 £3 00</td> <td>STK4181V</td> <td>£8 50</td> <td>STK5434</td> <td>.£5 70</td> <td>STK8280</td> <td>£18 50</td> <td>TDA2009</td> <td>£1 60</td> <td>TDA4600</td> <td>£2 00</td> <td>TDA7431</td> <td>£7 00</td> <td>TDA9302H</td> <td>£2 25</td>	IRF 340 IRF 350	£3 25 £7 50	MJE 15031	£4 00 £3 00	STK4181V	£8 50	STK5434	.£5 70	STK8280	£18 50	TDA2009	£1 60	TDA4600	£2 00	TDA7431	£7 00	TDA9302H	£2 25
Intrasu         Lb SU         M/LE 18006         £1 20         STK4171         £9 00         STK543         £5 75         STR17068         £5 00         TDA2030H         £1 00         TDA4601D         £0 65         TDA7500         £4 25           RF510         £0 70         M/LE 18006         £1 50         STK4171         £9 00         STK5446         £3 05         STR20005         £4 00         TDA4601D         £1 00         TDA6000         £4 25           RF520         £0 75         M/LE 18006         STK4171         £6 80         STK5446         £3 05         STR20005         £4 00         TDA4605         £1 90         TDA6116         £3 00           IRF530         £0 75         M/LE 23         £0 85         STK4174         £6 80         STK5451         £3 90         STR3115         £2 75         TDA2050V         £2 00         TDA4610         £3 00         TDA6116         £3 00           IRF540         £1 00         M/LE 23         £0 85         STK4141         £6 80         STK5451         £3 90         STR315         £2 75         TDA2050V         £2 00         TDA4650         £3 00         TDA6116         £3 00           RF540         £1 00         M/LE 2400         £2 50         STK4172         <	IRF440	£5 50	MJE 18004	£125	STK4164 II	£11 75	STK5441	£3 50	STR11006	£3 25	TDA2030	£0 80	TDA46001	£1 20	TDA7439	£4 25	TDA9500	£9 00
IRF520         £0 75         MJE243         £0 60         STK4172 II         £6 80         STK5451         £3 90         STK30115         £2 75         TDA2050V         £2 00         TDA4610         £3.70         TDA6116         £3 00           IRF530         £0 75         MJE253         £0 86         STK4181         £6 80         STK5451         £3 90         STR30115         £2 75         TDA2050V         £2 00         TDA4610         £3.70         TDA6116         £3 50           IRF540         £1 00         MJE243         £0 85         STK5451         £5 00         STR3155         £2 75         TDA2051V         £4 50         TDA4610         £3.30         TDA6120B         £4 40           IRF540         £1 00         MJE340         £0 25         STK3451         £5 00         STK3451         £6 00         TDA6137         £2 00	IRF510	£6 50 £0 70	MJE18006 MJE18008	£1 20 £1 50	STK4171 STK417-130	£9 00	STK5443 STK5446	£5 75 £3 50	STR17008	£5 00 £4 50	TDA2030H	£1 00 £6 00	TDA4601D	£0 65	TDA7560	£18 00	TDA9610H	. £9 50
IRF540 £1.00 MJE340 £0.25 STK4181 £0.80 STK5461 £5.00 STR3315 £2.75 TDA2051V £4.50 TDA4650 £3.00 TDA8120B £4.00 IRF540 £1.00 MJE340 £0.25 STK4182 II £9.00 STK5462 £3.50 STR370 £3.00 TDA2052V £5.25 TDA4651 £8.00 TDA8137 £2.00	IRF 520	£0 75	MJE243	£0 60	STK4172 II	£6 80	STK5451	£3 90	STR30115	£2 75	TDA2050V	£2 00	TDA4610	£3.70	TDA8116	£3 50	10/30140	10 00
	IRF540	£1 00	MJE340	£0.85 £0.25	STK4181	£9 00	STK5462	£3 50	STR3315 STR370	£2 75 £3 00	TDA2051V TDA2052V	£4 50 £5 25	TDA4650	E3 00 E8 00	TDA8120B	£4 00 £2 00		

Please note that this a very small selection of the transistors and IC's that we stock.

We stock a full range of Japanese Transistors 2SA,2SB, 2SC,2SD,2SJ,2SK series , Diodes , CMOS , TTL Logic ICs , Computer ICs , Zenor Diodes...etc

K.P. House, Unit 15, Pop In Commercial Centre, Southway, Wembley, Middlesex. FAS Unit England Tel: (020) 3900 2329 Fax: (020) 8903 6126 Email: sales@grandata.co.uk

distributor of electronic components

## Line Output Transformers

Part No Goo	io Prico	Part No Codo	Price	Port No	Godo	Priso	Part No	Code	Price	Part No	Codo	Prigo
ALBA		HITACHIcontin	lod	PANASON	lCcontin	uad	PHILIPS		bod	THOMSO	Ncontine	bea
3714002LOT	02£12.00	2433453LOT82	£12.50	TLF 14568 F	LOT40	£15.00	AT 2079 / 21	LOT395	£12.00	10588080.P2	LOT1505	£19.00
043714002JLOT	02£12.00	2433751LOT01	£13.00	TLF 14584 F	LOT41	£17.00	AT 2079 / 24	LOT392	£15.00	151128140	LOT1505	£19.00
43700000LOT	02£12.00	2433752LOT01	£13.00	TLF 14586 F	LOT42	.£17.00	AT 2079 / 40	LOT73	£11.50	151281.4	LOT1505	£19.00
		2433891LOT23	£12.50				AT 2079 / 99	LOT276 .	£14.00	15128140	LOT1505	£19.00
AMSTRA	D	2433892LOT84	£14.50	PG	nlips		AT 2079/30 01	LOT106 .	£12.50	153144.6	LOT1505	£19.00
1810951LOT	55£14.00	2433893LOT23	£12.50	3119 108 31260	LOT90	£12.50	AT 2079/30102	LOT106 .	£12.50	15314460	LOT1505	£19.00
3714002LOT	02£12.00	2433952LOT33	£10.00	3119 108 31290	LOT73	£11.50		-		1531447 A	LOT1505	£19.00
043714002JLOT	02£12.00	2434002LOT226	£14.50	3119 108 31440	LOT433	£16.00	St	ansho Alsho	642.00	1532873 A	LOT1505	E19.00
43700000LOT	02£12.00	2434141LOT33	£10.00	3119 108 31441	LOT433	£16.00	3714002	LOT02	£12.00	3233500	LOT244	£14.50
AM152591LOT	55£14.00	2434274LOT44	£10.50	3119 108 31442	LOT433	£16.00	043714002J	LOT02	£12.00	3233900	LOT244	C14.50
		2434393LOT405	£22.50	3119 198 62930	LO157	£11.00	43700000	LOT02	£12.00	40011200	LOT244	C14.50
Ferous	ON	2434593LO144	£10.50	3122 108 10246	LOT111		/140021	LOT02		40140300	EO1244	
00 D-3-508-002LOT	381£15.50	2435006LO1401	£17.00	3122 138 36070	LOT111			14 4 70 / 70	- 1	576	രമ്പരം	
06 D-3-083-001LOT	82£12.50	2435131LOT251	£14 50	3122 138 36072	LOTE7	C11 00	DTONE 4000 CE	7710720	619 50	1910051	LOTSS	\$14.00
06 D-3-083-002LOT	82£12.50	2436201LOT90	£12 50	3122 130 30920	LOT57	£11.00	DTDNE 2001 CE	771 0139	£17.50	2423754	LOTOI	£13.00
06 D-3-084-001LOT	23£12.50	23236465LOT392	£15.001	3122 130 30922	LOT57	£11.00	DTRNE 2006 CE	ZZLOT338.	£13.50	23236098	LOT288	£14.00
06 D-3-087-001LOT	23£12.50	2433091HLU123	£12.50	3122 130 30923	LOT432	£15.00	PTPNE 2000 CE	ZZLOT300.	£15.00	23236198	LOT288	£14.00
06 D-3-088-001LOT	84£14.50	45150504LOT362		3122 130 37030	LOT90	£12.50	111111 2023 CE	22201010.		23236:01	LOT395	£12.00
06 D-3-093-001LOT.	204£16.00	MA 579000		3122 138 37020	LOT120	£14.00	2	SOMY		23236245	LOT395	£12 00
06 D-3-508-003LOT	270 £ 14.00	20070	£16 00	3122 138 37002	LOT1116	£19.00	1-439-286-00	LOT46	£13.00	23236255	LOT289	£15.00
06 D-3-512-001LOT	204£ 18.00	20070 LOT438	£16.00	3422 438 38040	10773	£11 50	1-439-286-11	LOT46	£13.00	23236-25	LOT288	£14.00
29201-022-01 LOT	204 045 50	20071 LOT438	£16.00	3122 138 38123	LOT395	£12.00	1.439.286.12	10746	£13.00	23236427	LOT395	£12.00
4/319/ LOT	304£15.50	20072	£16.00	3128 138 20200	LOT433	£16.00	1-439-286-13	LOT46	£13.00	23236428	LOT289	£15.00
D 0597 37LOT.	200	20074 LOT438	£16.00	3128 138 20201	LOT433	£16.00	1-439-286-21	LOT46	£13.00	23236424	LOT129	£14.00
COODWA	MG	20075 107438	£16.00	3128 138 20202	LOT433	£16.00	1-439-332-41	LOT100	£15.00	TFB 4090 AD	LOT395	£12.00
1142 5057	1164 €15.00	3714002 10T02	£12 00	3138 108 30100	LOT106	£12.50	1-439-332-42	LOT101	£14.50	TFB 4124 AE	LOT392	£15.00
1142 5077 LOT1	1164 £15.00	3221008 LOT438	£16.00	3138 108 30101	LOT106	£12.50	1-439-332-52	LOT100 .	£15.00	TFB 4'24 AP	LOT392	£15.00
1142 5079 LOT1	1164 £15.00	043714002J LOT02	£12.00	3138 108 30103	LOT106	£12.50	1-439-363-11	LOT268 .	£14.00	1		
1142 5081 LOT1	164 £15.00	043221088PLOT438	£16.00	3139 128 30400	LOT90	£12.50	1-439-363-21	LOT268 .	£14.00	Mo are st	ockist of	Eboth
1152-5016 LOT1	934. £19.00	43700000LOT02	£12.00	40348-08	LOT1577	£18 00	1-439-387-11	LOT311 .	£14.50	We are su		boun
1179.0387 LOT1	147£16.00	7140021LOT02	£12.00	40348A-08	LOT1577	£18.00	1-439-387-21	LOT311 .	£14.50		nia	
1192.0527 LOT1	147£16.00			40348A-09	LOT1577	£18.00	1-439-416-11	LOT255 .	£16.00		Jing	
1352.5008 LOT1	1167£15.00	MITSUBISHI		4812 140 10246	LOT111	£15.00	1-439-416-12	LOT255 .	£16.00			
1352.5008ELOT1	1167£16.00	731003LOT51	£15.50	4812 140 10349	LOT106	. £12.50	1-439-416-21	LOT255 .	£16.00		and	
1352.5016LOR1	1934£19.00	334 P 18506LOT51	£15.50	4812 140 10369	LOT90	£12.50	1-439-416-23	LOT255 .	£16.00		1	
1352.5027LOT1	1270£16.00		_	4812 140 10421	LOT90	£12.50	1-439-416-41	LOT255 .	£16.00	I AR L	лет	en
1352.5033LOT1	1270£16.00	ORECA		4822 140 10246	LOT111	. £15.00	1-439-416-51	LO1255 .	£16.00			
		40153201LOT349 .	£17.50	4822 140 10274	LOT123	£14.50	5300	000000			OPT's	
HINAR	0	0,000		4822 140 10306	LO157	£11.00	14050000	DINSON	C40.00			
3714002LO1	r02£12.00	ORION	040 00	4822 140 10349	LOT106	£12.50	105009.8	LOT 1505.	£19.00	This is ju	st a sele	ction
043714002JLO1	F02£12.00	3/14002LOT02	£12.00	4822 140 10381	LOT128	C45 50	10500980	LOT1505	£19.00			
43700000LOI	102£12.00	1043714002JLOT02	£12.00	4822 140 10364	LOT73	C11 50	10531460	LOT1505	£19.00	of the LC	PT's tha	at we
CF 124 BLO	167£14.50	43700000LOT02		4822 140 10400	LOT433	£16.00	105660.6	LOT1505	£19.00			
CF 124 ELUI	107	DAMAGOMAR		4822 140 10544	LOT433	£16.00	105660060	LOT1505	£19.00	stockP	lease ca	iii on
201520.00	20	TIF 14512 F LOT39	£18.50	AT 2076 / 10	LOT57	£11.00	10566060	LOT1505	£19.00	020 8000	2220 for	CONK
2424593	T44 £10.50	TLF 14520 F 10T40	£15.00	AT 2077 / 81	LOT121	£15.00	10566060.P2	LOT1505.	£19.00	020 8900	2329 101	copy
2432461 LOT	169 £15.00	TLF 14521 F LOT39	£18.50	AT 2078 / 21	LOT395	£12.00	105880.8	LOT1505.	£19.00	of our LO	PT catal	logue
2432761 LOT	169£15.00	TLF 14567 F LOT39	£18.50	AT 2079 / 15	LOT129	£14.00	10588080	LOT1505.	£19.00		- Catal	ogue
Lot			_			_				A COLORADO AND A COLORADO ANDO AND A COLORADO AND A COLORADO AND A COLORADO AND A COLORADO AND A		

### **CD Pick Ups and Mechanisms**

Part No Pric	e Part No	Price	Part No Pri	ce
CDM12.1 Mechanism£14.0	0 KSS 213 B	£8.75	OPTIMA 6 S £11.	50
KHM220AAA	KSS 213 C	£9.50	OPTIMA 5£11.	50
DVD Laser£ 40.0	0 KSS 213 D	£16.00	RCTRTH8151£20.	00
KSS 210A Original£11.0	0 KSS 213 F	£12.00	RCTRTH8112£14.	00
KSS 210A Replacement .£9.5	0 KSS 240 A	£30.00	RCTRH8147 Mech£ 10.	00
KSS 210 B£15.0	0 NKS 240 A Replacment fo	r KSS240A£20.00		

![](_page_25_Picture_6.jpeg)

Website : www.grandata.co.uk

![](_page_26_Picture_0.jpeg)

## Service Casebook

### **Michael Maurice**

### Tatung TYN9801P (B series chassis)

This set had failed during a thunderstorm. Checks in the power supply revealed that there was a short-circuit across the supply to the chopper control chip. So a new UC3844N chip was fitted. When I switched the set on it remained dead though the HT was now at 58V. Many fruitless checks were carried out, then I eventually tried replacing all three BY399 diodes in the chopper FET's snubber circuit. Although the diodes all read OK when cold, the power supply – and the rest of the set – then worked.

### LG WE32Q10IP

This set's relay kept clicking on and off and there was no picture. The cause of the problem was the microcontroller chip IC01. I was told by LG technical that an updated version, part no. 0ISO770011A, should be fitted. As I don't have an account with LG I ordered the chip from SEME. When it arrived I fitted it along with a new EEP-ROM, part no. 0IAL241600B. After switching the set on however all I got was EHT with no picture and no on-screen menus. A few phone calls and faxes to LG brought the response that the microcontroller chip should be obtained from LG direct. There is apparently a difference between the version sourced from LG Europe and the UK version, though the part numbers are the same .

I obtained the UK version through an LG dealer and fitted it. There was now snow on the screen, which would blank when you changed channels, but there were no on-screen menus and I couldn't get into the service mode. More faxes, phone calls and emails brought the suggestion that I must be doing something wrong. But eventually LG technical sent me another chip from an older batch. When I fitted it, with a new EEPROM, the set worked.

I've lost count of the number of phone calls and faxes involved and the amount of time I had to spend on the job. But credit where credit is due: LG technical was very helpful and provided support even though I'm not an account holder. Most other manufacturers would leave you high and dry.

### Sony KVX2162U (AE2 chassis)

This set had died during a thunderstorm. Checks showed that the chopper FET Q601 was short-circuit, so I fitted a new BUZ91A and also replaced the TDA4605-3 control/driver chip IC601. When I switched the set on these two items failed again. I also found that the HT rectifier D611 (D5L60), which had been OK when I first checked the power supply, was now shortcircuit. When I replaced all three items the set worked, to my relief.

It would appear that a short-circuit on the secondary side of a power supply of this type can kill the chopper FET and its control IC.

### Panasonic TX25T2 (Alpha 2W chassis)

The complaint with this set was white flyback lines. This time the flyback boost capacitor C455 ( $100\mu$ F, 50V) in the field output stage wasn't the culprit. The AN5521 output chip (IC451) was the cause.

### Hitachi C2514T

The sound was poor and muffled, as if one of the transistors in the audio output stage had failed. The cause was the loudspeaker however, though there was no physical damage. A replacement proved the point.

### Sanyo CB5949

This set was intermittently dead. Resoldering dry-joints on the secondary side of the power supply put that right, but the set wouldn't respond to the front-panel controls – remote-control operation was OK. Checks showed that the switches worked, and that the correct pulses reached the microcontroller IC. The 5V supply was also present and correct. So it seemed that the microcontroller IC was faulty. A replacement proved the point, restoring front-button operation.

### Toshiba 2512DB

This set had died during a thunderstorm. Only a faint ticking came from the power supply. Checks revealed that several of the BC547B transistors in the standby power supply circuit were faulty, but replacing them made no difference. The set worked when I replaced the two TLP621 optocouplers D814 and D830 and the SE140N voltage-error detector/optocoupler driver IC833.

### Finlandia C59JZ5 (Nokia Eurostereo 2 chassis)

This set would cut out intermittently. Checks showed that the set tripped when it cut out, there being no standby or any other output from the power supply. There was 300V across the mains bridge rectifier's reservoir capacitor however. The clue to the cause of the fault was that the set would run happily for hours when the contrast was turned down to about mid-way and, conversely, tripped more frequently when the contrast was set at maximum. So attention was turned to the beam-limiter circuit, where I found that C858 ( $1.5\mu$ F) had a  $1.5k\Omega$  leak. A replacement restored reliable operation, even at maximum contrast

# Introduction to computer networking

In this concluding instalment Fawzi Ibrahim<sup>\*</sup> describes the Domain Numbering Service, which enables host computers belonging to one company/organisation but located in a number of cities, countries or continents to be grouped together by a single domain name

So far we have considered two ways in which a host PC/workstation on a network can be identified: by its MAC or physical address, and by its IP address. In addition, it's desirable that a host has a unique domain name that corresponds with its IP address. This enables host computers that belong to an organisation, for example BA or ICI, which operates in a number of cities, countries or continents to be linked together by a single 'domain' name known as an FQDN (Fully Qualified Domain Name).

An FQDN specifies the position of a host in the internet DNS (Domain Naming Service) tree. The internet is organised in an hierarchical structure with a root at the top beneath which there is a layer of top-level or primary domains that are divided into sub-domains that in turn can be divided into further sub-domains and so on. See Fig. 1.

At the end of any branch there's a host or node. The host FQDN has the dotted format

Host\_name.Sub\_domain.Sub\_domain.Top\_domain.

In the example shown in Fig. 2, the FQDN of host server 1 is

server1.animalcare.org.uk

server 1 is the host name, animalcare is the lowest sub-domain, org the highest sub-domain and uk the top domain.

Basically an FQDN has two parts, the host name and a suffix. In the above example the host name is server1 and the suffix animalcare.org.uk. A suffix can be added to the computer name manually or dynamically, by DHCP. With Windows 2000, a suffix can be added manually as follows: starting at the desk top > right click my computer > properties > network identification > more > enter suffix.

For the TCP/IP suit the DNS name, i.e. FQDN, of a host is the responsibility of the presentation/application layer, while the IP and MAC addresses are the responsibilities of the internet and the physical layers respectively.

\*Fawzi Ibrahim is senior lecturer at the College of North West London and is the author of several books, including *PC Operation and Repair*.

![](_page_27_Figure_12.jpeg)

Fig. 1: The hierarchical structure of the internet.

In the same way that a host IP address has to be resolved into its MAC address and vice versa. FQDN host names have to be resolved into their respective IP addresses. This is carried out by the DNS server, which builds up a database of FQDNs and their IP addresses in a lookup table.

When a host requires a DNS name resolution it sends its request to a DNS server which will check its database and, if the host name is present, will send it back to the enquiring computer. For this reason the TCP/IP configuration of a host computer contains a field for the IP address of the DNS server.

In the case of the simple network shown in Fig. 2, the DNS server for workstations I and 2 (Wks1 and Wks2) has the IP address 10.0.0.10. This IP address must be entered when configuring the TCP/IP of each workstation.

The DNS server holds a list of fully qualified domain names and their IP addresses. This list can be constructed manually or dynamically. For the network shown in Fig. 2. the list will be as follows:

SERV1.animalcare.org.uk 10.0.0.10 Wks1.animalcare.org.uk 10.0.0.12 Wks2.animalcare.org.uk 10.0.0.11

Once a DNS server is known, a host can be contacted by using its DNS name rather than its IP address. For example, if you are sitting at Wks1, you can ping Wks2 by entering the following command at the command line:

#### ping wks2.animalcare.org.uk

When this command is carried out, Wks1 looks at its TCP/IP configuration to ascertain the DNS server. If a DNS server is entered, a request for a resolution is sent to that server which, for the network shown in Fig. 2, means sending the request to IP address 10.0.0.10. The DNS server then checks its lookup table to find the address of Wks2, i.e. 10.0.0.11, and sends this back to Wks1 which then stores it in a temporary memory (cache). Wks2 proceeds to send the ping command to 10.0.0.10 and awaits a reply.

The IP address for Wks2 remains in memory at Wks1 for a specified period of time so that, if a subsequent attempt is made to contact Wks2, it doesn't need to go to the DNS to find the IP address. This is the reason why the first attempt to contact a remote host takes longer than the first attempt. Stored DNS name resolutions are however wiped out following a reboot.

### **Dynamic configuration**

Manual TCP/IP configuration of each host for DNS server and the suffix is time-consuming and in most cases impractical. Instead, dynamic configuration with a DHCP is used. This is done by setting the appropriate options of the scope or server list. The relevant options are

06 DNS and . . . suffix options.

Thus when a host computer requests an IP address from the DHCP server it will be allocated an IP address from the pool of addresses and will also be informed of the DNS server for the name resolution and given a fully qualified domain name.

Fig. 3 shows a simple network with a DNS and a DHCP server. In small networks, where the traffic is light, one server may be used as both the DNS and the DHCP.

Fig. 4 shows a typical host TCP/IP configuration listed by the command IPCON-FIG/ALL.

**Secondary DNS servers** A single DNS server may be used to service a network. With a large network that contains hundreds of computers however the DNS's workload may be so large that the network is slowed down. Furthermore if only one DNS server is available in a multi-segment network requests for name resolution may have to go across routers, which will slow the network even more. For this reason secondary DNS servers are used.

Secondary DNS servers contain an uneditable (i.e. read only) copy

of the primary database constructed by the primary DNS server. Typically a secondary DNS server will be attached to each segment of a network as shown in Fig. 5.

In very large networks more than one secondary DNS server

![](_page_28_Figure_15.jpeg)

![](_page_28_Figure_16.jpeg)

![](_page_28_Figure_17.jpeg)

Fig. 3: Simple network with a DNS and a DHCP server.

States of States		- 0
	Node Type	
Etherne	adapter Local Area Connection 2:	
	Connection-specific DNS Suffix : : outsmart.co.uk Description	
Etherne	adapter Local Area Connection:	
on	Media State : Cable Disconnected Description : Intel(R) PRO/100 VE Network Conn Physical Address : 00-08-0D-5E-8F-0A	ect
C:\>_		

Fig. 4: A typical host TCP/IP configuration listed by the command IPCONFIG/ALL.

![](_page_28_Figure_21.jpeg)

Fig. 5: A network with primary and secondary DNS servers.

may be attached to the same segment. Hosts are then allocated to one of the DNS servers to share out the work. Normally hosts are configured with more than one DNS server: if one server fails, the host switches over to the next in the list and so on.

Replacing the Painter chip

> Philips refers to the main microcontroller IC in the A10E chassis as the Painter. It's a small, surface-mounted 100-pin device that can be the cause of many symptoms. Particular care is required when replacing it. Martin Cole explains how to carry out the repair.

he Philips A10E 50Hz chassis was introduced in 2000. It's very reliable except for one component, the Painter IC, a small surface-mounted device with 100 pins. Painter is a Philips colloquialism for the main microcontroller chip in this chassis, IC7064. It's mounted on the small-signals board (SSB), a computer-type PCB that slots into a SIMM-type socket on the main board, and can be the cause of all sorts of symptoms. These include no remote-control operation, no sound, Ext 1 switching on automatically, failure to come on, cutting out to standby and many more.

#### Versions

There are several versions of the chip, the three main types being ET, EP and ED. Before you tackle faults it's best to check the IC version fitted. To do this, enter the customer-service mode by pressing the remote-control handset's mute button and any button on the set's keypad for five seconds. The top line will then tell you the version number, for example A10EP1-1.3. Press any button to exit the customer service mode.

If the fault is no remote-control operation you can't use this method. You have to look at the IC itself to read the version type. EP is the most common version, with the part number 3111 250 54501. It has recently been recoded 9352 710 77557. The latest version is A10EP1-2.0.

#### **Preliminary** action

To replace the IC you ideally require the Philips Computer Aided Repair system (COMPAIR) to enable you to enter different settings in the EEPROM (NVM) chip. But in my experience this is very rarely required. A comprehensive instruction leaflet comes with the new IC: it should be followed very carefully. You also require a hot-air surfacemounted device IC removal tool. You cannot do the job with a 25W soldering iron and solder wick. If you don't have the right equipment, *do not* attempt the repair.

Before you start it's best, if the remote-control functions are OK, to enter the service-alignment mode (SAM) and note all the options. This will make it much easier to set up the picture after the replacement. You can enter the SAM by pressing the 'align' button on the Philips Dealer Service Tool (RC7150) or numbers 062596 followed by the OSD button with the standard remote-control unit - the OSD button is the teletext i (index page) one. The SAM menu will then appear on the screen. Before starting I always make a note, for service records, of the hours counter.

Use the remote-control unit's cursor buttons to go down to options, and select with the right cursor. Then use the cursor buttons to go down the list (not all items can be displayed at once, just keep pressing the down cursor to reveal the next item), making a note of each line, until you get to the option numbers OB1-OB8. These are the options that should be the same as the codes on the sticker on the back of the CRT. Do the same for the white-tone, geometry, Super-wide geometry and Smart settings. You don't need to bother with the tuner or sound.

You will probably find error code 13 in the error buffer. This is an IC tuner error, but the tuner will be OK. If you want to cure this problem, change the value of R3267 and R3268 to  $10\Omega$ . The cause of the problem is an incorrect logic level at the relevant input to the microcontroller chip.

When you are satisfied that you have all the details, you can remove the SSB and proceed with the replacement.

### Carrying out the replacement

I allow two days for the repair as I use Chemtronics Chemask, which is best left overnight to cure, to isolate the surrounding components thermally before using a Leister Hot Jet S tool. Other equipment with shields and suction to remove surface-mounted devices is available, but is unfortunately very expensive – beyond the budget possibilities for many engineers.

Use gentle heating to remove the chip, with tweezers to flick it away from the solder lands. Then clean up the PCB with flux and solder wick, using a standard soldering iron.

When soldering the replacement IC in place, take the usual static precautions and line up all the pins very carefully. I use a bench magnifying lamp and two more magnifying glasses to see the pins. Extra care at this stage pays off, as poorly aligned pins will cause problems later.

Tack two corner pins to hold the IC in place before full soldering. There are different schools of thought on how to go about soldering the hundred pins. I use a Pace Mini-Wave tip, which holds a reservoir of solder and can solder them all in seconds. Some flood the whole lot with solder, then wick off the excess. Others use a solder paste or solder each pin individually with a fine-point soldering tip. To perfect my preferred method, I practised with old scrap VCR panels.

When the soldering has been completed, clean the board with isopropyl alcohol and inspect it. If the soldering at any pin appears to be suspect, try moving the pin gently with a fine point. Resolder if necessary. It is most important that every pin is correctly soldered. More on this later.

### Testing

Once the IC has been fitted, it's time to try it out. After replacing about fifty Painter ICs I still find this the most heart-stopping moment - when you fit the SSB and switch on. First make sure that the mains socket switch and the set's mains switch are both in the off position. If you plug the SSB into a set that's already powered up you will have to buy another IC and do it all again! This is important: the new IC has to download to the EEPROM chip and vice versa. and you get loads of problems if this process is interrupted. If there are other engineers working on equipment in the workshop and you have sensitive mains safety trips, ask them to stop work while you switch on. Someone causing the workshop supply to go or using a Philips remote-control unit can cause trouble.

Plug an aerial in before you switch the set on. When you switch on nothing seems to happen for what seems to be ages, then you hear the degaussing and the set comes on with no picture. Be patient. The picture will appear and the set will start the auto-tuning search. Leave it alone until it has finished and the sound appears.

### Setting up

If all this happens you have been successful. All you need to do is to go into the SAM and check the option numbers, then re-enter the geometry and white-tone settings. Pay particular attention to the cathode-drive settings. They are always too high with a new IC.

To change the option numbers OB1-0B8 as per the numbers on the CRT sticker, go to Options and, using the cursor buttons, work your way down to the end of the list until you get to OB1. If it is incorrect, enter the right number. You have to enter a three-digit number so, if any number has only two digits, enter a zero first, e.g. 023 for 23. Do this for OB2, OB3 etc. Option numbers OB5-OB8 are usually zeros. The option numbers vary with model, screen size and CRT type. With the Smart settings, use those you noted previously or follow the instruction sheet supplied with the IC. To store your settings, press the menu key until you get the main menu, right cursor to brightness, down cursor to 'store' and store. Press menu twice to return to the SAM menu and press standby.

### When things go wrong

What if things go wrong? The most likely outcome is that the set doesn't come on. Remove the SSB and check your soldering again. If you find a poor connection, it is possible that the download didn't go to plan. This is the worst possible situation.

As I understand it, during the download the Painter talks to the EEPROM and the EEPROM talks to the Painter. The Painter is then 'write-protected', and whatever you try from then on will not get the set going again. The instruction sheet refers to changing the EEP-ROM IC on the other side of the PCB, but it won't help in this situation. Even using COMPAIR to wipe the EEPROM clean, then downloading from a floppy disk a known-good EEPROM file for the exact model being repaired will not provide a cure. The only cure is to replace the Painter again, an expensive outcome!

Philips technical engineers have given me conflicting advice on what actually happens during the download, suggesting that the Painter is write-protected all the time. But if this is the case why can't a suspect IC be used on another panel?

Other faults I've had are incorrect menu colours and text colours. Again the cause was the relevant IC pin not being correctly soldered. At one stage Philips had a faulty batch of 'blank' ICs – the set would not come on – but supplies of these should have been exhausted by now.

### An alternative approach

If you feel that you cannot carry out this repair, there are repairers who will change the Painter IC for you if you send them the PCB. I have known cases where an engineer simply puts the repaired panel back in the set and does nothing about setting it up.

This means that the set operates with incorrect option codes, awful geometry and excessive cathode drive!

I hope that you will find this

article of use and, after reading it, will feel able to replace the Painter IC. If you are still unsure however it's probably best not to try, as damage to the SSB is terminal and I don't think it is available any longer. If you use a third-party repairer, always set up the options and geometry etc. before returning the set to the customer. These sets produce excellent pictures, especially when they are fitted with a Philips CRT.

### Costs

It seems to me that engineers in this trade are expected to carry out very difficult repairs, to component level, for little reward. If this was a PC instead of a TV set, the SSB panel would probably cost about £40 and be a throwaway item. When it was available, I believe it cost in the region of £220 plus VAT!

An estimate for the replacement of this IC is always met with much resentment. After all, the ICs started to fail when the sets were just out of guarantee, and people were not pleased at the prospect of having to pay nearly £130 to repair a set that was just over a year old. The sets, up to three years old, are still coming in.

Customers tend to think that they are being ripped off, and don't appreciate the cost of the equipment needed to carry out such repairs. As mentioned earlier, desoldering stations are expensive quite often in excess of £1,000. The COMPAIR system with all the software costs nearly £300, and annual software updates have to be purchased. Our charge also includes two people to collect and return the set. I have had two cases where the customer has written off the set and bought a supermarket model for £199.

If you require an A10E service manual, the part number is 3122 785 10430. There are several errors in it – a separate sheet is available with all the corrections. The SSB in the Philips A10E chassis slots into a Simm-type socket on the main PCB. The Painter IC is towards the centre.

![](_page_30_Picture_25.jpeg)

# Vintage repairs

Pete Roberts describes a couple of 'no-reception' faults with vintage radio equipment, a Radford FM tuner and a Motorola car radio.

![](_page_31_Picture_2.jpeg)

y latest vintage equipment servicing efforts involved two nice items, a Radford hybrid FM tuner. Model FMT1, and a Motorola 124 car radio. The latter was typical of dozens I repaired as a callow youth about thirty years ago. The problem with both was said to be "no reception".

### The FM tuner

The Radford tuner matches in appearance the firm's contemporary preamplifier control unit and power amplifier. That is, it's housed in a strong battleship-grey metal cabinet and weighs as much as a light destroyer. Going by the date codes on the electrolytic capacitors. I assume that this particular example hailed from the mid-Sixties. The valve line-up is as follows: an ECC85 RF amplifier/mixer-oscillator: three EF89 vari-mu IF amplifiers: an EF80 limiter: and an EM87 tuning indicator. Two germanium diodes are used for demodulation, which is followed by a twotransistor audio amplifier that uses

![](_page_31_Picture_6.jpeg)

an odd Texas Instruments device with an unreadable number and an AC128. The IF strip and audio amplifier are both built on PCBs that are mounted on cut-puts in the metal chassis. The RF amplifier and self-oscillating mixer stages are contained in a screened, permeability-tuned tuner head.

After checking for any obvious faults I applied power and switched on. The heaters all came up to normal brightness, but the magic-eye's display was very dim and showed no movement as I spun the dial across the band. I'd already checked that the permeability tuner's cores were free and moving. Then I saw it. balefully staring at me from the centre of the chassis: a Sen-Ter-Cel selenium bridge-rectifier block. So out came the meter, which showed that the HT supply was less than 90V – with an input from the mains transformer of about 250V AC! Knowing these things from long ago. I discharged the HT reservoir and smoothing capacitors ( $3 \times 16+16\mu$ F, 350V wkg, 450V surge, with each having both sections wired in parallel) and measured their capacitances.  $32\mu$ F in each case – not bad for 35-year old capacitors!

Suspicions confirmed, out came the selenium rectifier block: old hands may recall that meter checks on this type of rectifier could never be relied upon. I just happened to have a fairly substantial 1kV, 8A silicon bridge in stock. So in it

went, with a 1,000pF, 250V AC class Y ceramic capacitor wired across the AC input to protect it from transients – always advisable when using silicon rectifiers with a transformer-derived high-voltage supply. OK. so 8A is a bit over the top, but it saved having to use tagstrip to mount a 1A part. After fitting it I was rewarded with success. With the valves heated the HT was now at about 270V, confirmed

by a nice, bright magic-eye. Better still, the display flickered when I spun the tuning knob. As the magic-eye's control voltage is derived from the ratio-detector circuit, audio should have been present. But there was still silence.

### **Audio** section

This tuner's audio section is odd to say the least. The post-detector transistor audio amplifier's output goes to a 5-pin DIN socket which is mounted on the rear panel. The twin-gang front-panel volume control is connected to the same socket, via a pair of screened leads. Another pair of screened leads connects a set of phono sockets, again mounted at the rear, to the wipers of the ganged volume-control potentiometers. My customer told

April 2004 TELEVISION

The IF strip in the Radford FM tuner.

Inset: the tuner head in the Radford Model FMT1.

![](_page_32_Picture_0.jpeg)

![](_page_32_Picture_1.jpeg)

me that he took the mono signal from the DIN socket, which is obviously there to connect an external stereo decoder – bearing in mind that this tuner was built a couple of years before stereo transmissions started in the UK. Needless to say the volume control has no effect when the output is taken in this way.

The loss of audio was caused by a broken transistor lead. After repairing this I was able to tune across an FM band solid with signals. The audio amplifier is powered from the main HT line via a 2W carbon resistor that was rather cooked. When measured, the amplifier's supply was found to be 34V. As the AC128 transistor has a maximum Vce of 32V, I decided that this was not a good idea! I don't have a circuit diagram, and couldn't make out the original value of the dropper resistor (it measured  $27k\Omega$ ). So I replaced it with a  $33k\Omega$ , 3W flameproof metal-film resistor mounted well off the preamplifier's little PCB. The audio amplifier's supply then measured 28V. With the replacement resistor running just comfortably warm and the audio quality unaffected, I decided to leave it at that. Reasonable longevity should be assured. I wonder why Radford didn't stabilise the preamplifier's supply with a zener diode?

Quite a few soldered joints on the IF amplifier PCB looked a bit past their best, so I did a blanket resoldering job, taking particular care to make good the joints that secure the valveholders. The unit was soak tested for a fortnight, then parcelled up for its journey home to the north of Scotland.

### The Motorola

The Motorola 124 car radio was in excellent cosmetic condition for its age. It was one of the later all-silicon models made during the very late Sixties, with an output stage that features those odd little Motorola 'liquorice allsort' power transistors that have a distinctive, gold-plated heatsink tab. There's an RF amplifier stage prior to the mixer/oscillator stage, both being permeability tuned to provide full LW and MW coverage. The IF is 470kHz, and the single IF amplifier stage has two double-tuned IF transformers.

The reported fault was "no reception", but when I connected a speaker and my 13.8V bench power supply there was the usual MW noise – though not very much. After a few minutes even this disappeared, but wiggling the aerial plug in its socket would bring the set back to life. No need to 'hunt the fault' here: the symptoms were those of a duff detector diode. A new OA90 diode restored reception.

But the sound was thin and the volume a bit low. Turning up the wick produced obvious clipping at a still modest level. The output stage is of the familiar complementary-symmetry 'totem-pole' type, with capacitive coupling to the speaker. The  $1,000\mu$ F, 25V coupling capacitor was the cause of the trouble, being almost open-circuit.

The electrolytic capacitors were all those nice golden and usually very reliable German Frako types. But the radio had no doubt been regularly toasted during its thirty odd summers, so I thought it prudent to replace them all. When refurbishing old radios I find that modern radial electrolytics aren't right from the appearance point of view. So I use those awfully nice blue BC Components axial capacitors which, though smaller, otherwise look just like their Sixties Philips predecessors. To many vintage radio enthusiasts the appearance of "the works" is as important as that of the case.

Dry-joints are a common fault with these radios. The PCBs appear to be flow-soldered and, sometimes, there are just minimal amounts of solder with the component leads clearly visible. So I undertook a blanket resoldering. This is particularly important as car radios are subject to vibration, which can also shift cores. Because of this I checked the alignment – a tweak of the IF cores provided a useful increase in gain.

Finally, never forget to check the voltage and polarity before applying power when repairing a vintage car radio: 6V radios weren't all that rare, and most Sixties models will be set for positive earth. The polarity setting is usually indicated by the position of a switch, but Radiomobile models use soldered links on the PCB - the position of these will need to be checked. Always ensure that the polarity is set as originally. It might be a good idea to note the polarity on the customer's invoice. Impress on the owner the need to fit a suitably-rated fuse in the supply lead. A 3A rating is adequate for most radios of the period.

Top left: The Motorola car radio Model 124.

Top right: Internal view of the Motorola Model 124.

Below: Electrolytics in the Motorola 124.

![](_page_32_Picture_17.jpeg)

![](_page_33_Picture_0.jpeg)

Coverage of the Newark Network.

# broadband

# Steve Beeching on the advantages of having a wireless broadband link for internet connection

live at a rural location and run a business from my home. Grove Farm. It was still a working farm back in the Fifties and Sixties, and thus had the outbuildings that go with such an enterprise. These were in fact what attracted me to the farm when, in the mid-Eighties, I decided to concentrate on repairing the then revolutionary camcorders for a major manufacturer. It provided sufficient workshop accommodation and storage and there were five telephone lines. So there was no need to move to an industrial estate. I suppose that, in 1986, I would have been a pioneer in the trend to non-agricultural business location in a rural setting.

In the early days, around 1990, I started to use PCs for drawing and writing, in order to update technical publications including my book Domestic Video Recorders – a Servicing Guide. Since then the PC has also become a tool for adjusting the high-tech products that come my way. I've had to upgrade many times, which is not a problem when one can build a PC for a specific purpose.

### Use of the internet

During the mid-Nineties the internet became a normal part of business, for communications, web sites, publishing and downloading product data files and service software. As the files became larger, the communication periods became longer, tying up the PC and phone lines for hours on end.

So broadband was to be the next step – and that was where progress came to a halt for a while.

When I asked BT about ADSL (broadband) I discovered that there were two stumbling blocks. The local exchange, somewhere in a field, would not be upgraded to ADSL. And I was too far from it more than 2km. The distance from the exchange has increased to 6km. and there is also the problem that the 1km 5-pair cable along the driveway to Grove Farm has quite a few knots in it. These would impede BT's high-frequency carriers. The local NTL cable network comes nowhere near the local village. and again there would be the long driveway to cable. So no chance there.

Then a local entrepreneur and his small IT and computer company decided that, for social and financial (in the longer term) reasons, it would be a good idea to

![](_page_34_Picture_0.jpeg)

have a wireless communications system in Newark-on-Trent. John Harris, of JHCS Computers, gave a short presentation about his idea for a Newark Network to members of the Newark Business Club. John already had a 'pipe' connection to the internet world, and hosted sites as an ISP. I was very interested, but again there was a stumbling block: I am five miles from Newark.

But over the past year the network has grown and progressed and, as newer and more efficient communications equipment has become available, its range has increased. This has been achieved by technical advances in weak-signal recovery and error-correction techniques rather than increased transmission power. The network equipment is being continually upgraded as newer and better transceivers become available, increasing the coverage.

### **Broadband at Grove Farm**

I am now on broadband, with full 512 kbits/sec access for 24 hours seven days a week, at a very reasonable cost, without changing ISP, email or web addresses – except for outgoing emails, but even here there is no change to the source address.

My 'aerial', see Photo 1, is a data-communications link that works at the standard WiFi frequency of 2·4GHz. This frequency was chosen because it is widely used for networks, thus making possible the use of a wide range of

### Left: Steve's chimney-mounted data link.

equipment, in turn lowering costs. The link is connected to the workshop PC's network port. This will make possible future expansion with other PCs, using a smaller internal WiFi network. The roofmounted data-link unit is more sensitive and efficient than a passive aerial. I get 70 per cent signal data quality over a distance of two and a half miles to an access point at Fernwood 2 (see map, Fig. 1). This is a temporary arrangement - an adjacent water tower is likely to become available in the future. There will be no need to reposition the 'aerial' as it has a beam width of 32°.

### Newark Network development

JHCS had a favourable response from local organisations to requests for access to tall buildings to site equipment – access points

and bridges. These consume very little power, an access point 100mW, a bridge 24mW. A lot less than a 10W light bulb!

The first experimental link provided an access point at the Fernwood 1 site, just outside the BT broadband (ADSL) range. To achieve this two data bridges were installed, at Hawtonville and Balderton. They were subsequently upgraded to access points. The link to Farndon, along the A46, followed soon after. There were signal problems at Fernwood 1: help was provided by British Gypsum, which allowed a bridge to be installed on a high construction. This gave better signals to Fernwood 1 and 2 the latter is isolated from Fernwood 1 by trees - and made a link to the village of Claypool possible. A recent addition to the network is an access point on a high tower at the British Sugar factory to the north of Newark. The full extent of this coverage has still to be assessed. A total area of about 100 square miles is now covered, within the blue line in Fig. 1, with the possibility of reaching some 90,000 subscribers.

#### Costs

Some local schools have access to the internet via cable at a cost of up to £250,000 per school. A wireless link with a 1:1 connection, at a speed of 2Mbits/sec, would cost virtually nothing in comparison. There would be no need for digging and laying expensive cable.

The cost of a wireless broadband link is very reasonable. The initial installation cost of £400 can be offset by a grant application to rabbit-broadband.org.uk, leaving the subscription charge of £29.99 plus VAT per month. This charge increases to £49.99 a month for network connection via a router. Because of the modest cost and the advantage of continuous 24/7 internet access, local businesses are changing from their current providers to Newark Network. Domestic users have a small WiFi card fitted to their PCs. The card is connected to an external aerial (see Photo 2) and the cost is much lower - £55 for the card, plus installation and a monthly subscription charge of £19.99 plus VAT.

### In conclusion

JHCS plans to introduce smaller access points around the town for laptops. There are also plans to introduce VOIP for voice communication, providing local phone calls via the Newark Network.

Newark Network is a great advantage to me and to farms and businesses around Newark at locations where a broadband connection was, a year ago, inconceivable – and the main telecommunications provider was just not interested.

Anyone interested in a similar project can contact John Harris at info@ihcs.com, or call 01636 682 244. An external broadband datalink aerial for domestic use.

![](_page_35_Picture_0.jpeg)

# DX and Satellite Reception

Terrestrial DX and satellite TV reception reports. Broadcast, satellite and digital TV news. Could Bluetooth be an interference problem? The early days of ITV. Roger Bunney reports

![](_page_35_Picture_3.jpeg)

Firework display as the Queen Mary-2 leaves Southampton on her maiden voyage. Picture from BT TES-9, downlinked via Telecom 2D.

R eception conditions have been poor at best so far this year, perhaps reflecting the dreadful weather up to the time of writing (end January). We can however look back on a reasonable year for DXing in 2003, with the bonus that propagation tended to be on a north-south axis, bringing in plenty of Band I signals from TVE (Spain).

Unfortunately at least one Band I TVE transmitter (ch. E4) closed down last July, and there are indications that the rest will follow before long. While on holiday in the Canary Is Garry Smith noted that Izana ch. E3 closed down on 10 December: it was there one morning at 0300 but not the next! Strange, as I had a report of reception on the 11th, while Hugh Cocks in Portugal reported on 5 January that Madrid ch. E2 and Izana ch. E3 were still on air. In an email on 28 January Hugh said he could not confirm Izana but that a steady video buzz could be heard in ch. E2 from the direction of Madrid, which suggests that Madrid was transmitting a caption rather than programmes. I'll probably have further news next time.

Digital terrestrial TV is to start in France within the next twelve months. By the end of 2005 it's expected that 60 per cent of the population will be covered, then increasing to an eventual 85 per cent.

Clearly there will be analogue TV closing dates in many countries across Europe over the next few years. Even the local RSL station Solent TV, on the Isle of Wight, tried to get included in a digital multiplex from Rowridge. Access was refused on the grounds that "there's no room". The multiplexes seem to have plenty of space to me!

### Satellite sightings

First, an easy one. Check out EPG no. 238 via Astra at 28·2°E. You'll probably find a channel called BEN, a curious selection of entertainment items. But, late at night, AFT (African Independent Television) appears. It consists of various items from African TV stations, including Nigeria and the SABC. Try after 2300 hours GMT.

Not such good news over at NSS-7 (21.5°W), where the CNN Newsource feeder has been telling subscribers to contact CNN for information on upgrading their receivers. It seems that from April the Atlantic CNN feed will be encrypted, using Scientific Atlanta scrambling, possibly PowerVu. A pity, as this frequency carried unique live relays of breaking news from affiliates across North America.

An Algerian multiplex appeared in mid-January via NSS-7, with Arabic- and French-language programming. There were four video channels (one unused) that had material from Algerian stations across the country, plus twenty or so radio channels. By late January the multiplex had disappeared, but may return. Check at 12·736GHz H (symbol rate 16.625, FEC 3/4). The uplink service was provided by Telediffusion d'Algerie. An Iranian TV channel popped up on Eutelsat W1 (10°E) at 11·155GHz V (5.632, 3/4), signing as TVBN 2 with a website (ertebatm@IRANNTV.com). The program cut abruptly at 2200 hours.

A scan over NSS-7 on the 17th revealed a couple of feeds with a religious theme. A presentation for the New Apostolic Church, LA. California, as part of the NAC TV Network, appeared to be live from the Los Angeles Central Church, Pasedena. It was uplinked by DSNG3 AMLX (identification with colours bars) at 11:659GHz H (5.632, 3/4). The other presentation, at 11:668GHz H (6.617, 3/4), was called Cap sur Jesus. This French-language programme started at 1750 and ended, including part repeats, at 1851.

There was a lot of evening sports from Germany in the middle of the month. A check at 10°E on a couple of evenings provided a rich variety for those feeling athletic. For example Friedrichafen v. Tours VB was a hard-fought volleyball match, uplinked by INTEAX 62/LBR at 11.016GHz H (6.109, 3/4), while ice-hockey action on an adjacent frequency (not logged!) appeared courtesy of AKK-TV UE6. Volleyball appears to be a popular sport in mid-Europe. On the 14th the Poland v. Holland match was downlinked via Eutelsat W2 (16°E) at 12.654GHz H (5.632, 3/4) by VTM DSNG 5 EN. For several nights German TV ran, also via W2, its version of a jungle celebrity challenge. Ich-bin-ein-B. This was at 12.548GHz H (5.632, 3/4). On 10 January there was local interest in the maiden voyage from Southampton of the Queen Mary-2. It was bad luck for Meridian Tonight, which broadcasts at 1800-1830 hours, that the QM-2 delayed its cast off. This could be seen live via the local BBC South programme, which is transmitted at 1830-1900! The BT sat truck Meridian 8MBI delayed its departure however, recording pictures from Hythe (opposite Southampton Docks) of the spectacular fireworks as the QM-2 slowly cruised into the night. These were downlinked, as usual, via Telecon 2B (8°W) at 12:592GHz H (5,632, 3/4).

Bomb outrages in Iraq continue. Reuters Baghdad has been using Europe\*Star-1 (45° E) for its intermittent feeds. A Germanlanguage VT package on troops' welfare was transmitted in the clear. A few days later there was a live feed for BBC2 Newsnight using MPEG 4:2:2. Check at 12·688GHz V (5,632, 3/4). The usually slumbering Sesat (36°E) was rudely awakened for Reuters Baghdad Flyway at 11·598GHz V with the unusual characteristics (for news feeds) of SR 27,500 and FEC 5/6. For its Iraqi news hookups APTN Baghdad continues to use Eutelsat W1, at 10·961GHz V (4,167, 5/6). CBS New York, entrenched at the Rimal Hotel, prefers to use W2, usually at 12·525GHz H (5,632, 3/4) or an adjacent frequency – its current service ident is simply 523209.

I rarely check Intelsat 707/Thor (1°W), but the capsized freighter tragedy in a Norwegian fjord in late January initiated a scan. What I found, at 11.659GHz H (5,632, 3/4), was the Baghdad output from ABC Scopus feeding NTSC to NY, possibly direct. It seems to be present much of the time. Roy Carman subsequently told me that there was a live feed from the fjord at 11.485GHz H (6,111, 3/4).

The BBC produced dramatic, live pictures via a videophone of the destruction caused by the earthquake at Bam, Iran at the end of December. It was a considerable improvement on the results seen during the invasion of Iraq last spring. The flyaway terminal UKI-511 Coder was quickly in operation on 1 January, showing live rescue operations. This was via W1 at 11·108GHz V (6,109, 5/6). There was an 'Iran Bam Default' at 10·980GHz V (6,109, 3/4) with live updates.

Live broadcasters were kept guessing for a few evenings as to when Flight BA223 would actually leave Heathrow for Washington. The BT TES-10 truck was present during the time, providing live reports for Sky News via W2 at II·127GHz H (5,632, 3/4).

The usual coverage of the Paris-Dakar rally was missing this year, but Roy Carman found a couple of live broadcasts via PanAmSat-1R (45°W), at 11.575 and 11.583GHz H (6,111, 3/4). He also drew my attention to increased activity via Intelsat 901 (18°W): there are German channels Bundestag at 11.586GHz, IVBB-BPK at 11.593GHz, IVBB-BPA at 11.598GHz and IVBB-Bundesra at 11.603GHz (all H with 3,906 and 3/4); also Prima TV, a Romanian channel, at 10.982GHz H (4,199, 3/4).

Intermittent news for INA News/www. ina.tv/UKI-801 is being carried by Hellas-Sat (39°E). Check at 11:082GHz V (5,632, 3/4) and 12:633GHz V (6,111, 3/4). There are also soft-porn offerings at 12:689GHz H (27,500, 3/4)!

Curious results were seen at 33°E, the E-Bird satellite. When I stopped my dish here on 15 January the 'spectrascope' display revealed several downlinks, but there was a cyclic movement of signal levels from normal to zero then up again. This was repeated over and over.

Our best wishes to corespondent Alan Richards who had to move from his mobile home near Nottingham when the site owner sold out to a property developer. He has relocated to Lincolnshire, and I hope to receive fresh reports from him soon.

#### **Broadcast** news

Malaya: The national TV network RTM-1 intends to start operating on a 24-hour basis by the middle of the year and plans to broadcast via satellite to Asia, Australia, the Middle East and Eastern Europe. For cost reasons downlinking will be via Chinese satellite capacity instead of Malaya's Mesat bird. The 8TV terrestrial channel started broadcasting in

![](_page_36_Picture_11.jpeg)

Is this a caption or a test card? Seen via Europe\*Star-1, from the news agency IHA in Afghanistan.

early January, with coverage along the heavily populated west coast, offering entertainment, music and news in Chinese and English. This is the fourth commercial TV service to open in Malaya.

France: Several DTT launch dates have been announced previously. The latest is December 2004 to March 2005.

South Korea: The country is to continue to use US analogue and digital TV standards. Tests of the US and European DTT systems have been going on for five years. The latter seems to have been rejected on cost grounds.

**Finland:** YLE has authorised the expansion of DTT across the country. 95 per cent of the population should be covered by this autumn, and most populated areas by late 2005 – low-power transmitters will be used for small settlements.

**Nigeria:** Channels Television, which is based at Abuja, has started to transmit from its studio site. This is unusual, as you can get interference problems when a transmitter is close to the studio.

The station expects to be available shortly across Africa in digital satellite form. It opened nine years ago and specialises in news and current affairs.

New Zealand: The Maori Television Service is due to start in mid-March in the North Island, the intention being to increase knowledge of and interest in Maori culture. It's a non-commercial, publicfunded channel.

**Iraq:** After much delay the contract to operate the Iraqi Media Network for the next twelve months has been awarded to the Harris Corporation (US). Two national TV channels, two radio services and a national newspaper are to be set up. Transmitters will be located in Baghdad and at thirty other locations across the country.

UK: A new RSL TV station has opened in York, using ch. 54. More information can be obtained from York TV on 01904 700 464 or by emailing info@york.tv

RSL service Solent TV has installed a new transmitter at Rowridge, increasing the output to 2kW ERP. Nicam stereo sound was introduced at the same time.

Iran/Azerbaijan: The Iranian TV channel Sahar-2 has resumed transmissions across the border to Azerbaijan, in retaliation for claims that Azerbaijan TV has been transmitting anti-Iranian material across the border to Iran. Late last year the two countries had signed an agreement to terminate the Sahar-2 transmissions to Azerbailan. Sahar-2 also broadcasts across the Middle East via satellite.

### Satellite news

Amos-2, the new Israeli satellite, was successfully launched on 28 December from Baikonur, Kazakhstan. The orbital slot is 4°W, where the footprint will cover Europe, the Middle East, North Africa and across into the Canadian Eastern Seaboard. It has 22 Ku-band transponders.

The new Telstar-14 at 63°W is just above the horizon in the UK for those with a flat take-off to the SW. This 41 Ku-band transponder satellite will be used mainly for coverage of Brazil, with additional capacity for North America and "the North Atlantic". In the latter region it will provide live connection to aircraft, on behalf of Boeing, for internet services. The launch was on 11 January from a platform in the Pacific, but once in orbit it was found to have deployed its northern solar panel only partially. Efforts are being made to correct this. If these fail, the effect will be a shortened life span.

The new Saudi news channel Al-Ikhbariya was launched on 11 January, initially with twelve hours a day of Arabic transmissions but with its output to be expanded to 24 hours a day, including Englishlanguage programming. The 'rolling news' format has been lacking with Saudi terrestrial channels and it is hoped that this will attract viewers. One aim is to provide an alternative to the mainstream channel Al-Jazeera, which most people in the region watch for breaking news. Al-Jazeera plans to open an English-language news channel later this year, from a studio at Doha in Qatar. It has high credibility in the region as a news source but operates on a tight budget, with funds derived from programme and advertising sales and the Qatar government.

The Hong-Kong based Star News channel has been given 'landing rights' for the sub-continent and permission to open a news base and uplink centre in India. The Indian government had for some years refused to allow Star access to ground-based operations in the country.

Satellite enthusiasts in Shanghai, China are being offered cheap dish systems despite it being illegal since 1993 to own and operate a satellite receiving terminal. Typical receiver prices range from \$US360 to \$US420. Odd that most domestic satellite receivers are now produced in China and incorporate the latest technology, such as the blind-search feature used in more complex models.

### **Band I filters**

I've received a letter from Ian Moody, a well-established TV-DXer, on the subject of Band I filtering. He has made several channel-pass filters for ch. E2, E3 or E4, using typically three pairs of tuned circuits. During the 2003 SpE season he found that local 49MHz interference was blocking out ch. E2. He was able to clear the interference with the filter design shown in Fig. 1, using the six trimmers C1-6 to peak the three pairs of tuned circuits in sequence. The filter was incorporated after the preamplifier to overcome, in part, the throughput losses. The design is straightforward and is inexpensive to make, but ensure that it is built in a metal, preferably diecast, case.

A previous wideband VHF amplifier design by Ian (select the required band with different inductors) has been further modified to reduce breakthrough problems – if you live next door to a main transmitter! A one input, two output version for DXing is being developed. Hopefully Ian will publish his design in these pages.

Ian draws attention to the following websites which are of general DX interest: http://www.g4fbz.freeserve.co.uk http://perso.libertysurf.co.uk/ade/knott/buttons.htm The former is run by William F. Kitching, G4FBZ, the latter by Adrian Knott, G6KSN.

![](_page_37_Figure_10.jpeg)

Fig. 1: lan Moody's channel-pass filter for ch. E2. The value for Ca is 4-7nF and for Cb is 18pF. C1-C6 are 2-10pF dielectric trimmers. L1-6 consist of 13 turns of 24 SWG EC wire, 5/32in. in diameter, close spaced.

![](_page_37_Picture_12.jpeg)

Channel information display provided by the Coship blind-search satellite receiver.

### Humpty Dumpty had a great fall

Here's a serious warning for those who ascend ladders to install aerials etc. For the past 35 years I've been rigging aerials, also a few dishes, have scaled roofs, chimneys and lattice masts, and have even replaced a few tiles. So, on 27 December, Mr Confidence is outdoors in the darkness on the platform of a 4ft high, three-rung domestic stepladder, completing a minor aerial task. I'm only about 8ft above ground. Then I reach across for the grease, and the ladder topples over complete with me. When I come round on a tarmac drive and roll away from the wreckage, I think that all bones and a hip have been broken. This is real pain. I eventually manage to stagger indoors.

A few days later I am still in pain and a large haematoma (caused by internal bleeding from ruptured blood vessels) has grown on my back and is enormous. The doctor says it will disperse in a few weeks. But it's very painful, and I may have to be 'referred'. Fortunately it does go down, but the pain in my legs, arm and back continued. The moral is obvious: never be over-confident on a ladder!

Bill of Wright's Aerials comments that most aerial-rigging accidents involve stepladders and low heights. When you think there can't be an accident, there may well be one. Bill says that the main dangers associated with aerial rigging have in his experience been stepladders, loft-access hatches, bad lifting technique, Yorkshire Terriers, traffic when working with the van on a busy road, rotten roof timbers – and too many others to recall.

I've not drawn attention to aerial-rigging dangers before in this column. It has taken an accident after 35 years to make me appreciate that even a short-distance fall can cause severe physical darnage and pain. So think safety!

### IN MEMORIAM

An old friend and DXer, George North, has passed away in Quito, Ecuador. He suffered a massive heart attack at the relatively young age of 48. In earlier years he had lived at Walton-on-Thames, then travelled across the Americas where he was able to obtain employment.

Grant Dixon, one of the pioneers of Amateur Television and a stalwart of the British Amateur TV Club (BATC), died on 20 December. He was born in 1916 and grew up with radio and television, building his first radio in 1927 and then, in the early Thirties, a 30-line spinning-disc televisor. He even introduced some improvements to John Logie Baird's mechanical colour system. In the post-war period he built 405-line sets for reception from Holme Moss and Alexandra Palace then, when amateur TV took off in the early Fifties, he joined the BATC. In 1955 he was first to start amateur TV colour transmission. Slow-scan TV was another of his interests. Grant's involvement with the BATC continued until 'retirement' in 1981. He continued to support the club for some years after that.

![](_page_38_Picture_0.jpeg)

# MONITORS

Fault reports from Gerry Mumford Ian Field and Bob Bradley

We welcome fault reports from readers – payment for each fault is made after publication.

Reports can be sent by post to:

Television Magazine Fault Reports, Highbury Business, Media House, Azalea Drive, Swanley, Kent BR8 8HU

or e-mailed to: t.winford@highburybiz.com

### SAM M1766-10

This quite old 17in. monitor appeared to be completely dead. But when the cover was removed a very slow and quiet ticking noise was just audible. A short-circuit was quickly found across the 75V output from the power supply. This feed goes to the CRT base board, where the video amplifiers live. Removal of the connector cleared the short. The cause was eventually found to be C258 (100nF, 100V), which is one of the many ceramic decoupling capacitors for this supply, mounted around the edge of the board. Once a replacement had been fitted the monitor powered up correctly and produced a perfect display. G.M.

### Panasonic E50i (TX5F71)

The fault symptom with this monitor was flickering colours: either red, blue or green would be missing from the display randomly. Visual inspection of the CRT base board revealed big dry-joints on the CRT socket. These were resoldered, then the monitor was given a soak test. After a few hours the colours started to fade away randomly – it was quite unlike the previous abrupt flickering. Application of heat and freezer showed that the cause was the 2SC945 transistors Q301, Q321 and Q341. The display was reliable once these had been replaced. G.M.

### Escom KT90-7134TL

The complaint with this Acer-made monitor (F8T version) was starts sometimes, more often the power LED flashes then no-go. Once or twice it stayed on long enough for a display to appear. I should have realised that it couldn't be the startup resistors R603/4 (33k $\Omega$ , 2W) as, once they start the monitor, a supply from the chopper transformer takes over. In fact the cause was the on/off switch.

There were no obvious signs of any failing low-value, high-voltage electrolytics. These seem to be grouped in a cluster next to the line output stage heatsink, by the EW driver transistor. Had the repair not been so simple, I would eventually have investigated the TO126-packaged transistors just forward of the cluster of electrolytics on the secondary side of the chopper power supply.

Instead of using a continuously-variable B+ PWM regulator, many Acer chassis use a selection of secondary tappings that are switched in as appropriate for the video mode in use. There is always one more voltage selection than the number of switching transistors, as the lowest voltage required is taken directly from the relevant rectifier. Switching to any higher voltage reverse-biases this 'default' diode. The lower-voltage selections are used for the slower scan rates, where the line output transistor is on for a longer time. If operated at too high a voltage the result would be excessive EHT or, in an extreme case, core saturation with the line output transistor having a short-circuit collector-base junction and the base-emitter junction tom open.

Failure of any of the B+ switching transistors can result in over-voltage protection shutdown. Since some of the choppersupply rectifiers also act as switches (turned off by a higher voltage being switched on to the B+ rail), failure of almost any of them could have produced the observed symptoms. **I.F.** 

### Dell D1428LS

This monitor was dead because the power supply failed to start. It uses a '3842 type control chip (Samsung KA3882). The start-up resistors were OK, and pin 7 had the required start-up voltage (16V), but there was no Vref supply at pin 8. There are several ways in which the chip can be shut down, and a lot of time was spent checking possible components. As every item I checked was found to be OK, in desperation I replaced the reservoir capacitor connected to pin 7, C616 ( $47\mu$ F, 25V). When I switched the monitor on again the power supply sprang to life! C616 read off the scale when checked with an ESR meter.

I subsequently had the same fault with another of these monitors. They both needed CRT reactivation to obtain a reasonable display. **I.F.** 

### IBM G74

This 17in. monitor failed to produce a display. But the green LED was on constantly after power was applied, with a somewhat disconcerting random flash. I didn't hear the EHT rustle up at switch on, so out came the EHT probe to confirm whether there was voltage at the CRT's anode cap. There wasn't. Some scope checks showed that the line drive was missing, while voltage checks showed that the outputs from the power supply all seemed to be correct. So I replaced the TDA4859 deflection processor IC. Unfortunately this didn't cure the fault.

I was beginning to suspect that the line output transformer (FBQ-17A001) might be faulty, but didn't have one available for a substitution test. So I decided to carry out a closer check on the power supply. This revealed that the 13V output was on the low side. I then removed various capacitors to check them individually and found that C622 (1,000 $\mu$ F, 25V) produced a poor ESR reading. A replacement capacitor cleared the fault. **B.B.** 

![](_page_39_Picture_0.jpeg)

# AUDIO FAULTS

Reports from Eugene Trundle Roy Blaber David I Scott Keith Wevill Philip Rosbottom and Geoff Darby

We welcome fault reports from readers – payment for each fault is made after publication.

Reports can be sent by post to:

Television Magazine Fault Reports, Highbury Business, Media House, Azalea Drive, Swanley, Kent BR8 8HU

or e-mailed to: t.winford@highburybiz.com

### Sony TA-VE100

This is a surround-sound 'multi-amplifier'. The problem with it was intermittent crackling and cutting out – probably because the overload-protection circuit was coming into operation. On investigation I found that there were dry-joints at the leadouts of two of the four power-amplifier chips, and at the legs of the two 12V regulator chips IC402 and IC403. The leadout wires of these warm-running devices should be double-kinked to take thermal expansion into account: this would remove the stress from the soldered joints. E.T.

### Denon DRA265R

No sound was the problem with this amplifier. Checks around the sound output transistors revealed that TR323 (2SA1633) was short-circuit collector-to-emitter while TR317 (2SD667) had been getting very hot. In addition R329 (330 $\Omega$ ), R331 and R333 (both 0·22 $\Omega$ ) were either open-circuit or burnt. Normal operation was restored by replacing these components and attending to various dry-joints, which I think were the initial cause of the failures. **R.B.** 

### Peavy Studio Pro 112

"Loud buzzing without any other sound" said the report that accompanied this Chinese-made guitar amplifier. The point was proved when it was plugged in, the very loud hum confirming that there was at least a power-supply fault.

Construction differs from most audio equipment. The pre- and power amplifiers, control circuitry and power supply are built into a chassis that's housed at the top of the unit. A separate unit for reverberation etc. is mounted at the bottom of the cabinet, with the heavy-duty speaker frontmounted. At the rear there are sockets for special effects, remote operation and an external loudspeaker. Clearly the cause of the problem lay in the main chassis, which had to be removed (several screws plus leads to the lower chassis and the speaker) before diagnosis could begin.

Once this had been done I was surprised to find that the bridge rectifier had overheated to the extent that its case was being melted. I replaced it and the associated reservoir capacitors but the fault was still present. Attention was turned to the output section, where I found that some 40V DC with a high ripple content was present at the output terminal of the LM3886T power-amplifier IC. As this was directly coupled to the loudspeaker it was evident why such a loud hum was present!

A replacement LM3886T chip cured the fault but left me wondering what had caused the failure in the first place. It was likely that a short-circuit external speaker cable had damaged the power amplifier IC. overloaded the positive and negative power supplies and led to failure of the bridge rectifier.

The power-supply design is interesting, being based on a transformer with a centretapped secondary winding. The centre tap is used in conjunction with the bridge rectifier, which is fed from the ends of the secondary winding and provides separate positive and negative supplies. **D.I.S.** 

### Marantz CD73

Having seen how much these 20-year old CD players are being sold for on the internet I decided to retrieve mine from the back of the cupboard and power it up. There was no illumination from one of the track-indicator LEDs and hum in both channels. When a CD was played there was considerable distortion in both channels. Several years earlier I had cured a similar distortion fault by replacing the LM317T 5V regulator and ensuring that there was thermal grease between this IC and the heatsink. This time I replaced all the electrolytics, using 105°C capacitors. This cured the hum, the distortion and the lack of light from the track indicator LED.

These capacitors lead a hard life, as they are next to a heatsink that runs hot – the player consumes 45W. Incidentally the service manual shows that the decoder is fitted with Philips ICs, but in my CD73 a Sony decoder board is fitted.

Now that it's fixed, what am I bid?! K.W.

### Technics SU8055

One of this 50W amplifier's channels had failed. Replacing the encapsulated output transistors restored normal operation – they are similar to the STK module package. **P.R.** 

### Yamaha CR1000

This classic tuner-amplifier from the Seventies didn't produce any output. You first have to remove the chassis from the wooden sleeve. Make sure that the tuning cursor is towards the left-hand side of the scale, or a bracket will rip the wires from the pointer bulb. Remove the screws at the left- and right-hand sides of the front, and two screws just behind the tuner PCB. The whole of the front then pivots upwards, revealing the power supply PCB. The front two transistors are  $\pm/-$  regulators for the supplies to the driver stages in the power amplifier. The right-hand one ( $\pm$ 50V) dies because of an inadequate heatsink.

Another of these units had low output with distortion. At the back of the powersupply board there's a mute signal (MU) that swings from about 0V to -15V at switch on. Two wires are connected to this. One goes to a PCB that swings up with the chassis, to mute the preamplifier output. I never did find out where the other one goes to, but there's a similarly coloured wire on the tuner PCB. This second wire produced a low-resistance reading to chassis. Leaving it disconnected cured the fault and didn't cause any problems. **P.R.** 

### Akai GX912

This is a semi-pro cassette deck that dates from the late Eighties. During eject the left-hand pinch wheel fouled the cassette holder. The grease on the pivot had solidified, which prevented the mechanism from returning to the rest position. Stripping and cleaning provided a cure. **P.R.** 

### Sony TA88

This mini-amplifier dates from 1975. The right-hand channel produced terrible noises. I found that the two input transistors on the power amplifier PCB had horrid dry-joints. Blanket resoldering gave the unit a new lease of life. **P.R.** 

### Sony MZ-R501

When this personal MD recorder came in the season for 'sand in the works' had just ended. I don't know in which part of the world the MiniDisc sand-burying championships take place, but wherever it is the grains are microscopic and exactly the right size to fit in all the gear teeth... This one had been rejected elsewhere as being beyond economic repair. Over the years I've repaired many of these recorders because of the sand problem, and have never found one to be uneconomic to repair. What is needed is a fair amount of patience and, if your eyes are anything like mine, appropriate optical assistance.

It's not a particularly lengthy job if you strip the unit properly. You will need to remove the lid from the upper chassis, the bottom cover, the PCB and the main chassis from the sub-chassis. When the main chassis has been separated, remove the laser unit and its drive gears. All this should take no longer than fifteen minutes.

You now need to employ a strong light source and a bench or head-band magnifier, a soft brush, and a scalpel tip to remove the sand grains from everywhere they have lodged. You must, at this stage, make your best effort to find every last grain and get it out. If you leave as much as one stray grain in the unit, I guarantee that it will find its way into a gear tooth two days before your repair warranty runs out.

Check wherever there is grease very carefully, particularly behind the doorcatch slide. Check gear teeth in minute detail. The tiniest obstruction here will cause trouble as the motors, being so small, are only just powerful enough to do their job.

Once you've removed every grain that

you can see, I recommend that you take a coffee break and let your eyes settle for a few minutes. When you return to the bench, check all the components again. You will inevitably find a couple of grains that you missed the first time round. The clean-up procedure normally takes 20-30 minutes, including coffee.

Finally, rebuild the unit in the reverse order, reapplying grease wherever you've cleaned it off. When the deck has had the laser refitted, check that the optical block runs smoothly up and down its track. Also check that the overwrite head up/down drive and motor run smoothly.

Once the unit has been fully reassembled, run the auto-diagnostic/set-up program. This should be done after any repair to a personal MD player, particularly after a major mechanical rebuild. This will ensure that correction is applied for all deck and electronic tolerances. Note however that the program can be run successfully only by using the official Sony test discs. While other discs may appear to work for some tests, the results can be unreliable.

If you've worked on the job steadily, the grand total of time taken should be about an hour. I've found that the owners of these recorders are prepared to pay well for a repair. A replacement is expensive, and your repair bill is likely to be less than the excess on their insurance policy. **G.D.** 

# Test Case 496

The fault descriptions provided by some customers can be very wide of the mark. As an example, a recent patient in the workshop, a Tatung Model T25TE61 (E-series chassis), had with it a note saying "negative picture". Cathode Ray, who had been assigned to this repair, concluded that the receiver was set up for the wrong TV transmission standard, even before it arrived at his bench – in fact he had the service manual open at the software-option bytes page by the time it got there. When he switched the set on however it produced a bright pink picture, with bad streaking in red from all picture highlights. He suspected the tube itself, and plugged in his trusty tube tester – after discharging the residual EHT voltage held by the bowl's coatings of course. The tester proclaimed that the tube was OK, though with somewhat tired emission. So it seemed that the cause of the fault had to be elsewhere.

To be certain about this, Ray interchanged the red and blue cathode drives at the tube base panel. Sure enough the picture now came up with excessive blue on the screen. This exonerated the tube and pointed to the red video drive circuit as the cause of the trouble. The original connections were then restored, so that Ray could start to look for clues. He began by playing with the customer controls, and found that with zero colour and very low brightness and contrast settings a picture with almost normal overall hue could be obtained. As the control settings were advanced, the red flared up again. An oscilloscope connected to the tube's red cathode told a similar story: the black-level voltage was about the same as with the G and B drives, but the signal amplitude (drive) in the red channel was much greater. To confirm that the fault was on the tube base panel, Ray next checked at the signal inputs to the panel. At pin 3 of PL902 the R-signal amplitude, with a monochrome input, was identical to the G- and B-signal amplitudes at pins 1 and 2. So the fault was proved to be on the tube base panel, but where? There are over twenty components in each channel here, with a cascode driver stage and a complementary-symmetry output stage in each one.

Ray vaguely recalled trouble with the load resistors in the driver stages. There are three series-connected  $6.8k\Omega$  resistors in each channel. He started by checking those in the red driver stage, R907/8/9. They were all OK. He then disconnected two legs of each of the four transistors in the red channel, and again carried out checks with his ohmmeter. The transistors produced normal readings. The four 1N4148 diodes in the circuit were next given the same treatment, which proved correct conduction and no leakage. Was this 'blind' passive component testing the right way to tackle the problem? It seems that it was as far as Cathode Ray was concerned: he eventually found the culprit, with the aid of Television Ted. It was not conduction in the PCB itself, as he was beginning to suspect! By the time a normal picture had been restored, Ray had spent over two hours on his diagnosis. A more experienced (or more thoughtful?) technician might have spent fifteen minutes or maybe less.

So where did the problem lie, and could it have been sussed out with less physical activity? For the solution, turn to page 379.

![](_page_41_Picture_0.jpeg)

# **Extended** Fault Reports

**Reports on complex or** tricky TV fault conditions are sometimes too long for inclusion in our regular fault-finding section. We've put a few of them together in this extended fault report feature

> **Reports from** Martin J. Abbott and David I. Scott

### Hitachi C2186TN (A7 chassis, **3D** stereo)

There were no off-air signals with this set: the screen remained blank and the volume control had no effect. Sound and picture were normal with an AV input. I replaced the ST24W16-1 EEPROM chip IC005. which had been corrupted - the replacement was obtained from Chas Hyde.

Before you start on the process of setting up it's worth noting that this is a multi-system capable set and that, peculiar

to modern Hitachi TV sets, an external AV input can be assigned to any channel by programming the manual-tuning menu.

All service-mode adjustments produce bar-graph displays. I found it helpful to measure the bar lengths with a tape measure and keep a record of these before taking out the old memory chip. It also saved time to take a note of the customised naming and frequencies on the manual-tuning menu. These can be re-entered - it saves having to do this in the customer's home.

The far-right box on the manual-tuning menu has to be set to system I. If it is set to DK or BG the sound will be poor. If you are pre-setting all the frequencies manually, it's easy to go down each box, setting the correct system letter. Likewise the second box from the right has to be set to the correct input. When the new EEP-ROM was fitted this box had 'mon' in it. For tuner input selection, leave this box blank.

Under the tuner adjustment heading in the service mode no system box should be ticked except I (for the UK). There's a list of 34 models under options. You have to select the correct one.

If you decide to reset the bar indicators by measurement, the horizontal adjustments must be carried out first. M.J.A.

### Mitsubishi CT25A5STX (Euro 14SF chassis)

"Faultless for ten years" this set's owner said. There was certainly plenty of dust inside. The set was now dead apart from the initial degaussing action. My first step was to disconnect the HT feed to the line output stage and fit a dummy load (60W bulb) with a voltmeter across it. When I switched on again the bulb glowed dimly and, surprisingly, the HT was correct at 145V. So the basic problem was excessive loading on the power supply. It didn't take long to find the cause: the 2SD1555 line output transistor (Q551) was very leaky.

The dilemma I then faced was what had caused the transistor's failure? Excessive HT is the usual culprit. but didn't seem to be the cause this time. But as a precaution I replaced the usual two suspect capacitors, C905 (470µF) and C914 (47µF), and carried out a blanket resoldering in the line driver/output stages. A check on the HT after doing this showed that it was still steady at 145V

All was revealed when the HT feed to the line output stage was reconnected and power was applied. The set burst into life, accompanied by sparking from the S-correction capacitor C567, whose rivet connection had burnt away from the PCB. This hadn't been obvious before, because the joint is hidden by a red wire strap that's glued on top of it. A PCB clean up, followed fresh solder, completely cured the problem – and I had the satisfaction of knowing what the original fault mechanism had been. D.I.S.

### Sharp 66FW-53H (DA100 chassis)

The fault originally reported with this set was that the picture was displaced upwards, i.e. the top inch or so of the picture/text was missing, though the field linearity was apparently correct. Before I had a chance to look at it however a more serious problem had arisen: the set was stuck in standby.

Investigation showed that the power supply had shut down because of a virtually full short-circuit across the 150V HT supply. There was severe leakage in the BUH515 line output transistor Q601. As I couldn't see anything else wrong, I assumed that an excessively high HT supply had killed the transistor. So I replaced Q601 and, in addition, the MOC8106 regulation feedback optocoupler IC705.

When I switched the set on everything seemed to be working and I could see the original offset picture symptom. But I then noticed random picture-width variations, which could be instigated by tapping the PCB. Careful examination of the PCB revealed several poor joints, the most serious being at R613 where one end barely penetrated the board and C613 which was completely dry-jointed at the end connected to the line scan coils. In addition C611 and R624, whose leads were oxidised, hadn't been soldered properly. Once these connections had been remade the line scanning was rock steady, and I concluded that the dry-joints, not high HT voltage. had been the cause of Q601's failure.

All that was needed to complete the repair was to enter the service mode, adjust the vertical centring and store the new setting. After that I gave the set a lengthy soak test. D.I.S.

# Profilo Telra Brand New PT92 Complete Working PCB's (Widescreen Version)

As used in the following makes of TV Bush, Fidelity, Wharfedale, Akura, JMB, Naiko & Watson

# **BUY ONE GET ONE FREE**

Buy one carton of Perfect PCB's and get one carton of damaged PCB's FREE for spares Only £90 per carton + VAT Carton content 9 panels Next day Carriage £9.95 Most major credit cards accepted Showroom ready B-grade stock also available For more information contact Contact Ian Botterill Key Electronics Ltd 01388 819525

![](_page_43_Picture_0.jpeg)

# **TV FAULT** FINDING

Reports from Michael Dranfield Dave Husband Philip Salkeld Philip Laws Dave Packham James Grant David Kerrod Les Mainstone Bob Flynn and Martyn S. Davis

We welcome fault reports from readers – payment for each fault is made after publication.

Reports can be sent by post to:

Television Magazine Fault Reports, Highbury Business, Media House, Azalea Drive, Swanley, Kent BR8 8HU

or e-mailed to: t.winford@highburybiz.com

### Goodmans GTV34T6SIL (Vestel 11AK36 chassis)

I have had this fault several times with sets that are fitted with the 11AK36 chassis – various brands use it. The symptom is EHT brushing lines on the picture, i.e. a horizontal ripple that changes with beam current. In days gone by it could, with the Philips G11 chassis, be cured by replacing the EHT lead assembly – assuming that the cap had not fallen off and got stuck in the line output transformer. The first time I came across the problem with the 11AK36 chassis I assumed that a new line

output transformer would be required, but this is not so.

If you peel the rubber seal back from the base of the EHT lead you can prise out the EHT wire. In all the sets I've come across with this problem there has been green corrosion on the wire. It must have been there from new, as none of the sets showed any other signs of dampness – and the rubber seal appears to be watertight. Clean off the corrosion and everything should be OK. M.D.

### Matsui 28DW01

This set, which has a built-in digital decoder, was tripping. The customer said that smoke had come from the back 1 told him that the cause could be a faulty line output transformer, which would be expensive. The line output transistor was OK however, and there was no burning apparent on the transformer. I then noticed that a hole had been burnt in the front of the TA8427K field output chip. A check on the associated flyback boost capacitor C421 ( $100\mu$ F, 35V) showed that it was open-circuit. So this is why the IC had failed.

When I had replaced these two items the set continued to trip. I found that the 27V supply rectifier D411 was short-circuit. It's marked G6, but a BYW36 works well in this position. M.D.

### Akura AB280W-S

This set was tripping. In between trips it displayed a blank white screen. A check revealed that the HT voltage was low and contained HF hash. The cause was the smoothing capacitor C627 ( $100\mu$ F, 200V), which was open-circuit. Once it had been replaced the set came on normally but with very low contrast.

This cannot be adjusted without the remote-control unit, so I phoned the customer and told him that there may or may not be another fault but I needed the remote-control unit in order to check on this. He then told me that over the past few months he had been lowering the contrast as this kept the set running for longer. Funny that he failed to mention that when he brought the set in. **M.D.** 

### Sharp 56FW-53H (DA100 chassis)

If the set is dead and R613 ( $3\cdot 3k\Omega$ , 3W) in the line output stage is getting red hot, check the line scan coupling capacitor C613 (560nF, 250V). R613 is part of a network that shunts C613. You might also find that the 2SD2391 EW modulator driver transistor Q506 has been damaged. M.D.

### Hitachi C2156TN-311

There was a colour purity problem with this set, so I replaced the posistor in the degaussing circuit. The replacement made no difference, and the coils tested OK. What next? I then spotted a 2AT glass fuse, F902, near the degaussing posistor. It was open-circuit. It's the first time I have come across a separate fuse for the degaussing circuit. **M.D.** 

### Toshiba 32WD98B (C95S chassis)

At switch on this widesceen set produced an HT supply of 60V for a second then shut down, with zero HT and no light from the standby LED. When I carried out a random check on the components in the power supply I found that the two 22V zener diodes D810 and D818 on the primary side were short-circuit. I replaced them and confidently restored power. There was full HT (125V). a burst of EHT, then the HT voltage dropped to 60V with, this time, the standby LED remaining alight.

The power supply operation is similar to that in the C5SS chassis, so I looked at the article on this chassis in the April 2003 issue. It suggested that the symptom can be caused by an excessive load on the line-output stage derived 27V supply. This is used by the LA7846N field output chip, so I fitted a replacement. At switch on the set worked normally – but why had the two zener diodes in the power supply failed? **D.H.** 

### Bush WS6673 (11AK19 chassis)

When this just out of guarantee set was powered the LED glowed red as normal. It should turn to green when the set is brought out of standby. Instead it went out then came back in red. The BUZ90AF chopper transistor was overheating, so I decided to carry out some cold checks. This brought me to D807 (MR852). which was short-circuit – it's in the snubber network. A replacement restored normal operation. I've not seen these symptoms before with the 11AK19 chassis. **P.S.** 

### Beko NR21231ND

This set was dead. A check on the HT voltage produced a low reading of 30V, though no short-circuits were apparent. I decided to remove the BU808DF1 line output transistor T552 and try again. This time the HT voltage was correct. Resistance checks between the pins of the transistor produced lowish readings, and when I looked at the PCB I noticed a dryjoint at C555 (7.5nF). A quick resolder and a new line output transistor restored normal operation. The transistor is available from SEME at a very reasonable price. **P.S.** 

### Sharp 66FW-53H (DA50W chassis)

A number of these sets have come in recently with excessive width and EW distortion. The important thing is to establish in which part of the circuit the fault lies. The control signal comes from pin 32 of the video/deflection processor chip IC801, where a parabolic waveform should be present. Enter the service mode, select EW width and adjust it (use the volume minus and plus buttons). If the waveform varies horizontally, you know that the IC801 is OK. So the cause of the fault will be in the drive or output circuitry. The possibilities here are Q506, L603. L604, D502, D503, D504, D516 and C528. Provided Q506 (2SD2391, part no. RH-TX0151BMZZ) is OK, the most likely offender is L603 (part no. RCLIP0286BMZZ) which develops shorted turns. **P.S.** 

### LG WF32A12T (MC52C chassis)

This set was totally dead. On inspection 1 found that C810 (470 $\mu$ F, 16V) was swollen and IC801 (STR-S6709) had blown in half. The set was OK once these two items had been replaced. IC801's part no. is 01SK670900A. **P.S.** 

### Beko NR28128NX

I've not previously had the no-sound symptom with this model. On investigation I found that R417 ( $0.1\Omega$ , 0.5W) in the LT feed to the TDA1521 audio output chip IC601 was open-circuit. It seemed likely that IC601 was faulty and had been the cause of R417's failure. All was well once these two items had been replaced. **P.S.** 

### Tatung T14RF71 (F series chassis)

This portable was stuck in standby. Voltage and resistance checks produced no clues as to the cause. So the hairdryer and freezer were brought into action, paying particular attention to the power supply. This restored normal working. Time and patience brought me to zener diode D409, which was the actual cause of the fault. Its part no. is 6615016730. **P.S.** 

### Samsung WS28W6NG

This set was tripping, with the relay chattering. The power supply ran normally when the feed to the line output stage was disconnected, but the symptom returned when a dummy load was connected. The HT reservoir capacitor  $(330\mu F, 200V)$ was open-circuit. **P.L.** 

### Sanyo 25DN2

This set reverted to standby after a few seconds, with the LED flashing. Pin 45 of IC801 seemed to be a good place to start. as it's labelled protection. Sure enough the voltage here was low at 1V instead of 4.7V. A long drawn-out process followed, while I checked the various protection lines. They are mostly connected via diodes, and are thus easy to check. I found that D445 was conducting. It seems to monitor the CRT heaters! When I disconnected D445 and switched the set on again it worked, with the picture intermittently fading. The cause of the problem was simply a dry-joint at R451 in the heater feed line. P.L.

### Samsung CI5079T

The original fault with this set had been a dead power supply. I obtained and fitted

the repair kit, then found that the HT output was only 75V. The line output stage worked to the extent that it was producing outputs, though these were not correct. When the feed to the line output transformer was disconnected the HT rose to approximately 150V.

I have to thank Samsung technical for help with this one. Make sure that you have removed the mica washer from IC801 and cleaned the compound from the heat sync. **D.P.** 

### Thomson 28DG24U (ICC17 chassis)

The standby light flashed twice then seven times – error code 27. This usually means a faulty line output transformer or field output IC, or the supply to it, but not this time. I disabled the protection circuit by connecting the collector of transistor TL71 to chassis, but the set still flashed error code 27. I then tried disconnecting the inputs to TL71, DL72, DL73 and DL74. Still no change.

A check on the HT line (Usys), using a scope with DC input, produced a reading of about 170V for the brief moment during which the EHT rustled up. With this 4:3 set (A66EHJ43X15 CRT) it should have been 132V. Cold checks in the HT sensing network revealed that RP63 (432k $\Omega$ ) had risen in value to 570k $\Omega$ . A replacement cured the problem.

This sort of fault used to be quite common with many makes of sets. I hate these ones! J.G.

### Panasonic TX24DX1

For the first half an hour there was no teletext, only the header page number. The cause, proved by a squirt of freezer. was the microcontroller chip IC1101 (type SDA5450C59). **D.K.** 

### Panasonic TX28PL1 (Euro-4 chassis)

If there's no picture, with very low-contrast text and graphics and the sound OK, replace the EEPROM chip IC1103 (X240RZ-0 GA). Do a self-check after replacing it, by pressing the status button on the remote-control unit and the V- button on the set then switching off with the mains switch. Switch on again, retune and run the set for about 45 minutes to allow for auto grey-scaling. **D.K.** 

### Hitachi C2164TN

This set was dead. When I dismantled it I found that it was in very poor condition, with dry-joints all round the power supply. These were attended to, and all the electrolytics on the primary side were replaced at this stage. Some proved to be leaky, but they weren't the cause of the

problem. The start-up resistor R901 ( $82k\Omega$ , 1W) was faulty. L.M.

### Panasonic TX25MD3/TX28LD1 (Euro-2 chassis)

These two sets arrived within a day or two of each other. One had a good picture and sound for a short time, then the picture gradually faded out. At first I thought that the CRT's heater voltage was dropping. The second set produced a reasonable picture except that there were faded vertical yellow bars down the left-hand side, in a band about six inches wide. In both sets the cause of the trouble was eventually traced to the VDP3108-PP-A1 chip IC601. Sadly, because of the price of the chip, only one estimate was accepted. L.M.

### Hitachi C2858TN (GQ8 chassis)

This set was dead. Checks in the power supply revealed that zener diode ZD901 was short-circuit. So there was no supply to the UC3844 chopper-control chip IC901. I replaced these two items, and the two series-connected chopper transistors Q901 and Q902. When I switched the set on again the HT at the secondary side of the chopper circuit was almost normal but was pulsing, with the twin front indicators flashing. Checks in the line output stage showed that the S2000AF output transistor Q702 was leaky.

A new S2000AF produced an EHT rustle for a few seconds each time the set was switched on. Attention was then turned to the LT supplies and, after much delving, the 12V regulator IC932 (7812) was found to be leaky. The smoothing capacitor at its output, C937 (1 $\mu$ F, 50V). read only 0.5 $\mu$ F. These two items were replaced, along with C933 (2,200 $\mu$ F, 25V). The set then remained on, but the sides of the picture were bowed in. The cause was the TEA2031A EW control/driver chip IC651. Fortunately a fairly high estimate had been accepted by the customer. L.M.

### Sony KV32FX20U (BE3E chassis)

This heavy monster sat on my bench ticking loudly. When I isolated the power supply it ran normally, so attention was turned to the line output stage where I found that the 2SC5251 output transistor was short-circuit. A replacement was obtained and fitted, then the set was powered via a variac. At 160V input the line output transistor died a horrible death, emitting a loud crack in the process.

My home-made line output transformer tester, coupled to my scope, told me that the transformer was OK. But it seemed the most likely cause of the trouble. The expensive replacement, along with another transistor, finally restored normal operation. L.M.

### Proline CTV28N1-T

At switch on this fairly new set produced a bright white screen with flyback lines. A check on the 200V supply at the CRT base panel showed that it was missing. The relevant rectifier is D28 (BA157), which was short-circuit. Naturally the  $4.7\Omega$  safety resistor R174 was open-circuit. Replacement of these two items cured the fault. L.M.

### Alba CTV3419 (11AK36 chassis)

When this set was first turned on there was no sign of life. There would then be a crackle on the sound, after which a picture would appear with tearing and interference that gradually cleared. The item to replace is C822 (470 $\mu$ F, 16V), which gets slowly cooked by a nearby regulator. Use a high-temperature capacitor. **B.F.** 

### Philips 14PV162

The 4Å input fuse in this combi unit had blown, but no short-circuits could be found. At switch on with a new fuse fitted a cloud of smoke appeared from the degaussing posistor and the fuse blew again. The posistor was a black one with the marking T209-9716 on its case. The more usual type 96209 was fitted in another of these units, so I used this type as the replacement. **B.F.** 

### Sharp C3703H (7PS chassis)

Power would be lost intermittently. The fault could be instigated by pressure on the board, but no obvious dry-joints could be found. Investigation with a magnifying glass however revealed a problem connection at D502. Resoldering this cured the fault. **B.F.** 

### Matsui 2890

The sound was OK but the screen was blacked out because of field collapse. Voltages are marked on the main PCB, and I found that the 28V supply was missing. It comes from the power supply panel, where R515 ( $3\cdot3\Omega$ , 1W) was open-circuit. No reason could be found for its failure, but a lot of poor joints in the field and line stages were in need of attention. **B.F.** 

### Sharp 59DS-03H (CA10 chassis)

The line output transistor was short-circuit because of a faulty capacitor, C613 (680nF, 250V). After replacing these two items there was field collapse with a smell of burning. Q501 (IRFR9020) and Q502 (IRFR010TM) had failed, and as a result F601 and F602 (both 1.5A) were opencircuit. You can obtain the necessary parts from Charles Hyde – a BUH515 transistor (order no. SH1054), a 680nF, 250V capacitor (order no. SH2094) an IRFR9020 transistor (order no. SH919) and an IRFR010TM transistor (order no. SH920). **B.F.** 

### Proline 28N1 (F19 chassis)

D25 (BA157) had burnt to a cinder. I dealt with some poor connections and fitted a new diode. When I switched on there was an oversized picture with bowed sides. The cure was to replace C69 (22nF, 400V). **B.F.** 

### Philips L6.1 chassis

After a while the picture would collapse to a line down the centre of the screen (line collapse). This was cured by replacing C2422 (560nF, 250V). When the set was working again most channels would constantly flick off tune then back on again: any station that remained on looked off-tune. Coil L5100 in the IF circuit was found to be intermittent. **B.F.** 

### Bush 1438 (11AK20S chassis)

The height was reduced to about an inch. Before it became permanent the fault had been intermittent. The cause was D702 (1N4007) which was breaking down intermittently. **B.F.** 

### Sanyo 24WN4

There was no red in the picture. Scope checks seemed to show that the TDA6103Q RGB output chip IC701 on the tube base panel was faulty, but a replacement failed to restore the red picture content. To prove that the red gun in the CRT was OK, I carefully desoldered and wired the blue and then green drives to the red cathode. This cleared the tube of suspicion and I subsequently found that R706 ( $100k\Omega$ ) was open-circuit. It biases the red input to IC701, and had probably died with the chip. The TDA6103Q is part no. 4094688403. **M.S.D.** 

### Sanyo 28WN4

There was no red in the picture. This set came in at the same time as the 24WN4 (see above) in which the cause of the trouble was on the tube base panel. In this case however there was an open-circuit gun within the 28in. tube. I used the same technique to prove exactly where the fault was: careful desoldering/soldering to link the green/blue drives to the red cathode (no picture) and the red drive to the blue/green cathodes (this did produce a picture). This was quite an unusual fault, as in my experience tube guns tend to go short-circuit. A new tube provided a full cure. **M.S.D.** 

![](_page_46_Picture_0.jpeg)

VCR CLINIC

Reports from Eugene Trundle Roy Blaber Dean Ratcliffe David Kerrod Mike Leach and Michael Dranfield

We welcome fault reports from readers – payment for each fault is made after publication.

Reports can be sent by post to:

Television Magazine Fault Reports, Highbury Business, Media House, Azalea Drive, Swanley, Kent BR8 8HU

or e-mailed to: t.winford@highburybiz.com

### Wharfedale NV6

There was a very elusive intermittent fault with this machine, which was barely a year old. When selecting or changing a deck mode it would sometimes shut down with an ERROR caption in its display. The cause is the grease used in the rotary mode switch. The cure is to dismantle and degrease the switch, clean the stator and rotor fingers with a fibre pen, retension the tingers then reassemble it with a whiff of switch cleaner. My thanks to Key Electronics for this tip.

Incidentally this is the first VCR I've come across with no cassette LED and no end sensors. It's got a very clever microcontroller instead. E.T.

### Hitachi VT-M610EUK

With an RF output the E-E and playback sound were spasmodic, sometimes drowned by a vision-type buzz. Sound from the scart socket was consistently good. I found that the symptom could be made to come and go by wiggling the aerial input plug and socket. There was a dry-joint inside the tuner/modulator assembly, at one of the earthing lugs between the sockets and the first IC.

This VCR is similar inside to many **Philips** models. **E.T.** 

### Toshiba V632

The complaint with this VCR was that the picture rolled when it played back its own recordings. There were also obvious head-switching problems with prerecorded tapes. The cure is to play back a test tape, wait for the machine to finish auto-tracking, press SW703 then the SP/LP button on the remote-control unit. Switch off to store. SW703 is hidden behind the front of the machine. **R.B.** 

### Sanyo VHR3100

This old machine had lines across the screen in the E-E mode, similar to co-channel interference. Checks in the power supply led me to C11 (1 $\mu$ F) which was the cause. **R.B.** 

### Hitachi VTFX860

The front display was OK in standby but went out when the machine was turned on. This seemed odd until I realised that the machine uses an LC display. Three LEDs are used to light the display dimly in standby. Conventional lamps are used when the machine is brought out of standby. All three were open-circuit. Old cassette lamps proved to be OK. **R.B.** 

### Ferguson FV33H

This old Nicam machine wouldn't restart after a power cut. I used my ESR meter to carry out some checks on the primary side of the power supply and found that C13 (180 $\mu$ F) and C14 (1 $\mu$ F) were virtually opencircuit. As 180 $\mu$ F is an unusual value I fitted a 220 $\mu$ F capacitor in this position. **R.B.** 

### Sharp VCM27HM

There was no playback colour. The cause was dry-joints at crystal X501 on the main PCB. D.R.

### Panasonic NVHV60

This VCR was completely dead. I found that the start-up feed resistor R1150 ( $1M\Omega$ ) was open-circuit. **D.K.** 

### Akai VSJ719EK-N

For no functions, no display and the standby light flashing, try replacing C116  $(1,000\mu$ F, 16V) in the power supply. I fitted a capacitor rated at 25V to be on the safe side. M.L.

### Panasonic NVSJ220B-S

The tape would be ejected immediately after loading. It's becoming a common symptom with various different machines nowadays. In this case the fault was cured by replacing the capstan motor. The problems didn't end there however. The machine subsequently came back with a report that said "erratic play". It would sometimes unlace then lace up again, sometimes fast rewind wouldn't operate properly, and sometimes the machine would just shut down. These problems were eventually cleared by replacing the two take-up sensors IC1501 and IC1502 on the main PCB.

How can a machine develop two different, genuine faults at the same time, such as a duff capstan motor and faulty sensors as in this case? I'll just file it under 'one of those things'. where most stuff seems to end up nowadays! M.L.

#### Sony SLVSE720

This machine is made by Samsung and is fitted with the Scorpio II chassis. The silkscreen printing is incorrect in one position and because of this C701 (470 $\mu$ F, 16V) in the AL5V supply is inserted the wrong way round. Sony seems to think that fitting a new capacitor the right way round will prevent corruption of the EEPROM - typical symptoms are display not lit. no video playback picture, incorrect head switching or incorrect front-panel button operation. This is not the case however. If you simply replace C701 and reprogram the EEPROM the machine will fail again later. The true cause is the surface-mounted microcontroller chip.

You may, depending on how corrupt the EEPROM has become, have difficulty using the hidden switch to enter the service mode. In this case press any button on the front panel. This will provide access to the EEP-ROM map. M.D.

![](_page_47_Picture_0.jpeg)

![](_page_47_Picture_1.jpeg)

Fault reports from Chris Bowers and Geoff Darby

We welcome fault reports from readers – payment for each fault is made after publication.

Reports can be sent by post to:

Television Magazine Fault Reports, Highbury Business, Media House, Azalea Drive, Swanley, Kent BR8 8HU

or e-mailed to: t.winford@highburybiz.com

### Sony DVP-NS705V

This DVD player was dead, i.e. there was no power up. Multimeter checks on the power board showed that IC101 was short-circuit. As a result, D103 had gone open-circuit. A check with Sony revealed that IC101 has to be replaced with a new. improved device, part no. 9-885-030-35. I managed to obtain a replacement diode from a spare board in the workshop. This was fortunate, as the diode is not available from Sony as a separate part: a full power-board block has to be ordered. Replacement of the two items restored normal operation.

Note that power boards with part nos. 1-468-648-12 and 1-468-651-13 are already fitted with the new IC. C.B.

#### Sony HT-BE1

At power up this unit produced a load chirp from all the speakers. The cause of the problem was C914 ( $47\mu$ F, 50V). Simply replace it to restore the normal power-up sound. C.B.

#### Aiwa HT-DV90HK

The job ticket said that this home-cinema unit "went bang". In view of this suggestion of violent behaviour I removed the top before applying power. As visual inspection of the chopper power supply didn't reveal any major problems and the mains fuse was intact. I plugged in. The power supply remained dead.

I then checked with an ohmmeter between each pin of the mains plug and each pin of the power supply's mains input connector, and found that there was continuity between the live pin of the 13A plugtop and the blue wire going to the power supply and between the neutral pin and the brown wire. Oh dear!

The 13A plugtop is actually an adaptor that links the moulded-on 2-pin Europlug (non-polarised) and a standard UK plug, enabling the manufacturer to use the same mains lead throughout the EU. The top of this adaptor hinges open when the screw is undone, the 2-pin Europlug sitting inside the space with its pin tips connected to a pair of brass hooks that are connected to the 13A pins. I've never been happy with this arrangement, as the Europlug can be reversed within the body of the adaptor. This probably isn't a problem with transformer-isolated equipment, but could be with a chopper power supply

- depending on the front-end design. Whether the adaptor had come from the factory like it or whether the owner had undone it and inadvertently reversed the Europlug is hard to say. If he was looking for a fuse, the one concerned is readily and clearly accessible from outside the adaptor. In my opinion the screw that secures the adaptor should at least be a tamperproof type, not a regular Phillipshead type.

Having fitted the Europlug the right way round and confirmed that the live pin was now connected to the brown wire, I removed the power supply from the unit. There's a plastic cover under the 'hot' end of the PCB. Through this two added components could be seen, with large amounts of black glue around them and stuck to the cover. There was a nice blast mark between them.

I finally managed to unstick the cover and clean up around these components, then saw that about 1cm of print between them had been vaporised. They appeared to be resistors which were soldered to tracks that came directly from the vicinity of the mains bridge rectifier. The bodies of these resistors had been sleeved but, unbelievably, the legs had been left as bare wire. Where one of these was pressed right down to the PCB it had shorted to an adjacent track and blown it out.

When you consider the onus that is placed on us as engineers to carry out reliable and, above all, electrically safe repairs, it beggars belief that manufacturers can get away with such poorly-executed modifications, which are at best going to be unreliable and at worst downright dangerous.

Once the positions of the resistors had been redressed and the exposed legs had been sleeved I repaired the blown-out printed track. After that the unit came to life and worked normally.

As a final point with this repair, two very thin flexiprints connect the front panel to the main PCB. They pass over the power supply, lying against a heatsink that runs too hot to touch. There was just enough slack to pull them to one side and Tywrap them to the power supply's output harness. I also noticed that every hotspot in the power supply has an electrolytic capacitor sited by it, and that there are no cabinet ventilation slots over the power supply. So the units should be good earners in the not too distant future, when these capacitors start to fail. **G.D.** 

Economic Devices PO BOX 73; Ozkergates TF2 BWR For Hot 74 (0)1952 273130 Fac ++44 (0)1952 27310 Fac	
Stock held for over 53000 different models SEMICONDUCTORS over 340000 types of trensisters, IC's, disclose of consultations stocked We take your hassle Some suppliers just won't help. We will work really hard to find those difficult parts - just ask and let our 'no holds barred' enquiry hound work for you. [ ]	
special offers. BUT11A@ Deach BUT11AF @ Deach BU508A@ EDeach Fully wired scart lead Deach a slight inconvenience	Rin
BU208A X 5 75p ea TEA2018A X 5 99p ea BU508A X 5 79p ea UC3842 X 5 59p ea BU508AF X 5 85p ea CNX62A X 5 29p ea BU508D X 5 85p ea S2000AF X 5 84p ea BUT11A X 5 29p ea TDA3653B X 5 55p ea BUT11AF X 5 47p ea TDA3654 X 5 82p ea Phillps type 1,2 volt Back up battery X 5 120p ea Phillps type 2,4 volt Back up battery X 5 120p ea Phillps type 2,4 volt Back up battery X 5 120p ea Phillps type 2,4 volt Back up battery X 5 120p ea Positor PT37,TH98009 (White) X 5 59p ea Phom TX100 Chassis 110 DGR LOPTX each £11,24 Phillps CP90 Chassis LOPTX each £11.63 CHART COMPARENT CO	
the verb says e first you can be due to the proceeding of the same set of the verb says e first you can be due to the proceeding of the same set of the verb says the same set of the verb same set of the v	ι "Πη
ONLINE SHOPPING CHEAPER AND EASIER www.elclondon.co.uk	FR Look A pho result range
	databa

![](_page_48_Picture_1.jpeg)

ELC EAST LONDON COMPONENTS 63 PLASHET GROVE, LONDON E6 1AD. TWO MINUTES WALK FROM UPTON PARK TUBE STATION TEL: 020 8472 4871 FAX: 020 8503 5926 E-mail: sales@elclondon.co.uk

![](_page_48_Picture_3.jpeg)

# LETTERS

![](_page_49_Picture_1.jpeg)

### The Philips LO1 chassis

Thank you Brian Storm for an excellent article on this chassis (March issue). The protection circuitry in the line output stage is quite elaborate, so it may be helpful to show this. I've sketched it out in Fig. 1. Brian Storm explained the basic action of the circuits connected to pin 7 of the line output transformer in his article. The beam current is also monitored for protection (and limiting) purposes. This is done at pin 10 of the line output transformer, i.e. the earthy end of the EHT system. There's a connection between this and pin 11 of the UOC chip IC7200. When the voltage at pin 11 of this IC exceeds 6V the line drive at pin 30 is switched off. The voltage at pin 11 then falls and line drive is restored after the slow-start procedure. There is also a link between the beam current monitoring line and the circuitry shown in Fig. 1. via R3247. Cuthbert Merryweather. London W4.

### Send letters to "Television", Highbury Business, Media House, Azalea Drive, Swanley, Kent, BR8 8HU or e-mail t.winford@highburybiz.com using subject heading 'Television Letters'.

Please send plain text messages. Do NOT send attachments. Be sure to type your full name, address, postcode, telephone and e-mail address (if any). Your address and telephone number will not be published but your e-mail address will unless you state otherwise.

Please send ONLY text intended for the letters page. Correspondence relating to subscriptions and other matters must be sent to the office address given above.

![](_page_49_Figure_7.jpeg)

Fig. 1: Protection circuitry in the line output stage, Philips L01 chassis.

### Picture quality and an aerial mystery

I would like to support the view expressed by Martin McCluskey in his letter last month. With the current trend to larger screens, picture quality matters more. I have installed Freeview for my elderly parents, and find that the results via the RGB scart connection look decidedly soft. When I change the digibox to video, then use the sharpness control on the ninemonths old TV set, the picture is almost as good as with an analogue signal.

I certainly agree with the comments about the Philips G8 chassis. I am still using one as my main TV set, though the tube was changed about 18 years ago. I have two others in working condition, with their original tubes.

I wonder if anyone could clear up a mystery? In the late Sixties my parents had a combined Band I/III aerial installed. It was of the H type, with five Band III elements in front of the Band I dipole. After two-three years the Band I elements all fell off. This seemed to happen with lots of similar types of aerial, though others have remained intact. A few weeks ago my parents had the guttering replaced. and the missing elements were found there. I was amazed to discover that they were filled with coaxial cable. This explained why they had snapped off so quickly, because of the weight in them. But what was the coaxial cable in the elements for? Do any older aerial riggers know the answer? Could it have been to shorten the aerial life deliberately? Steve Ball.

### Peterborough.

I agree with Martin McCluskey's comments in the March issue about digital picture quality, but would like to go further – what about the sound quality? It's a fact that with digital terrestrial transmissions the dynamic sound range is much narrower in comparison with analogue terrestrial transmissions. So the public misses out on two fronts, poor picture and poor sound. Why? As always, the simple answer is money. Why transmit one very goodquality channel when, by lowering the data transmission rate, you can transmit two channels in the same bandwidth?

More channels introduces another problem, one that's even more significant than lower-quality pictures and lower-quality sound: more programmes are needed to fill the gaps between the adverts! Hence reality and lifestyle TV. Fills lots of airtime at minimum cost.

So, in its current format, digital offers the public lower picture quality, lower sound quality and poorer programme content – now at a lower retail price of £60. Yet another winner for our trade then! John Halstead. Sent by email.

### Burn ups

Several letters and articles in past issues have commented on fire hazards with TV set PCBs. In computer monitors the small, resin-covered high-voltage ceramic disc capacitors tend to burn up. They don't seem to be able to cope with high-frequency, high-voltage stresses.

The small ceramic capacitors in Acer monitor line output stages often burn up. So do the ones used on the inverter board in LCD flat-screen monitors made by NEC. The customer complains of smoke from the monitor, and you find that the inverter PCB is a blackened, charred mess, the cause being a 22pF, 3kV capacitor that goes short-circuit and burns the board. I wonder if these capacitors were designed for lower-frequency operation? *Mark Garton*, *Bromsgrove*.

### Scam messages

Further to the letters on this subject in the January and February issues, I thought I had better mention another scam that's going about. I've had it in the form of a text message that says "you have won £1,000 cash or a £2,000 prize". To claim you are told to phone an 087 number, then you are asked to ring an 09 number from a land line. This number costs £1.50 a minute, and the call can last about ten minutes. As soon as I was told that I had to ring 09## I saw three lemons whizzing before my eyes, as if on a one-armed bandit. I simply said this sounds like a scam and not to ring again. Two days later this scam was reported on, I think, ITV News 24. It was said to come from abroad.

Nothing to do with TV servicing, but it's best to be warned. David Smith, Leigh, Lancs.

![](_page_50_Picture_9.jpeg)

The help wanted column is intended to assist readers who require a part, circuit etc not generally available. Requests are published at the discretion of the editor.

Send them to the editorial department or email to t winford@highburybiz.com

Wanted/for sale: I need a uPD552C-045 microcontroller chip, or a used display driver card, for the Ferguson VCR Model 3V23 (or JVC HR7700). Have for sale the following parts from a brand new, unused but damaged current Decca Model 21N21B2: CRT

(A51LMV10X16), LOPT, tuner, remotecontrol unit, chopper transformer, all ICs, speaker etc. – but no case or PCB. £25 the lot. Phone David Scott on 01564 779 003 (evenings) or email

david@scott6692.freeserve.co.uk Wanted: IC type M5840H-84 for the Philips Model 16CT2216 (CTX-E chassis). Laurie Jones, 56 Southridge Rise, Crowborough, E. Sussex, TN6 1LQ. Phone 01892 654 867.

Wanted: Circuit diagram for the Goodmans Compact 210 TV set (sold by Comet). Photocopy OK. Any help appreciated. R.E. Potter, 9 Monks Brook Close, Eastleigh, Hants, SO50 9NQ. Wanted: Does anyone know of an equivalent for the E13007F2 chopper transistor used in the Acoustic Solutions Model DVD451? I have had intermittent start-up problems with this unit, but replacing the start-up resistors and all the electrolytics in the power supply hasn't helped. When the units work they are fine: all the supply lines are smooth and stabilised. Has anyone solved this problem? I suspect that other models in other brand ranges use the same power supply unit. Roger Burchett, Haytor, Stone Street, Lympne, Hythe, Kent, CT21 4JY. Phone 01303 267 969. For sale: *Television* magazines from 1984 to date, £50; 1,700 service manuals (TV, VCR, audio, MWO, miscellaneous) £50. Lawrence Smith, 12 Swanzy Road, Sevenoakes, Kent, TN14 5EE. Phone 01892 664 821.

Wanted: A number of encoder/decoder chips type UM3750. Peter Ward, Petgra, Forest Corner, Ringwood, Hants, BH24 3JW. Phone 01425 475 445.

Wanted: Remote-control units for the Sony VCR Models SLV70 and SLV315 (they were lost during a house move). Willing to pay. Phone Derek on 01722 335 590.

Wanted: For spares, Quad 33 or 44 control units and 303 or 405 power amplifiers. Also panels and boards for these models. Working or non-working. Phone Mike on 01758 613 790.

Wanted/for sale: Require a power supply panel for the Tandberg Model CTV2-6-133, new if possible or from an existing set. This 26in. model with remote control was top of the CTV2 range. Have for sale a Tandberg Model CTV1 and a new A56-540X tube. S. Mann, 12 Levens Way, Silverdale, Carnforth, Lancashire, LA5 OTG. Phone/fax 01524 701 431. Wanted/for sale: Require a circuit diagram for the Xcom Multimedia Xsat CDTV200 digital satellite receiver. Have for sale a Telequipment D32 10MHz, dual-trace portable oscilloscope with leather case. It works with battery or mains powering but needs a service. £75 o.n.o. Vi Smith, 175 Lyon Park Avenue, Wembley, Middx, HA0 4HD. Phone 020 8902 5447.

For sale: A 37in. Grundig Model M95-1159 IDTV set with PIP, remote-control unit, cabinet and circuit diagram. In 'good condition' with good tube. Also a Philips projection set, Model 46PP912A-05 (PTV FL1 AB chassis), in good condition complete with remote-control unit. All tubes OK. Went off in a power cut. Neither set works but could be repaired or used for spares. Phone G. Howe on 01502 713 942.

Wanted/for disposal: Require a tuning scale and a telescopic aerial for the Grundig Yacht Boy 202E radio. Have for disposal the following: a Decca Model CS2032 fitted with the Bradford chassis; a JVC CR-6000E U-matic VCR; and a Rank 55 405/625-line pattern generator. Also the following CRTs: A66-510; 560DYB22 (56-001); 560BWB22. Michael Ashley, South Normanton, Derbyshire. Please email mick@mickash.fsnet.co.uk Wanted: Video heads for the Sony SLC9UB Betamax video, Sony part no. DSR-21R. Phone Andy on 01902 880063.

# To reserve your web site space telephone Tel: 01322 611289 Fax: 01322 616339 E-MAILS L.Baldock@highburybiz.com

![](_page_51_Picture_1.jpeg)

SERVICE

### **Alban Electronics**

http://www.albanelectronics.co.uk

Alban stocks, supplies and provides technical support for a range of terrestrial/cable/satellite and analogue/ digital TV equipment. PROMAX (manufacturers electronic test equipment including signal level meters, spectrum analysers, BER/CSI/MER analysers for QPSK, QAM & COFDM, optical fibre light sources and power meters, 16:9 test pattern generators), ALCAD (manufacturers of R.F. wide band and adjacent channel amplifiers, aerials for MATV, SMATV & IRS systems) and ANTARES (cascadeable multi-switches). ALBAN has a complete after sales repair and calibration service that is fully supported by the manufacturers, in addition provides a free system design service using only reliable high quality components.

### **Irwin Electronics**

http://www.irwinelectronics.co.uk

As Classic Distributors we complement our existing mail and trade counter business with our website. You can order parts on-line quickly and easily. We intend to explore alternative ways of assisting engineers to run their business successfully.

![](_page_51_Picture_8.jpeg)

### Alltrade Aerials & Satellite Ltd

www.alltrade.co.uk

Leading distributor to the trade Full e-commerce site with over 1500 products with in-stock quantities! We supply everything associated with Digital/Analogue Terrestrial & DTH/Motorised Satellite reception. • All Antennas • All Brackets •

All Cables
All Amplifiers
We provide a free MATV/SMATV planning service as well.
Phone 0845 075 0751
Fax 01273 425700

![](_page_51_Picture_13.jpeg)

![](_page_51_Picture_14.jpeg)

### Repairhelper's – Storefinder UK

www.storefinder.repairhelper.co.uk

We specialise in promoting electronic repair services throughout the Internet. It's a well known fact that the Internet is the fastest growing advertising medium today but the majority of repair companies and repair engineers are not making use of the Internet to gain more custom. Repairhelper's Storefinder is a UK Search Engine dedicated to the electronic repair trade (i.e. TV, VCR, DVD repair etc). Sign up with Repairhelper's Storefinder - you get your own optimized pre-built web page with a built-in online contact form and complete listings within the Repairhelper Network of sites.

### Charles Hyde & Son Ltd

http://www.charleshyde.co.uk

Search for both original and copy spare parts in our extensive database covering Akai, Alba, Bush, Ferguson, Goldstar, Hitachi, LG, Matsui, Nokia, Saisho, Sanyo, Sony, Sharp, Thomson, Panasonic, Philips, Samsung, Tascam, Teac, Toshiba, Yamaha and many more. In addition huge ranges of Lasers, Lopts, Remote controls and Semiconductors may be accessed.

![](_page_52_Picture_0.jpeg)

### **Swires Research**

### http://www.swires.com

Swires Research produce high quality instruments for the television industry, including portable signal level meters and spectrum analysers for digital and analogue RF signal measurements.

### **J W Hardy Communications**

http://www.jwhardy.co.uk

R.F. Network Specialist. Shop online - for R.F. network components. We supply a full range of TV, radio reception equipment to receive analogue/digital signals from both terrestrial and satellite sources. We provide a free planning service for your R.F. networks, MATV and SMATV etc

![](_page_52_Picture_7.jpeg)

### **Televes**

http://www.televes.com

Televes website was launched as an easier way to keep in contact with our World-wide Network of Subsidiaries and Clients. This site is constantly updated with useful information/news plus you can download info on our range: TV Aerials & accessories, Domestic and Distribution amplifiers, Systems Equipment for DTT and Analogue TV, Meters and much more.

![](_page_52_Picture_11.jpeg)

### Wiltsgrove

http://www.wiltsgrove.co.uk

WILTSGROVE LTD founded in 1984, is renowned as a leading supplier of Audio, Video, TV, Spare parts and Accessories. We are now pleased to announce the

launch of our ONLINE CATALOGUE:

### http://www.wiltsgrove.co.uk

Our easy to use search engine will allow you to find the products you require via:

- Make / Model.
- Product Category.
- Key Word search.
- Manufacturers part number.

• Our Order Code. All orders before 5pm will be dispatched the same day.

Tel: (0121) 772 2733 Fax: (0121) 766 6100 Email: sales@wiltsgrove.co.uk

## Make sure of your copy of Television

It can be difficult finding a copy of *Television* at local newsagents. The number of magazines being published keeps increasing, which means that newsagents have less shelf space for the display of individual titles. Specialist magazines in particular get crowded out.

There's a solution to the problem. Most newsagents provide "shop-save" and/or home-delivery services. There's no charge for a shop save. You simply ask your newsagent to order a copy for you: it will be kept on one side each month ready for you to collect. Home-delivered copies are ordered in the same way, but generally incur a delivery charge.

A newsagent can order any magazine for you, whether or not the shop normally stocks it.

If you buy your copies of *Television* from a newsagent and want to make sure you get every issue, just ask at the counter.

# TELEVISION BOOKS

The Television Book Service offers access to our team of specialist publishing experts. We can order any book or CD-ROM currently in print from War And Peace to the Newnes Guide to Television and Video Technology. All books are delivered free of charge within the UK unless otherwise stated. Contact us at the numbers below:

### Telephone: 01737 812727 or 01737 812676

Fax: 01737 813526

Email: salesteam@boffinbooks.demon.co.uk

![](_page_53_Picture_5.jpeg)

### **CLOSED CIRCUIT TELEVISION: CCTV** INSTALLATION. MAINTENANCE AND OPERATION

**DICTIONARY OF** 

**VIDEO AND** 

**TELEVISION** 

Jack Tsatsoulin

Published in UK

Code 1 878707 99 X

**TECHNOLOGY** 

This work provides comprehensive and contemporary information on the essential

concepts and terms in video and television,

including coverage of test and measurement procedures. The CD accompanying the text

includes an electronic version of the book.

Sept 2002 🔺 365 pages & CD-Rom

£29.99

![](_page_53_Picture_7.jpeg)

CCTV surveillance is one of the fastest growing areas in the security industry, and this is a tharaugh guide to the technical side of CCTV including installation, maintenance, video recording, cameras and monitors. The second edition is fully dual-standard for PAL and NTSC systems.

2nd edition A Sept 2003 A 256 pages Glossary A Index A PB A Published in UK £24.99 Code 0 7506 5728 6

![](_page_53_Picture_10.jpeg)

![](_page_53_Picture_11.jpeg)

![](_page_54_Picture_0.jpeg)

![](_page_55_Picture_0.jpeg)

# WHAT A LIFE!

### The shop to myself for a while. Some faulty TVs and a dead VCR. Then a visit from the shop steward... Donald Bullock's servicing commentary.

They are clever lads. "There's a fine new restaurant in town" Steven said to Greeneyes and me the other day as we were closing the shop, "and Paul and I would like to take you both out for a meal tonight." In less than no time we were enjoying the best nosh-up of our lives, wine and all. So instead of being suspicious when, afterwards, they gave us a great joint smile, I smiled back benignly. Then they drove us back home. They're good lads.

"Oh, there's just one thing" they said when we reached the door. "We've got a little trip planned for tomorrow morning, down Meadow Pool way. Pike spinning, you know. Won't take us many hours. Do you think you could open the shop and look after things until we arrive a little later?"

Well of course I didn't mind. and said so. "Take as long as you like" I added. "Oh, and there's one other little thing"

Steven said, "we've a couple of repair jobs due in soon after eight. Best open the shop at eight instead of nine, wouldn't you think?"

#### **Next morning**

At twenty past eight next morning a car drew up outside and a sleek, gentle figure, like a dressed-up and bearded eel, slid out. The day had hardly begun, yet he was smiling happily.

"Ah, you will be being Mr Bullock!" he said softly, "the 'old man' as your sons say."

I shot him a look.

"I am being Mr Ng, and very pleased to meet you."

"I am being, er, pleased to meet you too" I replied, pulling on the best smile I could muster at twenty past eight. "What is being the aah" then I couldn't control a big yawn. "Sorry about that – television trouble is it?"

"Yes indeed. My misfortune, your gain!" he smiled, "so it is being good

for you that I am unfortunate you see." We managed to extract two sets from

his car, a monster widescreen Bush model and an Aiwa TV/VCR combi unit. Then he was off.

### Mr Ng's sets

The Bush set was fitted with the 11AK19 chassis and was stuck in standby. As I was the only one there, I had no choice but to have a go at it myself. I began by getting to the chassis and giving it a keen examination in the hope of discovering a simple remedy. like a dryjoint. Yes, there it was! A beauty at the anode of D825 in the power supply. Although it had been arcing, the diode was undamaged. I resoldered it feverishly, then tried the set again. To my delight the EHT rustled up and the screen brightened. But there was no video, just a bright screen with no display

I noticed a video output IC on the tube base panel and decided that it could well be the cause of the problem. I was right. It's a TDA6108JF, and the lads had one in stuck. When I fitted it the set produced an exceptionally good picture.

The Aiwa combi was slow to start up from cold. When it did, it produced murky video and audio wow from our test tape. I have always found that the cause of the trouble is, with these units, low-capacitance electrolytics. This one was no exception. C523 ( $100\mu$ F, 16V) had fallen in value to  $60\mu$ F, and C522 ( $2\cdot2\mu$ F, 50V) had fallen to  $1\mu$ F. Replacements cured the trouble.

#### Interlude

As I was boxing the unit up the telephone rang. I made a grab at the phone, which slipped off the counter. "What's the bloody matter" I barked when I recovered it just before it hit the ground.

"Mrs Wellington-Harper here" an educated voice boomed. "My tom cat Marmaduke is bothering Phyllis, my brand new, delightful little girl cat. Will you come out and, er, attend to Marmaduke for me?"

"No" I snarled, and slammed the phone down.

It rang again, and once more I rattled it from its rest. "What is it now?" I shouted.

"What do you mean, Mr Bullock, what is it now?" bumbled an ancient voice. "I haven't telephoned you since 1992."

I wiped my face with my dry hand. "Oh, hello, Mr Dodd" I said, "er, ha ha, was that a crossed line we had there? These things happen, don't they? Ha ha."

"What an odd fellow he must have been" said Old Dodder, "hope he's done - for good."

"Sure to be" I continued, "now what can I do for you Mr Dodd?"

#### A Beko

"It's my telly, Mr Bullock. A Beko it is. Got it in Snoddies Sale last week. But when I told the tall thin chap there that it had gone wrong he was most unhelpful, unpleasant in fact, and hung up. Shall I ask my sister Molly to help me bring it along?"

"Er, good idea Mr Dodd" I replied, "in fact spot on!"

There was a pause. "What's 'spot on' Mr Bullock?" he asked.

"Well yes, do bring it along" I said, then gently hung up.

A little while later he drew up outside in his car, with his woolly sister. I went out to help them carry the Beko in. He was tugging it from his side of the car.

"Lift your end, Molly" he shouted "now push it to me."

"No, you push it to me" Molly said. Old Dodder straightened. "Molly,

you're not being at all helpful. Just confusing things. Same as always."

"Stop bullying me Cyril. Did you hear

that, Mr Bullock? He's always been the same."

I waved to them to stop, grabbed the set and took it into the shop.

Old Dodder toddled in after me. "Can I visit your loo?" he ventured. "Over there" I said, then hastily

moved Mr Ng's Bush out of the way.

The Beko was stuck in standby. I checked the line output transistor and found that it was short-circuit. So I fitted a replacement and tried again. The core of the line output transformer then arced violently to the chassis. It was type 1352-5048. The HR8368 is an equivalent and, after finding one in the stores, I fitted it. The set then produced an excellent picture.

Old Dodder reappeared. "Oh that's good" he said when he saw the set. I suppose I must owe you some money." "You've got it in one" I smiled.

Old Dodder stepped back and looked at me. "What do you mean, Mr

Bullock, I've got it in one?" he asked. Molly had come in. "Cyril" she exclaimed, "concentrate on the Beko.

I'm glad we chose it instead of the one you wanted."

"You backed a winner" I pronounced. Old Dodder frowned. "A winner, Mr Bullock? My sister doesn't bet on horses, you know."

"Definitely not" Molly rejoined.

#### **Another Beko**

As the old pair left I saw that they had forgotten their umbrella, and picked it up to chase after them. But just then Greeneyes came in, looking quite ravishing in the new green and beige outfit she had worn the week before for son James's wedding to Dawn at Porthmadog in North Wales. And, as if by magic, Mr Flighty also entered the shop, jauntily with his fetching smile and pencil moustache. He was wearing a cravat and a black blazer with a gaudy. club-type red and gold crest. "Hello dear" he sang out to

Greeneyes, "my you do look sparklingly attractive today. As always, of course."

Greeneyes smiled demurely and, at that, Flighty pretended to notice me for the first time.

"Oh, hello Donald old chap. My! Time passes! Bad night last night? Still on the tablets? Do you always carry an umbrella, Donald?"

I smiled at him as best as I could manage. "Some sort of trouble, Mr Flighty?" I enquired.

"Well yeah, Don. It's a Beko telly that belongs to my neighbour. She's a young widow, poor thing ...," "I understand," I said simply.

He did a double-take at my sincere face. "Er, black lines keep coming and going on the picture. When they appear there's none of the usual writing to tell us what it's on. Only I'd like to help her, you know ...."

"I'm sure you would" I replied. "why not bring it in then?"

He went back out to his car and returned with the set, a Beko Model NR20242-8R. Then he smirked at Greeneyes and departed.

We've had this trouble before. The TV trouble, I mean. It led us a merry dance until we discovered the cause, which is a tiny 1,000pF surface-mounted capacitor, C410. It often disintegrates as soon as it's warmed by the iron.

I fitted a replacement then turned to Greeneyes. "What shall we charge him dear. Eighty quid maybe?"

"How could you!" she exclaimed. "Aw, well, it would be quite easy" I said.

#### A Mitsubishi VCR

Colonel Starch marched in shortly afterwards. He retired twenty five years ago and still goes on and on.

"Hello Donald, old boy" he rasped, pumping my hand energetically. "Always good to see you, and your charming young wife. What a lucky chap you are! And so you should be. One of us. True British! But, as you know Donald, my dear wife is so silly. Bought one of those Jap video recorders. Against my advice, I might add. Told her British is best! Always was!"

"Er, what did she buy?" I ventured.

"Told you! I'll go get the thing in." He strode off to his vintage car and returned with a Mitsubishi VCR, Model HS641V.

"Says she can't see the dial thing, or whatever it is" he continued. "Don't know why she'd want to, but there it is! We have to make allowances, I suppose." When he'd departed I put it on the bench. It was dead, with no display. Faults like this mean something wrong in the power supply of course. Sure enough one of the outputs was very low indeed. The relevant reservoir capacitor is C910 ( $4.7\mu$ F, 50V). I wasn't surprised to find that it was opencircuit. A replacement worked wonders, with everything then working correctly.

#### The shop steward

During the late afternoon, as I was beginning to look at my watch, we had our last caller that day. He was a forthright, formidable-looking fellow. We soon learnt that he was Jim Fargill, the top shop steward at a nearby factory.

"Still working hard at this end of the day?" he commented. "You want to join a union, you know. What's your boss like? I'll bet he's taking it easy somewhere luxurious."

I wondered whether he meant Steven or Greeneyes, but never mind. We need his patronage.

"Look" he said, raising his left palm and tapping it with the forefinger of his right hand. "Point 1, I've got a

Goodmans TVC46 combi unit, right?" I nodded.

"Right. Point 2 it's as dead as a doornail, right?"

I nodded again.

"Point 3, I want it repaired. Got it? Can you manage that?"

I nodded weakly, then he went out and returned with the TV/VCR unit. He placed it on the counter, shook my hand and announced that he would be back the following day.

I was feeling tired, but opened the unit and headed for the power supply section. An easy one. The power switch SW08 was badly dry-jointed.

I resoldered it and tried the machine out. There didn't seem to be anything wrong with it, so I boxed it up and turned to Greeneyes

"Time for home I think, dear" I said.

#### Keep it up!

Many thanks to all who have sent me interesting emails recently. These are welcome, and I'll be commenting on some of the points raised. You can reach me at

donald@ wheatleypress.com

![](_page_57_Picture_0.jpeg)

# SATELLITE NOTEBOOK

Reports from Christopher Holland Hugh Cocks Michael Dranfield and Robert Philpot

### Audio narrative setting

From time to time we receive a complaint from a customer about someone speaking in parallel with the main sound track, describing what's happening on the screen at the time. This happens particularly with channel 5. The cause is that some programmes have an added audio narrative track to assist those who are visually impaired to follow the action.

To prevent a digibox adding narration to the sound, go to the 'System Setup' menu, choose option 3 'Language and Subtitles', and change the 'Favourite Language/Audio' setting from 'Narrative' (see Photo 1) to 'English'. If it's set to another language. say Italian, this will be heard on the Euronews channel (EPG no. 528) and any other channel that transmits the relevant soundtrack. C.H.

### **Digital channel update**

The latest channel additions at  $28 \cdot 2^{\circ}E$  are listed in Table 1. Where allocated, the EPG number is shown in brackets after the channel name.

The various radio channels mentioned last month, via Eurobird transponder D9S (11-623GHz H), have been given the following EPG numbers: Kiss Radio 920. Smash Hits 922. Kerrang 928. The Hits 929, Magic 930, Mojo 931, Q 932 and Heat Radio 933. **C.H.** 

### Recording MPEG-2 signals on a DVD

I recently installed a DVD recorder drive in my PC. It can be used in conjunction with the PC-based SkyStar 2 satellite receiver (described in the September 2003 issue of *Television*) to record material on a DVD for playback via any DVD player – this provides an alternative to recording on the hard disk. This month I'll describe installation of the drive and becoming

![](_page_57_Picture_12.jpeg)

Photo 1: Favourite Language/Audio setting with a Sky digibox.

![](_page_57_Picture_14.jpeg)

Photo 2: The software disc with DVD-RAM driver on it.

![](_page_57_Picture_16.jpeg)

Photo 3: Windows has assigned letter F to the new driver.

![](_page_57_Picture_18.jpeg)

Photo 4: Georgian TV via Express 3A at 11°W.

familiar with its use: next month I'll deal with recording off-air signals.

The drive  $\overline{I}$  installed was an LG GSA4040B, which cost less than  $\pounds 100 - it$  has since been replaced by the GSA8081B. It works with DVD+R/RW.

![](_page_58_Picture_0.jpeg)

Photo 5: Georgian TV via Express 3A at 11°W.

![](_page_58_Picture_2.jpeg)

Photo 6: Kurdsat TV via Express 3A at 11°W.

![](_page_58_Picture_4.jpeg)

Photo 7: A Mediaset feed via Express 3A at 11°W.

![](_page_58_Picture_6.jpeg)

Photo 8: An RAI feed via Express 3A at 11°W.

### Table 1: Latest digital channel changes at 28.2°E

Channel and EPG no. Sat		ТР	Frequency/pa
Globecast test card	EB	D12S	11.681GHz/V
Information TV (692)	EB	D9S	11.623GHz/H
UK History + 1	2A	15	11.922GHz/H
TP - transponder EB - Eu	robird 2	$\Lambda = \Lambda otro 2\Lambda$	

IP = transponder. EB = Eurobird. 2A = Astra 2A.

DVD-R/RW and DVD-RAM discs, also CD-R and CD-RW discs, but will record on only single-layer, 4.7GB DVDs (sometimes referred to as DVD 5 discs, while dual-layer types are referred to as DVD 9 discs). Drives for dual-layer. 9.4GB recordable DVDs are due to become available later this year. At the time of writing there is debate as to whether these recordable dual-layer discs will be readable by many existing DVD players, which should work fine with current prerecorded DVD 9 discs.

Drive installation is straightforward. The minimum PC requirements are a 700MHz Pentium processor, 128MB of RAM. 5GB of spare hard-disk space and a Windows 98 or later operating system. Full fitting instructions come in a booklet that's supplied with the unit. When installing any software or hardware with a Windows XP or ME operating system it's a good idea to create a 'system restore' point beforehand, so that should anything unexpected happen the PC can return to its settings prior to the new work being undertaken! You can find the 'System' Restore' menu via the 'System Tools' menu. Windows 98 and 2000 don't have this facility

I already had a CD-RW drive in my PC, so the jumper connector at the rear of the new drive was set to slave, leaving the CD-RW drive as the master one. The new drive was connected to the motherboard via spare flat 40-pin IDE and power-supply cables.

No special device drivers have to be loaded into the PC which, once booted up, should detect the new drive and assign it a drive letter (hopefully not moving all the PC's existing drive letters around!). The instruction book has a section on procedures to follow should you have an installation problem – fortunately I didn't encounter any.

A software disc with a DVD-RAM driver on it (see Photo 2) is supplied. This is useful as a DVD-RAM disc (one is supplied with the drive) can then be used effectively as another hard disk within the PC. Windows will immediately save anything to the drive letter it assigns to the new driver (see Photo 3). The DVD-RAM disc is rewritable and can be reformatted at any time with the software provided.

Unfortunately not all PC DVD drives

can read DVD-RAM discs: check on this should you plan to use a DVD-RAM disc to transfer data between PCs. If inserting the DVD-RAM disc produces a 'Disc Not Recognised' or 'No Disc' message, you will have to use a DVD+/- R/RW type disc and a form of burning software such as Nero.

Unfortunately inserting any other type of recordable DVD disc into the new drive and trying to save something to it directly, similar to the DVD-RAM procedure, doesn't work. It produces an unhelpful Windows message about not having authorised access to the drive! This is because direct recording by Windows on to the drive has to be disabled for the RAM driver to work. There is no point in enabling Windows to record to the drive however as to my knowledge there's no DVD burning facility within Windows XP and earlier versions. If you are using Windows to burn directly with an existing CD-RW drive, this will not be affected by the new installation.

To get round this problem, and for general CD/DVD burning. I also installed the well-known Nero version 6 CD/DVD burning program (it's available from www.nero.com). Upgrading from version 5 or 5.5 to version 6 is worthwhile, as this includes full DVD burning facilities. Installation of Nero is straightforward. It automatically detects the available recording drives, which can be selected prior to burning a disc. Nero will record on any type of DVD, using the new drive. The discs with the widest DVD player compatibility are the DVD-R/RW types. These are also slightly cheaper to buy, which helps!

When you initially try out the DVD drive it's a good idea to use DVD-RW discs. These can be overwritten, and the players I've tried them in accept them without any problems. If you buy DVD-R discs, which can be written on only once, they may end up being thrown away should the initial DVD writing tests go wrong. As with recordable CDs, I've found that some of the cheaper brands can be of variable quality. So stick with a well-known brand to start with, even if it means paying a bit extra. This will avoid blaming the drive when the culprit is a dodgy disc. It's important to avoid scratching the disc surface of course. H.C.

### Table 2: Express 3A's active Ku-band transponders

Frequency	Symbol rate	FEC	Services
11.463GHz	4,340	1/2	Georgian TV. See Photos 4 and 5. Also Georgian radio
11.469GHz	3,254	2/3	Kurdsat TV. See Photo 6
11·483GHz	12,800	3/4	Mediaset (Italy) feeds. See Photo 7
11.516GHz	2,200	5/6	Mediterraneo TV (Italy)
11.520GHz	2,894	3/4	RTS TV (Serbia). Also Radio Belgrade
11.525GHz	3,864	2/3	Playlist Italia. Also Radio Italia
11.529GHz	3,254	2/3	Coming Soon TV (Italy)
11.532GHz	2,033	3/4	ETV (Italy)
11.611GHz	5,632	3/4	RAI feeds
11.620GHz	5,632	3/4	RAI feeds. See Photo 8
11.629GHz	5,632	3/4	RAI feeds
11.638GHz	5,632	3/4	RAI feeds
11.660GHz	6,400	3/4	Mediaset (Italy) feeds. See Photos 9 and 10
11-669GHz	6,400	3/4	Mediaset (Italy) feeds
11.683GHz	12,800	3/4	Mediaset (Italy) feeds

### **Express 3A**

Table 2 lists the active Ku-band transponders aboard the Russian Express 3A satellite at 11°W. Its C-band transponders were listed here last April. The Ku-band footprint covers most of Europe. All the Ku-band transponders use vertical polarisation.

Several Italian feeds come and go during the day. After closedown the Georgian TV transmissions revert to colour bars. displaying a 'No Signal' message in English! Hotbird at 13°E relays the Kurdsat and Georgian TV transmissions, picking them up from Express 3A. H.C.

### Grundig GDS2000

Although this digibox had 13V at the LNB socket none of the front-panel LEDs lit up. The problem is sometimes caused by the Amtel chip that controls the LEDs and buttons at the front. Not this time however. The fault was cured by replacing the STi5512SWE BGA-type chip U16. M.D.

### Grundig GDS3000

This digibox produced a pixellated picture with no sound, but the information banner at the bottom of the screen was OK. While this can be caused by a faulty AV SRAM chip, I have found that the usual cause is a defective STi5512SWE BGAtype chip (U12), especially when the chip is running a bit cooler than its normal working temperature of 68°C. Note that this digibox has no ventilation holes at the top, which could possibly contribute to the early failure of U12. M.D.

![](_page_59_Picture_9.jpeg)

Photo 9: A Mediaset feed via Express 3A at 11°W.

### **ODM 300CI FTA receiver**

This free-to-air digibox, the later CI model, was made in Scotland in 2000. It was suffering from the after-effects of a thunderstorm – when power was applied

![](_page_59_Picture_13.jpeg)

Photo 10: A Mediaset feed via Express 3A at 11°W.

the power supply just 'squigged'. I replaced the surface-mounted 1N4148type diode D63, which was short-circuit, and the KP1010 opto-isolator, which was open-circuit, but the unit then ran for just a few seconds before again 'squigging'. Several zener and other diodes were suspected, but they all proved to be blameless. I then brought my large magnifier into play and found that the surfacemounted resistor R63, which is in series with D63, was askew and was marked  $10k\Omega$ . I don't have the circuit diagram but the application notes for the TOP224Y chopper device show a very similar circuit in which the relevant resistor has a value of  $10\Omega$ ! Ah, a bodger at work! When I fitted a resistor with the correct value the unit sprang to life.

Success – except that after just a few minutes' viewing the unit froze: the decimal point on the front panel kept flashing, no channels could be tuned in and no menus could be selected. "Look for the heat" TV Ted said many years ago. It didn't take long to find a large 5V regulator in the middle of the board with a heatsink that almost encircled two  $100\mu$ F, 50V capacitors, C165 and C191. When these were checked they were both found to be low in value. Obviously the digital circuitry hadn't been happy with a dirty supply. The repair was completed by fitting nice new 105°C capacitors.

The time wasted looking for a 'fault' caused by the customer's 'neighbour' fitting a wrong-value resistor meant that it would probably have been cheaper for the customer to have bought a new receiver. **R.P** 

# Solution to Test Case 496

The video channel on which Cathode Ray spent so much time and effort is of relatively straightforward design, with DC coupling throughout. The initial cascode driver stage has a gain of about 33dB and provides signal inversion. This is followed by a complementary-symmetry emitter-follower output stage. The input to the first stage is via two seriesconnected resistors, R903 and R905, one of which has a 12pF HF boost capacitor (C902) in parallel for frequency equalisation. The gain of this stage is governed by negative feedback, via R906, so that it is independent of the individual transistor characteristics and the tolerances of the passive components. Amplification is set by the ratio of R906's value to the combined value of R903 and R905.

Because the gain of the R channel had increased so much, logically the first thing for Cathode Ray to check would have been the feedback loop. Other factors, such as the 4.2V bias provided by transistor Tr913, are common to all three channels. In fact the guilty item was the feedback resistor R906, whose value had increased from  $180k\Omega$  to over  $2M\Omega$ . It's rated at 0.5W and has a tolerance of 2%. A replacement cured the fault and, to be on the safe side, the corresponding resistors R926 and R945 in the G and B channels were also replaced – they would have come from the same manufacturing batch.

All that remained was to set up the first anode voltage and the primary-colour drive levels. The latter is done in software, using the installation menu. The black levels are set automatically by the colour decoder/drive chip IC501.

### NEXT MONTH IN TELEVISION

### Spares Guide 2004

The annual *Television* TV/VCR spares guide, an updated list of sources of spares for TV and video products. It's essential reference information for the service department.

### Servicing the Toshiba C8SS chassis

The Toshiba C8SS chassis is used in projection models, including the 43PJ93B. John Coombes provides a guide to fault conditions and how to tackle them.

### Days of DC

Here's a nostalgia piece with a difference! We nowadays never have to think about the mains supply: just plug into it. Not so in the period up to the early Fifties however, when AC was distributed at several voltages and there were still quite a lot of areas that had a DC supply. Keith Cummins looks back to the days of DC, including generation and distribution.

### **Digital Radio Mondiale**

Last year saw the launch of Digital Radio Mondiale, a new digital radio system for use in the long-, medium- and short-wave bands. The DRM consortium was formed in 1998, with the aim of replacing existing analogue services in these bands with something better, and in 2001 the ITU recommended the system for worldwide use. J. LeJeune describes the technology and lists current transmissions.

### PLUS ALL THE REGULAR FEATURES

### **TELEVISION INDEX & DIRECTORY 2004**

### Plus hard-copy index and reprints service

Here's the essential repair information you need! The Television Index & Directory 2004, in CD-ROM form, contains the text of over 15,000 high quality fault reports on TVs, VCRs, Camcorders, DVD players, Monitors, Satellite TV units, Audio equipment and CD players, searchable by make and model, plus the text of 200 Test Cases and over 250 major servicing articles, from sixteen years of Television magazine. It also contains a full sixteen-year index of Television, a Spares Guide, a directory of Trade and Professional Organisations, an International TV Standards guide, a satellite TV Channel Finder, a TV transmitter list and a compendium of internet resources for service engineers. The software is quick and easy to use, and runs on any PC with Windows 95, 98, ME, NT, XP or 2000.

### Television Index & Directory 2004 CD-ROM, £199

Television Index & Directory 2004 CD-ROM upgrade, £46 (to qualify for this upgrade you need to have purchased a previous version of the Television Index on floppy disk or on CD-ROM)

A six-month update of the index and fault reports will be available in May 2004. If you wish to take advantage of this, £10 should be added to your order.

Television Index only, 1988–2003, £36

Television Index only upgrade from previous versions, £18

**Hard-copy indexes** of Television magazine are available for Volumes 38 (1988) to 53 (2003) at £3.50 per volume.

**Reprints of articles** from Television back to 1988 are also available, at the flat rate of  $\pounds4.00$  per article — you can order through our web site, or write to the address below.

The above prices include UK postage and VAT where applicable. Add an extra £1 postage for non-UK EC orders, or £5 for non-EC overseas orders, although Channel Island residents do not need to add any extra postage. Cheques should be made payable to SoftCopy Ltd. All major credit and debit cards are accepted. Please use our new secure website for your orders, details below. Allow up to 28 days for delivery (UK).

### SoftCopy Limited, 1 Vineries Close, Cheltenham, GL53 ONU, UK

### Telephone 01242 241 455 Fax 01242 241 468

e-mail: sales@softcopy.co.uk web site: http://www.televisionmag.co.uk

Published on the third Wednesday of each month by Highbury Business, Media House. Azalea Drive, Swanley, Kent, BR8 8HU. Highbury Business is a division of Highbury House Communications PLC. Filmsetting by Impress, Unit 2, Parkway, Southgate Way, Orton Southgate, Peterborough PE2 6YN. Printed in England by Polestar (Colchester) Ltd., Newcomen Way, Severalls Industrial Park, Colchester, Essex CO4 4TG. Distributed by Comag, Tavistock Road, West Drayton, Middlesex UB7 7GE (tel. 01895 444 055). Sole Agents for Australia and New Zealand, Gordon and Gotch (Asia) Ltd.; South Africa. Central News Agency Ltd. *Television* is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover. excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# TUBES

### NEW and GRADED Philips CRTs

**28" WIDESCREEN** 

from .....ONLY £130

### **32" WIDESCREEN**

from .....ONLY £195

Prices include carriage but are subject to VAT

Quantity reductions

Other makes and sizes of CRT available

**De-scratching service** 

### **EXPRESS TV SUPPLIES LTD**

The Mill, Mill Lane, Rugeley, Staffs WS15 2JW Tel: 01889 577600 Fax: 01889 575600

![](_page_61_Picture_12.jpeg)

![](_page_61_Picture_13.jpeg)

Order Code : FREEDOMTALK Price : £ 25.50 + vat

See our 6 page advert for more Special Offers

K.P. House, Unit 15, Pop in Commercial Centre, Southway, Wembley, Middlesex, HA9 0HB England Tel: (020) 3909 2329 Fax : (020) 3903 5125 Email : sales@grandata.co.uk  WEB SITE WWW.JOHNSRADIO-UK.COM WWW.JOHNSRADIO.COM JOHNSRADIO ELECTRONICS TEST AND COMMUNICATION EQPT MASSIVE 10,000 SQ FT WAREHOUSE CLEARAANCE SALEE
 DC-MICROWAVE TO 300 GHZ - OPTICAL - LIGHT - EQPT - PARTS TEKTRONIX - HP - AGILENT - MARCONI PHILIPS - RACAL - B&K - R&S - W&G - ETC
 Sales Warehouse, Jahnsradia, Smithies Mill, Birstal Smithies Lights, 883-885 Bradford Rd, Barley, West Yorkshire, WF17 8NN.
 Tel: 01924 442905 Fax: 01924 448170 E-mail: johnsradia@btronnect.com
 Directions M62 Junction 27, A62 to Huddersfield, 1 mile to Birstal Smithies Lights, (6 roads) left under factory chimney aerial, Smithies Moor Lane 50 YDS second left red gate.
 HOURS M-F 9AM - 1PM AND 2PM - 5PM, SAT 9AM - 1PM Phone for appointment or to request item lists, photos, site map. All welcome, Private or trade, for sales, workshop repairs or calibration.
 PLEASE CONTACT PATRICIA AT WHITEHALLL WORKS, 84 WHITEHALL ROAD, EAST BIRKENSHAW, BRADFORD, WEST YORKSHIRE, BD11 2ER Tel: 01274 684007 Fax: 01274 651160
 WEB SITE WWW.JOHNSRADIO-UK.COM WWW.JOHNSRADIO.COM

10,000 potential customers To advertise in this space call Luke on

This Magazine reaches over

in Store

171 HAREHILLS LANE, LEEDS LS8 3QE Tel: 0113 240 1114. Tel/Fax: 0113 240 7275. Mobile: 07976 403134 Email: sales@instoreleeds.freeserve.co.uk

### MANUFACTURES GRADED PRODUCTS ALL PRICES PLUS VAT: ALL PRODUCTS FULLY GUARANTEED

PHILIPS 32PW6506 32" WIDESCREEN REAL FLAT, FM RADIO, 50HZ **£329.00** 

PHILIPS 32PW9527 32" WIDESCREEN REAL FLAT, DOLBY, 100HZ, PIXEL PLUS **£469.00** 

PHILIPS LX3000 DVD PLAYER 5.1 SURROUND SOUND SYSTEM, 75W RMS **£139.00** 

PHILIPS 14" TV/VCR COMBI FROM **£84.00** PHILIPS 14" PORTABLES FROM **£59.00** 

PHILIPS VCR'S FROM **£39.00** PHILIPS AUDIO SYSTEMS FROM **£44.00** 

FURTHER OFFERS AVAILABLE PLEASE CALL FOR A PRICE LIST CREDIT CARDS WELCOME: NEXT DAY DELIVERY

### www.sdstrade.co.uk sky Sky Freeview

OR

FREEVIEW

SPECIALISTS IN ALL MAKES AND **MODELS OF SATELLITE EQUIPMENT** 

ALL ORDERS WELCOME - LARGE OR SMALL

**REPAIRS FROM ONLY £35 + VAT** 

SKY & SKY+ SPARES - MOST MAKES AND MODELS

**NEW MODEL SKY+ INCLUDING DELIVERY AND INSTALLATION KIT - £199** 

HUNDREDS OF REFURBS AND NEW BOXES **CALL FOR PRICES OR VISIT OUR WEB SITE** 

![](_page_62_Picture_8.jpeg)

![](_page_62_Picture_9.jpeg)

FAX: 01271 329163

SILVER PACE 2200 DIGIBOXES **CALL FOR TRADE PRICES 1 HOWARD AVENUE** BARNSTAPLE DEVON EX32 80A Satellite & TEL: 01271 325888

**Digital Services Ltd** 

P.J.HILL **TV. VCR. SPARES** FLYBACK TRANSFORMERS BY ELDOR, OREGA, TERMAL, CLASSIC ALSO BUDGET RANGE.

Enquire by No's off old transformer & model No. For Akai, Akora, Alba, Aiwa, Bush, Beko, Daewoo, Ferguson, Formentii, Goodmans, Grundig, Hinari, ITT, JVC, Matsui, Net, Orion, Panasonic, Philips, Samsung, Sanyo, SEG, Sharp, Sony, Thomson, Tatung, Toshiba, etc

### **REMOTE CONTROL BY CLASSIC**

Video heads & spares, CD Lasers, belts, mains switches, semi conductors, valves, switch mode transformers (including Matsui 2196N) service kits, T/V, VCR & satellite resistors, capacitors, valves, tuners, triplers etc.

ASK ABOUT OUR SERVICE MANUAL LIBRARY FOR T/V VIDEO & MICROWAVE & AUDIO.

MOST CREDIT & DEBIT CARDS

![](_page_62_Picture_17.jpeg)

E7 NORTHWAY TRADING EST. NORTHWAY LANE, TEWKESBURY, GLOS, GL20 8JH, TEL: 01684 296902 Fax: 01684 294317

![](_page_62_Picture_19.jpeg)

15 Lostock Road Davyhulme Manchester M41 0ES E-mail: sales@mces.co.uk

> Phone: 0161 746 8037 Fax: 0161 746 8136

# **NEW TUBES**

Due to overstocking, we have been instructed by our supplier of Philips Widescreen tubes to sell as many 16:9 tubes this month as possible, all types are in stock inc. W56/W66 W76 ESF/ECK and ERF types.

Call us with your current price quote and we will try our best to beat it.

> Tel 01474 361276/327677 Fax 01474 335228 E-mail: sales@dlec.co.uk

D'Lec Components Ltd 3 Manor Court, Sole Street, Cobham, Kent DA13 9BU England

Visit www.dlec.co.uk

![](_page_63_Picture_0.jpeg)

# Multimetter FSM Indispensable Installer's TOOL

THE ULTIMATE RANGE FIELD STRENGH METERS (FSM)

- 3 or 5" TFT screen
- High resolution 0.1dB
- High accuracy +-1d8 MATV & +-2SAT
- C/N measurement
- (analogue and digital measurements)

![](_page_63_Picture_8.jpeg)

- Up to 4hours battery Shock protection (rubber)
- Quick menu keys
- RS232 & Scart sockets
- Easy and friendly to use

![](_page_63_Picture_13.jpeg)

![](_page_63_Picture_14.jpeg)

# Repair SMDs on PCBs in seconds with the **NEW** Hot Jet'S'

Desoldering and soldering of SMDs by hot air and without contact is the fast and efficient way for the modern repair workshop. And now, Welwyn Tool can offer the complete package - a range of hot air tools, SMD Rework Stations, nozzles to suit all SMD requirements, free demonstrations and free colour instructional brochure ... all available from Distributors nation-wide.

For further information, please ask for Reference No. TMS

WELWYN TOOL CO.LTD.

4 SOUTH MUNDELLS, WELWYN GARDEN CITY HERTS AL7 IEH. TEL: (01707) 331111 FAX: (01707) 372175.

- PUT HOT AIR TO WORK FOR YOU

![](_page_63_Picture_21.jpeg)

![](_page_64_Picture_0.jpeg)

## Largest selection nf

MAJOR MANUFACTURERS **NEW "B" GRADE PRODUCTS** 

### T.V. VIDEO AUDIO MICROWAVE OVENS

### **Contact Paul Bean**

BSMART (CRAWLEY) LTD. 10/11 LLOYDS COURT, MANOR ROYAL. CRAWLEY, SUSSEX RH10 2QX

> Tel: (01293) 618000 Fax: (01293) 400133

## \*PERIFELEC MC 30 A Spectrum Analyser

· Synthesized satellite cable and TV field strength meter with panoramic reception on 14 cm (5,5") screen and digital carriers measurement

Complete microprocessor and IspLSI logic control Continuous frequencies from 46 to 860 MHz and from 920 to 2150 MHz on 4 bands · Selectable 4, 1 and 0,2 MHz spectrum band-width, picture measurement 1 MHz

-

W 

-

:

measurement 1 MHz, D Display of picture of selected synthesized channel, FM (Radio) UL, B/G, I, D/K/K', M/N TV standards and Ku and C satellite standards. Possibility of 32 programs memorized per frequency band. Display (2 Lines of 16 characters). Range of measurement of signal strength from 20 to 120 dB/V, manual or automatic attenuator. 8 Sattery life about 1 hour 20 minutes, weight 5,8 Kg

play of full-band and 4 possible expanded spectrum

Drappy of numbers and a possible expanded spectrums. Channels and frequency plans of cable and IV standards memorized Frequency, signal strength in dByV or bargraph, displayed on a digital display (2 lines of 16 characters). Voltage of remote power supply in 14 vor 16 van d22 KHz in satellite & DiSEq C<sup>re</sup> v1.2 switching

The panoramic field strength meter MC30A combines in one instrument all the functions necessary for installing and checking TV or satellite reception, both analogue and digital. The visualization of the spectrum and the picture allows the carrying out of all the necessary adjustments with this one instrument. The high technology used in the MC30A allows a range of possibilities unhead of in a instrument in this price category.

![](_page_64_Picture_15.jpeg)

# Campion **Electronics Ltd.**

**SUPPLIERS OF QUALITY EX-RENTAL TV'S** 

and video equipment to independent retailers across the UK and EIRE.

FREE DELIVERY SERVICE to most areas of UK

WORLDWIDE EXPORT SERVICE Large stock of TVs suitable for export Experts in UHF/VHF conversion

Visit our large warehouse at:

Units 1 & 2 Tenat Works. Worcester Rd, Kidderminster, Worc, DY10 1JR

Tel: (01562) 746000 (2 Lines)

Just 20 miles from Birmingham City Centre

### Gran<u>data Ltd</u> distributor of all

Universal Remote Control with Menu

Operate upto 8 devices

Comes with a menu function

Operates ON Digital , Sky<sup>w</sup> Digital and most of all major brands

Available as a Box of 10

**Order Code : RC81** Price : £ 35.00 + vat (£ 3.50 + vat each) Carriage charged at £ 5.00 + vat

2 Stroke 850W Electricity Generator Ideal for powering Small Power Tools Lighting .... ote Small, Compact & Lightweight Quiet Runnig (65dB at 7 Wetres) Overload Streak Breaker 3.8 Hours Running Time Anti - Vibration Foot 4 Libro Fuel Tank BS Output Socket **Order Code : G850** Carrying Handle Price : £ 100.00 + vat Rosoll Starter Carriage charged at £ 5.00 + vat K.P. House, Unit 15, Pop in Commercial Centre, Southway, Wandbley, Middlessex. MA9 UHB England

Tel: (020) 3900 2329 Fax : (020) 8903 6126 Email : ani so @grandata. so. uk

#### SERVICE DATA **SERVICE DATA** Service SERVICE **NEED HELP NOW?** MANUALS Then ring the Link Have you ever turned away ★ ELECTRON TECHNICAL work for want of a Service HELPLINE ★ Manual? Have you ever brought a Service Manual and never Genuine help available to all used it more than once? repairers of Then why not join T.V. - V.C.R - SAT - AUDIO **TELEPHONE 01322 611289** THE MANUALS LIBRARY (Inc Valves) For details and membership Over 30 years experience and FAX 01322 616376 application form write. vast data base phone or fax: 0906 470 1706 HARVEY ELECTRONICS PROJECTOR FOR SALE 43 Loop Road, Beachley, Chepstow, Mons, NP16 7HE Calls cost 60p per minute **SPARES** Hours of Business Mon to Fri Tel/Fax No: 01291 623086 9.00 am - 12.30pm : 2.15pm - 5.30pm Visa: Mastercard accepted Sat. Morn 9am - 12.30pm ? STOP VIDIKRON LOPT'S. REMOTES **SERVICE DATA** Frverns projector spare parts and ALL TV COMPONENTS service information. Circuit Service TIDMAN MAIL ORDER LTD Diagrams Information 236 SANDYCOMBE RD PROJECTSPARES OPEN 6 DAYS 7 DV/CR CIRCUITS (WE DO NOT STOCK AUDIO OR MONITOR INFORMATION) KEW RICHMOND Tel: 01444 831769 TV's. VCR's. SATELLITE SURREY TW9 2EQ Fax: 01444 831580 CAMCORDERS, AUDIO & (1/2 MILE FROM KEW BRIDGE) E-mail: HI-FI's PHONE: 020-8948-3702 Prices are from £5.50 + £2.75 P&P add a further £5.50 per item projectspares@btinternet.com TEL A.T.V. on 0114 285 4254 in the same order ote: some items priced individually RECRUITMENT ICC17 LOPTX Kit CTV Circuits ...... from £5.00 we now supply universal VCR Circuits ...... from £7.00 ty/video remotes at competitive prices Widescreen Special CTV Manuals..... from £10.50 Payment by credit card, PO or cheque VCR Manuals ...... from £14.50 Ferguson W7023U etc. **BENCH/FIELD** Tel:Fax 01206 211570 User instructions also available Thomson 24WK23U etc **ENGINEER** e-mail: colin@fryerns.fsbusiness.co.uk (P/P add £2.50 to each order) Pt no. 10608670P1 REQUIRED 2 The Lodge **419 LANGSETT ROAD** TEL: 01322 611289 Easthorpe Green **ONLY £24.95** Small family business, based near SHEFFIELD S6 2LL Marks Tey, Colchester Inverness requires a qualified CO6 IHA MANUAL COLLECTIONS PURCHASED, TV/VCR/Audio Bench/Field **IrwinElectronics** (POST 1995) Engineer. Minimum of 3 years VISA Telephone 0114 273 9622 experience. Salary negotiable, dependant on experience and qualifications. WANTED SERVICE DATA Starting date. April 04. For Sale Send CV to: Manager, Homevision, 55 High St, Dingwall, Ross-Shire IV15 9HL **ESTABLISHED BEST CASH SERVICE INFO REPAIR BUSINESS PRICES PAID ESTABLISHED 20 YEARS** TV - VIDEO - AUDIO **NORTH DEVON AREA REPAIRS** FOR VALVES KT88, Prices- any make/model Beautiful beaches and countryside. CTV s/man 9.50 **PX4 AND MOST** Fully equipped workshop. Many spares and service manuals VCR 13.50 s/man **AUDIO/OTHER** CTV circs 4.50 Trade repairs to £15,000 TYPES. VCR 6.00 circs Sky digiboxes Phone 01271 322158 Other items POA Tel: 01403 784961 Pace, Amstrad, Grundig, Panasonic, All prices include p/p. Do not add any VAT (including Fluid Ingress). **Billington Export Ltd** All makes repaired at a fair fixed price. Sussex RH14 9EZ SSIFIF, D Fax 01403 783519 Scan Digital Services AMTel **Ex Rental TVs** Email: sales@bel-tubes.co.uk Huna, Caithness KW1 4YL For details Visitors by appointment Give Alan a ring on Sony, Philips, 01955 611313 Tel/Fax: 01633 25 40 50 www.amtel.co.uk LINEAGE E-Mail: alan@scansat.globalnet.co.uk Hitachi 32 and 28 Widescreens For a FREE consultation on how best CHEAPEST: CABLE TIES, FUSES, Portables, Combis plug-tops, crimps, tapes, tv/video, handsets, to market your products/services to a extension leads, fax, printers, baskets, ladies trousers. Tel: 020 7232 2266. Fax: 020 7232 For stock and price professional audience contact 2288 Telephone Barry McDonald LUKE on ENGINEERS PLEASE CHECK OUT: www.modecontrollers.co.uk for a device, which will save time money & change the 07836 789528 01322 611289 way you repair equipment forever. Tel: 07905 135920

![](_page_66_Picture_0.jpeg)

same time and take advantage of our special offer, saving you £10!

Visit <u>www.peakelec.co.uk</u> to download the data sheets, user guides and copies of independent reviews. You can pay using a cheque, postal order, credit or debit card and even pay securely online. Please contact us for your volume requirements.

![](_page_66_Picture_3.jpeg)

Atlas House, Kiln Lane Harpur Ind. Est., Buxton Derbyshire, SK17 9JL, UK Tel. 01298 70012 Fax. 01298 70046 Also available from Farnell, Maplin, Rapid and CPC (prices vary)

### **TELEVISION TEST PATTERN GENERATORS**

- The new GV 998 is a digital pattern generator offering more advanced features at again a realistic price. Those features include :
- MPEG-2 format Transport Stream generation
- Video and audio
- included in the TS Video and audio inputs
- Generation of a variable frequency sound carrier for decoding verification
- Multistandard and multisystem analogue TV signal generation Possibility to edit different fields of the TS database to present the name of the
- service provider Remote control via a personal computer
- Moving video patterns to check MPEG-2 decoders

![](_page_67_Picture_10.jpeg)

![](_page_67_Picture_11.jpeg)

![](_page_67_Picture_12.jpeg)

PROMAX

![](_page_67_Picture_13.jpeg)

ALBAN ELECTRONICS LIMITED THE PROMAX SERVICE CENTRE 6 Caxton Centre, Porters Wood,

St. Albans, Hertfordshire, AL3 6XT. TEL: 01727 832266 FAX: 01727 810546 WEB : www.albanelectronics.co.uk EMAIL : info@albanelectronics.co.uk SALES + SERVICE + CALIBRATION

**TEST EQUIPMENT** AE 767 Spectrum Analyser ----

![](_page_67_Picture_17.jpeg)

PROMAX

SELECTED ITEMS FROM THE PROMAX

![](_page_67_Picture_18.jpeg)

Satellite & Terrestrial, Analogue & Digital, Spectrum Analyser with BER (optional on P3) www.albonelectronics.co.uk

FOR ALL MELATEST NEWS