

## WARM UP THE IRON!

## Home-brew

220-MHz Transverter
Attenuator for pennies
More 10 GHz Test Equipment
Meter Mods

## Reviews

Tale of Two Wattmeters:
Bird 4381 and Co-Ax Dynamics
Cheap CAD

Must See! VisiTel Review/Mod





# HOW DO YOU PACK 7 WATTS, 20 MEMORIES AND SCANNING INTO A HANDHELD?

IC-2GAT: 7 Watts Rx 138-174MHz; Tx 140-150MHz

IC-4GAT: 6 Watts 440-450MHz

IC-32AT: 5 Watts Rx 138-174MHz/440-450MHz; Tx 140-150MHz/440-450MHz

A New Generation of Powerful, Versatile Handhelds.

Select a new "G Series" or dual band ICOM transceiver and enjoy full base station luxury in a portable unit designed especially for you!

- Maximum Frequency Coverage. The IC-2GAT receives 138-174MHz, including NOAA, and transmits 140-150MHz to include CAP and MARS frequencies. The IC-4GAT operates 440-450MHz, and the IC-32AT receives 138-174MHz and operates 140-150MHz/440-450MHz.
- Most Powerful Handheld! The IC-2GAT delivers seven watts! The IC-4GAT is six watts and the IC-32AT is five watts! One watt level selectable for local QSO's.
- 20 Memories. Store any frequency, Tx offset and subaudible tone in any memory. Total flexibility!
- Programmable Scanning of band and memories plus easy lockout and instant memory recall.
- Additional Features. Battery saver, call channel, all subaudible tones, multi-function LCD readout and DTMF pad.
- Compatible Accessories. All ICOM IC-2AT/02AT series battery packs, headsets and speaker mics are interchangeable.
- Optional UT-40 Beeper silently monitors a busy channel for your calls. When the pre-programmed subaudible tone is received, the unit beeps and the LCD flashes.



2 Meters and 440MHz IC-2GAT 2 Meters

IC-4GAT 440MHz

## COM

First in Communications

ICOM America, Inc., 2380-116th Ave. N.E., Bellevue, WA 98004

Customer Service Hotline (206) 454-7619

3150 Premier Drive, Suite 126, Irving, TX 75063


1777 Phoenix Parkway, Suite 201, Atlanta, GA 30349

ICOM CANADA, A Division of ICOM America, Inc., 3071 - #5 Road, Unit 9, Richmond, B.C. V6X 2T4 Canada

All stated specifications are subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. HH488.

**CIRCLE 354 ON READER SERVICE CARD** 
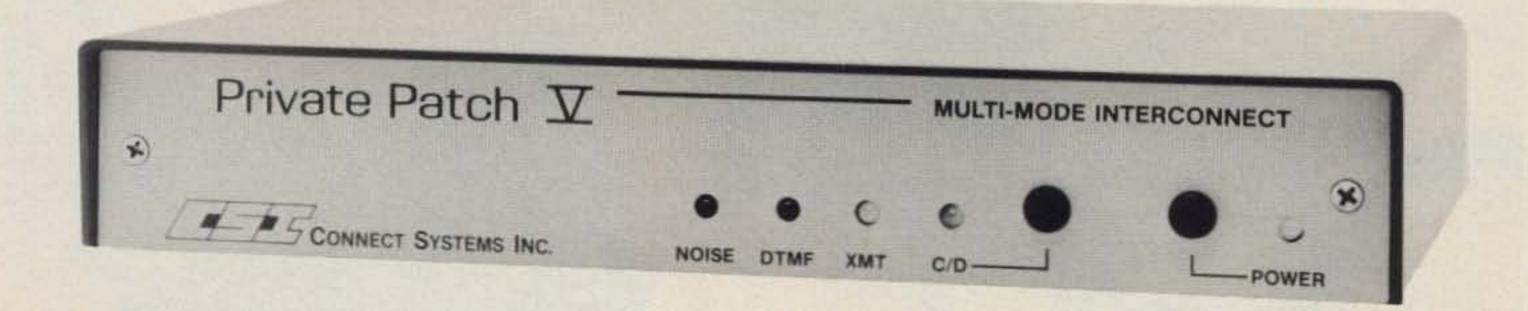
## FOUR user selectable operating modes and a 90 number autodialer make Private Patch V the ONLY choice!



## SELECT AN OPERATING MODE USING THE BUILT-IN KEYBOARD...

#### 1. SIMPLEX SAMPLING PATCH

Private Patch V achieves a level of sampling patch performance unobtainable in any other product. Crucial to performance is the noise squelch filter. Compare our five pole filter to the competition's two pole filter. Advanced software algorithms perform noise correlation tests which result in greater useable range than the competition. Nine selectable VOX enhancement ratios allow you to vary performance from straight sampling to highly VOX enhanced. (sampling rate decreased while the land party is speaking). The mobile is in full control and can breakin at any time.

#### 2. SIMPLEX VOX PATCH

VOX mode offers superb simplex operation with any radio, including synthesized and relay switched models. VOX mode has other advantages too. 1. A linear amplifier can be used to extend straight simplex range. 2. You can operate through any remotely located repeater to greatly extend range. 3. If desired you can connect Private Patch V to the MIC and speaker jack of your radio. NO INTERNAL CONNECTIONS ARE REQUIRED. Control is maintained automatically with built-in dial tone detection, busy signal detection and fully programmable activity and time out timers. An optional electronic voice delay board eliminates first word clipping with slow switching radios.

#### 3. DUPLEX PATCH

Select duplex mode when connecting Private Patch V to your existing repeater or duplex base station. Many features including semi-duplex privacy mode are user programmable. The mobile is in full control at all times.

#### 4. REPEATER CONTROLLER

Private Patch V will convert any receiver and transmitter into an outstanding performing repeater with duplex autopatch. Features such as repeater on/off code, hangtime, activity timer time, CW ID interval etc. are fully user programmable. Private Patch V is the right choice for your club system.

Private Patch V is a totally new concept in automatic phone patches. A built-in keyboard and menu driven display allow you to customize all modes, features, and functions specifically to your application.

Private Patch V can be a sampling patch today. A VOX patch tomorrow. And a repeater controller next year!

You may never need another patch again.

#### COMPARE THESE FEATURES...

- · 90 phone number autodialer
- · Last number redial
- Regenerated tone/pulse dialing
- Toll restrict: 1st and 2nd digit restrict, prefix lockout and digit counting
- 1-5 digit connect/disconnect code
- 2-5 digit secret toll override code
- User programmable CW ID
- Remote hook flash
- Auto disconnect on dialtone/busy signals
- Telephone remote base
- Remote controlled relay (relay optional)
- Lightning protected


Call or write today for your FREE brochure.



Phone: (213) 373-6803

AMATEUR ELECTRONIC SUPPLY: Mitwaukee WI, Wickliffe OH, Orlando FL, Clearwater FL, Las Vegas NV • BARRY ELECTRONICS CORP.: New York NY • ERICKSON COMMUNICATIONS: Chicago IL • HAM RADIO OUTLET: Anaheim CA, Burlingame CA, Oakland CA, Phoenix AZ San Diego CA, Van Nuys CA, Atlanta GA • HENRY RADIO: Los Angeles CA • INTERNATIONAL RADIO SYSTEMS: Miami FL • JUNS ELECTRONICS: Culver City CA • MADISON ELECTRONICS SUPPLY: Houston TX • MIAMI RADIO CENTER CORP.: Miami FL • MIKES ELECTRONICS: Ft. Lauderdale, FL • N&G DISTRIBUTING CORP.: Miami FL • OMNI ELECTRONICS: Laredo TX • PACE ENGINEERING: Tucson AZ • THE HAM STATION: Evansville IN • VALLEY RADIO CENTER: Harlingen TX • CANADA—COM-WEST RADIO SYSTEMS, LTD.: Vancouver BC

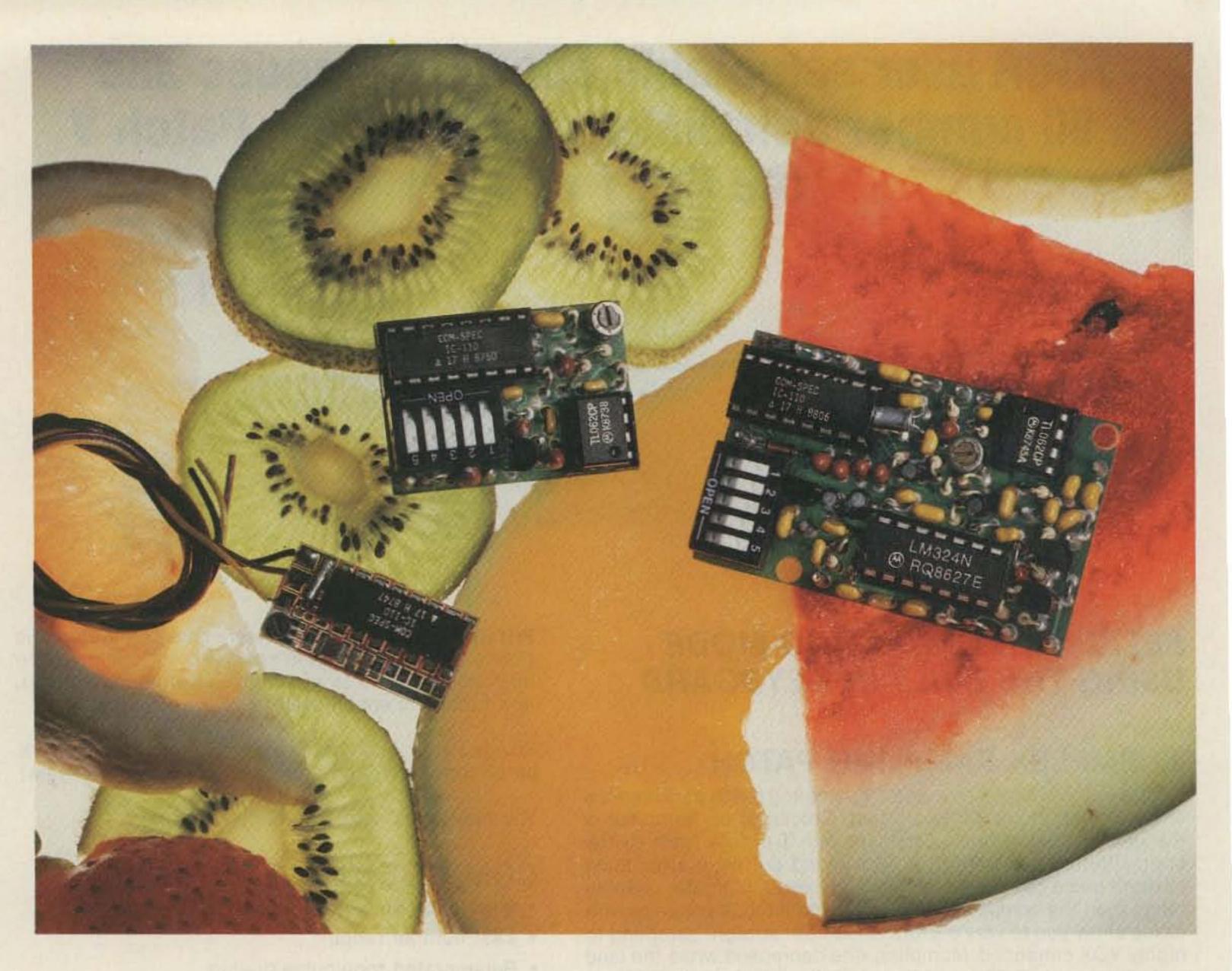CSI is a registered trademark of Connect Systems, Inc.



## Choice Selection.

Now you can have it all! Take all the qualities you've come to depend on in our programmable CTCSS tone equipment: Astonishing Accuracy, Instant Programming, Unequaled Reliability; and add full spectrum tone versatility, multi-tone capability without diodes, a reprogrammable memory...It's our new harvest of CTCSS tone equipment.

The choice is yours! If standard CTCSS EIA tones do not suit your taste, select any 32 tones of your liking from 15.0Hz to 255.0Hz. And if you change your mind, no problem; the memory can be changed in your shop with our HHP-1 programmer, or at our factory for free. Your working tone is accessed by a simple DIP switch, so there's no fussing with counters or other test equipment.

Call today toll-free and find out more about this fresh new flexibility in tone signalling, and don't forget to ask about multi-tone switching without cumbersome diode networks or binary switches.

It's all brought to market by the people who introduce the freshest ideas in tone signalling, and of course our customary same day shipping and one year warranty apply. TS-32P CTCSS ENCODER-DECODER Based on the time proven TS-32, the industry standard for over a decade. The TS-32P gives you the added versatility of a custom, changeable memory base. A low price of \$57.95 makes it an even sweeter deal.

SS-32P ENCODER Based on the equally popular SS-32 encoder. Available for CTCSS, or audible burst tones up to 6550.0Hz. Price is \$28.95.

SS-32SMP SUB-MINIATURE ENCODER Our smallest encoder for handheld applications. Now you can satisfy that customer that needs to access multiple repeater sites with a radio that has precious little space inside. At \$27.95, the price is small too.

HHP-1 HANDHELD PROGRAMMER For programming the 32 memory locations in any of our new programmable products, including our SD-1000 Two-Tone Sequential decoder. The HHP-1 is battery operated for field use, and will program ANY 32 tones from 15.0 to 6550.0Hz in .1Hz. increments. Price is \$199.95.



#### COMMUNICATIONS SPECIALISTS, INC.

426 West Taft Avenue • Orange, CA 92665-4296 Local (714) 998-3021 • FAX (714) 974-3420 • Entire U.S.A. 1-800-854-0547

Invest in the world's finest 3 KW roller inductor tuner with dummy load, new peak reading Meter and more

The MFJ-989C is a compact 3 KW roller inductor tuner with a new peak reading Cross-Needle SWR/Wattmeter. The roller inductor lets you get your SWR down to absolute minimum.

With three continuously variable components -- two massive 6 KV capacitors and a high inductance roller inductor -- you get precise control over SWR and the widest matching range possible from 1.8-30 MHz.

You get a new lighted peak and average reading Cross-Needle SWR/Wattmeter with a new more accurate directional coupler.

You get a giant two core balun wound with teflon wire for balanced



MFJ-989C

lines and a 6-position antenna switch with extra heavy switch contacts.

You get a 50 ohm 300 watt dummy load for tuning your exciter, a tilt stand for easy viewing and a 3-digit turns counter plus a spinner knob for exact inductance control.

Its compact 103/4x41/2x15 inch cabinet slides right into your station.

The MFJ-989C is not for everyone. However, if you do make the investment, you'll get the finest 3 KW tuner money can buy -- one that will give you a lifetime of use, one that takes the fear out of high power operation and one that lets you get your SWR down to absolute minimum

#### MFJ's Best VERSA TUNER II



MFJ-949C

the MFJ-949C gives you more precise matches than any tuner that \$1 3 95 uses two tapped inducters. Why? Because you get two continuously

variable capacitors that give you infinitely more positions than the limited number on switched coils.

This gives you the precise control you need to get your SWR down to a minimum. After all isn't that why you need a tuner.

You also get a dual range lighted Cross-Needle SWR/Wattmeter, 6-position antenna switch, 50 ohm 300 watt dummy load, balun for balanced lines and continuous 1.8-30 MHz coverage -- all in a compact 10x3x7 inch cabinet that fits right into your station.

With MFJ's best 300 watt tuner you get an MFJ tuner that has earned a reputation for being able to match just about anything -- on that is highly perfected and has years of proven reliability.

#### MFJ's smallest VERSA TUNER

MFJ-901B \$5995 The MFJ-901B is our



inches -- and most affordable) 200 watt PEP Versa tuner -- when both your space and your budget is limited. Matches dipoles, vees, random wires, verticals, mobile whips, beams, balanced and coax lines continuously 1.8-30 MHz. Excellent for matching solid state rigs to linears. Efficient airwound inductor. 4:1 balun for balanced lines.

#### 144/220 MHz VHF TUNERS

MFJ-920 \$4995

MFJ-921 MFJ's newest VHF



tuners cover both 2 Meters and the new Novice 220 MHz bands. They handle 300 watts PEP and match a wide range of impedances for coax fed antennas. MFJ-921 has SWR/Wattmeter.

ORDER ANY PRODUCT FROM MEJ AND TRY IT -- NO **OBLIGATION. IF NOT SATISFIED RETURN WITHIN 30** DAYS FOR A NO-HASSLE REFUND (less shipping).

 One year unconditional guarantee
 Add \$5.00 each shipping/handling . Call or write for free catalog, over 100 products.



The MFJ-941D is MFJ's fastest selling MFJ-941D 300 W PEP antenna tuner! Why? \$995 Because it has more features than tuners costing much more and it matches everything continuously from 1.8-30 MHz.

It matches dipoles, vees, verticals, mobile whips, random wires, balanced and coax lines.

SWR/Wattmeter reads forward/reflected power in 30 and 300 watt ranges. Antenna switch selects 2 coax lines, direct or through tuner, random wire/ balanced line or tuner bypass. Efficient airwound inductor gives lower losses and more watts out. Has 4:1 balun. 1000 V capacitors. 10x3x7 inches.

#### MFJ's Mobile TUNER



Don't leave home without this mobile tuner! Have an uninterrupted trip as the MFJ-945C extends your antenna bandwidth and eliminates the need to stop, go outside and readjust your mobile whip.

You can operate anywhere in a band and get low SWR. You'll get maximum power out of your solid state or tube rig and it'll run cooler and last longer.

Small 8x2x6 inches uses little room. SWR/ Wattmeter and convenient placement of controls make tuning fast and easy while in motion. 300 watts PEP output, efficient airwound inductor, 1000 volt capacitors. Mobile mount, MFJ-20, \$3.00.

#### 2 KW COAX SWITCHES

MFJ-1702 \$1995

\$2995



MFJ-1701

MFJ-1702, \$19.95. 2-positions. 60 dB isolation at 450 MHz. Less than .2 dB loss.

SWR below 1:1.2. MFJ-1701, \$29.95. 6-positions. Unused

positions grounded.

For desk or wall mount.

MFJ-945C

\$7995

#### MFJ's Fastest Selling TUNER | MFJ's 1.5 KW VERSA TUNER | III



For a few extra dollars, the MFJ-962C lets you use your barefoot rig 95 now and have the capacity to add a 1500 watt PEP linear amplifer later.

Two continuously variable 6 KV capacitors give you precise control for getting your SWR down to a minimum. And lots of inductance gives you the widest matching range possible.

You can read both peak and average power with the lighted 2-color Cross-Needle SWR/Wattmeter. A new directional coupler gives you more accurate readings over a wider frequency range.

Has 6-position ceramic antenna switch and a teflon wound two-core balun with ceramic feedthru insulators for balanced lines. 103/4x41/2x14 7/8 in.

#### MFJ's Random Wire TUNER

MFJ-16010 \$3995

You can operate all bands anywhere with any transceiver when you let the MFJ-16010 turn any



random wire into a transmitting antenna. Great for apartment, motel, camping operation. Tunes 1.8-30 MHz. Handles 200 watts. Ultra compact 2x3x4 in.

#### MFJ artificial RF ground \$7995 MFJ-931

You can create an artificial RF ground and eliminate RF "bites",



feedback, TVI and RFI when you let the MFJ-931 resonate a random length of wire and turn it into a tuned counterpoise. The MFJ-931 also lets you electrically place a far away RF ground directly at your rig -- no matter how far away it is -- by tuning out the reactance of your ground connection wire.

FOR YOUR NEAREST DEALER OR TO ORDER







MFJ ENTERPRISES, INC.

Box 494, Miss. State, MS 39762

## Welcome, Newcomers!

This month's column is devoted to a different kind of newcomer—the home-brewer who has not yet published his or her project.

#### Is Home-brew Really Dead?

Some hams seem to think so—or at least they think that this activity has shrunk to the domain of a small core of dedicated hackers and techno-peasants. These hams poured forth with all the "logical" reasons. They cited, for example, the increased availability of sophisticated commercial equipment, the growing "Grab-It-Now" ethic in our (American) society, and the influx of less technically-oriented members into our ranks because of relaxed licensing requirements. Do we now sound the death knell for home-brewing?

#### It's In The Cards

Our reader feedback responses fly in the face of the above reasoning.

Each month, I read through the stack of monthly reader feedback cards. (These are found in between the pages of the magazine.) On these, we ask the readers to rate the editorial content of the issue on a three-level scale of "Great," "OK," and "No Way." Below the rating grid, we ask in what areas they would like to see more, and see less. The responses ranged from DC to daylight, but one item came up through the noise floor loud and clear: MORE SIMPLE CONSTRUCTION ARTICLES.

Recently, we began sending our readers, along with their subscription mailings, a more detailed satisfaction survey. Three out of four of the returns echo the same message: MORE SIMPLE CONSTRUCTION ARTICLES.

Many of these are not just polite, offhand requests. They are out-and-out demands, scrawled in bright red caps across the card. It's clear to us the readership clamors for the nuts-and-bolts of this hobby; the simple tale that tells how to build a simple project; the "this is what I did and how I did it."

#### What To Do?

Since so many of you want to build, then a goodly number of you have already built one or more projects. Yet we receive relatively few manuscripts on light home-brew projects despite many lures: showing off your project to over 100,000 readers, getting paid quite well for it, having a nice feather to stuff in your resume (for you are now an "authority" on the subject), and even enjoying the warm, fuzzy feeling of carrying out an important part of our mandate set forth by the FCC, that of furthering and disseminating the state of the art. Why is it that so many of those who design and build don't put their brainchilds to paper?

It's true some home-brewers simply can't be bothered. Yet many I've talked to really want to write, but are convinced they can't—even those who have never tried! The next section attempts to dispel common confidence-blockers.

#### The Four Fallacies

Fallacy #1: "I don't have the talent to write."
Reality: This statement assumes that writing and design and building are fundamentally different skills. Actually, they're very closely related!

A home-brewer usually systematically executes an idea—he sketches out the project in block diagram form, then works out the circuit details within each block, then interfaces the circuit blocks. He first works out the plan generally, and then in gradually greater detail.

Effective writing is no different! You first sketch out a general three-point outline, in which you include sub-outline points (see below), and then you fill in the details under each outline point.

#### Introduction

What led to the birth of this idea? What are its advantages?

#### Main Body of Text

Circuit theory and description
Parts List
Where to obtain parts
Step-by-step construction sequence
Construction caveats

#### Conclusion

Summarize the project, highlighting its advantages.

Fallacy #2: "My project is too simple or too left-field for anyone to want to bother with it."

Reality: The simplest projects are often the best! Remember, too, the project the veteran home-brewer passes over is often right up the greenhorn's alley. 73 strives to present a range of simple-to-challenging home-brew projects.

The readers, too, always surprise us. Many so-called marginal projects became popular beyond our wildest imaginings. Woe to us in Editorial if we ever stop surveying the readership, thinking we "really know" what the reader wants!

Finally, our readers often read through something simple and short, even if they have no immediate plans to build it. How often have you wanted to find an article published years back? We run a thriving article reprint business here.

Fallacy #3: "My schematics, parts placement diagrams, etc., are too poorly drawn to appear in a magazine."

Reality: You may have noticed a consistency in the style of our printed figures—they're the

work of our excellent draftsman. Bill's been with 73 from the beginning—there's not much he hasn't seen!

Fallacy #4: "No editor will wade through my awful grammar and spelling."

Reality: Often, it's not as bad as you think. Even if it is, you're in good company—many noted writers, such as Ernest Hemingway, were terrible spellers. Most had editors, like you do—us! Fortunately, there are many checks, both on the author's and editor's side.

First, write or call for, or download from CompuServe, our Writer's Guide. By following the Guide and the outline above, we can more easily estimate your meaning through context. Be sure to clearly state your objective both in the cover letter and in the Introduction of the article. If the idea is strong, we go to great lengths to show it the light of day.

Second, more and more authors have access to microcomputers with enough memory to run spelling checker programs. We have been using WordStar's sophisticated spelling checker for many months, and we will be using, by this printing, "Grammatik III"—a program that analyzes text for several dozen different common grammatical problems.

Third, on particularly confusing points, we call you for on-the-spot clarification. (Be sure to include a phone number on your cover letter!)

Fourth, when your article is scheduled and prepared for a given month, we send you copies of the final edit for your review. These are called Author's Proofs. Rarely are there problems at this stage. Nonetheless, conscientious authors read these carefully in the event that a major fault or two remain.

Finally, you may want to team up with a writer. It can be a very effective, even synergistic, relationship. Some of our authors do this, with wonderful results. The article payment split two ways is often more than offset by the time saved and the enjoyment.

#### Let's Hear From You

It should be clear that most writing problems are imagined, and the real problems are most often very manageable. If doubts remain, call and talk with us—we're friendly and receptive, and we're here for you. Ditto if you want to home-brew and write, but are not sure where to start. We have a stack of letters from readers looking for a myriad of different designs.

Remember: If you can design or build it, you can effectively write about it—and everyone will be the richer for it!

...de NS1B

The 73 Magazine Writer's Guide is available on CompuServe's HamNet, Library Ø, filename "73WRIT"

#### QRM

**Editorial Offices** 

WGE Center Peterborough NH 03458-1194 phone: 603-525-4201

**Advertising Offices** 

WGE Center Peterborough NH 03458-1194 phone: 800-225-5083

Circulation Offices

WGE Center Peterborough NH 03458-1194 phone: 603-525-4201

#### Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, selfaddressed envelope with each submission. Payment for the use of any unsolicited material will be made upon publication. A premium will be paid for accepted articles that have been submitted electronically (CompuServe ppn 70310,775 or MCI Mail "WGEPUB") or on disk as an IBM-compatible ASCII file. All contributions should be directed to the 73 editorial offices. "How to Write for 73" guidelines are available upon request. US citizens must include their social security number with submitted manuscripts.

Reprints: The first copy of an article-\$3.00 (each additional copy-\$1.50). Write to 73 Amateur Radio Magazine, WGE Center, Rt. 202 North, Peterborough, NH 03458. ATTN: Article Reprints.

#### Subscription Information

One Year (12 issues) \$24.97; Two Years (24 issues) \$44.98. Canada, Mexico and Foreign Surface: One Year \$31.75 (US Funds); Two Years \$57.00 (US Funds). Foreign Airmail: One Year \$39.00 (US Funds); Two Years \$70.00 (US Funds). Send new or renewal notices, inquiries, and change of address to 73 Amateur Radio, P.O. Box 58866, Boulder CO 80322-8866. Allow 4-6 weeks for subscription and change of address processing. For Customer Service, call toll-free at 1-800-525-0643. Colorado/Foreign subscribers call 1-303-447-9330. For renewals and changes of address, please include the address label from your most recent issue of 73. For gift subscriptions, include your name and address as well as those of the gift recipients. Second class postage paid at Peterborough NH 03458, and at additional mailing offices. Canadian second class mail registration number 9566. Microfilm Edition-University Microfilm, Ann Arbor MI 48106.

Postmaster: Send address changes to 73 Amateur Radio, P.O. Box 58866, Boulder CO 80322-8866.

Contract: Reading this binds all you electronikers out there in Hamdom to perform the following: 1) Send for our Writer's Guide. 2) Following the instructions therein, apply at least one of your brainchilds to film, paper, and/or diskette. 3) Send to us in article form for everyone to benefit. No cavilling about how you can't write-everyone can! You'll feel better, and you even get paid.

73 AMATEUR RADIO (ISSN 0889-5309) is published monthly by WGE Publishing, Inc., a division of Wayne Green Enterprises, Inc., WGE Center, 70 Rte. 202N, Peterborough, NH 03458-1194. Second-class postage paid at Peterborough, NH and additional mailing offices.



JANUARY 1989

Issue # 340

#### **TABLE OF CONTENTS**

#### **FEATURES**

44 Hacker's Shack N4RVE Where hardware fantasy and reality meet. ..... 50 Trouble-shooting Guide For Switching Power Supplies .W9NGP HOME-BREW 12 More Microwave Test Equipment For 10 GHz WB6IGP 14 Super Simple Attenuator ..... K3OF

18 The 220 MHz All-Mode Transverter 

29 Cheap and Dirty Oscillator Fast audio frequency source..... ..... VE1VO

35 Inexpensive Marker Generator Tightwad's way to stay in calibration...... WB6DFQ

38 Which End Is Up? Now it's a snap to find the co-ax short. . . . . . W7RXV 40 C-64 Voltage Protector 

58 New Uses For Old Meters 

61 Simple LED Checker . Thompson Great starter homebrew project! . .

#### REVIEWS

46 Hamcall

30 AutoSketch and Amateur Radio Economy CAD for home and shack. . . . . .

32 Bird Model 4381 RF Wattmeter Nice complement to the venerable 43. ....

36 VisiTel On-The-Air 

Dial-up callsign directory......NS1B 80 Coaxial Dynamics Model 81000-A Directional RF Wattmeter

**BOOK REVIEWS** 

54 1934 Official Short Wave Radio Manual

#### **DEPARTMENTS**

#### FEEDBACK... FEEDBACK!

It's like being thereright here in our offices! How? Just take advantage of our FEEDBACK card on page 17. You'll notice a feedback number at the beginning of each article and column. We'd like you to rate what you read so that we can print what types of things you like best. And then we will draw one Feedback card each month for a free subscription to 73.

88 Ad Index

79 Above and Beyond

94 Ask Kaboom 53 ATV

85 Barter 'N Buy

82 Dealer Directory

17 Feedback

72 Ham Help

91 Hamsats

77 Homing In

86 Index: 1/89

60 Letters

6 Never Say Die

63 New Products

92 Propagation

71 QRP


9 QRX

59 RTTY Loop

98 73 International

66 Special Events

4 Welcome Newcomers

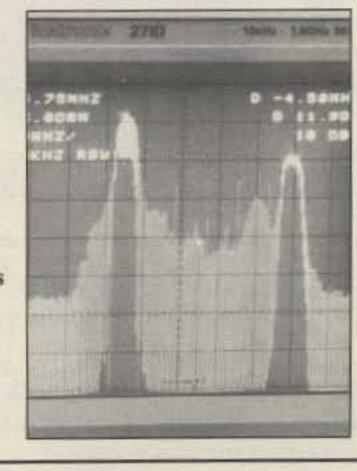


..... VE6BGL

. W8ASF

Cover by Deborah Smith

## NEVER SAY DIE

Wayne Green W2NSD/1

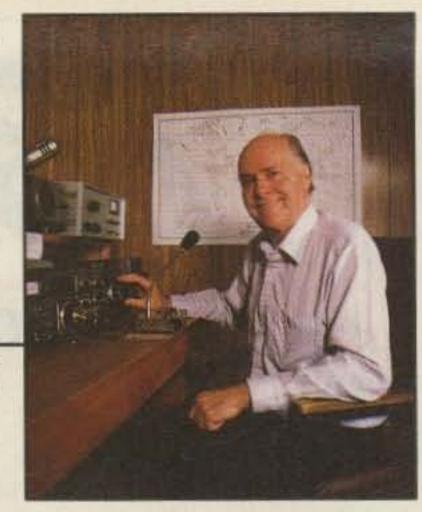

#### Do We Fight Or Give Up?

Amateur radio has what growingly appears to be a terminal illness. What can we-what should we-do about it? We can try to pretend there's no real problemignoring the loss of new hams and our frequencies. We can give up. After all, there are plenty of other interesting hobbies-right?

Almost 30% of us have paid our dues to the ARRL-what more could possibly be expected of us? What can one person do that would make any difference?

The fact is, if you want to, you can have a profound influenceand not only toward saving amateur radio. In the process, you might be able to help solve some of America's growing problems. It's never going to happen if you wait for someone else to do it. Are we hams a bunch of wimps, willing to let our hobby die without a fight?

Yes, I know, hams are wimps when shown on TV. The ham on ALF is a megawimp, for example. But I haven't seen one single copy of a letter to the network, the producers or the show's advertisers

protesting this outrageous defamation of our character. Are we wimps?

What are our resources? Well, we have about 400,000 reputedly alive and semi-alive licensed hams. About 50% are even remotely active. Now, if these 200,000 of us pooled our efforts, we'd mow 'em down. An average investment of \$100 per ham would provide \$20,000,000 to get some clout in Congress. \$20 million toward re-election campaigns buys tons of clout in Washington. A \$100 campaign donation buys about four thousand times the attention of a letter.

Just flexing our political muscles isn't going to save our hobby. At best it can stave off more frequency losses and give us a chance to start rebuilding the infrastructure the League almost totally destroyed 25 years ago. This was the network of thousands of school radio clubs that provided us with 80% of our newcomersour youngsters. These clubs were virtually wiped out in 1963 by the ARRL's self-promoting Incentive Licensing proposal.

It's their thousands of school radio clubs that have fueled Japan's ability to provide their country with the engineers, technicians, and scientists with which they've destroyed our consumer electronic industry. If you read at all, you know that twenty years ago we produced virtually 100% of our consumer electronic equipment. Today, we make less than 5% of it.

#### Just Say No To'em

Yes, I know I've been on you about dieting and smoking-and I should be on you about alcohol too. I often throw guilt around about your lousy reading habits. Okay, I'm a nag. But I'm nagging for your benefit-and for amateur radio. Other than having you thank me at hamfests for having pushed you to slim down, exercise (get out there and walk every day), stop your drug habits (alcohol and nicotine-both of which shorten your life, make things miserable for others and waste money)-I don't get a lot of benefits.

Now, let's discuss drugs. I see you slurping 807s at hamfests. And don't think I don't see you trying to hide your cigarette as you try to sneak by the 73 booth with me glowering at you.

There's a lot of political excitement over our drug problems in America. And they're serious, I agree. But when we kill 30 times as many Americans with booze (and that mainly means beer) as we do with cocaine, heroin and crack combined, let's put this into proportion. Even worse is nicotine, that kills 60 times as many. I've lost a lot of friends to cigarettes and a few to alcohol, but none personally to drugs.

The only results of the war on drugs so far have been an escalating cost to the government and a steadily dropping of drug prices as ever more are smuggled in.

Continued on page 8

#### OMSK \* USSR Association REG 146 ZONE 17 RST 2-WAY TO RADIO DATE **GMT** MHZ PSE-QSL-TNX VIA P.O.B. 88 IN MOSCOW TX.

#### **QSL OF THE MONTH**

To enter your QSL, mail it in an envelope to 73, WGE Center, 70 Rte. 202 N., Peterborough NH 03458, Attn: QSL of the Month. Winners receive a one-year subscription (or extension) to 73. Entries not in envelopes cannot be accepted.

Wayne Green W2NSD/1

ASSOCIATE PUBLISHER Stuart Norwood

> **EDITOR IN CHIEF** Bryan Hastings NS1B

> MANAGING EDITOR Hope Currier

SENIOR EDITOR Linda Reneau

TECHNICAL EDITOR David McLanahan WA1FHB

**EDITORIAL ASSISTANT** Martha Gouse

INTERNATIONAL EDITOR Richard Phenix

ART DIRECTOR

Deborah Smith

JAPANESE TRANSLATOR David Cowhig WA1LBP

ASSOCIATES Mike Bryce WB8VGE Leon Fletcher N6HYK Jim Gray W1XU Chod Harris VP2ML Dr. Marc Leavey WA3AJR Andy MacAllister WA5ZIB Bill Pasternak WA6ITF

Arliss Thompson W7XU **ADVERTISING** 

1-603-525-4201

1-800-225-5083

Peter Putman KT2B

Mike Stone WB@QCD

SALES MANAGER Ed Verbin

**ADVERTISING SALES** Jim Bail

SALES SERVICES MANAGER Rebecca Niemela

#### WGE PUBLISHING, INC.

CHIEF FINANCIAL OFFICER Tim Pelkey

CIRCULATION DIRECTOR Rodney Bell

TYPESETTING/PAGINATION Bob Dukette, Systems Supervisor Steve Jewett KA1MPM, Linda Drew, Susan Allen, Ruth Benedict

> **GRAPHICS SERVICES** Richard Clarke, Manager Dale Williams

**GRAPHICS PHOTOGRAPHER** Dan Croteau

**Editorial Offices** WGE Center Peterborough, NH 03458-1194 603-525-4201 Subscription Customer Service 1-800-525-0643 Colorado/Foreign Subscribers call 1-303-447-9330

Wayne Green Enterprises is a division of International Data Group.

73 Amateur Radio (ISSN 0889-5309) is published monthly by WGE Publishing, Inc., a division of Wayne Green Enterprises, Inc., WGE Center, Peterborough NH 03458-1194. Entire contents @ 1988 by WGE Publishing, Inc. No part of this publication may be reproduced without written permission from the publisher.

## KENWOOD

... pacesetter in Amateur Radio

## Double Take!



### TM-621A/721A

#### 144/220 and 144/450 MHz **FM Dual Banders**

Once again, Kenwood brings you another Dual Bander First! The TM-621A is the first 144/220 MHz FM Dual Bander. The Kenwood TM-621A and TM-721A (144/450 MHz) redefines the original Kenwood "Dual Bander" concept. The wide range of innovative features includes a dual channel watch function, selectable full duplex operation, 30 memory channels, extended frequency coverage, large multi-color dual digital LCD displays, programmable scanning, and more!

- Extended receiver range (138.000-173.995 MHz) on 2 m; 70 cm coverage is 438.000-449.995 MHz; 1-1/4 m coverage is 215-229.995 MHz. (Specifications guaranteed on Amateur bands only. Two meter transmit range is 144-148 MHz. Modifiable for MARS/CAP. Permits required.)
- Separate frequency display for "main" and "sub-band."
- Call channel function. A special memory channel for each band stores frequency, offset, and sub-tone of your favorite channel. Simply press the CALL key, and your favorite channel is selected!

- 30 multi-function memory channels. 14 memory channels and one call channel for each band store frequency,
- Channels "A" and "b" establish upper and lower limits for programmable band and receive frequencies independently
- 45 Watts on 2 m, 35 watts on 70 cm. 25 watts on 1-1/4 m. Approx. 5 watts low power.
- Automatic Band Change (A.B.C.) Automatically changes between main and sub-band when a signal is present.
- Dual watch function allows VHF and UHF receive simultaneously.
- Programmable memory and band scanning, with memory channel lock-out and priority watch function.

- repeater offset, CTCSS, and reverse. scan. Channels "C" and "d" store transmit for "odd splits."
  - Each function key has a unique tone for positive feedback.
    - Illuminated front panel controls and keys.

CTCSS encode/decode selectable

from front panel or UP/DWN keys on

microphone. (Encode built-in, optional

- 16 key DTMF mic. included.

TM-621A has auto offset.

TSU-6 needed for decode.)

Full duplex operation.

- Handset/remote control option (RC-10).
- · Frequency (dial) lock.
- Supplied accessories: 16-key DTMF hand mic., mounting bracket, DC cable.

Complete service manuals are available for all Kenwood transceivers and most accessories. Specifications, features, and prices are subject to change without notice or obligation.



TM-721A shown with optional RC-10.

#### Optional Accessories:

 RC-10 Multi-function handset/remote controller • PS-430 Power supply • TSU-6 CTCSS decode unit . SW-100B Compact SWR/power/volt meter • SW-200B Deluxe SWR/power meter • SWT-1 2 m antenna tuner • SWT-2 70 cm antenna tuner • SP-40 Compact mobile speaker • SP-50B Deluxe

mobile speaker • PG-2N DC cable • PG-3B DC line noise filter . MC-60A, MC-80, MC-85 Base station mics. MA-4000 Dual band 2 m/70 cm mobile antenna (mount not supplied) • MB-11 Mobile bracket • MC-43S UP/DWN hand mic. MC-48B 16-key DTMF hand mic.

### KENWOOD

KENWOOD U.S.A. CORPORATION 2201 E. Dominguez St., Long Beach, CA 90810 P.O. Box 22745, Long Beach, CA 90801-5745

#### Continued from page 6

The enormous profits involved assure that there are an unlimited number of potential criminals. Any "war" on drugs is un-winable.

Indeed, my proposed solution to America's drug problem would be to legalize drugs and sell all of them through state drug stores. And that means beer and cigarettes as well as cocaine and heroin. Further, I'd prohibit all advertising of these destructive products.

By controlling the sale through state stores we'd take the profits out of the drug industry. This would tend to stop the present pyramid sales system where addicts have to entrap new users in order to pay for their needs.

Once you take the profits out of drugs, you'll get crime out of the business. This could eliminate about 75% of today's crime for starters. And without the pressures of advertising and crime to get more customers, our educational programs to keep youngsters from trying drugs might take hold.

The barrage of ads pushing beer and cigarettes glamorizes these destructive drugs. Nicotine, being so viciously addictive, and our worst killer, has been difficult to fight. But even with the advertising and government subsidies (which are obvious government approval), tobacco use has been dropping.

Yes, I realize that the above is idealistic and that we live in a practical world where idealism doesn't pay off. If I were a crime boss I'd spend whatever it takes in congress to make sure that drugs are not legalized. This cash pressure makes it difficult for us voters to know whether a legislator has been bought or is driven by other convictions. We should remember that money will usually overcome even the most strongly held congressional convictions.

Newspapers, magazines, radio, and TV will fight every attempt
to eliminate drug advertising—as
will the bottlers, tobacco companies, distributors and retailers.
We're talking a lot of campaign
donations, so unless we get more
information on who's paying off
whom in Congress, we're going to
keep killing hundreds of thousands of people a year with alcohol and nicotine.

Which is why I started by pointing out the value of investing in your legislators. Not even 200,000 of us can match the resources of the crime syndicates, so we probably can't do much about solving the stupid drug "war." But we sure can tip the balance when it comes to our losing more ham bands—at least until we can get amateur radio growing again.

#### **Business Encroachment**

The commercial pressures for our bands are growing rapidly. Communications is exploding and not just with fiber optics—it also means more radio spectrum will be needed.

UPS needs a system of high speed digital communications that will allow them to be in constant touch with every truck so they'll know at any instant where any package is. This means microwave satellite links, UHF repeaters, and frequencies. More and more businesses are going to demand the same depth of service and a bunch of aging old timers idling away what's left of their lives on 2m isn't going to stop progress for long.

High Definition TV, America's last opportunity to get back into consumer electronics, is going to need at least twice the bandwidth presently used. Do you think our present level of ham activity at 900 MHz is going to keep HDTV and other new services from being considered there?

The FCC is under strong pressure to open more UHF TV channels to make room for thousands more one watt TV translators—to extend TV into more small towns. And wait until we start with interactive TV!

Okay, I've proposed a step toward our holding our bands until we can get ham radio growing again. But without a practical plan for growth, we'll be spinning our wheels. Unless we come up with something good—and quickly we're dead ducks.

#### Young Blood Needed

The ARRL has suggested working on getting more retired people licensed. Well, that's great for the retired—such an interest could keep them alive longer by giving them something interesting to do and helping them find new friends. I've no complaint with that.

But this isn't going to have any significant effect on our growth. Our growth has been a net 1% for the last five years—and that's if you don't admit that anyone has died. Even ten times that growth is too little. We need twenty to fifty times our present "growth."

I've mentioned that the number of new hams has been dwindling.

The FCC figures show that they've dropped by 54% in the last four years! It's almost enough to worry a sensitive person. We need to get youngsters into the hobby. We even need to find a way to attract Black, Hispanic, and other minority youngsters. Yes, I have some suggestions.

I've already written too often, about the need for our ham clubs to work with their local schools to get school radio clubs restarted. This is happening in a few areas. I'd love to see some articles and pictures from clubs who have been successful in this. I know you're out there—you tell me about it at hamfests—but until you write about it, it's a well-kept secret.

We'd have more of a chance of attracting youngsters to amateur radio if our educational system hadn't self-destructed so badly. Part of the blame for this lies with TV, part with parents, part with teachers and their unions, and part with Dr. Spock and his let-the-kids-do-what-they-want philosophy that was fervently embraced by the yuppie generation. That's a lot of problems to solve.

Add to those the problems facing lower income families—the trap of welfare—the fast track of drug profits—the street gangs that entrap virtually every inner city youngster. If we're ever going to turn these kids into engineers, we've got a long row to hoe. We have to get the profits out of drugs, offer something more attractive than welfare as a way of family life, and replace street gangs with something more beneficial to the kids—and to society.

That's a lot to accomplish. Well, we've got 200,000 active hams, so we should be able to do a lot. And we can, if we want to. It depends on what's more important to you.

It seemed to me that we have three major problems with education. First, the present educational system hasn't encouraged teachers to make their material exciting to the students. I proposed to the new president of RPI, Dr. Roland Schmitt, and to the dean of the School of Management, Robert Hawkins, that Rensselaer initiate a study of teaching technology in order to find out what is working best in teaching productivity today. I was pleased that Dr. Schmitt has just announced the formation of a Center for Innovative Undergraduate Education. This will be "devoted to improving the quality and effectiveness of undergraduate education through innovative approaches in curriculum and course development, explorations of the role of technology in education, and partnerships that support science and mathematics education in primary and secondary schools." See Electronic Engineering Times 10/3/88 p.29 for the story.

I'm working through my Congressional Technology Newsletter to put pressure on Congress to consider my solution to the drug problem. The present demagoguery, with threats to bring in the military and embargo products from drug supplier countries isn't going to work. Our military is neither trained nor equipped for drug interdiction. And we don't want to retrain and re-equip them for this, since that would leave us without the strength to discourage the USSR from further adventurism.

The welfare mess? Of course I've got a good solution to this one-but not one that would work without solving the drug problem too. Here I looked for a similar situation that another country had solved successfully. There was a close parallel with Israel, to where millions of virtually destitute people suddenly immigrated. Israel put'em into kibbutzes where they were able to work together cooperatively. They farmed and started small manufacturing businesses-and were very successful at it. Their system for educating their children made them part of their communities and kept them from forming gangs. As the kibbutzes became successful they spun off entrepreneurs who started their own businesses.

I believe that we could get American businesses to buy shares in New American Communities that would encourage welfare families to move from the inner-city ghettos to farms. Surveys show that an overwhelming number of welfare families really want to work, but the system prevents it. I say it's time to change the system and give these people a chance to succeed. I also believe we should do everything we can to get their kids interested in setting up ham stations in every New American Community.

As part of the holding action to keep amateur radio from getting gutted while we're rebuilding our infrastructure, I've formed a National Industry Advisory Committee (NIAC) to work with the FCC Commissioners. Amateur radio

Continued on page 78

## QRX.

#### Space Station Mobile!

There are, or soon will be, amateur radio operations from the Soviet space station Mir! Reliable Western European sources report that a 2 Watt 2 meter FM transceiver has been placed aboard Mir, possibly during a recent resupply mission. Sources also indicate that the crew has placed a 1/4-wavelength ground plane antenna on the outer surface of the space station. The split frequency is not yet known.

The Mir cosmonauts have the callsign U1MIR. Amateur operations were planned to begin the first week of November.

A meeting was to be held in Moscow on Friday, 28 October, with Soviet authorities, to resolve schedule and frequency issues related to this activity.

Reports indicate that U1MIR will most probably be active for the duration of the stay of the current cosmonaut team aboard Mir. When a relief crew replaces the current team of cosmonauts, a 10 Watt 2 meter FM transceiver will likely be placed aboard Mir and the callsign of the operation changed to U0MIR.

Observers feel that operations from U1MIR/

U0MIR will most likely involve international amateur radio contacts. Watch AMSAT news service bulletins for late-breaking details.

#### November March

Hams in Omaha, Nebraska, called on amateurs nationwide to join with them in the Save 220 MHz Protest Marches planned for Sunday, 27 November. According to John Gebuhr WB@CMC, one of the march organizers, the march's aim was to demonstrate the anger of radio amateurs over the FCC's decision to reallocate 220-222 MHz to land mobile business interests. The Omaha demonstration will have taken place in front of the federal court building, and hopefully in front of FCC facilities in those cities that have them, especially in Washington, DC. WB@CMC noted that television news organizations are always pressed to find newsworthy stories on this particular weekend, which is one of the reasons it was chosen.

It's interesting to note that this protest originated not in one of the

areas where the 220 band is most heavily crowded, but in a part of the nation where the rapid growth on the band is just beginning.

#### Missile Restriction

The United States Army is testing a new missile guidance system in northern Alabama that will temporarily heavily restrict amateur operations on the 70 cm band in that area. The ARS shares the 420-450 MHz band with the government. Amateurs in Alabama are being requested to observe quiet hours up to five hours a day. As a result, at least three voice repeaters in Huntsville and Florence are off the air. Packet, fast-scan amateur television, and amateur satellite operations are among the other modes FOG-M affects. The hams are requested to make the job of the Army easier, and avoid further restrictions, by staying off the air.

According to David Black KB4KCH, a TV news reporter in Birmingham, the system is a new Fiber Optic Guided Missile (FOG-M), now under development at the Redstone Arsenal in Huntsville. Testing of FOG-M involves lowpower airborne sensors. 70 cm amateur band use is only for testing purposes and will not be used when the system is actually deployed.

The Army expects the tests to last into late December.

There have been mixed reactions about this from the affected amateur community. While most amateurs in the affected area say they are happy to cooperate, some claim that the Army has plenty of its own spectrum in which they could perform FOG-M experiments.

#### International **News Snippets**

Canada: The Radio Society of Ontario (RSO) has decided to disband. In announcing the decision following a special meeting on 15 October, RSO officials noted that many former RSO people were responsible for the creation of Canada's two National Amateur Radio Organizations—CRRL and CARF—and that these two groups were serving the needs of Ontario amateurs quite well. The matter will now be turned over to the RSO's solicitor (attorney) who will handle the legal aspects of disbanding and the distribution of the RSO's assets. These include the Clifford Marsh Amateur of the Year Award, which will be turned to CARF; and the Keith Russel and Rusty Brennan Field Day Awards which the CRRL admin-

> istration will now handle. CRRL will also become sponsor of the RSO Ontario Amateur Radio Service Net (ONTARS).

> Canada: Jack Ravenscroft VE3SR passed away 19 October, of a brain tumor.

> You will remember Jack as the ham from Ottawa, Canada who was hauled into court by a neighboring family because they claimed VE3SR's operations caused interference to their home entertainment and consumer electronic gear. Jack spent thousands of dollars and four years fighting the case. With the support of the ham community, Jack finally won an appeal that will impact on the lives of every Canadian ham in a most positive way-Communications Canada (formerly DOC) is now considering mandatory RFI immunity standards for consumer electronics.

Ironically, the court-ordered RFI suppression on his neighbor's electronic gear was just being completed as Jack fell ill. Our condolences to Jack's family on their tragic loss.

Germany: The Radio Berlin International (RBI) DX Club provides its members with monthly forecasts for amateur and SWL DXers free of charge on request.

#### \$\$ HOME-BREW IV \$\$

73 Magazine again invites all home-brewers to turn their hot solder into cold cash and prizes, and to get their name in print to boot. All projects have a chance to appear in the magazine, and we will handsomely reward the authors of the crème de la crème of these.

Now for the bounty. Ramsey Electronics graciously contributed from their line of frequency counters. First prize is \$300, a ten-year subscription to 73, and a CT-125 1.25 GHz frequency counter. Second prize is \$150, a two-year sub, and a CT-90 600 MHz frequency counter. Third prize is \$75, a two-year sub, and a CT-70 525 MHz frequency counter. All this is in addition to the payment every author receives for publishing in 73.

#### **Contest Rules**

- 1. Entries must be received by 1 April 1989.
- 2. To enter, write an article describing your best home-brew construction project and submit it to 73. If you've never written for 73, send an SASE for a copy of our Writer's Guide, or download it from CompuServe (Hamnet forum, Library 0., filename "73WRIT").
- 3. Here's the real challenge: The total cost of your project must cost under \$73, even if all the parts were bought new. Be sure to include a detailed parts list with prices and sources.
- 4. Our technical staff will evaluate each project on the basis of originality, usefulness, reproducibility, economy of design, and clarity of presentation. The decision of the judges is final.
- 5. All projects must be original. That is, they must not be published elsewhere. There is no limit to the number of projects you may enter.
- 6. All purchased articles become the property of 73 Magazine.
- 7. Mail your entries to:

73 Magazine WGE Center 70 Rte. 202 N Peterborough, NH 03458-1194 Attn: Home-Brew IV

## KENWOOD

... pacesetter in Amateur Radio


## Affordable DX-ing!

### **TS-140S**
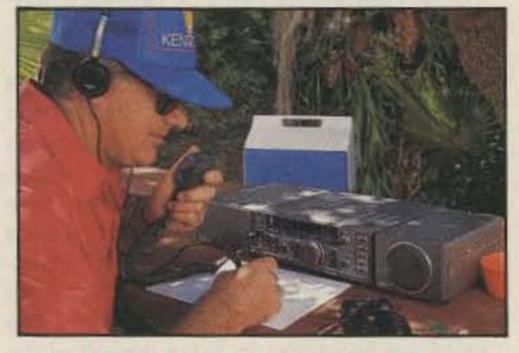
#### HF transceiver with general coverage receiver.

Compact, easy-to-use, full of operating enhancements, and feature packed. These words describe the new TS-140S HF transceiver. Setting the pace once again, Kenwood introduces new innovations in the world of "look-alike" transceivers!

- Covers all HF Amateur bands with 100 W output. General coverage receiver tunes from 50 kHz to 35 MHz. (Receiver specifications guaranteed from 500 kHz to 30 MHz.) Modifiable for HF MARS operation. (Permit required).
- All modes built-in. LSB, USB, CW, FM and AM.
- Superior receiver dynamic range Kenwood DynaMix™ high sensitivity direct mixing system ensures true 102 dB receiver dynamic range.



- New Feature! Programmable band marker. Useful for staying within the limits of your ham license. For contesters, program in the suggested frequencies to prevent QRM to nonparticipants.
- Famous Kenwood interference reducing circuits. IF shift, dual noise blankers, RIT, RF attenuator, selectable AGC, and FM squelch.

- M. CH/VFO CH sub-dial. 10 kHz step tuning for quick QSY at VFO mode, and UP/DOWN memory channel for easy operation.
- Selectable full (QSK) or semi break-in CW.
- · 31 memory channels. Store frequency, mode and CW wide/narrow selection. Split frequencies may be stored in 10 channels for repeater operation.
- RF power output control.
- AMTOR/PACKET compatible!
- Built-in VOX circuit.
- MC-43S UP/DOWN mic. included.

#### **Optional Accessories:**

- AT-130 compact antenna tuner AT-250 automatic antenna tuner . HS-5/HS-6/HS-7 headphones • IF-232C/IF-10C computer interface
- MA-5/VP-1 HF mobile antenna (5 bands)
- MB-430 mobile bracket
   MC-43S extra UP/DOWN hand mic. . MC-55 (8-pin) goose neck mobile mic. MC-60A/MC-80/MC-85 disk mics.
- PG-2S extra DC cable
   PS-430 power supply
- SP-40/SP-50B mobile speakersSP-430 external speaker • SW-100A/SW-200A/SW-2000 SWR/power meters • TL-922A 2 kW PEP linear amplifier (not for CW QSK) . TU-8 CTCSS tone unit YG-455C-1 500 Hz deluxe CW filter, YK-455C-1

New 500 Hz CW filter.



#### TS-680S

#### All-mode multi-bander

- 6m (50-54 MHz) 10 Woutput plus all HF Amateur bands (100 W output).
- Extended 6m receiver frequency range 45 MHz to 60 MHz. Specs. guaranteed from 50 to 54 MHz.
- Same functions of the TS-140S except optional VOX (VOX-4 required for VOX operation).
- Preamplifier for 6 and 10 meter band.



Complete service manuals are available for all Kenwood transceivers and most accessories. Specifications, features. and prices are subject to change without notice or obligation.

### KENWOOD

KENWOOD U.S.A. CORPORATION 2201 E. Dominguez St., Long Beach, CA 90810 P.O. Box 22745, Long Beach, CA 90801-5745

The forecasting method conforms to that used by the WARC-High Frequency Broadcasters Committee in Geneva, Switzerland. Membership application request must include three correct reception reports. For further information write to Radio Berlin International, DX Bulletin, 1160 Berlin, GDR.

Great Britain: Necessity is certainly the mother of advancement in amateur radio, all over the world. In England, a recent postal strike hampered the delivery of the Radio Society of Great Britain's (RSGB) GB2RS newscast script to its readers. The RSGB relied on other channels to distribute the document to its anchor people throughout the nation. They FAXed it to some 20 individuals, and made it available to the others via the Prestel database service and packet radio links. The system worked flawlessly, making the GB2RS newscast available to most British hams despite the postal work stoppage. That job action was finally settled on 12 September.

Great Britain: The Radio Amateur Invalid and Blind Club (RAIBC) announces the installation of a new telephone help-line. The number inside England is (01) 346-5372 and the line is open between 1000–1700 UTC each day to take calls from RAIBC members and supporters, as well as those wanting more information about this unique club. On those occasions when there is no one to take a call, an answering machine will record messages.

Israel: A reminder to those hams planning a visit to Israel. You can apply for a reciprocal license directly to the Ministry of Communications office in Tel Aviv, provided that your home nation has a reciprocal operating agreement with Israel. The Israel Amateur Radio Club (IARC) offers help to obtain this license and mail it to you. The IARC will also deliver it to you when you arrive. (See last month's "73 International," p. 103, col. 1.)

Several points to bear in mind: Repeater access in Israel requires a 91.5 Hz CTCSS encoder, and the country's main power is supplied at 230 V AC/50 Hz.

For further assistance, write to Aaron Kirshner 4X1AT, Box 4099, Tel Aviv, 61040, Israel.

Japan: Ham Fair '88—Japan's answer to the Dayton Hamvention—attracted 57,000 visitors to the Tokyo International Trade Center this year.

This is up some 3000 attendees over 1987, making a new record for this event. Highlights included the showing of the latest techniques and equipment for the 1.2, 2.4, and 5.4 GHz band operation. Seminar sessions included a short course in CW while various competitions, including a receiving contest, were also part of the festivities. Visitors to Ham Fair were also able to attend the Japan Amateur Radio Industry Association's "JAIA" Fair which featured the latest commercial gear.

Both exhibitions shared the same facilities this year.

Korea: The annual General Meeting of International Amateur Radio Union (IARU) Region Three took place in Seoul, Korea from 10–14 October 1988.

Approximately sixty representatives from twelve countries out of the twenty-four member societies of Region Three attended. The main topic discussed was preparation for a possible World Administrative Radio Conference as early as 1992. It's expected at that conference that many amateur allocations will come under attack from other spectrum-hungry users. They will also discuss actions on band plans for 160 and 80 meters in Region Three, beacon plans, satellite operations, contests, and emergency operations.

#### **MACC Attack**

The Big MACC is again on the attack. The Mid-America Coordination Council (MACC) voted to accept Colorado, the tenth state to join this group. In addition to Colorado, MACC oversees coordination activities in Kansas, Missouri, Illinois, Iowa, Minnesota, Nebraska, Oklahoma, South Dakota, and Wisconsin. These states encompass an area of 721,210 square miles, and contain almost 18% of the amateur radio population of the nation.

## KC Coordination Dispute Settled

A long-standing dispute over amateur radio repeater frequency coordination in the Kansas City area has been laid to rest. Representatives of the Missouri Repeater Council, Kansas Amateur Repeater Council, and Mo-Kan Council of Amateur Radio Clubs, have initialed an agreement on how the frequency coordinators for the various parts of Missouri and Kansas should be listed in the ARRL Repeater Directory. The organizations have agreed also to exchange the information contained in their databases. Paul Grauer WØFIR, played a key role in resolving the dispute.

Full details on the settlement will appear soon in "Looking West."

#### Atlas

Herb Johnson W6QKI is the founder and chief designer of Atlas Radio, Inc. of Oceanside, California. He has asked 73 Magazine to stress two points about his company, which was liquidated in late 1979.

- When Atlas Radio was liquidated, it was not sold to any other company.
- There is currently only one qualified service organization for original genuine Atlas Radio

equipment. It is: RF Parts, 1320 Grand Ave., San Marcos, CA 92069; (619) 744-0728.

#### **Big Thanks**

Glen Baxter K1MAN, net manager for the International Amateur Radio Network (IARN) of Belgrade Lakes, Maine, gratefully thanks, on behalf of all the members of the IARN, all the manufacturers and individuals who donated equipment to help in the Hurricane Gilbert and future relief efforts. The Heath Company gave an IBM-PC compatible computer to the IARN, complete with a 20 MB hard disk drive; Advanced Electronic Applications donated a pair of PK-232 packet radio terminals; Hal Communications donated an ST-7000 communications terminal system; and Dr. Ernie Adams gave the group a Yaesu FT-757GX transceiver and power supply. Earlier, IARN received the donation of another ST-7000 from Tetsuju Yamada JA1EQZ who is chairman of E-Net and IARN Director for Japan. As the communications demand from Hurricane Gilbert diminishes, Baxter says that the gear will be assembled to serve as a fulltime IARN HF Packet BBS on 20 meter, similar to one already in operation on 14.109 MHz by KB1PJ/8 in Cleveland, Ohio.

Glenn reminds all amateurs, especially contesters, that the 14.270–14.280 MHz segment is still very active for handling emergency traffic. While no longer protected by the FCC Mandate issued during Hurricane Gilbert, the IARN still uses 14.275 MHz to handle important medical emergency, relief, and health/welfare traffic.

#### ITU

A ham will be heading the United States delegation to the next major ITU conference. The State Department announced that C. Travis Marshal W3HPS has been appointed as Chairman of the US Delegation to the 1989 Plenipotentiary Conference of the International Telecommunications Union.

Marshall, who is a Senior Vice President of Motorola Incorporated, will attend the 23 May-29 June conference in Nice, France.

#### Thanks...

To all who contributed news items to this month's QRX column. They are: Westlink, NABET News, GB2RS, Radio Berlin, NO9X, AMSAT-NA, Tselil Harmomi, RSGB, ARRL, JARL, and CRRL. Keep your news items and photos rolling in! Address is: 73 Magazine, WGE Center, 70 Rte. 202N, Peterborough, NH 03458-1194. Attn: QRX

## MORE MICROWAVE TEST EQUIPMENT FOR 10 GHZ

#### The Backfire Antenna/Boomerang

by C.L. Houghton WB6IGP

recall my article in the October 1988 issue of 73 (pp. 40-41). In it, I describe how to build a 10 GHz detector mount to use with frequency measuring wavemeters and an amplifier. In this article, I will describe the backfire antenna or boomerang, its construction and operation, and the two meter injector. Both devices use a detector mount—either a commercial unit that accepts a 1N23 type diode, or the home-brew mount described in Part 1.

#### The Backfire Antenna

Industry has used the backfire antenna for many years. Even some of the early amateur microwave pioneers in the 1940s used them. It's a simple concept and easy to apply—I've wondered why it hasn't surfaced earlier in some of our amateur radio publications.

The backfire, or boomerang, antenna is a waveguide-mounted detector to which a source of RF energy is directly inserted into the 1N23 diode, producing a flow of current. The RF comes from a single-stage 2N2222 transistor oscillator, crystal-controlled at 30 MHz (our IF frequency) for stability. This is all you need, besides a small horn antenna to receive and to act as the transmit antenna for the boomerang. You can build the oscillator or use an International Crystal oscillator board powered by a 9 volt transistor radio battery. See Figure 1 and system photographs.

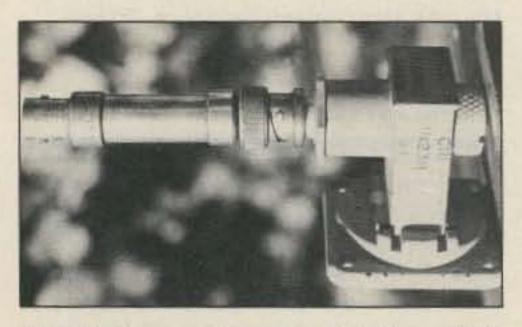


Photo B. Commercial mount with 1N23 type diode now fitted with varactor for connection to a 2-meter HT. Home-brew mount works just as well.



Photo A. Some members of the San Diego Microwave Society having a little fun with ten-foot dishes. Kerry Banke N6IZW with 10 GHz transceiver in hand.

The 30 MHz signal injected into the detector diode mount by itself is not productive, but when it is injected with microwave energy via the horn antenna, it produces upper and lower mixer products detectable by your full-duplex transceiver. Modulation isn't usually detectable unless it is imposed on the 30 MHz oscillator. You will detect a return CW carrier when your antenna is pointed in the direction of the boomerang. You will detect modulation from the source when even when the boomerang is fairly distant from the Gunn oscillator. Signals at this point are very weak and are a result of the time/path differences.

With the microwave injection mixed with the 30 MHz oscillator, it doesn't matter which microwave frequency you use to obtain a return from the boomerang. I tried this same operation at other microwave frequencies, and operation is just as good as it is on 10 GHz. Design is not critical. Just use a resonant waveguide for the frequency and inject your IF frequency into the detector mount.

Ed Munn K6OYJ has even used a tin can fitted with a diode as part of a polaplexer for boomerang operation on our 3 GHz band. See Figure 2. When I finish my 5 GHz Gunn oscillator, I intend to build another boomerang out of some scrap 5 GHz waveguide, or possibly a used Sardine can, just for fun. If you don't play, how can you have any fun with these microwave bands?

#### **IF System Required**

The IF system must operate around 30 MHz. If your system uses a different intermediate frequency, change the crystal to match. Operation is the same. There will be some problems if your IF is high, say 100 MHz, because of the input matching and loading of the 1N23 crystal.

If you slowly separate the receiver and the boomerang, you will see a very defined peak, and as you move them further apart still, you will see a null. The phase difference between the 30 MHz signals, which can be used to measure distance, causes this change. You can also change the

frequency of your microwave transmitter in small kHz steps and observe the null and peak at each frequency. You can measure distance from this.

#### Bore Sight

The boomerang or backfire antenna shines when used as a target for your antenna. With the unit perched at some distance, you can sight down the axis of your antenna and draw a straight line between the two. You can use it for antenna measurements to peak your system. Be sure your transceiver is on the frequency you wish to peak up, as it does not matter to the boomerang. As you increase the

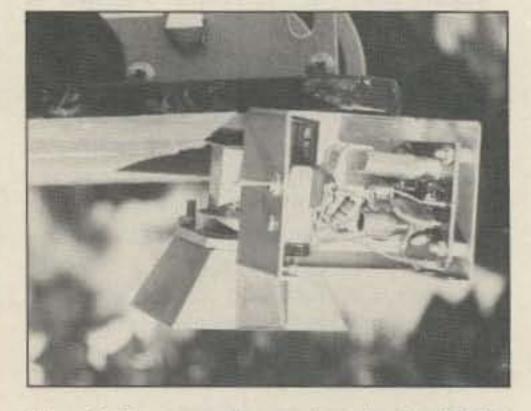


Photo C. Boomerang bottom view showing 30 MHz oscillator (International Crystal) mounted in small LMB box.

distance, you obtain a weaker signal and a much more defined antenna pattern. If the boomerang is moved about the front of your antenna, you will be able to detect the main lobe and the focus of the electrical axis. Moving around the sides, we would expect to see some side lobes, but the null and peak previously mentioned makes these measurements very difficult.

Just for fun, one day members of the San Diego Microwave Group gathered around several large dish antennas located in the backyard of Kerry, one of the members. We speculated on the pattern we would obtain if we tried a new frequency, DC or

sound, instead of electronics. We moved our heads into prime focus and whispered to other members about a hundred feet away. Not bad. The gain of the ten-foot dish at audio frequency was very good, in fact. Stepping into the main lobe quite a distance away from the dish, you were soon pelted by very loud, focused sound-full duplex! You could whis-

per so low that a person standing three feet away could not hear you, yet the person at the feedpoint of the dish was copying solid and very loud. Now if we took the boomerang with a 1 kHz audio oscillator and . . .?

When you know the distance your system will work at with a very narrow antenna beamwidth, try setting your microwave dish in a new spot, and then aim it at the oscillator turned off. When you think you are on target,

turn on the boomerang and recheck for maximum signal and antenna orientation. This way you will become more familiar with the aiming characteristics of your antenna. I thought I was pretty good until I tried it, but I had to do some re-evaluating. It is like learning how to hold a camera steady when triggering the shutter. By dry-running the antenna, you improve your accuracy in pointing

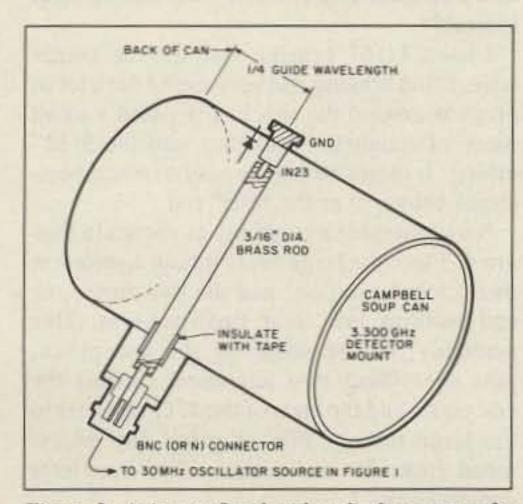


Figure 2. A tin can fitted with a diode as part of a polaplexer for boomerang operation on the amateur 3 GHz band.



Photo D. Rear view of Boomerang showing back construction used on home-brew detector mount.

your system and make more contacts. One to two degrees beamwidth is not much to play with.

Use a map to point your dish antenna on distant points. Don't get one from your local service station; instead, obtain a quality survey map. US Geological Survey quadrangles describe in detail the topographic areas of interest from small to large. You'll also need

#22 ON 1/4" ADJ. FORM BATTERY CONNECTOR V IN23 SHIELD/METAL BOX

boomerang with the 30 MHz Figure 1. Schematic of oscillator that produces the RF that drives the 1N23 diode in the wave-guide mounted detector.

a good compass. For aiming your antenna, Sears has several levels that will give you an indication of mount positioning and inclination. I found a General bubble bull's-eye level, the size of a quarter, at our local hardware store for \$2.39. It has 45 degree markings and is quite sensitive. It proved useful in adjusting antenna orientation.

The other advantage of the boomerang is that it will tell you quickly when your transmitting Gunn oscillator is putting out microwave energy. It does not care what frequency you are on. It will return a CW signal, which tells you that your receiver is operating and gives a quick reference for system evaluation.

#### Two-Meter Injector

The 2-meter injector is a detector mount that uses a varactor or step-recovery diode as the driven element. We have used an input pad to limit the RF drive from our two-meter HT which, on low power, puts out 200 mW. Pad values were 10 dB to limit the drive to about 10 mW, and 3 dB for 100 mW of drive to the SRD diode. See Figure 3. The diode is rated at 1 watt dissipation. The pad also serves as a DC return for the SRD diode in the detector mount. The best mount possible for

the SRD diode would be a commercial unit, as I am not crazy about threading the tip of a somewhat expensive diode. You might want to construct the second version (with the brass tubing on top) with the BNC connector. Either mount will work well, and each has advantages over the over. One offers ease of construction, while the other requires more soldering expertise. Details on both mounts were described in Part 1 of this article. See Photo B, a surplus mount with 3 dB pad, and Photo C, my second version with a BNC connector.

Ed Munn K6OYJ, a member of our San Diego Microwave Group, provided the diode I used. It worked quite well. We knew it was a varactor with a reverse breakdown of 42 volts at 10 micro amps and a junction capacity of 2.31 pF at 6 volts (1 MHz test frequency) and the same case style as a 1N23. The closest commercial diode that I find listed is the Microwave Associates MA-44641D Step Recovery Varactor. I'm cur-

rently trying to find one of these devices to test in the mount. Check your local surplus dealers and put that old scrounging effort to work. See Photo B, varactor mount.

I will make available high power Gunn diodes, case style 118 with silver plated brass rivets, for modifying Solfan type cavities operating on 10 GHz. These devices have power outputs from 50 to approximately 100 mW (+15 to +20 dB) for \$5 each, postpaid conti-

nental US. Some select higher power devices for 6 GHz, 10 GHz, and 18 GHz. Output power varies from cavity to cavity and post mounting arrangements, but all devices are tested prior to shipping for RF. I would be happy to answer any questions regarding this or any other microwave related project. Please contact me at 6345 Badger Lake, San Diego, CA 92119.78

2 METER HT ON LOW POWER BNC COAXIAL PAD PROVIDES DC 3.08 RETURN FOR VARACTOR DIODE OUTPUT 2 METERS SMALL HORN TO INPUT OF TRANSCEIVER DETECTOR MOUNT

Figure 3. Diagram for the 2-meter injector system. It loads a step-recovery diode (in the detector mount), which generates many harmonics. The 70th harmonic of 146 MHz is 10.220 GHz.

## SUPER SIMPLE ATTENUATOR

#### A construction project for many uses

by W.C. Cloninger, Jr. K30F

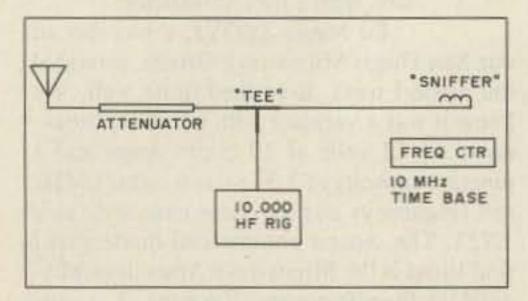


Figure 1. The attenuator balancing two 10 MHz signals into an HF receiver.

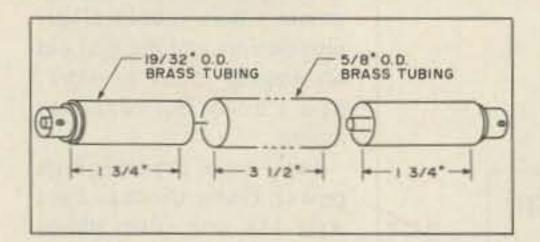


Figure 2. Tube dimensions for the attenuator.

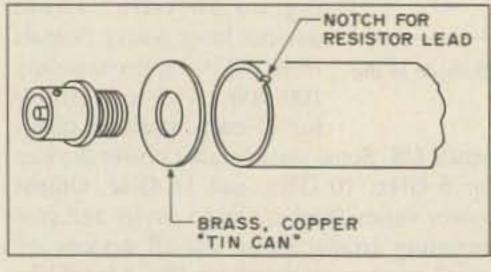


Figure 3. BNC connector attachment details.

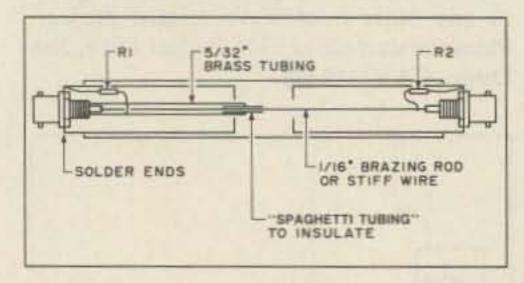


Figure 4. The final assembly of the attenuator.

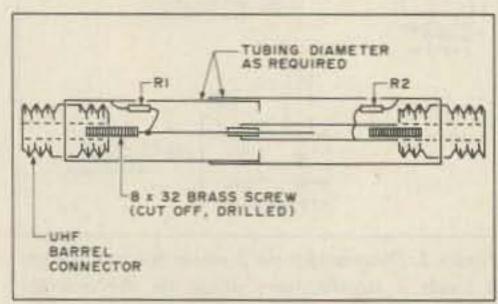


Figure 5. Two-tube attenuator system.

ere is a simple, adjustable, and easy to build attentuator, which has a variety of uses. It uses a simple capacitive coupling with an attempt at a reasonable impedance match. It is a simple one evening project using easy to obtain materials.

#### Some Practical Uses

Before getting involved in the construction of the attenuator, look at several of its uses. The constructor can think of additional uses to fit his own needs.

I first constructed the attenuator for "rabbit hunting" (DFing 2 meter hidden transmitters). It is a little difficult to get a beam heading when the S-meter on the rig is at full scale all the time. The attenuator provides the answer for adjusting the received signal for a less than full scale reading. With the attenuator I could determine the peak or null

depending on the type of antenna I was using. The attenuator is an absolute must for reducing any strong or weak signals when close to a transmitter.

In addition to the original use, I found that it has been just the item I needed to use with test equip-

ment. Figure 1 shows how I used it to "balance" two 10 MHz signals into my HF receiver to zero beat my frequency counter. (Hint: If considering to purchase a frequency counter, give strong consideration to the one with a 10 MHz time base that can easily zero beat with WWV on 10 MHz. It is easily worth a few dollars more to be able to check and adjust the counter time base by hand.)

Other routine uses are to limit input to my frequency counter and my FM deviation meter. I use a "gimmick" in my dummy load to pick up RF and causing the level to be significant at high power levels. I quite often feed this RF directly into the test equipment. It ensures that the signals do not overload the input of the equipment, and more importantly do not damage the equipment. This attenuator is for use with low level RF and receive type signals. It is not to be used with a transmitter since R1 and R2 are 1/2-watt resistors.

#### Construction

"The attenuator

is an absolute must

for reducing any strong

or weak signals when

close to a transmitter."

Construction is very simple, and the only items I did not have in my junk box were the pieces of brass tubing. The local hobby shop had an assortment of brass tubing from about 1/16" to 1". It comes in so many different sizes that each larger size will just slide over the next smaller size. Just pick the size that suits the need of the type of connector being used. Dimensions are given in Figure 2 for the attenuator I built when using BNC connectors. There is nothing critical about dimensions. I used a three tube system, but the constructor can just as easily use the two tube system seen in Figure 5.

I made the end plates from a piece of tin can stock shown in Figure 3. I drilled the appropriate hole for the BNC connector, installed the connector and tightened the nut. It is im-

portant to tighten the nut before assembly, since access to the nut is impossible after soldering the end plate to the tubing. Now solder the solid wire and the small diameter brass tubing to the appropriate connectors. Use care to keep the tubing or wire in good align-

ment with the axis of the center conductor. Add a 47Ω ½-watt resistor to each center conductor as shown, but leave the other end of the resistor free for soldering during final assembly.

I used 1/16" brazing rod for the center wire. I find brazing rod very useful for a lot of projects around the shack. I inserted a small piece of spaghetti insulation into the 5/32" tubing. It might be just as easy to place heatshrink tubing over the 1/16" rod.


Now assemble everything as shown in Figure 4. Place the large brass tubing sections in their closed position, and the two connector end sections into their final position. This assembly, before soldering the end plates, puts everything into alignment. Solder the end plates and the ends of the  $47\Omega$  resistors to the large tubing. File or grind any excess metal from the end plates. This completes construction.

This is a handy addition to any workbench or shack. Enjoy! 73

#### The Supertemp XY7 Soldering Station The Ultimate in Controlled Temperature Hand Soldering
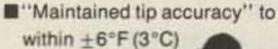
#### Features:

- "Selectability" in 54° increments between 608°F and 824°F-also C° readings.
- "Zero voltage switching" protecting voltage & current sensing devices.









**CIRCLE 310 ON READER SERVICE CARD** 

#### QRV Antenna Emergency Packs

EmergencyPacks contain QRV All Band kink-proof wx-sealed multi-band Dipole-V-Sloper antenna, 70 coax feedline, Quick Launch system, rotproof dacron support braid, 52 p Tech Manual. Complete. Ready for Action. One person installs in 15 minutes. Infopack \$1 by 1st class mail.

Fastest Antennas in the West Box 50062-S, Provo, UT 84605 Emergency Pack 50095 Add \$10 S & H.

Antennas West = (801) 373-8425

CIRCLE 304 ON READER SERVICE CARD


FOR THE BEST IN LINEAR AMPLIFIERS, ANTENNA TUNERS, TRANSCEIVERS, METERS ETC. REPLACEMENT PARTS, FAC-TORY SERVICE, NEW PRODUCT INFO. DOMESTIC, INTER-NATIONAL DEALER INQUIRIES INVITED.

PO Box H E. Rockaway, LI NY 11518, USA TLX 4758244 516/536-2620



**CIRCLE 263 ON READER SERVICE CARD** 

#### **GET YOUR BEARINGS STRAIGHT**

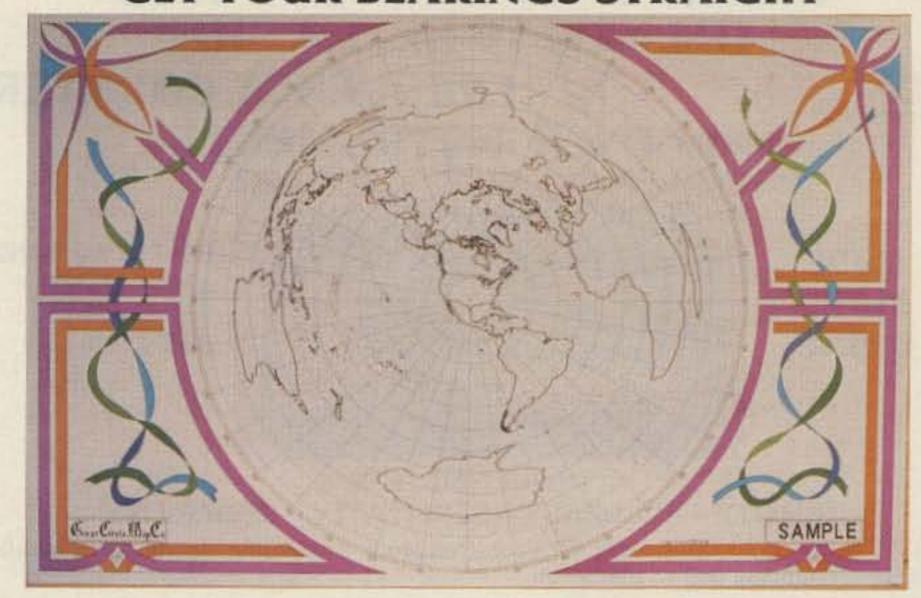

at last! A map dedicated to the radio amateur. Announcing the Azimuth-Equidistant wall map from At last! A map dedicated to the Great Circle Map Co.

An azimuth map provides information about heading and range to any place on Earth. No longer will you have to guess at which way to aim your beam antenna for that rare DX.

Each map is specially drawn with your station at the exact center. The rest of the world is spread out around you. To use the map, simply find the target station and read the compass heading from the border of the map. To find the range, count the number of rings from the center. Each ring is spaced 1000 miles apart. Voila! You now know the true heading and range to the target station.

The maps are custom drawn with computer accuracy for your location and are personalized with your station's call sign at the lower right. Each map measures 35"x23", is brightly colored, and is printed on high quality poster stock making it suitable for framing.

To order, send \$39 check or money order and your station's call sign and location (if you live in a large city, state which side of town) to: Great Circle Map Co.

P.O. Box 691401 • San Antonio, TX 78269

DEALER INQUIRIES INVITED

**CIRCLE 346 ON READER SERVICE CARD** 

### ACCURACY DIGIMAX PERFORMANCE



10 Hz to 1.2 GHz .1 PPM ACCURACY



50 Hz to 512 MHz 1 PPM ACCURACY TCXO

ALL MODELS HAVE 1 YEAR WARRANTY

Optional factory installed rechargeable battery pack available

#### DIGIMAX INSTRUMENTS CORP.

Marie To	PRICE	PRICE FREQUENCY	I I I I I I I I I I I I I I I I I I I	READ	SENSIT	IVITY TYP.	POWER REQ.
MODEL				OUTS	50 Hz-25 MHz	25 MHz-450 MHz	
D500	\$149.95	50 Hz-512 MHz 1 PPM 17*-35*C	1 PPM 171.3510 TOXO TIME BASE		15 to 50 MV	20 to 50 MV to 450 MHz 50 to 100 MV to 1 GHz	8-15 VDC 300 MA
8510	\$179.95	50 Hz-1 0 GHz					AC-12
D612	\$259.95	50 Hz-1.2 GHz	0.1 PPM 20"-40°C		15 to 50 MV	2 to 20 MV	REQ. FOR
D1200	\$299.95	10 Hz-1.2 GHz	PROPORTIONAL 10 MHz OVEN		15 to 50 MV	20 to 30 MV to 1 GHz	8-15 VDC 500 MA

AC-12 AC-ADAPTER \$8.95

T-1200 BNC-BASE 21" ANT, \$8.95

BAC12 \$34.95 BAC5 \$29.95

FOR DEALER LOCATIONS OR PHONE ORDERS 800-854-1566 8560 Production Avenue San Diego, CA 92121 California Call 619-578-7171 Telex #697120-DATAMAX-103

EXPORT AGENT: MAGNUS 3500 Devon Avenue Chicago, IL 60659 312-679-6070 Telex #253503 MAGNUS CGO

#### NTRODUCING THE NEW 10-Hz-1.4 GHz

### ATASCAN) FREQUENCY COUNTER

FROM B&BINSTRUMENTS

MADE IN THE U. S. A.



COVERS ALL BANDS 160-2 METER 150-220-450 850-1296 MHz

#### THE ULTIMATE IN QUALITY - ACCURACY - SENSITIVITY - RELIABILITY

DATASCAN will meet all your frequency measuring needs from mobile, marine, hilltopping and on the bench.

- \* Delivers years of reliable service, constructed of a rugged all-metal case with 8 digit display.
- \* Adaptable for any job, operates on 8 AA dry cells\*, 11-18 V DC, 110 V AC adapter or with optional nicad pack.
- \* You can use it to check disc drives, VTR's, TV's, HT's or tune your HF rig to meet a special QSO.
- \* The C 1400 also comes with a built-in 18 dB preamp for increased sensitivity. You can even add an optional sniffer probe for finding local OSC and multipliers.

	Suggested	Time Base	Sensitivity Typ.		Digit	1.Hz	10 Hz	Inputs	Power	Case	
Model	Price	Accuracy	150 MHz	440 MHz	850 MHz	Type Size	Resolution	Resolution	- STATE OF THE STA	Req.	Type-Size
C900	139.95	1 PPM TCXQ	25 MV	35 MV		8 Digit .4 in. 7 Segment LED	10 Hz to 5 MHz	5 MHz to 512 MHz	BNC 50Ω Pre 1 Meg Dir	117 VAC 11-18 VDC	All Metal RFI Shielded
C1200	169.95	1 PPM TCXO	15 MV	25 MV	35 MV	8 Digit 1/3 in. 7 Segment LED	10 Hz to 5 MHz	5 MHz 10 1000 MHz	2BNC 8 AA Dry Cell Batt. 50Ω Pre Optional	8 AA Dry Cell Batt.	All Metal RFI Shielded Case
C1400	199.95	(17*-40°C)	5 MV	15 MV	20 MV < 50 MV @ 1300 MHz	8 Digit % in. 7 Segment LED	10 Hz to 5 MHz	5 MHz to 1400 MHz		Optional Nicad Pk	2×6×5

ALL UNITS ARE COVERED BY OUR 5 YEAR LIMITED WARRANTY

#### ALL MODELS INCLUDE: AC Adapter plus Antenna

ACCESSORIES

SPECIAL \$10 WITH ORDER BAC-8 8 AA Nicad Pack ...... \$19.95 Sp-2 Sniffer Probe (HI-Z) ..... \$19.95 AM 1200 X10-X100 Audio Multiplier . . . . \$49.95

ORDER TODAY

(619) 579-2258 or send check or money order to:

DON'T GAMBLE ON YOUR FREQUENCY


TERMS: Shipping, handling and insurance please add 5% (\$2.00 minimum) to a maximum of \$10.00 each order. CA res. please add 6% sales tax.

manufactured by **B&BINSTRUMENTS** 

408 La Cresta Hgts Road El Cajon, CA 92021

\*Batteries not included. \*Nicad not available with model C900.

CIRCLE 137 ON READER SERVICE CARD

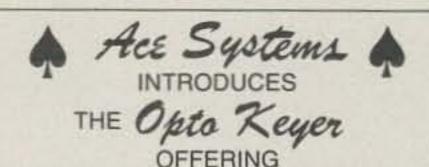

- BATTERY OPERATED BUILT-IN SPEAKER OPTO ISOLATED OUTPUT WITH NO MECHANICAL T/R SWITCHING
  - REVERSE POLARITY PROTECTION
  - SELF COMPLETING DOTS AND DASHES

POWER LOGIC LED INDICATES KEYING AND BATTERY STATUS

SPECIAL S&H \$3

OUR WARRANTY IS THE BEST IN THE BUSINESS: All products guaranteed for 1 year under our ZERO CUSTOMER COST warranty. No charge for shipping and repairs.

Ace Systems A

18141 965-5937 BOX 83; WILCOX, PA 15870





**CIRCLE 335 ON READER SERVICE CARD** 

#### MADISON SHOPPER

CALL FOR ORDERS 1 (800) 231-3057 1-713-520-7300 OR 1-713-520-0550 TEXAS ORDERS CALL COLLECT FAX 1-713-771-7759

ALL ITEMS ARE GUARANTEED OR SALES PRICE REFUNDED

New Icom IC 781 Kenwood TH215A, TH25AT.....Trade in your old HT New Kenwood TM-621A, 144/220 MHz FM



Kenwood TS 140S

.Call for trade



New Kenwood TM-721A, mobile. ICOM 28H/TTM



IC 781	Call
Icom 761	2300.00
Shure 444D	56.95
HEIL BM10 Boom Mike, wired 8 pin	69.00
HEIL HM5 Desk Mike	62.00
NYE MB5A Tuner	569.00
Alpha Delta Transitrap HV	33.00
CSI Private Patch IV	469.00
Ameco PT 3 Pre Amp	99.00
Larsen 2-meter on glass	49.95
Anteco 2M, 5/8, Mag. Mount, Comp	
Van Gordon G5RV	
Valor AB5 mobile	
Thousands of panel meters	
Aerovox 1000 pt/500 V feedthrough caps	
Transformer 120 V Pri., 1050 V/1A. (Sec. #18	
100 mfd/450V Axial Cap	
120 mfd/450V Axial Cap	
Arista SWR Bridge 3-30 MHz	
831SP-PL259 Silverplate (Amphenol)	
82-61 N Male (Amphenol)	
82-202-1006 N Male (9913)	
Double Female UHF	
UG176 RG8X	each .40
Receiving tubes 50-90% off list price	Call
Santec Boom Mike/Headset (fits ICOM)	
Rohn SA 25G 67 (67 inside arm)	each 125.00

USED EQUIPMENT

All equipment, used, clean, with 90 day warranty and 30 day trial. Six months full trade against new equipment. Sale price refunded if not satisfied.

Call for latest used gear (800) 231-3057

Don's Corner:

Have you tried the new "Delta Loop" Antenna? I have and it works great! Contact Delta Loop Antenna P.O. Box 8063

New Fairfield, CT 06812 See CQ June '88 Review

GNU PROD

TE Systems 2m Amp 30-160 watts GaAs fet ......\$229.00 POLICIES

Minimum order \$10.00. Mastercard, VISA, or C.O.D. All prices FOB Houston, except as noted. Prices subject to change without notice. Items subject to prior sale. Call anytime to check the status of your order. Texas residents add sales tax. All items full factory warranty plus Madison warranty.

Bird and Belden products in stock. Call today.



3621 FANNIN HOUSTON, TEXAS 77004



### FEEDBACK

In our continuing effort to present the best in amateur radio features and columns, we recognize the need to go directly to the source-you, the reader. Articles and columns are assigned feedback numbers, which appear on each article/column and are also listed here. These numbers correspond to those on the feedback card opposite this page. On the card, please check the box which honestly represents your opinion of each article or column.

Do we really read the feedback cards? You bet! The results are tabulated each month, and the editors take a good, hard look at what you do and don't like. To show our appreciation, we draw one feedback card each month and award the lucky winner a free one-year subscription (or extension) to 73.

To save on postage, why not fill out the Product Report card and the Feedback card and put them in an envelope? Toss in a damning or praising letter to the editor while you're at it. You can also enter your QSL in our QSL of the Month contest. All for the low, low price of 25 cents!

#### Feedback# Title

- 1 Welcome Newcomers!
- 2 Never Say Die
- 3 Book Review: 1934 Official Shortwave Radio Manual
- 4 QRX
- 5 Home-brew: Microwave Test Equipment
- 6 Home-brew: Super Simple Attenuator
- 7 Feedback
- 8 Home-brew: 220-MHz Transverter
- 9 Home-brew: Cheap And Dirty Oscillator
- 10 Review: AutoSketch
- 11 Review: Bird 4381 Wattmeter
- 12 Home-brew: Inexpensive Marker Generator
- 13 Review/Home-brew: Visitel SSTV
- 14 Home-brew: Which End Is Up?
- 15 Home-brew: Commodore 64 Voltage Protector
- 16 Review: Hamcall

#### Feedback# Title

- 17 Guide For Troubleshooting Switching Power Supplies
- 18 Hacker's Shack
- 19 New Products
- 20 ATV
- 21 Special Events
- 22 Homebrew: New Uses For Old Meters
- 23 RTTY Loop
- 24 Letters
- 25 Homing In
- 26 Barter 'n' Buy
- **27 ORP**
- 28 Ham Help
- 30 Above and Beyond
- 31 Review: Coaxial Dynamics 81000-A Wattmeter
- 32 Dealer Directory
- 33 Index: 1/89
- 34 Ad Index
- 35 Hamsats
- 36 Propagation
- 37 Ask Kaboom
- 38 Homebrew: LED Checker
- 39 73 International

## FELLOW RADIO AMATEURS,

You've discovered the greatest hobby in the world. And 73 Amateur Radio captures the excitement of amateur radio like no other ham magazine in print today. With 73, you'll have fun discovering the thrills of this great hobby. And while you're at it, you'll also learn more about ham radio.

Don't take the risk of missing out on all 73 has to offer. You can have your issue of 73 delivered to your home every month for just \$19.97 (12 issues)-that's 43% off the cover price! And with every paid subscription we'll send you a FREE GIFT: a great looking 73 baseball cap.

A home delivered copy of 73 means you'll never miss out on these tremendously popular monthly columns:

- Construction projects: The most homebrew projects anywhere.
- •Product reviews: Belly-to-belly matchups of new gear.
- · Aerial View: Everything you'll ever want to know about antennas.
- •QRP: For low power aficionados.
- . WEATHERSATS: Get the latest fax on the weather.
- •Never Say Die: And you bet I won't.
- •73 International: 73 Amateur Radio is the only ham magazine with monthly news from every corner of the world.

## I want to receive my copy of 73 Amateur Radio at home ery month. Please start my subscription immediately:

#### SUBSCRIBE TODAY.

And remember-with every paid subscription order, you'll receive a FREE 73 BASEBALL CAP, and SAVE 43% OFF THE COVER PRICE!

Address			
City		State	Zip
☐ Bill Me	□ Che	ck Enclosed	☐ Charge my credit card
Account #			
□ MC	□ Visa	☐ Amex	Exp. Date
Signature	Mary		

## THE 220 MHZ ALL-MODE TRANSVERTER

Designed for the dedicated home-brewer.

by Robert E. Bloom W6YUY

B ecause of the increased interest and activity in 220 MHz single sideband and the positive response to my Two-Meter Transverter project in July 1987 73 (pps 32-43), I have now designed an improved, 220 MHz version of the transverter. This transverter is capable of FM repeater operation as well as CW and SSB, and it's much more sophisticated than the usual FM transceivers and hand-helds on the market. All frequencies on this unit can be set with direct read-out to the nearest 10 Hz. Of course, DX simplex operation on both FM and SSB is one of its most exciting features.

Like the earlier unit, this is an all-mode transverter specifically designed to interface with the Kenwood TS-940S HF transceiver. It will also work with other full-frequency coverage transceivers equipped with a transverter access plug. The transverter has a CW output of 3-1/2 watts. I will cover in a later article a 220 MHz DMOS linear amplifier with a power output of 60 watts.

#### Why Not PC Cards?

The construction of this unit uses point-topoint wiring in a soldered PC-card structure that provides several benefits.

- A printed circuit board would require foil circuits on both sides, making double-deck construction impossible.
- Compartmentalizing would require a separate PC board for each stage or section.
- A PC card would require more space because of restrictions on parts placement.
   With this type of construction you can use the walls of the compartment as well as the floor for mounting parts.
- Exact duplication of components is not required.
- 5. Excellent interstage isolation.
- More freedom and ease of modification than normal printed circuit board techniques.

Your TS-940 transceiver must be modified, of course, to work with the 220 MHz transverter, because 222 to 225 MHz will be mapped into 22 to 25 MHz and the unmodified transceiver will not transmit outside the ham bands. (Obviously, it is not legal to transmit with the modified Kenwood outside the amateur bands authorized by your class of license.)

#### Take It Step-by-Step

Realizing the apprehension you may feel

when looking at a complex project, I provided, in Figures 5 and 6, drawings of the layout of the major parts. By showing the approximate placement of coils, tuning capacitors, and transistors, I hope to simplify the placement of the rest of the components for you. Since you are building this unit step-by-step, you won't have to place the shields between stages in exactly the locations shown in the drawings. Also, your components may be of different sizes, but the compartments should have enough space in most cases.

#### THE HOUSING

#### Case and Module Fabrication

The 220 MHz transverter is a one-piece module with a housing made up of double-sided PC board material. The top of the chassis contains the receiver and oscillator chain; the bottom has the transmitter and control circuitry.

The outside dimensions of the transverter assembly are 8-% x 4-¼ x 2-%". The height of the partitions is 1/16" less than the depth of the compartment, so the top and bottom covers fit flush with the side panels. Similarly, the front and back panels are ½" wider than

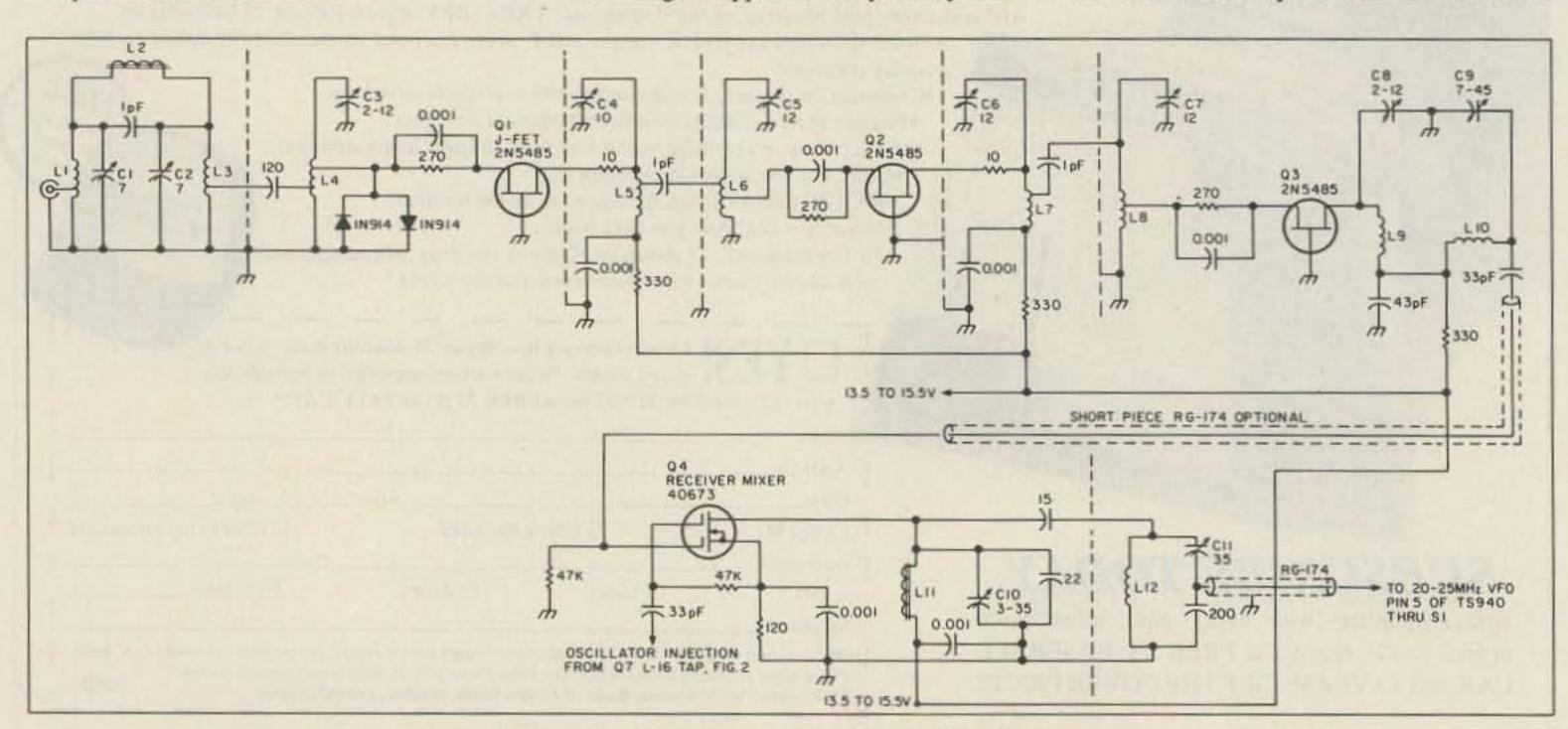


Figure 1. Schematic of the receiver portion of the 222-225 MHz transverter.

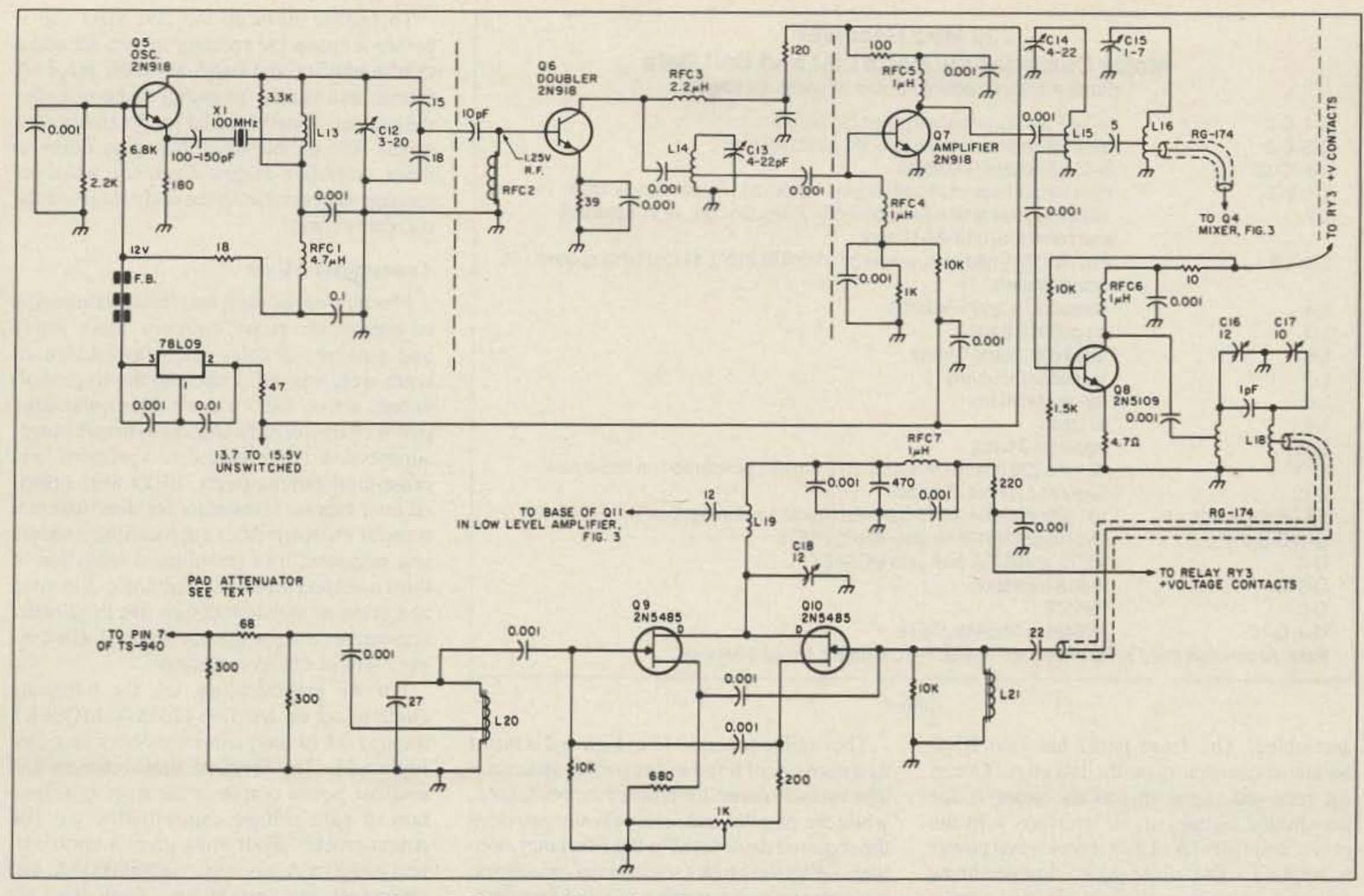


Figure 2. Schematic of crystal oscillator circuit (100 MHz) and doubler.

the main circuit board chassis to allow for the 1/16" side panel thickness.

Draw a pencil line down the middle of each side piece to help in locating the main center board that separates the top from the bottom. Start by tack-soldering just inside each end, making sure that the sides are at exact right angles with the center board. Then tack the end pieces into position. When the box is square, solder the corners and then seam-solder the sides from the inside.

Figures 5 and 6 are parts layout drawings showing the individual compartment sizes,  $\pm 1/16''$  and do not allow for the  $\pm 1/16''$  thickness of the separators. These dimensions are flexible and can be used as an indication of how much room you need and how much space you have left as you go along.

The compartment separators are also made

up of double-sided PC card stock and construction is serial: you complete one stage and install a separator before going on to the next stage. This way, you won't be caught either short or long on space. Drill all feedthrough holes in the compartment separators before soldering the separators indrilling afterwards is difficult!

Single-sided PC stock is used for the terminal mounting pads to which component leads are soldered. If all the PC material you have is double-sided, you can remove the foil from one side by holding the material in a bench vise, heating one side gently with a propane torch, and pulling off the foil with pliers.

Make up a supply of single-sided strips-1/8", 5/32", and 3/8" wide—and snip off pieces as needed with diagonal cutters. Using a single drop of Eastman 910 cement (Crazy

Glue), position these pads where needed with long-nose pliers. Four seconds later, you can solder to the pad. Should you decide that the pad is not in exactly the right position, you can remove it by prying with a pocket knife or small sharp screwdriver. Do not re-use a pad, as it will not hold securely the second time.

The unit will operate well without the covers in place. However, when the top cover is removed exposing the receiver's pre-selector stages, the unit will pick up strong signals even if it isn't connected to an antenna. Rather than secure the covers permanently, you can hold them in place with transparent tape for easy access to the circuitry.

#### **Panel Hardware**

You can drill the holes in the front and back of the case either before or after the box is

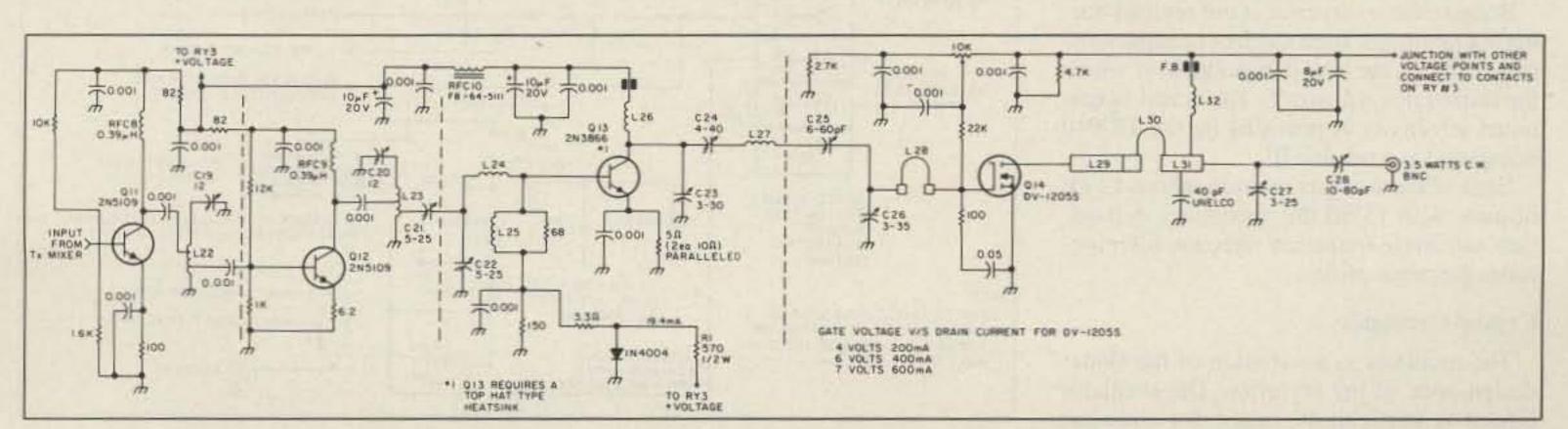


Figure 3. 220 MHz transmitter low-level amplifier section.

	220 MHz Receiver  Major Components Parts List and Coil Data (Small resistors, capacitors, and inductors not listed)
C-1, C-2	1–7-pF quality miniature piston capacitors
C-3-C-8	2–12 pF Johnson air variable, PC board ceramic
C-9-C-12	3–35 pF ceramic variables
L-1, L-3	Four turns #16 or 18 tinned wire 1/4" inside dia., tapped at 1-1/4 turns
L-2	19 turns #20 enameled wire on T-50-12 Amidon core, or 21 turns #24 enameled wire on T-37-12 core
L-4-L-9	4 turns #16 tinned wire, wound on #3 drill (0.212"), all four turns spaced 1-1/2 wire diameters
L-4	tapped at ¾ and 2-1/2 turns
L-5	tapped at 2 turns
L-6	tapped at ½ and 3 turns
L-7	tapped at 2-1/2 turns

tapped at 3 turns L-8 L-9 no taps L-10 tapped at 3 turns

22 turns #28 enamel wire on T-25-6 Amidon powdered-iron toroid core L-11

L-12 Same as L-11 but 19 turns

101 size of 43, 64, or 75 material; typical Amidon designation, FB-43-101 FB Ferrite Beads

Q-1-Q-3 2N5485 or 2N5486 (or equivalent) JFETs Q-4 40673 or 40673A dual gate MOSFET

Q-5-Q-7 2N918 transistor Q-8 2N5109

Q-9, Q-10 2N5485 or 2N5486 JFETs

Note: All resistors used in the project are 1/4 watt ±10% unless stated otherwise.

#### Table 1.

assembled. The front panel has two BNC bulkhead connectors on the left edge. One is for received signal in and the other is for transmitted signal out, to interface with the power amplifier. An LED shows when power is applied. The three-pole, double-throw miniature switch and eight-pin male mike bulkhead connector complete the panel. The eight-pin connector couples to the TS-940 interfacing cable. The back panel has a foursection miniature barrier strip for source power to the transverter.

#### CIRCUIT SECTIONS

#### Receiver Converter

The receiver portion (shown in Figure 1) has three JFET pre-amplifier stages. Dual gate MOSFETs would provide twice the gain, but much less stability and more noise. The bandwidth of these stages is set by positioning the taps on the RF coils (see the Coil Tapping sidebar). A tap placed closest to the top or high impedance point of the coil provides heavy loading, driving the Q of the stage down for a broader bandwidth. The lower the tap point, the higher the circuit Q, and the more selectivity and gain per stage.

Because the transverter is not retuned during operation, the bandwidth or bandpass discussed here is the total bandwidth over which the transverter will work. The actual operational selectivity is provided by the TS-940 being used as a tunable IF.

Each of these stages provides about 12 dB of gain, with 15 dB the maximum. A bandpass and image frequency rejection filter precedes the preamplifier.

#### Crystal Oscillator

The oscillator is a variation of the Butler design—one of my favorites. The oscillator circuit is particularly suited for overtone crystals, and, with light loading, is very stable.

The oscillator coil L-13 in Figure 2 is tuned by a network of fixed and variable capacitors. The variable capacitor is tuned for resonance, while the parallel and series divider provides the required drive level to the frequency doubler. (With the proper selection of capacitors, we can retain the correct parallel [productover-the-sum] capacity, and we can select a correct drive level for the frequency doubler. In addition, we reduce loading on the oscillator output circuit.)

The selection of coil tap on L-13 provides the oscillator feedback voltage required for stable oscillation. The 100 MHz crystal oscillator feeds the doubler, which retains about 66% of the oscillator's energy. Using a 100-MHz crystal and a doubler, the 200 MHz is much cleaner than it would be if you used a tripler. A simple doubler circuit provides the required 200-MHz output frequency, while the amplifiers with double-tuned bandpass circuits clean up the frequency from the output of the doubler stage.

To further clean up the 200 MHz signal before it enters the receiver mixer, we add a third amplifier and bandpass filter stage. A fourth, and similar amplifier stage provides the heavier signal required for the transmitter mixer. The double-tuned bandpass filters in these amplifier stages clean up whatever garbage is generated in the early stages of the oscillator chain.

#### Transmitter Mixer

Much research went into the determination of transmitter mixer circuitry. Both active and passive, double- and single-balanced types were studied. I selected the single-balanced, active JFET circuit after comparing major characteristics such as dynamic range, suppression of intermodulation products, and cross-modulation effects. FETs were selected over bipolar transistors for their inherent transfer characteristics approaching a square law response, thus providing a reduction of third overtone products. Harmonic distortion and cross-modulation effects are third-order dependent, and are greatly reduced when using FETs in a balanced mixer.

For RF amplification, use the following guide to set up the DV-1205S V-MOSFET stage Q-14 in the main transverter unit (see Figure 3). The level of drain current and ultimate power output of the stage is a function of gate voltage controlled by the 10k potentiometer. Four volts gives a drain current of 200 mA, six volts yields 400 mA, and seven volts sets up 600 mA. If you don't get an increase in power output with increased drain current, you don't have enough drive power and it isn't economical to increase the drain current further. Since this project has three MOSFET linear amplifier stages, set the output levels for only what you require. On the other hand, if the drive is much greater than you need, don't worry about blowing the FETs, since you cannot hurt them by overdriving.

#### Control Circuit Function

Refer to Figure 4 and Table 4. Plugging the DIN plug into the TS-940 mechanically switches the TS-940's input circuitry to desensitize it to HF signals. At the same time,

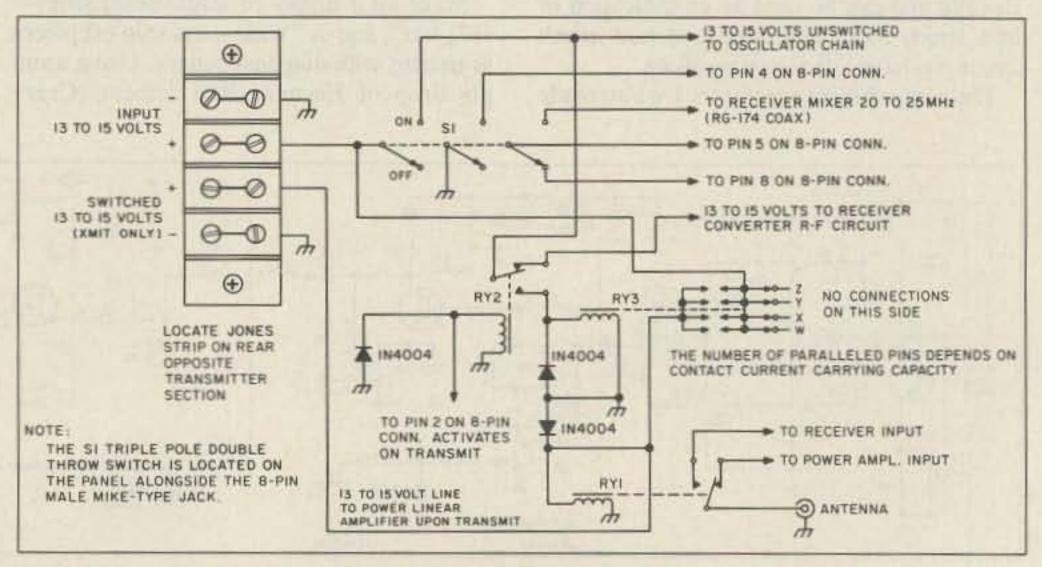


Figure 4. Control circuit wiring diagram.

With SW-1 ON, the first set of switch contacts applies 13 to 15 volts from the input terminals of the barrier strip to the RY-2 armature contact, providing voltage to all of the receiver circuitry and the oscillator chain (except for the Q-9 stage). The second set of switch contacts grounds the coil of RY-3 in the TS-940S, closing the relay, disconnecting the VFO, and disabling other LF circuits in the TS-940.

When you press the microphone push-totalk (PTT) switch, the Kenwood puts 12 volts at 50 mA on pin 2 of the 940's DIN plug, activating the transverter RY-2, which in turn removes the supply voltage from the receiver and activates transverter RY-3. RY-3 then applies supply voltage to the Q-9 output stage along with all the source voltages to the transmitter section. In addition, plus voltage is supplied to the barrier strip for the outboard linear amplifier and antenna relay #1. Releasing the PTT switches the transmitter and its associated circuitry off, and returns the unit to receive.

Toggling SW-1 to OFF, the arm of the third pole connects pin 5 with pin 8 on the 940's transverter plug. This allows the TS-940 to operate in the normal manner on HF, even though the transverter is still connected.

When purchasing the RY-2 control relay, keep in mind that its 12-volt actuating voltage comes from the TS-940, and the maximum current available is 50 mA. Many 12-volt relays require more than twice this level. The unit you select should have a field coil resistance of no less than 250 ohms.

#### TS-940

#### TS-940 Interface Cable

A 30" cable connects the transverter to the XVTR plug on the back of the TS-940 (see Table 4). Get the eight-pin DIN plug from Kenwood. Don't try to buy this plug elsewhere, as the plug you get probably won't fit the Kenwood's jack. I purchased three from other sources; no two were the same and none of them fit the TS-940. Just connect like numbers on the DIN plug and the eight-pin mike jack. You'll need three runs of small-diameter coax for pins 5, 7, and 8. Use

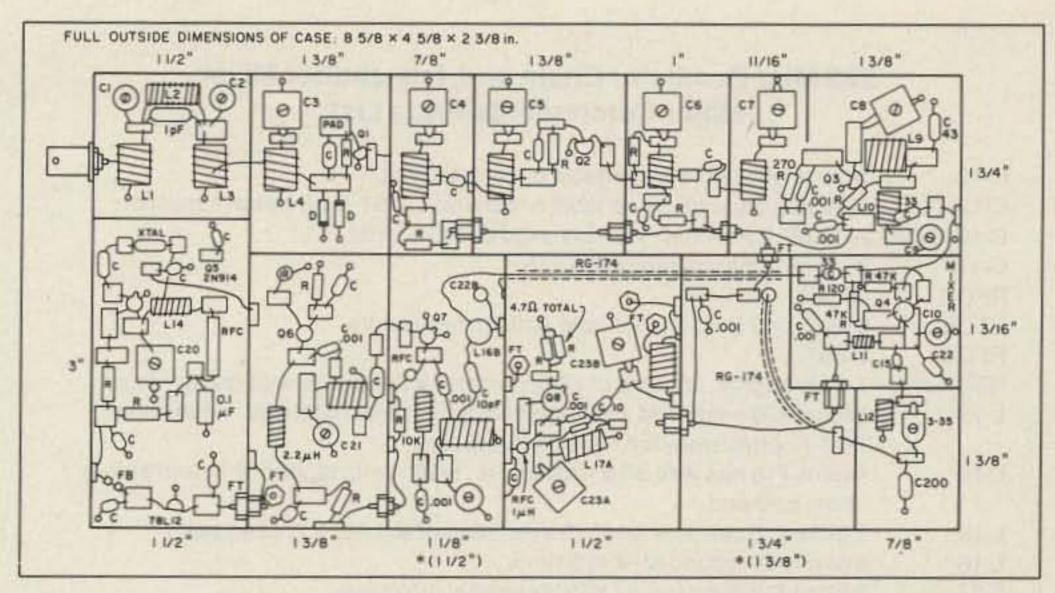


Figure 5. Major parts positioning (approximate dimensions) for the receiver and oscillator, top section.

cable with a Teflon dielectric. Don't use RG-174—the dielectric can melt during soldering, causing a short. Pins 1 and 3 are shield ground. Use a good grade of #20-stranded between the two number 2 pins and the two number 4 pins. Pin 6, ALC on the transceiver, is not used. Pin 6, by the way, is the center pin on the DIN plug, while pin 8 is the center pin on the eight-pin mike connector . . .

Recall that the very act of inserting the DIN plug into the 940 transverter jack disconnects the HF front end in the 940 to avoid leakthrough of HF signals at what is now the first intermediate frequency. In order to use the Kenwood on HF when the transverter is plugged in, a switch in the transverter connects pins 5 and 8 when the transverter is turned off.

Pin 2 provides 12 volts (at a maximum of 50 mA) during transmit for use as PTT in the transverter. A ground on pin 4 by the transverter disables the TS-940's power amplifier. RF/IF input signals between 22 and 25 MHz come from the transverter to the Kenwood on pin 5 with the outgoing (transmitted) signal at a level of about 100 mW on pin 7. Pin 8 is the TS-940's HF input, which must be connected to restore HF operation.

#### DIMENSIONS SHOWN ARE APPROXIMATE FOR INSIDE OF THE PARTICULAR COMPARTMENT 2 11/16" RY2 MULTI-CONTACT 2 11/16" RELAY ALL CONTROL CABLES AND WIRING TO 8-PIN CONN. AND SWITCH ROUTE THRU HERE DOUBLE THROW SWITCH UNELCO 1 25/32" 4 5/8" 2 1/4 1 7/16"

Figure 6. Major parts positioning for the transmitter and control, bottom side.

#### TS-940 Modification

To enable the TS-940 to transmit outside the regular ham bands, cut diode D-130 from the circuit. The transceiver will then transmit anywhere between 1500 kHz and 30 MHz. D-130 is located on the unit "B" PC board just behind the LCD display on the panel. (The diode is identified, as are other components, by screening on the PC board.) I removed the five screws on the module containing the board, but the board is still difficult to access and requires patience. A letter from a New Zealand reader of my previous transverter article suggested loosening the panel to the point where it could be tilted forward, exposing the diode, which is then cut free at one end using a diagonal cutter. The VFO frequency for the tunable IF is 22 to 25 MHz. Thus, the TS-940 dial read-out for a frequency of 223.259.81 MHz will be 23.259.81. The first digit "2" is understood, as all of the frequencies are in the 200-MHz range. For example, 22 on the dial indicates 222 MHz, plus all of the subsequent digits. Note that the frequency is read to the closest 10 Hz, so be sure to zero-beat both the TS-940 crystal and the transverter oscillator to WWV.

#### **Construction Aids**

Figure 4 shows the control circuit wiring diagram. Schematics for the receiver and transmitter sections, as well as separate major parts list for each section, are furnished. See Tables 1-3. In addition, see the photographs of both top and bottom views of the transverter.

If you follow the coil winding data, you should not have a problem attaining resonance in any of the stages. Coil construction has been further simplified by using toroidal cores. These are readily available in small quantities at under a dollar each from Amidon Associates, Inc., 12033 Otsego St., North Hollywood CA 91607. Tell them you saw the cores mentioned in 73 Magazine.

#### **Potpourri of Technical Construction Notes**

In the bandpass filter in the Q-4 transistor stages, L-10 is lightly coupled and at right

#### 220 MHz Oscillator Chain and Transmitter Mixer **Major Components Parts List**

C-12	3-20 pF miniature air variable or ceramic disk
C-13, C-14	4-22 pF miniature air variable or ceramic C-151-7 pF piston capacitor
C-16, C-18	2-12 pF Johnson air variable used on PC boards
C-17	2-10 pF Johnson similar to C-16
RFC-1	4.7 μΗ
RFC-2	3 turns on FB-64-5111 6-hole Amidon ferrite core
RFC-3	2.2 μΗ
RFC-4-7	1.0 μH approx. 25 turns of #28 enameled wire on a ½-watt resistor form
L-13	7 turns #20 enameled wire tapped at 2 turns from cold end, wound on a
	T-37-12 powdered-iron Amidon toroid core
L-14	4 turns #18 bus wire 3/16" inside dia., 9/16" long, tapped at ¾ turn at 3-¾" from cold end
L-15	5 turns #18 bus wire 3/16" ID x 1/2" tapped at 1-1/2, 21/2 at 4 turns
L-16	6 turns #20 tapped at ¾ at 5 turns
L-17	5 turns #18 bus wire 1/4" x 1/2" tapped at 1-1/2 turns
L-18	4 turns #18 bus wire 1/4" x 1/2" tapped at 1-1/2 turns
L-19	4 turns #16 bus wire wound on #3 drill (0.212") tapped at 1-1/2 turns from cold end

Table 2.

angles to the center of L-9. Do not place L-9 and L-10 closer than \4" to each other. The bandpass filters of both the Q-7 and Q-8 circuits also have their coils at right angles for minimum coupling. Here, the coupled coils should be placed at least 1" apart, so that coupling is primarily through the 5 pF and 1 pF capacitors, respectively. Even at this distance, there's some mutual coupling.

There are a number of places where RF chokes are called out. Most of these are wound using 14- and 1/2-watt resistors as the coil forms. The following should assist in coil winding.

A reactance vs. frequency, capacity, and

inductance chart or a cardboard reactance slide rule are great tools. A grid dip meter is another. You'll need several 0.39-µH eled wire on the resistor, and grid-dip with a capacitor to check the value.

You'll also need some 1.0-µH chokes.

chokes. A 0.39-µH choke will resonate at 50 MHz when shunted with a 27-pF capacitor. By using this point, you can locate other capacitance and inductance values on the scales. You can make the 0.39-µH unit with a 1/2-watt resistor of 3000 ohms or more. Make notches at the ends of the resistor with a jeweler's file to prevent the wire from slipping. Close-wind 25 turns of #28-gage enamonates at 70 MHz when shunted with 27 pF. Refer to the dimensions of stage components. Notice that on the receiver side, a compartment of 1 ¾ " has only a few components. This compartment originally had a redundant stage. Notice also that the Q-7 stage is a bit crowded. If you expand the width of this compartment, you will be able to move

These should resonate at 16 MHz when

shunted with 100 pF. Fill a 1/2-watt resistor

with #31 wire. Wire size is important. Note

that 25 turns of #28 wire on a 1/2-watt form

also makes the same 1-µH value. As an addi-

tional aid, note that a value of 0.18 µH res-

the Q-8 stage down.

On the front panel, the BNC connectors are located 1" in from the case edge and are 1-1/4" on center from one another. The eight-pin mike-type connector is % " in from the opposite edge of the case. Positioning of these parts is not critical.

I had no problem laying out the complicated transmitter section. If you need more width, the Q-12 adjacent stage has plenty of room and can be moved further to the right.

A number of relatively long conductor and RG-174 (1/4" coaxial cable) runs enter and leave compartments that are not adjacent, but opposing. Also, some of the feedthrough terminals are not bypass capacitor feedthroughs. These also come out on the opposite side of the box (top or bottom). Carefully check to make sure that there is nothing in the way on the opposite side, and that the feedthrough enters the proper stage on that side. The component layout drawings represent relative positioning. In order to keep the drawing clear, only major components have been drawn in.

Caution: The Q-13 2N3866 transistor requires a top-hat heat sink. The case of this transistor is connected to the collector and it takes unkindly to being shorted, even for an instant. Make sure the top hat clears other parts when positioning this transistor on the board.

#### 220 MHz Unit RF Chain **Major Parts List for Transmitter**

ı		
l	C-19, C-20	2-12 pF Johnson air variable for PC boards
l	C-21-C-23	5–25 pF Arco 400 series compression
١	C-26, C-27	5–35 pF Arco 400 series compression
l	C-24	4-40 pF Arco 400 series compression
١	C-25	6-60 pF Arco 400 series compression
l	C-28	10-80 pF Arco 400 series compression
l	Q-11, Q-12	2N5109 transistor
l	Q-13	2N3866 transistor with top-hat heat sink
١	Q-14	M/A COM PHI RF power MOSFET DV-1205S 5 watt
	L-22	5 turns #18 bus wire, wound on #3 drill, 9/16" long, tapped at ½ and 1-1/2 from cold end
١	L-23	Same as L-22, tapped at 1/2 and 1-1/4 turns
ı	L-24	3 turns #18, 0.3" diameter spaced 2 wire diameters
ı	L-25	7 turns #28 wound on a 62 or 68 ohm 1/4 watt resistor
l	L-26	5 turns #18 bus wire on #3 drill, 9/16" long
I	L-27	3 turns #18 bus wire on #3 drill, spaced 3 wire diameters L-28, L-303/4" of
l		#16 tinned bus wire bent into a hairpin 1/3" diameter
l	L-32	8 turns #22 Teflon covered wire, close wound 1/4" diameter
	L-29	1/4" wide strip of single-sided PC board material, epoxied as though it were another pad 0.66" long
	L-31	As in L-29, but 1/2" long
	R-1	Part of Q-18, 2N3866 bias circuit 570 ohm, made of a 1k ohm and 1.3k ohm
1		

#### **Test Equipment**

In order to test and align your transverter, you will need the following test equipment.

- 1. A stable signal generator or calibrated oscillator and adjustable 50 ohm attenuator covering the appropriate RF range.
- 2. An electronic frequency counter covering the appropriate frequency range.
- 3. A VHF range RF vacuum tube voltmeter or a good DC VTVM with UHF RF probe. (Solid state is fine, too.)
- 4. A VHF grid dip meter to check coil resonance. (Not absolutely necessary if you follow coil winding data closely, but a real aid.)
- 5. A capacity bridge to confirm small values of capacity marked, and to set a given capacity in a test circuit. (See Ham Radio, March 1980, page 54.)
- 6. A Bird Model 43 wattmeter or other power measuring device, and a 50 ohm load (termination).
- 7. A multi-range Volt-Ohm milliammeter.

1/4-watt resistors paralleled

## TRAVEL FIRST CLASS, PAY COACH.



MS-101 Now, full feature 9, 10, and 12 Band World Receivers in a convenient shirt pocket size. Priced right for your budget including FREE Stereo Headphones. 1 year Limited Warranty on parts and labor. For a FREE full color catalog and a listing of dealers near you, write to Sangean America, Dept. 73AR-1

> SANGEAN A World of Listening™

9060 Telstar Ave., Suite, #202 El Monte, CA 91731 Telephone: (818) 288-1661 FAX (818) 288-8231

#### DATONG/GILFER for better listening





DATONG AUTOMATIC FILTERS/BLANKERS **CLEAN UP RECEPTION FL-3 Audio Filter provides** 12 poles of tunable filtering to dig out weak signals, remove interference automatically. Easy to connect. \$229.95 (+\$4). Model SRB2 Woodpecker Blanker blanks out Russian radar interference automatically. \$169.95 (+\$2.50).



DATONG ACTIVE RECEIVER ANTENNAS FOR BIG PERFORMANCE ANYWHERE 3-meter (91/4') dipoles with low-noise amplifiers at the dipole and at the interface. Indoor model (AD-270) uses flexible wire elements; outdoor model (AD-370) uses stainless steel whips. Mount anywhere. 6 dB gain at the dipole, 12 dB at the interface. 100 kHz-70MHz. AD-270 \$114.50 (+\$3); AD-370 \$129.50 (+\$4.50); power converter \$15,95.

ORDER PHONE: 1-800-GILFER-1

52 PARK AVE. PARK RIDGE, NJ 07656 Ph 201/391-7887

CIRCLE 98 ON READER SERVICE CARD

### BATTERIES "R" US...

You've bought our replacement batteries before... NOW YOU CAN BUY DIRECT FROM US, THE MANUFACTURER!



CM2, PB2 7.2v @ 500MAH CM5, PB5 10.8v @ 500MAH **SUPER 7S & 8S** 13.2v @ 1100MAH 9.6v @ 1200MAH (base charge only) Introductory Offer! SUPER 7S & 8S - \$64.95 each




KENWOOD KNB-1 10.8v @ 500MAH KNB-4 7.2v @ 2000MAH KNB-5 12v @ 1000MAH 12v @ 1000MAH PB-1



YAESU/MAXON FNB-10 7.2v @ 600MAH FNB-12 12v @ 500MAH \*FNB-10(S) 7.2v @ 1000MAH \*same size case as FNB-12

Introductory Offer!

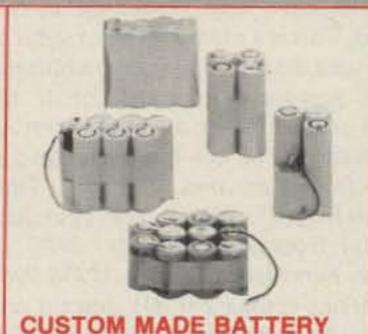P4W 11v @ 500MAH - \$22.63 FNB-2 11v @ 500MAH - \$22.63



**PACKS & INSERTS** Made to your specifications. Introductory Offer! KENWOOD PB-25-\$20.00; BP-5-\$23.00 BP-3-\$18.95

ICOM

BP-5-\$23.00; BP-3-\$18.95





MasterCard and Visa cards accepted. NYS residents add 81/4% sales tax. Add \$3.00 for postage and handling.



SOURCE FOR ALL YOUR COMMUNICATION BATTERY REPLACEMENT NEEDS.

Prices subject to change without notice.

W & W ASSOCIATES

29-11 Parsons Boulevard, Flushing, N.Y. 11354

WORLD WIDE DISTRIBUTORSHIPS AVAILABLE. PLEASE INQUIRE.

In U.S. & Canada Call Toll Free (800) 221-0732 • IN NYS (718) 961-2103 • Telex: 51060 16795 • FAX: (718) 461-1978

**OUR PRICES** CAN'T BE BEAT!

SEND FOR FREE CATALOG & PRICE LIST!

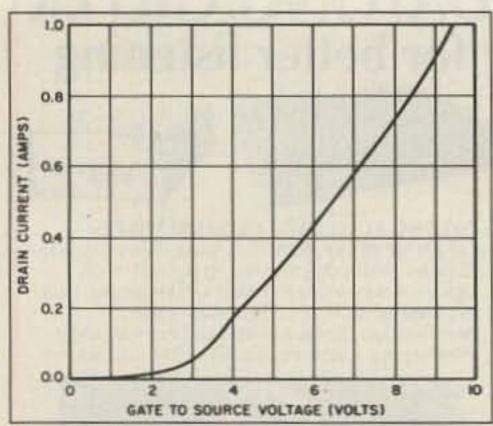


Figure 7. Drain current vs. gate-to-source voltage for the DV-1205S, located in the low-level amp section.

#### Where To Find Components at Reasonable Prices

In this project you will use quantities of miniature plate capacitors, various sizes of compression capacitors, disc ceramic variables and fixed capacitors, and dipped silver micas (dog bone) components. Fixed disc ceramic of 0.001 mF are sprayed around the source voltage lines as bypasses and as both coupling and decoupling circuits. In circuits requiring a degree of stability, use silver mica. Miniature PC board air variables, Johnson 2-12 pF, usually 8 plates total, are used in stable RF circuits. These plates and small, high quality Arco compression type resonate coils.

You will notice lots of tuning capacitors. This adds up to a nice piece of change. Many of the stages in the receiver could be tuned temporarily with a good-quality variable capacitor. Remove the variable carefully so as not to change its setting and measure its value with a capacitance bridge. Now insert a dipped silver-mica of that value in that spot. You can make minor adjustments by compressing or expanding the coils on the toroidal core until resonance is re-established. This is a mildly complex substitution I have seen described in many publications.

All powdered iron and ferrite toroidal cores and baluns are available from Amidon Associates. You can buy the eight-pin DIN plug from Kenwood. Get two. The price ranges from \$2 to \$2.50 each. I purchased my crystal from Jan Crystals, 2400 Crystal Drive, Fort Myers, Florida 33906-9989. Order series resonant 0.001 percent accuracy and enclose a schematic diagram of the oscillator circuit.

MHz Electronics Inc., 3802 N. 27th Ave., Phoenix, AZ 85017 advertises in most ham

#### Coil Tap Mystery

Many hams throw up their hands when it comes to determining the position of a tap on a coil. In many cases, the tap impedance must match that of the following stage. Many hams who understand why the tap is there, think, "That's fine. I can find the proper point if only I know the base impedance of the transistor, or the collector impedance." Mathematical analysis can dissuade almost anyone, but don't despair!-several aids are available.

The impedance Nomogram, found in most handbooks, is practically indispensable for the RF builder. Better still are the cardboard reactance slide rules usually found in technical book stores.

AC or RF calculations are more complex. For example, you might want a capacitor coupling for an RF circuit, but you don't know which size capacitor to use. You can determine the size by relating the capacitor resistance to DC. Here the slide rule or Nomograph comes in handy. Since you know the frequency and you know what would be a tolerable resistance, you can line up the arrow with the frequency and look at the resistance scale adjacent to the capacitance scale. Select the capacitance that is opposite the lowest resistance you want.

We call the AC resistance "reactance" or "impedance." In a resonant circuit, to find a coil impedance, take the value of the capacitance that resonates with this circuit, set the rule to this frequency, and look up the reactance. In a circuit at resonance, the inductive and capacitive reactances are equal.

Often, instead of a tapped coil, you will find a capacitive divider across the coil with the tap at the junction of the two capacitors. The total capacitance of two capacitors in series can be compared to two resistors in parallel (the product of each over the sum of each):

$$C_{ST} = \frac{C_1 \times C_2}{C_1 + C_2}$$

After you get the resultant capacitance, use the slide rule to determine the reactance. You can find the reactance of each of the capacitors individually. See them as two resistors in a series across the coil, and you can visualize the proportions of voltage across the two resistors, i.e., frequency is 25 MHz. Two capacitors of 62 pF in series are across the coil. The reactance of the capacitors at that frequency is 100 ohms. The tap is at the 50 ohm point of the coil. Do not confuse this as the center of the coil, as the inductive reactance across the coil follows a square law rather than a linear law. The reactance of the coil at this point is 1/4 of the total.

#### **Coil Tap Loading**

This is the meat of coil tapping! You might wish to make some changes in the bandwidth of the receiver section of your transverter. Possibly, if you are interested in only a portion of the band, you may want to sharpen the selectivity.

Occasionally, when tuning a capacitor for resonance, you find a really sharp peak. Another time you might find the capacitor to have a much broader peak. Why is this? You have seen resonant curves in handbooks. If the circuit Q is high, the curve will have steep sides and a narrow bandwidth at some point down the curve, usually the half power point (3 dB). Measure the frequency at the half-power point on the low frequency side of the peak and again on the high-frequency side. The difference in frequency will be the bandwidth. If the coil Q is low, the bandwidth will be greater than if the Q is high.

How do you vary Q by tapping the coil? We can assume that in this circuit (a receiver RF amplifier stage) you don't know the collector impedance or the base impedance of the following stage. But you do know that there will be two taps on the coil, and that the taps will affect its Q and thus its selectivity or bandwidth. Here you have a coil and capacitor which will resonate this circuit at the desired frequency. If the coil wire is sufficiently large, and the coil diameter is 1/3 to 1/2, the length of the coil, the circuit should have a high Q called "unloaded Q." The selectivity will be high and the bandwidth will be very narrow.

Now you have to get this combination into the circuit to do some work. Ground one side of the coil to make the low impedance point. You want to feed energy into the coil from the collector of the transistor of that stage. The collector impedance will load the Q of this coil. If the impedance is high, you can connect it to the high end of the coil. The ideal point is where the Q drops to one-half. Though the ideal is not always possible, at any rate the bandwidth will increase. If the collector impedance is relatively low, you might wish to tap down the coil. Choose a point from 1/4 to 1/2 down. Collector impedance of a bipolar transistor is generally higher than the base impedance of the following stage.

Let's say you decide on a point 1/3 down the number of coil turns. Now comes the real loading, getting energy from this tank circuit into the base of the following stage. The base tap will be much closer to the bottom or low impedance point of the coil. Place it 1/2 turn up from ground. Generally at this point it takes somewhat sophisticated equipment to determine what is truly happening.

A sweep frequency signal generator, a calibrated marker generator, and a spectrum analyzer are used in the design laboratory. But when these are not available, there are other ways to make a satisfactory measurement. An RF vacuum tube voltmeter can really help.

Sending a steady signal into the receiver and using some type of indicator, possibly an S-meter on the transceiver, the capacitor is tuned to resonance. If the tuning is sharp, you know the bandwidth will be limited. Tapping the base further up on the coil will load the coil more heavily, and cut down the selectivity, because the tuning will be broader, and the receiver will cover a wider frequency range. One point: the further down the coil (toward ground) that you place the collector tap, the more stable the circuit; but circuit gain will be reduced.

publications. They also have crystals, transistors, and Unelco noninductive capacitors

for the power amplifier. (Send for a catalog.)

15-9	40/Transverter Jack-Pin numbers
8-pin DIN pin number	Function
1	Ground
2	PTT to transverter (12VDC @ 50 mA max.)
3	Ground
4	TS-940 Final Amplifier disable (Ground from transverter)
5	Received (input) signal from transverter
6	ALC from TS-940 (not used here)
7	Transmitted (output) signal to transverter
8	Internal TS-940 HF signal—connect to pin 5
	to restore TS-940 HF when transverter off.

Table 4.

Another excellent source for dipped silver mica capacitors, miniature variables, JFETs (15c), 4067 (25c) relays, and the small heat sink 2N3866 is Hosfelt Electronics, Inc., 2610 Sunset Blvd., Steubenville, OH 43952. The eight-pin mike type plug and jack are available from Henry Radio and Radio Shack.

Parts are also available at ham swap meets, and I have some items at very reasonable prices. If you have questions or comments, feel free to write me. Enclose an SASE for a response. Upon completing this project (I wish to emphasize taking your time, step by step), the gratification and pride you will feel cannot be expressed on paper.

The 220 power amplifier will appear in a subsequent issue of 73 Magazine. 78

## THE MOST AFFORDABLE REPEATER

ALSO HAS THE MOST IMPRESSIVE
PERFORMANCE FEATURES
(AND GIVES THEM TO YOU AS STANDARD EQUIPMENT!)

KIT, ONLY \$675
WIRED \$975
VHF OR UHF



#### **FEATURES:**

- SENSITIVITY SECOND TO NONE! GaAsFET front end on vhf models gives 12dB SINAD of 0.12uV (vhf), 0.15uV (220). UHF model 0.25uV std, 0.1uV with optional helical resonator preamp.
- •SELECTIVITY THAT CAN'T BE BEAT! Both 8-pole xtal filter & ceramic filter for > 100dB at only ± 12kHz. Helical resonator front end to combat desense & intermod.
- CLEAN, STABLE TRANSMITTER, up to 18W output standard; 50W with accessory power amplifier.
- •FCC TYPE ACCEPTED for commercial high band and uhf.
- Courtesy beep, field-programmable CWID, flutter-proof squelch, automatic frequency control to compensate for off-frequency transmitters (all standard features).
- •Full range of options available, such as autopatch, phone line or radio remote control, sub-audible tones, duplexers.

## ## HIGH PERFORMANCE TRANSMITTERS & RECEIVERS FOR REPEATERS AUDIO & DIGITAL LINKS, TELEMETRY, ETC.

#### •FM EXCITERS:

Kits \$99, W/t \$179. 2W continuous duty. TCXO & xtal oven options available.

•TA51 for 10M, 6M, 2M, 150-174, 220 MHz.


•TA451 for uhf.

FCC type accepted for commercial bands.

- Call for latest information on 900 MHz transmitters.
- •VHF & UHF AMPLIFIERS. For FM, SSB, ATV. Output from 10 to 50 Watts. Several models, kits starting at \$79.

## •R144/R220 FM RECEIVERS for 2M, 150-174, or 220 MHz. GaAs FET front end, 0.12uV sensitivity! Both crystal & ceramic filters plus helical resonator front end for exceptional selectivity: > 100dB at ±12kHz (best available anywhere)! Flutter-proof squelch. AFC tracks drifting transmitters.

Kit \$149, w/t \$229.

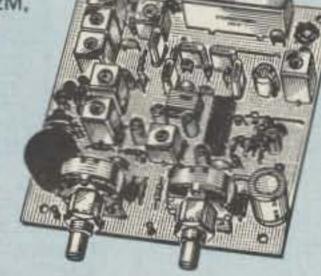

•R451 UHF FM RCVR. Similar to above. Tuned line front end, 0.25uV sens. (0.1uV with optional hel. res. preamp). Kit \$149, w/t \$229.

- •R901 FM RCVR FOR 900 MHZ. Triple-conversion, GaAs FET front end, 0.2uV sens. Kit \$169, w/t \$259.
- •R76 ECONOMY VHF FM RCVR for 10M, 6M, 2M, 220. Without hel res or afc. Kits only \$129.
- •Weather satellite & AM Aircraft receivers also avail.

FCC TYPE-ACCEPTED TRANSMITTERS & RECEIVERS AVAILABLE FOR HIGH-BAND AND UHF. CALL FOR DETAILS.

- Send \$1 for 36 page catalog by return mail.
   (Send \$2.00 or 4 IRC's for overseas mailing)
- Order by phone or mail
   Min \$3 S & H per order
- Use Visa, Mastercard, Check, or UPS COD.

#### GaAs FET PREAMPS at a fraction of the cost of comparable units!

## LNG -(\*) GaAs FET PREAMP ONLY \$59!

#### **FEATURES:**

Wired/tested

•Very Low Noise: 0.7dB VHF, 0.8dB UHF

•High Gain: 13-20dB, depending on frequency

- •Wide Dynamic Range: to resist overload
- •Stable: new-type dual-gate GaAs FET
- \* Specify tuning range desired: 26-30, 46-56, 137-150, 150-172, 210-230, 400-470, or 800-960 MHz.



400

\$39 Wired/tested

GaAs FET Preamp

& small size. Only 5/8"W x 1-5/8"L x 3/4"H. Easily mounts in many radios.

\* Specify tuning range desired: 25-35, 35-55, 55-90, 90-120, 120-150, 150-200, 200-270, or 400-500 MHz.



GaAs FET Preamp with features similar to LNG series, except automatically switches out of line during transmit. Use with base or mobile transceivers up to 25W.

\*Specify tuning range desired: 120-175, 200-240, or 400-500 MHz.

#### HELICAL RESONATOR PREAMPS

Low-noise preamps with helical resonators reduce intermod & cross-band interference in critical applications.

MODEL HRA-(\*), \$49 vhf, \$84 uhf.


\* Specify tuning range desired: 143-150, 150-158, 158-162, 162-174, 213-233, 420-450, 450-465, or 465-475 MHz.

## MEN

#### HIGH-SPEED DIGITAL RF LINKS

You've waited a long time for a simple, reliable, low-cost 9600 baud PACKET NETWORKING system. Now you've got it! Our new MO-96 MODEM and direct FSK Transmitters and Receivers for 220 or 440 MHz interface directly with most TNC's. Fast diode switched PA's output 15 or 50W. Call for complete info on the right system for your application.

#### **ACCESSORIES**

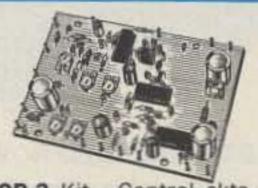

 COR-3 Kit. Control ckts and audio mixers needed to make a repeater. Tail & time-out timers, local spkr ampl, courtesy beep

• CWID Kit. Field programmable, timers, the works . . . . . . \$59

•AP-3 AUTOPATCH Kit. Use with above for repeater autopatch. Reverse patch and phone line remote control std. . . . \$79

•AP-2 SIMPLEX AUTOPATCH TIMING BOARD Kit. Use with above for simplex autopatch

• M O - 2 O 2 F S K D A T A MODULATOR Kit. Run up to 1200 baud digital signals through any fm transmitter with full handshakes. Radio link computers, telemetry gear, etc. \$39

#### RECEIVING CONVERTERS

Simple	-	Antenna Input Rang	Receiver (e Output
VHF MODELS Kit with Case Kit less Case Wired w/case	\$59 \$39 \$89	28-32 50-52 50-54 136-138 144-146 145-147 146-148 220-222 220-224 222-224	144-148 28-30 144-148 28-30 28-30 28-30 28-30 28-30 50-54 28-30
UHF MODEL: Kit with Case Kit less Case Wired wicase	\$69 \$49 \$99	432-434 435-437 432-436 432-436 439-25 902-928 902-928	28-30 28-30 144-148 50-54 61-25 422-448 430-450

See catalog for full line of 2w transmitting converters for vhf & uhf. Kits only \$79. Linear Amplifiers avail, up to 50 w.

Our 25th Anniversary

hamlronics, inc.

65-J MOUL ROAD HILTON NY 14468-9535
Phone: 716-392-9430 Hamtronics' is a registered tradomark

Spectrum Repeater/Link

**High Performance Boards & Sub-Assemblies** 

These are professional "Commercial Grade" Units-Designed for Extreme Environments (-30 to 60° C.) All Equipment Assembled & Tested.

For 10M, 2M, 220 MHz, & 440 MHz



COMPLETE SHIELDED RCVR. ASSY.

•8 Pole Front End Fltr. + wide dynamic range-

Sel. -6dB @ ± 6.5 KHz. -130dB @ ±30KHz. (8 Pole

e'S Meter', Discriminator & Deviation Mtr. Outputs!

**Complete Receiver Assemblies** 

Completely assembled & tested, w/F.T. caps,

·As used in the SCR 1000. Ready to drop into your

•UHF Rcvr. Assy. Now Available w/Super Sharp FL-

4 Helical Resonators. Greatly reduces IM & "out of

Receiver Front-End Preselectors

•FL-6: 6Hi Q Resonators with Lo-Noise Transistor

•FL-4H: 4Hi Q Helical Resonators & Lo-Noise Tr.

Provides tremendous rejection of "out-of-

band" signals w/out the usual loss! Can often be

Extremely helpful at sites with many nearby trans-

mitters to "filter-out" these out-of-band signals.

Call or Write for

**Data Sheets** 

Amp. in shielded housing. (420-470 MHz)

used instead of large expensive cavity filters.

Rcvr. Board mounted in shielded housing.

Exc. audio quality! Fast squelch! w/0.0005% Crys-

Reduces Overload, Spurious Resp. & Intermod.

VHF & UHF Receiver Boards

Totally Advanced Design!

•Sens. 0.25 μV/12dB SINAD typ.

Crystal + 4 Pole Ceramic Fltrs.

 New! 30 KHz B.W. IF Filter for High Speed Packet.

SO239 conn.

FL-4H

band" interference!

Amp (2M or 220 MHz)

system!

tal. ("Super Sharp" IF Fltr. also avail.)

SCR200A-VHF SCR450A-UHF

**New FL-4 UHF** 

or FL-4H Preselector Unit

Installed in Receiver

Helical Resonators


#### & Audio Mixer Board

ID250A CW ID

- •Improved! Now includes "audio mute" circuit and "Emergency Power ID" option.
- 4 input AF Mixer & Local Mic. amp.
- PROM Memory—250 bits/channel.
- Up to 4 different ID channels!
- Many other features. Factory programmed.
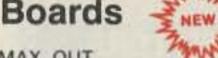
#### CTC100 Rptr. COR Timer/Control Bd.

- Complete solid state control for rptr. COR, "Hang" Timer, "Time-Out" Timer, TX local & remote Shutdown/Reset, etc.
- Includes inputs & outputs for panel controls & lamps.



- SCP12 12 VDC @ 0.3A MAX. OUT.
- SCP512 12 VDC @ 1A & 5VDC @ 0.4A out. (1.1A total max. out.)

#### **Power Supply Boards**

- SCP512A As above, but also w/−12VDC @ 0.1A

## Plug-in Coding Card

#### TTC300 TOUCH TONE CONTROLLER


- \*High performance, Super versatile design. To control any ON/OFF Function at a remote site via DTMF Radio Link.
- Uses new high quality Xtal Controlled Decoder IC, w/high immunity to falsing
- \*Decodes all 16 digits
- •3 ON/OFF Functions per Main Card. Easily expandable to any no. of functions w/Expansion Cards.
- Codes quickly field programmable via plug-in Coding Cards. Many unique 3-digit codes available. Not basically 1-digit as with competitive units.
- Latched or pulsed outputs.
- Transistor Switch outputs can directly trigger solid state circuitry or relays, etc. for any type of control function.
- Low Power Consumption CMOS Technology. 5VDC Input. Gold-plated connectors.



#### SCP30 HEAVY DUTY 30 AMP RACK MT. POWER SUPPLY

- 13.8 VDC out. 115/230 in, 50/60 Hz.
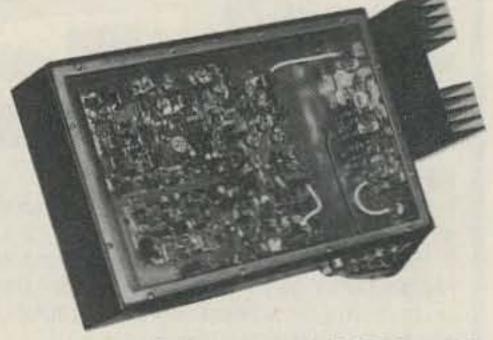
#### 30A @ 70% duty, 25A @ 100% duty. Massive 30 lb. Transformer & Heat Sinks.



#### Improved SCT410B Transmitter Assy.

#### SCT110 VHF Xmtr/Exciter Board


- •10 Wts. Output. 100% Duty Cycle!
- Withstands High VSWR
- True FM for exc. audio quality
- Designed specificially for continuous rptr. service. Very low in "white noise."
- Spurious 75 dB. Harmonics 60 dB.
- With .0005% precision grade xtal.
- BA-30 30 Wt. Amp board & Heat sink, 3 sec. L.P. filter & rel. pwr. sensor.
- BA75 75 Wt. unit also available

#### SCT110 Transmitter Assembly

- SCT110 mounted in shielded housing
- Same as used on SCR 1000 & 2000X
- Completely assmbld. w/F.T. caps, SO239 conn.
- •10, 30, or 75 Wt. unit.
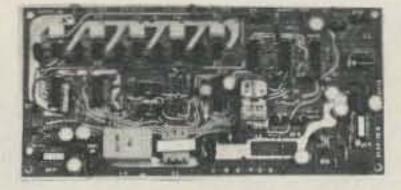
#### SCT 410B UHF Transmitter Bd. or Assy.

- Similar to SCT110, 10 Wts. nom.
- ·Includes "on board" proportional Xtal Osc./Oven circuitry for very high stability!
- \*BA-40 40W. U HF AMP, BD. & HEAT SINK



#### SCAP Autopatch Board

- Provides all basic autopatch functions
- \*Secure 3 Digit Access; 1 Aux On-Off function, Audio
- AGC; Built-in timers; etc. Beautiful Audio!
- 0/1 inhibit bd. also available
- Write/call for details and a data sheet

#### **RPCM Board**

- Used w/SCAP board to provide "Reverse Patch" and Land-Line Control of Repeater
- \*Includes land-line "answering" circuitry

#### Lightning Arrester For Autopatch •Gas Discharge Tube shunts phone line surges to

- ground Handles up to 40,000 Amps!
- The Best device available to protect Autopatch equipment from lightning damage. \$17.00 + S/H.

### PECTRUM COMMUNICATIONS CORP.

1055 W. Germantown Pk, S9 . Norristown, PA 19403 . (215) 631-1710 . Telex: 846-211

#### GORDON WEST'S RADIO SCHOOL

#### 21 DAY NOVICE



2 code topes 112 page book World maps Frequency charts Course certificate free magazine coupon 50 piece literature set!

\$70 in equipment certificates from ICOM, \$19.95 KENWOOD, and YAESU

COMPLETE NOVICE COURSE	\$49.95
4 code tapes, 2 theory tapes, 2	text books,
code oscillator set, examiner test p	backet, and
\$70 discount coupons.	
NOVICE TEXTBOOK	\$4.95

Written by Gordon West, this 112 page book contains all Novice questions and answers.

NOVICE CODE COURSE 6 tape stereo code course for learning the code from scratch. Includes certificates. TECHNICION THEORY COLLEGE

411777
\$19.95
\$19.95
with 4 topes

and 1 book. \$49.95 THE COMPLETE GENERAL 4 tapes & 2 books for theory plus 6 tape

stereo code set for CW speed building. GENERAL CODE COURSE 6 tope stereo code course for CW speed building from 5 wpm to 13 wpm.

THE COMPLETE ADVANCED 4 topes & 2 books for theory plus 6 tope stereo general or extra class code course. (Specify which CW tapes you want.) ADVANCED THEORY CLASS \$19.95

4 tope stereo theory course plus fully illustrated theory book.

\$49.95 THE COMPLETE EXTRA 4 tapes & 2 books for theory plus & tape stereo code set for CW speed building 13 wom to 22 wpm+!

\$39.95 **EXTRA COD€ COURS€** 6 tope stereo code course for CW speed building from 13 wpm to 22 wpm+.

**EXTRA THEORY CLASS** 4 tope stereo theory plus fully illustrated theory book.

GORDON WEST ELECTRONICS BOOK

200 page marine electronics book plus \$19.95 marine mobile antenna hints. \$29.95 COMMERCIAL TEST PREP BOOK \$19.95 BRASS CODE KEY & OSCILLATOR \$14.95 PLASTIC CODE KEY & OSCILLATOR 60¢ FOOT COPPER GROUND FOIL

#### SINGLE CODE TAPES \$9.95 EACH . BUY 2 GET 3rd ONE FREE

• 5 wpm Novice Tests • 5 wpm Random Code

5-7 Speed Build
 7-10 Speed Build
 10 Hump Jump

\* 10-12 Speed Build \* 12-15 Calls & Numbers 13 Random
 13 Test Prep
 5-15 General Quiz

13 Car Code13-15 Speed Build15-17 Speed Build

• 17-19 Speed Build • 20 Random • 20 Test Prep

20 Car Code
 10-24 Extra Quiz

Shipping: Please Add \$3.00 Each For Courses. \$1.00 Each For Single Tapes.

Please Direct All Orders And Inquiries To The New Publishers:

RADIO AMATEUR CALLBOOK INC. 925 SHERWOOD DR., BOX 247 LAKE BLUFF, IL 60044 USA Mon-Fri 8-4 PM (312) 234-6600

**CIRCLE 273 ON READER SERVICE CARD** 

#### National Tower Company

P.O.Box 15417 Shawnee Mission, KS. 66215

Hours 8:30-5:00 M-F Price Subject to Change Without Notice

**EACH BX SERIES TOWER** 

#### FREE BASE STUBS WITH

25G	10° section	\$59.50
25AG2 & 3	model 2 or 3 top section	
25AG4	model 4 top section	Contraction of the last time
45G	10' section	THE PERSON NAMED IN
45AG3 & 4	model 3 or 4 top section	
55G	10' section	THE RESIDENCE
M200	10' mast, 2"o.d.	
BX-40	40'self supporting [6 sq.ft.]	\$215 SD
BX-48	48'self supporting [6 sq.ft.]	2074 ED
BX-56	56'self supporting [6 sq.ft.]	eaca sa
BX-64	64'self supporting [6 sq.ft.]	CATA EA
HBX-40	40'self supporting [10 sq.ft.]	
HBX-48	48'self supporting 10 sq.ft.	#220 DD
HBX-56	56'self supporting [10 sq.ft.]	6422 00
HDBX-40	40 self supporting 18 sq.ft.	2040 00
HDBX-48	48'self supporting 18 sq.ft.	# 400 FB
THURN TO	* GUY WIRE SPECIAL *	- Medon
3/16EHS	500° galvanized 7 strand	\$40.00
1/4FHS	500' galvanized 7 strand	<b>#FO 00</b>

HYGAIN/TELEX ANTENNAS HF ANTENNAS Tribands 3 element 'Junior Thunderbird' TH3JRS \$221.00 \$510.00 5 element 'Thunderbird'..... TH5MK2S 2 element 'Thunderbird'..... TH2MK3S

\$202.00 7 element "Thunderbird"..... \$537.00 TH7DXS Explorer 14 triband beam..... \$365.00 EXP 14 30/40 M conv. Exp 14.....\$91.00 QK710 Monoband 103BAS 'Long John' 3 element 10 mtr .... \$78.00 105BAS 'Long John' 5 element 10 mtr...... 155BAS 'long John' 5 element 15 mtr..... \$265.00 204BAS 4 element, 20 meter \$408.00 205BAS "Long John" 5 element 20 mtr..... 'Discoverer' rotary dipole 30/40mtr., \$150.00 7-15 'Discoverer' 2 elem. 40 meter beam. \$420.00 7-25 converts 7-2S to 3 elem. beam..... 7-35 **Multiband Verticals** 'Hy-Tower' 10 thru 80 meters \$502.00 18HTS

18VS trap vertical 10 thru 20 meters..... \$49.00 12AVQS trap vertical 10 thru 40 meters \$84.00 14AVQ/WBS trap vertical 10 thru 80 meters \$123.00 18AVT/WBS **Multiband Doublets** portable tape dipole 10-80 meters .... \$139.00 18TD trap doublet 40 and 80 meters..... \$59.00 2BDQS trap doublet 10 thru 80 meters..... \$109.00 5BDQS Beams & Verticals VHF ANTENNAS \$29.00 2 meter 3 element beam.....

base loaded, 10 thru 80 meters..... \$39.00

2 meter 5 element beam. \$33.00 25BS 28BS 2 meter 8 element beam..... 2 meter 14 element beam..... 214BS 6485 4 element 6 meter beam. colinear gain vertical 138-174 MHz. \$56.00 V-2S colinear gain vertical 220 MHz...... \$49.00 V-35 colinear gain vertical 430-470 MHz. \$67.00 V-45 base, 2 mtr. ground plane 3 dB..... \$24.00 **GPG2A** 

VHF & UHF Mobiles figerglass 2 mtr, 6dB gain 3/8-24 mt \$69.00 HR144GRI HB144GRI HyBander 2mtr 6dB gain 3/8-24 mt. \$49.00 HyBander 2 meter \$24.00 HB144MAG ferrite balum for 10-80 meters...... \$23.00 OSCAR LINK ANTENNA 70cm, 435 MHz. 2158

Complete Oscar link system \$256.00 2185 CUSHCRAFT ANTENNAS complete Oscar Link system \$169.00 ADP-1 8band 1/4 wave vertical \$152.00

3 element triband beam \$246.00 7 & 10 MHz add on kit for A3 ..... \$81.00 A743 7 & 10 MHz add on kit for A4 ..... \$81.00 A744 18 element 2 mtr. 28.8' boomer .... \$125.00 4218XL 10,12,15,20 meter vertical \$204.50 4 element triband beam \$344.00 80-10 mtr. vertical \$111.00 AV5 2 mtr\_ 'Ringo Ranger' ..... \$39.25 ARX2B 450 MHz. Ringo Ranger \$39.25 ARX450B 144 MHz. 11 ele. VHF ...... \$50.50 A144-11 \$50.50 11 element 146-148 MHz, beam .... A147-11 22 element 'Power Packer' \$141.75 A147-22 10 element 2 mtr. 'Oscar' \$54.00 A144-10T 20 element 2 mtr. 'Oscar' A144-20T 15 element 2 mtr. 'Boomer' ...... 215WB 220B 230WB 32-19 424B

17 element FM 'Boomer' ...... \$101.25 144-148MHz, 30 element........\$216.00 19 element 2 mtr. 'Boomer' ...... \$101.25 24 element 'Boomer' \$81.00 4 element 10 mtr. 'Skywalker' ..... \$124.75 10-4CD 4 element 15 mtr. 'Skywalker' ..... \$145.00 4 element 14 MHz 'Skywalker' .... \$310.50 15-4CD 20-4CD **HUSTLER ANTENNAS** 40-10 mtr. vertical \$79.00 4BTV 80-10 mtr. vertical \$105.00 5BTV 6 band trap vertical \$124.00 **6BTV** 

ROTORS HD73 [10.7 sq.ft.] \$104.00 Alliance \$47.00 Alliance AR40 TV, 3 sq ft..... TELEX CD45-II [8.5 sq.ft.] CALL TELEX HAM IV [15 sq It.] GALL TELEX T2X [20 sq. ft.] TELEX CABLE [2-18 & 6-22] 4080 - per foot ..... 4090 - per foot 2-16 & 6-20] \$0.17 RG8U Mini 8 low loss foam per foot \$31.00 RG8U Columbia superflex 100 1198 RG8U Low loss 100% bended foil shield 1180 88% tin copper braided shelld -per foot

## BC100XLT

\$199.90 100 Ch 11 band, with aircraft, 10 priority channels, lockout, scan delay, auto search, track tuning, direct Ch access. w/AC adapter, carry case & ear phone.





weather search, AC/DC \$114.90 BC55XLT 10 Ch 10 Band hand held. 200 Ch 12 band hand held 800 MHz \$269.90 BC200XLT \$149.90 16 Ch 11 band aircraft AC/DC BC175XL 40 Ch 11 band aircraft & weather \$179.90 BC210XLT 40 Ch 12 band aircraft & 800 MHz \$239.90 **BCBOOXLT** \$99.90 16 Ch 10 band mobile weather BC560XLT 100 Ch 11 band mobile weather \$189.90 BC580XLT \$279.90 100 Ch 12 band aircraft & 800 MHz BC760XLT



60 Channel 8 band, w/aircraft, programmable, 60 preprogrammed Channels, search or scan, alarm clock, priority, permanent backup, ch lockout, scan delay, AC/DC with both cords.

R1070 . . . . . . . . . . . \$79.90 10 Ch 6 band, programmable. permanent memory backup, dual step control, AC only.



AC powered Turbo Scan\* , preprogrammed by state to receive any type of police transmission plus fire & weather, scans at 50 channels per second, digital display, instant weather

INF1 ..... \$119.90 Pre-programmed mobile, receives 50 states police, plus instant level digital display. Ch lockout, weather, scans 40 channels per second, DC

\$39.00

\$50.00


10 meter transceiver, 25 watt can be programmed to split transceive, SSB, CW, AM, FM, programamble scanning, fully automatic noise blanker, 21/2H, 73/4W, 11D.

AR3500 ... \$299.90



25 WATT 10 Meter Transceiver. all mode operation, backlit multi function LCD meter, frequency lock, auto squelch, NB, RF gain, PA, external speaker jack, 71/4 Wx91/4 Dx21/2H.

HR2510 \$249.90

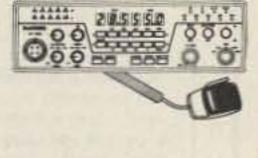



MAXON....\$26.95 Model 49SA - 49 MHz, FM 2-WAY RADIO hands free operation, voice activated transmit up to 1/2 mile Batteries optional

model 498 ..... \$34.95 same features as 49SA except uses "AA" nicad batteries and comes with battery charger

#### TENNA PHASE III POWER SUPPLIES

Fully regulated, 13.8 VDC - 4 amps constant with surge protection, overload protection w/instant auto reset. 




surge capacity: Fully regulated, 10 amp constant 13 amp surge, electronic overload protection w/instant auto reset.

Fully regulated, 25 amp surge capacity, 13.8 VDC, 17 amp constant

Regulated 4.5-15VDC-25 Amp constant 27 amp surge, instant auto reset, dual meter for current & voltage. 

from 10 to 15 volts Fully regulated 50 amp. adjustable voltage 11-15VDC, dual metering. short circuit protection, multiple binding posts (4), carry handles

**CIRCLE 323 ON READER SERVICE CARD** 

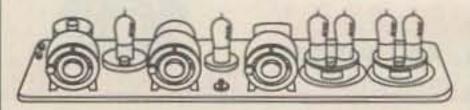

IF YOU BUY, SELL OR COLLECT OLD RADIOS, YOU NEED ...

Antique Radio's Largest-Circulation Monthly Magazine

Articles - Classifieds - Ads for Parts & Services Also: Early TV, Ham Equip., Books, Telegraph, 40's & 50's Radios & more...

Free 20-word ad each month. Don't miss out! Free Sample. 6-Month Trial - \$11. 1-Year: \$19 (\$28 by 1st Class). Foreign - Write.

A.R.C., P.O. Box 2-E4, Carlisle, MA 01741

CIRCLE 271 ON READER SERVICE CARD



CIRCLE 89 ON READER SERVICE CARD

#### THIS MONTH'S GOODIE FROM THE CANDY STORE: KENWOOD TM-221A



\$399.00 (January ONLY)

O

R


E

SIMILAR SAVINGS ON KENWOOD, ICOM, YAESU, HY-GAIN, ETC. ALL L.T.O. KENWOOD MC-60A \$107.90 OVER 8788 HAM RELATED ITEMS IN STOCK, ALL PRICES CASH FOR PRESTON

> More specials in HAM-ADS LOOKING FOR SOMETHING NOT LISTED? CALL OR WRITE

ROSS DISTRIBUTING COMPANY (P.O. Box 2340) 78 South State Street, Preston, Idaho 83263 Telephone (208) 852-0830. We Close at 2:00pm MONDAYS & ALL DAY SATURDAY.

CIRCLE 254 ON READER SERVICE CARD

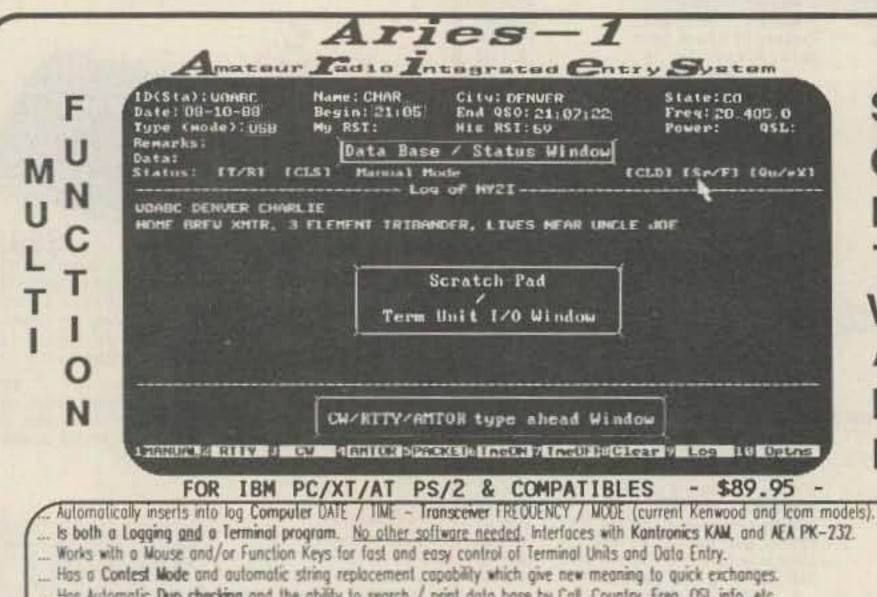

... Has Automatic Dup checking and the ability to search / print data base by Call, Country, Freq. OSL info, etc.

... Lets you run other programs (or access DOS) while staying resident in memory along with your data.

... Allows, logging while simultaneously connected to a packet mail box and down-loading messages into a capture file. An Extremely useful program! Most Aries-1 Users "fire up" the program whenever they are in the shack. Whether operating Voice AMTOR, Packet or any other mode, you will enjoy having your log available on screen simultaneously with your Terminal Unit and access to your other ham software just a keypress away.

- - Our 10th Year of delivering Quality Software to the International market - -

MasterCard



PO Box 1067 - Vestal, NY 13851 - (607-748-9028)

CIRCLE 338 ON READER SERVICE CARD

#### SUPER PERFORMANCE BATTERIES

#### SUPER KENWOOD



#### BY POPULAR REQUEST

SUPER KENWOOD PB-25S/PB-26S. 8.4 volts, 900ma, double the capacity of the PB-25/PB-26 for the 2500/2600/3500/3600. Charge with either the standard wall charger or drop in charger. 3 inches high. \$65.00\*

Exact replacement FNB-2 Nicad pack for Yaesu FT-404R/207R/208R/708R \$27.00\*

\*Add \$4.00 shipping & handling, CT residents add 71/2% tax.

#### SUPER ICOM


SUPER ICOM BP-78.13.2 volts, 900ma, double the capacity of the Icom BP-7, 5w output.

SUPER ICOM BP-8S, 9.6 volts, 1200ma, 50% more capacity than the Icom BP-8.

Both are rapid base charge only, or slide in wall charger. 4 inches high. BP-7S or BP-8S \$69.00\*

Inserts for:

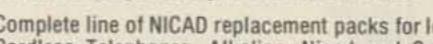Kenwood PB-25, 25H, 26 \$29.00\* Icom BP-3 \$22.00\* (com BP-5 (500ma) \$30.00\* Icom BP-7 (500ma) \$35.00\* Icom BP-8 \$34.00\*



Complete line of NICAD replacement packs for Icom, Kenwood, Yaesu, Tempo, Santec, Azden, Cordless Telephones, Alkaline, Nicad and Gell-Cells. All NICAD packs include a 1 year guarantee. Commercial Radio Packs also available.

For all your battery needs, write or call today for a complete catalog. Dealer inquiries invited.







#### PACKET TNC INTERFACE PROGRAM (\$34.95) TNCLINK-64/128 provides a menu-driven

PACKET RADIO SOFTWARE

FOR COMMODORE 64 / 128 COMPUTERS

operating environment for Packet Radio operation of any TNC requiring external software. FAST Machine Language program is more than a terminal emulator. Features include:

- Computer data transfer rates of up to 1200 baud
- User defined split-screen size and colors
- Complete Disk and printer support
- Operating setups can be saved on disk
- Ten 256-character message buffers
- 8192 character receive and transmit buffers

#### PACKET NETWORK MAPPING PROGRAM (\$29.95)

PATHFINDER-64/128 monitors a Packet frequency and forms a table of all active paths between stations heard. Up to 128 calls are stored in a table which can be saved on disk. This allows you to quickly find the best paths to use for accessing stations. Features include:

- Find all stations and digipeaters available to you
- · Find one or two digipeater paths between stations
- Highlight stations used as digipeaters
- · Print lists of calls, paths, or digipeaters

#### PC VERSION NOW AVAILABLE

Terms: To order send check or Money Order. Money back guarantee. Mass, residents add 5% sales tax. Add \$2.50 shipping per order.

> ZELTWANGER ELECTRONICS P.O. BOX 4995 NATICK, MA 01760

> > CIRCLE 351 ON READER SERVICE CARD

#### **NEW ONLINE CALL DIRECTORY**

Our new HAMCALL service gives you 494,114+ Hams, via your computer. \$29.95 per year — unlimited use!

#### **BUCKMASTER PUBLISHING**

Mineral, Virginia 23117

703: 894-5777 800: 282-5628

CIRCLE 156 ON READER SERVICE CARD

#### HI-PERFORMANCE DIPOLES-

Antennas that work! Custom assembled to your center Iring inal band ladvise ht, of center and each end hang as inverted "V" horizontal, vert dipole, sloping dipole - commercial quality - stainless hardware - legal power - no-trap, high-efficiency design. Personal check, MO or C.O.D. (\$3) 80-40-20-15-10M max-performance dipole 87' long 80-40M max-performance dipole, 85' long \$62 95'-\$66 ppd HPD-31 160-80-40M hi-performance dipole 113' long \$79 ppd 160-80-40-20-15-10M space saver dipole 71' long. 55D-6" \$125 ppd 40-40-20-15-10M space-saver dipole-specify L. 42' \$105 . 52' \$108 ppd SSD-5" SSD-4" "9-bands with wide-matching-range tuner.

SASE for catalogue of 30 dipoles, slopers, and space-saving, unique amannas 312-394-3414 BOX 393 MT. PROSPECT, IL 60056

CIRCLE 38 ON READER SERVICE CARD

#### KENWOOD DICOM YAESU

We want to be Your Radio Store Full Line of Amateur Radio and Computer Interfacing

& Accessories. - Tim W7IQY or Preben K7KMZ

(801) 467-8873

1057 E. 2100 So. Salt Lake City, Utah 84106

**CIRCLE 343 ON READER SERVICE CARD** 

#### Half-Square QRV-DX Monobanders

Work DX with No Tower and No Amplifier. Cut noise, cut near sigs, build DX sigs, kill QRM.

10 Meters 15 Meters 20 Meters 40 Meters \$29.95 \$39.95 \$49.95 \$69.95 Coax Feed, Broadside Pattern, Low Profile, Ready to Use

Highest DX Gain per Dollar To order add \$5 Postage & Handling

-Antennas West by 1st class mail. Box 50062-S, Provo, UT 84605 (801) 373-8425

CIRCLE 90 ON READER SERVICE CARD

## CHEAP AND DIRTY OSCILLATOR

#### An audio frequency source for pennies

by Dave Marling VE1VQ

A s long as it still works like the experimenter would want it to, simple is always best! Take electronics test equipment. Why build a complicated piece of test gear when a simple one will do the same job? This project costs less, is easier to put together, and less likely to fail.

The audio oscillator in this article serves to illustrate this point. It couldn't get much simpler. Don't forget that the output is far from being a sine or square wave. This project is simple and functional, not laboratory grade.

#### Circuit Operation

When switch S1 is closed, voltage is connected to the circuit through the diode CR1. Resistors R1 and R2 act as a voltage divider initially holding the base of transistor Q1 (PNP) and the collector of Q2 (NPN) to 6 volts. Capacitor C2 begins to charge through R3. When the voltage across C2 reaches about 6.7 volts, Q1 turns on. This forces the base of Q2 high, turning on Q2. The emitter of the second transistor goes high and since the output is taken from across R5 this also goes high. When Q2 switches on, the output resistor R5 is effectively placed across the PNP base resistor R2 to ground.

Now Q1 base voltage drops from 6 to about 3.6 volts turning on Q1 even harder. C2 starts to discharge through R4 until the voltage across the capacitor is less than the 0.7-volt difference required across the base-emitter junction needed to keep the transistor turned on. Q1 turns off. Q2 turns off. The output

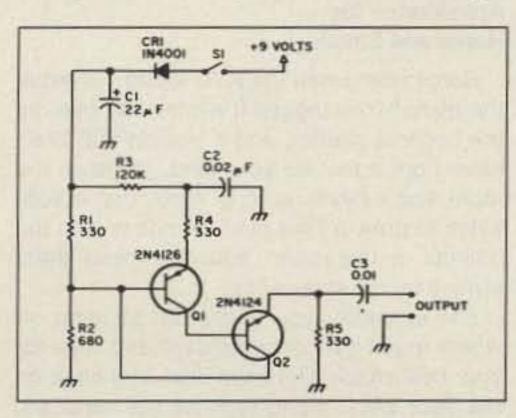


Figure 1. Resistors are 1/4 watt.

goes low. Q1 base voltage returns to 6 volts and the whole thing starts again. Eureka—an oscillator!

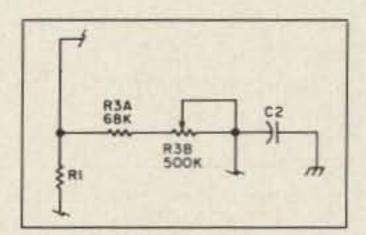


Figure 2. A  $500k\Omega$  volume control with a switch can replace S1 and R3.

The transistors are not critical. PNP and NPN types with fiT's of between 200 MHz and 1.1 GHz, plastic low power, metal signal, RF power output, and even a couple of unmarked TO-3's were tried, and all worked fine with very little difference in the frequency.

Two components do affect the frequency.

Make R3 smaller and frequency goes up.

Make C2 larger and it goes down.

Voltage is another non-critical. Varying the supply voltage from 4.5 to 15 volts changed the frequency somewhat but oscillator start-up occured every time power was switched off and on.

If money is no object, make this thing variable by changing the value of R3 to  $68k\Omega$  and adding a  $500k\Omega$  potentiometer in series.

As mentioned before, the output has a definite lack of purity. The waveform is actually a spike with a repetition rate of about a thousand hertz. If the experimenter views the output on an oscilloscope he will see all kinds of fuzz and garbage along with the original one kilohertz pulse.

#### Uses

In the bygone days of ham radio when the experimenter used to fix his own stuff instead of shipping it back to the importer, one of the more indispensable pieces of test gear was the signal injector. Starting at the speaker in a receiver or audio amplifier and working backward along the signal path with the injector, the defective stage was found when the signal disappeared.

All of that garbage from the oscillator actually has some use. While checking the audio stages, the 1000 Hz comes through. Once into the IF and RF sections the fuzz shows its true stuff. The oscillator has usable output out beyond 30 MHz.

I run a burglar alarm business. One of the things that makes the alarms ring in the night is the four-wire cable that runs from each of the many sensors to the alarm panel. Things go fine until a couple dozen of these come through a hole in the back of the panel and the ID tags have fallen off half of them. What to do? Connect the output of the oscillator to two of the four wires in one of the lines at the far end of the run. Back at the panel I check out the unknowns by listening to each in turn with a small battery powered audio amp.

How about a code practice oscillator? Simply connect a key in series between the output capacitor C3 and an audio amp and pound away.

Simple test equipment-simple to build, simple to get working and simple to use with all kinds of uses. That's the best kind!

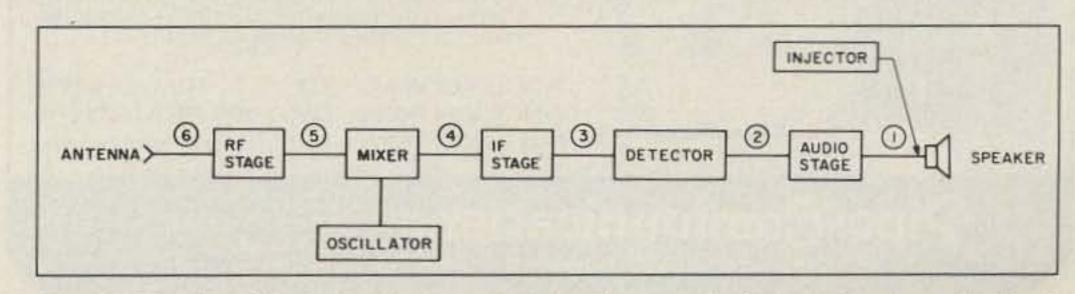


Figure 3. Move the oscillator output from test point 1 through to test point 6. Output from the speaker should increase as the experimenter gets closer to the antenna connector, because of the gain in each stage.

## 73 Review by W.S. Gardiner VE6BGL

## AutoSketch and **Amateur Radio**

Inexpensive CAD program for both shack and home.

AutoDesk Inc. 2320 Marinship Way Sausalito CA 94965 415-332-2344 Price Class: \$80

ast April, I bit the bullet and went shopping for a new computer because the old one was, well, old! I snuck the new beast through the door with the usual ham stories: it'll be great for word processing, the kids will use it, computer literacy is important, etc. The XYL had probably figured out that the new computer would soon be spewing out RTTY or Morse dit-dah beeps! I gave the old computer to the kids, and they and the neighbors' kids are now happily shooting Martian invaders.

Software was next. The local BBS system had a bunch, and I soon became interested in graphics programs for drawing circuit boards. However, the BBS software couldn't do the job. The commercial stuff could do the job, and had features galore, such as auto-routing, sixteen-layer handling, pretty colors; all explained by manuals as thick as phone books. These programs, however, would put a dent in anybody's wallet.

#### Little Brother Does the Job

Onto the scene creeps AutoSketch. This is the low-buck brother of AutoCAD the industry standard. AutoCAD costs-well, let's say it's not in my budget, while the list price of Auto-Sketch is affordable at under \$100. It doesn't have all the features of AutoCAD, but does a noble job just the same!

So far, I have used it for the chassis layout, a circuit board design, some furniture arranging, and guy wire calculations. Chassis layout is particularly neat. (See Figure 1.) After you draw a box layout like this one, you can use the AutoSketch STRETCH feature to make the

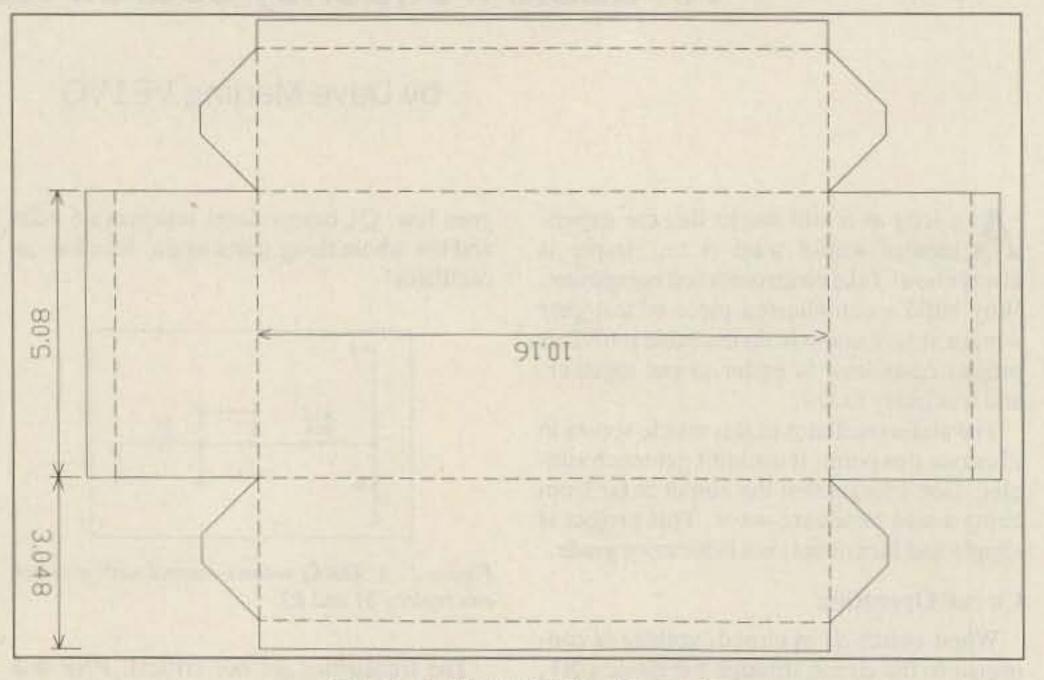


Figure 1. AutoSketch drawing of a chassis.

box longer or wider. The dimensions are automatically recalculated! You can also change the size of the box by scaling it up and down when you plot it on the printer. With enough computer paper on hand, it would be possible to lay out a full-size floor plan of the Queen Mary, paste the strips together, and start building from your plans.

#### **Commanding Designs**

Circuit board layout is easy with Auto-

**FMF/steel keys!** 

sealed gold contacts!


Sketch. Until now, I drew all my layouts on 0.1" graph paper and transferred the finished design onto copper. This meant a lot of timeconsuming erasing. AutoSketch has a GRID feature you can set to 0.1" x 0.1". A series of dots appear exactly 0.1" apart. MOVE, COPY, and MIRROR commands make drawing a 14-pin DIP socket a breeze. I drew one pad, used COPY to copy it seven times, then GROUP so the computer would treat it as a unit, and MIRROR to create a finished PART. (See Figure 2.)

Once you have created a PART, you can add it to other drawings, or move, copy, or modify it. You can create a PART library for frequent use. Just pull them up from the menu, put them in position, and keep going! Talk about fast!
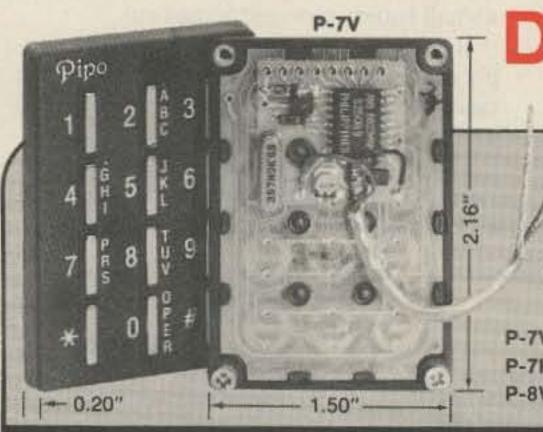
#### AutoSketch for Home and Shack

Remember when the XYL wanted to move the piano? You lugged it all the way over by the begonia planter, and it wouldn't fit! Well, have I got a tool for you. First, measure the room and everything in it. Next, use AutoSketch to draw a floor plan, complete with the objects in the room. You can move them around on the screen first!

For example, you might be deciding on where to put the operating desk and chair for your new shack. Draw the desk and chair on the floor plan, along with all the windows, doors, closets, etc. Then you can MOVE the



 COLOR: All keyboards come in BLACK. OPTIONAL: Specify DARK BROWN \* Contacts are: WATER PROOF/DUST PROOF . Completely self contained - NO RFI \* Simple 3-wire connection \* Output level adj. . Wide operating range 4 to 16 VDC . Wide temperature range -22° to + 160°F \* Supplied with instructions, schematic, template & hardware.

P-7V 12 KEY VERT. \$53\* CALL OR WRITE P-7H 12 KEY HORIZ. \$53\* FOR FREE CATALOG P-8V 16 KEY VERT. \$57\* \*Request quantity pricing

mmunications® Emphasis is on Quality & Reliability

P.O. Box 2020 Pollock Pines, California 95726 916-644-5444 FAX-916-644-PIPO

CIRCLE 66 ON READER SERVICE CARD

Order

To:

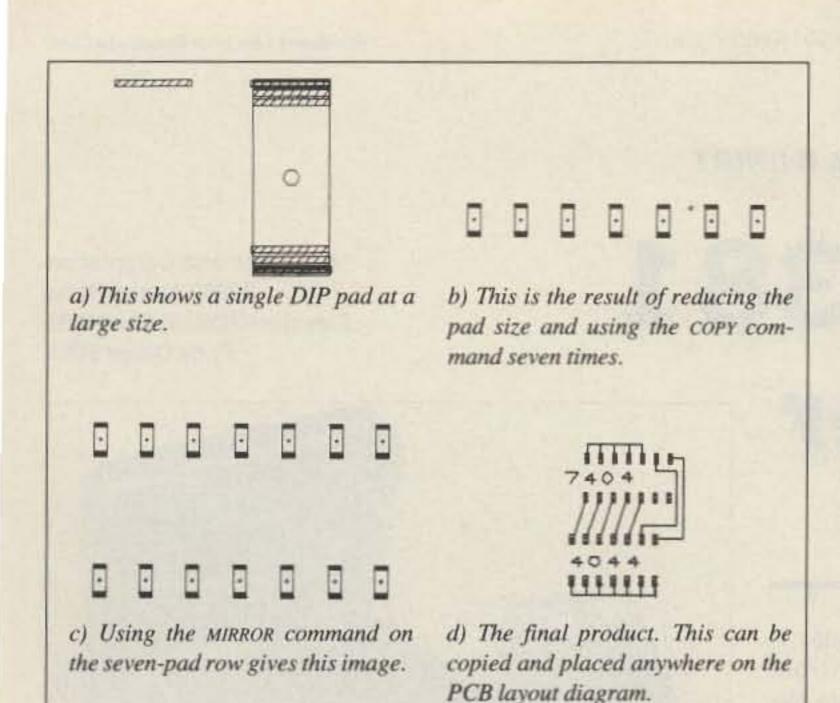


Figure 2. Using AutoSketch to draw a 14-pin DIP socket for PC board layout.

furniture around on the computer screen with ease. ROTATE lets you turn the chair or desk around to any angle, and MEASURE tells you the distance between two specified points. The ANGLE command is, of course, for angles, and AREA/PERIMETER figures out how much carpet you'll need for your dream shack!

How about guy wires for the tower outside? Again, draw a plan, move the lines around on the screen until they look OK, then use the MEASURE/ANGLE feature to do the calculations. Simple! If you make a mistake, Auto-Sketch has an UNDO command to fix up the blunders.

#### The Computer and Printer

A couple of hints: Leave about 100K workspace on your disk to allow the program to store data. If the program suddenly stops printing, the disk is probably full. My copy of

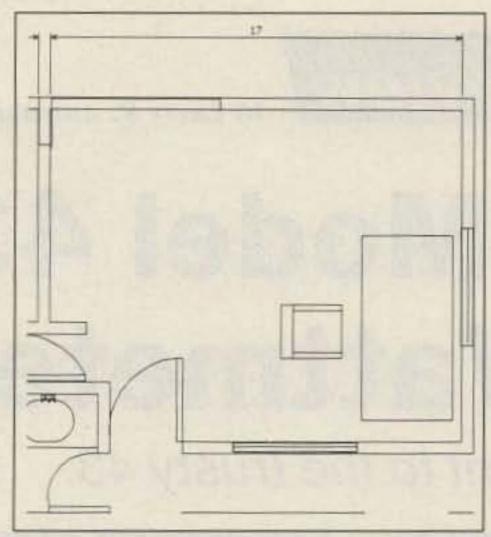


Figure 3. Room layout. AutoSketch can reposition components in the room, such as the desk and chair (lower right).

AutoSketch has a read-me file with instructions for using dot matrix printers, which I should have read first!

You can print big drawings in sections and tape them together. Remember that a box of computer paper is 8-1/2" wide by several hundred feet long. You could draw a fullsize wall section of the new house!

To use AutoSketch you will need an IBM compatible computer (512K minimum) with two 51/4" disk drives.

and a Hercules, EGA or CGA monitor. I recommend a mouse, but you may use keyboard control. You'll also need a plotter or dot-matrix printer. I use an Epson FX86e. The program is very fussy about what it talks to, and if you aren't sure that your printer is compatible, take it with you to the computer store and try it out before buying.

A final word to my drafting teacher way back in Grade 10, who never liked my arrowheads, who said I never could center a drawing, who despised my lettering . . . Hah! 73



#### YOUR HAM DOLLAR GOES FURTHER AT...

CALL OR WRITE FOR SPECIAL QUOTE

When it comes to FAST DELIVERY, HONEST DEALING and PROMPT/DEPENDABLE S.E.R.V.I-C.E back-up We don't just advertise it - WE GIVE IT!

we'll treat you

SELECTION

S.E.R.V.I.C.E

SATISFACTION!

In 1937, Stan Burghardt (WØIT), because of his intense interest in amateur radio, began selling and servicing amateur radio equipment in conjunction with his radio parts business. We stand proud of this long-lasting tradition of Honest Dealing, Quality Products and Dependable "S-E-R-V-I-C-E"!

Above all, we fully intend to carry on this proud tradition with even more new product lines plus the same "fair" treatment you've come to rely on. Our reconditioned equipment is of the finest quality with 30, 60 and even 90-day parts and labor warranties on selected pieces. And always remember:

#### — WE SERVICE WHAT WE SELL —

AEA	Belden	Icom	Nye
Alinco	Bencher	Jerold/Delhi	Palomar
Ameritron	Bird	Kantronics	Radio Callbook
Amphenol	Butternut	KDK/Encomm	Rohn
Amp Supply	Centurion	KLM	Telex/Hygain
Antenna	CES	Larsen	Ten-Tec
Specialists	Cushcraft	MFJ	Trio-Kenwood
Astron	Daiwa	Mirage	Unadilla/Reyco
B&W	Hustler	Moseley	Yaesu

Write today for our latest Bulletin/Used Equipment List.



#### SELL-TRADE

**New & Reconditioned** 

HAM EQUIPMENT

Call or Write Us Today For a Quote! You'll Find Us to be Courteous, Knowledgeable and Honest

> PHONE (605) 886-7314 FAX (605) 886-3444





182 N. Maple P.O. Box 73 Watertown, SD 57201



CALL TODAY FOR SPECIAL QUOTE

CIRCLE 92 ON READER SERVICE CARD

### 73 Review

by Larry R. Antonuk WB9RRT

## Bird Model 4381 RF Wattmeter

Complement to the trusty 43.

nyone who has worked his way up through the two-way radio business is intimately familiar with the Bird Model 43 Thruline® Wattmeter. The "Bird" is found next to every toolbox, on every bench, in permanent installations, and anywhere where there's RF. Have lunch with a few old-timers in the land mobile industry, and you're bound to hear stories about the time "the Bird fell from the seventy-foot mark on the tower and survived," or how "when I started out in this business, I had nothing but a box of fuses, a tube caddy, and a Bird." Tough, portable, and accurate . . . "take my wife, take my car, but keep your hands off my Thruline"...the Bird would never let you down.

#### **New Bird Model 4381**

Progress, of course, did not stop with wattmeters. The Bird Model 4381 Thruline wattmeter is one of the latest high-tech additions to the Bird line; the new kid on the block. Boasting a dazzling array of bells and whistles, the 4381 is quite a contender. (It needs to be, considering how firmly entrenched the incumbent is!)

The Model 4381 is the next logical step in the Bird line. It makes use of a similar 50Ω line section, with the same "Quick-Change" connectors, and the same power sensing elements. In a move totally contrary to industry trends, Bird designed a new product that uses the same "slugs" that we've been using in the Model 43 for years. This means that the 4381 can make use of existing inventories of elements, which keeps the cost lower and ensures compatibility with all the other Birds (and Bird clones) in the shop.

The 4381 uses two "slugs" at once—one at a given power level to sense forward power, and a second at one-tenth of the power level of the first to sense reflected power. The ten-to-one ratio provides higher resolution when sensing reflected power, and allows the unit to provide instantaneous SWR readings, or forward or reverse power, at the touch of a button. If the convenience of one-touch readings is not necessary, it's perfectly OK to use only one element, and manually reverse it to read reflected power.

#### Past the RF Sensor

Once past the RF-sensing portion, all simi-

larities cease. The 4381 is housed in a slant-front table-top case, the two elements fit near the top, the digital read-out is in the middle, and the multi-function keypad is near the bottom.

The keypad selects the current operating mode of the device. Hit the FWD CW

button, and you're reading the continuous wave power going in the forward direction—forward being the direction that the arrow on the element in the forward socket is pointing. All in all, the unit will read CW or PEP power in watts, milliwatts, or kilowatts from 2.5 to 1000 units in the forward direction, and 0.25 to 1000 units in the reverse direction. SWR can be directly read from 1.00 to 99.99, modulation percentage from 0.0 to 99.9, and return loss over the range of 0 to 36.1 dB. For convenience, you can display forward and reflected power as dBm. As a bonus, the 4381 provides two types of useful over-range features.

To begin with, you can read each element up to 120% of its stated range. In other words, the 100 watt slug can now read up to 120 watts, and with higher accuracy, than switching to the next higher element and reading it on the low end of the scale. Furthermore, when used with the dBm mode, sensing elements can be over-ranged by 6 dB (or 400%). This means that you can actually measure up to 400 watts with the 100 watt slug if you're willing to convert from dBm to watts yourself!

The digital read-out will probably be seen as both a blessing and a curse. On the one hand, if the radio is supposed to put out fifty watts, there's no question that 49.8 is pretty close, but it's not fifty watts regardless of how crosseyed you look at the display. On the other hand, some techs might spend the whole afternoon getting a radio from 50.0 to 50.2 watts—yes, it is higher, but so what? The bottom line concerns the actual accuracy of the unit.

#### Accuracy

As we should all know by now, accuracy is a function of the sensing device, and not simply the number of decimal places in the display. In this case, since the elements are the same as those on the good of Bird, the power accuracy

Bird Electronic Corporation 30303 Aurora Road Cleveland (Solon) OH 44139 Price Class: \$695



is the same as the good of Bird: +/-5% full scale. (Using the two-element, ten-to-one ratio system, the reflected element, being closer to the value of the reflected power, will provide higher resolution and more accurate SWR readings than would be obtained by simply reversing the high-power element to read reflected power.) The display uses a "greater than/less than" symbol in place of the last digit to indicate increasing or decreasing levels. Used in conjunction with a MIN/MAX level memory, the "delta" function makes transmitter tuning a snap. (A snap, perhaps, but still not quite as comforting as watching that needle swing back and forth...)

The 4381 runs on NiCd batteries. One charge is good for about eight hours. This makes it portable, of course, but the unit is obviously meant to spend its life sitting on a bench. The digital display is certainly more shock-proof than the Model 43's meter movement. Lacking any sort of a handle, however, the 4381 will probably not find its way up too many seventy-foot towers. The higher price tag will probably ensure that the unit stays in the shack—or at least carefully guarded during Field Day.

#### Versatile and Compatible

After all the dust has settled, the contest ends in a draw. The 4381 performs many functions not available with the standard line of wattmeters—it measures SWR, peak power, and greater over-range. Due to its capabilities and size, the 4381 will find greater use on the test bench, in a production facility, or in a base station. Due to its portability and lower cost, the 43 (and the 43 series) will continue to be used in the field and in situations where economics play a greater role. Rather than the newcomer ousting the old-timer, Bird has provided us with a competent and experienced father and son team.

## Tandy National Parts

Supplying parts and service information for Radio Shack/Tandy products for more than 20 years. Over 75,000 parts in stock for antennas, meters, radios and many other consumer electronic products.

CRYSTALS - ICs - CABLES - CORDS - MANY OTHER COMPONENTS
AVAILABLE OFF-THE-SHELF

Discounts are available for service centers, OEMs, schools, qualified agencies with a tax-exempt number, and large-volume purchases!

#### **COMPARE OUR PRICES!**

- Standard and Specialty Components
- **International Sources**
- 24 Toll-Free WATS Lines

- Overnight Delivery Upon Request
- Quality Guaranteed
- 130,000 Sq. Feet of Warehouse Space

To Order, Call Toll Free 1-800-442-2425

We accept most major credit cards \$3.50 minimum parts order 900 E. North Side Drive, Fort Worth, Texas 76102 (817) 870-5600

#### Tandy National Parts

A DIVISION OF TANDY ELECTRONICS

## Tandy Consumer Parts

#### Announcing a New Service

Now! One-Stop Shopping for Your Consumer Electronics Needs Get low, low prices on original replacement parts for over 40 famous-name brands. Also save on popular tools, test equipment and service literature.

THIS MONTH'S SPECIALS	Mfr's Price	Our Price
■ Astron RS-20A Power Supply	121.95	87.00
■ Astron RS-20M Power Supply	144.95	107.00
■ Astron VS-20M Power Supply	170.95	126.00
■ B&K 388-HD Test Bench	139.00	118.00
■ B&K 1851 520 MHz Frequency Counter	641.00	545.00
■ Leader LBO-2060 60 MHz Digital Display Scope	1525.00	1296.00

Tandy Consumer Parts

A DIVISION OF TANDY ELECTRONICS

To Order, Call Toll-Free 1-800-243-1311

7439 Airport Freeway, Fort Worth, Texas 76039 (817) 284-8691

## uniden \$12,000,000 Scanner Sale

Uniden Corporation of America has purchased the consumer products line of Regency Electronics Inc. for \$12,000,000. To celebrate this purchase, we're having our largest scanner sale in history! Use the coupon in this ad for big savings. Hurry...offer ends December 31, 1988.

#### \*\*\*MONEY SAVING COUPON\*\*\*

Get special savings on the scanners

C

OUPON

listed in this coupon. This coupon must be included with your prepaid order. Credit cards, personal checks and quantity discounts are excluded from this UPO offer. Offer valid only on prepaid orders mailed directly to Communications Electronics Inc., P.O. Box 1045 - Dept. UNI11, Ann Arbor, Michigan 48106-1045 U.S.A. Coupon expires December 31, 1988. Coupon may not be used in conjunction with any other offer from CEI. Coupon may be photocopied. Add \$9.00 for shipping in the continental U.S.A. Regency TS2-T .....\$259.95

Regency INF1-T .....\$119.95 Regency INF5-T.....\$79.95 Regency R1090-T.....\$114.95 Regency UC102-T .....\$109.95 Regency RH606B-T.....\$419.95 Regency RH256B-T....\$294.95 Bearcat 200XLT-T ..... \$249.95 Bearcat 100XLT-T .....\$184.95 Bearcat 800XLT-T .....\$249.95 Uniden TALKER-T ..... \$179.95

#### \*\*\*\*VALUABLE COUPON \*\*\*\*

#### NEW! Bearcat® 760XLT-T

List price \$499.95/CE price \$244.95/SPECIAL 12-Band, 100 Channel . Crystalless . AC/DC Frequency range: 29-54,118-174, 406-512, 806-956 MHz. Excludes 823.9875-849.0125 and 868.9875-894.0125 MHz. The Bearcat 760XLT has 100 programmable channels organized as five channel banks for easy use, and 12 bands of coverage including the 800 MHz. band. The Bearcat 760XLT mounts neatly under the dash and connects directly to fuse block or battery. The unit also has an AC adaptor, flip down stand and telescopic antenna for desk top use. 6-5/16" W x 1%" H x 7%" D. Model BC 590XLT-T is a similar version without the 800 MHz, band for only \$194.95. CTCSS squelch option now available.

#### SALE! Regency® TS2-T

List price \$499.95/CE price \$269.95/SPECIAL 12-Band, 75 Channel . Crystalless . AC/DC Frequency range: 29-54, 118-175, 406-512, 806-950 MHz. The Regency TS2 scanner lets you monitor Military. Space Satellites, Government, Railroad, Justice Department, State Department, Fish & Game, Immigration, Marine, Police and Fire Departments, Aeronautical AM band, Paramedics, Amateur Radio, plus thousands of other radio frequencies most scanners can't pick up. The Regency TS2 features new 40 channel per second Turbo Scan" so you wont miss any of the action. Model TS1-T is a 35 channel version of this radio without the 800 MHz. band and costs only \$199.95.

#### Regency® RH256B-T

List price \$799.95/CE price \$299.95/SPECIAL 16 Channel • 25 Watt Transceiver • Priority The Regency RH256B is a sixteen-channel VHF land mobile transceiver designed to cover any frequency between 150 to 162 MHz. Since this radio is synthesized, no expensive crystals are needed to store up to 16 frequencies without battery backup. All radios come with CTCSS tone and scanning capabilities. A monitor and night/day switch is also standard. This transceiver even has a priority function. The RH256 makes an ideal radio for any police or fire department volunteer because of its low cost and high performance. A 60 Watt VHF 150-162 MHz. version called the RH606B-T is available for \$429.95. A UHF 15 watt, 16 channel version of this radio called the RU156B-T is also available and covers 450-482 MHz. but the cost is \$454.95.

#### \*\*\* Uniden CB Radios \*\*\*

(R) The Uniden line of Citizens Band Radio transceivers is styled to compliment other mobile audio equipment. Uniden CB radios are so reliable that they have a two year limited warranty. From the feature packed PRO 810E to the 310E handheld, there is no better Citizens Band radio on the market today.

PRO310E-T Uniden 40 Ch. Portable/Mobile CB...\$83.95 PRO330E-T Uniden 40 Ch. Remote mount CB...\$104.95 PRO500D-T Uniden 40 Channel CB Mobile ...... \$38.95 NINJA-T PRO310E with rechargeable battery pack \$99.95 B10-T 1.2V AA Ni-cad battery for Ninja (set of 10)...\$20.95 KARATE-T Uniden 40 channel rescue radio ...... \$53.95 PRO510XL-T Uniden 40 channel CB Mobile. ..... \$38.95 PRO520XL-T Uniden 40 channel CB Mobile..... \$56.95 PRO540E-T Uniden 40 channel CB Mobile......\$97.95 PRO640E-T Uniden 40 channel SSB CB Mobile ... \$137.95 PRO710E-T Uniden 40 channel CB Base ...... \$119.95 PRO810E-T Uniden 40 channel SSB CB Base ... \$174.95

\* ★ ★ Uniden Radar Detectors ★ ★ ★ Buy the finest Uniden radar detectors from CEI today. TALKER-T Uniden talking radar detector......\$184.95 RD7-T Uniden visor mount radar detector ...... \$99.95 RD9-T Uniden "Passport" size radar detector ....\$114.95 RD9XL-T Uniden "micro" size radar detector ..... \$144.95 RD25-T Uniden visor mount radar detector ...... \$54.95 RD500-T Uniden visor mount radar detector..... \$74.95

Bearcat® 200XLT-T

List price \$509.95/CE price \$254.95/SPECIAL 12-Band, 200 Channel . 800 MHz. Handheld Search . Limit . Hold . Priority . Lockout Frequency range: 29-54, 118-174, 406-512, 806-956 MHz. Excludes 823.9875-849.0125 and 868.9875-894.0125 MHz The Bearcat 200XLT sets a new standard for handheld scanners in performance and dependability. This full featured unit has 200 programmable channels with 10 scanning banks and 12 band coverage. If you want a very similar model without the 800 MHz. band and 100 channels, order the BC 100XLT-T for only \$189.95. Includes antenna. carrying case with belt loop, ni-cad battery pack. AC adapter and earphone. Order your scanner now.

#### Bearcat® 800XLT-T

List price \$549.95/CE price \$259.95/SPECIAL 12-Band, 40 Channel . No-crystal scanner Priority control . Search/Scan . AC/DC Bands: 29-54, 118-174, 406-512, 806-912 MHz The Uniden 800 XLT receives 40 channels in two banks. Scans 15 channels per second. Size 9\" x 4\" x 12\"." If you do not need the 800 MHz. band, a similar model called the BC 210XLT-T is available for \$178.95.

#### Bearcat® 145XL-T

List price \$189.95/CE price \$94.95/SPECIAL 10-Band, 16 Channel . No-crystal scanner Priority control . Weather search . AC/DC Bands: 29-54, 136-174, 406-512 MHz. The Bearcat 145XL is a 16 channel, programmable scanner covering ten frequency bands. The unit features a built-in delay function that adds a three second delay on all channels to prevent missed transmissions. A mobile version called the BC560XLT-T featuring priority, weather search, channel lockout and more is available for \$94.95. CEI's package price includes

Regency® Informant™ Scanners Frequency coverage: 35-54, 136-174, 406-512 MHz. The new Regency Informant scanners cover virtually all the standard police, fire, emergency and weather frequencies. The INF1-T is ideal for truckers and is only \$129.95. For base station use, the INF5-T is \$84.95. Order your scanner today.

mobile mounting bracket and mobile power cord.

NEW! President® HR2510-T List price \$499.95/CE price \$239.95/SPECIAL 10 Meter Mobile Transceiver • Digital VFO Full Band Coverage . All-Mode Operation Backlit liquid crystal display 9 Auto Squeich RIT e Preprogrammed 10 KHz. Channels Frequency Coverage: 28.0000 MHz. to 29.6999 MHz.

The President HR2510 Mobile 10 Meter Transceiver made by Uniden, sets a new standard in amateur radio communications. Fully Featured-The HR2510 has everything that you need. Up to 25 Watt PEP USB/LSB and 25 Watt CW mode. Noise Blanker. PA mode. Digital VFO. Built-in S/RF/MOD/SWR meter. Channel switch on the microphone, and much more! The HR2510 lets you operate AM, FM, USB, LSB or CW. The digitally synthesized frequency control gives you maximum stability and you may choose either pre-programmed 10 KHz. channel steps, or use the built-in VFO for steps down to 100 Hz. There's also RIT (Receiver Incremental Tuning) to give you perfectly tuned signals. With receive scanning, you can scan 50 channels in any one of four band segments to find out where the action is. Order your HR2510 from CEI today.



BC760XLT 800 MHz. mobile scanner SPECIAL!

#### \*\*\* Facsimile Machines & Phones \*\*\* If you need an excellent facsimile machine, CEI has the

full featured Faxtel 3300 fax by Pactel at a special price. FAX3300-T Pactel Fax machine with phone .... \$1,099.95 XE750-T Uniden Cordless Phone with speaker....\$99.95

\*\*\* Extended Service Contract \*\*\* If you purchase a scanner, CB, radar detector or cordless phone from any store in the U.S. or Canada within the last 30 days, you can get up to three years of extended service contract from Warrantech. This service extension plan begins after the manufacturer's warranty expires. Warrantech will perform all necessary labor and will not charge for return shipping. Extended service contracts are not refundable and apply only to the original purchaser. A two year extended contract on a mobile or base scanner is \$29.99 and three years is \$39.99. For handheld scanners, 2 years is \$59.99 and 3 years is \$79.99. For radar detectors, two years is \$29.99. For CB radios, 2 years is \$39.99. For cordless phones, 3 years is \$34.99. Order your extended service contract today.

OTHER RADIOS AND ACCESSORIES BC55XLT-T Bearcat 10 channel scanner ......\$114.95 BC70XLT-T Bearcat 20 channel scanner......\$159.95 BC175XLT-T Bearcat 16 channel scanner ...... \$156.95 R1090-T Regency 45 channel scanner......\$119.95 UC102-T Regency VHF 2 ch. 1 Watt transceiver...\$114.95 BPS5-T Regency 16 amp reg. power supply.....\$179.95 MA549-T Drop-in charger for HX1200 & HX1500 .... \$59.95 MA518-T Wall charger for HX1500 scanner ...... \$14.95 MA553-T Carrying case for HX1500 scanner.....\$14.95 MA917-T Ni-Cad battery pack for HX1000/1200 ... \$39.95 BP205-T Ni-Cad batt, pack for BC200/BC100XLT ... \$49.95 B8-T 1.2 V AA Ni-Cad batteries (set of eight).....\$17.95 FBE-T Frequency Directory for Eastern U.S.A.....\$14.95 FBW-T Frequency Directory for Western U.S.A....\$14.95 ASD-T Air Scan Directory ......\$14.95 SRF-T Survival Radio Frequency Directory ...... \$14.95 TSG-T "Top Secret" Registry of U.S. Govt. Freq. ... \$14.95 TTC-T Tune in on telephone calls......\$14.95 CBH-T Big CB Handbook/AM/FM/Freeband......\$14.95 TIC-T Techniques for Intercepting Comm. ...... \$14.95 RRF-T Railroad frequency directory .....\$14.95 EEC-T Embassy & Espionage Communications....\$14.95 CIE-T Covert Intelligenct, Elect. Eavesdropping ...\$14.95 MFF-T Midwest Federal Frequency directory.....\$14.95 A60-T Magnet mount mobile scanner antenna....\$35.95 A70-T Base station scanner antenna ......\$35.95 A500-T 10 & 11 Meter - 500 Watt antenna ...... \$38.95 A1300-T 25 MHz.-1.3 GHz Discone antenna....\$109.95 USAMM-T Mag mount VHF ant. w/ 12' cable ..... \$39.95 USAK-T 4" hole mount VHF ant, w/ 17' cable .....\$35.95 USAK450-T%" hole mount UHF ant. w/ 17' cable. .... \$35.95 Add \$4.00 shipping for all accessories ordered at the same time. Add \$9.00 shipping per radio and \$4.00 per antenna.

#### **BUY WITH CONFIDENCE**

To get the fastest delivery from CEI of any scanner, send or phone your order directly to our Scanner Distribution Center." Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability. acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on backorder automatically unless CEI is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. CEI warehouse in Ann Arbor, Michigan. No COD's. Most items listed have a manufacturer's warranty. Free copies of warranties on these products are available by writing to CEI. Non-certified checks require bank clearance. Not responsible for typographical errors.

Mail orders to: Communications Electronics," Box 1045, Ann Arbor, Michigan 48106 U.S.A. Add \$9.00 per scanner for U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are three times continental U.S. rates. If you have a Discover, Visa, American Express or Master Card, you may call and place a credit card order. 5% surcharge for billing to American Express. Order toll-free in the U.S. Dial 800-USA-SCAN. In Canada, dial 800-221-3475. FAX anytime, dial 313-971-6000. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today. Scanner Distribution Center" and CEI logos are trademarks of Communications Electronics Inc. Sale dates 10/15/88 - 12/31/88 AD #110188-T Copyright © 1988 Communications Electronics Inc.

For credit card orders call 1-800-USA-SCAN

COMMUNICATIONS ELECTRONICS INC.

Consumer Products Division

P.O. Box 1045 Ann Arbor, Michigan 48106-1045 U.S.A.

For orders call 313-973-8888 or FAX 313-971-6000

CIRCLE 121 ON READER SERVICE CARD

# INEXPENSIVE MARKER GENERATOR

Calibrate and stay in band.

by Ron Wong WB6DFQ

A device capable of generating marker signals at precise intervals throughout the HF spectrum is a handy device to have around the shack. Amateurs can use this simple generator to calibrate receivers and identify band edges. By providing marker signals at precise intervals, the generator helps the radio amateur verify that he is operating within the prescribed band limits of his license.

The circuit shown in Figure 1 is just such a beast. It is capable of generating signals at 1 MHz, 100 kHz, 50 kHz, and 25 kHz intervals. Most of the parts for this project are inexpensive and available at any local Radio Shack store. Beginners can handle the construction of this project with good results.

#### **Circuit Description**

The oscillator section uses three sections of a 7400 quad NAND gate integrated circuit. The 1 MHz signal from the oscillator is fed into a 7490 decade counter configured to divide by ten, providing the 100 kHz signal. To obtain the 50 and 25 kHz outputs, the 100 kHz signal is further divided by a 7473 dual J-K flip-flop. The first half of the 7473 divides the 100 kHz signal by two, yielding the 50 kHz signal. The second half of the 7473 again divides by two, giving the 25 kHz signal. S-2 selects the output, a square wave rich in harmonics.

The generator may be powered from any convenient 6 to 12 DC volt source. A 7805 fixed voltage regulator supplies the regulated voltage for the oscillator and the divider chips. The generator described here is powered by a 9-volt transistor radio battery.

#### Construction

Construction of the generator is not critical. The entire unit is built on a Radio Shack multi-purpose board (276-150). This board has two bus strips at the center, and the PC pattern printed on the board is indexed to accept integrated circuits. The components mount on the board with ample room. Other construction techniques are acceptable, such as Vectorboard and flea clips. I mounted the Radio Shack board in a small 2½" x 4" x 2½" chassis box, with a small on/off toggle switch (S-1) and a rotary switch (S-2) on the front panel. On the rear panel, I used a binding post (J-1) for the output. Inside the box, I placed a Radio Shack 270-326 battery holder for mounting the battery.

#### Operation

After you build the generator, you will need to calibrate it. The easiest way to do this



Photo A. The finished project. The entire unit is housed in a chassis box purchased at a local flea market.

is to use a receiver capable of receiving WWV at 5, 10, 15, or 20 MHz.

Tune WWV and couple the output of the generator to the antenna terminal of the receiver. Turn on the generator, set S-2 to the 1 MHz position, and adjust C-1 until it zero-beats with WWV. The marker signal should be very strong. If the 1 MHz signal blocks the receiver, loosen the coupling to the antenna terminal, or go to another marker position. You should hear the marker signals well into the VHF region.

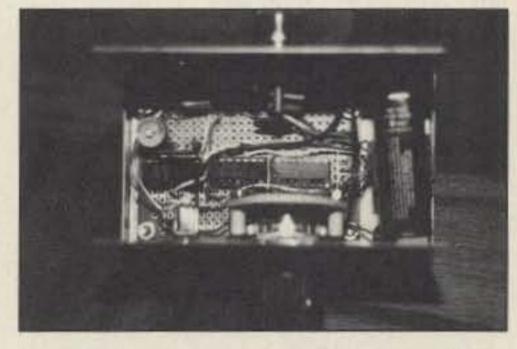


Photo B. The components are mounted on a Radio Shack multi-purpose board (276-150) and wired breadboard style.

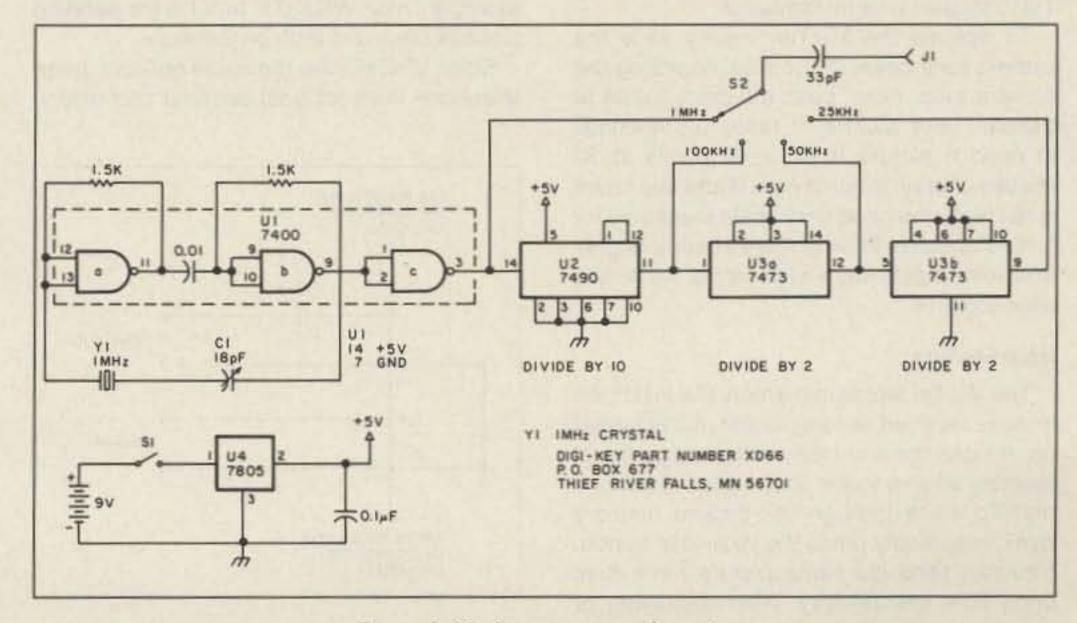


Figure 1. Marker generator schematic.

### VisiTel On-The-Air

Heath Company Hill Top Road St. Joseph, MI 49085 1-800-444-3284 Price Class: \$400


#### A visual phone display you can interface with your transceiver.

ooks like we may finally have affordable SSTV after all, and better yet, something we can share with the XYL (or OM). This is in the form of the Mitsubishi VisiTel visual telephone display system.
 
#### Here's Looking At You

The VisiTel is a complete black and white SSTV transceiver designed for telephone service. It comes with a husky line cord power adapter ready to plug in to a modular telephone jack. The

compact unit measures 63/4" x 63/4" x 7" and weighs 31/2 pounds. It features a built-in 41/2" monochrome monitor with miniature fixed-focus vidicon camera. The size of the image is 31/4" x 21/2".



This is very simple. Just plug the VisiTel cable into your phone line, and plug your telephone into the VisiTel, and send pictures of the kids to Grandma in Los Angeles or Greece! Of course, Grandma will need a Visi-Tel to receive your transmission.

To operate the VisiTel, merely slide the camera tube cover to the side, exposing the camera tube. Next, push the SEND button to transmit your picture. It takes 5.5 seconds to send a picture in 90 x 90 pixels at 32 shades of gray. While the pixel and line count is not high, the good gray scale makes up for it. You're better off with more shades of gray and less pixels than vice versa-ask any slow-scanner.

#### **Neat Feature**

The VisiTel stores in memory the last three images received as long as the unit is turned on. It kicks the first memorized image out of memory when a fourth image goes into memory. To scroll through the picture memory bank, repeatedly press the VIEW/POSE button. You can send the same picture more than once from the memory. After displaying or sending the stored picture sequence, the Vis-



The Mitsubishi VisiTel visual telephone display.

iTel screen once again displays the user's live

The brightness control (up and down) keys enable the user to adjust the contrast in relation to ambient lighting. The keys affect the picture as it is displayed and received.

#### Interfacing VisiTel and Your Transceiver

The unit interfaces with any VHF or HF transceiver, so you can send and receive the same pictures on the air or record them on audio tape for playback. The other night, for example, Rick WB8RTK and I were sending pictures back and forth on 2 meters.

Since VisiTel uses the same red and green telephone lines for both sending and receiv-

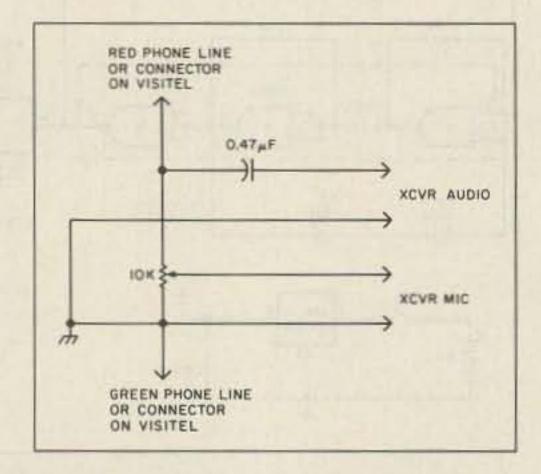


Figure 1. Transceiver audio coupling circuit.

ing, you have to couple the transceiver audio through a capacitor. A simple hookup is shown in Figure 1 with the green line as ground.

Leave everything as it is for receiving, but for transmitting, you'll have to use your SEND/RECEIVE switch to turn on your carrier before pushing the SEND button. I installed a pot to adjust the output to about 1 volt. Radio aShack's #279-355 quick connect jack is ideal for housing the pot and capacitor. The box contains a modular

telephone jack.

The ideal interface would key the VisiTel's push-to-talk line, and change from receive to transmit automatically when you press the SEND button. To sense the tone output of the VisiTel, I first tried using an optocoupler, and then I tried the 567 tone decoder chip, but neither method worked. The tone is present on both receive and transmit, which causes your rig to transmit on receive as well as on transmit. I decided it was impossible to interface without going inside the VisiTel.

#### Under the Cover

Three self-tapping screws free up the entire cover. Don't worry, no springs will jump out at you and no nuts will drop into some unreachable corner of the chassis. The mother board is easily recognizable and readily accessible, and just two connections are tack-soldered on top of the board. They are shown in Figure 2. They are +5 volts DC and ground.

You will notice that the interface in Figure 2 is the same as the one in Figure 1, except that its ground is common to the ground in the push-to-talk circuit. The interface draws about 3 mA maximum current so you can use #26 or even #30 wire-wrap wire. This size is very easy to thread through the expanded metal grill on the back of the unit.

Now you only need to connect one of the pins on the SEND switch. This requires further disassembly, but this is not a difficult

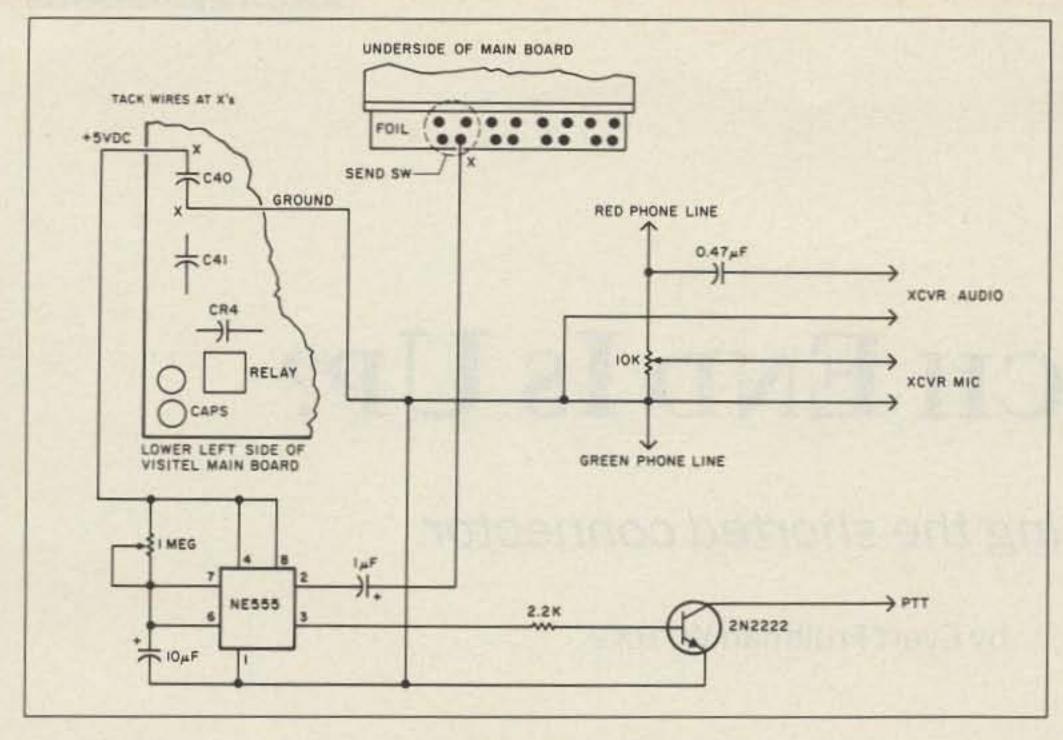


Figure 2. VisiTel/transceiver interface schematic.

procedure. When you have finished the 5 volt and ground connections, make this connection on the bottom of this same board. Free the board by removing the two large self-tapping screws from the edges of the metal cover that shields the foil side of the board. You don't have to take out all the little screws that hold this shield to the board. Fortunately, you make the connection on the exposed edge of the board, and not the part of the board covered by the shield.

The negative-going trigger pulse is applied to pin 2 through a 1 mF capacitor. The combination of the 10 mF capacitor (tantalum, please) and the 1 meg pot make up the RC network to set the time delay on the output at pin 3. Before pin 2 is triggered, pin 3 is low. When pin 2 is triggered, pin 3 goes high and turns on the 2N2222 transistor via the 2.2k base resistor. With the transistor emitter at ground and the collector connected to the transceiver push-to-talk, the transceiver is

#### "You're better off with more shades of gray and less pixels than vice versa..."

Remove the board by lifting sideways, disengaging the head pins from the connecting strip on the top side. You will see two white wires connected to the board which you do not need to remove. Tack-solder a wire to the SEND switch terminal as shown in Figure 2. This is a negative-going pulse which will trigger a 555 timer chip configured in the monostable mode. Bring this wire out with the +5 volt and ground wires. Re-insert the header pins in the connecting strip and fasten the two self- tapping screws. Before buttoning up the cabinet again, turn on the VisiTel and check for +5 volts, ground, and a negative-going pulse on the last wire tacked to the SEND switch. (A scope or logic probe will be helpful.) Close up the case, and you're ready to connect the interface as shown in Figure 2.

#### Operating the Interface

The operation of the interface is quite simple. You don't have to switch the red and green telephone lines. The push-to-talk circuit is just one way of using the miraculous 555 timer.

turned on for a period of time set by the RC network.

Because picture transmission time is 5.5 seconds, set the pot so that the transceiver is keyed on for about 6 seconds and then drops out. This setting is close to the center of the pot or around 500 k $\Omega$ . A little experimenting with pot settings will get the delay just right.

After you've made all the connections, plug everything in, open the VisiTel door, and get a picture on the monitor. Press the SEND button on the VisiTel and your push-to-talk will be keyed, and you'll be transmitting your picture. At the end of transmission, your push-to-talk relay will drop out and you'll be ready to receive.

Since the picture information is sent on a bandwidth of 3 kHz or less, you can transmit on any of the amateur frequencies permitting SSTV transmission, including HF. A little DIN plug or some such connector on the leads coming out of the VisiTel might be handy for quickly disconnecting the VisiTel when your XYL wants to use it to see her grandchildren in Sheboygan! Have fun!

### RF POWER TRANSISTORS

We stock a full line of RF Transistors, Modules, and Tubes for Amateur, Marine & Business Radio

Net/Ea

SEE YOU AT THE MIAMI HAMFEST

#### Partial Listing of Popular Transistors in Stock

Net/Ea

Denne	/WW/La		HUULA	F-11	MENT
	\$ 2.75	MRF497	\$14.25	2SC2630	\$28.0
MRF134	16.00	MRF515	2.50	2SC2640	15.0
MRF136	21.00	MRF555	3.00	2SC2641	16.0
MRF136Y	47.00	MRF557	5.25	2SC2694	46.7
MRF137	24.00	MRF559	2.25	2SC2695	
	-54/05	Contract of the Contract of th		The last of the last of	29.7
MRF138	35.00	MRF607	2.50	2SC2879	22.0
MRF141G	A POTATION OF A	MRF630	3.75	40582	9.5
MRF148	34.00	MRF641	18.00	LOW NOISE	FIGUR
MRF150	87.50	MRF644	21.00	MRF901	1.2
MRF151G		MRF646	25.00	MRF911	2.0
MRF171	34.50	MRF648	31.00		2.0
200122033555-1			153212004	MRF966	
MRF172	58.75	MRF653	13.25	NE25537	2.7
MRF174	80.00	MRF654	18.75	NE41137	2.50
MRF208	11.50	MRF660	10.75	J310	1.00
MRF212	16.00	MRF837	2.25	U309	1.73
MRF221	11.00	MRF843,/F	CATALON	U310	1.75
MRF222	18.50	MRF846	37.75	2N4416	21 2 3 2 2 5
6-6 LL 2 1/2 1/2 1/2	1001000	Transfer Company	Control Control of the		1.00
MRF224	13.50	MRF873	29.75	3N204	2.00
MRF226	14.50	MRF1946,/A	14.00	3N211	2.00
MRF227	3.00	PT9847.	21.00	OUTPUT M	ODULES
MRF237	2.00	RF120	22.00	SAU4	49.50
MRF238	12.50	SD1229	12.00	SAU17A	50.00
THE COUNTY	- 10 x - 110 x -		CONTRACTOR OF THE PARTY OF THE	22/20/20/20/20	10472
MRF239	14.00	SD1272	12.00	SAV6	42.50
MRF240	15.00	SD1278-1	13.75	SAV7	42.50
MRF240A	15.00	SD1405	16.00	SAV12	23.50
MRF245	27.50	SD1407	25.00	SAV15	48.00
MRF247	24.75	SD1428	27.00	M57713	49.50
MRF248	33.00	SD1429-3	16.00	THE CONTRACTOR	I DOMEST
PERSONAL PROPERTY.			2/2/202	M57726	57.75
MRF260	7.00	SD1434	30.00	M57727	69.50
MRF261	8.00	SRF2072	12.75	M57729	59.75
MRF262	8.75	SRF3662	24.00	M57732L	33.00
MRF264	10.50	SRF3775	13.00	M57735	57.50
MRF309	29.75	SRF3800	17.50	M57737	48.50
MRF314	28.75	2N1522	11.95	M57745	87.00
MRF314A	29.75	2N3553	2.25	M57755	78.75
MRF315	41.75	2N3771	3.50	M57762	69.75
MRF315A	32.50	2N3866	1.25	M57764	74.00
MRF317	59.75	2N4048	11.95	M57712,M577	33 use
MRF321	23.75	2N4427	1.25	M57737,SC10	
MRF327	57.00				
CONTRACTOR OF THE STATE OF THE		2N5109	1.75		se SAU4
MRF401	12.00	2N5179	1.00	MHW710-1,-3	
MRF406	12.00	2N5589	7.25	MHW820-1	76.00
MRF412	18.00	2N5590	10.00	MHW820-2	82.00
MRF421	24.00	2N5591	13.50	SPECIAL 1	ALCOHOLD THE COMMISSION OF THE
MRF422	36.00	2N5641	9.50	6L6GC	A TOTAL SALES OF THE SALES OF T
EUGENELI-DONE-		Annual Control			9.95
MRF427	17.00	2N5642	13.75	6CL6	9.95
MRF428	50.00	2N5643	15.00	6GK6	7.95
MRF429	39.00	2N5944	10.00	6HF5	14.95
MRF433	11.00	2N5945	10.00	6JB6	14.95
MRF435	68.50	2N5946	12.00	6JS6C	14.95
MRF449	22.50	2N6080	6.25	6KD6	
MRF449A	The second secon			1011000	15.95
AND STREET, ST	18.25	2N6081	8.00	6LF6	15.95
MRF450	13.50	2N6082	9.50	6LQ6/6MJ6	and the second second
MRF450A	14.25	2N6083	9.75	12BY7A	7.95
MRF453	17.00	2N6084	11.50	572B/T160L	69.50
MRF453A	18.50	2N6097	20.00	811A	17.95
MRF454	14.00	2N6255	2.50		
LEFTHANDS CT TO COLUMN		PERSONAL SECTION SECTI		833A	110.00
MRF454A	17.00	2SC730	4.25	5894	43.00
MRF455	11.25	2SC1307	3.00	6146B	12.95
MRF455A	12.75	2SC1946,/A	15.00	6550	14.95
MRF458	20.00	2SC1947	9.75	7581/KT66	14.95
MRF460	19.50	2SC1969	3.00	8950	18.00
A STATE OF THE STA		A THE DISCOUNT OF		The Carlot Control	
MRF464	25.00	2SC2029	2.25	4CX250B	74.50
MRF466	18.75	2SC2075	3.00	3-500Z	114.50
MRF475	6.75	2SC2097	28.00	We stock: 30	X800A7
MRF476	4.00	2SC2166C	3.50	3CX1200A7, 4	and the second second
MRF477	11.75	2SC2237	7.00	3CX1500A7,	
MRF479	V1000000000000000000000000000000000000				
LATERAL TRANSPORTATION OF THE PARTY OF THE P	13.75	2SC2289	13.75	3CX3000A7,	
MRF485	8.50	2SC2290	16.75	4CX1000A7,	8874
MRF485MP	19.75	2SC2312C	4.95	4CX5000A, 88	75,8877
MRF492	16.00	2SC2509	9.00	Sockets Ava	
2411 24 2 4 4 4					

Hi-Gain, Matched, and Selected Transistors Available MATCHED TUBE FINALS IN STOCK FOR HAM EQUIPMENT

RF Power transistors in stock for Atlas, KLM, Collins, Yaesu, Kenwood, Cubic, Mirage, Motorola, Heathkit, Regency, Johnson, Icom, Drake, TWC, Wilson, GE, etc. Cross-reference on CD, PT, SD, SRF, JO, and 2SC P/Ns. We Service Atlas & Swan—Call for Information

Quantity Pricing Available COD / VISA / MC

Ship/Hand. 1 lb. U.S. or Foreign Sm Pkt Air 8 oz. \$5.00
Orders received by 1 PM PST shipped UPS same day.
Next day UPS delivery available

PARTS ORDERS ONLY — NO TECHNICAL (800) 854-1927

ORDER LINE and/or TECH HELP (619) 744-0728 FAX 619-744-1943



### WHICH END IS UP?

Stalking the shorted connector.

by Evert Fruitman W7RXV

he boss handed me a 4-foot coaxial cable and told me to replace the shorted end. Since he wouldn't settle for two 2-foot cables, one good and one bad, I would have to figure out which end had the short.

For a few minutes, we talked about using an RC bridge to find a break in a cable, and joked about replacing both ends of the cable, which would shorten it too much. Finally, we came up with the following idea.

#### **Smart Thinking**

Supply a fairly heavy current from a constant current source to the cable and measure the voltage drop at the end. The key here is that the the shorted end will have a lower voltage drop than the other end. The difference would be in millivolts but easily readable with a digital multimeter. Figure 1 shows the setup.

Apply the current to one end of the cable and connect a digital voltmeter directly to the cable end. Write down the reading; say, 70-150 mV. Then, without changing its setting, connect the current source and the meter to the other end of the cable and write down that reading, possibly 20-50 mV. The low reading indicates the end with the least resistance. Unless there is a pin in the cable, or the short is in the middle of the cable, the end showing the lowest voltage is the one with the problem in the fitting.

Sometimes, just applying a heavy current will burn the short out, especially if it was caused by just one strand of the fine wire used in many coaxial cables. Burning out a strand or two, however, may leave a carbon path on

"The key here is that the the shorted end will have a lower voltage drop than the other end."

the cable. Even if the short clears up after you hit the cable with a couple of amps, redo the end for safety, depending on how you plan to use the cable. Especially take precautions for high frequency, high power applications. For low frequency, low power applications, it may not make much difference.

#### The Current-Limiting Power Source

Tying a 10-20 volt 2 amp power supply

across a shorted cable could damage the power supply, the cable, or both. Finding a suitable current source is easier than it sounds. A good laboratory power supply, and many home-brew supplies, have a current-limit adjustment on the front panel. Set it for 1 or 2 amps and proceed as above. If your power supply will deliver 1-2 amps, but lacks a current-limiting circuit, add an external limiter. A large resistor or even a car headlight will do the job. Car headlights draw about 3 amps each on low beam and about 5 amps each on high beam at 13 volts. They make handy, high power resistors. Figure 2 shows the setup using a load (here, a resistor) to limit current.

While 1/4 to 1/2 amp should furnish enough voltage drop to see on some voltmeters, the higher values will be easier to see, and they will more accurately indicate which end of the cable has the short.

Using this method, in minutes we had one cable the correct length and in service, and the shorted fitting in the waste basket. The boss was so pleased that he almost bought us lunch.

Perhaps the next time someone hands you a shorted cable, you will be able to tell which end is up. 73

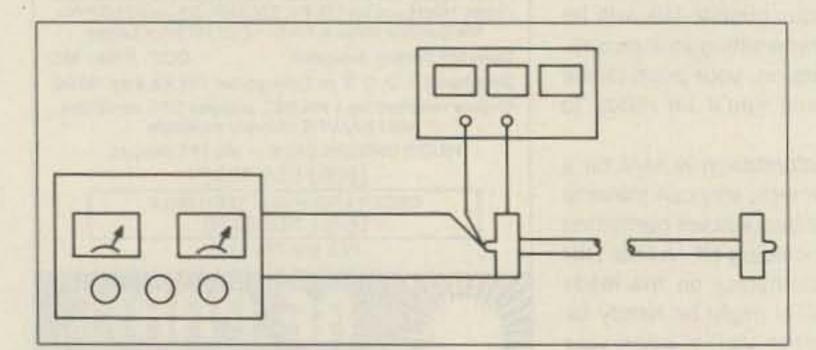


Figure 1. Basic setup to test cable. Power supply with built-in current-limiting set for 1-2 amps.

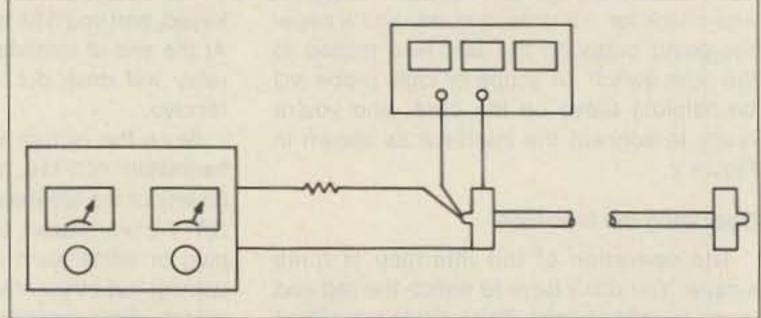


Figure 2. Setup with external current-limiting resistor. For a 1 amp 12 volt supply, use 10\Omega 25 W resistor or car headlight.

### RAMSEY ELECTRONICS

Quality Test Gear & Electronic Kits for Professionals and Hobbyists



THE COMMUNICATIONS \$249500 SERVICE MONITOR THAT WORKS HARDER FOR LESS.

Introducing COM-3... the new service monitor designed by service technicians for service technicians. It works harder for less...giving you advanced testing capabilities at a very affordable price. FEATURES . Direct entry keyboard with programmable memory · Audio & transmitter frequency counter · LED bar graph frequency/error deviation display . 0.1-10,000 µv output levels . High receive sensitivity, less than 5 µv • 100 KHz to 999.9995 MHz Continuous frequency coverage . Transmit protection, up to 100 watts . CTS tone encoder, 1 KHz and external modulation



**\$49**95

AC adapter PR-2 kit \$39.95



**\$69**95 PS-2 kit \$49.95

#### PREAMP The PR-2 is ideal for measuring weak

**PR-2 COUNTER** 

signals from 10 to 1,000 MHz . flat 25 db gain . BNC connectors . great for sniffing RF . ideal receiver/TV preamp . 3 db NF

#### PS-2 AUDIO

The PS-2 is handy for high resolution audio resolution measurements, multiples Up in frequency . great for PL tone measurements . multiples by 10 or 100 . 0.01 Hz resolution & built-in signal preamp/conditioner



100% manufactured in the USA

PS-10B 1.5 GHz PRESCALER

FREQUENCY COUNTERS

Ramsey Electronics has been manufacturing electronic test gear for

over 10 years and is recognized for its lab quality products at break-

through prices. All of our counters carry a full one year warranty on

turer of low cost counters in the entire USA. Compare specifications. Our counters are full featured, from audio to UHF, with FET high

impedance input, proper wave shaping circuitry and durable high quality epoxy glass, plated-thru PC Board construction. All units are

High impedance probe, light loading ...... 16.95

Tilt bail for CT-70, 90 & 125 Nicad pack for CT-70, 90 & 125

**ACCESSORIES FOR COUNTERS** 

parts and labor. We take great pride in being the largest manufac-

Extends the range of your present counter to 1.5 GHz . 2 stage preamp . divide by 1000 circuitry . super sensitive (50 mV typical) . BNC connectors . 1.5 GHz in, 1.5 MHz out · drives any counter.

#### CT-70 7 DIGIT 525 MHz

\$139.95 WINES INCLUDES

CT-50 8 DIGIT 600 MHz



\$189.9



\$169.95 WINED INCLUDES

CT-125 9 DIGIT 1.2 GHz

CT-90 9 DIGIT 600 MHz

me a	•••	1001	
15	WIRES INCLUDES AC ADAPTER	\$189.95 W	DAPTER
	FREQ RANGE	SENSITIVITY	ACCI
	20 Hz-550 MHz	< 50 mv To 150 MHz	17

MODEL	FREQ RANGE	SENSITIVITY	ACCURACY	DIGITS	RESOLUTION	PRICE
CT-70	20 Hz-550 MHz	< 50 mv To 150 MHz	1 PPM	7	1 Hz, 10Hz, 100Hz	139.95
CT-90	10 Hz-600 MHz	< 10mv To 150 MHz < 150mv To 600 Mhz	1 PPM	9	0.1Hz, 10Hz, 100 Hz	169.95
CT-50	5 Hz-600 MHz	LESS THAN 25 mv	1 PPM	8	1Hz, 10Hz	189.95
CT-125	10 Hz-1.25 GHz	< 25mv @ 50 MHz < 15mv @ 500 MHz < 100mv @ 800 MHz	1 PPM	9	0.1Hz, 1Hz, 10Hz	189.95
CT-90 WITH 0V-1 OPTION	10 Hz-600 MHz	< 10mv To 150 MHz < 150mv To 600 MHz	0.1 PPM	9	0.1Hz, 1Hz, 10Hz	229.90

#### MINI KITS—EASY TO ASSEMBLE—FUN TO USE

TONE BECODER

tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, volt-

age regulation, 567 IC. Useful for touch-

tone burst detection, FSK, etc. Can also

be used as a stable tone encoder. Runs

on 5 to 12 volts.

\$5.95 Complete kit. TD-1.

40 WATT 2 mtr PWEAMP

Simple Class C power amp features 8 times power gain 1 Win for 8 out, 2 Win for 15 out, 5 W in for 40 W out. Max output of 50 W, incredible value, complete with all parts, less case and T-R relay

\$27.95 PA-1, 40 W pwr amp kit TR-1, RF sensed T-R relay kit 6.95 COLOR ORGAN

See music come alive! 3 different lights flicker with music. One light each for, high, mid-range and lows. Each individually adjustable and drives up to 300 W. runs on 110VAC

\$8.95 ML-1-Kit.

VOICE ACTIVATED SWITCH

Voice activated switch kit provides switched output with current capability up to 100 mA. Can drive relays, lights, LED or even a tape recorder motor. Runs on 9 VDC VS-1 KIT

\$6.95

VIDEO MODULATOR

Converts any TV to video monitor. Super stable, tunable over ch 4-6. Runs on 5-15V \$7.95 accepts std. video signal. Best unit on the market! Complete kit. VD-1

LED BLINKY KIT Alternately flashes 2 jumbo LEOs. Use for

name badges, buttons, warning panel lights. Runs on 3 to 15 volts

\$2.95 BL-1Kit

UNIVERSAL TIMER Provides the basic parts and PC board required to provide a source of precision timing and pulse generation. Uses 555 timer IC and includes a range of parts for most

timing needs.

on 6-15 VDC \$4.95 MB-1Kit

MAD BLASTER

Produces LOUD ear shat-

tering and attention get-

supply up to 15 watts of

obnoxious audio. Runs

ting siren like sound. Can

WHISPER LIGHT An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light Includes mike, controls up to 300 W. runs on 110 VAC. UT-5KI \$5.95 WL-1Kit \$6.95 MIKE

WIRELESS

Transmits up to 300' to any FM broadcast radio. uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage.

FM-1Kit \$3.95 \$4.95 FM-2 Kit

SIREN

Produces upward and downward wail. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker.

Complete kit, SM-3 \$2.95

A super sensitive amplitier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2W rms output, runs on 6 to 15 volts, uses 8-45 ohm.

SLEUTH

BN-9Kit \$5.95

**60 Hz TIME BASE** Runs on 5-15 VDC Low current (25ma) 1 min/month accuracy

TB-6Kit \$5.50 18-6 ASSY \$9.95



TELEPHONE TRANSMITTER

Low cost with professional performance. Features include, self phone line powered, tunable from 76 to 100 MHz. polarity antisensitive. compact size (%" x 1%"). easily installs anywhere on the phone line or inside the instrument itself PB-1 KIT

\$14.95



**FM RECEIVER** 

For built-in applications or hobby experimentation. Full fledged superhetrodyne receiver, microvalt sensitivity, 10.7 MHz iF. Integrated Circuit detector, 50 mw audio amplifier, 9V external power source. operation on standard FM broadcast band as well as large portions on each side, compact (6" square), for bug detection or reception FR-1 KIT \$14.95



A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available.

\$14.95 FM-3Kit FM-3 Wired and Tested

12 VDC.

MICROWAYE INTRUSION ALARM A real microwave doppler sensor that will detect a human as far as 10 feet away. Operates on 1.3 GHz and is not affected by heat, light or vibrations. Drives up to 100 ma output, normally

NEW

\$16.95

open or closed, runs on

#### SPEECH SCRAMBLER Communicate in total

privacy over your tele-

NEW

phone or radio. This scrambler kit features full duplex operation using frequency inversion. Runs on a 9 volt battery. Both mike and line or speaker output/ inputs. Easy to connect to any radio-telephone use requires no direct connection! Easy to build, uses IC DBM circuitry Can also be used

Complete kit, SS-7 \$29.95 Case kit,

to descramble most

com. scramblers.

12.95 CSS-7



TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 . foreign add 15% for surface mail . COD add \$2.50 (COD in USA only) . orders under \$20.00 add \$1.50 . NY residents add 7% sales tax . 90 days parts warranty on all kits . 1 year parts & labor warranty on all wired units.

**PHONE ORDERS CALL** 716-586-3950

FAX 716-586-4754

RAMSEY ELECTRONICS, INC., 2575 Baird Rd., Penfield, N.Y. 14526

#### **ALL NEW KITS**



PERSONAL

New low cost microwave doppler radar kit "clocks" cars. planes, boats, horses, bikes, baseballs, models, runners or virtually anything that moves. Operates at 2.6 GHz with over 1/4 mile range. LED digital readout displays speeds in miles per hour, kilometers per hour or feet per second? Earphone output permits listening to actual doppler shift Uses two 1 lb coffee cans for antenna (not included) and runs on 12 VDC. Easy to build-all microwave circuitry is PC stripline. Kit includes deluxe ABS plastic case with speedy graphics for a professional look. A very useful and



#### **40 & 80 METERS** HAM RECEIVERS

RADIOS

Sensitive all mode, AM, CW, SSB receivers for 3.5-4.0 or 7.0-75 MHz. Direct conversion design. using NE602 IC as featured in QST and ARRL handbooks. Less than 1 µv sensitivity, varactor diode tuned, 50 mw audio output. Runs on 9VDC, has RF gain control. This kit is very easy to build, lots of fun and educational-ideal for the beginner or the old pro. The optional matching case kit features a rugged ABS plastic case with screened graphics. Included are machined aluminum knobs for a well-finished professional look.

#### **ORP TRANSMITTER KITS, 40 & 80 METERS**

Operate a mini ham shack. These little CW rigs are ideal mates to our 40 and 80 meter receivers: Features include smooth variable tuning, one watt output and excellent keying characteristics. Runs on 12 VDC and is VSWR protected. See how far you can stretch your signal with one of these mini rigs. Optional ABS cases are available

80 meters QRP rig. QRP-80

AIRCRAFT RECEIVER KIT



Hear exciting aircraft communications—picks up planes up to 100 miles away. Receives 110— 136 MHz AM air band, varactor tuned superhet design with AGC, ceramic lifter and adjustable squelch. Runs on 9V battery, 50 mw audio output, 1 µV sensitivity. Optional matching ABS plastic case lets you take it anywhere, features screened graphics and machined aluminum knobs for a real professional look. Compact—great for airshows or for just plain hanging around the airport

\$24.95

#### SHORTWAVE RECEIVER KIT

A fantastic receiver that captures the world with just a 12" antenna! Receives 4-11 MHz in 2 MHz bands, varactor funed, superhet design with AGC, RF gain control, and 50 mw audio output. Uses new Signetics mixer chip for less than a microvolt sensitivity, runs on 9V battery. This is a fascinating scout, school or club project, and will provide hours. of fun even to the most serious DX er. Add the optional case kit and you have a real nice looking

\$24.95

Receiver case \$12.95

#### **PACKET RADIO**

Commodore C64/128 packet radio interface. Uses famous German Digicom software. Features EXAR IC chip set for reliable operation—runs HF or VHF tones. Includes FREE disk software. PC board, all necessary parts and full documentation

Complete kit, PC-1 \$49.95

#### FM COMMUNICATIONS/2 METER RECEIVER

Sensitive superhet FM receiver tunes any 5 MHz segment from 135—175 MHz. Listen to 2 mfr. ham operations, high band police calls, weather or mobile phone calls! Easy to build receiver features varactor tuning, IC mixer stage, ceramic IF filters and dual conversion design with adjustable squelch. Less than 1 µv sensitivity, runs on 9 V battery, with 50 mw audio output. Optional ABS case with screened graphics and machined aluminum knobs provide a nice pro-

Complete \$29.95

Receiver case \$12.95

#### **NEW MINIKITS—NEW MINIKITS**

#### BROADBAND PREAMP

fessional look

A sensitive all purpose preamp, ideal for scanners, TV sets, VHF UHF rigs, counters, etc. Features low noise, 4 db NF, 20 db gain, 100 KHz-1 GHz operation Runs on 9-12 VDC, 50 ohms input.

Complete \$12.95

LOW COST

CASE

#### LIGHT BEAM COMMUNICATORS

Transmits modulated infrared light up to 30 feet without lenses. up to 1/4 mile using lenses. Uses 30 KHz carrier for hum-free operation, transmits thru windows, etc. Ideal for "bugs" or listening to IR remote controls. Transmitter has sensitive mike input, receiver uses PIN detector and drives speaker output. Units operates on 9-12 VDC

Transmitter kit. LB-6 Receiver kit.

\$8.95 sg.95

#### HIGH POWER FM WIRELESS MIKE

A high power unit that will transmit up to 1/2 mile to any FM broadcast radio. Sensitive input accepts any type of mike, will pick up normal voices 10 feet away using the available mini-electric mike cartridge. Operates on 9-12 VDC


FM-4 kit

Sensitive microphone cartridge

\$2.95

\$9.95

#### 2 MTR & 220 BOOSTER AMP

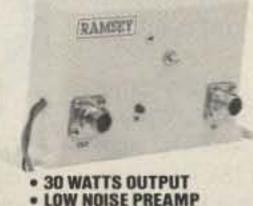

ONE YEAR WARRANTY

MHz hand-held unit. These power boosters deliver over 30 watts of output allowing you to hit the repeaters full quieting while the low noise preamp remarkably improves receptions. Ramsey Electronics has sold thousands of 2 mtr amp kits but now, we offer completely wired and tested 2 mtr as well 220 MHz units. Both have all the features of the high priced boosters at a fraction of the cost. PA-10 2 MTR POWER BOOSTER (10 X power gain)

Here's a great booster for any 2 meter or 220

Fully wired & tested . . . . . . . . . . . \$59.95 PA-20 220 MHz POWER BOOSTER (8 X power gain) RUGGED CAST ALUMINUM Fully wired & tested ...... \$59.95

# COMMODORE 64 VOLTAGE PROTECTOR

An inexpensive project, a valuable safeguard

by R.T. Saponas WØYJO

When you turn on your Commodore computer, do you ever have visions of the voltage regulator going bad in the power supply, ruining ICs? Put your worries to rest. Build a Commodore 64 Voltage Protector for less than twelve dollars.

The above unpleasantness appeared on my horizon one morning as I was working on a manuscript. The screen on my monitor blinked, filled with garbage, and then went black.

I checked the power supply. As I suspected, the 10.9 volt AC supply was still working, but the 5.08 volt DC supply was now a 10 volt DC supply. I don't have to tell you what happens when an IC designed for five volts receives double that!

After buying a new power supply and having the computer repaired, I spent some time looking through electronics magazines for voltage protection devices. I found several variations of "crowbar circuits" described by Jack Eschmann in the August 1979 issue of 73; by Ken Wyat in the November 1982 issue of 73; by W1SL in the August 1973 issue of QST; and by John Pelham in the October 1980 issue of QST. All I had to do was lay out an experimental circuit and make it work with the Commodore supply.

Of course any regulated power supply needs an excess voltage to regulate and is thus capable of destroying sensitive circuits it's powering. It doesn't take a lot of imagination to apply this idea and circuit to other situations.

#### Circuit Description

Variations of the basic crowbar circuit have been used for fifteen or more years in over-voltage protection devices for commercial equipment.

See Figure 1. You place a 1.5A fast-acting fuse—fifty percent over the C-64's requirement—in series with the 5.08 volt DC line. The silicon-controlled rectifier (SCR) is connected from the output of this fuse to ground.



Photo A. The completed Commodore 64 Voltage Protector.

A 4.6 volt zener diode goes from the fuse output to ground through a  $47\Omega$  current-limiting resistor and a 1k resistor. Trigger voltage for the SCR is obtained from the junction of these two resistors. Use an 0.01  $\mu$ F disc ceramic capacitor to bypass the gate of the SCR.

Should the DC voltage suddenly rise due to a failure in the Commodore power supply, the zener diode will start conducting. This will produce a trigger voltage on the gate of the SCR which causes the SCR to latch on. This shorts the output of the fuse to ground. The fuse will then blow, saving the computer's expensive ICs from destruction.

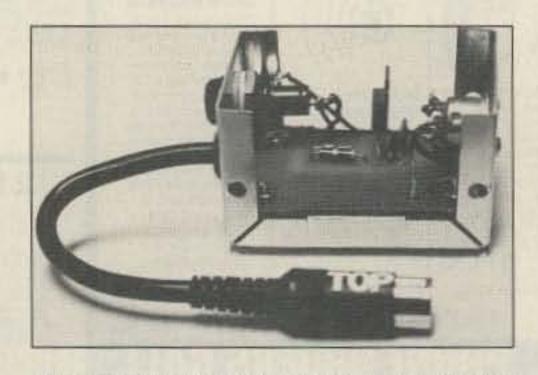


Photo B. The unit with the cover removed, showing the placement of the parts.

#### Construction

Begin construction by cutting the circuit board to size (see Figure 2). These dimensions allow adequate room to run the 10.8 volt AC leads under the circuit board. Drill the mounting holes in each corner. Next, use the board as a template to drill similar mounting holes in the bottom of the box. Make certain that the template is placed so that the spacing is even on all four sides. The holes in both the board and the bottom of the box should accommodate the four 6-32x½" mounting screws.

Now, prepare the circuit board for etching. Since all the traces are straight lines, you may use any method of masking. I covered the copper surface with masking tape, then used a razor blade to remove the tape from areas to be masked. Next, I applied a coat of fast drying enamel. After the enamel dried, I removed the masking tape between the sprayed areas. The board was now ready for the etching bath.

If etching a circuit board is distasteful to you, you can substitute a piece of perfboard of similar size, and hand-wire the circuit.

While waiting for the paint to dry, you can begin marking and drilling the front and back of the aluminum box for mounting the rubber grommet, the fuse, and the input DIN socket. Use a 3/8" drill for the grommet, a 1/2" drill for the fuse holder, and a 3/4" punch for the DIN socket. If your shack doesn't have all of these tools, use the drills you have, then carefully ream out the holes with a small rat-tail file. If you use the Radio Shack fuse holder shown in the parts list, you will have to slightly enlarge the 1/2" hole. The manufacturer apparently used a metric measurement for this fuse-holder. Since these boxes are made of very soft aluminum, take care with the rat-tail file. A hole becomes large very rapidly.

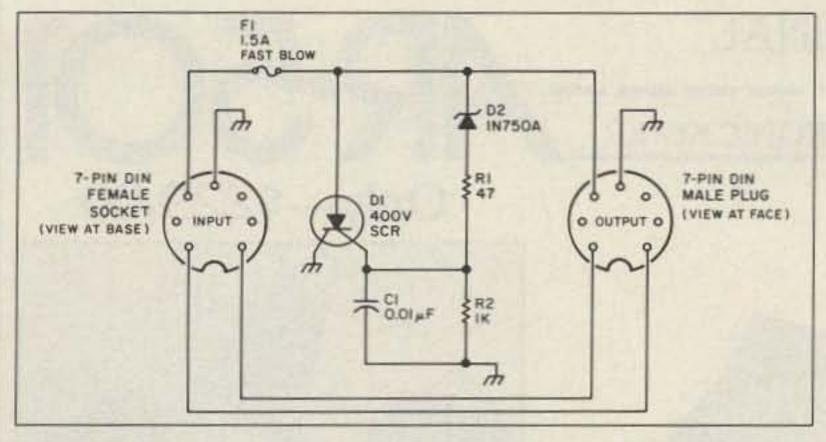


Figure 1. Schematic for the Commodore 64 Voltage Protector.

the positive 5 volt pin on the input socket to the input side of the fuse holder.

Now, dress and cut the 4" DC lead, which you previously soldered to the circuit board, and solder it to the output side of the fuse holder. Do the same for the remaining ground lead from the circuit board, but solder it to the ground pin on the input socket. The unit is now ready for testing.

#### **Testing and Troubleshooting**

After you have finished assembling and wiring the Commodore 64 Voltage Protector, visually inspect it for wiring errors. The easiest error to make is to wire the input socket and the output plug improperly. At this point, it's a good idea to use an ohmmeter to check out this circuitry.

Apply a variable, current-limited DC voltage source to the output side of the fuse. With a voltmeter across the source, gradually raise the voltage from 5 volts until current-limiting causes the voltage to drop to zero. This means that the SCR has been triggered and is now shorting out the power supply. Turn off the power supply, and the SCR will drop out of conduction. The SCR should trigger at a point between 5.1 volts

and 5.5 volts.

**Parts List** 

1.5A Fuse (fast acting) Radio Shack #270-1243

4.7 V

Radio Shack #272-131

Radio Shack #276-1020

Radio Shack #271-009

Radio Shack #271-023

Radio Shack #270-362

Radio Shack #270-235

Radio Shack #276-1591

\$ .20

1.19

.62

.35

.10

.10

1.29

1.79

1.00

1.65

1.85

.50

If you do not have a current-limited variable supply, you can make a fixed supply variable by using a potentiometer across the output. Use a 6 volt pilot lamp as an indicator of SCR firing. Solder two leads to the bulb and connect it across the fuse holder in your Protector. Remove the fuse from the fuse holder and apply voltage to the input side of the fuse holder. Again, place a voltmeter across the output voltage and gradually increase the voltage until the SCR triggers. The triggered SCR causes the pilot lamp to light, since it shorts one side of the pilot lamp to ground, placing it directly across the power supply.

If you use parts from your junk box, remember that the SCR and the zener diode are the critical parts. The tests above will help you determine if your components are okay.

After you have assured yourself that the unit is working, plug your regular Commodore power supply into it. Plug the unit into the computer, and you're ready to go. Always make certain to match the keys in plugs and sockets when you plug them together. If you force the plug into another position, you may short out your supply.

If the fuse in your Commodore Voltage Protector blows during normal operation, unplug the computer power supply from the wall socket and from the computer. Take it to your work bench and measure both the AC and the DC output voltages. If either voltage is missing, you need a new power supply. If the AC voltage is normal, but the DC voltage is 9 volts or higher, your Protector is doing its job. Buy a new supply and pat yourself on the back! 73

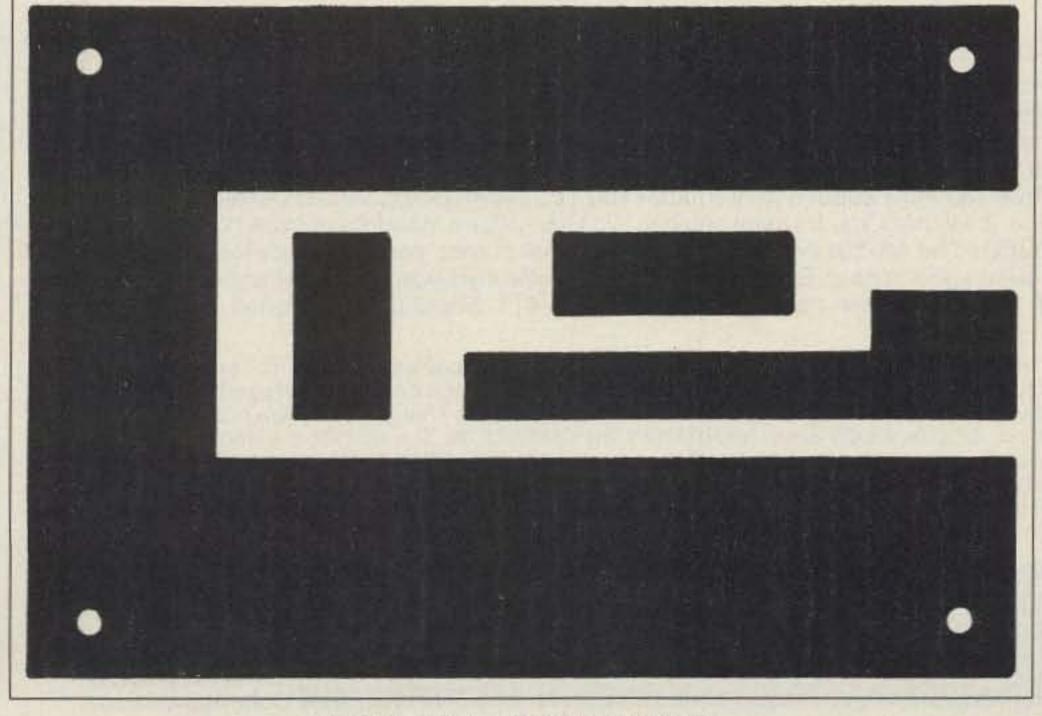


Figure 2. Full-size circuit board, foil side.

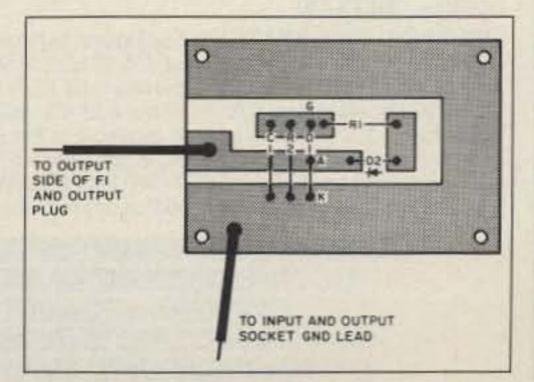


Figure 3. Parts placement layout guide.

If you use fast-dry enamel, your circuit board should now be ready for the etchant bath. After you have etched and washed the board, bend the leads on the components and drill the holes as indicated in the parts layout sketch. Don't forget to drill one hole in the output trace and another hole near it, in the ground trace. Solder a 4" piece of wire in each of the holes. Later, you can cut these wires to the correct length and solder them to the input plug and to the fuse. Solder the

components in place. Mount the 7-pin socket with the socket key towards the top of the box. Next, solder the ends of the 12" piece of four-wire cable to the appropriate pins on the 7-pin plug. Strip five inches of the outer covering from the opposite end of this cable. Thread the cable through the %" grommet, leaving the stripped portion inside the box. Dress and cut these wires so the two AC leads and the ground lead will lie

under the circuit board after it is mounted. Solder these three leads to the proper pins of the input socket.

box, using 6-32x1/2" machine screws and 1/4" metal spacers.

Mount the circuit board to the bottom of the

Mount the fuse-holder. Solder a lead from

C1

D1

D2

F1

R1

R2

0.01 µF Ceramic

400V-6A SCR

1N750A Zener

47Ω ½W

1kΩ 1/2W

Fuse Holder

Chassis Box

(21/4" x 11/2")

7-pin DIN plug

(23/4" x 21/8" x 15/8")

Copper-clad board

12" piece of 4-wire cable

7-pin DIN socket

#### RADIO TELEGRAPH TERMINAL

MORSE CODE DECODER

**ELECTRONIC KEYER** 

Only-\$229.00

#### MORSE CODE TRAINER



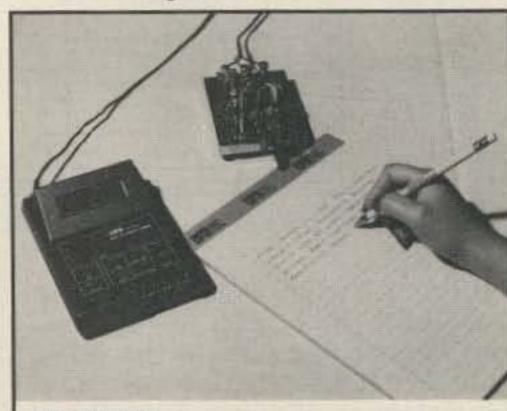
#### DECODER

Input level Input impedance Decoding speed Audio filter

- . 10mV to 2V RMS.
- 8 to 1kΩ-600Ω typical
- 5 WPM to 30 WPM
- 800 Hz ± 80 Hz Active and PLL filters 700 Hz to 900 Hz internally adjustable.





#### TRAINER

Code generator

Speed

- Random code generator 5 characters/code group • 5 WPM to 30 WPM
- 1 WPM increment



#### **ELECTRONIC KEYER**

Paddle input

• TTL level

-LO/Actuating, HI/Stop Contact input

-ON/Actuating, OFF/Stop

Key input

 TTL level -LO/Mark, HI/Space

Contact input

-ON/Mark, OFF/Space

5 WPM to 30 WPM

Keying speed

Keyer output

1 WPM increment Transistor switching,

Open collector type

#### **SPECIFICATIONS**

Model

Power source

Size Weight

Controls

Display

Indicators

Front connections

 AR-501 Radio telegraph terminal

DC 12V to 13.8V—165mA

• 4.5"-W x 2.24"-H x 6.25"-D

12.5 oz. (358 g)
 Power On/Off

Random code generator On/Off
 Print-out On/Off

· Monitor speaker level

· Electronic keyer mode select

· Speed Up & Down

. LCD 32 characters-16 per line

Power On—Green LED

• Tuning-Red LED

Paddle—Standard/lambic

· Ordinary telegraphic key

· Headphone/Earphone

• DC 13.8V input Rear connections

Audio input

· External speaker

 Keyer output · Printer output



#### PRINTER PORT

· Compatible with Centronics 8-bit parallel printer. At least 4K byte data buffer is required in a printer.

#### BACK TO BASICS - • - • But far more advanced - - • -

The AR-501, triple mode CW terminal in a small package, is a powerful gear to practice and play with. For the Novice, SWL and Amateur radio operators it detects Morse code between 5 to 30WPM. Just plug the AR-501 to your receiver to start translating the Morse code onto full 32 character LCD display. Very simple and easy to operate. You ask; for code practice?, both receive and transmit? Yes, the AR-501 does just that. It will improve your cord reception and keying technique at the speed you want. More?. it operates as an electronic keyer both standard and iambic. More Yet? How about a printer port? You bet, the AR-501 provides parallel printer port for hard copy. You can Log the QSO, and Practice. It will help you immeasureably. We even offer a standalone Nicad operated thermal printer as an option. ACCESSORIES SUPPLIED: The AR-501 Radio telegraph terminal comes complete with Receiver cable, DC Power cable, Miniature Phone plug, Miniature stereo phone plug, Spare fuse, Wall receptacle style power adaptor and Instruction manual. ACCESSORIES AVAILABLE: CC-501 Parallel printer cable - \$30.00/DPU-411 Standalone Thermal printer with 8K buffer.-\$235.00

ORDERING INFORMATION: For fastest service, call 800-523-6366 from 9 A.M. to 4 P.M. P.S.T. Send mail orders to: ACE Communications, Inc. 22511 Aspan Street, Lake Forest, CA 92630. VISA and MasterCard orders and certified or cashier's check or money order shipped within 48 hours of receipt. Rush service by UPS/Overnight, UPS/2nd Day Air and Federal Express is available at extra shipping charges. Purchase orders accepted from Government agencies. CA residents add 6% sales tax. COD is \$3.00 extra. WARRANTY INFORMATION: The AR-501 covered by One Year Warranty. Extended warranty service available at the following rates: 3 Years-\$25.00, 2 Years-\$15.00. SATISFACTION GUARANTEE: If, for any reason, the ORIGINAL PURCHASER, is not satisfied with the unit purchased, a full refund of the purchase price will be issued if the unit and all accessories are returned to us UNDAMAGED WITHIN 25 DAYS of the date of original purchase (Invoice date). This policy excludes any additional freight that may be incurred, and in no event modifies or limits the limited warranty.



22511 Aspan Street • Lake Forest • California • 92630-6321 • (714) 581-4900 • Toll Free 1-800-523-6366

WE SHIP WORLDWIDE

### ectronics Corp.

Your one source for all Radio Equipment!



Ring in the New Year With the best of Barry's New Gear KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK. Saturday & Sunday 10 to 5 P.M.

Monday-Friday 9 to 6:30 PM Thurs. to 8 PM Come to Barry's for the best buys in town.



YAESU

Concepts

**ONV Safety** belts-in stock

<u>a</u>esu

FT-767GX, FT-757GXII, FT-311 RM, FRG-8800, FT-736, FRG-9600, FT-4700RH, FT 212/712RH.

KENWOOD



Antennas

A-S, AES, Cushcraft, Hy-Gain, Hustler, KLM, METZ, Mosley, MODUBLOX, TONNA, Butternut

TS440S/AT, R-5000, R-2000, TS-940 S/AT, TM 221A/421A, TM-2570A/50A/30A, TR-751A, Kenwood Service Repair, TM-721A, TS-711/811A, TM3530A, TH205AT, TH215A, TM-621A, TM-321A, TS140S, TS680S, RZ-1, TS-790A.

**Budwig ANT. Products** NEL-TECH DVK-100 Digital Voice Keyer **FLUKE 77 Multimeter** 

Media Mentors-

Amateur Radio Course \$99.95

VoCom/Mirage/Alinco Tokyo Hy-Power/TE SYSTEMS Amplifiers &

5/8 \ HT Gain Antennas IN STOCK

MICROLOG-ART 1, Air Disk, SWL, Morse Coach

Soldering Station 48 Watts \$68.



**METRON MA-1000 B STOCKED** 

AEA 144 MHz AEA 220 MHz AEA 440 MHz

ANTENNAS

EIMAC 3-500Z 572B, 6JS6C 12BY7A & 6146B BIRD Wattmeters &

In Stock

Elements

Computer Interfaces

Stocked: MFJ-1270B

AR 900 Hand Held Scanner 100

ch. Covers 27-54, 108-174.

406-512, 800-950 MHz \$299

W/FAX.

MFJ-1274, MFJ-1224, AEA

PK-88, MFJ-1278, PK-232

FT-23/73/33/727R IC2AT/12AT FT-2/1/709R/H ICO2AT-32AT FT-1903/1123 IC2/4GAT FTH-2005/7005 II IC-A2/U16 IC-448A

**V** ICOM

Landmobile HT's ICOM: U16, H16, V100, U400 MAXON, MOTOROLA, YAESU: FTH 2005/2007 UNIDEN, REGENCY, KING, TAD MARINE ICOM: M5, M55, M700 AVIATION ICOM: A20 H.T

ALINCO ALD 24T

FREQUENCY COUNTERS: 1MHz-1.3GHz \$169.95

COMMERCIAL & HAM REPEATERS STOCKED. WRITE FOR QUOTES

MOTOROLA AUTHORIZED DEALER KACHINA COMMUNICATIONS DEALER

SHORTWAVE RECEIVERS STOCKED

DIGITAL FREQUENCY COUNTERS Opto electronics model 1300H, 0-1300MHz Trionyx, Model TR-1000, 0-600 MHz

Long-range Wireless Telephone for export in stock

BENCHER PADDLES. BALUNS, LOW PASS FILTERS IN STOCK


MIRAGE AMPLIFIERS **ASTRON POWER SUPPLIES** Saxton Wire & Cable, Int'l Wire For the best buys in town call: 212-925-7000 Los Precios Mas Bajos en Nueva York WE SHIP WORLDWIDE!



IC-R71A, 751A, 781, 28A/H, 38A, 48A, Micro2/4, R-7000, IC-761, IC-375A, 275A/H, 3210A, 475A/ H, 735, IC-900, IC-228H



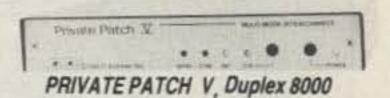CES Simplex Autopatch 510 SA Will Patch FM Transceiver To Your Telephone Great For Telephone Calls From Mobile To Base. Simple To Use, 510SA/510SAII



TUNERS STOCKED: **NYE MBV-A3 Killowatt Tuner** 



MFJ-989C



Ten-Tec Tuner 229B

COMET ANTENNAS STOCKED



HEIL **EQUIPMENT** IN STOCK

**SANGEAN Portable Shortwave Radios** 



Hy-Gain Towers & Antennas, and Rotors will be shipped direct to you FREE of shipping cost.

New TEN-TEC Corsair II, PARAGON

KANTRONICS

KAM

UTU, KAM, UTU-XT,

IIX Towers, Antennas, Mobile Radio mounts stocked. Call.

**AMERITRON AUTHORIZED DEALER** 

MAIL ALL ORDERS TO: BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012 (FOUR BLOCKS NORTH OF CANAL ST.)

#### LARGEST STOCKING HAM DEALER **New York City's** COMPLETE REPAIR LAB ON PREMISES

#### "Aqui Se Habla Espanol"

BARRY INTERNATIONAL TELEX 12-7670 MERCHANDISE TAKEN ON CONSIGNMENT FOR TOP PRICES

Monday-Friday 9 A.M. to 6:30 P.M. Thursday to 8 P.M. Saturday & Sunday 10 A.M. to 5 P.M. (Free Parking)

IRT/LEX-"Spring St. Station". Subways: BMT-"Prince St. Station". IND-"F" Train-Bwy Station" Bus: Broadway #6 to Spring St. Path-9th St./6th Ave. Station.

COMMERCIAL RADIOS STOCKED: ICOM, Motorola, MAXON, Standard, Yaesu. We serve municipalities, businesses, Civil Defense, etc. Portables. mobiles, bases, repeaters...

> ALL SALES FINAL

We Stock: AEA, ARRL, Alinco, Ameco, Ameritron, Antenna Specialists, Astatic, Astron, B&K, B&W, Bencher, Bird, Butternut, CDE, CES, Cushcraft, Daiwa, Eimac, Henry, Heil, Hustler, Hy-Gain, Icom, KLM, Kantronics, Larsen, MJF, J.W. Miller, Mirage, Nye, Palomar, RF Products, Saxton, Shure, Tempo, Ten-Tec, TUBES, Yaesu, Vibroplex, Duplexers, Repeaters, Scanners, Radio Publications, Uniden, Kenwood, Maxon, RFC.

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS HAM DEALER INQUIRES INVITED PHONE IN YOUR ORDER & BE REIMBURSED

COMMERCIAL RADIOS stocked & serviced on premises. Amateur Radio Courses Given On Our Premises, Call Export Orders Shipped Immediately. TELEX 12-7670

FAX: 212-925-7001

### THE HACKER'S SHACK

Transceiver from a spectrum analyzer and tracking generator?

by Steven K. Roberts N4RVE

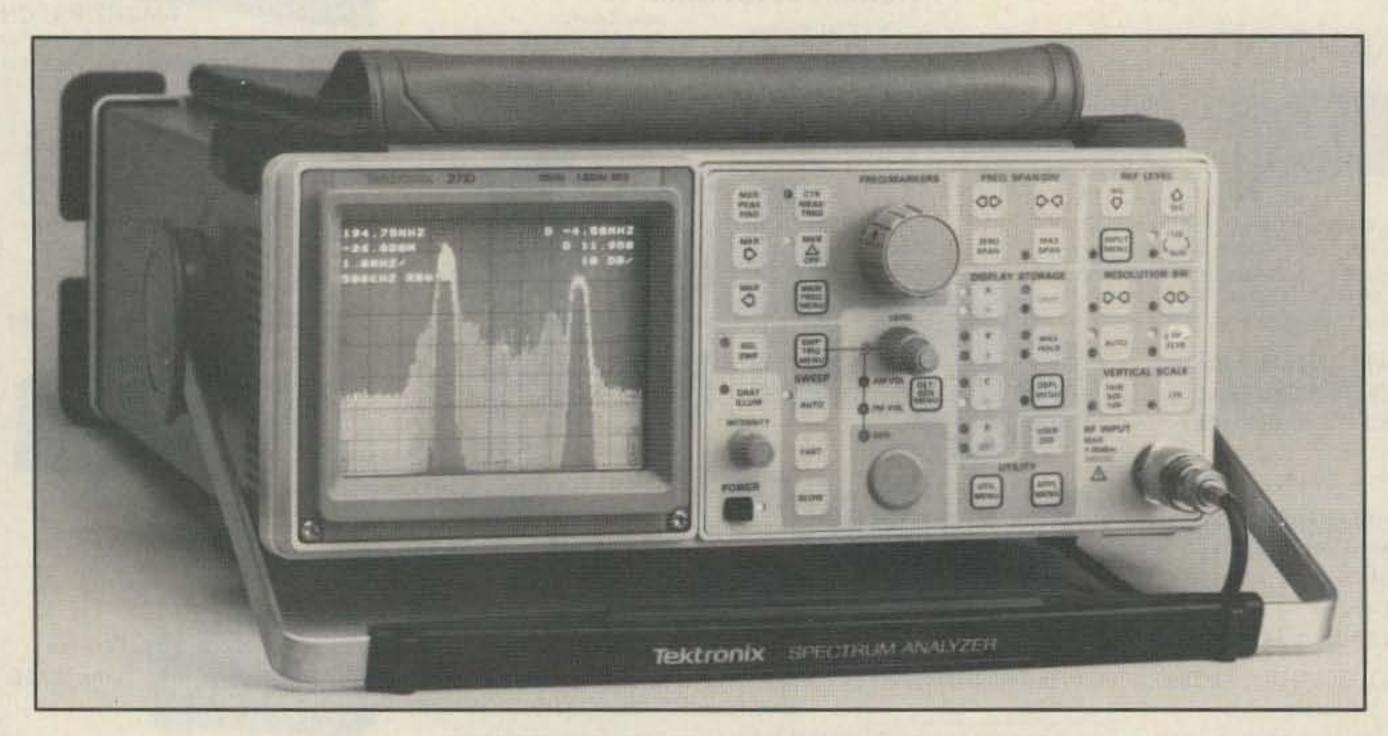


Photo A. Tektronix spectrum analyzer model 2710.

This is an interim of sorts—a time of misleading stability between bouts of nomadness. It's a respite from tire itch, a chance to develop a pot belly with unspent kilocalories, and a time to collect new equipment to further burden the already overloaded bicycle. Maggie and I are in a Silicon Valley layover, dedicated full-time to the creation of the Winnebiko III.

In the coming months, there will be plenty of space in these pages to discuss in satisfying detail the components of the new bicycle-mobile supershack. I've just started surgery on the multimode Ranger 3500 (for the 10 meter season is upon us), and many other strange projects are beginning as well. But I want to take a different approach this month, one inspired by the Hacker's Conference, rooms full of state-of-the-art test equipment, and a mad vision of future radio.

#### Bizarre and Colorful

A hacker, contrary to the recent slanderous allegations of CBS News, is not a computer criminal or some kind of evil-minded revolutionary. Those do exist, of course, but not in the subculture of creative genius that lies behind every new technology. A hacker, quite simply, is one who derives the greatest possible pleasure from circumventing limitations; a designer who leaps the boundaries of convention, pushes new ideas past the skeptical mainstream of an industry, and stays up all night in the wild-eyed fervor of creative insanity. Hackers are a bizarre and colorful bunch, and when I attended a whole conference of them in the Santa Cruz mountains this month, I witnessed an unrestrained intellectual energy that was almost frightening. It certainly seemed to frighten CBS...which showed images of my bike while speaking ominously of a band of revolutionaries gathered in the hills, plotting their next attack on the valley below.

The hacking phenomenon is generally associated with computers, for it has spawned such phenomena as the Mac, Hypermedia, and all manner of whiz-bang software and graphics magic. But any technology with a future is, by definition, eminently hackable...so let's consider the "radio

hacker" and what his or her station might look like.

#### The Ultimate Rig?

First of all, let's agree on something. This rig has to be realistic, something you could assemble today. We're talking real technology here, not dreams of future offerings from the Big Three. The fantasy is that these tools will someday be available for less than the hundred grand that they would cost right now... One of our general requirements is total agility in the electromagnetic spectrum, along with the ability to generate and demodulate any communication mode. We should be able to track mysterious signals, even if they're drifting, and determine their spectral content. We need to freeze events in time, pretriggering if necessary. All types of signal encoding, analog or digital, should be emulated in software. There should be plenty of clean power to the legal limit, robust antennas, and convenience features such as total remote control and automated operation. And, to satisfy the hacker within, there must be endless reserve capability for trying out new ideas and probing the limits of existing systems.

In a sense, any radio receiver is a spectrum analyzer, but one with a narrow window that moves with the cursor. What if we opened up the view of the spectrum, covering the famed "DC to daylight" range at any level of magnification? It turns out we don't have to invent this at all; they're available off the shelf from Tektronix and Hewlett-Packard.

One of the least expensive spectrum analyzers in this class also has some of the most interesting features. The Tektronix 2710 (see Photo A), covering the fairly modest range of 10 kHz to 1.8 GHz (most of their models go to 325 GHz), offers the interesting feature of demodulating any signal highlighted by the cursor, with AM, FM, and rasterized video the basic options. What if we take one of these analyzers and give it a high-gain tunable front end, a product detector, and a GPIB interface

cable to a host computer? Do we have a passable receiver?

To find out, I spoke with a few Tek engineers, and sure

To find out, I spoke with a few Tek engineers, and sure enough, it's not a mad idea at all. In fact, Stan W7NI and Ken N6RO have dreams of making an all-Tektronix QSO between Portland and San Francisco using only off-the-shelf test equipment. The transmitter? How about a tracking generator that follows the spectrum analyzer's sweep, locked on frequency by setting the instrument to zero span during a QSO? I've watched the machine handle video, 2 meter FM, and AM broadcast with equal felicity. You just set the cursor to an interesting peak or a specific frequency and tell it to demodulate to a built-in speaker or the screen. All bands, all modes, any bandwidth, computer control, graphic user interface . . . not bad for \$10,000!

Once a true hacker starts thinking like this and ignoring price, things rapidly get out of hand. By the time we add a broadband kilowatt linear, a full-size log periodic along with other appropriate antennas, and full remote control of the whole system via laptop computer and 9600-baud TNC...we have a pretty hard-core ham station.

#### A License to Tinker

In reality, of course, commercial spectrum analyzers are not optimized to perform as receivers. There are many features we have come to expect in communications gear, including IF passband tuning, and so on. But I suggest this not-entirely-absurd concept to make a point: we've grown so accustomed to buying special-purpose boxes to handle the essence of our hobby that the original spirit of ham radio has become almost vestigial, present only in the hard-core cadre of wizards

and inventors who keep bringing us new toys.

It's a dangerous pattern. I've met a number of packeteers, for example, who really don't know what's going through those wires between computer, TNC, and HT, other than something vaguely defined as "data." While there's a lot to be said for a turnkey radio data communications technology available to the masses (I'm all for it), we hams carry a license to tinker. Even though this hardly constitutes an obligation, it sure as hell is a pleasure . . . and as the average intelligence and education of the American human slowly falls, we find ourselves in the position of being the only ones outside the engineering labs who can actually make electronics work. That the designers among us are on the decline, I find disturbing.

The energy at the Hackers' conference typified the spirit that should appear in the top 1-2% of ham radio operators: a mad,

Photo B. The Createc SC02.

almost obsessive desire to build new systems (or make the old ones perform beyond the dreams of their creators). If this touches something within you, by all means...go for it!

#### Radical Oscilloscopes

All this talk of test equipment reminds me: a few months back in these pages, I lamented that I carry no oscilloscope on the bike. That has finally changed. There are too many situations where the complexities of the system demand something a little more capable than a logic probe and multimeter.

The Createc SC02, shown in Photo B, is a West German marvel that packages, in less than 2 pounds, a complete dual-channel 20 MHz storage scope with 46 waveform memories. It can perform calculations between the incoming channels, or between either of them and any stored waveform. It has four cursors per channel, with digital read-out of their relative time and amplitude values. Ten "setup memories" allow you to recover weird configurations, and the 50-key keyboard lets you define every conceivable scope parameter with a structured command language. There is even a multimeter mode, which is more exciting than it sounds: a replica of the waveform is displayed in the lower right corner while the bulk of the screen presents a constantly updated table of peak-to-

> peak, zero-to-peak, average, RMS, period, and frequency...complete with calculated maximum error percentages based on the position of attenuators and various internal factors!

> This unit is quite a departure from traditional oscilloscope designs, and the company is introducing a model early in 1989 that carries the concept to its logical conclusion: an optically-isolated RS-232 link will allow the SC04 to serve as a data-acquisition front end for digital signal processing, QC, or any other "smart instrumentation" application.

Power for the scope is provided through an external cable that carries +5 and +/-12, power easily derived from the existing switching supplies on the bike. I also carry a small AC supply for extended sieges at a bench, such as the one that's going on now. Interestingly, this little unit is so comfortable to operate and so easy on the eyes that I'm finding it preferable to traditional lab scopes, except in those rare cases when 20 MHz simply isn't enough bandwidth.

In next month's installment, we should have a look at an important part of the new bicyclemobile ham shack, the Ranger 3500 10 meter rig. Until then,

cheers from somewhere in the electromagnetic spectrum! 73

NOTE: For further information on the Createc SC02 hand-held oscilloscope, contact Ken Pine, Createc, 337 Kifer Road, Santa Clara, CA 95051; 408-738-3744.

For information on the Tektronix 2710 Spectrum Analyzer, call 800-835-9433 and ask for your nearest sales office.

Finally, my Computing Across America book continues to be available for \$9.95 plus \$2 shipping from: Computing Across America, 1306 Ridgeway Ave, New Albany, IN 47150.

### Hamcall

#### Callsign info on your microcomputer.

Buckmaster Publishing
Whitehall
Rt 3, Box 56
Mineral VA 23117
(703) 894-5777
Price Class: \$30/year

(long distance connect calls not included)

It was bound to happen. With the explosion of on-line services—into which anyone with a computer and a modem can call to get all kinds of information and perform all kinds of interactions, such as reading the up-to-the-hour UPI news, booking a plane ticket, or participating in one of hundreds of forums covering topics from (yes, Amateur radio!) to Zoology—someone would get around to putting a callsign information service on-line. This "someone" is Buckmaster Publishing, and the service is Hamcall.

#### **Getting Set**

After signing up for the service, Buckmaster sent me a page and a half of instructions. It supplied the necessary information for getting on-line and using the service. This included a five-digit password, access phone number, modem settings, and baud rates (Buckmaster

supports 300, 1200, and 2400 baud modems), and extra help with the service, which is basically menu-driven.

#### Operation

I had to follow the instructions carefully when I first signed on. Unlike most on-line services, no introduction appears when Hamcall answers the call. As stated in the instruction sheet, the service waits for the user to send two returns in order to determine the user's system baud rate. (My system is a Standard Turbo 10 micro (a PC Turbo clone), BCN Smartlink II modem, and Crosstalk XVI communications software.)

The service then asked for my password (five digits). After having called in a few times, I discovered that it always tells you on the first entry that the password is incorrect, whether or not you entered it cor-

rectly. Typing in the password correctly the second time brought me to the next step, where it asked for my callsign. After giving that, I had access to the directory.

Operation was basic from then on. The service simply asked, "What Call:" After I gave it a callsign, it took a few moments to display the associated name and address, and then immediately repeated the query. When I gave it a call for which it had no information, it came up with "No Match." Typing "bye" signed me off the system. That's all there was to it!

Once I gained some facility with getting on the service, it took about two minutes to get to the directory, which cost between 50 cents and a dollar for the toll call.

#### HamCall vs. Callbook


There are three elements, or "fields," involved-callsign, name, and address. Both Hamcall and The Callbook have only the callsign as the search field, i.e. they are useful only to find an unknown address and/or name from a known callsign. On the down side, Hamcall gives information only on hams with US licenses. On the up side, Hamcall's directory is updated every month-compared to the Callbook's quarterly updates, which involves referencing up to four different sources (the yearly Callbook and three supplements). It also retains previous callsigns of upgraders for up to one year. Buckmaster flushes out the old calls every December. I changed my call from KA1HY to NS1B on 14 June, and Hamcall, in early October, produced my name and address under both calls.

#### Time and \$\$\$ Considerations

Hamcall doesn't offer any real advantage to a ham who looks up only one or two calls every once in a while. US VHF and above contesters and DXers, WAS chasers, and others who need to find the addresses of many US licensed hams, however, would find Hamcall a real eye- and time-saver. Since the system operates in full-duplex mode (i.e., it can receive and transmit simultaneously), if you are equipped to do the same, you can lessen connect time by typing ahead of the service response. Just turn on the capture function to save to disk, and enter the calls one after another. Hamcall spends about 4-6 seconds per search for a callsign. One hundred searches thus means between 7-10 minutes of connect time. At ATT evening rates (35% off), this comes out to a maximum of \$2 for the toll from anywhere in the US. With a little ingenuity, and the appropriate software, you can print out these addresses onto mailing labels and affix them to QSL cards!
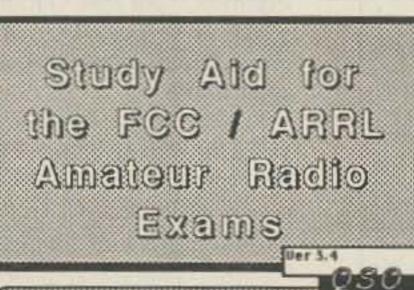
#### Conclusion

Hamcall is convenient and easy to use, especially for those already familiar with the workings of micros and modems. Hopefully, Buckmaster Publishing plans to get international callsign information, and perhaps even name and address search field options, on-line in the not-too-distant future. (Until recently, Buckmaster published Name and Geographical Index Callbooks). All in all, however, Hamcall is a good start for a service very much needed in the ham community.





by N4CST

#### Program Features:

 Runs on IBM Personal Computers and compatibles with minimum 256K RAM and CGA EGA or VGA graphics capability.

Copyright @ 1988

- Contains entire question pool for each license class. The Extra class version contains the question pool that will become effective in November 1, 1988.
- Work with the entire pool or selected areas, ie. "Rules and Regulations", "Practical Circuits" etc.
- Includes full screen graphics on appropriate questions.
- Logs multiple study sessions and allows resuming at a later time
- · Returns to review missed questions if desired.
- Creates ramdonly generated sample tests and analyzes results showing areas for additional study.

\*"After unsucessfully trying the Techniciam test twice, I passed with a perfect score by using your tutor"


-"Thanks for thinking of us hams. Your program has eliminated the worry of the Theory part of the test for me" KA3RHW


"As a computer professional, I can recognize a quality piece of software. As a student I can appreciate a study tool that helps me gain the confidence I need to pass the amateur exams. By the way, I passed with 100% of the questions answered correctly." Dan Derence Jr.

Public Domain disk also available contains excellent mores code tutor as well a contest logger, propagation predictors, beam plotter and others. Cost is \$3 to cover materials and handling, \$2 if shipped with QSO TUTOR.

Call or write to order:

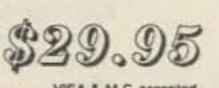QSO Software 208 Partridge Way Kennett Square, PA 19348 215-347-2109



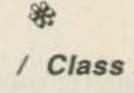

\* PA residents add 6%

CIRCLE 145 ON READER SERVICE CARD

### Hi Pro Repeaters

MAGGIORE ELECTRONIC LAB

**Manufacturers of Quality Communications Equipment** 

- Repeaters
- Links
- Remote Base
- VHF,UHF
- Receivers
- Transmitters
- Antennas



- Standard and Computerized Controllers
- Standard and Computerized **Auto Patches**
- Duplexers

HIPOE EXPANDABLE REPEATER SYSTEM

- A NEW CONCEPT IN REPEATER DESIGN. THE HI Pro "E" IS AN EXPANDABLE REPEATER WITH THE FOLLOWING FEATURES: A BASIC REPEATER WHICH WOULD IN-CLUDE A COMPLETE RECEIVER, TRANSMITTER, COR, FRONT PANEL CONTROLS AND INDICATORS, LOCAL SPEAKER AND MIC JACK AND CAPABLE OF FUTURE EXPANSION. ALL HOUSED IN AN EXTREMELY RUGGED, ENCLOSED, 19-INCH RACK MOUNTABLE CABINET.
- THIS SYSTEM CAN BE EXPANDED AT TIME OF PURCHASE OR CAN BE AN AFTER-PURCHASE ADD ON. THE ADD ONS ARE—HIGHER POWER, 110/220 VAC POWER SUPPLY, IDENTIFIER, AUTO PATCH, OR COMPUTER CONTROLLERS. IN ADDITION TO THESE ADD ONS AN ADDITIONAL RECEIVER AND TRANSMITTER CAN BE MOUNTED INTERNALLY FOR USE AS CONTROL LINKS, REMOTE BASE OR DUAL BAND OPERATION, ETC.
- AN EXTENSION PANEL IS AVAILABLE FOR LOCAL MONITORING OF THE REPEATER AND CONTAINS ALL NECESSARY METERING, STATUS LIGHTS AND INDICATORS. ALL ADD ONS ARE AVAILABLE FROM THE COMPANY AND ARE COMPLETE INCLUDING INSTRUCTIONS.

MAGGIORE ELECTRONIC LAB.

600 Westtown Rd.


West Chester, PA 19382

Phone (215) 436-6051

Telex 499 0741 MELCO

WRITE OR CALL FOR OUR COMPLETE CATALOG

**CIRCLE 47 ON READER SERVICE CARD** 

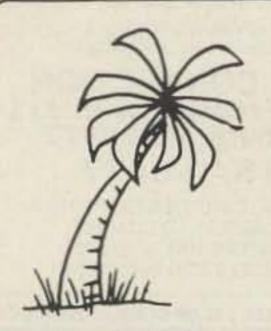

#### 29th ANNUAL


### TROPICAL HAMBOREE

A.R.R.L. FLORIDA STATE CONVENTION

FEBRUARY 4-5, 1989

TAMIAMI PARK FAIR GROUNDS

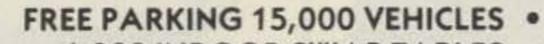10901 S.W. 24th Street (Coral Way), Miami, Florida HOURS: 9 A.M.-5 P.M. SATURDAY . 9 A.M.-4 P.M. SUNDAY



- 1,000 INDOOR SWAP TABLES .
- 300 CAMPSITES WITH FULL HOOKUPS .
- 200 COMMERCIAL EXHIBIT BOOTHS
- COMPUTERS & SOFTWARE
- LICENSE EXAMS

Registration: \$5.00 Advance - \$6.00 Door. Valid Both Days. (Advance deadline January 30th.) Swap Tables, 2 Days: \$16.00 each. Power: \$10.00 per User.

All swap table holders must have registration ticket.

Campsites: \$12.00 per Day • Includes Water, Power, Sanitary Hookups & Showers. (All RV vehicles, tent campers, vans, trailers welcome - no ground tents, please.)

Headquarters Hotel: Miami Airport Hilton, 5101 Blue Lagoon Drive, \$75.00 Single or Double Alternate Hotel: Airport Lakes Holiday Inn, 1101 N.W. 57 Avenue, \$50.00 Single or Double Reservation forms available through Hamboree Chairman, December 1st

Make Checks for Registration, Swap Tables & Campsites Payable to: Dade Radio Club Mail to: Evelyn D. Gauzens, W4WYR, Chairman, 2780 N.W. 3rd St., Miami, FL 33125

> Exhibit Booth & Program Booklet Advertising: Call Evelyn (305) 642-4139 (Home) - or - (305) 233-0000 (Office) (BROCHURE WITH FULL DETAILS AVAILABLE DECEMBER 1st)

> > 73 Amateur Radio • January, 1989 47

#### QEP's CLOSE-OUT SALE

You're not too late, copper prices WILL drive up the price of coax even more. Better buy it NOW.

#### AMPHENOL SPECIALS

PL-259 silver (mica filled)	\$1.25
UG-21D 'N' male cable end	2.75
UG-21D 'N' (fitted for 9913)	3.50
UG-29A 'N' Barrel (jack-jack)	4.50
UG-57B 'N' Barrel (plug-plug)	5.20
UG-58A 'N' Chassis receptacle	3.50

Copper-clad 14 ga (7x22) 7¢ a foot (any length) Identical to Belden 8000

VISA & MASTERCARD ACCEPTED SHIPPING IS ADDITIONAL Call TOLL FREE

> 1-800-USA-9913 in NJ 201-887-6424

110-4 Route 10 East Hanover NJ 07936

TNX JIM N2GKW & BILL KA2QEP

CIRCLE 30 ON READER SERVICE CARD

#### SPECIALISTS IN FAST TURN P.C. BOARDS

PROTO TYPE P.C. BOARDS AS LOW AS \$25.00

- SINGLE & DOUBLE SIDED
- PLATE THROUGH HOLES
- TEFLON AVAILABLE
- P.C. DESIGN SERVICES

FOR MORE INFORMATION



Midland **Technologies** 

34374 EAST FRONTAGE ROAD BOZEMAN, MT 59715 (406) 586-1190

CIRCLE 252 ON READER SERVICE CARD



WE HAVE EXPANDED AND NOW STOCK MANY NEW PRODUCTS: WE CARRY:

AEA, ALINCO, AMECO, AMP SUPPLY, APHA DELTA, ANTECO, ARRL, B&B INSTRUMENTS, BARKER & WILLIAMSON, BENCHER, BOMAR, BUTTERNUT, BEE, CUSHCRAFT, COMMUNICATION SPECIALISTS, CRB RESEARCH, DAIWA, DIAMOND, HENRY, HUSTLER, HAM RADIO, INTL. CRYSTAL, INTL. WIRING & CABLE, KANTRONICS, KACHINA, KENPRO, KDK, KLM/MIRAGE, LUNAR, LARSON, MOBILE MARK, MFJ, NEUTECH, NCG, NYE, PERIPHEX, QST, RF INDUSTRIES, RADIO PUBLICATIONS, RADIO AM. CALLBOOK, SAMSON, SPI-RO, SMILEY ANTENNA, SANTEC, SYN. TEXTILES, 73MAG, STANDARD, TAD, TEN-TEC, VALOR, VECTOR, GORDON WEST, WELZ, YAESU, AND ICOM.

In house service available. Just write, or give us a call!

(713) 879-7764 Telex 166872 MCON UT

CIRCLE 187 ON READER SERVICE CARD

#### NEW! MOBSE ELLOW

#### **Made Easy & Fun**


Introducing the most Comprehensive and Easyto-Use code course available today! -MORSE TUTOR is available for IBM PC, XT, AT, PS/2 and compatibles.

#### FEATURING!

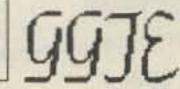- 1-100 word/minute code speeds
- Standard or Farnsworth modes
- Adjustable code frequency
- Over 1 Billion possible random QSOs
- Letter, number, and punct. mark coverage
- Self calibrating/menu driven design \* Display text-while listening or after copying

To Upgrade or learn CW, Send check or M.O. for \$19.95 + \$2 S&H to:

"Morse Tutor is, guite simply, a suberb value Bryan Hastings, KA1HY July, 1988, 73 Magazine



REFER TO QST JULY '88 P. 49

#### 21881 Summer Circle, Dept. MTS Huntington Beach, CA. 92646

CA. Residents add \$1.20 sales tax

NOW AVAILABLE THRU UNCLE WAYNE'S BOOKSHELF, THE ARRL & FINE DEALERS EVERYWHERE

**CIRCLE 339 ON READER SERVICE CARD** 

#### PC HF FACSIMILE \$79.95

A complete facsimile reception system for your IBM PC or compatible. Receive grayscale images in up to 16 shades or psuedo color depending upon your graphics card and printer.

Includes:

Demodulator Software

50 Page Manual **Tutorial Cassette** 

Requires:

HF receiver PC with 320K Graphics card Serial port



Software Systems Consulting 1303 S. Olá Vista San Clemente, CA 92672 (714) 498-5784

**CIRCLE 250 ON READER SERVICE CARD** 

#### RC-1000 REPEATER CONTROLLER

From Micro Computer Concepts

- Complete RX-TX-Phone Line Interface
- Repeater Control
- Autopatch
- · CW ID
- Tailbeeps
- · Reverse Patch
- Remote Base/Tape
   12 V AC/DC Oper.
- DTMF Decoder
- Pulse/Tone Dialing
   90 Day Warranty

Wired & Tested w/manual ...\$219.95 Distributed by:

R & L Electronics

575 Main St. / Hamilton, OH 45013 1-800-221-7735



in Ohio 513-868-6399



#### Discover CAROLINA WINDOM 80-10M High performance Use transmatch

132' overall

Line Isolator

Coax fed

\$69.95

Assembled

Vert Radiator

Matching XFMR

**Proven Results** \$70 Beam?

Passport To a world Of new ideas And exceptional HF wire antennas

Rugged new baluns Full range of HF, VHF mobile antennas, ducks, wire, coax, parts, line, accessories.

#### SEE WHAT WE'RE DOING NOW!

Contact Jim, W4THU—free discount catalog Send \$1 for catalog by 1st Class mail. Box 6159, Portsmouth, VA 23703 (Dealer Inquiries Welcome)

#### CAROLINA WINDOM

SEE THE REVIEW IN JUNE '88 WORLD RADIO MAGAZINE. Enthusiastic users say it's the best wire antenna. Outperforms wire antennas previously used. Knock-you-socks-off performance on 80-10. A \$70 beam?

If you hear one, you'll want one. Made with pride by the RADIO WORKS in VA/USA

CIRCLE 150 ON READER SERVICE CARD

#### THE RF CONNECTION

"SPECIALIST IN RF CONNECTORS AND COAX"

j	Part No.	Description	Price
١	PL-259/USA	UHF Male Phenolic, USA made	\$ .60
	83-1SP-1050	PL-259 Phenolic, Amphenol	.85
	83-822	PL-259 Teffon, Amphenol	1.50
1	PL-259/ST	UHF Male Silver Teflon, USA	1.50
1	UG-175	Reducer for RG-58	.20
1	UG-176	Reducer for RG-59 & MINI 8	.20
	UG-21D/U	N Male RG-8, 213, 214, Amphenol	2.95
	UG-21B/U	N Male RG-8, 213, 214, Kings	4.00
	9913/PIN	N Male Pin for 9913, 9086, 8214	
	40.2416.05	fits UG-21D/U & UG-21B/U N's	1.50
	UG-21D/9913	N Male for RG-8 with 9913 Pin	3.95
1	UG-21B/9913	N Male for RG-8 with 9913 Pin	4.75
	UG-146/U	N Male to SO-239, Teflon USA	5.00
	UG-83/U	N Female to PL-259, Teflon USA	5.00

"THIS LIST REPRESENTS ONLY A FRACTION OF OUR HUGE INVENTORY'

THE R.F. CONNECTION 213 North Frederick Ave. #11 Gaithersburg, MD 20877 (301)840-5477

PRICES DO NOT INCLUDE SHIPPING PRICES SUBJECT TO CHANGE VISA, MASTERCARD, ADD 4% UPS C.O.D. ADD \$2.25 PER ORDER

**CIRCLE 115 ON READER SERVICE CARD** 




#### R-7000 Widespan Panadaptor

Panadaptor especially designed for the R-7000 receiver. For use with a standard scope. Variable span width from 1 to 10 Mhz. Uncover unknown elusive signals. Complete with all cables, & 90 day warranty. \$349.95 Shipped. Pa. res. add 6%.

#### **GTI Electronics**

RD 1 BOX 272 Lehighton, Pa. 18235 717-386-4032

**CIRCLE 326 ON READER SERVICE CARD** 

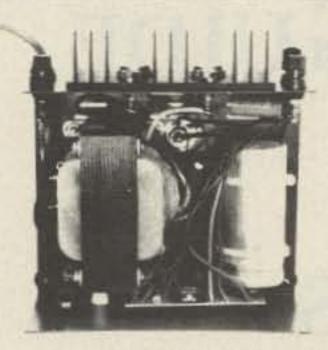

INSIDE VIEW - RS-12A

#### **ASTRON POWER SUPPLIES**

. HEAVY DUTY . HIGH QUALITY . RUGGED . RELIABLE .

#### SPECIAL FEATURES

- SOLID STATE ELECTRONICALLY REGULATED
- FOLD-BACK CURRENT LIMITING Protects Power Supply from excessive current & continuous shorted output
- CROWBAR OVER VOLTAGE PROTECTION on all Models except RS-3A, RS-4A, RS-5A.
- . MAINTAIN REGULATION & LOW RIPPLE at low line input
- . HEAVY DUTY HEAT SINK . CHASSIS MOUNT FUSE
- THREE CONDUCTOR POWER CORD
- ONE YEAR WARRANTY MADE IN U.S.A.

#### PERFORMANCE SPECIFICATIONS

- INPUT VOLTAGE: 105-125 VAC
- OUTPUT VOLTAGE: 13.8 VDC ± 0.05 volts (Internally Adjustable: 11-15 VDC)
- . RIPPLE Less than 5mv peak to peak (full load & low line)
- . Also available with 220 VAC input voltage




MODEL RS-50A





#### **RM SERIES**

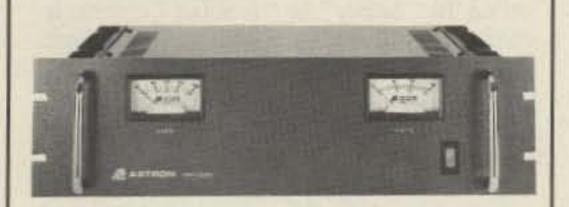

MODEL RM-35M

#### 19" × 51/4 RACK MOUNT POWER SUPPLIES

MODEL RM-12A RM-35A RM-50A	Continuous Duty (Amps) 9 25 37	ICS* (Amps) 12 35 50	Size (IN) H × W × D 5¼ × 19 × 8¼ 5¼ × 19 × 12½ 5¼ × 19 × 12½	Shipping Wt. (lbs.) 16 38 50
Separate Volt and Amp Meters     RM-12M     RM-35M     RM-50M	9	12	5¼ × 19 × 8¼	16
	25	35	5¼ × 19 × 12½	38
	37	50	5¼ × 19 × 12½	50

#### **RS-A SERIES**



MODEL RS-7A

MODEL	Continuous	ICS.	Size (IN)	Shipping
MODEL	Duty (Amps)	(Amps)	$H \times W \times D$	Wt. (lbs.)
RS-3A	2.5	3	$3 \times 4\% \times 5\%$	4
RS-4A	3	4	$3\% \times 6\% \times 9$	5
RS-5A	4	5	3½ × 6½ × 7¼	7
RS-7A	5	7	3%×6%×9	9
RS-7B	5	7	4 × 7½ × 10¾	10
RS-10A	7.5	10	4 × 7½ × 10¾	11.
RS-12A	9	12	$4\frac{1}{2} \times 8 \times 9$	13
RS-12B	9	12	4 × 7½ × 10¾	13
RS-20A	16	20	5 × 9 × 10½	18
RS-35A	25	35	5 × 11 × 11	27
RS-50A	37	50	6 × 13% × 11	46

#### **RS-M SERIES**



MODEL RS-35M

MODEL .	Continuous Duty (Amps)	ICS* (Amps)	Size (IN) H × W × D	Shipping Wt. (lbs.)
<ul> <li>Switchable volt and Amp meter RS-12M</li> </ul>	9	12	4½ × 8 × 9	13
Separate volt and Amp meters				
RS-20M	16	20	5 × 9 × 10½	18
RS-35M	25	35	5 × 11 × 11	27
RS-50M	37	50	6 × 13 <sup>3</sup> / <sub>4</sub> × 11	46

#### **VS-M AND VRM-M SERIES**



MODEL VS-35M

 Separate Volt and Amp Meters • Output Voltage adjustable from 2-15 volts • Current limit adjustable from 1.5 amps to Full Load

to t dir codo		Continuous		ICS*	Size (IN)	Shipping
MODEL		Duty (Amps	)	(Amps)	$H \times W \times D$	Wt. (lbs.)
	@13.8VD	C @10VD	C @5VDC	@13.8V		
VS-12M	9	5	2	12	$4\frac{1}{2} \times 8 \times 9$	13
VS-20M	16	9	4	20	5 × 9 × 10½	20
VS-35M	25	15	7	35	5 × 11 × 11	29
VS-50M	37	22	10	50	6 × 13% × 11	46
· Variable rack mount	power supplie	s				
VRM-35M	25	15	7	35	5¼ × 19 × 12½	38
VRM-50M	37	22	10	50	51/4 × 19 × 121/2	50

**RS-S SERIES** 



· Built in speaker

MODEL	Continuous Duty (Amps)	ICS*	Size (IN) H × W × B	Shipping Wt. (lbs.)
RS-7S	5	7	4 × 7½ × 10¾	10
RS-10S	7.5	10	4 × 7½ × 10¾	12
RS-12S	9	12	$4\frac{1}{2} \times 8 \times 9$	13
RS-20S	16	20	5 × 9 × 10½	18

# TROUBLESHOOTING GUIDE FOR SWITCHING POWER SUPPLIES

Trace the problem quickly with just a scope and a DC meter.

by Ed F. Rice W9NGP

E ver had trouble with your switching power supply, but didn't know where to start to find the problem? Well, the troubleshooting guide in Figure 4 presents a sequence of tests to follow when there is no output from a switching supply. It outlines strategic tests that quickly eliminate testing of whole sections of the circuitry at once, so the defect can be quickly isolated without the need to test a large number of individual components.

Switching supplies are subject to all the failures of conventional supplies: destruction of diodes in the input rectifier due to transients on the AC line; chokes, diodes, and transistors damaged by shorted load (because of the high efficiency of switching supplies, a shorted output results in a very high voltage elsewhere in the circuit); and overheating due to inadequate ventilation or skimpy heat sinks.

#### Switching Supply Components

The block diagram of a switching power supply in Figure 1 shows the overall relationships between the circuit divisions.

The input rectifier is often a simple ½wave system which rectifies the line voltage and sends low voltage DC to the switch signal generator and the AC power switch. A bridge rectifier is used in high power units.

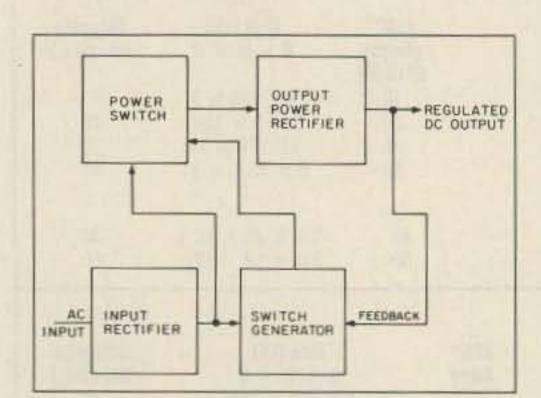


Figure 1. Box diagram of the relationships of the different circuits in a switching power supply.

The AC power switch is composed of a power MOSFET feeding the output choke and damper diode. The MOSFET is switched on and off at 50 kHz to 100 kHz by square waves of varying duty cycles applied to the gate. Regulation is accomplished by changing the duty cycle (not the frequency) to correct for variations in the output voltage. Figures 2a and 2b show a transformer-less single MOSFET circuit and a push-pull version used in high power supplies.

"It (the troubleshooting chart) outlines strategic tests that quickly eliminate testing of whole sections of the circuitry at once"

The output power rectifier, shown in Figure 3, is always a full wave center-tapped circuit in high power units. D3 is a type of damper diode which conducts when the field

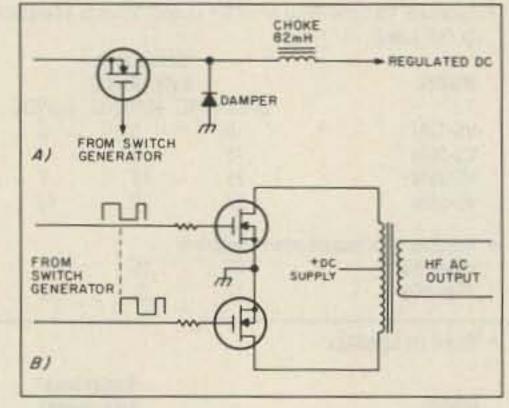


Figure 2. a) Transformer-less single MOSFET circuit. b) A push-pull version for high-power power supplies.

around the choke collapses, charging the output filter. This is the source of output power.

The combination of C3, R1, and D4 is called the "buffer" or "snubber" circuit. It shorts out the energy contained in the high voltage spike across the transformer secondary when the field collapses at MOSFET cutoff. An open diode, D4, can be disastrous to the transformer, MOSFETs, and diodes.

The switch signal generator is usually a chip containing a flip-flop, a comparator to sense the feedback, a soft-start circuit to protect the MOSFETs from being overdriven before the output voltage builds up, and shutdown circuitry in case of an overload.

#### Troubleshooting Strategy

When there is no output voltage, begin the process of troubleshooting by observing the waveshape at the gates of the MOSFETs.

As indicated on the chart in Figure 4, the result of this test divides the power supply into two parts and confines further testing to one-half of the circuits. If you find any waveshape at the gates when the output is zero, it is likely to be very distorted from the normal because the regulator will be straining to increase the output voltage.

The presence of any signal at the gates indicates that the input rectifier and the switch signal generator are probably working fine. This leads to a check of the DC voltage across the damper diode. A DC meter will not read accurately at this point because of the

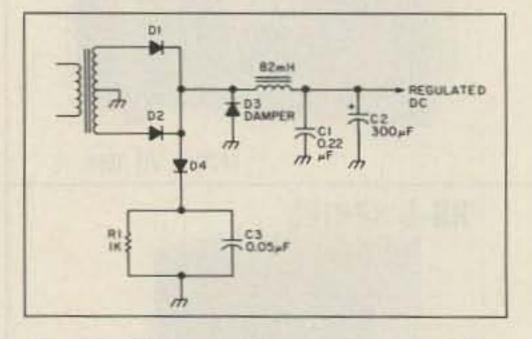


Figure 3. Schematic of the output power rectifier.

presence of an AC component. For most troubleshooting, at this point it is enough to know if DC is present or completely absent, so your meter will do the job. When you find a DC voltage across the damper, and there is no DC output, the chart in Figure 4 suggests three parts that could be defective.

If the damper voltage is missing, a check for the presence of any signal at the secondary of the power switching transformer is in order. As before, at the MOSFET gates, any signal at the secondary will be considered acceptable. The chart indicates three parts to check when there is a signal. And, if the signal is missing, the four possible causes of failure are shown.

"When no output voltage, begin troubleshooting at the gates of the MOSFETs."

The right side of the troubleshooting guide suggests a procedure when there is no signal at the MOSFET gates. It is not necessary to test anything in the power switch

REGISTRATION \*

\$6.00 Advance

(Until March 15th)

\$8.00 at the door

Children under 12 Free!

"C'mon down and enjoy

our Southern Hospitality"

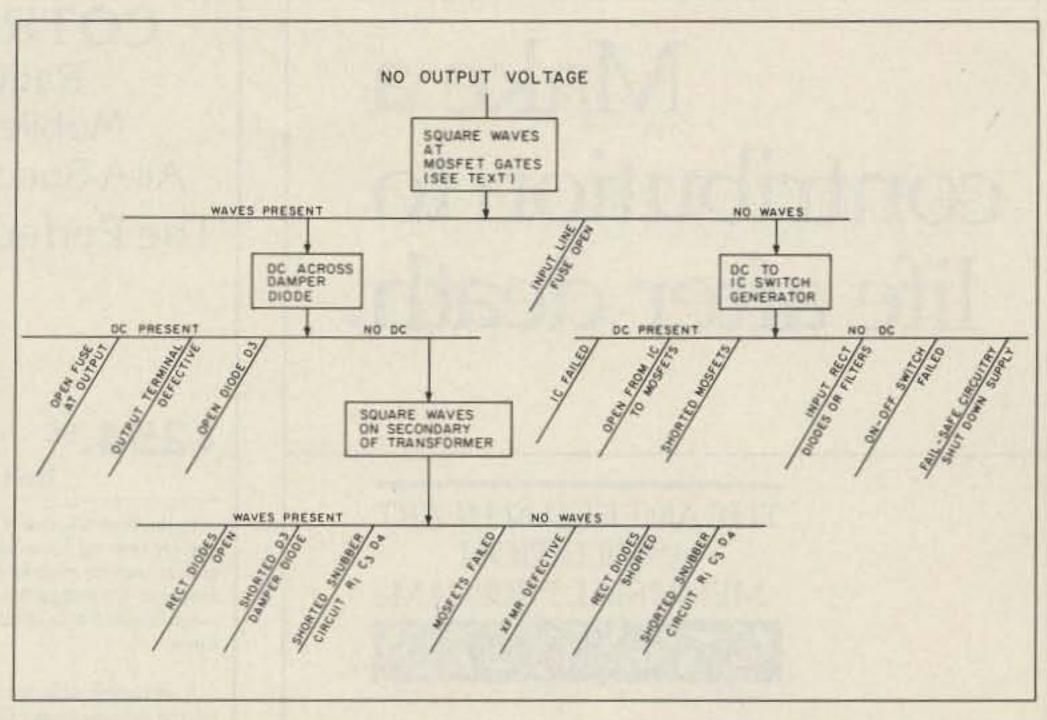


Figure 4. Troubleshooting guide for your switching power supply.

or output rectifier systems. Tests are confined to the input rectifier and the IC, beginning with a check of the input line fuse. This is followed by a test for DC input voltage to the chip.

Often, troubleshooting a switching type power supply is easy because the

high power available leads to charring or total destruction of the components involved in the failure, and it may not be necessary to make many tests. However, even when the failure is not obvious, you can usually trace it quickly with a scope and a DC meter. 73

Build your next vacation around the southland's most popular Hamfest, at the hub of the greatest entertainment and activity center in the east.

#### Hamcation only minutes away from Florida's main attractions!

- \* Disney World \* EPCOT Center
- ★ Sea World ★ Wet n' Wild ★ Water Mania \* Boardwalk & Baseball
- ★ Church Street Station ★ Gatorland Zoo ★ Church Street Station

#### at ORANGE COUNTY CIVIC CENTER (at INTERSTATE 4, EXIT 29) -

#### ARRL

Northern Florida Section Convention

April 7th, 8th, 9th -1989-

**NOW BIGGER & BETTER** THAN EVER!

- \* FREE PARKING for all vehicles. 24 hour RV sites at nearby campground.
- \* Continuous Forums Saturday and Sunday
- \* FCC EXAMS Sunday at 9:00 am \*FREE Novice Exam - all others \$4.00 Form 610 provided. Register for exams on Saturday. Bring credits and license.

**EXPANDED INDOOR SWAP TABLES** (\$25.00 for all three days) Commercial Exhibit Areas

#### Watch this space for more details next month!

For General Information & Tickets - Registrants and Exhibitors contact: Hamcation Information • P.O. Box 547811, Orlando, FL 32854 ORLANDO HAMCATION & COMPUTER SHOW

Sponsored by: Orlando Amateur Radio Club, Inc.


CIRCLE 96 ON READER SERVICE CARD

### Make a contribution to life after death.

THE AMERICAN HEART ASSOCIATION MEMORIAL PROGRAM®

WERE FIGHTING FOR YOUR LIFE

American Heart Association

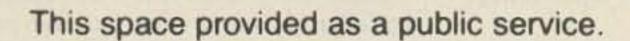

#### COTRONICS OFFERS

Radio Shack's 10 Meter Mobile SSB/CW Transceiver At A Special Introductory Discount The Perfect First Radio for Novices



\$254.95

Regularly \$279.95 (\*supply limited) No tax for out-of-State Residents

Radio Shack's new HTX-100 is the perfect first rig for a beginning Ham and a superb mobile radio for any amateur. It's compact—2 "x 7 x 7 " -yet loaded with most-wanted features.

Pushbutton selectors on the mike permit safe and easy QSY while mobiling and a 10-channel memory stores favorite frequencies. A frontpanel frequency-lock switch prevents accidental frequency changes. You can fine-tune reception with ±1.5 kHz RIT and select 25-watt or 5-watt QRP output. Coverage is 28.0 to 29.6999 MHz, SSB or CW with con-

> Lowest Price Nationwide

venient built-in sidetone and semi break-in keying.

The HTX-100 also has an easy-tosee backlit LCD display, hefty 3-watt audio output, built-in speaker, and rear-panel jack for adding an external speaker. Bracket and DC cord included. The 10-meter fun is just beginning. Be a part of it with this affordable, top-quality transceiver!

#### Cotronics Inc.

Radio Shack Dealer 2200 S.E. Federal Highway Stuart, FL 34994

1-800-848-3004

#### **NOW HEAR THIS**



Phone: (813) 885-6091 Telex: 289-237 (NAVL UR) Fax: (813) 885-3789

CIRCLE 349 ON READER SERVICE CARD

#### DEALERS Sell 73 Amateur Radio

Selling 73 Amateur Radio will make money for you. Consider the facts:

- If you carry 73 Amateur Radio it will increase your store traffic-and our dealers tell us that 73 is the hottest selling amateur radio magazine on the newsstands today.
- Increased store traffic means increased sales for you. Hams will come into your store to pick up the latest 73 and end up buying the latest all-band, all-mode transceiver (or at least a few feet of coax).
- 73 Amateur Radio guarantees each issue you pay only for the copies that you sell. We pay for all shipping.

For information on selling 73 Amateur Radio, call Peter Murphy at 800-722-7790, or write to 73 Amateur Radio, WGE Center, Peterborough, NH 03458.



WGE Center, Peterborough, NH 03458 800-722-7790

5417 Jet View Circle, Tampa, Florida 33634

ATV

#### Ham Television

Mike Stone WB@QCD PO Box H Lowden IA 52255

#### 75 Meter USATVS Net

Old man winter has arrived, and I hope all you UHFers in TVland got a chance to install your hard-line, mast-mounted preamps and multi-element, highgain antenna arrays before the cold weather hit. If you didn't, now is the time to do it! I also hope you had time to get your 75 meter dipole up in the air, pruned for the 3.871 MHz national ATV user's net hotspot and DX coordinating frequency.

The USATVS sponsored net meets regularly every Tuesday night for about two to three hours, from 8 to 10 p.m. Eastern time. WB8ELK, WA4UMU, WB0ZJP, and WB@QCD usually handle net control duties. Many ATVers use this HF frequency on week days, as well as on the weekends at night and in the early morning, during the best hours for band enhancement. So far, all states except California check in.

AA0P, WB0CZI, and the new Denver, Colorado, ATV troops talk cross-country into the lowa BRATS, Indiana and Ohio ATCO group areas, while WA2OSW, W2RPO, and others in New York talk with W3SST, W3QNI, WA3USG, and the Pennsylvania group. WBØYNH, WA9NJR, and WB@QOX of the 3M Minnesota ATV Club exchange FSTV ideas with K4NHN and WA4UMU of the Palmetto, South Carolina, ATV group. Even W3LGV and W4PLA in the Orlando, Florida, ATV Club have talked about ham TV with WA8AHY, WA8ASH, WB8AMZ, and others in the Michigan area. It's a lot of fun keeping in touch with other ATV groups/clubs on a weekly schedule. The USA is finally uniting in the sharing of ideas and opinions, and helping to solve problems by coordinating on frequencies to work each other on video UHF TV mode.

#### **New AEA FSTV-430** Transceiver

As hinted at in previous columns, a major amateur radio manufacturer has come out with a product in a new line of fast scan

television gear. Advanced Electronics Applications, Inc., of Lynnwood, Washington, unveiled their new FSTV-430 model UHF 70 cm transceiver last September at the Virginia Beach, Virginia, and Portland, Oregon (National ARRL Conference), hamfests. I have known about this development since Dayton in April, but Mike Forsyth and Mike Lamb of AEA asked me to keep a lid on the information. It was tough to do, and a few who saw the smile on my face at local hamfests figured something was up.

No doubt Kenwood and ICOM will be watching the sales of this new piece of AEA gear, as they have already begun asking amateurs if they own a camera and VCR or not. Hopefully, AEA's introduction of reasonably priced, straightforward, and simple to operate fast scan TV equipment is the beginning of a new surge of interest in a mode that has yet to reach its prime in the ham world. This competition also forces existing ATV manufacturers to become more responsive to customers' needs. That has been a sought-after condition in ATV for a long, long time!

AEA's new FSTV-430 ATV transceiver is a crystal-controlled transmit and receive system. Two channels are available. The unit comes stocked with the popular 439.250 MHz national ATV calling and operating frequency. I wrote to AEA to ask them to take a second look at producing a tunable downconverter receive system, since many ATVers (especially DXers) monitor more than just one UHF frequency. Many also need to check both ends of the 70 cm band for the more than one hundred 421.250 MHz ATV repeaters in the country.

The unit comes standard with a 4.5 MHz FM audio subcarrier offset, and all the usual camera video and audio input connections. RF output power is 1 watt AM. Higher power amplifiers are readily available from Mirage, Tokyo Systems, Alinco, and others, to boost power from the new AEA exciter to a 20 or 50 watt level. I have asked to do 73 Magazine and Spec-Com Journal reviews on this new product. By the time this column appears, the first finished models should be in the

stores. Look for this hot, new item at Dayton in 1989. The October issue of QST and the November/ December issue of The Spec-Com Journal 1988 carried the first information, with pictures, on the AEA FSTV-430 rig. Thank AEA for this new addition to an already impressive line of digital components! Who will be the first on your block to own one?

#### For Info On . . .

For Slot antenna information, contact Merle Reynolds W9DNT of Moline, Illinois, and Gerald Cromer K4NHN of Cayce, South Carolina.

Pauldon Associates (W2WHK, 210 Utica Street, Tonawanda NY 14150; 716-692-5451) has some interesting 400, 900, and 1200 MHz bricks, preamps, exciters, switchers, and power modules. We have one of their 10 watt amplifiers on our BRATS 910.25 MHz weather radar transmitter running twenty-four hours a day, and it works great! Send an SASE for a catalog of their products.

Rutland Arrays now has a new broadband, high-gain ATV modified K1FO 22-element 70 cm yagi antenna for \$88.95. Contact Tom at 1703 Warren Street, New Cumberland PA 17070.

Don and Sue Miller of Wyman Research, PO Box 95, Waldron IN 46182, are promoting FM TV gear, and a new on-carrier sound TV receive module adapter for \$90.

#### Welcome ATV Mode Newcomers

As AEA begins selling their new FSTV product, hundreds and hopefully thousands of new ATVers will be getting on the 70 cm band! AEA is counting on new ATV purchasers, not those already on ham TV. Most sales will hopefully be generated from this area. I agree with that. Therefore, to help AEA and 73 Magazine, in the next issue of this column, I will begin a series of "newcomer" ATV articles. This might be a bit boring for you old-timers, so please be patient in your future reading. We need to go over ATV basics-how to get started, antennas and feedlines, and so forth, for the benefit of those who are just getting involved with ham TV. The future of this mode depends on it! 73

#### **AMATEUR TELEVISION**

#### **NOVICES: NOW YOU CAN TRANSMIT VIDEO WITH OUR NEW TX23-1**

Did you know that you as well as all classes of licensed amateurs can easily transmit live action color and sound video just like broadcast TV with our TX23-1 transmitter. Use any home TV camera and/ or VCR, computer, etc. by plugging the composite video and audio into the front 10 pin or rear phono jacks. Call or write now for our complete ATV catalog including downconverters, transceivers, linear amps, and antennas for the 70, 33, & 23cm bands.



Only \$299

Designed and built in the USA Value + Quality from over 25 years in ATV...W6ORG

TX23-1 one watt ATV transmitter crystaled for 1289.25 MHz runs on 12-14 Vdc @ .5A. PTL T/R switching. 7x7x2.5". TVC-12G Downconverter \$109. Transmitters sold only to licensed amateurs for legal purposes verified in the latest Callbook or with copy of license sent with order.

(818) 447-4565 m-f 8am-5:30pm pst. P.C. ELECTRONICS

2522 Paxson Ln Arcadia CA 91006

Visa, MC, COD

Tom (W6ORG) Maryann (WB6YSS)

### 73 Book Review

## The 1934 Official Short Wave Radio Manual

Gernsback classic reprinted for old-timers and young squirts alike.

Reviewed by Douglas Stivison NR1A

Lindsay Publications, Inc. Box 12 Bradley, IL 60915-0012 (815) 468-3668 \$14.95 (plus 75¢ shipping) 260 pages, paperback

The "Never Say Die" column has often lamented that, for many of us, the hobby just isn't as much fun as it used to be. Something very special was lost when we abandoned our home-brew rigs and tinkering skills in favor of the vastly superior performance of today's mass produced, high-performance transceivers. Certainly we gained mind-boggling performance, but somehow we lost our innocence in the process. And we lost the magic, the excitement, and the romance that always accompanies innocence.

Today we routinely fill our logbooks with 5-9 reports from the far corners of the world, but somehow the romance is gone. If we ourselves have forgotten the excitement and the magic of radio, it is no wonder that we can't convey these feelings to the next generation, and why we cannot attract newcomers to our ranks.

#### "Radio" Was Synonymous with Adventure

In the 1930s, however, things were entirely different, and the very word "radio" was synonymous with adventure and the call of faraway places. Technology was a lot simpler then and much more approachable. Time was plentiful, and if cash was hard to come by, there was no lack of ingenuity and scrounging to take over where the pocketbook left off.

Certainly no individual was a more powerful force behind the popularization of radio than Hugo Gernsback. In a variety of magazines, books, and contests, he not only showcased the excitement and romance of the burgeoning science, but he pioneered a style of nitty-gritty, how-to-do-it articles that have never been surpassed for their clarity or completeness. Circuits appearing in any Gernsback book were meant to be duplicated, and just about every radio tinkerer of the era had built at least one radio out of a Gernsback book.

Gernsback became better known for his publication of "pulp" science fiction, and to this day, the highest award a science fiction writer can win is the prestigious "Hugo" award named in his honor. But to a generation of radio amateurs, the Gernsback name is associated with a plethora of radio magazines. And of this range, Radio Craft and later Short Wave Craft were among the most enduring.

#### Hugo Gernsback's Classic

Lindsay Publications has come out with a reprint of Gernsback's classic 1934 Official Short Wave Radio Manual: Complete Experiments, Set Building, and Servicing Guide. No longer is this gem just for the cognoscente able to pay the auction price at collectors' meets. No, today everyone can afford this fascinating and fully illustrated book.

"We routinely fill our logbooks with 5-9 reports from the far corners of the world, but somehow the romance is gone."

The work was originally put out under Gernsback's Short Wave Craft label and it contains over 250 pages of classic how-to-do-it articles for a host of early radio projects. Everything, from one-tube regen receivers to 5 meter transmitters and receivers, is covered. Here are "portable" radios that look like they outweigh a typical Toyota.

This book is a road map through the lost world of grid leaks and tickler coils. It is like a time capsule, made when the hobby was going through one of its most exciting eras. There are also about a hundred schematics of the most popular commercial radios of the day, including such immortals as the Pilot Super-Wasp, the National NC-5 "Thrill Box" and the Hammarlund "Comet."

There are also some intriguing feature articles, including one by the late Don Wallace W6AM on improving antenna performance, and one by the legendary John Reinartz titled "A Receiver That Laughs at Static."

#### Not Just Nostalgia

But the book is much more than just a stroll down memory lane. Publisher T.J. Lindsay augments this reprint with a final chapter of totally new material, showing how to adapt the classic circuits in the book to construction using modern semiconductors for the original expensive and hard-to-find tubes. The book then becomes a hands-on build-ityourself book, and I am sure that Gernsback himself would want it this way.

Without any heavy mathematical formulae (that would be totally out of keeping with the seat-of-the-pants tone of the original book), Lindsay lists his own experimentally determined values for modifying biasing components, "grid leaks," and coupling capacitors when substituting JFETs, such as the ubiquitous MPF102, for a wide variety of early triodes, and using dual gate MOSFETs, such as the workhorse 40673, for the popular screen-grid tetrodes.

Lindsay uses bipolar transistors as alternatives to early audio amplifiers. He gives a wealth of information on scrounging parts, and on building breadboards and cabinets to recreate the feel of the old radios...even if they are using modern semiconductors as the active devices. I feel that just this final chapter of seat-of-the-pants experience would justify the price of the book.

This is a great book for nostalgia fans who lived through the radio era of the early 1930s. It is an equally great book for those who were born later, but who are the heirs to the home-brewing and experimenting legacy that this era produced. And with the final chapter on building simple regenerative receivers with a combination of old and new parts, it is a gateway to building a circuit that is not sealed in a chip or wired by a robot on a Japanese assembly line. It is a hands-on guide to using radios that you actually build yourself. In fact, while reading Lindsay's comments on using a grid dipper, I could not help recalling hundreds of classic 73 Magazine how-to-do-it articles by the likes of W6BLZ, W7OE, K5JKX, W1DTY and K1CLL in the 60s and early 70s.

For anyone who might have lost touch with the magic that first attracted them to our hobby, this book is a superb way to get the fires burning again. 73

#### QRZ CONTEST!™

VHF Contest Software for PC Compatibles

- → Now only \$19.95 postage paid
- Covers: ARRL Sprints, VHF QSO Parties, UHF, Jan. Sweepstakes, & the CQ World Wide VHF WPX
- Menu driven and user friendly
- Color and options user configured
- → Grids worked display on-line!
- → Full dupe checking & log editor
- Full cursor control for data entry
- Handles multi-op contest stations
- → Handles 4000 contacts with 256K
- + HF Version available Jan. 1989

ATFAB Computers and Electronics P.O. Box 4766



Maineville, OH 45039 (513) 683-2042






- Accepted

**CIRCLE 357 ON READER SERVICE CARD** 

#### ANTENNA MODELING

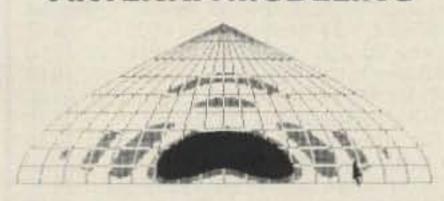

Easy to use, with menus, and optional mouse. Enter parameters, and get a color coded sinusoidal projection of a MW or SW antenna. Move over the projection with a mouse or cursor and read the gain at that point. LONG WIRE PRO models long wires, vee s, dipoles, and rhombics displaying a sinusoidal projection. \$40 VERTICAL PRO models single verticals or arrays displaying a sinusoidal projection, a ground wave plot, and the impedance of each element. \$80

IBM PC compatible, DOS 2.0 or higher, 256K, CGA or EGA color required. International orders add \$5 shipping.



**EPSILON CO** 

Box 715, Trumbull CT, 06611, (203) 261-7694

**CIRCLE 324 ON READER SERVICE CARD** 

#### INTERNATIONAL RADIO AND COMPUTER, INC. ANNOUNCES



It is the newest ICOM dealer in the South East. ★ We stock a complete line of ICOM radios and acces-

- \* We guarantee the reliability of everything we sell with a complete performance and function check.
- ★ We offer complete and efficient service of all our ICOM and other quality products with Factory Service parts.
- ★We have been servicing the amateur radio community for eight years and have 1000's of satisfied customers across the country.

Call us for a quote before you make your next ICOM purchase.

(407) 879-6868

Send for our FREE catalog including KENWOOD, YAESU and our complete line of radio and computer accessories.

> INTERNATIONAL RADIO AND COMPUTERS, INC. 751 South Macedo Blvd. Port St. Lucie, FL 34983

> > **CIRCLE 97 ON READER SERVICE CARD**



#### FREE IBM - PC SOFTWARE CATALOG

- For Hams, Electrical Engineers and Finicky PC
- Hundreds of programs tested to IDS's rigid standards.
- IDS's president is a HAM and hard to please. Only 30% of the programs submitted for testing make it to the catalog.

. He's also a Cheapskate! .

Programs Include:

CW CODE PRACTICE · CONTEST LOG · accurate BEAM HEADINGS • GRAPHIC on-screen-plotting CALCULATORS • CIRCUIT DESIGN AIDS • supertested PROPAGATION FORECASTING • TERMI-NAL EMULATION

NONE OF OUR DISKS COST OVER \$3.95!!

Please send your Name and Address (we would be grateful for \$.65 cash or stamps for postage, but not required) to:

**INTERCON Data Systems** Dept. 7, P.O. Box 696

Gambrills, MD 21054-0696

CIRCLE 358 ON READER SERVICE CARD

### AR-2002 **Owners**

Never buy another fast scan ATV receiver converter! Convert your AR-2002 Professional Monitor Receiver to receive VIDEO on 439.250 MHz, 910.250 MHz through 1289.250 MHz. AM or FM TV with our IF/Detector Modules.

Send SASE for information to:

Bill Trulock—ATV P.O. Box 11254 Fort Wayne, IN 46856

**CIRCLE 94 ON READER SERVICE CARD** 

#### FREE CATALOG!

Features Precision Tools, Tool Kits, Test Equipment



Jensen's new catalog features hard-to-find precision tools, tool kits, tool cases, test equipment and computer accessories used by sophisticated hobbyists, scientists, engineers, laboratories and government agencies. Call or write for your free copy today.

#### JENSEN TOOLS INC.

Dept. 158, 7815 S. 46th St. Phoenix, AZ 85044-5399 (602) 968-6231

**CIRCLE 245 ON READER SERVICE CARD** 

# SHORTWAVE




Build Tesla coils, induction coils, Wimshurst and other lightning bolt generators! Rewind and repair motors! Design and build electrical generators! Get high power from auto alternators! You'll find quality books on these topics and much more!

You'll find plans and info on all types of unusual equipment from lasers to centuryold induction coils! Build equipment your friends haven't even heard off
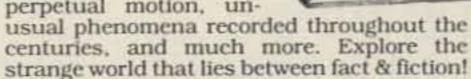
### Fringe

You'll even discover a strange collection of books on "Fringe Science" - lost continents, perpetual motion, un-



**New Catalog!** 


Write for your copy of Lindsay's new Electrical Books catalog and see for yourself what you've been missing! Send \$1.00 (US & Canada) or \$3.00 foreign airmail. We'll send your catalog immediately! Write today!



#### Lindsay's Electrical Books PO Box 12-WB2, Bradley IL 60915

		ne a copy of catalog via first	
Name			
Address			
City	St	Zip	

CIRCLE 138 ON READER SERVICE CARD

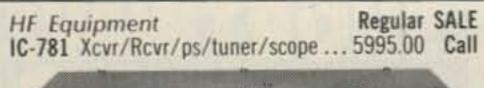




IC-761 Xcvr/Rcvr/ps/tuner	2699.00 2	2369
HM-36 Scanning hand microphone	47.00	
SP-20 Ext. speaker w/audio filter	149.00 1	3999
FL-101 250 Hz 1st IF CW filter	Control Control Control	
FL-53A 250 Hz 2nd IF CW filter	115.00 1	0995
FL-102 6 kHz AM filter		
EX-310 Voice synthesizer	59.00	



IC-751A 9-band xcvr/.1-30 MHz rcvr	1699.00	1469
PS-35 Internal power supply		
FL-32A 500 Hz CW filter (1st IF)		
FL-63A 250 Hz CW filter (1st IF)	59.00	
FL-52A 500 Hz CW filter (2nd IF)	115.00 1	10995
FL-53A 250 Hz CW filter (2nd IF)	115.00 1	10995
FL-33 AM filter	49.00	
FL-70 2.8 kHz wide SSB filter	59.00	
RC-10 External frequency controller	49.00	

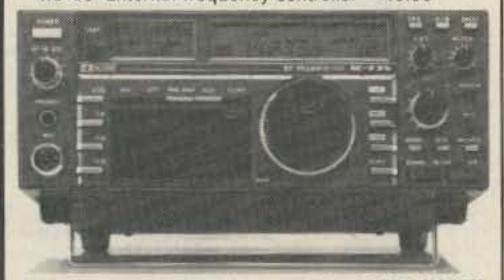

IC-735 HF transceiver/SW rcvr/mic 1	099.00 94995
PS-55 External power supply	219.00 19995
AT-150 Automatic antenna tuner	445.00 36995
FL-32A 500 Hz CW filter	69.00
EX-243 Electronic keyer unit	64.50
UT-30 Tone encoder	18.50
Other Accessories	Regular SALE
IC-2KL 160-15m solid state amp w/ps !	1999.00 1699
PS-15 20A external power supply	175.00 15995
PS-30 Systems p/s w/cord, 6-pin plug	349.00 31995
MB Mobile mount, 735/751A/761A	25.99
SP-3 External speaker	65.00
SP-7 Small external speaker	51.99
CR-64 High stab. ref. xtal for 751A	79.00
PP-1 Speaker/patch	179.00 16495
SM-6 Desk microphone	47.95
SM-8 Desk mic - two cables, Scan	89.00
SM-10 Compressor/graph EQ, 8 pin mic	149.00 13995
AT-100 100W 8-band auto, antenna tuner	445.00 38995
AT-500 500W 9-band auto, antenna tuner	589.00 51995
AH-2 8-band tuner w/mount & whip	659.00 58995
AH-2A Antenna tuner system, only	519.00 44995
	91.95 7995
GC-5 World clock	31.33 /3

\* Large Stocks \* Fast Service **★ Top Trades** at AES®

VHF/UHF base multi-modes Regular SALE
IC-275A 25W 2m FM/SSB/CW w/ps 1299.00 1069
IC-275H 100W 2m FM/SSB/CW 1399.00 1129
IC-375A 25W 220 FM/SSB/CW (c/o) 1399.00 89995
IC-475A 25W 440 FM/SSB/CW w/ps 1399.00 1099
IC-475H 75W 440 FM/SSB/CW 1599.00 1289
IC-575A 25W 6/10m xcvr w/ps 1399.00 1129
IC-575H 100W 6/10m xcvr
IC-471H 75W 430-450MHz base (c/o) 1399.00 98995
PS-35 Internal power supply 219.00 19995
AG-35 Mast mounted preamp 99.95
AG-35 (Purchased with IC-471H) 99.95 995
SM-6 Desk microphone 47.95
EX-310 Voice synthesizer 59.00
TS-32 CommSpec encode/decoder 59.95
UT-15 Encoder/decoder interface 34.00
UT-15S UT-15S w/TS-32 installed 96.00
VHF/UHF/1.2 GHz Mobiles Regular SALE
IC-37A 25w 220 FM/TTP mic (c/o) 499.00 34995
IC-47A 25w 440 FM/TTP mic (c/o) 549.00 39995
PS-45 Compact 8A power supply 145.00 13495
UT-16/EX-388 Voice synthesizer 34.99
SP-10 Slim-line external speaker 35.99
IC-28A 25W 2m FM, TTP mic 469.00 40995
IC-28H 45W 2m FM, TTP mic 499.00 43995
IC-38A 25W 220 FM, TTP mic 489.00 34995
IC-48A 25W 440-450 FM, regular mic 459.00 36995
IC-48A 25W 440-450 FM, TTP mic 509.00 44995
HM-14 Extra TTP microphone 59.00
UT-28 Digital code squelch 39.50
UT-29 Tone squelch decoder 46.00
HM-16 Speaker/microphone 34.00
IC-228A 25W 2m FM/TTP scan mic 509.00 44995
IC-228H 45W 2m FM/TTP scan mic 539.00 47995
UT-40 Pocket beep function 45.00
IC-900A Transceiver controller 639.00 56995
+ Dackage Special

#### \* Package Special . . .

IC-900A Transceiver controller with UX-29H 2m/45W and UX-39A 220/25W band units.

#### \$96995

HV 104 10- 10W band and	200.00	20095
UX-19A 10m 10W band unit	299.00	
UX-29A 2m 25W band unit	299.00	
UX-29H 2m 45W band unit	349.00	31995
UX-39A 220MHz 25W band unit	349.00	28995
UX-49A 440MHz 25W band unit	349.00	
UX-59A 6m 10W unit	349.00	
UX-129A 1.2GHz 10W band unit	549.00	49995
IC-1200A 10W 1.2GHz FM Mobile	699.00	54995
IC-3200A 25W 2m/440 FM/TTP (c/o)	695.00	49995
UT-23 Voice synthesizer	34.99	
IC-3210A 25w 2m/440 FM/TTP	739.00	64995
AH-32 2m/440 Dual Band antenna	39.00	
AHB-32 Trunk-lip mount	35.00	
Larsen PO-K Roof mount	20.00	
Larsen PO-TLM Trunk-lip mount		
Larsen PO-MM Magnetic mount	22.00	
RP-1210 1.2GHz 10W 99 ch FM xcvr	1529.00	1349
RP-2210 220MHz 25W repeater	1649.00	1469
RP-3010 440MHz 10W FM repeater		
Due to the size of the ICOM product line, s	ome acc	essory

items are not listed. If you have a question, please call. All prices shown are subject to change without notice.



#### VISA'

Hand-helds	Regular SALE 289.00 25995
IC-2AT with TTP	319.00 27995
THE REPORT OF THE PROPERTY OF THE PARTY OF T	
	369.00 299 <sup>95</sup> 429.00 379 <sup>95</sup>
IC w2A for 2m a	Control of the Party of the Par
	IC-2A 2-meters IC-2AT with ITP IC-3AT 220/TTP (c/o) IC-4AT 440 MHz, TTP IC-02AT/High Power IC-03AT for 220 MHz IC-04AT for 440 MHz IC-u2AT for 2m w/TTP IC-u4AT 440 MHz, TTP IC-2GAT for 2m, TTP IC-4GAT 440MHz, TTP IC-32AT 2m/440MHz

IC-u2A for 2m w/o TTP Reg. \$299 - Closeout \$24995

neg. \$255 - Closeout \$245**
IC-12AT 1W 1.2GHz FM HT/batt/cgr/TTP 473.00 36995
IC-12GAT Dix 1/7W 1.2GHz FM HT/TTP 529.00 46995
Aircraft band handhelds Regular SALE
Aircraft band handhelds Regular SALE A-2 5W PEP synth, aircraft HT 525.00 47995
A-20 Synth. aircraft HT w/VOR 625.00 56995
Accessories for all except micros Regular
BP-7 425mah/13.2V Nicad Pak - use BC-35 79.00
BP-8 800mah/8.4V Nicad Pak - use BC-35 79.00
BC-35 Drop in desk charger for all batteries 79.00
BC-16U Wall charger for BP7/BP8
LC-11 Vinyl case for Dlx using BP-3 20.50
LC-14 Vinyl case for Dlx using BP-7/8 20.50
LC-02AT Leather case for Dlx models w/BP-7/8 54.50
Accessories for IC and IC-O series Regular
BP-2 425mah/7.2V Nicad Pak - use BC35 49.00
BP-3 Extra Std. 250 mah/8.4V Nicad Pak 39.50
BP-4 Alkaline battery case
BP-5 425mah/10.8V Nicad Pak - use BC35 65.00
CA-5 5/8-wave telescoping 2m antenna 19.95
CP-1 Cig. lighter plug/cord for BP3 or Dlx 13.65
CP-10 Battery separation cable w/clip 22.50
DC-1 DC operation pak for standard models 24.50
MB-16D Mobile mtg. bkt for all HTs 25.99
LC-2AT Leather case for standard models 54.50
RB-1 Vinyl waterproof radio bag
HM-9 Speaker microphone
HS-10 Boom microphone/headset
HS-10SA Vox unit for HS-10 & Deluxe only 24.50
HS-10SB PTT unit for HS-10 24.50
SS-32SMP Commspec 32-tone encoder 27.95
For other HT Accessories not listed please CALL
Receivers Regular SALE
R-71A 100kHz to 30MHz receiver \$999.00 86995
RC-11 Infrared remote controller 70.99
FL-32A 500 Hz CW filter 69.00
FL-63A 250 Hz CW filter (1st IF) 59.00
FL-44A SSB filter (2nd IF) 178.00 15995
EX-257 FM unit
EX-310 Voice synthesizer 59.00
CR-64 High stability oscillator xtal 79.00
SP-3 External speaker 65.00
CK-70 (EX-299) 12V DC option 12.99
MB-12 Mobile mount 25.99
R-7000 25MHz to 2GHz scan rcvr 1199.00 1049
RC-12 Infrared remote controller 70.99
EX-310 Voice synthesizer 59.00
TV-R7000 ATV unit
AH-7000 Radiating antenna 99.00 (16)

#### HOURS • Mon. thru Fri. 9-5:30; Sat. 9-3

Milwaukee WATS line: 1-800-558-0411 answered evenings until 8:00 pm Monday thru Thursday. WATS lines are for Quotes & Ordering only, use Regular line for other Info & Service dept.

Order Toll Free: 1-800-558-0411 In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195

### EUR ELECTRONIC SUPPL

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 ● Phone (414) 442-4200

**AES® BRANCH STORES** 

**Associate Store** 

WICKLIFFE, Ohio 44092 28940 Euclid Avenue Phone (216) 585-7388 Ohio WATS 1-800-362-0290 Outside 1-800-321-3594

ORLANDO, Fla. 32803 621 Commonwealth Ave. Phone (407) 894-3238 Fla. WATS 1-800-432-9424 Outside 1-800-327-1917

CLEARWATER, Fla. 34625 LAS VEGAS, Nev. 89106 CHICAGO, Illinois 60630 1898 Drew Street Phone (813) 461-4267 No In-State WATS

No In-State WATS No Nationwide WATS

Outside 1-800-634-6227

1072 N. Rancho Drive

Phone (702) 647-3114

**ERICKSON COMMUNICATIONS** 5456 N. Milwaukee Avenue Phone (312) 631-5181

Outside 1-800-621-5802





### VISA (D) ICOM





FEATURING W2DRZ 902 MHz TRANSVERTER. NOW ONLY \$299 FREE WITH PURCHASE 140 MHz 3W AtTENUATOR A \$49 VALUE DEALER INQUIRIES INVITED ICOM, AEA, LARSEN, VAN GORDEN, VIBROPLEX, NYE-VIKING, FALCON COMM, LEADING EDGE, ARRL PUBLICATIONS, KAGLO, HAMTRONICS, PROWRITER, **ELEPHANT DISKS, DEBCO, TRIONYX** 

915 North Main Street Jamestown, New York 14701 Western New York's finest amatuar radio dealer.

PH. (716)664-6345

CIRCLE 298 ON READER SERVICE CARD

### BATTERIES

Nickel-Cadmium, Alkaline, Lithium, Etc. INDUSTRIAL QUALITY

#### YOU NEED BATTERIES? WE'VE GOT BATTERIES!

CALL US FOR FREE CATALOG



E.H.YOST & CO.

EVERETT H. YOST KB9X1 7344 TETIVA RD. SAUK CITY, WI 53583 ASK FOR FREE CATALOG

(608) 643-3194

CIRCLE 112 ON READER SERVICE CARD

#### N6KW QSL Cards

The finest QSL Cards at reasonable prices. Basic cards, map cards, cartoon cards, photo cards and more. Your idea converted to ink, or use standard designs. 525 ink colors, any type of card stock. Photos in b/w or beautiful color. Have a card that fits your style. Call or write for free samples and details. Postage appreciated.

> Chuck Miller N6KW KW Litho - Dept. 73 P.O. Box 17390 Ft. Worth, TX 76102 (817) 332-3658

#### RAISED PRINT QSL CARDS

From Dennis, WA5QMM Offset Printed - High Quality Nothing like it anywhere! You can actually FEEL the type! 17 beautiful designs including a Full-Color Eagle.


For Free samples & Info. call (318) 443-7261

Network QSL's - P.O.B. 13200 - Alexandria, LA 71315-3200

CIRCLE 114 ON READER SERVICE CARD

#### SYNTHESIZED SIGNAL GENERATOR

MADE IN USA

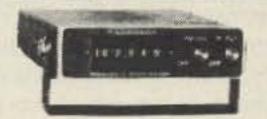

MODEL SG-100F \$429.95 delivered

. Covers 100 MHz to 199,999 MHz in 1 kHz steps with thumbwheel dial . Accuracy +/- 1 part per 10 million at all frequencies . Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate . External FM input accepts tones or voice . Spurs and noise at least 60 dB below carrier . Output adjustable from 5-500 mV at 50 Ohms • Operates on 12 Vdc @ 1/2 Amp • Available for immediate delivery \* \$429.95 delivered \* Add-on accessories available to extend freq range, add infinite resolution, AM, and a precision 120 dB attenuator . Call or write for details . Phone in your order as fast COD shipment.

#### VANGUARD LABS

196-23 Jamaica Ave., Hollis, NY 11423 Phone: (718) 468-2720 Mon.-Thurs.

**CIRCLE 79 ON READER SERVICE CARD** 

#### Multiband QRV Dipole/V/Sloper

Ready to Use Fastest Install Coax Feed 2500 V Insul

Tough Flexible Kink-Proof

Full Legal Power No Lossy Traps Low Noise Never Corrodes

QRV- \$49.95 Includes 52 page Tech Manual.

QRV-760-10 \$59.95 Add \$5 Post & Handling.

Infopack \$1 by 1st class mail. Box 50062-S. Provo, UT 84605

**AntennasWest** H801) 373-8425

CIRCLE 236 ON READER SERVICE CARD

#### \* OMAR ELECTRONICS \*

FOR ALL YOUR AMATEUR NEEDS SPECIAL PRICES on all

MFJ PRODUCTS \* A.R.R.L. PUBLICATIONS and other Ham Radio equipment!

404-466-3241



OMAR ELECTRONICS • Omar Pupo WASFON

RTE 1 HIGHWAY 81 SO. • LOGANVILLE, GA 30249

CIRCLE 292 ON READER SERVICE CARD

JERROLD, HAMLIN, OAK AND OTHER FAMOUS MANUFACTURERS

- FINEST WARRANTY PROGRAM AVAILABLE
- . LOWEST RETAIL/WHOLESALE PRICES IN U.S. ORDERS SHIPPED FROM STOCK WITHIN 24 HOURS

FOR FREE CATALOG ONLY 1-800-345-8927 FOR ALL INFORMATION 1-818-716-5914



PACIFIC CABLE CO. INC. 73251/2 RESEDA BLVD DEPT 1823 RESEDA, CA 91335

**CIRCLE 178 ON READER SERVICE CARD** 



### TEST INSTRUMENTS & **HARD-TO-FIND TOOLS**

Packed with over 5,000 quality products for testing, repairing, and assembling electronic equipment. A full selection of test instruments, power protection equipment, precision hand tools, tool kits, soldering supplies, and much more. Products are shown in full color with detailed descriptions and pricing. All products come with a 100% satisfaction guarantee. SAME-DAY shipment program.

In a hurry to receive your catalog?

Call (800) 225-5370 In Massachusetts call (508) 682-2000

Contact East, Inc., Dept. R433 P.O. Box 786, No. Andover, MA 01845

CIRCLE 334 ON READER SERVICE CARD

#### PACKET MAPS

Finally an easy way to determine the best digipeater path to distant PBBS or packet stations. Several call area maps (up to 5) for 145.01, 145.03, 145.05, 145.07, and 145.09 MHz for any U.S. call area.

\$5.00 per call area

Specify call area(s) desired and send check or money order to:

> **Packet Products** 1 Great Hill Way Eliot, ME 03903

**CIRCLE 366 ON READER SERVICE CARD** 

#### WHEN DOES ONE EQUAL TWO? WHEN IT'S A TAD M8 FM TRANSCEIVER COMMERCIAL & AMATEUR BANDS IN ONE UNIT





430-480 mHz

- Ideal for MARS, Vol. Fire,
- EMT, B'cast RPU, Police, etc. Fully Field Programmable
- 99 Channels
- True 40 Watt Power
- Extremely Rugged
- Multi Function LCD display Frequency Range 138-174 or
- FCC & DOC type accept.
- Low Cost DTMF mike avail. Overnight Shipping Available
- · Shipped Complete w/Mike, Mobile Slide Mount & Power Cable
- · Base Station P.S.; mobile Antennas etc. in Stock



AXM Incorporated 11791 Loara St. Garden Grove, CA 92640-2321

Write or Call 714-638-8807 for immediate information

CIRCLE 243 ON READER SERVICE CARD

### NEW USES FOR OLD METERS

#### Have the meter measure what you want it to.

by John R. Somers KC3YB

R ecently, while I was assembling parts for a power supply I was building, I found I had everything I needed in my junk box except a suitable meter. While I had no shortage of meters of all shapes and sizes, I had nothing that would give me the right full-scale reading.

Inspecting the meter faces, I discovered many of them had, in addition to the scale markings, identification as to the type of movement they contained. Unfortunately, there seemed to be little standardization. Some of the meters indicated the amount of current required to give a full-scale indication, such as 0-1 mA, while others rated the movement in a certain number of ohms per volt. None of this seemed to have anything to do with the original function of the meter.

#### Meter Discoveries

With a little thinking about that most basic of formulae—Ohm's Law—I realized the current rating of the meter movement and the ohms-per-volt rating are intimately related. One is merely the reciprocal of the other! The number 1 divided by the full-scale current will result in the ohms-per-volt rating, and vice versa.

I then recalled that the value of a very low resistance shunted across the meter determines the range of an ammeter. A voltmeter has a much higher resistance in series with the meter for the same reason. This seemed simple enough until I realized the internal resistance of the meter would, in either case, be part of the circuit. Before I could determine the required resistance of either a shunt or multiplier, I was going to have to know the internal resistance of the meter. A quick check with an ohmmeter convinced me I was likely to burn up the internal workings of the meter before I could determine its resistance. How, then, was I going to do it?

#### A Full-Scale Meter Reading

To test the meter, I placed it in a circuit containing a battery and a variable resistor

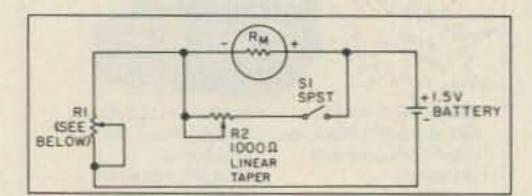


Figure 1. A simple circuit for determining the internal resistance of a meter. R1 is a  $100k\Omega$  linear-taper variable resistor. If full-scale current of the meter is known, the following formula yields greater accuracy:

R1 = 2x battery voltage (Volts) full-scale meter current (Amps) (R1 in Figure 1) that adjusts to limit the current flow to the point at which the meter gives a full-scale reading. I placed a second variable resistor, R2, across the meter to divert part of the current. When the meter reads half-scale, both meter and R2 present the same resistance to the current flow. Removing R2 from the circuit and measuring its resistance reveals the resistance of the meter movement. This is a simple system, complicated only by the fact that some meters have internal shunts or series resistors that must be removed before measuring the meter.

#### Meter Circuits

After selecting a meter that suited my application, I used the formula in Figure 2 to determine the shunt value I needed to add to produce a full-scale reading. Because a meter typically has a low internal resistance, the shunt value will generally be much smaller in value so that most of the current flows through the shunt rather than through the meter. This resistance may be  $0.01\Omega$  or less. A resistor of such a small value may not be easy to get, but you can make a perfectly workable substitute with a length of wire. Table 1 lists a number of common wire gauges and the resistance per foot. You can easily calculate the length of a wire you need to equal a desired resistance.

Remember to keep power-handling capability in mind. This will not generally pose a problem, but be on the safe side. Use the largest gauge wire you can. Although the table refers to bare wire, insulated wire can be used just as well. You can wind a wire shunt around a dowel and solder it to the meter terminals to conserve space.

The voltmeter circuit in Figure 3 uses a series or voltage multiplier resistor to extend the meter's range. In this case, a suitable external resistor will be easier to locate, as it will be many times the internal resistance of the meter. If you can't come up with the exact value you need, combine junk box resistors in whatever manner necessary to produce the desired resistance. In both

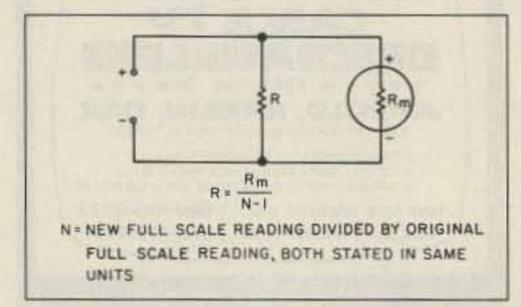


Figure 2. An ammeter circuit, and the formula for determining the shunt value for a meter of known internal resistance.

circuits, meter polarity must be observed.

#### Calibrating Your Meter Circuit

Once you have completed the desired meter circuit, it must be calibrated before it is much good to you. The voltmeter is the easiest to calibrate accurately. Using a variable voltage source, connect the meter in parallel with another voltmeter of known accuracy across the supply. A digital voltmeter works best. As the voltage is adjusted, make light pencil marks on the face. Dry transfer numerals can then be added.

To calibrate the ammeter, place it in a series circuit that contains a known voltage and resistance. If you have a large, adjustable, wire wound power resistor, it will be perfect for the job. Otherwise, you can mix and match a handful of power resistors of various resistances to produce desired amounts of current flow. Make certain your resistors are up to the job.

Throughout this article, I have referred to voltmeters and ammeters. Actually, with proper shunt and multiplier resistances, your surplus meters can display a wide range of current or voltage readings, regardless of the uses for which they were originally designed.

#### References

- 1. Radio Amateurs Handbook, 1967.
- 2. Allied Electronics Data Handbook, 1966.

#### Resistance of Standard Annealed Copper Wire

	1000		
Gauge	Ω per foot	Gauge	Ωperfoot
4	0.0003	18	0.006
6	0.0004	20	0.010
8	0.0006	22	0.016
10	0.001	24	0.026
12	0.002	26	0.041
14	0.003	28	0.065
16	0.004	30	0.103

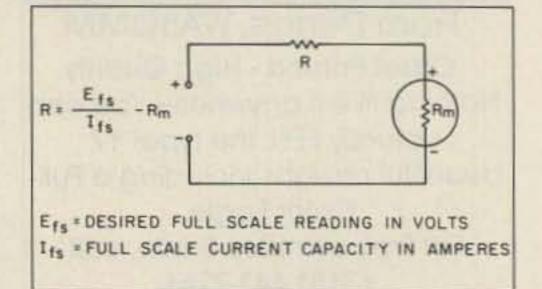


Figure 3. A voltmeter circuit, and the formula for determining the voltage multiplier resistance for a desired meter range.

### RTTYLOOP

#### Amateur Radio Teletype

Marc I. Leavey, M.D. WA3AJR 6 Jenny Lane Baltimore, MD 21208

#### Trying Harder to Be Friendly

Let's begin right off with that traditional, friendly greeting that rings in your ears this season— HAPPY NEW YEAR!

Friendliness is an interesting concept, because this hobby of ours often exhibits two opposite poles of the emotion. Certainly many of us were brought into this hobby by a friend. The tradition of lending a helping hand, teaching each other, and kindling that amateur spirit makes amateur radio a unique hobby.

But often enough, this hobby of ours, with its wires, gizmos, blinking lights, and high-tech talk, can be downright unfriendly and even hostile. The facet of amateur radio that I write about, radioteletype and digital communications, may well be one of the hardest for the newcomer to get to know.

Of course, that's why I have been writing this column. One of my primary goals has been to convert technological gobbledy-gook into easy-to-understand concepts that leave the newcomer saying, ''Oh, that's what it means." Long-time readers may even remember my elementary introduction to RTTY many years back, including the "One if a hamburger, Two for fries" signaling scheme to introduce the digital concept.

#### New Digital Communications Book

One of the items that I have wanted to see, and would even write if I had the time, is a basic introduction to digital communication. While I have reviewed several books on this subject, few were comprehensive enough to serve as a solid guide to digital circuits. Now, however, I have a new book in my hands that does appear to serve this function admirably.

The book is Digital Communications With Radio Amateurs. It really is not a book, but "books," which I will explain later. Although it is subtitled, "The Complete Packet Radio Book," it is a rather complete introduction to conventional RTTY and AMTOR as well.

The first chapter introduces you to the history of digital communication, especially packet, with a tip of the hat to our Canadian neighbors who started the ball rolling in that fascinating mode. Digital mode operating privileges for a given license class, and basic equipment, are also covered.

The next chapter investigates the analog and digital worlds, using many diagrams, some descriptions of methods of transmitting RTTY, such as FSK and AFSK. Finally, the book examines ASCII and AMTOR codes, and gives a few simple circuit suggestions for interfacing computers and radios.

Next, the how and why of packet. You will learn every four-letter abbreviation known to the packet world, along with two letters, three letters, and who knows what else. It briefly describes protocols, emphasizing the AX.25 protocol commonly used in amateur circuits.

#### The TNC—Coming Attraction

Of course, in order to run packet, you will need a terminal node controller (TNC), and that is the

"The author (in Digital
Communications With Radio
Amateurs) clearly explains simplex,
half- and full-duplex modes; data rate
transmission in bauds and words per
minute; and synchronous and
asynchronous transmission
schemes."

like those in earlier RTTY Loop columns. Analog and digital data, as well as both serial and parallel transmission, are differentiated.

Other possibly troubling concepts are tackled here as well. The author clearly explains simplex, half- and full-duplex modes; data rate transmission in bauds and words per minute; and synchronous and asynchronous transmission schemes. This chapter concludes with some nuts-and-bolts information, including modem use and RS-232 connector wiring. This eighteen-page chapter is all meat, with no fat or other by-products!

Amateur digital communication comes next, with the initial focus on Morse code. Surprised? Morse code is really the first digital mode in amateur radio! Baudot/Murray code, with familiar diagrams of old-fashioned transmitting distributors, complement the pages at this point, followed by

topic of the next chapter. You can use your personal computer as a dedicated TNC, along with the more common stand-alone TNC. It examines the functions which take place within the TNC, and lists some of the basic types of machines out there to help you select just what you would like to use.

Once you choose a TNC, this chapter will hold your hand while you connect the device to your computer, and begin attempting to contact another station. It gives a bare-bones interface circuit. It is biased towards AEA equipment, but most commands are standardized, and the information should be of help no matter whose TNC you have.

Not all voice QSOs or packets are simple "Hello, Howdy Do" transmissions. The next chapter details the different operating modes, from keyboard through file transfer to bulletin boards, and explores the differences between VHF and HF packet.

#### One Network Better Than Two Packets

While two packet stations are nice, a network is better. Chapter Seven shows how the network concept progressed from the early RTTY days to the digipeater of the packet world. LANs, WANs, and GateWays; trunks, datagrams, and wormholes—they are all covered in a thorough, crystal-clear manner.

One chapter takes a detailed look at the question, "Why can't I use my computer to do all the work?" It gives programming ideas and offers solutions. Again, the AEA bias is present, but anyone can use the material.

"neat stuff" for packet. Whether a program is for the Macintosh computer or a high speed digital modem, this chapter presents some of the latest and greatest for the digital world. The book concludes with amateur satellite communication and tomorrow's technology.

My copy of Digital Communications With Amateur Radio is earmarked "Special AEA Edition," with a forward by Mike Lamb, and is available only from AEA or authorized dealers for \$9.95. A slightly different version, written by Jim Grubbs, minus Mike's forward and with minor changes, is also available at your local Radio Shack store, catalog number 62-1332, for \$6.95.

This book meets the need, which has existed so long, for a widely available introductory text on digital communications. It belongs on every amateur's, and club's, bookshelf.

With the New Year in, let me remind you that I have an index to back issues of RTTY Loop. I try to keep it as up to date as the column, and it is yours for an SASE and postage for two ounces (see above address). Feel free to bug me on Compu-Serve (ppn 75036,2501) and Delphi (username MAR-CWA3AJR) as well. I love hearing from you, and some of the questions I have received lately have sent me scurrying back to my texts!

More in store next month, featuring everything that you want to see, right here in RTTY Loop. 73

### LETTERS

#### From the Hamsack

#### Military Net

I would like to get visibility for the amateur radio operators who are on active duty in the US military so we could institute phone patches within the US or overseas areas where authorized. It would also serve to give recently transferred hams a point of contact in their new area. If you're on active duty and would like to be listed, regardless of branch, please write to:

Robert T. Godlewski HMC 593rd ASG, Box 66 Ft. Lewis WA 98433-5410.

#### New Ham

This letter is from a person who, until a few weeks ago, was completely ignorant about amateur radio. Now, thanks to your magazine and the book Amateur Radio, Super Hobby, by Vince Luciani K2VJ, I am a little smarter.

Though you must write for everyone from beginner to expert, I have enjoyed reading 73. I even found myself enjoying some of the technical articles I didn't understand!

> Mike Sanderson Janesville CA

### RDFing in Chicagoland

RDF has demanded much of my effort for the last 12 of 25 years as a ham. In Chicagoland, there are unsponsored hunts every first and fourth Saturday, attended by a core of dedicated hunters. The second Saturday of each month, the Arlington Communications League sponsors a hunt, and the third Saturday, the Chicago FM Club sponsors a hunt. Once or twice a year on a fifth Saturday, the Greater Chicagoland Foxhunt is run. It pits teams of hunters, usually representing clubs, against one another to find two foxes and win the Trophy. They keep this prize until the next hunt. The Lake County Amateur Radio club of Indiana has been a regular participant, along with the Chicago FM Club.

We would like to involve other organizations in this. RDF does

not require an expensive outlay of exotic equipment. Also, it is not a slow and methodical activity, but perhaps the most physical and fastest paced activity in amateur radio.

I have participated in DX contests, sweepstakes, Field Day, public service events, and packet, but for sheer excitement, I find foxhunting to be my favorite. I would like to see a calendar of regularly scheduled hunts published so local and regional contacts can be made. I intend to contact other groups in the country to get information on their hunts and, if possible participate. This will be on a local level, but could conceivably cover a larger area. Vacations would be ideal for hams to take along some of their gear and participate on a hunt in another part of the country-but first, we need to know where and when the hunts are being held. We have to start this before we can have a National Championship.

> Mike Brost WA9FTS Norridge IL 60656

#### Legalities, Legalities

This refers to the news item about Net-Rom vs Nord Link (Sept. '88 QRX). It is highly likely that in some countries Nord-Link could be charged with violating a copyright. Different countries have different copyright laws, but... Net-Rom is copyrighted under US law.

They say that it is a valid copyright. However, everything connected with packet radio was invented in recent years. So most of the information in their copyright was available from previously copyrighted documents, such as the technical manuals issued with different pieces of equipment. Does Net-Com have releases from all the previously copyrighted material owners giving them the rights to use their copyrights? And where there may be conflicts in the previous copyrights, does Net-Com also have releases from the conflicting copyright owners?

It is impossible to have a copyright in this field that has not used previously copyright items. The words "Packet Radio" were previously used in copyrighted documents. Parts of any circuit must have been previously copyrighted documents. Does anyone have a listing on all this, and releases from all the people involved?

If Nord-Link used this question of whether the Net-Rom copyright is free of any copyright infringement itself, then the courts would probably throw it out.

> Paul J. Franzel New City NY 10956

#### Tasty 73s

I am a Novice, stationed in Iceland with my family, in the Navy. My mother heard me passing 73s over the air and asked me what "73s" were. When I told her, she said she'd been passing 73s for years, with a product both nutritious and delicious. This ice cream is named "73s" because it contains seven ingredients in proportions of three's, as follows:

3 bananas

3 cups milk

3 lemons, juiced

3 cups heavy cream or

3 pints half and half in place of milk and cream

3 oranges, juiced

3 cups sugar

Mash bananas in blender, add juice of lemons and oranges. Add remaining ingredients and stir well. Freeze. For variety, use other fruits instead of bananas. Serves 8–10 regular people or five amateurs on the air.

Bill Smallwood KB2EHK/TF Keflavik, Iceland

#### More Mobile

You asked about my opinion of your magazine. Well, it's the best in its field by far. Next, you asked about what I would like to see in your mag. Your coverage of ham radio is far better than the rest, but I would like very much to see articles about mobile operation, mobile antennas, and antennas that are portable and/or can be used in apartments.

one thinks we have hundred-foot towers and 1500 watts of power on all bands, when in fact we have so many restrictions we're lucky we can operate radio at all. Most people have to live in apartments, condos, or mobile home parks where antennas are not allowed.

I'm sure that you and your staff could cover these topics completely in future magazines. It will probably help your sales, also, which should be tops.

#### Jerry Delettera N5KKR California

Thanks very much for your rave comments! Be on the lookout in the April '89 issue for reviews of several mobile and compact base-station antennas for VHF and HF. Also, there are plenty of these reviews in '87 and '88. Refer to the December issues of 73 for the Annual Index of articles and reviews. Failing that, give us a call and we'll look these up for you...

de NS1B

#### Story of 10-10

Sometime in the 50s, a group of hams got together and started 10-10 International. They required 10 contacts with 10 members as a prerequisite to join the organization. From that point, an individual could upgrade to different awards as he contacted more members. Each contact had to be made on 10 meters. This quickly branched out to local chapters in communities throughout the US and then the world. We are the City of Roses Chapter. To keep activity high, each chapter has awards for contacts with other members on 10 meters.

each week, originating in California, with the intent of upgrading its members and collecting new 10-10 members. Each active local chapter also holds a weekly net for the same purpose. You will find that on any given day, there is a 10-10 net going on somewhere in the country and also throughout the world. Some members have made more than 10,000 10-10 contacts on 10 meters.

With the advent of Novice Enhancement, which for the first time has given voice privileges to Novices on an HF band, we have added a net in the Novice band so that the Novices may join an active group of hams and also join 10-10. 10-10 International and other chapters have done this also. Novices are eligible for any of the awards; there are no restrictions other than the band limitations of their license. All contacts must be made on 10 meters, individually or on nets.

10-10 International has over 50,000 members, and it's growing daily. This camaraderie is probably the single greatest force in preserving this valuable 1.7 MHz bandwidth of the HF spectrum.

Bob McElhatton KF7AK City of Roses Chapter Head Boring OR 97009

### A SIMPLE LED CHECKER

#### Get the bad LED out

by Tom Thompson

Have you ever been in a hurry and needed to test an LED for proper operation or polarity? You look for your DVM, and when you find it, you're not quite sure about what to do with it? If you've experienced this, I have something better, faster, and easier to use, and costs less than \$5.

#### Theory

The theory for testing LEDs is quite simple. Apply the proper voltage, limit the current, insure proper polarity, and the LED comes on! The circuit in Figure 1 does this with a minimum of components. When you press S1, the battery supplies the test current to the LED. R1 is a  $680\Omega$  resistor that limits the current to just a little over 10 mA with a new battery. This allows good test current throughout the life of the battery.

#### Construction

The reprint of the label is the actual size. You can use it to determine the proper spacing of the mounting holes for both the switch and the socket. Use an X-acto knife to remove the area inside the two squares where the socket and switch are mounted. Place the label on the plastic box cover and mark the centers of the two cut-out areas. Once this is done, you can remove the label and drill the two holes. S1 is ¼" and the socket is 5/16" in diameter.

Any transistor socket will work. If you substitute, choose the pins you want to use and drill the mounting hole to the appropriate size.

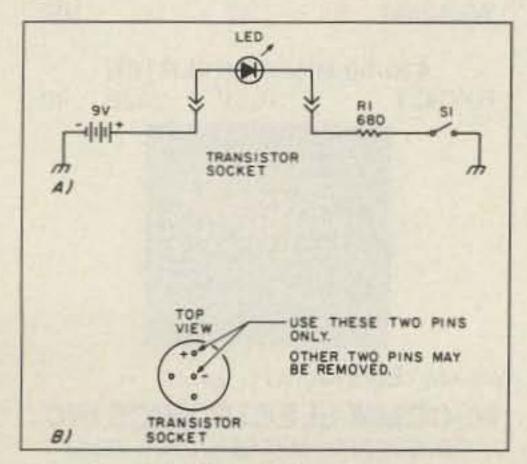


Figure 1. a) The LED Checker schematic. b) Top view of the transistor socket.



Photo A. The LED checker.

The switch is held in place by the mounting hardware that comes with it. The socket is pressure-fit and held in place with a good cement, such as super glue.

Solder the black (-) wire of the battery connector to one side of S1, and solder the red (+) wire to one of the solder contacts on the test socket. Next, solder the  $680\Omega$  resistor between the unused connector on the test socket and S1. (Refer to Figure 1.)

A battery compartment spacer is constructed by cutting two pieces of cardboard %" x 2 ¼" and gluing or taping them together. A small piece is cut off the bottom to allow access to the battery wires (Figure 2).

Cut the label to the correct size and cover the back with rubber cement. This will attach your label securely to the plastic case. Be sure to line up the cut-outs in the label with the socket and S1.

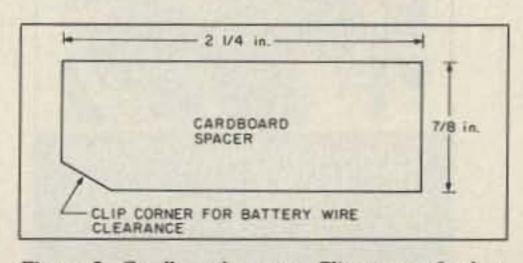


Figure 2. Cardboard spacer. Clip corner for battery wire clearance.

#### Testing

Insert the LED into the socket and press S1. If the LED does not come on the first time, remove it from the test socket, swap the leads, and reinsert it into the test socket. Press S1 again and the LED will come on. If it doesn't, it's defective. To check your tester after construction, it's a good idea to use an LED you believe is good.

There you have it—a useful item to have in the shack, and a real quickie to put together. Have fun! 73

#### Parts List Part Part #, Description 9 Volt battery clip RS270-325 9 Volt battery Standard 9 volt Switch S1 SPST MOM. RS 275-1547 Jim-pak TO-5 Transistor socket Socket, RS 276-548 RS270-221 Plastic case Resistor R1 680Ω RS271-021 1/2 watt Cardboard spacer (%" x 21/4") See Figure 2


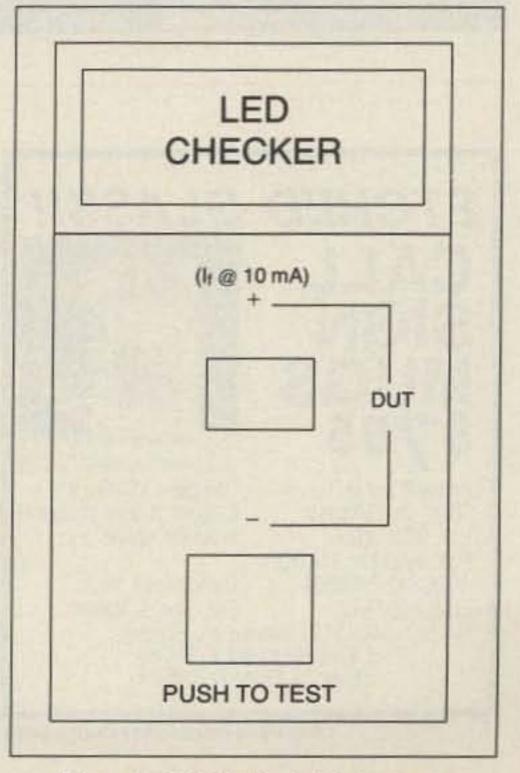


Figure 3. LED Checker label, to cut out.

#### HITACHI SCOPES AT DISCOUNT PRICES

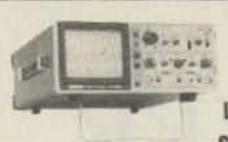

V-212 \$379

List \$560 Save \$181

#### 20MHz Dual Trace Oscilloscope

All Hitachi scopes include probes, schematics and Hitachi's 3 year guaranty on parts and labor. Many accessories available for all scopes.



V-425 \$835 List \$995

40MHz

40MHz

80MHz

V-1065 100MHz

V-1100A 100MHz

V-1150 150MHz

V-223

V-422



 Compact Size List \$1595



\$1,285 - 2mV Sensitivity


400	\$2 (A), 9.00	- DC 10 100M
103	(国会社会社会会)	Dual Chann
		<ul> <li>Delayed Sw</li> </ul>
Section 1	上加速从数	CRT Reador
	MANAGE	. Sweep Time
450	The state of	+ Autoranging
000	100000000000000000000000000000000000000	• Tringer Loc

reep

D.T., 1mV sens, Delayed Sweep, DC Offset, Vert Mode Trigger \$770 \$695 \$75 D.T., 1mV sens, DC Offset Vert Mode Trigger, Alt Mag \$875 \$695 \$180 D.T., 1mV sens, Delayed Sweep, DC Offset, Alt Mag. \$955 \$795 \$160 D.T., 2mV sens, Delayed Sweep, CRT Readout \$990 \$1,195 \$205 D.T., 2mV sens, Delayed Sweep, CRT Readout, Cursor Meas \$1,895 \$1,575 \$320

#### ELENCO PRODUCTS AT DISCOUNT PRICES

#### 20MHz Dual Trace Oscilloscope

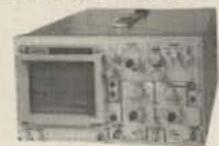

\$349

- MO-1251 \* 6" CRT . Built in
- component tester TV Sync

\$135

True RMS 41/2

Digit Multimeter

05% DC Accuracy

with Freq. Counter

.1% Resistance

and deluxe case

SCOPE PROBES \$19.95 P-1 85MHz, 1x, 10x P-2 100MHz, 1x, 10x \$23.95 with 5 accessories 10 Meg ohm Input

impedance Fits all scopes with BNC connector TL-3 BNC to Minigrapher \$3,49



Digital Capacitance Meter

9 Ranges

1pf-20,000ufd

Zero control

with case

Solderless Breadboards

.5% basic accy

Q.T., 1mV sens, Delayed Sweep, CRT Resdout, DVM, Counter

Q.T., 1mV sens, Delayed Sweep, Cursor Meas, DVM, Counter

35MHz Dual Trace Oscilloscope \$498

MO-1252 . High luminance 6" CRT

. 1mV Sensitivity . 6KV Acceleration Voltage

\$2,295 \$1,995 \$300

\$3,100 \$2,585 \$536

- . 10ns Rise Time
- . X-Y Operation . Z Axis Delayed Triggering Sweep

LC-1800

\$138

Coils 1uH-200H

Caps 1pt-200ut

M-1600

\$25

Res .01-20M

Top quality scopes at a very reasonable price. Contains all desired features. Two 1x, 10x probes, diagrams and manual. Two year guarantee.



9 Functions Memory and Data hold 1/2 % basic acc

31/2 digit LCD AC Clamp-On **Current Adapter** 

> ST-265 \$22 0-1000A AC

most DMM 11% accy

NEW! Bench DMMS

M-3500 M-4500 Works with 31/2 digit \$125 41/2 digit \$175 WEN! Wide Band Signal Generators

RF Freq 100K-450MHz

Variable RF output

AM Modulation of 1KHz

\$119

Capacitance and Transistor Tester \$55 CM-1500A Reads Volts, Ohms,

Multimeter with

Current, Capacitors, Transistors and Diodes with case 50MHz Logic Probe

LP-700 \$23 Logic Pulser LP-600 \$23

31/2 Digit Probe Type DMM

1,100 pins \$15 9434 2,170 pins \$25 9436 SHOWN

2,860 pins \$35 All have color coded posts

CM-1550

\$58.95

31/2 digit LCD 1% DC Accy 10A Scale Auto zero /polarity GF-8016 Function Generator

Freq Counter .1 - 10MHz

Low Cost Multimeter

with Freq. Counter \$239 Sine, Square, Triangle Pulse, Ramp, 2 to 2MHz

GF-8015 without Freq. Meter \$179

#### SG-9500 with Digital Display and 150MHz built-in Freq Ctr \$249 Digital Triple Power Supply



\$249 0-20V at 1A 0-20V at 1A 5V at 5A

XP-765

Fully Regulated, Short circuit protected with 2 Limit Cont., 3 Separate supplies XP-660 with Analog Meters \$175

1 to 1MHz sine, sq wave 20 resistors 47-1M ohm

UPS Shipping: US 5%

(\$10 Max) IL Res., 7% Tax I

WE WILL NOT BE UNDERSOLD!

#### Convenient one hand operation Measures DCV, ACV, Ohms



Audible Continuity check, Data hold

Fully regulated and -5V at 5A short circuit protected XP-575 without meters \$44.95

1245 Rosewood, Deerfield, IL 60015 (800) 292-7711 (312) 541-0710

2-20V at 2A 12V at 1A 5V at 3A

M-1900

with batteries

XP-580

\$59.95

and case


#### Four-Function Frequency Counters TO ALLEGE PARTY OF

F-1000 1.2GH \$259 F-100 120MH

9550 7.50

Frequency, Period, Totalize, Self Check with High Stabilized Crystal Oven Oscillator, 8 digit LED display

#### NEW!

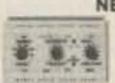

"GREAT IDEA" FUNCTION BLOX FOR EASY BREADBOARDING All blox interlock to make your design work a snap. You can change the configuration

FUNCTION GENERATOR RESISTOR DECADE BLOX CAPACITOR DECADE BLOX DIGITAL CLOCK BLOX





POWER BLOX 5V at 1A -5 at .4A

22.95 LOGIC PROBE BLOX 4 logic level ind.

15 Day Money Back Guarantee 2 Year Warranty WRITE FOR FREE CATALOG

**CIRCLE 356 ON READER SERVICE CARD** 

### **ETCHED GLASS!!**

# SIGN

Checks Payable To: TODD W. SKOGEN P.O. BOX 3025 FOX VALLEY STATION AURORA, IL 60504 (312) 805-5972



Company LOGOs & Custom Orders Welcome Write for Quote

Clearly Print Your Call Sign & Name

Add \$2.50 Shipping and Handling III. Residents Add 6.75% tax Allow 1-2 Weeks for Delivery

CIRCLE 268 ON READER SERVICE CARD

#### PC Slow Scan \$149.95

A complete slow scan television station for your IBM PC or compatible. Send and receive images in up to 10 shades of gray depending upon your graphics card and printer.

Includes: Demodulator

Modulator 75 Page Manual **Tutorial Cassette** 

Software Requires:

Ham transceiver PC with 640K Parallel Port Graphics Card Tape Recorder Serial port Slow Scan Formats: 8,12,17,23,34,36,48,72 sec.



Software Systems Consulting 1303 S. Olá Vista San Clemente, CA 92672 (714) 498-5784

CIRCLE 244 ON READER SERVICE CARD

#### SATELLITE ENTHUSIASTS!

We are pleased to announce the SAT TRAC II - a completely self-contained automatic satellite tracking controler which drives all popular azimuth and elevation rotors. This unit stands alone.

SAT TRAC II uses satellite and station data along with time to calculate the satellite position and antenna pointing angle in real time. This information is then used to control antenna rotors.



Satellite Tracking Made Easy

For more information, call or write to:

Applied Digital Research, Inc. P.O. Box 10184 Sarasota, FL 34232 (813) 378-3410

**CIRCLE 328 ON READER SERVICE CARD** 

#### LOGWRITE"

Are you tired of wasting your time and money on sub-par logging programs? Bring your station into the computer age with LOGWRITE, the quality menu driven, user friendly logging program written by Ed Troy (NG3V). LOGWRITE is the perfect accessory for the complete ham station. It simplifies your operation and gives you the competitive edge in contesting and DXing. LOGWRITE works with all IBM PCs and compatibles.

LOGWRITE's unique split screen feature allows for simultaneous logging and text processing. Logging features include:

- -Instant callsign or prefix search
- -Print, Edit, or View records

 Plenty of room for notes & addresses -Automatic time/date stamping Text processor features automatic word wrap, backspace cor-

rect, and scrolling. Throw away your pen and paper! To order your copy of LOGWRITE, complete with instruction manual, send \$24.95 (Pa. residents add \$1.50 sales tax) to:

Aerospace Consulting P.O. Box 156, Gwynedd, Pa. 19436

30 day money-back guarantee Or call 1 (800) 345-4156 ext. 54 to order with Visa/ Mastercard (Please specify 3.5 or 5.25 inch floppy.)

CIRCLE 88 ON READER SERVICE CARD

#### 5-1000 MHz PREAMPLIFIERS

	NF	G	P(1dB	) \$
WLA21M	3dB	13dB	8dBm	57
WLA22M	4	11	12	61
WLA23M	4	22	12	87
WLA24M	3	20	18	109

430/50 MHz CONVERTER **RXC431** 20dB .15uV 99



WILAM TECHNOLOGY, Div. of

#### WI-COMM ELECTRONICS INC.

P.O. Box 5174, MASSENA, N.Y. 13662 (315) 769-8334

CIRCLE 319 ON READER SERVICE CARD

### NEW PRODUCTS

Compiled by Linda Reneau




#### PRODUCT OF THE MONTH

Aries-1™ Software

Ashton ITC announces Aries-1™ database software. Aries-1 unites multi-mode Terminal Units and transceivers with computer interfacing capabilities. It also has a real-time logging function. It lets you display the Logbook and Transceiver status simultaneously, and remains resident in memory while other programs run. In addition, Aries-1 features a Contest Mode; uploading and downloading files through packet and RTTY; CW speed control; and searching and printing of log data by band, mode, country, and other fields you set up.

Transceivers currently supported are Kenwood models TS-940S, 440S, 140S, 640S, 711A, and 811A (with appropriate Kenwood IC-10 Kit and IF-232C interface) and ICOM models IC-735, 761, 275, 375, 475, and 575 (with the ICOM CT-17 interface). Terminal units currently supported include the AEA PK-232, Heathkit HK-232, and Kantronics KAM all-mode units.

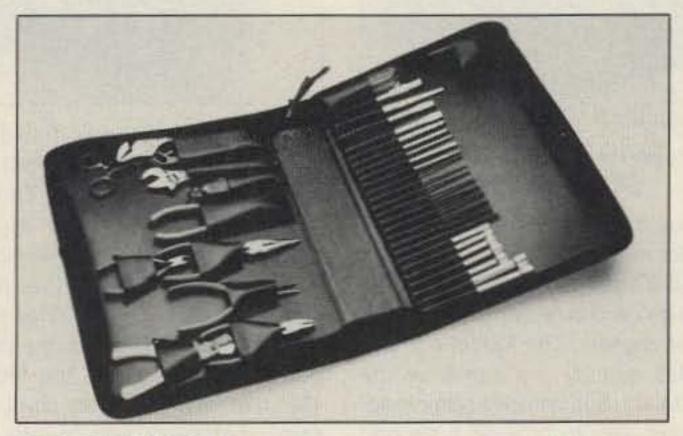Aries-1 includes sample message files, a demo-log, and a User's Guide. It is available on 51/4" or 31/2" disks, and runs on the IBM and compatibles with at least 256K of memory. Price, \$39.95 plus shipping and handling. For further details, contact Ashton ITC, PO Box 1067, Vestal NY 13851. 607-748-9028. Circle Reader Service number 201.



#### **COOPERTOOLS™**

CooperTools™ offers a new TCS200 soft-sided tool case made of Cordura® leather-like material, designed for the Xcelite® line of tool kits. The kit is available with 10 tools, which include five pliers, a wrench, an electronic snip, a wire stripper-cutter, an electrician's knife, and a curved-nose

seizer. In addition, it contains 27 interchangeable screwdriver/nutdriver blades (a selection of slotted, Phillips, and hex) that fit into straight or Tee handles. Price of the tool kit is \$447 with tools and \$150 without tools. Contact Xcelite Soft Kit, CooperTools, Box 728, Apex NC 27502. Circle Reader Service number 203.

#### ICOM AMERICA, INC.

The IC-12GAT hand-held transceiver from ICOM has wideband coverage from 1240-1300 MHz, 1 W power output, 20 memory channels, programmable scan and memory scan, repeater monitor, and built-in 1750 Hz repeater access tone. It is also splash-resistant for outdoor conditions.

The new "G" series is compatible with all ICOM IC-2AT/IC-02AT battery packs, headsets, and speaker mikes. Optional UT-40 beeper. List price, \$529.

Also from ICOM is the IC-228A 2-meter 25 W mobile rig (the 45 W version is the IC-228H). It features wideband receive 138-174 MHz and transmit 140-150 MHz; multi-color LCD; 20 memory channels with programmable and memory scan capability; priority watch while operating on another frequency; and an optional UT-40 tone squelch unit which acts like a beeper/pager.

This compact unit measures 5.5" W x 2" H x 5.4" D (the IC-228H is 6.2" D). There are 13 front panel controls for easy operation.

Suggested retail prices are



\$509 for the 25 W IC-228A, and \$539 for the IC-228H 45 W version. ICOM America, Inc., Corporate Headquarters, 2380 116th Ave. N.E., PO Box C-90029, Bellevue WA 98009-9029. 206-454-8155. Telex: 152210. FAX: 206-454-1509. Circle Reader Service number 202.



#### **HEATH COMPANY**

Heath is offering the first kit laptop computer, the HS-2860. It is fully PC and AT compatible. It has a 12 MHz 80286 processor, 1 MB of standard RAM (expandable to 3 MB), and a 1.4 MB 3.5" disk drive (second internal drive, 20 and 40 MB internal hard disks, optional). It can handle spreadsheets, databases, word processing, and a variety of graphics.

Standard features include: 640 x 400 pixel resolution; supertwist LCD screen; removable battery pack providing up to six hours of continuous operation; Expanded Memory Specification (EMS); parallel port; serial port; RGB video port; and an external floppy drive jack. The HS-2860 is 3.07"H x 12.2"W x 15.4"D.

You may order the HS-2860 by calling 1-800-253-0570. The kit sells for \$2,999. The HS-2860 is

also available as part of a portable computer workstation with a Brother 9-pin printer, nine-foot parallel cable, and software package. These items are features in the 1988 Heathkit Christmas catalog, which you may order by calling 1-800-44-HEATH, or by writing Heath Company, Department 350-038, Benton Harbor MI 49022. Circle Reader Service number 204.



#### MFJ ENTERPRISES, INC.

MFJ Enterprises, Inc., has three new software upgrades to give previous MFJ Packet units the features of their latest MFJ TNC units. These upgrades are:

MFJ-40A: Firmware release 1.1.5. Supports basic Packet features for TNCs with 16K RAM. Price, \$19.95.


MFJ-40B: Firmware release 1.2.6. 32K with 32K RAM upgrade. Price, \$39.95. This release also includes KISS, MFJ Easy-Mail™, and WEFAX receiving capability for the IBM, compatible, or Macintosh computers, using an MFJ Starter Pack option for \$19.95.

MFJ-40C: This is the same as the MFJ-40B without the RAM for TNCs that already have 32K RAM. Price, \$19.95.

MFJ Enterprises, Inc., PO



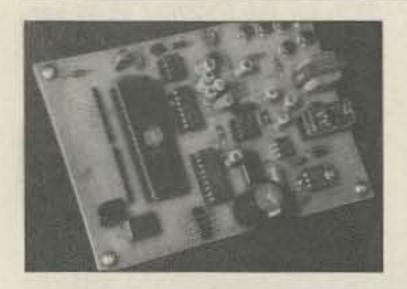Box 494, Mississippi State MS 39762. 800-647-1800 or 601-323-5869. Circle Reader Service number 205.



#### MICRO COMPUTER CONCEPTS

Micro Computer Concepts' RC-1000 Repeater Controller is available from R&L Electronics, complete with manual, schematics, and assembly drawings, for \$219.

The RC-1000 is a microprocessor-based (Intel 8751) repeater controller with an autopatch, pulse or DTMF dialing, reverse patch, and control lines for remote base. Contained on a 5.1" x 3.6"

PCB are the Mitel 8870 DTMF decoder, audio switching with DTMF muting, six pots for audio adjustments to and from the receiver, transmitter, and phone line.

A relay driver is included for active low PTT and transistor buffered selectable active high or low COS input, 10 jumpers for selecting controller options, and a remote base (interface optional). The RC-1000 has 32 control codes and 10 user codes, all accessible via the repeater receiver or phone line. The on-board rectifier/regulator allows powering of the controller via 12 AC or DC requiring only 200 mA. Wired and tested, the RC-1000 is distributed through R&L Electronics, 1315 Maple Ave., Hamilton OH 45011. 800-221-7735 or 513-868-6399 in Ohio. Circle Reader Service number 206.



#### ATLANTIC SOLAR PRODUCTS, INC.

The Pocket Power Inverter, a 12 V DC to 115 V AC power supply from Atlantic Solar Products, measures 1.2" x 3.5" x 4.5", and weighs 14 oz. Plug it into a cigarette lighter and you have an AC power supply to operate

sound and video equipment, electronic test equipment, small appliances, and communications equipment, such as FAX and answering machines. You can also use it to recharge batteries.

It features an automatic shutdown to prevent overloading and excessive discharge, audible low-battery voltage alarm, 90% extended use of the DC source. The Pocket Power Inverter's operating range is 10-15 V DC with a voltage out of 115 AC 200 Watt surge capability. Price, \$149.95.

Atlantic Solar Products, Inc., 9351-J Philadelphia Road, Baltimore MD 21237. Circle Reader Service number 207.

#### GTI ELECTRONICS and SOFTWORKS, INC.

WeatherTrac™ is a combined hardware/software weather satellite imagery system jointly developed by Softworks, Inc., and GTI Electronics. It combines a 64-level gray scale with a 256,000+ color palette at 640 x 480 resolution (scrollable to 800 lines). Weather-Trac also supports 1024 x 768 mode with a 16-level gray scale and the same palette; plus image "looping," 3-D projection, histogram analysis, and AVHRR radiance calibration for direct read-out of scene equivalent temperatures. VGA+ image analysis tools use a standard mouse interface. Among others, the system captures analog weather satellite imagery from GOES-WEFAX, NOAA/TIROS-N APT (single or dual channel), SOVIET METEOR, METEOSAT, GOES-TAP, and NAFAX (high frequency FM).

The basic WeatherTrac Audio



Decoding System includes an external audio interface, an internal acquisition and control card, enhanced VGA+ graphics card, software, and manual, for \$3495. The EGA version, without the mouse-driven image analysis tools, and excluding an EGA graphics board, is \$1895.

Required are an IBM PC/XT/AT or compatible, a matching graphics monitor, and an appropriate audio front-end (antenna/receiver) for the mode(s) of interest.

Contact Softworks, Inc., POB 3114, Allentown, PA 18106. 215-395-4441. Circle Reader Service number 208.



#### **BIRD ELECTRONIC** CORPORATION

The new Bird Model 43P Wattmeter measures true peak power of SSB and AM modulated RF, as well as certain rectangular limited pulse signals. The Model 43P operates exactly the same as the Model 43, but includes peak reading circuitry to provide a second operating mode which lets you measure peak power to an 8% F.S. accuracy without affecting the CW measurement capabilities. This circuitry is powered by two 9 V NEDA 1604 batteries with an anticipated life of forty-eight hours in peak mode.

You need no special elements for peak measurements. The 43P uses the full array of the standard Bird plug-in elements. Depending on the element you select, your overall frequency range is 450 kHz to 2.3 GHz, and your RF power range is 100 mW to 10,000 W. The new Bird Model 43P is \$279.



For owners of the standard Model 43, Bird offers a Retrofit Kit, Model 4300-400, for \$90. The kit includes a PC board which mounts inside the Model 43 housing. Conversion time is less than fifteen minutes. This enables your Model 43 to make the same peak power measurements the Model 43P can make. It also uses the same batteries and meets the same F.S. accuracy.

For more information on the new Bird Model 43P Wattmeter or the Model 4300-400 Retrofit Kit, contact your Bird distributor or Bird Electronic Corporation, 30303 Aurora Road, Solon OH 44139-2794. 216-248-1200. FAX 216-248-5426. Circle Reader Service number 209.

#### antenneX

"The mini-magazine for antenna experimenters" DO YOU -

- Have a lousy mobile signal on all bands?
- Need an inexpensive directional antenna for 10 meters?
- Can't choose between a vertical or horizontal antenna? Need a low noise antenna for 160 meters?
- . Want to design an antenna but don't want to redo the wheel? Need a program for antenna design and antenna plotting?
- . Want to find out if someone else has solved your problem?
- . Don't know what antenna is best for hamsats or others?
- Need a disguised mobile antenna for the car?
- Want a cheap automatic antenna coupler for any type rig?
- . Just want to learn more about antennas?

#### THEN YOU MUST SUBSCRIBE TO - antenneX

antenneX is a mini-magazine for antenna experimenters from the new ham to the oldtimer. There is something for everyone. From computer-aided design to reference table of dipole measurements to a question and answer column. Everyone will find something of interest!

A one year subscription is only \$11.97 for Continental USA and possesions. \$17.00 for foreign surface mail.


Send your subscription to:

#### antenneX

P.O. Box 8995 Dept. 19 Corpus Christi, TX 78412

CIRCLE 82 ON READER SERVICE CARD

#### **SRC-10** REPEATER/LINK CONTROLLER

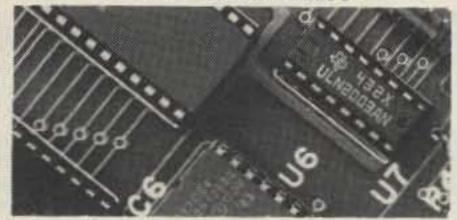

DTMF muting Intelligent ID'er **Auxiliary outputs** Easy to interface Alarm monitor input

Telemetry response tones Low power CMOS, 22ma @ 12v Detailed application manual Programmable COS polarities Repeater & link courtesy tones Synthesized link/remote base capability Assembled &

E CONTROL PRODUCTS

3185 Bunting Avenue Grand Junction, CO 81504 (303) 434-9405



**CIRCLE 306 ON READER SERVICE CARD** 



#### Wideband Preamp 10-1000 Mhz

Dual GasFet low noise preamplifier for HF, UHF or VHF systems. Just perfect for the R-7000. Excellent for Spec Analyzers, Scanners, etc. Gain 20 Db +/- 1 DB, -3 Db at 2 & 1100 Mhz. 1 Db compression of >10 Dbm. Intercept points > 45 Dbm. New shipped price of only \$124.95. Pa. residents please add 6% state tax.

#### **GTI Electronics**

**RD1 BOX 272** Lehighton, Pa. 18235 717-386-4032

**CIRCLE 327 ON READER SERVICE CARD** 

#### Rocky Mtn. Shortwave **Amateur Specialists**

YAESU • TEN-TEC • NRD525 • GRUNDIG SONY · MAGNAVOX · AMERITRON · MFJ METZ • ICOM • DAIWA • KLM/MIRAGE ALPHA DELTA • FAX/RITTY • KENWOOD BENCHER • and others

FT-757 GXII



#### Allied Appliance & Radio

4253 So. Broadway • Englewood, CO 80110 VISA/MC • Discount Prices • \$1.00 For List

303-761-7305

#### OuicKit G5RV, Loop, & Dipole Kits,

Fast & Easy to Build Everything included \* Failsafe visual instructons \* No measuring / cutting

· Finish antenna in minutes Quality Components Presoldered Amphenol PL259 Kinkproof Superflex wire

· Fully insulated, wx sealed, no-corrode, low noise design Antennas West"

(801) 373-8425

· Full Size GSRV 534.95 dipole coverage 80-10 · Half Size GSRV \$24.95 dipole coverage 40-10

• Quarter Size GSRV \$19.95 dipole coverage 20-10 Marconi Adapter kit \$ 4.95

\* 200' Dacron 250# line \$11.95 · Loops, dipoles, feedlines, etc. Add \$5 Shipping & Handling Catalog \$1 by 1st class mail Box 50062-S. Provo. UT 84605

\* Antenna Launcher kit \$14.95

#### **CIRCLE 302 ON READER SERVICE CARD**

#### 1988 CALL DIRECTORY

(On microfiche) Call Directory .....\$8 

All three - \$20 Shipping per order \$3

**BUCKMASTER PUBLISHING** Mineral, Virginia 23117

800: 282-5628 703: 894-5777

CIRCLE 7 ON READER SERVICE CARD

#### Jo Gunn Enterprises

CB Antennas

- Mobile Antennas

- 10 Meter Antennas - Coax

JGAR - 4H

Specifications: TYPE: Horizontal Polarization

UPS SHIPPABLE

GAIN: 15 DB

FRONT TO BACK RATIO: 40 DB

SIDE REJECTION: 45 DB WEIGHT: 22 Pounds LENGTH: 13 Feet 5 Inches

FREQ. COVERAGE: (10 Meter) 28.000 -29.999

WIND LOAD: 3.5 WIND SURVIVAL: 100 MPH

POWER HANDLING CAPABILITIES: 2000 Watts plus PEP

Call or send \$2.00 for Complete Catalog and Pricing of Antennas.




Route 1 - Box 383 Ethelsville, AL 35461 (205) 658-2229 Hrs: 10am - 6pm (CST)

DEALER INQUIRIES, PLEASE CALL
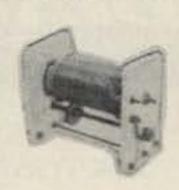
#### **VARIABLE INDUCTORS**

CERAMIC ROLLER INDUC-TOR, 14.3 uH; 24 turns #12 tinned-copper wire in 3.3"Lx2" dia coil. Shaft 36"Lx14" dia. 0/a 3x5x6, 4 lbs #339-L44-MED.



used......\$26 \$24 103 uH ROTARY INDUCTOR using moving contactor, 61 turns #10 wire from 8.8x3.4" dia coil. 0/a 8x8x14, 18 lbs sh. #339-L6-LG, used......\$36 \$29

#### COUNTER DIALS



100-turn counter with crank, 0.1 to 99.9 indicated. 3x3 front plate; shaft 21/4"L x 1/4" dia with coupler. 3 lbs sh. #CR-100T-339. used.....\$19.95 #KN-100T-339, as above but with knob ......\$16.95

Prices F.O.B. Lima, O. - VISA, MASTERCARD Accepted Allow for Shipping - Write for 1989 Catalog Address Dept. 73 - Phone 419/227-6573

FAIR RADIO SALES 1016 E. EUREKA . Box 1105 . LIMA, OHIO . 45802

CIRCLE 75 ON READER SERVICE CARD

#### Let the Sun Power your Station!




The \$289.95 Bullet-Tested QRV Solar Power Supply keeps your repeater on the air round the clock or powers your 100w HF station 60 hrs a month. Control circuit speeds charge, protects gel cells & sealed batteries. Fully assembled, QRV, portable. Easily expanded. Add \$10 S&H Air Mail Into \$1 Antennas West (801)373-8425 Box 50062-S Provo UT 8460.

**CIRCLE 303 ON READER SERVICE CARD** 
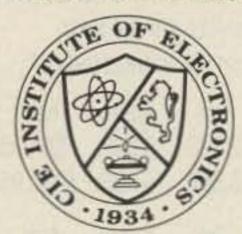
#### E Cleveland Institute of Electronics

Accredited Member National Home Study Council



CIE is the world's largest independent study electronics school. We offer ten courses covering basic electronics to advanced digital and microprocessor technology. An Associate in Applied Science in Electronics Engineering Technology is also offered.

Study at home — no classes. Programs accredited and eligible for VA benefits.

CIE Cleveland Institute of Electronics 1776 East 17th St., Cleveland, Ohio 44114 YES! I want to get started. Send me my CIE school catalog including details about the Associate Degree

program. Print Name\_ Address\_\_\_\_ Zip\_\_\_ City \_\_\_\_ State\_\_

Age\_\_\_\_\_ Area Code/Phone No.\_\_

Check box for G.I. Bulletin on Educational Benefits ☐ Veteran ☐ Active Duty MAIL TODAY!

AAR97

CIRCLE 157 ON READER SERVICE CARD

### DIAMOND

KNOWN WORLD-WIDE FOR PREMIUM QUALITY ANTENNAS AND METERS

#### POWER/SWR METERS



- Forward & Reflected Power & SWR
- · Selectable RMS or PEP switch
- 3 Power Ranges: 5/20/200 Watts 30/300/3KW (SX-100 only)
- Power Meas. Accuracy 5% (typ.)
- · Insertion Loss: 0.2 dB Max.
- Wideband Performance

#### FOUR MODELS TO CHOOSE FROM

SX-100	1.6-60 MHz	\$109.95
SX-200	1.8-200 MHz	\$89.95
SX-400	140-525 MHz	\$99.95
SX-600	Dual-Band	\$139.95
	1.8-200 MHz	1


#### **DUAL-BAND ANTENNAS**

140-525 MHz

We believe that DIAMOND Dual-Band Antennas are the best antennas on the market today!\*

BASE 2m 70cm Net DX-50 2.8dB 5.8dB \$94.95 DX-200 5.5dB 8.0dB \$139.95

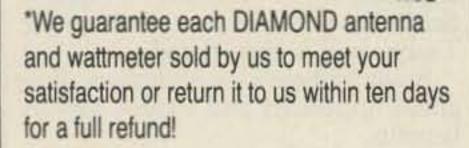MOBILE 2m 70 cm Net NR-770S unity 3.0dB \$34.95 NR-770R 3.0dB 5.5dB \$47.95



Orders received by 1 PM PST shipped UPS same day.

Next day UPS delivery available

PARTS ORDERS ONLY - NO TECHNICAL (800) 854-1927

> ORDER LINE and/or TECH HELP (619) 744-0728

> > FAX 619-744-1943

"QUALITY NEED NOT BE EXPENSIVE"



### SPECIAL EVENTS

#### SOUTH BEND IN JAN 7

A Hamfest Swap and Shop will be held at Century Center, Downtown off US 33 Oneway North between the Trustcorp Bank Building and the river. Four-lane highways to door from all directions. Tables: \$5/5-foot round; \$15/8x2.5-foot rectangular; \$20/8-foot wall locations. Talk-in on: 6, 52, 99–39, 69–09, 34–94, 145.29. For information, contact Wayne Werts K9IXU, 1889 Riverside Drive, South Bend IN 46616 or phone (219) 233-5307.

#### RIO DE JANEIRO JAN 7 and JAN 14

The Lions Club International is sponsoring this contest, commemorating the birthday of Melvin Jones, their founder. Their goal is to create and foster a spirit of international understanding and cooperation. Coordinated by the Rio de Janeiro Arpoador Lions Club, the contest is open to all licensed radio operators. Bands permitted are 80, 40, 20, 15 and 10 meters, phone and CW. Phone and CW must be entered into separate logs. Jan 7: CW Mode, starting at 12:00 GMT and continuing for 24 hours. Jan 14: Phone Mode, starting at 12:00 GMT and continuing for 24 hours. For information, write Hunting Lions in the Air Contest Committee, Rio de Janeiro Arpoador Lions Club, PO Box 2155, Rio de Janeiro 20011, RJ, Brazil, South America.

#### MILWAUKEE WI JAN 14

The 17th Annual Midwinter Swapfest will be held at the Waukesha Co. Expo Center from 8 AM to 3 PM. Directions: I-94 to Co. J, south to FT, west to Expo. Admission: \$2 in advance, \$3 at the door. Tables (4-foot): \$3 in advance, \$4 at door. Electrical outlet, as available, \$5. Advance deadline is Jan. 2, 1989. Dealers welcome. Amateur exams given (write for details). Food available. Sponsored by the West Allis Radio Amateur Club. For tickets and information, write WARAC SWAPFEST, PO Box 1072, Milwaukee WI 53201. Enclose SASE.

#### JAMAICA NY JAN 16

The Hall of Science Amateur Radio Club will issue a commemorative certificate to anyone working HOSARC club station WB2JSM, in celebration of their 17th anniversary. SSB operation: 14.335 and 21.365. CW operation: 14.065 and 21.135. All frequencies are plus or minus 15 kHz due to QRM from 1500 to 2100 UTC. QSL with a large SASE (50 cents or 2 IRCs) to HOSARC QSL Manager Arnie Schiffman WB2YXB, 81-22 250th Street, Bellrose NY 11426.

#### HAMMOND LA JAN 21

The Southeast Louisiana ARC Hamfest will be at the SE Louisiana University Recreation Center. Talkin on 147.0/46.4. Exams, tables, and fun. Wheelchair accessible. Contact Joe Farris, 390 Piney Woods, Ponchatoula LA 70454. 504-386-8393.

#### SOUTHFIELD MI JAN 22

The Southfield High School Amateur Radio Club is sponsoring their 23rd Annual Swap and Shop at Southfield High School. Doors open at 6 AM for exhibitors. Open to the public from 8 AM to 3 PM. Admission is \$3. Reserved tables are \$20 for two 8-foot tables, paid in advance. Additional reserved tables are \$10 each. Plenty of parking, food, and door prizes. For information and reservations, con-

#### Ham Doings Around the World

tact Robert Younker, Southfield High School, 24675 Lahser, Southfield MI 48034, 313-746-8637.

#### APO SAN FRANCISCO CA JAN 27

The Kwajalein Amateur Radio Club will operate KX6BU from 0600Z, Jan. 27, to 0600Z, Feb. 6, to commemorate the 45th anniversary of the Battle of Kwajalein and Roi-Namur. Frequencies are SSB: 14.250, 21.350, 28.550; and CW: 7.025, 14.050, 28.050. For \$7, KX6BU will send you a QSL, a certificate, and a 64-page book on the Battle of Kwajalein and Roi-Namur. \$3 will bring a QSL and certificate. Send requests to KX6BU, Box 444, APO San Francisco CA 96555-0008

#### CRYSTAL RIVER FL JAN 29

The 9th Annual Citrus County Hamfest, sponsored by the Sky High Amateur Radio Club, will be held at the National Guard Armory, located on Seven Rivers Drive just south of the Crystal River Airport off Route US 19. Talk-in frequency on 146.355/.955. Hourly door prizes, Grand Prize at 2 PM. Packet radio forum, lots of food, and RV parking available. Admission is \$3 until Jan 14 (send SASE) and \$4 thereafter. XYLs FREE with OM. Swap tables \$5. Friday afternoon set-up hours available by pre-arrangement. Doors open at 7 AM for exhibitor set-up, and only admissions purchased with tables will be allowed entry. Open to public at 9 AM. For tickets, tables, and information, contact Bob Gordon W1KUL, 904-628-5045 or SHARC Hamfest, 5334 S. Forest Terrace, Homosassa FL 32646.

#### ST. CATHARINES ONT FEB 4

The Niagara Peninsula Amateur Radio Club Inc. is holding the 11th Annual Big Event, a hamfest and dinner dance at the C.A.W. Hall, 125 Bunting Road. Admission is \$3, tables are \$12 each commercial and \$5 each non-commercial. Talk-in on 147.24/.84. For information, write N.P.A.R. Inc., PO Box 692, St. Catharines, Ontario L2R-6Y3, Canada, or phone 416-937-0590.

#### MELVILLE LONG ISLAND NY FEB 5

The Long Island Mobile Amateur Radio Club, Inc., will sponsor a hamfest at the Electricians Hall, 41 Pinelawn Road. Doors open from 9 AM to 3 PM. Admission \$4, \$3 after 11:30 AM. Sellers' 4' x 6' tables are \$12 each, or bring your own at \$1.50 a foot, 6-foot minimum. Helpers pay admission. Registration in advance only, check payable to LIMARC. Talk-in on 146.85. L.I.E. Route 495 to Exit 49 North, 1/4 mile right turn onto Pinelawn Road. For information, contact Mark Nadel NK2T, 22 Springtime Lane East, Levittown NY 11756. 516-796-2366, or Hank Wener WB2ALW, 201-694-1811.

#### MONTPELIER VT FEB 4-5

The Central Vermont Amateur Radio Club W1BD is having its 1989 QSO Party on the above dates from 0001Z the 4th to 2400Z the 5th. Suggested frequencies are Phone: 80–15 meters; the first 25 kHz up from the beginning of the General Phone band edge; Novice 10 meter phone portion, 50.110, 144.2; CW: 3540, 3720, 7040, 7120, 14040, 21040, 21140, 28040; and RTTY: 3620 and 90 kHz from lower edge of other bands. For rules on exchanges and scoring, information about awards, and official score and log sheets, send an SASE (two, if you want to receive the results) to D. Loverin WA1PDN, 50 Liberty Street, Montpelier VT 05602.

## How to Read **Electronic Circuit**

\$20.95




2980 \$28.95 Counts as 2






2655P \$16.95

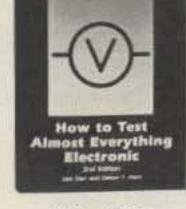

2925 \$16.95



2735P \$13.95

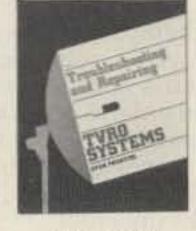

2992 \$24.95



2910 \$24.95




2701P \$17.95

READING

SCHEMATICS



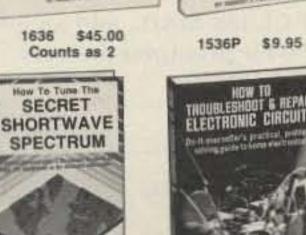

1185P \$10.95


1218P \$16.95

### SELECT 5 BOOKS for only \$395



The Beginner's Handbook of

2965 \$24.95

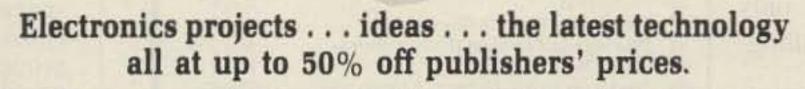

Membership Benefits • Big Savings. In addition to this introductory offer, you keep saving substantially with members' prices of up to 50% off the publishers' prices. . Bonus Books. Starting immediately, you will be eligible for our Bonus Book Plan, with savings of up to 80% off publishers' prices. . Club News Bulletins. 14 times per year you will receive the Book Club News, describing all the current selections-mains, alternates, extras-plus bonus offers and special sales, with hundreds of titles to choose from. . Automatic Order. If you want the Main Selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no book at all, simply indicate your choice on the reply form provided. As a member, you agree to purchase at least 3 books within the next 12 months and may resign at any time thereafter. . Ironclad No-Risk Guarantee. If not satisfied with your books, return them within 10 days without obligation! . Exceptional Quality. All books are quality publishers' editions especially selected by our Editorial Board.


©1989 ELECTRONICS BOOK CLUB, Blue Ridge Summit, PA 17294-0810
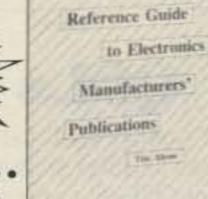
#### FREE when you join!

Reference Guide to Electronics Manufacturers' Publications

A time- and money-saving list of product literature from all the major electronics suppliers.







#### ELECTRONICS BOOK CLUB®

Blue Ridge Summit, PA 17294-0810

Please accept my membership in the Electronics Book Club® and send the 5 volumes listed below, plus my FREE copy of Reference Guide to Electronics Manufacturers' Publications (2683P), billing me \$3.95 plus shipping and handling charges. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase at least 3 books at regular Club prices (plus shipping and handling) during the next 12 months and may resign any time thereafter.

HILLS TO THE	The state of the s	The latest Division in	
Name			
Address		1969	
City			
State	Zip	Phone	
Signature	The second second		
gnature of parent or guardian	required for all new members ur	nder 18 years of age.	

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada. must remit in U.S. currency. This order subject to acceptance by the Electronics Book Club®. All books are hardcover unless numbers are followed by a "P" for paperback.



2750P \$17.95




1740P \$10.00



\$21.95






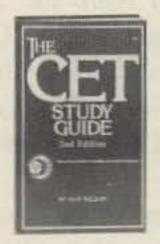

\$21.95



2975 \$24.95

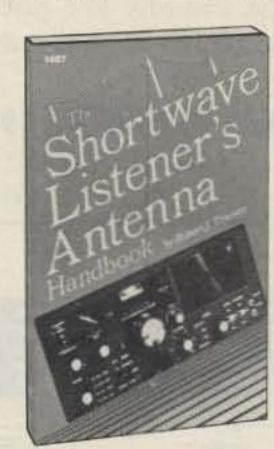

1487P \$12.95



2947 \$21.95



2653P \$13.95



2722P \$14.95



1665P \$19.95



1367P \$17.95

3017 \$15.95

### THE WORLD

Is Yours For Only \$5.00



Yes, places you've never even heard of! Nearly 400 DX countries gleaned from the Awards Lists of dozens of IARU members—more countries than any other map available anywhere! ARRL's DXCC map doesn't even come close!

73 Magazine offers readers our giant DX Map of the World for the absurdly low price of only \$5.00 plus \$1 postage & handling.

#### Mail Your Order To:

73 Magazine, WGE Center, Peterborough, NH 03458


#### **CB-TO-TEN**


73 has led the way on CB-to-10 meter conversions. Take advantage of our offer to help you get on 10 meters before the sunspots peak again. It's easy and saves you money!


#	Title	Issue
1	Bandplan and Crystal Info	May 77
2	Conversion Data	May 77
3	Radio Shack TRC-47	Jul 77
4	E.F. Johnson Messenger 123A	Jul 77
5	Hy-Gain 670B	Jul 77
6	Antenna Suggestions	Dec 77
7	Radio Shack Realistic TRC-II	Dec 77
8	The Publicom I	Feb 78
9	How about SSB Conversions?	Jul 78
10	Radio Shack TRC-11 and TRC-74	Aug 78
11	Radio Shack Realistic Mini 23	Sep 78
12	Hy-Range 681A (Hy-Gain)	Sep 78
13	Kraco KCB-2310B	Oct 78
14	Lafayette Telsat SSB-75	Nov 78
15	Radio Shack Realistic TRC-452	Nov 78
16	CB Walkie-Talkie Conversion	Nov 78
17	Sharp Model CB-800A	Jan 79
18	SBE Sidebander III and Pace 123A	Jan 79
19	Midland 13-882C and Other PLL Rigs	May 79
20	Lafayette SSB-75 and SSB-100	Jun 79
21	Royce I-655	Nov 79
22	Johnson Viking 352	Nov 79
23	CB to 10 FM - Part I	Jan 80
24	CB to 10 FM - Part II	Feb 80
25	More Talk Power for the TRC-11	Mar 80
26	Sears RoadTalker 40	Mar 80
27	Penney's SSB Rig	Apr 80
28	The Poly-Paks 40-Channel CB Board	Jun 80
29	The Cobra 132	Jul 80
30	New Life for SSB CB Rigs	Jul 80
31	Double Your Channels in SSB Conversions	Jul 80
32	On Ten FM	Aug 80
33	Put That Hy-Gain CB Board to Use	Sep 80
34	Peaking and Tweaking Hy-Gain Boards	Mar 82
35	CB to CW? (Hy-Gain)	Jul 82
36	Maximum Modulation for CB Conversions	Dec 82
37	Beef Up Your CB-to-CW Conversion	Feb 83
38	Add a Digital Readout to Your CB Conversion	Feb 83


Send \$3.00 for the first article and \$1.50 each thereafter. Just choose the article numbers and call with a credit card number or send a check or money order to: CB to Ten, 73 Amateur Radio Magazine, WGE Center, Peterborough NH 03458 [603-525-4201].

### QSL Cards

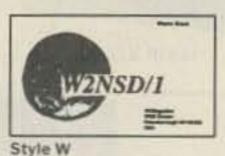

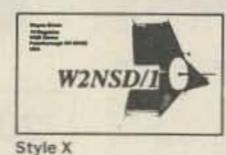

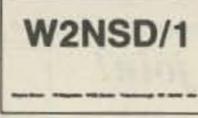

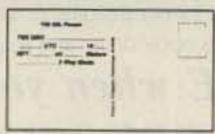

Style Y

Reverse

#### **QSLs**

Now you can get the highest quality QSL cards without spending a fortune! We put these cards on our press as filler between jobs; it gives the pressmen something to do and lets us print QSLs for you at an absurdly low price.

Not that we skimp: All three styles are produced in two colors (blue globe or satellite with black type). At these prices, you can start the new year out right by QSLing all those disappointed hams who've been waiting for your card. Tell 'em the card was printed by Wayne!

Send me the cards and qu	antities indicated b	elow.	
Style: W X Y	Quantity	/: □ 100—\$8.97	
Please print your name and address		□ 250—\$19.97	
exactly as it will appear on your		□ 500—\$39.97	
cards:	Please add \$1 pc	stage & handling	
Name	Call		
Address			
City	State	_Zip	
□ Check □ Amex	□ MC	□ VISA	
#	Expires	DETERMINENT TO SELECT	
Please allow 4 to 6 weeks for delivery 73 Magazine Wi	GE Center Peterborough NH 03	3458 Attn: OSI Orders	

### UNCLE WAYNE'S CODE TAPES

We've had so many phone calls from people wanting our famous 73 code tapes that we've decided to bring them back!

#### "Genesis"

\$6.95

5 wpm-This is the beginning tape, taking you through the 26 letters, 10 numbers and necessary punctuation, complete with practice every step of the way. The ease of learning gives confidence even to the faint of heart.

#### "The Stickler"

\$6.95

6+ wpm-This is the practice tape for those who survived the 5 wpm tape, and it's also the tape for the Novice and Technician licenses. It is comprised of one solid hour of code. Characters are sent at 13 wpm and spaced at 5 wpm. Code groups are entirely random characters sent in groups of five—definitely not memorizable!

#### "Back Breaker"

\$6.95

13+ wpm-Code groups again, at a brisk 13+ wpm so you'll be really at ease when you sit down in front of a steely-eyed volunteer examiner who starts sending you plain language at only 13 per. You'll need this extra margin to overcome the sheer panic universal in most test situations. You've come this far, so don't get code shy now!

#### "Courageous"

\$6.95

20+ wpm-Congratulations! Okay, the challenge of code is what's gotten you this far, so don't quit now. Go for the Extra class license. We send the code faster than 20 per. It's like wearing lead weights on your feet when you run; you'll wonder why the examiner is sending so slowly!

PA	da	Ta	DAG	i
LU	ac.	11 61	pes	ĺ
-	40		Peo	

Genesis	\$6.95	-:-	
The Stickler	\$6.95		
Back Breaker	\$6.95		
Courageous	\$6.95		
For FIRST C tional \$1.50			delivery.
Address	retou.		
City		State	Zip
□ AE □ M	C [	VISA	□ Check/MO
Card#		Ex	p. Date
リルアファンシェンス かっかい ディー	our order to	The state of the s	

### UNCLE WAYNE'S BOOKSHELF

Aw right, a'ready! NOW, the popular electronics and amateur radio books you've been hounding poor old Uncle Wayne for are here! Now you can build up your hamshack library with these soft-cover favorites . . .

#### The Packel Radio Handbook

by Jonathan L. Mayo KR3T "...an excellent piece of work. Well worth reading for both the experienced and the new packeteer...the definitive guide to amateur packet operation."

-Gwyn Reedy W1BEL Only \$14.95

#### . The Beginner's Handbook of Amaleur Radio


- 2nd Edition by Clay Laster

Combines theory and practice in an easy-to-understand format, and provides information for choosing and installing radio receivers and transmitters, antennas, transmission lines, and test equipment. 400 pages, 291 illustrations \$16.95

PACKET RADIO

HANDBOOK

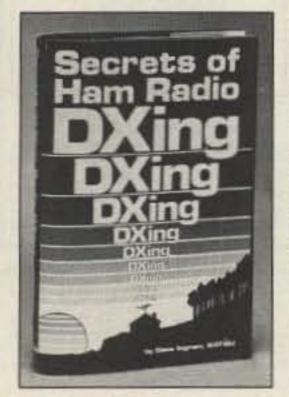•DX Power: Effective Techniques for Radio Amaleurs by Eugene B. Tilton K5RSG 256 pages, 10 illustrations \$10.00



#### · Secrets of Ham Radio DXing

by Dave Ingram K4TWJ (Hard Cover only) 176 pages, 102 illustrations \$12.95

 Transmitter Hunling: Radio Direction Finding Simplified

by Joseph D. Moell KOOV and Thomas N. Curlee WB6UZZ 336 pages, 248 il-

lustrations \$17.95

• The Digital Novice

by Jim Grubbs K9EI

Your guide to the fascinating worlds of communication that have just opened for thousands of amateur radio operators. Now you can learn about everything from Morse code to the latest in packet radio technology. \$9.95

#### The Commodore Ham's Companion

by Jim Grubbs K9EI

160 pages of useful information on selecting a Commodore computer for the ham shack, where to find specialized programs, the Commodore-packet connection, and more! \$9.95

#### Master Handbook of 1001 Circuits—Solid-State Edition

by Kendall Webster Sessions

With this outstanding reference in hand, electronics hobbyists and professionals will never have to search for schematics again. Completely updated, the book is thoroughly indexed and all 1001 circuits are clearly illustrated. 420 pages. \$19.95 soft cover

#### The Contest Cookbook

by Bill Zachary N6OP

One of ham radio's winningest contesters lets you in on the tips and techniques of the Big Guns. You'll learn which duping method to use, find out what equipment you'll need, and discover the secret of building a pileup. Includes separate chapters on DX and domestic contests. \$5.95 while they last!

• The Magic of Ham Radio by Jerold Swank KW8HXR, begins with a brief history of amateur radio and Jerry's involvement in it. Part 2 details many of ham radio's heroic moments. Hamdom's close ties with the continent of Antarctica are the subject of Part 3. In Part 4 the strange and humorous sides of ham life get their due. And what of the future? Part 5 peers into the crystal ball. Only \$4.95

#### by Thomas Harrington W80MV World Press Services Frequencies (RTTY)

A comprehensive manual covering Radioteletype news monitoring-contains all information-antenna, receivers, terminal units, plus three extensive frequency lists. Covers 65 World Press Services broadcasting in English. "The Original Press Book." 84 pages. \$8.95

#### •RTTY Today

by Dave Ingram K4TWJ

The new and only up-to-date RTTY book in existence. Covers all facets of RTTY-RTTY and Home Computers-most comprehensive RTTY guide ever published. Fully illustrated. A must for RTTY fans. 112 pages. \$8.95

#### Shoriwave Clandesline Confidential

by Gerry L. Dexter

Fascinating reading-new book covers all clandestine broadcasting, country by country-tells frequencies, other unpublished information-spy-insurgentsfreedom fighters-rebel-anarchist radio-secret radio-covers all. Current publication. 84 pages \$8.95

#### Salcillic and Cable TV

Scrambling and Descrambling by Brent Gale & Frank Baylin. This new book was written for readers who do not have a technical education, but who want to have an understanding of the technology of satellite and cable scrambling and descrambling. 256 pages. \$19.95

#### · Shortwave Directory

by Frank Baylin

A complete directory listing all domestic and foreign station frequencies data from 1.6 MHz to 30 MHz. Over 6,000 listings of Air Forces, Navies, Army, energy, emergency, spy, smugglers, pirate/clandestines, aero federal space, interpol and many more services. Covers all types of transmission modes. SSB, RTTY, FAX, CW and AM. \$17.95

#### • The Hidden Signals on Salellile TV by Thomas P. Harrington and Bob Cooper Jr. New book shows and tells how to tune in the many thousands of Telephone, Data, Telex, Teletype, Facsimile Signals on most of the TV Satellites, covers equipment, hook-ups, where to tune. Only book covering these secret signals on the satellites, plus all subcarriers. 234 pages. \$19.95

#### • GGTE Morse Tulor


Floppy disk for IBM PC, XT, AT and compatibles. Learn the International Morse code or improve your capabilities. One diskette will take you from beginner through extra class in easy self-paced lessons. Standard or Farnsworth mode. Code speeds from 1 to over 100 words per minute. \$20.00

#### • THE WORLD IS Yours For Only \$5.00

Yes, places you've never even heard of! Nearly 400 DX countries gleaned from the Awards Lists of dozens of IARU members-more countries than any other map available anywhere! ARRL's DXCC map doesn't even come close! 73 Magazine offers readers our giant DX Map of the World (in classic black and white) for the absurdly low price of only \$5.00 plus \$1.00 postage and handling.

Uncle Waune's Bookshell Order Form

☐ The Magic of Ham Radio	. \$4.95
☐ The Contest Cookbook	
☐ The Packet Radio Handbook	\$14.95
☐ The Beginner's Handbook of Amateur Radio	\$16.95
DX Power: Effective Techniques for Radio Amateurs	
☐ Transmitter Hunting: Radio Direction Finding Simplified	
☐ The Digital Novice	
☐ The Commodore Ham's Companion	9.95
☐ Master Handbook of 1001 Circuits	. 19.95
☐ World Press Services Frequencies (RTTY)	8.95
□ RTTY Today	
☐ Shortwave Clandestine Confidential	8.95
☐ Satellite and Cable TV Scrambling	. 19.95
☐ Shortwave Directory	. 17.95
☐ The Hidden Signals on Satellite TV	\$19.95
☐ GGTE Morse Tutor floppy disk	\$20.00
Add \$1.00 for postage & handling. For FIRST CLASS MAIL a additional \$1.50 for prompter delivery Please Print!  Total Enclosed	dd an
Name	
CallAddress	
CityStateZip	
□AE □MC □VISA □Check/Money Orde	er i
ard # Exp. Date	

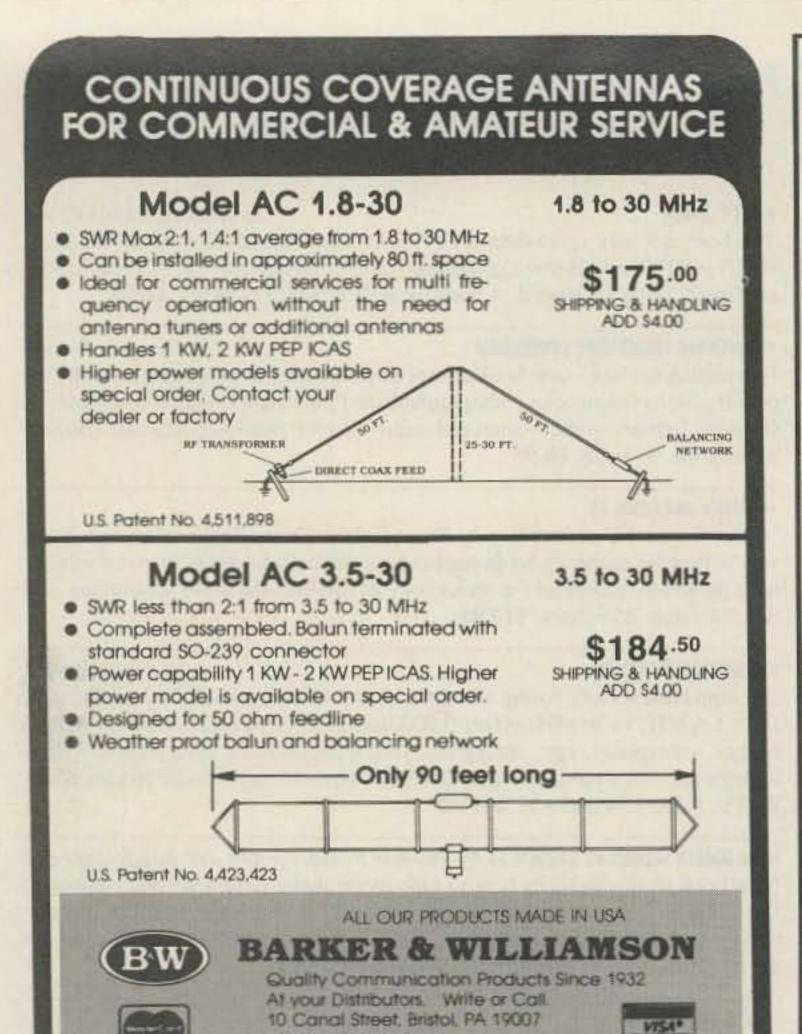

**CIRCLE 53 ON READER SERVICE CARD** 

#### HIGH PERFORMANCE PRESELECTOR-PREAMP

(215) 788-5581

The solution to most interference, intermod, and desense problems in AMATEUR and COMMERCIAL systems.




- . 40 to 1000 Mhz tuned to your frequency
- · 5 large helical resonators
- · Low noise High overload resistance
- 8 dB gain ultimate rejection > 80 dB . 10 to 15 volts DC operation
- Size 1.6 x 2.6 x 4.75" exc. connectors
- FANTASTIC REJECTION!

Typical rejection: ±600 Khz@144 Mhz: -28dB ±1.6 Mhz@220 Mhz: -40dB ±5 Mhz@450 Mhz: -50dB

Price - CALL bipolar w/RCA jacks Connector options: BCN \$5, UHF \$6, N \$10

SUPER HOT! GaAs Fet option \$20

#### **AUTOMATIC IDENTIFIERS**

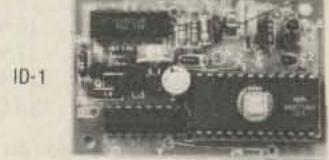



ID-2

- For transceivers and repeaters AMATEUR and COMMERCIAL
- · Automatic operation adjustable speed and amplitude
- . Small size easy installation 7 to 15 volts DC
- · 8 selectable, reprogrammable messages each up to 2 min. long

· Wired, tested, and programmed with your message(s)

Model ID-1 - \$54.95 Model ID-2 w/2 to 10 minute timer - \$79.95 We offer a complete line of transmitter and receiver strips and synthesizers for amateur and commercial use. Request our free catalog. Mastercard and VISA welcome

GLB ELECTRONICS, INC.

151 Commerce Pkwy., Buffalo, NY 14224 716-675-6740 9 to 4


**CIRCLE 17 ON READER SERVICE CARD** 
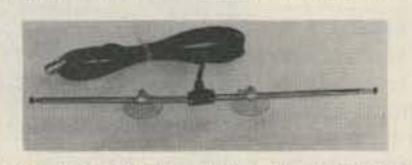
#### SUPER VAK-TENNA Only \$149. 55



500kH: - 800MH: ACTIVE RECEIVE ANTENNA

The revolutionary SUPER VAK-TENNA advances the stateof-the-art by providing superb reception, extremely wide coverage, small size and SUCTION CUP MOUNTING in one compact antenna! Low noise/High gain 14 db (or better) active amplifier is built in for unsurpassed reception. A female BNC connector connects to your receiver. 15 feet of coax cable and 115VAC power unit are also supplied.



SUCTION CUP MOUNT VAK-TENNA! Only \$29. 95

IDEAL FOR APARTMENTS OR OFFICES!

Mount this antenna to your window for the BEST coverage. Two VERY powerful suction cups hold firmly for weeks. Whips telescope to 79" yet fold to only 12". This antenna is a MUST for people who travel! Receives 30-500 MHz or transmit 70-230 MHz with up to 50 watts! Complete with 15' of coax and choice of PL259, BNC, Motorola or F connector.



**ELECTRON PROCESSING, INC.** P.O. BOX 708 MEDFORD, NY 11763 (516) 764-9798

SEND FOR MORE DETAILS! US MADE!



Kathy Sez "These products are A-OK!"

#### SIGNAL INTENSIFIERS

Priced from \$29. 95

A HEARING AID FOR YOUR RECEIVER OR SCANNER!

- The State of the Art in WIDEBAND preamps!
- Make small antennas perform like BIG ones!
- Fully Assembled and BUILT TO LAST!
- 110 VAC or 12 VDC powered!
- VHF/UHF or MF/HF available!
- Many models! Send for specs!



Add \$3 Shipping/Handling. NY add Sales Tax.

SATISFACTION GUARANTEED!

Order any product (except software) from EPI and if not satisfied return it within 15 days for a full refund (less shipping/handling).


CIRCLE 291 ON READER SERVICE CARD

#### Look at our MOBILE MARK "ON WINDOW" Line

PATENTED
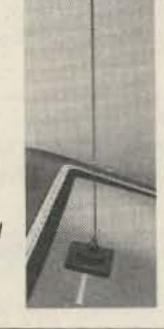
#### VHF (140-175)

- No Hole
- · Easy to Mount
- Rugged
- Superior Performance
- Radiator Snaps On and Off
- Competitively Priced



#### UHF


· 3 db gain

(420-520)

- No Hole
- Easy to Mount
- Rugged
- Superior Performance
- Radiator Snaps On and Off
- Competitively Priced
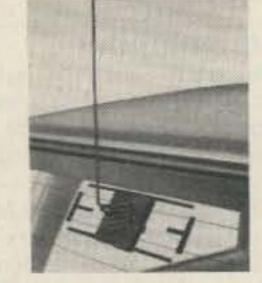
#### Cellular/Trunking (800-895 MHz)

- 3db Gain
- · No Hole
- · Easy to Mount
- · Rugged Goes through Car Wash Without Removal
- Superior Performance
- Broad Bandwidth
- Small Size
- Competitively Priced



3900-B River Road Schiller Park, IL 60176 312-671-6690

brings imagination and innovation to antennas .... and has been since 1948!!

CIRCLE 163 ON READER SERVICE CARD



## Low Power Operation

Mike Bryce WB8VGE 2225 Mayflower N.W. Massillon, OH 44646

## The Captive Electrolyte Battery

Using the proper method, you'd be surprised at the amount of power you can save up in a couple of sunny days. A relatively new innovation in lead-acid battery construction uses a captive electrolyte. The Gel/Cell™ from Globe Battery and the Absolyte™ absorbed-electrolyte battery from **GNB Battery Company work** about the same as the liquid leadacid battery, only the electrolyte is jelled. The batteries are then fully enclosed, allowing operation in any position. They will not leak, spill, or emit gas. Of course, some gassing occurs, but special chemicals inside the battery recombine the gas back into the electrolyte. If excessive gas is generated, a special one-way vent allows the gas to escape.

In these gell-cell batteries, you can't add water or take specific gravity readings. They stand up to freezing temperatures without harm. The captive electrolyte concept provides a solution to many of the basic problems inherent in lead-acid batteries, and although these batteries are more expensive per unit of capacity than their liquid-filled counterparts, their advantages often outweigh the cost differential. You should consider them for all photovoltaic applications, especially those in which site access for regular periodic maintenance is impractical.

## Batteries for Photovoltaic Energy Storage

Armed with this information, how do you go about choosing the proper battery for PV storage? First, I don't recommend using used batteries, unless you know where they came from and what they where used for. The best method is to use batteries of the same make, type, manufacturer, and age. When the batteries age together, the whole bank will age at the same rate, unless you get a bum battery in your purchase.

One of the strong indications of a battery that it is deep-cycle is its heavy weight. Don't be fooled, however, into buying a large truck battery or Cat™ battery just because it is heavy. All you really get is a heavy starter battery. Truck batteries are not deep-cycle; neither are most Die-Hards™. Since advertising is always a bit less than accurate, be persistent, skeptical, and slow-moving. Because of the weight, purchase your batteries from a local source, unless you can get together with a group and purchase in large lots.

Who makes the best deep-cycle battery? A loaded question, but some of the better manufacturers are: Exide, Trojan, Douglas, and GNB. I use the Exide EV-IV and Exide GC-4. These are designed for electric golf carts. Each battery weighs about sixty-five pounds. The nominal voltage is 6 volts, so you need two batteries for a 12 volt system. The Exide EV-IV and GC-4 are both rated at 220 amp/hr at a 20-hour rate. That means I can draw 11 amps for over 20 hours on each string of two batteries. My system has eight of these batteries, so I can pull about 44 amps from the bank for 20 hours!

## Installing and Mounting the Batteries

In a recent test, I loaded the entire storage bank down at 5 amps, and five days later the load was still going. The condition of the battery bank was at a 65% depth of discharge. Since it takes two of the Exide EV-IVs to get a nominal 12 volt system, sixty-five pounds per battery can add up quickly. I have roughly one quarter ton of lead and acid in the basement, not counting the extra six portable 105 amp/hr jobs. Mounting the batteries clearly can become an engineering task!

In my original setup, I used twoby-fours bolted to the cement floor. Over these I placed 34" external plywood. Then I installed wood runners on the plywood, and onto these I set the batteries. Besides keeping the bottoms of the batteries from sitting right on top of the plywood, the runners provided a path for air exchange between the individual batteries. Lastly, I gave everything several coats of polysealer.

Keep in mind you need two batteries to make up a 12 volt system. You can connect them together with battery connectors like those in your car. I soldered the connection and then used the built-in clamp, making sure not to tighten

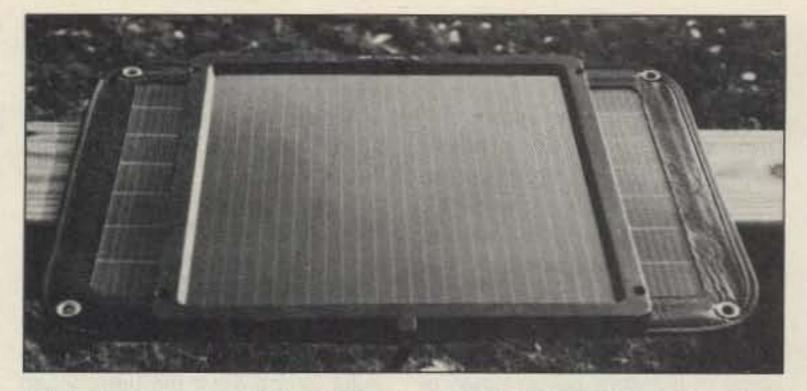


Photo A. These small 5-watt panels operate quite a bit of gear when hitched to a good storage system.

the bolts too much. The connectors are made of lead, and the bolts can pull through. I used a "flex" size double-"O" multistrand copper wire for the interconnecting cable. If you can't find such a critter, ask for welder cable at your local welding supply house. You won't need too much for interconnections, so ask for the loose odds and ends.

In designing your storage bank, remember that voltage is additive when batteries are connected in series. Ampere-hour (capacity) is additive when batteries are connected in parallel. You can use almost any type of configuration provided you follow the above requirements concerning battery age, make, etc. You can add more parallel batteries when your pocket book permits. While this may contradict my advice to use batteries of the same age, you can add batteries later as long as you provide enough charge current to the battery bank. The new cells and the old cells will then equalize the charge. It's not a GOOD idea, but you can do it. If you use a lot of energy from your battery system, and your PV array is undersized for maintaining energy storage, it would then be best to replace all the batteries. Otherwise, go ahead and mix the new with the old.

## **Measuring Battery Charge**

No one has yet invented a "fuel" gauge for batteries, and it is not easy or cheap to determine how much "juice" is in your batteries at any instant. All you can do is measure the amp/hr out of the battery system and the amp/hr into the system. But this is expensive and not worth it. There are two other ways of ball-park guessing the battery state-of-charge: measuring specific gravity or terminal voltage.

## Measuring Specific Gravity and Terminal Voltage

Let's look at specific gravity

first. As you know, a discharging battery will show a drop in the specific gravity when measured with a hydrometer. This reflects the state-of-charge only within these guidelines: The battery electrolyte must be at 80°F, and the battery must have been discharged at the proper amp/hr rate.

A higher than normal discharge rate gives false readings, as does too-high or too-low electrolyte temperatures. At very high rates of discharge, the electrolytes on the plates are weaker than those in the rest of the cell (because they can't mix with the rest of the electrolytes), giving a false and misleading result.

As lead-acid batteries discharge, the drop in specific gravity is quite linear. A plot of the results shows a nice curve. When charging the batteries, however, the specific gravity doesn't return the same linear reading. You have to charge, and charge, and charge some more before the hydrometer starts to show an increase in specific gravity.

Measuring battery terminal voltage is by far the most common method of checking the state-of-charge. The actual battery voltage within each cell of a battery bank varies, depending on whether it is being charged or discharged, and whether it is standing open-circuit (unconnected) or not.

For single cells, the voltage generally ranges from 1.75 to 2.5 volts, with 2.1 volts nominal. So a fully charged six-cell lead-acid battery terminal voltage is 12.6 volts-not 13.8! We can and do float the terminal voltage at 13.0 to 14.5 volts, but the actual battery voltage, after the surface charge is removed, settles down to 12.6 volts. Keep this in mind when running RF gear. Almost all commercial RF transmitters spec their amplifiers at 13.8 volts. Running the same radio from your battery bank will produce a lower RF output. You can really see that one

volt drop, especially in high-power RF equipment. All the same conditions that affect the results in hydrometer readings also raise their ugly heads in terminal voltage measurements, especially a very high charge current.

There's a lot going on with batteries, but I'm not quite done yet! Just as we have learned that batteries come in different voltages and capacities, they also come in different percentages of acid. We have 1300, 1280, and 1265 batteries. If your local friendly battery person asks you which kind you want, tell him 1280. What do these numbers tell? They indicate the full charge specific gravity acid concentration.

A fully charged 1300 battery reads 1.300 on the hydrometer. Likewise, a fully charged 1280 shows 1.280 on the hydrometer. Golf cart batteries and your Exide HC-27-106 battery are 1280 batteries. All the very large batteries built for heavy industrial use are 1300 batteries, as are the batteries for electric personal carriers, tow motors, and floor sweepers. The batteries your local phone

company uses are 1265, which have a life of over 25 years. The lower concentration of electrolytic acid will not eat away at the insides as fast as a higher one would.

## **Last Word on Battery Testing**

How do you test a battery to find out if it is up to par? Charge it up and then discharge it at the recommended rate. Next, plot the results to find out if the battery can deliver its rated capacity. This is not practical for most of us, especially in measuring a large battery bank. At many larger battery shops, they use a load meter to check each battery they sell. It's simple to use. You load the battery down at three times the total amp/hr rating of the battery for 15 seconds. A good battery will hold its terminal voltage to at least 9.6 volts. For example, to test one 6 volt Exide battery, load the battery at 660 amperes for 15 seconds. The battery must hold its terminal voltage at 4.8 volts (half the required 12 volt rating) to pass...

Working with your own energy production is a fulfilling pastime.

Checking battery fluids, cleaning and checking cables, and removing accumulated dust and debris becomes routine.

## **Taking Precautions**

When working around batteries, you must be aware of the danger, as deadly as it is silent, of voltage. While most of us use a nominal system voltage of 12 volts, some of you may use higher battery systems of up to 140 volts DC. It's easy to become careless, especially if your system is 12 volts, and I know of no one who has been zapped with 12 volts. But imagine-you're wearing a ring, get it across two terminals, and 1000 amps of current flow through it. Instant meltdown! You lose a finger!

Gas is another major danger. Because of gassing, you must provide adequate ventilation for the storage room. Besides the unpleasantness of the "dry throat" you get from the presence of free hydrogen, there's always the excitement of the Hindenburg effect: it only takes 4% hydrogen and one match to demonstrate it. If

you don't have tight connections at the battery terminals, or if you drop a wrench between the posts, you don't even need the match! Even if only one battery, instead of the whole bank, explodes, you've still got a good chance of getting a cardiac arrest from the shotgun noise at close quarters, or some nasty burns from sprayed acid.

Carelessness and batteries don't mix—not quietly, that is. For goodness' sakes, use an eye shield—battery acid is the third major danger.

#### Let's See Those Pix!

I still have not received any photographs of QRPer shacks. Looks like I'll have to be the first and use one of my shacks. That means I'll have to clean it up first! I'll be reprinting the HW-8 handbook. I'm still looking for mods for the HW-8 and the newer HW-9, and I hope to have the books done by the spring of '89.

Next month I'll have a lot of odd and ends to distract you from the cold. Miss one month and you'll miss a lot. Slow that electric meter down, go QRP!

Number 28 on your Feedback card

## HAM HELP

## Your Bulletin Board

We are happy to provide Ham Help listings free, on a space-available basis. To make our job easier and to insure your listing is correct, please type or print your request clearly on a full (8½" x 11") sheet of paper. Double-space and use upper and lower case letters where appropriate. Also, write numbers carefully—a 1, for example, can be read as an I or an i or a 7 as a 1. Thanks for your cooperation.

Need schematic, etc., for Delco 30BCTS1 from Sam's AR-339. Will pay postage and copying costs.

> Lisle T. Hines K2QLA 11 Meadow Drive Homer NY 13077

Wanted: Manual and schematic for KLM Linear Amplifier, Model No. 30-140B. Will gladly pay copying and mailing costs.

Edward Moiser N8IOV 4376 Coolidge Road Coleman MI 48618 I am looking for the following items (please state price and/or condition in correspondence): Two MRF-455 A transistors; MFJ-962, -949C, -941D, or 989 antenna tuner; five 7868 tubes; ten #12 6-V lamps for Bogen PA Amps; one bandswitch each for the Panasonic RF 2800 receiver #RSR 98W or equivalent; one printer and disk drive for the Tandy Color Computer II Model 26-3127; and one Z-80/CPM and Modem Board for the Apple IIe Pro System.

Mike Adams
Haney Vo-Tech Center
3016 Hwy 77
Panama City FL 32405

I'm looking for manuals and/or schematics for a Heathkit model GR-91 receiver. I'll gladly pay for any costs incurred.

> Darrel L. Daley KL7DN Radio Free Vermont P.O. Box 445 Putney VT 05346

Does anyone know where I might purchase a new or used TK-1/BC-1 memory backup power supply for my Kenwood TR-7800? It is a small AC adapter that plugs into a wall outlet and retains the memory frequencies in the TR-7800. Thank you.

Michael A. Horn 516 Union Place Fremont OH 43420

I would like to hear from anyone who uses the Tandy Model 100 and 200 for amateur radio. I am interested in any programs, especially satellite tracking.

Scott Harvey KA7FVV 2517 N. Calispel Spokane WA 99205

Gentlemen: I just "inherited" an old Gonset Communicator II, 2 meter AM transceiver! Someone removed the mike jack and didn't sketch the location of the wires. I need a schematic for this unit. If you have one, I'd be glad to pay for copying and mailing costs. Thanks for helping me get this old rig back on the air!

Bert Voth WA@PWE 802 Forest Drive Olathe KS 66061 Wanted: Machine language program for the TRS-80, model 1, level 1 or 2 (prefer level 1) to TX/RX RTTY via expansion port. Will pay nominal fee.

Frank Brinson 5113 Richland Ave. Chillicothe IL 61523

I need a schematic for Swan 350B and schematic/manual for Swan HF 700S transceiver. Will pay for any charges. Thanks.

Charlie Wallace Rt. 3, Box 223K Big Pine Key FL 33043

I need a service manual or at least a schematic for an Edgecom System 3000A VHF FM 2 meter transceiver. I will pay for copying or other costs.

> Chuck Crowley K5BER 215 Clower Ave. Long Beach, MS 39560

I need a diagram and part values for my ailing Hickock Teaching Aids Scope, Model OSK-4, and will be glad to reimburse someone for copying costs and postage.

> Paul Hinkamp W8YOU 1304 Ashly Ct. Midland, MI 48640

\*QUALITY PARTS \*DISCOUNT PRICES

\*FAST SHIPPING

10 AMP SOLID STATE RELAYS

ELECTROL# S2181 CONTROL: Rated 5.5 to 10 Vdc (will operate on 3-32 Vdc). LOAD: 10 amp @ 240 Vac 2 1/4" X 1 3/4" X 7/8"

CAT# SSRLY-10B \$9.50 each QUANTITY DISCOUNT

10 for \$85.00 • 25 for \$175.00 50 for \$300.00 • 100 for \$500.00



Variable rate strobe kit, flashes between 60 to 120 times per minute. Will operate on either 6 or 12 Vdc depending upon how you wire the circuit.

Comes complete with P.C. board and instructions for easy assembly. CAT# STROBE-1 \$7.50 each

CASSETTE MECHANISM

Alpine cassette transport mechanism. Includes stereo tape head,

WALL

TRANSFORMERS

8 Vdc @ 200 ma. CAT# DCTX-820 \$2.25

6 Vdc @ 750 ma. CAT# DCTX-675 \$3.50

9 Vdc @ 250 ma. CAT# DCTX-925 \$2.50

12 Vac @ 930 ma. CAT# ACTX-1293 \$3.50

18 Vac @ 1 arrp. CAT# ACTX-1885 \$3.50

SWITCHES

Push to close. RATED: 0.1 amp switching, 0.25

65¢ each + 10 for \$6.00 + 100 for \$50.00

10 POSITION MINI-ROTARY

amp carry current, P.C. mount. CAT# PB-8

ITT PUSH BUTTON

Grayhille 56P36-01-1-10N-C

the panel depth. P.C. pins.

Mini rotary switch. Non-shorting.

1 deck, 10 positions. .125° dia.

shaft X 375" long. 377" behind

ITT MDPL series, 3/4" X

key cap. S.P.S.T. N.O.

1/2" gray rectangular

ALL PLUG

OUTLET

DIRECTLY

INTO 120 VAC

Mitsubishi # MET-3RF2B 13.2 Vdc motor, belt, pulleys, capstan, fastforward, rewind and eject actuator. Does not include amplifier section. 6 1/2" X 5 1/4" X 1 3/4".

CAT# CMEC-5 \$7.50 each

### **PIEZO** WARNING DEVICE

Murata Erie # PKB8-4A0 High pitched audible slarm. Operates on 3 - 20 Vdc @ 20 ms. 1\* righ x 7/8" dia, P.C. board mount. CAT# PBZ-84 \$1.75 such

## XENON TUBE

I\* long flas/mube with 3 1/2" red and black leads, ideal for electronic flash or strobe projects. CAT# FLT-3 2 for \$1.00

#### NICKEL-CAD BATTERIES (RECHARGEABLE)

SPECIALII AAA SIZE Panasonio# P-18AAA 1.2 volt @ 180 MAh CAT# NCB-AAAX \$1.50 each 10 for \$13.50 + 100 for \$125.00



AA SIZE \$2.00 each 1.25 volts 500 mAh CAT# NCB-AA AA SIZE \$2.20 each WITH SOLDER TABS CAT# NCB-SAA C SIZE \$4.25 EACH 1.2 volts 1200 mAh CATE NCB-C D SIZE \$4.50 each

CAT# NCB-D

#### TRANSISTORS TYPE CASE PRICE PN2222 NPN TO-92 5 for 75e 2N2904 PNP TO-5 3 for \$1.00 PNP TO-18 3 for \$1.00 2N2906 PNP PN2907 TO-92 5 for 75e 2N3055 NPN TO-3 \$1.00 each PN3569 NPN TO-92 5 for 50e. NPN TD-92 5 for 75e 2N3906 PNP TO-92 5 for 75¢ 2544400 NPN TO-92 5 for 75e 25/4402 PNP TD-92 5 for 75¢ 2N5400 TO-92 4 for \$1.00 TO-3 \$2.00 each \$2.00 each MJ2955 PNP TO-3 \$1.50 each MJE2955T PNP TO-220 75¢ each MJE3055T NPN 75¢ each TO-220 TIP30 PNP TO-220 75¢ each TIP31 NPN 75¢ each TO-220 PNP TO-220 75¢ each TIP41 75e each 75¢ each TIP42 PNP TO-220 TIP121 NPN. TO-220 75¢ each

TIP126 PNP TO-220 75¢ sach WIDE BAND AMPLIFIER NEC# UPC1651G. 1200 Mhz @ 3 db. Gain: 19db @ 1+500 hz. 5 volt operation.

Small package 4mm dia, X 2.5 mm thick. CAT# UPC-1651 2 for \$1.00 10 for \$4.50 - 100 for \$35.00 N-CHANNEL MOSFET

IRF-511 TO-220 case CAT# IRF 511 \$1.00 each • 10 for \$9.00 LARGE QUANTITY AVAILABLE

OPTO SENSOR

U shaped package with mounting

10 for \$4.50 + 100 for \$40.00

ears. 1/6" opening. 3/4" mounting



#### CAT# MRS-10 \$2.50 each HALL EFFECT SWITCH MICROSWITCH# 48E3 Stanted keyboard switch with half effect sensor. Snaps into 5/8" square chassis hole. Hall effect sensor slides easily from switch and can be used in other applications. CAT# HESW 4 for \$1.00 10 for \$2.00 . 100 for \$15.00 SPDT PUSHBUTTON Marguard# 1843 Rated 6 amps @ 125/250 Vac. Black plastic pushbutton. CAT# PB-18 \$1.65 each - 10 for \$1.50 each

10 for \$65.00

## LED'S

STANDARD JUMBO DIFFUSED T 1-3/4 size RED CATE LED-1 10 for \$1.50 • 100 for \$13.00 GREEN CATH LED-2 10 for \$2.00 - 100 for \$17.00 YELLOW CATE LED-3 10 for \$2.00 - 100 for \$17.00 FLASHING LED

with built in flashing circuit operates on 5 volts... CAT# LED-4 10 for \$9.50 GREEN \$1.00 each CAT# LED-4G 10 for \$9.50 BI-POLAR LED

Lights RED one direction, GREEN the other. Two leads. CAT# LED-8 2 for \$1.70 LED HOLDER Two piece holder. CATE HLED 10 for 65e

#### RELAYS 12 VOLT D.C. COIL S.P.D.T.

Ormona G2E-184P 4 Amp contacts 335 ohm coil. Sugar cube size. .61" X .42" X .44" high. P.C. mount with pins on DIP spacing. CAT# RLY-787 \$1.50 each 120 VOLT A.C. - D.P.D.T.

GUARDIAN# 1220U-04 10 Amp contacts. 1,100 ohm coil 1.700° X 1,578° X 1.687\*, Clear

CAT# RLY-228 \$3.50 each

## CALL OR WRITE FOR OUR FREE CATALOG OVER 4000 PARTS!



MAIL ORDERS TO: ALL ELECTRONICS P.O. BOX 567 VAN NUYS, CA 91408

TWX-5101010163 (ALL ELECTRONIC)

OUTSIDE THE U.S.A. SEND \$2.00 POSTAGE FOR A CATALOG!!

## ORDER TOLL FREE 800-826-5432

FAX: (818)781-2653 MINIMUM ORDER \$10.00 QUANTITIES LIMITED CALIF. ADD SALES TAX USA: \$3.00 SHIPPING

FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING. NO C.O.D.



CIRCLE 194 ON READER SERVICE CARD

## IRON POWDER and FERRITE PRODUCTS

AMIDON

Fast, Reliable Service Since 1963

Small Orders Welcome

Free 'Tech-Data' Flyer

Toroidal Cores, Shielding Beads, Shielded Coil Forms Ferrite Rods, Pot Cores, Baluns, Etc.

12033 OTSEGO STREET, NORTH HOLLYWOOD, CALIFORNIA 91607

CIRCLE 4 ON READER SERVICE CARD

# 7/3/3/4/10 N

SUNDAY, JAN. 29, 1989 THE ODEUM **VILLA PARK, ILLINOIS** 


DOORS OPEN 8 A.M. TO 3 P.M.

SUPER GRAND PRIZE! THE ICOM IC-781 PLUS HOURLY PRIZES

> **3 PRIZE STUBS** WITH EVERY ADVANCE TICKET

TICKETS: \$4.00 Advance \$5.00 At Door

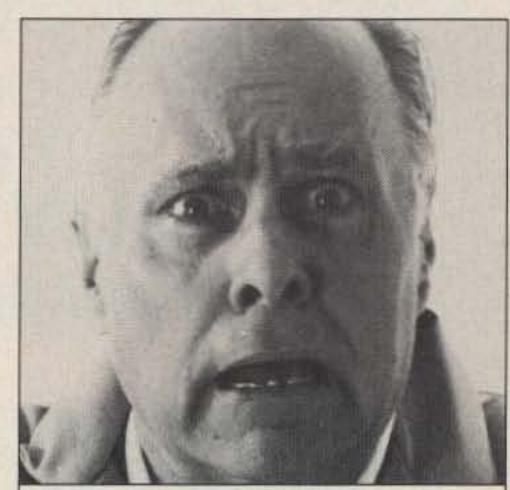SEND SASE TO: W.C.R.A. P.O. BOX QSL WHEATON, IL 60189 INFO PHONE: (312) 629-8006 TALK-IN: 146.01/.61 MHz



An OM of yours borrowed a prized copy of 73, and now it's among the missing. Let Uncle Wayne help restock the issues in your almost complete 73 yearly volumes from July 1980 to the present.

Write us today for the copies you need from July 1980 to the present only. Sorry, but we've sold out all but a few collector's copies prior to July 1980.

JULY 1980 to present . . . \$4.00 each including postage and handling

73 Amateur Radio

ATTN: Uncle Wayne 70 Route 202-N Peterborough, NH 03458

## here is the next generation Repeater


## MARK 4CR

The only repeaters and controllers with REAL SPEECH!

No other repeaters or controllers match Mark 4 in capability and features. That's why Mark 4 is the performance leader at amateur and commercial repeater sites around the world. Only Mark 4 gives you Message MasterTM real speech • voice readout of received signal strength, deviation, and frequency error . 4channel receiver voting . clock time announcements and function control • 7helical filter receiver • extensive phone patch functions. Unlike others, Mark 4 even includes power supply and a handsome cabinet.

Call or write for specifications on the repeater, controller, and receiver winners.
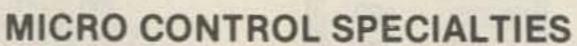
> TELEX: #4932256 KENDECOM FAX: #5083737304



Division of Kendecom Inc.

23 23 Elm Park, Groveland, MA 01834 (508) 372-3442

Create messages just by talking. Speak any phrases or words in any languages or dialect and your own voice is stored instantly in solid-state memory. Perfect for emergency warnings, club news bulletins, and DX alerts. Create unique ID and tail messages, and the ultimate in a real speech user mailbox - only with a Mark 4.



2 meters 220 440

## IATED RADIO

OVERLAND PARK, KANSAS 66204







STATIONS-ESTATES ETC. Call 913/381-5900 FAX 913 648 3020

SEND \$2 FOR CATALOG AND WHOLESALE LIST





## Early Reservation Information

- · General Chairman, Bill McNabb, WD8SAY
- Giant 3 day flea market Exhibits
- License exams Free bus service
- CW proficiency test
   Door prizes

Flea market tickets and grand banquet tickets are limited. Place your reservations early, please.

## Flea Market Tickets

A maximum of 3 spaces per person (non-transferable). Tickets (valid all 3 days) will be sold IN ADVANCE ONLY. No spaces sold at gate. Vendors MUST order registration ticket when ordering flea market spaces.

Special Awards

Nominations are requested for 'Radio Amateur of the Year,' 'Special Achievement' and 'Technical Achievement' awards. Contact; Hamvention Awards Chairman, Box 964, Dayton, OH 45401.

## License Exams

Novice thru Extra exams scheduled Saturday and Sunday by appointment only. Send FCC form 610 (Aug. 1985 or later) - with requested elements shown at top of form, copy of present license and check for prevailing ARRL rates (payable to ARRL/VEC) to: Exam Registration, 8830 Windbluff Point, Dayton, OH 45458

· Asst. General Chairman, Ed Hillman, N8ALN

## 1989 Deadlines

Award Nominations: March 15

Lodging: April 7

License Exams: March 26

Advance Registration and banquet: USA - April 4 Canada - March 31

Flea Market Space:

Spaces will be allocated by the Hamvention committee from all orders recieved prior to February 1. Express Mail *NOT* be necessary! Notification of space assignment will be mailed by March 15, 1989.

## Information

Oeneral Information: (513) 433-7720 or, Box 2205, Dayton, OH 45401 Lodging Information: (513) 223-2612 (No Reservations By Phone)

Lodging

Please write to Lodging, Dayton Hamvention, Chamber Plaza, 5th & Main Streets, Dayton, OH 45402 or refer to our 1988 Hamvention program for lodging information which includes a listing of hotel/motels located in the surrounding areas of Dayton. Reservations for the surrounding area will then become the responsibility of the individual.

HAMVENTION is sponsored by the Dayton Amateur Radio Association Inc.

## Advance Registration Form

Dayton Hamvention 1989 Reservation Deadline – USA-April 4, Canada-March 31 Flea Market Reservation Deadline: February 1

Enclose check or money order for amount indicated and send a self addressed stamped envelope.

Please Type or Print your Name and Address clearly.

Ho	w Many	
Admission (valid all 3 days)	@ \$10.00*	\$
Orand Banquet	@ \$20.00**	\$
Women's Luncheon (Saturday) (Sunday)	@ \$7.00 @ \$7.00	\$
Flea Market  (Max. 3 spaces)  Admission ticket must be ordered with flea ma	\$25/1 space \$50/2 adjacent \$150/3 adjacent arket tickets <b>Total</b>	\$
* \$12.00 at door	** \$22.00 at door,	if available

Name		Charles and the same of the sa
Address		WE THE REAL PROPERTY.
City	State	Zip

Make checks

payable to -

**Dayton HAMVENTION** 

Mail to -

Dayton Hamvention Box 2205 Dayton, OH 45401

## AMERITRON

## SYMBOL OF ENGINEERING INTEGRITY. . . QUALITY WORKMANSHIP. . . RELIABLE LONG-LIFE PERFORMANCE



## AL-80A LINEAR AMPLIFIER

The AL-80A will provide a signal output that is within 1/2 "\$" unit of the signal output of the most expensive amplifier on the market—and at much lower cost.

The Ameritron AL-8OA combines the economical 3-500Z with a heavy duty tank circuit to achieve nearly 70% efficiency from 160 to 15 meters. It has wide frequency coverage for MARS and other authorized services. Typical drive is 85 watts to give over 1000 watts PEP SSB and 850 watts CW RF output. A new Pi-L output circuit for 80 and 160 gives full band coverage and exceptionally smooth tuning.

Size: 151/2"D. x 14"W. x 8"H. Wgt. 52 lbs.



## AL-1200 LINEAR AMPLIFIER

3CX12OO TUBE

Full legal output with 100 watts drive.

## AL-1500 LINEAR AMPLIFIER

Full legal output with 65 watts drive.

The cooling system in both amplifiers keeps the tube safely below the manufacturers ratings even when operating at 1500 watts output with a steady carrier. The filament supply has inrush current limiting to insure maximum tube life.

Size: 181/2"D. x 17"W x 10"H. Wgt. 77 lbs.



## AL-84 LINEAR AMPLIFIER

The Ameritron AL-84 is an economical amplifier using four 6MJ6 tubes to develop 400 watts output on CW and 600 watts PEP on SSB from 160 through 15 meters. Drive required is 70 w typical, 100 w max. The passive input network presents a low SWR input to the exciter. Power input is 900 watts. The AL-84 is an excellent back-up, portable or beginner's amplifier.

Size: 111/2"W. x 6"H. x 121/2"D. Wgt. 24 lbs.

## ATR-15 TUNER

The Ameritron ATR-15 is a 1500 watt "T" network tuner that covers 1.8 through 30 MHz in 10 dedicated bands. Handles full legal power on all amateur bands above 1.8 MHz.



Five outputs are selected from a heavy duty antenna switch allowing the rapid choice of three coaxial lines, one single terminal feed or a balanced output. An internal balun provides 1:1 or 4:1 ratios (user selectable) on the balanced output terminals.

A peak reading wattmeter and SWR bridge is standard in the ATR-15. It accurately reads envelope powers up to 2KW.

Size: 6"H. x 131/4"W. x 16"D. Wgt. 14 lbs.

## RCS-4 FOR CONVENIENT INSTALLATION

No control cable required.
Selects one of four antennas.

VSWR: under 1.1 to 1 from 1.8 to

30 MHz.

Impedance: 50 ohms.

Power capability: 1500 watts average, 2500 watts PEP

maximum.

## **Remote COAX Switches**



## FOR SPECIAL APPLICATIONS

Selects up to five antennas.

Loss at 150 MHz: less than .1 dB.

VSWR: under 1.2 to 1 DC to 250

MHz.

Impedance: 50 ohms.

Power capability: 5 kW below 30 MHz, 1 kW at 150 MHz.

Available at your dealer. Send for a catalog of the complete AMERITRON line.

## AMERITRON

9805 Walford Avenue • Cleveland, Ohio 44102
For more information: (601) 323-9715 • Technical inquiries: (216) 651-1740

## HOMINGIN

## Radio Direction Finding

Joe Moell PE KØOV PO Box 2508 Fullerton, CA 92633

## Quads And Yagis: The Winners' Choices

Here in Southern California, all but one of our monthly hunts are on the 146 or 220 MHz bands, and almost all competitors use a small beam, either a quad or a yagi, as the primary radio direction finding (RDF) antenna. The mast either goes through the window and is fastened to the door handle with some sort of bearing lash-up, or there's a hole in the roof with a thrust bearing and a compass rose at the bottom of the mast.

Why would anyone choose such an unwieldy RDF setup? After all, it's large and cumbersome compared to loops, L-Pers, SuperDFs, Dopplers, and other available schemes. The answer, as we'll see, is that it's a simple but very effective solution to a number of RDF problems.

Beam hunting is so simple that you may already have everything you need to get started: a quad or yagi antenna, a receiver with an S-meter, and an attenuator to knock down strong signals. (More on attenuators in a future column.)

Intuitively, you've probably guessed that the way to hunt with this setup is to swing the beam around until the hider's signal peaks on the meter. Then drive in the direction that the beam points. It's almost that simple, which is one reason why beam hunting is so popular. The S-meter will bounce around with the usual mobile flutter as you whiz down the road, but with a little practice you'll find it easy to take bearings on the fly, using "eyeball integration" of the meter reading.

The hilly terrain and large boundaries of southern California hunts make a high gain antenna system a necessity. Starting points are on hilltops, and as often as not the hider is dozens of miles away running a couple of watts from a canyon or river bed. It's important to keep hearing the signal after coming off the hilltop, if it's at all possible. There is nothing more frustrating than having to continue to go in the direction from which the signal was last heard, hoping to catch some signal again soon. After all, the idea

is to hunt down the signal, not to hunt for the signal.

A 4-element optimum-spaced quad has a gain of around 10 dB. Other popular RDF antenna systems for the 100 to 500 MHz range have no gain, and may even be quite lossy. You can make the sensitivity of your beam hunting setup even greater by adding a lownoise preamp in the antenna line.

## Beams Shine in Multipath

VHF RDF is much more difficult when the signal is bounced around by nearby and distant features of the terrain. The signal may arrive at the hunter's location from more than one direction, via more than one path. Sorting out the direct and reflected bearings takes good equipment and lots of practice.

In a severe multipath situation, a sharp beam provides more information than a Doppler or other RDF system. As you rotate your beam around a full 360 degree turn, each of the apparent signal sources gives a peak on the S-meter. You can mark all these directions on your map for comparison with previous and future bearings along the way. (You do have good maps, don't you?)

Your S-meter will tell which of the signal sources is strongest. Usually that's the direct signal, and smaller peaks are reflections, but there are enough exceptions



Photo A. A yagi—an excellent starter antenna for RDFing.

to that rule to make for some really tough hunts.

#### Select Your Polarization

If you've experimented with OSCAR satellites, you know how important it is for transmitting and receiving antennas to have the same polarization. It's every bit as important in T-hunting. On most hunts, the hider is free to select any polarization, so hunters must be prepared.

Incorrect polarization of your RDF antenna not only diminishes the level of the direct signal, it also increases the relative level of unwanted multipath. That's because when the signal bounces, the polarization often shifts. If the fox is

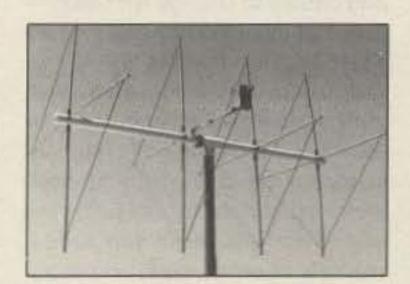


Photo B. The wire-quad antenna.

horizontally polarized and your RDF antenna is vertical, you'll lose 10 to 20 dB system gain for directly received signals. You'll have less loss than that for reflections, because some scattered back signal components will be near vertical. The net effect is to accentuate the reflections.

The ability to select polarization is an important reason why beams are the most popular VHF RDF antenna. The antennas in the photos are oriented for vertical polarization, but are designed so that they can be readily changed to horizontal (or angles in between). Smart hunters always check polarization at the beginning of the hunt, then check again later on in a clear signal area while closing in. Many other RDF systems, including Dopplers, have only vertically polarized antenna elements.

### Quad or Yagi?

What kind of beam is best for two meter RDF? Is a quad better than a yagi? Many hams think so, though each type is commonly used. A quad is half as tall as a same-band vertically polarized yagi. This can either give lower profile on the vehicle, or allow a higher center of radiation for the same maximum height—take your choice.

Proximity to the vehicle roof affects performance of a quad less than a yagi. Best of all, a quad has about two dB more gain than a yagi for the same boom length. Clearly, the performance of a lightweight quad makes it worth the effort to build it.

Quad elements don't have to be diamond-shaped like the ones in Photo B. You can make the sides parallel and perpendicular to the car top (box configuration) for a lower profile, if you feed the driven element properly for the desired polarization. You could also make the elements triangular (delta quad) or even circular. Local hunters have used all of these types successfully. The circumferences of the elements remain the same fractional wavelengths, no matter what the shape.

While some other RDF systems require a carrier-type signal to work properly, a beam/receiver setup will get bearings on any signal that the receiver can detect. AM, FM, SSB, CW—no matter. Just rotate the antenna and peak up the S-meter or listen for the cleanest, strongest signal.

Want to hunt ATV? Simply aim the beam for the least snow and fewest ghosts. What about pulsed noise sources? Peak them up on the meter or by ear using the receiver's AM or SSB mode.

## Radon Gas?

So what do you tell those passers-by who ask if you're using that big antenna to watch the ball game? I've been tempted to say that it's a setup for searching out radon gas levels, and I'd be happy to check out their houses for a small fee!

Actually, such encounters are an excellent way to get good PR for our hobby. Anyone who is interested enough to ask will probably be interested in hearing about ham RDF and the public service it can provide. If the ham turns the inquirer away with a flip answer, he'll just reinforce the "hams are weird nerds" stereotype.

On the other hand, I know there's no time to explain the finer points of transmitter hunting to a stranger while you're on a timed hunt. So I came up with an information sheet on T-hunting and ham radio that you can give to curious onlookers, and let you get on with your hunt. I'll be glad to send you one (then you can make your own copies), if you'll send me an SASE. While you're at it, tell me about the hunts in your town.

Next month this column will feature more on beam hunting, including plans for building a popular hunting quad. Continued from page 8

has a tremendous lot to offer America. Indeed, with technology being the future and with consumer electronics being the engine that drives technologyand the real power behind the Japanese miracle-we have no other practical plan for regaining our technological superiority other than through a reborn American amateur radio community.

It's a big responsibility and we're only 200,000, so there's no room for anyone to beg off. You're not too busy. You're not too short of money. You're not too old. Every one of our 200,000 active hams needs to accept the responsibility to make a difference. When one single person can make a difference, imagine what 200,000 can do!

## Stay Informed!

Less than half of the active hams are reading 73. I need your help to get 100% of them reading 73. What can I do to get 'em? YOU tell me. I don't ask that 73 make money, only that it doesn't lose so much that it goes out of business. You can help by finding out why your ham friends are not reading 73 and letting me know.

Do I need to change 73? The previous owners tried cutting my editorials and that wasn't the answer. Please start asking and then drop me a note. Is 73 boring? Yes, of course I want to publish more construction projects-and we've got some coming. But finding 'em these days is tough. I may have to have them translated from the Japanese ham magazines, since they're doing most of the building today.

If we had more advertising we'd have a fatter magazine—the way it used to be ten years ago. Ask the advertisers why they are not advertising in 73. I know that those who are, tell me their ads sell their products for them. Getting people to change isn't easyand that includes non-advertisers as well as non-readers.

If any of you are involved with your educational systems in your states, I'd love to have you arrange for me to talk with the decision makers about instituting an eight-year course in the fundamentals of electronics, communications and computers-grades 5-12. Every youngster in America should take such a course-and it should be fun. I've got a way, as I've written several times, to

provide it so that there isn't any need to train science teachers first. It's a sneaky approach that I believe can bring us tens to hundreds of thousands of new hams a year. We could use 'em. I haven't found any educators who don't believe my system will work-and I've discussed it with over thirty college presidents so far.

Now, those pesky parents-I've a plan for getting them onto their kids' cases too. This involves producing some videos to help parents come to grips with their responsibilities as parents. You haven't even seen a PBS program covering this problem-and it needs the impact of a video.

The average father talks with his children less than 15 minutes a day. We see what a fantastic difference parental involvement makes with our new Asian families, where their kids are running circles around American kids. We need some videos to help parents work with their kids and to motivate them. Such a series should make a bundle. Anyone want to work with me on the project?

You might note that none of my proposed solutions involve any heavy government investment.

No spending. To the contrary, my proposals will end up saving the government billions. This could go toward reducing the deficit, but being practical about that I expect that as soon as a billion is saved that liberal congressmen will find at least two ways to spend every dollar saved.

I believe that tens of billions in military and government expenses could be saved, if we set up a federal commission to protect whistle-blowers. Virtually every government and military ham I meet has a long list of horror stories of flagrant waste, but they don't dare say anything about it or they're washed up. And why bother if the billions saved will just be thrown into some other stupid government project or given to some dictator to keep in Switzerland for his retirement?

So let's work toward rescuing amateur radio-toward a temporary block on further frequency losses-toward rebuilding our school radio club infrastructure. If we can get the 200,000 active hams all reading 73, perhaps we can make all this happen. Do you know any other approach that has even a slight chance of working? 73



## A BOVE AND BEYOND

## VHF and UHF Operation

Pete Putman KT2B 3335 Fieldstone Dr. Doylestown PA 18901

#### QTH K2OWR

As I write, the fall tropo season is well underway, and the September VHF Contest is a pleasant memory. Although conditions were not as good as expected, our multi-operator group still had a great time, and even got a few licks in during the Sunday aurora session on 6, 2, and 220.

Understandably, most of the SCORE members were a bit weary after the ambitious Chincoteague trip in June! Disassembling and reassembling your station every few months is a lot of work and gets to be a bit tedious. However, a few of the gang decided to have a "low-key" effort from Bill Radice K2OWR's QTH in the hills of northwestern New Jersey, using the long-dormant K2XR callsign.

Only Bill, Ivars KC2PX, and I were present from the June operation. Jerry Meckenberg K2JWE agreed to put in a few hours, and we recruited three new operators from the local area-Leroy KA2UHS, Harry N2GUF, and Bill KB2ENE. None had any practical VHF/UHF contesting experience, but all turned in a first-class job with a little bit of encouragement.

Bill's house is in an enviable lo-

cation, sitting near the top of a long ridge 1,000 feet in elevation that forms the northern side of the Pequest River valley. It's a rural, scenic location, with great views in every direction except west by southwest. Bill designed his own modular house and (with great difficulty) managed to get all the pieces in place at the edge of a steep cliff. It was just a matter of time before two towers sprang up, just up the hill, topping out at 70 and 50 feet, carrying a full load of yagis for 50, 144, 432, and 1296 MHz.

Most of the antennas and one tower trailer from Chincoteague wound up in Bill's yard. It was a simple matter to round up the other trailer, plus additional yagis from Ivars, and our "low-key" effort shifted into high gear rather quickly. The band complement expanded to include everything from 50 MHz through 2304 MHz, with dedicated stations on each band scattered throughout the house, and even down the hill in a mobile camper.

## **Murphy Strikes**

Murphy hit us hard the Friday before the contest. I had spent over an hour repairing the direction indicator in a CDR CD-45 rotor, and installed it atop the W-67 crank-up to support 2 x 19 yagis on 220, 4 x 25 yagis on 2304, and 4 x 23 yagis on 903.



Photo A. Putting together the 220/903/2304 station.

All went well until the tilt cable that everyone was "going to get around to replacing someday"snapped with the tower at about 45 degrees. Our microwave hopes nearly went up in smoke with a thunderous crash, as the tower dropped back into its cradle and (A) smashed two of the 2304 antennas beyond recognition; (B) severely bent several elements on the 220 yagis; (C) snapped four elements clean off the 903 array; and (D) completely flattened a 5foot aluminum ladder.

To make matters worse, the impact sheared the base of the CD-45 completely off the rotor, cracking the bottom casing in half and stripping two bolt threads-an hour's work completely wasted. Leroy, Bill, and I just stood there in shock for about five minutes. It was amazing that none of us was lying prone on the ground waiting for the rescue squad!

No sense feeling sorry for ourselves. I pulled out my portable machine-shop-in-a-toolbox and began repairing the 2304 yagis, that were ready for the scrap heap. Leroy set about removing the other yagis so the mast could be extracted, and Bill made sure the heroic ladder got a decent burial for its valiant efforts under attack.

The W-51 trailer had originally been intended to carry the 4 x 17 element 2 meter array that proved so successful at Chincoteague, but our near disaster quickly changed those plans. Believe it or not, we were able to repair all of the antennas and reinstall everything atop the W-51 in just under two hours, snatching a victory of sorts from the jaws of defeat. Just for laughs, we added a single 7-element yagi for 440 MHz FM before the W-51 was cranked up-this time with no sudden surprises from Mr. Murphy!

### Loaded for Bear

The station complement was competitive: 1 kW to a Hy-Gain 8-element yagi atop the 50-foot tower on 6; 1 kW to 19 elements at 70 feet on 2; 600 watts to the 2 x 19 array at 60 feet on 220; and 2 x 22 elements with 700 watts on 432 at 70 feet. In addition, we ran 20 watts to 92 elements on 903; 60 watts to 92 elements on 1296; and finally, 8 watts to 100 elements (give or take a few) on 2304. We were truly loaded for bear!

I printed up a few explanatory

sheets to give our three new operators a quick introduction to the world of grid chasing, including the principles of making schedules on other bands to boost the overall grid count. Boy, did they pick that up quickly! As the contest evolved, Bill's QTH resembled a firehouse with operators constantly running between 2/ 432/1296 upstairs and 220/903/ 2304 downstairs with little slips of paper. I suggested turning a spare mast into a fireman's pole to save time. (The suggestion was promptly ignored.)

The 6 meter stalwarts were about a hundred feet down the road, ensconced in Bill's comfy camper and connected to the "firehouse" by an intercom system. Some of the guys preferred to sprint down the road to the trailer with sked information for exercise. This system worked! Our own record was working W9IP/2 from FN24 on four different bands within the space of five minutes, using both the intercom and "winged messenger" systems.

Conditions and activity levels were fairly typical for September. Plenty of grid squares were active, but the number of signals was down considerably from June. Tropo conditions were mediocre at best, except for an occasional "ping" from the Midwest, such as a contact we made on 432 into EN72 (southern Michigan) that came as a bolt out of the blue. The number of stations we had to operate made up for the activity levels, as we spent considerable time making long-haul contacts on 903, 1296 and 2304.

### Help from the Aurora

Finally, it came, as the oldtimers say it always does-an aurora. At first it was just a whisper here and there on 2 meters, then a crescendo of raspy CW signals burst from the noise, signing 8, 9, and even 0 prefixes. The chase was on! Since we had some "hashing" on 2 meters from the 220 station, we decided to stay on 6 and 2 only for the duration of the contest. And a good move it was, as our first 31 contacts during the aurora on 2 yielded 21 new grid squares-even ten in a row at one point!

Six meters was even crazier, working as far west as EN34 in western Wisconsin. But there was plenty of activity to the north and northeast, as we made contacts in

Continued on page 102

## Coaxial Dynamics Model 81000-A **Directional RF Wattmeter**

## Enter the competition.

here's no question that an accurate RF wattmeter can be one of the more useful test instruments in your shack. With it, you can measure forward and reflected power, transmission line loss, and VSWR of antennas and coaxial lines. You can find many varieties of wattmeters in the marketplace, but by far the most accurate are those using directional couplers. To make such a meter usable at any frequency, the detecting element should couple to a section of transmission line of, ideally, 50Ω. This would allow insertion in virtually any section of a  $50\Omega$  line without affecting the impedance of that line.

Great idea, and it has already been done. (Do thoughts of a winged creature flying about Cleveland, Ohio, suddenly cross your mind?) For many years the industry standard for  $50\Omega$ thruline directional-coupler wattmeters has been the Bird Model 43. You can find them everywhere in a variety of applications. Owners of clean used Model 43s often sell them used for more than they paid for them! This phenomenon is due largely to two factors: (1) Bird's almost annual price increases and (2) the virtual absence of competition.

## New Kid in Town


Well, hold on to your hats. Coaxial Dynamics, also of Cleveland, produces the Model 81000-A inline directional-coupler wattmeter that works just as well as a Model 43. The design of this instrument is essentially identical to the Model 43: a 50Ω transmission line section runs through the shell. A rotatable diode coupler/detector element is inserted into a socket coupled at the midpoint of the line section. You can rotate it 180 degrees for reading forward or reflected power.

Many different elements are available to cover the 2-1300 MHz range, with power levels from 100 milliwatts to 10 kilowatts (yes-10,000 watts), using various Quick Match connectors. Coaxial Dynamics also makes special elements for use with larger line sections, such as 1 %" and 31/8" hard-line. And here's the kicker: All Coaxial Dynamics plug-in elements are fully interchangeable with Model 43 elements. This means that if you already own a Model 43 or two, your existing elements

will fit the 81000-A. . and its elements will drop into your Model 43 nicely. Clever!

There are other similarities between the two lines. One of these is the grouping of elements by power and frequency range (Bird lists them as "Table XX Elements;" Coaxial Dynamics as "Schedule XX Elements"), and the many different kinds of connector options (Bird calls theirs "Quick

 Change," Coaxial Dynamics "Quick Match").



Is the Model 81000-A a Bird "clone?" Not entirely. For one thing, the meter scale is considerably larger. Next, the surface contains a small mirror band to make readings easier. On the other hand, the movement is 30 microamperes full scale, like the 43 (the elements otherwise couldn't be swapped). The housing is about 10% larger than the 43, and the front panel slopes backwards from bottom to top, which allows more ambient light to fall on the meter scale. Also, the 81000-A carries two spare elements on the rear panel, as opposed to the sides.

The elements are also similar, being identical in size but different in case markings and colors. One disadvantage of the Coaxial Dy-



The Coaxial Dynamics Model 81000-A. Note the large, easy-to-read meter scale.

Elements: \$48-\$95 namics elements is their identification system; a five-digit code refers to one of the three Schedules. This is more of a serial code than an identifying mark. For example, a Bird 250 watt 50-125 MHz slug is called a

Coaxial Dynamics, Inc.

Cleveland, OH 44135

216-267-2233

1-800-COAXIAL

Price Class: \$159

15210 Industrial Parkway

How well does it work? Very well. In fact, I was unable to detect any differences between a late-model 43 and the 81000 using

250B, whereas the

same slug in the Coax-

ial Dynamics line is

called an 82025.

both brands of slugs on 50, 144, 432, and 903 MHz. Measurements were made at 10, 25, 100, and 250 watt levels. I didn't bother to print the data simply because there was no significant variation at any power level.

I did check for insertion loss at 1296 MHz using a 25 watt coaxial resistor. With 25 watts of RF from an LT-23S through a short piece of 9913, I connected the 81000-A at the end of the line and installed a Termaline load at the other port of the 81000-A. I measured no reflected power, so insertion loss is certainly better than 1:05:1, as the owner's manual claims.

### Verdict

The burning question is: Why should you buy a Model 81000-A instead of a Model 43? Two possible answers are that: (1) You prefer

the color blue to gray, or (2) You'd like to save about \$20 on the meter and from \$2-\$6 on the more common elements. If you plan on picking up a wattmeter with 3 elements-say, one for HF and 2 for VHF-you'll wind up pocketing about \$30 over a comparably-equipped Bird Model 43. This price difference may or may not be offset by other factors, such as customer support. The 81000-A, however, will do the job every bit as well. 73

## Coaxial Dynamics Model 81000-A **RF Wattmeter Specifications**

Power Rating Depends on element used 50Ω nominal Impedance Insertion VSWR 1.05:1 max. with "N" connector Weight 3.6 lbs.

Element weight 3 oz.

Accuracy 5% of full scale 5" W x 71/4" H x 4" D Size

## DEALER DIRECTORY

## **CALIFORNIA**

#### Burbank

New HAM store open and ready to make a DEAL. We carry all lines, ship UPS, and are open Sunday. A-TECH ELECTRONICS, 1033 Hollywood Way, Burbank CA 91505; (818) 845-9203.

#### San Diego

Hard to find parts, surplus electronics, standard line items. Hams, hobbyists, industrial professionalsfrom nuts & bolts to laser diodes... Electronically speaking, Gateway's got it! M-F 9-5:30 Sat. 9-5. **GATEWAY ELECTRONICS, 9222 Chesapeake** Drive, San Diego CA 92123; (619) 279-6802.

## **COLORADO**

#### Denver

Hard to find parts, surplus electronics, standard line items. Hams, hobbyists, industrial professionalsfrom nuts & bolts to laser diodes... Electronically speaking, Gateway's got it! M-F 9-5:30 Sat. 9-5. GATEWAY ELECTRONICS, 5115 N. Federal Blvd. #32, Denver CO 80221; (303) 458-5444.

### Englewood

Rocky Mountain Amateur/Shortwave Specialists. Ten-Tec, Yaesu, JRC-NRD, Sony, MFJ, KLM, and other fine gear. New and Used. Visa/MC. Antennas, Books, and Discount Prices, too! ALLIED APPLI-ANCE & RADIO, 4253 South Broadway, Englewood, CO 80110; (303) 761-7305.

## DELAWARE

### New Castle

Factory authorized dealer! Yaesu, ICOM, Ten-Tec, KDK, Kenwood, AEA, Kantronics, Santec. Full line of accessories. No sales tax in Delaware. One mile off 1-95. DELAWARE AMATEUR SUP-PLY, 71 Meadow Road, New Castle DE 19720; (302) 328-7728.

## **FLORIDA**

### Stuart

Radio Shack 10 meter ham transceiver, computers, scanners, and all other equipment. Nationwide. Best prices. COTRONICS INC., Radio Shack Dealer, 2200 S.E. Federal Highway, Stuart, FL 34994 1-800-848-3004.

## IDAHO

### Preston

Ross WB7BYZ has the largest stock of amateur gear in the Intermountain West and the best prices. Call me for all your ham needs. ROSS DIS-TRIBUTING, 78 S. State, Preston ID 83263; (208) 852-0830.

## KANSAS

#### Wellington

We have it! ASTRON, BUTTERNUT, ENCOMM, HEATHKIT, GORDON WEST, KANTRONICS, LASER COMPUTERS, MFJ, RADIO SHACK, TEN-TEC, VALOR ANTENNAS & more. Small town service with discount prices. DANDYS, 124 So. Washington, Wellington, KS. 67152, (316) 326-6314.

## MISSOURI

#### St. Louis

Hard to find parts, surplus electronics, standard line items. Hams, hobbyists, industrial professionalsfrom nuts & bolts to laser diodes... Electronically speaking, Gateway's got it! M-F 9-5:30 Sat. 9-5. GATEWAY ELECTRONICS, 8123 Page Blvd., St. Louis MO 63130; (314) 427-6116.

## **NEW HAMPSHIRE**

#### Derry

Serving the ham community with new and used equipment. We stock and service most major lines: AEA, Astron, B&W, Cushcraft, Encomm, Hy-Gain, Hustler, ICOM, Kenwood, KLM, Larsen, Mirage, Mosley; books, rotors, cable and connectors. Business hours Mon.-Sat. 10-5, Thursday 10-7. Closed Sun./Holidays. RIVENDELL ELECTRONICS, 8 Londonderry Road, Derry NH 03038; (603)434-5371.

## **NEW JERSEY**

### Eatontown

Electronics Supplies for amateurs. Ten-Tec, Barker and Williamson, Cushcraft, Hustler, etc. ATKIN-SON AND SMITH, 17 Lewis St., Eatontown NJ 07724 (201) 542-2447.

### Lyndhurst

A full service Ham Radio Store! Discount sales and service on most major brands. Monday to Friday 10:00am to 7:00pm, Saturday 9:00am to 3:00pm 14 mile south of Rt.3. ABARIS SYSTEMS, 227 Stuyvesant Avenue, Lyndhurst NJ 07071; (201) 939-0015.

### Park Ridge

Bergen County's oldest and only SWL/Amateur dealer. Specializing in HF receiving systems, antennas, ham/SWL accessories, books. Kenwood, JRC, Yaesu, Icom. 1 mile from Garden State Parkway Exit 172. Tu-Fri 10-5; Sat 10-3. GILFER SHORTWAVE, 52 Park Avenue, Park Ridge, NJ 07656; (201) 391-7887.

## **NEW YORK**

### Jamestown

Western New York's finest amateur radio dealer

featuring ICOM-Larsen-AEA-Hamtronics-Astron. New and used gear. VHF COMMUNICA-TIONS, 915 North Main St., Jamestown NY 14701, (716) 664-6345.

#### New York

New York City's Largest Full Service Ham and commercial Radio Store. BARRY ELECTRON-ICS, 512 Broadway, New York NY 10012; (212) 925-7000.

## NORTH CAROLINA

#### Greensboro

9a.m. to 7p.m. Closed Monday. ICOM our specialty-Sales & Service. F&M ELECTRONICS, 3520 Rockingham Road, Greensboro NC 27407; (919) 299-3437.

## OHIO

#### Columbus

Central Ohio's full-line authorized dealer for Kenwood, ICOM, Yaesu, Ten-Tec, Info-Tech, Japan-Radio, AEA, Cushcraft, Hustler, and Butternut. New and used equipment on display and operational in our 4000 sq.ft. store. Large SWL department, too. UNIVERSAL AMATEUR RADIO, 1280 Aida Drive, Reynoldsburg (Columbus) OH 43068; (614) 866-4267.

## PENNSYLVANIA

#### Trevose

Authorized factory sales and service. KENWOOD, ICOM, YAESU, featuring AMERITRON, B&W, MFJ, HYGAIN, KLM, CUSHCRAFT, HUS-TLER, KANTRONICS, AEA, VIBROPLEX, HEIL, CALLBOOK, ARRL Publications, and much more. HAMTRONICS, INC., 4033 Brownsville Road, Trevose PA 19047; (215) 357-1400. FAX (215) 355-8958. Sales Order 1-800-426-2820.

## TEXAS

### Dallas

In Dallas since 1960. We feature Kenwood, ICOM, Yaesu, AEA, Butternut, Rohn, amateur publications, and a full line of accessories. Factory authorized Kenwood Service Center. ELECTRONIC CENTER, INC., 2809 Ross Ave., Dallas TX 75201; (214) 969-1936.

### Houston

Hard to find parts, surplus electronics, standard line items. Hams, hobbyists, industrial professionalsfrom nuts & bolts to laser diodes... Electronically speaking, Gateway's got it! M-F 9-5:30 Sat. 9-5.GATEWAY ELECTRONICS, 9890 Westpark Drive, Houston TX 77063; (713) 978-6575.

### Southwest Houston

Full line of Equipment and Accessories, in-house service, Texas #1 Ten Tec Dealer! MISSION COMMUNICATIONS, 11903 Alief-Clodine, Suite 500, Houston TX 77082; (713) 879-7764.

## DEALERS

Your company name and message can contain up to 25 words for as little as \$300 yearly (prepaid), or \$175 for six months (prepaid). No mention of mail-order business permitted. Directory text and payment must reach us 60 days in advance of publication. For example, advertising for the April '88 issue must be in our hands by February 1st. Mail to 73 Amateur Radio, Rebecca Niemela, WGE Center, Peterborough, NH 03458.

## **Measure Up With Coaxial Dynamics** Model 81000A RF Directional Wattmeter

Model 81000A is a thoroughly engineered, portable, insertion type wattmeter designed to measure both FWD/RFL

C. W. power in Coaxial transmission lines. 81000A is comprised of a built-in line section, direct reading 3-scale meter protected by a shock-proof housing. Quick-match connectors, plus a complete selection of plug-in elements, gives the FRONT RUNNER reliability, durability, flexibility and adaptability with a two year warranty.

Contact us for your nearest authorized Coaxial Dynamics representative or distributor in our world-wide sales network.



COAXIAL DYNAMICS, INC.

15210 Industrial Parkway Cleveland, Ohio 44135 216-267-2233 1-800-COAXIAL Telex: 98-0630

Service and Dependability... A Part of Every Product

CIRCLE 186 ON READER SERVICE CARD



## Protect Your Antenna & Home!

A must in every shack. Now you can scan...heavy Wind Gust...Wind Direction... Temp Hi/Lo and more! Get your own computerized weather station at an incredibly low, affordable price.

The New Azimuth Weather Star by Digitar is a high quality, powerpacked weather computer, just loaded with features. Gives you accurate weather data ... right in your shack ... at the touch of a finger. Created with the latest CMOS micro-chip technology.

You Get All These Exciting FUNCTIONS & FEATURES with the TW2... HANDY, COMPACT SIZE: 21/2" × 21/2" × 11/2"

LARGE, EASY TO READ LCD READOUT Gives you Wind Speed . Records High Wind Gusts . Wind Direction . Wind Chill Factor . Outside Present Temperature (Remote sensor included) . Records High/Low Temperature . Reads in Fahrenheit, Celsius, Miles/Hour, or KM/Hr \* Programmable Scan! \* Operates on DC (Batteries Not.)


Included) or AC with Optional adaptor. Your TW2 SYSTEM COMES COMPLETE WITH \* TW2 Weather Computer . Anemometer & Wind Vane made of high impact, UV

resistant plastic, with stainless bearings & shaft for years of trouble free service • 40 Feet of Cable lead-in with connectors • Outside Temperature Sensor . & Mounting Hardware .



And it's MADE IN AMERICA! YOUR SATISFACTION GUARANTEED! Or return in 10 days for a complete refund!

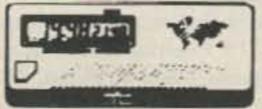1 YEAR Limited WARRANTY from Manufacturer!



Your SPECIAL FREE BONUS

Order TODAY!

Get the famous Azimuth World Time, Dual-Zone 24-Hour Station Clock. Displays Local & Intl. in 15 Cities Zones Retail Value \$29.95

## **ACT NOW! SEND TODAY!**

### **AVAILABLE OPTIONS:**


 Stainless Desk Stand (DSK22) @ \$9.95
 Rechargeable Ni-Cad Battery Pack (BP3) @ \$7.95 • 40 Ft. Extension Control Cable (EC40) @ 14.95 (Requires 2) • AC Power Adaptor (PS12) @ \$9.95 • Please add \$3.95 for Shipping & Handling of TW2. For each option add \$1.00.

### CREDIT CARD ORDERS ONLY

CALL TOLL-FREE 1-800-882-7388 TODAY!

Other Service Call 213-473-1332


(9AM to 6PM PST) Ca. Res. add sales tax.

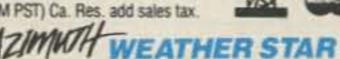

11845 W. Olympic Bl. Suite 1100, Los Angeles, CA 90064 USA (Dept. A8)

ALSO AVAILABLE AT HENRY RADIO & ALL HAM RADIO OUTLETS!

**CIRCLE 158 ON READER SERVICE CARD** 

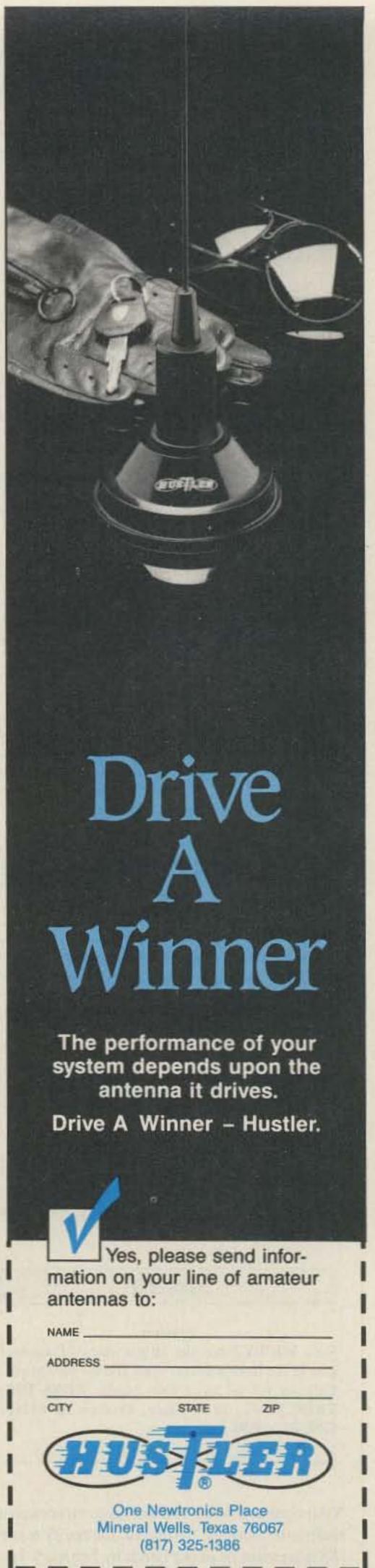

CIRCLE 269 ON READER SERVICE CARD

## INDUSTRIAL PRINTER SALE

IDEAL FOR INVOICING, BUSINESS FORMS, PACKET RADIO, TELETYPE, OR ANY HEAVY PRINTING APPLICATION. WHY USE A GOOD LETTER QUALITY DOT MATRIX OR DAISY WHEEL FOR PRINTING INVOICES AND FORMS, MONITORING PACKET & RTTY WHEN A HEAVY DUTY DOT MATRIX PRINTER IS ALL THAT IS NECESSARY?

## VICTOR 5080

- MADE FOR CONTINUOUS DUTY
- 4 INTERFACES STANDARD: PARALLEL, RS-232. TTY, IEEE-488
- BI-DIRECTIONAL
- 80 COLUMN—100 CPS
- . FANFOLD OR ROLL PAPER
- RE-INKABLE RIBBON
- HANDLES 6 PART FORMS
- COMMERCIALLY SOLD AT\$1195.00



## NEW & FACTORY SEALED \$109.00

FOR MORE INFORMATION, OR TO ORDER, PLEASE CALL:

## HORIZON MANUFACTURING

# 690 GREENLEAF AVE., ELK GROVE, IL 60007 #

PHONE: 312-439-1234 FAX: 312-439-3799

ALL ORDERS SHIPPED BY UPS IL AND TX RESIDENTS INCLUDE APPLICABLE SALES TAX

CIRCLE 308 ON READER SERVICE CARD

# AUTOPATCH

TH REPEATER CONTROLLER



## **CES 510SA-II FEATURES:**

- Simplex sampling for fixed station operation
- Half or full duplex operation for repeater use
- Variable sample window and sample rate in simplex
- Mobile access via single- or multidigit DTMF codes
- Remotely programmable functions include connect code, activity timers, and toll restrict
- Supplies programmable logic for use as a repeater controller, including XMIT hang time, TOT, CW ID interval, and courtesy beep
- Remote base station operation enabled by special security code
- Reverse patch capable, automatic
- ring-out upon receipt of an inbound call Four selectable CW IDs for repeater or patch time out, patch on, and error message

Regardless of your autopatch requirements, the CES Model 510SA-II will supply reliable, long term service for amateur fixed station or remote repeater sites.

Make The RIGHT Connection



Communications Electronics Specialties, Inc.

931 S. Semoran Blvd./Suite 218 Winter Park, FL 32792





P.O. Box 6522 220 N. Fulton Ave. Evansville, IN 47719-0522

Store Hours MON-FRI: 9AM - 6PM SAT: 9AM - 3PM **CENTRAL TIME** 

SEND A SELF ADDRESSED STAMPED **ENVELOPE (SASE) FOR NEW AND USED EQUIPMENT SHEETS** 

WARRANTY SERVICE CENTER FOR: ICOM, YAESU, TEN-TEC

FOR SERVICE INFORMATION CALL (812) 422-0252 MONDAY - FRIDAY 9:00 AM - 12:00 NOON



## FT-747GX

- 100 Watts of Economical Performance
- Dual VFO's, 20 Memories
- · Receives from 100 kHz-30 MHz
- . Built-in CW Filter + More

## **ICOM**

## IC-32AT

- New Dual Band HT
- RX-138-174 MHz 440-450 MHz
- TX-140-150 MHz 440-450 MHz
- . 5 Watts Output on Both Bands
- . Full Duplex & 40 Memories





### PARAGON

- Full Featured Synthesized HF Transceiver
- General Coverage Receiver
- . 100w Output
- . SSB, CW, FSK, Optional FM
- 62 Programmable Memories
- · Made In USA



## FT-212 RH

- 2 Meter Mobile
- · Optional, Internal Digital Voice Recorder
- RX 138-174 MHz
- TX 144-148 MHz
- 45 Watts Output
- FT-712 RH Available for 70cm



### IC-228A

- 25 Watt, 2 Meter FM Mobile
- RCV 138-174 MHz
- TX 140-150 Mhz
- 20 Memories






## VHF/UHF **AMPS**

- Overdrive Protection
- . 5 Year Warranty, 6 Months on RF Transistors
- · All Units have GaAsFET Receive Pre-amps
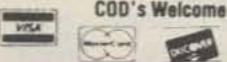
### TERMS:

Prices Do Not Include Shipping. Price and Availability Subject to **Change Without Notice** Most Orders Shipped The Same Day










## & Kantronics

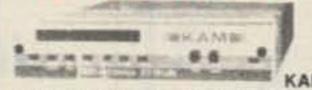

- Packet, WEFAX, ASCII, AMTOR. RTTY, CW
- . Simultaneous Operation on HF



. Dual Band Mobile 140-149 995 MHz/ 440-450 MHz

 21 Programmable Memories . 25 Watts Output on Both Bands Loaded with Extra Features



### MFJ-1278

- Multi-Mode Data Controller
- . Packet, RTTY, ASCII, CW. WEFAX, SSTV. Contest Memory Keyer

Orders and Price Checks Call 800-523-7731

Indiana and Information Call 1-812-422-0231

## "The '850 Found a New Friend"



## The industry standard RC-850 Repeater Controller can now talk with your computer.

And there's so much for them to say!

The '850 computer interface improves the management of your voice repeater system. It allows you to command and program interactively from your terminal or personal computer using a MODEM or packet TNC. Even preview and edit repeater messages by typing words from the controller's vocabulary directly into message slots.

Retrieve and catalog data relating to your site measurements, equipment status, and repeater and command activity. Download and print out the information programmed into your controller. And view your system "front panel" on your computer screen.

You'll find the RC-850 controller on the leading voice repeaters around the world. ACC pioneered remote programming of repeaters - and continues to pioneer with remote computer access. While the rest of the world just talks about catching up, ACC continues to lead the way in advanced repeater technology.

Now, with its computer interface, the '850 can be best friends with your computer.



advanced computer controls, inc.

2356 Walsh Avenue, Santa Clara, CA 95051 (408) 727-3330

CIRCLE 1 ON READER SERVICE CARD

## CONVERTERS . HF LINEAR AMPLIFIERS



AMATEUR TELEVISION CONVERTERS ATV2 420-450 \$ 44.9 \$ 44.95 Kit ATV3 420-450 (GaAS-FET) \$ 49.95 Kit. ATV4 902-928 (GaAS-FET) \$ 59.95 Kit

AUDIO SQUELCH CONTROL for ATV \$ 39.95 Kit

2 METER VHF AMPLIFIERS 35 Watt Model 335A. \$ 79.95 Kit 75 Watt Model 875A \$119.95 Kit Available in kit or wired and tested

HF AMPLIFIERS per MOTOROLA BULLETINS Complete Parts List for HF Amplifiers Described in the MOTOROLA Bulletins. AN758 300W ..... \$160.70 EB63 140W ... \$ 88.65 AN762 140W \$ 93.25 EB27A 300W \$139.20

AN779 20W ...... \$ 83.79 EB104 600W .. \$448.15

NEW!! 300 WATT 10-150 MHz Amplifier

POWER SPLITTERS and COMBINERS (2-30MHz) 600 Watt 2-Port \$ 59.95 1200 Watt 4-Port \$ 69.95

100W 420-450 MHz PUSH-PULL LINEAR AMPLIFIER - SSB-FM-ATV KEB67-PCB (PC Board) \$ 18.00

KEB67-I (Manual)

For detailed information and prices, call or write for our free catalog.

\$ 5.00

**FERROXCUBE DEVICES** 

VK200-20/4B RF Choke 56-590-65-3B Ferrite Bead HEAT SINK MATERIAL

Model 99 Heat Sink(6.5x12x1.6) \$ 22.00 CHS-6 Copper Spreader(6x6x1/4) \$ 18.00 Add \$2.00 additional shipping.

We also stock Hard-to-Find parts

CHIP CAPACITORS METALCLAD MICA CAPACITORS RF POWER TRANSISTORS MRF141G. \$209.20 MRF151G. \$186.80 MINI-CIRCUIT MIXERS SBL-1... \$ 6.50 SBL-1X. \$ 7.95 ARCO TRIMMER CAPACITORS

Add \$ 2.00 for shipping and handling



Communication Concepts Inc. 121 Brown Street \* Dayton, Ohio 45402 \* (513) 220-9677



CIRCLE 99 ON READER SERVICE CARD



## SAVE TIME and MONEY with THE HAZER

## Bring things down for safety and convenience.

Never climb your tower again with this elevator system. Antennas and rotator mount on HAZER, complete system trams tower in vertical upright position. Safety lock system operates while raising or lowering. Never can fall.

Complete kit includes winch, 100 ft. of cable, hardware and instructions. For Rohn 20 and 25 G Towers.

Hazer 2-Heavy duty alum. 12 sq. ft. load Hazer 3-Standard alum. 8 sq. ft. load Hazer 4-Heavy galv. steel 16 sq. ft. load

\$297.00 ppd. \$213.00 ppd.

#### \$278.00 ppd. NEW for ROHN 45 and 55 Towers

Hazer 8-Heavy duty galv. steel 16 sq. ft. load Ball Thrust Bearing TB-25 for any of above

CALL \$64.50 ppd.

Send for free details of aluminum towers specifically engineered for use with the Hazer. Two sizes; M-13 (13" wide) and M-18 (18" wide). All bolted construction, no welds. Easy to install hinge base, walk up erection. Complete tower UPS or air freight shippable. Pre-assembled or kit form.

Satisfaction guaranteed. Call today and charge to Visa, MasterCard or mail check or money order.

GLEN MARTIN ENGINEERING INC. Rte 3, Box 322 Boonville, MO 65233

(816) 882-2734 FAX 816-882-7200 CIRCLE 72 ON READER SERVICE CARD

## "MADE IN U.S.A."



SINCE

We've been supplying quality crystals since 1965...long before the flood of cheap imports.

We're still supplying quality crystals with:

- QUICK TURNAROUND
- LOW PRICE
- HIGH QUALITY

TO SOLVE YOUR CRYSTAL **PROBLEMS** CATALOG:



## JAN CRYSTALS

P.O. BOX 06017 FORT MYERS, FL 33906 (813) 936-2397



TOLL-FREE: 1-800-237-3063

IN FLORIDA: 1-800-226-XTAL FAX ORDERS: 1-813-936-3750

## BARTER 'N' BUY

QSLs TO ORDER. Variety of styles, colors, card stock. W4BPD QSLs, PO Drawer DX, Cordova SC 29039. BNB260

THE DX'ERS MAGAZINE Up-to-date, informative, interesting. Compiled and edited by Gus Browning W4BPD, DX-CC Honor Roll Certificate 2-4. Send for free sample and subscription information today. PO Drawer DX, Cordova SC 29039. BNB261

QSL CARDS- Look good with top quality printing. Choose standard designs or fully customized cards. Better cards mean more returns to you. Free brochure, samples. Stamps appreciated. Chester QSLs, Dept A, 310 Commercial, Emporia KS 66801. BNB434

SUPERFAST MORSE CODE SU-PEREASY. Subliminal cassette. \$10. LEARN MORSE CODE IN 1 HOUR. Amazing new supereasy technique. \$10. Both \$17. Moneyback guarantee. Free catalog: SASE, Bahr, Dept 73-1, 2535 Marietta, Palmbay FL 32905. BNB531

SB-220 OWNERS!-Enhance performance-add new features. 17 stepby-step mods which include: tuned-input 6- and 160-meter operation, heavyduty power supply mods, full QSK operation, solid-state bias control, and many more. Source of parts included. One time 50% rebate for new mods submitted and two free updates. 10 pages of tech info on the 3-500Z. Order today-\$10 per copy plus \$1 postage. SASE for info. Bob Kozlarek WA2SQQ, 69 Memorial Place, Elmwood Park NJ 07407. BNB581

WRITTEN EXAMS SUPEREASY. Memory aids from psychologist/engineer cut studytime 50%. Novice, Tech, Gen: \$7 each. Advanced, Extra: \$12 each. Moneyback guarantee. Bahr, Dept 73-1, 2535 Marietta, Palmbay FL 32905. BNB624

COMMUNICATIONS BATTERIES NiCd Packs/Inserts/Rebuilding, Exact Replacement Packs: Yaesu FNB2/ Wilson BP4 \$22.95, Santec 142/ 1200(3 pin) \$23.95, Commercial Packs-All Types, Call. Replacement Battery Inserts: ICOM: BP2/CM2 \$18.95, BP3/CM3 \$16.95, BP5/CM5 \$24.95, BP7/BP8/Rap \$29.95, Kenwood: PB21 \$13.95, PB24 \$21.95, PB25/25H/26 \$25.95, Azden: 300 \$21.95, Standard BP1/C118/Pace MX-BT2 \$25.95, Tempo: S1/270 \$23.95, S1,2,4,5,/450 \$23.95, S15 \$24.95, Yaesu: FNB9 \$14.95, FNB4/4A \$33.95, TenTec 2991 \$24.95, Santec: KTBP \$16.95, KTBP2 \$23.95, KTBPH \$24.95, Rebuilding: Add \$4 to insert price for factory rebuilding, or send pack for quote. S.A.S.E./catalog. In PA add 6%. M/C & VISA add \$2/order.

Add \$3 Shipping per order. Phone: (814) 623-7000 (9 to 7). Ask about replacement ducks, telescopic & mobile antenna. CUNARD ASSOCIATES. Dept. 7, R.D. 6 Box 104, Bedford PA 15522. BNB628

ROSS \$\$\$\$\$\$ NEW January SPECIALS: KENWOOD TS-140S. \$789.90; TS-440S, \$1039.90; TM-2530A, \$389.90; TW-4100A, \$474.90; TM-721A, \$619.90; ROBOT 450C. \$664.99; 800H, \$329.99; ALLIANCE HD-73, \$114.90; AEA PK-232, \$287.50; BT-1, \$79.90; MP-20, \$89.99; ICOM IC-27A, \$334.99; IC-3200A, \$497.99; IC-735, \$939.90; IC-2KL, \$1699.90; Yaesu FT-109RH, \$276.99; FT-726R, \$799.99; FT-747GX, \$657.50; MFJ-989B, \$279.90. ALL L.T.O. (Limited Time Offer) LOOKING FOR SOMETHING NOT LISTED?? CALL OR WRITE. Over 8780 ham-related items in stock for immediate shipment. Mention ad. Prices cash, F.O.B. PRESTON. WE CLOSE AT 2:00 P.M. MONDAYS & ALL DAY SATURDAY. ROSS DISTRIBUTING COMPANY, 78 SOUTH STATE, (P.O. Box 234H), PRESTON ID 83263. 208-852-0830. BNB654

COMPUTER CODE PROGRAM for IBM PC. New. Does most everything and more! Best value. \$12. Moneyback guarantee. Free details: SASE. Bahr, Dept 73-1, 2535 Marietta, Palmbay FL 32905. BNB691

CHASSIS AND CABINET KITS SASE: K3IWK, 5120 Harmony Grove Road, Dover PA 17315. BNB698

ROSS \$\$\$\$\$\$\$ USED January SPECIALS: KENWOOD PS-30, \$134.90; TR-8400/WMC-46TTM, \$229.90; VFO-240, \$159.90; TM-401A/ TU-3, \$279.90; TH-415, \$269.90; COLLINS KWM-2, \$499.90; 312B-4, \$259.90; ICOM IC-471H, \$799.90; IC-271H/WPS-35, \$799.90; PS-20, \$158.90; IC-740/W, PS-35, EX-242,241,FL-45, \$695.90; ROBOT 400 & RGB T.V., \$359.90; YAESU FRG-7, \$179.90; FRV-7700A, \$75.90. LOOK-ING FOR SOMETHING NOT LIST-ED?? CALL OR WRITE, WE HAVE OVER 315 USED ITEMS in stock. MENTION AD. PRICES CASH, FOB PRESTON. WE CLOSE AT 2:00 P.M. MONDAYS & ALL DAY SATUR-DAY. ROSS DISTRIBUTING COMPA-NY, 78 SOUTH STATE, P.O. BOX 234H, PRESTON ID 83263; 208-852-0830. BNB709

\$50 PACKET DIGICOM > 64-software based PACKET system for Commodore 64. Software is public domain and requires a modem for the C-64 which is provided by our kit. Board plugs directly into cassette port or remote mounted via cable, both

connectors included. Watchdog timer, reed relay PTT and PTT inversion options included. Power derived from computer. Uses 7910 chip - no alignment required. Switch allows HF or VHF operation. Order KIT#154 for \$49.95 or ASSEMBLY#154 for \$79.95, both include FREE DISC. Add \$2.50 S&H per order. A & A Engineering, 2521 W. La Palma, #K, Anaheim CA 92801; 714-952-2114. MC or VISA accepted. BNB732

HAM TRADER YELLOW SHEETS. In our 27th year. Buy, Swap, Sell ham radio gear. Published twice a month. Ads quickly circulate-no long wait for results. Send #10 SASE for sample copy. \$13 for one year (24 issues). P.O.B. 2057, Glen Ellyn, IL 60138-2057. BNB741

SSSSS SUPER SAVINGS SSSSS on electronic parts, components, supplies, and computer accessories. Free 40-page catalog for Self Addressed & Stamped Envelope. Get on our mailing list. BCD ELECTRO, P.O. Box 830119, Richardson TX 75083 or call 214-343-1770. BNB749

HAM RADIO REPAIR, all makes, models. Experienced reliable service Robert Hall Electronics, Box 280363, San Francisco, CA 94128-0363; 408-729-8200. BNB751

WANTED: Ham Equipment and other property. The radio club of Junior High School 22 NYC, Inc., is a non-profit organization, granted 501(C)(3) status by the IRS, incorporated with the goal of using the theme of ham radio to further and enhance the education of young people. Your property donation or financial support would be greatly appreciated and acknowledged with a receipt for your tax-deductible contribution. We sponsor the "Classroom Net" on 7.238 at 1200 UTC daily and encourage your QSL for our weekly award. Please write us at: PO Box 1052, New York, NY 10002, or call our round-the-clock hotline: (516) 674-4072. Thanks! BNB762

COMPUTER CODE COURSE. Apple II +/c/e/GS. C-64/128. 37 Modes, Graphics, 1-100 WPM, menus, proportional spacing, variable frequency, more (\$29.95). With wordprocessor (\$39.95). Manual (\$10). Check/MO. LARESCO, POB 2018-ST, Calumet City IL 60409. 1-312-891-3279. **BNB764** 

INDIVIDUAL PHOTOFACT FOLD-ERS. #1 to #1400, \$4.00. #1401 up, \$6.00. Sam's books, \$7.00. Postpaid. Allen Loeb, 414 Chestnut Lane, East Meadow, NY11554, BNB766

VHF TO MICROWAVE: GaAsFETs. MMICs, transistors, etc. SASE; WA31AC, 7148 Montague St., Philadelphia PA 19135. BNB771

HAMLOG COMPUTER PROGRAM Full features. 17 modules. Auto-logs, 7-band WAS/DXCC. Apple \$19.95. IBM, CP/M, KAYPRO, TANDY, CR8 \$24.95. 73-KA1AWH, PB 2015, Peabody MA 01960. BNB775

WANTED: Sunair GCU-910A or GCU-935 Antenna Coupler. Ray Dunham, 1030 Hillside Ave., Pacific Grove CA 93950. BNB790

**ELECTRON TUBES:** All types & sizes. Transmitting Receiving, Microwave...Large inventory = same day shipping. Ask about our 3-500Z special. Daily Electronics, PO Box 5029 Compton, CA 90224. 800-346-6667. BNB792

KENWOOD 430s OWNERS! Stop Scan stops the scanner on busy frequencies resumes scanning automatically after an adjustable 1-10 second delay. SASE for 1989 catalog. \$19.95 kit. \$29.95 assembled. \$3.50 shipping. JABCO ELECTRONICS, R1 Box 386, Alexandria, IN 46001, BNB794

**VOICEGATE** communications noise reduction with audio squelch, noise reduction, VOX cassette recorder control, 3 adjustable audio filters, & more! SASE for 1989 catalog. \$3.50 for demo tape. \$109.95 complete (till 1/1/89). JABCO ELECTRONICS, R1 Box 386, Alexandria, IN 46001. BNB795

	Barter 'N' Buy advertising must pertain to ham radio products or services.  Individual (noncommercial)
-	for claims made by the advertiser. Liability will be limited to making any necessary corrections in the next available issue. Please print clearly or type (double-spaced).
14	
1	No discounts or commissions are available. Copy must be received in Peterborough by the first of the second month preceding the cover date. Make checks payable to 73 Magazine and send to: Rebecca Niemela, Barter 'N' Buy, 73 Magazine, WGE Center, Peterborough NH 03458.

R-390A RECEIVER PARTS: Info. SASE. CPRC-26 military Manpack Radio, 6 meter FM, with antenna, crystal, handset: \$22.50, \$42.50/pair. CPRC-26 Radio only: \$9.50. Add \$4.50/piece shipping, \$9 maximum. Baytronics, PO Box 591, Sandusky OH 44870. BNB798

QSLs & RUBBER STAMPS—TOP QUALITY! States, World Maps, USA, Key, Shuttle, Globe QSLs. Report Form Rubber Stamps. More! Samples, \$1.00 [Refundable With Order]. Ebbert Graphics D-7, Box 70, Westerville OH 43081. BNB807

FLOOD YOUR MAILBOX! You get 100's of radio & electronics specialty catalogs. Send \$5.00, name & address to: Electronic List Services, Dept. B, PO Box 1683, Brookline MA 02146. BNB811

stamps, envelopes and printed letterhead. Large selection at attractive prices. Sandollar Press, PO Box 30726, Santa Barbara CA 93130. BNB812

WANTED: Azden PCS-4500 Regency HR-6, or Genare GTX-600. Reason-

10.10

able. Jim, 469 Jayson Avenue, Pittsburgh PA 15228. BNB814

WANTED: Yaesu FT-625RD, FT-627RA, or FT-680R. Also wanted: ICOM IC-505, IC-551, IC-551D, IC-560, or IC-502A. Reasonable. Jim, 469 Jayson Avenue, Pittsburgh PA 15228. BNB815

SLEP SPECIALS, TEN-TEC, NEW BOXED LATEST PRODUCTION MODELS, USA MADE, 561 CORSAIR II, 562 OMNI V, 585 PARAGON TRANSCEIVERS, 425 TITAN 1.5KW LINEAAR AMPLIFIER, HERCULES II 1KW SOLID STATE LINEAR AMPLIFIER, 229B ANTENNA TUNER, MOBILE HF ANTENNAS, PLUS ACCESSORIES, ALL MODELS, TAKE GEAR IN TRADE, VISA/MC OR CHECK. FOR BEST DEAL, WRITE OR PHONE BILL SLEP, 704-524-7519, SLEP ELECTRONICS COMPANY, HIGHWAY 441, OTTO NC 28763. BNB816

COMPUTERIZE with the "Amateur Radio Operating System." This MS/ DOS based software features auto-log-ging, QSL management, AWARD summaries, Contesting, and MORE. Base System \$39.95, Demo disk \$10.00 (credited). SASE brings details. Fun-

Issue #340

damental Services, 1546C Peaceful Lane, Clearwater FL 34616. BNB817

FREE HAM EQUIPMENT, details \$1. P.O.B. 1631, Arvada CO 80001. BNB818

WANTED: Panasonic RFB600, Grundig Satellite, Magnavox D2999 or any good quality general coverage multi-band receiver. Wade, 657 14th Ave., Prospect Park PA 19076. BNB822

COMMERCIAL HF CW IDENTIFIER: Quartz 10-Minute Timer, Sinewave Oscillator, Complete Instructions, Guaranteed, \$79.95. DMR, 6126 Rex Drive, Dallas TX 75230-3429. (214) 891-0509. BNB823

MACINTOSH, ATARI XL/XE/ST & AMIGA Amateur Radio software. We have several public domain disks available for trade or \$4.00 each. Send business size SASE specifying computer for list. Write WA4EFH, P.O. Box 1646, Orange Park FL 32067-1646. BNB824

PRO2004 OWNERS INCREASE CHANNELS to 400, SCAN SPEED TO 30 CPS. COMPLETE KIT \$35.00. IN-STALLED \$55.00. LESTER JERNI- GAN, P.O. BOX 2406, ORANGE PARK FL 32067-2406. BNB825

WANTED: SB220 or SWAN MARK II Linear—AS IS condition—Samuel Lack W5DOE, Box 577, DeRidder LA 70634. Call collect (318) 463-8964. BNB826

WANTED: Xtal controlled 220 MHz transceivers (such as the model made by Midland). (517) 627-4095. 10100 North Cochran, Grand Ledge MI 48837. BNB827

NEED SCHEMATIC/SVC MANUAL for Hallicrafter SX-140. Will pay cost and parcel. Pedro L. Candelario, Bobadilla JT-1, Levittown, Puerto Rico 00949. BNB828

QUALITY HAM SOFTWARE for the IBM-PC and compatibles. Many share-ware and public domain programs for all aspects of ham radio. Business SASE for catalog. JK&S, Dept. SB, P.O. 50521, Indianapolis IN 46250-0521. BNB829

WANTED: HW-101 and HP-23 for parts. Need not be working. Write stating condition and price. RTO, 4166 Maple St., Berrien Springs MI 49103. BNB830

Number 33 on your Feedback card

## **INDEX: January**

10-10		ASSESSED.	17,17110	U
10 GHz				13
220 MHz				
2 meter injector				1:
7400 quad NAND gate				
7473 dual J-K flip-flop				3
1N23 diode				
2N2222 transistor				
2N3866				
AEA FSTV-430				
AMSAT-OSCAR				9
Atlas				1
attenuator				
AutoSketch				3
bandwidth				9
battery testing	٠.		71-	-7
Bird Model 4381			-	3
boomerang/backfire antenna				
callsign software				4
coil tapping				2
Commodore 64			40-	-4
contest, home-brew				
coordination, repeater				
digital communications book				
Exide batteries			71-	-7
filters				9
graphics software				3
Hamcall	<		1000	4
horn antenna				1
KØOV, Joe Moell				
K3OF, W.C. Cloninger, Jr				1
KC3YB, John R. Somers		-00		5
Kenwood TS-940S		18	, 20,	2
KT2B, Pete Putman				7

Mir	. 9
N4RVE, Steve Roberts	
networking	
NR1A, Douglas Stivison	54
oscillator, audio	
packet	
power supplies	,71
propagation	
quad antenna	. 77
RDF 60	,77
RS 270-326 battery holder	. 35
RS 276-150 board	. 35
RS 279-355 jack	. 36
satellites	. 91
short wave manual	. 54
solar power storage	. 71
spectrum analyzer 44	-45
troubleshooting	, 58
VE1VQ, Dave Marling	. 29
VE6BGL, W.S. Gardiner	. 30
VHF/UHF contesting	
VisiTel modification	
voltage protector 40	1-41
W1XU, Jim Gray	. 92
W8ASF, Fred R. Sharp	. 36
W9NGP, Ed F. Rice	
WA3AJR, Marc I. Leavey, M.D	
WA5ZIB, Andy MacAllister	. 91
W6YUY, Robert E. Bloom	. 18
WB0QCD	. 53
WB6DFQ, Ron Wong	. 35
WB6IGP, C.L. Houghton	
WB8VGE, Mike Bryce	
WB9RRT, Larry R. Antonuk	
yagi 77	, 79



## COMPUTERIZE YOUR SHACK

Control up to eight digital radios simultaneously from your MS-DOS microcomputer! DataCom, Inc. offers a series of software/hardware packages that interface with many current synthesized rigs. These include:

ICOM 735, IC-761, IC-781, IC-R7000, IC-R71A Yaesu 747, 757GX, 757GXII, 767, 9600 Kenwood TS-440, TS-940, TS-140, TS-680, 711, 811, R5000

Datacom couldn't be simpler to install. The user doesn't need to know anything about MS-DOS-the installation program does it all! After installation, the user sets the parameters with menus.

These packages allow complete control of these rigs from the keyboard, and more! Datacom adds:

\*Scan functions added to radios that don't allow this from the front panel.

\*Frequency and associated info memory limited only by disk storage.

\*Tabular screen display of all of the channels stored in memory, along with a full description of each, including:

-mode (LSB, USB, FM, etc.)

-eight character alphanumeric description

-signal bandwidth

\*continuously variable scan delay from 100 milliseconds up

\*a full-featured logging utility

AVAILABLE FOR IBM PC, XT, AT, 80386 256K RAM 1 SERIAL PORT AND 1 FLOPPY MINIMUM

99.95 PROGRAM WITH INITIAL LIBRARIES RS-232 TO TTL INTERFACE ONLY (NEEDED IF DON'T HAVE

MANUFACTURERS INTERFACE) 99.95 EXTERNAL INTERFACE ALLOWS 4 RADIOS INTERNAL PC INTERFACE W/1 SERIAL & 1 RADIO PORT 129.95 (CALL FOR PRICE) SPECTRUM ANALYZER MODULE COMPLETE SYSTEMS INCL. RADIO, INTERFACE, COMPUTER,

(CALL FOR PRICE) AVAILABLE

## DATACOM, INT.

8081 W. 21ST LANE HIALEAH, FL 33016 AREA CODE (305) 822-6028

CIRCLE 147 ON READER SERVICE CARD



Now you can turn free time into powerful code building time. For novice, CW, and advanced

ORDER TOLL FREE: 1-800-346-7283

Or Mail Check, Money Order to: Ca., or info STARTONE ELECTRONICS

662-2659

P.O. Box 404, Aptos, CA 95001-0404

Rush Shipped, 1st-Class Each order add \$3.50 ship./hand.

## **BEST NOVICE KIT! \$19.95**



2 Code Tapes 112 pg Study Guide **FCC Test & Answers** Maps, Charts, Coupons

**BUY BOTH** FOR ONLY

CIRCLE 37 ON READER SERVICE CARD

## fordable Packet



TINY-2 is our new low-cost highperformance standard for packet controllers. Thousands already in use, worldwide. A perfect beginner's unit. Complete, wired \$110 95 and tested, only

BENEFITS and features of both units:

- ☐ Optional personal message system (mini-BBS) Add \$10.00
- ☐ Tiny enough for briefcase/portable, yet large enough for easy experimentation or repair.
- ☐ 1-year limited warranty, excellent customer support.
- ☐ RS-232 and TTL compatible—all connectors supplied.
- ☐ Latest AX.25 software, TCP/IP (KISS) module included.

State



MICROPOWER-2 is our remarkably compact, 18-ounce unit using upgraded TAPR TNC-2 technology that requires less than 40 milliamps! For very portable operation, solar or battery, you need not pay more for a TNC that's about the size of your HT! Was \$179.95, \$159.95 now at a low

☐ Fully compatible with ROSE & NET/

- ROM EPROMs.  $\square$  32K RAM, 32K ROM, 4.9 mHz CPU.
- ☐ Xtal controlled modem, compatible with use on 10m HF/VHF/UHF.

TO ORDER, toll-free with major charge card, call: 1-800-223-3511

Technical support line: 813-874-2980

3652	West Cypress	St., Iampa FL	33607
v2 🗆	MicroPower-2	☐ TNC-220 info.	☐ FREE Packet

Please send:   Tiny 2	☐ MicroPower-2	☐ TNC-220 info.	☐ FREE Packet Catalog.
Name			Call

City Address

Money Back Guarantee. Add \$3. shipping/bandling per order, FL addresses add 6%. Major Credit Card: give number, expiration and signature. FAX: 813-872-8696

CIRCLE 152 ON READER SERVICE CARD

Exp. Date

Card Number

## 73 ADVERTISERS INDEX

R.S	.# page	R.S	.# page	R.S	.# page	R.S	.# page
279	Ace Communications 42		CES Inc		Indiana Hamfest 102	145	QSO Software
355	Ace Communications 97	157	Cleveland Inst. of Electronics 65	358	Intercon Data Systems 55	34	Ramsey Electronics 39
335	Ace Systems		Coaxial Dynamics		International Radio 55	142	RF Enterprises 90
1	Advanced Computer Control 84		Commpute Corp 28	22	Jan Crystals 84		RF Microtech 97
65	Advanced Electronic Appli 95		Communication Concepts 84	245	Jensen Tools & Alloys 55		RF Parts 37, 66
67	Alinco Electronics 104	121	Communications Electronics 34		Jo Gunn Enterprises 65	254	Ross Distributing
194	All Electronics Corp 73	10	Communications Specialist 2	272	Jun's Electronics 101		Sangean America
	Allied Appliance & Radio 65		Connect Systems	94	K9RKA-ATV 55	332	
	Amateur Electronics Supply 56		The state of the s		Kenwood U.S.A. Corp C4		73
		367	Cotronics Inc 52		Kenwood U.S.A. Corp 7		Back Issues 73
	Amidon Associates 73	306	Creative Control Products 65		Kenwood U.S.A. Corp 10		CB to Ten
89	Antennas West	147	Data Com International 87		KW Litho 57		Code Tapes 68
90	Antennas West	310	Davle Tech, Inc		Lindsay Publications 55		Dealer 52
236	Antennas West		Dayton Hamvention 75		Madison Electronic Supply 16		DX Map 68
302	Antennas West 65		Delaware Amateur Supply 78		Maggiore Electronics Lab 47		QSLs
303	Antennas West 65	263	Dentron Radio Corp 15	336	Magnaphase 97		Subscription
304			Digimax	101	Maxcom Inc		Uncle Wayne's Bookshelf 69
	Antennas West 103		Digital Radio Systems Inc 103	114	Metro Printing 57	244	Software Systems 48
107	Antennas West 89		E. H. Yost		MFJ Enterprises 3		
271	Antique Radio Classified 28	291	Electron Processing 70	162	Michigan Radio 88	51	Spectrum Communications 26
328	Applied Digital Research 62		Electronic Equipment Bank 96	348	Micro Computer Concepts 48	183	Spectrum International 97
	ARRL 101		Electronics Book Club 67	295	Micro Cont Specialities 74	37	Star Tone Electronics 87
338	Ashton ITC		Engineering Consultants 102	252	Midland Technologies 48	82	Stone Publishing 65
	Associated Radio 74	324	Epsilon Co		Mission Communications &		T.S. Skogen Etchings 62
	Astron Corporation		Fair Radio Sales 65		Consulting		TAB Books 61
357	ATFab55		GGTE 48	163	Mobile Mark 70		Tandy Parts 33
243			Gilfer Shortwave 23	127	Motron Electronics 103		The Ham Station 83
158	Azimuth Communications 81		GLB Electronics 70	323	National Tower Co		The Meadowlake Corp 89
137	B & B Instruments 16		Glen Martin Engineering 84		Naval Electronics 52		The Radio Works 48
53	Barker & Williamson 70	273	Gordon West Radio 27		Nemal Electronics 97	115	The RF Connection 48
41	Barry Electronics Corp 43	346		292	Omar Electronics 57		Tropical Hamboree 47
42	Bilal Company	327	GTI Electronics 65	96	Orlando Hamcation 51	136	Unadilla/Antennas Etc 52
176	Bird Electronics Corp 101	326	GTI Electronics 48		P.C. Electronics 89	79	Vanguard Labs 57
156	The state of the s	309	Hamtronics 103		P.C. Electronics 53	298	VHF Communications 57
7	Buckmaster Publishing 65		Hamtronics, Inc 25	152	Pac-Comm 87	38	W9INN Antennas 28
365	Buckmaster Publishing 103		Heath Co	178	Pacific Cable Co. Inc 57		Wheaton Hamfest (WCRA) 73
92	Burghardt Amateur Radio 31		Heath Co	366	Packet Products 57		Wi-Comm Electronics 62
	Butternut Electronics 89		Horizon Manufacturing 83	68	Periphex	191	WNW Associates 23
356	C & S Sales Inc 62		Hustler, Inc		Pipo Communications 30		Yaesu Electronics Corp C3
	CB City International 103		ICOM America		QEP's	351	



# SALES





## **WE NOW** HAVE



\*ALL PRICES SUBJECT TO CHANGE







1000	O	W. H. DOLLOW	NA STATE	(S
YAESU FT-767 FT-757II FT-747GX FT-736R FRIG-8800 FRIG-9600 FT-727RH FT-109RH FT-709RH	Super scivilps/at/mic accepts modules for VI- New, improved version 757 NEWII Economy HF XCVR NEWIII multimode VHFIUHF Griff oving rx/10 memsikey entry. Scanning VHF/UHF receiver 2m/440 ht NEW CPUI The first dual band H 220 HT/5w/scanning/memories 2m HT/5w/scanning/memories 440 HT/5w/scanning/memories		LIST 1929 95 1129 95 889 95 1749 95 759 95 699 95 439 95 389 95 389 95	494.95 359.95 329.95
	HOURS TUE WEDS THU FRI	10-6		

Come see our Holiday Specials at our New Location

Ī	FT-23R	Mini 2m HT/DTMF	334.95	289.95
	FT-33R	Mini 220 HT/DTMF	389.95	329.95
	FT-73R	Mini 440 HT/DTMF	349.95	319.95
	FT-211RH	2m 45w autodialer mobile	449.95	399.95
	FT-311RM	220 25w version FT-211RH	439.95	384.95
	FT-7118H	440 35w FM autodialer mobile	479.95	414.95
		Limited number w/ autodial microphone		
	Please note	the 211 series no longer comes from Yaesu with t	he autodial micropi	hone. We
		ed number of them in stock with the autodial mic-		
	FT-212RH	High Tech 45w 2m mobile	459.95	399.95
	FT-712RH	High Tech 35w 70cm mobile	499.95	434.95
			19152	
		WE STOCK A COMPLETE LINE OF VAERU AC	CESSORIESI	

7777	FOR INFORMATION, RECOMMENDATIONS AND OU (313) 469-4656.			
KENWOOD		LIST	OURS	
TS-940s	Super griff ovrg your. The Ultimate Weapon! w/at	2499.95	2119.95	
	without at	2269.95	1924.95	
TS-930s	Gruf ovrg xicyr/ps/notch wist DXcellencel	1199.95	1014.95	
TS-440s	Compact xcvr/99 mems 102db dynamic ranget w/at	1449.95	1224.95	
	without at.	1249.95	1059.95	
TS-140s	Compact grirl ovrg xovr DXciting price!!!!!	949.95	804.95	
TS-680s	Compact girl evrg sevr WITH SIX METER COVERAGE	H 1149.95	974.95	
FI-5000	102 dB range SW receiver 100 Memory Channels!!	1049.95	854.95	
R-2000	General coverage receiver 10 memories/2 clocks	799.95	649.95	
RZ-1	Wide band receiver, 100 memories	599.95	488.40	
TL-922A	160-15 meter linear amp. 2w PEP	1649.95	1399.95	
TM-2530A	25w 2m mobile/DTMF	499.95	424.95	
TM-2550A	45w 2m mobile/DTMF	519.95	440.00	
TM-2570A	70w 2m mobile/DTMF	623.95	529.95	
TM-3530A	25w 220 mobile/DTMF	519.95	440.00	
	Kenwood's 25/35 series radios are DCS/DCL compa	table.		
TW-4100A	2m/440 dual band mobile	599.95	514.95	
TM-621A	2m/220 deluxe dual band	729.95	619.95	
TM-721A	2m/440 deluxe dual band	729.95	619.95	
TH-318T	220 version 21BT	299.95	254.95	
TH-418T	440 version 21BT	299.95	234.95	
TH-25AT	NEW MINI 2M SYNTHESIZED HTIII	369.95	314.95	
TH-45AT	440 deluxe pocket HT w/ DTMF	389.95	330.00	
TH-205AT	2m 3w ht/3 memories Affordable HTItt	314.95	269.95	
TH-215AT	2m 3w ht/10 memories/ctcss	399.95	339.95	
TH-315A	220 3w ht/10 memories/ctcss	419.95		
TH-415A	2.5w 440 ht/10 memblotoss	419.95		
TM-221A	45w mobile w/DTMF mic	459.95	389.95	
TM-321A	220 version of 221	469.95	399.95	
TM-421A	35w mobile 440 w/DTMF mic	469.95	399.95	
TR-751A	2m all mode mobile	669.95	599.95	
TR-851A	440 25 watt FM sideband & CW	771.95	654.95	
TS:711A	Deluxe 2m all mode wips	1059.95	894.95	
TS-811A	Deluse 70cm all mode wips	1265.95	1069.95	
TS-790A	2m/70cm/1200 MHz tribander 1.2 GHz optional	1999.95	1694.95	
901	SATELLITE IN A BIG WAY - USE THE KENWOOD TWI	NS - 711/81	11	

WE STOCK A COMPLETE LINE OF KENWOOD, ACCESSORIES, RECOMMENDATIONS, AND OUR LOW PRICES 469-4656

RX-325

WE STOCK THE FULL LINE OF TEN TEC ACCESSORIES - CALL US FOR

INFORMATION, RECOMMENDATIONS, AND OUR DISCOUNT PRICES!!!

2245.00 1924.95

1445.00 1239.95

745.00 639.95

899.00 574.95

565 PARAGON Super HF transceiver. THE transceiver.

Sateline station

Compact grid every rever

561 CORSAIR II HF transceiver

525D ARGOSY II Economy HF tranceiver

## MAKE CIRCUIT BOARDS THE NEW, EASY WAY



## WITH TEC-200 FILM

## JUST 3 EASY STEPS:

- Copy circuit pattern on TEC-200 film using any plain paper copier
- Iron film on to copper clad board
- Peel off film and etch

convenient 8½ x 11 size With Complete Instructions SATISFACTION GUARANTEED 5 Sheets for \$3.95 10 Sheets only \$5.95 add \$1.25 postage NY Res. add sales tax

The MEADOWLAKE Corp. Dept. D, P.O. Box 497 Northport, New York 11768

**CIRCLE 55 ON READER SERVICE CARD** 


here's the Beam? Unobtrusive DX Gain Antennas for 80 thru 10

> Easily hidden \* Install Fast \* Fixed or Portable \* There's a 20 meter antenna with real DX Punch hidden in this picture. You can't see it, and your neighbors can't either. But it works DX barefoot

anyway. How about a low profile 80/40/30 tribander? Or a 2 element monobander for the attic? All easily fit the pocketbook--Priced \$29 to \$99. Work DX without telling the neighbors

AntennasWest Airmail Infopack \$1 Box 50062-S. Provo, UT 84605 (801) 373-8425

CIRCLE 107 ON READER SERVICE CARD

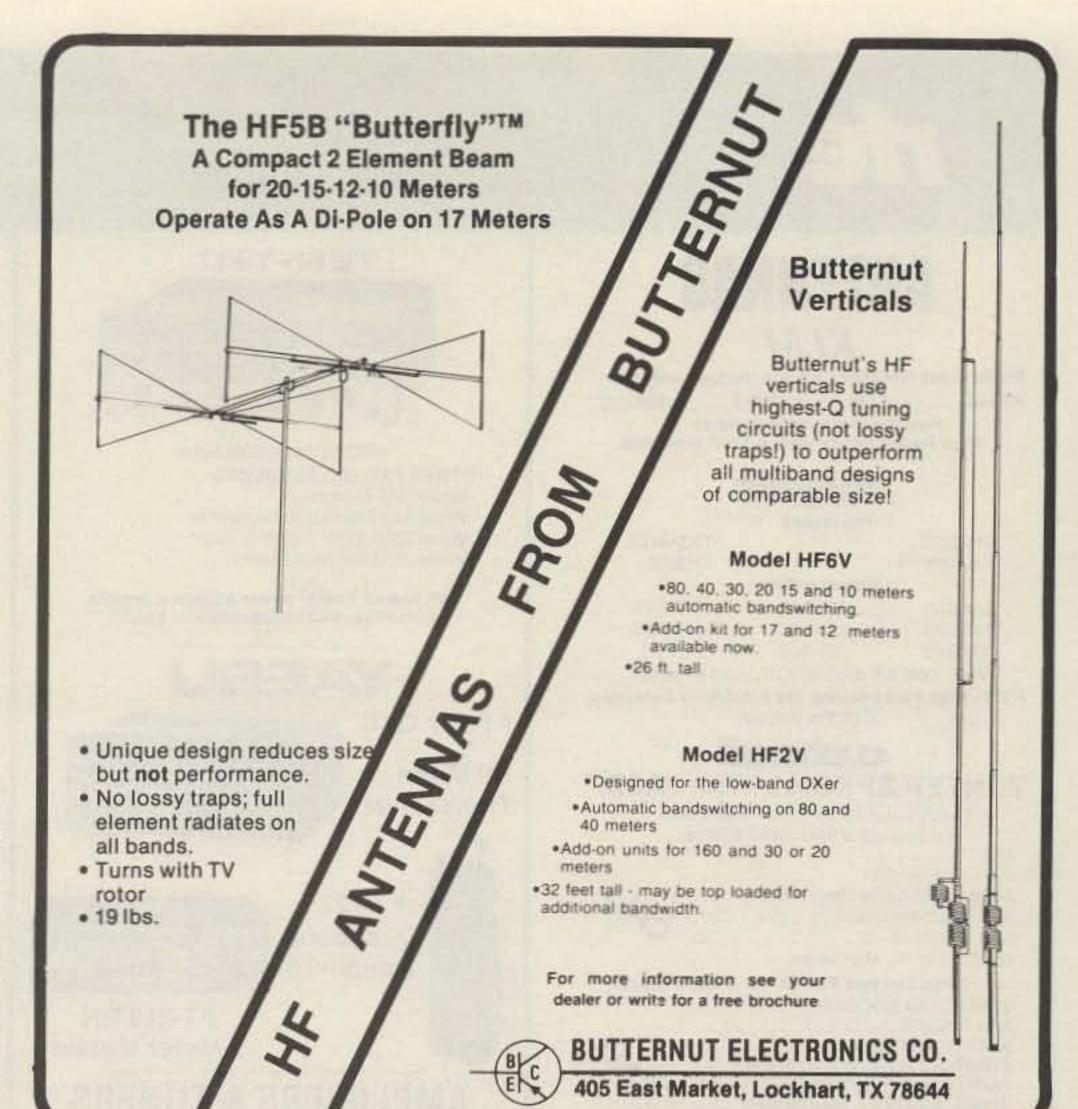

## **JANUARY 4, 1983** A CURE WAS FOUND

FOR THESE DISEASES :

1. REFLECTED POWER-ITCH

2. KNOB-ITUS

3. QRM-DEAFNESS

**BUTTON-PHOBIA** 

5. SWITCH-CANKER

6. SUPER TUNER-BLUE

7. CROSS NEEDLE-EYES

THE CURE IS:



MAXCOM

FOR ALL S.S.B. RADIOS

\* ONE SHOT GUARANTEED TO LAST AT LEAST FIVE YEARS!

MAXCOM, INC. BOX 502, FT. LAUD., FL. 33302


305-523-6369

THE BOTTOM LINE: "MAXCOM WORKS"

CIRCLE 101 ON READER SERVICE CARD

## AMATEUR TELEVISION

## SMILE! YOU'RE ON TV

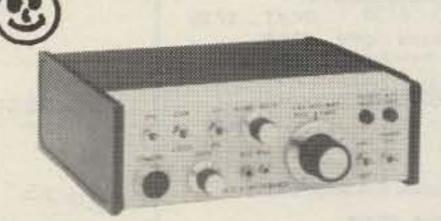

Only \$299

Designed and built in the USA Value + Quality from over 25years in ATV...W6ORG

With our all in one box TC70-1 70cm ATV Transceiver you can easily transmit and receive live action color and sound video just like broadcast TV. Use any home TV camera or VCR by plugging the composite video and audio into the front VHS 10 pin or rear phono jacks. Add 70cm antenna, coax, 13.8 Vdc and TV set and you are on the air...it's that easy!

TC70-1 has >1 watt p.e.p. with one xtal on 439.25, 434.0 or 426.25 MHz, runs on 12-14 Vdc @ .5A, and hot GaAsfet downconverter tunes whole 420-450 MHz band down to ch3. Shielded cabinet only 7x7x2.5". Transmitters sold only to licensed amateurs, for legal purposes, verified in the latest Callbook or with copy of license sent with order.

Call or write now for our complete ATV catalog including downconverters, transceivers, linear amps, and antennas for the 70, 33, & 23cm bands.

(818) 447-4565 m-f 8am-5:30pm pst.

Visa, MC, COD

P.C. ELECTRONICS 2522 Paxson Ln Arcadia CA 91006

Tom (W6ORG) Maryann (WB6YSS)





We Specialize In Antennas & Towers.

· We Ship Worldwide.

KLM

World Class Antennas for the Serious Amateur! KT34A.....\$395.00 KT34XA.....\$585.00 Monobanders: 80-10 Meters! High Performance VHF & UHF antennas.

hy-gain

Tribanders

TH7DXS TH5Mk2S Explorer-14 TH3JrS

Monobanders

203 BAS **205 BAS** 204 BAS 105 BAS 153 BAS 155 BAS 66 BAS 103 BAS

"VHF, OSCAR & VERTICAL ANTENNAS! NEW! High Performance 144 & 432 MHz Antennas. Call For Prices!

WINTER SPECIAL! The "A3S."

The Popular A3 with Stainless Steel Hardware at a Special RFE Price.

A4S .... A744 Add on Kit...... A3SK & A4SK Stainless Kits..... AV3 & AV5 Verticals..... AP8 & APR 18.....

40-2CD 2-el. 40 Mtr. Beam..... Monobanders For 10, 15, & 20 in Stock!

617-6B 6 Mtr BOOMER..... A50-5, A50-6..... A147-11, A147-20T..... 215WB & 230WB 15 & 30 el 2 Mtr ..... AOP-1 Satellite System..... 4218XL & 3219 for 144-146 MHz ...... 220B, 424B BOOMERS...

Large Inventory Of Other Antennas & Accessories

FMK II Kit..... TBR-180S Coll ...... C

HF2V..... STR II Kit..... SC-3000 Antenna... C

HF5B ..... CALL ALPHA DELTA

DX-A....\$46.95 DX-DD . . 64.95 DX-KT.... 27.50 NEW! DX-CC All band dipole....\$79,95 Full line Alpha Delta switches & Transi-traps!

5BTV ..... \$124.95 6BTV . . . . . . . \$134.95 G6-144B...... 86.95 G7-144 ...... 114.95 G7-220 ..... 114.95

Complete HF Mobile Systems. CALL!

MOSLEY

TA-33 TA-34 CLASSIC 33 **PRO-67** 

TONNA **ANTENNA SPECIALISTS** 

TELEX HDR-300.....CALL T2X.....CALL HAMIV ..... CALL CD46 II.....CALL AR-40......CALL

ALLIANCE

YAESU G400/400RC . . . . . CALL G600RC......CALL KR2000RC . . . . . . . CALL G5400B..... CALL

DAIWA

TEN-TEC



MODEL 561 CORSAIR II OTHER TEN-TEC PRODUCTS:


Model 585 Paragon

Model 425 Titan Linear Amplifier Model 229A 2KW Antenna Tuner Model 2510 Satellite Station

Full line of filters, power supplies, mobile antennas, and accessories in stock.

FT-757 GXII All Mode

Transceiver

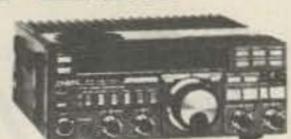



FT-727 **Dual Band** Handheld



FT-212 RH 2 Meter Mobile

**AMPLIFIERS & TUNERS** 



NYE-VIKING MB-V-A

MAGNUS SOLID STATE HF LINEAR AMPS

MFJ

CLOCKS

KEYERS ACCESSORIES



SPECIAL!

989B Tuner \$275.00

**ASTRON POWER SUPPLIES** 

Rack mount and speaker models in stock! RS-4A . . . \$37.95 RS-7A . . . . 49.95 RS-12A . . . 69.95 RS-20A . . . 88.95 RS-35A . . 135.95 RS-50A . . 193.95 RS-20M .. 106.95 RS-35M .. 153.95 RS-50M .. 216.95 VS-20M .. 124.95 VS-35M .. 171.95 VS-50M .. 232.95

SSB ELECTRONIC & MICROWAVE MODULES TRANSVERTERS, PREAMPS, & ACCESSORIES. CALL!

## **TOWERS**

HY-GAIN

Crank-up, self-supporting, galvanized steel towers. SS rated at 9 ft; HD at 16 ft.

**HG-37SS** HG-54HD

CALL FOR PRICES

**HG-52SS** HG-70HD

ROHN

Self-supporting: Ratings: HDBX at 18 ft, HBX at 10 ft, BX at 6 ft.

Galvanized steel with base and rotor plate. Today's best buy. Freight additional but you save with our volume shipper's discount!

GUYED TOWER SECTIONS:

25G, 45G, 55G Sections and All Accessories in Stock, Call for Current Prices.

FOLD-OVER TOWERS:

FK2548.....

FK2568.....

FK4554..... FK2558...... FK4564..... Prices 10% higher in western states.

ROOF TOWERS & CLIMBING BELTS ..... Call! **TOWER HARDWARE** 

Guywire: 3/16EHS / 1/4 EHS, per ft......\$0.15/0.18 CCM Cable Clamps: 3/16 / 1/4 ......0.39/0.49 Guy Insulators: 500 D/502 ...... 1.69/2.99

PHILLYSTRAN GUY SYSTEMS

0.30/.50/.70 HPTG-2100/-4000/-8700 Cable..... Cable Ends: 9901LD/9902LD..... Socketfast Potting Cmpd.....

**BELDEN COAX** 

9913 low loss \$0.45/ft RG-8X(9258) . . . . 0.20 RG-11A/U(8261) . . 0.41 RG-213/U(8267) . . . 0.46 RG-8/U(8237) . . . . 0.36 RG-58A/U(8259) . . 0.15 RG-8/U(8214)....0.40 RG-59/U(8241) . . . . 0.18 RG-214/U(8268) \$2.25/ft. 450 Ohm Ladder Line.....

COPPERWELD ANTENNA WIRE

Solid: 12 ga......0.10 14 ga..... Stranded 14 ga..... 0.10

Plus Wide Selection Baluns, Insulators, Accessories

ROTOR CABLE

Std (6-22, 2-18)......0.19 Hvy (6-18, 2-16)...0.36 Others in stock.

AMPHENOL CONNECTORS

PL-259: std/silver/teflon ...... 0.89/1.25/1.45 UG-21B (8261) Type N Male.....2.95 T's, angles, adaptors, jacks, & BNC in stock!

COAX AVAILABLE IN PRECUT LENGTHS WITH CONNECTORS ATTACHED.

. COAXIAL SWITCHES .

**ANDREW HELIAX & CONNECTORS** 1/2" LDF4-50A ..... CALL 7/8" LDF5-50A ..... CALL


THANK YOU ... AND HAPPY HOLIDAYS TO OUR CUSTOMERS AROUND THE WORLD RALPH-KOIR, GEORGE-ADOS, GWEN-WDODZL, RANDY-KAOVVO, MEL, CHERYL, AND BRIAN





RETURNS REQUIRE AUTHORIZATION &

SUBJECT TO 15% RESTOCKING CHARGE

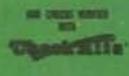

Prices subject to change without notice.

Minnesota residenta add 6% tex.

Shipping additional except as noted.

ORDER ONLY:

1-800-233-2482 SHIPPING, INFO., TECHNICAL, MN & DX.

TELEX: FAX 4933032 RFE UI 218-765-3308 rf enterprises

HCR Box 43 Merrifield, MN 56465 (Located at Jcn. Co. 3 & 19)

## HAMSATS

## Amateur Radio Via Satellite

Andy MacAllister WA5ZIB 14714 Knightsway Drive Houston, TX 77083

#### Hamsats a Year Older

The dawn of a new year represents new beginnings. The new year brings the inevitable resolutions. Some good ones for the current or potential satellite operator include joining or renewing AM-SAT membership, finishing antennas or radio projects, and getting more operating time on the satellites.

For example, AMSAT-OSCAR-7 was last heard in the summer of 1981. There have been no contacts via this satellite since then. Unless something remarkable happens, it is history. The shortwave bands won't disappear tomorrow, but we can only guess the life spans of RS-11, Fuji-OS-CAR-12 or AMSAT-OSCAR-13.

Amateurs who are already active via satellite, and who have all the HF, VHF, UHF, and microwave equipment they need for satellite fun, might consider helping someone else get started with satellite chasing this year-explain it, or better yet, demonstrate a functional earth station.

Station descriptions can be pieced together by reading through all of the Hamsat columns during the last two years. New rigs, antennas, and accessories can out-perform the older equipment, but many of the systems that performed well for A-O-10, still do great for A-O-13, five years later. What is the average A-O-13 operator using today?

### What It Takes

Many how-to's written on satellite operation tell you that you can make contacts with simple systems using inexpensive radios and home-brew antennas. They are right. Many AMSAT-OSCAR-10 enthusiasts proved that (with the right conditions) a few watts to a small manually-pointed yagi, or more power into a mobile magmount, provides good uplink signals; and that a dipole hung on the wall, followed by a small receive converter and an HF rig, can hear signals from space. It may not be a piece of cake at times, but it has been done many times.

## Successful A-O-13 Activity

The following is not a description of a QRP (low power) satellite station or an indoor antenna system, but a brief guide for successful A-O-13 Mode B activity.

The easier a station is to use, the more it will be operated. Very rarely does a new satellite chaser put together all of the ingredients for the ultimate earth station at one time. It is a process of experimentation and learning.

So, how does one get a station ready for A-O-13? The most popular transponder on A-O-13 is Mode B. This requires an uplink signal from the operator, using CW or lower sideband from 435.423 to 435.573 MHz. This 70 cm up, and 2 meter downlink-type transponder worked successfuly on A-O-7. For A-O-13, most contacts are made on uplink frequencies close to 435.500 MHz. Downlink reception is from 145.975 to 145.825 MHz, CW, or upper sideband.

Note the frequency guide in last month's column. The Mode B transponder is inverting, thus a lower sideband transmission on 435.443 MHz will result in an upper sideband signal on 145.955 MHz, while an uplink on 435.553 MHz will come out on 145.845 MHz. CW activity is usually heard below 145.900 MHz, while sideband users stay above 145.900 MHz.

Since the VHF and UHF bands used by A-O-13 are primarily lineof-sight, satellite access is only possible when A-O-13 is above the operator's horizon. The best way to predict when A-O-13 will be available from a specific location is to use a good satellite tracking program on your computer. AM-SAT offers software for many computers. Some programs provide simple tabular listings showing basic tracking information, while others can produce world maps with real-time, multisatellite tracking. Regardless of the program's complexity, the point is to know when to operate and where to aim the antennas. If a computer is not available, there are mechanical aids for tracking, or a friend may be able to print predictions. Due to the elliptical shape of A-O-13's orbit, guessing the satellite's position won't work.

Long-term commitment to satellite chasing requires access to a computer with tracking software.

Most active operators have multi-mode, 2 meter, and 70 cm transceivers. Commonly heard rigs include the Yaesu FT-726R or FT-736R, the ICOM IC-271 and IC-471 pair (A or H suffix), the IC-275 and IC-475 pair (A or H suffix), and the Kenwood TS-711A and TS-811A pair. For those with the H-suffix ICOM rigs (high power of 75 watts) no external amplifiers are used. Others with 25 watt radios usually buy an amplifier. The idea is not to overpower the satellite, but to have the extra output available when the satellite does not favor the user's location. An example is when A-O-13 is at apogee (highest point of the orbit) with its gain antennas pointed away. Amplifiers commonly used include Mirage, TE Systems, and RF Concepts. You can expect consistent and satisfying results with 50 to 100 watts.

Quality coaxial cable and good antennas up in the clear round out the complete earth station. For the cable, most use Belden 9913 coax with N-connectors for the slightly larger center conductor of the 9913. Keep the coax runs short. If the rig or antennas use SO-239 connectors, then use PL-259A connectors (Teflon dielectric) on the cable. Avoid jumpers and extra coax adapters.

Satellite antennas don't need to be high; they just need to be able to "see" the sky. It's best to have an unobstructed view of the horizon in all directions. Trees and buildings attenuate both received and transmitted signals. Commonly used antennas are circularpolarized, commercially-built crossed yagis. Manufacturers include Cushcraft, Telex/Hy-Gain, Mirage/KLM, Tonna, and others from Spectrum International. The first three brands are the easiest to find.

The AOP-1 package from Cushcraft includes a 20-element 2 meter crossed yagi, a 16-element 70 cm crossed yagi, and a mounting boom with a mounting plate for the Alliance U100 rotor (for elevation control). It does not come with polarization switching, and it does not use stainless steel hardware, but it is the least expensive. The cable harness typically is set for RHCP (right hand circular polarization) to conform with most satellites. You can buy the antennas, crossboom, and mounting plate separately, if necessary. A polarity switch is available for the

70 cm antenna and a 10-element 2 meter crossed yagi is an alternative for those with space constraints. The smaller antenna exhibits less gain.

The OSCAR Link antenna system from Telex/Hy-Gain offers advantages over the Cushcraft system, but averages about \$100 more. It includes a 16-element 2 meter crossed yagi, a 30-element 70 cm crossed yagi, and a heavywalled fiberglass crossboom. Hardware is stainless steel with ultra-violet stabilized plastic insulators. Many other items have been carefully engineered, including polarization switching relays rated at 200 watts. For a costeffective system with excellent performance, this antenna array is the best choice.

The finest antennas are made by Mirage/KLM. Two versions of the 2 meter crossed yagi are available. One has 14 elements and the other has 22. Just the 2M-22C (22-element antenna) costs more than the complete Cushcraft package, but it includes a switch and stainless hardware. For 70 cm there is either an 18-element or 40-element antenna.

Most stations have preamps. For a few, signals from the satellites are sufficient without a preamp. These stations have state-of-the-art radios with GaAs-FET front ends and large antenna arrays. For those with long coax runs, preamps are placed at the antenna. This way, weak downlink signals are amplified before they are lost in the coax. With a short coax run, you can place the preamp near or in the radio. Advanced Receiver Research, Hamtronics, Landwehr (from Henry Radio), and Microwave Modules Ltd. (from Spectrum International) manufacture many of the commonly used preamps.

There are many ways to get a functional satellite station on the air. Other manufacturers of VHF and UHF rigs and antennas exist, and tracking software has been written and sold by companies and individuals other than AM-SAT. Several transponder modes are available via A-O-13, but getting a fully functional Mode B station on the air is an important start.

73

For further information, consult The ARRL Handbook, The ARRL Operating Manual, The Satellite Experimenter's Handbook, the many AMSAT publications, and the AMSAT HF and satellite nets.

# TALK IS CHEAP.

Have you heard? For less than \$90 your AT or XT-compatible computer can talk! All it needs is the HV-2000 Computer Voice Kit from Heathkit.

Reading letters, transcriptions and computerized instruction can be easier and quicker than you ever thought possible. Computer games gain a new dimension. Your computer can even entertain children



Computer Voice will allow your computer to recite reference and research information from time-sharing services. Or, speak radio transmitted ASCII information.

The HV-2000 Computer Voice Card, containing speech synthesizer and audio amplifier, plugs into any AT or XT-compatible computer's expansion slot. An external speaker is also included. Versatile, Heath-developed software gives you a wide variety of voices and easy interface to high and low level languages.

The HV-2000 Computer Voice. At less than \$90, talk IS cheap. To order, call toll-free 1-800-253-0570. Use your Visa, MasterCard, American Express or Heath Revolving Charge card. Or call 616-982-3614 for the nearest store location.

## Heath Company

A subsidiary of Zenith Electronics Corporation

Prices, product availability and specifications are subject to change without notice.

## PROPAGATION

Jim Gray W1XU

Jim Gray W1XU PO Box 1079 Payson AZ 85541

### January 1989

January will provide some excellent DX on all bands from 160-10 meters. You may find, however, that the week between the 9th or 10th and the 16th or 17th will be spotty. In fact, days in these two periods may be poor with

high magnetic index (A) values due to an unsettled-to-active geomagnetic field. Otherwise, static levels will be generally low during the month, and great DX should be available on the lower HF bands of 160, 80, and 40 meters.

Thirty meters will also be good, but, as the frequency increases, the HF high bands will close earlier. Ten will close just before dark on most days, and 15 meters will soon follow. Twenty will stay open quite nicely for an hour or two after local dark.

January is not generally considered a good DX month, but with sunspots increasing rapidly and solar flux values holding well above 150, the conditions will be better than they have ever been in a long time.

For those interested in astronomical events, Earth will be closest to the Sun on January 2, the Moon will be closest to Earth on the 11th, and a full Moon will occur on the 22nd. No eclipses are in the forecast for January. January is not exactly a "ho-hum" month, but it is generally far less exciting than March or September.

You may find some very good VHF openings in January, however, so keep your ears tuned. As always, listen to WWV at 18 minutes after each hour for up-to-date broadcasts of solar flux and geomagnetic (A) and (K) indexes. The higher the flux and the lower the (K) and (A) indexes, the better conditions will be for propagation on the HF bands.

### The Source

Readers often ask me about the source of my predictions. I use the Shortwave Propagation Handbook—Principles, Theory, Predictions edited by George Jacobs W3ASK and Theodore J. Cohen N4XX. The edition I have was published in 1979 by the Cowan Publishing Corporation, 14 Vanderventer Avenue, Port Washington, NY. The book

is priced quite reasonably at under \$10.

The book assumes the reader is a neophyte to propagation matters and gives a good understanding of the mechanisms of long-distance transmission and reception of radio signals.

If you read this book thoroughly, you'll be able to make your own forecasts with reasonable accuracy for any time of the year, for any year in any sunspot cycle.

## EASTERN UNITED STATES TO:

GMT:	00	02	04	06	DB	10	12	14	16	18	50	22
ALASKA	15:	20	-	191	-	33	20	30	7.1	-	-	15
ARGENTINA	20	40	40	40:	-	-	20	1.5	15	1.0	10	15
AUSTRALIA	15	20	20	-	40	40	40	2	-	20	20	15
CANAL ZONE	20	.20	20	20	20	20	20	15	10	10	15	15
ENGLAND	40	40	40%	40%	-	20	1.5	10	15	20	20	-
HAWAII	15	20	*	-	2	12	20	20	20	10	10	15
INDIA	-	-	-	_	-	-	20	20	-	-	-	-
JAPAN	15	20	4	-	+	-	20	20	-	-	-	15
MEXICO	10	20	20	20	20	20	20	15	10	10	15	15
PHILIPPINES	(40)	(te	-	-		-	20	20	-	-	-5	-
PUERTO RICO	20	20	20	20	20	20	20	15	10	10	15	15
SOUTH AFRICA	20	404	10	-	-	1	20	10	10	10	15	20
U. S. S. R.	+	-	-	-	-	-	20	15	20	20	-	-
WEST COAST	15/20	20/40	80	160	160	160	-	-	0	10	10	15
The second second	23.4						Section 1		-	No. of Concession, Name of Street, or other Designation, Name of Street, Name	COLUMN TWO	No.

CENTE	RAI		UI	TIL	EC	)	ST	A٦	TE:	S	TC	):
ALASKA	15	-	Let		-	-	-	20	-		13	15
ARGENTINA	20	20.	20	40	40	+	20	20	15	10	15	15
AUSTRALIA	15	20	20	-	-	100	40	-	-		15	10
CANAL ZONE	15	20	40	404	40*	-	20	15	10	10	10	15
ENGLAND	40	40	80	2	-	1	Bei	20	15	.15	20	40
HAWAII	15	20	-	40	40	40+	404	20	20	15	10	15
INDIA	-	-	-	-	-	-	-	20	-	-	=	10
JAPAN	15	4	-	-	-	-	-	20	140	200	-	15
MEXICO	1.5	20	40	40+	40*	-	20	15	10	10	10	15
PHILIPPINES	15	20	-	-	-	-	(10)	20	175	-	-	15
PUERTO RICO	15	20	40	40#	40*	-	20	15	10	10	10	15

10

15 20

SOUTH AFRICA

U. S. S. R.

#### WESTERN STATES TO: ALASKA AD: 40 40 15 ARGENTINA 15 20 40 40 20 10 10 15 AUSTRALIA 10 15 20. 40\* 40\* 20 15 15 CANAL ZONE 15 20 20 15 10 10 10 ENGLAND 20 20 15 20 15 HAWAII 40 20 20 15 10 40 15 INDIA 20 JAPAN 40 40 40 20 MEXICO 15 20 10 10 10 PHILIPPINES 40 40 20 PUERTO RICO 40 40 40 -20 SOUTH AFRICA 20 15 10 15 15 20 U. S. S. R. 20 20 EAST COAST 15/2020/40 80 160 160 160 10 10 15

sun	4	MON	91	TUE		NU		Y		FRI		SAT	ră.
1		2		3		4		5		6		7	18
	G		G		G		G		F		G		G
8		9		10		11		12		13		14	
1000	G	G-	-F		F	F	-P	1	Р		P		P
15		16		17		18		19		20		21	
	P		P	P	-F		F	F-0	G		G		G
22		23		24		25		26		27		28	
	G		G	in n	G		F	F-0	G		G	d'Un	G
29		30	1120	31						n v		H	
	G		G		G					1100			

# Heathkit



## You're In A Separate "Class" With The SB-1400 Transceiver

AM-451R1

The world is at your fingertips with the NEW Heath SB-1400 All-Mode Transceiver featuring dual VFOs and 20 memory channels. With a price tuned into your budget, the SB-1400 is an assembled SSB/CW/AM and optional FM transceiver that delivers 100W of PEP output on all nine HF amateur bands, with 100kHz-30MHz general coverage reception.

The SB-1400 is the latest addition to Heath Company's full line of amateur radio equipment – everything you need to complete your ham shack.

Heath Company also carries an extensive line of other electronic products. From computers to television sets, from test instruments to stereos, every Heathkit® product – kit and assembled – is backed by 40 years of dedicated attention to design, quality and durability.

For a FREE Heathkit catalog, send in your QSL card, mail the coupon below, or call 24 hours a day TOLL FREE:

1-800-44-HEATH (1-800-444-3284)

Send to: Heat	h Company, Dept. 011-734 on Harbor, Michigan 49022
Name	
Address	Apt
City	
State	Zip

A subsidiary of Zenith Electronics Corporation

**Heath Company** 

## ASK KABOOM

## The Tech Answer Man

Michael J. Geier KB1UM 7 Simpson Court S. Burlington, VT 05403

#### Bandwidth!

The other day, I was having a nice conversation on 20 meters with a guy who was running S-7 to S-8. Suddenly, another station came on 1 kHz below us, running about 10 over 9, and wiped us out. I went down to his frequency and politely requested that he move, as we were only 1 kHz up. His response: "I'm a kilohertz below you, I shouldn't be bothering you!"

For a moment, I didn't know what to say. Understanding the concept of bandwidth is one of the most basic requirements of station operation (not to mention licensing), yet here was a ham who clearly didn't know (or didn't recall) what it was!

While most hams are familiar with the concept, judging from the QRM on the bands, at least some hams have a less-than-clear mental picture of what goes on spectrally when we speak into our mikes. This month's column seeks to clarify this.

## The 3 kHz Range

In a properly operating SSB rig, the transmitted bandwidth is equal to the modulating frequencies. For us, that's 3 kHz maximum, as required by law on the amateur HF bands.

Look at Figure 1. It represents a portion of the 20 meter band. The section over which the curve sits represents your USB signal on 14.300 MHz. Now look at the measure below the curve below the graph. Depending on your sex,

voice qualities, what you are saying, and especially the type of microphone you use, the distribution of the transmitted energy may favor the low voice frequencies, high voice frequencies, or somewhere in between. The areas bounded by the curves in the two figures, for example, shows a concentration of voice frequencies in the middle ranges.

For all practical purposes, you are using up your entire 3 kHz allotment at any time. So you're not really on 14.300; you're on 14.300 to 14.303! 14.300 is merely where your carrier WOULD be if you were operating AM and, of course, what your dial or digital read-out shows. It is clear, then, that stations can be 3 kHz apart without interference. (In practice, a bit more room is required because receiver filters are not perfect.)

## "Monkey Chatter" and Rumblings

Now, look at Figure 2. If a station has moved only 1 kHz below you, the bandwidths will overlap, and his or her upper voice frequencies will appear where your receiver will interpret them as LOWER frequencies. You will hear unintelligible rumblings. On the other hand, if a station is, say, 2 kHz ABOVE you, you will hear squeaky "monkey chatter" because his lower voice frequencies will appear where your receiver will interpret them as UPPER frequencies.

On LSB, everything's reversed. Your bandwidth extends for 3 kHz BELOW your dial frequency. On the diagrams, the lows and highs will be reversed. Monkey chatter

comes from stations below you and rumblings come from above.

Nearly all of today's rigs have a control which allows you to narrow the bandwidth of your receiver and filter out some of the QRM. (A notable exception is the new Yaesu FT-747. Shame!) The technique is pretty effective, especially on the monkey- chatter type of QRM, but the price you pay is that the signal you want to hear is also degraded. Cutting the monkey chatter muffles reception, and reducing the rumbling makes the voice tinny. But, at present, there is just no other way.

## Dear Kaboom,

I have a problem. I bought a car with fuel injection, and have I got a noise in my mobile HF rig! It sounds like the ignition, but only on 20 meters. I've never had trouble like this in my other cars. I'm disgusted with this computer junk. What can I do to clean up the noise?

Signed, Annoised

## Dear Annoised,

Obviously, something in that car has a harmonic on 20 meters!
Generally, computer-generated

"Nearly all of today's rigs have a control which allows you to narrow the bandwidth of your receiver and filter out some of the QRM."

#### **Notch Filters**

By the way, reduction of this type of interference is not the purpose of a notch filter. These filters put a narrow, deep null in your passband and are intended only to remove heterodynes ("tuner-uppers"). The null isn't wide enough to remove the wide band of frequencies present in a voice signal.

Finally, don't forget to keep your bandwidth in mind when deciding how close to the band edge to set your dial, or some of your signal could wind up outside the band. A friend of mine forgot this and got a pink warning slip from you know who!

Now that we've vanquished QRM from the bands (hah!), let's look at this month's letters. noise sounds very different from ignition noise, so I doubt that the car's central processor is the culprit. Especially if the noise is very broadband (covering the entire band), I would say it is not caused by a computer.

Does the car have digital instrumentation? Those big fluorescent read-out tubes seem like logical noise suspects to me, but again, the noise should sound very different from ignition.

The most likely cause is from pulses delivered to the fuel injectors, or by good old ignition. As always, shielding wires may help. Also, check to see if the noise is present only when the car moves. Hash could be coming from wheel bearings, tires, the transmission, or any other moving mechanical system.

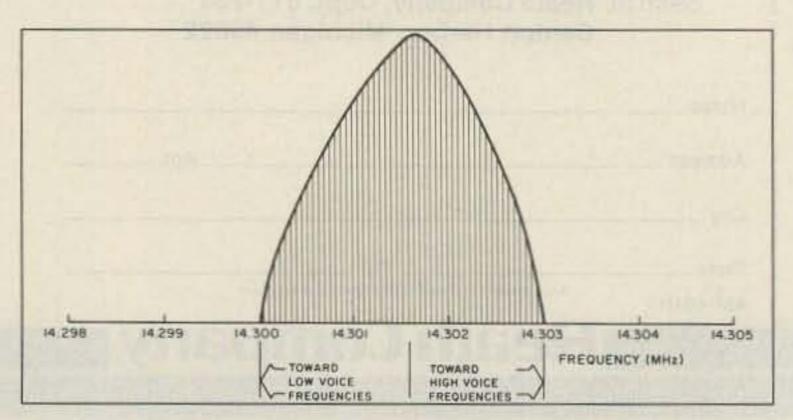


Figure 1. A diagram of a USB signal when the rig is tuned to 14.300 MHz transmit.


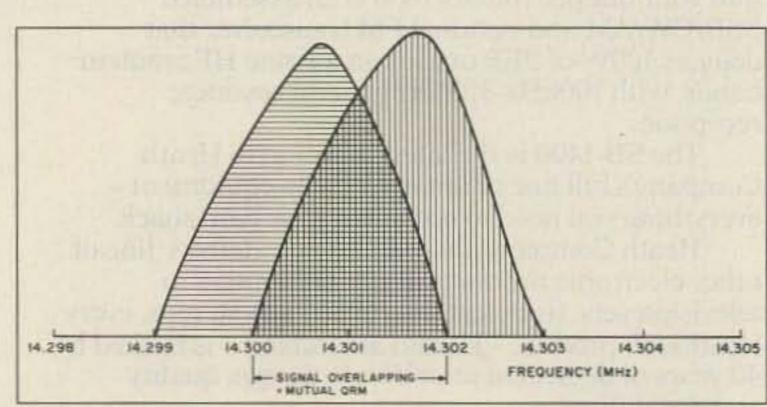


Figure 2. Two USB signals, tuned to 14.299 MHz, and 14.300 MHz respectively. Note their overlap, which extends from 14.300 to 14.302 MHz. When signal bandwidths overlap, you will hear, on the frequency in question, rumblings on its lower frequencies and monkey chatter on its higher frequencies.

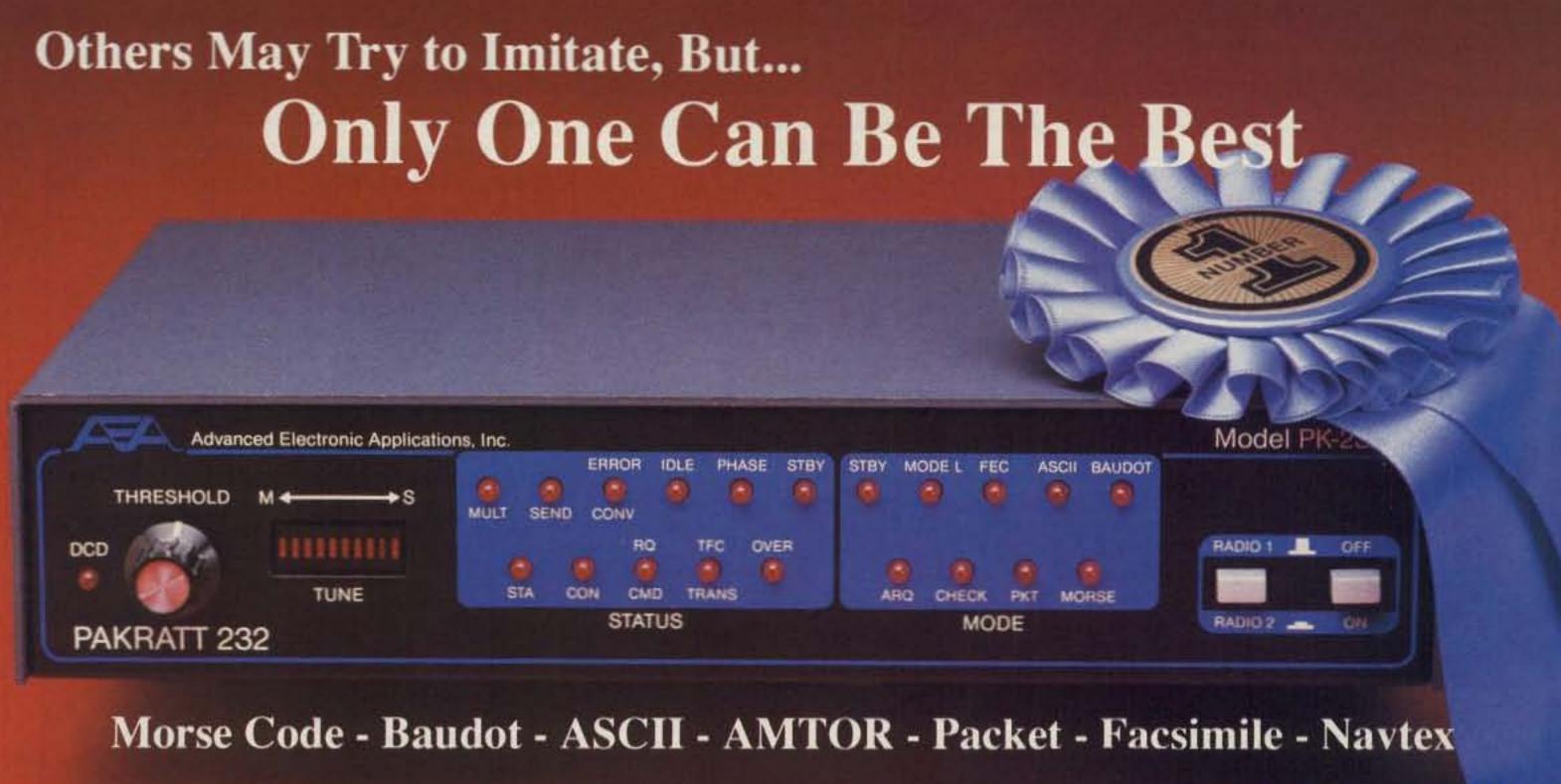

Amateur Net Price \$319.95

It's a lesson you learn very early in life. Many can be good, some may be better, but only one can be the best. The PK-232 is the best multi-mode data controller you can buy.

## 1 Versatility

The PK-232 should be listed in the amateur radio dictionary under the word Versatile. One data controller that can transmit and receive in six digital modes, and can be used with almost every computer or data terminal. You can even monitor Navtex, the new marine weather and navigational system. Don't forget two radio ports for both VHF and HF, and a no compromise VHF/HF/CW internal modem with an eight pole bandpass filter followed by a limiter discriminator with automatic threshold control.

The internal decoding program (SIAM<sup>tm)</sup> feature can even identify different types of signals for you, including some simple types of RTTY encryption. The only software your computer needs is a terminal program.



PC Pakratt Packet TX/RX Display



Facsimile Screen Display

## 2 Software Support

While you can use most modem or communications programs with the PK-232, AEA has two very special packages available exclusively for the PK-232....PC Pakratt with Fax for IBM PC and compatible computers, and Com Pakratt with Fax for the Commodore 64 and 128.

Each package includes a terminal program with split screen display, QSO buffer, disk storage of received data, and printer operation, and a second program for transmission/reception and screen display of facsimile signals. The IBM programs are on 5-1/4" disk and the Commodore programs are plug-in ROM cartridges.

## 3 Proven Winner

No matter what computer or terminal you plan to use, the PK-232 is the best choice for a multi-mode data controller. Over 20,000 amateurs around the world have on-air tested the PK-232 for you. They, along with most major U.S. amateur magazines, have reviewed the PK-232 and found it to be a good value and excellent addition to the ham station.

No other multi-mode controller offers the features and performance of the PK-232. Don't be fooled by imitations. Ask your friends, or call the local amateur radio store. We're confident the PK-232 reputation will convince you that it's time to order your very own PK-232.

Call an authorized AEA dealer today. You deserve the best you can buy, you deserve the PK-232.

## **Advanced Electronic** Applications, Inc.

P.O. Box C-2160 Lynnwood, WA 98036 206-775-7373






## EEB THE PROFESSIONAL AMATEUR STORE

## **NOVEX**

DM4061 Dip Meter every ham needs one

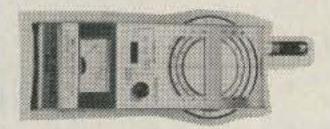

A must for every ham shack - check coils, tank circuits, antennas, use as RF generator, internal modulation, look for harmonics. 1.5 - 250 MHz 6 plug-in coils. only \$79.95 + \$4 S&H

#### SWR-3P SWR/Power/Field Strength



- Measures output/SWR. while on the air
- 10 & 100 watt scales 1.7 to 150 MHz SO 239 conectors

· 5" whip antenna only \$19.95 +\$4 S&H

## PM330 RF Power Meter/Dummy Load



- 1.8 to 500 MHz
- 50 ohms "N"f
- 5/20/120 watt ranges · measures your HF & HT power output

only \$99.95 + \$4 S&H

#### FC5250 Counter know your transmit frequency · 10 Hz to 150 MHz

THE RACK IS BACK

 save space - go vertical · organize your radio room + get the professional look

· hide all the unsightly wires

· protect your investment

forward facing speakers.

· have finger tip access to your radios

NOVEX rack mounts are standard EIA

19 inch size aluminum panels and are

optionally equipped with handles and/or

Now available for most ICOM.

KENWOOD, and YAESU radios and

Prices start at a low \$79.95 each.

· keep your equipment safe and clean



- · 7 digits
- · Accurate to ±1 count
- · Gate times 1 or 5 sec.
- · HF & VHF inputs
- · Excellent for audio AC power adapter PA9P

included only \$129.95 + \$4 S&H

## NOVEX

## RF Signal Generator/Counter




- .1 150 MHz
- Harmonics to 450 AM modulation XTAL input/check

Digital readout

NOVEX SG4162AD only \$249.95 + \$4 S&H

NOVEX SG4160A same as above except no digital readout/counter only \$149.95 + \$4 S&H

## AF Audio Generator/Counter

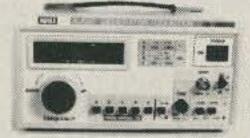


- 10 Hz 1 MHz Sine - sq wave
- Low distortion 8V RMS output Digital readout

NOVEX AG2603AD only \$249.95 + \$4 S&H

NOVEX AG2601A similar to above except no digital readout/counter only \$149.95 + \$4 S&H

## Function Generator

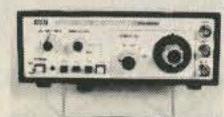


or FSK signals

- Sine, sq, triangle
- .5 Hz .5 MHz DC offset
- 20 Vpp output / 120 VAC power

includes test leads External inputs can control AM (VCA) or FM (VCF) and produce AM, FM, sweep, ASK.

NOVEX FG2020A only \$149.95 + 4 S&H

## NOVEX Speaker Mics

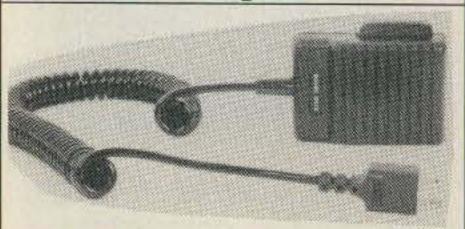

Rotatable lapel clip .

High quality audio . Privacy earphone jack Hi-Lo volume switch

ICOM DMC 5371 Kenwood DMC 537K Yaesu DMC 537Y

SUPER VALUE only \$19.95

## NOVEX Handsets



PTT handset · backlit DTMF · Private listening Wired for most current ICOM, Kenwood, Yaesu & others (on special request)

ICOM HSC7011, Kenwood HCS701K, Yaesu HCS701Y Available for many other radios at slightly higher prices.

Introductory price \$79.95

## ARD 9100 SUPER ROTATOR **Exclusively Distributed by EEB** The Rotator for the Big Guns



- Computer/Remote Control
- · Rotating torque: 10,000 inch lbs
- Braking torque: 24,000 inch lbs
- · Vertical load: 2,000 lbs
- Mast size: 2 3.5 inch O.D.
- Motor: 1/3 HP 120/220V 50/60Hz
- Rotation speed: 1 RPM
- · Weight: 230 lbs.

List \$4395.

• Size: 15 × 25 × 15 inch

Call for Quote

## CRIS 6000 COMPUTER/RADIO INTERFACE SYSTEM. IBM PC OR COMPATIBLE.

Starting at \$349.95



- Auto Log/Sort 800 memories
- Log Date/Time/Freq/Mode (Opt Signal Strength)
- · Build your own data base
- · Scan Bands/Freg/Service
- · Auto create a local database
- · Key stroke set radio to memory channel
- · Unlimited logging on disc
- Spectrum analysis option
- Free Newsletter subscription-Call

## ARD 230 SERIES AMPLIFIER





List \$5495. Call for Quote

- Cool 1500 watts output always available
- All HF Bands 1.8 21 MHz (10MT user install)
- 50 80 watts drive for full output
- Harmonic Supp -45dB INTMOD -35 dB
- · Completely automatic Full QSK
- Micro processor controlled/protected
- Remote AMP up to 250 ft from controller Export and Commercial Versions available
- AMP only  $14 \times 22 \times 13$  inch 86 lbs

## SDU 8000

SPECTRAL DISPLAY UNITS (SDU) Allow user to "SEE" up and down the band for activity or



lack of. You won't miss anything. Sweep width 50 KHz - 10 MHz

- Input 10.7 MHz
- Direct plug-in to R7000 no mods
- Variable sweep rate 3 inch CRT
- 120V 50/60 Hz

Introductory Price \$595.

accessories.


Orders: 800-368-3270 **Electronic Equipment Bank** 516A Mill St. NE, Vienna, VA 22180

Local & tech info 703-938-3350

(Just minutes from Washington, DC)



**CIRCLE 355 ON READER SERVICE CARD** 

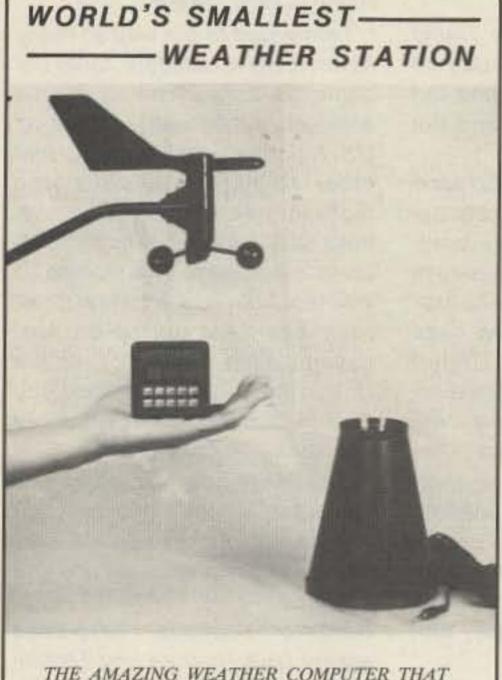

THE AMAZING WEATHER COMPUTER THAT YOU CAN HOLD IN THE PALM OF YOUR HAND.

DIGITAR's new TWR-3 Micro Weather Station includes a computer, precision wind vane and speed sensor with mounting hardware, and 40 feet of cable. For only \$159.95. With the optional, automatic-emptying RG-2 Rain Collector (\$49.95) you can even monitor rainfall!

- \* WIND SPEED
- \* WIND DIRECTION
- \* WIND CHILL
- \* WIND GUST RECORD
- \* TEMPERATURE
- \* HI/LOW TEMP RECORD
- \* RAINFALL (Optional)

- \* TIME OF DAY
- \* AUTO SCAN
- \* METRIC / STANDARD
- \* NICAD READY \* ONE YEAR WARRANTY

MAGNAPHASE INDUSTRIES, INC.

MADE IN U.S.A. AUBURN, WA 98001. ORDERS ONLY: 800-322-1502

M/C & VISA

INFORMATION: 206-735-0374

FAX: 206-735-9044

## NEMAL ELECTRONICS

\*Complete Cable Assembly facilities MIL-STD-45208

\*Commercial Accounts welcome- Quantity pricing \* Same day shipping most orders

\*Factory authorized distributor for Alpha, Amphenol, Belden, Kings, Times Fiber

Call NEMAL for computer cable, CATV cable, Flat cable, semi-rigid cable, telephone cable, crimping tools, D-sub connectors, heat shrink, cable ties, high voltage connectors.

HARDLINE 50 OHM FLC78 7/8" Cablewave corr.copper blk jkt ....... 3.92/ft NM12CC N conn 1/2" corr copper m/f ......25.00

COAXIAL CABLES (per ft)

1705 RG142B/U dbl silver shid, tellon ins .......... 1.50 1310 RG217/U 50 ohm 5000 watt dbl shid .............98

ROTOR CABLE-8 CONDUCTOR

CONNECTORS-MADE IN USA

FLC12 1/2" Cablewave corr. copper blk jkt ...... 1.59/ft NE723 Type N jack for Belden 9913....... 4.95 PL259AM Amphenol PL259 ......89 1102 RG8/U 95% shield low loss foam 11ga............36 UG83B N Jack to PL259 adapter, teflon ................................ 6.50

UG146A SO239 to N plug adapter, tellon ............... 6.50 1130 RG213/U 95% shield mil spec NCV jkt.....................39 UG255 SO239 to BNC plug adapter, Amphenol....................3.29 

GS38 3/8" tinned copper braid .......35/ft GS12 1/2" tinned copper braid ......50/ft 

All prices plus shipping, \$3.00 min, Visa/Mastercard \$30 min, COD add \$3.00 Call or write for complete price list. Nemal's new 36 page CABLE AND CONNECTOR SELECTION GUIDE is available at no charge with orders of \$50 or more, or at a cost of \$4 with credit against next qualifying order.

NEMAL ELECTRONICS, INC. 12240 NE 14th Ave. N. Miami, FL 33161 (305) 893-3924 Telex 6975377 24hr FAX (305)895-8178

## Entry Level Price. Extra Class Performance.



Scanning Microphone

New Optional

Now Novices and Technicians can enjoy their new 10 Meter phone privileges and DXing with our new Ranger AR 3500 Mobile Transceiver!

• Two Models to Fit Your Budget & Power Needs: 30 Watt & 100 Watt

Microprocessor Controlled Circuitry
 Exceptional RX Specifications

· Very Compact · Manufactured in Japan & Quality Checked in U.S.

· Low Breakthrough Price · New Optional Scanning Microphone

East Coast Warranty Center

Exclusive NI-Cad Battery Backup Dealer Inquiries

Welcome

ORDER TODAY

RF MicroTech (508) 667-8900 WISA

4 Carmel Drive N. Billerica, MA 01862

## **GOES 1691 MHz RECEPTION**

S-BAND CONVERTER FOR YOUR 137 MHz RECEIVER

1691-LY (N)

PREAMP MMg1691

CONVERTER MMk 1691-137.5

RECEIVER 137.5 MHz

1691-LY (N) GAIN: 20dB BOOM: 6'

MMg 1691 GAIN: 13dB

\$250.00

N.F.: 1.2dB 12VDC @ 40 ma

GAIN: 30dB TYPICAL N.F.: 6.8dB MAXIMUM 12VDC @ 150 ma

MMk 1691-137.5

\$330.00

Send 75¢ (3 stamps) for detailed specs on all VHF & UHF products. Shipping FOB Concord, MA PRICES SUBJECT TO CHANGE WITHOUT PRIOR NOTICE



\$91.50

SPECTRUM INTERNATIONAL INC. P.O. Box 1084S, Concord, MA 01742, USA

(508) 263-2145

VISA

**CIRCLE 183 ON READER SERVICE CARD** 

## 73 INTERNATIONAL

edited by C.C.C.

## Notes from FN42

Korea and the Olympics. Sometimes things just plain go wrong-and our planned coverage of the Olympics just plain went wrong. Byong-Joo Cho HL5AP did his part, but a combination of postal services and office confusion led to our failure to get two of his reports and to temporarily (from February 18 to September!) mislay another one. HL5AP earned his subscription to 73 and he'll get it; for those of you who may have been looking for our coverage-apologies. CCC hopes you got the information you needed elsewhere.

As usual we have much more material than can fit in these pages, but the IARN information from Sam Voron VK2BVS, Peter ZS6ET's first Hambassador report from the Republic of South Africa, and Hambassador UA9MA's material clearly deserved priority attention. (Even so, two-thirds of the report from ZS6ET will have to be held over for the future.)

Anyway, HAPPY NEW YEAR to those who are starting 1989 on the 1st of January (with the 2nd being Dia del Ano Nuevo, Nouvel An, Neujahrstag, and New Year's Holiday in Scotland), and a plain old wish for happiness to those whose new years begin later; we'll celebrate the dates of theirs at the appropriate times. Other January dates to note for your QSOs: January 1 is Haiti's Independence Day (on the 4th for Burma and the 31st for Nauru); 7-Ethiopian Christmas; 9-Martyrs' Day, Panama (the 29th for Nepal); 15-Adults' Day, Japan; 23-National Holiday, Australia; 24-Economic Liberation Day, Togo; 26-Anniversary of the Proclamation of the Republic, India.

### Roundup

Australia. (And Jamaica, USA, El Salvador, Mexico, New Zealand, Great Britain, Germany, Belgium, Sweden, Israel, Cayman Islands, United Kingdom, Japan...other countries).

## HURRICANE GILBERT

Emergency.....!
The following is from a report by the IARN Director for Australia, Sam Voron VK2BVS (4071066), 2 Griffith Avenue, East Roseville

2069, Australia. Chris CK3YID in Melbourne, 036014222, has just attempted to telephone Glenn Baxter K1MAN (Network Manager of the International Amateur Radio Network (IARN) in the USA... he is told K1MAN busy handling emergency traffic...something about a hurricane in the ocean off the eastern US coast...halfway around the world...

Nothing to concern me, weather lovely in Sydney. But let's tune in on NBC's "Today" show, which is aired every night over a VHF Sydney commercial TV channel...

Jamaica hit by biggest hurricane ever recorded in the northern hemisphere, 500 miles wide...

Mexico City and San Salvador were halfway around the world, too, and they sure needed all the help Australian hams could give...

The Australian Traffic Network is activated ... VK3CKK 037291624 notified Red Cross ... VK6OP 092774661 and VK6RQ 092771514, Perth, to handle Red Cross-referred calls on health & welfare matters... 14.275 MHz declared emergency frequency (with ±5 kHz guard band), to be controlled by IARN to carry messages from the Jamaican Defense Force station 6Y5B64...many on this frequency because all power, phones, navigational aids at airfields out: aircraft, US State Department, Salvation Army, Red Cross... only well-prepared hams, with generators and fuel, able to provide vital remaining links... 14.325 MHz (±3 kHz), other FCC channel for emergencies, controlled by National Hurricane Center in Miami...hurricane planes use this as they fly through the storm to measure and track it . . .

Australia and New Zealand relay important info when conditions make coverage difficult...we watch the Caribbean and jump in when needed...over 100 health & welfare messages generated now, relayed to Jamaica through the US since no third-party agreement with Jamaica—so direct service without delays involved when third-party agreements get negotiated before help can be provided...

New Zealand authorities mean-

while ruled that NZ radio amateurs could not help the public despite no telephone communication existed...G4SCA on British RAYNET (the RSGB emergency group) activated and helping the British High Commission...DA2GY in Germany active as well as full US Army Military Affiliate Radio System (MARS)...Belgium, Sweden also; all providing health & welfare message help...Israel amateurs stay alert....

Weekend of 17 September coming up; would everything settle down so we can go ahead with our annual 48-hour Amateur Radio Display at El Park, which was supposed to coincide with our simulated emergency test?...

Cayman Islands hit...storm headed for Mexico...annual Australian Fun in the Sun and Under the Moon amateur radio display and simulated emergency test cancelled...five US amateurs deployed to set up facilities in Jamaica—Dave K2BPP, Ralph N4HTU at Montego Bay with access to commercial telephone satellite link...Bill WB2TUU with Oral Roberts medical team near Kingston...Bob N4MHV at Sandy Bay...Al W9ELR at Kingston Salvation Army station....

September 19: Australian Traffic Net sends Happy Birthday to IARN: it's three years since the Mexico City earthquake and the birth of IARN...

Relief agencies not able to send in medical volunteers without assurance of radio amateurs available full time and US volunteers in Jamaica have to leave (a wife having a baby, etc.) and new ones getting hard to find ... United Kingdom offers two, Australia requested by IARN to send one, Japan asked for volunteers...as of September 20...no transport available for non-US volunteers, but Gordon VE3FBU an exception-accompanied Jamaican Consular General, set up communications at Runaway Bay, and this message broadcast:

Situation in Jamaica now urgent. Need food, building material, antibiotics of all kinds, clothing. We have no beds and water is very bad. The people of Jamaica are making all efforts to ensure all tourists are being taken care of.

Australia active 0500 to 1000 hours universal time when, although many net control stations monitoring 14.275, North America mostly asleep and/or coverage into Jamaica difficult...so man-

ning net control . . . assisting traffic from Europe to Jamaica and Jamaica to US, so Jamaica stations can come on frequency anytime, get messages off, and go off the air to conserve fuel or batteries... Ashley 6Y5GR can operate only Morse code, battery low, but reports excellent, relayed to US: all water has to be boiled, bananas and sugar cane all gone ... VE3FBU reports people sucking on sugar cane to survive . . . above message causes Australian Dept. of Foreign Affairs to donate \$20,000 to help Jamaica...US asked for \$400 million: 95% of Jamaica's economic base destroyed . . .

October 1, 1988 summary (as of this writing). 14.275 remains as the emergency frequency and IARN continues to look for volunteers to go to Jamaica to man field stations. More Jamaica stations coming on the air as the president of the Jamaica Amateur Radio Association (JARA), Selvin 6Y5SG, mobilizes resources. Dave K2BPP draws up disaster communication plan, is debriefed by US representative assessing Jamaica's needs. IARN has donated quantities of gear-aerials, generators, you name it-personally owned as well as from AEA, Heath, Tandy, others.

I am proud of the way so many newcomers to amateur radio became so fully involved in this emergency, and want to thank all US Novices, Technicians, and other 10-meter operators who monitored 14 MHz and kept Australia fully informed when 14 not open to Australia. This worked so well that from now on when a disaster hits there will be an Australian station looking...into the USA in the US Novice voice band, 28.3 to 28.5 MHz as a part of our plan for the Australian net.

The IARN now is seeking any volunteers whether with amateur licenses or not, to serve as gobetweens between radio ops and the local people. On the 10-meter band from Australia, I have been asking USA Novices and Technicians to contact the public via local radio stations, talk shows, CB airwaves, SWLs, scanner listeners, to tell that volunteers are needed to be the eyes and ears of Jamaica.

Volunteers can always phone Glenn Baxter K1MAN (207) 495– 2215. or FAX (207) 495–2069. [Ed. note: As of January the foregoing may be out of date, but the need for IARN volunteers to be available never is.—CCC]

Japan. From The JARL News for August: "It is essential that all hams be aware of the current worldwide trends that affect amateur activities. Amateur radio communications means worldwide communication and thus worldwide interaction." Living up to this, JARL sent a delegation to the Region III annual meeting in Seoul, South Korea (in October), which included the president, vice president, and managing director (JA1AN, JA6AV, and JA1HQG). "Japan has the most amateurs in the world and is expected by other countries to play a leadership role in Region III and shoulder responsibility for the development of international amateur radio."



Jeff Maynard G4EJA 32 Waldorf Heights Hawley Hill Camberley GU179JQ England

The UK Scene The major news is the publication of the new UK amateur license by the UK regulators, the Department of Trade and Industry. It incorporates a number of significant changes, all of which are for the better. Although largely cosmetic or administrative, they have relieved the amateur of a number of bureaucratic chores and should, if nothing else, ease the conscience of those who did not fully stick to the rules.

Until now a multipage document, the license is in two parts. A single-sheet validation document confers legality and is renewed annually (when the fee is paid!), and a separate booklet sets out the terms and conditions of the license. The same documents serve all types of amateur stations-club, reciprocal, maritime mobile (but not aeronautical mobile, despite the efforts of the RSGB).

The Europeanization of the UK continues apace with the adoption in the new license of the standard CEPT draft agreement, allowing visiting CEPT license holders to operate in the UK and UK amateurs to operate in most European countries without special permission. (CEPT is the European PTT 'club' which sets many international telecommunications standards.) US amateurs can still, of

course, apply for a reciprocal license.

Other changes:

- The rather strange UK suffix /A (for operation from a so-called 'alternate' address) has been replaced with /P for operation away from the main station, and may be used for unlimited periods instead of for only four weeks at a time.
- The DTI has recognized the arrival of the computer age and now permits the station log to be kept on magnetic tape or disk and has relaxed rules defining what must be recorded.
- Computer buffs can now legally operate their 'digipeaters' and can receive and transmit digital messages without the (theoretical) need to review each one.
- · Low power beacons may now be set up without special permission, and low power links are OK for remote control.
- · When operating other than with telephony, it is no longer necessary to ID with a CW transmission of at least 15 wpm-it can be sent in Morse at any speed. When retransmitting a recorded transmission from another station, it no longer is required that the recorded callsigns be deleted before retransmission.
- Restrictions have been removed for operating an amateur station on behalf of social organizations—such stations are no longer required to notify the DTI of their names. (Helpful. I remember the problems of trying to organize GT4EJA/MM for charitable purposes a few years ago.)
- · And it is now permissible to conduct crossband contacts using receive frequencies not licensed in the UK (but presumably legal in the country of origin).

The very observant of you might have noticed all-American spelling this time (license not licence, organization not organisation). This is due to my use of the US version of a word processor (Professional Write); I now have an IBM PS/2 operating under PC-DOS. Good news in that the IBM is much faster than my old Apple 2 and much more versatile and I have access to a wide range of software. Any helpful contributions from you would be most welcome because the bad news is that all my amateur software (SSTV, RTTY, CW send and receive, satellite orbital predictions) is no more, and I don't know what is available. While home computers are popular in the UK, things tend to be home-grown nonstandard such as the BBC. There is,

therefore, a complete lack of amateur software for industry standard machines. What PC-DOS program disks do you have?



HONG KONG

Phil Weaver VS6CT PO Box 12727 Hong Kong

They say lightning never strikes twice; I sincerely hope that this is true as once again HARTS suffered a major loss of equipment when the digipeater operating very successfully on 29.010 MHz was zapped by lightning in early August, leaving the antenna looking like a sad tail after the night before and the equipment full of little holes! I had never seen the likes of it. We still have not resumed that service [written in mid-September-Ed.] but I am hoping that the two beacons which have been established for a few years will be back up on the air shortly, after having been down for reconstruction of the building they are in. To remind those interested. the 10-meter beacon will be operating on 28.290 MHz and on 6 meters at 50.075, with the callsigns VS6TEN and VS6SIX respectively.

After my departure from HARTS (see column in the June, 1988, issue) I established a new society aimed at providing service for the expatriate community in the form initially of the provision of an English-speaking repeater. This is up and running on 145.575-600 with a CTCSS tone needed on the transmissions. If you are coming to Hong Kong and would like to learn more, drop me

a line at the above address or phone me on arrival at 5-772313. The group is the English Language Amateur Radio Communications Society (ELARCS), and we have quarterly meetings at which all are welcome.

The PO address above is because I expect to move into a new apartment the first quarter of 1989 and don't yet have the new address. The saga of the flat move is an ongoing pain in the neckshould have moved a long time ago but a fire in the high rise, put out with helicopters using salt water from our 'fragrant' harbor, meant that the top two floors had to be demolished and reconstructed!



SOUTH AFRICA

Peter Strauss ZS6ET PO Box 35461 Northcliff, ZA-2115 Republic of South Africa

Guest licenses in South Africa. South Africa decided in 1980 no longer to follow the example of the British and US administrations, as they issue licenses to bona fide tourists only if a bilateral agreement has been concluded between the home country of the tourist and the administration of the country to be visited. In South Africa this was considered discriminatory against tourists from rare DX countries whose administrations would not be willing to conclude an agreement for maybe one tourist in five years.

After extensive research by a select committee of SARL (the South African Radio League) into license procedures of other coun-



Lion Bob ZS1ABO, coordinator of joint amateur and Lion activities in South Africa. (Photo by Bob Adshade)


tries, a proposal was submitted to the authorities with the result that since 1981 any amateur from any country may apply for a 3 month permit to operate while in the Republic of South Africa. A fee of Rand 12 (approximately US\$5) is payable on arrival. Two license classes compatible with the CEPT class I and CEPT class II are available. (No compatible license class to the US Novice license exists in South Africa.)

In order to cater for amateurs entering for longer periods and to allow for the permanent conversion of

foreign licenses to South African callsigns, agreements with Israel, Portugal, the German Federal Republic, Chile and the USA followed. Agreements with Great Britain, Swaziland, Zimbabwe, Botswana, Bophuthatswana, Venda, Transkei, South West Africa and Ciskei have been in force for some time. Amateurs from agreement countries are not limited to a three-month permit. Their permits are issued free of charge and they may apply for the conversion of their home callsign to a South African callsign if they intend to stay permanently or semi-permanently in South Africa.

Any person, regardless of nationality, may sit for the multiple choice RAE exam in South Africa. In fact the Wits Central Repeater covering the greater Johannesburg area is typical for the cosmopolitan nature of amateur radio in South Africa. While QSOs are predominantly in English and Afrikaans, callers in German, Portuguese and Hebrew are very likely to get an instant answer even late at night.

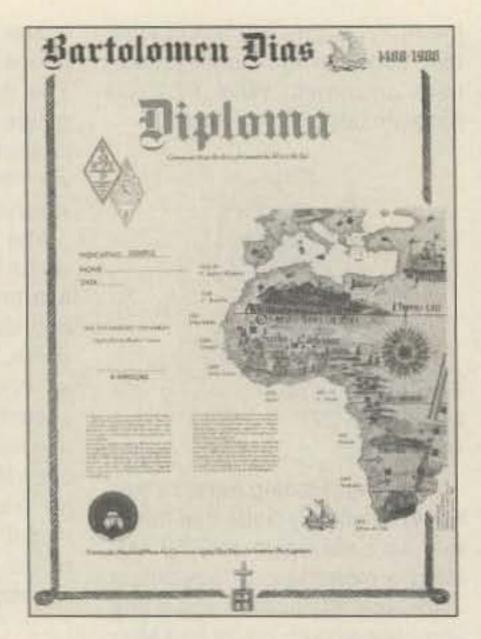Portuguese nationals living in South Africa may sit for the RAE in



South Africa in their own language and obtain a certificate by their own administration in Portugal. Such license may by used to apply for a callsign in South Africa, easing the language problem for the many Portuguese speakers.

The IARU Region I band plan applies in South Africa and visitors should use the two-meter band from 144,000 MHz to 145,999 MHz only. The 220-MHz band is not available for the amateur radio service in South Africa.

Further information may be obtained by writing to the SARL at PO Box 3911, Cape Town 8000, Republic of South Africa.

Lions in South Africa. The days of the lions roaming free in the country are a thing of the past, with mining, agriculture, and urbanization claiming their share. Today's Lions can be found regularly teaming up with radio amateurs for events like the "Hunting Lions in the Air," held every January. This year's will be on January 7th and l4th.

This event seems to be very popular in South Africa, looking at the results of the 1988 event. First place in the Club category (phone)

went to ZS6TJ. This station is located in the Johannesburg Amateur Radio Center (Louis Botha Ave., corner Duff Rd. Houghton, Johannesburg). Second place went to ZS6TVL located right next to the world famous Kruger National Park where one can still find real lions!

In the Club category (CW) the first place went also to ZS6TJ in Johannesburg. In Cape Town the third place was retained by ZS1VP in the individual operator CW category. Overall participation was also very high with South Africa fielding the second largest number of stations in the world, with only the USA fielding more stations. Considering there are only just over 5000 radio amateurs licensed in the Republic, this is no mean feat.

With many rare club and event stations scheduled to participate in this event again, this could be your opportunity to get a rare QSL card.

The Dias Award. The Bartolomeu Dias Award is a unique award issued to commemorate 500 years of some of the most important sea voyages which demanded a complete revision of geography and led to a new phase in the life of humanity.

The voyage of Bartolomeu Dias sue.—CCC] 73

when he arrived in the Indian Ocean with his caravels in 1488 stands out above all others. It allowed for the encounter of civilizations until then unknown to each other and led to great consequences in science, culture, economics, politics, and demography.

Issued in cooperation between the Johannesburg Branch of SARL and the National Amateur Radio Society Portugal (REP), the award is a further step to increase the good relations of South African and Portuguese radio amateurs and their friends in the world.

To qualify, 5 contacts with South African (ZS/ZR) stations and 5 contacts with stations in Portugal (CT) in the period January I, 1988 to June 1989 are required by stations other than those two countries. Applications must be submitted not later then December 31, 1990. All bands; CW, RTTY, and phone. Also available to SWLs. QSLs not required. Applicants should submit certified logs with 10 IRCs or US\$5 to the Awards Manager SARL Johannesburg, PO Box 2327, Johannesburg 2000, Republic of South Africa.

[Packet radio report in a future is-

## WEST SIBERIA DX CLUB BEGINS SWDXC AWARDS PROGRAM

Gennady Kolmakov UA9MA, our Russian Hambassador, writes that "We have founded one of the first DX clubs in the USSR . . . with UA9MC as president . . . and UA9MD, secretary." UA9MA is vice president, and he sends us the following.

- 1. AOA (Arctic Ocean Award) Details next month. 2. WAWS (Worked All West Siberia)-Work following oblasts: 099, 100, 130, 145, 146, 158, 161, 162, 163. Class 1-40 QSOs in 9 oblasts, Class 2-30 and 8, Class 3-20 and 7.
- 3. U-PX-A (USSR Prefix Award)—Class 1—200 prefixes, Class 2-150, Class 3-100, Class 4-50.
- 4. U-1,000,000-C (USSR million-population Cities)- Work: Alma-Atu, Baku, Cheliabinsk, Dniepropetrovsk, Donetsk, Gorky, Kharkov, Minsk, Moscow, Novosibirsk. 5. PX-9-A (Prefix 9 Award)-Work stations with figure 9 in their prefixes. Class 1-50 prefixes from 20 countries on 6 continents, Class 2-40 from 15 on 4, Class 3-30 from 10 on 3.
- 6. WSA (West Siberia Award)-Work stations from Zone 17 (WAZ) with the last callsign letters from which spell the title of the award. For example: UA9AW, UL7CE, UA9MS, UH8BT, and so on for all 16 letters.

All contacts (or SWLs) must be made after January 1, 1980. No QSLs; send certified list to Serge F. Kruglov UA9MC, PO Box 836, 644099 Omsk, USSR.

"Rules for WSDXC membership: 1) 100 awards and certificates, including 'R-150-S' (or DXCC with 150 countries) and 3 ones from WSDXC, or; 2) 200 countries (R-150-S or DXCC with 200 countries) and 3 awards from the WSDXC. The entering fee is 20 IRCs. All applications must be signatured by 2 licensed amateurs."

## SOUTH AFRICA FIRST COUNTRY TO ACCEPT 73 UNIVERSAL APPLICATION

Peter ZS6ET writes: "If you intend to visit South Africa, address your application for an amateur radio permit to The Department of Telecommunications, Private Bag X74, Pretoria 0001, Republic of South Africa. The Universal Permit Application published in '73 International' [see October's issue, page 88] offers more information than required and should suffice." Peter's statement is based on information from the Department, but this is not an official approval, of course; that will not be sought until the form is further revised, based on comments and criticisms from around the world over the next two or three months.

## 800-882-1343





HF Equipment IC-735	List	JUN's
ICOM		
IC-781 New Deluxe HF Rig	\$5995	Call \$
IC-761 Loaded with Extras	2699	Call \$
IC-735 Gen. Cvg Xcvr	1099	Call \$
IC-751A Gen. Cvg Xcvr Receivers	1699	Call \$
IC-R7000 25-1300# MHz Rcvr	1199	Call \$
IC-R71A 100 kHz-30 MHz Rcvr VHF	999	Call \$
IC-228A/H	509/539	Call \$
IC-28A/H FM Mobile 25w/45w	469/499	Call \$
IC-02AT FM HT	409.95	Call \$
IC-2GAT 2m 7w HT	429.95	Call \$
IC-900 Six Band Mobile UHF	639	Call \$
IC-48A FM Mobile 25w	509	Call \$
IC-04AT FM HT	449	Call \$
IC-4GAT 440MHz HT 220 MHz	429.95	Call \$
IC-38A 25w FM Xcvr	489	Call \$
IC-32AT 2m/70cm HT	629.95	Call \$

## KENWOOD

1 / 1 4 1 1	0	
RZ-1 WIDEBAND RCVR	599.95	Call\$
HF Equipment		
TS-940S/AT Gen. Cvg Xcvr	2449.95	Call \$
TS-440S/AT Gen. Cvg Xcvr	1449.95	Call \$
TS-140S Compact Gen. Cvg		
Xcvr	949.95	Call \$
VHF/UHF		
TS-790A 2m-70cm 1.2 GHZ	1999.95	Call \$
TS-711A All Mode Base 25w	1059.95	Call \$
TR-751A All Mode Mobile 25w	699.95	Call \$
TM-221A 2m 45w	459.95	Call \$
TM-2550A FM Mobile 45w	519.95	Call \$
TM-2570A FM Mobile 70w	623.95	Call \$
TH-215A 2m HT Has It All	399.95	Call \$
TH-25AT 5w Pocket HT NEW	369.95	Call \$
TM-721A 2m/70cm FM Mobile	729.95	Call \$
TM-421A Compact FM 35w	469.95	Call \$
TH-45AT 5w Pocket HT NEW		Call \$
220 MHz	389.95	
TM-3530A FM 220 MHz 25w	519.95	Call \$
TM-321A Compact 25w Mobile	469.95	Call \$
TH-315A Full Featured 2.5w HT	419.95	Call \$

YAESU		
HF Equipment		
FT-767 GX Gen. Cvg Xcvr	1929.95	Call \$
FT-757 GX II Gen. Cvg Xcvr	1129.95	Call \$
FT-747 GX New Economical		
Performer	889.95	Call \$
FL-7000 15m-160m AMP	1995.00	Call \$
VHF		
FT-212RH NEW 2m 45w	459.95	Call \$
FT-712RH 70cm 35W	499.95	Call \$
FT-290R All Mode Portable	599.95	Call \$
FT-23 R/TT Mini HT	344.95	Call \$
FT-209RH FM Handheld 5w	389.95	Call \$
VHF/UHF Full Duplex		
FT-736R, New All Mode		
2m/70cm	1749.95	Call \$
Dual Bander		
FT-727R 2m/70cm HT	439.95	Call \$
FT-109RH New HT	399.95	Call \$



3919 Sepulveda Blvd. Culver City, CA 90230 213-390-8003

CIRCLE 272 ON READER SERVICE CARD

## NEW

## **New Mod Kit** for Bird Model 43 Wattmeter

MEASURES PEAK POWER OF SSB AND OTHER AM SIGNALS

Bird Model 4300-400 modification kit quickly adapts any Bird Model 43 Wattmeter to measure audio peak power

of single sideband and other AM modulated signals.

The 4300-400 kit pc board mounts inside the Model 43 housing, on the meter studs. Estimated conversion time is only 15 minutes from start to finish.

Once modified, you can measure peak power to an 8% F.S. accuracy, without affecting cw operation or accuracy.

And, the Model 4300-400 is surprisingly inexpensive. Contact your Bird distributor or factory for details.

30303 Aurora Rd., Cleveland (Solon), Ohio 44139 — 2794 216-248-1200 TLX: 706898 Bird Elec UD FAX: 216-248-5426 WESTERN REGION OFFICE: Bird Electronic Corp. 621 Ojai Ave., Suite F. P.O. Box 28, Ojai, CA 93023 805-646-7255

**Electronic Corporation** 

CIRCLE 176 ON READER SERVICE CARD

## BENEFITS FOR YOU

QST, QSL Bureau, Awards, Low Cost Insurance, Operating Aids, Government Liaison and More-Much More!

Name	IP APPLICATION	Call
City	Prov./State	PC/ZIP

\$25 in U.S. \$36 elsewhere (U.S. funds) Licensed amateurs, or age 65 or over, upon submitting proof of age, may request the special dues rate of \$20 in the U.S. \$28 elsewhere, in (U.S. funds) Persons age 17 and younger may qualify for special rates, write for application.

For postal purposes, fifty percent of dues is allocated to QST, the balance for membership.

Charge to □ VISA □ Mastercard □ AMEX □ Discover Expires \_\_\_\_\_ Card Number \_\_\_\_\_ Signature \_\_\_\_\_

> The American Radio Relay League Newington, CT. 06111 225 Main St.

USA

73

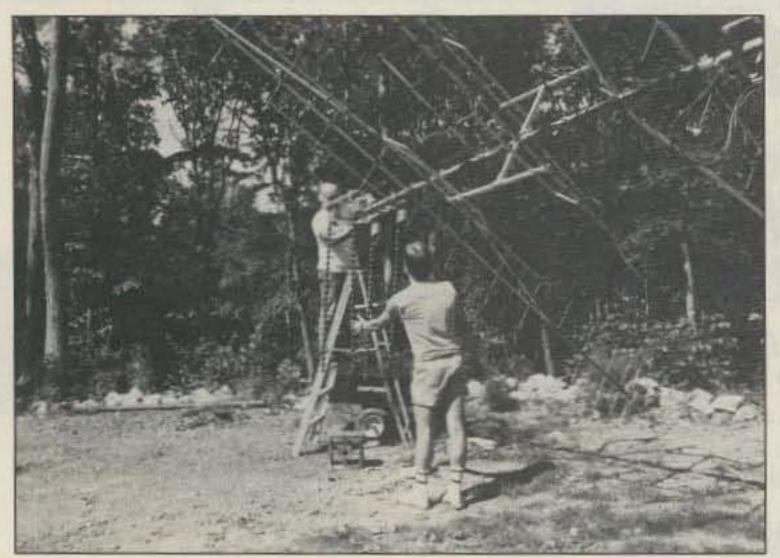


Photo B. Reinstalling the "phoenix" 2304 array. It worked well enough to bag five grids.

FN55, 64, 74, and even FN48, a grid located in a very remote section of Quebec, far north of Quebec City. The 2 meter station worked most of these same grids and bagged a fairly rare one in EM77 in central Kentucky. Our new operators couldn't have had a better introduction to the wacky world of VHF contesting!

#### After The Battle . . .

After the dust cleared, we wound up with about 550 QSOs and more than 165 grid squares, 51 of which were on 2 meters alone. And I've heard about even higher 2 meter totals from the Midwest, pushing well over 80. The best part was being able to knock all the stations down and leave for home just thirty minutes after the contest ended. Now that our new operators have survived basic training, maybe we'll give it a go again this January.

### Mid-Atlantic Conference

The Mt. Airy VHF Radio Club, better known as the Pack Rats,

just wrapped up another successful doubleheader weekend with the 12th Mid-Atlantic VHF Conference and Hamfest. They offered a good dose of technical presentations, an expansive flea market, and lots of fun. This was the first year I attended the banquet, and I managed to make a few of the seminars, which covered a variety of topics. Among them were: Propagation Enhancement

prizes were awarded. Coaxial Dynamics graciously donated a wattmeter that I reviewed for 73, and Avantek Corporation came up with several MMICs, bipolar, and GaAsFET devices, along with application sheets and PC boards. The evening concluded with a showing of the SCORE 1987 FM27 multi-projector show, after which all hands were off to the hospitality suite to talk shop while watching the Olympics.

Sunday brought overcast skies, that eventually cleared for a perfect sunny day. I brought some items to the flea market, many of which sold very quickly. There was more of a buying frenzy this year than last year (probably because it rained in 1987), and there were many good deals on antennas, coax, amplifiers, preamps, and just about any parts you can think of. If you live within a few hundred miles of Bucks County, try to make it in 1989. There's plenty of motel space for overnight stays, and it's fun to meet many of the faces that go with the familiar callsigns.

## **Project Time**

From time to time, I will mention

. . . we wound up with about 550 QSOs and more than 165 grid squares, 51 of which were on 2 meters alone."

Indicators, 6 meter Contest Arrays, VHF/UHF QRP Contesting, Water Cooling UHF Power Amplifiers, and Home-brew Microwave Dish Feeds.

About 100 people attended the banquet, and some great door sources for microwave parts in this column. One of those sources is Steve Kostro N2CEI, who was selling at the Pack Rats flea market, and who has a nifty line of "roll your own" preamplifiers for 50 through 2304 MHz. I had already picked up a 903 MHz version and added a 1296 kit for good measure, with the idea of putting up mast-mounted preamps. Since I already had a pair of Dow-Key 260 relays in the parts box, it seemed like the thing to do.

The preamps sell for just \$35 and include a Bud minibox, etched PC board, and all parts, including a NEC 720 series GaAs-FET (typically a 72089 device). Steve claims a noise figure of better than 1 dB for these kits when properly tuned, and they are small enough to tuck away just about anywhere. They look like good weekend projects, and I'll let you know next month how they work.

## Nice Tip

Incidentally, just how do you set up a preamp for lowest noise figure without a Noise Figure Meter? Well, it's easy if you have a weak signal source (such as a beacon), and you can switch to FM mode on your transverter/receiver combination or multimode. Then you just tune for best quieting. I tried this with a 432 and 220 preamp, and it works quite well, as the trimmer setting is not quite at maximum gain. Conversely, adjusting for maximum gain did degrade the signal-to-noise ratio somewhat. Thanks to W1VD for this tip.

Maximum quieting can be measured with a standard VTVM or FETVOM, using the AC scale and taking a signal from the quad detector or ratio detector. You can even take it from the speaker output, if necessary. It's not hi-tech, but it's a lot cheaper than purchasing an NF meter.

Once that preamp is set right, you'll want to put it in a weatherproof enclosure, add a few relays, build a sequencer, and run extra coax up the tower-it's all part of going Above and Beyond! 78

## INDIANA HAMFEST

## **SUNDAY, MARCH 12, 1989**

Open at 8:00 A.M. Located on the Indiana State Fairgrounds Indianapolis, IN

· All Indoors · Free Parking - Paved Lots · Forums - Nationally Advertised Commercial Dealers . Flea market . VEC DEVRY Testing . Ladies Forums and Activities Over 500 Tables

> Enjoy a show by our "Quality" Dealers Talk-in on the "Mighty (2.1 KW) 525" - 145.25 MHz

> > NOTE: TABLES SOLD OUT IN 1987 AND 1988

For Tables: SASE To: Aileen Scales KC9YA, 3142 Market Place, Bloomington, IN 47401, 812-339-4446



PLUG INTO PACKET!

## Simple and Easy.

Here's the easiest packet radio yet, you don't even have to buy a TNC to join the digital revolution. Just let your PC do the work. Plug a PC Packet Adapter into any expansion slot and get on the air in minutes, just like an expert. And you'll still be able to use the PC for other work! The complete VHF system is only \$139.95!

## Sophisticated, Too.

When you've mastered the basics, use the PC\*Packet Adapter for simultaneous dual-band HF/ VHF, multiconnect, BBS, TCP/ IP, DXer's PacketCluster, 2400 baud (and higher). Even use the Developer's Package to write your own packet application.


## Software Included.

Unlike others, DRSI includes all the software you need. The THS terminal package has split screen, file save/send, binary file transfer, print, scroll, review and more.
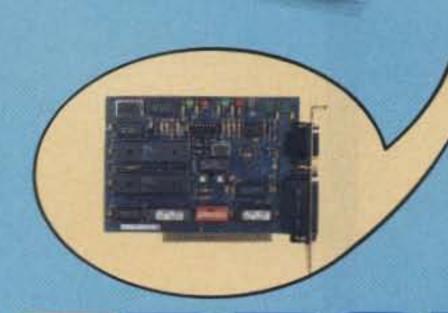
## 2400 BAUD

Many areas are upgrading their packet nets to this higher speed. DRSI's M-24 modem for 2400 baud connects simply with no modifications to your rig and lets you operate both 1200 and 2400 simultaneously with your present radio. Step up to this new speed for just \$79.95, today!

> Call or Write for complete **Product Catalog**



2065 Range Road Clearwater, FL 34625

ORDERS: 1-800-999-0204

**CIRCLE 239 ON READER SERVICE CARD** 

NO TUNERS! NO RADIALS! NO RESISTORS! NO COMPROMISE!

THREE EXCELLENT REVIEWS JUST DON'T HAPPEN BY CHANCE. CALL US FOR A FREE CATALOG

BILAL COMPANY

137 Manchester Dr. Horissant, CO 80816 PH: 719-687-0650

CIRCLE 42 ON READER SERVICE CARD

## CB-TO-10 METERS

We specialize in CB radio modification plans and hardware. Frequency and FM conversion kits, repair books, plans, high-performance accessories. Over 12 years of satisfied customers! Catalog \$2.

**CBC INTERNATIONAL** 

Charles / Antons The Sparky J-Antenna is a flexible half wave radiator fed by 1/2 wavelengths of low loss coax through an efficient linear matching transformer. Sparky J's beat duckies, 1/4, & 5/8 wave antennas, need no ground plane. Low flat SWR curve gives edge to edge band coverage. Great portable-rolls up to fit in pocket. Completely assembled with BNC connector,

· Easily hidden · Effective indoors or out. · Money-back guarantee · Available for every band from 14 to 440 MHz \$3995 each Two for \$6500 Add \$5 P & H Infopack \$1 by 1st class mail AntennasWest Box 50062-S, Provo, UT 84605 (801) 373-842

CIRCLE 5 ON READER SERVICE CARD

## Six Function DTMF Controller



Auto-Kall AK-4

- Outputs: 2 or 3 latched, 1 or 2 momentary, 1 timed and 1 manually reset group-call latched for remote alarm
- Different codes for turning outputs on/off NOT toggle on/off like most others! . Wrong number reset
- 4-digit acess code can use \* up # down
- · Multiple group-call response · On-board 1-amp relay

MoTron Electronics

695 W. 21st Ave.

Eugene, OR 97405

\$69.95 (board/kit) . . . .

(wired/tested board) . . \$89.95 AK-4C (Complete unit in metal enclosure with in/out jacks, built-in speaker, etc.) . . . . . . \$139.95 Plus \$3 00 shipping & handling


Call Toll Free 1-800-338-9058 or (503) 687-2118

CIRCLE 127 ON READER SERVICE CARD

P.O. BOX 31500X, PHOENIX, AZ 85046

## ORDER TOLL FREE (800) 426-2820



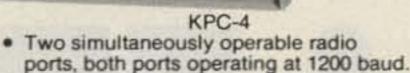

- · Automatic gateway operation between Kantronics Personal Packet Mailbox
- feature included. RS-232 or TTL level operation by jumper selection.

Price

27900



KPC-2

- Compatible with any computer having a serial, asynchronous I/O.
- Includes VHF and HF modem software selectable.
- Full duplex capability.

Price


14900

HAMTRONICS, INC. 4033 BROWNSVILLE ROAD

TREVOSE, PA. 19047 (215) 357-1400

Hours M,T,W - 9-6 Th-F - 9-8 Sat. - 9-3

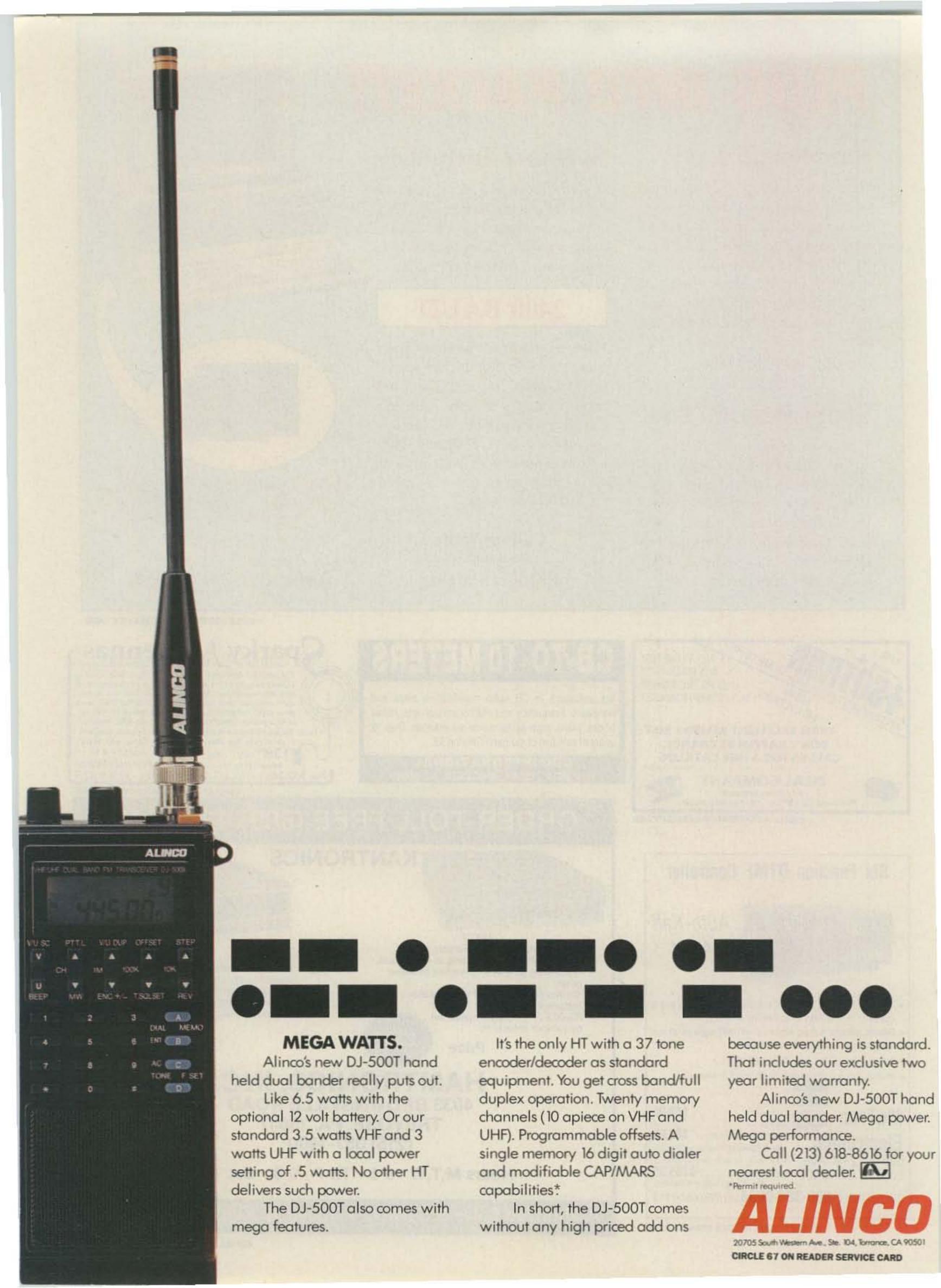Authorized Sales & Service — Yaesu ■ Kenwood ■ Icom



A high-performance HF rig... with a great receiver and full-power transmitter. Light in weight and low in price.

This is Yaesu's FT-747GX.

Whether you're a novice or a veteran, it's a great way to start. And a great way to go.

DX ready. The 747 packs a full 100-watt RF punch on 160 to 10 meters, with continuous receive from

100 kHz to 30 MHz.

And its control panel is refreshingly simple. So you can hop around the band *fast* to nail those DX stations. While other guys are warming up their amplifiers, you can be working the DX!

Multimode versatility. The FT-747GX is ready to go on LSB, USB, CW, and AM. With provision for the FM-747 FM unit—great for watching 10-meter repeaters.

You get 20 memories to store frequency and mode. Dual VFOs with split frequency operation for DX-pedition work. And manual band scan plus auto-resume memory scan via the microphone up/down buttons.

Great receiver. Utilizing a directly-driven mixer, the FT-747GX receiver features superb overload protection. You also get factoryinstalled narrow CW and AM filters. A one-touch noise blanker. All-mode squelch. RIT. And a 20-dB attenuator for local QSOs.

Lightweight construction. Housed in a metallized high-impact plastic case, the FT-747GX weighs in at about 71/4 pounds! With the loudspeaker mounted on the front panel for maximum audio transfer. And internal heatsinking for the transmitter, rated at full power for FM, packet, RTTY, SSTV, and AMTOR when

used with a heavy-duty power supply.

Available options. FC-1000 or FC-757AT Automatic Antenna Tuners. FL-7000 500-watt Automatic, Solid-State Linear Amplifier. TCXO-747 Temperature-Compensated Crystal Oscillator, FAS-1-4R Remote Antenna Selector. FRB-757 Amplifier Relay Box. FP-700 Standard Power Supply. FP-757HD Heavy-Duty Power Supply. MMB-38 Mobile Mounting Bracket.

Discover the price/performance leader. Check out Yaesu's low-cost FT-747GX at your Yaesu dealer today. Because now, Yaesu puts priceless DX into your price range.

Yaesu USA 17210 Edwards Road, Cerritos, CA 90701 (213) 404-2700. Repair Service: (213) 404-4884. Parts: (213) 404-4847. Prices and specifications subject to change without notice.

MESU

CIRCLE 165 ON READER SERVICE CARD

## Fill your logbook. Without emptying your pocketbook.



# KENWOOD

... pacesetter in Amateur Radio





## TH-25AT/45AT

## New Pocket Portable Transceivers

The all-new TH-25 Series of pocket transceivers is here! Wide-band frequency cov erage, LCD display, 5 watt option, plus...

- Frequency coverage: TH-25AT: 141-163
   MHz (Rx); 144-148 MHz (Tx). (Modifiable for MARS/CAP. Permits required.)
  - TH-45AT: 438-450 MHz.
- Automatic Power Control (APC) circuit for reliable RF output and final protection.
- 14 memories; two for any "odd split" (5 kHz steps).
- Automatic offset selection (TH-25AT).
- 5 Watts from 12 VDC or PB-8 battery pack.
- Large multi-function LCD display.
- Rotary dial selects memory, frequency, CTCSS and scan direction.
- T-ALERT for quiet monitoring. Tone Alert beeps when squelch is opened.
- Band scan and memory scan.
- Automatic "power off" circuit.
- Water resistant.
- CTCSS encoder / decoder optional (TSU-6).
- Supplied accessories: StubbyDuk, PB-6 battery pack for 2.5 watts output, wall charger belt hook, wrist strap, water resistant dust cap



### Optional accessories:

PB-5 72 V, 200 mAh NiCd pack for 2.5 W output PB-6
7.2 V, 600 mAh NiCd pack PB-7 7.2 V, 1100 mAh NiCd pack
PB-8 12 V, 600 mAh NiCd for 5 W output PB-9 7.2 V, 600 mAh NiCd with built-in charger BC-10 Compact charger
BC-11 Rapid charger BT-6 AAA battery case CC-1/PG-2V DC adapter HMC-2 Headset with VOX and PTT SC-14, 15, 16 Soft cases SMC-30/31 Speaker mics. TSU-6 CTCSS decode unit WR-1 Water resistant bag

## KENWOOD

KENWOOD U.S.A. CORPORATION 2201E. Dominguez St., Long Beach, CA 90810 P.O. Box 22745, Long Beach, CA 90801-5745

Complete service manuals are available for all Kenwood transceivers and most accessories. Specifications, features, and prices are subject to change without notice or obligation.