







focus on communications technology

in this issue: stacking Yagis properly • 0.5-30 MHz active antenna • vary your take-off angle • switchable vertical wire array • alternative method of feeding phased arrays • multiband sloping vee beam • 160-meter transmission line antenna • RF transmission cable for microwave applications • baluns • convert your fixed tower to a tilt-over • plus W1JR, W6SAI, K0RYW, and the Guerri report

#### **ICOM UHF Transceiver**



## For Maximum UHF Base Station Performance

Whether your interest is simplex, repeater operation, or satellite work, the IC-471H 430-450MHz base station transceiver will give you maximum UHF operation.

75 Watts. The IC-471H provides 10 to 75 watts of adjustable power in all modes. This enables adjusting the drive level to a linear amplifier for higher power uses such as moonbounce. For a portable UHF station, the optional IC-PS35 internal power supply is available.

IC-471H With IC-PS35 Internal Power Supply Installed Compare these exceptional Standard Features:

- 430 450MHz
- Variable tuning steps, FM 5KHz and 1 KHz; SSB 10Hz, 50Hz and 1KHz
- 32 full-function Memories
- with lithium battery backup 75 Watts, fully adjustable
- on all modes 32 built-in Subaudible Tones
- High visibility display
- Scanning systems...
- Memories, Modes or Programmable Band RIT/XIT with separate
- readout
- S-Meter and Center Meter
   IC-HM12 Microphone with
   Up/Down Scan
- 11¼"W x 4%"H x 12%"D

Optional Features. AG-35 switchable mast-mounted GaAsFET preamp, UT-15S

C-471H

CTCSS encoder/ decoder (encoder is standard), IC-EX310

voice AG-35 Mast Mounted synthesizer, GaAsFET Preamplifier IC-SM8

two-cable desk mic and IC-SM6 desk mic. PLUS a variety of power supplies...the IC-PS35 internal power supply, the IC-PS30 system power supply or the IC-PS15 external power supply.

The IC-471A. The 25 watt IC-471A is also available and has the same outstanding features as the IC-471H, plus ar optional IC-PS25 internal power supply for portable operation.

To complete your VHF/UHI base station, the IC-471's 2-meter companions, the IOC watt IC-271H and the 25 wat IC-271A are also available.



See the IC-471H and othe ICOM equipment at your loca authorized ICOM dealer.

# **ICOM**

#### First in Communications

ICOM America, Inc., 2380-116th Ave NE, Bellevue, WA 98004 / 3331 Towerwood Drive, Suite 307, Dallas, TX 75234 All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. 471H108

#### What To Look For In A Phone Patch

The best way to decide what patch is right for you is to first decide what a patch should do. A patch should:

- Give complete control to the mobile, allowing full break in operation.
- Not interfere with the normal operation of your base station. It should not require you to connect and disconnect cables (or flip switches!) every time you wish to use your radio as a normal base station.
- Not depend on volume or squelch settings of your radio. It should work the same regardless of what you do with these controls.
- You should be able to hear your base station speaker with the patch installed. Remember, you have a base station because there are mobiles.
   ONE OF THEM MIGHT NEED HELP.
- The patch should have standard features at no extra cost. These should include programmable toll restrict (dip switches), tone or rotary dialing, programmable patch and activity timers, and front panel indicators of channel and patch status.

ONLY SMART PATCH HAS ALL OF THE ABOVE.

#### Now Mobile Operators Can Enjoy An Affordable Personal Phone Patch...


- Without an expensive repeater.
- Using any FM tranceiver as a base station.
- The secret is a SIMPLEX autopatch, The SMART PATCH.

#### SMART PATCH Is Easy To Install

To install SMART PATCH, connect the multicolored computer style ribbon cable to mic audio, receiver discriminator, PTT, and power. A modular phone cord is provided for connection to your phone system, Sound simple? .... IT IS!

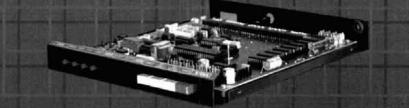
## With SMART PATCH You are in CONTROL

With CES 510SA Simplex Autopatch, there's no waiting for VOX circuits to drop. Simply key your transmitter to take control.



SMART PATCH is all you need to turn your base station into a personal autopatch. SMART PATCH uses the only operating system that gives the mobile complete control. Full break-in capability allows the mobile user to actually interrupt the telephone party. SMART PATCH does not interfere with the normal use of your base station. SMART PATCH works well with any FM transceiver and provides switch selectable tone or rotary dialing, toll restrict, programmable control codes, CW ID and much more.
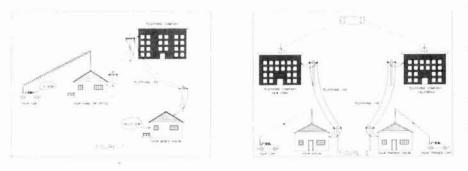
#### To Take CONTROL with Smart Patch – Call 800-327-9956 Ext. 101 today.





Communications Electronics Specialties, Inc. P.O. Box 2930, Winter Park, Florida 32790 Telephone: (305) 645-0474 Or call toll-free (800)327-9956

#### How To Use SMART PATCH

Placing a call is simple. Send your access code from your mobile (example: \*73). This brings up the Patch and you will hear dial tone transmitted from your base station. Since SMART PATCH is checking about once per second to see if you want to dial, all you have to do is key your transmitter, then dial the phone number. You will now hear the phone ring and someone answer. Since the enhanced control system of SMART PATCH is constantly checking to see if you wish to talk, you need to simply key your transmitter and then talk. That's right, you simply key your transmitter to interrupt the phone line. The base station automatically stops transmitting after you key your mic. SMART PATCH does not require any special tone equipment to control your base station. It samples very high frequency noise present at your receivers discriminator to determine if a mobile is present. No words or syllables are ever lost.

#### SMART PATCH Is All You Need To Automatically Patch Your Base Station To Your Phone Line.

Use SMART PATCH for:

- Mobile (or remote base) to phone line via Simplex base. (see fig 1.)
- Mobile to Mobile via interconnected base stations for extended range. (see fig. 2.)
- Telephone line to mobile (or remote base).
- SMART PATCH uses SIMPLEX BASE STA-TION EQUIPMENT. Use your ordinary base station. SMART PATCH does this without interfering with the normal use of your radio.

#### WARRANTY?

YES, 180 days of warranty protection. You simply can't go wrong. An FCC type accepted coupler is available for SMART PATCH.

## KENWOOD

... pacesetter in Amateur radio

## **The Smallest HT!** H-21AT/31AT/41AT

Kenwood's advanced technology brings you a new standard in pocket/handheld transceivers!

- . High or low power. Choose 1 watt highenough to "hit" most local repeaters; or a batterysaving 150 mW low.
- Pocket portability! Kenwood's TH-series HTs pack convenient, reliable performance in a package so small, it slips into your shirt pocket! It measures only 57 (2.24) W x 120 (4.72) H x 28 (1.1) D mm (inch) and weighs 260 g (.57 lb) with batteries!
- Expanded frequency coverage (TH-21AT/A). Covers 141.000-150.995 MHz in 5 kHz steps. includes certain MARS and CAP frequencies. TH-31AT/A: 220.000-224.995 MHz in 5 kHz steps. TH-41AT/A: 440.000-449.995 MHz in 5 kHz steps.





- Repeater offset switch. TH-21AT/A: ±600 kHz. simplex
- TH-31AT/A: -1.6 MHz. reverse, simplex TH-41AT/A: ±5 MHz.
- simplex.
- Standard accessories: Rubber flex antenna, earphone, wall charger. 180 mAH NiCd battery pack, wrist strap.
- Quick change, locking battery case.
- The rechargeable battery case snaps securely into place. Optional battery cases and adapters are available.
- Rugged, high impact molded case. The high impact case is scuff resistant, to retain its attractive styling, even with hard use.

See your authorized Kenwood dealer and take home a pocketful of performance today!

So KNEU

\* Easy-to-operate, functional design. Three digit thumbwheel frequency selection and handy top-mounted controls increase operating ease.

Note: Specifications guaranteed for the 144 000-148 000 MHz Amateur band only TH-21AT shown. Standard versions TH-21A/31A/41A without DTMF pad also available Specifications and prices are subject to change without notice or obligation

A C (H) TH-21AT

Optional accessories:

- HMC-1 headset with VOX
- SMC-30 speaker microphone
- PB-21 NiCd 180 mAH battery
- DC-21 DC-DC converter for mobile use
- BT-2 manganese/alkaline battery case • EB-2 external C manganese/alkaline
- battery case
- SC-8 soft case for TH-21A/31A/41A
- SC-8T soft case for TH-21AT/31AT/41AT
- TU-6 programmable sub-tone unit
- AJ-3 thread loc to BNC female adapter Service manual

More information on the TH-series HTs is available from authorized Kenwood dealers.



TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220



## MAY 1985

#### volume 18, number 5

T. H. Tenney, Jr., W1NLB publisher

> Rich Rosen, K2RR editor-in-chief and associate publisher

Dorothy Rosa, KA1LBO assistant editor

> Joseph J. Schroeder, W9JUV Alfred Wilson, W6NIF associate editors Susan Shorrock editorial production

#### editorial review board

Peter Bertini, K1ZJH Forrest Gehrke, K2BT Michael Gruchalla, P.E. Bob Lewis, W2EBS Mason Logan, K4MT Ed Wetherhold, W3NQN

publishing staff J. Craig Clark, Jr., N1ACH assistant publisher Rally Dennis, KA1JWF director of advertising sales

> Dorothy Sargent, KA12K advertising production manager Susan Shorrock circulation manager Therese Bourgault circulation

ham radio magazine is published monthly by Communications Technology, Inc Greenville, New Hampshire 03048-0498 Telephone: 603-878-1441

#### subscription rates

United States: one year, \$19.95; two years, \$32.95; three years, \$44.95 Canada and other countries (va surface mail) one year, \$22.95; two years, \$41.00; three years, \$58.00 Europe, Japan, Africa (via Air Forwarding Service): one year, \$28.00 All subscription orders payable in U.S. funds, via international postal money order or check drawn on U.S. bank

#### international subscription agents: page 140

Microfilm copies are available from University Microfilms, International Ann Arbor, Michigán 48106 Order publication number 3076

Cassette tapes of selected articles from ham radio are available to the blind and physically handicapped from Recorded Periodicals, 919 Walnut Street, Philadelphia, Pennsylvania 19107

Copyright 1985 by Communications Technology, Inc. Title registered at U.S. Patent Office

> Second class postage paid at Greenville, New Hampshire 03048 0498 and at additional mailing offices ISSN 0148 5989

Send change of address to *ham radio* Greenville, New Hampshire 03048-0498

## ham radio magazine

## contents

- 18 stacking Yagis is a science Steve Powlishen, K1FO
- 37 active antenna covers 0.5-30 MHz Peter Bertini, K1ZJH
- 46 control your take-off angle: the JR vari-lobe antenna R.R. Schellenbach, W1JF
- 53 the end-fed 8JK: a switchable vertical array R.R. Schellenbach, W1JF
- 58 feeding phased arrays: an alternative method Al Christman, KB8I
- 66 ham radio techniques Bill Orr, W6SAI
- 71 a sloping terminated vee beam Robert Ross
- 87 160-meter transmission line antenna Ted S. Rappaport, N9NB
- 95 VHF/UHF world: stacking antennas, part 2 Joe Reisert, W1JR
- 106 RF transmission cable for microwave applications Howard Weinstein, K3HW
- 113 balun chop suey John J. Nagle, K4KJ
- 125 tilt-over conversion of a fixed antenna tower Dick Rollema, PAØSE
- 165 the Guerri report Ernie Guerri, W6MGI

166 advertisers index and reader service
79 DX forecaster


140 flea market

144 ham mart

- e 11 presstop
- 4 reflections
- 121 short circuits

157 new products

May 1985 🜆 3

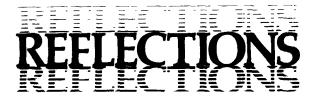

#### the readers speak . . .

We asked — and you answered our call for solutions to the problems facing our hobby today (see "Reflections," February, 1985, page 5. Each and every one of your letters was read, and we're proud to act as a clearinghouse for your many ideas and suggestions.

Foremost you recognized that Amateur Radio has changed, and that hams have to accept that fact before any effective improvements can be made.

Here are some of your comments on the problems, followed by some suggested solutions:

"The challenge is gone. Want to hear China? Just turn on the TV."

"Equipment is just too expensive and complex for us to do our own repairs."

"Our kids are into computers, not radio."

"Hams are boring and don't know how to communicate any more."

"Consumer electronics and RFI - what a nightmare!"

"Enforcement, what a joke - the FCC's a paper tiger."

Can we expect the general public to help? I doubt it. Many of them see us as "the ham down the block with the ugly tower and wires all over." Don't expect too much sympathy from the neighbors — especially if their brand-new VCR is carrying our conversations as well as their programming. So what do we do?

**SCHOOLS.** Talk to your local school board. Could some space and time — say an hour a week — be set aside for a Novice course taught by local hams? What about high school science teachers? Would they be interested in having guest speakers address classes on Amateur Radio subjects? Radio clubs, how about sponsoring radio-related science fairs, with prizes or scholarships awarded for the best projects? How about donating software — morse code tutors and technical Q&A's, for example — to school libraries? Besides the school environment, summer camps and community centers would also be logical places for reaching and teaching prospective hams.

**PUBLICITY.** We need more of it — the good kind, that is. Make a personal effort to contact and provide details of Amateur Radio events to your local newspaper and radio or TV stations. Every little bit helps. There's a move afoot to produce and distribute a brochure describing the "fun" aspects of our hobby. When it becomes available, get some and hand them out to the neighborhood kids. Do any of you work in the media or public relations? How about using your skills to help improve our image?

**PARTICIPATION.** This means all of us. No contribution is too small. Participate by helping out at the club, helping newcomers to the hobby even *after* they're licensed. (This in itself might help reverse the "dropout" rate.) How about being an Elmer and forming a "ground wave net" to bring together new hams in a local net designed to help them overcome their initial shyness? I'm sure we can all remember how we felt during those first few weeks on the air.

Dear Senior Citizens, you have the time, the knowledge, and the political clout. Your active leadership and participation are essential.

What would happen if, for the good of Amateur Radio, we set aside our individual concerns and pooled our talents in a single "umbrella" organization dedicated solely to protecting and preserving our hobby? Perhaps then it would be more difficult for commercial interests to nibble away at our spectrum. We have to lobby from a position of unity and strength.

**PERSONAL GROWTH**. Hams used to be interesting people to talk to. We could converse on diversified subjects at length. Now too many of us appear to be overly involved in contesting and card-collecting - i.e., doing the same old thing all the time, when we should be advancing our knowledge, experimenting with different modes, and searching for new frontiers.

Perhaps we can act on some of the advice offered by our readers and help improve the hobby.

Rich Rosen, K2RR Editor-in-Chief


# FACESSOR

#### 300 WATT ANTENNA TUNER HAS SWR/WATTMETER, ANTENNA SWITCH, MATCHES VIRTUALLY EVERYTHING FROM 1.8 TO 30 MHz.



\$99.95 MFJ-941D

## RTTY/ASCII/CW COMPUTER INTERFACE

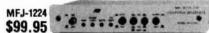

Free MFJ RTTY/ASCII/CW software on tape and cable for VIC-20 or C-64. Send and receive computerized RTTY/ASCII/CW with nearly any personal computer (VIC-20, Apple, TRS-80C, Atari, TI-99, Commodore 64, etc.). Use Kantronics or most other RTTY/CW software. Copies both mark and space, any shift (including 170, 425, 850 Hz) and any speed (5-100 WPM RTTY/CW, 300 baud ASCII). Sharp 8 pole active filter for CW and 170 Hz shift. Sends 170, 850 Hz shift. Normal/reverse switch eliminates retuning. Automatic noise limiter. Kantronics compatible socket plus exclusive general purpose socket, 8x11/4x6 in, 12-15 VDC or 110 VAC with adapter, MFJ-1312, \$9.95.

## RX NOISE Bridge

#### Maximize your antenna

performance!

\$59.95 MFJ-202B Tells whether to shorten or lengthen antenna for minimum SWR. Measure resonant frequency, radiation resistance and reactance.

New Features: individually calibrated resistance scale, expanded capacitance range (±150 pf). Built-in range extender for measurements be yond scale readings. 1-100 MHz. Comprehensive manual. Use 9 V battery. 2x4x4 in.

INDOOR TUNED ACTIVE NEW! IMPROVED! ANTENNA

with higher gain "World Grabber" rivals

of outside long wires! Unique tuned Active Antenna minimizes intermode, improves selectivity, reduces noise outside tuned band, even functions as preselector with external antennas.

Covers 0.3-30 MHz. Tele scoping antenna. Tune, Band, Gain, On-off bypass controls. 6x2x6 in. Uses 9V battery, 9-18 VDC or 110 VAC with



adapter, MFJ-1312, \$9.95. MFJ-1020A \$79.95

ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO OBLIGATION. IF NOT DELIGHTED, RETURN WITH-IN 30 DAYS FOR PROMPT REFUND (LESS SHIPPING). One year unconditional guarantee
 Made in USA. · Add \$4.00 each shipping/handling · Call or write for free catalog, over 100 products.

NEW FEATURES

#### POLICE/FIRE/WEATHER 2 M HANDHELD CONVERTER \$39.95

Turn your synthesized scanning 2 meter handheld into a hot Police/ MFJ Fire/Weather band scanner! a. 144-148 MHz handhelds MFJ VHF receive Police/Fire on 154-

158 MHz with direct frequency readout. Hear NOAA maritime coastal plus more on 160-164 MHz. Converter mounts between handheld and rubber ducky. Feedthru allows simultaneous scanning of both 2 meters and Police/Fire bands. No

missed calls. Crystal controlled. Bypass/Off switch allows transmitting (up to 5 watts). Use AAA battery, 21/4x11/2x11/2 in. BNC connectors.

#### MFJ/BENCHER KEYER COMBO

**MFJ-422** \$109.95 The best of all CW worlds-



-313

112

a deluxe MFJ Keyer in a compact configuration that fits right on the Bencher iambic paddle! MFJ Keyer - small in size, big in features. Curtis 8044-B IC, adjustable weight and tone, front panel volume and speed controls (8-50 WPM). Builtin dot-dash memories. Speaker, sidetone, and push button selection of semi-automatic/tune or automatic modes. Solid state keying. Bencher paddle is fully adjustable; heavy steel base with non-skid feet. Uses 9 V battery or 110 VAC with

#### VHF SWR/WATTMETER MFJ-812 \$29.95

Low cost VHF SWR/ Wattmeter!

Read SWR (14 to 170 MHz) and forward/



reflected power at 2 meters. Has 30 and 300 watts scales. Also read relative field strength. 4x2x3 in.



MFJ ENTERPRISES, INC. Box 494, Mississippi State, MS 39762

#### MFJ's fastest selling tuner packs in plenty of new features!

· New Styling! Brushed aluminum front. All metal cabinet. · New SWR/Wattmeter! More accurate. Switch selectable

300/30 watt ranges. Read forward/reflected power

· New Antenna Switch! Front panel mounted Select 2 coax lines, direct or through tuner, random wire/balanced line or tuner bypass for dummy load.

· New airwound inductor! Larger more efficient 12 position airwound inductor gives lower losses and more watts out. Run up to 300 watts RF power output. Matches everything from 1.8 to 30 MHz; dipoles, inverted vee, random wires, verticals, mobile whips, beams, balanced and coax lines. Built-in 4:1 balun for balanced lines. 1000V capacitor spacing. Black. 11x3x7 inches. Works with all solid state or tube rigs. Easy to use, anywhere.

#### **1 KW DUMMY LOAD**

Tune up fast, extend life of finals, reduce **QRM!** Rated 1KW CW or 2KW PEP for 10 minutes. Half rating for 20 minutes, continuous at 200 W CW, 400 W PEP VSWR under 1.2 to 30 MHz, 1.5 to 300 MHz. Oil contains no PCB.



BALUN.

50 ohm non-inductive resistor. Safety vent. Carrying handle, 71/2x63/4 in.

24/12 HOUR CLOCK/ ID TIMER

\$19.95 NEW Switch to 24 hour UTC or 12 hour format! Battery backup

MFJ-106



maintains time during power outage. ID timer alerts every 9 minutes after reset. Red LED .6 inch digits. Synchronizable with WWV. Alarm with snooze function. Minute set, hour set switches. Time set switch prevents mis-setting. Power out, alarm on indicators. Gray and black cabinet. 5x2x 3 inches, 110 VAC, 60 Hz.

#### DUAL TUNABLE SSB/CW/RTTY FILTER MFJ-752B \$99.95



Dual filters give unmatched performance! The primary filter lets you peak, notch 0W pass or high pass with extra steep skirts Auxiliary filter gives 70 db notch 40 Hz beak Both filters tune from 300 to 3000 Hz with variable bandwidth from 40 Hz to nearly " at Constant output as bandwidth is varied linear frequency control. Switchable hoise imiter for Inequency control, switchable horse imiter for impulse noise. Simulated stered sound for CW lets ears and mind reject 0814, inputs for 2 rigs Plugs into phone jack. Two watts for speaker Off bypasses filter: 9-18 VDC or fro VAC with optional adapter. MFU-1312, \$9.95



## optional adapter, MFJ-1305, \$9.95.



6 May 1985





## THE ULTIMATE CONTACT . . . MAKE IT WITH ROBOT COLOR SSTV



ROBOT RESEARCH, INC. 7591 Convoy Court San Diego, California 92111 Phone (619) 279-9430 Step aboard the Shuttle from your shack with the world's most advanced slow scan video system! **YES!** Tell me about how I can participate in SSTV aboard the Space Shuttle.

CALL

ZIP

ADDRESS CITY/STATE

NAME

- 108

# <section-header><section-header>

- State-of-the-art circuitry
- . LED to indicate dish movement
- · Available in 18" or 24" ball actuators
- · Modern, attractively styled control box
- · Dial control always showing dish location
- · Dial channels same as in program listings.

Your wisest choice in automatic dish positioners. To learn more about the finest in low cost, high performance dish positioners, contact...

ELECTRO-SCAN 85

ELECTRO-COM DIST. SALES 8459 North Main Street • Suite 112 • Dayton, Ohio 45415 • Phone (513) 454-0232

More Details? CHECK-OFF Page 166



# 

THE 2-METER CHANNEL SPACING ISSUE MAY RESULT IN A CONFRONTATION that could leave Amateur Radio with some bad long-term wounds. Repeater operators from the mid-Atlantic and New England states met March 2 to strongly endorse 15 kHz spacing not only for 146-148 MHz, but even possibly for 144.5-145.5 MHz as well, thus picking up another six channels. In a similar action southern California's 2-Meter Area Spectrum Management Association met March 23 to also endorse 15 kHz spacing across the whole band, despite serious interest in northern California in shifting to 20 kHz as their neighbors in Oregon and Washington have done. By their action the southern California group's decision puts them in direct conflict with Mexican Amateurs, whose government has mandated 20 kHz on the 2-meter band. It's believed that Mexican representatives who attended that meeting may even ask their government to lodge a formal objection with the U.S. State Department.

formal objection with the U.S. State Department. 20 kHz Proponents Seem Equally Determined In Their Choice, with Texas the latest in a number of western states to endorse the change. Michigan was the first state east of the Mississippi to adopt 20 kHz, and it's under heavy pressure to reconsider. Alabama is reported to have voted to implement 20 kHz by July 1, but Missouri opted to stay at 15 kHz at a February meeting. Midwestern repeater representatives plan to meet at Dayton for further discussions.

have voted to implement 20 kHz by July 1, but Missouri opted to stay at 15 kHz at a February meeting. Midwestern repeater representatives plan to meet at Dayton for further discussions. <u>Despite The FCC's Strong Desire For A National Coordinator</u>, formalized in PR Docket 85-22, the escalating 15 vs 20 kHz conflict seems to offer little hope for simple or early resolution of the increasing number of repeater conflicts that led to that NPRM. Indeed, the FCC may even be asked to endorse 15 kHz through a Petition for Rule Making. Such a move was considered by the East Coast group at its recent meeting in support of 15 kHz. However, it is hard to see how such a petition would find any support at all within the Commission, which is trying very hard to get away from regulating details of Amateur operations. Furthermore, in this case such an FCC mandate would put it in direct conflict with the Mexican government and thus risk diplomatic repercussions.

AMATEUR RADIO PROBABLY WON'T FLY ON THIS SUMMER'S SPACE SHUTTLE, according to late word from NASA. The official reason is problems of integrating the exotic Amateur equipment that Tony England, WØORE, was to use on Flight 51F with shuttle equipment. Though strong lastditch efforts are being made to salvage the Amateur operation, at presstime it looks very much like there won't be an Amateur operating from space this year.

AMATEUR RADIO VS CABLE TV IS YET ANOTHER CONFRONTATION that seems to be escalating. In late February the FCC proposed in Mass Media Docket 85-38 that cable TV radiation limits be relaxed by another 8 dB, to 50 microvolts per meter, and that various other restrictions including the requirement for annual system inspections be dropped. In view of the number of Amateurs who've had problems with cable leakage interfering with their 144 or 220 MHz operations, this proposal presents a real threat to Amateur Radio. Comments were due in late March Amateurs have a strong ally against the proposal in the broadcast industry

Late March. Amateurs have a strong ally against the proposal in the broadcast industry. <u>Amateurs Have Been Shut Down Due To Cable Interference</u> in two recent unrelated cases. In the first, WB20TK/4 was ordered off the air by the Engineer-In-Charge of the FCC Atlanta Field Office for interference with the Greenville, S.C., cable system. FCC Amateur rule 97.73(d) on interference to other stations was cited, despite checks that showed the cable system was so badly maintained that a 150 mW hand-held's signal caused problems for viewers. The FCC inspected WB20TK's station but did not even contact the cable operator in an apparent violation of the FCC's own rules requiring a cable system to take responsibility for resolving interference problems. In the other case, WB4NMA was shut down, again by the Atlanta Field Office, for interfering with cable viewers in Gainesville, Georgia.

Atlanta Field Office, for interfering with cable viewers in Gainesville, Georgia. <u>2-Meter Privileges Were Restored To Both Operators</u> following the intervention of the ARRL through its General Counsel Chris Imlay, N3AKD. However, the Commission's proposed cable rules relaxation combined with the kind of FCC Field Office attitude that led to these two cases could spell serious trouble for future Amateur Radio VHF/UHF operation.

BASH EDUCATIONAL SERVICES IS OUT OF BUSINESS. Writing to subscribers to his FCC Rules Part 97 update service, Dick Bash, KL7IHP, stated that his FCC exam study materials business had subsidized the rules updating service but, under the volunteer exam program, there was no longer a unique niche in training for him to fill. Bash was very controversial for his publishing of word-for-word correct answers to all FCC-administered Amateur exams.

A SUGGESTION THAT ARRL ASSUME CALLSIGN ASSIGNMENT RESPONSIBILITY is receiving some interest in Washington, as the FCC looks at tighter budgets. It's likely, however, that callsign responsibility would be delegated only as part of a total program that would include the entire licensing function now done by FCC's Gettysburg facility.

THE ANTENNAS VS LOCAL RESTRICTIONS ISSUE seems to be heading toward an FCC Notice of Proposed Rule Making, which will probably consider it from the private satellite dish view-point. Just what this means for PRB-1 and Amateur Radio remains to be seen.

<u>NEW WARC BAND AVAILABILITY HAS BEEN DELAYED</u> by at least three months. An extension of the Reply Comment period, requested by the Personal Radio Steering Group, bumped expected action on the 10, 24, and 902 MHz bands off the FCC's first quarter agenda. The PRSG is believed to be pushing for allocation of part of 902-928 MHz to a Personal Radio Service.

A NATIONAL VEC NET IS OPERATING on 20 meters Sundays, starting at 1700Z. The 40-meter midwestern VEC net has moved to 1800Z, still on 7280 kHz. DeVry is now officially a national VEC.



## Nothing matches the MACC in voltage surge protection and component-by-component on-off control

- compact, attractive desk-top console
- eight clean AC power outlets
- individual and master on-off control
- superior three-stage auto-restore circuit with manual reset circuit breaker
- individually lighted rocker switches

Lightning striking miles away, electric motors running on the same power line, fluorescent lighting and even wind-driven snow static buildup can cause problems with delicate circuits and miniature electronic chips. But the MACC, within nanoseconds, can recognize the current disturbance, then clip it off and dissipate it, while maintaining clean current flow to your system's equipment. The MACC protects all semi-conductor, solid-state circuitry.

The MACC is designed with three 2000-amp surge discharge protection circuits — one between each of the AC input's hot, neutral and ground lines. Other surge devices may use a single 100-amp surge protector between the hot and neutral lines only. Its resettable circuit breaker adds further protection. MACC gives you control convenience, too. It provides 8 plug-in "U" ground outlets for your components — including one "hot" outlet for a continuously powered application such as your clock. Seven "on/off" rocker switches let you control individual components. And you can turn your entire system on or off with a single master rocker switch.

#### ALPHA DELTA'S MASTER AC CONTROL CONSOLE PROTECTS AGAINST ALL THESE DAMAGING SURGE PROBLEMS

Problems caused in circuitry by surging and transient voltages:

- Melting of "hot spots" within
- semi-conductor devicesThermal runaway of transistors
- Welding, pitting and metal
- transfer on switch contactsSwitch contact corrosion
- Insulation breakdown causing
- arcing of components
  Shortening of component life

The MACC is tested to IEEE pulse standards and rated at 15A, 125V-AC, 60 Hz, 1875 watts continuous duty total for the console. A label on the unit describes the surge protection limitations.

#### MACC Specs


Alpha Delta Master AC Control Console Amperage 15 Volt (AC) 125 Hertz 60 Total Wattage 1875 Size MACC 11" x 2-3/4" x 2-3/4" MACC-4 5-1/2" x 2-3/4" x 2-3/4" Shipping Weight 4-1/2 lbs. approximately

Alpha Delta Model MACC Systems are designed to reduce the hazards of lightning-induced surges. These devices, however, will not prevent fire or damage caused by a direct stroke to an AC line or a structure. Specifications, availability and price are subject to change without notice.


Warranted against defects in materials or workmanship.



current solutions to current problems

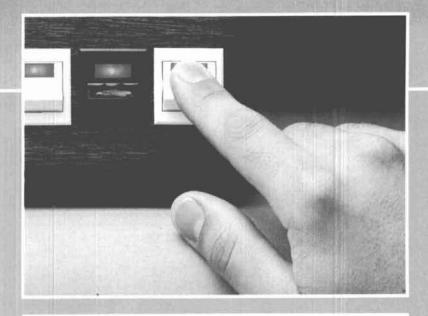

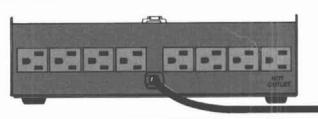The MACC is unique in voltage surge/transient suppression and convenient, desk-top individual component control. Nothing matches the MACC in value and performance. Put one on duty on your AC line.



MACC only \$79.95 MACC-4 only \$59.95



MASTER

ALPHA D

At your Alpha Delta dealer. Or in U.S., order direct, adding \$4 for postage/handling to check or money order. (Approx. shipping wt.; 4-1/2 lbs. each) MasterCard and VISA accepted. Ohio residents add Sales Tax. Sorry no C.O.D.'s Circuit Breaker (automatic pop-up)

The MACC-4 is a four clean-line output version of the MACC with all the same features. It gives you a cost- and spacesaving solution for your application, without sacrificing performance. Rated a full 1875 total wattage. Includes master rocker switch, three independently switchable lines, one "hot" line and resettable circuit breaker.

(UL

LISTED

#### Associated Banner BK PRECISIO RA CTRONICS, INC.

New and Used Electronic Test Equipment Sales . Service . Rental . Leasing

Polaroid DS-34

Now you can get an instant picture in black & white or color from any oscilloscope screen. Includes CRT hood. \*Large hoods also available to fit computer terminals and CAD/ CAM screens.

\$369.00



#### \$198.00 **MODEL 1301**

#### Fully regulated triple output

- Fixed 5VDC, 1A V1 + 5 VDC to 18 VDC .5A V2 5 VDC to 18 VDC .5A .
- Fully automatic current limiting .




MODEL 3002A/0-30 VDC/0-2A



TRIPLE OUTPUT

POWER SUPPLY

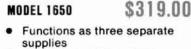

- Exclusive tracking circuit
- Fixed output 5 VDC, 5A
- Two 0 to 25 VDC outputs at 0.5A
- Fully automatic, current-limited
- overload protection + and - terminals of each output
- are fully isolated, in all modes All three outputs may be connected in series or parallel for
- higher voltage or current
- PROBE **Oscilloscope Probes** MASTER

ATTENUATION	BAND WIDTH (MHZ)	PRICE
10X	100	\$35.00
10X/1X	100/5	\$39.00
10X	250	\$59.00
10X	60	\$30.00
	10X 10X/1X 10X	10X 100 10X/1X 100/5 10X 250



(0)

БШТ

(0)

111

HSm



KEITHLEY

\$139.00
ADD FOR SHIPPING AND INSURANCE
\$0 to \$250.00 \$4.50
\$251.00 to \$600.00 \$6.50
\$501.00 to \$750.00 \$8.50
\$751.00 to \$1000\$12.50

RAG ELECTRONICS, INC. / 21418 Parthenia Street / Canoga Park, CA 91304 / 1-818-998-6500

WATEL


- Audio Sine/Square Wave Generator Distortion from <0.03% 10 Hz to 1 MHz \$259.00 LAG-120B BK PRECISION mann FUNCTION GENERATOR \$189.00 **MODEL 3010** Sine, square and triangle output Variable and fixed TTL outputs 0.1 Hz to 1 MHz in six ranges Typical distortion under 0.5% from 1 Hz to 100 KHz Variable DC offset VCO input for sweep tests VIZ MULTI-FUNCTION COUNTER MODEL WD-755 \$259.00 5 Hz to 125 MHz 8 Digit LED Display ٠ Period Measurement 5 Hz to 2 MHz Totalizes to 99,999,999 Plus Overflow Frequency Ratio Mode **Time Interval Mode** Switchable Attenuator & Low Pass Filter SIALD VARIABLE TRANSFORMER \$145.00 MODEL 3PN1010V RAG CARRIES THE COMPLETE STACO VARIABLE TRANSFORMER LINE CALL US WITH YOUR REQUIREMENTS. DIGITAL CAPACITANCE METER ٠ Battery operated .
  - 3½ digit LCD display Range 1 PF to 2,000 UF 0.2% basic accuracy GLOBAL **MODEL 3000** A100.00

LEADER INER

# SCOPE SPECTACULAR

#### PORTABLE OSCILLOSCOPES HITACHI Hitachi Denshi, Ltd

ELUK

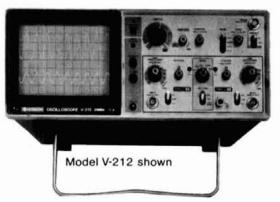


\$461.00 MODEL V-212 DC to 20 MHz, 1 mV/div, Dual Trace Features 6" Rectangular CRT Full 2 year parts and labor warranty (w/two X10 probes).

\$536.00 MODEL V-222 DC to 20 MHz, 1 mV/div, Dual Trace, D.C. offset for DMM Output, Verticle Mode Trigger 6" CRT (w/two X1/X10 probes).

\$694.00 MODEL V-422 DC to 40 MHz, other features same as V-222 (w/two X1/X10 probes)

\$535.00

Polaroid

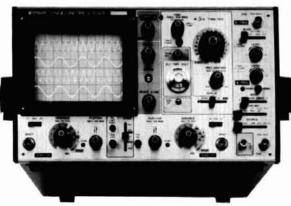

GLOBAL SPECIALTIES

HAMEE

Model V-1050F shown

#### MODEL V-1050F

\$1276.00

DC to 100 MHz, .5 mV/div, Quad Trace, Delayed Sweep, Full T.V. Triggering, alternate time base (w/two X10 probes)

#### **MODEL V-650**

#### \$956.00

DC to 60 MHz, 1 mV/div, tripple trace, delayed sweep, Full T.V. Triggering, variable trigger hold-off (w/two X10 probes)

#### PORTABLE OSCILLOSCOPES WATEL




**MODEL SS-5702** 

PROBE

DC-20MHz, 5 mV/div **Dual trace** 


6 inch rectangular internal graticule CRT.

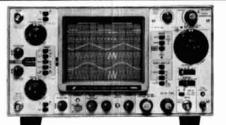Includes 2 each X1/X10 probes and full factory warranty; 2 years on parts, labor and CRT.



\$899.00 MODEL SS-5705 DC to 40MHz Vertical and horizontal deflection accurate within ±2%. CRT acceleration voltage 12KV. 3 channels, 6 traces. High precision calibrator (±1%). Fastest sweep rate: 10 ns.

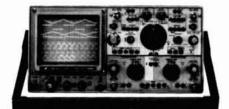- High sensitivity 1 mv/div
- . CH1 signal output
- Beam finder
- **Delayed** sweep
- Alternate time base
- 2 ea. X1/X10 Probes .



\$1695.00 **MODEL 5711** DC to 100MHz (typically over 120 MHz), 5 mV/div, True 4 channel input, eight trace, Delayed sweep, alternate time base, CRT acceleration voltage 20 KV, (w/saddle bag, front cover, 2 ea. X10 probes).


\$2495.00 **MODEL 5711D** '5711 with counter and DMM).

17/ 調園

Shimpo

112

PRIMELINE

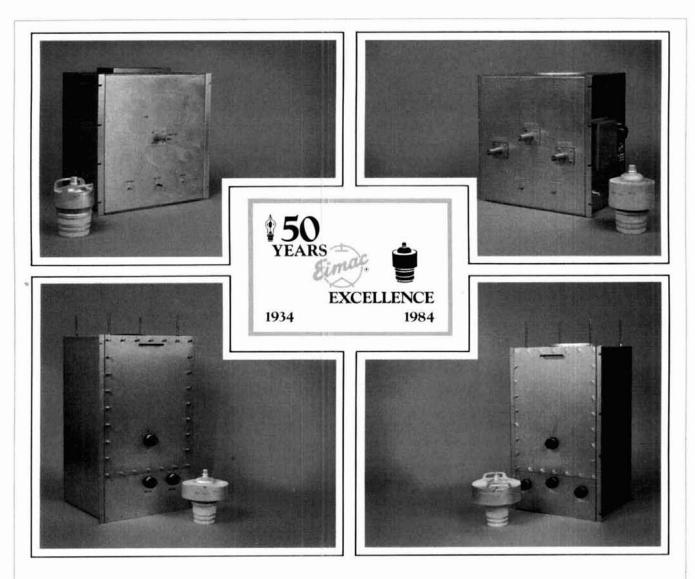

## EIMAC celebrates its 50th Anniversary with an extensive line of FM Broadcast Cavity Amplifiers.

Varian EIMAC celebrates 50 years of service to the broadcast industry with a spectrum of FM from a powerful 60 kW to a mini power 150 W solid state IPA.

## The cost-effective path to a modern FM transmitter.

No one knows more about broadcast tubes and cavities than EIMAC. Our strong cavity development capability reduces RF engineering problems. EIMAC cavities are inexpensive and simple to use. For more information call or write Varian EIMAC or contact any Varian Electron Device Group sales office worldwide.

#### EIMAC FM BROADCAST CAVITY PRODUCT LINE

POWER	CAVITY	EIMAC TUBE	
60 kW	CV-2230	4CX30,000G	
30 kW	CV-2202	4CX20,000C	
25 kW	CV-2200	4CX20,000A	
15 kW	CV-2210	4CX12,000A	
10 kW	CV-2228	4CX7500A	
5 kW	CV-2225	4CX3500A	
1.5 kW	CV-2220	3CX1500A7	
150 W	AM-2215A	Solid State	

Varian EIMAC 301 Industrial Way San Carlos, California 94070 Telephone: 415+592-1221

Varian AG Steinhauserstrasse CH-6300 Zug, Switzerland Telephone: 042+23 25 75



When we set out to make the best amateur radio equipment in the world, we had some pretty tough standards to live up to ...



So we designed the **RC-850 Repeater Controller**, the industry's top of the line repeater control system. Now in it's "third wave" of innovation, thanks to its designed for the future architecture and new software releases. The '850 defines the industry standard in repeater control systems.

- Fully remotely programmable with Touch-Tone commands or computer terminal
- · Front panel LED display, or terminal based display
- Over 300 word customized male and female speech synthesis vocabulary
- Time/day of week Scheduler with 10 set-up states, 30 changeovers and events, over 100 scheduled items for hands off operation and automatic reminders.
- Full or half duplex autopatch, autodial (200 numbers), emergency autodial, reverse autopatch, antidialer, toll restrict including telephone exchange tables, supports remote and multiple phone lines
- Informative remotely programmable ID's (17), tail messages (13), bulletin boards (5)
- 16 channel voice response analog metering, automatic storage of min/max values on each channel, values may be read back on command or may be included in any programmable messages
- · Supports synthesized remote base transceivers and full duplex links
- Individual user access codes to selectable features
- Mailbox for user-to-user, and system-to-user messages
- Paging two-tone, 5/6 tone, DTMF, CTCSS, HSC display, GSC digital display, user commandable and may be included in programmable messages (i.e. alarms)
- Logical to physical I/O mapping and internal "toolbox" for easy customizing of the controller to meet your needs and minimize external wiring
- Easy hookup to any repeater

Our new Digital Voice Recorder lets you remotely record ID's, tail messages, and various other response messages for automatic playback through your repeater. Audio is stored digitally with no-compromise reproduction quality in up to eight megabits of memory. The DVR can support up to three independent repeaters for a low per-channel cost. Its Touch-Tone activated voice mailbox lets your users easily record messages for other users when they aren't around.

#### QST: Attention All Hams

If you own a shack, you should know about ShackMaster"

ShackMaster lets you carry your home station with you in the palm of your hand. It acts as your gateway to the world, linking your handheld transceiver to your high performance HF station. Now, instead of your valuable home equipment being available to you 1% of the time, it's available 99% of the time! Whether around the house, in the yard, or across town, ShackMaster let's you take it with you.

But that's just part of ShackMaster's story. It lets you communicate with the family by handling third party traffic – its electronic mailbox and intercom let you keep in touch. And a simplex patch lets you place important calls directly through your home phone.

- Crossband linking VHF/UHF to HF
- Telephone access to your home station
- BSR Home Control interface
- Electronic Mailbox
- ShackPatch<sup>\*</sup> intercom into the shack
- PersonalPatch<sup>®</sup> simplex autopatch



#### ... and ours.

If your repeater budget can't afford the '850, we offer the RC-85 Repeater Controller, which we like to call the "second best repeater controller in the world". It's a scaled down, simplified version of our '850, but overall, it offers more capability and higher quality than anyone elses control equipment at any price.

- Remotely programmable with Touch-Tone commands
- Over 175 word customized male speech synthesis vocabulary
- · Selectable "Macro sets" for easy control operator selection
- · Autopatch, autodial (200) numbers, emergency autodial, reverse patch
- Remotely programmable informative ID's (7), tail messages (3), bulletin board (2)
- · Supports synthesized remote base transceiver, control receiver, alarm
- Selectable, informative courtesy tones
- Talking S-meter, Two-tone paging
- Easy hookup to any repeater

For those who like to "roll their own", we can get you off to a rolling start with our **ITC-32 Intelligent Touch-Tone Control Board.** Much more than just a decoder, it's a mini-control system of its own, with the basic repeater and remote base functions built-in. And it can be tailored by you with its Personality Prom.

- 28 remotely controllable latched or pulsed logic outputs
- 4 alarm or remote sensed logic inputs
- · Response messages to confirm command entry
- Repeater functions including COR, IDer, timers, courtesy tone, etc.
- Remote base functions including control of synthesized transceiver
- Remotely recordable, variable length audio tracks, accessed from controller messages
- Top quality, no compromise audio reproduction
- · Supports up to three repeaters for cost effective installation
- Expandable to roughly 6 minutes of speech in 8 megabits of memory
- Easy interface to RC-850, RC-85 controllers, or to any stand-alone repeater

All our products are designed and manufactured with industrial grade reliability. Little things that many people don't notice, like machine contact IC sockets for all ICs, gold on gold signal connectors, high performance CMOS for minimum power drain, and transient supression. And the products are documented with high quality, easy to read manuals. Our goal is to advance the state of the repeater art. But most of all, our products put the FUN back into the FUN MODE!



To order one of these advanced control products, call 408-749-8330 and speak with Tim or Catherine. Visa and Mastercard accepted. Technical manuals are available for purchase and the amount paid is applied as a deposit on the equipment. For specifications and a copy of our ACC Notes newsletter, just write or send in your QSL card to:



More Details? CHECK-OFF Page 166

10816 Northridge Square 
Cupertino, CA 95014

(408) 749-8330

## stacking Yagis is a science

Determining E/H plane patterns results in optimized performance

Several years ago I began a project designed to develop a means of determining gain of a particular 144 MHz Yagi. Knowing that number, I would be able to calculate the aperture. Once the aperture was known, I would know the correct stacking distance and would then be able to build the perfect 144-MHz array.

As one might expect, things didn't quite work out as planned. But eleven years and seven EME arrays later, I believe I have found an improved method of determining the optimum stacking distances for multiple Yagi VHF and UHF arrays.

#### what is optimum stacking?

"Best array performance" is a matter of opinion, and depends on how the antenna is used; an array can be optimally stacked, for example, to deliver maximum gain, or for a controlled azimuthal pattern that produces a deep null in the direction of interference. This

table 1. Typical temperatures of "objects" at 144 MHz and 432 MHz.

	144 MHz	432 MHz
object	degrees K	degrees K
cold sky	175	10
hot sky	3,200	190
earth	290	<b>29</b> 0
arcing power line	100,000	6,000


article primarily addresses Yagi stacking for use in EME (Earth Moon Earth or moonbounce) communications. However, this technique is also appropriate for other space communications applications such as satellite communications and radio astronomy. It could also be used for land-based communication requiring high gain such as tropospheric scatter.

For EME and other weak-signal VHF/UHF work, optimum stacking distance can be defined as that distance which yields the greatest array gain versus lowest array temperature. Used by professional space communications engineers, this definition refers to maximizing the G/T ratio. With Yagis, the best G/T usually never occurs at the distance which yields maximum stacking gain. It normally occurs at significantly closer spacing. In simpler terms, optimum stacking distance is that stacking distance which yields the greatest array gain increase while simultaneously keeping all sidelobes at an acceptable level.
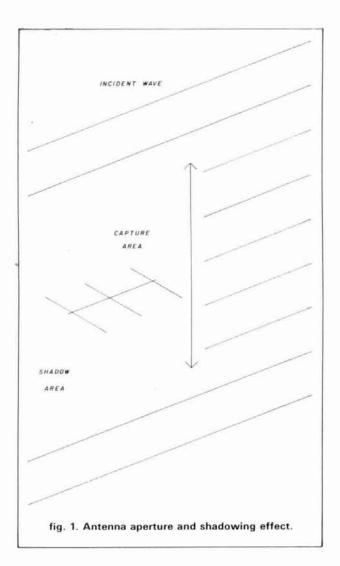
#### the effect of antenna temperature

Several good sources of information are available for those unfamiliar with the concept of antenna temperature.<sup>1,2</sup> To review, antenna temperature is the temperature of the object at which the main lobe of the antenna is pointed - i.e. the Earth. Moon. Sun, hot sky, or cold sky. However, if the array has sidelobes of significant area and amplitude, unwanted noise can be picked up from noise sources in the direction in which the sidelobes are pointed. This unwanted noise reception will increase the net antenna temperature. (Table 1 lists typical temperatures of several "objects" at 144 MHz and 432 MHz.) A 432-MHz array with large sidelobes pointed at the Earth will suffer a significant receive signal-to-noise loss because of the reception of Earth noise; likewise, a 144-MHz array with sidelobes directed toward a hot sky or a leaky power line will experience a similar degradation in receive performance.

By Steve Powlishen, K1FO, 816 Summer Hill Road, Madison, Connecticut 06443




As a point of reference, commercial satellite Earth station antennas that use parabolic dish antennas with Cassegrain or Gregorian subreflector systems have antenna temperatures as low as 18 degrees K. In comparison, an Amateur dish using a simple dipole or horn feed at 432 or 1296 MHz has a typical antenna temperature of 65 degrees K, while a 16-Yagi 432-MHz array with the Yagis spaced for maximum gain may have an array temperature over 170 degrees K (or even worse if low-loss phasing lines are not used). Conversely, stacked 432-MHz EME Yagi arrays incorporating optimized stacking distances have been built to provide array temperatures lower than 85 degrees K including phasing line losses. These antenna temperatures were measured by pointing the antenna at the Earth and then at the cold sky and comparing the noise ratios. The noise contribution due to the receiver can then be factored out if the receiver system noise temperature is accurately known. The significance of the lower array temperature cannot be overstated. If we assume a high performance receiver with a 0.45 dB system noise figure, lowering a 432 MHz array temperature from 170 degrees K to 85 degrees K results in a receive signal-to-noise improvement of about 2.3 dB or almost the equivalent of doubling the array size! These results have been obtained using standard Yagi designs such as the NBS Yagis and the K2RIW 19-element Yagi. I expect further improvements can be obtained when Yagis designed with best G/T in mind are available to Amateurs.

#### methods of determining optimum stacking distances

There are three methods of determining optimum stacking distances. The first method to be examined briefly, is based on classic antenna theory. The second, which will be emphasized, is experimental. Computer analysis, currently used by the professional community is the third, and will not be discussed here. With programs for Yagi analysis now readily available to the Amateur, it is hoped that the more mathematically inclined and computer-knowledgeable Amateurs will carry on where this article leaves off and extend computer modeling to include optimum stacking.

The concept of antenna directivity, (**fig. 1**), put forth by Kraus<sup>3</sup> and introduced to Amateurs by Orr and Johnson,<sup>4</sup> holds that all antennas have an effective capture area, or area around the antenna that "captures" or extracts the electromagnetic energy from space. The higher the gain of the antenna, the

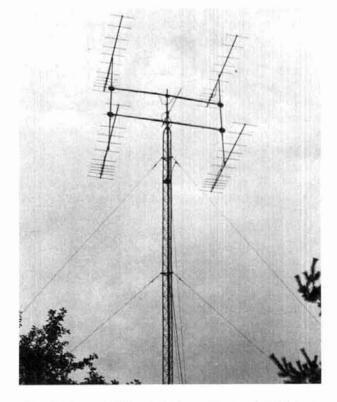

Four 12-element LPYs stacked on a telescoping H-frame.

larger the area from which energy will be extracted. Behind the antenna there will be a shadow area, or space where the field strength of the incident wave is reduced in magnitude. (This concept is analogous to putting an object in front of a light source and creating a shadow behind it.) In mathematical terms the capture area is directly proportional to gain and is defined in **eq. 1**.

$$A_{em} = 0.13 \cdot 10^{dBd/10}$$
 (1)

Where  $A_{em}$  is the effective capture area in wavelengths squared and dBd is the gain of the antenna in decibels over a half wave dipole. For antennas such as Yagis, which have an elliptically shaped aperture, the size of the effective aperture will be slightly different between the E and H planes. The aperture dimensions in wavelengths squared can be calculated by using **eqs. 2** and **3**.


$$A_H = 2 \sqrt{\frac{A_{em} \cdot \theta_E}{\pi \cdot \theta_H}}$$
 (2)

$$A_E = 2 \sqrt{\frac{A_{em} \cdot \theta_H}{\pi \cdot \theta_E}}$$
(3)

Where  $A_E$  is the E-plane aperture dimension,  $A_H$  is the H-plane aperture dimension,  $\theta_E$  if the E-plane half power beamwidth, and  $\theta_H$  is the H-plane half power beamwidth.

There are two problems with using these formulas to calculate stacking distances. First, an antenna's aperture is not an ellipse with a clearly defined boundary, with radio waves being extracted on one side of the boundary and nothing happening on the other side. Instead, an antenna progressively extracts less and less energy from space continuously. In addition, the half power beamwidths of an antenna are merely a point on the field strength gradient of the antenna. Therefore, proper stacking distance becomes a question of determining where two *unclearly* defined volumes separate. It is not a solid boundary like a brick wall.

The second problem, largely self-inflicted by Amateurs eager to believe they could defy the laws of physics and discover something that antenna engineers could not, is that of believing inflated gain figures produced by both Amateurs and some manufacturers of Amateur antennas. (In defense of Amateur equipment manufacturers, their claims are restrained in comparison to their CB and home TV counterparts). Using these optimistic gain claims, which in some cases are typically 3-dB high, leads to arrays which have grossly oversized stacking dimensions. The gain figures shown in the recommended stacking distance

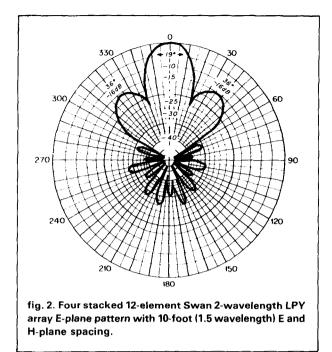

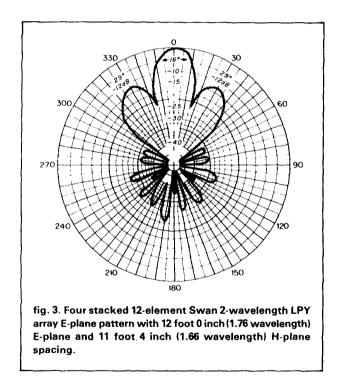


table (**table 2**) represent hundreds of hours of antenna measurements I have performed, the compilation of data from ten years of antenna gain contests, and finally, computer analysis of almost all the antennas listed in the table. The result is a listing of gain figures closer to reality, I believe, than anything previously available. (For further discussion of how much gain can be expected from a given boomlength Yagi, reading DL6WU's article is suggested.)<sup>5</sup>

#### measuring antenna gain

As part of my experiments to measure antenna gain and determine proper stacking distances, a telescoping H frame was constructed on my 60-foot (18.3 meters) tower to measure the 144-MHz antenna. This arrangement allowed for rapid placement of Yagis along with a simple method of adjusting the spacing to any separation of up to 16 feet (4.9 meters). A smaller frame (6 feet/1.9 meters) was used to measure the 432-MHz Yagis.

The next step was to figure out a relatively accurate means of making pattern measurements. Over the years I tried a variety of measurement techniques, including use of strip chart recorders, spectrum analyzers, and RF voltmeters. Out of all this came a relatively simple and reasonably accurate method that is within the reach of most serious VHF/UHF experimenters.

The basic requirements for pattern measurement are:

an accurate direction indicator;

• a receiver with a calibrated signal strength indicator; and

• a signal source located so as to minimize reflection problems.

Satisfying each requirement was surprisingly simple. The direction indicator I used was a selsyn readout\* with close to 1 degree accuracy. Alternatively, the digital readout system using 10 turn pots and popularized by many EMErs<sup>6</sup> could be used. The availability of signal generators such as the Hewlett-Packard 608 series (or their military counterparts, the TS-510 series)\* solves the receiver calibration problem. My method of measurement consisted of connecting a digital voltmeter (DVM) to the AGC (automatic gain control line) of the station receiver (an R-4C and TR-7). Care must be taken to keep signal strengths high enough above the noise (floor) to eliminate signal-tonoise plus noise ratio correction problems. The signal level must not be so high that it causes gain compression problems. The quick way to get a pattern was to run the antenna through 360 degrees while recording the AGC voltage readings on the DVM. The antenna was then replaced with the signal generator and the AGC readings were converted to a dB scale. (A 10 dB attenuator was placed between the converter and antenna or signal generator to eliminate impedance problems.) This "calibration" of the receiver was done after every measurement to eliminate receiver gain drift errors.

The signal source presented the trickiest problem, but again a simple solution was found. A number of signal sources were tried including locating signal sources in my back yard, in the woods about 1000 feet (305 meters) away, and at a local ham's QTH about 2 miles (1.3 km) away. All of these solutions gave marginally repeatable results. That is, an antenna would look different from day to day and from source to source. Because I believed the problem to be reflections from various objects, I decided to try a signal source located above the clutter. My location at that time was 105 feet (32 meters) above sea level. The antennas were located at 65 feet (20 meters), well above the nearby trees. My location was surrounded by hills up to 1200 feet (366 meters) high, 10 to 12 miles (16 to 19.2 km) away. The ground between my location and the hills dropped in elevation, which made the tops of the hills a completely clear shot at about a 0.5 degree elevation angle. A fellow ham located on one of the hills was called upon; by using high gain source antennas (stacked 3.2 wavelength NBS Yagis on 144 MHz and RIW19s on 432 MHz), repeatable pattern measurements became a reality. After performing many measurements I was able to "calibrate" my range such that I could see how different antennas gave the same false lobes or left to right unbalance. The patterns shown in this article have been cleaned up to eliminate known range errors. Various NBS antennas were constructed and their patterns measured. My measured patterns correlated very well with the NBS published patterns and offered proof of the method's validity.


It was also found that accurate relative gain measurements were possible. Gain measurement calibration was made by putting two identical antennas on the frame and measuring the relative signal level between them. The antennas were then switched in position and the measurement repeated. In this manner any differences in signal strength could be factored out before a test antenna was measured. Results were found to be repeatable to within 0.2 dB over the twoyear period the gain tests were made. A similar method was used to measure the gain increases to be had from stacking antennas.


#### the effects of antenna spacing

To get an indication of what happens when the spacing of Yagi arrays is changed, an array of four 12-element LPY (log periodic Yagis, as introduced by Oliver Swan and later produced by KLM) was set up on the telescoping H-frame. Pattern measurements were made at one foot (0.3 meter) spacing increments from 10 feet (3.0 meters) up to 16 feet (4.9 meters) (1.4 to 2.3 wavelengths). The resultant patterns are

<sup>\*</sup>Available from Fair Radio Sales, P.O. Box 1105, Lima, Ohio 45802

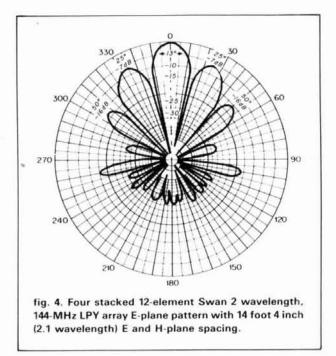typical of all two-wide Yagi arrays. As the spacing between Yagis is increased, the main lobe beamwidth narrows, the sidelobes increase in amplitude and the nulls get much deeper. The E-plane pattern at 10 feet




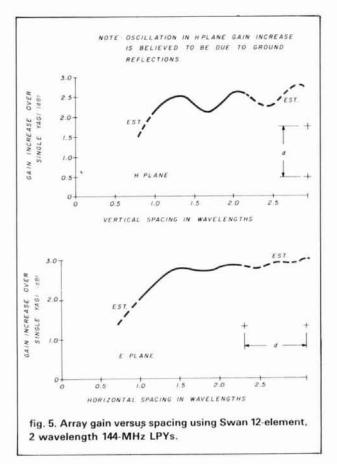

(3.0 meters), 12 feet (3.7 meters) and 14 feet 4 inches (4.4 meters) spacings is illustrated in **figs. 2**, **3**, and **4**. Looking at the sample patterns, it can be seen that the beamwidth of the first sidelobes is close to that of the main lobe for each spacing and that its amplitude increases rapidly at larger separations. Other minor lobes start to have significant amplitudes at the greater separations.

The question of which distance is the proper one still remained to be answered. Gain and individual pattern measurements on the 12-element LPY indicated an actual gain of about 11.2 dB over a half-wave dipole (dBd). By using eq. 1, 2, and 3 (single antenna pattern of 36 degrees E-plane by 40 degrees H-plane), stacking distances of 10 feet 8 inches E-plane (3.3 meters) 9 feet 7 inches (2.9 meters) H-plane were calculated. The 10 foot 8 inch (3.3 meter) E-plane spacing gave a pattern similar to fig. 2, but with first sidelobes down 14 dB. Next relative gain measurements were attempted between one and two antennas. Resultant gain curves showing stacking gain versus spacing are shown in fig. 5. The general shape of the curves are similar to those given in the now-famous NBS Technical Note 688,7 (fig. 6) except I did not see any gain decrease as the spacing was increased to large distances, only a flattening of the gain curve. I also saw an apparent larger gain increase in the E rather than the H-plane. This is again indicated in NBS Note 688. As illustrated in fig. 5, the knee in the gain increase occurs at about 2.7 to 2.8 dB in the E-plane and at 2.5 to 2.6 dB in the H-plane. (When phasing line losses are factored out.)

Next, I attempted to relate first sidelobe levels to position on the gain increase curve and found that the gain increase started to flatten out when the first sidelobes were -12 to -13 dB down. It should be pointed out that at the time these measurements were made,

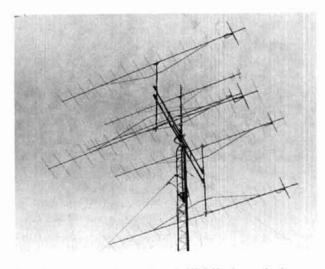

Four 17-element, 3.2 wavelength NBS Yagis stacked on an H-frame.

## WITH PRIVATE PATCH II YOU SPEND YOUR TIME COMMUNICATING .... **NOT** WAITING TO TAKE CONTROL

PRIVATE PATCH II allows communications to proceed back and forth as rapidly as on a telephone. There is no waiting for sampling circuits to acquire each time the mobile transmits.


- The PRIVATE PATCH II VOX system offers a substantial improvement over sampling autopatches in time spent waiting for control!
- EXAMPLE: Suppose you made 10 phone calls 9 completed, 1 busy - assume the completed calls average 20 talk exchanges each, 180 total.
- You would spend 360 seconds (6 minutes!) waiting for control if you were using a sampling patch that samples every two seconds (180 waits × 2 seconds = 360 seconds). It is a severe inconvenience to have to press the button for a seeming eternity before you can be heard on each and every mobile reply.
- With PRIVATE PATCH II there is no lost time waiting for control on all 9 completed calls. However, the busy call would cause a 15 second wait for the control interrupt timer to return control to the mobile.

	SUMMARY	
	CONTROL WAITS	TIME WAITED
Private Patch II	1	15 seconds
Sampling	180	6 minutes


If the sampling patch has a circuit that "slows the sample rate when telephone audio is present," the speed of acquisition is made even slower. The wait time increases, and the phone party can say perhaps 25 or more words before they can be cut off.
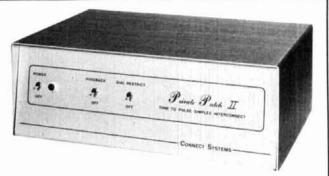
#### WHY LAND MOBILE PROFESSIONALS AVOID SAMPLING PATCHES ....

- The majority of radios on the market (especially synthesized and relay switched types) do not T/R quickly enough to give acceptable results. Often engineering level modifications are required to improve T/R response time.
- The slower the T/R response time, the longer the sample must last. And of course no telephone audio is heard during the sample. Just noise. The result is lost words and syllables which are proportional to T/R response.
- Acquiring and maintaining control (in order to communicate) becomes erratic when the mobile is less than full quieting. This causes a severe loss of range.
- The base station radio can not be equipped with a linear amplifier, and operation through repeaters (that have hangtime) is not possible with a noise sampled patch.
- VOX autopatches overcome each of these shortcomings. In fact, nearly all simplex patches sold in commercial service are the VOX type.
- Could these be some of the reasons that the competition refers to their VOX patch as "our favorite commercial simplex patch"?
- FORGET AMATEUR GRADE SAMPLING AND STEP UP TO A COMMERCIAL GRADE PATCH. PRIVATE PATCH II!



#### THE SMARTER AUTOPATCH

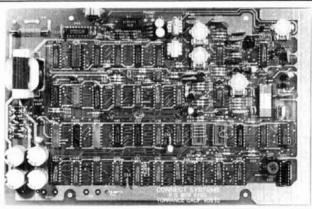

AEROSPACE LEVEL QUALITY

#### FEATURES

• CW ID (free ID chip) • Selectable tone or pulse dialing • User programmable toll restrict . Five digit access code . Ringback (reverse patch) . Busy channel ringback inhibit (will not transmit on top of someone) . Three/six minute "time-out" timer is resettable from the mobile . Modular phone jack and seven foot cord . Available in 12 VDC or 115 VAC version

#### ALSO

- 14 day return privilege when ordered factory direct.
- One year warranty compare to their six months. -

#### CONTACT A LOCAL DEALER TODAY


MIKES ELECTRONICS Ft. Lauderdale, Miami FL AMATEUR ELECTRONIC SUPPLY Milwaukee WI, Wickliffe OH, Oriando FJ, Clearwater FL, Las Vegas NV AMARADIO OUTLET Anaheim CA, Burlingame CA, San Diego CA, Van Nuys CA NAG DISTRIBUTING CORP. HENRY RADIO Los Angeles CA, Anaheim CA, Butler MO PACE ENGINEERING C&A ROBERTS INC. Torrance CA THE HAM SHACK COLES COMMUNICATIONS JUNS ELECTRONICS Culver City CA, Reno NV ERICKSON COMMUNICATIONS CANADA: DOLLARD ELECTRONICS

MIAMI RADIO CENTER CORP.



23731 MADISON ST., TORRANCE, CA 90505 PHONE: (213) 373-6803

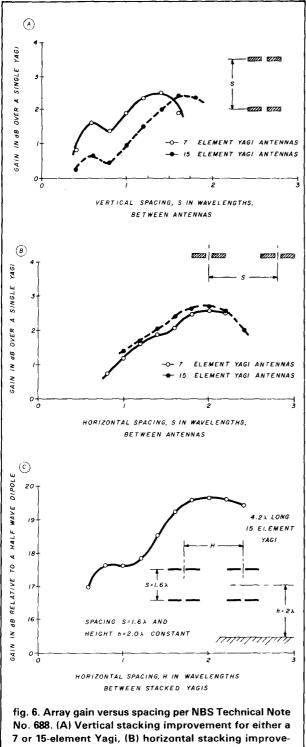very wide spacing was very popular and many Amateurs, including myself, thought the NBS report with its relatively close spacings was in error. The correlation between my measurements to the NBS curves




7 or 15-element Yagi, (B) horizontal stacking improvement for either a 7 or 15-element Yagi, and (C) horizontal stacking improvement for two sets of stacked Yagis spaced vertically 1.6 wavelength apart. was truly amazing, especially considering that I was intent on proving NBS *wrong*.

The additional rule of thumb used by Amateurs was to stack Yagis so that the first sidelobes were 13 dB down. This seemed to correspond to where the gain increase curves flattened out; however, when the sidelobes were - 13 dB, the main lobe was less than one half that of a single antenna. When I attempted to find out where the - 13 dB rule of thumb came from, the only explanation I could find was that two sidelobes at - 13 dB were, in total, - 10 dB from the main lobe and anything 10 dB down (or 1/10 amplitude) was insignificant. This seemed plausible except that the Hplane should have a pattern similar to the E-plane -and if it also had two sidelobes 13 dB down (with similar beamwidth to the main lobe), the sum of just those four lobes would be  $-7 \, dB$  relative to the main lobe or 20 percent of the amplitude of the main lobe. Thus if all four sidelobes were looking at noise sources 10 times stronger (in reality, it is not very likely all the sidelobes would be facing similar noise sources) than the background noise the main lobe was looking at, the array would suffer a 6 dB signal-to-noise loss on receive.
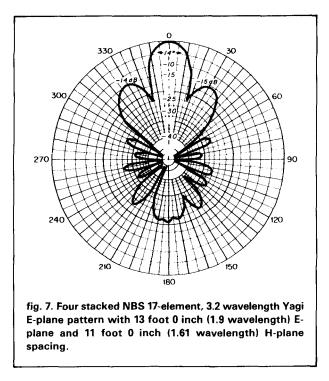
#### improving a 144-MHz EME array


With this information in mind, I began to look at the 144-MHz EME array I was using at that time. It consisted of 4 Cushcraft A32-19, 19-element 3.2-wavelength 22 foot (6.7 meter) long Yagis patterned after the NBS 17-element Yagi, with a tri-reflector added. The gain of a single A32-19 is about 13.2 dBd with -3 dB beamwidths in the E and H-plane of approximately 28 by 33 degrees. By using the previously defined aperture calculation method, spacings of 2.1 by 1.75 wavelength or 14 feet (4.3 meters) E-plane by 12 feet (3.7 meters) H-plane were calculated. The manufacturer of the antenna was recommending the same spacings, so it seemed reasonable to use them when constructing the array.


The performance of the array seemed acceptable. I usually received good signal reports, but on receive, signals always were poorer than expected. I easily dismissed the lack of hearing on a noisy urban environment. Looking at the NBS stacking curves, NBS was recommending 2.0 by 1.6 wavelength spacing for the 15-element 4.2 wavelength Yagi, an antenna with about 0.8 dB more gain than the A32-19. I then made some sidelobe measurements and found that the first E-plane sidelobes were down about 12 dB and the H-plane sidelobes were down only 10 dB. A quick decision was made to move the antenna spacing in to 1.9 by 1.6 wavelenghts or 13 by 11 feet (4.0 by 3.4 meters) E by H-plane, respectively. The results were startling. During the first two months of operation at the closer spacing, about 20 new stations were worked on EME,



many of them stations I had tried to work in the past without success.


After that I obtained four more A32-19 Yagis. I modified them to standard NBS dimensions and removed the tri-reflectors. I then set them up on the telescoping H-frame and set out to find what was going on. The E-plane pattern of the 17-element  $3.2\lambda$ NBS array spaced at 13 feet (4.0 meters) E-plane is shown in fig. 7. The pattern looks very good, with first sidelobes down 14 to 15 dB and all other lobes down 25 to 30 dB. H-plane patterns are usually more difficult to measure. Reflections from objects such as trees and utility poles, which are essentially vertically polarized, complicate the problem. Tilting the array back causes changes in ground reflections, which can induce errors if that method is used. Because of that I did not make a complete H-plane pattern measurement, but I did check the first H-plane sidelobes and found them to be only 12 dB down at the 11 foot (3.4 meter) spacing. The aperture calculations indicated that the spacing was already too close - however, NBS had indicated that 1.6-wavelength or 11-foot (3.4 meter) spacing was correct for the higher gain 15-element Yagi. To explain this wide discrepancy between calculated spacings and measured patterns, the patterns of the individual Yagis were examined. Figure 8 is a computergenerated plot of the E and H-plane patterns of the 3.2 wavelength NBS Yagi. The H-plane pattern is noticeably less directive than the E-plane with larger sidelobes over the entire pattern. The array pattern of a number of Yagis is the resulting interference pattern of the individual Yagi patterns interacting with each

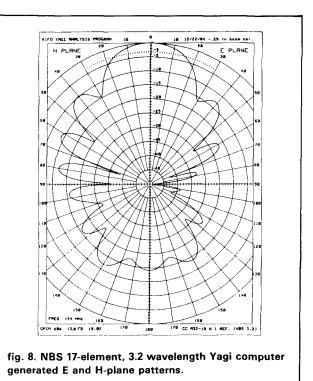

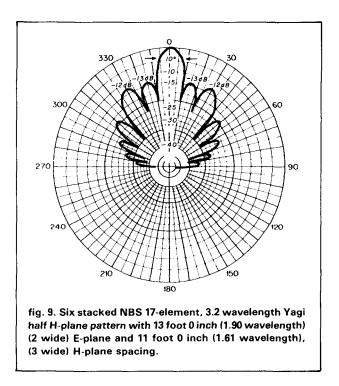


other. It follows that the resulting array pattern of multiple Yagis will have larger sidelobes in the H-plane.

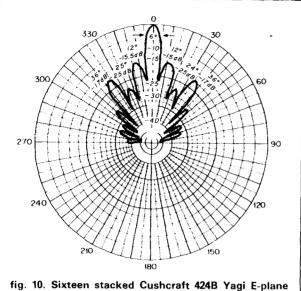While measuring the four 3.2-wavelength NBS Yagi array, it was decided to attempt to relate array main lobe beamwidth to sidelobe level and array gain increase. The 3.2 wavelength NBS Yagis reacted similarly to the 12-element LPY antennas previously meas-



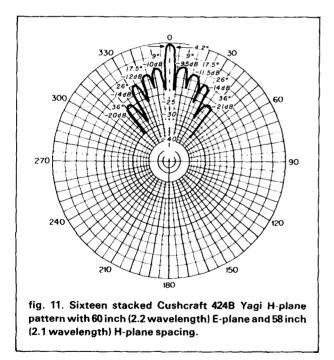pattern with 60 inch (2.2 wavelength) E-plane and 58 inch (2.1 wavelength) H-plane spacing.




ured. When the first sidelobes were -13 dB, the main lobe was narrower than one half that of a single Yagi. Likewise, the main lobe was approximately one half the beamwidth of a single Yagi when the first sidelobes were -14 to -15 dB. *This relationship of first sidelobes at* -14 to -15 dB when the main lobe beamwidth is half that of a single Yagi has held up in all subsequent arrays I have measured. This also includes arrays that are three and four Yagis wide where the array -3 dB beamwidth is approximately equal to the

beamwidth of a single Yagi divided by the number of Yagis in that plane. As an example, my 144-MHz array was expanded to six 3.2 wavelength Yagis. The vertical spacing was kept at 11 feet (3.4 meters). The array's H-plane pattern is shown in fig. 9. The number of major sidelobes in an array is equal to the number of elements in a plane minus 1. Thus the six-Yagi array will have two major H-plane sidelobes. In this case, the first sidelobe is -13 dB down and the second is - 12 dB down. As expected, the main lobe is narrower than one third that of a single Yagi at 10 degrees. Note that as the number of elements in an array are increased (and consequently the number of major sidelobes increase) it becomes much more important to keep the sidelobe amplitudes under control. A look at a 16 Yagi 432-MHz EME array will expand on this point.
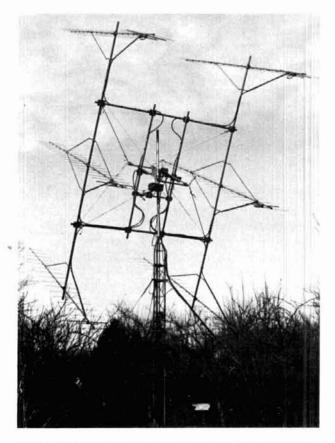
#### more dramatic results at 432 MHz

Frank Potts, WA1RWU, had erected a 432 MHz EME array consisting of 16 Cushcraft 424B 24-element 7.6 wavelength Yagis. The instruction sheet for the 424B recommended 66-inch E-plane by 60-inch Hplane spacing. This was considerably closer than the spacings determined from calculating the aperture. Based on actual antenna gain of 15.8 dBd and a pattern of 20 degrees by 22 degrees (E by H), the spacings were calculated to be 72 inches (1.8 meters) by 65 inches (1.7 meters) E-plane by H-plane. When Dave Olean, K1WHS, of Cushcraft was contacted, he recommended the use of even closer spacings for an EME array — as close as 60 inches (1.5 meters) by 54 inches (1.4 meters). Because of mechanical considerations, the array was assembled using 60-inch (1.7 meter) horizontal (E-plane) by 58-inch (1.5 meter) vertical (H-plane) spacing. Phasing lines consisted of 1/2-inch and 7/8-inch hardline and were cut on a return loss bridge known to be accurate. The performance of the array had a familiar ring to it; Frank would receive excellent signal reports, but on receive, signals were far poorer than expected. Checking into the 432-MHz EME activity, Frank found that there had been a considerable number of other hams who had erected 16-Yagi EME arrays for 432 MHz that never worked well, and as a result, their stations had disappeared from the EME ranks.

At this point I began helping Frank to improve the array. The first priority, I decided, was to obtain a pattern measurement. The height of the array, 20 feet (6.1 meters) above ground, made the likelihood of taking accurate measurements remote. However, with the amount of array gain available (close to 26 dBd) I decided it should be possible to make adequate measurements by using Sun noise.<sup>8,9</sup> The E-plane pattern looked excellent, with the three major side-lobes down over 15, 25, and 17 dB, respectively



Six stacked NBS 17-element, 3.2 wavelength Yagi 144-MHz EME array.

(fig. 10). The main lobe beamwidth was close to 6 degrees or greater than one quarter that of a single antenna. The H-plane was a shock with the -3 dB beamwidth of 4 degrees or much narrower than the expected 5.5 degrees. The major sidelobes were very large, at only 9.5, 11.5, and 14 dB below the main lobe (fig. 11). No EME signals had ever been copied when the array elevation was below 18 degrees. The fact that this angle was the same as the second sidelobe direction was no coincidence.

Some tests with a pair of K2RIW 19-element Yagis were run to measure changes in H-plane sidelobe levels. It was found that the first sidelobes changed at about 1 dB for every 2 inches of spacing change. Since the gain of the RIW19 (15.1 dBd) is close to the 424B it was felt that the results would be similar with the 424B. The vertical spacing was moved in by 6 inches (15 cm) to 52 inches (1.3 meters). The first sidelobes were expected to drop down to - 12.5 dB. The results of that spacing change were amazing. The major sidelobes were now -12.3, -20.7, and -14.4 dB (fig. 12). Sun noise was up over 2 dB.\* The onthe-air performance improvement was even more spectacular, with 41 QSOs made with 34 different stations during the first ten days of operation at the new spacing. Fewer than 20 QSOs were made in over


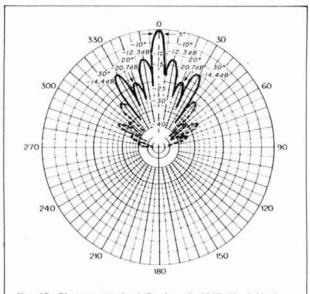


fig. 12. Sixteen stacked Cushcraft 424B Yagi H-plane pattern with 60 inch (2.2 wavelength) E-plane and 52 inch (1.9 wavelength) H-plane spacing.

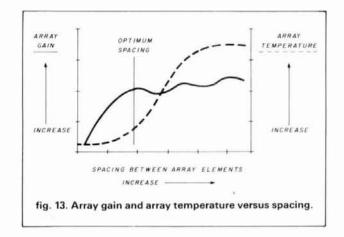



two months of operation at the wider spacing. Most of the contacts were on random operation (as opposed to pre-arranged schedules) and included several 8 Yagi and one 4 Yagi stations. EME signals, including echoes, were now consistently copied down to 2 degrees elevation (the elevation angle where the main lobe would be clearing the earth). The main lobe beamwidth was still narrower than one quarter that of a single 424B at 5 degrees. This again supports previous measurements which indicated that a 1/4 beamwidth (5.5 degrees) would not occur until the first sidelobes are down 14 to 15 dB. The pattern indicates that the array has not yet been optimized. It is estimated that the best performance would occur at 62

<sup>\*</sup>Sun noise is measured by pointing the array at cold sky, noting the noise level, and then pointing the array at the sun and measuring the noise increase. Sun noise is a combination measurement of overall receiver temperature and array gain.

inches (1.6 meters) E-plane by 50 inches (1.27 meters) H-plane spacing.

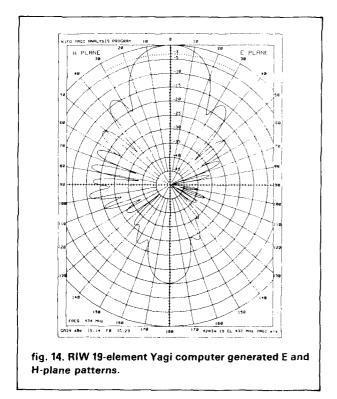The reason for this dramatic improvement can be explained by looking at the approximate Earth noise pickup from the major sidelobes when the array was operated at low elevation angles. The main lobe at 432



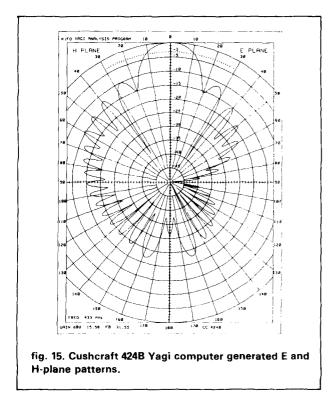

MHz may typically see a sky temperature less than 20 degrees K. The sum of the first three sidelobes at -9.5, -11.5, and -14 dB would be equivalent to a single lobe 6.5 dB below the main lobe. Pointed at Earth (290 degrees K), those lobes would contribute about 65 degrees K of noise or cause a 5.1 dB degradation in signal-to-noise ratio. With the reduced sidelobes at the closer spacing, the sum of the three major sidelobes is about -9.8 dB and would cause about a 1.8 dB signal-to-noise degradation. This represents a 3.3 dB receive improvement, which is quite significant on EME. The actual array noise is much more complicated; to calculate it would require summing all the sidelobes and accounting for the strength of the noise sources toward which they pointed. The over-2 dB Sun noise improvement nonetheless confirms the performance improvement.

An alternative method for checking system temperature without taking array gain into account is to measure Earth noise. This is done by pointing the array at cold sky and then at the Earth and then comparing the noise levels. A well-performing 432-MHz EME system should see over a 4 dB ratio. Since this measurement does not take array gain into account it should not be used for array optimization because doing so could result in significant gain loss. **Figure 13** is a graph of typical array temperature versus stacking gain increase. The temperatures are not "real world" because they are quite different for the various Amateur frequencies.

#### easier method for measuring array beamwidths

Measuring the -3 dB beamwidths on high gain arrays with very sharp beamwidths can be a difficult task. WA1RWU's 16-Yagi 432-MHz array uses a proppitch motor for an azimuth rotator and has a 360degree rotation time of over 3 minutes. The elevation leadscrew drive takes over 2 minutes to run 90 degrees. Even with such a rotating system, attempting to measure a 5 degree beamwidth can be a taxing experience. With a conventional commercial rotator it appears to be impossible to get an accurate measurement. It was discovered very early on that the halfpower beamwidth was always equal to slightly less than 1/2 the spacing of the first nulls on either side of the main lobe. Interestingly, DL6WU has said that the beamwidth of a single Yagi is equal to 0.485 times the first null spacing. The measurement of the first nulls provides a much easier and most likely more accurate means of determining antenna half-power beamwidths.

The H-plane pattern measurements on the RIW19 Yagi provided yet another surprise. A pair of RIW19s had first H-plane sidelobes down 13 dB at a spacing of 54 inches (1.37 meters). The 424Bs had first H-plane



## We just might beat that "unbeatable" deal



Rudy N9CC



Morgan KB4GFJ Talk with everyone else. Then call us. We're hams with over 50 years of combined experience. We know communications and equipment. We also listen to what you want. And at what price. Then we work with you to put it all together.

We specialize in a total systems approach to communications. It's a concept that takes you to the top in operating performance.

Call us. We don't mind being your last chance to save.

We carry all the top names in amateur equipment.

Hours: Tuesday-Saturday, 10 am-6 pm. Closed Mondays.

#### 800/845-6183 803/366-7157 Inside SC

Service Department 803/366-7158





Ken N4FYO



Marji KA4LPW






OCK HIII, SC 29730

- 116
 
#### THE MOST AFFORDABLE HIGH QUALITY XMTR & RCVR MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC. REPEATER ALSO HAS THE MOST IMPRESSIVE • R144/R220 FM RCVRS for 2M or 220 MHz. 0.15uV sens.;8 pole xtal filter & ceramic filter in i-f, helical PERFORMANCE FEATURES resonator front end for exceptional selectivity, (AND GIVES THEM TO YOU AS STANDARD EQUIPMENT!) >100dBat ± 12kHz, best available today. Flutter-proof squelch. AFC tracks drifting xmtrs. Xtal oven avail. Kit only \$138. Band Kit Wired R451 FM RCVR Same but for uhf. Tuned 10M,6M, line front end, 0.3 uV sens, Kit only \$138. \$880 2M,220 \$680



- R110 VHF AM RECEIVER kit for VHF aircraft or ham bands or Space Shuttle. Only \$98.
- . T51 VHF FM EXCITER for 10M, 6M, 2M, or 220 MHz. 2 Watts continuous, up to 3 W intermittent. \$68/kit.
- T451 UHF FM EXCITER 2to 3 Watts. Kit only \$78. Xtal oven avail
- VHF & UHF LINEAR AMPLIFIERS. For either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Several models. Kits from \$78.

NOW-FCC TYPE-ACCEPTED TRANSMITTERS & RECEIVERS AVAILABLE FOR HIGH-BAND & UHF. CALL FOR DETAILS.

#### ACCESSORIES

- MO-202 FSK DATA MODULATOR. Run up to 1200 baud digital or packet radio signals through any FM transmitter. Automatically keys transmitter and provides handshakes. 1200/2200 Hz tones. Kit only \$45.
- DE-202 FSK DATA DEMODULATOR. Use with any FM receiver to detect packet radio or other digital data in "202" modem format. Provides audio conditioning and handshakes. Kit only \$38.
- COR-2 KIT With audio mixer, local speaker amplifier, tail & time-out timers. Only \$38.
- COR-3 KIT as above, but with "courtesy beep". Only \$58.
- CWID KITS 158 bits, easily field programmable, clean audio. Kit only \$68.
- A16 RF TIGHT BOX Deep drawn alum. case with tight cover and no seams.  $7 \times 8 \times 2$  inches. Designed especially for repeaters, \$20.
- DTMF DECODER/CONTROLLER KITS. Control 2 separate on/off functions with touchtones®, e.g., repeater and autopatch. Use with main or aux. receiver or with Autopatch. Only \$90
- AUTOPATCH KITS. Provide repeater autopatch, reverse patch, phone line remote control of repeater, secondary control via repeater receiver. Many other features. Only \$90. Requires DTMF Module.
- SIMPLEX AUTOPATCH. Use with your FM transceiver. System includes DTMF & Autopatch modules above and new Timing module to provide simplex autopatch and reverse autopatch. Complete patch system only \$200/kit. Call or write for details.

#### Call or Write for FREE CATALOG (Send \$2.00 or 4 IRC's for overseas mailing)

- Order by phone or mail Add \$3 S & H per order (Electronic answering service evenings & weekends)
- Use VISA, MASTERCARD, Check, or UPS COD.

LOW-NOISE PREAMPS

the Price Barrier! \*

Hamtronics Breaks

No Need to Pay \$80 to \$125 for a GaAs FET Preamp.

#### FEATURES:

· Very Low Noise: 0.7 dB VHF, 0.8 dB UHF

High Gain: 18 to 28 dB, Depending on Freq.

MODEL	TUNES RANGE	PRICE
LNG-28	26-30 MHz	\$49
LNG-50	46-56 MHz	\$49
LNG-144	137-150 MHz	\$49
LNG-160	150-172 MHz	\$49
LNG-220	210-230 MHz	\$49
LNG-432	400-470 MHz	\$49
LNG-800	800-960 MHz	\$49


#### HELICAL RESONATOR PREAMPS

Low-noise pream helical resonat duce intermo cross-band inter in critical applic 12dB gain.

nps with	10-170-0-
tors re-	
d and	
ference	1 PC
cations.	C- Offering

Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49
HRA-220	213-233 MHz	\$49
HRA-432	420-450 MHz	\$59
HRA-()	150-174 MHz	\$54
HRA-( )	450-470 MHz	\$64
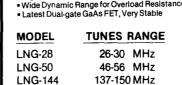
## Wide Dynamic Range for Overload Resistance Latest Dual-gate GaAs FET, Very Stable



#### FEATURES: SENSITIVITY SECOND TO NONE; O.15 uV (VHF), 0.2 uV (UHF) TYP. SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE XTAL FILTER

- & CERAMIC FILTER FOR > 100 dB AT ± 12KHZ. HELICAL RESON-ATOR FRONT ENDS TO FIGHT DESENSE & INTERMOD.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMIT-TERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY TUNE TRANSMITTER; UP TO 20 WATTS OUT (UP TO 50W WITH OPTIONAL PA).

\$980

#### **RECEIVING CONVERTERS**

440

\$780

Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.

	<b>2</b>	Antenna Input Range	Receiver Output
	A Carton and	28-32	144-148
hanitronics MCEVING CC	NVERTER	50-52	28-30
K11 .	7	50-54	144-148
		144-146	28-30
		145-147	28-30
		144-144.4	27-27.4
-		146-148	28-30
VUE NODELS		144-148	50-54
VHF MODELS		220-222	28-30
Kit with Case	\$49	220-224	144-148
Less Case	\$39	222-226	144-148
		220-224	50-54
Wired	\$69	222-224	28-30
UHF MODELS		432-434	28-30
Kit with Case	\$59	435-437	28-30
	+	432-436	144-148
Less Case	\$49	432-436	50-54
Wired	\$75	439.25	61.25


SCANNER CONVERTERS Copy 806 MHz band on any scanner. Wired/tested ONLY \$88.

#### **TRANSMIT CONVERTERS**


For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 Watts output vhf, 1 Watt uhf.

ForVHF	Exciter Input Range	Antenna Output
For VHF, Model XV2 Kit \$79 Wired \$149 (Specify band)	28-30 28-29 28-30 27-27.4 28-30 50-54 144-146 50-54 144-146	144-146 145-146 50-52 144-144.4 220-222* 220-224 50-52 144-148 28-30
For UHF, Model XV4 Kit \$99 Wired \$169	28-30 28-30 50-54 61.25 144-148	25-30 432-434 435-437 432-436 439.25 432-436* :20 for 2M input

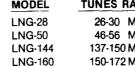VHF & UHF LINEAR AMPLIFIERS. Use with above. Power levels from 10 to 45 Watts. Several models, kits from \$78.





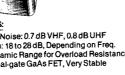




hamlronics, inc. 65-E MOUL ROAD • HILTON NY 14468 Phone: 716-392-9430

Hamtronics® is a registered trademark

118

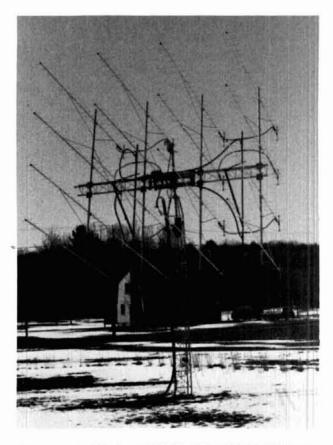

Sixteen stacked Cushcraft 424B Yagis in a 432-MHz EME array.

sidelobes down 12.3 dB at a spacing of 52 inches (1.32 meters). Considering that the 424B has an appreciably narrower H-plane beamwidth (22 inches versus 26 inches) and that it has more gain (15.8 dBd versus 15.1 dBd), just the opposite might be expected. The explanation again lies in the patterns of the individual antennas. Figures 14 and 15 are computer-generated patterns for the RIW19 and the 424B. The RIW19 has, in general, sidelobes significantly lower than the 424B which would explain the different spacings for best array sidelobe levels. This effect has been noted in other Yagis also, and unfortunately makes most of the methods of calculating stacking distances (such as the aperture equations, or any of the various beamwidth formulas) of little use when array temperature is of concern. I spent a considerable amount of time trying to come up with a clever little formula for calculating stacking distances, but every one I tried had more Yagis disobey its numbers than ones that would.

This causes the optimum stacking distances to be different for different Yagis *even if they have the same gain*. Likewise a Yagi with a very clean pattern may have an optimum stacking distance greater than another with more gain but a poorer pattern. Keep in mind that "optimum" has, in this case, been defined as the highest G/T ratio.

#### mounting different frequency antennas on the same tower

The effect of having antennas for different bands located in close proximity has not received much attention. The interaction between antennas can be understood by looking again at fig. 1. If another antenna is located in the shadow of the first, it will not be able to extract as much energy as the first simply because the field strength is reduced behind the first antenna. To quantify the effect of having different antennas located nearby can be complicated. To evaluate the effect of a 144-MHz antenna on a nearby 432-MHz antenna, the aperture of the 144-MHz antenna at 432 MHz would have to be calculated in order to see how much of the capture areas overlapped. Next it would have to be determined who had "first dibs" on the signal or which antenna was in the other's shadow.

The only conclusive measurement I have been able to make has been to measure the Sun noise of a given array by itself and then add the other antennas and again measure Sun noise. I have found a consistent degradation in Sun noise by having arrays interlaced. Surprisingly, in most cases it is the lower frequency array that suffers. A side effect also appears to be the occurrence of stray sidelobes. The explanation of that phenomenon is that the unused antenna is re-radiating signals it had captured. Although not conclusive, terminating the unused antennas in a 50-ohm load appears to minimize the effect.

To be on the safe side, antennas should be located such that their apertures do not overlap. This can sometimes lead to very large spacings. As a practical matter the casual VHF/UHF operator may never see the performance degradation. The EME operator or enthusiastic weak signal worker who is looking for the last bit of performance is advised to either not mix arrays or to maintain sufficient spacing between them.

#### alternate stacking arrangements

This article has addressed only arrays with the Yagis arranged in uniform rows and columns. It may be possible to obtain additional stacking gain while controlling sidelobes by using other arrangements such as circle or diamond configurations. This would be due to the lower amount of aperture overlap required for sidelobe level control. I have not examined these alternative arrangements because of the difficulty in adapting them to an array with elevation control.

#### conclusions

Since most readers are likely to be more interested in a guide to how far apart to stack various antennas than in duplicating my work, **table 2** is provided. It covers a number of popular 144 MHz and 432 MHz antennas and their recommended stacking distances.

table 2. Measured performance of 144 and 432 MHz antennas.							
144 MHz ANTENNAS							
ANTENNA	GAIN	PATTERN	BOOML	ENGTH	SIDEL	OBES	STACKING
TYPE	dBd	ЕхH		feet	ExH		feet E x H
6 el NBS	10.2 a	40 x 42	1.2	8.2	17	9	9.6 x 7.5
9 el F9FT	10.6	38 x 46	1.6	10.9	18	14	9.9 x 7.0
11 el Swan/KLM	10.8	40 x 44	1.8	12.3	13	10	9.6 x 7.5
11 el Cushcraft	10.8 Б	40 x 46	1.7	11.8	19	13	10.0 x 7.5
12 el Swan/KLM		36 x 40	2.0	14.1	14	10	10.6 × 8.6
14 el Swan/KLM		34 x 37	2.5	17.4	15	10	$11.0 \times 9.5$
20 el CC Colin		45 x 26					9.8 × 13.2
14 el Hy-Gain		35 x 35	2.3	15.5			11.0 x 9.9
12 el NBS		34 x 36	2.2	15.0	15	11	$11.0 \times 9.6$
14 el Cushcraft		34 x 36	2.2	15.0	15	12	$11.2 \times 9.6$
16 el KLM		29 x 31	2.2 3.0	20.7	12	9	$11.2 \times 7.8$ $11.4 \times 9.6$
			2.3				
11 el KLM 11X		34 x 38	2.9 3.0	15.3	19	14	$11.5 \times 9.9$ $12.2 \times 10.2$
16 el F9FT		32 x 34		20.8	17	13 12	$12.2 \times 10.2$ 12.4 × 10.2
11 el LUNAR	12.6 c,g		2.6	17.4	16		
13 el KLM LBA		31 x 32 30 x 32	3.1	21.5	14	10	$12.7 \times 10.6$ $12.8 \times 10.7$
15 el Cue Dee			3.1	21.3			
17 el NBS		28 x 33	3.2	22.0	13	10	$13.0 \times 10.4$
19 el Cushcraft		28 x 33	3.2	22.0	14	11	$13.0 \times 10.5$
13 el W2NLY		27 x 29	3.5	23.5	12	9	$13.3 \times 11.2$
15 el Telrex		26 x 28	4.1	27.8	12	9	$13.3 \times 11.3$
14 el K1FO		29 x 31	3.6	24.3	15	13	$13.7 \times 11.2$
15 el NBS		26 × 29	4.2	28.7	14	11	13.7 x 11.4
16 el KLM LBX		28 × 30	4.1	28.1	17	14	$13.8 \times 11.6$
18 el Cushcraft	14.5	27 X 28	4.2	28.7	15	12	14.0 × 11.8
		432 MHz	ANTENN	IAS			
TYPE	dBd	ЕхН		feet	ЕхН	~dB	inches
11 el Tilton	11.8 f,g		2.6	6.0	17	13	46 x 40
13 el W6QKI		27 × 29	3.4	7.8	12	9	53 x 44
13 el K2RIW		27 x 29	3.4	7.8	13	10	54 x 45
15 el NBS		26 x 29	4.2	9.6	14	11	55 x 46
16 el KLM LB		24 x 25	5.3	12.0	11	9	56 x 48
19 el K2RIW	15.1	24 x 26	5.6	12.8	16	14	60 x 54
21 el F9FT	15.2 h	24 × 26	6.6	15.0	14	12	58 x 52
26 el DL9KR	15.5 u,i	24 × 25	6.1	13.8	17	15	62 x 58
24 el Cushcraft	15.8	$20 \times 21$	7.5	17.1	12	10	62 x 50
22 el DL6WU	15.8 u,l	23 x 24	6.9	15.6	15	14	64 x 58
24 el K1FO		22 × 23	7.5	17.2	16	15	66 x 60
28 el W1JR/DL6WU	17.0 u	20 x 21	9.3	21.1	14	13	70 x 64
30 el KLM LBX	17.3 u	19 x 20	9.6	21.9	15	13	72 x 66
31 el W1JR∕DL6WU	17.5 u	19 × 20	10.4	23.7	14	13	74 x 68
a These NBS yag b Gain peak is i c Has incorrect d Figures are fo f Is tuned to 4 g Design based o h Is designed fo i Uses 8 element k Is a modified l Is designed fo u Design based o	11.1 dBd a balun len or 0.125 i 40 MHz. Re on Greenbl or 435 MHz t screen r 424B usin or 435 MHz	t 146 MHz, ogth. With nch taper tuned to 43 um / Tiltor Gain peak eflector. g a single Gain peak	38 x 4 stock version 32 MHz infor ( is 15 reflec ( is 16	4 degree balun ga with 20 gain wou mation. .5 dBd a tor and	patter in is 1 in. re ld be 1 t 436 M 22 dire	rn. 12.4 dBd sflector 12.6 dBd 1Hz. sctors.	spacing

Although a few tenths of a dB additional gain may be obtainable at larger spacings, the added size, weight, and windload would most likely not justify the wider spacing even if EME or satellite communications are not anticipated.

It should be emphasized that gain alone does not

tell the whole story. A Yagi with a cleaner pattern may be a better choice for an EME array than one with higher gain and a "messy" pattern. The highest gain Yagi in the world is of little use if it splits into 5 pieces the first time a storm passes by.

Finally, the following summary should serve as a guideline in building multiple Yagi arrays:

 Optimum stacking distance is a compromise between gain increase and sidelobe level (G/T).

 Array – 3 dB beamwidth will be equal to single element beamwidth divided by the number of elements in a plane when the first sidelobes are -14 to 15 dB. This usually represents optimum stacking or best G/T.

 The H-plane's inherently less directive pattern requires substantially closer spacing than the E-plane to achieve optimum sidelobe levels.

 Negating phasing line losses, doubling the number of elements in an array at optimum spacing will give approximately 2.7 to 2.8 dB gain increase in the E-plane and 2.5 to 2.6 dB in the H-plane.

 The greater the number of elements in an array, the more critical it is to have that array optimally spaced.

 The higher the frequency of operation, the more critical it is to have an array with small sidelobes (i.e. optimally stacked).

 The cleaner the pattern of an individual Yagi, the greater the optimum stacking distance will be - hence the greater the array gain.

· Although spacings closer than the maximum gain distance can cause the loss of a few tenths of a dB in array gain, the closer spacing can result in several dB of signal-to-noise ratio improvement on receive.

 If you are going to make a mistake, put your antennas "too close together" rather than "too far apart."

· Placing different band antennas in close proximity can degrade performance.

#### references

1. Jim Kennedy, K6MIO, "The Real Meaning of Noise Figure," ham radio, March, 1969, page 26.

2. "Reference Data for Radio Engineers," Howard W. Sams & Co., Inc., New York, Sixth Edition, 1975, pages 29-1 to 29-6.

3. John D. Kraus, "Antennas," McGraw-Hill Book Company, New York, NY, 1950, pages 41-56.

4. William I. Orr, W6SAI, and H.G. Johnson, W6QKI, VHF Handbook, Radio Publications, Inc., Wilton, Connecticut, 1956, pages 91 to 96.

5. Gunter Hoch, DL6WU, "More Gain With Yagi Antennas," VHF Communications, April, 1977, pages 204 to 206.

6. Jerry Haigwood, KY4Z, "A Digital Readout Antenna Position Indicator," The Lunar Letter, March, 1983, pages 11 and 12.

7. Peter Viezbicke, WØNXB, "Yagi Antenna Design," NBS Technical Note 688, U.S. Department of Commerce, Washington, D.C., December, 1976, pages 6 and 11

8. William L. Smith, W3GKP, "On Decibels and Noise," QST, January, 1968, pages 34 to 36

9. D.W. Bray, K2LMG, and P.H. Kirchner, W2YBP, "Antenna Patterns from the Sun," QST, July, 1960, page 11.

ham radio

## Two great ways to get O5 copy Ask:

G4HUW **KB5DN** K61MV KJ2E K4XG K8MKH KA4CFF KBØTM KA5DXY W4YPL

WA4FNP WD5DMP WD4BKY WD8QHD WD4CCI WB9NOV WD4CCZ WD9DYR W5GAI

#### 444D SSB/FM **Base-Station Microphone**

Shure's most widely used basestation microphone is a ham favorite because it really helps you get through ... with switchselectable dual impedance low and high for compatibility with any rig! VOX/NORMAL switch and continuous-on capability make the 444D easy to use even under tough NB 9XYZ conditions. If vou're after more Q5's, you should check it out.

> 526T Series II SUPER PUNCH Microphone


Truly a microphone and a half! Variable output that lets you adjust the level to match the system. The perfect match for virtually any transceiver made, regardless of impedance. Turns mobile-NBFM unit into an indoor base station! Super for SSB operation, too. These and many other features make the 526T Series II a must-try unit.

FREE! Amateur Radio Microphone Selector Folder. Write for AL645.


THE SOUND OF THE PROFESSIONALS ... WORLDWIDE Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204

		Λ			P. O. Box 280298 D	allas, Texas 75228
	5.			MICRO	(214) 271-5546	
		V	U			
	74L	9		EPROM	8000	SOCKETS
LS00	.20	LS163	.45	2708 1KX8 450 n.s	Z8002 20.00 8085 4.75	Low Profile SOLDER TAIL
LS01	.20	LS164	.65	2758 1KX8 +5V 450 n.s 2.00	8035 4.50 8086-2 24.95	6 Pin 14/1.00
LS02 LS03	.20	LS165	.90 .99	2716 2KX8	8039 4.50 8087-3 149.00 8080A 1.25 8088 15.00	8 Pin 13/1.00
LS03	.20 .20	LS166 LS169	1.25	450 n.s. 3.20	8200	14 Pin 10/1.00 16 Pin 8/1.00
LS05	.20	LS174	.45	2716-1 2KX8 350 n.s. 4.95	8202A 10.00 8255-5 5.00	18 Pin 8/1.00
LS08 LS09	.20 .20	LS175 LS181	.40 1.50	2732 4KX8 450 n.s. 4.00 2732A 5.50	D8203-1 29.95 8257 6.00 8212 1.50 8259A 3.50	20 Pin 7/1.00 22 Pin 7/1.00
LS10	.20	LS191	.90	2732A-35 4.75	8214 2.00 8259C-5 5.00	24 Pin 6/1.00
LS11 LS12	.20	LS192 LS193	.80 .80	2532 4KX8 450 n.s. 3.00	8216 1.75 8275 14.95 8228 3.25 8279-5 5.75	28 Pin 6/1.00
LS12	.35 .40	LS193	.65	2764-25	8237-5 7.50 8284 3.20	40 Pin 5/1.00
LS14	.40	LS195	.60	27128-25 10.00	8250B 9.95 8287 5.75 8251 4.20 8288 7.50	BUY \$10
LS15 LS20	.32 .20	LS196 LS197	.70 .85	27128-3	8253-5 6.75	GET \$1.00 - FREE CHOICE
LS21	.25	LS221	.65		<b>Z80</b>	2114 SPECIAL!
LS27 LS30	.28 .20	LS240 LS241	1.00 .80	EPROM SPECIAL	Z80 2.5 MHZ CPU	COMPUTER
LS32	.25	LS242	1.00	We bought a large quantity of 2708s from a computer manufacturer who	Z80DMA-DMA	MANUFACTURERS
LS33 LS37	.40 .33	LS243 LS244	1.00 1.00	redesigned their boards. We	Z80PIO	EXCESS INVENTORY
LS38	.30	LS245	1.00	removed them from sockets, erased	Z80A-4MHZ CPU 1.99	SALE! PRIME! 2114-300 n.s.
LS42 LS51	.40 .24	LS251 LS253	.50 .50	and verified them, and now we offer the savings to you. Complete	Z80A-CTC 1.99 Z80A DART 7.50	INCREDIBLE PRICE
LS51	.24 .25	LS253	.50	satisfaction guaranteed.	Z80A-DMA 9.00 Z80A-PIO 1.99	YOU SAVE!
L\$55	.24	LS258	.55	2708	Z80A SIO/O 5.99	8/\$8.00 GUARANTEED
LS73 LS74	.35 .30	LS259 LS260	2.00 . .50	\$1.49 or 10/\$12.00	Z80B 6 MHZ CPU 7.95	
LS85	.60	LS266	.40	STATIC RAM	F.D. CONTROLLERS	CRYSTALS
LS86 LS90	.25 .50	LS273 LS279	1.00 .40	2016-2KX8 200 n.s 8/20.00	1771 Single Density 12.95	32.768 Khz SPECIAL
LS90	.50	LS280	1.00	2101-1 - 256X4 500 n.s	1791 Double Density 20.00 1793 Special 12.50	262.144
LS107	.37	LS283	.50	21L02-1 350 n.s	1797 17.50	300.000
LS109	.25 .30	LS290 LS293	.85 .85	2111-1 256X4 500 n.s 2.00	2793	1.5432 Mhz
LS122	.45	LS298	.75	2114L-3 1KX4 300 n.s 1.50 8/10.00		2.000000 2.49
LS123 LS124	.55 2.75	LS299 LS323	1.60 2.60	2125A-2 1KX1 70 n.s 2.20	CONTROLLER SET	2.560
LS125	.40	LS348	.75	2142-3 1KX4 300 n.s 1.50	THREE CHIP SET	3.120 1.20
LS126 LS132	.49 .50	LS364 LS366	1.10 .45	2147 4KX1 3.95 TMS4044 (MCM6641 C-25)	1797 or 1793, 2143-03, 1691	3.2
LS132	.30	LS360 LS367	.45	4KX1 250 n.s	by W.D. Compare at up to 86.85.	3.579545
LS138	.45	LS368	.40	6116P-4-2KX8	B.G. SPECIAL	4.000 1.75
LS139 LS151	.40 .45	LS373 LS374	1.00 1.00	200 n.s. CMOS 8/20.00	All 3 for only \$22.95	4.194304 1.50 4.433618
LS153	.50	LS375	.50	4K STATIC RAMS	UART	4444.000 1.25
LS154 LS155	1.20 .50	LS377 LS378	1.00 .85	LESS THAN 50¢ EACH		4.9152 2.49 4.916 Bd. Rate 1.25
LS155	.50	LS390	1.00	MK4104J-4 - 250 N.S. 18 Pin	TR1602B (COM 2017) 1.75 IM6402-(1863)+5v High speed	5.000000
LS157	.40	LS393	1.00	Ceramic Computer Mfg. Surplus, PRIME, Fully Static.	AY5-1013 pin out 2.95	5.0688 2.50
LS158 LS160	.50 .65	LS399 LS670	1.25 1.50	Easy to Use. Has Same Pin Out	INS 8250B 9.95	5.616
LS161	.50	25LS2569	3.00	as TMS4044, but slightly	6800	6.176 1.49
LS162	.65			different timing. With Specs. (Mostek)	6800 2.50 6840 10.00 6802 3.50 6845P 7.50	7.164112
	TI			8 for 5.00 32 for 15.95	6803 5.00 6845S 7.50	8.000 1.49
7400	.22 7472	.25 74161	.60	VERY LOW POWER!	6809EP 3.99 6850 2.60 6810 2.00 68A09EP 4.99	9.000 1.49 9.90000 1.25
	.22 7473			DYNAMIC PAM	6820 3.25 68A21 3.00	10.69425 2.50
	.22 7474			DYNAMIC RAM	6821 2.00 68B45 10.00	10.8864 1.49 10.920 1.49
	.33 7483 .33 7485			2108-4 8KX1 1.50 2118-4 16KX1-5Volt 1.50	6500	11.088 1.59
	.24 7486			4027-4KX1-250 n.s	6502 2.60 6545 5.00 6522 6.95 6551 5.00	12.000
	.19 7490			4116-16KX1-250 n.s. 8/6.00		13.440 1.00 14.31818 1.00
	.33 7493			4116-16KX1-200 n.s 8/7.00 4116 16KX1-150 n.s 8/10.00	SPECIALS	15.2 1.10
7420	.22 7496	40 74175		4164- +5v 64K 200 n.s 8/16.00	9216 4.95	16.00000 1.50 16.5888 1.49
	.25 74109			4164 150 n.s 8/18.00 TMS4416-16KX4-150 n.s 3.95	ТМ599532 19.95	17.430 2.49
7428	.25 74121	.27 74192	70	MK4516-15 16KX1-50 n.s 3.95	BR1941L	18.000
	.20 74123			5280N-5 (2107B-4 • TMS4060)	LF356	18.4320 1.49
	.27 74125			4KX1	TL494	20.000
	.19 74148				9401	22.092 1.00
7442	.40 74151		1.75	SPECIAL	MC4024P 2.50	32.000 2.49
	.65 74153			AY3-8910	NE592	40.000
	.20 74154			W/60 Page Manual New Price \$7.00	LM2917 1.00	91.000 1.00
	.22 74157			58321 Clock-Calendar	LM339	104.8 1.00
					ver \$50,00 add 850 for insurance. No C/O.D	Torne Beg. add6 1 /8º Tex 90 Day Monay

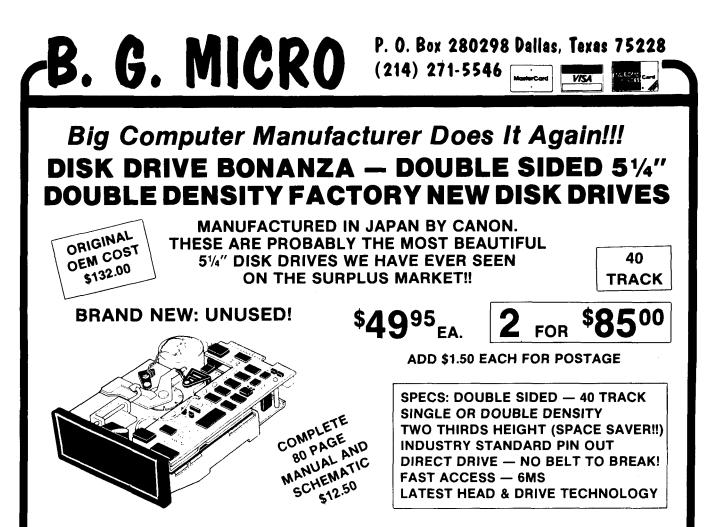TERMS: (Unless specified elsewhere) Add \$1.50 postage, we pay balance. Orders over \$50,00 add 85¢ for insurance. No C.O.D. Texas Res. add 6-1 / 8% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico, Countries other Than Canada, add \$3.50 shipping and handling.



The same poor purchasing agent who nearly got lynched for over buying so many D.C. switchers has gotten carried away again. The Big Boss found another hiding place crammed with a truckload of the brand new precision manufactured 5<sup>1</sup>/<sub>4</sub>" disk drives. Fortunately for us, the Big Boss remembered us from the switchers deal and he gave us an opportunity to make the "Second Best" surplus buy of the decade. Even though we bought a huge quantity, please order early to avoid disappointment. Please do not confuse these sleek, 2/3 height, high quality Japanese disk drives with the flimsy domestic units sold by others.

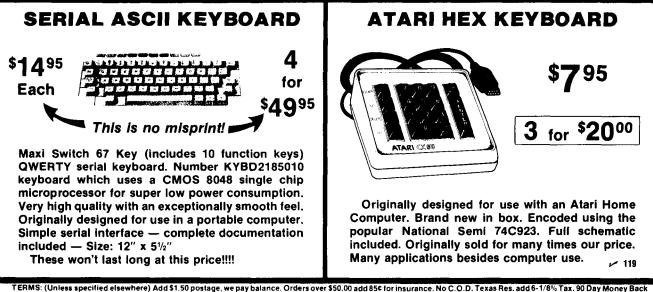

TERMS: (Unless specified elsewhere) Add \$1.50 postage, we pay balance. Orders over \$50.00 add 85¢ for insurance. No C.O.D. Texas Res. add 6-1/8% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico. Countries other than Canada, add \$3.50 shipping and handling.



## active antenna covers 0.5-30 MHz


Double duty allows 2-meter operation as well

Active antennas have been available commercially for several years, but relatively little practical information about them has appeared in the Amateur journals.<sup>1,2</sup> This article illustrates how to build a simple one covering from 500 kHz to at least 30 MHz using commonly available components. As an added bonus, the antenna works as an omnidirectional 2-meter antenna when not in use for HF reception. It will also meet the needs of SWL's for casual monitoring on the HF bands.

First, some clarification is in order. True active antennas (sometimes referred to as voltage probe antennas) use circuitry somewhat more sophisticated than what is presented here.<sup>3</sup> Antenna probe lengths of 2 inches have been used in some commercial models intended for military markets. Their circuitry does not match impedances in the usual sense, as does the simple approach used here.3.4 Instead, their reactive components are made small in comparison to the extremely high source-follower FET input impedance, effectively swamping out the reactive component. A short probe antenna, at the lower HF frequencies, may have a capacitive reactance in the millions of ohms, while its effective radiation resistance is only a very small fraction of an ohm.<sup>2</sup> Despite its lack of eloguence the antenna presented here works well, and can be built in a weekend for very little cost.

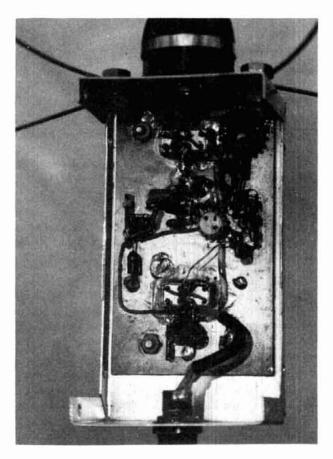
### general coverage antenna needed

Amateur Radio manufacturers have caught on to the market for general-coverage reception — today many transceivers will receive from the lower LF ranges continuously up to 30 MHz and beyond. While the benefits of general-coverage receivers are obvious, some problems await those seeking a single antenna capable of spanning several octaves. The simple link-coupled LC preselector circuits used in vintage tube-type receivers were capable of matching to a wide variety of loads, and an "antenna" tuning control served in tweaking the most out of any antenna. But the situation is somewhat different today. Modern receivers are carefully designed for proper gain distribution. The tracking preselectors and high-gain front ends are gone; in their place are mod-



Internal view of unit shows the construction details of the active antenna. The ASP-677 commercial antenna was used. Because of the softness of the minibox aluminum, the 3/8-inch snap-mount washer was removed and installed on the inside wall of the minibox. This washer is part of the ASP snap-mount assembly.

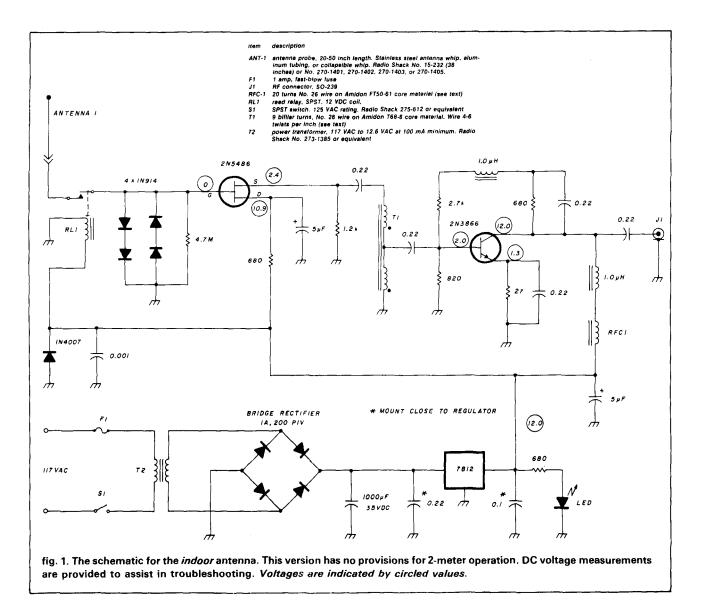By Peter J. Bertini, K1ZJH, 20 Patsun Road, Somers, Connecticut 06071




ern electronically-switched broadband filters. But these filters are not tolerant. If the load is not 50 ohms, their performance is no longer predictable and losses can become excessive. Consider the use of an 80meter antenna for shortwave reception in the 40-meter region. An 80-meter dipole at 40 meters is virtually unusable because as the feedpoint impedance soars to a very high value the shunt capacity of the coax greatly attenuates incoming signals.

### impedance transformation needed

Did you ever wonder how an automobile's AM antenna could work effectively on FM and yet be so short? The answer lies in the special high-impedance coax and special front-end design used in these receivers. (If you've ever tried to replace this coax with a length of RG-58 you've quickly learned a lesson in capacitive losses.)

If a short antenna will work at 550 kHz, it will work elsewhere as well. All that's needed is an impedance transformation network to change the extremely high termination impedance of our short "probe" antenna into a usable 50-ohm impedance for our receiver, across a range of several octaves. The size of an antenna has little bearing on its performance — full-size antennas do offer 50-ohm feedpoint impedances and low enough resistance losses to allow efficient RF radiation.<sup>5</sup> For receiving applications, many Amateurs have found that antennas such as the Beverage, ferrite-loop, and active antenna often out-perform fullsize transmitting antenna arrays because of their lower susceptibility to noise pickup — and in some cases, their excellent directivity in the lower HF regions.

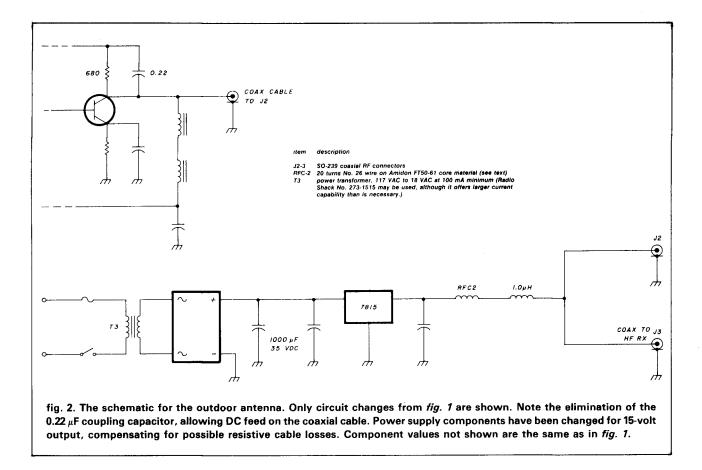A JFET source-follower stage provides the desired high-to-low impedance transformation. (While a 2N5486 was used here, an MPF102 will also work.)



The antenna is a length of wire, about 48 inches (1.22 meters) long. A length of stainless-steel wire salvaged from an old VHF whip or automobile antenna or even a section of aluminum tubing may be used for the antenna probe.

Two versions of this antenna were built and tested; one was designed for indoor use and the other for outdoor mounting. The indoor unit was built in a small enclosure. The exact dimensions are not critical, providing all components can be comfortably mounted inside. The only difference between the indoor and outdoor models is in the packaging — the outdoor model uses a remote weather-proof housing for the preamp and antenna probe. Everything is self-contained in the indoor version.

Referring to **fig. 1**, for the schematic for the indoor model, note the back-to-back diode protection from the JFET gate to ground. I found that the static discharge generated from shuffling across the shack floor was responsible for the untimely demise of several 2N5486 devices before I realized what was going on. These diodes do not guarantee total protection — the best safeguard is to avoid touching the antenna probe. To prevent generation of an insidious form of TVI in the outdoor antenna caused by diode rectification of RF radiated from nearby HF or VHF transmitters, a small reed relay is used to disconnect the antenna probe from the preamp stages when the antenna is not in use. This also offers some protection to the JFET during electrical storms, when static charges might build up on the antenna. The reed relay should be used in the indoor model as well for protection against static discharges. The reed relay is used only in the HF model — for 2-meter operation a more involved switching scheme using DPDT relays is needed. (This will be addressed in greater detail below).

The schematic shown in **fig. 2** serves as the basis for the outdoor HF active antenna. The only difference is in the power feed arrangement. In the outdoor model, power for the preamp head is fed through the coax from the indoor power supply.

### additional gain needed

Following the JFET device, which does not provide voltage gain, is a class-A bipolar stage using a 2N3866 transistor. (A 2N5109 could be used here instead.) "Hotter" transistors such as the TRW LT1001 might offer some improvement, especially at higher frequencies, but they might also require some circuit revisions to prevent self-oscillation. This stage does provide gain, building up the very small signals captured by the short antenna. The transistor must be heatsunk; the stage draws about 25 mA resulting in considerable

## "I LEFT PLACES WITHOUT POWER FOR MAN TO CREATE"

And the people at Photocomm are creating this needed power. Their solution is being the best in Photovoltaic engineering and design to service all your remote electrical energy needs from design to installation in a multitude of areas:


- Telecommunications
- Navigational Aids
- Water Pumping
- Railroad Signalling
- Cathodic Protection

Photocomm has the total service and professionalism that those of higher authority demand.



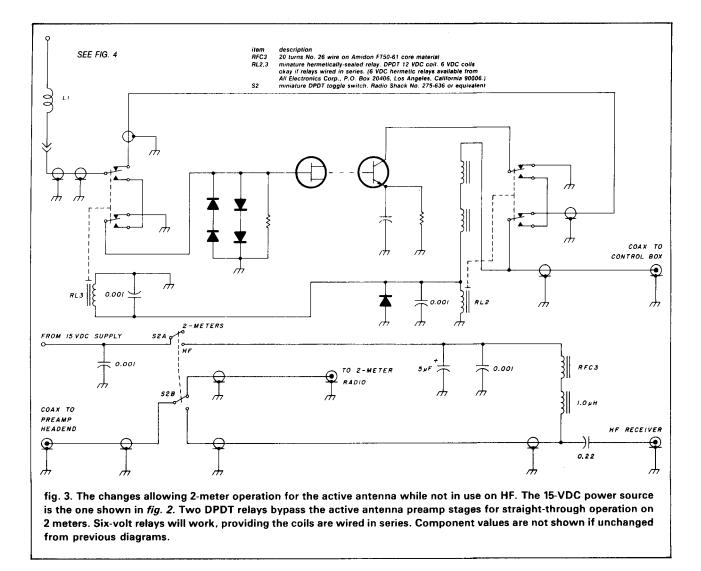PHOTOCOMM INC. PHOTOVOLTAIC SYSTEMS 7735 E. Redfield Rd. Scottsdale, AZ 85260 (602) 948-8003 TELEX 6835043






device dissipation. Shunt feedback sets the stage gain and insures stable operation. A series choke in the feedback network allows greater gain at higher frequencies, this is necessary because the  $f_T$  (the gainbandwidth product, or the frequency at which the current gain reduces to unity) of the 2N3866 is only 500 MHz. A broadband interstage matching transformer is used between the source follower and bipolar amplifier. Using 20 bifilar turns allows enough inductive reactance for operation through the AM broadcast band. If AM broadcast band coverage is not desired, the windings may be reduced to nine bifilar turns. This will cause gain to start rolling off below 1800 kHz, while yielding a slight improvement above 30 MHz.

All models were constructed and tested using pointto-point wiring techniques on double-sided PC board material. Phenolic soldering strips provide the mechanical support needed for components and wiring. While the results are not overly photogenic, the circuit works as intended. Etched printed-circuit construction is not needed here. The outdoor model works best.<sup>1</sup> Mounted high and in the clear, it is not subjected to the man-made noises carried and radiated on the home's wiring. Many common home appliances will generate copious amounts of broadband hash across the HF spectrum: vacuum cleaners, television horizontal-sweep circuits, fluorescent lights, light dimmers, computers, and numerous other devices will cause grief for the serious HF operator. While the antenna can be side-mounted to an existing tower leg, it is best to mount it away from nearby metal objects. If at all possible the antenna should be top-mounted on the tower masting. Leadin coax can be either RG-59 or RG-58 type cable. RG-8 coaxial cable can be used with the outdoor combination 2-meter/HF model to limit the VHF losses.
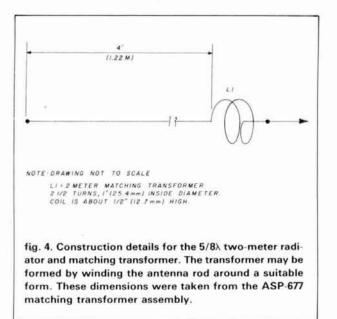
### use for 2 meters as well

Since the antenna probe is 48 inches long, we have the basic foundation for a 5/8-wavelength vertically polarized antenna for 2 meters. All that's required is a matching transformer (**fig. 4**) to match the




5/8-wavelength radiator to 50 ohms. Given a length of stainless steel antenna rod, it is possible to make the coil and whip one continuous piece. A commercial 5/8-wavelength antenna, such as the Antenna Specialists model ASP-677, could serve here as well, and was my choice for my outdoor HF/VHF combination antenna. Note that the ASP whip is cut for about 46 inches (1.17 meters); this is because of the added length introduced by the spring assembly. *Half-wave* or 5/8-wavelength antenna designs using grounded, tapped matching transformers will not work. The extremely small inductances will short circuit HF signals.

Three or four ground radials are needed for the 2-meter/HF combination active antenna. These should be a little longer than a quarter-wavelength, 20-inch lengths of stainless steel antenna whip wire or aluminum tubing will serve here. SWR is adjusted by trimming the radiator length; 48 inches will be about optimum for the upper 2 MHz of the band. If trimming the antenna does not yield an SWR under 1.5 to 1, compressing or expanding the transformer coil should provide a good match. The radials must make good electrical contact to the metal enclosure housing the antenna. A Radio Shack catalog No. 270-238 mini-box houses my unit. Its 5-1/4 × 3 × 2-1/8 inch (13.34  $\times$  7.62  $\times$  5.52 cm) size is roomy enough to comfortably mount the preamp components. The PC board used for mounting the active antenna components must also make a good low-impedance RF ground connection to the enclosure. This provides the needed RF ground path for the 2-meter antenna. If the ASP antenna is used, a short length of RG-58 coax should be used between the 3/8-inch snap-mount and preamp changeover relay. Use short coax lead connections to the relay and ground.

Figure 3 outlines the electrical details for the dualpurpose antenna. Two miniature hermetically sealed relays are used to bypass the preamp stages, allowing straight-through operation for 2 meters when the power is removed from the antenna. Metal-can 6 VDC hermetic relays can be used, providing the coils are connected in series. Six-volt relays are often more easily available, and cheaper, than their 12-volt counterparts. A 1N4007 silicon power diode protects the amplifier from reversed supply voltages; and from the counter-EMF generated by the relay coils as power is removed. Depending on the length of coax used, the power supply voltage may have to be increased to compensate for voltage drops in the coax cable. The 2-meter version draws over 100 mA; at least 12 volts should be available at the antenna preamp.

Short leads are mandatory for good VHF operation. The straight-through 2-meter operation uses a short piece of coax cable between the relays. RG-174 is okay for this, but extremely short ground and center wire connections must be made at the relays. The shackmounted power supply unit should be as carefully constructed, to keep the losses at a minimum. Note the use of the DPDT switch; it does "double-duty" in switching the power to the antenna preamp and also changing the feedline between the HF receiver and

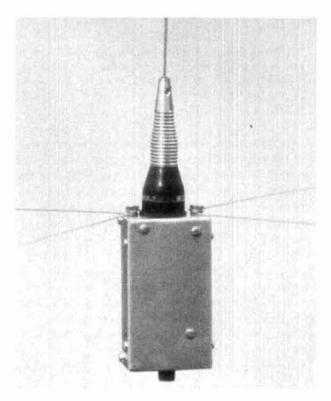

The finished dual-purpose active antenna. Note the installation of the 1/4-wave 2-meter radials. (See W6SAI's November, 1984, column in *ham radio* for a timely discussion on improving radial performance for 5/8-wave 2-meter antennas used in this fashion.)

2-meter FM rig. Very short leads are used for the coax connections at the switch terminals, avoiding severe impedance bumps at 146 MHz. Use care in soldering; overheating the center insulation may result in a short to the coax braid. The outdoor antenna enclosure should be weatherproofed. (Silicone bathroom caulk will do well for this purpose.) Be sure to allow for condensation; a small drain hole on the bottom of the enclosure is needed. Also spray the PC board and components with clear acrylic spray to prevent corrosion. Anti-moisture and fungicidal varnish, carried by some electronic suppliers, is what I used, and it is also ideal for sealing the coax connections after they have been taped.

#### what to expect

Although performance of either model is adequate for casual monitoring, it is difficult to evaluate these antennas unless an antenna test range equipped with full-size antennas for all of the frequencies involved is available. S-meter comparisons alone can be deceptive. A higher S-meter reading may be obtained with an active antenna with excessive internal gain, while the signal-to-noise ratio may be best on the comparison antenna. This lesson was demonstrated some years ago when I tried using an old RME preselector ahead of a 51J3 Collins receiver. Above 15 MHz the S-meter was very "busy". Switching off the preselector often dropped S-9 signals to an S-1 or less, even though the readability increased dramatically.

With the active antenna connected to your HF receiver and turned on, a slight increase in receiver noise should be heard. Disconnecting the whip antenna from the preamp should cause a noticeable reduction in receiver noise. This is a good indication that everything is working as it should. The gain of this active antenna is not as great as some commercial units I've used in the past. Do not expect signals to produce the same S-meter readings as a full-size antenna.

Some variations of the design are possible. SWL's with a need for coverage in the LF ranges below 550 kHz might consider eliminating the interstage matching transformer. However, without the matching transformer, 60-cycle cross-modulation from strong nearby AC powerline fields will be an annoying problem. This can be especially troublesome in the indoor model where the probe and preamplifier stages are near to the power transformer. The limiting factor for LF performance is the choke values used to isolate the DC supply voltages. They will have to be increased to allow operation below 500 kHz. There is no magic in the antenna probe length - antennas as short as 20 inches might prove adequate. The 48-inch length was selected to allow 5/8-wave 2-meter operation. An 18-inch (45.7 mm) probe could serve as a 1/4-wave

2-meter radiator and eliminate the need for the 2-meter matching transformer.

A few words of caution: the 2-meter antenna will handle about 25 watts. More than this invites damage to the 1- $\mu$ H chokes. When using the antenna on an HF transceiver, never transmit into the antenna. Always disconnect the mike and key and set the drive and mike controls at minimum *before* connecting to the active antenna!

There you have it, all in one package: an all-band HF antenna for SWL'ing on your transceiver and a 2-meter antenna for your FM rig. Considering the obstacles facing many Amateurs — lot size, restrictive zoning regulations, and unsympathetic landlords — this antenna will offer a lot of performance in a small, inexpensive and inconspicuous design.

#### references

1. Henry S. Keen, W5TRS, "Selective Receiving Antennas: A Progress Report," *ham radio*, May, 1978, page 20.

 Douglas Blakeslee, N1RM "A Very Short Receiving Antenna," Ham Radio Horizons, June, 1979, page 24.


 James R. Fisk, W1DTY, "Voltage-Probe Receiving Antenna," ham radio, October, 1970, page 20.

Robert Fischer, "Voltage Probe Antenna," *Kollmorgen Corporation Report ER848.1*, January 29, 1968, Kollmorgen Corporation, Northampton, Massachusetts 01060.

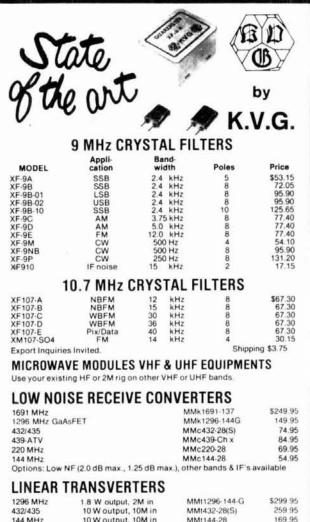5. James Kennedy, K6MIO, "Antennas and Capture Area," ham radio, November, 1969, page 42.







432/435	10 Woutput, 10M in	MM1432-28(S)	259
144 MHz	10 Woutput, 10M in	MM1144-28	169
Other bands &	k IFs available.		


### LINEAR DOWER AMPLIFIERS

LINEAK	PUWER A	MPLIFIE	KS	
1296 MHz	20 W o	utput	UP1296-20-L	439.95
432/435	100 W 0	utput	MML432-100	369.95
	50 W o	utput	MML432-50	199.95
	30 W o	utput	MML432-30-LS	209.95
144 MHz	200 W o	utput	MML144-200-S	374 95
	100 W 0	utput	MML144-100-LS	239.95
	50 W o		MML144-50-S	149.95
	30 W a	utput	MML144-30-LS	109.95
	or 3W drive, of	switching. hers 10W drive.	- 7	in
Shipping: FO	B Concord, Ma	55.	indext	aler.
ANTE	NNAS		every	100
	z MULTIBEA	MS	1	- 123
28 Element	70/MBM28 12		549	95- \$39.95
48 Element	70/MBM48 15		-75	75 59 95
88 Element	70/MBM88 18	3.5 dBd	-105	50 - 89 95
144-148 MH	7 LSI OTS			
8 over 8 Hor.		12 3 dBd		\$63.40
8 by 8 Vert p				79 95
10 + 10 Twis		11.3 dBd		69.95
UHF LOOP	VAGIS			
	z 29 loops 129	1 V 20 dBi		47.95
	z 29 loops 169			57.95
	agi connector e		Type N \$14.9	
0.00.2000				1
Send 40¢ (2 sta	mps) for full detail systal product requ	s of all your VHF & irrements	UHF equip	VISA
			(617) 26	63-2145
	and the second second		SPEC	TRUM
	<b>a</b> [11]	INITE	DNATIONA	I INC
		INIE	RNATIONA	L, INC.
	1 182	P	ost Office Bo	x 1084
		ALL AND		2011년 관계 원이
	4	Concor	d, MA 01742.	11 C A





# HE FIRST NAME IN LECTRONIC TEST GEAR

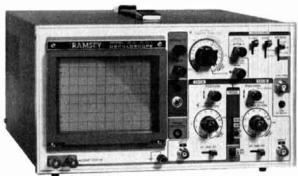

### 20 MHz DUAL TRACE OSCILLOSCOPE

**RAMSEY D-1100** 

.

۲

**VOM MULTITESTER** 

Compact and reliable, designed to service a wide variety of equipment. Features include \* mirror back scate \* double-jewieled precision moving coil \* double overload pro-tection \* an ideal low cost unit for the beginner or as a spare back-up unit.

\$1995 test leads and battery included

RAMSEY

.

EV) # /

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a com-ponent testing circuit for relistor, capacitor, digital circuit and diode testing + TV video sync filter + wide bandwidth & high sensitivity + in-ternal graticule + front panel trace rotator + 2 axis + high sensitivity + in-scy mode + regulated power supply + built-in calibrator + rock solid triggering. \*USA — add \$10.00 per runt for postage, overseas orders add 15% ed total order for insured surface mail.



### 45 MHz DUAL SWEEP OSCILLOSCOPE

The Remark 655 is a dual time base, defend sweep unit that includes a built in signal heavy faces type mice class viewed by derive year access in a time of built in the series instances includes evaluate trigger heads? • 20 calibrated sex to their sample from 0.5 acts, to 0.2 c3c5rd + shull y adjustable sevene (tries) evenes mice strateger to the sample trigger sources; CH1, CH2, LINE EXTernal and INTernal (V mode) • tring rease mice to CH1, and CH2 eventorms designed as single trice + sweep gass and sweep output - auto tocus + single seven 'USA — and strateger visited to 20 10.00 per trible or wall order to mixed suitable single seven. \$79995\*

「日本日本日日

11

...

uality

**NEW RAMSEY 1200** 

**VOM MULTITESTER** 

Check transistors, diodes and LEDs with this professional quality meter. Other features include, decibel scale • 20K volt metering system • 3x<sup>3</sup> mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case

\$2495 test leads and battery included



Digital ML MULLIMETER Reliable, accurate digital mea-surments at an amazingly low cost • in-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed inpul tacks • overload protection on all ranges • 3% digit LCD dis-play with auto zero, auto polarity 8 low BAT. indicator


\$4995 test leads and battery included



More Details? CHECK-OFF Page 166
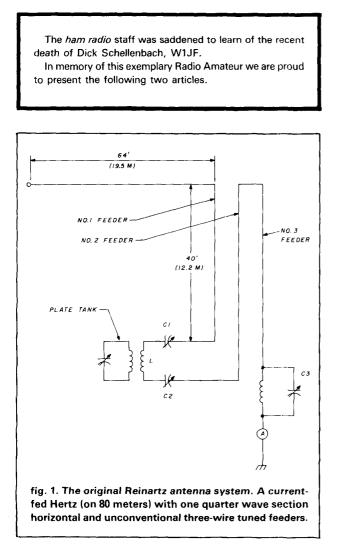
## control your take-off angle: the JR vari-lobe antenna

Dial in your skip distance and maximize your signals



Most Radio Amateurs, I'm sure, are guite familiar with the directional properties of simple halfwave antennas. In these antennas, the majority of radiation is broadside to the radiating element, in the case of a horizontal type antenna. Some Amateurs may be familiar with, or may have experienced, the effect of raising or lowering an antenna and have seen how its launch angle, as well as its impedance, was significantly affected by the change in height. In this respect, a lower angle of vertical radiation usually produces a stronger signal further out in distance than one that has an extremely high angle of radiation when the communication path is governed by sky waves. This path distance versus launch angle phenomenon is very noticeable on the lower frequency Amateur bands of 160, 80, and 40 meters, where both high and low angles of radiation are useful in radio communications.

Given the fact that a half-wave antenna generally radiates most of its signal broadside to the antenna, what would you think of a simple modification that would permit controlled selection of its radiation angle? This would allow the Amateur station to take advantage of the prevailing ionospheric conditions, night or day, and therefore enhance signals to and from a particular distant location. Such an antenna system *is* feasible.

The basic idea for the variable lobe system was developed fifty years ago by the legendary John L. Reinartz, W1QP.<sup>1</sup>

In developing this new concept and publishing the results of his experiments Reinartz discovered he truly had a multiband antenna system as well as one providing versatile radiation angle control allowing him to maximize signal strengths at different locations. Reinartz also found out he could compensate for timevarying propagation conditions, especially when the

By R.R. Schellenbach, W1JF, 12 Whitehall Lane, Reading, Massachusetts 01867

reflective layer was in the process of changing heights, thereby requiring a different radiation angle while he was communicating.

The ability to alter an antenna's vertical lobe characteristics is one solution to the thoughtprovoking question, why does it often seem that signal reports appear to differ drastically between individual stations, even when the stations are located only a few miles apart in the same general direction?


The causes for inconsistencies between signal reports include a myriad of possibilities such as polarization differences, vagaries of the ionospheric reflective layers, multi-hop propagation, launch radiation, and receiving station antenna angle differences, to name a few. Because of the large number of variables affecting sky-wave propagation, the solutions to these problems are complex. However, if a radio station possesses the capability to adjust to any potential condition, the inconsistencies are not at all important — only the corrective measure capability matters.

Reinartz recognized the same perplexing propagation differences between the station he worked and proposed that if he were to vary the vertical angle pattern of his antenna, he should maintain a maximum signal strength at both ends of the communication path. In his model, Reinartz developed an antenna system which is basically a simple current-fed Hertz type antenna with one guarter-wave horizontal section and another sixth-wave feeder section, the latter consisting of two normal operating feeders and a third, vertical wire carried into his ham shack for tuning and compensation control. The original Reinartz version of the controlled radiation angle antenna is shown in fig. 1. The model as shown, operating on the 80-meter band, proved to be capable of operating under vertical angle of radiation control at twice or even four times its fundamental design frequency.

In spite of the antenna's multiband capability, it was used primarily on the 80-meter band, where daily and seasonal propagation effects were more pronounced and allowed Reinartz to do a lot of experimentation during variable band conditions.
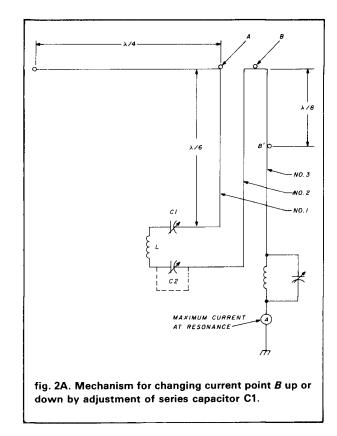
### how it works

Referring again to **fig. 1**, illustrating the original Reinartz antenna system, it should be mentioned that the variable capacitor C2 was found to be unnecessary in the 80-meter application and that all vertical angle lobe changing was affected by varying C1 while maintaining resonance of the parallel L/C network against ground for each particular operating frequency. Reinartz used an RF current reading ammeter to determine resonance in the third (vertical) feeder wire, but the meter is deemed unnecessary, as other means are available to determine proper resonance of the vertical wire section.



More details of the mechanism for changing the antenna's vertical field pattern is shown in figs. 2A and 2B, where on the 80-meter band these figures indicate the voltage and current distributions on the model and the method employed to change the radiating current points on the system. The horizontal wire section of the antenna in fig. 2A is only one-sixth wavelength above the ground and hence, most of its radiation is directed upward - a real "cloud burner." During nighttime conditions, for example, this pattern would produce strong local signals because of the high angle and short distance skip zone; if we were to move the current point from the top of feeder number 3 downward, however, then the radiation characteristic would be reversed and the antenna's radiation would become predominately low angle - good for DX.

The change in vertical radiation pattern with relationship to the RF current maximum point on the third (vertical) wire section is illustrated in **fig. 3**. As one may surmise, the third vertical wire section of the antenna functions to provide the vertically polarized and low angle lobe control for the system. By controlling the current distribution by altering capacitor C1 in the series tuning circuit of **fig. 2**, the Vari-Lobe antenna changes from a high vertical angle radiator to a low vertical angle radiator quite simply. When capacitor C1 is slowly tuned, the antenna's vertical pattern may be finely adjusted anywhere between the two extremes dipicted in **fig. 3**. This tuning control


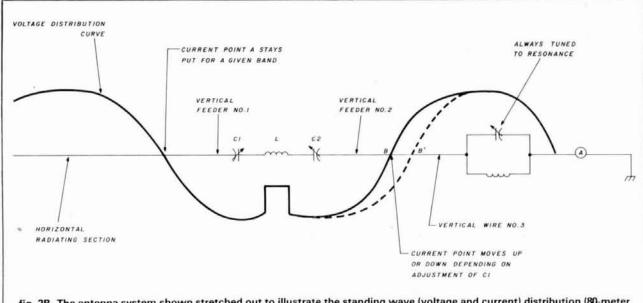


fig. 2B. The antenna system shown stretched out to illustrate the standing wave (voltage and current) distribution (80-meter example).

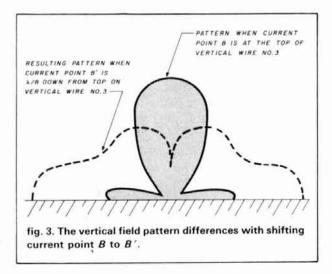

effectively allows the operator to "tune in" the required skip distance to another station for maximum signal strength. Large departures in current control by changes in capacitor C1 will require slight readjustment to the resonance of the parallel tuned circuit between the vertical section wire number 3 and ground.

According to tests by Reinartz in which he instrumented the vertical wire from top to bottom with small pilot lamps to indicate antenna current distributions, the further downward the current maximum was toward the one-eighth wavelength point, the greater the low angle effect and the further out the skip became.

It is interesting to note that Reinartz performed many of his early experiments and collected data on the shifting field strength patterns on the 10-meter band. Later, actual on-the-air tests using a full-scale 3.5 MHz (80 meter) model was used to communicate with a number of Amateurs up and down the east coast of the United States.

Concluding remarks by Reinartz indicate that his repeated tests showed that compensation for the advance of time from early evening to past midnight must be made by a change in the location of the maximum current point on the vertical section in order to maintain maximum signal strength at the receiving station. During daytime operation, he noticed that although there was one generally satisfactory setting of C1, slight changes could be made in the lobe adjustment to provide a maximum signal at some particular receiving station. He noticed too, that some stations were always consistent in the antenna's lobe setting for obtaining a maximum signal strength.

### a modern version of the JR antenna


By carrying Reinartz's ideas further and adding modern improvements, the JR Vari-Lobe antenna came into being. The new system offers more operating frequencies with ease of controlled radiation from either the ham shack or by remote control. The modern version is shown in **fig. 4** and its control section in **fig. 5**. I prefer the remote tuning method because it keeps the necessary radiating elements away from the surrounding objects such as houses, trees, telephone and power lines, etc. The JR Vari-Lobe antenna's performance could be adversely influenced by such local obstructions because the antenna is a relatively low height system and it utilizes low angle vertical polarization. As an additional feature of modernization, I incorporated a 15-meter "high gain" capability by using the "JF Array"<sup>2</sup> principally on the horizontal section. When used, the JF Array mode is automatically invoked when the system is tuned up on the 15-meter band. On this frequency, the antenna acts as a twoelement, wide-spaced collinear array producing a good 3-dB gain broadside to the horizontal sections. Vertical angle selectivity is not used on this higher frequency band because the system is operated in its "Zepp" mode, in which feeders A and B are used and B and C are tied together as shown in **figs. 4** and **5**.


The reader will notice that there are small differences between the original Reinartz antenna and the modern version. Most of the recent changes were brought about by the addition of the JF Array feature and a more compatible feeder length to handle multiband applications. In a departure from the original antenna system, we have taken advantage of using a multiband tuning network to implement the third wire to ground resonance of the system. This expedient is in keeping with modernization of the compensation tuning, since in practice, only one adjustment needs be made for each operating band segment, and one that holds for a bandwidth of 40 to 60 kHz on the 80-meter band and greater than 60 kHz on the 40-meter band.

The coaxial transmission line to the radio station equipment may be provided by either a 50 or 75-ohm coaxial cable through a 1:1 balun transformer connected across a few turns at mid-point on inductor L of fig. 5. As discussed previously, capacitor C1 of fig. 5 is the vertical lobe angle control, where decreasing its effective capacity corresponds to raising the current maximum point on the vertical wire number 3 corresponding to a high lobe angle for the antenna. Conversely, an increase in capacitance by C1 results in lowering the current maximum point on the vertical wire number 3 corresponding to a low angle of radiation for the antenna. Each extreme capacitance change of C1 must be followed by an adjustment of the parallel tuned resonance circuit, especially if the operating frequency has also been changed beyond the bandwidth restrictions previously mentioned.
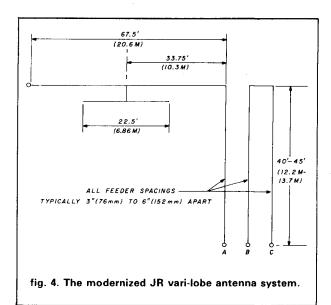
### performance

Because the JR Vari-Lobe antenna system is intended to be used primarily on the 80 and 40-meter bands with infrequent excursions to 15 meters, it is important to have a good ground in order for the system to work well. Ground radials should be employed beneath the horizontal section of the antenna and extend outward in a fan shape from the third (vertical) wire section. A good ground system will not only enhance the lobe selectivity feature, but will also significantly diminish ground losses surrounding the



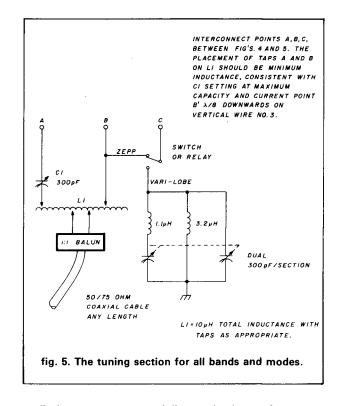

radiating system, especially on the lower frequency bands.

On-the-air tests were conducted on the 80, 40, and 15-meter bands over a period of three months. Based on these tests, it may be stated that the JR Vari-Lobe radiation characteristics on the 80 and 40-meter bands successfully proved to correspond to Reinartz's theory. The variable angle selectivity feature has enabled maximum signal strength adjustment over different path distances both during night and daytime conditions. While operation on the 15-meter band does not include variable angle control, it has proven to be an effec-

### AMATEUR TELEVISION NEW 70 CM ATV TRANCEIVER ALL YOU NEED IN ONE BOX



\$299 delivered TC70-1

- FULL COLOR, SOUND, & LIVE ACTION just like broadcast TV. Get on this exciting amateur video mode at our affordable ready to go price.
- WHAT IS REQUIRED FOR A COMPLETE OPERATING SYSTEM? The TC70-1s downconverter outputs to any TV on ch 3 for receiving. Connect a good 70 cm antenna and low loss coax. Plug in any composite video source you want to transmit: Camera, VCR, computer, etc. Plug in any low Z dynamic mic or use color camera mic for Standard 4.5 mHz TV sound. Connect to 13.8 vdc for base, mobile, or portable. See chapt. 20 1985 ARRL Handbook. That's it!
- WHAT CAN YOU DO WITH THE TC70-1 ATV TRANCEIVER? Show the shack, projects, computer program listings, home video tapes, repeat Space Shuttle audio and video if you have a TVRO, repeat SSTV or RITY, Weather Radar, do
   public service events such as parades, marathons, races, CAP searches and rescues...the list goes on. DX depends on antennas and terrain, typically 1 to 40 miles. We have video compensated RF linear amps for 20 (\$119) or 50
- (\$189) watts pep for greater DX.
   FEATURES: Small 7x7x2.5". Push to Look (PTL) T/R switching. GaAslet downconverter tunes whole 420-450 mHz band. Two switch selected video & audio inputs... RCA phone jacks and 10 pin color camera jack. Xmit video monitor output. Over 1 watt pep RF output on one or two (add \$15) selected crystal controlled frequencies. 439.25, 434.0, or 426.25 mHz.

CALL OR WRITE FOR OUR CATALOG for more info or who is on in your area. We stock antennas, modules, and everything you need on ATV.

TERMS: Visa, MC, or cash only UPS CODs by phone or mail. Checks must clear bank before shippent. Price includes UPS surface shipping in cont. USA, others add 3%. Transmitting equipment sold only to licensed Tech class or higher amateurs, verifiable in 1985 call book or copy of new license.

(818) 447-4565 m-f 8am-6pm pst. **P.C. ELECTRONICS** Tom W60RG Maryann WB6YSS



2522 Paxson Lane Arcadia CA 91006



tive radiating system of modest size and relative simplicity. Although tests were not performed on the 10 and 20-meter bands, Reinartz has shown the antenna system will operate as a conventional Zepp on all bands and if desired, with variable angle control as well. Conventional Zepp configurations do not require the parallel tuning network to ground for the third (vertical) wire. Thus, the simple expedient of tying together feeders B and C of fig. 5 changes the antenna into a Zepp configuration. The Zepp mode may be used on all bands higher than 80 meters, providing a flexible multiband antenna system if you don't mind the coupling adjustments and tuning of two feeder wires. The system is a natural for the Amateur who has limited antenna space but would like something different and more versatile than other systems.

### resonance tuning features

The original Reinartz antenna system used an RF ammeter in series with the ground connection to determine resonance of the antenna when excursions were made in lobe angle and frequency. A diode detector probe positioned near the top of the parallel tuning network will work as well and could be remoted quite easily if desired. However, it is also posssible to tune the system "by ear." When the parallel tuned circuit is tuned to the correct resonant point, a noticeable increase in received signal strength or background noise is apparent, thereby dispensing with the requirement for remote meter reading.

The multiband tuner operates satisfactorily over all of the harmonically related Amateur Radio bands to maintain resonance of the system. Obviously, if only limited operation is contemplated on 80 or 40 meters, then the multiband tuning function may be eliminated and a single-band network would serve as well. In my installation, using remote controlled tuning proved to make the operation of the Vari-Lobe a joy to use. Small 24-VAC furnace valve control motors were coupled to the shafts of both tuning capacitors to provide remote tuning control from the shack. These small, economical motors rotate slow enough to allow sufficient tuning resolution and accuracy even though they are turning only in one direction. An alternative to these AC-type control motors are surplus stepping motors featuring bi-directional incremental DC pulse control with 3.65 degree/step resolution. These devices are available from a number of sources for a nominal price. Some even include additional gearing for slower response.

### references

1. J.L. Reinartz, "A New Antenna System For Operating Control of Radiation," QST, February, 1935, page 9.

2. R.R. Schellenbach, W1JF, "The JF Array," QST, November, 1982, page 26.

ham radio



Please allow 4-6 weeks for delivery of first issues.

Foreign rates: Europe, Japan and Africa, \$28,00 for one year by air forwarding service. All other countries \$22.95 for one year by surface mail.



# 

### BUSINESS REPLY CARD

First Class Permit No. 1 Greenville, NH

Postage Will Be Paid By Addressee



Greenville, NH 03048



## the end-fed 8JK: a switchable vertical array

30/40-meter antenna radiates at low angles and requires little space

This array was developed to provide maximum gain in a compact, convenient low-vertical angle antenna system. The 40-meter version requires only 1225 square feet of area, and the 30-meter version, less than half that amount.


The 30- and 40-meter bands were selected because of the increased activity on those bands — especially for DX — resulting from the diminishing MUF caused by declining solar activity. The selectable directivity and low radiation angle of this system should offer significant performance advantages as interference and competition on these bands increase. While the gain of this phased array is modest, the system will effectively double the RF radiated power of a single vertical in the preferred direction. The array also provides deep nulls spaced 90 degrees apart on each side of the main beam pattern, thus improving rejection of unwanted signals.

### theory of operation


The 2 x 2 phased array is a pair of two parallelelement end-fire vertically polarized matched arrays, each of which is similar to W8JK's single section beam, with elements fed 180 degrees out of phase and spaced 1/8 wavelength apart. A composite simplified view of the array is shown in **fig.** 1. By folding the top and bottom 1/16-wavelength end sections of each element, a useful height reduction results without significantly effecting similar normal full-size array characteristics caused by element folding. Because each connecting wire at the base and the elevated end sections are only 1/16 wavelength long and carry very little current, little radiation and pattern distortion result from these folded sections

### construction and implementation

Figure 2 depicts the 2 x 2 phased array configuration; table 1 provides the element lengths and spacing as well as mast height requirements. Figure 3 illustrates the matching 1/4-wavelength stub and

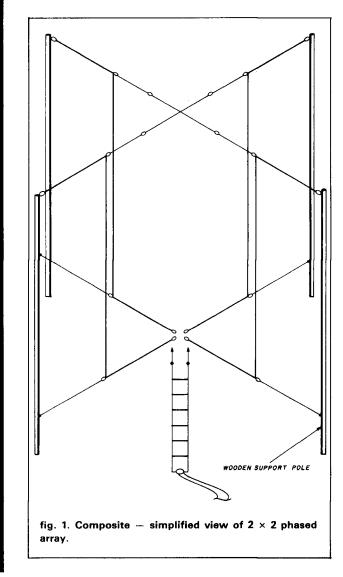

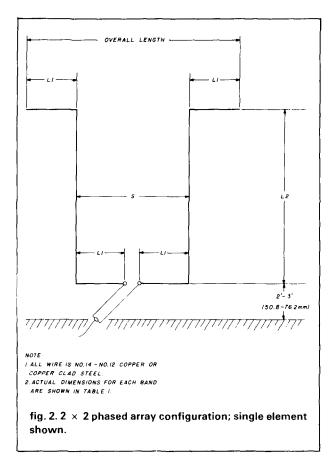By R.R. Schellenbach, W1JF, 12 Whitehall Lane, Reading, Massachusetts 01867



remote relay switching scheme including a balun for mating with coaxial cable. The length and physical positioning of the coaxial cable into the station are not critical.

Because the 2 x 2 phased array consists of two identical two-element arrays crossing at right angles to each other, a simple DPDT relay controls the selection of the array to be connected to the common 1/4-wavelength stub and hence through the balun transformer and coaxial cable into the station.

Once the 1:1 balun transformer tap position has been adjusted for a low VSWR at the desired operating frequency, no tuning or matching are required between the station and the system. The actual tap position depends on the stub line impedance and interwiring characteristics of the relay switching.

In order to reduce difficulties in array matching as much as possible, each element on an array — as well as the overall symmetry of the arrays — should be made as identical as possible to preserve balance and uniformity when changing directivity. Because a common 1/4-wavelength stub is used for matching into the antenna system, it is important that all wire connections to the DPDT relay be made equal in length. In placing the tap point for the balun transformer, you will find that with 75-ohm coaxial cable, the tap loca-


table 1.	Physical	dimensions	for	the	2	×	2	phased
array on	40 or 30	meters.						


	40-meter operation	30-meter operation
L1	8.75 feet	5.80 feet
L2	43.00 feet	29.00 feet
L3 (stub)	34.00 feet*	23.25 feet*
S	17.50 feet	11.60 feet
overall length	35.00 feet	23.25 feet
pole height (min.)	45.00 feet	31.00 feet
*May be laid horizontal a		01.00 166

tion will be a few inches higher toward the relay end than that of 50-ohm coaxial cable. More detail on proper matching is provided later, but the process is simple and provides wide bandwidth on either band of operation.
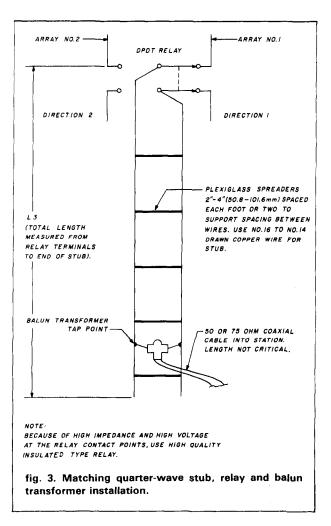
#### site and space requirements

Four poles, preferably wooden, are required to sup-



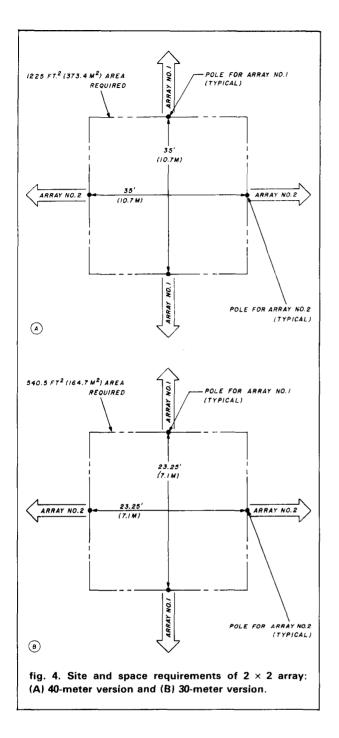

port the array. While they are oriented as shown in **fig. 4**, the distance between them can be increased to meet individual requirements. **Figure 4** also indicates the principal beam directions with respect to the DPDT relay position that is controlled from the station end. Using this directivity characteristic of the array, the individual beam patterns may be oriented in the most favorable compass directions.

To assure maximum low angle radiation and deep null beam pointing performance --- and to eliminate

effects of pattern distortion and RF absorption — the array should be located in an area free of structures or power lines for at least 250 feet from its center on 40 meters and 190 feet on 30 meters.

### technical performance

The 2 x 2 phased array provides approximately 4 dB gain over conventional 1/2-wavelength dipoles and 6 dB gain over 1/4-wavelength ground mounted single verticals. The azimuthal bi-directional beam pattern, although relatively broad, (approximately 80-degree half-power beamwidth) has quite deep nulls, better than 20 dB down from the main lobe maximum. The nulls are also bi-directional in either case and are located at right angles (90 degrees) to the two major beam lobes produced by each active array.

In operation, these nulls may be used to advantage to eliminate strong interference coming from an undesired direction. The major radiating point on each active element occurs at a point 42 percent up from the bottom end of each vertical. The distance between the bottom horizontal 1/I6-wavelength interconnecting wires and earth ground should be no more than 2 to 3 feet for proper performance.

### remote switching and balun tap alignment

The simple arrangement of a common 1/4-wavelength stub switching to activate either array provides controlled directivity for both transmitting and receiving. The length of the 1/4-wavelength stub for either band is given in **table 1** as a starting point for the balun tap position.

The tap should be made progressively upward from this overall dimension. Each time the tap location is changed a few inches at a time, the operator should observe an in-line measurement of SWR. The proper tap point will result in the lowest VSWR reading when matching into appropriate coaxial cable using a 1:1 ratio type balun transformer. The use of a balun in this array application is highly recommended to maintain a complete balance of the array system and to minimize beam pattern distortions as well as deterioration of noise pick-up immunity so characteristic of poorly matched or unbalanced feed systems.

The coaxial cable, whose length is not critical, may be buried and its outer shield grounded for further immunity from noise pick-up in severe cases.

Because of weather considerations for rain or snow, the DPDT relay should be mounted inside a waterproof enclosure. This may be combined with supporting the four bottom horizontal 1/16 wavelength wires if the enclosure is elevated by a post at the recommended 2 to 3 feet above the ground level.

### ham radio



### Uncle Ben says...

### "I give you much more than just the lowest price...

When you get that exciting new piece of equipment from me, you know you are going to be completely happy ... I see to it, personally! I also give you earliest delivery, greatest trade-in allowances, my friendly assistance in every possible way.

Just ask any of the many thousands of hams all over the world who have been enjoying my friendly good service for over a half a century. 73, Uncle Ben, W2SOH



"Uncle Ben" Snyder, W2SOH the head man of "HAM HEADQUARTERS. USA®" ....Since 1925!

(516) 293-7995 HARRISON HAS THEM ALL! **KENWOOD** 



CALL ME...

Kenwood TL-922A



 SEE ME... At one of the world's largest Ham Supply Centers!



Kenwood TH-21A, TH-41A



Kenwood TS-940S

Since 1925!






Kenwood TS-711A

Kenwood TR-2600, TR-3600



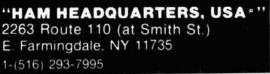

RADIO

## feeding phased arrays: an alternative method

Carefully chosen feeder lengths provide good match

This article describes a method of feeding a twoelement phased-array antenna without using impedance-matching or phase-delay networks at each element. The method requires determining the length of the feedline from each antenna to the "common point" (the point at which the feedlines are combined) and installing a matchbox or antenna tuner at this location (or in the shack) in order to transform the paralleled impedance to 50 ohms.

### network method of matching

As was clearly pointed out by Forrest Gehrke, K2BT, in his extensive series of articles on phased arrays, the insertion of a 90-degree delay line into a feeder will, in most cases, *not* guarantee a 90-degree phase shift in the feeder current.<sup>1</sup> If the actual driving-point impedance of each element is known (for a specified current amplitude and phase), then the voltage amplitude and phase at any point on that feeder can be calculated. The technique given by K2BT allows one to choose any convenient length for the antenna feeders and then design suitable networks to alter the feeder voltages so that they are all transformed to the same value of voltage amplitude and phase. These terminals can then be safely and correctly joined together (at the "common point") since they are all at the same voltage. The impedance-matching and phase-delay networks are used to force all the voltages to be the same. Any convenient length of 50-ohm transmission line (the main feeder) can then be utilized to span the distance from the common point to the shack. The main feedline will be "flat" (the SWR will be low) because the networks at the ends of the antenna feeders are designed to present a combined impedance of 50 + j0 ohms (pure resistance) when "looking" into the common point toward the antennas (see fig. 1A).

The method shown in this article calculates the voltages that must exist at various points along the antenna feeders. When a point is found on one antenna feeder where the voltage (both amplitude and phase) is identical to the voltage at some point on another antenna feeder, then those two points can be connected together without altering the relationship of the currents at the driving points of the two antennas. Rarely will the impedance seen looking toward the antennas from this common point be 50 ohms.\* Thus, the main feedline running from this point into the shack will not be flat (the SWR will be high) and a matchbox or tuner will be needed at the operating position to present a well-matched load to the transmitter, (see **fig. 1B**). Note: the matchbox could be

**By Al Christman, KB8I**, Department of Electrical and Computer Engineering, Ohio University, Clippinger Lab, Athens, Ohio 45701-2979 placed into this circuit at the common point if desired. Then the main feeder into the shack would be "flat" as in **fig. 1A**. Of course, the matchbox would then be "dedicated" to the array and could not be used for other purposes unless removed.

### calculations are simple

Only one formula, used repeatedly, is needed to calculate the voltages at all points along the antenna feedlines. It's best to utilize a personal computer or programmable calculator to reduce the drudgery of this task.

$$\overline{E}_{IN} = \overline{I}_{OUT} (A \overline{Z}_L + B)$$
 (1)

where  $\overline{E}_{IN}$ 


 voltage at the input end of the antenna feeder

- $\bar{I}_{OUT}$  = current at the output or load end of the antenna feeder
  - current at the driving-point of the antenna
- $\overline{Z}_L$  = impedance at the output or load end of the feeder
  - driving-point impedance of the antenna
- $A = \cos \theta$
- $B = jZ_0 \sin \theta$
- $Z_0$  = characteristic impedance of the antenna feeder
- $\theta$  = electrical length of the antenna feeder, in degrees (360 degrees =  $\lambda$ )

Note that  $\overline{E}_{IN}$ ,  $\overline{I}_{OUT}$ , and  $\overline{Z}_L$  are all complex numbers; that is, they have both magnitude and phase. The equation therefore requires the use of complex, or vector, arithmetic. *A* and *B* are two of the "ABCD" parameters discussed by K2BT in Part 5 of his series.<sup>2</sup> (In addition, both "*A*" and "*B*" can be complex numbers as well. "*A*" is complex if the cable attenuation is taken into account.)

The goal is to find a place on the antenna No. 1 feeder where the voltage is identical to the voltage somewhere on the antenna No. 2 feeder. To do this, make a list for each antenna, labeling one column for "feeder length in degrees" and the other "voltage at end of feeder." Then calculate and record the voltage on each feeder at 10 degree intervals. After finding 10 or 15 values for each feeder, stop calculating and compare the lists. It is better to record the voltages in polar form (amplitude and phase angle) for easier

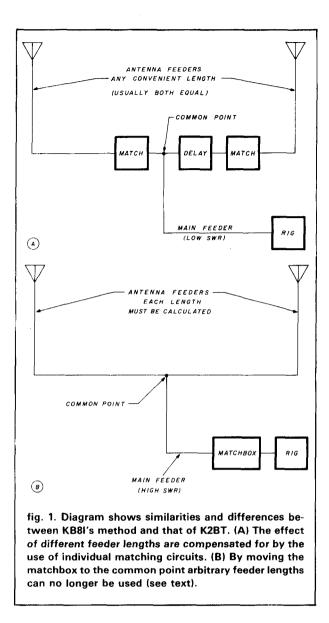\*A 1:1 VSWR occurs only when the paralleled driving-point impedance of the elements equals the characteristic impedance of the line. Editor.



comparison. Also, keep all the angles less than or equal to  $\pm$  180 degrees. (For example, an angle of -230 degrees is equivalent to +130 degrees. Always use the smaller number.) When two amplitude values are found that are close to each other, check the angles to see if they are similar. If both amplitude and phase are "in the ballpark," redo the calculation at 1 degree or 1/2 degree increments until two lengths are found where the voltages are identical, or nearly so. If none of the recorded values on one list are comparable to those on the other list, continue the calculations and add more data points to the lists — in other words, make the antenna feeders longer. It should be possible to find the required line lengths within a reasonable amount of time.

#### cutting the coax

After the required length of each antenna feeder has



**R.F. Power Monitoring** 







**Receiver Multicoupling** 

# **The Problem Solvers**



**Duplexers & Preselectors** 

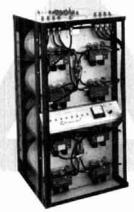

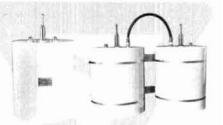

Bandpass, Pass-Reject and Notch Cavity Filters

Transmitter Combining 150 – 900 MHz

### **\*COMPLETE SYSTEM ENGINEERING ASSISTANCE\***



been calculated, it's time to actually cut the coax, remembering to take the velocity factor of that particular cable into account. It's a good idea to actually measure the velocity factor of the cable, rather than relying upon the manufacturer's data. Since the electromagnetic fields travel more slowly inside the cable than they do in free space, the physical length of the cable will be shorter than the electrical length:

$$L = 2.734 (L_{e}) (V_{F})/f$$
 (2)

- where L = physical length of antenna feeder, in feet (1 meter = 3.281 feet)
  - $L_e$  = electrical length of antenna feeder, in degrees
  - $V_F$  = velocity factor of the cable, as a decimal (i.e., 0.66)
  - f = operating frequency, in Megahertz

#### switching directions

For a two-element array, the pattern may be reversed by interchanging the antenna feeder cables at the antenna terminals. One way to do this, shown in **fig. 2**, is to cut the longer of the two antenna feeders into two pieces, one of which is the same length as the shorter antenna feeder. These two equal-length cables are then connected directly to the antenna feeder points and the remaining third piece of cable is switched back and forth from one antenna feeder to the other using a DPDT relay. For best results when building a switchable array, the lengths of the radiators and the ground systems under each antenna should be adjusted until both antennas have the same self-impedance.<sup>3</sup>

#### 20-meter array


I became interested in phased arrays while accumulating the contacts necessary for WAS on 20 meters. A home-brew three-element wire beam suspended from trees at 18 feet (5.5 meters) seemed to be performing satisfactorily, and I was working new states at a good pace. However, a phone call revealed that I was also "quite strong" on my neighbor's (just to the west) color TV set. I wasn't too surprised because his portable TV - equipped only with rabbit ears for an antenna — was less than 50 feet (15.2 meters) from my wire beam, and I was running the legal limit. It became vitally important that I construct an antenna that would concentrate all the RF energy toward the east and place a big null right over my neighbor's living room - he is, after all, not only my neighbor, but my landlord.

My backyard was too small for a two-element array with 1/4 wavelength spacing, but the literature revealed that 75 degree spacing (0.208 wavelength)

table 1. Voltages at various points along the antenna feeders.

	a (i -	=1/0 degrees)
θ		E <sub>IN</sub>
(degrees)		(volts)
0	15.56	/ - 45 degrees
10		/ - 11.23 degrees
20		/33.2 degrees
30		/58.4 degrees
40		/70.4 degrees
50	32.02	/77.2 degrees
60	38.2	/81.7 degrees
70	43.4	/85 degrees
80	47.37	/87.7 degrees
90	50	/90 degrees
100	51.19	/92.1 degrees
110	50.89	/94.2 degrees
120	49.11	/96.4 degrees
130	45.92	/98.96 degrees
140	41.43	/101.7 degrees
150	35.82	/105.4 degrees
160	29.32	/110.6 degrees
170	22.32	/119 degrees
180	15.56	/135 degrees
θ	nna (I =	1 <u>/-105 degrees</u> ) E <sub>IN</sub>
(degrees)		(volts)
0		/ - 64.9 degrees
10	54.92	/ - 57.95 degrees
20	59.16	/ - 52.13 degrees
30	59.16 62.14	/ - 46.98 degrees
30 40	59.16 62.14 63.69	/ - 46.98 degrees / - 42.2 degrees
30 40 50	59.16 62.14 63.69 63.74	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees
30 40	59.16 62.14 63.69 63.74 62.27	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees
30 40 50	59.16 62.14 63.69 63.74 62.27 59.37	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees
30 40 50 60	59.16 62.14 63.69 63.74 62.27 59.37	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees
30 40 50 60 70	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees
30 40 50 60 70 80	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees
30 40 50 60 70 80 90	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees
30 40 50 60 70 80 90 100	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18 38.31	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees / - 6.41 degrees
30 40 50 60 70 80 90 100 110	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18 38.31 33.26 30.18	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees / - 6.41 degrees / 4.83 degrees / 19.84 degrees / 39.02 degrees
30 40 50 60 70 80 90 100 110 120	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18 38.31 33.26 30.18	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees / - 6.41 degrees / 4.83 degrees / 19.84 degrees
30 40 50 60 70 80 90 100 110 120 130	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18 38.31 33.26 30.18 30.09 33.02	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees / - 6.41 degrees / 4.83 degrees / 19.84 degrees / 39.02 degrees / 60.32 degrees / 79.71 degrees
30 40 50 60 70 80 90 100 110 120 130 140 150 160	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18 38.31 33.26 30.18 30.09 33.02	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees / - 6.41 degrees / 4.83 degrees / 19.84 degrees / 39.02 degrees / 60.32 degrees / 79.71 degrees / 94.96 degrees
30 40 50 60 70 80 90 100 110 120 130 140 150	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18 38.31 33.26 30.18 30.09 33.02 37.99 43.84	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees / - 15 degrees / - 6.41 degrees / 4.83 degrees / 19.84 degrees / 39.02 degrees / 39.02 degrees / 60.32 degrees / 94.96 degrees / 106.39 degrees
30 40 50 60 70 80 90 100 110 120 130 140 150 160	59.16 62.14 63.69 63.74 62.27 59.37 55.19 50 44.18 38.31 33.26 30.18 30.09 33.02 37.99 43.84	/ - 46.98 degrees / - 42.2 degrees / - 37.53 degrees / - 32.77 degrees / - 27.65 degrees / - 21.87 degrees / - 15 degrees / - 6.41 degrees / 4.83 degrees / 19.84 degrees / 39.02 degrees / 60.32 degrees / 79.71 degrees / 94.96 degrees

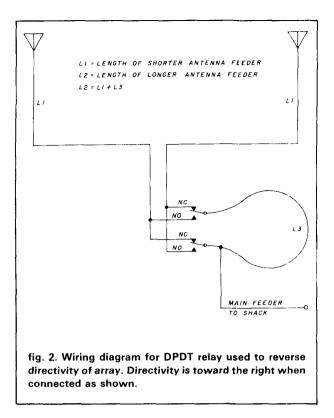combined with 105-degree phasing would yield the desired cardioid end-fire pattern. Measurements showed that I could squeeze this array into the yard without the radials protruding onto the property of my neighbor to the east. Two tri-band trap verticals were



erected, each atop a 15-foot (4.6 meter) mast. They were spaced 75 degrees apart (14.4 feet or 4.4 meters at 14.25 MHz) on an east-west line, and each had twenty 1/4 wavelength radials. The feed system would be designed so that each antenna received the same current amplitude, but the east antenna would lag the west antenna by 105 degrees, placing the null directly on my landlord's living room.

After everything was built, I used an antenna noise bridge and calculator to analyze the system according to the procedure described by K2BT.<sup>3</sup> I measured the self-impedance and driving-point impedance of each vertical at the end of a known length of coax, and then "rotated" each of these values to the antenna feedpoint. This may be done on a Smith chart or through the use of the following formula:

$$Z_L = \frac{D\overline{Z}_{IN} - B}{A - C\overline{Z}_{IN}}$$
(3)

where

- $Z_L$  = load impedance at the output end of the transmission line
- $Z_{IN}$  = impedance measured at the input end of the transmission line
- $A = D = \cos \theta$
- $B = jZ_0 \sin \theta$
- $C = j \sin\theta/Z_0$

- Z<sub>0</sub> = characteristic impedance of the transmission line
- $\theta$  = electrical length of the line, in degrees

While it's better to measure all the impedances right at the antenna feedpoint, I didn't enjoy the prospect of standing on tiptoe perched 10 feet (3 meters) above the ground. I opted for the easier way, and the data obtained enabled me to calculate the mutual impedance between the two verticals. I used this figure to determine the actual driving-point impedance of each element when fed by the currents I had specified for the array. The product of the driving-point impedance and current gives the actual voltage at the feedpoint of each antenna:

west antenna:

- $I_1 = 1/0$  degrees amperes  $Z_1 = 11$ -j11 ohms = 15.56 / -45 degrees ohms  $E = I_1Z_1 = 15.56 / -45$  degrees volts east antenna:
  - $I_{2} = 1 / -105 \text{ degrees amperes}$   $Z_{2} = 38 + j32 \text{ ohms}$  = 49.7 / 40.1 degrees ohms  $E_{2} = I_{2}Z_{2} = 49.7 / -64.9 \text{ degrees volts}$

The antenna currents were assumed to have a magnitude of 1 ampere for ease of calculation. The actual current magnitudes will be determined by the amount of drive power. What *is* important is that the actual currents be equal in magnitude, and that the east antenna current lags the west antenna current by 105 degrees.

My lists of the voltages that will occur at various points along each antenna feedline are shown in table Scanning the table, we can see that the voltage on the west antenna feeder at a point 50 degrees from the antenna is 32.02/77.2 degrees volts, while the voltage on the east antenna feeder at a point 150 degrees from the antenna is 33.02/79.71 degrees volts. These two values are close to each other, and we can now calculate more voltages, this time at 1 degree intervals centered around 50 degrees for the west feeder and 150 degrees for the east feeder. This information is shown in table 2. Comparing the voltages on the two feeders, we can see that the values are nearly identical for a 51-degree west feeder (32.67/77.77 degrees volts) and a 149-degree east feeder (32.61/77.95 degrees volts).

table 2. Voltages at 1 degree intervals along the antenna feeders.

west antenna (I = 1/0 degrees)			
θ		E <sub>IN</sub>	
(degrees)		(volts)	
47	30.02	/75.53 degrees	
48	30.69	/76.12 degrees	
49	31.36	/76.7 degrees	
50	32.02	/77.2 degrees	
51	32.67	/77.77 degrees	
52	33.32	/78.27 degrees	
east anten	ina (I =	1 <u>/-105 degrees</u> )	
east anten θ	ina (I =	1 <u>/-105 degrees</u> ) E <sub>IN</sub>	
	ina (I =		
θ		E <sub>IN</sub>	
θ (degrees)	31.87	E <sub>IN</sub> (volts)	
θ (degrees) 147	31.87 32.23	E <sub>IN</sub> (volts) /74.29 degrees	
θ (degrees) 147 148	31.87 32.23 32.61	<i>E<sub>IN</sub></i> (volts) /74.29 degrees /76.14 degrees	
θ (degrees) 147 148 149	31.87 32.23 32.61 33.02	<i>E<sub>IN</sub></i> (volts) /74.29 degrees /76.14 degrees /77.95 degrees	
θ (degrees) 147 148 149 150	31.87 32.23 32.61 33.02 33.45	<i>E<sub>IN</sub></i> (volts) /74.29 degrees /76.14 degrees /77.95 degrees /79.7 degrees	
θ (degrees) 147 148 149 150 151	31.87 32.23 32.61 33.02 33.45	<i>E<sub>IN</sub></i> (volts) /74.29 degrees /76.14 degrees /77.95 degrees /79.7 degrees /81.43 degrees	


table 3. Theoretical front-to-back ratio of the 2-element phased vertical array.

elevation angle, heta (degrees)	front-to-back ratio (dB)
0	00
10	39.72
20	27.68
30	20.61
40	15.56
50	11.59
60	8.26
70	5.31
80	2.60


Notice that the driving-point currents are 105 degrees out of phase, yet the points on the feeders where the voltages are in phase are only (149 degrees - 51 degrees =) 98 degrees apart. Also notice that the east feeder, which has the lagging feedpoint current, is longer than the west feeder, which one would expect.

Measurements on the RG8X cable used for the antenna feeders showed that its actual velocity factor was 0.725 rather than the advertised value of 0.81. Using eq. 2, the actual lengths of coax needed were 7.094 feet (2.162 meters) and 20.726 feet (6.317 meters). These two antenna feeders were cut to length and installed. A piece of RG-8 about 30 feet (9.1 meters) long extended from the Tee connector, where the antenna feeders were joined, to the matchbox in the shack.

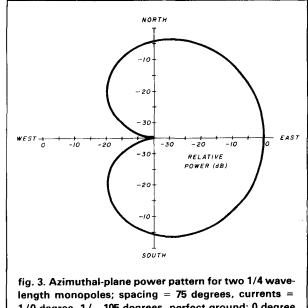The array performed as expected. State number 50



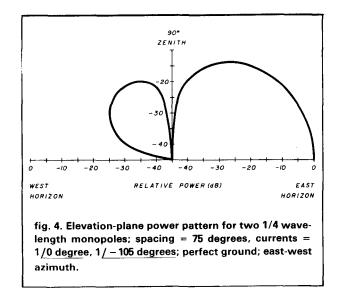1/0 degree, 1/-105 degrees, perfect ground; 0 degree elevation angle.



(Delaware) was worked shortly thereafter, along with contacts in Africa. There were almost no contacts to the west - but there also were no further TVI problems. The major azimuthal and elevation-plane radiation patterns are shown in figs. 3 and 4; the front-toback ratio in the main elevation plane is provided in table 3. Notice that the front-to-back ratio is infinite only on the horizon (0 degree elevation angle) and deteriorates to just one or two S-units at high angles. There is actually a fairly large rear lobe whose maximum occurs at an elevation angle of about 60 degrees. Thus, there will be a fair amount of radiation and signal pickup off the back of the array if propagation favors this high angle.

### **STUMPED FOR A GIFT IDEA?**

### I.D. BADGES

No ham should be without an I.D. badge. It's just the thing for club meetings, con-ventions, and get-togethers, and you have a wide choice of colors. Have your name and call engraved in either standard or script type on one of these plastic laminated I.D. badges. Wear it with pride! Available in the following color combina-



tions (badge/lettering): white/red, woodgrain/white, blue/white, white/black, yellow/blue, red/white, green/white, metallic gold/black, metallic silver/black \$2.50

UID Engraved I.D. Badge



HERE'S A GIFT IDEA!

How about an attractive BASE-BALL style cap that has name and call on it. It's the perfect way to keep eyes shaded during Field Day, it gives a jaunty air when worn at Hamfests and it is a great help for friends who have never met to spot names and calls for easy recognition. Great for birthdays, anniversaries, spe-

cial days, whatever occasion you want it to be. Hats come in the following colors: GOLD, BLUE, RED, KELLY GREEN. Please send call and name (max-imum 6 letters per line). UFBC-81 \$5.00

REGULAR PRICE HAT AND BADGE \$8.50 (\$7.50 + \$1.00 shipping)



### conclusion

A technique has been demonstrated for feeding two-element phased arrays based upon the premise that the feeders from individual radiating elements may be directly connected together if the voltages at the point of connection are identical in magnitude and phase. A method was shown for determining the voltage at any point on an antenna feeder when the impedance and current at the driving-point of the antenna are given. Using these ideas, an actual 2-element array can be built and operated successfully on the air.

### acknowledgements

The author would like to thank Forrest Gehrke, K2BT, for his encouragement, especially during the early stages of this project in 1983. Appreciation is also expressed to Margaret Shields in the Department of Electrical and Computer Engineering at Ohio University for typing the manuscript.


### references

1. Forrest Gehrke, K2BT, "Vertical Phased Arrays," ham radio, May, June, July, October, December, 1983, and May, 1984.

2. Forrest Gehrke, K2BT, "Vertical Phased Arrays, part 5," ham radio, December, 1983, page 59.

3. Forrest Gehrke, K2BT, "Vertical Phased Arrays, part 3," ham radio, July, 1983, page 26.

### ham radio

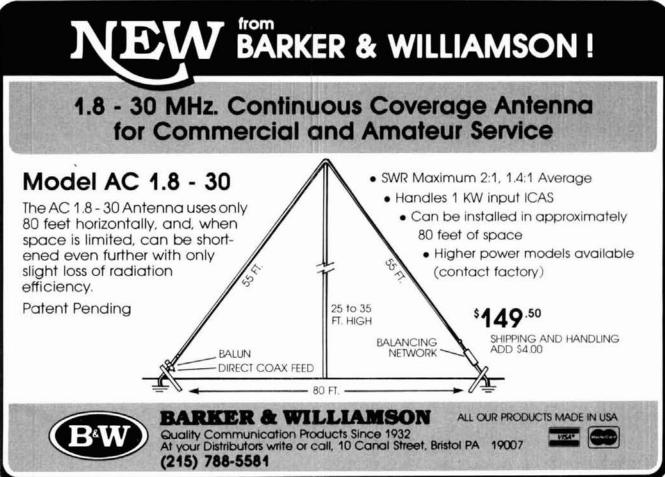



### RF TRANSISTORS

FRESH STOCK - NOT SURPLUS TESTED — FULLY GUARANTEED

	- FULL I	GUANAI	
	2-30MHz 12V	(*=28V)	
P/N	Rating	Ea.	Match Pr
<b>MRF406</b>	20W	\$14.50	\$32.00
<b>MRF412</b>	80W	18.00	40.00
MRF412A	80W	18.00	40.00
<b>MRF421</b>	100W	25.00	54.00
MRF421C	110W	27.00	58.00
MRF422*	150W	38.00	82.00
MRF426*	25W	17.00	40.00
MRF426A*	25W	17.00	40.00
<b>MRF433</b>	13W	14.50	32.00
MRF435*	150W	42.00	90.00
<b>MRF449</b>	30W	12.00	27.00
MRF449A	30W	11.00	25.00
<b>MRF450</b>	50W	12.00	27.00
MRF450A	50W	12.00	27.00
<b>MRF453</b>	60W	15.00	33.00
MRF453A	60W	15.00	33.00
MRF454	80W	16.00	35.00
MRF454A	80W	16.00	35.00
<b>MRF455</b>	60W	12.00	27.00
MRF455A	60W	12.00	27.00
<b>MRF458</b>	80W	18.00	40.00
<b>MRF460</b>	60W	16.50	36.00
<b>MRF475</b>	12W	3.00	9.00
<b>MRF476</b>	3W	2.50	8.00
<b>MRF477</b>	40W	13.00	29.00
<b>MRF479</b>	15W	10.00	23.00
MRF485*	15W	6.00	15.00
<b>MRF492</b>	90W	18.00	39.00
SRF2072	75W	15.00	33.00
CD2545	50W	24.00	55.00
Selected H	High Gain Mato	ched Quads A	vailable
11 A 4	VHF TRANS		Match De
Type	Rating	Ea.	Match/Pr
MRF221	15W	\$10.00	_
MRF222	12W	12.00 13.50	\$32.00
MRF224	40W		\$32.00
MRF231	3.5W 25W	10.00	39.00
MRF234 MRF237	1W	2.50	35.00
		12.00	_
MRF238	30W		-
MRF239	30W	15.00	
MRF240	40W	16.00 25.00	59.00
MRF245	80W	25.00	59.00
MRF247 MRF260	80W 5W	6.00	33.00
	30W	13.00	
MRF264 MRF492	70W	18.00	39.00
MRF607	1.8W	2.60	_
MRF627	0.5W	9.00	-
MRF641	15W	18.00	_
MRF644	25W	23.00	_
MRF646	40W	24.00	59.00
MRF648	60W	29.50	69.00
SD1416	80W	29.50	_
	125W		
		37.00	
SD1477 2N4427		37.00	_
2N4427	1 W	1.25	Ξ
2N4427 2N5945	1 W 4 W	1.25	Ξ
2N4427 2N5945 2N5946	1W 4W 10W	1.25 10.00 12.00	
2N4427 2N5945 2N5946 2N6080	1W 4W 10W 4W	1.25 10.00 12.00 6.00	
2N4427 2N5945 2N5946 2N6080 2N6081	1W 4W 10W 4W 15W	1.25 10.00 12.00 6.00 7.00	ШШ
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082	1W 4W 10W 4W 15W 25W	1.25 10.00 12.00 6.00 7.00 9.00	
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083	1W 4W 10W 4W 15W 25W 30W	1.25 10.00 12.00 6.00 7.00	   29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W	1.25 10.00 12.00 6.00 7.00 9.00 9.50 12.00	   29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083 2N6084	1W 4W 10W 4W 25W 30W 40W TMOS	1.25 10.00 12.00 6.00 7.00 9.00 9.50 12.00	   29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W 7 MOS 30 W	1.25 10.00 12.00 6.00 7.00 9.00 9.50 12.00 FET \$22.50	   29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138	1 W 4 W 10 W 4 W 25 W 30 W 40 W 7 MOS 30 W 30 W	1.25 10.00 6.00 7.00 9.00 9.50 12.00 FET \$22.50 35.00	  29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W 7 MOS 30 W 30 W 150 W	1.25 10.00 12.00 6.00 7.00 9.00 9.50 12.00 FET \$22.50	  29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140 MRF150	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W 7 MOS 30 W 30 W 150 W	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00	  29.00 
2N4427 2N5945 2N5945 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140 MRF150 MRF172	1 W 4 W 10 W 25 W 30 W 40 W 7 MOS 30 W 30 W 150 W 80 W	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00	29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140 MRF150	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W 7 MOS 30 W 30 W 150 W	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00	  29.00
2N4427 2N5945 2N5946 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF138 MRF140 MRF150 MRF172 MRF174	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W 7 MOS 30 W 30 W 150 W 150 W 80 W 125 W	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00	11111
2N4427 2N5945 2N5946 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140 MRF150 MRF172 MRF174 <i>Technical</i>	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W 7 MOS 30 W 30 W 150 W 150 W 80 W 125 W Assistance	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-fr	eference
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF138 MRF130 MRF150 MRF172 MRF172 MRF174 Technical information	1 W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 150W 150W 80W 125W Assistance on CD, PT	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-rr , <i>RF</i> , <i>SRF</i> ,	eference SD P/Ns
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF138 MRF130 MRF150 MRF172 MRF172 MRF174 Technical information	1 W 4 W 10 W 4 W 15 W 25 W 30 W 40 W 7 MOS 30 W 30 W 150 W 150 W 80 W 125 W	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-rr , <i>RF</i> , <i>SRF</i> ,	eference
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF138 MRF140 MRF150 MRF172 MRF174 Technical information Call Engine	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 150W 150W 80W 125W Assistance on CD, PT eering Dept.	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-fr <i>RF, SRF,</i> (619)	= = = = SD P/Ns 744-0728
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF137 MRF138 MRF140 MRF172 MRF174 Technical information Call Engine	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 30W 150W 150W 80W 125W Assistance on CD, PT eering Dept. F Parts Catal	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-rr , <i>RF</i> , <i>SRF</i> , (619) 7 og Available	eference SD P/Ns '44-0728
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF137 MRF138 MRF140 MRF172 MRF174 Technical information Call Engine	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 150W 150W 80W 125W Assistance on CD, PT eering Dept.	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-rr , <i>RF</i> , <i>SRF</i> , (619) 7 og Available	eference SD P/Ns '44-0728
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF137 MRF138 MRF140 MRF150 MRF172 MRF174 Technical information Call Engine	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 150W 150W 150W 150W 80W 125W Assistance on CD, PT eering Dept F Parts Catal EM & Quanti	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-rr , <i>RF</i> , <i>SRF</i> , (619) 7 og Available	
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF137 MRF138 MRF140 MRF172 MRF172 MRF174 Technical information Call Engine O Minimum C	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 150W 150W 80W 125W Assistance on CD, PT bering Dept. F Parts Catal EM & Quanti	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-r( , RF, SRF, (619) og Available ty Discounts Add \$3.50	
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF137 MRF138 MRF140 MRF172 MRF172 MRF174 Technical information Call Engine O Minimum C	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 150W 150W 150W 150W 80W 125W Assistance on CD, PT eering Dept F Parts Catal EM & Quanti	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-r( , RF, SRF, (619) og Available ty Discounts Add \$3.50	
2N4427 2N5945 2N5945 2N6080 2N6080 2N6083 2N6083 2N6084 MRF137 MRF137 MRF138 MRF140 MRF150 MRF172 Technical information Call Engine Q Minimum C WE SHIP S	1W 4W 10W 4W 15W 30W 30W 7MOS 30W 30W 150W 150W 150W 150W 80W 125W Assistance on CD, PT eering Dept. F Parts Catal EM & Quanti Drder \$20 AME DAY	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-r/ , RF, SRF, (619) 7 og Available ty Discounts Add \$3.50 C.O.D./	eference SD P/Ns 744-0728 139 Shipping /ISA/MC
2N4427 2N5945 2N5945 2N6080 2N6080 2N6083 2N6083 2N6084 MRF137 MRF137 MRF138 MRF140 MRF150 MRF172 Technical information Call Engine Q Minimum C WE SHIP S	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 150W 150W 80W 125W Assistance on CD, PT bering Dept. F Parts Catal EM & Quanti	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-r/ , RF, SRF, (619) 7 og Available ty Discounts Add \$3.50 C.O.D./	eference SD P/Ns 744-0728 139 Shipping /ISA/MC
2N4427 2N5945 2N5945 2N6080 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140 MRF172 MRF172 MRF174 Technical information Call Engine O WE SHIP S ORDER	1W 4W 10W 4W 15W 30W 30W 7MOS 30W 30W 150W 150W 150W 150W 80W 125W Assistance on CD, PT eering Dept. F Parts Catal EM & Quanti Drder \$20 AME DAY	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-r/ , RF, SRF, (619) 7 og Available ty Discounts Add \$3.50 C.O.D./	eference SD P/Ns 744-0728 139 Shipping /ISA/MC
2N4427 2N5945 2N5945 2N6080 2N6081 2N6083 2N6083 2N6084 MRF137 MRF137 MRF140 MRF150 MRF172 MRF174 <i>Technical</i> <i>information</i> <i>Call Engine</i> RI O Minimum C WE SHIP S	1W 4W 10W 4W 15W 30W 30W 7MOS 30W 30W 150W 150W 150W 150W 80W 125W Assistance on CD, PT eering Dept. F Parts Catal EM & Quanti Drder \$20 AME DAY	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-r/ , RF, SRF, (619) 7 og Available ty Discounts Add \$3.50 C.O.D./	eference SD P/Ns 744-0728 139 Shipping /ISA/MC
2N4427 2N5945 2N5945 2N6080 2N6080 2N6081 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140 MRF172 MRF172 MRF174 Technical information Call Engine O WE SHIP S ORDER	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 30W 150W 150W 150W 150W 150W 150W 150W 15	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 80.00 65.00 80.00 65.00 80.00 65.00 80.00 65.00 80.00 65.00 80.00	
2N4427 2N5945 2N6080 2N6080 2N6083 2N6083 2N6084 MRF137 MRF138 MRF140 MRF150 MRF172 MRF174 Technical information Call Engine O Minimum C WE SHIP S ORDER	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 30W 150W 150W 150W 150W 150W 150W 125W Assistance on CD, PT eering Dept. F Parts Catal EM & Quanti Order \$20 AME DAY	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-rr , RF, SRF, (619) 7 og Available ty Discounts Add \$3.50 C.O.D.// 800-854	eference SD P/Ns 744-0728 139 Shipping /ISA/MC -1927
2N4427 2N5945 2N5945 2N6080 2N6080 2N6082 2N6083 2N6084 MRF137 MRF138 MRF140 MRF172 MRF172 MRF174 Technical information Call Engine O WE SHIP S ORDER	1W 4W 10W 4W 15W 25W 30W 40W 7MOS 30W 30W 30W 150W 150W 150W 150W 150W 150W 150W 15	1.25 10.00 12.00 6.00 7.00 9.50 12.00 FET \$22.50 35.00 92.00 80.00 65.00 88.00 & cross-rr , RF, SRF, (619) 7 og Available ty Discounts Add \$3.50 C.O.D.// 800-854	

May 1985 / 65

# ham radio TECHNIQUES Bill WE SHI

### the first Radio Amateur

The world in 1900 was a far different place than the world we know. No one had heard of credit cards or ball point pens; time sharing meant togetherness, not computers. There were no fluorescent lights, instant coffee, antibiotics, Frisbees or frozen foods. There was no television, no radio – and no Amateur Radio.

Into this late Victorian era there stepped a Giant. In 1896 a young Italian arrived in England with some mysterious scientific apparatus in his luggage. The Customs officials, who had seen nothing like it before, examined it so thoroughly that the delicate apparatus was completely wrecked. This was the inauspicious beginning of a venture destined to remold the pattern of 20th-century living.

Guglielmo Marconi, at 26, had come to England to seek aid in developing his latest invention, a means of signalling at a distance without wires. The hub of a great Empire, Britain possessed the world's greatest mercantile fleet and the mightiest Navy — and it was in shipping that Marconi could see his dream come true. For once a ship left the sight of land it was isolated from the world. When disaster struck — as it often did — some form of communication between ship and shore was sorely needed. Marconi demonstrated his equipment to the War Office and the British Post Office. The War Office was interested, but the idea of an alternative means of communication seemed to be unpleasant to the Post Office; it was unenthusiastic.

By 1898 Marconi had successfully demonstrated overland and ship-toshore communication and had formed the Wireless Telegraph and Signal Company Limited. From time to time, communication across distances of up to 100 miles could be established. Yet therein lay an enigma. Hertz's early experiments showed that the invisible "wireless" waves obeyed the laws of light and travelled in straight lines. How, then, could Marconi communicate beyond the visible horizon? The scientific community regarded Marconi's experiments with caution.

The Post Office monopoly on long distance telegraph communication and other restrictions made it impossible for Marconi to set up a revenueearning inland wireless telegraph service. His company was rapidly going bankrupt. What to do?


### the transatlantic gamble


Marconi had two ambitions: one, to prove his system offered dependable long-range capability and two, to compete directly with the Post Office, breaking its monopoly, and maintaining a profitable wireless telegraph service. He conceived a bold stunt to draw attention to his plan: he would send a wireless signal across the Atlantic! Marconi proposed a station of breathtaking power, size, cost, and complexity. It was like proposing to build a cathedral in a world which had seen nothing more grandiose than a log hut. The directors of his company objected to taking such a risk. His grand idea was met with scorn and disdain.

But Marconi convinced his colleagues to go along with his plan. The station, to be built in Poldhu, Wales, was staggering in concept; a 25 kilowatt power plant would drive a twostage spark transmitter (fig. 1) connected to a 400-wire antenna supported by 20 masts, each 200 feet high.

By early 1901 the station began to take shape. Preliminary tests indicated a range of at least 225 miles. Despite a myriad of troubles, the station could be heard as far away as Ireland. It had already proven that wireless waves followed the curvature of the globe; Marconi was certain that his signal could be extended to North America.

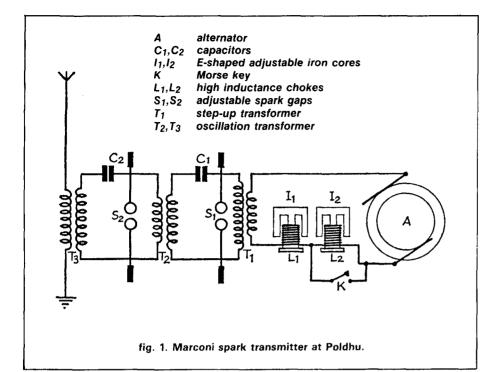In March, 1901, Marconi sailed for America and chose the site for a second station: South Wellfleet, a small town on the eastern shore of Cape Cod, Massachusetts. Leaving his chief engineer there, Marconi returned to England.



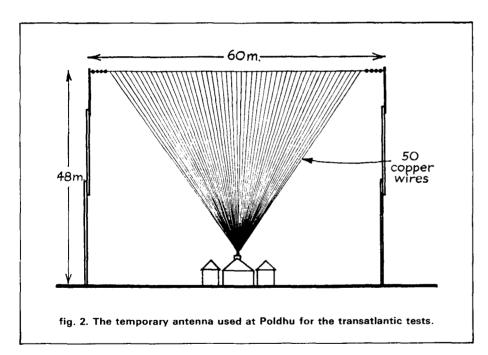

Catastrophe struck in September when a vicious gale hit the coast of Wales, breaking one of the many guy wires. All 20 masts collapsed into a shambles of broken timber and tangled wire. Just a month later a second storm destroyed the antenna system at South Wellfleet.

The directors of the Marconi Company were appalled. Over a quarter million dollars had been spent with nothing to show for it but chaos. Marconi would not give up; he cleared away the wreckage, erected a temporary antenna (**fig. 2**) and had the station back on the air in 11 days.

Because of the diminished capacity of the makeshift station, Marconi decided to abandon the Wellfleet site and set up temporary receiving equipment in Newfoundland, the point of landfall nearest to Wales. In great secrecy he set sail for St. John, with a small stock of kites and balloons to keep a single wire aloft in the stormy weather.


A site was chosen on Signal Hill, and on December 9 the apparatus was assembled in an abandoned military hospital. The balloon was prepared for inflation and ground plates were buried. A cable was sent to Poldhu requesting that the Morse letter "S" be transmitted continuously from 3 to 7 PM. Marconi chose his message wisely. He knew the fragile state of his equipment, and that the transmission of dashes, rather than dots, would have imposed too great a strain on the keyer and the transformers.

On December 10th the weather was fair. A balloon-supported kite antenna was sent aloft. The transmissions started at a power level of about 10 kilowatts and on a wavelength of about 366 meters (820 kHz). Since there was no means of measuring frequency, the actual wavelength remained a matter of speculation.

As the wind picked up, the balloon bobbed and weaved about in the sky above Signal Hill. Marconi adjusted his new "syntonic receiver" — a glass tube within which a globule of mercury was held between two iron or carbon rods, forming a crude semiconductor. Nothing which could be identified as the letter "S" could be heard amid the static. The wind picked up and the antenna crashed to earth as the balloon was swept away.
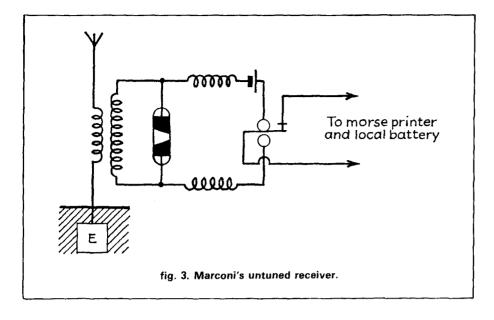
### December 12, 1901

On the 12th the wind increased in intensity. A kite was launched bearing a 510-foot wire. The wind carried it away. A second kite was launched with a 500-foot wire attached. Because he had observed that the buffeting of the antenna by the wind made it impossible to keep the newer receiver in tune, Marconi sat listening intently at an older, untuned receiver (**fig. 3**). Time slipped by. Suddenly, at 12:30 PM, Newfoundland time, he handed the earphone to George Kemp, his



assistant, and quietly asked, "Can you hear anything, Mr. Kemp?"

George Kemp took the headphone. Through the static crashes he could hear, faintly, the unmistakable rhythm of three clicks, followed by a pause, then three more and a pause, and so on, until — all too soon — the signals were lost once more in static. Marconi, a cool-headed man if there ever was one, wrote in his laboratory notebook: Sigs at 12.20, 1.10 and 2.20.

### Marconi a fraud?

Marconi was in a quandry. What conclusive proof did he have? He and Kemp were not exactly unbiased. Should he make a public statement?

Finally on December 14th Marconi cabled his company the news. It was made public on December 16th, 1901.

The first reaction came from the lawyers of the Anglo-American Telegraph Company, whose cable line had carried the message to England two days previously. It was sharp and to the point. Marconi was told that the company had a monopoly on communication in Newfoundland and it forbade any future infringement of their rights under pain of legal action.

The public interest, however, was aroused and both the Canadian and American governments expressed interest in the experiment. The technical journals treated the incident with a combination of skepticism and indignation. Marconi had no proof to substantiate his claim, which challenged the fundamental laws of physics and the proven knowledge of Newton, Maxwell, Hertz, and others. It was not until later, when the reception of signals across the Atlantic was demonstrated beyond any shadow of doubt, that Marconi's achievement was recognized.

Even today, it is difficult to believe that the 366-meter signals could actually have been heard. The receiving equipment after all, consisted of an inefficient antenna coupled to an untuned receiver which had no means of amplification whatsoever and was even less sensitive than crystal detectors, which evolved a few years later. If, in fact, the wavelength was 366 meters, the tests took place at the worst possible time of day because the entire path would have been in daylight. Today we know that radio signals can travel across the Atlantic and far beyond. But in 1901, anyone who believed that they could, and did, believed so as an act of faith based upon the integrity of one man -Marconi.

### Marconi at the World's Fair

It was 1932. Marconi, an internationally acclaimed scientist, inventor, and businessman was in the United States. He was scheduled to make an official visit to the Chicago World's Fair, a breathtaking exhibition of the modern world of technology. Fair officials were in a dither as Marconi arrived in the company of other important dignitaries. The Great Man toured the Fair, expressing great interest in the scientific exhibits. News photographers crowded around Marconi and he was followed by a large gathering, all craning their necks to see the Father of radio communication.

As he was about to leave, Marconi expressed a wish to visit the Amateur Radio station at the Fair. So, Marconi's big, black limousine, with colorful American and Italian flags flying from the fenders, drew up in front of a building on the edge of the fairground, followed by a horde of officials and newsmen. Marconi was escorted up the stairs to the World's Fair Amateur station, W9USA.

The young operators of W9USA appeared thunderstruck as the famous visitor strode into the station, introduced himself, and studied the homemade kilowatt trasmitter and the superheterodyne receiver. He examined the station log book. The Fair officials were mystified by the incomprehensible collection of equipment that seemed to fascinate Marconi.

One of the operators apologized to Marconi, saying that the equipment had been built by mere Radio Amateurs. Marconi nodded and smiled, shaking the hand of the operator warmly. "Yes, yes," he said. "I understand — after all, I am a Radio Amateur myself."

### radio silence

Marconi died in July, 1937. On the evening of the following day, at the state funeral in Italy, the Italian Radio Service observed an official period of radio silence. In England, and throughout the world, thousands of radio stations — broadcast, commercial, and Amateur — fell silent. The radio silence which Marconi had broken when he switched on his first transmitter came down in sorrow at his passing. Shortly before he died, Marconi, in an address at St. Andrews University in Edinburgh, Scotland, stressed his original intention to make the high seas safe by giving ships a means of communication. Then, perhaps talking more to himself than to his audience, he added, "Have I done the world good — or have I added a menace?"

#### in retrospect

Much speculation has taken place during the decades following Marconi's famous transatlantic experiment. lonospheric studies and a review of the sunspot cycle suggest that propagation across the Atlantic at that time of day, in that month and year, was highly unlikely on 820 kHz.

What, then, might Marconi and his assistant have heard? A few clues exist. Marconi's spark transmitter emitted a rough wave, high in harmonic content. He used a broadband (untuned) receiver. Perhaps Marconi was not hearing the fundamental transmitter signal, but instead a harmonic of the signal, in particular the fourth harmonic on about 3280 kHz. If that is so, then a few hundred watts of harmonic power would have easily made the transatlantic journey.

Of course, with a broadband receiver, Marconi could have heard many harmonics at the same time! So we shall never really be sure what transpired on that stormy day in Newfoundland. It is interesting, however, to think that if Marconi had elected to listen to his tuned receiver, used in the previous day's unsuccessful tests, he might have heard nothing at all!


### acknowledgements

Thanks to the Official Historian of the Marconi Company (England) for the background information on Marconi's early experiments. The story of Marconi's visit to the Chicago World's Fair appeared in the November, 1932 issue of *QST*.

\*Drawings adapted from A History of the Marconi Company by W.J. Baker, Methuen & Co., Ltd., London, 1970. (Distributed by the Marconi Co., Ltd.) ham radio



141

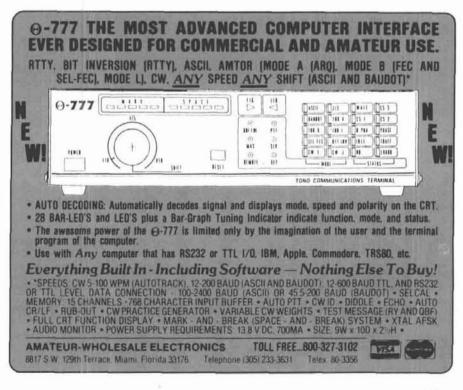

r 140

"I am very pleased with my Cayson Satellite TV System. I recommend it to anyone interested in Satellite TV,"

> Champion Race Car Driver BOBBY ALLISON

# CAYSER I CENTURION ANTENNAS

WITH



Look to Cayson Electronics for durable and accurate satellite antennas. We are pioneers in the business and still growing. Here are two 10' antennas that you can be sure are winners.

The four-piece fiberglass features a highly reflective aluminum foil material for superior reception. The heavy duty polar mount utilizes a 3½ OD ground pole. This antenna has been around since 1979.

The 10' aluminum mesh antenna is becoming more popular for those who value attractive satellite equipment. The two-tone reflector features black mesh and aluminum ribs. The mount has declination adjustment and also uses a 3½ OD ground pole.



10 FT. MESH DATA		
TYPE	EXPANDED MESH	
WEIGHT	135 LBS. UPS	
DIAMETER	127″	
FOCAL DISTANCE	431/2"	
f/D	.35	

### CAYSON ELECTRONICS

Rt. 3 Box 160 • Fulton, MS 38843 2235 W. Mound • Decatur, IL 62526 Nation Wide 1-800-892-4916 1-800-382-1811 In MS 1-601-862-2132 In IL 1-217-877-7954

10 FT. FIBERGLASS DATA				
TYPE	4-PIECE FIBERGLASS			
WEIGHT ( APPROX.)	200 LBS. SHIPPED			
DIAMETER	122"			
FOCAL DISTANCE	43"			
f/D	.35			

/ 215

# a sloping terminated vee beam

Low SWR across ham and SWL bands

This is the antenna that every ham has probably dreamed about: a beam antenna that works on every Amateur band and on all the spaces in between . . . an antenna that's cheap and requires just a single tree or pole for support . . . an antenna that doesn't require precision measurements, special tuning instruments, or almost anything else out of the ordinary. *Everything* needed can be purchased inexpensively or built at home, and the hardest part will be building a toroid transformer with about 25 turns of wire.

This is the same antenna used as a back-up by the Voice of America, so you know it works.

According to transmission line theory, a single conductor placed a few feet above and parallel to the ground can be used as an antenna. If the wire is raised more than a few feet above ground, the impedance approaches a value of 400 ohms according to the following formula:

$$Z_0 = 83.7 \log_{10} (4H/d)$$
 (1)

where  $Z_0$  = impedance of single wire above ground

- H = height of the wire above ground in any units
- d = diameter of the wire in the same units

The nonresonant "vee" antenna and a large family of

similar antennas such as rhombics are based on transmission line theory. When used as an antenna, however, the transmission line has spacing which is large compared with normal lines. As a result it is leaky and can be used as an antenna. The radiation field from a single wire transmission line may be calculated<sup>1</sup> and the two maximum gain lobes discovered by the equation:

$$E(a) = \frac{60 \sin a \cdot \sin \left[\frac{\pi L}{W} (1 - \cos a)\right]}{1 - \cos a}$$
 (2)

where E(a) = normalized field strength at angle a

a = the angle from the axis of the wire  $\pi = 3.1416$ 

= length of the wire in any units


L

W = one full wavelength in the same units

If two terminated transmission lines are aligned so that the major lobes of each wire are additive, the lines then become a "vee" antenna. (Two vees placed end-toend form a rhombic.) Because the line is terminated in a matching impedance, the wires are nonresonant — just like any correctly matched, well-behaved transmission line — and the antenna will accept power at any frequency.

Several good things happen with terminated transmission line antennas. One desirable result is broadbanding operation; another is that the reverse lobes (toward the pointed side of the vee) are cancelled or greatly reduced. The resulting antenna can be used to both transmit and receive at every frequency within its range, much like a log periodic antenna. But, it will

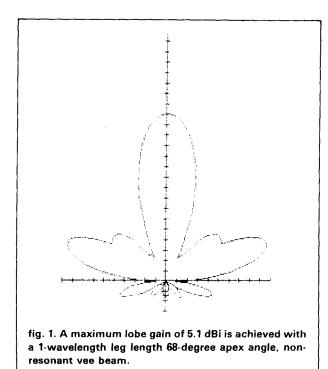
By Robert Ross, 17904 Muncaster Road, Derwood, Maryland 20855




vee leg length in half waves	apex angle in degrees	gain in dBi
2	68	5.1
3	56	5.7
4	48	6.1
5	44	6.4
10	32	7.4
20	22	8.4

produce its best gain only over a relatively narrow frequency range where the major lobes align for best gain. This frequency range depends on the angle of the apex of the vee and the length of the legs. For many purposes, +100 percent to -50 percent frequency excursion is reasonable, (see **table 1**). The worst thing that happens is that the beam splits and you find a null in the center with the gain lobes on either side.


In this case the vee has been optimized for the 14 to 15 MHz band — but it also works reasonably well from 40 to 10 and even radiates modestly on 160 and 80 meters. Optimization can be done for any band by calculating the major lobes and adjusting the apex angle for that band. Ordinarily, however, not much is gained by changing the apex angle of such a short vee. **Figures 1** through **6** illustrate the azimuthal pattern of vee beams with leg lengths from 1 to 10 wavelengths.

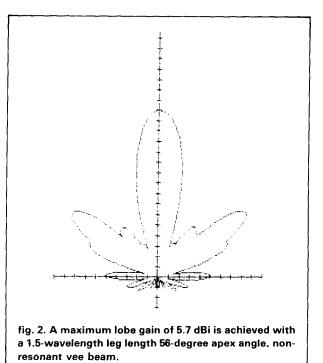

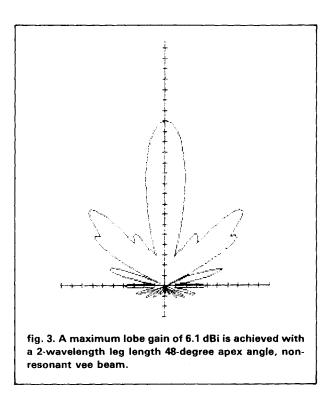
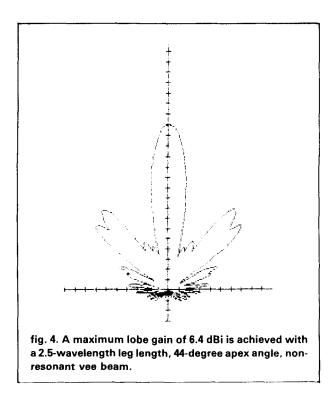
### construction is easy

The vee is probably the simplest of all wide band beam antennas to build. A single support roughly 65 feet (20 meters) tall is required for the high end and two supports about 3 feet (1 meter) tall for the low ends. The only critical item is the pointing of the





antenna. The position of the two low point anchor poles must be selected to direct the antenna at your target by using a compass bearing corrected for local magnetic variations. In Washington, D.C., the variation is 8 degrees west; thus 8 degrees must be added to the compass reading to get a true bearing. The legs must be located so that they are 22 degrees on either side of the great circle line of bearing to your target and to make the open end of the vee point toward the target. For example, on my globe London and Europe are 48 true (not magnetic) degrees from Washington, D.C.
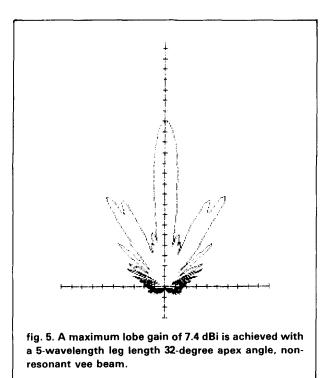
### materials are inexpensive

The wire and insulators can be of almost any kind. However, I prefer No. 14 AWG copperweld wire and No. 500 strain insulators (also known as guy wire insulators). Strain insulators are particularly good if you use a tree for your antenna pole because they won't break when the tree sways in the wind. I also advise soldering all antenna connections to avoid long-term problems from corrosion and the resulting bad connections.

The transformer can be purchased from at least one company for about \$150,<sup>2</sup> but building your own transformer is not difficult. Only a few turns of wire on a 2-inch diameter RF toroid core will do the job.<sup>3</sup> Generally the largest RF toroid core which the manufacturer says will cover the desired frequency range will work reasonably well. On my transformer I used 20 turns of soft No. 12 AWG enameled copper wire for the sec-



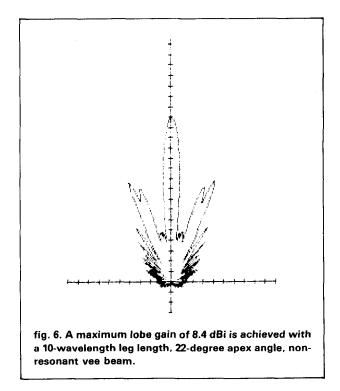

ondary, spacing it evenly around the core and making sure that there were at least a few millimeters between the two wire ends to prevent RF voltage flash-over. If you leave the ends of the secondary about two feet long you can also use them for antenna connections later. Anchoring the wire in place with silicone rubber is a messy but a very effective measure. Then slip

# POCKET SIZE FAST CHARGER

Fast charge your hand held radio battery packs to full capacity in as little as 45 minutes. Example: Fully charge I-COM BP-3 in 30 to 45 minutes.

VERSATILE - Works on 115V, A.C. or 12V, to 24V. D.C. and turns itself off automatically when battery reaches full capacity. Use at home or in auto, airplane, boat, R.V. or anywhere there is house current or 12V. to 24V. D.C. available.

### FEATURES -

1. New Hybrid thick film integrated circuit developed for this charger contains all measuring and control circuitry in a single chip. Laser trimmed precision resistors.

- 2. Small size can be carried in your pocket.
- 3. High impact molded plastic case.
- 4. Reverse polarity protection built in
- 5. Internally fused.
- 6. Full 1 year warranty.

7. Completely solid state circuit measures charge constantly and turns off automatically when cells reach full capacity.

8. Charges at optimum rate without any perceptible heating of cells.



Price \$65.00 Dealer inquires invited

19780 Temescal Canyon Corona, Calif. 91719 (714) 734-6179 143 Mail orders to: P.O. Box 2679 Corona, Calif. 91718

### **BEAM ANTENNA HANDBOOK** by Bill Orr, W6SAI

Recommended reading. Commonly asked questions like: What is the best element spacing? Can different yagi antennas be stacked without losing performance? Do monoband beams outperform tribanders? These questions and more are fully answered. Lots of construction projects, diagrams, and photos. 198 pages. © 1983. 5th edition. RP-BA

Softbound \$7.95

### SIMPLE LOW-COST WIRE ANTENNAS by Bill Orr, W6SAI

Learn how to build simple, economical wire antennas. Apartment dwellers take note! Fool your landlord and your neighbors with some of the "invisible" antennas found here. Well diagrammed. 192 pages. ©1972, 2nd edition

### BRP-WA

Softbound \$7.95

### THE RADIO AMATEUR ANTENNA HANDBOOK by William I. Orr, W6SAI and Stuart Cowan, W2LX

Contains lots of well illustrated construction projects for vertical, long wire, and HF/VHF beam antennas. There is an honest judgment of antenna gain figures, information on the best and worst antenna locations and heights, a long look at the quad vs. the yagi antenna, information on baluns and how to use them, and new information on the popular Sloper and Delta Loop antennas. The text is based on proven data plus practical, on-the-air experi-ence. 190 pages. ©1978. 1st edition. CRP-AH Softbound \$7.95

# ALL ABOUT CUBICAL QUAD ANTENNAS by Bill Orr, W6SAI - New 3rd Edition

Includes NEW data for WARC bands The cubical quad antenna is considered by many to be the best DX antenna because of its simple, lightweight design and high performance. You'll find quad designs for everything from the single element to the multi-element monster quad. There's a wealth of data on construction, feeding, tuning, and mounting quad antennas. 112 pages. © 1982. 3rd edition.

CRP-CO Softbound \$6.95 Please add \$1.50 for one book, \$2.50 for two or more books to cover shipping and handling.

Ham Radio's Bookstore Greenville, NH 03048

some tube insulation over a second piece of the No. 12 AWG enameled wire and wrap five primary turns evenly over the outside of the first twenty turns. Getting even a semblance of a smooth wrap will be the hardest thing you'll have to do for this antenna. Again, use some silicone rubber to tack down the primary and give it at least twenty-four hours to harden. After stripping the enamel from the ends of toroid primary wire, solder on the coax connector of your choice. Resist the urge to use the hole through the middle of the toroid to hold up the high end of the antenna or attach the coax - powdered iron cores are brittle and are subject to breaking at the most inconvenient times.

The 390-ohm termination resistors, are noninductive resistors made specially for terminating antennas, and are available from electronic wholesalers,<sup>4</sup> at ham fests (your best chance) or at surplus houses. On the other hand, you can also make a 200-watt terminating resistor out of one-hundred, 2-watt, 39 kilohm, carbon composition resistors. A simple way to do this is to lay out two tinned No. 12 AWG wires spaced the width of the resistor body and solder the 100 resistors to them.

Operating this antenna is pure joy. It loads my transmitter well from one end of the short wave bands to the other. My antenna also shows a maximum of about 1.5:1 SWR on 15 meters and about 1.2:1 maximum on all other bands. Adding or subtracting a turn or two on the transformer optimizes the SWR for any desired frequency.

At last I have an antenna that works smoothly from 160 to 10 meters and even works as an effective allband antenna for my general coverage short-wave receiver. For cost and coverage, it's hard to beat this nearly foolproof sloping vee beam.

### references

1. Landee, Davis & Albrecht, Electronic Designers Handbook, McGraw-Hill, New York, 1957, (see section 21).

2. The vee antenna feeding transformer, 1.8 to 30 MHz, is available from Apcom Inc., 625 Loffstrand Lane, Rockville, Maryland 20850, (301-294-9060). Note: this company and others will supply the complete antenna, mast, ground rods, earth anchors and everything else, optimized for your frequency and adjusted to fit various larger pieces of land. This is a good deal for commercial stations, but the cost is very high by ham standards.

3. Type F240-Q1 toroid core to cover 1.8 to 30 MHz is available from Amidon Associates, 12033 Otsego Street, North Hollywood, California 91607, or Palomar Engineers 1924-F W. Mission Road, Escondido, California 92025.

4. Carborundum Co., Graphite Products Division, Box 339, Niagara Falls New York 14302. Please note that this is a manufacturer, not a retail outlet. If you can put together a large order, then request noninductive resistor type 888SP, 390 ohms (2 for each antenna). If more power is required, order type 891SP, 450 ohms (2 for each antenna).

# ham radio

# PACKET MADE

Suggested Retail \$389.95

# Kantronics Packet Communicator"

Kantronics wants you to join one of the fastest growing segments of Amateur Radio today . . . Packet Radio. With the Kantronics Packet Communicator we've made getting on Packet as easy as getting on RTTY.

The Kantronics Packet Communicator is a fully assembled and programmed terminal node controller ready for operation. Simply connect the Packet Communicator to the Serial TTL or RS232 port of your computer, and the microphone and external speaker jacks of your transceiver. The power supply, cables, and most connectors are included.

PACKET

COMMUNICATOR

12

The Kantronics Packet Communicator has both the AX.25 and Vancouver protocols, making it

Because the Kantronics Packet Communicator uses internal microprocessors for protocol and signal processing, the operator simply follows procedures and commands outlined in the operators manual.

POWER

Kantronics

Any communications or terminal program, like those used with telephone modems, can be used to set up the computer to communicate with the Packet Communicator. Special Packet Terminal (Pac-Term™) programs for many popular personal computers will be available soon from Kantronics.

compatible with most existing Packet terminal node controllers. Added features include both Bell 103 and 202 tones, and the ability to use the unit as a 1200 baud radio modem without special protocols.

Error free data communication via computer makes Packet Radio technology exciting, and the Kantronics Packet Communicator lets you get in on the action.

For more information contact your local Kantronics dealer, or write Kantronics.

awrence, Kunsas 66046

CAR

# <u>NENCONNENCONNENCONN</u>EN

# **KOKK** DO YOU HAVE AN HEIRLOOM RADIO?

Well... they might not last forever. However, there are certainly many older model KDKs out there in 'Ham Radio-land' just chuggin away. Every day calls come from all over asking for information and advice on care and feeding of an FM-144sx or a '2015 and there are even a few older than that but some of them seem to be in disguise. That's a tribute to the folks who design and make the KDK. They care about building a radio to last longer because their name and their pride are on the front of each one. BUT . . . What we are really getting to is we would really like for all you folks who have known and loved your KDK's all these years to go and update yourselves by purchasing a newer KDK, one like, say, the FM-2033 or maybe an FM-7033 UHF. That way you can start your own collection of heirloom KDK radios. Right there in your own hometown. Take a look at the chart of available models and visit your nearest KDK dealer and check them out. We think you will drive home with one.



SPECIFICATION	FM-2033 144 MHZ	FM-4033 220 MHZ	FM-7033 440 MHZ	FM-6033 50 MHZ				
NUMBER OF MEMORIES Memory Scanning Band Scanning	Memories may be scanned	10 Memories + CALL CHANNEL organized as two banks of 5 channels each. (CH 1-5, CH 6-10, CALL.) Memories may be scanned A(1-5), B(6-10), A+B(1-10) or A×B(1-5) Programmable band scan between values loaded into memories 5 and 10, step size set in INIT module.						
FREQUENCY RANGE OUTPUT POWER HI/LO REPEATER OFFSET SUB AUDIBLE TONE SENSITIVITY BANDWIDTH SELECTIVITY	142.000-149.995 MHZ 25/2.5 Watts 600 kHZ UP or Down 103.5 @ 500 Hz Dev 0.2 uV @ 12dB SINAD ±5 kHZ @ -6 dB ±12.5 kHZ @ -60 dB	220-224.995 MHZ 25/2.5 Watts 1.6 MHZ UP or Down 103.5 @ 500 Hz Dev 0.35 uV @ 12 dB SINAD ±5 kHZ @ -6 dB ±12.5 kHZ @ -60 dB	440-449.975 MHZ 10/2 Watts 5 MHZ UP or Down Dipswitch Select 0.4 dB @ 12 dB SINAD ±5 kHZ @ -6 dB ±12.5 kHZ @ -60 dB	50.00-53.995 MHZ 10/2 Watts 600 kHZ UP or Down 103.5 @ 500 Hz 0.2 uV @ 12 dB SINAD ±5 kHZ @ -6 dB ±12.5 kHZ @ -60 dB				


MAXPAC STACK

# THL CORP.

AMPLIFIERS • PREAMPS • COUPLERS

TEAM THL LINE-UP FOR '85 SEASON

TEAM THL brings competition class performance to everyday operation. Whether you're looking for a little more performance or a "super-charger" boost, TEAM THL products can get you out of the pits and back in the race better and faster almost every time. Three different power performance classes in either VHF or UHF band capability give the TEAM THL a broad spectrum of performance options. So remember the next time you get beat in the race, soup-up yourself with a product from TEAM THL.

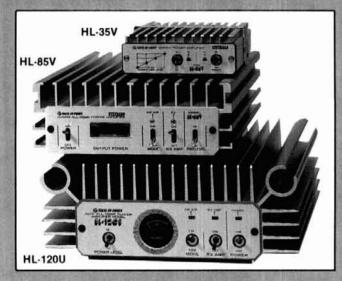

Specifications	HL-30V	HL-35V	HL-35VL	HL-85V	HL-110V	HL-160V	HL-160V25	HL-20U	HL-30U	HL-60U	HL-1200
Pre-Amp Type	N/A	Gaas-FET	Gaas-FET	Gaas-FET	Gaas-FET	MOS-FET	MOS-FET	N/A	Gaas-FET	Gaas-FET	Gaas-FET
Power Metering	N/A	LED	LED	Meter	Meter	Meter	Meter	N/A	LED	Meter	Meter
Input (Watts)	.25-5	.25-5	.25-5	10-14	3-14	3-14	20-30	.1-4	1-4	8-14	8-14
Output (Watts)	2.5-30	2.5-30	2.5-30	70-90	90-110	140-160	140-160	18-22	25-30	45-60	90-110
SSB Mode	NO	NO	YES	YES	YES	YES	YES	YES	NO	YES	YES
Sugg. Retail	\$69.95	\$79.95	\$89.95	\$169.95	\$239.95	\$349.95	\$299.95	\$114.95	\$129.95	\$229.95	\$379.95

2000 Avenue G, Suite 800, Plano, Texas 75074 Phone (214) 423-0024 TLX 79-4783 ENCOMM DAL



Priced at a level to make your budget smile, the ST-200ET and the ST-400ET are direct hardware replacements for the famous ICOM\* series of thumbwheel switched hand held radios. Present accessories for the 2AT and the 4AT should work on the ST-200ET (VHF) and ST-400ET (UHF) with no modifications.\*\* Same slip off battery pack style and the same mic and speaker jack arrangements provide as much compatibility as possible.

These units are made in Japan and sold by SANTEC and backed by the famous Encomm TWO YEAR EXTENDED SERVICE PLAN and Encomm service facilities located in Plano, Texas. Priced at \$199.95 for the ST-200ET (VHF) and \$249.95 for the ST-400ET (UHF). No it's not a misprint. Those are the Suggested retail prices. Now smile. Please see your favorite SANTEC dealer for his best price.



SPECIFICATION	ST-200ET	ST-400ET
GENERAL		
Frequency Range	144-147.995	440-449.995
Battery Pack (V/mAHr)	8.4/250	8.4/250
Receive Squelched Norm	18 mA	22 mA
RX At Full Volume	130 mA	130 mA
Transmit (Low Power)	220 mA	300 mA
Transmit (High Power)	550 mA	700 mA
Dimensions mm	$60 \times 170 \times 40$	$60 \times 170 \times 40$
Weight (with Battery)	490 gms	490 gms
TRANSMITTER		
Output Pwr. (Hi, Lo)	1.5W, 0.15W	1.5W, 0.15W
Spurious Transmitted	< - 60dBc	< - 60dBc
Deviation Limit	5 kHz	5 kHz
Pickup Device	Condenser Mic	Condenser Mic
RECEIVER		
Receiving System	Dbl. Superhet.	Dbl. Superhet.
I.F. Frequencies	10.695 1st	21.6 1st
	455 kHz 2nd	455 kHz 2nd
<b>Receive Sensitivity</b>	<0.25 uV @ 12dB	<0.35 uV @12 dB
I.F. Bandwidth	30 kHz @ - 60dB	30 kHz @ - 60 dB
Operating Temp	-10-+60 C	- 10- + 60 C

**SKT-BA Battery Case** SKT-PA DC/DC Conv. ST-MC Mobile Charger **SKT-LC** Leatherette Case HSA-1/HBM-1 Headset/Mic **STK-BP Battery Pack** STK-BC Battery Charger

NOTICE: These specifications are typical unless stated otherwise. They may be changed in the future without notice or obligation. Conditions of measurement may be obtained from Encomm, Inc.

\* ICOM is a registered trademark of ICOM, INC of JAPAN. \*\* ST-200ET/400ET Batteries are not fully compatible with BC-30/35 drop in chargers.

# WELZ CORP. PEP • POWER • VSWR COMPACT STYLE SUPERIOR ACCESSORIES

These new compact HF/VHF/UHF meters from WELZ provide multi-mode operation in auto or home station. Utilizing the WELZ toroidial core based wide-band sensor technology, these VSWR/POWER meters are the next generation of accuracy and reliability. Pictured here is the model SP-420 covering the VHF/UHF band from 140-525 MHz. In addition there is the SP-220 covering 1.8 to 200 MHz and the SP-122 covering 1.6-60 MHz with PEP peak hold mode. All three of these new models are ready for PEP output measurement with either the "PEP Monitor" function or the "Instantaneous PEP HOLD" function, back-lighted easy-to-read meters, high sensitivity and very attractive styling. Check your favorite dealer and check out the new WELZ COMPACT VSWR/POWER meters.

MODEL	SP-122	SP-220	SP-420	SP-230	SP-430
Freq. Range Sensor Mnt. Pwr Ranges No. Meters	1.6-60MHZ FIXED 20/200/2KW	1.8~200MHZ FIXED 2/20/200	140 ~ 525MHZ FIXED 2/20/200	6-1400MHZ DETACHABLE 15W/150W	1.8 ~ 150MHZ DETACHABLE 5W/60W 1
Peak Mode? Impedance Functions	YES + HOLD 50 OHMS PWR/VSWR	YES 50 OHMS PWR/VSWR	YES 50 OHMS PWR/VSWR	NO 50 OHMS PWR/VSWR	NO 50 OHMS PWR/VSWR
Accuracy	PEP + HOLD 10% READING	PEP 10% READING	PEP 5% READING	5% F.S.	CAR VOLTS 5% F.S.

SP-122 HF PEP HOLD SP-220 HF PEP MONITOR SP-420 VHF/UHF PEP MONITOR



2000 Avenue G. Suite 800, Plano, Texas 75074 Phone (214) 423-0024 TLX 79-4783 ENCOMM DAL



Doctor QSO™ Is The Code Buster

DOCTOR QSO" Part

101111111111



# Doctor QSO Relieves All Symptoms Of Morse Code Phobia!

Doctor QSO™ is a plug-in cartridge for the Commodore 64 computer that provides a very realistic simulation of on-the-air two-way Morse Code ragchew contacts (QSOs). AEA, the undisputed leader in Morse training, has introduced Doctor QSO to amateur radio for the purpose of making Morse skill upgrading FUN and EASY. With Doctor QSO you can look forward to practicing your Morse Code skills in a non-confusing manner. Forget about all the drudgery you associated with Morse Code in the past; Doctor QSO ushers in a totally new era in Morse Code learning.

Doctor QSO is based on the same technology that has made the Doctor DX<sup>™</sup> contest trainer so famous. The Doctor QSO simulator is so realistic that most skilled operators find it every bit as rewarding as the real thing. You can operate anytime you want; the only extra equipment you need is a Commodore 64 and a TV set.

Doctor QSO also removes the mystery of the CODE BEHIND THE CODE. Many people go so far as to learn the Morse Code characters, only to be frightened of getting on the air the first time because the QSO format is so confusing. With Doctor QSO, you will be a pro before you turn on your first transmitter. The Doctor QSO trainer/simulator is ideal for the aspiring Amateur Radio operator with little or no contact with helpful hams.

With Doctor QSO you will become familiar with all the U.S. call areas and associated call letter prefixes. The standard international QSO format is observed along with all the common amateur radio abbreviations which are explained thoroughly in the operator's manual. All Morse skill levels are addressed by Doctor QSO, from the person who has not yet learned the Code, to the person comfortable with sending and receiving at 40 + WPM.

Who says Morse Code can't be fun? You can even have fun with Doctor QSO before you have learned the Code. To begin with, the operator can view the messages being sent by the computer generated stations in real-time. The operator can also send Morse with the keyboard. In addition, the operator can select simulation of static interference (QRN) and adjacent CW interference (QRM). Normally, the beginner would operate in the novice band where stations will be sending as slow as 3 WPM. Later as the user becomes more skilled, he can move down the band to faster speeds, and he has the choice of using a key or keyer for sending.

If you have tried every other method known to learn the Morse Code and failed, then Doctor QSO has just the prescription for you. Now you can upgrade your Amateur Radio license in record time. Doctor QSO is more than the written word can describe. To fully appreciate all the merits of this trainer, see your dealer for a demonstration or contact AEA for more information.

Prices and specifications subject to change without notice or obligation.

Advanced Electronic Applications, Inc. P.O. BOX C-2160 • LYNNWOOD, WA 98036 (206) 775-7373 • TELEX: 152571 AEA INTL

/ 145

Brings you the Breakthrough!



## what's this Sporadic E?

In these minimum years of the 10.7-year sunspot cycle when the 10-meter band is at best open only a few hours per day and only to the southern directions for long skip, it's still possible for propagation modes to exist on 6 meters and occasionally even the 2-meter band for short-skip openings. Signals appear suddenly, out of nowhere, and frequently rise to amazing strength. They may stay in for just a few minutes at a time - or the band may remain open for hours. Occasionally in June or July DX signals might be heard around the clock. Signals can be received from distances of 500 to 1200 miles and occasionally, due to multiple reflections, from distances as far away as 2500 miles.

How do you recognize such  $E_s$  openings? Say you're monitoring a beacon. The band is quiet. Suddenly you hear a buildup of "antenna noise." Almost instantly there are DX stations all over the band. Signal levels fluctuate rapidly as the session opens and as it declines. When the signal is there it usually pegs your S-meter, but it is also subject to rapid fades on the order of 60 dB or more that chop it into a garbled mess.

One way to recognize the probable opening of Es on 6 meters was reported by George Jacobs, W3ASK, in the June, 1962, issue of CQ. Working a lower frequency band, say 15 or 10 meters, listen to the stations being worked. If the minimum skip distance is decreasing, the skywave geometry is such that the maximum usable frequency will be increasing by reflection from an E<sub>s</sub> (more dense than F2 and lower height) cloud. W3ASK's rule of thumb states that when stations are heard less than 500 miles away on 10 meters, or less than 350 miles on 15 meters, the chances are good that 6 meters will open in that same direction. It's worth a try! (More on  $E_s$  DXing next month.)

### last-minute forecast

DX conditions on the higher HF bands, 10 through 30 meters, are expected to be very good the first two weeks of the month and also again during the last week of this five-week month. The propagation at these times can be via long-skip if the radio flux is very high -- above about 85 units. Sporadic E (E<sub>s</sub>) short-skip is expected to occur occasionally, with the probability of occurrence increasing as the month goes by. The middle two weeks of the month will offer the best nightime DXing. Geomagnetic disturbances are expected to occur around the 4th through the 8th and again on or about the 15th. Concurrently, the thunderstorm noise background level will also be higher on the lower bands.

Moonbounce DXers can take advantage of the lunar perigee (and full moon) that will occur on the 3rd and 4th of this month. An Aquarid meteor shower of interest to meteor-scatter and meteor-burst DXers peaks between May 4th and 6th with rates of 10 and 25 per hour for the Northern and Southern Hemisphere, respectively.

Two eclipse events are calculated to occur in May. The first is a total eclipse of the moon on May 4 from 1817 to 2135 UTC. The path of its shadow starts near New Zealand and travels west through Australia, Asia, Africa into the Atlantic Ocean. The width extends from the Antarctic to Europe. The second event, partial eclipse of the sun, (with 84 percent coverage) will occur on May 19 from 1925 to 2342 UTC. Its path begins at Greenland, travels across Canada and then moves on to Alaska and Japan. The second eclipse provides an opportunity to evaluate propagation effects on the path between the United States and Europe. Schedule contacts for the day before the day of the eclipse and the day after. Compare signal strengths and quality on each band used (suggestion: try 40, 30, 20 and 15 meters). A club-coordinated effort is a good way to cover the bands needed.

### band-by-band summary

Six meters may provide an occasional opening to South Africa and South America by short-skip  $E_s$ . These will occur around local noontime, toward the end of the month.

Ten and fifteen meters will provide a few short skip  $E_s$  openings and many long-skip openings, especially during high solar flux conditions, to most areas of the world during daylight. Some transequatorial (TE) openings, associated with a mildly disturbed geomagnetic field may occur in the evening hours. This is about the last month that affords many good TE openings until next fall.

Twenty, thirty, and forty meters will support DX propagation from most areas of the world during the daytime and into the evening hours almost every day. Forty meters has joined this daytime DX group because of lower signal absorption, lower LUF (lowest usable frequency) during these sunspot minimum years. During unusually high 27-day solar flux days 40 meters may not be usable and both 30 and 40 meters may not be usable in the predawn hours after a high flux day. The DX on these bands may be either longskip to 2500 miles (4000 km) or shortskip Es to 1250 miles (2000 km) per hop. The length of daylight is approaching maximum, providing many hours of good DXing.

Thirty, forty, eighty, and one-sixty are all good for nighttime DX. Although the background thunderstorm noise is beginning to be noticeable these bands are still quiet enough to provide good DX working conditions. Sproadic-E propagation may be a contributing factor toward enhanced conditions at local sunset and will occur more often during the next three months.

# New From Butternut® **HF2V** DX The 80 & 40 Meter Bands

The HF2V is the perfect complement for the Ham who already has a beam antenna for 10-15-20 meters. Add 80 and 40 meters (160 meters with an optional resonator kit) with a trim-looking vertical that can be mounted almost anywhere.

With the decline in sunspot activity, the HF2V's low angle of radiation will get you DX on the low bands - - even when 10-15-20 meters are ''dead.''

Automatic bandswitching. No lossy traps. Double wall tubing on the bottom section. Stainless steel hardware. Full ¼ wavelength on 40 meters. Height: 32 ft. --Self supporting Power rating: legal limit VSWR: 2:1 or less


> 40 Meters: Full CW & Phone band 80 Meters: 90 kHz

Add-on resonator kits available for 160-30-20 meters.
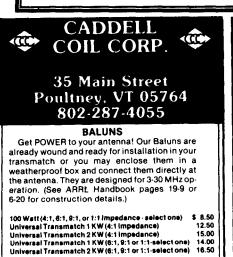
# Write for our FREE CATALOG.



BUTTERNUT ELECTRONICS 405 East Market Street Lockhart, Texas 78644 (512) 398-9019





### manship. • Safety - speed - convenience smooth travel. • Complete kit for 50' or less tower includes winch, cable, hardware and instructions. Hazer 2-Heavy duty alum. 12 sq.ft load \$297.00 ppd. Hazer 3-Standard alum. 8 sq.ft load \$287.00 ppd. Hazer 4-Heavy galv steel, 16 sq.ft load \$278.00 ppd. Hazer 4-Heavy galv steel, 16 sq.ft load \$278.00 ppd. As an alternative, purchase a Martin M-13 or M-18 aluminum tower engineered specifically for the HAZER system. GLEN MARTIN ENGINEERING INC. P.O. Box H 253 816-882-2734 147

 HAZER YOUR ROHN 25 G Tower
 Antenna and rotator mount on HAZER, complete system trams tower in verticle

 Safety lock system on HAZER operates while raising-lowering & normal position.

 Weight transferred directly to tower. Winch cable used only for raising & lowering. Easy

Will support most antenna arrays.
High quality materials & work-

upright position.

Never can fail.

o install and use.

# HANDI-HAM SYSTEM MANAGER (Amateur Radio System)

Courage Center, an internationally recognized leader in providing innovative services to physically handicapped children and adults for more than 50 years, is searching for a middle level manager to direct the operation of the Courage HANDI-HAM System. This unique program, providing training, education and radio equipment, is made available to disabled amateur radio operators worldwide who join a total network membership exceeding 5,000. Position qualifications include a bachelor's degree, 2+ years administrative experience, strong verbal and written communication skills, and a general or higher level amateur radio operator license. Resumes received in confidence. Appointment will be made as soon as possible after June 1st, 1985. For more information contact Todd Johnson, Director of Human Resources.



COURAGE CENTER 3915 Golden Valley Road Golden Valley, MN 55422 Equal Opportunity Employer



Presents

**"STATION MANAGER"** 

# ADVANCED

Professional Software For The Radio Amateur Terence L. Jones (KB8OA) Author

Stop At Our Booth At The Hamvention, Dayton, Ohio, April 26



	2300	2200	2100	2000	1900	1900	1700	1600	1500	1400	1300 000	1200	1100	1000	9900	9900	0700	0600	0500	9400	0300	0200	0100	000	GMT	
MAY	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	POT	
ASIA FAR EAST	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	- <b>&gt;</b> 2	
EUROPE	20	20	20	20	20	20	20	20	20	20	20	20	30	30	30	30	30	20	20	20	20	20	20	20	XA	
S. AFRICA	15	10	10	10	10	10	15	15	15	15	15	15	20	20	20	20	20	20	20	20	20	20	20	15	<b>1</b> m	۲E
S. AMERICA	15	15	15	15	15	15	15	20	20	20	20	20	20	20	20	15	15	15	10	10	10	10	10	15	SE 🖌	ST
ANTARCTICA	20	20	20	20	20	20	20	20	20	30	30	30	30	30	30	30	30	30	20	20	20	20	20	20	ه <b>مه</b>	ERN
NEW ZEALAND	10	10	10	15	15	15	15	15	20	20	20	20	20	20	20	20	20	15	15	15	10	10	10	10	S S	USA
OCEANIA AUSTRALIA	15	15	15	15	15	20	20	20	20	20	20	20	20	20	20	20	15	15	15	10	10	10	10	15*	<b>↑</b> ₹	Ø
JAPAN	20	20	20	20	20	20	20	30	30	30	30	30	30	20	20	20	20	20	20	20	20	20	20	20	12	
	6		ω	N	-	1	=	ă	ور	80	7	6	Ch .		ω	N		15	=	đ				6	Z	
	5:00	8	3:00	2:00	1:00	12:00	11:00	10:00	8		7:00	6:00	8	8	8	8	8	2:00	11:00	10:00	88	8	8	6:00	9	
ASIA FAR EAST	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	→ z	
EUROPE	20	20	20	20	20	20	20	20	20	20	20	20	30	30	30	30	20	20	20	20	20	20	20	20	N M	
S. AFRICA	15	15	10	10	10	15	15	15	15	15	15	15	15	20	20	20	20	20	20	20	20	20	20	15	<b>↓</b> m	7
S. AMERICA	15	15	10	10	10	10	10	15	15	15	15	15	15	20	20	20	20	20	20	20	20	20	20	15	<b>*</b> SE	MID
	20	20	20	20	20	20	20	20	30	30	30	30	30	30	30	30	30	30	30	30	20	20	20	20	<b>~</b> 0	USA
NEW ZEALAND	10	10	10	15	15	15	15	15	20	20	20	20	20	20	20	20	20	15	15	15	10	10	10	10	¥ ×	
OCEANIA AUSTRALIA	15	15	15	15	15	15	20	20	20	20	20	20	20	20	20	20	15	15	15	10	10	10	10	10	<b>†</b> ₹	
JAPAN	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	12	
	6:00	5:00	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8:00	7:00	CDT	
		6	5		ω	N		12	Ξ	10	G		7	6	cŋ.	4	ω	N	_	r.	=	5	<u>م</u>		EDT	
	8	8	5:00	8	3:00	20	:: 8	12:00		10:00	9:00	8	7:00	<u>6:</u> 08	8	8	8	8	8	12:00	11:00	8	8	8:00	4	
ASIA FAR EAST	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	-+ Z	
EUROPE	20	20	20	20	20	20	20	20	20	20	20	20	30	30	30	30	30	30	20	20	20	20	20	20	N. N.	_
S. AFRICA	15	15	10	5	10	10	15	15	15	15	15 15	15	15	20	20	20	20	20	20	20	20	20	20	15	<b>↓</b> <sup>™</sup>	EAS
CARIBBEAN S. AMERICA	15	15	10	10	10	10	10	15	15	15	15	15	15	20	20	20	20	20	20	20	20	20	20	15	se 🖌	TER
	20	20	20	20	20	20	20	20	30	30	30	30	30	30	30	30	30	30	30	30	20	20	20	20	<b>~</b> 0	EASTERN USA
NEW ZEALAND	10	10	10	15	15	15	15	15	20	20	20	20	20	20	20	20	20	15	15	15	10	10	10	10	N S¥	SA
OCEANIA AUSTRALIA	15	15	15	15	15	15	20	20	20	20	20	20	20	20	20	20	15	15	15	10	Б	10	10	15	<b>↑</b> ₹	
JAPAN	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	20	12	

The italicized numbers signify the bands to try during the transition and early morning hours, while the standard type provides the MUF during "normal" hours. \*Look at next higher band for possible openings.

ham radio

# Your Ham Tube Headquarters !

TUBES BOUGHT, SOLD AND TRADED SAVE \$\$\$—HIGH \$\$\$ FOR YOUR TUBES

# Call Toll Free 800-221-0860


Tu	bes
3-400Z\$85.00	7360\$10.00
3-500Z85.00	7735A27.50
4-400A80.00	8122
4CX250B50.00	8156 12.50
572B55.00	8643 82.50
811A12.00	884426.50
813	8873 175.00
6146B6.50	8874 195.00
63604.25	8877
6883B6.75	890812.50

### MAJOR BRANDS ON RECEIVER TUBES 75% off list

Semiconductors

MRF 245/SD1416 \$30.00	SD108819.95
MRF 45414.95	2N305575¢
MRF 455 10.95	2N608412.50
RF Cor	nectors
PL25910/\$4.95	M3582.50 ea.
PL25810/8.95	M3591.75 ea.
110 175/170 10/1 00	Tune "NI" Twist on

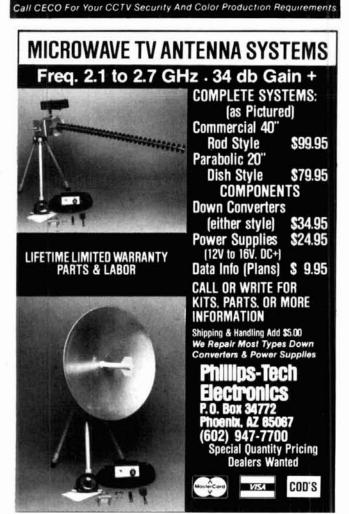2115 Avenue X Brooklyn, NY 11235 SERVING THE INDUSTRY SINCE 1922 Phone (212) 646-6300





The monthly magazine with a natural blending of two popular hobbies — Ham Radio and Computers

\* Articles on Ham Radio & Most Personal Computers

- \* Hardware & Software Reviews
  - \* Various Computer Languages
    - + Construction Articles
      - \* Much Much More. . .

"...received my moneys worth with just one issue..."

—J. Trenbick

"...always stop to read CTM, even though most other magazines I receive (and write for) only get cursory examination..."

-Fred Blechman, K6UGT


U.S.A	. \$15.00 for 1 year
Mexico, Canada	\$25.00
Foreign\$35.00(	(land) · \$55.00(air)
(U.S. funds only)	
Permanent (U.S. Subscription	) \$100.00
Sample Copy	\$3.50



Circulation Manager 1704 Sam Drive Birmingham, Alabama 35235

Phone 205/854-0271

Name	
Call Sign	
Address	
City	State
Zip	Phone
Date	
Signature	- 15

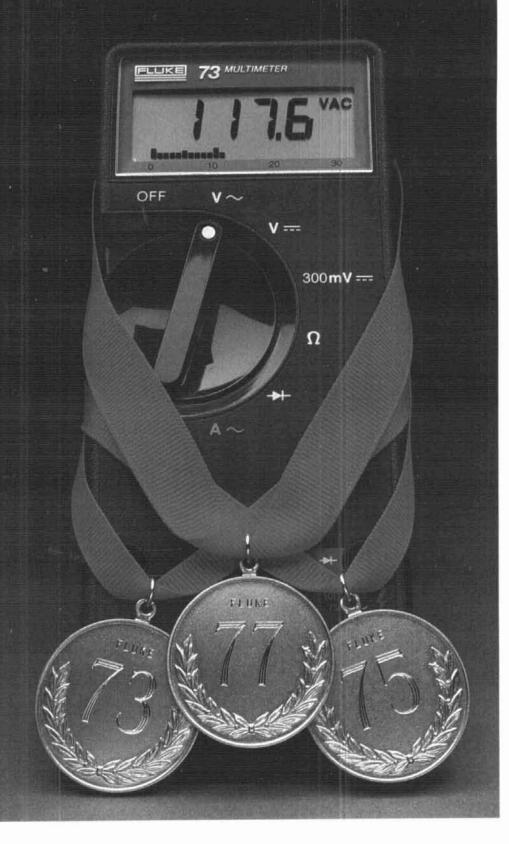

# Take home a world champion.

\$85<sup>\*</sup> gets you a technical knockout. The Fluke 70 Series.

Winners of the digital vs. analog battle. Since their debut, they've become the worldwide champions of the industry.

Never before have such tough, Americanmade meters offered so many professional features at such unbeatable prices.

Each comes with a 3-year warranty, 2,000+ hour battery life, and instant autoranging.

You also get the extra resolution of a 3200count LCD display, plus a responsive analog bar graph for quick visual checks of continuity. peaking, nulling and trends.

Choose from the Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own protective holster and unique "Touch Hold" function \*\* that captures and holds readings, then beeps to alert you.

So don't settle for just a contender. Take home a world champion.

For your nearest distributor or a free brochure, call toll-free anytime

1-800-227-3800, Ext. 229. From outside the U.S., call 1-402-496-1350, Ext. 229.

# FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.

FLUKE 75



## FLUKE 73 \$85\*

fest.

Analog/digital display Analog/digital display Volts, ohms, 10A, mA, Volts, atims, 10A, diode diodé test Autorange 0.7% basic dc acouracy 2000 + hour battery life Autorange/range.hole 5% basic dc accuracy 000+ hour battery life 3-year warranty year warranty

# FLUKE 77

Analog/digital display Volts ohms 10A mA diode test Audible continuity "Touch Hold" function Autorange/range hold 0.3% basic de accurac 2000 + hour battery life 3-year warranty hiltipurpose ho

\* Suggested U.S. list price, effective July 1, 1984. \*\* Patent pending





# ANTENNA/TOWER SALE!


CRANKUP SALE! All Models Shipped Factory Direct— Freight Paid*! Check these features: • All steel construction • Hot dip galvanized after fabrication • Complete with base and rotor plate • Totally self-supporting— no guys needed Model Height Load Price Ho375S 37 ft 959 ft \$744 Ho325S 52 ft 959 ft \$744 Ho325S 52 ft 959 ft \$749 Ho34HD 54 ft 1659 ft \$169 Ho34HD 54 ft 1659 ft \$269 Ho34HD 70 ft 1659 ft \$269	Ant.         Delivered           Model         Height         Load*         Weight         Price*           HBX40         40 ft         10 sq ft         164         \$329           HBX48         48 ft         10 sq ft         303         \$429	Model         Height Up Down Wind Load List         Sale           Model         36.0 ft         20.5 ft         9.0 sq ft         \$5195           Model         Mage 100 ft         10.5 ft         9.0 sq ft         \$5195           Model         Height Up Down Wind Load List         Sale         \$60 ft         \$5195           Model         Height Up Down Wind Load List         Sale         \$61 ft         \$694 \$579           W151         54.0 ft         20.5 ft         9.0 sq ft         \$1514 \$695 \$1599	BUTTERNUT ELECTRONICS CO. HF6V \$129 Delivered (Cont. USA) • Full Legal Power 80/10 Meters • Optional Stub Tuned Radial Kit Model STR II \$29 • Optional Roof Mounting Kit Model RMK II \$49 (includes STR II) • Optional 160 Meter Resonator Kit Model TBR 160HD \$49 New 80/40 Meter Vertical Antenna HF2V \$129 Delivered (Continental USA) • Optional 160 Meter Resonator Kit Model TBR 160S \$49 Delivery Anywhere In The Continental
Masts—Thrust Bearings— Other Accessories Available —Call! Prices Shown Are Your Total Delivered Price	HDBX48 48 ft 18 sq ft 363 \$489 *Your Total Delivered Price Anywhere in Conti- nental 48 States. Antenna Load Based on 70 MPH	LM470D 70.0 H 22.0 H 16 sq ft \$4195 \$3199 (Motorized) DX86 B6.0 H 23.0 H 25 sq ft \$7200 Call (Motorized)	USA At No Additional Cost. (Free Ship- ping On Butternut Accessories Also When Purchased With Antenna.)
In Continental U.S.A.! R6-213U \$.29/ft \$279/1000 ft Up to 600 ftvia UPS Up to 600 ftvia UPS • RG-213/U -95% Bare Copper Shield • Mil-Spec Non-contaminating Jacket for longer Ilfe than R68 cables. • Our R6-213/U uses virgin materials. • Guaranteed Highest Quality! R6-8X \$.19/ft \$179/1000 • R68X-95% Bare Copper Shield • Low Loss • Non-contaminating Vinyi Jacket Foam Dielectr Castial Cable Loss Characteristics (DB/100 ft) Cable TypeImped 10MHz30MHz150MHz450MHz R6-213/U 50 .6 9 2.3 5.2 R66X 52 .8 1.2 3.5 6.8 R6-58/U 52 1.4 1.9 6.0 12.5 * Alum 50 .3 5 1.2 2.2 * Heliax 50 .2 4 .9 1.6	VHF/UHF BEAMS A50-5 \$ 79 6178 \$199 2148 \$ 79 3219 \$ 95	MINI-PRODUCTS H0-1 LIST \$182.50 SALE \$159 • Wing Span - 11 ft • Boom - 54 in. long • Wind Area - 1.5 sq ft 1200W P.E.P. Input ALPHA DELTA COMMUNICATIONS Transi-TrapTM Surge Protectors—In Stock Now! Model LT 200W UHF Type \$29 RT 200W Deluxe N Type \$32 HT 200W Deluxe N Type \$32 HV 2KW Deluxe N Type \$32 HV/N 2KW Deluxe N Type \$35	ROHN GUYED TOWERS           10 ft Stack Sections           206 \$39.50         256 \$49.50           456 \$112.50         556 \$134.50           All 206, 256, 456 and 556 Accessories           In Stock at Discount Prices - CALL!           Fridowers           Fx558           58           FX558           456           58           All 206, 256, 456 and 556 Accessories           In Stock at Discount Prices - CALL!           Fx558           Fx2588           58 ft 13.3 sq ft \$399           Fx4554 44 ft 13.4 sq ft \$1199           Fx4554 54 ft 29.1 sq ft \$1299           Fx4554 54 ft 29.1 sq ft \$1299           Fx4564 64 ft 28.4 sq ft \$1399           7265 Foldower Double Guy Kit \$249           *Above antenna loads for 70 MPH winds and Guys at Hinge & Apex.
¼* Heliax         50         1         2         5         9           HARDLINE/HELIAXTM         Lowest Loss for VHF/UHF!         Lowest Loss for VHF/UHF!           ½* Alum. w/poly Jacket.         \$.79/ft           ½* L0F4-50 Andrew Heliax TM         \$.39/ft           %* L0F5-50 Andrew Heliax TM         \$3.99/ft           select connecto.: below.         HARDLINE & HELIAX TM           HARDLINE & HELIAX TM         CONNECTORS           Cable Type UHF FML[UHF MALE  N FML  N MALI % * Heliax TM \$22         \$22           % * Heliax TM \$24         \$49           \$49         \$49           AMPHENOL CONNECTORS         \$300 N Female \$2.95           Silver PL259         \$1.25         UG230 N Female \$2.95           ANTENNA WIRE & ACCESSORIES         \$400	HY-GAIN           Discoverer 2-el 40-mtr Beam         \$319           Discoverer 3-el Conversion Kit         \$199           EXPLORER-14 SUPER SPECIAL         \$309           QK710 30/40 mtr. Add-On-Kit         \$79           Y2S 2-mtr Base Vertical         \$49           TH5MK2S Broad Band 5-el Triband Beam         \$389           TH7DXS 7-el Triband Beam         \$189           TH2MK3S 2-el Triband Beam         \$189           TB5BAS 5-el 10-mtr Beam         \$199           105BAS 4-el 6-mtr Beam         \$158           66BS 6-el 6-mtr Beam         \$158           18HTS 80-10 mtr Hy-Tower Vertical         \$435           18HTS 80-10 mtr Hy-Tower Vertical         \$435	KLM         KT34A 4-ei Broad Band Triband Beam         \$339           KT34XA 6-ei Broad Band Triband Beam         \$489           40m-1 40-mit Rotatabe Dipole         \$179           40m-2 2-ei 40-mit Ream         \$409           40m-3 3-ei 40-mit Beam         \$459           40m-44-40-mit Beam         \$649           2m-13LBA 13-ei 2-mit Satellite Antenna         \$79           2m-14C 14-ei 2-mit Satellite Antenna         \$89           2m-2CC NEW-22-ei 2-mit Satellite Antenna         \$19           432-30LBX NEW-30-ei -432 MHz Antenna         \$19           432-30LBX NEW-30-ei -432 MHz Antenna         \$19           432-30LB 16-ei 432 MHz Beam         \$59           432-40CX 435 MHz Satellite Antenna W/CS-2         \$159           ROTORS & CABLES         Alliance H073 (10.7 sq tt rating)         \$109           Alliance U110 (3 sq tt rating)         \$49           Flex HAM 4 (15 sq tt rating)         \$249	3/8 *EJ (3/8 *Eye & Jaw Turnbuckle)         \$7 95           1/2 *EE (1/2 *Eye & Eye Turnbuckle)         \$9 95           1/2 *EJ (1/2 *Eye & Jaw Turnbuckle)         \$10.95           3/16 * Preformed Guy Grip         \$2.49           1/4 * Preformed Guy Grip         \$2.49           6 * Diam * at Long Earth Screw Anchor         \$14.95           5000 Guy Insulator (5/32 * or 3/16 * Cable)         \$1.69           502 Guy Insulator (1/4 * Cable)         \$2.99           5/8 * Diam - 8 ft Copper Clad Ground Rod         \$12.95
14 Ga Stranded Copperweld         \$.10/1           450 Ohm H. D. Line         \$.16/1           16 Ga Copper coated steel wire ¼ mile long         \$.33           H. D. End Insulators         \$.2/e           Van Gorden 1.1 Balun         \$.1           Van Gorden 1.1 Balun         \$.1           Wan Gorden Center Insulator         \$.1           HUSTLER         6BTV 80-10 mtr Vert           6B1V 40-10 mtr Vert         \$.8           Mebile Resonators         10m           Mebile Resonators         10m           400W Standard         \$.16           320 \$.22         \$.25           8umper Mounts - Springs - Folding Masts in Stock	214BS 14-ei 2-mtr Beam         \$49           2BD0 80/40 mtr Trap Dipole         \$65           5BD0 80-10 mtr Trap Dipole         \$129           BN86 80-10 mtr KW Balun W/Coax Seal         \$22           9         MOSLEY           9         Pro37 7-ei Triband Beam         \$249           CL-33 e-ei Triband Beam         \$279           TA-33 3-ei Triband Beam         \$249           TA-33 JR 3-ei Triband Beam         \$249	Telex Tailtwister (20 sq ft rating)       \$269         Telex HDR300 Heavy Duty (25 sq ft rating)       \$519         Kenpro KR-500 Heavy duty lefvation rotor       \$189         KLM EL-3000 Moon Tracker Elevation Rotator       \$369         Standard 8 cond cable \$ 19/ft       (vinyl jacket 2+#18 & 6+#22 ga)         Heavy Duty 8 Cond cable \$ 3.6/ft       (vinyl jacket 2-#18 & 6+#18 ga)         SOUTH RIVER ROOF TRIPDDS       HDT-3 3 ft Tripod       \$19         HDT-3 3 ft Tripod       \$19       HDT-5 5 ft Tripod       \$29         HDT-10 10 ft Tripod       \$49       HDT-15 15 ft Tripod       \$29         Heavy Duty Tripods include mtg hdw-UPS Shippable       \$29       \$20	HPTG2100 Guy Cable (2100 lb rating)         \$.29/ft           HPTG4000 Guy Cable (4000 lb rating)         \$.49/ft           HPTG6700 Guy Cable (6700 lb rating)         \$.69/ft           9901LD Cable End (for 2100/4000 cable)         \$7.95           9902LD Cable End (for 6700 cable)         \$8.95           Socketfast Potting Compound         \$14.95           GALVANIZED STEEL MASTS         Heavy Duty Steel Masts 2 in 0D - Galvanized Finish           Length         \$ FT         10 FT         15 FT         20 FT           12 in Wall         \$29         \$49         \$59         \$79           18 in Wall         \$39         \$69         \$129         \$249

VISA

-

Div. of Texas RF Distributors Inc. 1108 Summit Ave., Suite 4 • Plano, Texas 75074 Store Hours: Mon-Fri: 9am - 5pm

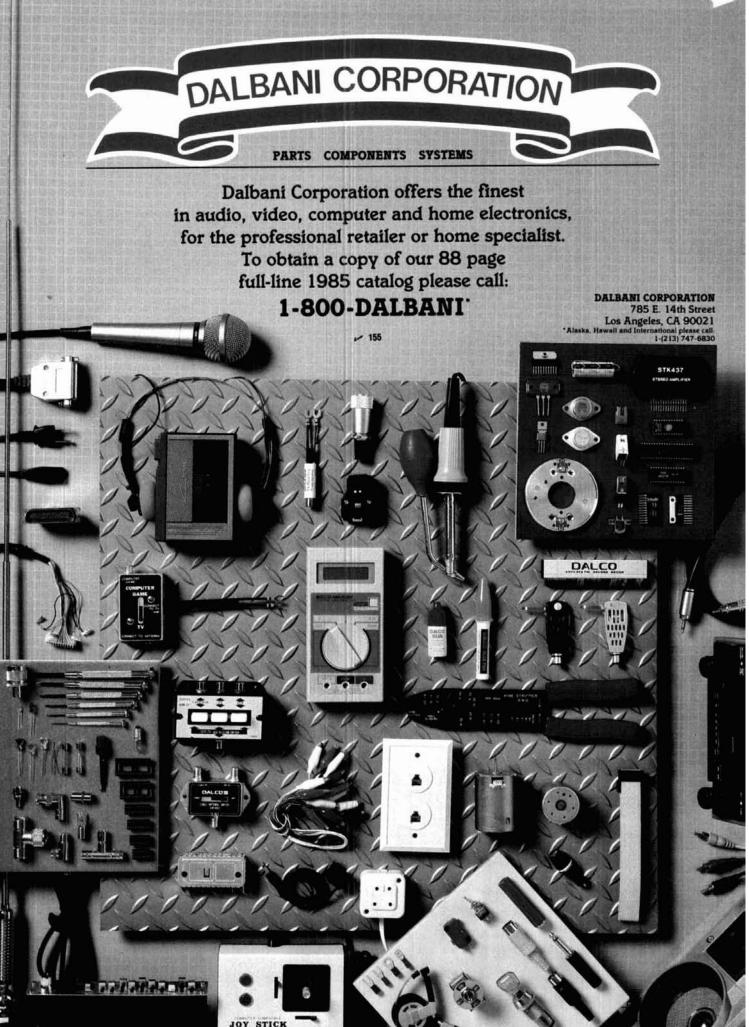(Prices & Availability Subject To Change Without Notice)



# 160-meter transmission line antenna

If height or space is a problem, try this

If you're like me, you don't have adequate yard space to put up a half-wave dipole on the 160-meter band or a tower to load as a short vertical. In the past, I tried not to let this discourage me from getting on 160, but the RF burns and unanswered calls that resulted from loading up a 40-meter dipole forced me to come up with a better antenna!

Short transmission line antennas have been used at UHF and microwave frequencies for quite some time.<sup>1</sup> Small slots carved into the bodies of fast-moving vehicles (airplanes and rockets) have been used to effectively radiate RF energy using transmission line principles. In fact the folded dipole, commonly used with FM receivers, uses these same principles to receive RF signals. Other types of transmission line antennas include the "low-profile" type used on trains and emergency vehicles, where the antenna structure protrudes just fractions of a wavelength above the vehicle body. These antennas are advantageous when antenna size and height are extremely limited.

I live in an apartment complex. The tallest structures are a couple of 30-foot trees in my small backyard. I have also found that good grounding is a problem, making the use of an "RF-free" tuner difficult. After attempting to work the top band with my existing 20meter and 40-meter dipoles (none too successfully), I decided to give these transmission line ideas a try. The results have been gratifying, to say the least. I now have a resonant 160-meter antenna that requires no tuner, is directly coax-fed, has given no trace of RF in the shack, and provides enhanced reception due to very low noise pick-up.


### how it works


Many people associate the term "transmission line"

with the coaxial cable or ladder line that feeds their antenna — something that "carries power to the antenna," and not something that should, itself, radiate RF. Of course, it is undesirable to have our feedline radiate, but many successful antennas, such as the longwire, the rhombic, and the Beverage are indeed unbalanced (radiating) transmission line extensions of their feed systems. By configuring these lines properly, resulting current distributions along the wires enable these transmission line extensions to emit and receive far-field RF energy. By analyzing a familiar transmission line antenna, the half-wave folded dipole, we can get a feel for how and why a transmission line antenna works.

Consider a folded dipole made of twin-lead transmission line (fig. 1). This type of feedline typically has a 300-ohm characteristic impedance. We can think of this antenna as being driven by our transmitter, an unbalanced RF source voltage. A common and useful technique used to analyze transmission lines is the superposition principle, where the original source voltage is replaced by several different sources which, when combined, add to give the equivalent voltage of the original source. Superposition is used to reconfigure the folded dipole as shown in fig. 2. By breaking down the superposition model, it is possible to construct and identify distinctive modes that characterize the behavior of the antenna. Figure 3A shows "pushpush" or even-mode feeding, in which both wires in the twin-lead transmission line are excited by the same voltage, and have currents traveling in phase. Figure 3C illustrates "push-pull," or odd-mode feeding, where the two wires of the twin-lead have currents traveling in opposite directions at any time. The impedances presented by the even and odd modes in terms of the excitation voltage and currents are easily found with the superposition model.

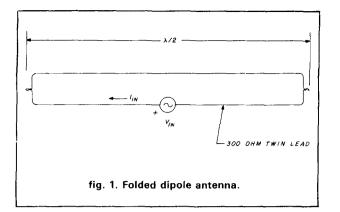**By Ted S. Rappaport, N9NB**, Box 283, Electrical Engineering, Purdue University, West Lafayette, Indiana 47907



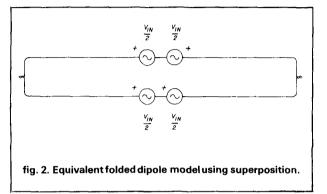

For the even mode case:  $Z_{even} = \frac{\left[\frac{V}{2}\right]}{I_{even}} = \frac{V}{2I_{even}} (even mode)$ 

(1)

Since the pair of voltage sources in push-push are similar to just a single source voltage V/2 driving two parallel strands of wire (assuming the twin-lead spacing is much less than a wavelength), the even-mode impedence is that of a "wide" dipole ( $Z_{even} = 50 \text{ to } 75 \text{ ohms}$ ). This simplification is shown in **fig. 3B**. Because the even (push-push) mode does the radiating, it is sometimes called the antenna mode. Note that the value of current in each of the transmission line wires is half of the total even-mode current.

For the push-pull case, the odd mode impedance is given by:

$$Z_{odd} = \frac{\left[\frac{V_{in}}{2}\right]}{I_{odd}} = \frac{V_{in}}{2I_{odd}} (odd-mode)$$
(2)

 $Z_{odd}$  is the parallel combination of the impedances of each of the short-circuited ends of the folded dipole, reflected 1/4 wavelength back to the center feedpoint. Recall that a short-circuited transmission-line offers a near infinite impedance when the source is placed onequarter wavelength from the short. The odd mode (sometimes known as the transmission line mode) impedance is made very high in this manner. Instead of short circuits, resistors can be placed at various nodes to alter even and odd mode impedances, as well as current distributions. This is sometimes done with rhombic antennas and vee beams. For our folded dipole example, we can observe that the antenna mode offers an impedance to RF on the order of a dipole antenna, whereas the transmission line mode offers extremely high resistances to RF.

Specifically, the input impedance to the antenna is easily computed (using superposition) as:

$$Z_{in} = \left(\frac{V_{in}}{I_{in}}\right) = \frac{V_{in}}{\left[\left(I_{even}/2\right) + I_{odd}\right]}$$

$$= \frac{V_{in}}{\left[\left(\frac{V_{in}}{4Z_{even}}\right)^{+} \left(\frac{V_{in}}{2Z_{odd}}\right)\right]}$$

$$= \frac{4Z_{even}Z_{odd}}{\left(2Z_{even} + Z_{odd}\right)}$$
(3)

Observe that for  $Z_{odd}$  very large (as is the case here):


$$Z_{in} = 4Z_{even} \cong 300 \text{ ohms}$$

We find that not only does this transmission-line antenna radiate, but it also has an input impedance of four times that of a conventional dipole. Conveniently, this structure can be fabricated out of 300-ohm twin-lead, and can also be fed with 300-ohm twin-lead, providing a good match to a 300-ohm receiver. In the case of Yagi antennas, where the mutual impedance effects drop the antenna feedpoint to below 20 ohms, a folded driven element can be used to increase feedpoint resistance by roughly a factor of four.<sup>2</sup>
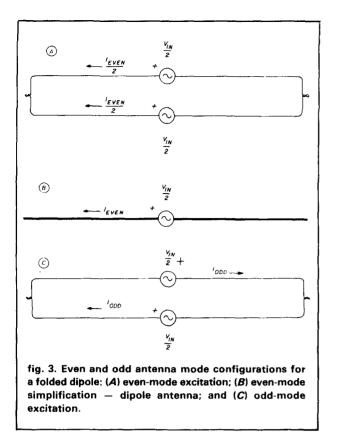
### using the ground as an image

By using the ground to electrically provide half of the antenna system, we can think in terms of a single wire above ground. **Figure 4** shows something that looks like a folded-dipole using an image. Note that the wire height must be much less than a wavelength for the transmission line principles to hold. Since horizontal image currents always travel in opposite directions as do the wire currents, the horizontal portion of this structure, unlike the original folded dipole, will tend to cancel out in the far-field (i.e., the even mode impedance for this antenna is extremely high). The vertical shorting segments, however, will provide a vertical radiation pattern, enabling this antenna to emit and receive RF energy.

Closer inspection reveals that the antenna of fig. 4A is identical to the odd-mode excitation of the original folded dipole. Recall that the odd-mode impedance was calculated by considering the parallel combination of the two transmission lines transferred back to the feedpoint. By this technique, it is easy to predict that the input impedance of the structure in fig. 4A will be very high, and the radiation will be due primarily to the short vertical segments at the ends of the structure.



Now suppose instead of folding both sides of the antenna to ground, we open one of them and move the feedpoint to a "strategic" location **fig. 4B**). This type of antenna is known as a low-profile antenna, and has effectively been used at low frequency (LF) and medium frequency (MF) bands, as well as at microwave frequencies.<sup>3</sup>

### low profile antenna

To calculate the input impedance of the low profile antenna at a particular feedpoint we need only deal with the odd mode, since, as was the case for the antenna in **fig. 4A**, the even mode offers an extremely high impedance because of image current cancellation.

Again, we must combine in parallel the impedances of the open and shorted (folded) sides of the structure. For any transmission line, input impedance values may be found by:

$$Z_{short}(x) = Z_0 Tanh(\gamma x) \text{ and } Z_{open}(y)$$
  
=  $Z_0 Coth(\gamma y)$  (4)

where *Tanh*() and *Coth*() are hyperbolic trigonometric functions,  $Z_0$  is the characteristic impedance of the transmission line, x is the distance from the feedpoint to a short-circuit termination, y is the distance from the feedpoint to an open-circuit termination, and  $\gamma$  is the complex propagation constant of the transmission

line, made up of a real attenuation factor,  $\alpha$ , and imaginary term,  $j\beta$ , representing the emission wavelength of the source ( $\gamma = \alpha + j\beta$ ).

The characteristic impedance of the single wire (and its image) is dependent upon many factors. These include height above ground, ground conductivity, and moisture of the air, to cite just a few. At 1.8 MHz, an approximate value for the characteristic impedance of a wire 6 meters above ground is about 800 ohms. The value of  $Z_0$  is really not important, though. The success of this antenna lies in the parameter  $\gamma$ .

Naturally occurring losses in the ground and in the wire cause some slight attenuation in electromagnetic waves as they propagate through the line. This attenuation,  $\alpha$ , is expressed in units of relative voltage decrease per unit length (dB/m), and yields the real part of  $\gamma$ . It is instructive to compare a lossy and lossless model of the low-profile antenna to see exactly how it loads.

For lossless transmission lines, where  $\gamma = j\beta$ , the expressions for short-circuit and open-circuit transmission lines simplify to:


$$Z_{short}(x) = jZ_0Tan(\beta x) \text{ and}$$
  

$$Z_{open}(y) = -jZ_0Cot(\beta y)$$
(5)

where Tan() and Cot() are trigonometric functions, and *j* is the imaginary operator, or a 90-degree phase shift. For this ideal case, the parallel combination of the open and short-circuited line yields an imaginary result for any value of *x* or *y* ! Since it is impossible to deliver power to a purely reactive load the SWR is infinity for the ideal case. However, when losses are considered, it is possible to solve for values of *x* and *y* which yield a purely real  $Z_{in}$ . This indicates that we are using the naturally occurring losses of a transmission line to provide a purely resistive RF load for our transmitter! The end result is an antenna that can be made to resonate at any real impedance, provided the correct lengths of open and short-circuited transmission line are used.
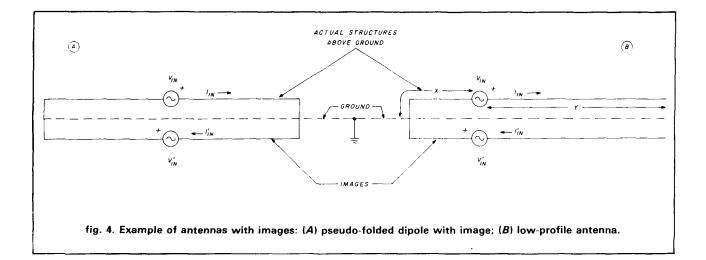
### implementation

Solving for the lengths x and y is much too impractical because of the many variables that exist at an antenna site. Trial and error is the easiest way to "zero in" on the particular lengths needed for a desired impedance and a given configuration. For a 50-ohm antenna impedance, I wound up with the dimensions shown in **fig. 5**. Only four tries were required to get the SWR below 1.5:1 in the 1800 kHz to 1850 kHz band, pruning only the longer (open) length of wire. I also discovered that other configurations are possible, at the expense of some bandwidth (**fig. 5B**). Since different locations will use slightly different configurations, it is impossible to derive explicit formulas for the



wire lengths; however, it is safe to say that the opencircuit length will not exceed 40 meters (0.24  $\lambda$ ), and the short-circuit length should not exceed 9 meters  $(0.05 \lambda)$ . To tune the antenna, start with these lengths and trim the longer wire (open-circuited transmissionline) by removing 0.5 meter lengths of wire until the SWR approaches 3:1 at the frequency of interest. Then, very finely prune both the open and short-circuit lines for best SWR. Small lengths of wire may have to be re-inserted after course pruning to optimize the match to the transmitter. It is important to be sure that all antenna SWR measurements are made with the antenna at its operating height, as the wire height above ground critically effects the tuning (in fact, this is another parameter that can be varied in the pruning process to provide the best match). It should be possible to achieve an SWR well below 1.5:1 if patience is exercised in trimming the antenna.


Wire heights from 2 to 8 meters make the transmission line approximation valid, although I would think that heights greater than this could also be made to resonate. The antenna feed system is simply a random length run of RG-58U coaxial cable. The opencircuit wire is connected to the coax center conductor, while the coax braid is soldered to the short-circuit wire, which is terminated at a ground stake (**fig. 6**).

### antenna performance

I was able to obtain an SWR of less than 2.0:1 from 1800 kHz to 1900 kHz using the configuration shown in **fig. 5A** while obtaining the same SWR over a 70 kHz bandwidth for the set-up shown in **fig. 5B**.


My first evening on 160 meters with this antenna was most enjoyable, as I rag-chewed with stations from Delaware to California! Never before have I been able to call CQ and get an answer. It sure beat the RF burns and weak signals I had been used to!

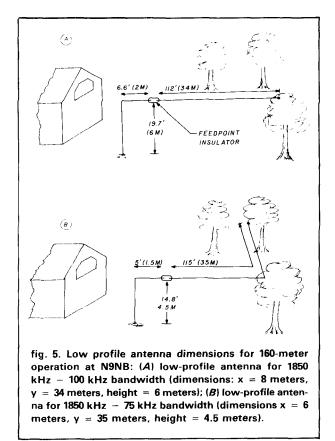I've worked over 30 states and several DX stations (including two Europeans) in the past month using



only a 1-meter long ground pipe and 100 watts of transmitter power. Also incredible is the low receiver noise level. There have been many times when I could copy DX stations, while many other stateside operators could not. This antenna may be of interest to those who don't have room for Beverage antennas but want to get away from the received noise characteristics of verticals and dipoles.

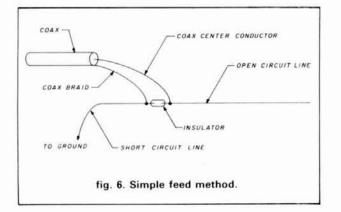The antenna seems to exhibit a moderately high angle of radiation and has a radiation pattern similar to that of a short dipole combined with a short verti-



cal. The short-circuit line provides a vertical pattern, making this structure similar to a short vertical antenna. The open circuit wire provides some horizontal radiation, and is effective in tuning the antenna to resonance. The efficiency of this antenna is determined primarily by the ground conductivity at the antenna site. Unfortunately, soil is a very imperfect conductor. Ground radials may be used to increase efficiency, although they are not essential. In fact, a poor ground may actually be beneficial as it would prohibit complete cancellation of the horizontal current components in the far-field.

KS9J and WA2JQW have reproduced this structure at their locations using wire heights as low as 6 feet (1.9 meters) and short-circuit wire lengths as short as 8 feet (2.6 meters). They have indicated that low SWR is obtainable using an arbitrary wire configuration, at an arbitrary height, as long as care is taken to prune the antenna patiently.

## conclusion

After many frustrating attempts to work the 160-meter band without an adequate antenna, I have finally found something that keeps both me and my transmitter happy. The low SWR allows for operation without an antenna tuner, and the direct coax feedline minimizes RF in the shack. Most gratifying, though, are the many new friends I have made on 160 meters and the enjoyment that contacts on the "gentleman's band" can bring!

Those who are fortunate enough to have plenty of yard space, tall trees, or a tower might not want to use this type of antenna for 160-meter operation. But those of you who think you don't have the room to get on "top band," may want to give this tuner-less, trap-less transmission line antenna a try.

### references

1. Walter L. Weeks, Antenna Engineering, McGraw-Hill, Inc. 1968.

2. Technical Correspondence, QST, January, 1984, page 48.

 Rudolf J. Guertler, "Isotropic Transmission line Antenna and its Toroidpattern Modification," *IEEE Transactions on Antennas and Propagation*, May, 1977, page 386.

ham radio

# The HD-73 Rotator by Alliance A precision instrument built to last.

The HD-73 combines Dual-Speed rotation and a single 5-position switch with the clear visibility of a backlit D'Arsonval meter. So you get precise control for fast and fine tuning. And the advanced technology of HD-73 is backed by quality construction. Heavy duty aluminum casings and hardened steel drive gears. Lifetime factory lubrication that

withstands -20°F. to 120°F. temperatures. The superior design of the HD-73 mast support bracket, with optional no-slip positive drive, assures perfect in-tower centering with no special tools. Automatic braking minimizes inertia stress.

Easy to install, a pleasure to use. The HD-73 is on your wavelength. Write for performance details today.

# PICK A COMPUTER INTERFACE TO MATCH YOUR NEEDS

COMPUTER PATCH™ MODEL CP-1



**COMPUTER PATCH MODEL CP-100** 

# COMPUTER PATCH™ MODEL CP-1

The AEA Model CP-1 Computer Patch has earned a solid reputation for being the best overall interface value on the market today. We at AEA have now reaffirmed what our competitors already know; for the money, the CP-1 cannot be beat! That is why we have chosen to leave the popular CP-1 in our product line and to introduce new computer interface/terminal units with differing features and performance at different prices.

# MICROPATCH™ MODEL MP-1

The new AEA model MP-1 Micropatch represents the best features and performance available for under \$140.00. Featuring true dual-channel filtering of Mark and Space tones with an AM detector and Automatic Threshold Correction (ATC) circuit, the MP-1 is in a totally different performance class than competitive units that often have only a single channel filter or no filtering at all.

The MP-1 also offers a high performance CW capability. With respect to the CP-1, overall performance is nearly as good; but the CP-1 offers a few more advanced features such as variable shift tuning, RS-232 option, and a more advanced tuning indicator.

# **COMPUTER PATCH MODEL CP-100**

The new CP-100 Computer Patch offers all the following exciting features in addition to the CP-1 features:

- 170, 425, 850 Hz Calibrated Shifts for Transmit and Receive
- 75 to 1000 Hz Variable Receive Shift Range
- Normal and Reverse FSK Outputs
- Input AGC
- Direct Coupled Automatic Threshold Control
- Front Panel Squelch
- Discriminator Style Tuning Indicator
- Current Loop Option
- Built-in Monitor Speaker
- Baud Rate Switch
- Improved AM Detector

HEATY RADIO 2050 S. BUNDY DRIVE LOS ANGELES, CA 90025 (213) 820-1234

TOLL FREE OUTSIDE CALIF (800) 421-6631 931 N. Euclid, Anaheim, CA 92801 (714) 772-9200 • Butler, MO 64730 (816) 679-3127 Brings you the Breakthrough! MICROPATCH™ MODEL MP-1

ATU-1000" ATU-1000" Atvanced Terminal Unit



More Hardware Features And Performance Than Any Other Morse, Baudot, ASCII, AMTOR, SITOR, or H.F. Packet Terminal Unit Anywhere At Any Price!

We recognize that there are few amateurs who can appreciate or afford the outstanding value of the ATU-1000, but those who can are in for some very pleasurable operating. The ATU-1000 is a commercial/military unit with all the performance and flexibility that is attainable from today's technology. Just check out the features below.

- 32 poles, active filtering
- Morse/Baudot/ASCII/AMTOR/SITOR/H.F.
   Packet
- Set receive filters to one Hz accuracy
- Set receive MARK & SPACE filters
- independently from 1000 to 3000 Hz
- All shifts, 170 Hz fixed or 0 to 2000 Hz adjustable
- Set AFSK output tones independently from 1000 to 3000 Hz to one Hz
- 5mV to 5V AGC
- Front-panel squelch control

- Built-in 4 digit counter
- . CW filter adjustable 700 to 2500 Hz
- D.C. coupled automatic threshold correction
- Twin full-wave detectors

.

- Built-in TTL/RS-232/and loop keyer I/O
- Discriminator-type tuning indicator
- . FSK, AFSK, and scope outputs
- 13 VDC operation, 110 VAC adaptor supplied
- TTL I/O logic inversion for use with virtually any software
- · Optional 19 inch rack mount kit

Ask your favorite dealer for a demonstration of the world's finest RTTY/CW advanced terminal unit/ computer interface—the AEA model ATU-1000. If you cannot see your dealer, send for our latest specification sheet.

Prices & Specifications Subject To Change Without Notice Or Obligation.



COLUMN CONTRACTION 2050 S. BUNDY DRIVE LOS ANGELES, CA 90025 (213) 820-1234 TOLL FREE OUTSIDE CALIF. (800) 421-6631

931 N. Euclid, Anaheim, CA 92801 (714) 772-9200 • Butler, MO 64730 (816) 679-3127

Breakthrough!

Brings you the

J 157

# ICOM 144, 220 and 440MHz MOBILES



DUP + SPEECH PRIO

ICOM's three ultra compact mobiles...the IC-27A 2-meter, the IC-37A 220MHz and the IC-47A 440MHz... are the smallest mobiles available.

Even in such a small package the 25 watt mobiles contain an internal speaker which makes them fully selfcontained and easy to mount.

Size. The ICOM compacts measure only 5½"W x 1½"H x 7"D (IC-47A is 9" deep)... which allows them to be mounted in various "compact" locations. Yet the compacts have large operating knobs which are easy to use in the mobile environment. More Features. Other IC-27A/37A/47A standard features include a mobile mount, IC-HM23 DTMF mic with up/down scan and memory scan, and internally adjustable transmit power. An optional IC-PS45 slim-line external power supply and IC-SP10 external speaker are also available.

Sn

-

14

110

VFO-A

SARE

ow

RX

DUP-

M/VFO



32 PL Frequencies. The IC-27A/37A/47A come complete with 32 PL frequencies.

9 Memories. The compact mobiles have 9 memories which will store the receive frequency, transmit offset, offset direction and PL tone. All memories are backed up with a lithium battery.

Speech Synthesizer. To verbally announce the receive frequency, an optional UT-16 voice synthesizer is available.

Scanning. The ICOM compacts have four scanning systems...memory scan, band scan, program scan and priority scan. Priority may be a memory or a VFO channel...and the scanning speed is adjustable.



Stacking Mobile Mounts. The IC-27A/37A/47A can be stacked to provide a three band mobile station. Each band is full featured and will operate even when another band is in use.

The IC-27A/37A/47A provide superb performance in the mobile radio environment. See them at your local ICOM dealer.



First in Communications

✓ 158

ICOM America, Inc., 2380-116th Ave NE, Bellevue, WA 98004 / 3331 Towerwood Drive, Suite 307, Dallas, TX 75234 All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. MOBILES385

# VHF/UHF WORLD for Reisert

# stacking antennas, part 2

Last month's column discussed the theoretical aspects of stacking antennas.<sup>1</sup> It was pointed out that the optimum stacking distance for two antennas occurs when the beamwidth in the stacking plane is reduced to approximately 50 percent of the original antenna beamwidth and grating lobes are about 13 dB below the main lobe. It was further stressed that the antenna to be stacked should be "clean" (low side-lobe) in order to achieve effective stacking since the 13 dB grating lobe level can't be obtained if the antenna to be stacked has 13 dB or poorer side-lobe levels to start with! Finally, it was shown that if everything were done correctly, a gain increase of 2.5 dB, instead of 3 dB, would be a realistic figure every time the number of antennas was doubled.

Several tables and graphs were also presented to enable you to determine the optimum stacking distance for any antenna. While all the electrical parameters are necessary, the practical feeding and physical aspects of stacking antennas are also important. Therefore, this month's column will try to tie the subject of stacking together so that you can choose the optimum configuration for your particular application.

While working on part 2 of this article I noticed that there is one caveat I neglected to point out in part 1. *All the information presented on stacking is based on having no ground reflections* (antennas in theoretical space). However, once an antenna is over 2 to

3 wavelengths above ground (a typical situation on 2 meters and above), the antenna is, for all practical purposes, in free space. At 6 meters there may be a problem since the lower antenna should be at least 40 feet (12 meters) above ground.

# stacking configuration

There are literally dozens of ways that antennas can be stacked. However, only a few configurations are typically used by Amateurs.1 Some of these are shown in fig. 1. (For clarity, the mechanical considerations have been omitted from the illustrations.) The simplest stacking configuration places two Yagis in either the horizontal (fig. 1A) or vertical (fig. 1B) plane. The optimum spacing between the Yagis was discussed in last month's column. I'm often asked the reference point for measuring the spacing: it is the distance between the current points - usually the boom on a Yagi. In the special case of the loop Yagi, it is the center-to-center spacing between the loops.


One of the most popular stacking configurations for higher antenna gain is the "quad" or "box" shown in **fig**. **1C**. This is usually a simple mechanical arrangement and has almost identical beamwidth in both the vertical and horizontal planes.

An often-overlooked configuration is an array of six Yagis (**fig. 1D**), which yields a theoretical improvement of 1.75 dB and a typical increase of 1.6 dB over a four-Yagi array. This is only about 1 dB below an eight-Yagi array but with a 33 percent smaller area! This configuration is only recommended using vertical stacking as shown and has a more complex mechanical structure. However, it is particularly recommended for those who can't double their arrays but could expand a fourbay array to six antennas with minimum cost and mechanical impact. Other common high-gain configurations especially popular with EME'ers are shown in **figs. 1E, 1F,** and **1G**. These arrangements are usually the easiest to realize mechanically when very high gains are required.
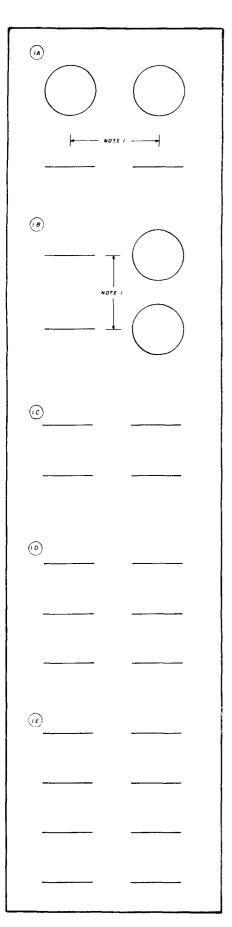
# vertical versus horizontal stacking

Last month's column discussed the problems associated with the side lobes in the H-plane (vertical) of a typical Yagi antenna and showed that they are normally 2 to 3 dB worse than in the E (horizontal) plane. Hence, Yagi antennas must often be stacked closer than desired in the vertical plane to control the vertical grating lobes. Consequently, vertical stacking may yield slightly less gain increase than horizontal stacking.

However, despite these negatives, there are reasons for stacking Yagis vertically. First, there is sometimes only one vertical mast available. Secondly, when very high gain is needed such as for EME, four or more antennas may be required and hence stacking some or all of the antennas vertically is often desirable. *Remember that the array beamwidth decreases only in the plane of the stacking*. Hence, if antennas are stacked verti-



cally, the horizontal beamwidth remains the same. This is particularly desirable when you don't want to "miss" stations that are slightly off the main beam such as when using tropospheric propagation. Likewise, vertical stacking is especially desirable when the signals may be up to 5 or 10 degrees off the great circle path such as in meteor scatter communications. Conversely, horizontal stacking is desirable for auroral propagation since the signal returning from the auroral curtain is usually elevated above the horizon. Horizontal stacking does not affect the vertical beamwidth of the antenna being stacked.


Finally, when high gain is required it is almost impossible to not stack in both planes as shown in **figs. 1C-1G**. If six or eight Yagis are used, you can still tailor the pattern by choosing which plane requires the greater beamwidth.

## electrical considerations

After choosing the stacking con-

figuration, there are some important electrical considerations such as choice of feed line and the placement of the power splitter/combiner(s). As mentioned in part 1, losses in the feed harness can severely reduce the gain when stacking antennas. The total loss in antenna gain due to the phasing harness is the sum of the insertion losses from the input of the first power splitter/combiner to the final antenna feed point on the individual antennas (see fig. 2). Generally speaking the major losses are in the transmission lines in the phasing harness. Note that the overall antenna gain loss shown in fig. 2 will only be 0.5 dB, not 2.0 dB as I sometimes hear! However, while 0.5 dB may sound low, remember that this loss reduces the stacking gain. Furthermore, a 0.5 dB phasing line loss can decrease the receiver signal-tonoise ratio by 2 or more dB when looking at a "cold" sky on 70 cm EME!

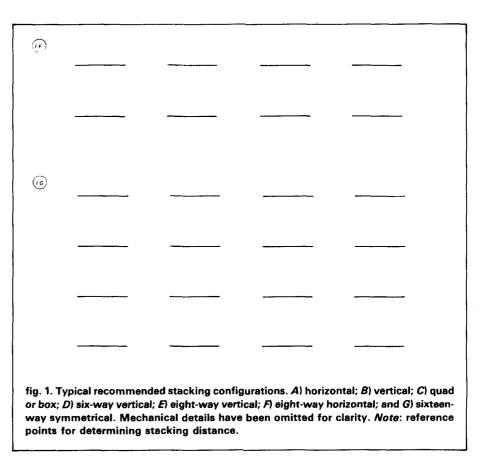From the above discussion, you can see another reason why I get so upset when I see antennas stacked too far



apart. The additional spacing not only increases the grating lobes and decreases the beamwidth unnecessarily but the hoped for gain increase of 0.1-0.2 dB by stacking wider than optimum may easily be offset by the extra phasing line loss. And that isn't all. The clincher against using unnecessarily greater spacing is the increased load that is placed on the rotator and structure.

### feeding the array

When stacking antennas, it is common practice to have a separate phasing line on each antenna. This line is then connected to a common splitter/combiner for each 2, 4, or 6 antennas being stacked. Eight-way splitter/combiners are sometimes seen. but I personally feel that they are more difficult to use and can add additional phasing line losses. If coax phasing lines are used, each is usually run down the antenna boom to a common power splitter/combiner which is centrally located on the main mast or boom. This method is mechanically sound but often adds excessive feedline losses.

A more recent trend popular with EMEers is to use a "back plane" feed system. In this arrangement each phasing line is routed to the rear of the array rather than down the boom. The power splitter/combiner is then mounted behind the antennas, usually on a separate small boom extending from the main mast. This allows very short low loss phasing lines. The main feedline(s), which are fewer in number, can now be made from a more expensive but low-loss air or foam dielectric coax.

# phasing line requirements

For best results all phasing lines should have the same overall electrical length within 22.5 degrees or 1/16 wavelength. This works out to be approximately 1.7 inches (4.3 cm) at 432 MHz. The longer the physical length of the phasing lines, the greater chance of having an unequal electrical length in these lines.

From my personal experience, I can

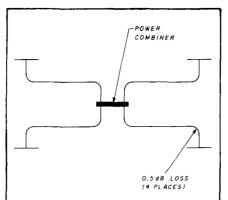


fig. 2. An example of a four-way power split showing the associated line losses. See text for full explanation and overall loss.

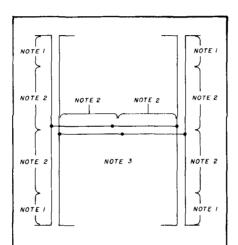


fig. 3. Recommended configuration for an open-wire line type of phasing harness. *Note 1:* quarter-wavelength of 283-ohm open-wire line. *Note 2:* identical lengths of 400-ohm open-wire line. *Note 3:* 200-ohm balanced feed point. Can be connected to a 4:1 balun or connected to another bay using similar matching schemes as shown. See text for further explanations.

offer the following suggestions. Always make all phasing lines from the same roll or piece of feedline. Stay away from small diameter (e.g., RG-58/U) and low-cost feedlines. If foam dielectric coax is used in a phasing harness, it should be treated carefully; it can "cold flow" when sharp bends are made and is more susceptible to variations with ambient temperature changes.

From practical phasing line measurements I have conducted at 70 cm using a slotted line, I have found that a physical tolerance of 0.25 inch (6mm) on 20 feet (6.5 meters) of 50-ohm RG-213 type coax cable is more than adequate when using the same spool or length of coaxial feedline.


I offer another important observation. Always lay feedlines out in a straight line and measure them in a cool place such as a garage or cellar out of the direct rays of the sun. In some tests I conducted in my back yard, it was impossible to hold the null on a slotted line constant long enough to take an accurate reading since the sun kept changing the temperature of my coax line and hence varying the length!

## open wire lines

I'm frequently asked, "Why not use open wire lines since they are low cost and low loss?" I will not argue with this statement but add the following caveat: open wire line is a fair weather feedline. Whenever deposits (water, snow, ice, or industrial wastes) build up on the spacers, the impedance and hence the VSWR changes.

If you decide to use open wire lines, try to keep a low VSWR on all the lines. The extended expanded collinear has a problem in this regard because the VSWR on the feedlines is very high.<sup>2</sup> An array of Yagis with a resistive (non-reactive) impedance is a good open wire candidate. However, use a "Q" or quarter-wave matching section at each point where the impedance changes. A recommended example using 200-ohm antennas and feed point is shown in **fig. 3**.

Low impedance (less than 250 ohms) open wire lines are not easy to realize since spacing is close and the conductors have a large diameter. Always use the fewest number of spacers possible and still maintain the mechanical integrity of the line. My experience with extended expanded collinears showed that the maximum power split for open wire lines should be two per junction since four ways can pose symmetry problems and congestion of lines which often leads to unequal splitting and lower gain.

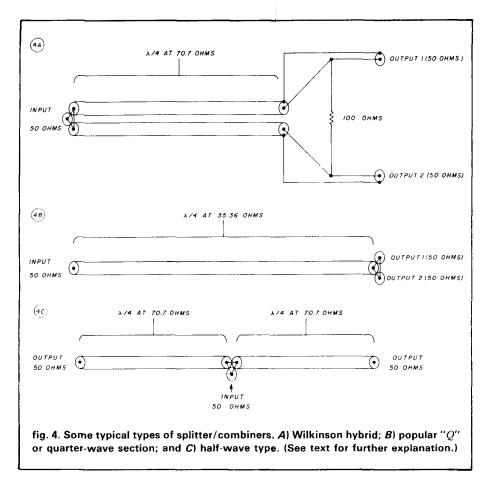

## phasing line lengths

Finally, I am often asked, "Should the length of the phasing lines be a multiple of half-wavelengths?" This practice apparently started on 2 meters when two antennas were closely spaced and the feedlines were also acting as an impedance transformer.

Ideally speaking, the feedline length is unimportant if the antennas to be stacked have a reasonably low VSWR. However, when antennas are stacked, there is always some mutual impedance. It has been pointed out by Roy Lewallen, W7EL, that whenever any mutual impedance exists between antennas, the ideal phasing line length should be an odd multiple of quarter wavelengths which will enhance the proper distribution of power to each branch of the antenna.<sup>3</sup> He further pointed out that this practice has been in use on TV antennas for many years.<sup>4</sup> Although this may be difficult to realize in practice (especially on 70

cm), if possible cut your phasing lines to an odd multiple of quarter wavelengths.

### power splitter/combiners

All the foregoing stacking information would be for naught if there weren't a convenient way to do splitting or combining at the antennas in the array. The methods shown in **fig. 3** are fine for open-wire line. Coax, however, requires different handling.

There are two basic types of power splitter/combiner(s) that work well with coax. They are the isolated (hybrid) and the non-isolated quarter wavelength types.

The isolated type shown in **fig. 4A** is often referred to as the Wilkinson power divider.<sup>5</sup> It uses quarter-wavelength lines between a floating resistor. The resistor doesn't consume power unless the loads are unequal or missing. This type of power splitter/combiner is not too popular with Amateurs since the resistors must be able to dissipate high power (at least half the power entering the splitter/combiner) and isolated from ground. Lewallen also indicated that this type of splitter/combiner is not recommended for antenna phasing especially when mutual impedances are present.6 One of the most popular types of power splitter/combiners used by Amateurs with coax phasing lines is the quarter wave coaxial matching section shown in fig. 4B. Its impedance is the geometric mean between the input and output impedances and can be easily calculated using the following equation:

$$Z_{LINE} = \sqrt{Z_{IN} Z_{OUT}}$$
 (1)

where  $Z_{IN}$  is usually 50 ohms and  $Z_{OUT}$  is the parallel impedance of the loads. This method can easily be used to split or combine two, three, or four ways. For instance, the impedance of the line should be 25 ohms for a fourway split in a 50-ohm system since the source is 50 ohms and the load is 12.5 ohms (50/4). Likewise a two-way split would require a 35.36 ohm impedance. Both of these impedances are easy to realize using standard square 1 inch (2.54 cm) tubing and hobby shop brass tubing.<sup>7.8.9</sup>

An important attribute of well designed air dielectric splitter/combiners is that they have inherently low loss. There is no reason why they can't be extended internally as described in reference 9. Also, it is often forgotten that most quarter-wave type of power splitters are usable at the third harmonic. Therefore, a good 2-meter power splitter may be also usable at 70 cm and a 70 cm splitter at 23 cm.

Let us not forget to mention the so called half-wave power splitter/combiner. Actually it is still a quarter-wave type since it consists of two quarterwave sections back to back as shown in **fig. 4C**. It has the added advantage that as a four-way splitter/combiner, the internal impedance is 50 ohms.

# mechanical aspects of stacking

In general, try to use symmetrical

# KENWOOD

... pacesetter in Amateur radio

# "Digital DX-terity!"



TS-430S

Digital DX-terity—that outstanding attribute built into every Kenwood TS-430S lets you QSY from band to band, frequency to frequency and mode to mode with the speed and ease that will help you earn that dominant DX position from the shack or from the mobile!



- Covers all Amateur bands
   160 through 10 meters, as well as the new 30, 17, and 12 meter WARC bands.

   High dynamic range, general coverage receiver tunes from 150 kHz to 30 MHz.
   Easily modified for HF MARS operation.
- Superb interference reduction
   Eliminate QRM with the IF shift and tuneable notch filter. A noise blanker supresses ignition noise. Squelch, RF attenuator, and RIT are also provided.
   Optional IF filters may be added for optimum interference reduction.

 Reliable, all solid state design. Solid state design permits input power of 250 watts PEP on SSB, 200 watts DC on CW, 120 watts on FM (optional), or 60 watts on AM. Final amplifier protection circuits and a cooling.

tion circuits and a cooling fan are built-in.

- Memory channels.
   Eight memory channels store frequency, mode and band data. Channel 8 may be programmed for split-frequency operation.
   A front panel switch allows each memory channel to operate as an independent VFO or as a fixed frequency. A lithium bat
- fixed frequency. A lithium battery backs up stored information.
- Programmable, multi-function scan.
- Speech processor built-in.
- Dual digital VFOs.
- VOX circuit, plus semi break-in with sidetone.

Optional accessories:

PS-430 compact AC power supply
 SP-430 external speaker 

 MB-430
 mobile mounting bracket 
 AT-130
 compact antenna tuner covers 80-10



meters, incl. WARC bands • AT-250 automatic antenna tuner covers 160-10 meters, incl. WARC bands • AT-230 base station antenna tuner

UP/DOWN hand mic. • MC-60A deluxe desk mic., with UP/DOWN switch • SW-2000 SWR/power meter

- SW-2000 SWR/power/volt meter
- PC-1A phone patch
   HS-4, HS-5,
  - HS-6, HS-7 headphones



TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

# ENTER SOAR CORP. **MENU OF INSTRUMENTS**

# Featuring — Superb Performance, Great Accuracy, Rugged Construction, Meticulous Quality, Incomparable Prices

# **Resistance Substitution Box**

31/2 Digit Multimeter

.



- 1Ω to 11 MΩ in 1Ω steps.
- ±1% accuracy.
- 1 watt resistors. Size: 4" × 6" × 2".

MODEL RD-111 \$49.00

# 20k Ohm/V VOM

- Measures AC/DC volts, resistance, decibels, capacitance, battery test and continuity buzzer, also temperature scale with optional temperature probe TP-150 for \$19.50.
- 10 ampere DC range.
- Size: 3½" × 5%" × 1½".

MODEL SX-220 \$29.95

# **DC Power Supply**



- · Fully regulated 0 to 25V and 0 to 1.5A.
- LED 3 digit readout.
- Size: 6¼" × 4%" × 13½"
- Other units 0 to 36V at 0 to 3A.
- Duals, triples also available.

### **MODEL 7400** \$235.00

# 31/2 Digit Bench Multimeter Auto/Manual Ranging

- · Measures DC volts 0.1 mV to 1000V; ACV, 1 mV to 1000V; resistance,  $0.1\Omega$  to 20 M $\Omega$ ; DCA, 0.1 µA to 10A; ACA. 0.1 µA to 10A; diode test, with continuity beeper.
- · Supplied with batteries, test leads, spare fuse.
- AC adaptor Model MQ-62 available separately for \$12.00.
- Size: 2¼" × 7¼" × 7¼".



**MODEL 5030** \$169.00

NORTH

AMERICAN



# **MODEL 8050** \$76.50

# 20 MHz Dual Trace Oscilloscope with Component Tester

- 5 mV to 20V on 12 ranges.
- 20 sweep ranges from 0.2 µs to 0.5 s/div plus ×5 mag.
- · Built-in component tester. Ideal for trouble-shooting in cold circuits.
- Complete with 2 probes, spare fuse.

MODEL MS-6022 \$599.00



# Auto-Ranging AC Clamp Tester



- Measures 0.1A to 1000A; 0.1 VAC to 1000 VAC; resistance, 0.1Ω to 2 kΩ.
- 3½ digit LCD readout.

30 ranges, 8 functions, full overload protection.

Super fast continuity beeper (<0.4 sec. response).

Large bold 1/2" LCD readout with low battery indicator.

Optional carrying case CC531, \$9.90; transistor test

Complete with test leads, battery and spare fuse.

10 Amperes AC and DC ranges.

Diode test plus transistor hFE.

extension leads UP-11, \$4.50.

- Has data hold switch, continuity beeper.
- Model 2210 with temp. meas. \$110.00.
- Model 2220 with temp. meas. and peak hold \$135.00
- Complete with carrying case, probes and battery.

**MODEL 2200** \$85.00

# 150 MHz Frequency Counter

- · Measures 5 Hz to 150 MHz on 2 ranges; sensitivity, 30 mV.
- Crystal frequency 3.2768 MHz.
- Accuracy at 0.01 sec 100 PPM ±1 dgt.
- Battery portable or AC optional.
- Size: 1¼" × 4" × 4¼"

MODEL FC-845 \$149.00

All prices shown are for 1 to 3 pieces of a type. Discounts are available for larger quantities. All models shown and over 70 other SOAR manufactured instruments are available from selected distributors in the USA

JAPAN SOAR CORP. Sakaki Machi, Nagano, Pref. Phone (02688) 2-4191


EUROPE SOAR EUROPA Munich, W. Germany Phone (089) 6097094

**1126 CORNELL AVENUE** CHERRY HILL, NJ 08002 corporation PHONE (609) 488-1060

159

CANADA WATERGLOW Montreal, Quebec Phone 514-389-8051

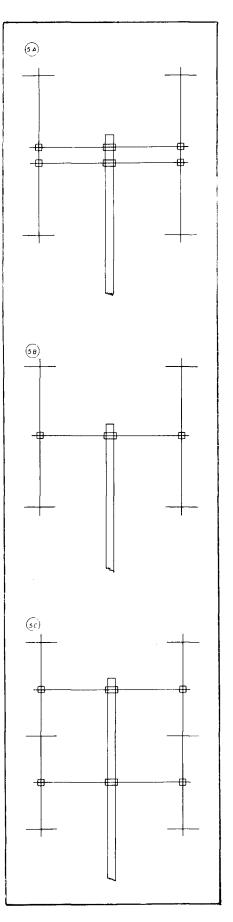SINGAPORE SOAR ELECTRONICS Singapore Pte. Lt. Phone 7796111



stacking configurations because they are less likely to be distorted by sagging resulting from wind or ice loading and are able to return to their intended shape after any external forces or loads are removed. Furthermore, in symmetrical configurations twisting moments are more likely to only cause a moderate decrease in performance if the mechanical structure varies more than 1/16 wavelength or 22.5 electrical degrees (as discussed earlier). Several configurations are shown in **fig. 5**. Stacking frames should be strong mechanically. Excessive weight should be avoided at all cost because it can cause mechanical distortion. The materials used — as well as their diameter and weight — should be carefully examined. The

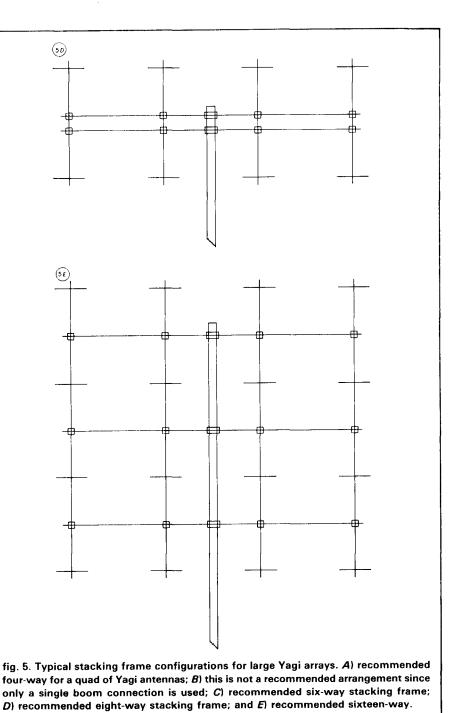




table 1. Calculated section moduli for various popular sizes of aluminum tubing using eq. 2 in text.

outside	diameter	wall thi	ckness	
inches	(mm)	inches	(mm)	section modulus
0.250	(6.35)	0.050	(1.27)	0.00134
0.375	(9.53)	0.050	(1.27)	0.00368
0.500	(12.70)	0.062	(1.57)	0.00839
0.750	(19.10)	0.050	(1.27)	0.01810
0.750	(19.10)	0.062	(1.57)	0.02140
1.000	(25.40)	0.062	(1.57)	0.04060
1.000	(25.40)	0.125	(3.18)	0.06710
1.250	(31.80)	0.062	(1.57)	0.06590
1.500	(38.10)	0.062	(1.57)	0.09740
2.000	(50.80)	0.062	(1.57)	0.17870
2.000	(50.80)	0.125	(3.18)	0.32500
2.500	(63.50)	0.062	(1.57)	0.28450
3.000	(76.20)	0.050	(1.27)	0.33610
3.000	(76.20)	0.062	(1.57)	0.41490
4.000	(101.60)	0.050	(1.27)	0.60510
4.000	(101.60)	0.062	(1.57)	0.74930

ARRL *Antenna Book* has an excellent table listing the weight per unit length of most popular aluminum tubing sizes.<sup>10</sup> Furthermore, to prevent bending moments, it is often better to use a slightly thinner wall larger diameter tubing than vice-versa.

The "section modulus" is an excellent way to compare the relative bending moment of various tubing diameters with different wall thicknesses.

section modulus = 
$$(D^4 - d^4)/D$$
 (2)

where *D* is the outside and *d* is the inside diameter of the tubing. Typical values of section moduli on some popular tubing sizes are shown in **table 1**. Note, for example, that a 3 inch (7.6 cm) diameter tube with a 0.050 inch (1.27 mm) wall has a higher section modulus and is lighter weight than a 2 inch (5 mm) diameter tubing with a 0.125 inch (3.2 mm) wall thickness. Other values not listed on the table can be easily calculated using **eq. 2**.

Mechanical symmetry of the stacking frame also tends to keep all antenna pattern blockages equal. Likewise, wherever possible, the phasing and feedlines should be neatly and symmetrically dressed and secured to a boom. Stacking frames should have several points of support. Sometimes tower sections are used for the main boom on large arrays! Judicious use of guy wires preferably at right angles to each other with adjustable turnbuckles is also recommended.

Finally, try to pass booms and masts at a mid-point between antennas rather than adjacent to them. If the material or boom used in the stacking frame passes through an antenna pattern, it will have little effect as long as it is at right angles to the plane of polarization and/or is less than 1/10 wavelength in diameter when passing through in the plane of polarization.

## other configurations

So far I have been discussing the common arrays. There are many other possibilities. When really high gain is required, a large array of antennas may be constructed. Amateur arrays using 24 Yagis are already in use on 2 meters and 70 cm and a 32-Yagi 2-meter array is under construction! Basically, these arrays are configured using combinations already mentioned. For instance, a 24-bay array can be constructed by stacking three eight-Yagi bays per fig. 1E along a main boom. A single three-way splitter/combiner at the center of the array combines the three eight-bay sub-arrays.

Besides the monstrous mechanical

problems associated with very large arrays, feedline losses and phasing errors are probably the biggest source of performance degradation. Always try to use the largest and lowest loss phasing lines available. Finally, before constructing a large array, consider whether you are willing to accept all the mechanical risks — it will be large enough! Failure to do so may reduce performance to the point that you may have no more gain than with a smaller array!

## final checkout

Whenever stacking is employed, each item should be checked in a methodical fashion. First off, the VSWR of each antenna in the array should be low, preferably 1.2:1 maximum. If coaxial lines are used, each antenna should be VSWR tested after the antennas are mounted in the array.

Next, connect the individual antennas into the associated power splitter/combiner in each grouping and test the VSWR again. Then, if applicable, test the entire array.

Be absolutely certain that all antennas are fed on the same side of the array so that 180-degree phase reversals do not occur. Preferably, mount all antennas the same way. If you decide to mount some upside down, make sure to reverse the feed attachment point. Recently, one major antenna manufacturer had a connector plate reversed on some of their antennas.<sup>11</sup> This did not affect performance until two antennas were stacked. Phase reversals of this type can cause radiation patterns to skew or even produce nulls where radiation would normally be present.

Finally, after final assembly and testing, measure antenna azimuthal and elevation patterns, if possible, using the methods described in reference 11. If the antenna pattern does not peak right on boresight (within 1 to 2 degrees) or if the anticipated beamwidth or level of the side lobes is not the value anticipated, as discussed earlier, recheck all electrical and mechanical parameters to find the problem.



**EPSILON RECORDS INTERNATIONAL: A** small business ideally suited for Ham radio Operators OR established company desiring to expand present operations. Founded in 1957 by famed educator (late) Russ Farnsworth. Epsilon produces educational tapes and records, teaching a course in the international Morse Code by the patented "Word Method". Customers include Electronic dealers (wholesale) on an established basis and private individuals (retail) on a mail-order basis through advertising in trade magazines. Gross dollar in-take can be expanded in excess of \$125,000 with present equipment. Operations require small area (home or studio) in any geographical location. Firm price of \$45,000 includes all equipment, machinery, stock, inventory, master tapes, copy-rights, patents, customer accounts, files and all records. For additional information contact: Peter Shaun Rivage, Epsilon Records International, P.O. Box 71581, New Orleans, LA 70172 (504) 242-5922


# **MULTI-BAND** TRAP ANTENNAS


fi


Completely assembled & ready to use - Commercial quality, built to last -Lightweight, sealed, weatherproof traos -Automatic band switching - Low loss end insulators - Handles up to 2000 watts PEP - For all transmitters, receivers & transceivers - Tuner usually never required -Deluxe center insulator, with built in lightning arrestor, accepts PL-259 coax connector -May be used as inverted "V" - Excellent for all class amateurs - Instructions included - 10 day money back guarantee!

4-Band-40,20,15,10 meters (55') 2 traps #D42 \$55.95 PPD 5-Band-80,40.20,15,10 meters (105') 2 traps#D52 \$59.95PPD SHIPPED POSTPAID! READY TO USE!

 90 ft. RG-58U, 52 ohm coax cable, with PL-259 connector on each end - Add \$12.00 to above price.



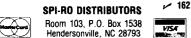

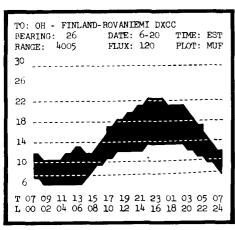

### summary

In this two-part series, I have tried to cover the major electrical and mechanical considerations required for properly stacking antennas for increased gain. Stacked antennas should be used only when the gain required is beyond that attainable using a single antenna. Remember at the outset that you will be lucky to achieve 2.5 dB of gain increase for every doubling of the array size.

Before building an array that requires stacking, plan carefully. Review both parts of this article several times. Many alternative configurations have been discussed, with pros and cons. Stacking antennas is not a simple job and there are many pitfalls. Both electrical and mechanical decisions must be made. If properly executed, the results can be rewarding. Hopefully the material presented will be useful in building your new super-high-gain array!

## acknowledgements

I would like to thank C.J. Beanland, G3BVU, for introducing me to the use of section modulus when comparing different tubing sizes.

### references

1. Joe Reisert, W1JR, "VHF/UHF World, Stacking Antennas, Part 1," ham radio, April, 1985, page 129. 2. Joseph H. Reisert, Jr., W6FZJ/1, "VHF Antenna Arrays for High Performance," QST, December, 1974, page 38

3. Roy W. Lewallen, W7EL, "Notes on Phased Verticals," QST, August, 1979, page 42.

4. Henry Jasik. Antenna Engineering Handbook. Chapter 2, page 11, and Chapter 24, page 8, McGraw Hill, 1961.

5. E.J. Wilkinson, "An N-Way Hybrid Power Divider," IRE Transactions on Microwave Theory and Technigues, Volume 8, #1, January, 1960, page 116.

6. Private Correspondence with Roy Lewallen, W7EL. 7. Don Hilliard, WØEYE, "50-Ohm Power Dividers," QST, October, 1973, page 97.

8. Jim Pruitt, KL7HIT, "Easy Matching Sections," ham radio, March, 1982, page 68.

9. George Chaney, W5JTL, "Extended/Expanded Power Dividers," ham radio, October, 1984, page 73. 10. The ARRL Antenna Book, American Radio Relay League, Newington, Connecticut, 14th Edition, Chapter 9, page 2,

11. Joe Reisert, W1JR, "VHF/UHF World, Determining VHF/UHF Antenna Performance," ham radio, May, 1984, page 110.

## important VHF/UHF coming events

<b>.......</b>	
May 1:	ARRL 70-cm Sprint Contest
May 3-5:	West Coast VHF Conference,
	Sunnyvale, California, (Con-
	tact W6RXQ for information)
May 4:	EME perigee
May 4:	1300 UTC, predicted peak of
	the Eta Aquarids meteor
	shower
May 9:	ARRL 23-cm Sprint Contest
May 17-19:	Eastern VHF/UHF Conference.
Way 17-15.	Nashua, New Hampshire.
	, , , ,
	(Contact W1EJ for
	information)
May 19:	ARRL 6-Meter Spring Contest
	(tentative date)
June 1:	EME perigee
June 5:	1930 UTC, predicted peak of
	Arietids meteor shower
June 8-9:	ARRL VHF QSO Party
June 29-30:	SMIRK 6-Meter Contest
June 15:	0400 UTC, predicted peak of
	June Lyrids meteor shower
June 21:	Mean date of the two-month
oune zr.	annual peak of sporadic-E
	· . ·
	propagation
June 29:	EME perigee
	ham radio

ham radio

# **Propagation by Mufplot**

MUFPLOT is being used by amateurs from HONG KONG to BAGHDAD, SOUTH AFRICA to ALASKA, by ailors, commerical companies and people who know the need of propagation forecasting at its best MUFPLOT will give you HPF, MUF, FOT with LUF plus distance and bearing (and time) to any target You can select over 400 listed targets by DX or ARRL prefix, lat/long, or state. The database will let you enter

arget data by what ever you want to call it and you can change it anytime. MUFPLOT will keep track of the stations you have worked for WAS, DXCC or for any other award. MUFPLOT gives you a video graph (and/or table) and printer display of band conditions. (A special DX function lets you see world conditions. You select the number of and locations you want). Band coverage for the C-64 is 6 to 30MHz video and less then 1 to more then 30MHz printer. The APPLE is 2 to 34MHz. You enter your QTH lat/long only once but you can change it anytime.

() denotes for the (C-64) only 64 MUFPLOT V2 disk only \$32.95 APPLE MUFPLOT disk only \$37.95 North American orders add \$2.00 for S/H all others \$5.00. VISA, M.C., personal checks accepted. APPLE is the trade mark of APPLE Computer Co. C-64 is a trade mark of Commodore Co MUFPLOT is a trade mark of BASE (2) SYSTEMS.

# **BASE (2) SYSTEMS**

2534 Nebraska St. Saginaw, MI 48601 Tel.517-777-5613



# Need A Storage Scope?




The Model 601 Scope Memory converts your oscilloscope into a storage scope. With the Scope Memory you can capture & display transiants, pulses and low frequency signals. Stores both analog & digital signals in a single sweep. Features a 1.4 MHZ sample rate, 2K memory. pre and post trigger capabilities.Price \$515

### Sibex, Inc.

2340 State Road 580 Suite 241 Clearwater FL 33515 (813) 797-9589

165



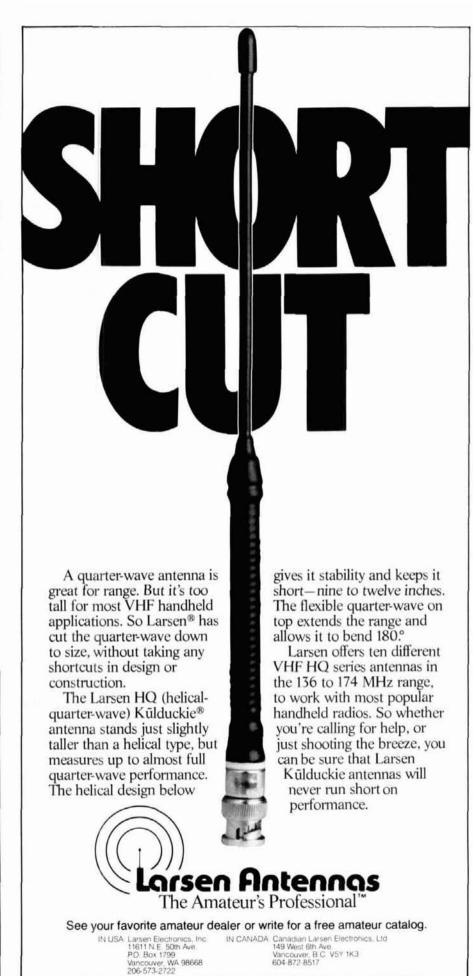

► 167

LARSEN\* KÜLROD\* AND KÜLDUCKIE\* ARE REGISTERED TRADEMARKS OF LARSEN ELECTRONICS, INC.

May 1985 🚾 105

# **RF transmission cable** for microwave applications

Detailed discussion examines all aspects of the vital link between radio and antenna

The correct selection of RF transmission cable requires proper analysis of the electrical and physical parameters of the system.

The amateur microwave enthusiast should be aware that even though materials and dimensions specified by manufacturers are usually accurate, changes in physical and environmental conditions as well as different types of manufacturing equipment or different manufacturing conditions can lead to cable with **substantially** different performance characteristics.

# VSWR uniformity

The VSWR of a cable assembly is the summation of reflections due to the connectors, the connector termination technique and the cable. The VSWR of the cable is the summation of random and periodic reflections within the cable, most commonly caused by variations within the processing equipment. The VSWR will vary with frequency. A common occurrence is the VSWR "spike" which is illustrated in fig. 1.

## characteristic impedance

The characteristic impedance of a coaxial cable is determined by the ratio of the inner diameter of the outer conductor to the outer diameter of the inner conductor and by the dielectric constant of the insulating material between the conductors. Select impedance to match your system requirements.

The most common values for coaxial cables are 50, 75, and 95 ohms. Other impedances from 35 to 185 ohms are available in coaxial configurations, but these are normally of interest only to the industry.

Note that the actual input impedance at a particular frequency may be quite different from the character-

istic, or surge impedance of the cable due to reflections in the line. The VSWR of a particular length of cable is an indicator of the difference between the actual input impedance of the cable and its average characteristic impedance.

The impedance **will** vary along the length of the cable. Variations of 5 percent are common and some mil spec cables are manufactured to 2 percent tolerance.

## capacitance

Capacitance values for standard coax lines depend only on cable impedance and dielectric material.

nominal	
capacitance	
pF/foot	cable types
30.8	50 ohm solid polyethylene
25.4	50 ohm foam polyethylene
29.4	50 ohm solid PTFE (Teflon)
20.6	75 ohm solid polyethylene
16.9	75 ohm foam polyethylene
19.5	75 ohm PTFE
16.3	95 ohm solid polyethylene
13.5	95 ohm air space
	polyethylene RG62B
15.4	95 ohm solid PTFE
10.0	125 ohm air space
	polyethylene RG63B
6.5	185 ohm air space
	polyethylene RG114A


# capacitance and impedance stability


The capacitance and impedance of long lengths of cable will exhibit very little change over their operating temperature ranges (less than 2 percent). Semi-flexible foam dielectric cables normally exhibit the least change in short cable lengths at frequencies over 1 GHz, although the VSWR can vary significantly if dielectric movement at the connector interface occurs.
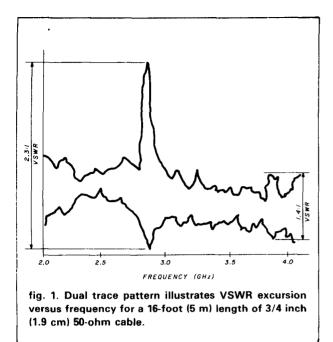
# average CW power rating

Coaxial cable power ratings must be derated by correction factors for the ambient temperature, altitude (admittedly not of much concern to the Radio Amateur) and VSWR encountered in a particular application. High ambient temperature and high altitude reduce the power rating of a cable by impeding the


**By Howard Weinstein, K3HW**, 15 Lakeside Drive, Marlton, New Jersey 08053



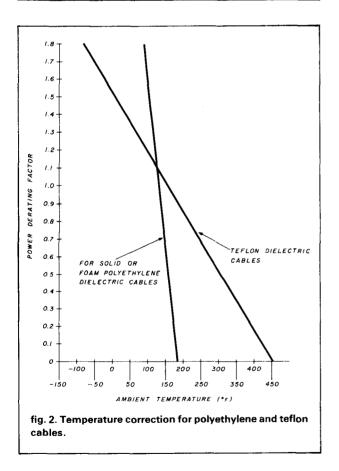

heat transfer out of the cable. VSWR reduces power ratings by causing hot spots.

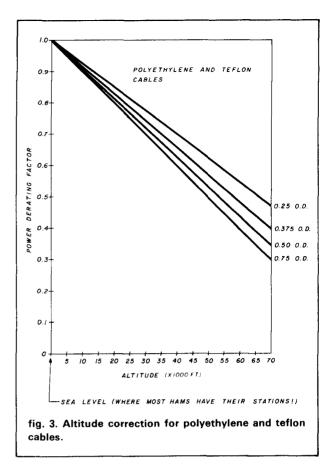To select the cable construction for a particular requirement, determine the average input power at the highest frequency from your station's requirements.



Then determine the effective average input power with the following formula:

#### effective power

$$= \frac{average \ power \times (VSWR \ correction)}{(Temp. \ correction) \times (Alt \ correction)}$$
(1)

Temperature and altitude corrections are illustrated in **figs. 2** and **3**.

VSWR correction factor

$$= \frac{1/2(VSWR + 1/VSWR) + 1/2K'}{(VSWR-1/VSWR)}$$
(2)  
(K' is shown in fig. 4.)

#### maximum AC operating voltage


A cable cannot operate continuously with corona because it causes noise generation, dielectric damage and eventual breakdown. The maximum operating voltage must be less than the corona level (extinction voltage) of the cable. This is not to be confused with the dielectric strength of the cable, which is the test voltage applied for one minute during manufacture.


Maximum operating AC (RMS) voltage levels or peak voltages are given for each type of cable in many manufacturer's catalogs. Usually the maximum permissible DC voltage level is 2.5 to 3 times the AC level. To determine the actual RMS value, divide peak voltage by 1.4. To determine the peak voltage, multiply RMS by 1.4. Then determine the effective input voltage by multiplying the actual input voltage by the square root of VSWR.

The cable you select should have a maximum operating voltage specification greater than the effective RMS voltage.
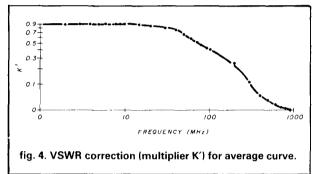
#### attenuation

The attenuation of any cable may not change uniformly as the frequency changes. Random and periodic impedance variations give rise to different attenuation responses. Narrow band attenuation spikes can occur.



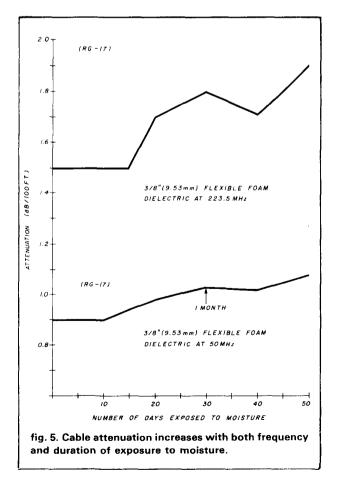

The attenuation of braided cables can increase with time and flexure. The change with time can be caused by corrosion of the braided shield, by contamination of the primary insulation caused by chemicals in the cable jacket, and by moisture penetration through the jacket. Attenuation degradation is more pronounced at frequencies above 1 GHz. Cables having bare copper and tinned copper braids exhibit far greater attenuation degradation than do cables having silver plated copper braids. Refer to **figs. 5, 6**, and **7**.

The following "rules of thumb" apply in Amateur service:

**Tin-plated braids.** Below 1 GHz, cables manufactured with tin-plated braids have at least 20 percent more attenuation than copper braids in the "as manufactured" condition, but are more stable than bare copper-braided cables.

Foam polyethylene. Flexible braided cables with foam polyethylene dielectrics have approximately 15 percent less attenuation that solid polyethylene cables of the same core size and impedance. However, as many of us have discovered, the attenuation of foam cables will increase if moisture is absorbed. In high humidity environments I suggest that foam cables not be used above 148 MHz. All of these problems can be eliminated by the use of semi-flexible cables; semi-

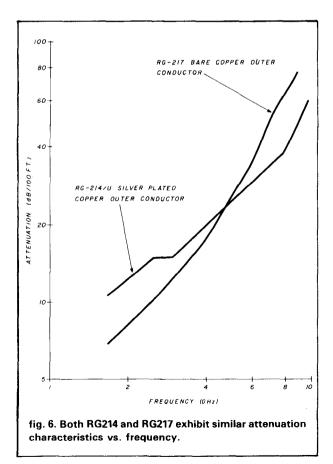


table 1. Formulas common to all coax cable.

$$Capacitance (C) = \frac{7.36E}{LOG(D/d)} Picofarads/ft$$
Inductance (L) = 0.140 LOG(D/d) Microhenries/ft
Impedance (Z\_0) =  $\sqrt{\frac{1}{L}} = \frac{138}{\sqrt{E}} LOG (D/d)$  ohms
Velocity of propagation as percentage of speed of
light =  $\frac{10}{\sqrt{E}}$ 
Time delay = 1.016  $\sqrt{E}$  nanoseconds/ft
Cutoff frequency =  $\frac{7.50}{\sqrt{E}} (D + d) = F_{co} (GHz)$ 
Reflection coefficient =  $\Gamma$ 
 $= \frac{Z_r - Z_0}{Z_r + Z_0} = \frac{VSWR - 1}{VSWR + 1}$ 
 $VSWR = \frac{1 - 1}{r}$ 
Peak voltage =  $\frac{1.15 S \cdot d}{K} (LOG D/d)$ 
 $\alpha = \frac{0.435}{20(D)} \left[ \frac{D}{d} \cdot K_1 + K_2 \right] \sqrt{F}$ 
 $+ 2.78 \sqrt{E} (P.F.) (F)$ 
where  $\alpha$  = attenuation in d8/100 ft
 $d$  = the outside diameter of outer conductor in inches
D = the inside diameter of outer conductor in inches
Cof Logarithm to base 10
K = safety factor
K, = strand factor
K, = strand factor
K, = strand factor
K, = strand factor
K, = brow Mitz
P.F. = power factor
TFE 2.1
polywitykene 1.42.1
polywitykene 1.42.1
polywitykene 1.42.1
polywitykene 1.42.1
polywitykene 1.42.1
polywitykene 2.08.000
silicone rubber 2.008.000
silicone rubber 2.008.000
silicone rubber 2.008.00
silico

flexible cable is generally not available to the average ham. Its price is also prohibitive, rising into the *dollars*per-foot price range.

It is possible however, to use foam polyethylene cable up to 12 GHz. The only catch is that it must be protected from the environment by either running it through a conduit with forced dry air pumped under pressure or sheathing it in a seamless metallic tube.

#### velocity of propagation

The velocity of propagation of cable is determined primarily by the dielectric constant of the insulating

And the second	_
THE REAL PROPERTY AND A RE	
time and the Differ of Sectors Sectors	
and the second s	
HF Equipment Regular SALE	
IC-740* 9-band 200w PEP xcvr w/mic 1099.00 869*5	
10-740* 9-Dand 200w PEP xcvr w/mic 1099.00 869*	
*FREE PS-740 Internal Power Supply &	
THELF 5-740 Internal rower Supply &	1.5
\$50 Factory Rebate - until gone!	
SJU FACIULY NEUALE - UIILII golle!	1.5
	12
PS-740 Internal p/s (Special!)\$159.00 9995	
	1.5
*EX-241 Marker unit 20.00	10
*EX-242 FM unit	11
*EX-243 Electronic keyer unit 50.00	
EA-245 Electronic keyer unit 50.00	1.5
*FL-45 500 Hz CW filter (1st IF) 59.50	12
#FL E4 270 Us OW Chas (1st IF) 47.50	1.2
*FL-54 270 Hz CW filter (1st IF) 47.50	
*FL-52A 500 Hz CW filter (2nd IF) 96.50 8995	
#FI FOA 000 HE OW EN- 10-4 ID 00.00 000	
*FL-53A 250 Hz CW filter (2nd IF) 96.50 89%	
*FL-44A SSB filter (2nd IF) 159.00 14495	1
	1
SM-5 8-pin electret desk microphone 39.00	
HM-10 Scanning mobile microphone 39.50	
in it scanning mobile incrophone 33.30	
MB-12 Mobile mount 19.50	
*Options also for IC-745 listed below	1.
IC-730 8-band 200w PEP xcvr w/mic 829.00 56995	
FL-30 SSB filter (passband tuning) 59.50	10
FL 44 COD FIL 10 11FL 10 100 100	1
FL-44A SSB filter (2nd IF) 159.00 14495	
FL-45 500 Hz CW filter 59.50	1
	11
EX-195 Marker unit 39.00	
EX-202 LDA interface; 730/2KL/AH-1 27.50	10
EX-203 150 Hz CW audio filter 39.00 EX-205 Transverter switching unit 29.00	1
EX-205 Transverter switching unit 29.00	1.
CA-205 Hansverter switching unit 25.00	11
SM-5 8-pin electret desk microphone 39.00	
HM-10 Scanning mobile microphone 39.50	11
	11
MB-5 Mobile mount 19.50	11
IC-720A 9-band xcvr/.1-30 MHz rcvr1349.00 799*5	11
	11
FL-32 500 Hz CW filter 59.50	
FL-34 5.2 kHz AM filter 49.50	
SM-5 8-pin electret desk microphone 39.00	1.1
MB-5 Mobile mount 19.50	
IC-745 9-band xcvr w/.1-30 Mhz rcvr 999.00 77995	
PS-35 Internal power supply 160.00 14495	1
CELAEEVE 2.0 http://do. CCD.Ellos	
CFJ-455K5 2.8 kHz wide SSB filter 4.00	1.2
HM-12 Hand microphone 39.50	
	13
*See IC-740 list above for other options (*)	
eccie interior de enter options ( )	
the second se	1
「「「「「「」」」」 (1) (1) (1) (1) (1) (1) (1) (1) (1) (1)	
and an an and a second to the association of the later	
atesta marana ( Cha	
ETTATATATA	
E7707#### (C) SE	
C-751 9-band xcyr/1-30 MHz rcyr 1399 00 1199	
IC-751 9-band xcvr/.1-30 MHz rcvr 1399.00 1199	
PS-35 Internal power supply 160.00 14495	
PS-35 Internal power supply 160.00 14495	
PS-35 Internal power supply 160.00 144 <sup>35</sup> FL-32 500 Hz CW filter (1st IF) 59.50	
PS-35 Internal power supply 160.00 144 <sup>95</sup> FL-32 500 Hz CW filter (1st IF) 59.50 FL-63 250 Hz CW filter (1st IF) 48.50	
PS-35 Internal power supply 160.00 144 <sup>95</sup> FL-32 500 Hz CW filter (1st IF) 59.50 FL-63 250 Hz CW filter (1st IF) 48.50	
PS-35         Internal power supply	
PS-35         Internal power supply         160.00         144 <sup>35</sup> FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup> FL-53A         250 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup>	A CONTRACT OF A
PS-35         Internal power supply         160.00         144 <sup>35</sup> FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup> FL-53A         250 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup>	
PS-35         Internal power supply         160.00         144 <sup>35</sup> FL-32         500         Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup> FL-53A         250 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup> FL-33         AM filter         31.50         31.50	
PS-35         Internal power supply         160.00         144 <sup>95</sup> FL-32         500         Hz CW filter (1st IF)         59.50           FL-63         250         Hz CW filter (1st IF)         48.50           FL-52A         500         Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-53A         250         Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-53A         250         Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-53A         250         Hz CW filter (2nd IF)         31.50         81.50           FL-70         2.8         Khz wide SSB filter         46.50         46.50	<ul> <li>A state of the sta</li></ul>
PS-35         Internal power supply         160.00         144 <sup>95</sup> FL-32         500         Hz CW filter (1st IF)         59.50           FL-63         250         Hz CW filter (1st IF)         48.50           FL-52A         500         Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-53A         250         Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-53A         250         Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-53A         250         Hz CW filter (2nd IF)         31.50         81.50           FL-70         2.8         Khz wide SSB filter         46.50         46.50	<ul> <li>(a) the second seco</li></ul>
PS-35         Internal power supply         160.00         144*5           FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89*5           FL-53A         250 Hz CW filter (2nd IF)         96.50         89*5           FL-33         AM filter         31.50         81*5           FL-70         2.8 Khz wide SSB filter         46.50           HM-12         Hand microphone         39.50	
PS-35         Internal power supply         160.00         144 <sup>35</sup> FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-53A         250 Hz CW filter (2nd IF)         96.50         89 <sup>95</sup> FL-33         AM filter         31.50         81.50           FL-70         2.8 Khz wide SSB filter         46.50           HM-12         Hand microphone         39.50           SM-6         Desk microphone         39.00	
PS-35         Internal power supply         160.00         144*5           FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89*5           FL-53A         250 Hz CW filter (2nd IF)         96.50         89*5           FL-33         AM filter         31.50         81.50           FL-70         2.8 Khz wide SSB filter         46.50           HM-12         Hand microphone         39.50           SM-6         Desk microphone         39.00	
PS-35         Internal power supply	
PS-35         Internal power supply         160.00         144*5           FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89*5           FL-53A         250 Hz CW filter (2nd IF)         96.50         89*5           FL-33 AM filter         31.50         81.50         89*5           FL-70         2.8 Khz wide SSB filter         46.50         39.50           SM-6         Desk microphone         39.00         39.00           CR-64 High stability reference xtal         56.00         80.00           RC-10         External frequency controller         35.00	
PS-35         Internal power supply         160.00         144*5           FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89*5           FL-53A         250 Hz CW filter (2nd IF)         96.50         89*5           FL-33 AM filter         31.50         81.50         89*5           FL-70         2.8 Khz wide SSB filter         46.50         39.50           SM-6         Desk microphone         39.00         39.00           CR-64 High stability reference xtal         56.00         80.00           RC-10         External frequency controller         35.00	
PS-35         Internal power supply         160.00         144 <sup>35</sup> FL-32         500 Hz CW filter (1st IF)         59.50           FL-63         250 Hz CW filter (1st IF)         48.50           FL-52A         500 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup> FL-53A         250 Hz CW filter (2nd IF)         96.50         89 <sup>35</sup> FL-33         AM filter         31.50         FL-70         2.8 Khz wide SSB filter         46.50           HM-12         Hand microphone         39.50         39.50         SM-6         Desk microphone         39.00           CR-64         High stability reference xtal         56.00         MB-18         Mobile mount         19.50	<ul> <li>A state of the sta</li></ul>
PS-35         Internal power supply	<ul> <li>A state of the sta</li></ul>
PS-35         Internal power supply	<ul> <li>A set of the set of</li></ul>
PS-35         Internal power supply	
PS-35         Internal power supply	





WICKLIFFE, Ohio 44092 28940 Euclid Avenue Phone (216) 585-7388 Ohio WATS 1-800-362-0290 Outside 1-800-321-3594

**AES BRANCH STORES ORLANDO, FIa. 32803** 621 Commonwealth Ave. Phone (305) 894-3238 Fla. WATS 1-800-432-9424 Outside 1-800-327-1917

CLEARWATER, Fla. 33575 LAS VEGAS, Nev. 89106 1898 Drew Street Phone (813) 461-4267 No In-State WATS No Nationwide WATS

1072 N. Rancho Drive Phone (702) 647-3114 No In-State WATS Outside 1-800-634-6227

Associate Store CHICAGO, Illinois 60630 ERICKSON COMMUNICATIONS 5456 N. Milwaukee Avenue Phone (312) 631-5181 Outside 1-800-621-5802 materials between the conductors. This property is expressed as a percentage of the velocity of light in free space.

cable dielectric	time delay nanosec/ft	velocity percentage
solid polyethylene	1.54	65.9
foam polyethylene	1.27	80.0
foam polystyrene	1.12	<b>91</b> .0
air space polyethylene	1.17	86.0
solid teflon	1.46	69.4
air space teflon	1.16	87.5

#### cable noise

An area often overlooked by Amateurs is selfgenerated cable noise, a phenomenon noted whenever a cable is flexed. Both acoustical and electrical noise are generated. This problem can be minimized by properly securing cable to rigid physical structures during antenna system installation.

Most prevalent in the "RG" series cables (RG-8, RG-213, RG-58, etc.) and should be carefully considered by hams who are concerned with feedline performance.

#### environmental resistance

The life of a coaxial cable depends on many factors other than the materials used in manufacture. The following factors all contribute to cable failure.

**UV exposure**. Polyethylene-jacketed cable has twice the life expectancy when exposed to direct sunlight as cable manufactured with PVC (Polyvinyl chloride) jackets.


**Humidity**. All cables experience vapor transmission through their plastic jackets. In Amateur applications it is advisable to install cable where it will not lie in or pass through an area where standing or running water is present.

**Salt-water immersion**. The electrical characteristics of cable will be rapidly affected if the conductors are exposed to salt water. If you live near a large body of salt water inspect your coax regularly for salt build-up. If your cable should become immersed, try to test the cable with a TDR (time-domain reflectometer) or find someone who can "sweep it" over the frequency range that your antenna system operates.

**Underground burial and galvanic action**. If you are going to install antenna cable underground, use armored/waterproof coaxial cable or regular "RG" cable installed in conduit or similar protective pipe or tubing.
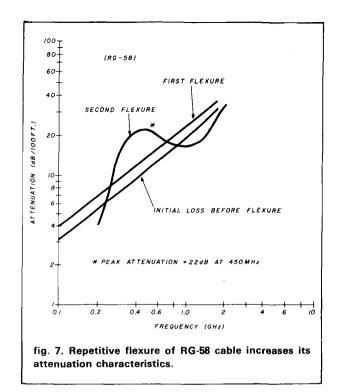
#### selection guide

For the Amateur interested in communications through 50-MHz, RG-58 and RG-59 are prudent and inexpensive choices, though their power handling



capability is limited to 250 watts for RG-58 and 450 watts for RG-59.

A station designed to operate through 148 MHz should incorporate RG-8 or RG-213 coaxial cable. Unfortunately, the 3-dB roll-off point is just below 200 MHz. 220-MHz operation is possible, but 50 percent of transmitted power will be lost in a typical 100 foot run.

Many exotic transmission lines are available for 220 MHz and above. Flexible foam dielectric cable (FM-8 or FM-11, similar to RG-8 and RG-11) is useful up to 450 MHz but very susceptible to moisture penetration.

Flexible low loss cables are manufactured with braids of flat strips of silverplated copper. This helps to lower the VSWR and reduce attenuation above 1 GHz. Type SF-226, for example, is good through 10 GHz and its outside diameter is not much larger than that of RG-8.

For operation above 10 GHz I suggest using corrugated tubular aluminum with foam teflon dielectric, which is available in 3/8-inch OD for operation through 15 GHz. This cable is similar in appearance to the "BX" type of electrical conduit. The bend radius of this cable is 2.0 inches — an important fact to remember during installation.

The most popular coaxial cable among microwave enthusiasts is "hardline" or semi-flexible foam dielectric cable. It is available in various ODs, but for coverage through 22 GHz 1/4-inch OD is your best choice. Although this cable is quite expensive, CATV companies will occasionally discard it because of minor imperfections or oxidation on the outer jacket. This

### AMATEUR TELEVISION



#### KPA51 WATT 70 CM ATV TRANSMITTER BOARD

- APPLICATIONS: Cordless portable TV camera for races & other public service events, remote VCR, etc. Remote control of R/C airplanes or robots. Show home video tapes, computer programs, repeat SSTV to local ATVers, DX depends on antennas and terrain typ. 1 to 40 miles.
- FULL COLOR VIDEO & SOUND on one small 3.25x4" board.
- RUNS ON EXTERNAL 13.8 VDC at 300 ma supply or battery.
- TUNED WITH ONE CRYSTAL on 426.25, 434.0, or 439.25 mHz
- a 2 AUDIO INPUTS for a low Z dynamic and line level audio input found in most portable color cameras, VCRs, or home computers.
- APPLICATION NOTES & schematic supplied for typical external connections, packaging, and system operation.
- PRICE ONLY \$159 delivered via UPS surface in the USA. Technician class amateur license or higher required for purchase and operation.

WHAT IS REQUIRED FOR A COMPLETE OPERATING SYSTEM? A TV set with a TVC-2 or TVC-4 420-450 mHz to channel 3 downconverter, 70 cm antenna, and coax cable to receive. Package up the KPA5, add 12 to 14 vdc, antenna, and any TV camera, VCR, or computer with a composite video output. Simple, eh?

CALL OR WRITE FOR OUR COMPLETE CATALOG & more into on atv downconverters, antennas, cameras, etc., or who is on in your area.


TERMS: Visa, Mastercard, or cash only UPS COD by telephone or mail. Telephone orders & postal MO usually shipped within 2 days, all other checks must clear before shipment. Transmitting equipment sold only to licensed amateurs verified in 1984 Callbook. Calif. include sales tax.

(818) 447-4565 m-f 8am-6pm pst.

P.C. ELECTRONICS Tom W60RG Maryann WB6YSS

\$319.00

Shipping extra

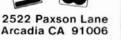

discarded cable is suitable for Amateur service. The only real problem with its use and installation is the proper attachment of connectors; this task should be farmed out to your local Amateur microwave expert or to your local cable connector technician!

For use above 22 GHz, tubular copper telfon dielectric cable has *no* radiation loss except at the connector interface. An example is CL-50087T, which is good through 60 GHz. Difficult to work with and very expensive, this type of cable is used in military avionics.

#### conclusion

Considering the many electrical and physical characteristics that must be analyzed, selection of RF coaxial cable is really quite complicated. Knowing these parameters is important when attempting to design a communications system for optimum performance.

I am willing to provide additional information on cable, connectors, and installation procedures. Please send requests to my home address, which appears at the beginning of this article. (Please be sure to enclose a legal-size SASE with 3 first-class stamps or IRCs; only inquiries with SASEs can be answered.)

ham radio



675 Great Rd., (Rte. 119) Littleton, MA 01460 1<sup>3</sup>/<sub>4</sub> miles from Rte. 495 (Exit 31) toward Groton, Mass.

## balun chop suey

A collection of odds and ends on 1:1 transmissionline baluns


In San Francisco's famous Chinatown, I learned a secret: the words "chop suey" mean "odds and ends," which is apparently what that familiar Chinese dish is composed of. This article, a collection of odds and ends about 1:1 transmission-line baluns, is based on comments and questions I have been asked as a result of my previous balun articles. None of the individual comments is long enough to warrant separate articles — hence the peculiar title. These odds and ends also refer to balun articles presented by other writers. I hope this discussion will interest balun users and designers alike.

#### introduction

First, to establish a frame of reference, I plan to discuss transmission-line baluns with input-output impedance ratios of 1:1. The transmission line is wound into an inductance, usually on a ferrite form, either a rod or a toroid.

A balun serves two purposes: first, to provide equal and opposite voltages to a balanced load, and second, to provide isolation between the coax outer conductor and the half of the balanced antenna connected to the outer conductor. Because the second is the more difficult problem, I will limit my discussion to it.

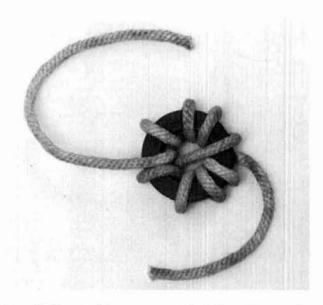The isolation requirement of a balun has been well defined qualitatively by Walter Maxwell, W2DU.<sup>1</sup>



A toroidal core with a super-toroid winding. This core is wound with clothesline for photographic purposes.

Maxwell's article was the first to describe, in the Amateur literature, the concept of separate currents flowing on the inside and outside of the outer conductor, representing the signal current and unbalanced currents, respectively. I have found this concept helpful in describing the isolation function of a balun, both in a previous article<sup>2</sup> and in this one. I will expand on Maxwell's comments by giving some numbers to specify isolation quantitatively.

#### isolation

The isolation function of a balun is to provide a high impedance between the outside of the outer conductor, and that half of the dipole antenna connected to the outer conductor, without affecting the current flowing on the inside of the outer conductor to its half of the dipole. Very little appears to have been published, at least in the Amateur literature, either quantitatively or qualitatively, on the isolation property of a balun.

Briefly, isolation is necessary to ensure that the signal current flowing on the inside of the outer conductor flows into the antenna, not back down the outside of the outer conductor to ground. Lack of sufficient isolation is one reason antenna currents become unbalanced.

By John J. Nagle, K4KJ, 12330 Lawyers Road, Herndon, Virginia 22071



220 N. Fulton Ave. Evansville, IN 47710 Technical 1-812-422-0252 Indiana 1-812-422-0231

5	SUPER ANT	ENNA SALI	-	
CUSHCRAFT MULTI-BAND A3         \$215.00           A4         269.95           A743/A744         75.00           B3 Motor Tuned Vert.         279.00           A5 80-10M Vertical         99.00           VHF-UHF         215WB 2M Wide Band         79.00           230WB Stacked 215's         219.00           32-19 Boomer 19ELE 2M         95.00	HY-GAIN         \$435.00           TH7 DXS Tribander         \$435.00           TH5 MK2S 5ELE         389.00           Explorer 14 3ELE         299.95           QK710 30/40Mtr Kit         79.00           205BAS 5ELE 20Mtr         349.00           204BAS 4ELE 20Mtr         259.00           66 BS 6ELE 6Mtr         135.00           18HTS 80-10M Vertical         439.00           18AV0/WBS 80-10M Vertical         104.95           14AV0/WBS 40-10M Vertical         75.00	KLM         \$335.00           KT-34         \$335.00           KT-34XA         485.00           2M-14C 2Mtr Circular         85.00           2M-18C 440 Circular         65.00           2M 16LBX 2 Mtr         105.00           2M 22C Circular         120.00           2Mx2C Stacking Frame         79.95           435-40CX Circular         149.95           Plus Much More         149.95	D         G6 144 2M Vertical         85.9           G 64 40 440 Vertical         109.9           O         6BTV 80-10M Vertical         129.9           0         MO-2 Mast         23.9           0         MR-80 400W PEP         19.9           0         RM-75 400W PEP         19.9	
A147-4         32.95           A449-6         34.00           A449-11         44.00           Ringo Rangers 2M, 6M, 220,         450           450         39.95           OSCAR TWIST         54.00           A144-10T         54.00           A144-20T         75.00	23BS 3ELE 2Mtr         28 00           25BS 5ELE 2Mtr         36 00           28BS 8ELE 2Mtr         49 00           V2S 2 Mtr Vertical         49 00           V3S 220 Vertical         55 00           V4S 440 Vertical         65 00           BN66 Balun         19 00           Telex Headsets in Stock—Call	BUTTERNUT           HF6V 80-10M Vertical         \$119.95           HF2V 80/40M Vertical         115.95           2MCV5 2 Mtr Vertical         55.00           TBR-160-S 160M Resonator         49.00           RMK-II Roof Mount Kit         49.00           STR-II Stub Tuned Radials         29.00	RM-15/RM10 400W PEP ea. 12.95 SF-2 2M Mobile 13.95 CG-144 2M Collinear 33.95 CGT-144 Collinear w/Trunk Mt. 53.95 Bumper Mounts—Springs in Stock CABLE	
A147-20T 75.00 416TB 64.00 AOP-1 Package 149.00 BOTORS	TOWER Large Stock of Rohn 25G in Stock Call for Your Discount Price	ANTENNA SPECIALISTS (Avanti) AP153.3G 2M on Glass \$34.00 AP200.3G 220 MHZ on Glass 38.00 AP450.3G 450 MHZ 34.00 AP450.5G 450 MHZ 38.00	Standard 8 Cond         25/tt           Heavy Duty 8 Cond         36/tt           RG8U 97%         35/tt           RG8X 97%         25/tt           RG213U         35/tt	
Alliance HD73         99.95           Alliance U110         49.95           Telex CD-45         139.95           Telex Ham 4         219.00           Telex T2X         269.00           KenPro KR 500         185.00		Prices—For Orders & Quol ome—Freight, F.O.B. Evansville—Prices	1949년 1949년 11 - 1851년 1841년 1841년 1871년 1871	
	PLUS RIGS	<b>RIGS RIGS</b>		
ICOM	TEN-TEC	ENCOMM	YAESU	
Call for Your Special Price           ICOM         \$1179.00           751 Top of the Line         \$1179.00           745 Gen. Cov. Xcvr         769.00           R71A Gen. Cov. Rcvr         629.95           271A 2M All Mode         599.95           271H 2M 100W         749.95           471A 430-450MHZ 25W         699.95           471H 430-450MHZ 75W         949.75           27A 2M 25W Mobile         319.95           27H 2M 45W Mobile         355.00           37A 220MHZ Mobile         299.95	Call for Discount Price           TEN-TEC         260 P.S./Spkr         \$ 170.00           263 VFO         170.00         249.95           229 ZKW Tuner         249.95         229.10           25D Argosy         525.00         2510 Satellite Station         399.95           2591 2M H.T         269.95         1715.00         220, 288, 285, 282 Filters         ea.55.95	List 339.00—Sale 265.00 TOKYO HY-POWER HL30V 2M Amp 2:30FM \$ 62.95 HL35V 2:30FM PreAmp 74.95 HL35V 2:0FM PreAmp 10-80 149.95 HL160V 2M, PreAmp 3/10-160 295.00 HL20U 440-450 2:20 105.00 HL90U 440-450 10-90 315.00 HRA-2 GasFet PreAmp 119.00 HRA-7 GasFet PreAmp 119.00	Call for Special Price           YAESU         F1980 Deluxe Xcvr         \$1425.00           FT757HD P.S. w/Fan         175.00           FC757AT Auto Tuner         235.00           MMB-20 Mounting Bracket         24.00           FT726R Tri-Band Xcvr         779.00           H.F. Module         205.00           6M Module         189.95           430 Module         249.95           FT203RH 2M H.T 5W         299.95           FT203RHT         229.95	
47A 440 MHZ Mobile         399.95           2AT 2Mtr H.T         199.95           3AT/4AT 220/440 H.T.'s         ea.229.95           NEW 3200 Dual-Bander         CALL           02AT 2Mtr H.T.         289.95           04AT 440MHZ H.T.         319.95           BC-35 Drop In Rapid Chgr         65.00           All Accessories in Stock         All Accessories in Stock	MIRAGE         \$ 89.95           B23A 2:30W PreAmp         \$ 89.95           B108 10-80W PreAmp         159.95           B3016 30-160W PreAmp         204.95           B1016 10-160W PreAmp         249.95           D24N 2:40W 430-450         184.95           D1010N 30-100W 430-450         279.95	KANTRONICS           Packet Communicator         \$349.95           U.T.U. Universal Terminal Unit         179.95           Interface II         229.00           The Challenger         89.95           All HamSoft, Hamtext, AMTOR Programs in Stock—Call for Discount Price	Much Much More in Stock           ASTRON POWER SUPPLIES           RS7A 5-7 Amp         \$ 49.00           RS10A 7.5-10 Amp         59.00           RS12A 9-12 Amp         69.00           RS20A 16-20 Amp         89.00	
AMERITRON AL84 \$ 399.95 AL80 3-5002 Tube 609.95 AL1200 1419.00 RCS-8 Remote Coax Switch 119.95 CALL FOR PRICES ON	AEA         \$189.95           CP-1 (C-64 or Vic 20 Software         229.95           Package         229.95           MP-20 or MP-64         149.95           MAP-64 w/AMTOR         199.95           MP-1—Micropatch         CALL           DR. DX         99.95           PKT-1 Packet Controller         459.95	MFJ         \$159.95           1229 Interface/Free Software         \$159.95           1224 Interface/Free Software         85.00           1228 Interface/Free Software         62.95           989 3KW Roller Inductor Tuner         289.95           941D 300W Full Feature Tuner         89.95           422 Keyer/Bencher Paddle         Combo           Combo         99.95           313 H.T. Converter         36.00           106 24 Hr. Clock         19.95	RS20M 16-20 Amp w/meter         109.00           RS35A 25-35 Amp         135.00           RS35M 25-35 Amp w/meter         149.00           RS50A 37-50 Amp w/meter         199.00           RS50M 37-50 Amp w/meter         225.00           VS20M Dual Mtrs, Adj. Voltage         175.00           VS50M Dual Mtrs, Adj. Voltage         250.00           DAIWA         DAIWA	
MON-FRI 9AM-6PM SAT 9AM-3PM	BENCHER     459.95       BSOOles, Hotrods, Software in Stock       BENCHER       BY-1 Black Base     \$39.00       BY-2 Chrome Base     49.00       ZA-1A Balun     19.00	B & W         370:15 80-10M Folded Dipole         \$135 00           AT-110 5 Band Trap Dipole         76 00           AT-55 4 Band Trap Dipole         58 00           CS-3G Coax Switch 3 Pos         27 25           CS-6B Coax Switch 6 Pos         32 00           CSP-5G Coax Switch 5 Pos         24 75           AC-1 Center Insulator         6 95	DAIWA         \$ 63.00           CN520 1.8-60 MHZ         \$ 63.00           CN540 50-148 MHZ         72.00           CN550 144-250 MHZ         81.00           CN620B 1.8-150 MHZ         110.00           CN630 140-450 MHZ         130.00           CN720B 1.8-150 MHZ         129.95           CS201 2 Pos. Switch         23.00           CS-401 4 Pos. Switch         62.00	


In its simplest terms, the situation can be considered as a circuit problem. To ensure that the transmissionline current flows into the antenna and not back down the outside of the outer conductor, the impedance provided by the path down the outside of the outer conductor should be many times that of one-half the dipole antenna. For example, if the impedance of the dipole antenna is assumed to be 70 ohms, the impedance of one-half the dipole will be 35 ohms. By making the impedance of the balun to these "outside" currents 10 times this impedance, or 350 ohms in this case, at least 90 percent of the transmission-line current will flow into the antenna and less than 10 percent back down the outside of the coax.

A balun impedance of five times the load impedance (as used above) is an arbitrary figure, although I feel it should be adequate for a general-purpose balun. For a precision balun, one might prefer an isolation of, say, 10 or more times the impedance presented by onehalf the total load. In a transmission-line balun, the isolation is provided by the inductive reactance of the winding. The isolation actually provided by a given balun can be determined by measuring the inductive reactance as described in reference 2.

Assuming a linear inductor, as long as the operating frequency is well below the self-resonant frequency of the inductor, the inductive reactance will be directly proportional to frequency. Therefore, there will be a frequency below which the inductive reactance will not be sufficient to provide the required isolation between the antenna and the coax feedline. This determines the low frequency limit of the balun.

The maximum usable frequency of a balun is limited by the stray capacitance across the winding. As the operating frequency increases, a frequency will be reached where the stray capacitance across the balun resonates with the inductance of the winding so that the winding is in parallel resonance. At this frequency the impedance of the balun, and hence its isolation, is the maximum it will be, so that this is a desirable frequency at which to operate. As the operating frequency is further increased, the reactance of the balun becomes capacitive and decreases with frequency until the balun becomes series-resonant. At this frequency the balun impedance is very low and the balun provides virtually no isolation at all. The upper useful frequency limit of the balun is usually between the parallel and series resonant frequencies. The actual frequencies are a function of the construction techniques, the object being to maximize the inductance and minimize the stray capacitance across the winding. (This problem is a subject in itself.)

Fig. 1 shows the inductive reactance versus frequency of a typical transmission-line balun. From a graph such as this, the useful frequency range of the balun can be easily determined for any value of load

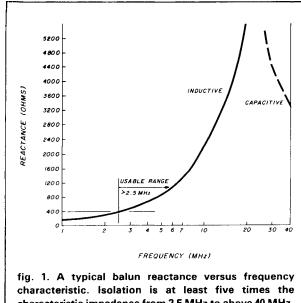

characteristic impedance from 2.5 MHz to above 40 MHz. (From reference 2.)

impedance. The assumed isolation impedance of five times the load impedance, based on VSWR considerations, has been arrived at by others.


To put the isolation property of a balun on a sound technical basis from the user's point of view, I believe balun manufacturers should specify the minimum ratio of the balun winding impedance to the characteristic impedance over the specified frequency range.

#### testing core saturation

The methods used for testing a balun for core saturation are simple; one method is to wrap a few turns of insulated wire around the balun, as shown in fig. 2, and then connect this winding to an oscilloscope to observe the waveform. Gradually increase the output power of the transmitter until a distorted waveform appears. Then back off the power until the waveform again becomes sinusoidal. This represents the maximum peak power a given balun can handle.

A more sensitive version of this method involves connecting the test winding to a spectrum analyzer, instead of an oscilloscope, and measuring the amplitude of the various harmonics. Care must be taken here, however, to make certain the harmonics measured are generated by the balun and not by the transmitter.

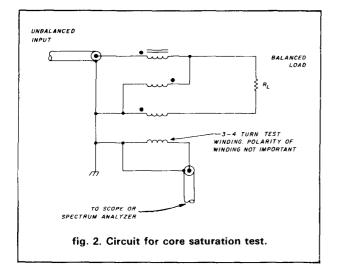An even more sensitive test is to use the RF equivalent of the two-tone test used to measure intermodulation distortion on high-fidelity audio equipment or receiver front-ends. Here two transmitters operating on slightly different frequencies are connected to the balun (and a dummy load) through a diplexer. This test



was proposed by Rich Rosen, K2RR, editor-in-chief of *ham radio*; I have not tried it myself.

If saturation is present, it can be corrected by increasing the number of turns, or by using a larger core (cross section), or both.

Increasing the number of turns will also have the effect of improving the performance of the balun at the low end of the frequency range. It will also lower the high-frequency end of the range by reducing the self-resonant frequency of the winding.

If the existing winding efficiently uses the available winding area, it will be necessary to increase the size of the core to accommodate the additional turns unless it is possible to use smaller wire. However, in a transmission-line balun the wire size may be dictated by the desired (or required) characteristic impedance of the winding; the wire diameter and spacing — being parameters — determine the characteristic impedance of the winding.

While the equipment needed and the procedures are relatively simple, the practical problems of testing baluns can be substantial. First, it takes a high-power transmitter and a high-power, preferably balanced, dummy load. Most Amateurs, however, will probably use an unbalanced load because this type is the most readily available. Care must be taken that the load case is well insulated from ground because the case will be at one-half the unbalanced line voltage when used as a balanced load.

The transmitter must be capable of providing the highest power level at which the balun is expected to operate. The balanced dummy load, of course, must be capable of dissipating this amount of power.

A more convenient load, at least if you are testing the balun for your own use, is to use the regular station antenna. (Choose a time when the band is dead!) The problem here is that the balun will be high in the air, requiring long test leads in a high-power antenna field, because RF can be picked up by the line and result in inaccurrate measurements.

#### transformers or inductors?

One of the principal sources of confusion in balun design, construction, and use seems to be the belief that all baluns are transformers. One well-respected writer recently stated "It is important to recognize that a 4:1 or a 1:1 balun . . . is essentially a broadband transformer." If he had stopped to think about it, I'm sure this writer would have known better. Strictly speaking, any device or collection of components which transforms a balanced line to an unbalanced line can be called a transformer; in electronics the expression "transformer" is usually reserved for one particular type of device where all, or part, of the energy passes from input to output by means of magnetic induction. The usual two-winding or three-winding 1:1 transmission-line balun, however, is not a transformer because none of the energy is transmitted from input to output by magnetic induction. This type of balun should not be designed, tested, or used as a transformer. A 1:1 transmission-line balun is an inductor wound with a transmission line and must be designed, tested, and used as an inductor wound with a transmission line. Failure to recognize this difference in design or application is almost certain to lead to disappointment in the use.

Further complicating the situation is the fact that a transmission-line balun can be constructed with impedance transformation ratios other than 1:1, although I have not seen this done in Amateur applications. The common 4:1 balun is really an auto-transformer and not a transmission line device.

A broadband transformer, on the other hand, must be designed in accordance with well-known transformer equations relating the number of turns, the peak voltage, and the allowable maximum magnetic flux density in the core.

A second means of distinguishing between transformer and transmission-line baluns is that with a transformer balun, the relationship between the load impedance and input impedance is the turns ratio squared. With a transmission-line balun, the load-toinput impedance ratio is calculated using the more complex transmission-line equation:

$$Z_{in} = \frac{Z_{ch} \left( Z_r \cos \theta + j Z_{ch} \sin \theta \right)}{\left( Z_{ch} \cos \theta + j Z_r \sin \theta \right)}$$
(1)

There are two problems in designing transmissionline baluns. The principal problem is designing a wideband inductor, i.e., an inductor whose reactance is above a given value — usually five to ten times the load impedance — over the desired range of frequencies. The second problem is designing a suitable trans-

### ham **radio** Reader Service

For literature or more information, locate the Reader Service number at the bottom of the ad, circle the appropriate number on this card, affix postage and send to us. We'll hustle your name and address to the companies you're interested in.

 101
 113
 125
 137
 149
 161
 173
 185
 197
 209
 221
 233
 245
 257
 269
 281
 293
 305
 317
 329
 341

 102
 114
 126
 138
 150
 162
 174
 186
 198
 210
 222
 234
 246
 258
 270
 282
 294
 306
 318
 330
 342

 103
 115
 127
 139
 151
 163
 175
 187
 199
 211
 223
 235
 247
 259
 271
 283
 295
 307
 319
 331
 343

 104
 116
 128
 140
 152
 164
 176
 188
 200
 212
 224
 236
 248
 260
 272
 284
 296
 308
 320
 332
 344

 105
 117
 129
 141
 153
 165
 177
 189
 201
 213
 225
 237
 249
 261
 273
 285
 297
 309
 3

Limit 15 inquiries per request.

NAME		CALL	_
ADDRESS			
CITY	STATE	ZIP	

	*		
		 _	

AFFIX POSTAGE OR POST OFFICE WILL NOT DELIVER

## ham **radio**

magazine

READER SERVICE CENTER P.O. BOX 2558 WOBURN, MA 01888

ATTN: Reader Service Dept.

mission line, with the required characteristic impedance, capable of being wound on a ferrite core.

Briefly summarizing, because of the similarity in the appearance and circuit configuration of different types of baluns and transformers, both of which use magnetic cores, there is considerable confusion about their operating characteristics. This in turn leads to improper design and application of the devices. Before criticizing a device, one should make certain it has been properly designed and used.

#### the super-toroid


The super-toroid balun design was introduced to the Amateur community by Reisert in his article on the two-winding transmission-line balun.<sup>3</sup> The concept of a super-toroid, however, was developed by Tom Gross in the early 1960's; Gross is a designer of precision magnetic components who specializes in devices operating at supersonic frequencies — 20 kHz to 500 kHz and up. The purpose of the super-toroid design is to reduce the sensitivity of the conventional toroidal coil to external magnetic fields.

Contrary to popular belief, a single-layer toroidal inductor is sensitive to external magnetic fields because of what is known as the one-turn effect. With a conventional, single-layer toroid, the winding is spirally wound around the core, as seen in **fig. 3**. Each turn is composed of two winding components: one component is aligned with the center of the toroid. The other component is at a right angle to the radial component and is known as the circumferential component. These two components are emphasized in **fig. 4**. The circumferential component provides the progression of the winding around the core. If there were no circumferential component, each turn would lie on top of the preceding turn.

The circumferential components constitute a singleturn loop antenna which, as is well known, has a response to extraneous signals originating in the plane of the toroid, as shown in **fig. 5**. This is known as the "one turn" effect of a toroidal winding. If the winding has more than one layer, the single-turn effect becomes an N-turns effect, where N is the number of layers.

The super-toroid design eliminates the one-turn effect by winding half the turns in one direction, then running the winding across the diameter of the core to the opposite side and winding the other half of the core in the opposite direction. The voltages induced in the circumferential components are therefore equal and opposite and therefore cancel. The photo shows a core wound in this manner. The winding in this case is clothesline rope to show up better in the photograph.

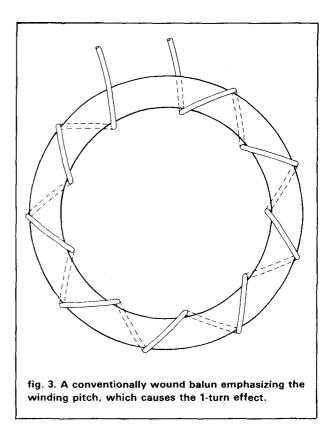This technique assumes that the *external* magnetic field is uniform through the diameter of the core and




the core material is homogeneous. If both these conditions are not met, even more complex types of windings must be used to provide isolation from external magnetic fields.

A secondary advantage of the super-toroid design, and one that is much more important to balun designers, is the fact that the effective capacitance across the winding is reduced, which increases the usable bandwidth of the device.

Any inductor consists of stray capacitance as well as inductance. In the design of an inductance, the object, of course, is to maximize the inductance and minimize the capacitance. As seen in **fig. 6**, this capacitance consists of an infinitely large number of incremental capacitances such as the capacitance between adjacent turns, capacitance between turns that are not adjacent, and between the ends of coil. From an engineering standpoint, it is not practical to evaluate an infinite number of small capacitances. Therefore, the "effective capacitance" of an inductor is defined as that of a physical capacitor connected across the ends of the inductor, which stores the same amount of energy as that stored by the incremental capacitors.

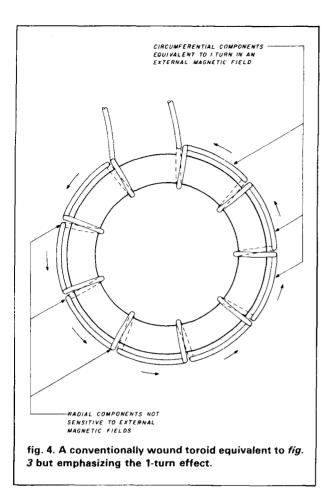The energy stored in a capacitor is proportional to the product of the physical capacitance and the voltage across the capacitor squared:  $Energy = \frac{1}{2}$  $CV^2$ . If the two plates of a capacitor are at the same potential, the energy stored by the capacitor is zero



and the effectiveness of the capacitor is nil. It is, therefore, important that the portions of an inductance that are at the greatest potential difference have the lowest possible physical capacitance. The ends of the winding are at the greatest potential difference, hence they should have the greatest separation to minimize the physical capacitance.

A super-toroid has the ends of the windings at opposite ends of the core diameter, which is about as far apart as it is possible to place them. A conventionally wound balun, on the other hand, has the ends of the windings adjacent to each other, where they have the highest capacitance. It is, therefore, easy to see why the super-toroid winding would have a lower effective capacitance and hence a greater bandwidth. Then why not use the super-toroid winding exclusively?

For a two-winding balun, the super-toroid winding is preferable. For a three-winding balun, the situation is complicated by the tertiary interconnections between the opposite ends of the two main windings. With a continuously wound toroid, these interconnections can be short and can have a low impedance. With a super-toroid winding, the two leads of the tertiary winding come out on opposite sides of the core, so that both tertiary leads must cross the core. This greatly increases the leakage reactance between the main winding and the tertiary winding and will prove detrimental to proper balun operation above 20 MHz.

Thus, even though the super-toroid winding inherently gives greater bandwidth, it should not be used for a three-winding balun. For three-winding baluns, it is necessary to use a continuous winding to ensure short, low impedance interconnections between the tertiary and main windings.

#### wide bandwidth?

Numerous *ham radio* readers have questioned the desirability, or necessity, of the wide bandwidths advertised for commercial baluns — typically 3.5 to 30 MHz, and more recently, 1.5 to 56 MHz. Are bandwidths this wide really necessary? Or desirable? The argument is that since few, if any, Amateurs use the same antenna for 80 through 10 meters, much less 160 through 6 meters, why insist that a balun cover a greater, wider bandwidth than the antenna?

My own opinion is that these wide bandwidths are unnecessay and may not be desirable. The antenna installation for a typical Amateur active in the HF region might be a dipole on 80/75 meters or 40 meters plus a triband beam for 20, 15; and 10 meters. If space permits, maybe a 6-meter beam, too. Therefore, a balun that gave high performance, say, from 3.5 to 10 MHz and a second balun optimized for 14 to 30 MHz could be designed to provide higher performance at the extreme edges of these bands than a single wideband balun covering the entire frequency range.

This has been substantiated by my own experience in building and measuring baluns. Wideband baluns - 80 through 10 meters - gave marginal but acceptable performance at the low end of 80 meters and at the high end of 10 meters. The isolation impedance was just barely equal to five times the characteristic impedance of the transmission line.


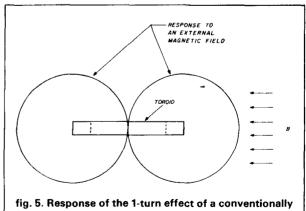


fig. 5. Response of the 1-turn effect of a conventionally wound toroid caused by the circumferential components to a magnetic field, B, parallel to the plane of the toroid.

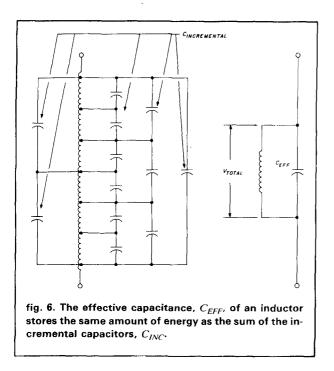

By adding one or two turns to the winding I could dramatically improve the performance at the low end of 80 meters, but the series resonant frequency occurred in the middle of the 10-meter band. Similarly, by removing a turn or two I could improve the isolation at 10 meters, but only at the expense of the 80-meter band.

In my opinion, the bandwidth performance of presently available baluns is limited by the following factors:

State-of-the-art in presently available core materials
 for example, higher permeabilities at the higher

frequencies.

• The limitations imposed on the design by having to wind the core with a transmission line of a specified characteristic impedance rather than a single conductor as with the usual inductor.

• The need to handle an appreciable amount of power.

The reasons commercial baluns for Amateur applications are all wideband devices may include:

• Competition: no manufacturer can afford to offer a balun with less bandwidth than any other manufacturer.

• Lack of published specifications concerning isolation impedance, balance, and isolation make it impossible to tell how effective a given balun may be at the band edges.

 Economy: it is much less expensive for manufacturers and distributors alike to stock a single balun than several different "sizes." For these reasons, I believe that if Amateurs want high-performance baluns optimized for particular bands, they will have to wind the balun themselves.

#### final comments

Physically, transmission-line baluns are very simple devices. This simplicity often causes some of the more subtle characteristics to be overlooked during design or use. Recognizing these subtleties may be the biggest problem in designing and using baluns.

#### reference

1. Walter Maxwell, W2DU, "Some Aspects of the Balun Problem,"  $\ensuremath{\textit{QST}}$  , March, 1983, page 38.

 John J. Nagle, K4KJ, "Testing Baluns," *ham radio*, August, 1983, page 30.
 Joe Reisert, "Simple and Efficient Broadband Balun," *ham radio*, September, 1978, page 12.

ham radio

### short circuits digital HF radio

In "Digital HF Radio: A Sampling of Techniques" (April, 1985) the author's name was misspelled. "Dr. Ulrich L. Rhode," as it appears on page 18, should be corrected to read, "Dr. Ulrich L. Rohde." *ham radio* regrets the error.

### harmonic mixer

In **fig. 2** of K1ZJH's "Harmonic Mixer for VHF Signal Generation" (March, 1985, page 40), T1 should be identified as a T37-6 toroid available from Amidon Associates, Inc., 12033 Otsego Street, North Hollywood, California 91607.


#### May 1985 low-voltage power supplies

In fig. 9 of the March article, "Designing Low-Voltage Power Supplies," Q1, Q2, and Q3 are shown incorrectly wired. The base leads of Q1 and Q2 should be connected to the *collector* of Q3, not its base.



COMPUTER PRODUCTS, Inc. ORDER TOLL FREE (800) 538-8800 (CALIFORNIA RESIDENTS) (800) 848-8008	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	1         MHZ         2         MHz           65022         4.90         65024         5.90           6504         6.90         65204         5.90           6505         8.90         65224         9.90           6507         8.90         65224         9.90           6507         8.90         65524         10.90           6522         4.30         65514         12.90           6532         9.90         3         MHz           6532         9.90         3         MHz           6551         9.90         65028         7.90           6800         1         9.90         65028         7.90           6800         2.90         2         MHz         6800           6801         7.90         68800         9.90         6802         1.90           6802         7.90         68800         9.90         6802         1.90           6802         7.90         68800         9.90         6802         1.90           6802         7.90         68800         9.90         6802         1.90           6802         7.90         68800         9.90         6802	4 POSITION 79 5 POSITION 85 6 POSITION 85 7 POSITION 85 8 POSITION 85 8 POSITION 85 14 pin 21F 485 16 pin 21F 485 24 pin 21F 586 24 pin 21F 586 24 pin 21F 586 26 pin 21F 5
V/SA         MasterCard           2101         255 1 4 (450m)         1.90           5101         255 1 4 (450m)         1.90           2102-1         1024 1 (450m)	741.833       59       741.8196       78       741.8669       1.85         741.836       58       741.819       78       741.8669       1.85         741.836       38       741.827       78       741.8670       1.45         741.836       38       741.827       78       741.8670       1.45         741.830       34       741.8270       94       741.8670       1.45         741.830       34       741.8240       94       741.8682       3.15         741.830       34       741.8243       98       741.8682       3.15         741.830       34       741.8243       98       741.8684       3.15         741.830       36       741.8243       98       741.8688       2.35         741.810       38       741.8245       98       741.869       3.15         741.8112       38       741.8249       98       81.857       1.45         741.8112       38       741.8251       58       81.857       1.45         741.8112       38       741.8253       58       81.857       1.45         741.8123       741.8253       58       81.8157       1.45	BOOO           8031         14.90         8253         6.90           8035         5.90         8253         7.90           8039         5.90         8255         4.45           185-8050         16.90         8255         4.80           185-8073         22.90         8257         7.90           8085         4.90         8257         7.90           8085         4.90         8259         5.90           8085.42         11.90         8259         5.90           8085.42         11.90         8259         5.90           8087.2         19.90         8274         28.90           8087.2         19.90         8274         28.90           8089         59.90         8275         28.90           8089         59.90         8274         28.90           8100         8282         6.45           8131         2.90         8284         4.90           8155         6.90         8286         6.45           8155         8.90         8286         6.45           8155         8.90         8286         6.45           8155         8.90         829	ZIF = TEXTOOL (Zero Insertion Force)           IC SOCKETS (1 to 99)           8 pin ST.         12         8 pin WW.         58           14 pin ST.         14         14 pin WW.         58           16 pin ST.         16         16 pin WW.         58           16 pin ST.         16         16 pin WW.         98           20 pin ST.         25         20 pin WW.         1.04           21 pin ST.         25         22 pin WW.         1.34           24 pin ST.         29         24 pin WW.         1.64           40 pin ST.         39         26 pin WW.         1.64           40 pin ST.         46         40 pin WW.         1.64           40 pin ST.         48         40 pin WW.         1.64           50 pin ST.         48         40 pin WW.         1.64           51 pin ST.         29         50 pin WW.         1.64           51 pin ST.         48         40 pin WW.         1.64           51 pin ST.         48         40 pin WW.         1.64           52 pin SCO         52 pin WW.         1.64         59           1.000         1.0000 MHz         6.99           1.843         1.8432 MH
IM8224U-12         BIB 2 is 8 [120s] [cms1](Im1 24.95         Mil           IP = Low Power         Getat = Quasi-Static         68           DYNAMIC RAMS         125s         1300s1         1.45           UP0411         4096 is 1 [300s1         1.95         1.45           UP0411         4096 is 1 [300s1         1.95         1.75           MX5280         4096 is 1 [300s1         1.95         1.75           MX5280         4096 is 1 [300s1         1.95         1.75           MX5280         4096 is 1 [300s1         1.95         1.74           MX106 8 1392 i [200s1         4.9         17         1.41           4116-15         16384 i [120s1         4.9         17           4116-12         16384 i [120s1         1.49         17           4116-12         16384 i [120s1         1.49         17           416-12         16384 i [120s1         1.49         17           4164-25         65535 i [120s1<[5v]	MC1372         6.90         TMS9918A         36.95           JB047         23.95         DP8350         48.95           DISC CONTROLLERS           171         14.95         2797         54.95           791         21.95         6843         33.95           793         25.95         6272         16.95	8224         220         8700           8228         1.75         8741         28.90           8228         3.45         8748         19.90           8237         12.90         8749         28.90           8237         12.90         8749         28.90           8238         4.45         80000         8755         23.90           8250         9.90         80186-6         99.90         80186         89.90           8251A         4.45         80188         89.90         80186         89.90           2260C2         MHz         2800-S10/2         9.95         280-S10/2         9.95           280-CFU         1.95         280A-S10/2         9.95         280-S10/2         9.95           280-CFU         1.95         280A-S10/2         9.95         280-F10         9.95           280-F00         1.95         280A-S10/2         9.95         280-F10         9.95           280-F10         1.95         6         84         9.95         280-S10/9         9.95           280-F10         8.95         6         MHz         6         8.95         6 <td>CRYSTALS 1.0000 MHz 2.69 8.0000 MHz 1.95 1.8432 MHz 2.69 10.0000 MHz 1.95 2.0000 MHz 1.95 10.7386 MHz 1.95 2.4576 MHz 1.95 12.0000 MHz 1.95 2.4576 MHz 1.95 14.3182 MHz 1.95 3.2786 MHz 1.95 16.0000 MHz 1.95 4.0000 MHz 1.95 16.0000 MHz 1.95 4.0000 MHz 1.95 18.0000 MHz 1.95 5.0000 MHz 1.95 19.6608 MHz 1.95 5.0000 MHz 1.95 19.6608 MHz 1.95 5.0588 MHz 1.95 19.6608 MHz 1.95 5.1850 MHz 1.95 20.0000 MHz 1.95 5.1850 MHz 1.95 22.1184 MHz 1.95 5.7143 MHz 1.95 32.0000 MHz 1.95 5.7143 MHz 1.95</td>	CRYSTALS 1.0000 MHz 2.69 8.0000 MHz 1.95 1.8432 MHz 2.69 10.0000 MHz 1.95 2.0000 MHz 1.95 10.7386 MHz 1.95 2.4576 MHz 1.95 12.0000 MHz 1.95 2.4576 MHz 1.95 14.3182 MHz 1.95 3.2786 MHz 1.95 16.0000 MHz 1.95 4.0000 MHz 1.95 16.0000 MHz 1.95 4.0000 MHz 1.95 18.0000 MHz 1.95 5.0000 MHz 1.95 19.6608 MHz 1.95 5.0000 MHz 1.95 19.6608 MHz 1.95 5.0588 MHz 1.95 19.6608 MHz 1.95 5.1850 MHz 1.95 20.0000 MHz 1.95 5.1850 MHz 1.95 22.1184 MHz 1.95 5.7143 MHz 1.95 32.0000 MHz 1.95 5.7143 MHz 1.95
1702     256 t 8   w      3.95       2708     1024 t 8 (450m)     2.46       2758     1024 t 8 (450m)     2.46       2716     2048 t 8 (450m)     2.46       2716-1     2048 t 8 (450m)     5.90       2716-1     2048 t 8 (450m)     5.90       7182516     2048 t 8 (450m)     5.90       71825232     4006 t 8 (450m)     5.90       7322 A-4     4095 t 8 (450m)     5.91       2732 A-4     4095 t 8 (450m)     5.95       2732 A-2     4096 t 8 (350m)     5.95       2732 A-2     4096 t 8 (350m)     5.95       2732 A-2     4096 t 8 (250m)     5.95       2734 A-2     4096 t 8 (250m)     5.95       2734 A-2     8192 t 8 (450m)     5.95       2764-25     8192 t 8 (450m)     5.95       2764-20     8192 t 8 (450m)     5.97       7122-45     1530 t 8 (250m)     5.97       7122-45     16324 t 8 (250m)     5.97       7122-45     16324 t 8 (250m)     5.97       27122-55     16324 t 8 (250m)     5.97       27122-55     16324 t 8 (250m)<	UV ERASERS QUV-T8/1 \$49.95 ECONOMY Model	280-510/1       8.95       2808-CPU       7.95         280-510/2       8.95       2808-CPU       8.95         280-510/9       8.95       2808-PIO       8.95         280-510/9       8.95       2808-PIO       8.95         280-510/9       8.95       2808-PIO       8.95         280-600-00000000000000000000000000000000	6 0000 MHz 195 36.0000 MHz 195 6.1440 MHz 195 48.0000 MHz 195 6.4000 MHz 195 49.4350 MHz 195 5.5535 MHz 1.95 49.8900 MHz 1.95 32.768 KHz 99 VOLTAGE REGULATORS 7805T 74 7905T 84 78005C 34 7908T 84 78005C 34 7908T 84 78005C 34 7908T 84 7805T 74 712T 84 7815T 74 7912T 84 7815T 74 7924T 84 7815T 74 7924T 84 7815T 74 7912K 144 7815K 134 7915 78 1845 88 79112 78 78115 58 79115 78 78115 58 79115 78 78155 78555 78 78155 7855555555555555555555555555555555



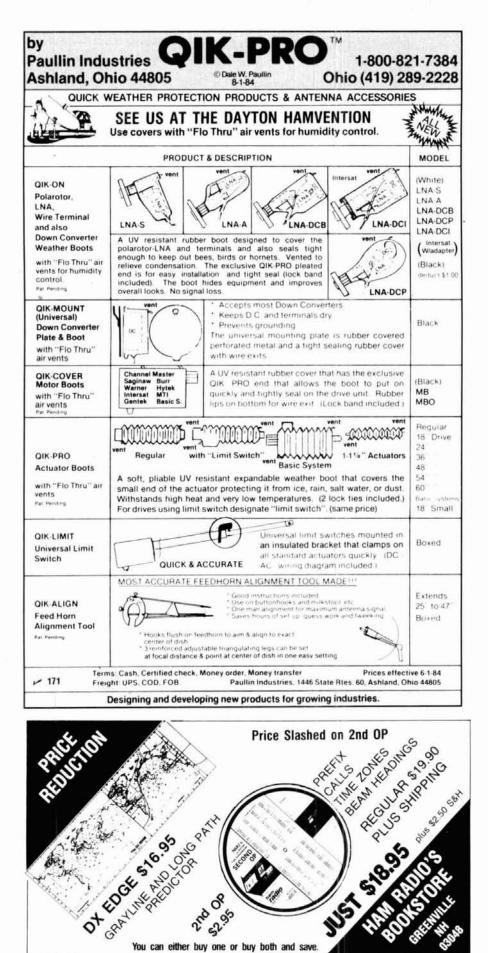



## tilt-over conversion of a fixed antenna tower

### Don't like climbing? Try this.

Since 1973 I have been the proud owner of a selfsupporting triangular steel lattice antenna tower. But because I'm afraid of heights, climbing this tower is out of the question. Changing antennas means engaging helpers, and even then it's not easy because the mast has an additional 10-foot (3 meter) long tube on top, making the rotator and antennas almost inaccessible.

It took a long time before I realized how I could convert my mast to a tilt-over. The 40-foot (12 meter) tower consists of two sections, each 20 feet (6 meters) long. (With the 10-foot, 3 meter tube on top, the total height comes to 50 feet, or 15 meters.) As shown in **fig. 1** the two sections are connected by three flanges with three bolts each; this division appeared to be the logical place for a hinge that would permit the upper section to pivot and be lowered to ground level.

The next problem to be solved was how to effect the tilt-over action by means of a winch and hoist line.

Sketches of the parts constructed by PAØDON are available from the author. Send a large self-addressed envelope; enclose three IRCs.

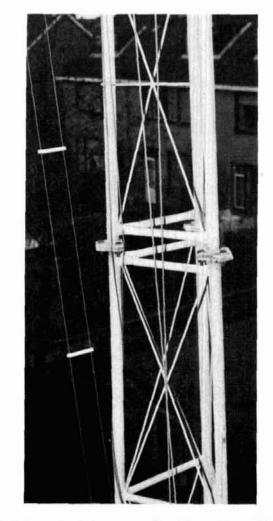


fig. 1. The tower before conversion. Hinge plates will be attached between the flanges connecting the upper and lower part of the tower.

By Dick Rollema, PAØSE, v.d. Marckstraat 5, 2352 RA Leiderdorp, Netherlands

# SPACE/STTI TULSA SHOW '85!




### TULSA CONVENTION CENTER TULSA, OKLAHOMA JUNE 21-22-23, 1985


Join the Thousands of Others Here To See the Fantastic World of Satellite TVRO!



FOR DETAILS: Call STTI at 1-800-654-9276 or (405) 396-2574 or Write STTI, P.O. Box G, Arcadia, OK 73007

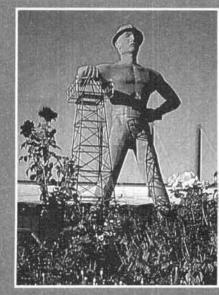- 700 Booths Displaying Latest Equipment for '85!
- 300 Operating Satellite TV Antennas!
- Intensive Seminar Programming!
- Plus Fun for Everyonel




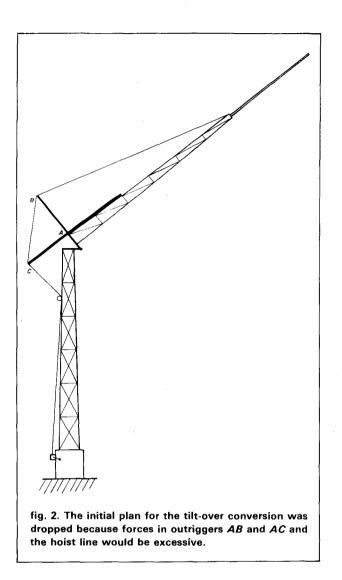

I first thought of using a method such as the one shown in **fig. 2**, similar to the cranes used by building contractors. But with the tower positioned immediately behind our house, outriggers *AB* and *AC* would have to be short enough to clear the structure. This would lead to high tension in the hoist line and cause too much stress on the overall system. So the idea was dropped.

The breakthrough occurred when I visited PAØWCW, who has a similar tower that had been converted into a tilt-over. PAØWCW used two adjacent gin poles permanently fixed to the tower. A pulley is mounted on top of each pole. Two hoist lines in parallel run from the winch over the pulleys to a point halfway up the upper section of the mast.

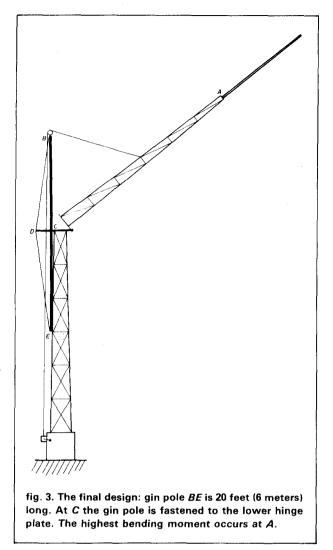My final design is shown in **fig. 3**. Here a single gin pole (*BE*) is fixed to the tower at the lower end *E* and in the middle at *C*. A few calculations showed that bending moment at *C* is so large that no pipe of acceptable size could endure this stress, so two stays designed to bear most of the load were introduced.



These are fastened to the gin pole at both ends and pushed away from the middle of the pole by a triangular outrigger. **Figure 4** shows the finished system.

#### calculation is a must

Before working out a project such as this, it is absolutely essential to determine the forces exerted on the different parts. Calculating stresses in mechanical construction projects is definitely not part of my daily routine, but after consulting some textbooks — and with some professional advice from PA@TO - Imanaged to do the job. It was not very difficult after all. I quickly discovered that the most critical point is at *A* in **fig. 3** where the pipe top mast leaves the tower. The bending moment here should not exceed a certain maximum value set by the resistance moment and the tensile strength of the material.

My starting point is a pipe mast of 2-inch (50.8 mm) inner diameter with a resistance moment of 0.63 inches<sup>3</sup> (10.25 cm<sup>3</sup>) that protrudes 10 feet (3 meters) out from the lattice mast. From a maximum admissible

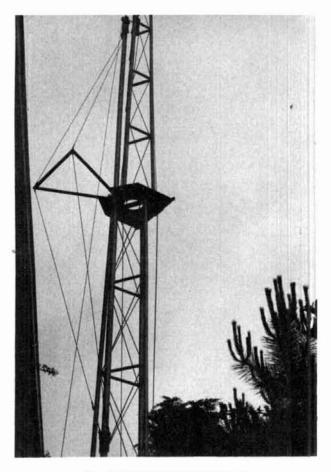


fig. 4. The completed structure.

stress of 23,205 pounds/inch<sup>2</sup> (160 N/mm<sup>2</sup>) it follows that the maximum admissible lateral force at the top of the pipe is 123 pounds (547 N). This is the maximum wind load on antenna plus rotator, if we neglect the wind load on the pipe itself for just a moment.

A second limitation occurs when the mast has been tilted to a horizontal position. Again at *A*, a bending moment occurs as the result of the gravitational force on the top mast, rotator, and antenna. Taking into account the mass of the top mast itself, we find a maximum admissible mass of about 99 pounds (45 kg) for the rotator plus antenna. With these numbers, the forces in the different parts of the system can be computed. Rather than bore you with the results, only the maximum force in the hoist line will be mentioned: almost 1,034 pounds (4,600 N), which represents the static load. During tilting of the tower, shocks can easily occur that considerably increase the force in the line.

#### construction

As already mentioned, a hinge has been installed at the 20-foot (6 meter) level where the lower and upper parts of the tower are joined by flanges. The flanges are bolted to steel plates that carry the hinge at one edge.

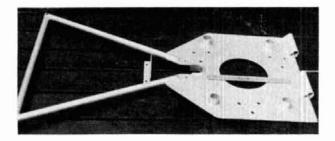


fig. 5. Lower hinge plate, made of 23/64-inch (9-mm) thick steel. The triangular outrigger is fabricated of 1-inch (25 mm) diameter steel tubing. The angle iron bracket secures the gin pole that is held in place in the half circular cutout. The central hole helps reduce the weight (64 pounds/29 kg).

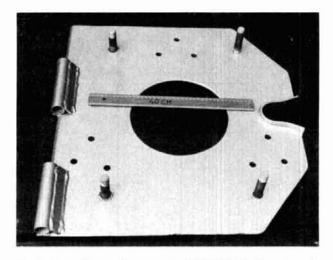


fig. 6. Upper hinge plate, made of 23/64-inch (9-mm) steel. The four bolts, welded on, keep the hinge plates together when the tower is upright. (Weight: 50 pounds/22.5 kg).

Figure 5 shows the lower plate and fig. 6 the upper. The hinge is fabricated from a piece of 2-inch (50.8 mm) steel tube sawed into four parts. These were welded, two by two, to both plates. Extra strength was provided by welding strips of steel to both pipe and plates, as can be seen in fig. 6. The hinge pivots around a 1-inch (25-mm) diameter shaft with bushings at both ends. One is permanently fixed to the shaft; the other is fitted after mounting and secured by a bolt and nut that traverse the shaft and bushing.

In the resting position, the two hinge plates are held together by four 25/32-inch (20-mm) bolts that have been welded to the upper plate and pass through oblong holes in the lower plate. Pieces of tubing are welded around these holes to keep the plates at the proper distance.

Before tilting the tower, the four nuts must be removed from the bolts on the bottom side of the lower plate.

In my original design one plate lay directly on top of the other without any distance in between. To pre-

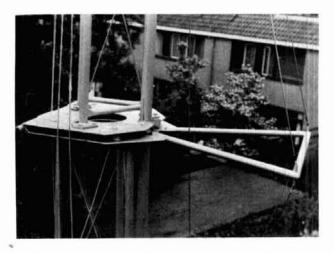


fig. 7. Tower in vertical position. The stainless-steel tubes that guide the stays through the outrigger can be seen at right.

vent the bolt heads in the upper and lower plates from interfering with each other, the upper part of the tower was rotated 60 degrees with respect to the lower part. This allowed the bolt heads of one plate to fall directly into holes drilled in the opposite plate. That 60-degree rotation has been maintained, though it is not necessary in the present construction. But while it presents neither advantage nor disadvantage, it does lead to an optical illusion: from whatever side the tower is viewed, it always seems that the center lines of the upper and lower part do not coincide.

The tower is hinged so that the top mast can be reached from the roof of the barn in the back of our garden, so it is easy to work on rotator or antenna. **Figure 7** shows the tower and hinge in its normal position. **Figure 8** shows it tilted over about 90 degrees.

The gin pole is a seamless steel tube 20 feet (6 meters) long and 2.5 inches (60.3 mm) outer diameter; its inner diameter is 2 inches (53 mm). The lower end is supported by the parts shown in the lower section of **fig. 9. Figure 10** shows the lower end in position on the tower.

The legs of the tower have a wall thickness of only 1/16 inch (1.5 mm). To spread the forces exerted by the U-bolts, my friend PAØDON fitted half-cylinder-shaped shells between the U-bolts and the tower legs. On the angle-iron bracket, a piece of tubing was welded over which the gin pole was placed. After mounting, a hole was drilled for a long bolt that pierces the gin pole and prevents turning.

On top of the gin pole a pulley was mounted by means of the method shown in **figs. 11** and **12**. As shown, precautions have been taken above and behind the pulley to prevent the hoist line from running off. The pulley, made of Novotex,<sup>™</sup> has an outer diameter of 4.7 inches (120 mm). It rotates around a piece of steel tubing of 1.3 inches (32 mm) diameter. The steel strips that hold the pulley on top of the gin

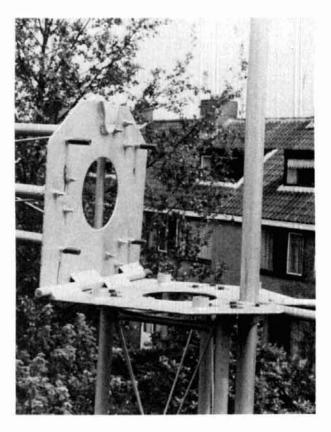


fig. 8. Tower tilted 90 degrees.


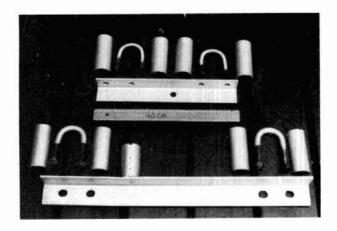


fig. 9. The parts that connect the hoist line to the upper tower section are shown above; the support for the gin pole is shown below.

pole also carry bolts for the stays. At the lower end the stays are connected with stainless steel turnbuckles with a breaking strength of 4,271 pounds (19,000 N). The lower hinge plate carries a triangular outrigger that keeps the stays at the proper distance from the middle of the gin pole (**fig. 7**). To prevent chafing, stainless steel tubes have been inserted in the outrigger that guides the stays. A nylon bushing inside the tubes provides extra protection.

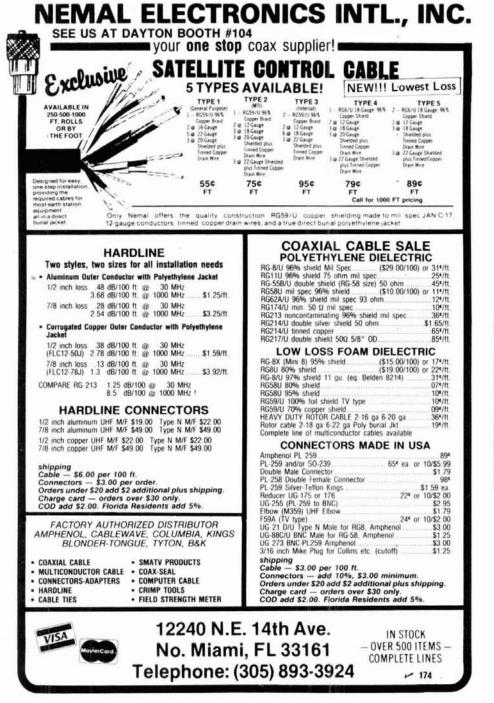Stays and hoist line consist of stranded stainless




## Weighing in at 8 tons, covering 5.9-30

COVER NOTE:

is BIGGER better?

MHz, the Allgon (of Sweden) 128-foot long Model 601 log periodic handles 500,000 watts of RF while providing continuous azimuthal coverage and tilt capability for optimum takeoff angle control.

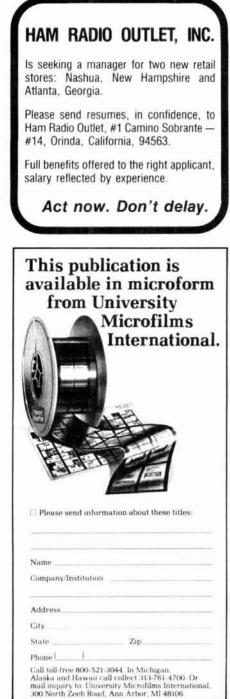Speaking of BIG, this is the largest issue of ham radio ever published. Our thanks to our readers and advertisers for your continued support and encouragement. - Editor



#### SATELLITE HANDBOXKS INTRODUCTION TO SATELLITE TV by Chris Bowick, WD4C and Tim Kearney, NZ40

Forty years ago, the most sophisticated piece of electronics in the average home was an AM radio Today, many homes are set up with state-of-theart receivers designed to pluck signals from satellites orbiting 23,000 miles in space. Instead of getting into a nuts and bolts approach to TVRO. this book gives you a broad overview of TVRO in general with emphasis on home use. Chapter 1 covers TVRO background and gives a generalized explanation of what TVRO is all about. Chapters 2-4 give you a braod overview of the equipment used to transmit and receive TVRO signals. Three appendixes also cover DBS, locating satellites and a glossary of TVRO terms. 1st edition. (© 1983) 142 pages. Softbound \$9.95

Foreign orders shipped FOB Greenville.

#### THE SATELLITE TV HANDBOOK by Anthony T. Easton

Answers virtually any question you might have on satellite TV. This new book gives you a complete overview of the satellite service, how satellites work, what programming is available, who operates the various satellites, networks and stations, how to engineer and install a system, and the legal background of TVRO. For the "homebrewer there is a section on building your own TV dish and receiver for around \$600. You also get a sec tion about the non-television services from satel lites — radio feeds, teletext, newswire and infor-mation on DXing international satellites. © 1983 439 pages First edition

Softbound \$16.95 22055 Please enclose \$3.50 for shipping HAM RADIO'S BOOKSTORE Greenville, NH 03048

130 May 1985

21978

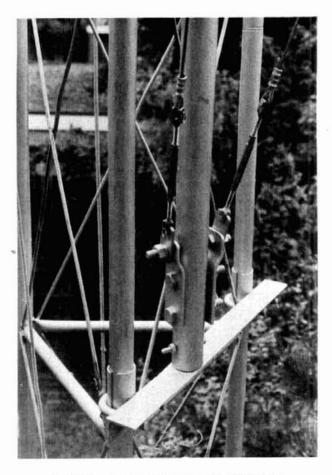


fig. 10. The lower end of gin pole, with stays.

steel cable measuring 0.2 inch (5 mm) in diameter and having a breaking strength of 3,147 pounds (14,000 N). The hoist line ends in a winch with a capacity of 1,200 pounds (5,338 N) and a reduction of 4.1:1. (If I were to build this system again I would select a larger reduction). The tower rests on a concrete block, and the winch is fitted to this block by three "chemical" anchors measuring 0.31 inch (8 mm) (fig. 13). The upper end of the hoist line ends halfway up the top section of the tower. A bracket of angle iron is shown in the upper half of fig. 9. This bracket is mounted to the tower legs with U-bolts, and half-cylinder shells are installed to distribute the pressure more evenly. The hole in the bracket is for a 0.625-inch (16 mm) bolt. (The hoist line is fitted to this bolt with parts purchased at a marine shop; I am, unfortunately, unable to translate their names into English.)

The hinge plates and all parts visible in **figs. 9** and **11** have been treated with zinc epoxy followed by two coats of aluminum paint. The gin pole, galvanized by the manufacturer, was given a coat of rust-preventive primer and two coats of aluminum paint. Although the tower was also galvanized, some traces of rust were visible at the upper end, so the whole thing was also treated with rust-preventer and aluminum paint.

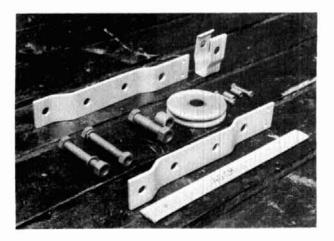


fig. 11. These parts support the pulley on top of the gin pole.

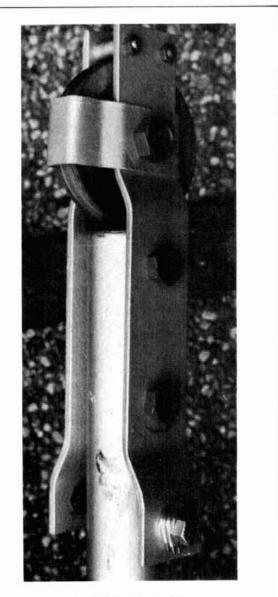


fig. 12. Pulley in position.

### NAMPA SATELLITE SYSTEMS, INC. TWO LOCATIONS



312 12th Ave. So. Nampa, Idaho 83651 (208) 466-6727 1-800-654-0795 6103 W. 34th St. Houston, Texas 77092 (713) 957-5140

For Service ONLY (208) 467-3204

NEW LOW, LOW PRICES! NATIONAL FINANCING AVAILABLE THROUGH NAMPA SATELLITE

MD9 - 9' Dish

FOR MORE INFORMATION CALL 208-466-6727

ALL SYSTEMS FREIGHT PRE-PAID FROM NAMPA, IDAHO OR HOUSTON, TEXAS

EACH OF THE FOLLOWING SYSTEMS CONSIST OF: Receiver, 100° LNA, LNB, or LNC, Wilson MD-9 Dish, 100 Ft. Cable Pack, LNA Cover, Polarmatic I Feedhorn, NSS Dish Drive, All Connectors and Instructions

Wilson YM1000 System \$1648	Uniden UST 3000 System \$1772
10% Down Payment-\$164.80 36 payments of \$54.00/mo.	10% Down Payment-\$177.20 36 payments of \$57.00/mc
Wilson YM400 System \$144.20	Uniden UST 1000 System \$1571
10% Down Payment-\$144.20 36 payments of \$46.00/mo.	10% Down Payment-\$157.10 36 payments of \$52.00/m
Little Wil LW5 \$1099	Sigma Mark 2A \$1438
10% Down Payment-\$109.90 36 payments of \$36.00/mo.	10% Down Payment-\$143.80 36 payments of \$46.00/m
Little Wil RV5 \$1399	Sigma Mark 3 BLOCK DC \$1662
10% Down Payment-\$139.90 36 payments of \$45.00/mo.	10% Down Payment-\$166.20 36 payments of \$54.00/m
Drake 240 A + APS24 \$1995	Sigma Mark 5 вLOCK DC \$2049
10% Down Payment-\$199.50 36 payments of \$65.00/mo.	10% Down Payment-\$204.90 36 payments of \$66.00/m
Luxor Mark 2 System BLOCK DC \$2512	M/A Com HI вLOCK DC \$2282
10% Down Payment-\$251.20 36 payments of \$75.00/mo.	10% Down Payment-\$228.20 36 payments of \$74.00/mc
Dexcel 1300-01 System \$1988	M/A Com TI вLOCK DC \$2182
10% Down Payment-\$198.80 36 payments of \$63.00/mo.	10% Down Payment-\$218.20 36 payments of \$71.00/m
Dexcel 1200-01 System \$1633 10% Down Payment-\$163.30 36 payments of \$54.00/mo.	STS MBS-SR-AA         \$2349           10% Down Payment-\$234.90         36 payments of \$76.00/ms

### **OPTIONS** WITH SYSTEM

PM 9' Dish\$	60
UM 10' Mesh Dish\$	80
Prodelin 10' Dish\$4	400
Continental Mesh Dish 10'\$4	100
85° LNA\$	

NSS Memory Tracker	\$100
MTI 2100	\$225
MTI 4100	\$345
Houston Tracker IV	\$325
Houston Tracker IV +	\$425

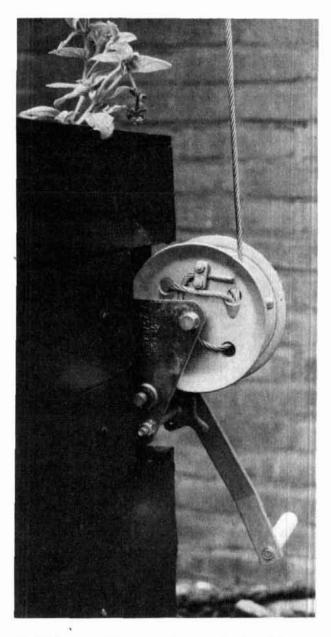


fig. 13. The winch is fastened to the concrete block that serves as base for the tower. Concrete block is concealed under a wooden cover for aesthetic purposes.

#### assembly

The first phase of the operation took place in early December, 1983, when the temperature was just below freezing. Our object was to take down the upper part of the tower, the top tube mast, the rotator, and the 2-meter beam. The gin pole was fitted temporarily to the tower. Because the hinge plates were not yet in place, the gin pole was tied to the upper end of the lower section with rope. The hoist line was also fitted. Using the winch, we gently lowered the upper part of the tower to ground. Now the holes in the flanges could be transferred to a template to be used later in drilling the holes in the hinge plates.



fig. 14. High level work: Jos (PA3ACJ) and SWLs Bert and Ed.

Final assembly and rigging of the tilt-over conversion occurred in mid-May, 1984, under more favorable weather conditions. Everything fit exactly, and it was a real pleasure to see the converted tower come together step by step (fig. 14).

#### acknowledgement

My sincere thanks to Ber van Dongeren, PAØDON, for his superb realization of my design. No operation like this can be performed without helpers: Piet de Bondt, PA3BGP; Jos Disselhorst, PA3ACJ; Ton Verberne, PA2ABV; Ben van Capel, PE1KCG; Gerrit van Zwam, PE1KAX, and SWLs Jo Chin-Chan-Sen, Bert Kraan and Ed Wassenburg helped disassemble the original tower and erect the new one.

#### ham radio

#### Invitation to Authors

*ham radio* welcomes manuscripts from authors all around the world. If you have an idea for an article you'd like to have considered for publication, send for a free copy of the *ham radio* Author's Guide. Address your request to *ham radio*, Greenville, New Hampshire 03048 (SASE appreciated).



#### W2AU and W2DU Baluns

Our baluns, center insulators and insulators have been preferred for 20 years by Hams, industry, and the armed forces. Protect against TVI and lightning 1.8–200 MHz.





#### **W2VS** Antenna Traps

Add these traps to your dipole and get low SWR on 2 to 6 bands, depending on how many you add. Antenna wire and custom kits also available.

#### Send For Yours Today

Don't delay. Call or write today, and we will send you free literature which fully describes our Ham antenna accessory product line.

Dealer inquiries also welcome.

A Division of Microwave Filter Co., Inc.

1	Anter	saories.	Center Anio	101 8	1
	Con	Amunicay	1220	_	/
		1	and a local division of the	-1	
	1	>	~	$\square$	
				-	

Real /

6743 Kinne St., East Syracuse, NY 13057 Toll Free 1-800-448-1666 TWX 710-541-0493 NY/HI/AK/Canada (Collect) 315-437-3953



Dealer Inquiries Invited

✓ 178

# NCG CO. NEW-TECHNOLOGY HIGH-QUALITY

AFFORDABLE TRANSCEIVERS FOR ALL. WINNERS IN COMPARISON HANDS DOWN

40-15-6 M NEW

TRI-BANDER

#### 10/160 M **HF TRANSCEIVER**



4 MEMORYS - 3 WAY AUTO SCAN. DUAL VFO, IF SHIFT, CW-W, 400 Hz CW -N 200 Hz, ALL 9 BANDS PLUS MARS. BUILT IN AC/DC POWER, SSB. CW OR RTTY. I.F. TUNE 3-STEP TUNING SPEED, 200 WATT PEP. MICROPHONE IMPEDANCE 600-50K OHM HAND MIC. INCLUDED.



#### JUST SLIGHTLY AHEAD! WITH THE QUALITY YOU HAVE ALWAYS LOOKED FOR!

40, 15 AND 6 METERS ARE YOUR BASE STATION OR MOBILE WITH AC/DC BUILT IN POWER SUPPLY CW-N 200 Hz OR USB 2 S0239 ANTENNA CON-NECTORS, HAND MIC. BUILT IN TVI. FILTER LITTLE TO NO TV INTER-FERENCE, 20 WATTS PEP, MARS ON 40 AND 6 METERS.

A GREAT ORP RIG WITH THE BIG RIG SIGNAL, 2 WATTS OR 10 WATTS OUT. BUILT IN CW SIDE TONE, DIGITAL DISPLAY, HAND MIC. TOP MOUNTED SPEAKER, MOBILE BRACKET, RIT OR FINE TUNE TX&RX +4KHz, 21 TO 21.450 MHz SIGNAL TO NOISE MORE THAN 10dB DOWN

15 M

**15 METER MOBILE** 

100 00



### SPECIAL

SPECIAL

r 179

#### SPECIAL

90 DAY WARRANTY ON ALL TRANSCEIVERS - DIRECT FROM NCG OR YOUR DEALER WE HAVE 12 GHz BASE/REPEATER & MOBILE ANTENNAS

1275 N. Grove Street, Anaheim, CA 92806 (714) 630-4541



	eneral Tech to Advanced
	> Extra <i>gust memorize the answers to</i> <i>e exam questions</i> .
C. L. PETERS, K	4DNJ, Director iy Amateur Radio Session
Name	Call
Address	

City/State/Zip



NOTE: PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE OR OBLIGATION



#### GO FOX TANGO - TO BE SURE! FOX-TANGO Corp. P.O. Box 15944, Dept. H W. Palm Beach, FL 33416 - 181 Telephone: (305) 683-9587



with dual conversion downconverter

#### FEATURES:

- Infrared remote control tuning
- · AFC, SAW filter
- RF or video output
- · Stereo output
- Polorator controls
- LED channel & tuning indicators

Install six factory assembled circuit boards to complete.

#### SEMIKIT

\$400.00

Completed downconverter add 100.00 Completed receiver and downconverter add 150.00

JAMES WALTER SATELLITE RECEIVER

2697 Nickel, San Pablo, CA 94806 🛩 182 Tel. 415-724-0587



### Join AMSAT...Today

Amateur Radio Satellite OSCAR 10 provides:

• A New Worldwide DX Ham Band open 10 hours a day.

• Rag Chew With Rare DX Stations in an uncrowded, gentlemanly fashion.

• Popular Modes In Use: SSB, CW, RTTY, SSTV, Packet

• Full Operating Privileges open to Technician Class licensee or higher.

Other AMSAT Membership Benefits:

**ORBIT Magazine Subscription:** Dependable technical articles, satellite news, orbital elements, product reviews, DX news, and more.

> Satellite Tracking Software Available for most popular PCs.

QSL Bureau, AMSAT Nets, Area Coordinator Support, Forum Talks

Construction of Future Satellites For Your Enjoyment!

**AMSAT Membership** is \$24 a year, \$26 outside North America. VISA and MC accepted.

AMSAT P.O. Box 27 Washington, DC 20044

301 589-6062

## John J. Meshna Jr., Inc.

Box 62 19 Allerton St. E. Lvnn, Ma. 01904 Tel: (617) 595-2275

Dual 8" F. D. D. Case by SMS w/ POWER ONE Power Supply & Cooling Fans


We were very fortunate to find these beautifully designed & constructed rack mount disc drive cases in the surplus field. These cases were made for Scientific Micro Systems for their FT Series of equipment. They are manufactured from heavy guage steel w/ a cast metal designer bezel. They were designed to house 2 8" floppy or hard drives. We offer you the case with the following components & features: hinged cover with restraining cable for simplified servicing of the interior components, 2 muffin fans for assured cool operation, studs for mounting the controller card listed below, and a heavy duty Power One power supply (their model no. CP 281A). The outputs of the power supply are as follows: +5 vdc 11 amps, +24 vdc 3.5 amps, +12 vdc .25 amps, -12 vdc .25 amps, & -5 vdc .25 amps. The input to the power supply is 115/230 vac 50/60 Hz. and is both filtered and fused. This assembly must have originally sold for well over \$300.00 each ! Only 25 on hand, so order early or be left out on this super bargain ! Shpg. wt. 38 lb. SPL-479-35 \$135.00 each

Scientific Micro Systems IBM 3740 Compatible 8" FDD Controller Card


The SMS FD 0502 8" floppy disc drive controller is a complete preprogrammed controller for single or double density recording on either single or dual headed disc drives. It performs control functions required to transfer data between 1 to 4 drives and a host system, performs all formatting functions required to read and write data and utilizes both IBM single and double density standards to achieve up to 630 Kilobytes of storage per disc surface. Some features are: programmable sector size, 128, 256, 512, or 1024 bytes, jumper selectable drive type, block transfer mode, sector buffer, overlapped head seek, on board General Purpose Host Interface with asynchronous 19 TTL signal lines for eight bit host system and input of only 5 vdc 6 amps. This board provides a direct interface to the following drives: Shugart 800-2/850, Pertec 511, Memorex 550/552, MFE 751B, Qume Data Trak and similiar drives. These boards were removed from the above cabinets which were in service prior to our reception of them. The manufacturers price on these IBM compatible boards is currently \$900.00 each. These boards all appear to be in excellent condition. If more information is needed, please call us. Shpg. wt. 3 lb. SPL 480 \$150.00



SEAGATE TECHNOLOGY ST 506 5¼" HARD DRIVES The Seagate Technology ST 506 hard disc drive utilizes proven Winchester teacnology for reliable storage of up to 5 megabytes of formatted data. Some features of this very popular drive are: 5 megabit/second data transfer rate, simple floppy like interface, high speed band actuator & stepper head positioning, requires only +5 & +12 vdc, and same physical size and mounting paramters as a mini floppy drive. This Shugart compatible drive is the same as used on many home personal computers. Each drive is checked out prior to shipment. Comes with data. Only a few on hand, so order early. Shpg. wt. 81b. ST-506 \$225.00

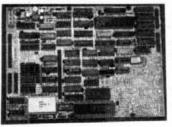

5 ¼" HARD DRIVE CONTROLLER CARD Finally, affordable, intelligent disc drive controllers are available at low, low surplus prices. The OMTI 20C controller boards we offer are unused, late style, surplus from a now defunct system house. OMTI is a division of Scientific Micro Systems. These boards will handle up to (2) 54 inch Winchester type hard drives that utilize a standard 34 pin SASI interface. Perfect for using with the above Seagate ST 506 drive, or other hard drives from 5 megabytes of storage on up. The controllers have buffered slew/seek modes, overlapped seeks, auto seek & verify, extensive fault detection, auto head & cylinder switching, full sector buffering, 256/512 bytes/sector, 33 or 18 sectors/track (jumper selectable), programmable disc parameters and much more. The board runs on +5 vdc & +12 vdc.. We supply users manual & pinout data. Guaranteed O. K.. Shpg. wt. 3 lb. OMTI 20 C \$150.00 each 2/\$275.00 Qty. pricing available.

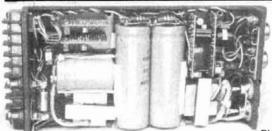

class service to P. O. Box 62 E. Lynn, Ma. 01904.


#### 5 VDC 25 AMP SWITCHING POWER SUPPLY

We just got in a small lot of ruggedly built, lightweight (4 lb.), compact (11" x 5" x 11/2"), fully enclosed (cover removed for pic.), regulated, switching, power supplies made by RO Industries. Input of 115/230 vac is attached thru convenient, clearly marked screw terminals. The hefty 5 vdc 25 amp output is via heavy duty, brass lugs with a Red LED sta tus indicator. All appear to be unused and in excellent condition. Shpg. wt. 6 lb. PS-8 \$50.00

Phone (617) 595-2275 to place your order by phone. Free 72 page catalogue available or send \$1.00 for 1st MC, VISA or American Express charge cards accepted.



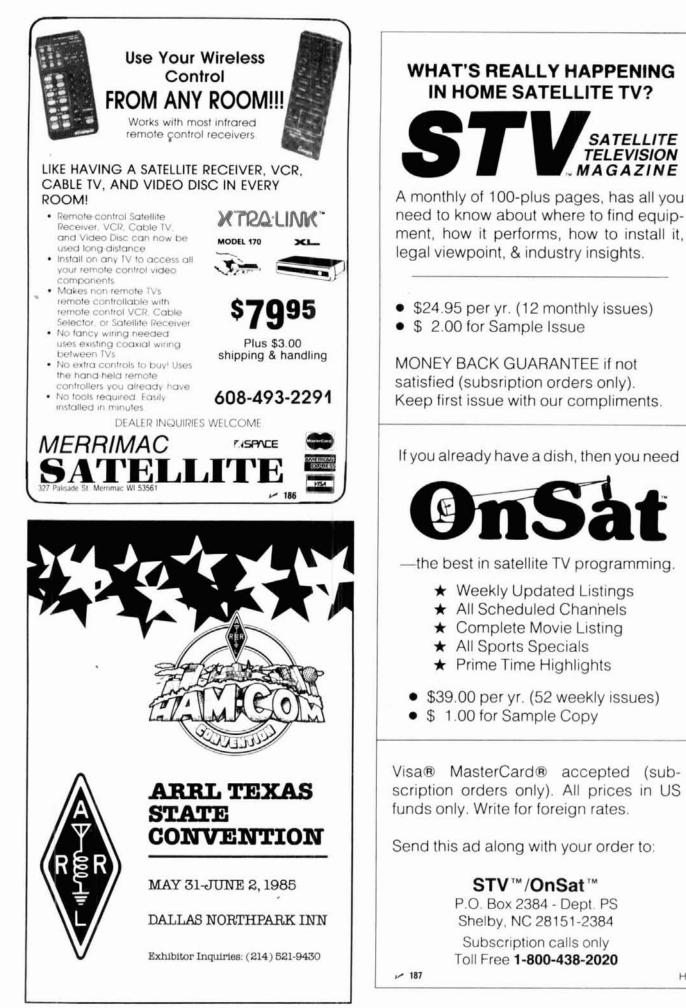Logic bd. not included in price of the case.



HR

### "TUNE IN" THE WORLD OF SPECIALIZED COMMUNICATIONS!

Thousands of "Ham Radio" operators across the country are enjoying "Specialized Communications" modes. Whether it's FSTV, SSTV, FAX, OSCAR, EME, RTTY, PACKET or COMPUTERS, today's Radio Amateur is a highly skilled Communications Specialist!

Providing full, in-depth coverage of these modes is our business and we've been doing it now for over 19 years! And now we're expanding!

Iowa Residents Must Add 4% Sales Tax. 4% Added To All Charge Card Orders.



Now published "monthly" 10 times per year, SPEC-COMTN readers are kept up-to-date in a world of fast moving modern technology.

Why not give us a try? Back issue samples are available for just \$2.00 ppd. (Master Article Indexes add \$1.00).

Special Six Month Trial Subscription -\$10.00. U.S./Canada/Mexico Annual Subscription \$20.00. (Foreign Subscriptions slightly higher).

### SPEC-COM"

Amateur Radio Specialized Communication Journal P.O. Box H Lowden, Iowa 52255 (319) 944-7669 (Membership Services)

188

SEMICONDUCTORS: P.C. BOARDS FOR MOTOROLA BULLETINS MRE-208 MHW-252 53.00 AN-762 12 00 14.00 MHW-710-1......61.00 10.00 FB-27A AN-791.... MRE-240 18 40 14.00 MPSH-81 .. 14.00 **MRF-247** 34.80 50 FR-63 14.00 EB-67 KEMET CHIP CAPACITORS: 56 pf. 82 pf. **MRF-309** 33.80 MV2205 58 **MRF-422** 41.40 78L08CP 50 100 pt, 390 pt, 470 pt 50 ea. MRF-454 2N4401..... 75 680 pl, 1000 pf .... 55 ea. MRE-901 1.75 2N5190 1.50 5600 pt, 6800 pt, .1 µt..... CAMBION RF CHOKES: .15 µh, .22 µh, .33 µh, 4.7 µh, 10 µh. ...1.20 ea. BROADBAND TRANSFORMERS PER MOTOROLA BULLETINS: AN-762, EB-27A, EB-63 UNDERWOOD/SEMCO METAL-CLAD MICA CAPACITORS: 5pf, 10pf, 15pf, 25pf, 30pf.

UNDERWOOD/SEMCO METAL-CLAD MICA CAPACITORS: 5pf, 10pf, 15pf, 25pf, 30pf, 40pf, 56pf, 60pf, 68pf, 80pf, 91pf, 100pf, 200pf, 250pf, 390pf, 470pf, 1000pf We, also carry a line of VHF, UHF amplifiers and ATV equipment. Call or write for our free catalog.




VISA Concepts Inc. 2648 North Aragon Ave. • Dayton, Ohio 45420 • (513) 296-1411 WHERE'S THE TURKEY? \* Synthesized Voice \* No Receiver Mods Doppler Direction Finding \* Mobile or Fixed ★ 12 VDC Operation \* VHF and UHF Coverage \* Digital and **Circular Display** ★ RS232C Computer \* 90 Day Warranty Interface

New Technology (patent pending) converts any VHF or UHF FM receiver into an advanced Doppler shift radio direction finder. Simply plug into receiver's antenna and external speaker jacks. Uses four omnidirectional antennas. Low noise, high sensitivity for weak signal detection. Call or write for full details and prices.

DOPPLER SYSTEMS, INC. 5540 E. Charter Oak, Scottsdale, AZ 85254 (602) 998-1151

## 1985 CALLBOOKS

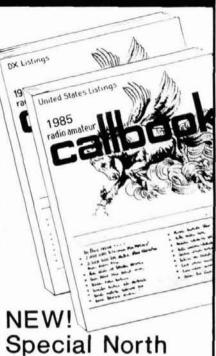

Special North American Edition As an added bonus, the 1985 U.S. Callbook

You get the complete and accurate U.S. listings (prepared by our own editorial staff), all the usual up-to-date Calibook charts and tables, PLUS Canada and Mexico. Now that's real value!

#### The best just got better!


Of course, Canadian and Mexican amateurs are also listed in the 1985 Foreign Callbook, Don't delay! The great new 1985 Callbooks were published December 1, 1984.

#### Order your copies now!

	Each	Shipping	Total
U.S. Callbook	\$21.95	\$3.05	\$25.00
D Foreign Callbook	20.95	3.05	24.00
Order both books \$45.00 including sh			

Order from your dealer or directly from the publisher. Foreign residents add \$4.55 for shipping, Illinois residents add 6% sales tax.

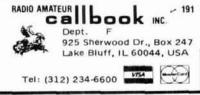Keep your 1985 Callbooks up to date. The U.S. and Foreign Supplements contain all activity for the previous three months including new licenses. Available from the publisher in sets of three (March 1, June 1, and September 1) for only \$15.00 per set including shipping. Specify U.S. or Foreign Supplements when ordering. Illinois residents add 6% sales tax. Offer void after November 1, 1985.





RATES Noncommercial ads 10¢ per word; commercial ads 60¢ per word **both payable in advance**. No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing) on a space available basis only. Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed (**not** all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N. H. 03048.

FOR SALE: Ham station, Swan 350-C, power supply-speaker, Heath Watt-SWR meter, Heath electronic keyer, Ham-M meter and rotator, 40 ft. steel tower and 3 element beam. Best offer. Write Ms. Virginia Ingham, 2636 Forest Park Blvd., Ft. Worth, TX 76110.

#### CX7 REPAIRS. 414-549-9210.

LETTERING and text for QSL pasteup and label usage. Stamp brings circular. Labelcraft, PO Box 412, W. Sand Lake, NY 12196.

CABLE TV EQUIPMENT. Jerrold, Hamlin, Zenith, many others. Factory units/lowest dealer prices. Complete illustrated catalog \$2.00. Pacific Cable Co., Inc., 7325½ Reseda Blvd., Dept. 1001, Reseda, CA 91335. (818) 346-5071.

ELECTRONIC CMOS keyer kit pcb & parts only \$9.95 plus \$1.50 shipping. WI res, add 5% tax. Send for free information. Bel-Tek, PO Box 125H, Beloit, WI 53511.

CUSTOM MADE embroidered patches. Any size, shape, colors. Five patch minimum. Free sample, prices and ordering information. Hein Specialties, Inc., Dept. 301, 4202 N. Drake, Chicago, IL 60618.

#### Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria Karın Ueber Postfach 2454 D-7850 Loerrach West Germany Ham Radio Belgium

Stereohouse Brusselsesteenweg 416 B-9218 Gent Belgium

Ham Radio Holland Postbus 413 NL-7800 Ar Emmen Holland

Ham Radio Europe Box 2084 S-194 02 Upplands Vasby Sweden

Ham Radio France SM Electronic 20 bis, Ave des Clarions F-89000 Auxerre France

Ham Radio Germany Karin Ueber Postlach 2454 D-7650 Loerrach West Germany Canada Send orders to Ham Radio Magazine Ham Radio Mag3048 USA Prices in Canadian funds 1 yr. \$29 95, 2 yrs. \$53 30 3 yrs. \$75.40 Ham Radio Italy Via Pordenone 17 I-20132 Milano Italy

naiy Ham Radio Switzerland Karin Ueber Postlach 2454 D-7850 Loerrach West Germany

Ham Radio England c/o R.S.G.B. Alma House Cranborne Road Potters Bar Herts EN6 3JW England

Holland Radio 143 Greenway Greenside, Johannesburg Republic of South Africa AWARDS DIRECTORY \$1.00 brings information. Refundable. Updated monthly. Computerized. Worldwide. List your awards free. Over 1000 now in files. KBØZP. RR#1B. Cumming, IA 50061.

EQUIPMENT SALE. HAL DS2000 KSR RTTY/CW keyboard \$100. Panasonic 9" monitor \$80. Collins SM280 microphone \$60. Six good used 4-400A's \$20. each. TR3/AC3/MS4 \$120. 1.6 kHz S-Line filter \$40, 4-1000A and parts for amp. Mike Paimer, K5FZ, 16707 Creeksouth, Houston, Texas 77068. (713) 444-7737.

CUSTOM EMBROIDERED Emblems -- Cloisonne' enameled pins, your design, low minimum, excellent quality, free booklet. A.T. Patch Co., Dept. 65, Littlev.NH 03561. (603) 444-3423.

TI 99/4A random, text, keyboard, send, receive code practice programs. Dr. Code "General" sends International Morse code and prints on screen; you choose: speed, tone, which characters to be send, spacing, and more! Dr. Code "Speech" same as "General" with speech; you choose how many characters before speech check. For cassette of both copyrighted programs and conditional copying privileges, send \$10.00 plus \$3.00 shipping and handling to NSESF, Rt. 1, Box 1326, Lake Charles, LA 70601. Phone (318) 436-2048, no collect calls please. Satisfaction or money back.

OST Magazines. 271 of them about 200 lbs. 1930, 1933 through 1940 solid, 1952 through 1965 solid. Best offer for the whole works only. W2LTJ.

FREE CATALOG of books for electronics professionals and hobbyists. Send SASE to Technical Advice, P.O. Box 4757, Englewood, Colorado 80155.

NEW low frequency products by K1RGO. L-101 VLF converter (2 kHz to 500 kHz), AM broadcast rejection 100 dB, i-f rejection 130 dB. L-201 VLF fixed tuned preamplifier (2 kHz to 500 kHz), 25 dB gain (adjustable). Free brochure. LF Engineering Co., 17 Jaffry Rd., East Haven, CT 06512.

RUBBER STAMPS: 3 lines \$4.50 PPD. Send check or MO to G.L. Pierce, 5521 Birkdale Way, San Diego, CA 92117. SASE brings information.

CHASSIS and cabinet kits. SASE K3IWK

IMRA, International Mission Radio Association, helps missionaries. Equipment Ioaned. Weekday net, 14.280 MHz, 2-3 PM Eastern. Eight hundred Amateurs in 40 countries. Brother Frey. 1 Pryer Manor Road, Larchmont, NY 10538.

WANTED: Old microphones, remote mixers other misc related items. All pre-1935. Box Paquette, 107 E. National Avenue, Milwaukee, WI 53204.

ELECTRON TUBES: Receiving, transmitting, microwave . . . all types available. Large stock. Next day delivery, most cases. Daily Electronics, PO Box 5029, Compton, CA 09224 (213) 774-1255.

RTTY-EXCLUSIVELY for the Amateur Teleprinter. One year \$7.00. Beginners RTTY Handbook \$8.00 includes journal index. P.O. Box RY, Cardiff, CA 92007.

TENNATEST — Antenna noise bridge — oul-performs others, accurate, costs less, satisfaction guaranteed, \$41.00. Send stamp for details. W8UUR, 1025 Wildwood Road, Quincy, MI 49062.

### 

"Places to go..."

INDIANA: Hamfest and Computer Show, Sunday, June 9. Sponsored by the Muncie Area Amateur Radio Club. 8 AM to 3 PM. Rain or Shine. Delaware County Fairgrounds. Tickets \$2.00 advance, \$3.00 at door. Large Flea Market. Overnight camping on grounds. Hookups \$5.00. Talk in on 146.13/.73. For tickets, table reservations or information: SASE to MAARC, PO Box 2102, Muncie, IN 47302.

OHIO: The Athens County Amateur Radio Association's sixth annual Hamfest and Computerfest. Sunday, May 19, City Recreation Center, East State Street, Athens. 8 AM to 3 PM. Admission \$3.00. Free paved outdoor tailgating or bring your own tables. Indoor space by advanced registration only. Contact Joe Follrod, NEBR, 15 Roy Avenue, The Plains. OH 45780. (614) 797-4874. This year there will be all level license exams. Mail completed FCC Form 610 and \$4.00 check payable to ARRL/VEC to John Cornwell, NC8V, exam coordinator, 101 Covenity Lane, Athens, OH 45701. Forms must be received by April 19. Talk in on club repeater 146.34/.94. For information: Carl J. Denbow, KA8JXG, Chairman, ACARA Hamfest Committee, 63 Morris Ave., Athens, Ohio 45701.

LOUISIANA: The Central Louisiana ARC (CLARC) will sponsor a Hamfest, Saturday and Sunday, June 8 and 9, Botton Avenue Community Center, 315 Botton Avenue, Alexandria. Free admission. Swap tables available. VEC exams. Talk in 0147.93/330 r146.04/64. For more information: CLARC, PO Box 7772, Alexandria, LA 71306.

GEORGIA: The John Ross Amateur Radio Club's annual Hamfest, June 8 and 9. New location — Lakeview — Ft. Oglethorpe High School, Ft. Oglethorpe on Hwy. 2A. Air conditioned dealer spaces. Indoor/outdoor flea market. Tables available. FCC exams both days. Refreshments and plenty of free parking. Talk in on 145.35/down. For reservations and information: JRARC, PO Box 853, Rossville, GA 30741. (404) 861-5610.

MICHIGAN: The Chelsea Swap and Shop, Sunday, June 2, Chelsea Fairgrounds. Gates open for sellers at 5 AM. General public 8 AM to 2 PM. Donation \$2.50 advance or \$3.00 at gate. Children under 12 and non ham spouses admitted free. Talk in on 146.520 simplex and 147.255 Chelsea repeater. For information: William Altenberndt, 3132 Timberline, Jackson. MI 49201.

MINNESOTA: The North Area Repeater Association will sponsor the state's largest swapfest and exposition, Saturday, June 1, Minnesota State Fairgrounds in St. Paul. Free overnight parking for self-contained campers May 31. Exhibits, dealers, giant flea market. Amateur license exams given. Admission \$4 in advance, \$5 at Fair. Talk in on 25/85 or 16776 repeaters. For tickets, information: Amateur Fair, PO Box 857, Hopkins, MN 55343. (612) 566-4000.

MARYLAND: The Maryland FM Association's annual Hamfest, Sunday, May 26, Howard County Fairgounds, West Friendship, I-70, 30 miles west of Baltimore. Gate opens 8 AM to 4 PM. Inside tables by advance registration \$6.00. At the door \$10.00 if available. Donation \$3.00. Talk in on 146.16/76, 222.16/223.76, 449.1/444.1. For tables or information: Craig Rockenbauch, WA3TID, 429 Severnside Drive, Severna Park, MD 21146. (301) 987-6042 (6-10 PM).

GEORGIA: The Anderson, Hartwell and Toccoa Amateur Radio Clubs will hold the 6th annual Lake Hartwell Hamfest, May 18 and 19, Lake Hartwell Group Camp, Highway 29, Hartwell. Free admission, free camping, and free flea market space. Left footed CW contest, horseshoes, fishing, swimming and camping available on site. Campgrounds open 6 PM Friday. Talk in on 146.19/.79, 147.93/.33 and 146.895/.295. For further information: Ray Pettit, WB4ZLG, Rt. #1, Dooley Drive, Toccoa, GA 30577.

MARYLAND: The Frederick Amateur Radio Club's 8th annual Hamfest, June 16, Frederick Fairgrounds. Admission \$3.00. YL's and children free. 8 AM to 4 PM. Tailgaters \$2.00 extra. Gates open for exhibitors 8 PM June 15. Overnight parking welcomed. Tables \$10.00 first, \$5.00 each extra. For information: Jim Kasunic, KA3LPC, 9419 Highlander Ct., Walkersville, MD 21793.

ILLINOIS: The Chicago Amateur Radio Club (CARC) is sponsoring a Mini Hamfest, Wednesday, May 15, 6 to 10 PM, Edgebrook Golf Course Fieldhouse, 5900 N. Central Avenue, Chicago. (North of Elston Avenue, south of Devon Avenue). For more information: (312) 545-3622.

NEW HAMPSHIRE: The 11th annual Eastern VHF/UHF Conference, May 17-19, Rivier College, Nashua. Friday night hospitality room. Saturday tech talks by well-known VHFers. Pre-registration \$13.50 to David Knight, KA1DT, 15 Oakdale Avenue, Nashua, NH 03062 before May 5. Registration at the door \$20.00. Saturday night banquet \$14.00 payable before May 5. Dormatory housing available, \$16.50 per night single, \$28.00 per night double, includes buffet breakfast. Include payment at time of pre-registration. Make checks payable to Eastern VHF/UHF Conference. There are also numerous hotels and motels nearby. For information: Lewis D. Collins, W1GXT, 10 Marshall Terrace, Wayland, MA 01778. (617) 358-2854 (6-10 PM).

OHIO: The 5th annual Columbus Hamfest sponsored by the Battelle Amateur Radio Club, Sunday, June 2, 8 AM to 3 PM. Ganyard Building on Franklin County Fairgrounds. Admission \$2 advance and \$3 at the door. Advance tables \$3; at the door \$4. Talk in on 146.37/97. For information Bill, W8LLU (614) 261-7053 or Kevin, WA8OHI (614) 766-5313. Advance sales SASE to Bill Welch, W8LLU, 396 Brevoort Rd., Columbus, Ohio 43214.

OHIO: The Sandusky-Ottaway Counties annual Hamfest, May 19, 8 AM to 3 PM. Ottawa County Fairgrounds, St. Rt. 163 east of Oak Harbor. Donation \$3.00 at gate; \$2.50 advance. Tables \$3.00. Gate opens 6 AM for dealers and 8 AM for general public. Trunk sale (donation 50¢), plenty of parking, food and refreshments. To reserve tables: Raymond Kruse, KalDA, 18980 W. S.R. 51, Elmore, Ohio 43416. (419) 862-2619 (8 AM - 5 PM).

PENNSYLVANIA: The Warmister ARC Hamfest, May 19, Middletown Grange Fairgrounds, Penns Park Rd., Wrightstown (about 15 miles north of Phila.) Admission \$3.00. XYLs and children free. Indoor space with table and elec \$5.00. Tailgating space \$5.00. Gates open 7 AM. Talk in on 147.69/09 and 147.52. Computer hardware/software vendors welcome. For information: Bill Cusick, W3GJC, Apt. 706, Garner House, Hatboro, PA 19040. (215) 441-8048.

NEW YORK — Long Island: The Suffolk County Radio Club's Indoor/Outdoor Electronic Flea Market, Sunday, May 5, 8 AM to 3 PM, Republic Lodge No. 1987. 585 Broadhollow Road (Rt. 110) Melville. Refreshments and plenty of free parking. General admission \$2.00. Wives and children under 12 free. Indoor seller's tables \$7.00. Outdoor space \$5.00 includes one free admission. Talk in on 144.61/145.21 and 146.52. For information: Richard Tygar, AC2P. (516) 643-5956 evenings.

NEVADA: The 10th International Convention of the YLRL will be held June 20, 21, 22 and 23 at the Sahara Hotel, Las Vegas. Deluxe accommodations and RV parking available at reasonable rates. Activities include a Hoover Dam tour, Lake Mead cruise, desert tour, gala stage show, cocktail party, luncheon buffet and awards banquet plus a DX YL show, slide shows and business meetings. A convention station will operate on 14,288 kHz and other frequencies. Registration forms are to be found in recent issues of YLRL's "Harmonics". For information packet send business SASE with 2 oz. of postage to Jan Weaver, NYYL, 2195 East Camero Avenue, Las Vegas, NV 89123.

NEW JERSEY: The Tri-County Radio Association's Hamfest, Sunday, May 19, rain or shine, Passaic Valley Community Center off Valley Road, Stirling. 9 AM to 4 PM. Indoors, free parking, refreshments. Tables \$10. Registration \$2.50. Reserved tailgating only. All reservations to: Dick Franklin, W2EUF, PO Box 182, Westfield, NJ 07090. (210) 232-5955 or 270-3193.

SOUTH DAKOTA: The Black Hills Amateur Club is celebrating its 50th anniversary by sponsoring the 1985 ARRL Dakota Divsion Convention, July 5, 6, 7, Howard Johnson's (1-90, exit 59) Rapid City. Registration Friday from 4 to 7:30 PM followed by a social hour. Saturday exhibits, registration, indoor flea market (free tables while they last) ladies' activities and fun for the whole family. VE exams (limited walk-ins) 1 PM. Banquet at 7 PM. Sunday brunch at 8:30 followed by the ARRL forum. Exhibits will be open. Pre-registration & banquet \$18.00. Pre-registration only \$6.50. Must be made prior to 6/10/85. Additional banquet tickets \$12.50. Sunday brunch 6.75, children 12 and under \$3.75. Registration after 6/10/86, \$7.50. Make check payable to Black Hills ARC, c/o Gene F. Bauer, KX@U, 713 Blaine Avenue, Rapid City, SD 57701. Confirmation by return mail.

WISCONSIN: The Central Wisconsin Radio Amateur's annual Swapfest/Family Picnic, June 16, Bukolt Park, Stevens Point. Swapfest will feature volunteer exams (by advanced registration only), dealers, food, refreshments and fellowship. Tables and tailgating \$2.00. Talk in on 146.07/67 and .385/985. For further information: Jim Benak, KA9ACE, 1775 Strongs Avenue, Stevens Point, WI 54481. To register for exams (by May 16): Gene Santoski, K9UTQ, 1220 – 18th Street South, Wisconsin Rapids, WI 54494.

KENTUCKY: The Armored Force Amateur Radio Nationwide Emergency Team (A FAR NET) will hold an Eyeball Bivouac, June 7 - 9, at the Best Western Gold Vault Inn in Badcliff, just outside Fort Knox. Campers will use the Fort Knox campground at Camp Carlson. On Friday, June 7, there will be an informal picnic. Saturday, the group will take a guided bus tour of Fort Knox ending at the Patton Museum. Saturday evening's cocktail party is followed by dinner at 8 PM. There will be a farewell breakfast Sunday morning. For additional information contact Carl Quickmire, WB4UBS, 6341 Cloverdale Drive, Columbia, SC 29209. Any Amateur Radio operator who has ever served with or been assigned to an armored unit of the U.S. armed forces or its allies is eligible for membership in A FAR NET. Family members holding an Amatuer license are eligible for associate memberships. Anyone interested in joining this unique organization can obtain infor-mation and an application from Harry B. Thomsen, W2PJH, 348 Jefferson Avenue, Apt. 15, Canandaigua, NY 11424. Please include business SASE.

PENNSYLVANIA: The 31st annual Breeze Shooters Hamfest, Sunday, June 2, 9 AM to 5 PM, White Swan Amusement Park, Rt. 60 near Greater Pittsburgh International Airport. Free admission and flea market. Family amusement park. Registration \$2.00, 3 for \$5.00 or 7 for \$10.00. Vendors tables by advance registration. Talk in on 146.28/.88 or 29.000 MHz. For information: John Colbert, K3SDL, 1831 Highland Ave., Irwin, PA 15642. (412) 863-5167 evenings only. **COLORADO:** The Longmont Amateur Radio Club's annual Boulder Spring Hamfest, Sunday, May 5, 9 AM to 2 PM rain or shine, Colorado National Guard Armory, 4750 North Broadway, Boulder. Donation \$3 per family. No sellers charge but bring own tables ... Hamswap, plus tech demonstrations and seminars. Food and drink available. Talk in on 146 16/76 and 146 52. For information: William Currie, WDØEHJ, 1232 East Fourth Ave., Longmont, CO 80501. (303) 776-2829.

NEW YORK: Long Island Hamfair sponsored by LIMARC, Sunday, June 9. 9 AM to 4 PM, Electricians Hall, 41 Pinelawn Road, Melville, Long Island. General admission \$3.00 \$2.00 after 1 PM Table space in advance from Hank Wener, WB2ALW, 53 Sherrard St., East Hills, NY 11577-1712. 4 × 6' table space \$10.00 or your own for \$6.00. Contact Hank at (516) 484-4322 evenings to 11:30 PM.

INDIANA: The 39th Annual Hamfest sponsored by the Wabash Valley ARA, Sunday, June 2, Vigo County Fairgrounds, Terre Haute. For information SASE to WVARA, PO Box 81, Terre Haute, In 47808.

CONNECTICUT: Flea Market, sponsored by the Newington Amateur Radio League, June 9, Newington High School, 9 AM to 2 PM. Admission \$2.00. Tailgating \$5.00. Talk in on 146.52 or W1AW/R 145.450, 224.840.

NEW YORK: The Rome Radio Club's 33rd annual Ham Family Day, Sunday, June 2, Beck's Grove in Rome. Games, contests and large Flea Market. Good food and beverages available throughout the day. Educational and scientific presentations. The day will end with dinner and the presentation of "Ham of the Year Award". For further information. Rome Radio Club. PO Box 721. Rome. NY 13440.

NEW YORK: The 26th annual Southern Tier Amateur Radio club's Hamtest, Saturday, May 4, Treadway Inn, Owego. Flea market opens 8 AM. Vendor displays and sales. Dinner at 6:30 PM by advance tickets only. Talk in on 22/82, 16/76 and 146.52. For further information SASE to KF2X, RD #1. Box 144, Vestal, NY 13850.

NEW YORK: The Antique Radio Club of America will hold an international convention at Niagara Falls, June 5-8. The club has 1000 members who collect and restore antique wireless and radio equipment and who study and record the history of early radio. For information on the convention or membership in ARCA please write NFWA, PO Box 68, Central Park Station, Buffalo, NY 14215.

WASHINGTON: The Yakima Amateur Radio Club will hold the Central Washington State Hamlest, May 18 and 19, Hobby Building at Central Washington State Fairgrounds, Yakima. Saturday 9 to 5 with lunch available. Sunday 7 to 2 with breakfast and lunch available. Registration \$4.00 advance, \$5.00 at the door. Free swap and shop with plenty of tables. Talk in on 146.01/61 and 146.34/94. For pre-registration contact Tom Plaisance, PO Box 9211, Yakima, WA 98909.

#### OPERATING EVENTS "Things to do..."

MAY 5 AND 5: The Mason County ARC will operate commemorative stations KB7MJ and W7KTI on SSB, KN7D RTTY and K7UAR on Packet to celebrate the Shelton, Washington, Centennial. Certificates will be exchanged for a QSL card and 9 x 12 SASE. Send to Loren Mercer, KA7GSV, 2213 Olympic Hwy. North, Shelton, WA 98584.

JUNE 2: SRRC Hamfest, Princeton, Illinois. Plans include FCC/VEC exams. Registrations \$2.50 before May 20. \$3.00 June 2: For advance registrations and/or complete information, furnish a long SASE to Starved Rock Radio Club, W9MKS, RFD #1, Box 171, Oglesby, Illinois 61348. (815) 667-4614.

JUNE 1 AND 2: The Southside Amateur Radio Club will operate station NØEWP in honor of President Harry Truman's 101st birthday. The station will operate near the old Truman farm home in Grandview, MO during the annual "Harry's Heydays" celebration. For a commemorative certificate send 9 × 12 SASE with 33¢ postage to Southside ARC, PO Box 412, Grandview, MO 64030.

MAY 4: The Sand Hills Amateur Radio Club will operate KZØM during a DXpedition to Moscow, KS to commemorate May Day. For a special QSL SASE via Box 88, Moscow, KS 67952.

MAY 25: The Bay Area Amateur Radio Society, Pasadena, Maryland, will operate KM3I and KA3HKB to commemorate "Samuel F.B. Morse Day". For a special certificate send QSL and large SASE to B.A.A.R.S., PO Box 805, Pasadena, MD 21122-0805.

CO CONTEST: VHF'ers please note! The first annual CO World Wide VHF WPX Contest is July 20-22, 50 thru 1296 MHz. For details, logsheets, etc., write to SCORE, PO Box 1161, Denville, NJ 07834 or to CQ Magazine. We need your entry to make this a success.


MAY 18: ARRL/VEC License Exam at 9 AM, United Community Services Building (Red Cross), 39 North Park Street, Mansfield, Ohio. Send SASE, 610 and check for \$4 payable to ARRL/VEC to Peggy Boyle, KC8NH, 1464 Marion Avenue Road, Mansfield, Ohio 44906.

MAY 18 AND 19: The Amateurs of Lima and Allen County, Ohio will commemorate the discovery of oil in Lima. Stations participating will sign /OIL and operate in the Novice, Technician or General portions of the bands. For a certificate SASE to Northwest Ohio ARC, PO Box 211, Lima, Ohio 45801.

JUNE 1: The Wireless Institute of Northern Ohio (W.I.N.O.) will be operating a special event station from an actual winery in Madison, Ohio to commemorate Ohio Wine Month. Listen for KO8O Saturday evening 7 and 11 PM EDST and Sunday 11 AM to 3 PM EDST. A special 8½ × 11 QSL certificate will be available from KO8O — WINO Weekend, 7126 Andover Drive, Mentor, Ohio 44060.

JUNE 8: Tri-City ARC will operate W7VPA from Ice Harbor Dam the highest lift navigable locks in the United States. Operation will be from 1700 to 2400Z. For a special QSL SASE to W7VPA, PO Box 73, Richland, WA 99352.

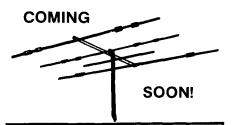MAY 10: The Owensboro ARC will operate K4HY from 0000Z to 0530Z May 11 to celebrate their International BBQ Festival. Certificate for SASE via N4EKG, 1615 East 23rd Street, Owensboro, KY 42301.



#### THE ARRL ANTENNA COMPENDIUM

This *new* League publication will consist of over 20 antenna articles never published before. Availability will be in late May — just in time for your warmweather antenna work! Watch *QST* for details.


Other books on antennas available from ARRL:

The ARRL Antenna Book 14th Edition, copyright 1982. 328 pages of comprehensive antenna, propagation and transmission line fundamentals. \$8.00 U.S., \$8.50 elsewhere. Cloth edition \$12.50 HF Antennas for All Locations, copyright 1982. From RSGB, 264 pages. \$12.00 Antenna Anthology The best hf antenna articles taken from QST. Copyright 1978, 148 pages. \$4.00 U.S., \$4.50 elsewhere.

#### THE AMERICAN RADIO RELAY LEAGUE 225 MAIN ST. <u>N</u>EWINGTON, CT 06111

✓ 240



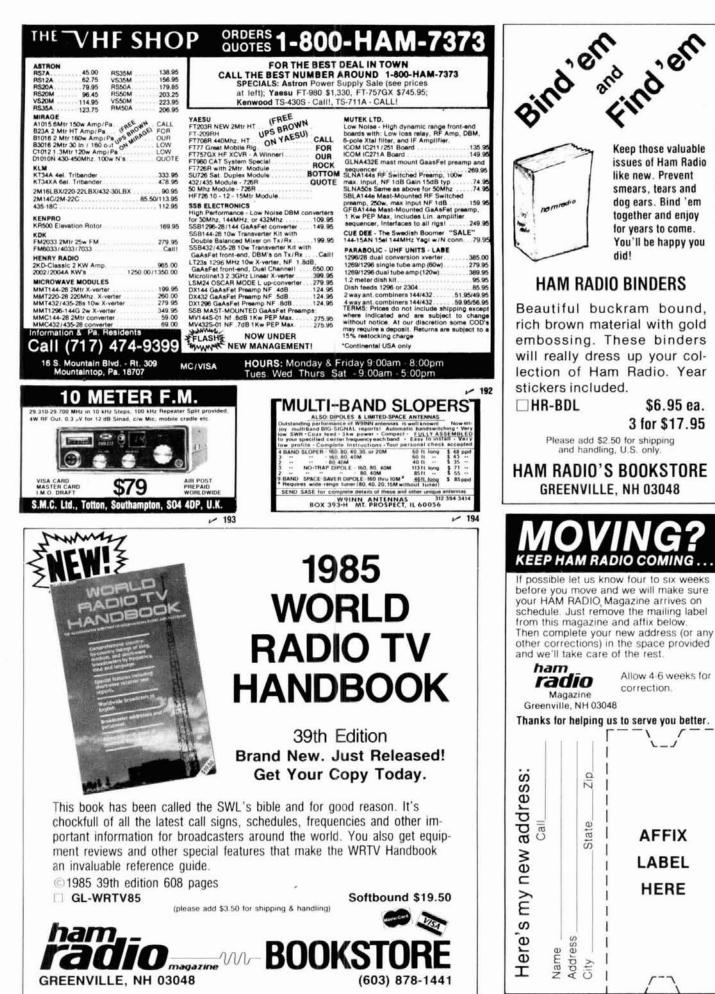

Tell 'em you saw it in HAM RADIO!

#### MICROCOMPUTER REPEATER CONTROL



Master code or upgrade in a matter of days. Code Quick is a unique breakthrough which simplifies learning Morse Code Instead of a confusing maze of dits and dahs, each letter will magically begin to call out its own name! Stop torturing yourself! Your amazing kit containing 5 power-packed cassettes, visual breakthrough cards and original manual is only \$39.95! Send check or money order today to WHEELER APPLIED RESEARCH LAB, P.O. Box 3261, City of Industry, CA 91744. Ask for **Code Quick #103**, California residents add 6% sales tax.

One User Comments: "First new idea in code study and the darn thing works! So much fun you don't realize how much you're learning.

196 M.S. Greneda, Miss.

Hundreds of satisfied customers! You can't lose! Follow each simple step. You must succeed or return the kit for a total immediate refund!



-Commercial quality, built to last -Light-weight, sealed, weatherproof trap(s) -Low loss end insulator -Handles up to 2000 watts PEP - Automatic band switching -For all transmitters, receivers & transceivers -Tuner usually never re-quired - Deluxe end feed connector, with built in lightning arrestor, accepts PL-259 coax connector -Use as sloper or vertical - Permanent or portable use - Easy to install -Can be used without radials . At. taches to almost any support Excellent for all class amateurs - Instructions included -10 day money-back guarantee!

4-Band-40,20,15,10 meters (27') 1 trap#VS-41 \$39.95 plus \$4.00 shipping 5-Band-80,40,20,15,10 meters (52') 2 traps #VS-52 \$54.95 plus \$4.00 shipping 50 ft. RG-58U, 52 ohm coax cable with PL-259 connector on each end - add \$8.00 to above price.



We accept VISA/MC - give Card#, Exp. date, Signature - 162 SPI-RO DISTRIBUTORS, Room 103, P.O. Box 1538 Hendersonville, NC 28793



MAGAZINE a unique publication. One year \$14.00 USA, Canada & Mexico. 199

Gus also prints high quality QSLs and other related items. Write today for a free sample of his QSLs and DX'ERS MAGAZINE.

Gus Browning, W4BPD • PO Drawer 405 • Cordova, SC 29039

More Details? CHECK-OFF Page 166

VISA

#### California

C & A ROBERTS, INC. 18511 HAWTHORN BLVD. TORRANCE, CA 90504 213-370-7451 24 Hour: 800-421-2258 Not The Biggest, But The Best -Since 1962.

#### FONTANA ELECTRONICS

8628 SIERRA AVENUE FONTANA, CA 92335 714-822-7710 714-822-7725 The Largest Electronics Dealer in San Bernardino County.

#### JUN'S ELECTRONICS

3919 SEPULVEDA BLVD. CULVER CITY, CA 90230 213-390-8003 800-882-1343 Trades Habla Espanol

#### Connecticut

HATRY ELECTRONICS 500 LEDYARD ST. (SOUTH) HARTFORD, CT 06114 203-527-1881 Call today. Friendly one-stop shopping at prices you can afford.

#### Delaware

**AMATEUR & ADVANCED** COMMUNICATIONS 3208 CONCORD PIKE WILMINGTON, DE 19803 (302) 478-2757 Delaware's Friendliest Ham Store.

#### **DELAWARE AMATEUR SUPPLY**

71 MEADOW ROAD NEW CASTLE, DE 19720 302-328-7728 800-441-7008 Icom, Ten-Tec, Microlog, Yaesu, Kenwood, Santec, KDK, and more. One mile off I-95, no sales tax.

#### Florida

AMATEUR ELECTRONIC SUPPLY 1898 DREW STREET CLEARWATER, FL 33575 813-461-4267 **Clearwater Branch** West Coast's only full service Amateur Radio Store. Hours M-F 9-5:30, Sat. 9-3

#### AMATEUR ELECTRONIC SUPPLY

621 COMMONWEALTH AVE. **ORLANDO, FL 32803** 305-894-3238 Fla. Wats: 1 (800) 432-9424 Outside Fla: 1 (800) 327-1917 Hours M-F 9-5:30, Sat. 9-3

AMATEUR RADIO CENTER, INC. 2805 N. E. 2ND AVENUE MIAMI, FL 33137 305-573-8383 The place for great dependable names in Ham Radio.

#### Hawaii

HONOLULU ELECTRONICS 819 KEEAUMOKU STREET HONOLULU, HI 96814 (808) 949-5564 Serving Hawaii & Pacific area for 51 years. Complete lines of Amateur equipment, accessories and parts.

#### Illinois

ERICKSON COMMUNICATIONS, INC. 5456 N. MILWAUKEE AVE. CHICAGO, IL 60630 312-631-5181 Hours: 9:30-5:30 Mon, Tu, Wed & Fri; 9:30-8:00 Thurs; 9:00-3:00 Sat.

#### Indiana

THE HAM STATION **808 NORTH MAIN STREET** EVANSVILLE, IN 47710 812-422-0231 Discount prices on Ten-Tec, Cubic, Hy-Gain, MFJ, Azden, Kantronics, Santec and others.

#### Massachusetts

James Millen Components by ANTENNAS ETC. 16 HANSOM ROAD ANDOVER, MA 01810 617-475-7831 Bezels, bindng posts, capacitors, condensers, chokes, coils, ceramics, H.V. connectors, plate caps, hardware knobs, dials, scopes and grid dippers. Inquire SASE or visit.

TEL-COM. INC. 675 GREAT ROAD, RTE. 119 LITTLETON, MA 01460 617-486-3400 617-486-3040 The Ham Store of New England You Can Rely On.

#### Michigan

**ENCON PHOTOVOLTAICS Complete Photovoltaic Systems** 27600 Schoolcraft Rd. Livonia, Michigan 48150 313-523-1850 Amateur Radio, Repeaters, Satellite, Computer applications. Call Paul WD8AHO

#### Nevada

AMATEUR ELECTRONIC SUPPLY 1072 N. RANCHO DRIVE LAS VEGAS, NV 89106 702-647-3114 Dale Porray "Squeak," AD7K Outside Nev: 1 (800) 634-6227 Hours M-F 9-5:30, Sat. 9-3

JUN'S ELECTRONICS 460 E. PLUMB LANE - 107 **RENO, NV 89502** 702-827-5732 Outside Nev: 1 (800) 648-3962 Icom - Yaesu Dealer

#### **NEW YORK**

ADIRONDACK ELECTRONICS, INC. **1991 CENTRAL AVENUE** ALBANY, NY 12205 518-456-0203 Amateur Radio for the Northeast since 1943

**BARRY ELECTRONICS** 512 BROADWAY NEW YORK, NY 10012 212-925-7000 New York City's Largest Full Service Ham and Commercial Radio Store.

**VHF COMMUNICATIONS** 915 NORTH MAIN STREET JAMESTOWN, NY 14701 716-664-6345 Call after 7 PM and save! Supplying all of your Amateur needs. Featuring ICOM "The World System." Western New York's finest Amateur dealer.

**Dealers:** YOU SHOULD BE HERE TOO! Contact Ham Radio now for complete details.

144 🚾 May 1985

# Ham Radio's guide to help you find your loca

### Amateur Radio Dealer

#### Ohio

AMATEUR ELECTRONIC SUPPLY 28940 EUCLID AVE. WICKLIFFE, OH (CLEVELAND AREA) 44092 216-585-7388 Ohio Wats: 1 (800) 362-0290 Outside Ohio: 1 (800) 321-3594 Hours M-F 9-5:30, Sat. 9-3 UNIVERSAL AMATEUR RADIO, INC.

1280 AIDA DRIVE REYNOLDSBURG (COLUMBUS), OH 43068

614-866-4267 Featuring Kenwood, Yaesu, Icom, and other fine gear. Factory authorized sales and service. Shortwave specialists. Near I-270 and airport.

#### Pennsylvania

HAMTRONICS, DIV. OF TREVOSE ELECTRONICS 4033 BROWNSVILLE ROAD TREVOSE, PA 19047 215-357-1400 Same Location for 30 Years.

LaRUE ELECTRONICS 1112 GRANDVIEW STREET SCRANTON, PENNSYLVANIA 18509 717-343-2124 Icom, Bird, Cushcraft, Beckman, Larsen, Hustler, Astron, Belden, Antenna Specialists, W2AU/W2VS, AEA, B&W, Amphenol, Saxton, J.W. Miller/Daiwa, Vibroplex.

THE VHF SHOP BOX 349 RD 4 MOUNTAINTOP, PA 18707 717-868-6565 Lunar, Microwave Modules, ARCOS, Astron, KLM, Tama, Tonna-F9FT, UHF Units/Parabolic, Santec, Tokyo Hy-Power, Dentron, Mirage, Amphenol, Belden

#### Texas

MADISON ELECTRONICS SUPPLY 1508 McKINNEY HOUSTON, TX 77010 713-658-0268 Christmas?? Now??

#### Wisconsin

AMATEUR ELECTRONIC SUPPLY 4828 W. FOND DU LAC AVE. MILWAUKEE, WI 53216 414-442-4200 Wisc. Wats: 1 (800) 242-5195 Outside Wisc: 1 (800) 558-0411 M-F 9-5:30 Sat 9-3 RADIO WAREHOUSE

**Division of HARDIN Electronics** 



## **TUBES**

TVDE	PRICE	ТУРГ		тург	DDICE
TYPE		TYPE	PRICE	TYPE	PRICE
2C39/7289	\$ 34.00	1182/4600A	\$500.00	ML7815AL	\$ 60.00
2E26	7.95	4600A	500.00	7843	107.00
2K28	200.00	4624	310.00	7854	130.00
3-500Z	102.00	4657	84.00	ML7855KAL	125.00
3-1000Z/8164	400.00	4662	100.00	7984	14.95
3B28/866A	9.50	4665	500.00	8072	84.00
3CX400U7/8961	255.00	4687	P.O.R.	8106	5.00
3CX1000A7/8283	526.00	5675	42.00	8117A	225.00
3CX3000F1/8239	567.00	5721	250.00	8121	110.00
3CW30000H7	1700.00	5768	125.00	8122	110.00
3X2500A3	473.00	5819	119.00	8134	470.00
3X3000F1	567.00	5836	232.50	8156	12.00
4-65A/8165	69.00	5837	232.50	8233	60.00
4-125A/4D21	79.00	5861	140.00	8236	35.00
4-250A/5D22	98.00	5867A	185.00	8295/PL172	500.00
4-400A/8438	98.00	5868/AX9902	270.00	8458	35.00
4-400B/7527	110.00	5876/A	42.00	8462	130.00
4-400C/6775 4-1000A/8166	$110.00 \\ 444.00$	5881/6L6 5893	8.00	8505A	95.00
4CX250B/7203	54.00	5893 5894/A	60.00 54.00	8533W	136.00
4CX250FG/8621	75.00	58947A 5894B/8737	54.00	8560/A 8560AS	75.00 100.00
4CX250K/8245	125.00	5946	395.00	8608	38.00
4CX250R/7580W	90.00	6083/AZ9909	95.00	8624	100.00
4CX300A/8167	170.00	6146/6146A	8.50	8637	70.00
4CX350A/8321	110.00	6146B/8298	10.50	8643	83.00
4CX350F/8322	115.00	6146W/7212	17.95	8647	168.00
4CX350FJ/8904	140.00	6156	110.00	8683	95.00
4CX600J/8809	835.00	6159	13.85	8877	465.00
4CX1000A/8168	242.50*	6159B	23.50	8908	13.00
4CX1000A/8168	485.00	6161	325.00	8950	13.00
4CX1500B/8660	555.00	6280	42.50	8930	137.00
4CX5000A/8170	1100.00	6291	180.00	6L6 Metal	25.00
4CX10000D/8171	1255.00	6293	24.00	6L6GC	5.03
4CX15000A/8281	1500.00	6326	P.O.R.	6CA7/EL34	5.38
4CW800F	710.00	6360/A	5.75	6CL6	3.50
4D32	240.00	6399	540.00	6DJ8	2.50
4E27A/5-125B	240.00	6550A	10.00	6DQ5	6.58
4PR60A	200.00	6883B/8032A/8552	10.00	6GF5	5.85
4PR60B	345.00	6897	160.00	6GJ5A	6.20
4PR65A/8187	175.00	6907	79.00	6GK6	6.00
4PR1000A/8189	590.00	6922/6DJ8	5.00	6HB5	6.00
4X150A/7034	60.00	6939	22.00	6HF5	8.73
4X150D/7609	95.00	7094	250.00	6JG6A	6.28
4X250B	45.00	7117	38.50	6JM6	6.00
4X250F	45.00	7203	P.O.R.	6JN6	6.00
4X500A	412.00	7211	100.00	6JS6C	7.25
5CX1500A	660.00	7213	300.00*	6KN6	5.05
KT88	27.50	7214	300.00*	6KD6	8.25
416B	45.00 62.50	7271	135.00	6LF6 6L06 G.E.	7.00
416C		7289/2039	34.00		7.00
572B/T160L 592/3-200A3	49.95 211.00	7325 7360	P.O.R. 13.50	6LQ6/6MJ6 Sylvania 6ME6	9.00 8.90
807	8.50	7377	85.00	12AT7	3.50
811A	15.00	7408	2.50	12AX7	3.00
812A	29.00	7609	95.00	12BY7	5.00
813	50.00	7735	36.00	12JB6A	6.50
NOTE * = USED T	TURF	NOTE POR = PRI	CE ON REQUEST		

NOTE \* = USED TUBE

NOTE P.

NOTE P.O.R. = PRICE ON REQUEST

"ALL PARTS MAY BE NEW, USED, OR SURPLUS. PARTS MAY BE SUBSTITUTED WITH COMPARABLE PARTS IF WE ARE OUT OF STOCK OF AN ITEM.

NOTICE: ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE.

Toll Free Number 800-528-0180 (For orders only) "All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item." MHZ electronics 3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE


For information call: 602-265-0731

		"FILTERS"				
COLLINS M	1echanical Filte	er #526-9724-010 MODEL F455Z32F				
		May be other models but equivalent. May be used or new,	\$15,99			
	<u>stal Filters</u>	May be outer indiers and equivarent. May be used of item	++0			
5.595	-2.7/8/LSB, 5.595-	2.7/LSB	19,99			
	e 2.7KHz wide Uppe -2.7/8/U, 5.595-2.	r sideband. Impedence 800ohms 15pf In/800ohms 0pf out. 7/USB	19,99			
8 pol	e 2.7Khz wide Uppe	r sideband. Impedence 800ohms 15pf In/800ohms 0pf out.	19,99			
4 pol	e 500 cycles wide	CW. Impedance 800ohms 15pf In/800ohms 0pf out.	19,99			
9.0US 6 pol		dB. Impedance 680ohms 7pf In/300ohms 8pf out. CW-1599Hz	19.99			
KOKUS	SAI ELECTRIC CO	, <u>Mechanical Filter</u> #MF-455-ZL/ZU-21H				
		ency of 453.5KC, Carrier Frequency of 455KHz 2.36KC Bandwi	dth. 19,99			
	er sideband. (ZU) er sideband. (ZL)	*****	19.99			
CRYSTAL F	**************************************	***************************************	******			
NIKKO	FX-07800C	7.3MHz	\$10.00			
TEW	FEC-103-2	10.6935MHz	10.00			
SDK	SCH-113A	11.2735MHz	10.00 19.99			
TAMA 'TYCO/CD	TF-31H250 001019880	CF 3179.3KHz 10.7MHz 2pole 15KHz bandwidth	5,00			
MOTOROLA	4884863B01	11.7MHz 2pole 15KHz bandwidth	5.00			
PTI	5350C	12MHz 2pole 15KHz bandwidth	5.00			
PTI	5426C	21.4MHz 2pole 15KHz bandwidth	5.00			
PTI	1479	10.7MHz 8pole bandwidth 7.5KHz at 3dB, 5KHz at 6dB	20.00			
COMTECH	A10300	45MHz 2pole 15KHz bandwidth	6.00 10.00			
FRC FILTECH	ERXF-15700 2131	20.6MHz 36KHz wide CF 7.825MHz	10.00			
	************	**************************************	*****			
CERAMIC_F	ILTERS					
AXEL	4F449	12.6KC Bandpass Filter 3dB bandwidth 1.6KHz from 11.8-13.	.4KHz 10.00			
CLEVITE	TO-01A	455KHz+-2KHz bandwidth 4-7% at 3dB	5,00			
	TCF4-12D36A	455KHz+-1KHz bandwidth 6dB min 12KHz, 60dB max 36KHz	10.00			
MURATA	BFB455B	455K11z	2.50			
	BFB455L	455KHz	3.50 6.65			
	CFM455E CFM455D	$455 \rm KHz$ +-5.5 KHz at 3dB , +-8 KHz at 6dB , +-16 KHz at 50 dB $455 \rm KHz$ +-7 KHz at 3dB , +-10 KHz at 6dB , +-20 KHz at 50 dB	6.65			
	CFR455E	$455$ KHz $\pm 5.5$ KHz at 3dB , $\pm 8$ KHz at 6dB , $\pm 16$ KHz at 60dB				
	CFU455B	455KHz +-2KHz bandwidth +-15KHz at 6dB, +-30KHz at 40dB	2.90			
	CFU455C	455KHz +2KHz bandwidth +-12.5KHz at 6dB , +-24KHz at 400	BB 2.90			
	CFU455G	455KHz +-1KHz bandwidth +-4.5KHz at 6dB , +-10KHz at 40dB	в 2.90			
	CFU455H	455KHz +-1KHz bandwidth +-3KHz at 6dB , +-9KHz at 40dB	2,90			
	CFU455I	455KHz +-1KHz bandwidth +-2KHz at 6dB , +-6KHz at 40dB	2,90			
	CFW455D	455KHz $+10$ KHz at 6dB , $+20$ KHz at 40dB	2.90 2.90			
	CFW455H SFB455D	455KHz $+-3$ KHz at 6dB , $+-9$ KHz at 40dB 455KHz	2.50			
	SFD455D	455KHz $+2$ KHz , 3dB bandwidth $4.5$ KHz $+-1$ KHz	5.00			
	SFE10.7MA	$10.7MHz$ 280KHz $\pm$ 50KHz at 3dB , 650KHz at 20dB	2,50			
	SFE10.7MS	10,7MHz 230KHz +-50KHz at 3dB , 570KHz at 20dB	2,50			
	SFG10.7MA	10.7MHz	10.00			
NIPPON	• .	455KHz +-1KHz	2.90			
	•	455KHz +-1KHz	2,90			
	LF-B8	455KHz	2.90 10.00			
TOKIN	LF-C18	455KHz 455KHz +→2KHz	5,00			
MATSUSHIRA	EFC-L455K	455KHz	7.00			
****** SPFCTRA P	**************************************	el 088 Hene LASER TUBES	****			
POWER OUTPU			IG VOLTAGE DC			
68K OHM 1WA		OVDC +- 100VDC At 3.7MA	\$59.99			
<u>RUTRON MUI</u> 115 VAC	FFIN FANS Model 14WATTS 50/	<u>MARK4/MUZA1</u> '60CPS IMPEDENCE PROTECTED-F 88CFM at 50CPS	\$ 7.99			
105CFM at 6	OCPS THESE	ARE NEW Toll Free Number	All parts may be new or			
SMGH Z electronics 800-528-0180 supplus, and parts may be substituted with comparable parts						
3802 North 27th	Ave., Phoenix, AZ 8	(For orders only)	e are out of stock of an item."			

		DE	TDAN		C			
		RF	IKAN	ISISTOF	5			
TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	
2N1561	\$25.00	2N5920	\$ 70.00 80.00	40608 RCA 40673 RCA	\$ 2.48 2.50	BFY90	\$ 1.50	
2N1562 2N1692	25.00 25.00	2N5921 2N5922	10.00	40894 RCA	1.00	BLW60C5 BLX67	15.00 12.25	
2N2857	1,55	2N5923	25.00	60247 RCA	25,00	BLX67C3	12.25	
2N2857JA		2N5941	23.00		100.00 60.00	BLX93C3	22.21	
2N2857JA 2N2876	NTX 4.50 13.50	2N5942 2N5944	40.00 10.35	62800A RCA 62803 RCA	100.00	BLY87A BLY88C3	7.50 13.08	
2N2947	18.35	2N5945	10.00	430414/3990RCA	50.00	BLY89C	13.00	
2N2948	13.00	2N5946	12.00	3457159 RCA 3729685-2 RCA	20.00 75.00	BLY90 BLY92	45.00 13.30	
2N2949 2N3118	15.50 5.00	2N5947 2N6080	9.20 6.00	3729701-2 RCA	50.00	BLY94C	45.00	
2N3119	4.00	2N6081	7.00	3753883 RCA	50.00	BLY351	10.00	
2N3134	1.15	2N6082	9.00	615467-902	25.00	BLY568C/CF	30.00	
2N 32 87 2N 32 88	4.90 4.40	2N6083 2N6084	9.50 12.00	615467-903 28C568	40.00 2.50	C2M70-28R C25-28	92.70 57.00	
2N3309	4.85	2N6094	11.00	2SC703	36,00	C4005	2.50	
2N3375	17.10	2N6095	12.00	2SC756A	7,50	CD1659	20.00	
2N3478 2N3553	2.13 1.55	2N6096 2N6097	16.10 20.70	2SC781 2SC1018	2.80 1.00	CD1899 CD1920	20.00 10.00	
2N3553JA		2N6105	21.00	2SC1042	24.00	CD2188	18,00	
2N 3632	15.50	2N6136	21.85	2SC1070	2.50	CD2545	24.00	
2N3733 2N3818	11.00 5.00	2N6166 2N6267	40.24 142.00	2SC1216 2SC1239	2.50 2.50	CD2664A CD3167	16.00 92.70	
2N3866	1,30	2N6304	1,50	28C1251	24.00	CD3353	95.00	
2N3866JA	N 2.20	2N6368	30.00	2SC1306	2.90	CD3435	26.30	
2N3866JA		2N6439 2N6459	55.31 18.00	2SC1307 2SC1424	5.50 2.80	CD3900 CM25-12	152.95	
2N3866JA 2N3866AJ		2N6567	10.06	2501424	5.00	CM2 3-12 CM40-12	20.00 27.90	
2N3924	3.35	2N6603	13.50	2SC1678	2.00	CM40-28	56.90	
2N3926	16.10	2N6604	13.50	2SC1729	32.40	CME 50-12	30.00	
2N3927 2N3948	17.25 1.75	2N6679 2N6680	44.00 80.00	2SC1760 2SC1909	1.50 4.00	CTC2001 CTC2005	42.00 55.00	
2N3948 2N3950	25.00	021-1	15.00	2SC1945	10.00	CTC 3005	70.00	
2N3959	3.85	01-80703T4	65.00	2SC1946	40.00	CTC3460	20.00	
2N4012	11.00	35005	15.00	2SC1947 2SC1970	10.00 2.50	DV2820S	25.00	
2N4037 2N4041	2.00 14.00	102-1 103-1	28.00 28.00	2SC1970 2SC1974	4.00	DXL1003P70 DXL2001P70	22.00 19.00	
2N4072	1.80	103-2	28.00	2SC2166	5,50	DXL2002P70	14.00	
2N4080	4.53	104P1	18.00	2SC2237	32.00	DXL3501AP100F	47.00	
2N4127 2N4416	21.00 2.25	163P1 181-3	10.00 15.00	2SC2695 A2X1698	47.00 POR	EFJ4015 EFJ4017	12.00 24.00	
2N4410 2N4427	1.25	210-2	10,00	A3-12	14.45	EFJ4021	24.00	
2N4428	1.85	269-1	18.00	A50-12	24.00	EFJ4026	35.00	
2N4430 2N4927	11.80 3.90	281-1 282-1	15.00 30.00	A209 A283	10.00 6.00	EN 15745 FJ9540	20.00 16.00	
2N4927 2N4957	3.45	482	7.50	A283B	6.00	FSX52WF	58.00	
2N4959	2.30	564-1	25.00	A1610	19.00	G65739	25,00	
2N5016 2N5026	18.40 15.00	698-3 703-1	15.00 15.00	AF102 AFY12	2.50 2.50	G65386 GM0290A	25.00	
2N5028 2N5070	18.40	704	4.00	AR7115	20.00	HEP 76	2.50 4.95	
2N5090	13.80	709-2	11.00	AT41435-5	6.35	HEPS 3002	11.40	
2N5108	3.45	711	4.00	B2-8Z B3-12	10.70 10.85	HEPS 3003	30.00	
2N5109 2N5160	1.70 3.45	733-2 798-2	15.00 25.00	B12-12	15.70	HEPS 3005 HEPS 3006	10.00 19.90	
2N5177	21.62	3421	28.00	BAL0204125	152.95	HEPS 3007	25.00	
2N5179	1.04	3683P1	15.00	BF25-35 B40-12	56.25 19.25	HEPS3010	11.34	
2N5216 2N5470	56.00 75.00	3992 4164P i	25.00 15.00	B70-12	55.00	HF8003 HFET2204	10.00 112.00	
2N5583	3.45	4243P1	28.00	BF272A	2.50	HP 35821	38.00	
2N5589	9.77	4340P3	18.00	BFQ85 BFR21	2.50 2.50	HP 35826B HP 35826E	32.00 32.00	
2N5590 2N5591	10.92 13.80	4387Pl 7104-1	27.50 28.00	BFR21 BFR90	1.00	HP 35826E HP 35831E	32.00	
2N5596	99.00	7249-2	10.50	BFR91	1.65	HP35832E	50.00	
2N5636	12.00	7283-1	37.50	BFR99 BFT12	2.50 2.50	HP <b>358</b> 33E HP35859E	50,00 75,00	
2N5637 2N5641	15.50 12.42	7536-1 7794-1	30.00 10.50	BFW16A	2.50	HP 35866E	44.00	
2N5642	14.03	7795	15.00	BFW17	2.50	HXTR2101	44.00	
2N5643	25.50	7795-1	15.00	BFW92	1.50	HXTR 3101	7.00	
2N5645 2N5646	13.80 20.70	7796-1 7797-1	24.00 36.00	BFX44 BFX48	2.50 2.50	HXTR5101 HXTR6104	31.00 68.00	
2N5651	11.05	40081 RCA	5.00	BFX65	2.50	HXTR6105	31.00	
2N5691	18.00	40279 RCA	10.00	BFX84	2.50	HXTR6106	33.00	
2N5764 2N5836	27.00 3.45	40280 RCA 40281 RCA	4.62 10.00	BFX85 BFX86	2.50 2.50	J310 J02000	1.00	
2N5842	8.45	40282 RCA	20.00	BFX89	1.00	J02001	25.00	
2N 584 7	19,90	40290 RCA	. 2.80	BFY11	2.50	J04045	24.00	
2N5849 2N5913	20.00 3.25	40292 RCA 40294 RCA	13.05 2.50	BFY18 BFY19	2.50 2.50	KD5522 KJ5522	25.00 25.00	
2N5913 2N5916	3.25	40294 RCA 40341 RCA	21.00	BFY 39	2.50	M1106	13.75	
Toll Free Nun	har			PRICES SUBJE		CHANGE WITHO		
800-528-0180	surpl	I parts may be us, and parts	may be	SMGH 7				
	substi	ituted with compa are out of stock of			el	ectro	IIICS	
(For orders o	For infe		: 602-265-0731			th 27th Ave., P		85017
·····		·						

٠

RF TRANSISTORS (CONTINUED)								
M1107	\$16.75	MRF458	\$20.70	NEO2160ER	\$100.00	SD1009	\$15.00	
M1131 M1132	5.15 7.25	MRF464 MRF466	25.30 18.97	NEO21350 NE13783	5.30 61.00	SD1009-2 SD1012	15.00 10.00	
M1132 M1134	13.40	MRF472	1.50	NE21889	43.00	SD1012-3	10.00	
M9116	29.10	MRF475	3.10	NE57835	5.70	SD1012-5	10.00	
M9579	6.00	MRF476	3.16	NE64360ER-A	100.00 94.00	SD1013	10.00 10.00	
M9580 M9587	7.95 7.00	MRF477 MRF479	20,00 8.05	NE64480 (B) NE73436	2.50	SD1013-3 SD1013-7	10.00	
M9588	5.20	MRF492	23.00	NE77362ER	100.00	SD1016	15.00	
M9622	5.95	MRF502	1.04	NE98260ER	100.00	SD1016-5	15.00	
M9623	7.95	MRF503	6.00	PRT8637	25.00 5.00	SD1018-4	13.00 13.00	
M9624 M9625	9,95 15,95	MRF504 MRF509	7.00 5.00	PT3127A PT3127B	5.00	SD1018-6 SD1018-7	13.00	
M9630	14.00	MRF511	10.69	PT3127C	20.00	SD1018-15	13.00	
M9740	27.90	MRF515	2.00	PT3127D	20.00	SD1020-5	10.00	
M9741 M9755	27.90 16.00	MRF517 MRF525	2.00 3.45	РТЗ127Е РТЗ190	20.00 20.00	SD1028 SD1030	15.00 12.00	
M9780	5.50	MRF559	1.76	PT 3194	20.00	SD1030-2	12.00	
M9827	11.00	MRF587	11.00	PT3195	20.00	SD1040	5.00	
M9848	35.00 13.50	MRF605 MRF618	20.00 25.00	PT3537 PT4166E	7.80 20.00	SD1040-2 SD1040-4	20.00 10.00	
M9850 M9851	20.00	MRF626	12.00	PT4176D	25.00	SD1040-4	5.00	
M9860	8.25	MRF628	8.65	PT4186B	5.00	SD1043	12.00	
M9887	2.80	MRF629	3.45	PT4209 PT4209C/5645	25.00 25.00	SD1043-1	10.00 3.75	
M9908 M9965	6.95 12.00	MRF641 MRF644	25.30 27.60	PT4209C/5645 PT4556	25.00	SD1045 SD1049-1	2.00	
MM1500	25.00	MRF646	29.90	PT4570	7.50	SD1049-1 SD1053	4.00	
MM1550	10.00	MRF648	33.35	PT4577	20.00	SD1057	10.00	
MM1552	50.00	MRF816 MRF823	15.00	PT4590 PT4612	5.00 20.00	SD1065 SD1068	4.75 15.00	
MM1553 MM1607	50.00 8.45	MRF823 MRF846	20.00 44.85	PT4612 PT4628	20.00	SD1068 SD1074-2	18.00	
MM1614	10.00	MRF892	35.50	PT4640	20.00	SD1074-4	28.00	
MM1810	15.00	MRF894	46.00	PT4642	20.00	SD1074-5	28.00	
MM1810 MM1943	15.00 1.80	MRF901 3 Lead MRF901 4 Lead	1.00 2.00	PT5632 PT5749	4.70 25.00	SD1076 SD1077	18.50 4.00	
MM2608	5.00	MRF901 4 Lead MRF902/2N6603JAN	15.00	PT6612	25.00	SD1077-4	4.00	
MM3375A	17.10	MRF902B	18.40	PT6619	20.00	SD1077-6	4.00	
MM4429	10.00 1.15	MRF904	2.30	PT6708	25.00 25.00	SD1078-6	24.00 - 7.50	
MM8000 MM8006	2.30	MRF905 MRF911	2.55 2.50	PT6709 PT6720	25.00	SD1080-7 SD1080-8	6.00	
MM8011	25,00	MRF965	2.55	PT8510	15.00	SD1080-9	3.00	
MPSU31	1,01	MRF966	3.55	PT8524	25.00	SD1084	8.00	
MRA2023-1.5 MRF134	5 42.50 10.50	MRF1000MA MRF1004M	32.77 31.05	PT8609 PT8633	25.00 25.00	SD1087 SD1088	15.00 22.00	
MRF134 MRF136	16.00	MRF2001	41.74	PT8639	25.00	SD1088-8	22.00	
MRF171	35.00	MRF2005	54.97	PT8659	25.00	SD1089-5	15.00	
MRF208	11.50	MRF5176 MRF8004	24.00 2.10	PT8679 PT8708	25.00 20.00	SD1090 SD1094	15.00 15.00	
MRF212 MRF221	16.10 10.00	MRF8004 MSC1720-12	225.00	PT8709	20.00	SD1094 SD1095	15.00	
MRF223	13.00	MSC1821-3	125.00	PT8727	29.00	SD1098-1	30.00	
MRF224	13.50	MSC1821-10	225.00	PT8731 PT8742	25.00 19.10	SD1100	5.00 18.00	
MRF227 MRF230	3.45 2.00	MSC2001 MSC2010	30.00 93.00	P18742 PT8787	25.00	SD1109 SD1115-2	7.50	
MRF231	10.00	MSC2223-10	245.00	PT8828	25.00		7.50	
MRF232	12.07	MSC2302	POR	PT9700	25.00	SD1115-7	2.10	
MRF237 MRF238	3.15 13.80	MSC3000 MSC3001	35.00 38.00	РТ9702 РТ9783	25.00 16.50	SD1116 SD1118	5.00 22.00	
MRF238 MRF239	17,25	MSC72002	POR	PT9784	32.70	SD1119	5.00	
MRF245	35.65	MSC73001	POR	PT9790	56.00	SD1124	50.00	
MRF247	31.00	MSC80064	35.00	PT31083 PT31962	20.00 20.00	SD1132-1	15.00 12.00	
MRF 304 MRF 306	36.00 50.00	MSC80091 MSC80099	10.00 3.00	PT31962 PTX6680	20.00	SD1132-4 SD1133	9.50	
MRF313	11.15	MSC80593	POR	RE3754	25.00	SD1133-1	10.00	
MRF314	29.21	MSC80758	POR	RE 3789	25.00	SD1134-1	2.50	
MRF315 MRF316	28.86 55.43	MSC82001 MSC82014	33.00 33.00	RF35 RF85	16.00 17.50	SD1134-4 SD1134-17	12.00 12.00	
MRF317	63.94	MSC82014 MSC82020M	130.00	RF110	21.00	SD1134-17 SD1135	10.25	
MRF412	18.00	MSC82030	33.00	S50-12	23.80	SD1135-3	12.00	
MRF420	20,12	MSC83001	40.00	\$3006 \$3007	15.00	SD1136	12.50	
MRF421 MRF422	25.00 38.00	MSC83003 MSC83005	82.00 70.00	S 3007 S 3031	10.00 22.00	SD1136-2 SD1143-1	12.50 10.00	
MRF427	17.25	MSC83026	POR	SCA3522	5.00	SD1143-3	17.00	
MRF428	63.00	MSC83303	POR	SCA3523	5.00	SD1144	4.00	
MRF433 MRF449/A	12.07 12.65	MSC84900 MT4150	60.00 14.40	SD345 SD445	5.00 5.00	SD1145-5 SD1146	15.00 15.00	
MRF449/A MRF450/A	12.65	MT5126	25.00	SD1004	15.00	SD1146 SD1147	15.00	
MRF452/A	17.00	MT5596(2N)	99.00	SD1007	15.00	SD1188	10.00	
MRF453/A	18.40	MT5768(2N)	95.00	SD1007-2	15.00	SD1189	24.00	
MRF454/A	20.12	MT8762 NEO2136	25.00 2.00	SD1007-4 SD1007-5	15.00 15.00	SD1200 SD1201-2	1.50 15.00	
MRF455/A	16.00				-	-		-
oll Free Num		All parts may be ne rplus, and parts ma		<b>XN 'H</b>	Z	elect	ronica	Ň
300-528-0180	sut	stituted with comparable	parts				Ave., Phoenix, A	
(For orders on	IV)	ve are out of stock of an it			3802 12 12 12		GE WITHOUT NO	TICE
	f For in	formation call: 60	2-265-073	PRICE	3 300JE	UT TO OTIAN	42 miniour 40	

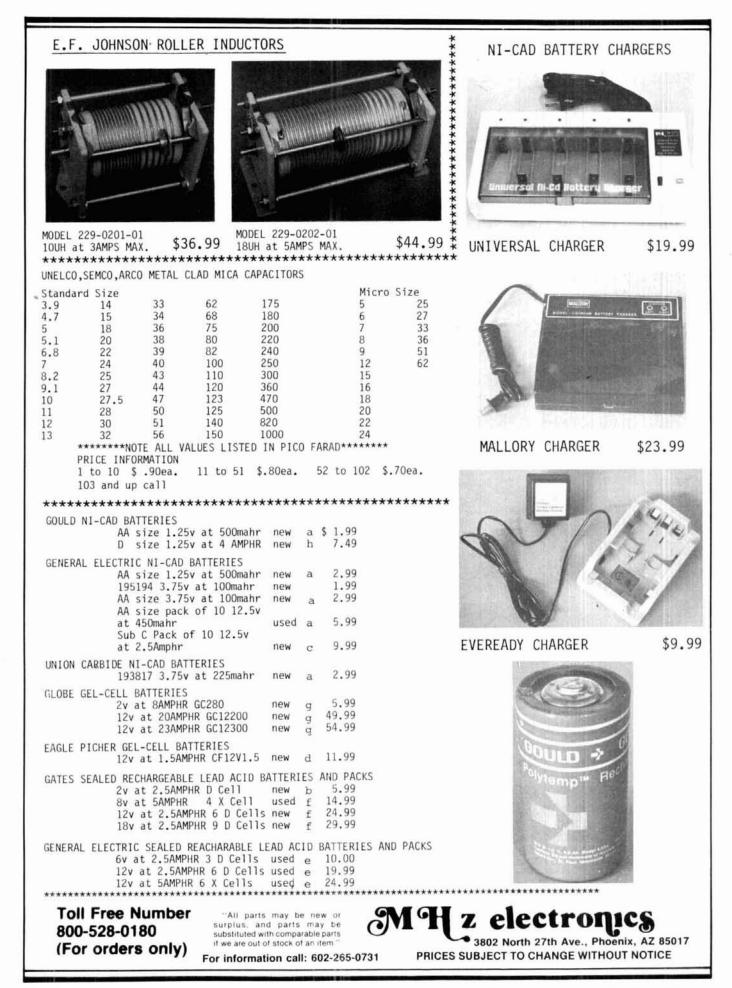

#### **RF Transistors (continued)**

SD1202	\$10,00	501304~8	5 2,50	101451-2	\$15.00	SHF1427	\$50.00	501244812	25.00	SD1410-8	21,00	501536-1	41.00	SRF2917	15.00
SD1212-8	4.95	SD1305	3,00	SD1452	20.00	5RF1431	40,00	\$01262	15.00	SD1413-1	18,00	5D1539H	100.05	SKF2918	15,00
501212-11	4.95	SD1307	1.00	501432-4	24,00	SRF1834	40,00	501263	15.00	501416	28,00	50154281	170.00	5882919	15,00
501212-16	4.95	SD1308	1,00	SD1453H1	20.00	58F2053-3	60,00	SD1263-1	15.00	SD1422-2	24,00	501544	26,00	5KF3071PF	50,00
501214-7	5,00	SD1311	1.00	SD1454-1	48,00	5RF2092	50,00	SD1272	10.95	501428	74,00	SD1545	33,00	554006	25,00
SD1214-11	5,00	SD1317	8,00	SD1477	35,00	SRF2147	22,00	5D1272-1	10,95	SD1428- 6084	12.00	SD1546H1	55.00	554152	15,00
5D1216	12.00	SD1319	2.50	SD1478	21,00	SRY2225	15,00	501272-2	10.95	SD1429-2	15.00	501561	79+00	TA7686	15,00
SD1219-4	15,00	SD1345-6	5.00	SD1480	53,00	58F2264	25.00	5D1272-4	10.95	501429-3	14.90	501574-1	6.95	TA8559	15,00
SD1219-5	15,00	SD1347-1	1.00	501484	1.50	SRF2265	100,00	SD1278	13.75	SD1429-5	15.00	SB1575	6.95	TA8561	15,00
SD1219-8	15,00	SD1365~1	2.50	SD1484-5	1.50	SRF2281	5,00	501278-1	13.75	501430	12,00	SF4557	25.00	TA8562	15.00
SD1220*	8.00	SD1365-5	2.50	SD1484-6	1,50	58¥2371	15,00	SD1278-5	13,25	501430-2	18.00	SK3048	5.00	TA8563	15,00
SD1220-1	9,50	SD1375	7,50	SD1484-7	1.50	58F2347	50,00	501279-1	18.00	501434	28,00	51,501-59	15.00	TAR564	15,00
5D1220-9	8,00	SD1375-6	7,50	SD1488	22.85	SHF2356	38,00	\$01279-3	18,00	SD1434-5	28,00	51.501-173	15,00	TA8894	15,00
SD1222-8	16,00	501379	15.00	SD1488-1	28,00	58F2378	16.00	SD1281-2	8,00	501434~9	28.00	SM7714	5.00	218180	3,55
SD1222-11	7,50	501380-1	1.00	SD1488-7	27,00	SRF2572	25.00	511283	10,00	531438	26.00	5HF312	15,00	TP312	2,50
SD1224-10	18,00	SD1380-3	1,00	SD1488-8	28,00	58F2584	40.00	SD1283-2	10,60	531441	56,90	SRF395	50,00	TP1014	5,00
SD1225	18,00	301380-7	1,00	501699-1	36,00	SRF2597	25,00	SD1283-3	10,00	501442	15.00	58F750	36,00	TF1028	15.00
501225-1	15,00	SD1405	21,00	SD1511H3	25.00	SRF2741	40.00	SD1283-4	10,00	5D1444	3.25	SRF769H	20,00	TRW3	5.00
5D1229~7	10,95	SD1408	25.00	SD1520-2	18,00	SEF2747	40.00	501289-1	15,00	SD1444-8	3.25	5RF887K3	2,50	TXVF2201/HP	450.00
SD1229-10	10,95	501409	18.00	\$01522+4	33.00	SRF2767H	40,00	501290-4	15,00	SD1444-9	3.25	SRF989K	15,00	V222-2	25.00
SD1232	4.00	SD1410	18,00	SD1528-1	24,00	SRP2821	25,00	501290-7	15,00	SD1446	4,03	SRF1005	50,00	V4101E	20,00
501240-8	15.00	SD1410+3	21,00	\$111528-3	34,00	58F2822/2N6503	13,50	SD1300	1.25	SD1450-1	28,00	SRF1018	5.00	V415	5,00
SD1244-1	14.00	SD1410-6	21,00	501530-2	38.00	SRF2857	20,00	501301-7	1,00	SD1451	15,00	SHF1074	50.00		

Relays

BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.



NUNQ ORDERS: We would prefer that continning orders not be sent after a telephone order has been placed. If con monoscillates a continning order, please mark "CONFIRMING" bothy on the order. It problems or duplicate shipmen to an order which is not properly marked, the customer will be held responsible for any charges incurred, plus a charge on the returned parts.

CREDIT CARDS: We are now accepting MASTERCARD, VISA, AND AMERICAN EXPRESS

DATA SHEETS: When we have data sheets in stock on devices we will supply them with the order

DEFECTIVE MATERIALS: All claims for delective materials must be made within 30 DAYS after receipt of the must include the defactive material for testing purposes), a copy of our involce, and a return authorization numr obtained prior to shipping the merchandres back to sur. This can be obtained by calling (602, 242-8016 or send) Dae to Manufacturer warranties we are unable to replace or issue credit on items which have been solderer attends in any way. All return items must be packed property or it will void all warranties. We do not assume resp ping and handling charges incurred. eipt of the parcel. All clai ation number which must 16 or sending us a posto an soldered to or have be sume responsibility for all

DELIVERY: Orders are usually shipped the same day they are placed or the next business day, unless we are out of stock on an item. The customer will be notified by post card if we are going to backorder the item. Our normal shipping method is UPS or U.S. Mail depending on size or the weight of the package. Test Equipment is shipped only by all and is freight collect, unless prior arrangements have been made and approved.

FOREIGN ORDERS: All foreign orders must be prepaid with a Cashier's Check, or Money Order made out in U.S. FUNDS ONLY. We are somy but C.O.D. is not available to foreign countries and letters of credit are unacceptable as a form of payment. Further information is available on resent

HOURS: Monday thru Friday 8:30 a.m. to 5:00 p.m. Saturdays 8:30 a.m. to 4:00 p.m.

INSURANCE: Please include 25¢ for each additional \$100.00 over \$100.00. UPS ONLY. All insured packages are shipped thru UPS only if you wish to have it shipped through the post office there is a \$5.00 fee which is additional to the shipping, handling and in surance.

OPEN ACCOUNTS: We regret that we do not issue open accounts

ORDER FORMS: New order forms are included with each order for your convenience. Additional order forms are available on

PARTS: We reserve the right to substitute or replace any item with a part of equal or comparable

PREPAID ORDERS: Orders must be accompanied by a check.

PRICES: Prices are subject to change without notice.

PURCHASE ORDERS: We accept purchase orders only when they are accompanied by a check

RESTOCK CHARGES: If parts are returned to MHZ ELECTRONICS, INC. due to customer error, the customer will be held responsible for all fees incurred and will be charged a 15% RESTOCK CHARGE with the remainder in CREDIT ONLY. The following must accompany any return, a copy of our invoice, return authorization number which must be obtained prior to shipping the merchandise back. Returns must be done within 10 DAYS of receipt of parcel. Return authorization numbers can be obtained by calling (602) 242-8916 or notifying us by post card. Return authorizations will not be given out on our 800 number.

SALES TAX: ARIZONA residents must add 6% sales tax, unless a signed ARIZONA resale tax card is currently on tile with us. All orders placed by persons outside of ARIZONA, but delivered to per-sons in ARIZONA are subject to the 6% sales tax.

SHORTAGE OR DAMAGE: All claims for shortages or damages must be made within 5 DAYS of receipt of parcel. Claims must include a copy of our invoice, along with a return authorization number which can be obtained by contacting us at (602) 242-8916 or sending a post card. Authoriza-tions cannot be on our 800 number. All items must be properly packed. If items are not properly packed make sure to contact the carrier so that they can come out and inspect the package before it is returned to us. Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY (800) 528-0180. INFORMATION CALLS ARE TAKEN ON (602) 242-8916 or (602) 242-3037.



"All parts may be new or

For information call: 602-265-0731

**Toll Free Number** 800-528-0180 (For orders only) PRICES SUBJECT TO CHANGE WITHOUT NOTICE

3802 North 27th Ave., Phoenix, AZ 85017

if we are out of stock of an item."

surplus, and parts may be substituted with comparable parts


VISA

More Details? CHECK-OFF Page 166







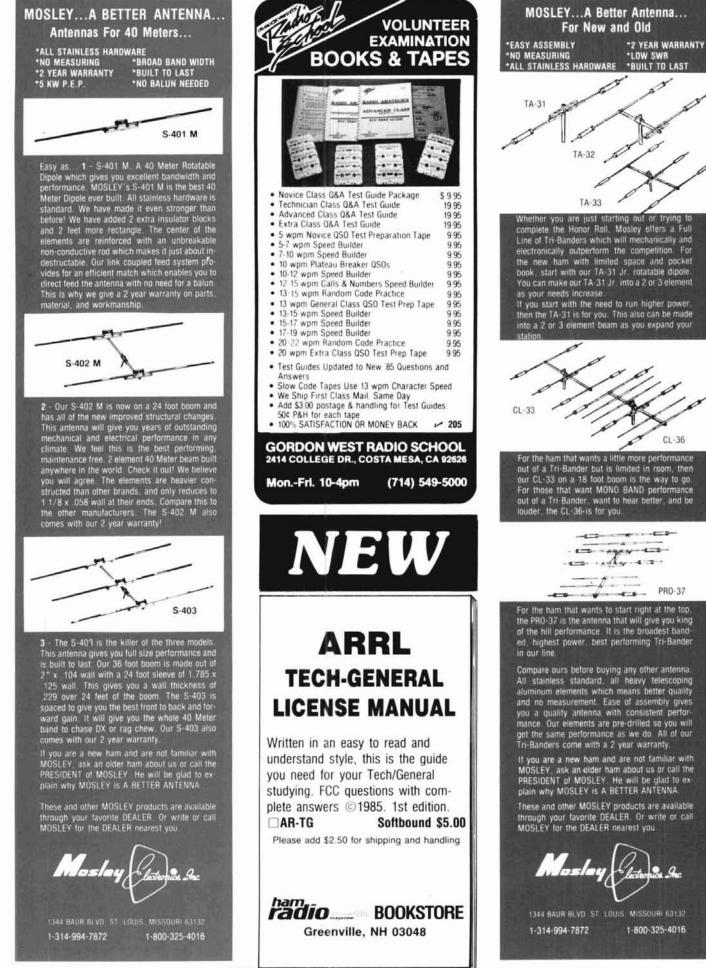

CL-36

4-1

PRO-37



TS-430S Most Advanced. Compact HF Transceiver

General Coverage Receiver
 USB/LSB/CWAM/Optional FM • 10Hz
Uual Step Digital VFO • Eight Memories
w/Lithium Back-up • Memory and Band
Scan



TS-930S Top of the Line General Coverage Receiver 
 Superior
Dynamic Range 
 All Solid State
 28
 VDC Final 
 OSK CW 
 Optional
Automatic Antenna Tuner 
 Dual VFO 
 w/8
 Memones 
 Dual Mode Noise Blanker

.....



 Large LCD Readout • 21 Multi-Function Memory • Lithium Back up • Automatic Offset • Built in Encoder • Memory or Band Scan

2.5W/300 mW (Switchable) 2 Meter Handheld Transceiver LCD Readout • Ten Memories w/Lithium Back-up • Band and Memory Scan • Built in Sub-tone Encoder

17 YAE YAESU 5 . R į, FT-209RH 1.0 1111 1 5 Watts
 10 Memories
 LCD
 Compact 3 8 61 FT980 FT-2700RH FT-757 GX CAT SYSTEM-ComputerAided Transceiver Dual Band **Compact General-Coverage Receiver**  Wide Dynamic Range • General Coverage • Low Noise Front End • 10 Hz Digital Readout • All Mode Transceive CWISSBIAM/FM/FSK<sup>1</sup> General-Coverage Receiver USB/LSB/CW/AM/FM • Dual VFOs . WHE FM 144/430 MHZ Memory/Band Scan • Speech Processor • CW Filter and CW Keyer included 25 WATTS .... **ICOM ICOM** ICOM **ICOM** 45.27 1.5.5 IC-02AT CL-F The IC-02AT 2-meter ICD readout handheld features 10 memories 32 PL tones scanning keyboard frequency en-try dial lock. 3W std 5W opt DTMF IC-R71A General Coverage IC-745 HF Base IC-27A Compact Mobile A breakthrough in 2-meter mobile com-munications: Most compact on the market (51° - 11° - HA? - D) contains internal speaker for easy mounting 25 waits 32 PL trequencies 9 memories scanning and touchtone mic The IC-R71A 100KHz - 30 MHz superior All ham band HF transceiver, 16 memories, 100KHz to 30 MHz general coverage receiver, and adjustable noise blanker and AGC The IC-HTAL book and the set of t FLOYD ELECTRONICS OUR ASSOCIATE STORE IN THE 2213 VANDALIA COLLINSVILLE, ILL 62234 207 ST. LOUIS AREA CALL 618-345-6448 CALL FOR SPECIAL SALE PRICES MFJ BUTTERNUT HYGAIN AEA MICROLOG ASTRON CENTURION ICOM AVANTI MIRAGE CES KANTRONICS AZDEN SANTEC COMM SPEC KENWOOD B & W VANGORDON CUSHCRAFT KLM BEARCAT WELZ DAIWA LARSEN BENCHER HUSTLER YAESU 2900 N.W. VIVION RD. CALL TOLL 1-800-821-7323 FREE KANSAS CITY, MISSOURI 64150 MASTERCARD, VISA & C.O.D.'s WELCOME 816-741-8118

## **TOUCH-TONE DECODER SALE!**

### SSI-202P CMOS WE OVER PURCHASED

Our over supply can be your gain.

We've just got to try and get even so we are going to let our ham friends share in some of these great circuits, for a great price.

#### FEATURES

- · Central office quality
- · Band-splitting filters included on chip
- Single, low-tolerance, 5-volt supply
- Detects either 12 or 16 standard DTMF digits
- 18-pin DIP package

- · Output in either 4-bit hexadecimal code or binary coded 2 of 8. Use 74159 decoder for 1 of 16 output
- Uses inexpensive 3.579545-MHz color-burst crystal for reference (Radio Shack P/N 272-1310 \$1.69)
- · Excellent speech immunity

All you need is a color-burst XTAL from Radio Shack & 1 meg resistor to make a C.O. Quality Touch Tone decoder. SSI-202 is a 5V part and unlike the older 201 is TTL compatible and will directly interface to personal computers.

These won't last long and are limited to available supply, so HURRY!!

**INCLUDING SPECS. & SCHEMATICS** In Wash, add 7.9% sales tax R.M. FULLER CO.

902 Industry Dr., Seattle, WA 98188 1-800-626-6662



CREWAT THE TH L DYNAMICS IN

In Wash. Call (206) 575-8640

# The Problem Solver.

The RF Wattmeter Model 81000-A from Coaxial Dynamics, Inc. does more than provide accurate rf measurements. Testing of transmission lines, antennas, connectors, filters and related components can reveal unknown problems and assure optimum equipment performance. The 81000-AK Wattkit features this easy-to-read RF Wattmeter (pictured here), with its optional carrying case and an array of elements and

208



COAXIAI

IAMICS, INC

Industrial Parkway, Cleveland, OH 44135 • (216) 267-2233 le Ohio, WATS: (800) Coaxial, Telex: 980-630

an array of elements and accessories. Coaxial Dynamics elements can be purchased separately for purchased separately for use in other manufac-turer's Wattmeters. For more information on the 81000-A Wattmeter or any of the complete line of Coaxial Dynamics RF products and OEM com-ponents please contact Coaxial Dynamics, Inc.

> SEE US AT OUR BOOTH IN DAYTON

> > 209



#### new IC-735 HF transceiver

ICOM has announced the IC-735 ultra compact all-ham band HF transceiver and general coverage receiver, said to be the most compact and advanced HF SSB unit on the market. Measuring only 3.7 inches high by 9.5 inches wide by 9 inches deep, the IC-735 is suited for mobile, marine, or base station operation.

To enhance receiver performance, the IC-735 has built-in receiver attenuator and preamp. It also has a 105-dB dynamic range and a new low-noise phase locked loop for rock-solid reception.

The IC-735 features a large LCD readout and conveniently located controls that allow simple operation, even in the mobile environment. VOX controls, mic gain, and other infrequently changed controls are kept out of sight behind a hatch cover on the front panel of the radio, but are immediately accessible.



Other standard features included at no additional cost are: built-in FM, a 500-Hz CW filter (FL-32), an electronic CW keyer, an HM-12 scanning mic, FM/CW/LSB/USB/AM (TX and RX). 12 tunable memories with lithium memory backup, and both program and memory scan. Adjustable AGC, automatic SSB selection by band, an RF speech processor, and 12 volt operation are also standard. Output power is continuously adjustable up to 100 watts.

A new line of accessories, including the AT-120 automatic programmable antenna tuner and the PS-55 power supply, will also be available. The IC-735 is also compatible with most of ICOM's existing line of HF accessories.

The IC-735 will be available in May, 1985, and pricing will be announced the end of April. The IC-735 will be displayed at the Dayton Hamfest.

For additional information, contact ICOM America, Inc., 2380-116th Avenue, N. E., Bellevue, Washington 98004.

Circle /301 on Reader Service Card.

#### PV voltage regulators

Photocomm, Inc., of Scottsdale, Arizona, has announced new design features on its Power Control Series voltage regulators for photovoltaic applications. A removable printed circuit board has been incorporated to simplify servicing and repairs; spare boards can also be purchased separately. These regulators now have a 30-amp load handling capability that allows for up to 12 40-watt solar modules in parallel to be controlled simultaneously. This benefit helps to lower overall system cost by using fewer regulators.



Standard features include temperature compensation, low voltage disconnect, analog meter package, transient protection and adjustable voltage setpoints. The controller is housed in a NEMA 3R weather-proof enclosure. 12 and 24 volt units are available off the shelf; other voltage units (36, 48, and 120 volts) can be provided upon request. Special options include Array Power Diversion, Manual Array Switching and a Severe Environment Package.

For further information, contact Photocomm, Inc., 7735 E. Redfield Road, Scottsdale, Arizona 85260.

Circle #302 on Reader Service Card.

#### multi-mode tuning indicator

Get on frequency quickly and accurately with the new HAL SPT-1 "Spectra-Tune" multi-mode tuning indicator. The SPT-1 may be used in the following modes of operation: RTTY (high tones) and RTTY (low tones), Fascimile (FAX), Slow-Scan Television (SSTV) and Morse Code (CW).



The frequency spectra of the received signal is displayed on a calibrated linear 40-segment red LED bar graph. The front panel calibration control allows the selection of which 1000 Hz range

## Electronics Supply 1508 McKinney Houston, Texas 77010 Call for Quotes 713-658-0268

EQUIPMENT	-
KENWOOD - We stock the KENWOOD line in new products. The TS-711A 2 meter all mode.	
70cm, all mode and the TS-670 all mode to	v 40. 15. 10
and 6 meters. These new rigs match the T	5-4305 and
make beautiful additions to any shack. We	e also have
the new little hand-held rigs, the TH-21AT a	Ind TH41-AT
CALL FOR PRICES	
KENWOOD SWL R-2000, R-1000, R-600 & R-	
KENWOOD TS-930S and TS-430S ICOM 02AT	299 95
VAESU FT203R	CALL
MIRAGE AMPS	less 12%
DENTRON GLT1000 1KW PEP tuner	
ICOM R-71A	649 95
CES 510 SA SMART PAICH	349 95
CES 510 SA SMART PATCH	
	~
KENWOOD TR-260	UA
SPARE PB-26 BATTERY P	
EDEE with nurchase	
HMC-1 HEADSET \$19.95 with TR-2600A p	urchase
ACCESSORIES	
	114.95
	less 10%
VIBROPLEX	less 10%
HEIL SOUND	less 10%
DAIWA NEW METERS	CALL
GORDON WEST code tapes (great) HI-MOUND Keyer paddles	9.95
ALPHA DELTA MACC 8	1055 10%
ALPHA DELTA MACC-8 surge protector AMPHENOL	/1.45
831-7 coax tee	4 00
PL-259 831 SP	1 25
UG-176 reducer, RG8X/RG59	
4400 N mule 10 50-234	6.00
2900 BNC male to SO-239	4 00
8261 N male 83-10 RCA to SO 239	3.00 3.00
승규가 흔들 것은 것을 많이 안 가지 않는 것 않는 것 같아.	3 00
82-97 N female chassis ANTENNAS	0.00
BARKER & WILLIAMSON Antennas	less 10%
BUTTERNUT HF-2V 80 & 40 mtr BUTTERNUT HF-6V 80 thru 10	125 00
BUTTERNUT HE-6V 80 thru 10	125 00
BUTTERNUT accessories stocks	CALL
AEA ISOPOLE 144 HYGAIN	39.95 CALL
LARSEN	CALL
HUSTLER 6BTV VERTICAL	119.95
CUSHCRAFT A147-11	49.95
215WB NEW!! 2 mtr beam	79.95
AOP1 complete OSCAR Antenno	149.95
we have a large CUSHCRAFT inventory	2011
HUSTLER ANTECO 2mtr 5/8 mag mount	CALL 24.95
KLM KT34A	349.95
KLM is always in stock. large selection of H	
& WORLD CLASS	CALL
NEW	
WM. NYE MB-V-A TU	NER
3KW. rating, back lit meters,	
RMS reading to 3KW, better shield	ang,
higher voltage caps.	
LIST \$585.00 SALE \$	509.00
NEW! NEW! NEV	NI
1	
AEA CP-100 INTERF	ACE
IMPROVED FILTERING & FEAT	\$319.95
IMPROVED FILTERING & FEAT LIST \$369.95 SALE TRADE IN YOUR CP1 call for definition	\$319.95 alls
IMPROVED FILTERING & FEAT LIST \$369.95 TRADE IN YOUR CP1 call for defe USED AEA CP1	\$319.95
IMPROVED FILTERING & FEAT LIST \$369.95 TRADE IN YOUR CP1 call for defin USED AEA CP1 POLICIES: MASTERCARD - VISA - COD	\$319.95 alls 125.00
IMPROVED FILTERING & FEAT LIST \$369.95 SALE TRADE IN YOUR CP-1 call for defu USED AEA CP-1 POLICIES: MASTERCARD VISA - COD All prices FOB Houston, TX except as noted	\$319.95 alls 125.00 Prices sub-
IMPROVED FILTERING & FEAT LIST \$369.95 SALE TRADE IN YOUR CP1 call for def USED AEA CP4 POLICIES: MASTERCARD - VISA - COD All prices FOB Houston, TX except as noted ject to change without notice, subject to prio	\$319.95 alls 125.00 Prices sub- r sale Used
IMPROVED FILTERING & FEAT LIST \$369.95 SALE TRADE IN YOUR CP-1 call for defu USED AEA CP-1 POLICIES: MASTERCARD VISA - COD All prices FOB Houston, TX except as noted	\$319.95 alls 125.00 Prices sub- r sale Used
IMPROVED FILTERING & FEAT LIST \$369.95 TRADE IN YOUR CP1 call for definition USED AEA CP4 POLICIES: MASTERCARD - VISA - COD All prices FOB Houston. TX: except as noted ject to change without notice subject to prio gear sale price refunded if not satisfied. Text subject to sales tax.	\$319.95 alls 125.00 Prices sub- rices sub- ricele Used as residents 210
IMPROVED FILTERING & FEAT LIST \$369.95 TRADE IN YOUR CP1 call for definition USED AEA CP4 POLICIES: MASTERCARD - VISA - COD All prices FOB Houston. TX: except as noted ject to change without notice subject to prio gear sale price refunded if not satisfied. Text subject to sales tax.	\$319.95 alls 125.00 Prices sub- rices sub- ricele Used as residents 210
IMPROVED FILTERING & FEAT LIST \$369.95 TRADE IN YOUR CP1 call for definition USED AEA CP4 POLICIES: MASTERCARD - VISA - COD All prices FOB Houston. TX except as noted ject to change without notice subject to prio gear sale price refunded if not satisfied. Text	\$319.95 alls 125.00 Prices sub- rsale Used as residents 210
IMPROVED FILTERING & FEAT LIST \$369.95 SALE TRADE IN YOUR CP-1 call for definition USED AEA CP-1 POLICIES: MASTERCARD - VISA - COD All prices FOB Houston. TX: except as noted ject to change without notice subject to prio gear sale price refunded if not satisfied. Text subject to sales tax.	\$319.95 alls 125.00 Prices sub- rsale Used as residents 210

## COMPUTERIZE YOUR HAM SHACK THE EASY WAY

## Computer Programs for Amateur Radio

by Wayne Overbeck. N6NB and Jim Steffen, KC6A

Wouldn't you like to use one of the popular, inexpensive home computers to handle a variety of your Amateur Radio chores? N6NB and KC6A have come up with a host of valuable computer progams and background information which are just the ticket to help you computerize such duties as: logging, duping contest logs, awards record keeping, calculating Gray line and beam headings to name just a few examples. You can either enter the programs from the book by hand or you can buy the programs already loaded onto easy-to-use disks for the four most popular home computers: C-64, TRS-80, Apple II or the IBM-PC. In fact, the complete package of this 367 big, page book and program disk costs no more than many of the game programs that your kids are now using. Without a doubt, this is the real bargain in Amateur Radio software. See how much easier your home computer can make your hamming activities. © 1984 1st edition. 327 pages.


#### **Program Listing**

- 1) Demo MiniLogger
- 2) Data Base Mgmt. Logbook Radio Awards Data Base Setup Program for Awards Data Base Gridlocator
- 3) Latitude/Longitude Programs Data file Beamheading chart DX Display Sunrise Chart Grayline Sunrise Anywhere DX Checker
- Contest and Duping Dupechecker (& Print) General Contest Logger Field Day Logger Sweepstakes Logger Log Print
- 5) Antenna Programs Anterina Scaler Antenna Matching Evaluator Vertical Pattern Plotter
- 6) *To the Moon and Beyond* EME System Calculator Sky locator Moontracker

Program disks available for: IBM PC-DOS, Apple II (DOS 3.3), TRS-80 Model I and III and Commodore C-64.

HA-0657	Softbound	\$16.95
Program Disk Alone	(No documentation included)	\$19.95
HA-0657 with dick	SAVE \$6.95 -	\$20 05

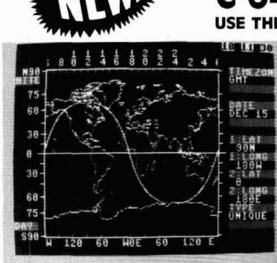(Please make sure you indicate which machine) (purchased separately \$36.95)



## C-64 + DX Edge = Fun

#### Now generate your own Grayline display.

Now that Commodore has reduced the price of the C-64 computer to \$150, there is little reason why you don't own one for your ham station. Xantek has adapted their best selling DX Edge to the computer world and it comes at a very reasonable price. Just \$34.95 brings into your ham shack the ability to know and predict when and where DX is going to appear. The DX Edge shows you the sun's path across the earth. When you are using the program, the computer will automatically update the information as the sun progresses across the face of the Earth. To make the computerized DX Edge even easier to use, the display is keyed to the DXCC list and the 40 CQ zones. Disk and documentation are just \$34.95. This is something you've **GOT** to have! ©1985.

🗆 XN-C64

\$34.95

Please enclose \$3.50 for shipping and handling. Prices U.S. Funds only.





from 300 Hz to 3000 Hz is to be displayed. Best of all, hookup is very simple — and audio input line from the receiver/transceiver and a  $\pm$  12 VDC line are all that's required for operation. The SPT-1 comes with a one-year limited warranty.

The SPT-1 Spectra Tune is priced at \$169.00. For more information, contact HAL Communications Corporation, P.O. Box 365, Urbana, Illinois 61801.

Circle #303 on Reader Service Card.

#### **KENPRO** rotator products

The KENPRO brand line of rotators and accessories — including the KR-400 and KR-500 pair of rotators for satellite and space communications — are now available from Encomm, Inc. Also available are the KR-600RC medium-duty and the KR-2000RC heavy-duty units for use on the U.S.A. voltage system.

For further details, contact Encomm, Inc., Suite 800, 2000 Avenue 'G', Plano, Texas 75074. Circle **/304** on Reader Service Card.

#### VHF and UHF transmitter and receiver modules

Hamtronics, Inc. recently announced commercial versions of its popular high-band and UHF FM transmitter and receiver modules, FCC Type Accepted under parts 15, 22, 74, and 90. The TA-51 VHF transmitter and the TA-451 UHF transmitter are each capable of operating at 2 watts continuous duty and up to 3 watts intermittent service. The companion R144 and R451 receivers feature high sensitivity and superior front-end and IF selectivity, automatic frequency control, and hysteresis squelch to lock onto drifting or fading signals.

The Hamtronics<sup>®</sup> transmitter and receiver modules are supplied as printed circuit board assemblies that can be housed in a variety of ways and adapted to many applications. The low-cost units are suitable for use in voice and data links to replace phone lines, for remote control, for wireless alarm systems, for telemetry, for monitor receivers, and for many other applications.

Other Hamtronics<sup>®</sup> products of interest include "202" type FSK modulators and demodulators to provide digital data operation with FM transmitters and receivers, low-noise receiver preamps, 806-MHz band scanner converters, VHF AM receivers, repeater CORs, CWIDs, simplex and duplex autopatches, DTMF control and many other products related to VHF and UHF transmission and reception.

For a copy of Hamtronics' new 40-page catalog, contact Hamtronics, Inc., 65-F Moul Road, Hilton, New York 14468-9535. (For overseas mailing, send \$2 or 4 IRCs.)





## **VOICE OPERATED SQUELCH**

- Fits inside most HF-SSB transceivers.
- Requires human voice to activate.
- · Ignores static, noise and hetrodynes.
- · On/off switch only-no adjustments!
- · Connects to audio leads and 9/12 VDC.
- · Fully assembled and tested \$99.95.
- · Complete with comprehensive manual.
- Used worldwide in commercial and military transceivers.

CMC COMMUNICATIONS, 5479 Jetport, Tampa, FL 33614 • (813) 885-3996

228

### Porta-Tenna

VHF/UHF Telescopic 1/4 & 5/8 Wavelength Antennas for Hand-Held Transceivers & **Test Equipment** 

#### 1/4 WAVELENGTH

Model No.	Freq. MHz	Description	Price
196-200	144-148	5/16-32 stud w/spring	\$5.95
196-204	**	BNC connector w/spring	7.95
196-214	**	BNC connector	6.95
196-224	144-UP	BNC conn. adj. angle	7.95
196-814	220-225	BNC connector	6.95

#### 5/8 WAVELENGTH

191-210	"	5/16-32 for old TEMPO	22.95
191-214	"	BNC connector	19.95
191-219	"	PL-259 w/M-359 adpt.	22.95
191-810	220-225	5/16-32 for old TEMPO	22.95
191-814		BNC connector	19.95
191-940	440-450	5/16-32 for HT-220	22.95
191-941	**	1/4-32 stud	22.95
191-944	**	BNC connector	19.95

Largest Selection of Telescopic Antennas. Write for Info. Prices are postpaid via UPS to 48 States. For air delivery via UPS Blue add \$2.25. Florida add 5% sales tax. Payment by M.O. or Cashiers Check only. × 212

products RF P.O. Box 33, Rockledge, FL 32955, U.S.A. (305) 631-0775

## ATTENTION **TECHNICIANS**

#### **Two-Way Radio Technician Wanted**

Trio-Kenwood Communications is seeking an experienced technician to service stateof-the-art Amateur Radio Communications equipment, HF-UHF. A qualified candidate should be currently experienced with PLL synthesizers, micro processors, transistorized RF, and must be able to service to the component level.

We have a well-equipped service shop and parts department. Our service manuals are acknowledged as the best in the industry. We offer a competitive, comprehensive benefits package. If you would like to work with the industry's pace setter, contact:

> Trio-Kenwood Communications Attn: Service Department

> **1111 West Walnut Street** Compton, CA 90220

> > KENWOOD

Base plates, flat roof mounts, hinged bases, hinged sections, etc., are not intended to support the weight of a single man. Accidents have occured because individuals assume situations are safe when they are not.

WARNING

SAVE YOUR LIFE OR AN INJURY


A NUM


Installation and dismantly ing of towers is dangerous and temporary guys of sufficient strength and size should be used at all times when individuals are climbing towers during all types of installations or dismantlings. Temporary guys should be used on the first 10' or tower during erection or dismantling. Dismantling can even be more dangerous since the condition of the tower, guys, anchors, and/or roof in many cases is unknown.

The dismantling of some towers should be done with the use of a crane in order to minimize the possibility of member, guy wire, anchor, or base failures. Used towers in many cases are not as inexpensive as you may think if you are injured or killed

Get professional, experienced help and read your Rohn catalog or other tower manufacturers' catalogs before erecting or dismantling any tower. A consulta-tion with your local, professional tower erector would be very inexpensive Insurance.

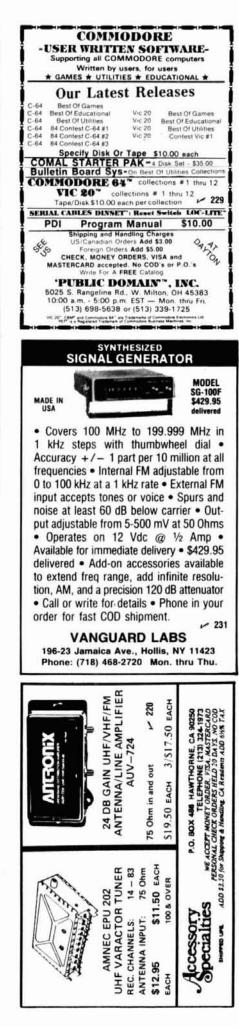Paid for By the Following: ROH P.O. Box 2000 Peoria, IL 61656



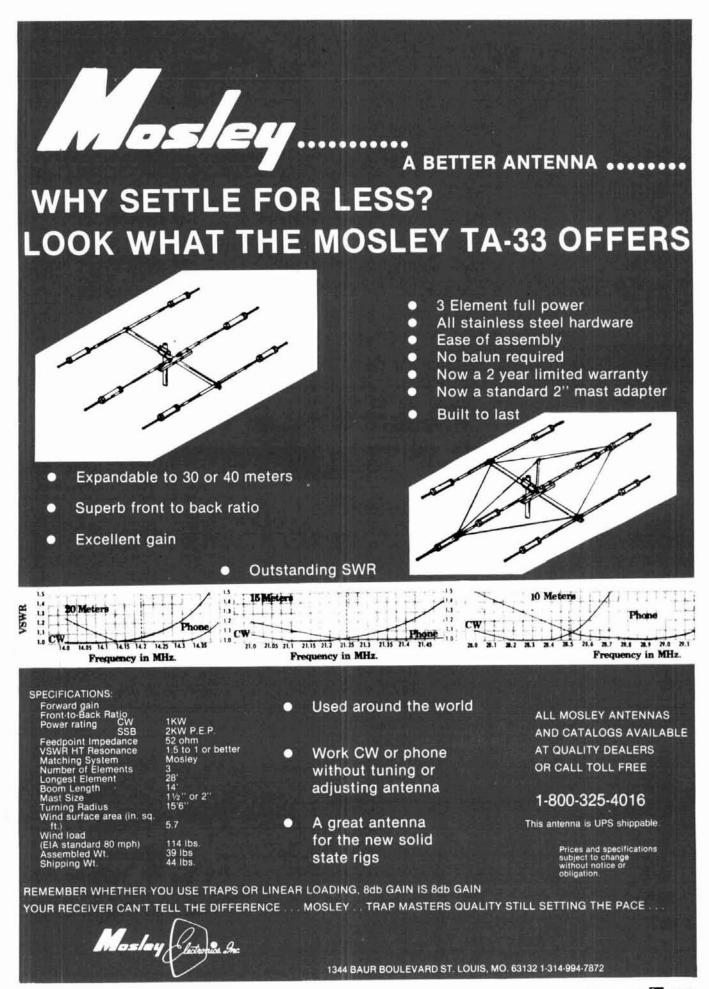

May 1985 161



### here is the next generation Repeater

MARK 4CR

No other repeaters or controllers match Mark 4 in capability and features. That's why Mark 4 is the performance leader at amateur and commercial repeater sites around the world. Only Mark 4 gives you Message Mastertm real speech • voice readout of received signal strength, deviation, and frequency error • 4channel receiver voting • clock time announcements and function control • 7helical filter receiver • extensive phone patch functions. Unlike others, Mark 4 even includes power supply and a handsome cabinet.

Call or write for specifications on the repeater, controller, and receiver winners.

SEE US AT DAYTON BOOTHS 225, 226 & 227

#### The only repeaters and controllers with REAL SPEECH!

Create messages just by talking. Speak any phrases or words in any languages or dialect and *your own voice* is stored instantly in solid-state memory. Perfect for emergency warnings, club news bulletins, and DX alerts. Create unique ID and tail messages, and the ultimate in a real speech user mailbox — only with a Mark 4.





## May the Morse Be With You

IC 02AT 2m HT, 10 Memories IC 04AT 440 HT/Touchtone

SWL RECEIVERS

220 MHz HT/Touchtone

IC 4AT 440 MHz HT/Touchtone 229 95

General Coverage Receiver

IC 290H 25-wt all-mode 2m XCVR 479.95

All-mode 2m Transceiver

63 

HF XCVR/Gen Cov RCVR

IC 751 HF XCVR/Gen Cov RCVR. 1179.00

M80 25-watt all-channel Scanner 387 26

**HF TRANSCEIVERS** 

Thursday

IC 2AT 2m HT/Touchtone

100KHz-30MHz

VHF/UHF

NEW IC 3200 2m/440

(3 335

00 0

With PS35 installed

M80C Commercial M80

New M5 all-channel HT

MARINE M12 12-ch Programmable HT

000

IC 271H 100-watt 2m XCVR

IC 27A 2m compact mobile

**B71** 

IC 271A

20 þ,

0

275.95

CALL

CALL

37.95

48.95

29./11

251/11

171/11

131/11

112.95

Call

for our

low prices

6

IC 745

LOOK FOR US AT ROCHESTER, NY

#### KENWOOD YAESU 🖸 ICOM HANDHELDS HF TRANSCEIVERS HF TRANSCEIVERS



NEW TS-940S HE Transceiver CALL With General Coverage Receiver

TS-930S HE Transceiver CALL With General Coverage Receiver

TS-430S HF Transceiver SUPER SPECIAL With General Coverage Reciever

TS 830S Transceiver CALL 160-10 Meter With Power Supply

TS-530SP 160-10 Meter XCVR CALL With Power Supply & Notch Filter

#### RECEIVERS

R-2000, R-600, R-1000, R-11 CALL General Coverage Receivers



TR-7950/7930 2-meter Mobile Units.	45	or	25	CAL Watts
TR-9130 2m All-mode.	25	Wa	itts	CAL
TS-711A/TS-811A				CAL
All-mode Tran 2m or 70cm mobile				ation

#### HANDHELDS

TR-2600A 2m FM Transceiver CALL With memories, LCD, scan

TH-21A 21AT/TH-41A 41AT CALL 2m/70cm Ultra-compact FM Transceiver

#### ANTENNAS

#### CUSHCRAFT

A3 3-element 10-15-20m	209	9
A4 4-element 10-15-20m	275	95
R3 10-15-20m Vertical	260	9
214B SSB/215WB FM 2m Boome	rs 75	9
ARX-2B 2m Ringo Ranger	35	.51
A3219 2m Boomer	89	9
KLM		
KT34A 4-element 10-15-20m	334	9
KT34XA 6-element 10-15-20m	479	9
2m-11X 11-element 2m	59	95
2m-16LBX 16-element 2m	91	95

#### MOSLEY

CL-33 3-element Triband Beam 265.95 TA-33 3-element 10-15-20m Pro 37 7-element 10-15-20m 239 95 465.95

#### HUSTLER

6-BTV 10-80m Vertical	with 30m	124.95
5-BTV 10-80m Vertical		104 95
MOBILE RESONATORS	Standard	Super
10 and 15 meter	10.95	16.95
20 meters	14 50	20.85
30 and 40 meters	16.95	22.95
75 meters	18 95	34.95

HY-GAIN (Limited Stock) 446.95 3915 TH70X 7-ele 10-15-20m 3935 TH5DX 5-ele 10:15:20m 386 95 395S Explorer 14 10-15-20m 304 95 Order Hy-Gain tower, Hy-Gain antenna, Hy Gain rotor - get tree shipping on all

#### MORE ANTENNAS

CALL AFA isopoles AVANTI HM 151 3G 2m on-glass 30.95 LARSEN LM-150 5/8 Mag Mount 38.95 MINIQUAD HO 1 139.95 RUTTERNUT HE6V 10-80m Vert 114.95 FOR OSCAR by Cushcraft & KLM CALL

#### FT 980 CAT System 1439.00 AC Power Supply, Full Break in CW SSB/AM/FM/FSK, Speech Processor SPECIAL 510.95 FT 77 with mic Compact HF XCVR A4444444444 TITITIT Ē 8ª ()

FT 757 HF XCVR with mic 769.95 with General Coverage RCVR includes CW keyer, AM/FM, CW filter

#### SWL RECEIVER NEW FRG 8800 SWL Receiver

Closeout 390.00 FRG 7700 Receiver Closeout 390.00 VHF Converters, Active Antennas available

#### HANDHELDS

FT 209RH 2m HT Intro Special 299.95 203 2m HT with TTP, VOX 229.95 FT 203 2m HT with VOX All accessories in stock 199 95

#### VHF/UHF

NEW FT 270RH 2m, 45-watt 379.95 Very small mobile rig NEW FT 2700HF 25-watt 519.95

Dual-band 2m and 440



FT 726R For 2m 770 05 (Optional modules for 6m 430 440 MHz) Great for Satellite Work

TOWERS

Guved foldover towers:

FK2558 58-feet, 25G FK4554 54-feet, 45G

Straight Sections:

206 Straight Section 256 Straight Section

45G Straight Section

HDBX40 Higher load with Base

HDBX48 Higher load with Base 375 95 Other BX, HBX, HDBX in stock

Other sizes at similar savings

Foldovers shipped freight paid 10% higher west of the Rockies

Complete Tower Packages CALL

- -

CABLE BY SAXTON

wire Rotator 2 #18, 6 #22

CABLEWAVE HARDLINE Call

RB213 Mil Spec RG8/U Foam 95% Shield

Mini 8 95% Shield

#### ACCESSORIES

M2 76-channel Synthesized HT

BENCHER PADDLES 37.95/47.95 Black/Chrome

		ASTRO	N POW	ER SUR	PPLY
Unarco-Ro	hn	RS7A	49.95	RS20M	104.95
Una CO-I i	21111	RS12A	69.95	RS35M	149.95
		RS20A	88.95	VS20M	124.95
Self-supporting towers:		RS35A	132.95	V\$35M	169.95
HBX40 40-teet with Base	219.95	RS50A	189.95	RS50M	209.95
HBX48 48 feet with Base	299.95	063/2023			
HBX56 56-feet with Base	379.95	AEA K	EYERS		

	THE FEITO
CK-2	Contest Keyer
MM-	2 Morsematic Keyer

#### TELEX HEADPHONES 99.95

Procom 450 Headset/Mic	49.95
MEIPRODUCTS	Call

1411 0	FRO	000	
Β&	w		

375 6-position Coax Switch 376 5-position Coax Switch 425 1 kW Low Pass Filter

DAIWA/MCM/J.W. MILLER 59.95/69.95 CN-520/CN-540 Meters CN-620B/CN-630 Meters 106.00/126.00 CN-720B 2kW HF Watt Meter 120.00 CNW-419 Antenna Tuner 500 W 174 95

#### AMPHENOL Connectors of all kinds in stock CALL

#### ROTATORS Alliance HD73 Kenpro KR500 Elevation Rotator



7	SANTE

CALL

309.95

199.95

629.95

CALL

732.95

319 95

599.00

270

759.95

1299.00

219.95

261.95

429.95

325.95

146 95

172.95

Call

22.50

22.50

25.50

94.95

à

E

ST 142 Handheld 249.95 STLC Leather Case with Strap 34.95 SM3 Speaker Mic 34 50 KDK

FM 2033 2m 25-walt 259.95



259 95 2591 2m Synth Handheid Century 22 CW XCVR 350.00 2510 Model B 410.95 Satellite Station for Oscar 10 999.95 CORSAIR Model 560 ARGOSY II 525D Digital 519.95 TRITON 425 HF Amp 1.5kW CALL

#### SCANNERS

#### REGENCY New MX4000 mobile 30-900 MHz Call HX1000 20-ch Handheld 215.95 New HX2000 Handheld 120-900 MHz Call

R1050 10-ch, 6-band Special 99 95 MX3000 30-ch, 6-band mobile 189 95 MX5000 20-ch 25-512 MHz cont 357 95

#### BEARCAT

259.95 260 16-ch mobile 201 16-channel/aircraft 179.95 2020 40-ch/aircraft 289.95 199.95 210XL 300 50-ch scanner/aircraft 347 00

#### SONY RECEIVERS

209 95 2002 SWI Receiver 4800 SWL Receiver 66.00 7500A SWI Receiver 139.95

#### AMPLIFIERS

TOKYO HY-POWER VHF & UHF amps CALL for Quotes

#### DAIWA

LA-2035 2m Amp, 2 in, 30 out LA-2035R 2m Amp with preAmp 74 95 MIRAGE

84 95

389.95

CALL

389 95

169.95

1399 95

B23A 2m Amplifier 2-30 B1016 2m Amplifier 10-160

242 95 83016 2m Amplifier 30-160 199.95 D1010N UHF Amp/N connectors 279 95 B215 2m Amp 2 in, 150 out 245 95 A1015 6m Amp 10 in 150 out 242 95

#### AMERITRON HF AMPS 580.05

AL84 HF Amp 160-15 AL1200 1.5 kW Amp
KENWOOD TL922 2kW

#### AMP SUPPLY

LA 1000A 160-15m Amp LK 500NT HF Amp no tune 1185 00 AT 1200A 1200 PEP Tuner

#### VOCOM AMPLIFIERS

69.95 2 watts in: 30 watts out 2m Amp watts in, 60 watts out 2m Amp 107 95 2 watts in: 120 watts out 2m Amp 169-95 200mW in: 30 watts out 2m Amp 84 95

ETO Alpha linear amps available Call

New VHF/UHF Amps from TE Systems with Low Noise GaAs FET Preamp **Call for Quotes** 

	6
APT 3100 Message Processor	2199.95
T 6000 RTTY Demodulator	620.95
T 2200 Communications Term	799.95
B 2100 Keyboard for CT 2200	145.95
WR 6850 Telereader	746.95
RI 100 RTTY/CW Interface	214.95
RI 200 RTTY/CW Interface	259.95

#### HARDWARE

MFJ 1224 with MFJ C-64/V-20	Soft 79.95
MFJ 1229	159.95
Kantronics Interface II	210.95
AEA CP-1 Interface	179.95

#### PACKAGES

179.95 Microlog AIR-1 Vic-20/C-64 AEA CP1 for Vic-20/C-64 AEA Microamfor Patch MAP-64 209.95 119.95

#### SOFTWARE Kantronics Hamtext

CALL Vic-20, C-64, Apple Kantronics Hamsoft/Amtor Vic-20, C-64, TRS-80 color, Atari 69 95

**Kantronics Hamsoft** Vic-20, Apple, Atari, TRS-80C, TI-99, CALL

#### Microlog Air Disk

Viç-20 and C-64 Disk Cartridge	39.95 56.95
AEA MBA Text Vic-20 or C-64	79.95
MBA-tor 64	89.95
Marstext Vic-20 or C-64	79.95

Dr. DX by AEA 99.95

HAM	Amateur Sof for the VIC-2 Commodore	0 and
BAIN	TAPE	DISK
Contest Log	18.95	29.95
Antenna Design	9.95	12.95
Computer Morse	9.95	12.95

Antenna Design	9.95	12.9
Computer Morse	9.95	12.95
Propagation Chart	18.95	21.9
Super Log IV		23.9

## inc

13646 Jefferson Davis Highway Woodbridge, Virginia 22191 Information & Service (703) 643-1063 Store Hours MTT 10 a.m. - 6 p.m. WF 10 a m - 8 p m

Sat 10 a m -4 p m


Order Hours: M-F 9 a.m. -7 p.m. Saturday 10 a.m -4 p.m.

Send 3 22\* stamps for a flyer Dealer Inquines Invited



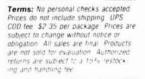Our associate store Davis & Jackson Road, P O Box 293 Lacombe Louisiana 70445 Information & Service: (504) 882-5355







For Orders and Quotes Call Toll Free: 800-336-4799 Virginia Orders and Quotes Call Toll Free: 800-572-4201



## a busy signal from space

For over twenty-five years various nations have been launching satellites of one type or another. Many of the early satellites were experimental in nature, primarily intended to develop and test space hardware. However, the past fifteen years have been devoted to the more utilitarian aspects of space. Because our only link to satellites has been through RF paths, the amount of the spectrum devoted to this purpose has grown dramatically.

The geosynchronous equatorial orbits are particularly popular. This is because satellites placed in this position appear to remain in one place all the time, and can illuminate a large portion of the earth's surface. Because of the desirability of this location, it has become imperative that there be global cooperation with respect to the placement of satellites in the general equatorial area. Current agreements allow satellites to be positioned every 2 degrees over the populous equatorial coverage areas.

The resulting proliferation in the number of equatorial satellites puts a significant burden on antenna designers. The 2- degree equatorial spacing requires that antennas have very narrow beams, in addition to low sidelobes, in order to prevent interference to transponders on adjacent satellites. The transmitters and receivers used in these satellites are very sophisticated, and must utilize adaptive techniques in order to maintain predetermined signal-to-noise ratios without interference problems.

The RF spectrum assigned to satellites includes band segments from 400 MHz to over 30 GHz. The most densely used portions are in the region between 1.5 and 12.5 GHz. Because of the limited availability of electric power, satellite transmitters tend to be limited to about 50 to 100 watts, but antenna gains of 20 dB or more are not uncommon. Obviously, satellites intended to provide broad geographic coverage cannot employ highly directive antennas. Some key applications for modern satellites include the following:

Earth resources and position location. Most of us have seen some of the dramatic photographs taken from earth resources satellites showing crops, earthquake faults, volcanoes, and of course, daily weather patterns. These satellites rely on a wide variety of sensors employing optical, thermal, and radar techniques to form images of the earth's surface. In most cases the resolution is sufficient to reveal major highways, airports, and other key land-based features.

Most of these satellites operate in the 137 MHz and 1.6 GHz portions of the spectrum. Fairly simple receiving equipment will permit the home experimenter to receive exciting weather photographs from the APT and GOES satellites.

An important additional function of this general class of satellites is mapping and position location. Virtually any satellite with high resolution sensors can function as an excellent mapping satellite since its orbit can be precisely determined and its position accurately known at any given time. Twenty continuous years of this process has resulted in highly accurate mapping of the earth's entire surface, permitting significant improvements in the efficiency and safety of commercial shipping and aviation. A series of Global Positioning Satellites (GPS) is being developed by the United States; when its 18 satellites are completed and in place a few years from now, the signals from these satellites will enable appropriately equipped vessels to determine their exact position on the earth's surface to within about 100 feet (30 meters).

**Telecommunications**. It is the telecommunications function performed by modern satellites with which most of us are familiar. Telephone communications, data transmission, video links, and broadcast television now unite the world in a massive satellitelinked network. Satellites designed for this purpose do not originate signals, but are simply repeaters in the sky. They typically consist of a number of channels, called "transponders," that repeat signals in a 24 or 36 MHz band.

#### **ADVERTISER'S INDEX AND READER SERVICE NUMBERS**

Listed below are the page number and reader service number for each company advertising in this issue. To get more information on their advertised products, use the bind-in card found elsewhere in this issue, select the correct reader service number from either the ad or this listing, check off the numbers, fill in your name and address, affix a postage stamp and return to us. We will promptly forward your request to the advertiser and your requested information should arrive shortly. If the card is missing, send all the pertinent information on a separate sheet of paper to: *ham radio* magazine, Attn: Reader Service, Greenville, NH 03048.

READER	SERVICE / PAGE /
	Accessory Specialties
	Advanced Computer Controls
	Advanced Receiver Research
	AEA
	All Electronics
	Alliance Mfg. Co
	Alpha Delta Communications
	Alpha Deta Communications
	Amateur Electronic Supply
	Amateur-Wholesale Electronics
	American Radio Relay League141
	Amidon Associates
	Azotic Industries
	Barker & Williamson
	Barry Electronics
	Base 2 Systems
	B.G. Micro
	Birch Hill Sales
	Britt's 2-Way Radio 50
	Buckmaster Publishing124
	Butternut Electronics
110 -	C & A Roberts 10
	Caddell Coil Corp 80
215 -	Cayson Electronics
150 -	CeCo
105 -	CES 1
228 -	CMC Communications
	Coaxial Dynamics, Inc
	Communications Concepts, Inc
	Communications Specialists
	Computer Trader Magazine
	Connect Systems
	Courage Center
	Dalbani Corp
	Digimax Instrument Corp
	Doppler Systems
	Dokay Computer Products, Inc122, 123
	Dynetic Systems163
	EGE
	Electro-Com
176 -	Electronic Equipment Bank
	Encomm, Inc 76, 77
* -	Engineering Consulting152
····· • ·	Epsilon
172 -	Fair Radio Sales
207 -	Floyd Electronics
	John Fluke Manufacturing Co., Inc
	Fox Tango Corp
	R.M. Fuller Co
	Gem Quad Products
	G.I.S.M.O
	GLB Electronics
	Gus Browning's DX'ers Magazine
	Hal-Tronix
	Ham-Com
	Ham Radio's Bookstore74, 124, 130, 142, 145, 152, 153, 158
	Ham Radio Outlet
	The Ham Station
	Hamtronics
	Harrison Radio
	Henry Radio
	Hustler, Inc
	ICOM America, Inc
	ICOM America, Inc
	Indianapolis Hamfest
	Jensen Tools, Inc
	Jun's Electronics
	Kantronics
	Trio-Kenwood Communications
	160, Cover IV
167 -	Larsen Electronics
	MFJ Enterprises

READER SERVICE	PAGE /
202 - MHz Electronics	146-151
210 - Madison Electronic Supply	
147 - Martin Engineering	80
186 - Merrimac Satellite	
185 - John J. Meshna, Jr., Co., Inc	137
222 - Micro Control Specialties	162
177 - Microwave Filter, Inc.	134
207 - Missouri Radio Center	155
183 - Morning Distributing	136
206 - Mosley Electronics, Inc	154, 161
175 · Nampa Satellite Systems	
179 - NCG	
174 - Nemal Electronics	130
159 - North America Soar Corp	
178 - Nuts & Volts	
* - Oak Hill Academy ARS	
149 - Omega Concepts	
184 - Orbit Magazine	136
171 - Paullin Industries	124
126 - P.C. Electronics	
168 - P.C. Electronics	50, 112
151 - Phillips-Tech Electronics	82
121 - Photocomm, Inc	40
195 - Processor Concepts	
229 - Public Domain	
191 - Radio Amateur Callbook	
198 - Radiokit	143
205 - Radio School	
* - Radio Warehouse	
112 - RAG Electronics, Inc	14, 15
125 - Ramsey Electronics	45
212 - RF Products	
143 - RND Design Corp	
108 - Robot Research, Inc	8
146 - Roensch Microwave	80
164 - Sartori Associates	105
187 - Satellite TV Magazine	
117 - Shure Brothers, Inc	33
165 - SIBEX	
193 · South Midlands Communications, Ltd	142
* · SPACE/STTI Tulsa Show	126
188 - Spec-Com	139
123 - Spectrum International	
162 - Spi-Ro Distributing	104, 143
169 - Tel-Com	
134 · Telewave, Inc	
154 - Texas Towers	
221 - TNT Radio Sales	
201 - Transleteronic, Inc	
* - UNR-Rohn	
166 - Unity Electronics	
* - University Microfilms International	
231 - Vanguard Labs	
113 - Varian/Eimac	
128 - Vector Radio	
137 - VHF Communications	
160 - VHF Communications	
192 - The VHF Shop	
182 · James Walter Test Equipment	
139 - Westcom Engineering	
200 - Western Electronics	
196 - Wheeler Applied Research Labs	
194 - WSINN	
214 · Yaesu Electronics Corp	
· · · · · · · · · · · · · · · · ·	. Gover III

#### PRODUCT REVIEW/NEW PRODUCT

304 - Encomm, Inc	159
303 · HAL Communications Corp	159
118 - Hamtronics, Inc	159
301 - ICOM America, Inc	157
302 - Photocomm, Inc	157

Each satellite can have as many as ten transponders. This means that a single satellite may handle as many as 50,000 phone calls simultaneously. The availability of these high quality RF links has dramatically improved intercontinental voice and data communications. These links can now reliably transmit a page of FAX data to another part of the world in just a few seconds. Satellites enable commercial broadcasters to bring us important events from virtually every corner of the earth as they occur; the societal ramifications of this news immediacy are still developing.

Defense. Not to be upstaged, the military establishments have also been busy in space. Since profitability, in the commercial sense, is not an issue for military users, some of the tasks which satellites are called upon to perform are indeed exotic. These include such things as very high-speed data links (1 Gbit/sec.) and very high resolution imagery for reconnaissance purposes. Charged coupled sensors, cooled with liquid helium to increase sensitivity and mounted at the focal plane of precision lenses, provide orbital images with stunning detail. The ability of radar to penetrate cloud coverage and provide high resolution images is particularly attractive to military users. In some cases, the orbital path of the satellite is used to synthesize an antenna of large aperture and provide a simulated very narrow beam. This technique, called "synthetic aperture radar" (SAR), is capable of revealing subtle details, not visible by any other means, hidden in the earth's surface. Techniques of this type are used by defense organizations to locate submarines concealed below the ocean's surface.

Next time you look at the evening sky, be sobered by the thought that at that very instant, there are probably more conversations being repeated through satellites than if all the world's Amateurs were on the air at the same time. The pros do it without QRM. Now *that's* what I call a band plan!

#### \*Please contact this advertiser directly.

Please use before June 30, 1985.

Limit 15 inquiries per request.

ham radio

## THE STANDARD OF EXCELLENCE

#### The world of CW, RTTY, and new DUAL AMTOR\* is as close as your fingertips with the new brilliantly innovative state-of-the-art microcomputer controlled EXL-5000E.

Automatic Sender/Receiver: Due to the most up to date computer technology, just a console and keyboard can accomplish complete

technology, just a console and keyboard can accomplish complete automatic send/receive of Morse Code (CW), Baudot Code (RTTY), ASCII Code (RTTY) and new ARQ/FEC (AMTOR). Code: Morse (CW includes Kana), Baudot (RTTY), ASCII (RTTY), JIS (RTTY), ARQ/FEC (AMTOR). Characters: Alphabet, Figures, Symbols, Special Characters, Kana. Built-in-Monitor: 5 " high resolution, delayed persistence green moni-tor — provides sharp clear image with no jiggle or jitter even under fluorescent lighting. Also has a provision for composite video signal mutout.

Time Clock: Displays Month, Date, Hour and Minute on the screen. Time/Transmission/Receiving Feature: The built-in timer enables completely automatic TX/RX without operator's attendance. Selcal (Selective Calling) System: With this feature, the unit only re-Selective Calling) System: With this feature, the unit only re-ceives messages following a preset code. Built-in Demodulator for High Performance: Newly designed high speed RTTY demodulator has receiving capability of as fast as 300 Baud. Three-step shifts select either 170Hz, 425Hz or 850Hz shift with manual fine tune control of space channel for odd shifts. HIGH (Mark Frequency 2125Hz)/LOW (Mark Frequency 1275Hz) tone pair select. Mark only or Space only with the control of the copy capability for selective fading. ARQ/FEC features incorporated. Crystal Controlled AFSK Modulator: A transceiver without FSK function can transmit in RTTY mode by utilizing the high stability crystal-controlled modulator controlled by the computer. Photocoupler CW, FSK Keyer built-in: Very high voltage, high current photocoupler keyer is provided for CW, FSK keying.

Convenient ASCII Key Arrangement: The keyboard layout is ASCII arrangement with function keys. Automatic insertion of LTR/FIG code makes operation a breeze.

Battery Back-up Memory: Data in the battery back-up memory, covering 72 characters × 7 channels and 24 characters × 8 channels, is retained even when the external power source is removed. Messages can be recalled from a keyboard instruction and some particular channels can be read out continuously. You can write messages into any channel while receiving.

Large Capacity Display Memory: Covers up to 1,280 characters. Screen Format contains 40 characters × 16 lines × 2 pages. Screen Display Type-Ahead Buffer Memory: A 160-character buffer

memory is displayed on the lower part of the screen. The characters move to the left erasing one by one as soon as they are transmitted. Messages can be written during the receiving state for transmission with baftery back-up memory or SEND function.

Function Display System: Each function (mode, channel number, speed, etc.) is displayed on the screen.

Printer Interface: Centronics Para Compatible interface enables easy connection of a low-cost dot printer for hard copy.

Wide Range of Transmitting and Receiving: Morse Code transmitting speed can be set from the keyboard at any rate between 5-100 WPM (every word per minute). AUTOTRACK on receive. For communica-tion in Baudot and ASCII Codes, rate is variable by a keyboard instruction between 12-300 Baud when using RTTY Modem and between 12-600 Baud when using TTL level. The variable speed feature makes the unit ideal for amateur, business and commercial use.

Pre-load Function: The buffer memory can store the messages written from the keyboard instead of sending them immediately. The stored

"RUB-OUT" Function: You can correct mistakes while writing messages in the buffer memory. Misspellings can also be erased while the information is still in the buffer memory

Automatic CR/LF: While transmitting. CR/LF automatically sent 64, 72 or 80 characters

WORD MODE operation: Characters can be transmitted by word groupings, not every character, from the buffer memory with keyboard instruction

LINE MODE operation: Characters can be transmitted by line group-ings from the buffer memory.

WORD-WRAP-AROUND operation: In receive mode, WORD-WRAP-AROUND prevents the last word of the line from splitting in

two and makes the screen easily read. "ECHO" Function: With a keyboard instruction, received data can be read and sent out at the same time. This function enables a cassette tape recorder to be used as a back-up memory, and a system can be created just like telex which uses paper tape

Cursor Control Function: Full cursor control (up/down, left/right) is available from the keyboard. Test Message Function: "RY" and

"QBF" test messages can be repeated with this function. MARK-AND-BREAK (SPACE-AND-BREAK) System: Either mark

or space tone can be used to copy RTTY. Variable CW weights: For CW transmission, weights (ratio of dot to dash) can be changed within the limits of 1:3-1:6.

Audio Monitor Circuit: A built-in audio monitor circuit with an automatic transmit/receive switch enables checking of the transmitting and receiving state. In receive mode, it is possible to check the output of the mark filter, the space filter and AGC amplifier prior to the filters.

EE

nee.

T

**CW Practice Function:** The unit reads data from the hand key and displays the characters on the screen. CW keying output circuit works according to the key

operation. CW Random Generator: Output of CW random signal can be used as CW reading practice. Bargraph LED Meter for Tuning: Tuning of CW and RTTY is very easy with the bargraph LED meter. In addition, provision has been made for attachment of an oscilloscope to aid tuning

Built-in AC/DC: Power supply is switch-able as required; 100-120 VAC; 220-240 VAC/50/60Hz + 13:8VDC

Color: Light grey with dark grey trim matches most current transceivers. Dimensions: 363(W) × 121(H) × 351(D) mm: Terminal Unit. Warranty: One Year Limited Specifications Subject to Change


Everything built in - nothing else to buy!

T

FOR YOUR NEAREST DEALER OR TO ORDER: EXCLUSIVE DISTRIBUTOR: DEALER INQUIRIES INVITED TOLL FREE . . . 800-327-3102 AMATEUR-WHOLESALE ELECTRONICS Telephone (305) 233-3631 8817 S.W. 129th Terrace, Miami, Florida 33176

#### **MasterCan** VISA

### Telex: 80-3356

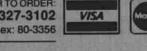

#### MANUFACTURER:

TONO CORPORATION

98 Motosoja Machi, Maebashi-Shi, 371, Japan

\*Dual Amtor: Commercial quality, the EXL-5000E incorporates two completely separate modems to fully support the amateur Amtor codes and all of the CCIR recommendations 476-2 for commercial requirements.



# Eureka!

We just struck gold with a miniature, high quality and very reliable DTMF decoder at a rock bottom price of \$59.95. Our DTD-1 will decode 5040, 4 digit codes with the security of wrong digit reset. It contains a crystal controlled, single chip DTMF decoder that works great in bad signal to noise environments and provides latched and momentary outputs. Why carry that heavy gear when its size is only 1.25 x 2.0 x .4 inches and it comes with our etched in stone, legendary, one year warranty.

Instead of sifting through the field...searching, use our super quick one day delivery and cash in on a rare find.

#### \$59.95 each





## Presenting two small cases for a lot of mobile power.

You won't find a 45-watt. 2-meter FM mobile rig that's built smaller than the Yaesu FT-270RH.

Nor will you find a dual-band FM mobile that offers the crossband full-duplex capability found in the 25-watt Yaesu FT-2700RH.

It shouldn't be surprising. We've been coming up with a lot of innovative concepts lately.

The FT-270RH measures just 2 x 6 x 7 inches. Conveniently fitting its high-power punch into many small spaces of your car. Places where other 45-watt mobiles just won't fit.

The FT-2700RH is small too. Smaller than other dual-banders. But with one big difference: a "DUP" button. Push it, and you're operating full duplex, 2 meters on one VFO, 440 MHz on the other. Each at 25 watts. So you can simultaneously transmit and receive in true telephone style.

Once installed, you'll find the FT-270RH and the FT-2700RH equally simple to operate. Just turn the rig on, dial up a frequency, select offset or duplex split, and you're on the air.

Each rig gives you 10 memories for storing your favorite frequencies. Dual VFO capability: A clean, uncluttered LCD display for easy readout. Push-button jumps through the band in 1 MHz steps. Band scanning with programmable upper and lower limits. And priority channel operation.

You don't even have to take your eyes off the road to determine your operating frequency and memory channel. An optional voice synthesizer announces them both at the push of a button on the microphone. The FT-2700RH announces both your 2-meter and 440 MHz operating frequencies.

Also, tone encode and encode/ decode capability is programmable from the front panel, using an optional plug-in board.

So when you need a lot of power in a compact mobile radio, discover Yaesu's FT-270RH and FT-2700RH. There's nothing else like them on the road.



Yaesu Electronics Corporation 6851 Walthall Way: Paramount, CA 90723 (213) 633-4007

Yaesu Cincinnati Service Center 9070 Gold Park Drive, Hamilton, OH 45011 (513) 874-3100

Prices and specifications subject to change without notice.  $\checkmark$  214



## KENWOOD

... pacesetter in Amateur radio

# "DX-cellence!"

## 5-94(

The new TS-940S is a serious radio for the serious operator. Superb interference reduction circuits and high dynamic range receiver combine with superior transmitter design to give you no-nonsense, no compromise performance that gets your signals through! The exclusive multi-function LCD sub display graphically illustrates VBT, SSB slope, and other features.

- 100% duty cycle transmitter. Super efficient cooling system using special air ducting works with the internal heavy-duty power supply to allow continuous transmission at full power output for periods exceeding one hour.
- Programmable scanning.
- Semi or full break-in (QSK) CW.

- . Low distortion transmitter. Kenwood's unique transmitter design delivers top "quality Kenwood" sound.
- Keyboard entry frequency selection. Operating frequencies may be directly entered into the TS-940S without using the VFO knob.
- Graphic display of operating features.
- Exclusive multi-function LCD sub-display panel shows CW VBT, SSB slope tuning, as well as frequency, time, and AT-940 antenna tuner status.
- QRM-fighting features. Remove "rotten QRM" with the SSB slope tuning, CW VBT, notch filter, AF tune, and CW pitch controls.

Optional accessories:

9 40

SL OPE

ANTENNA

AUTO TUNE

U-A

21:00off 0:00

.250.00

14.200.01

115

115

TUNER

READY

- AT-940 full range (160-10 m) automatic antenna tuner · SP-940S external speaker with audio filtering • YG-455C-1 (500 Hz), YG-455CN-1 (250 Hz), YK-88C-1 (500 Hz) CW filters; YK-88A-1 (6 kHz) AM filter • VS-1 voice synthesizer • SO-1 temperature
  - compensated crystal oscillator • MC-42S UP/ DOWN hand mic.

NEW

- MC-60A, MC-80, MC-85 deluxe base station mics.
- PC-1A phone patch
- TL- 922A linear amplifier
- SM-220 station monitor

TUNE

- BS-8 pan display SW-200A and
- SW-2000 SWR and

power meters.

20005 AF TUN H A/1

> SPLIT Att LOCK VOICE

- · Built-in FM, plus SSB, CW, AM, FSK.
- . High stability, dual digital VFOs. An optical encoder and the flywheel VFO knob give the TS-940S a positive tuning "feel."
- · 40 memory channels. Mode and frequency may be stored in 4 groups of 10 channels each.
- · General coverage receiver.
  - Tunes from 150 kHz to 30 MHz.



Complete service manuals are available for all Thio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

More TS-940S information is available from authorized Kenwood dealers.



TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220