



ICOM MICRO THE WINNING HAND

Deal yourself a winning hand in modern technology with ICOM's new micro-size 2-meter FM transceiver. The IC- μ 2AT combines maximum performance, reliability and easy operation in a thin-styled handheld that's perfectly suited for today's active lifestyles.

The IC-µ2AT. A breakthrough that ends every amateur radio operator's quest for that one true, go-anywhere 2-meter handheld.

Miniaturization. The MICRO gives you all the advantages and performance of a larger handheld, in a package so small, so refined, so well-built that only ICOM could build it.

Measuring only 4.6" high by 2.3" wide by 1.1" deep, the MICRO fits in your pocket or purse as easily as a cassette tape.

This miniaturization doesn't compromise ICOM quality. It's exactly what you'd expect from ICOM: high performance in a micro package.

Full Featured. And ICOM hasn't compromised features for size. The IC-µ2AT DTMF version includes ten



programmable memories, transmit offset capability from the back panel including odd offsets, an LCD readout on the top panel for easy readability, up to three watts of output (optional), 32 built-in subaudible tones AND wideband receive coverage from 138 to 162.995MHz in 5kHz steps for MARS and CAP operation plus weather broad casts.

There's also a simple-to-use digital **TouchStep Tuning System** for fast shirt-pocket frequency adjustments. The MICRO also includes a band or memory manual scan function. An A version is also available without DTMF and PL tones.

Personalize your ICOM MICRO. The MICRO utilizes most existing ICOM handheld accessories, plus it hosts a new line of versatile accessories including the BP-24 2.6 watt high-power battery pack, BP-23 long-life 1.6 watt battery pack, BC-50 desktop rapid charger, and a variety of carrying cases.

See the ICOM MICRO at your local ICOM dealer. Play your cards right with ICOM!



ICOM America, Inc., 2380-116th Ave. N.E., Bellevue, WA 98004 Customer Service Hotline (206) 454-7619 3150 Premier Drive, Suite 126, Irving, TX 75063 / 1777 Phoenix Parkway, Suite 201, Atlanta, GA 30349 ICOM CANADA, A Division of ICOM America, Inc., 3071 - #5 Road, Unit 9, Richmond, B.C. V6X 2T4 Canada All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. #24738*

Our Numbers Are Growing

Kantronics TUs & TNCs

UTU" UTU transmits/receives CW 6-99 WPM; RTTY 60, 67, 75, 100, and 132 WPM; ASCII 110, 150, 200, and 300 baud; and AMTOR modes A, B, and L. UTU features switched capacitance filters, and a ten-segment LED bargraph for extra easy tuning. Suggested Retail \$189.95.

UTU-XT/P" now operates HF PACKET along with CW 6-99 WPM, RTTY from 45-300 baud, ASCII from 110-300 baud, and AMTOR modes A, B and L. UTU-XT/P features user programmable parameters, such as MARK/SPACE tones, multiple RITTY shifts, and limiter/limiterless operation. UTU-XT/P utilizes a 6303 microcomputer, 8K RAM, NOVRAM, and 128K EPROM Suggested Retail \$289.95.

KAM[™] The Kantronics designed All Mode unit operates HF and VHF packet; CW 6-99 WPM; RTTY/ ASCII 45-300 baud; and AMTOR modes A, B, and L. KAM features HF and VHF radio ports; simultaneous HF and VHF packet connects and digipeating; HF/VHF gateway; bargraph tuning; and user programmable parameters, such as MARK/ SPACE. KAM's separate CW demodulator is also center

frequency and bandwidth programmable. Suggested Retail \$319.00.

KPC-2400TM Fully compatible with all other TNCs, the KPC-2400 includes all the features of KPC-2 plus 2400 bps packet. KPC-2400 operates at 300, 1200, and 2400 bps, software selectable. Suggested Retail \$329.00. Kantronics has also designed the 2400 TNC Modem* for TNC-1s and TNC-2s. This add-on modem adds 2400 bps packet, while retaining 1200 bps

operation. Suggested Retail \$149.00.


KPC-2™ This Kantronics designed AX.25 version 2 TNC features a built-in HF and VHF modem, full duplex operation, and multiple connects. The enhanced generic command structure fits any computer. KPC-2 includes 128K EPROM, 16K RAM expandable to 32K, and 4K EEPROM. Suggested Retail \$169.00.

Kantronics Terminal Programs

Pacterm/UTU-Term™ for IBM and compatibles, C-64, 128; TRS III, IV, IV/P. Operates KPC-2 KPC-2400, KAM, UTU-XT/P, and UTU. Disk \$19.95. Cartridge \$24.95, IBM disk \$29.95.

107

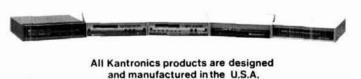Call or write Kantronics for a free catalog.



And There Are Good Reasons Why

Features and Support - Just a couple of reasons why so many amateurs are choosing Kantronics.

Take our packet units. Only Kantronics TNCs have always included the HF modem as standard

equipment. And only Kantronics offers high-speed 2400 bps packet. Our RS-232/TTL jumper makes all Kantronics "SMART" TUs and TNCs universally compatible. You won't need special interfacing for Commodores when you choose Kantronics.

Kantronics prices are compatible too! Check and see.

And what about support? --Kantronics full-time customer support departments have earned a reputation of excellence. From the time we answer your first call, our goal is to get you, and keep you on the air.

By providing updates and enhancements, Kantronics keeps you current too - like our 2.0 update.

Over 80% of our original Packet Communicator owners stayed current by updating to version 2.0.

We support our customers, and our products. And that's why **Our Numbers Are Growing.**



1202 E. 23rd Street Lawrence, Kansas 66046 (913) 842-7745

KENWOOD

... pacesetter in Amateur radio

"DX-cellence!"

TS-940S

The new TS-940S is a serious radio for the serious operator. Superb interference reduction circuits and high dynamic range receiver combine with superior transmitter design to give you no-nonsense, no compromise performance that gets your signals through! The exclusive multi-function LCD sub display graphically illustrates VBT, SSB slope, and other features.

- 100% duty cycle transmitter. Super efficient cooling system using special air ducting works with the internal heavy-duty power supply to allow continuous transmission at full power output for periods exceeding one hour.
- High stability, dual digital VFOs. An optical encoder and the flywheel VFO knob give the TS-940S a positive tuning "feel."
- Graphic display of operating features.
 - Exclusive multi-function LCD sub-

display panel shows CW VBT, SSB slope tuning, as well as frequency, time, and AT- 940 antenna tuner status.

- Low distortion transmitter. Kenwood's unique transmitter design delivers top "quality Kenwood" sound.
- Keyboard entry frequency selection. Operating frequencies may be directly entered into the TS-940S without using the VFO knob.
- QRM-fighting features. Remove "rotten QRM" with the SSB slope tuning, CW VBT, notch filter, AF tune, and CW pitch controls.
- Built-in FM, plus SSB, CW, AM, FSK.
- Semi or full break-in (QSK) CW.
 40 memory channels. Mode and frequency may be stored in 4 groups of 10 channels each.
- Programmable scanning.
- General coverage receiver. Tunes from 150 kHz to 30 MHz.


 1 yr. limited warranty. Another Kenwood First!
 Optional accessories:
 AT-940 full range (160-10m) automatic antenna tuner

 SP-940 external



Conputer Interface

speaker with audio filtering * YG-455C-1 (500 Hz), YG-455CN-1 (250 Hz), YK-88C-1 (500 Hz) CW filters; YK-88A-1 (6 kHz) AM filter * VS-1 voice synthesizer * SO-1 temperature compensated crystal oscillator * MC-43S UP/DOWN hand mic. * MC-60A, MC-80, MC-85 deluxe base station mics. * PC-1A phone patch * TL- 922A linear amplifier * SM-220 station monitor * BS-8 pan display * SW-200A and SW-2000 SWR and power meters.

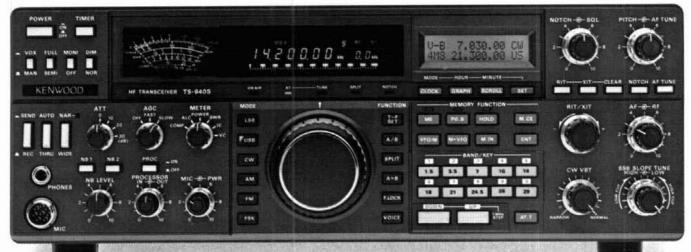

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to

change without notice or obligation.



More TS-940S information is available from authorized Kenwood dealers.

KENWOOD

TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220



contents

- 8 two-element hf beams: Les Moxon, G6XN
- 35 homebrew antenna mount Howard A. Bowman, W6QIR
- 42 Yagi triangular array John C. Cichowski, W2KIP
- 55 ham radio techniques: an inexpensive base station antenna for 2 meters Bill Orr, W6SAI
- 69 a no-compromise, multiband, low-VSWR dipole Maurice C. Hately, GM3HAT
- 81 practically speaking: grounding, shielding, and isolating – part 2 Joe Carr, K4IPV
- 87 gamma matching programs for the C-64/128 Fred A. Sontag, NØCAO
- 92 VHF/UHF world: optimized 2- and 6-meter Yagis Joe Reisert, W1JR
- 130 advertisers index and reader service 114 new products 6 comments
 - 110 ham mart
- 105 DX forecaster

hr_{wn}.

- 4 reflections
 - 64 short circuits
- 112 flea market

MAY 1987

volume 20, number 5

T. H. Tenney, Jr., W1NLB publisher

> **Rich Rosen, K2RR** editor-in-chief and associate publisher

Dorothy Rosa, KA1LBO managing editor

> Joseph J. Schroeder, W9JUV Alfred Wilson, W6NIF associate editors Susan Shorrock editorial production

editorial review board

Peter Bertini K17.1H Forrest Gehrke, K2BT Michael Gruchalla, P.E. Bob Lewis, W2EBS Mason Logan, K4MT Vern Riportella, WA2LQQ Ed Wetherhold, W3NQN

publishing staff J. Craig Clark, Jr., N1ACH assistant publisher Rally Dennis, KA1JWF director of advertising sales

> Dorothy Sargent, KA1ZK advertising production manager Susan Shorrock circulation manager Therese Bourgault circulation

Hans Evers, PAØCX cover ham radio magazine is published monthly by

Communications Technology, Inc. Greenville, New Hampshire 03048-0498 Telephone: 603-878-1441

subscription rates

United States United States: canada and other countries (via surface mains) canada and other countries (via surface main) one year, \$31.00, two years, \$55.00; three years, \$74.00 Europe, Japan, Africa Ivia Air Forwarding Service): one year, \$37.00 All subscription orders payable in U.S. funds, via international postal money order or check drawn on U.S. bank

international subscription agents: page 111

Microfilm copies are available from University Microfilms, International Ann Arbor, Michigan 48106 Order publication number 3076

Cassette tapes of selected articles from ham radio are available to the blind and physically handicapped from Recorded Periodicals, 919 Walnut Street, Philadelphia, Pennsylvania 19107

Copyright 1987 by Communications Technology, Inc. Title registered at U.S. Patent Office

Second-class postage paid at Greenville, New Hampshire 03048-0498 and at additional mailing offices ISSN 0148-5989

Send change of address to ham radio Greenville, New Hampshire 03048-0498



it used to be . . .

It used to be one of the major considerations in planning any antenna installation. After the wish list ("How many?" "What kind?" "How high?" "What bands?") was complete, reality entered the picture, raising such questions as "Can I really afford all this?" and "What kind of reception will I get?" This latter question often had less to do with performance and more to do with worry-ing about what the neighbors — and the zoning board — would say.

Radio Amateurs nationwide breathed (or should have breathed) a collective sigh of relief on February 12, 1987, when the courageous and persistent John Thernes, WM4T — who had taken on, at considerable personal expense, the city of Lakeside Park, Kentucky — won his case. In April, 1982, John had filed an application with the city zoning administrator for permission to erect a tower which was to include a triband beam at 70 feet and a two-element, 40-meter beam at 78 feet. (The specifics are important.) He was told, in effect, that the city's zoning regulations excluded *all* antenna towers. His application was rejected.

The details can be found in all the major Amateur Radio news reports (HR's *Presstop*, *The W5YI Report*, *The Westlink Report*, and *The ARRL Letter*) and in the other ham magazines, but basically what happened is that John took his struggle right on up to the Federal Appeals Court. And on February 12, the city of Lakeside Park agreed to sign a full consent judgment. What this meant to him was that he could now install his tower, his antennas, and his guy lines. There was a compromise — instead of a total height of 78 feet, he had to "settle" for 73 feet overall. (I believe I read that 73 feet would have been acceptable to John at the very beginning, before the city turned him down for any height at all.)

The significance of this case isn't that one Radio Amateur won his own personal antenna battle, but that *we all did*... because this was the first time that Memorandum Opinion and Order FCC 85-506, better known as PRB-1, was tested and supported in the higher courts. In its initial resolution, the Commission had declared that "local regulations which involve placement, screening or height of antennas based on health, safety or aesthetic considerations must reasonably accomodate amateur communications and represent the minimum practicable regulation to accomplish the purpose of the local authorities." In other words, it maintained that local and state governments cannot arbitrarily rule against the installation of Amateur Radio antennas.

John's legal fees, I believe, exceeded \$20,000. In deciding in his favor, the court ordered the city of Lakeside Park to pay all John's legal fees — almost \$14,000 — incurred since the enactment of PRB-1. It now appears likely that any municipality that contests other proposed Amateur installations could very well lose and be held responsible for costs.

This is our annual antenna issue. Personally, I couldn't have asked for a more appropriate time to acknowledge and discuss WM4T's victory.

You can get a copy of the consent decree from the Northern Kentucky Tower Fund (P.O. Box 17721, Lakeside Park, Kentucky 41017; SASE appreciated). John, by the way, is reportedly still out approximately \$7,000 of his own money; when you write for your copy of the decree, you may want to consider enclosing a donation to help minimize the impact.

Rich Rosen, K2RR Editor-in-Chief

Amateurs interested in further developments in this and other cases may want to attend the Amateur Radio And The Law Forum conducted by attorney Jim O'Connell, W9WU, at 1 PM on Sunday, April 26, at this year's Dayton Hamvention.

KENWOOD

... pacesetter in Amateur radio

TONE

1.0%

KENWOOD

LAMP OFFSET/R SCAN

2

5

8

0

1

4

7

*

3

3

6

9


#

Ultimate Affordable HT! H-205AT • 12 VDC input terminal—allows direct mobile or external / Heavy-duty final amplifier and heavy-

Affordable 5-watt hand-held transceiver. Ultimate Affordability!

It's here now! The affordable, "Kenwood Quality" hand-held transceiver. Standard features include a large, easy-to-read LCD display, wide-range power requirements (operates on 7.2 VDC-16 VDC). 3-channel memory, built-in battery saver circuit, and, when operated on 12 VDC, a robust five watts of power! The diecast metal rear panel/heat sink assures cool, reliable operation. **Receiver frequency coverage** from 141-163 MHz is also standard-you can even listen to the "weather channels" at 162.40 or 162.55 MHz!

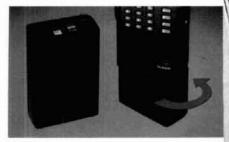- Monitor switch—to check frequency when PL encode/ decode switch is on.
- Extended frequency coverage for certain MARS and CAP operations.
- 3 memory channels store frequency and offset. And so easy to use! Simply press the memory channel number to recall your favorite channels!
- Night light, offset/reverse. —
- 16-key DTMF pad for repeater autopatch is standard.



 NEW! Twist-Lok Positive-Connect[®] battery case. A wide range of quickchange commercial duty battery packs are available.

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

 12 VDC input terminal—allows direct mobile or external power supply operation.
 When 12 VDC is applied, power output increases to 5 watts!

VHF

TUNE

M F.LOCK


D

TH-205AT

Heavy-duty final amplifier and heat sink. The die-cast rear panel assures reliable operation. With the optional 12-volt PB-1 battery pack, the TH-205AT provides 5 W output. The standard 8.4 volt PB-2 provides 2.5 W output. (300 mW low power).

Willing,

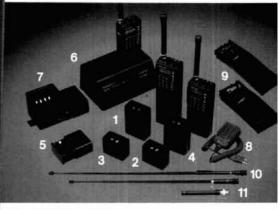- Large, easy-to-read LCD display. Frequency, offset, memory channel, TX, RX, and battery indicator.
- Frequency UP/DOWN keys. Used to select frequency or scanning direction.
- Scan function key.
- Automatic battery saver circuit extends battery life. No buttons to push!
- Supplied accessories include: Rubber flex antenna, belt hook, 8.4 V, 500 mAH NiCd battery pack, wall charger.



Optional Accessories:

PB-1 12 V 800 mAH NiCd batt, pack (5 W output).
 PB-2 8.4 V 500 mAH NiCd batt, pack (2.5 W output).
 PB-3 7.2 V 800 mAH NiCd batt, pack (1.5 W output).
 PB-3 7.2 V 800 mAH NiCd batt, pack (1.5 W output).
 PB-4 7.2 V 1600 mAH NiCd batt, pack (1.5 W output).
 PB-5 AA manganese/alkaline battery case.
 BC-7 Rapid charger for PB-1.2.3. or 4.7) BC-8 Compact battery charger
 SMC-30 Speaker microphone.
 SMC-30 Speaker mic



TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220



modifying the IC-02

Dear HR:

Readers may beinterested to know that the extended receive modification for the IC-02 described in my article, "Extending Receive Coverage for the IC-02 and IC-04" (July, 1986, page 77), will work for *all* IC-02 HTs, including those with serial numbers above 34,000.

Robert K. Morrow, Jr., WB6GTM Flora, Indiana

Yagi design program

Dear HR:

Early in 1984, Jerry Haigwood, KY4Z, and I wrote a computer program, based on DL6WU's article in the March, 1982 issue of VHF Communications, for designing long Yagi antennas. We presented that program at the West Coast VHF Conference held in May of that year at Paso Robles, California. Therefore, it should be no surprise that I have looked very carefully at the program developed by VK4ZF and described in his article "Computer-Aided Design of Long VHF Yagi Antennas," which appeared in the May, 1986 issue of Ham Radio [page 28].

Building a current ham radio project? Call the Building a current ham radio project? Call the Short Circuit Hotline any time between 9 AM and Noon, or 1 to 3 PM — Eastern time — before you begin construction. We'll let you know of any changes or corrections that should be made to the article describing your project.

- 603- 878- 1441

VK4ZF did an admirable job, but I believe that certain deficiencies should be pointed out. (The same could probably be done about the program Jerry and I wrote.)

First, the initial input requirement for the number of elements in the antenna is irrelevant. The initial criterion should be the desired gain or the available boom length. (Coincidentally, the irrelevance of the number of elements is covered by Joe Reisert in his column in the same issue [page 103]). Furthermore, in an earlier paper, DL6WU stated that the minimum boom length for an antenna of this type is about two wavelengths; a 2.2-wavelength boom will accommodate eight directors. There is no restriction as to the minimum number of elements in the program.

Second, the diameter of the elements is limited to the discrete values for which data files have been made. This makes it impossible to compare the program results directly with the example antennas described by DL6WU, although the differences are slight.

Third, the program is limited to 40 elements, which makes it impossible to compare the data for directors 39 through 47 of the 1296-MHz antenna described by DL6WU. There does not seem to be any valid reason for this limitation, since DL6WU states that his curves can be extrapolated almost indefinitely.

Fourth, the program limits the boom diameter to 0.05 wavelength, although this can be changed easily by modifying line 490. Without this change, it is impossible to use a boom diameter of 12.7 mm at 1296 MHz, which is the boom size used by DL6WU. Correspondence between DL6WU and KY4Z indicates that a minimum boom diameter of 0.075 wavelength is acceptable.

I have enclosed comparisons of the element lengths and spacings, showing DL6WU's figures, those obtained from VK4ZF's program, and those generated by the program written by KY4Z and me. A major discrepancy seems to be the length of the driven element in VK4ZF's program; it is far too short at 432 MHz, but slightly long at 1296 MHz.

None of the limitations described above exist in the program written by KY4Z and me, although the program does not include calculation of beam widths or stacking distances. Furthermore, it is a great deal easier to keyboard because the 16 data files are not required (which also conserves disk space).

Our program was written in Microsoft BASIC and will run under GWBASIC and BASICA. Minor editing may be required to convert it to other species of BASIC.

The program exists, under the filename DL6WU-1.BAS, on most of the RCPM bulletin boards in the San Francisco Bay Area, including KY4Z's AMPRO1 at 408-258-8128. I can also supply it in the following forms:

1. A listing, with a sample printout of results, for \$1.00 (U.S.) plus a No. 10 (business-size) SASE. (Outside of the United States and Canada, send 10 IRCs.)

2. A 5.25-inch soft-sectored floppy disk for virtually any CPM computer (except Apple) or for any PC/MS-DOS computer. Be certain to specify the disk format desired (and an alternate, if possible) or the version of PC/MS-DOS that is used. The cost in the USA and Canada is \$5.00 (U.S.), elsewhere, \$7.00 (U.S.); this covers the cost of the disk, mailer, and postage. The same costs apply to either a disk or tape cassette for the Commodore 64. Please address all requests to me.

Robert S. Stein, W6NBI 1849 Middleton Avenue Los Altos, California 94022

any ideas?

Dear HR:

A friend installed a plastic owl on his beam to discourage birds. A real owl appeared and attempted to court the plastic owl. When the plastic owl failed to respond, it was attacked by the real owl, causing commotion and damage. Any ideas, anyone?

Berand Kirschner Oceanside, California 92056

KENWOOD

... pacesetter in Amateur radio

220: Kenwood Style!

M-3530A The first comprehensive 220 MHz FM transceiver

TM-3530A-25 watts of 220 MHz FM-Kenwood style! Features include built-in 7-digit telephone number memory, auto dialer, direct frequency entry and big LCD. All this makes the TM-3530A the most sophisticated rig on 220 MHz!

- First mobile transceiver with telephone number memory and autodialer (up to 15 seven-digit telephone numbers)
- Frequency range 220-225 MHz
- Automatic repeater offset selection a Kenwood exclusive!
- Direct keyboard entry of frequency · 23-channel memory for offset, frequency and sub-tone



· Big multi-color LCD and back-lit controls for excellent visibility

 Optional front panel programmable 38tone CTCSS encoder includes 97.4 Hz

TH-31BT/31A

Kenwood's advanced technology brings you a new standard in pocket/handheld transceivers!

- = 1 watt high, 150 mW low
- Super compact and lightweight (about 8 oz. with PB-21!)
- Frequency range 220-224.995 MHz in 5-kHz steps
- . BT Series has built-in tone
- Repeater offset: -1.6 MHz, reverse. simplex
- Supplied accessories: rubber flex antenna, earphone, wall charger, 180 mAH NiCd battery and wrist strap
- Quick change, locking battery case

- Frequency lock switch
- Digital Channel Link (DCL) option
- High performance GaAs FET front
- end receiver
- TH-31BT/31A optional accessories:
- HMC-1 headset with VOX
- SMC-30 speaker microphone
- PB-21 NiCd 180 mAH battery
- PB-21H NiCd 500 mAH battery
- DC-21 DC-DC converter for mobile use
- BT-2 manganese/alkaline battery case
- EB-2 external C manganese/ alkaline battery case
- SC-8/8T soft cases with belt hook
- TU-6 programmable sub-tone unit
- AJ-3 thread-loc to BNC female adapter
- BC-6 2-pack quick charger
- * BC-2 wall charger for PB-21H
- RA-9A StubbyDuk antenna
- . BH-3 belt hook



- 16-key DTMF pad, with audible monitor
- Kenwood exclusive!
- New 5-way adjustable mounting system
- Unique offset microphone connector -relieves stress on microphone cord
- HI/LOW power switch (adjustable) LOW power)

MC-60A/MC-80/MC-85 desk mics.

SP-40 compact mobile speaker

SW-200B SWR/power meter

MC-43S UP/DOWN mic.

SP-50B mobile speaker

MC-48B extra DTMF mic. with UP/DOWN switch

MC-55 (8 pin) mobile mic. with time-out timer



TH-31BT with DTMF pad shown Optional RA-9A attached

KENWOOD 220MHz FM TRANSCEIVER

3 A

5

100

TH-31BT

TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220

- TM-3530A optional accessories:
- TU-7 38-tone CTCSS encoder = MU-1 DCL modem unit
- VS-1 voice synthesizer
- . PG-2N extra DC cable
- PG-3B DC line noise filter
- MB-10 extra mobile bracket
- CD-10 call sign display
- PS-430 DC power supply
- SW-100B compact SWR/power meter Complete service manuals are available for all Trio. Kenwood transceivers and most accessories.

Specifications and prices are subject to change without notice or obligation

Center-stop tuning—another

two-element hf beams

Tune these medium-sized high performance antennas right from the shack

Physically small beam antennas that represent the least compromise in gain and directivity have been discussed in the literature.1 Large antennas, for those for whom size is no problem, have received widespread coverage; the W2PV series of articles, for example, includes a wealth of material on large Yagis.² Yet the topic of medium-sized antennas - which includes the majority of Amateur beams - remains an area of uncertainty, about which many have sought without success for more information. The guad-versus-Yagi controversy continues unabated; conflicting claims are made for what might appear to be a bewildering variety of different beams, and an imperfect grasp of essentials has turned an inherently simple situation into one of needless complexity, with two-element beams deprived of their rightful status.

how small two-element beams work

In **fig. 1**, we have a bird's-eye view of two identical vertical elements carrying equal currents and spaced by a small fraction of a wavelength, with the plus and minus signs indicating that they are initially fed in opposite phase, thus tending to cancel each other.


At this point it's not important to know how the currents got there. Energy arriving at a specific point in space travels a different distance from each vertical element. This difference in path length and the opposite polarity of each vertical causes the maximum radiation from the array (two elements) to be along a line that goes through the elements. The two fields combine vectorially as shown in fig. 1B. For small angles, (ϕ_0) halving the angle halves the field. As one moves around the antenna, the difference is reduced; therefore the angle reduces, producing the directional pattern shown in fig. 1C, which is independent of spacing as long as the angle remains small. It follows that because energy remains similarly distributed throughout space, signal strengths must also be independent of spacing - provided there are no losses. Usually one introduces an electrical phase shift, ϕ . If this is equal

to the spatial phase shift, ϕ_0 , cancellation takes place in the reverse direction, producing the well-known cardioid pattern of **fig. 1D**. As the electrical phase shift, ϕ , is reduced, the null in the back direction splits into two. It gradually shifts around, with the back lobe increasing in strength until we arrive back at **fig. 1C**. However, for a given ratio of ϕ/ϕ_0 , the pattern remains independent of spacing.

In the case of horizontal beams the directional pattern of the individual elements is superimposed on the beam patterns derived in accordance with fig. 1, but the principles are the same. Because no dimensions are mentioned, it follows that for two elements the directive pattern — and therefore the gain — depend only upon the phase shift ratio, ϕ/ϕ_{o} , and are independent of the size, shape, or spacing of elements, provided the dimensions are not excessive. This rule is reasonably accurate for element lengths up to about 0.7 λ , and as shown in **fig. 2**, for spacings up to 0.2 λ . It starts to break down if there are regions of high current that are separated by a substantial fraction of a wavelength, the $\lambda/4$ separation between top and bottom of a quad loop not being appreciable in this context. In this case, a directive pattern results through the addition of fields - a completely different mechanism that is the basic principle of large arrays. Figure 2 shows the effect that element spacing has on gain and, from another source, a very similar curve for three elements.3

The basic statement emphasizing gain as primarily a function of the phase shift ratio rather than spacing - though it seems physically obvious - is in flat contradiction of widely published figures. These figures, derived mathematically for parasitic arrays, show gain and directivity to be critically dependent upon spacing and whether an element is tuned as a director or reflector. But although the calculations are indeed correct, they happen to be the wrong ones! More accurately stated, perhaps it's the designs to which they relate that are faulty, since I have assumed equal currents, whereas normally performance is sacrificed if the elements are straight.⁵ As can be inferred from fig. 3, this is the worst possible shape because it minimizes coupling, consequently precluding the possibility of the presence of equal currents, except with very close

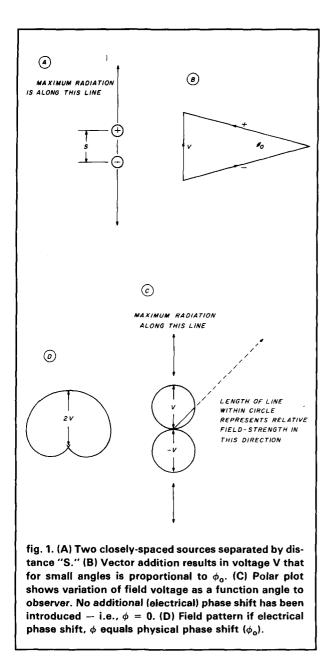Les Moxon, G6XN, Gorse Hill, Tilford Road, Hindhead GU26 6SJ Surrey, England




spacing (0.05 λ). Nulls in the directional pattern are filled in and gain is also adversely affected.


Coupling between straight elements can be increased by moving them closer together. But for this to be effective, spacing has to be reduced to about 0.05 λ , which is normally regarded as unacceptable because of reduction in bandwidth and efficiency. For this spacing, my calculations and those of W2PV are in close agreement. In my case, however, due to the assumption of equal current amplitudes, dependence on physical dimensions has been eliminated.

Inductive coupling (fig. 3A) isn't advised because of the reduction in radiation resistance. More often, natural coupling tends to be capacitive and needs only to be supplemented. One advantage of the quad is that loops couple more tightly than straight dipoles; this probably accounts for its popularity despite a poor reputation for survival in high winds. On the other hand, bent elements (see **figs. 3B** and **3C**) lend themselves to the design of more compact but equally efficient antennas with overcoupling rather than undercoupling as the more common fault. This is easy to correct either by an alteration of spacing or, if necessary, neutralization¹, as shown in **fig. 3C**.

mutual impedance

From the narrowing of the radiation pattern, it is evident that there must be gain relative to a dipole. But how, one might ask, can this be if the elements are tending to cancel each other? The answer lies in the fact that the element currents rise to whatever value may be necessary to account for the observed gain, and they can do so only by virtue of the mutual resistance between the elements which subtracts from the self-resistances when closely spaced elements are excited in antiphase. Without mutual resistance, there can be no power gain; these quantities are inseparable, so that given equal currents, one follows from the other. On the other hand, mutual resistance alone cannot achieve the degree of current equality necessary for obtaining deep nulls. This requires mutual reactance, which exists in most cases but may need to be increased or decreased, with reflector operation requiring negative reactance. Mutual resistance, R_m and reactance, X_m data appears to be available only for straight $\lambda/2$ elements (fig. 4), but the "size rule" implies that mutual resistance bears a constant relationship to the single-element radiation resistance (R), and so the mutual resistance can, if necessary, be inferred from it. Likewise, if the elements are self-resonant, mutual reactance can in principle be determined from

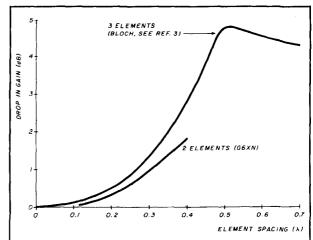

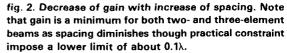

directions of minimum response by obtaining corresponding values of ϕ/ϕ_0 from fig. 5, since with no detuning the phase shift ϕ is determined solely by the phase angle of the mutual impedance - i.e. by X_m/ R_m so that by knowing ϕ , ϕ_0 and R_m we can evaluate X_m. This method has not been evaluated in practice and its use is restricted by the fact that with large departures of X_m from its optimum value the nulls will not be deep enough for their direction to be determined. In general, however, with two elements there should be no need to know the actual value of Xm since constructions are available which allow it to be adjusted by trial and error. Additionally, by virtue of the "size rule" calculations or measurements for a set of dimensions for which X_m is known can be applied to any other, with due allowances for differences in R. Calculations, simplified by assuming equal currents,⁵ have led to further results:


 \bullet Radiation resistance (R_B) for a parasitic array is given by

$$R_B = 2 (R - R_M \cos \phi)$$


• For an array in which each element has its own feedline, the radiation resistances are:

 $R \ director = R - R_M \cos \phi + X_M \sin \phi$ $R \ reflector = R - R_M \cos \phi - X_M \sin \phi$

With a resonant reflector and equal currents, the null directions are approximately 130 degrees relative to the beam heading in all cases. The total resistance is the same as before, but that of the reflector (or director if X_M is positive) can be zero or even negative, which bodes ill for the matching process. Until now, driven operation has been the usual method of trying to equalize currents, but the reason for some failures may now be apparent, particularly because the usual phasing lines must be matched for correct operation. Solutions to this problem have been discussed before.^{1,5} Driven operation remains a possible solution to the problem of obtaining equal currents with straight elements, and a number of such antennas have been described. Most of these, intended to be reversible, specify $\lambda/4$ spacing, which is too wide, or $\lambda/8$ spacing, which is convenient and simplifies the mathematics to the extent that X_M disappears. Unfortunately, because of mutual reactances of opposite sign, which each element induces into the other, a very high VSWR exists in each of the individual feeders. This high VSWR may not be noticed because it doesn't appear in the common feed from the transmitter; if it were corrected, the beam couldn't be reversed because the correction would then be of the wrong sign and make matters worse. Open wire lines can be used, but result in excessively narrow bandwidth (though I've overcome this by using folded dipole elements).

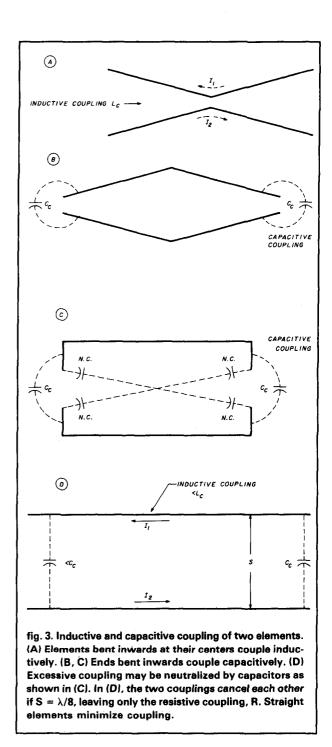

Overcoupling is a problem likely to be experienced in the case of quads with less than 0.15λ spacing. The "Swiss Quad" (with 0.1λ spacing) gets around this by driven operation, but as we'll discuss later, there are many advantages to be derived from resonant feeders, including the possibility of increasing coupling or neutralizing excess coupling by means of capacitance between the lines. **Figure 5** shows the dependence of gain, radiation resistance, and null directions on the phase shift ratio.^{1,5} If any one of these quantities is known, all the others except radiation resistance (R_B) follow from it. For the last parameter, we also need

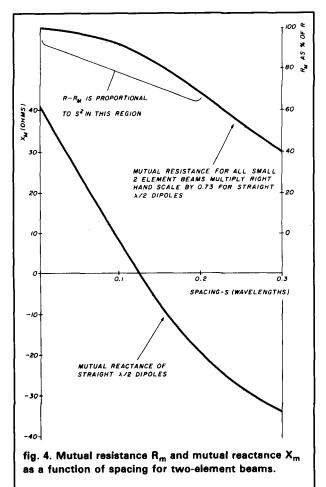


to know the value for a single element (R); with a few exceptions, this can be obtained from **fig. 6**. The method of calculation is explained in reference 5. **Figure 7** is a further extension of **fig. 5** showing the direction and magnitude of the back lobes in the radiation pattern. They demonstrate the crucial importance of the ratio ϕ/ϕ_0 in determining all aspects of the performance of two-element beams (including bandwidth, since this is linked to radiation resistance, as discussed later).

directivity gain

So far we've assumed that there are no losses. Apart from feeder loss, other losses may occur because of proximity to nearby structures, use of very thin wire, or as the limiting factor when trying to make an antenna as small as possible. Besides radiation pattern distortion, currents induced in booms or supporting structures due to lack of symmetry may introduce additional losses. If equal currents and correct phasing are maintained, losses as such have no effect on directivity which, because of high external noise levels, is usually the sole requirement in the case of reception on the hf bands.

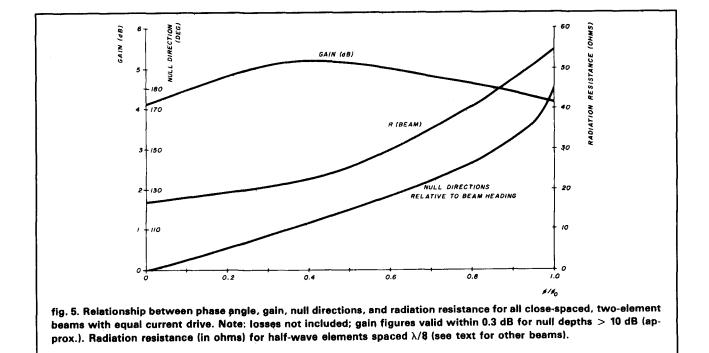Losses can make it impossible to equalize currents by means of increased coupling, but there is then no longer any problem with driven operation since the mutual resistance, as a result of these losses, is no longer in control of the situation. Because of this, it's customary to distinguish between directivity gain and power gain, the two being equal when there are no losses.



losses

Horizontal monoband hf beam losses rarely exceed a few ohms, and with radiation resistances of a few tens of ohms, can usually be neglected. In doubtful cases they can be roughly estimated from conductor sizes, assuming one has some idea of the current distribution.


Resistance data in graph form can be found in textbooks, but a handy figure to remember is one ohm per half-wavelength for 3-mm diameter copper wire (approximately No.10 AWG) at 14 MHz. The loss is inversely proportional to diameter and to the square root of frequency. However, divide by 2 for long conductors that have a sine wave current distribution, such as antenna wires or resonant feeders. This gives the resistance referred to a point of maximum current, which is standard practice also in the case of the radiation resistance with which it must be compared. For parallel wires, divide by the number of wires; for aluminum alloy, multiply by 1.6, and don't use iron or steel!


bandwidth


Bandwidth is roughly proportional to radiation resistance but also varies inversely with the length of the resonant system (which includes the antenna up to the point of matching). We are interested in two kinds of bandwidth:

• SWR bandwidth — i.e., the frequency range over which the SWR is less than 2.0. As might be expected by analogy with coupled circuits, bandwidth in this sense is improved by tighter coupling between elements. The better the SWR bandwidth, the less frequently the antenna tuner has to be readjusted, or the better the chance of being able to dispense with it. In general, SWR tends to rise steeply at the low frequency end of the tuning range, since tuning low is equivalent to tuning the reflector higher. This reduces ϕ , causing a shift to the left on the curves shown in **fig. 5**, with R_B dropping to a relatively low value.

• Pattern bandwidth, or the frequency range in which a specified null depth such as 10 dB is exceeded or the forward gain remains within 1 dB of maximum. Despite their relatively small size the antennas to be described here come close to meeting the above specifications on most bands without retuning the reflector. This is consistent with a reasonable degree of operating convenience, but to take advantage of very deep nulls it's essential for the reflector to be connected through its own feeder to a tuning device at the operating position. In this case, pattern bandwidth is less important but makes for added convenience. Use of two feeders provides an additional bonus: the ability to reverse beam direction.

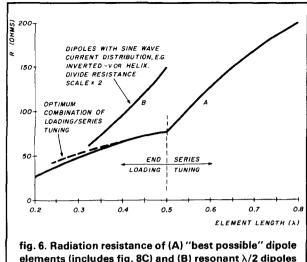

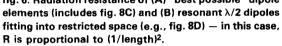

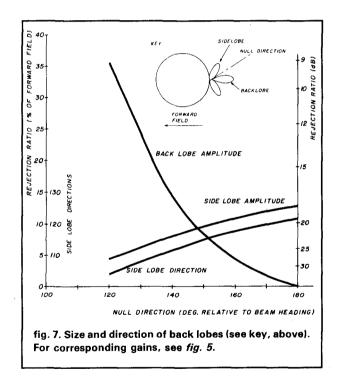

design of elements

Although elements don't have to be identical, it usually helps — and is essential if one wants to be able to reverse beam direction without having to retune. Figure 6 shows that half-wave elements can be reduced by 30 percent in length for only a trivial reduction (17 percent) in radiation resistance, provided capacitive end-loading (or its equivalent) is used. Figure 8 shows three practical ways of achieving this. In the case of fig. 8C, AB and CD act solely as end

MFJ TUNERS

This may be the world's most popular 3 KW roller inductor tuner because it's small, compact, reliable, matches virtually everything and gives you SWR/Wattmeter, antenna switch, dummy load and balun —

all at a great price! Meet "Versa Tuner V". It has all the features you asked for, including the new smaller size to match new smaller rigs-only 10% "Wx4½" Hx14 7/8"D.

Matches coax, balanced lines, random wires—1.8 to 30 MHz. 3 KW PEP —the power rating you won't outgrow (250pf-6KV caps).

Roller Inductor with a 3-digit turns counter plus a spinner knob for precise inductance control to get that SWR down to minimum every time. Built-In 300 watt, 50 ohm dummy load, built-In 4:1 ferrite balun.



MFJ989B \$34995

MFJ's Fastest Selling TUNER

MFJ-941D \$99.95



MFJ's fastest selling tuner packs in plenty of new features. New styling! Brushed aluminum front. All metal cabinet. New SWR/Wattmeter! More accurate. Switch selectable 300/30 watt ranges. Read forward/reflected power.

New antenna switch! Front panel mounted. Select 2 coax lines, direct or through tuner, random wire/balanced line or tuner bypass for dummy load.

New airwound inductor! Larger more efficient 12 position airwound inductor gives lower losses and more watts out. Run up to 300 RF power output. Matches everything from 1.8 to 30 MHz! dipoles,

inverted vee, random wires, verticals, mobile whips, beams, balanced and coax lines. Built-In 4:1 balun for balanced lines. 1000 V ca-

pacitor spacing. Black. 11 x 3 x 7 inches. Works with all solid state or tube rigs. Easy to use anywhere.

MFJ's 1.5 KW VERSA TUNER III

MFJ-9628 \$229.95



Run up to 1.5 kw PEP and match any feedline continuously from 1.8 to 30 MHz: coax, balanced line or random wire.

Lighted Cross-needle Meter reads SWR, forward and reflected power in one glance. Has 300 and 3,000 watt ranges. 6 position antenna switch handles 2 coax lines, wire and balanced lines. 4:1 balun. 250 pf, 6 kv variable capacitors. 12 position ceramic inductor switch. New smaller size matches new rigs: $10^{3/4} \times 4^{1/2} \times 14^{7/4}_{1/4}$ inches. Flip stand for easy viewing. Requires 12V for light.

ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO OBLIGATION. IF NOT SATISFIED, RETURN WITH-IN 30 DAYS FOR PROMPT REFUND (less shipping). • One year unconditional guarantee • Made in USA • Add \$5.00 each shipping/handling • Call or write for free catalog, over 100 products.



MFJ's best 300 watt tuner Is now even better! The MFJ-949C all-In-one Deluxe Versa Tuner II gives you a tuner, cross-needle SWR/Wattmeter, dummy load, antenna switch and balun in a new compact cabinet. You get quality conveniences and a clutter-free shack at a super price.

A new cross-needle SWR/Wattmeter gives you SWR, forward and reflected power—all at a single glance. SWR is automatically computed with no controls to set. Has 30 and 300 watt scale on easyto-read 2 color lighted meter (needs 12 V).

A handsome new black brushed aluminum cabinet matches all the new rigs. Its compact size (10 x 3 x 7 inches) takes only a little room.

You can run full transceiver power output—up to 300 watts RF output—and match coax, balanced lines or random wires from 1.8 thru 30 MHz. Use it to tune out SWR on dipoles, vees, long wires, verticals, whips, beams and quads.

A 300 watt 50 ohm dummy load gives you quick tune ups and a versatile six position antenna switch lets you select 2 coax lines (direct or thru tuner), random wire or balanced line and dummy load.

A large efficient airwound inductor—3 inches in diameter—gives you plenty of matching range and less losses for more watts out. 100 volt tuning capacitors and heavy duty switches gives you safe arc-free operation. A 4:1 balun is built-in to match balanced lines.

Order your convenience package now and enjoy.

2 KW COAX Switches	MFJ-1702 \$19.95	11
MFJ-1702. \$19.95. 2 60 dB isolation at 450 M Less than .2 dB loss.		11
SWR below 1:1.2. MFJ-1701, \$29.95. 6 positions. White	#23.35 Mr3-1	
for antenna positions.		
	IFJ	T

MFJ ENTERPRISES, INC. Box 494, Mississippi State, MS 39762 raised letters, tilt bail. MFJ's Smallest VERSA TUNER

binding post grounds.



Lighted Cross-needle Meter reads

SWR, forward and reflected power all in

one glance. Has 300 and 3,000 watt

6 position antenna switch (2 coax lines,

ranges. Meter light requires 12 VDC.

through tuner or direct, random/ba-

lanced line or dummy load). SO-239

connectors, ceramic feed-throughs.

Deluxe aluminum low-profile cabinet

with sub-chassis for RFI protection.

black finish, black front panel with

MFJ's smallest 200 watt Versa Tuner matches coax, random wires and balanced lines continuously from 1.8 thru 30 MHz. Works with all solid state and tube rigs. Very popular for use between transceiver and final amplifier for proper matching. Efficient airwound inductor gives more watts out. 4:1 balun for balanced lines. 5 x 2 x 6 inches. Rugged black all aluminum cabinet.

MFJ's Random Wire TUNER



MFJ's ultra compact 200 watt random wire tuner lets you operate all bands anywhere with any transceiver using a random wire. Great for apartment, motel, camping operation. Tunes 1.8-30 MHz. 2 x 3 x 4 inches.

MFJ's Mobile TUNER




Designed for mobile operation! Small, compact. Takes just a tiny bit of room in your car. SWR/dual range wattmeter makes tuning fast and easy. Careful placement of controls and meter makes antenna tuning safer while in motion.

Extends your antenna bandwidth so you can operate anywhere in a band with low SWR. No need to go outside and readjust your mobile whip. Low SWR also gives you maximum power out of your solid state rig—runs cooler for longer life.

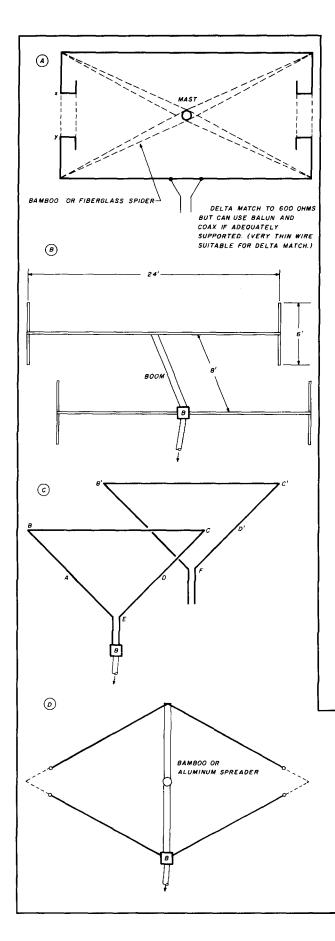Handles up to 300 watts PEP RF output. Has efficient airwound inductor, 1000 volt capacitor spacing and rugged aluminum cabinet. 8x2x6 inches. Mobile mounting bracket available for \$5.00.





loading because radiation from them is cancelled by that from *AE* and *DE*.

Most of the designs to be described are based on the small delta loop (fig. 8C), which can be suspended between the tips of fiberglass fishing rods angled upwards, thus achieving an effective height considerably in excess of the mast height, since there's little or no radiation from the sides of the loop. In this form it has become known as "The Claw" for reasons obvious from the photograph (fig. 15). In most cases there seems to be little point in exceeding an element span of about 35 percent of the longest wavelength to be used; further size reduction is governed by three main constraints: bandwidth, losses, and difficulty of folding enough loading wire into the space available. For a reasonable approximation to "full size" performance, the above length can be more than halved if some form of remote tuning is provided.1 Practical difficulties escalate rapidly as the span length drops below 0.25λ.

The arrangement shown in **fig. 8D** can be erected as an inverted V and is important as an alternative option though the sinusoidal current distribution halves the radiation resistance for a given span.

coupling and null depth

All four arrangements shown in fig. 8 provide increased coupling. In cases A and D, this is readily adjustable by altering the spacing between ends; 30 inches for a span of 20 to 24 feet at 14 MHz has been found suitable, but some experiments may be advisable. Ajustment of coupling isn't critical. I've found that "design by guesswork" frequently produces null depths in excess of 20 dB. It's best for errors to be corrected in the antenna itself, but for fine tuning, placing capacitors between convenient points on feeders has been found satisfactory. These can be connected either in phase to increase coupling or out of phase to neutralize excessive coupling. I then find it possible to get null depths usually in excess of 20 dB, and often much greater, for all back directions and inband (14 MHz) frequencies with single-knob tuning of

fig. 8. Two-element horizontal beams with reduced length and enhanced coupling. Reflector should preferably be a duplicate of the driven element (see text). Otherwise, if currents equal (i.e. if deep nulls are obtainable), tune reflector to the low edge of desired band. (A) Bent dipole elements (20 x 10 feet suggested, though dimensions are not critical) xy (nylon fishing line) \approx 30 inches. (B) End-loading by vertical rods. Single elements have been used successfully with the dimensions shown. Coupling may need augmenting. (C) Small delta loops (ABCD) should be just over $\lambda/2$. Size can be reduced by small loading stubs. BB' may be 0.12-0.2 λ ; EF < BB'/2. (D) Erect between posts or as inverted V. Spreader (or boom) may be 9-12 feet for 14 MHz.

KENWOOD

... pacesetter in Amateur radio

HF Superiority! SSB slope tuning—Another



All band transceiver with general coverage receiver

Throughout the contest and DX world, the TS-930S is recognized as THE HF rig to own-with the most outstanding performance per dollar ratio!

· Easily modified for HF

IF notch filter

MARS and CAP operation

- Excellent receiver dynamic range
- All solid state, 28 volt final amplifier for lowest intermodulation distortion
- Power input rated at 250 watts on SSB, CW, FSK, and 80 watts on AM
- Full break-in or semibreak-in CW

8 memories store mode,

frequency, band. Each

a separate VFO

channel may be used as

- Superior solid state
 - design VOX, semi break-in CW with sidetone
- Dual digital VFOs
- A complete line of accessories is available

5-43 Compact all band transceiver with general coverage receiver

Kenwood engineering brings you "Digital DXterity"—QSY from band to band, mode-tomode, and frequencyto-frequency with ease!

- Easily modified for MARS operation
- Superb interference reduction
- Programmable scanning


10 Hz display shown (see operating manual)


Complete service manuals are available for all Trio-Kenwood transceivers and most accessories Specifications and prices are subject to change without notice or obligation

LSB

TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220

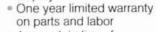- Kenwood First! CW VBT and pitch controls Tunable audio filter built in
- Dual mode noise blanker ("pulse" or "woodpecker") with threshold control
- Eight memory channels
- RF speech processor
- High stability, dual digital **VFOs**
- AC power supply built in
- Fluorescent tube digital
- display



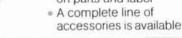



Cards and plaque courtesy W6TC

EIMAC's new DX champion! The 3CX800A7.

Varian EIMAC continues to commit its development of reliable tubes for HAM radio.

The new, rugged 3CX800A7 power triode provides 2 kW PEP input for voice service or 1 kW cw rating up to 30 MHz. Two tubes will meet the new, higher power ratings authorized by the FCC.


Designed for today's low profile, compact linear amplifiers, the 3CX800A7 powerhouse is only 2½ inches (6.35 cm) high. Cooling requirements are modest and a matching socket, air chimney and anode clamp are available.


A data sheet and more information is available from Varian EIMAC. Or the nearest Electron Device Group sales office. Call or write today.


Varian EIMAC 301 Industrial Way San Carlos, California 94270 Telephone: 415+592-1221



the reflector. "Deepest possible" nulls aren't thought to be worth additional effort, given the unstable nature of the ionosphere and sensitivity to local field disturbances — for example, trees blowing in the wind, the presence of other antennas, even aircraft reflections. Up to 30 dB can be useful, but deeper nulls require precise adjustments of phase and amplitude (two knobs). By the time these adjustments are made, the interference one is trying to remove has probably disappeared anyway! With deep nulls a tendency has been observed for non-reciprocity between transmission and reception, due probably to pickup on wiring in the shack. If a linear is used, this won't be identical for the two cases.

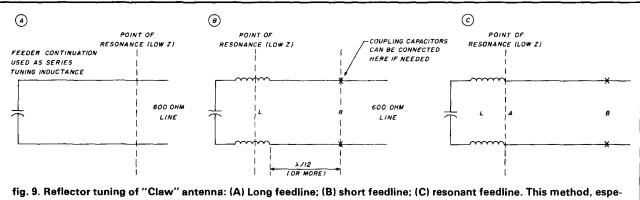

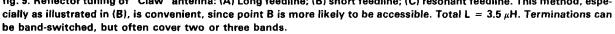

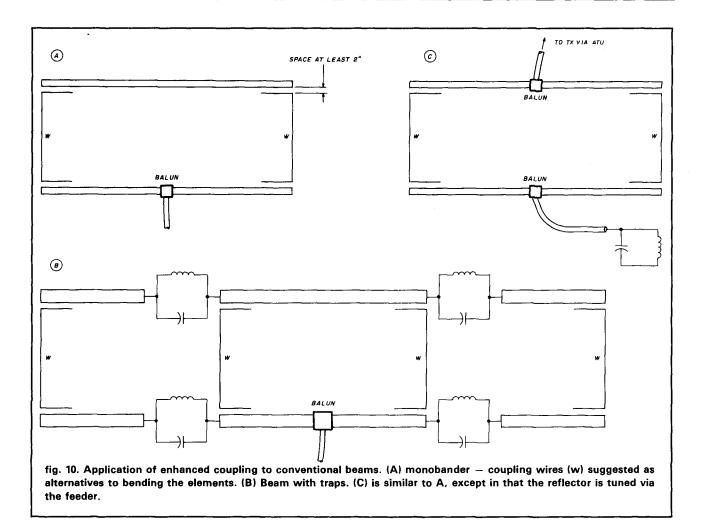

Expanding Our Horizons

Introducing Mirage/KLM 1.2-44 LBX

The first 1240 MHz to 1300 MHz Made in the U.S.A.

Factory Tested
Completely Assembled
Completely Weatherized Balun
Also Available Soon . . . Power Dividers


SPECIFICATIONS

Electrical

- Band Width 1240-1300 MHz
- VSWR Better than 1.5 to 1
- Feed Imp...... 50 Ohms
- Balun 4:1 Rigid Coax


Mechanical

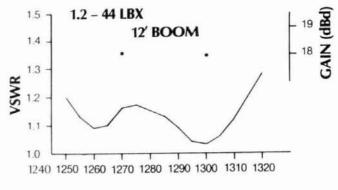- Beam Length 12' 4"
- Element Length 4.5"
- Mast 2" O.D.
- Windload 1 sq. ft.



FREQUENCY (MHz)

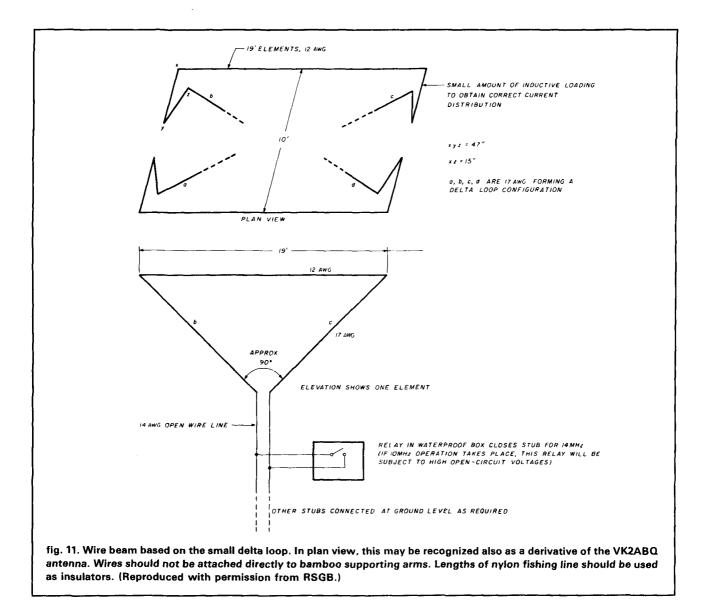Mirage Communications Equipment, Inc. P.O. Box 1000 Morgan Hill, CA 95037 (408) 779-7363



reflections from other antennas

These reflections can be large enough to seriously degrade forward gain at distances of over 30 meters at 14 MHz. (In one case I observed a loss of 2 S-units due to screening by another antenna at about 25 meters.) Their effect on front/back ratio is much greater. From mutual resistance data, it appears that another antenna 7 wavelengths away might be expected to degrade a 30-dB null by about 6 dB. Such effects depend, of course, on the extent to which the interfering antenna is in the beam path, so the effective radiation pattern varies with beam heading. The interfering antenna may be "removed" by detuning or rotating it to an end-on position, but any front/back ratio it may possess applies only to its own input terminals and does nothing to help. Unless such effects can be eliminated, the possibility for serious errors remains. This further emphasizes the importance of being able to make adjustments at the operating position to suit the needs of the moment. However good its f/b ratio, a large Yagi will still be wide open to reflected signals from other antennas in its beam path.

reflector tuners and t/r switching

Separate optimization of transmitting and receiving characteristics by switching between two different reflector tuners is a further important option. Tuning of the reflector to null out an interfering station can have a large effect on the SWR unless the antenna tuner is readjusted. Using an FS71OH automatic inline SWR meter, I haven't found this to be a problem, but without such a device and with modern solid-state amplifiers it can be an embarrassment. Because transmitting and receiving requirements aren't identical, it makes sense, in any case, to use separate tuners switched by a relay, not forgetting to use the "trans-



P.C. ELECTRONICS 2522 S. PAXSON LN. ARCADIA CA 91006 (818) 447-4565 TOM W6ORG MARYANN WB6YSS Compuserve 72405,1207

SEE US AT DAYTON





ATV MADE EASY WITH OUR SMALL ALL IN ONE BOX TC70-1 TRANSCEIVER AT A SUPER LOW \$299 DELIVERED PRICE! CALL 1-818-4474565 AND YOURS WILL BE ON ITS WAY IN 24 HRS (VIA UPS SURFACE IN CONT. USA).

TC70-1 FEATURES:

- Sensitive UHF GaAsfet tuneable downconverter for receiving
- * Two frequency 1 watt p.e.p. transmitter. 1 crystal included
- Crystal locked 4.5 mHz broadcast standard sound subcarrier
- * 10 pin VHS color camera and RCA phono jack video inputs
- * PTL (push to look) T/R switching
- Transmit video monitor outputs to camera and phono jack
- * Small attractive shielded cabinet 7 x 7 x 2.5"
- * Requires 13.8vdc @ 500 ma. + color camera current

Just plug in your camera or VCR composite video and audio, 70cm antenna, 12 to 14 vdc, and you are ready to transmit live action color or black and white pictures and sound to other amateurs. Sensitive downconverter tunes whole 420-450 mHz band down to channel 3. Specify 439.25, 434.0, or 426.25 mHz transmit frequency. Extra transmit crystal add \$15.

Transmitting equipment sold only to licensed radio amateurs verified in the Callbook for legal purposes. If recently licensed or upgraded, send copy of license. Receiving downconverters available to all starting at \$59 (TVC-2G).


WHAT ELSE DOES IT TAKE TO GET ON ATV?

Any Tech class or higher amateur can get on ATV. If you have a camera you used with a VCR or SSTV & a TV set, your cost will just be the TC70 and antenna system. If you are working the AMSAT satellites you can use the same 70cm antennas on ATV.

DX with TC70-1s and KLM 440-27 antennas line of sight and snow free is about 22 miles, 7 miles with the 440-6 normally used for portable uses like parades, races, search & rescue, damage accessment, etc. Get 50 watts p.e.p. with the Mirage D24N or D1010N-ATV amp for greater DX or punching thru obstacles.

The TC70-1 has full bandwidth for color, sound, like broadcast. You can show the shack, home video tapes, computer programs, repeat SSTV, weather radar, or even Space Shuttle video if you have a home satellite receiver. See the ARRL Handbook chapt. 20 & 7 for more info & Repenter Directory for local ATV repeaters.

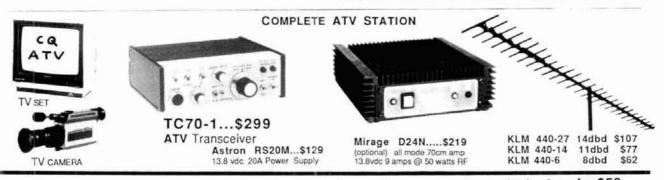PURCHASE AN AMP WITH THE TC70-1 & SAVE! 50 WATT WITH D24N-ATV....\$499 All prices include UPS surface shipping in cont. USA



HAMS! Call or write for full line ATV catalog downconverters start at only \$59

mit" (tuner) condition when checking for prior channel occupancy. While any feeder length can be used, it simplifies matters to choose one that allows series tuning as shown in **fig. 9**, preferably as shown in **fig. 9B**, which increases the chance that points such as *xx*, where the rf voltage is suitable for coupling adjustment, will still be available in the shack if required. With feeder impedances of both 50 and 600 ohms at 14 MHz, I have found a capacitance (C) of 40 to 250 pF and an inductance (L) of 3 to 4 μ H to be suitable, but this would depend on feeder length. The trick is to pick a likely-looking capacitor out of the junk box and, with a grid dip oscillator, find an inductance that allows the reflector to be tuned through the band and down to about 2 percent lower.

beam reversal

This reduces the average time required for changing beam heading since rotation can be limited to about 140 degrees. Also, in many cases an Armstrong method of rotation can be employed, with two ropes substituted for the usual heavy, expensive, and sometimes unreliable beam rotator. It can be particularly useful in multi-way contacts, and if there's uncertainty about whether propagation is short or long path. It also provides confirmation that the antenna is working correctly. Figure 10 includes suggestions for the addition of controlled coupling to conventional beams which, though as yet untried, may be useful to experimenters. In (A) and (C), it may be easier to pull the ends in toward each other with nylon fishing line. To permit beam reversal and null-steering, the reflector must be replaced by a replica of the driven element.

comparison between two and three elements

Two-element beams can be expected to produce deeper and more controllable nulls, but this may not help if more than one interference source is present. In this respect, three-element beams are superior, assuming fixed tuning of the reflector in both cases. With two elements, a rejection ratio better than 18 dB can be obtained for all back angles if the nulls are placed at 150 degrees to the beam heading; this is for a spot frequency, but can be obtained throughout the band if reflector tuning is synchronized with the main tuning. With three elements, W2PV² found null depths in excess of 20 dB over 2 percent bandwidth in the best case, but this was only for the 180 degree direction. It has also been shown that three elements can provide rejection in excess of 28 dB at all back angles simultaneously on a spot frequency.⁴ From tuning data given in this reference, I estimate a minimum rejection of around 18 to 20 dB over a 2 percent band, which is little better than the two-element result and requires very precise adjustment of the kind difficult

to obtain in practice because one is working with too many variables. The two-element beam, moreover, provides the option of deeper nulls in specific directions, though the rejection of QRM from several sources simultaneously may then be adversely affected. In practice, not more than 1 to 1-1/2 dB extra gain can be expected from the third element, and in terms of the low-angle radiation required for chordal-hop propagation (which is probably responsible for most long-haul DX⁵), this is equivalent to an antenna height increase of only 15 to 20 percent. The small size, light weight, and construction of antennas described in the next section should, in many cases, lead to height increases of this order. It is not suggested that these small beams can compete with a six-element monobander on a 100-foot tower, but they can hold their own in more ordinary circumstances, requiring only a modest means of support, indifferent results quoted by earlier authors being attributable entirely to the assumption of straight elements and the resulting current inequalities. Much of this ground has been covered in earlier publications; a complete bibliography can be found in reference 5.

multiband beams

Multiband beams have previously consisted mainly of tribanders involving some degree of compromise. Instead of using the whole of a 14-MHz $\lambda/2$ element on 28 MHz, it is cut down to size by traps, or 28-MHz loops are stacked inside 14-MHz loops which could be used to provide extra gain on 28 MHz. This sacrifices 2 to 4 dB of gain at 28 MHz¹, as well as incurring losses due to circulating currents in traps or "wrong way" currents induced in unused elements, which can reduce bandwidth and affect coupling.

Trapped beams rate highly in terms of convenience as well as off-the-shelf availability, and their popularity could no doubt be further enhanced by design improvements — for example, along lines suggested by W0JF.¹¹ At the same time, the fact that now we have, within 1-1/2 octaves, six bands instead of three, presents an exciting challenge unlikely to be met by traps or stacking without further compromises. The log periodic antenna, though simple in use, is large, heavy, expensive, and inferior in performance to a Yagi of the same size.

the "poor man's log periodic" (PMLP)

When short of new ideas, it often helps to take a fresh look at old ones, which is what I've been doing in the case of resonant feeders. Though these have been *blamed* for TVI, radiation from balanced lines is very small, and they've consequently also been *recommended* as cures for TVI. It's true that they can get themselves twisted around the mast or entangled in guy ropes, but there's no excuse for this if beams are

reversible as previously recommended, since rotation can then be restricted to less than 180 degrees. A more serious objection is the restriction of bandwidth. But with remote tuning, this becomes an inconvenience rather than a basic limitation. Now, through a fortunate accident, a solution to the bandwidth problem has also emerged and with it a family of small, lightweight antennas that provide the performance and other characteristics of the antennas described earlier, yet are tunable over the frequency range from 10 to 30 MHz. This largely achieves the object of the log periodic antenna, though the principle at work is entirely different.

the ideal antenna?

To establish the respectability of resonant feeders and provide a useful perspective, the design of a "best possible" multiband beam will be attempted.

Consider three identical straight tubing elements 44 feet long, spaced 8 feet apart, fed with about 46 feet of open wire line, and tuned to 14 MHz. The radiation resistance of a single element is 150 ohms and the bandwidth of antenna plus feeder for an SWR of 2:1 is about 8 percent, differing only slightly from that of a normal half-wave element. This should provide gain and f/b ratio in line with the previous three-element example. The larger value of radiation resistance, however, makes it much easier to use resonant feeders for remote tuning and beam reversal; even if this is not required, it helps to ensure reasonable bandwidth. The main benefit occurs at other frequencies, since on 28 MHz the elements are "extended double Zepp," which was the reason for the choice of length. The boom length is nearly optimum,² bringing the total gain to about 10.5 dBd. The spacing is too wide for good f/b ratio on 28 MHz, but this could be improved by additional coupling. On 10 MHz, omitting the center element provides for satisfactory spacing and achievable gain is in accordance with numbers indicated in fig. 5. Losses are negligible. The lower end of the feeders is assumed to be accessible near the antenna and can be lengthened or matched into, if necessary, utilizing band switching, depending either on local requirements or bandwidth considerations. With two elements, the boom length would have to be reduced, with 0.1 λ the minimum acceptable length at 10 MHz. The gain at 28 MHz is reduced to 7 dB, but remains high for two elements. For comparison, the gain of a log periodic will be in the region of 6 dBd, assuming a boom length of 50 feet, making the PMLP far superior except for the inconvenience of having to tune it. This can be done in the shack if the feeders aren't too long. Nevertheless even the PMLP in this ideal form is in the "monster" class, and much effort has been devoted to applying the same principles to smaller antennas.

the small delta loop

The antenna shown in fig. 8C, a fixed pair of loops supported by a tree, was selected for this purpose after being used initially as the quickest and easiest way of getting back on the air from a new location. Though it wasn't possible to make a direct comparison, the performance of a full-size quad - in the same tree at the same height - was later judged to be about the same. The first multiband version of this antenna⁶, shown in fig. 11, was used initially without the switched stubs, with correct coupling established by capacitance between the corner stubs (which also provided a small amount of loading) and by bringing the lower corners in towards the mast. The electrical lengths from top center to a shorting bar at ground level were arranged to be λ on 14 MHz, 1-1/2 λ on 21 MHz, and 2λ on 28 MHz, providing for 600-ohm feedline matching as well. Current nulls in the center of the sides on 14 MHz ensured that all the radiation was from the top of the system, while at higher frequencies the loops radiated as ordinary loops, with effective spacing reduced by bringing the lower corners together. The matched lines (120 feet) were taken respectively to an antenna tuner and a series-tuned circuit for reflector tuning via a beam-reversing switch which interchanged the feeders in the shack. The elements were supported by four 8-foot bamboo garden canes radiating outwards and upwards from an aluminum hub with four 4-foot spokes, for a total radial length of 12 feet. The SWR bandwidth for given settings of the antenna tuner and reflector tuning at 14 MHz was only 100 kHz which generated a tendency to stay in one part of the band. Differences in tuning between wet and dry weather were a nuisance. These were aggravated by short lengths of 300-ohm line initially used for bypassing the rotating joint. Checking the feasibility of operation on 10 MHz was difficult because it required the attachment of matching stubs at half the mast height, but it was achieved on one occasion, which resulted in an S8 report from VK with reasonable f/b ratio.

Despite the narrow bandwidth, such an arrangement may well be acceptable on the grounds that it is simple, cheap, versatile, and efficient, especially if the shack is located at the base of the mast. For me, however, it has one fatal flaw: the difficulty of living with the knowledge that identical performance could be obtained from a smaller antenna! To improve bandwidth on 14 MHz, the stubs were moved a half wavelength closer to the loops, with relays to disconnect them as shown in **figs. 11** and **12**. This enabled tuning for the 21- and 28-MHz band, where the radiation resistance is much higher, to be carried out at ground level as before.

The small delta loop is mechanically superior to a

Wide Dynamic Range and Low **Distortion – The Key to Superior HF Data Communications**

- Dynamic Range > 75 dB
- 400 to 4000 Hz
- BW Matched to Baud Rate
- BER < 1 X 10^{-5} for S / N = 0 dB
- 10 to 1200 Baud
- Linear Phase Filters



ST-8000 HF Modem

Real HF radio teleprinter signals exhibit heavy

fading and distortion, requirements that cannot be measured by standard constant amplitude BER and distortion test procedures. In designing the ST-8000, HAL has gone the extra step beyond traditional test and design. Our noise floor is at -65 dBm, not at -30 dBm as on other units, an extra 35 dB gain margin to handle fading. Filters in the ST-8000 are all of linear-phase design to give minimum pulse

- 8 Programmable Memories
- Set frequencies in 1Hz steps
- Adjustable Print Sauelch
- Phase-continuous TX Tones
- Split or Transceive TX/RX
- CRTTuning Indicator
- 8,600, or 10K Audio Input
- Signal Regeneration
- Variable Threshold Diversity
- RS-232 Remote Control I/O
- 100-130/200-250 VAC, 44-440 Hz
 8 or 600 Ohm Audio Output
- AM or FM Signal Processing
- 32 steps of M/S filter BW
- RS-232C, MIL-188C, or TTL Data
 Mark or Space-Only Detection
 - Digital Multipath Correction
- · FDX or HDX with Echo
- Spectra-Tune and X-Y Display
- Transmitter PTT Relay
- Code and Speed Conversion
- Signal Amplitude Squelch
- Receive Clock Recovery
- 3.5" High Rack Mounting

Write or call for complete ST-8000 specifications.



HAL Communications Corp.

Government Products Division Post Office Box 365 Urbana, Illinois 61801 (217) 367-7373 TWX 910-245-0784

Dayton Booth 231 & 232

Bandwidths of the input, Mark/Space channels, and post-detection filters are all computed and set for the baud rate you select, from 10 to 1200 baud. Other standard features of the ST-8000 include:

distortion, not sharp-skirted filters with high phase

avoids distortion due to frequency conversion or introduced by abnormally high or low filter Q's.

tone frequency; heterodyning is NOT used. This

distortion. All signal processing is done at the input



center-fed bent dipole (fig. 8A), since the center of



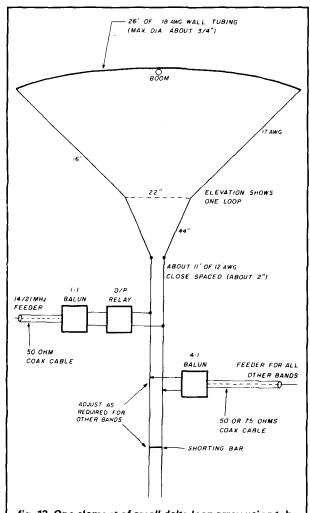



fig. 12. One element of small delta loop array using tubing end-fed with wires. These wires can be thin because current zeros occur at the crosspoints on 14 MHz, and on higher frequency bands Rg is relatively large. Element spacing is with the lower corners 4 feet apart. (Reproduced with permission of RSGB.)

the element doesn't have to support the weight of the feeder. Other features include higher radiation resistance and reduced effective spacing on 21 and 28 MHz, but on 14 MHz an adverse impedance transformation takes place at the bottom corner of the loops so that an estimated radiation resistance of 45 ohms referred to the top center is stepped down to only 20 ohms in the feeder. Using the relay as shown, this isn't important, since only a short length of line is affected. But with no relay and No. 14 AWG feeders, there's an estimated loss of 1 dB, as well as the narrow bandwidth already noted. With tubing elements as shown in fig. 12, the situation is more favorable, with an estimated impedance reduction of only 30 percent. There's also more flexibility because the impedance discontinuity at the ends of the tubing tends to offset the step-down at the bottom corner and the boom can, if necessary, be used to support a heavier feeder system.

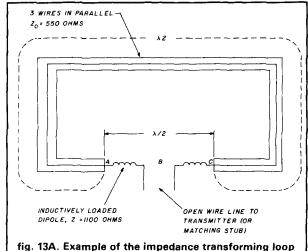

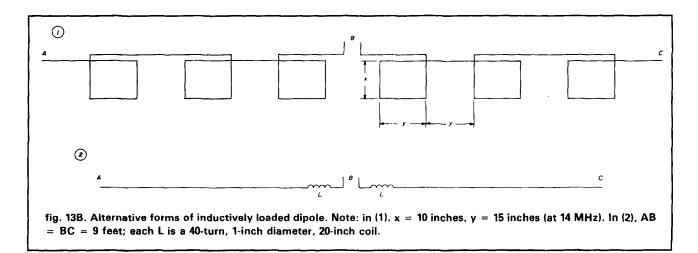showing principle of operation. (A) Loop acts as pair of $\lambda/4$ transformers so that a radiation resistance R appears (in this case) as 4R at the feedpoint.



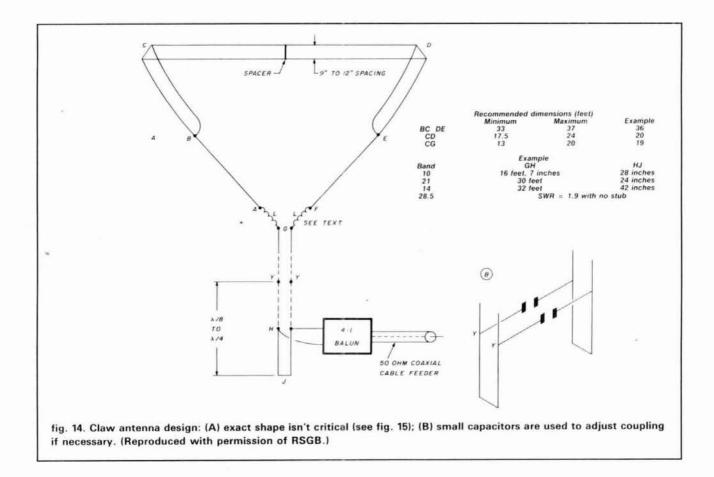

Figures 11 and 12 represent two extremes of design in which "anything goes." Typical observed SWR and f/b ratios are included in **table 1**. No additional coupling or neutralization was needed to obtain the results shown. In the case of the **fig. 12** configuration, it must

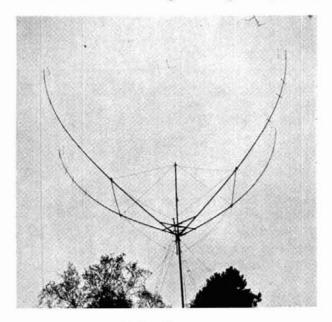


fig. 15. The Claw antenna.

be assumed that although on 14 MHz the radiation was coming from straight elements, the "quad loop effect" was operative with respect to coupling. In the antenna shown in **fig. 12**, it was found that for two-band operation (14 and 21 MHz), the relay could be omitted because of a chance combination of impedance transformations which caused the second harmonic resonance to occur at only 1-1/2 times the signal frequency. In general, I've not found it difficult to obtain efficient two-band operation of antennas without switching, but three bands are much more difficult.

the impedance transforming loop(ITL)

Disadvantages of the systems illustrated in **figs. 11** and **12** include the need for switches or relays in positions that are usually inaccessible. Even if this is acceptable, frequency coverage is restricted because as R decreases, switching devices have to meet increasingly stringent requirements with respect to capacitance and rf voltages.

Figures 13, 14, and 15 show a means of dispensing with relays and, to a large extent, the need for matching stubs. This was the outcome of an unsuccessful attempt to develop a small (i.e., 18-foot, 14 MHz) broadband folded dipole by slowing down the wave velocity.⁸ The idea was to trick the wave into thinking

BAND		Bandw	/idth for F/	B ratio	Bandwidth for SWR		
(MHz)	Antenna	>20dB	> 15dB	>10dB	< 1.25	< 1.5	<2.0
14	S.D.L. (wire)		140	280	110	190	300
	S.D.L. (tube)	150	220	385	225	390	
	Claw No. 1	40	120	220	160		330
	Claw No. 2		145	300		,	230
	Folded Dipole			230	100	260	350
21	S.D.L. (wire)			320	110	205	370
	S.D.L. (tube)			550	360		
	Claw No. 1	85	210	350	330	420	
	Claw No. 2			400		320	380
	Folded Dipole			260			450
28	S.D.L. (wire)				190		500
	S.D.L. (tube)			800	550	800	
	Claw No. 1		240-300	600	180	370	680
	Claw No. 2	170	840	1000		1000	
	Folded Dipole					280	1000

the element was larger, but this was unsuccessful. Being difficult to draw and of limited practical interest, its somewhat fearsome appearance will not be inflicted on the reader, though some performance figures are included in **table 1**. The surprise came in the form of a chance discovery that long feeders could be connected without degrading the bandwidth; the explanation, though elusive, led eventually to the design of a number of antennas bearing little resemblance to the original dipoles.^{7,9}

principles of operation

Figure 13A illustrates a small loop element which could be any shape. Two or more half-wave wires are used in parallel for the top part of the loop, resulting in a low value of characteristic impedance Z_{OT}.

The remainder of the loop consists of a second $\lambda/2$ dipole with a high value of characteristic impedance, Z_{OB} ; this can be a helix as shown, or inductively loaded in other ways. Each dipole functions as a $\lambda/4$ transformer so that the radiation resistance, R, after being stepped up to the value

$$Z_{OT}^2 / R$$

at the ends of the top dipole, is then stepped down to

$$(Z_{OB} / Z_{OT})^2 \cdot R$$

at the feedpoint. As illustrated, a typical R value of 50 ohms is stepped up to 200 ohms at the feedpoint, which is high enough to ensure that bandwidth remains an intrinsic property of the antenna and is free from serious degradation due to the feeder. A selection of Z values is given in **table 2**. Depending on size and construction, the lower dipole may be a thin wire unloaded V or one of the alternatives shown in **fig. 13B**. All of these arrangements have been used suc-

Table 2. Design data for ITL antennas.

Characteristic impedance for various wire sizes and combinations.


Number of conductors	Diameter (inches)	Spacing (inches)	Z₀(ohms)
1	0.04		1000
1	0.8		650
2	0.04	4	690
2	0.04	6	640
2	0.04	12	550
3	0.04	4	550
4	0.04	4	490

Equivalent $Z_{\rm O}$ of lower dipole (wire diameter, 0.04 inches) with inductive loading.

Physical length of dipole (wavelengths)	Equivalent Z₀ (oħms)	
(wavelengths)		
0.375	1200	
0.3	1500	
0.25	2000	
0.2	29000	
of some length dep		Iz. However, because e slightly different for pelical windings

cessfully. The usual objections to inductive loading don't apply because the radiation is mainly from the top part of the loop. This comes about because the current is stepped down in the ratio of the impedances; because the lower dipole is shorter; and because the current distribution in it is sinusoidal or triangular, in contrast to the almost uniform current in the top dipole. This constitutes a major advantage over the quad loop, in which the mean height is dragged down by radiation from the lower side. On the other hand, there is some radiation from the sides; it can be cancelled

AVCOM SATELLITE TEST EQUIPMENT

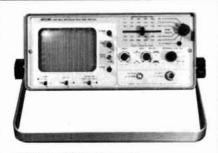


AVCOM PSA-35A PORTABLE SPECTRUM ANALYZER

\$1965

AVCOM's PSA-35A Portable Spectrum Analyzer is the first spectrum analyzer designed for the satellite communication industry. The AVCOM PSA-35A offers frequency coverages of 10 to 1750 MHz and 3.7 to 4.2 GHz. The PSA-35A is portable and can be operated from 115 VAC (220/240 VAC available) or its own rechargeable internal batteries. The AVCOM-PSA-35A will quickly become the most important test instrument you own for installing or servicing TVRO systems.

AVCOM PSA-35A ACCESSORIES

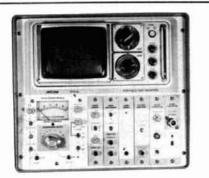TISH-40 - Terrestrial Interference Survey Horn - \$127 SSC-70 - Signal Sampler and Calibrator - \$175 AVSAC - AVCOM Spectrum Analyzer Carrying Case - \$69 WCA-4 - Waveguide to Coax Adapter - \$78 ORM-35 - Quick Release Rack Mount - \$124



AVCOM PTR-24 PORTABLE TEST RECEIVER

AVCOM's Portable Test Receiver has a full range of outputs to provide signals for large TV monitors, video recorders, and audio amplifiers. A special IF sampled output is available for observing 70 MHz IF signals including TI, if any.

\$1375

on the PSA-35A Portable Spectrum Analyzer. A large easy to read signal strength meter is located on the control module and an audible signal strength indicator function is also provided.



AVCOM STA-70D SCPC TEST ANALYZER

The AVCOM STA-70D conveniently connects to the 70 MHz IF output of your C or Ku band downconverter. Signal levels, interference, and all carriers appear on the spectral display. The display span is continuously adjustable from 0 to more than a full transponder, the display sensitivity is switchable from 2 dB or 10 dB per division.



MTG-3600 MICROWAVE TRACKING GENERATOR \$1865

Turn your HP 8566 Spectrum analyzer into a powerful network analyzer with scalar frequency response function. AVCOM's model MTG-3600 Tracking Generator outputs a -5 dBm (typical) tracked RF signal from less than 100 KHz to over 1.0 GHz. Flatness ±1.5 dB typical. IF feedthru below -65 dBm typical. L.O. is a phase locked cavity oscillator referenced to an oven stabilized crystal oscillator.



\$1960

AVCOM MSG-1000A 0 to 1000 MHz MICROWAVE SWEEP GENERATOR \$1565 The MSG-1000 generates signals from 100 KHz to 1000 MHz. Its LED frequency readout is accurate to ±1 MHz. The MSG-1000 can be used as a marker generator for the PSA-35B Spectrum Analyzer. Other possible uses include: sweeping IF filters and amplifiers. Built in 1 KHz FM modulation standard. Operates from 110 VAC or its own internal rechargeable batteries.

AVCOM MSG-5 3.7 to 4.2 GHz \$1087 MICROWAVE SWEEP GENERATOR AVCOM's MSG-5 Microwave Sweep Generator provides the capability of generating very accurate signals in the 3.7 - 4.2 GHz satellite communications band. A sweep capability is standard over the entire 3.7-4.2 GHz band to bandwidths less than one MHz at any center frequency between 3.7 and 4.2 GHz. Frequency can be read on an LED display with better than 1 MHz accuracy. A built-in modulation generator can verify TVRO system performance. An external video modulation input is included. The MSG-5 features line or battery operation, portability, and rugged construction.

AVCOM MSG-1750A .950 to 1750 MHz MICROWAVE SWEEP GENERATOR \$1275 The MSG-1750A digital frequency readout is accurate to \pm MHz. The MSG-1750 has been developed for international use with the wider block frequency band from 950 to 1750 MHz. Operation from 220 VAC is standard, 110 VAC is available. The MSG-1750A can be used as a marker generator for the PSA-35A Spectrum Analyzer to accurately specify TI filters or to establish performance criteria for satellite communications contracts.

AVCOM MSG-2000A 1000 to 2000 MHz MICROWAVE SWEEP GENERATOR \$1282 The MSG-2000A generates signals from 1000 MHz to 2000 MHz. Its LED frequency readout is accurate to ±1 MHz. The MSG-2000A can be used with the AVCOM PSA-35B Spectrum Analyzer to specify TI filters or to establish performance criteria for satellite communication installation contracts. Built-in 1 KHz FM modulation standard. The MSG-2000A can be operated from an 110 VAC external power source or from its own internal rechargeable batteries.

Terms and specifications subject to change without notice.



500 SOUTHLAKE BOULEVARD RICHMOND, VIRGINIA 23236 TELEPHONE (804) 794-2500 TELEX 701-545 FAX 804-794-8284



by reverting to a more or less triangular shape as shown in **fig. 14**. Assuming an ITL to be designed for 14 MHz, operation on the higher frequency bands differs little from that of the small delta loops described earlier; at 21 MHz there tends to be some "wrongway" impedance transformation, suggesting the desirability of matching stubs at ground level in the case of long feeders. Concentrated loading, as shown

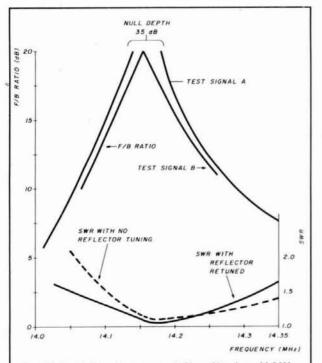


fig. 16. Typical performance of Claw No. 1 on 14 MHz. F/B ratio curves demonstrate null-filling due to any slight error in adjustment. In this case, one test signal was slightly too close. SWR rapidly increases as the π approaches zero. The reflector was adjusted for nulls at 140-150 degrees, but curves were roughly repeatable over a range of 110-180 inches without readjustment of coupling.


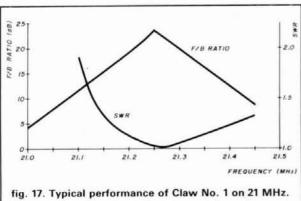



fig. 17. Typical performance of Claw No. 1 on 21 MHz. Note steep rise in SWR at low frequencies - i.e., as ϕ decreases.

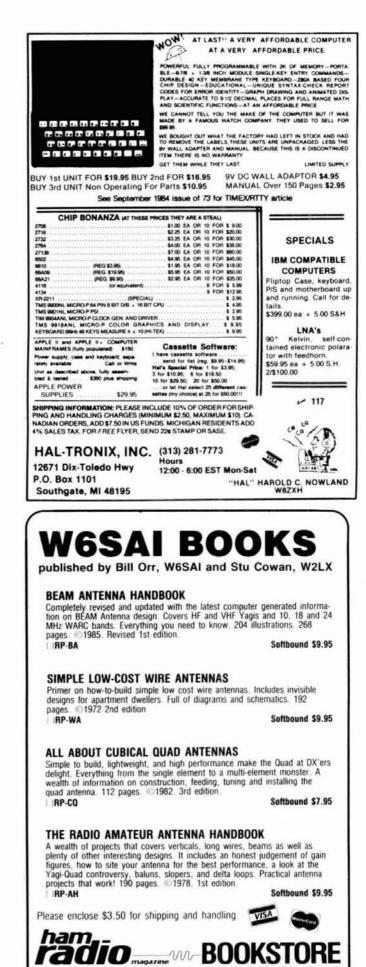

GREENVILLE, NH 03048

May 1987 🚾 29

(603) 878-144

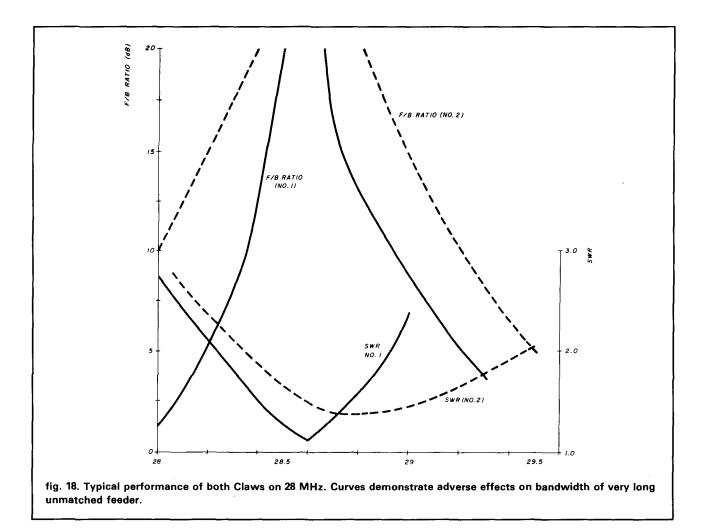


in **fig. 13B2**, improves matters on 14 MHz by increasing Z_{OB} (see **table 2**), but reference to a Smith Chart suggests that at 21 MHz this could lead to an increase of SWR in the open-wire line of 2 or more. On the other hand, with long coils of small diameter (20 inches x 1 inch), as shown in **fig. 14**, much better agreement between theory and practice resulted from regarding them as a harmless continuation of the traveling wave system.

construction

Figures 14 and **15** illustrate the latest version of the Claw antenna, which uses two pairs of fiberglass fishing rods 13 feet long, extended at their lower ends by an additional 6 feet of 1-inch diameter fiberglass tubing. These are plugged into alloy sockets which radiate outwards from the top of the mast. They are braced back with further lengths of fiberglass tubing to a short mast extension. The elements are held apart by 6-foot spacing rods of 1/2-inch diameter alloy tubing. Plastic rod end-pieces are used to keep the rods a few inches clear of the elements; even so, these may be responsible for some of the coupling. The tips of the fishing

rods are pulled in by nylon fishing line to give an element spacing of 12 feet. Points on the rods are guyed back to crosspieces at the top of the mast. The top wires are held 11 inches apart in the horizontal plane by fiberglass spacers cut from the discarded tips of the fishing rods. Additional spacers on the rods themselves (with fishing-line ties) are used to maintain even tension in the wires to avoid flexing and breakage. Earlier versions used three copper wires spaced 4 inches apart, but the benefit from the extra wire hardly justifies the added complication (see table 2). The latest version uses No. 16 AWG aluminum alloy wire, which reduces weight for a given rf resistance, but increases windage. Since the rf resistance is only half that of a single wire, mechanical considerations are more likely to be the deciding factor. Wires break if not kept under tension, but with two antennas over a period of three years - which has included periods of heavy winds - no fishing rods have broken, and there has been no other damage to the main structures.

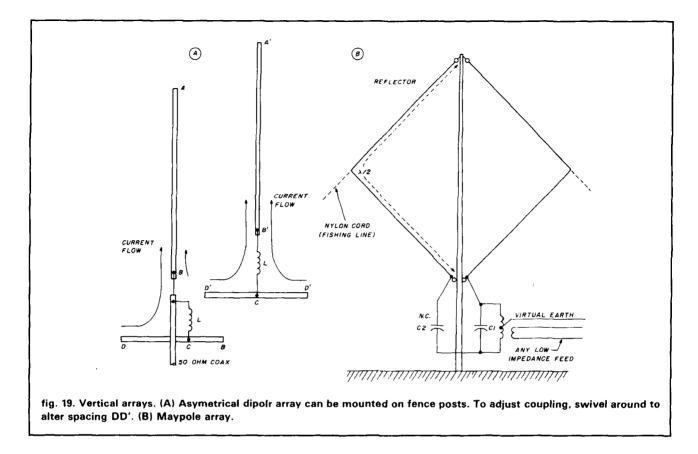The same wire gauge is used throughout. The loading helices are each wound with 40 turns over a total



length of 20 inches, partly near the lower end of the rod extensions and partly on the bracing struts. Because of the low radiation resistance on 10 MHz, it's advisable to provide matching as close as possible to the antenna. In one case, 28-inch stubs were placed 16 feet, 7 inches from the element. Later, for greater convenience I used a pair of series-connected 10-pF capacitors near ground level. The location could be determined by finding points of "zero" current and then moving 3 feet closer to the antenna. Matching on the other bands was used initially, but discarded because it made no difference in signal strengths, though table 1 suggests the loss of some bandwidth. Even on 10 MHz, despite the additional 120 feet of open wire line (No. 19 AWG), the loss without matching was less than one S-unit. Measured performance data for both Claw antennas is included in table 1. The plots of f/b ratio and SWR shown in figs. 16, 17 and 18 are typical of results obtained with Claw No. 1.

alternative designs

The loops can also be suspended from spreaders between two supports. In this case planar loading (an idea suggested to me by Steve Hart, VK5HA), as shown in **fig. 13B**, is suggested. The assembly can be supported by three lengths of nylon fishing line with small ring insulators cut from fiberglass tubing to keep adjacent edges apart. I find that nearly a 3:1 reduc-

tion in length can be achieved this way; because it uses less wire, its efficiency is greater than with helical loading. For this reason, it was used in the first two versions of the Claw,⁷ but helical windings in this case are easier and neater, with losses insignificant. Similar loops can be suspended from their centers in inverted V fashion. I've also built a rotary version of such an antenna modelled after the one shown in fig. 3B. This used a lightweight mast extension surmounted by a 1/2-inch diameter aluminum boom. Two fiberglass radial arms were used to hold up the dipole ends. Apart from the neutralization problem mentioned earlier, this worked well on 14 MHz. A three-element version of the Claw was also constructed; since only triband operation was required, I was able to use a coaxial feeder for the center element and a relay to switch in an additional length of helix on 21 MHz. The third element was effective on 28 MHz and was indirectly useful for 10 MHz because, though not in use, it allowed wider spacing between the other two elements without degradation of performance on 28 MHz. On 14 and 21 MHz, there was no improvement compared to using any one of the three possible pairs on its own. SWR on 14 MHz could be varied between 1.0 and at least 5.0 by tuning the parasitic elements! The problem was basically one of "too many variables," and it was concluded that for three elements to be viable, they would need to be spread out along



A magazine dedicated to quality and sportsmanship in amateur radio operating. Fresh, timely, practical and down to earth reading for little pistols and big guns. Written by the world's best in their fields: ON4UN, SMØAGD, LZ2CJ, VE3BMV, KH6BZF, DJ9ZB, ZS6BRZ, W1WY, N2AU, K7GCO, K4ZN, W4GF, VE3JTO, WB4ZNH, WB9TBU, K02M, NS6X, W3FG, KA3B, K1PLR, N7CKD, VE3XN, ABØX, JE1CKA and others.

Includes DX News, QSL Info, 160m, 80m, 10m, 6m columns, DXpeditioning, Propagation, Awards, Contest rules and results, Traffic - Emergency, FCC News, New Products, Antennas, Technical news and articles, equipment reviews and modifications, computer programs, Radio Funnies, Club Life, RTTY, VHF/UHF, Mail Box, Classified Ads and much more in a magazine format with the speed of a bulletin.

RADIOSPORTING sponsors DX Century Award, Contest Hall of Fame and World Radio Championship contest.

"Your publication is superb! Keep it up!" Joe Reisert, W1JR

"Your W2PV articles are priceless. Your magazine is super!" Rush Drake, W7RM

"Let me congratulate you on a very impressive magazine. Just what I've been looking for as a DXer and Contester!" Dick Moen. N7RO

"RADIOSPORTING, once received, cannot be tossed aside until it is read from cover to cover. Then reviewed again and again." Chas Browning, W4PKA

<u>Subscription rates:</u> 1 year USA \$18, Canada CDN\$26, Overseas US\$23; 2 years \$33, \$48, \$42 respectively. Single issue \$2. USA First Class Mail add \$8/year, DX Air Mail add \$15/year.

TRY US! SUBSCRIBE OR SEND \$1 FOR YOUR SAMPLE COPY.
RADIOSPORTING Magazine

PO Box 282, Pine Brook, NJ 07058, USA

a boom; the "Claw" concept would then lose most of its attraction in return for a relatively small improvement in performance.

vertical arrays

Vertical beams can also be constructed using controlled coupling.¹⁰ Figure 19 shows two examples. The first is an "asymmetrical dipole" array that uses inductively-loaded counterpoises to form the lower half of the dipoles. The inductances can take the form of linear loading.⁵ The elements are movable and can be plugged into sockets on fence posts. Coupling is varied by rotating the counterpoises towards each other and all adjustments are conveniently accessible. Each half of the dipole should be resonated separately against a $\lambda/4$ wire. The second can be regarded as a "vertical VK2ABQ" antenna. It's best to use four wires at right angles; adjacent pairs may be connected in parallel, though they can also be used in a threeelement configuration. In the two-element case, which is recommended, overcoupling was experienced, requiring neutralization as shown. ("Zepp feed" can also be used, provided the open end of the feeder is closed with a $\lambda/4$ stub^{5,10} as recommended by G6CJ.)

conclusion

My intention has been to provide guidelines, rather than blueprints, for the construction of antennas tailored to suit individual needs. The Claw designs will be useful even if the best mast available is only a garden post, and I hope that some who have decided regretfully that beams are "not for them" will have second thoughts. The null-steering and beam-reversal capabilities are particularly useful. In addition to coverage of six bands — with "monoband" performance on several — Claw elements are particularly suitable for use as top-loaded verticals for the lower-frequency bands.

references

1. L. A. Moxon, G6XN, "Small Beams with Big Performance," ham radio, March, 1979, page 12.

2. J. L. Lawson, W2PV, "Yagi Antenna Design," ham radio, May 1980, page 18.

 Bloch, Medhurst and Pool, "A New Approach to The Design of Superdirective Aerial Arrays," *Proceedings of the IEE*, Part III, September, 1953.
 W. Walkinshaw, "Theoretical Treatment of Short Yagi Aerials," *Journal of the IEEE*, Part IIIA, March-May, 1948, page 598.

5. L. A. Moxon, G6XN, "HF Antennas for All Locations," Radio Society of Great Britain, 1982.

 Pat Hawker, G3VA, "Technical Topics: Multiband Arrays with 'KISS," Radio Communication, August, 1983, page 705.

7. Pat Hawker, G3VA, "Technical Topics," Radio Communication, March, 1985.

8. Pat Hawker, G3VA, "Technical Topics: Antennas That Slow The Wave," Radio Communication, April 1984, page 316.

9. Pat Hawker, G3VA, "The 'Claw Mark 4' Antenna," Radio Communication, January 1987, page 28.

10. F. Charman, G6CJ, "Aerial Reflection," R.S.G.B. Bulletin, December, 1955.

11. Private communication.

G6XN's book, *HF Antennas for All Locations* is available from Ham Radio's Bookstore for \$11.95 plus \$3.50 S&H.

ham radio

Introducing...

The AR 2002 The Professional Monitor Receiver



Now! In America

For the first time, the AR2002 is available in the U.S.A.! Acclaimed worldwide for its full spectrum coverage, its superior sensitivity, excellent selectivity and convenient, compact design; it has all the features a sophisticated and discerning public service band radio user desires. Experts in Europe, and around the world report excellent performance in independent lab tests. For example: sensitivity across all bands will typically exceed .3 microvolts in NFM. And now the AR2002 is available to you exclusively through this offer.

Peformance Above and Beyond

You'll hear signals from 25 through 550 MHz, plus 800 MHz through 1.3 GHz. In any mode: narrow band FM, wide band FM, or AM. Search through entire bands, or enter selected frequencies into any of 20 memory channels. The sidelighted LCD gives full information on status and programming. Profession quality hinged keys and a digitized front panel control knob make tuning easier than ever before. There's even a real time clock with backup, a signal strength meter and a front panel head phone jack. Plus, programmable search increments, a laboratory quality BNC antenna connector with switchable attenuator, full memory backup, and power cords for AC or DC operation. A professional quality swivel mount telescoping antenna is also supplied.

...And More!

Every AR2002 has a special connector on the rear panel. It interfaces to our custom RC-pack. A little device that makes the AR2002 controllable by ANY computer with an RS-232C port. The possibilities that result from this option are nearly limitless. In effect, virtually your only monitoring constraint will be your imagination.

Yet Convenient to Own

The AR2002 is available exclusively through us — so call us direct, TOLL FREE. We'll be happy to answer any questions you may have. And if you respond like thousands of other monitor users the world over, we'll be shipping you an AR2002 within 48 hours by surface UPS for only \$455. Plus we pay all freight and handling charges. Remember to ask about our custom test and triple extended buyer protection warranty plans, and our express shipping option. If you're not satisfied within 25 days, return your AR2002. We'll refund your purchase and return shipping costs. There are no catches, no hidden charges.

The AR 2002 The Professional Monitor Receiver



10707 East 106th Street, Indianapolis, IN 46256



Warehouse: 22511 Aspan Street, Lake Forest, CA 92630 (7% "D \times 5% $_{16}$ "W \times 3% "H Wt, 2 lbs., 10 oz.)



9 Autry Irvine, CA 92718 (714) 458-7277 Canadian Distributor: Eastcom Industries, Ltd. 430 Signet Drive Weston, Ont. Can 49L 2T6 (416) 743-7801

219

	(416) 743-7801					
	ASTRON POWER SUPPLIES					
	HEAVY DUTY • HIGH QUALITY • RUGGED • RELIABLE •					
	RS and VS SERI	in Training		PERFORMANCE SPECIFICATIONS		
6 F4	SPECIAL FEATUR		-			
		ECTRONICALLY REGULAT RENT LIMITING Protects P		 INPUT VOLTAGE: 105 - 12 OUTPUT VOLTAGE: 13.8 \ 		
		urrent & continuous shorte		(Internally Adjustable: 11-1		
	 CROWBAR OVER 	VOLTAGE PROTECTION on		· RIPPLE: Less than 5mv pe	ak to peak (full load	
	except RS-4A.			& low line)		
		LATION & LOW RIPPLE at	low line			
	 Input Voltage. HEAVY DUTY HE 	AT SINK • CHASSIS MOU	INT FUSE			
	THREE CONDUCT		in root			
INSIDE VIEW – RS-12A	ONE YEAR WARK	RANTY • MADE IN U.S.A.				
and the second se	Contraction of	Print in the party of				
				Gunn	1 miles	
	1	100				
AP A U LACON		ARTHON		Parenos		
MODEL RS-50A		EL RS-50M		MODEL VS-50	M	
RM-A Series	17 X 5% KACK	MOUNT POWER SUPPLIES Continuous	105.	Size (IN)	Shipping	
	Model	Duty (AMPS)	(AMPS)	HXWXD	Wt. (lbs.)	
1	RM-35A	25	35	$5\frac{1}{4} \times 19 \times 12\frac{1}{2}$	38	
	RM-50A	37.	50	51/4 × 19 × 121/2	50	
distance -	 Separate Vo RM-35M 	It and Amp Meters	35	$5\frac{1}{4} \times 19 \times 12\frac{1}{2}$	38	
MODEL RM-35A	RM-50M	37	50	$5\frac{1}{4} \times 19 \times 12\frac{1}{2}$	50	
		Continuous	ICS*	Size (IN)	Shipping	
RS-A SERIES	MODEL	Duty (Amps)	(Amps)	HXWXD	Wt (lbs)	
	RS-4A	3	4	3¾ x 6½ x 9	5	
A DOWNER OF THE OWNER OF THE OWNE	RS-7A	5	7	3¾ x 6½ x 9 4 × 7½ × 10¾	9 10	
	RS-7B RS-10A	7.5	10	4 x 71/2 x 103/4	11	
gamme -	RS-12A	9	12	41/2 x 8 x 9	13	
	RS-20A	16	20	5 x 9 x 101/2	18	
MODEL RS-7A	RS-35A RS-50A	25 37	35 50	5 x 11 x 11 6 x 13¾ x 11	27 46	
RS-M SERIES	N3-30A					
NO-M OLINES	MODEL	Continuous Duty (Amps)	ICS* (Amps)	Size (IN) H x W x D	Shipping Wt (lbs)	
And and a second se	Switchable volt a		(runps)			
(法、法	RS-12M	9	12	41/2 x 8 x 9	13	
	· Separate Volt and				10	
	RS-20M	16 25	20 35	5 x 9 x 10½ 5 x 11 x 11	18 27	
	RS-35M RS-50M	37	50	6 x 13¾ x 11	46	
MODEL RS-35M	10.001		(852)	3650.2373.42374374		
VS-M SERIES	Separate Volt a	nd Amp Meters				
	 Output Voltage Current limit ad 	adjustable from 2-15 vol justable from 1.5 amps	to Full Load			
5442	- ourient mint au	Continuous Duty	ICS*			
See See		(Amps)	(Amps)	Size (IN)	Shipping	
and the second sec	MODEL	@13.8VDC@10VDC@5VDC	@13.8V	HxWxD	Wt (lbs)	
	VS-20M	16 9 4	20	5 x 9 x 101/2	20	
MODEL VS-20M	VS-35M VS-50M	25 15 7 37 22 10	35 50	5 x 11 x 11 6 x 13 ³ ⁄4 x 11	29 46	
RS-S SERIES))				
	 Built in speaker 	Continous	ICS*	Size (IN)	Shipping	
	MODEL	Duty (Amps)	Amps	HXWXD	Wt (lbs)	
	RS-7S	5	7	4 x 7½ x 10¾	10	
18 C	RS-10S	7.5	10	4 x 7½ x 10¾	12	
and a second sec	RS-10L(For		10	4 × 9 × 13	13	
	RS-12S	9 16	12 20	4½ x 8 x 9 5 x 9 x 10½	13 18	
	RS-20S					

homebrew antenna mount

Hand tools and standard hardware are all you need for this project

A number of years ago I visited a ham friend who proudly showed me his new tribander. Sitting atop a rotatable mast secured to a ground-mounted fixture, the antenna could also be lowered so that one could work on it comfortably.

We lived in an apartment then, and the only antennas I could install were dipoles for 80 and 40 meters and a vertical for 20, 15, and 10. Later, when we finally bought a home, I found that despite a large back yard, power and telephone lines — as well as trees we'd planted — put an end to my plans for an antenna farm.

Though finding antennas for 80 and 40 meters was no great chore, finding room for a tower or mast was. It was then I realized I already had a platform for working on my antenna — namely, the gently sloping garage roof. I decided I might be able to put up something similar to the arrangement my friend had shown me years before.

My plan was to use a push-up mast, supported somehow at the bottom, and drive it, with the antenna on top, from ground level. I did some shopping for parts and spent some time at the work bench; using hand tools only (with the exception of an electric drill), the result was a mast which has been in use now for a dozen years or more, with no problems (**Photo 1**).

initial considerations

One of the first things to realize is that your antenna isn't going to rotate at 5000 rpm. It turns *very* slowly (my rotor takes a full minute to turn 360 degrees), and hence puts little strain on the bearing you'll use. Aside from the inevitable accumulation of dirt, which is easily removed with a stiff brush and some paint thinner, I've had no problems with the bearing at all. The second thing to realize is that when you have everything done, extending the push-up mast with the antenna on top of it isn't easy unless you've made some advance preparations. Suppose you've acquired such a mast; it will probably have three or four sections, depending on the height you've chosen. Mine has four, and the outside diameter of the lowest section is 2-1/4 inches. The lifting problem isn't one of weight, but of having some way of knowing when you're reaching the point at which you should stop lifting and secure the section with the clamp provided, and maybe even drill to pass a 1/4-inch bolt through the two sections if you're a bit timid.

mast inspection

Lay the mast out on the ground, fully extended, and examine the point at which the smallest section emerges from the one below it.

Although the smaller section of my mast won't separate from the larger one, there's an illusion at work: when you're lifting the smallest section, with the antenna mounted on it, you become absolutely convinced that at some point the whole thing will pull out, leaving you on the roof with 10 feet of mast and an antenna in your hands and nothing else to hold them. To avoid this, use paint or some other marker to warn you when you're just a few inches from the clamp-off point. Do this with all of the sections. At this point, let me add a caution: whenever you're extending or collapsing the mast, wear heavy gloves! (I use a pair of leather gardening gloves.) The mast sections have a nasty habit of pinching your flesh between them. *Wear those gloves!*

mounting the mast

Decide where you'll mount the mast. For aesthetic reasons, an exterior garage wall is a good choice; you may prefer to attach hardware through to the exposed studs rather than to a finished interior or exterior wall of your house.

You'll also have to decide how far off the ground the lower end of the mast will be supported. This will

Howard A. Bowman, W6QIR, 5872 West 77th Place, Los Angeles, California 90045



Photo 1. Complete installation.

depend on the length of your rotor, which will hang below the "shelf" you'll build (see **photo 2**), and should clear the earth by a few inches. At this point, do one other thing as well: measure the inside diameter of the lowest section of your mast.

Before you head out to the plumbing supply shop, try to visualize what your array of mast, rotor, and connecting pieces of pipe will look like overall. A short length of pipe should fit snugly inside the lower end of the mast. (Though it doesn't have to be an exact fit, it should be fairly close.) It should be 5 or 6 inches long and threaded on both ends; you'll find it at your local plumbing supply house, described as a "nipple." You'll also need two lengths of pipe — one to run from the support you'll build to the upper clamp of your rotor, and the other to run from the lower clamp of the rotor to about a foot below the surface of the earth. One end of the upper piece must be threaded. Aside from this, it's probably simpler to get one long piece and cut it in half yourself.

You'll also need a reducing fitting. At its larger end, it should accept the threads on the nipple, and at its smaller end it should accept the threads on the longer piece of pipe. Caution: pipe sizes are guaranteed to confuse everyone in the world except plumbers. Pay no attention to the designated pipe sizes; use a tape or a scale and measure everything for yourself. Try the mating pieces to be sure they do what they're supposed to do. That way you won't encounter unwelcome surprises.

The next step takes place in your own workshop. Screw the nipple tightly into the reducing fitting, securing it by drilling and tapping for a machine screw of some convenient size. (The screw won't bear any load, but will keep the two parts from coming apart.) Then slide the nipple into the lowest section of the mast until the lower edge of the mast section rests on the reducing fitting.

At this point I drilled and tapped for 1/4 inch x 20 machine screws and used hex-head screws about 1/2 inch long. This was overkill, but, to some extent, the number of screws you use will depend on the snugness of the fit between the lowest mast section and the pipe inside it. The idea is to square things up as well as you can. If you need four screws 90 degrees apart, use them.

You'll need a bearing with an inside diameter large enough to accept the smaller end of the reducing fitting. The tapered shoulder of the fitting will ride on the inner race of the bearing. I've used two bearings — one a standard ball bearing and the other a tapered roller bearing. Either does fine. The inside diameter of each is 1-5/8 inches, and the outside diameter is just a bit over 3 inches. It's important that the slanted portion of the reducing fitting fit inside the bearing, so take careful measurements or take the fitting with you when you shop for the bearing at an establishment that stocks new and used machinery. In a pinch, you may find one at an automobile junkyard.

mast and rotor support

Having come this far, you've done all but the drudgery of making some kind of a support for the mast and rotor. Mine is made of ordinary 1-1/4 inch angle iron, which you can find at any iron fabricating shop or even at some large hardware stores. If you get it at a hardware store, it will most likely be sold in 6-foot lengths; you'll need three of them. If you get it from a shop, be careful. Be sure of your measurements, since the cutter may distort the metal where the cuts are made, making part of it unusable for your purpose.

In planning your shelf, be sure to consider its height above ground and its depth. The shelf must be high enough so that your rotor can hang below it with a few inches clearance above ground. Its depth depends upon the distance your mast will be positioned from the wall. In my case, eaves extend 7 inches from the wall, meaning that my shelf had to be about 15 inches deep to allow the mast to clear the eaves and still provide adequate support. If you have no eaves to contend with, you may be able to make the shelf only 8 or 10 inches deep. (Keep in mind that this dimension will have some effect on the amount of angle iron you'll need.)

triangular supports

The next step is to make two right-angled triangles out of angle iron. They should be made so that they're mirror images of each other; that is, each should have the open sides of the angle iron pieces facing the other. One leg of the triangle will extend outward from the wall, another will fit vertically against the wall, and the third will complete the triangle by extending from some point near the outer edge of the horizontal piece to some point toward the lower end of the vertical piece.

Start by drilling both the vertical and horizontal pieces where they overlap and bolt them together. I used 1/4-inch bolts on mine. Use a square to make certain that the angles form a 90-degree angle. Measure carefully for the third leg, cut it to size, and, once again, drill for bolts. Do the same with the other three pieces of angle iron, making sure that the open sides of the triangles face each other.

Now, try to mount these triangles — at least temporarily — to the wall to which they'll be bolted. Once you've decided how far your shelf is to be above ground, locate a point on a stud adjacent to where you want to mount the antenna. (That point should be 2 or 3 inches below the intended level of the shelf.) Drill a small hole through from the inside, keeping it as close to the center of the stud as you can. Now move to the stud on the other side of the intended location and drill a similar hole. These holes should go all the way through the studs and the outside covering of the wall.

Locate one of the triangles over the small hole, have someone hold it there, go back inside with your drill, and, using the hole through the stud as a pilot, drill into the metal of the triangle at least far enough to make a mark. Now both holes can be enlarged to accept a 5/16-inch diameter bolt. You can also drill another hole in the triangle vertical leg toward its lower end. Align things carefully so that the leg is vertical, then drill through the wall and the stud for a second bolt.

Studs are sometimes not exactly vertical, so this hole may be a bit off center. Don't worry. If the triangle is vertical and your bolt has a good bite on the wood of the stud, you'll be all right. Use a washer under the head of the bolt, and a fender washer (one that is larger in diameter), a lock washer, and a nut on the inside.

Locating the second triangle is a bit tricky because you want its top and the top of the first triangle to

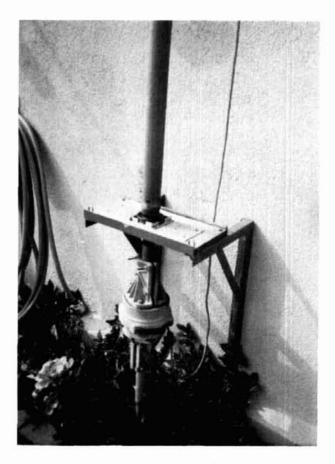


Photo 2. Lower support: the shelf.

be as level as possible. The easiest way to do this is to have someone hold the second triangle against the wall so that one edge of the vertical leg is beside the hole you've drilled through the wall, and so that a spirit level across from the first triangle to the second shows that both are at the same height. Carefully mark the angle iron beside the point at which you've drilled, then drill the angle iron for the bolt. Locate the position of the second bolt just as you did for the other triangle.

joining the triangles

At this point you have two triangles bolted to the outside wall of your garage. The next step is to join them, using two pieces of the same angle iron. One piece should join the outer ends of the triangles, and the other will be several inches closer to the wall, depending on just where the mast will come. It should be midway between these two crosspieces. Having located both pieces, and drilled them and the upper leg of the triangle to accept 1/4-inch bolts, secure them in place.

shelf assembly

You'll note that these two cross-pieces and the triangle legs to which they are bolted form a rectangle. Find a piece of wood about 3/4 or 1 inch thick and



Photo 3. Lower support viewed from different angle.

cut it to lie inside this rectangle. Then find a piece of aluminum about 1/8 inch thick to go on top of it. (I used marine plywood for the wood, but a solid piece would do just as well.) This assembly - the pieces of aluminum and wood — will form the actual shelf. Drill them for mounting with 1/4-inch bolts, but don't assemble them yet. With the two pieces clamped or bolted together, mark the center by drawing cross lines from the corners. This is where the bearing will rest. You'll need to drill a hole through both pieces that's large enough to clear the inner race of the bearing, and any ham who has had to make a hole for a meter can cope with this. One precaution: make a small pilot hole through both pieces first. You may find that a large socket-hole punch will do for the aluminum, and an expansion bit for the wood.

bearing placement

Once you've made this hole, you can mount everything but the bearing. Center the bearing over the hole and mark around the circumference of the bearing with a pencil. You'll need to devise something to make a "fence" around the bearing to hold it in place. I used some $1/2 \times 1/2$ -inch aluminum angle stock I happened to have. Almost anything will do, so use your imagination. You can use small machine screws to fasten this fence to the shelf; there's little strain on it. When it's complete, the bearing should drop neatly into the hole.

When the bearing is in place, lean over and sight down through it to the earth beneath and mark the spot with a chip of wood or some other marker. You may want to drop a plumb bob down to mark this spot; it's where the lower pipe on your rotor will enter the earth.

Your next job is to dig a square hole about a foot

deep with this point at the center. You can also prepare the length of pipe by drilling holes through it at a point which will be well below the surface of the earth. Run some long bolts through it, leaving them so they extend a couple of inches on either side of the pipe. Two or three of these should do nicely.

What will happen, you ask, when you get the mast, the various pieces of pipe, the bearing, the rotor, and everything else set up on the shelf? Answer: *it will all fall over*. To prevent this, you'll need an upper support, located directly above the shelf and as high on the wall as you can get it. Perhaps "support" is the wrong word, since it doesn't bear any load. All it does is hold the mast in a vertical position and allow it to rotate within a loose collar.

wall-to-mast structure

Install a piece of the angle iron horizontally on the wall, bolted between the same pair of studs as the shelf. Then put the mast up temporarily and make sure it's in a vertical position (use a spirit level). You'll probably need a helper to make sure the mast stays in this position while you measure the distance from the wall to the nearest edge of the mast.

Now, using the leftover pieces of angle iron, you'll need to assemble a rectangular structure as deep as the distance from the wall to the mast. It needn't be as wide as the distance between the studs; mine is only 8 inches wide. It must be wide enough, however, to accept either a band bent to go around the mast, or perhaps a large U-bolt. It should be braced cornerto-corner so that it retains its shape, and further braced by two supports running from the rectangle down to a point on the wall. These last two supports may be pieces of the 1-inch strap iron, suitably bent in your vise, and bolted to the wall. These bolts needn't go through the studs, but remember to put those large fender washers on the inside.

erecting the mast

Now put the mast up on the fittings you've made. Clamp the rotor to the pipe extending below the bearing. Clamp the other piece of pipe to the lower part of the rotor. Mix up some cement and pour it into the hole below the rotor. Go inside, wash your hands, and find yourself a good book that will take you a couple of days to read while the cement cures.

guying

When the curing process is complete, you may want to shovel some dirt back over the top of the cement block. You'll then be ready to install the antenna on the topmost section of the mast. At this point, you'll probably recall that your mast was supplied with a set of guy rings — one to fit atop each of the larger sections. In large part, whether you'll use any at all

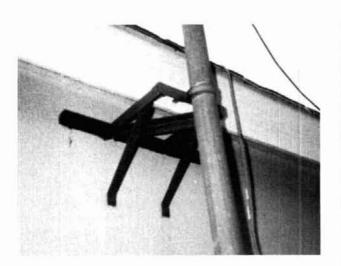


Photo 4. Upper support.

will depend on how high your mast is, how much support you can give it at the bottom, and whether experience has told you if you're likely to have a wind problem.

Consider the matter of support at the bottom. My lower installation is on a planter, but yours may be at ground level. Although I had eaves to contend with, you may have none. If your installation allows positioning your lower shelf close to the ground and your upper support near the top of the wall, you may have 7 feet or so between the bearing and upper support. (I have 4.) If there are no eaves to force you to extend your structures away from the wall, they'll be more rigid; you may be able to avoid guys entirely.

In my case I thought it best to have a set of guys at the bottom of the topmost section of the mast. Hams traditionally have followed the practice of using three guys spaced 120 degrees apart. However, the guy rings supplied, for reasons known only to the manufacturer, have four holes spaced 90 degrees apart, and a fifth hole midway between two of the others. It appears not to matter. Just use what you can, and don't tighten the guy wires as if they were violin strings. Remember, the mast is going to rotate inside that guy ring, so leave a bit of slack in the wires.

installing the antenna

At last you're ready to install the antenna atop the mast. I certainly wouldn't advocate installing a monster with a 30-foot boom, but I used to have a tribander on the mast, and all went well. My present antenna is a 10-meter monobander. Just raise that upper section to about eye level, mount the antenna on it when you get it clamped off, and do whatever final work is necessary while standing in reasonable safety and comfort on your roof.

Once the antenna is mounted, you'll have the task of extending the mast. Let me repeat my warning -

ANNOUNCING SOUND OFF MODEL 10



Sound Off Model 10 is a self-contained message generator complete with case and power supply. The Model 10 was designed specifically for applications where repetitive high guality natural voice announcements are reguired, i.e. Amateur repeater and commercial radio systems. The Model 10 stores your

natural voice message in nonvolatile EPROM with single message lengths of up to 32 seconds. The Model 10 provides for both single and continuous play modes. Factory setable internal timers can set timing intervals from seconds to 30 minutes or more. All control functions and timers are provided for this application. (COR sense, transmitter activity sense, PTT, ID timer.)

Models 20, 100 and 150 available for applications requiring random access multimessage capabilities in nonvolatile re-recordable message times of up to 4 minutes

Model 10 prices start at \$219.00.

Now for the first time you can enjoy the truly unique operation of a Digital Voice Announcement System, designed specifically for Amateur Radio communications. The DVK-100 represents the latest technology in digital audio processing.

Create your own natural voice contest calls, CQ's etc. Your voice is stored in digital memory, ready to be played back at the touch of a key. The Digital Voice Keyer is not a tape recorder or robotic sounding synthesizer but a true full fidelity natural voice record/playback system. The DVK-100, is a must for the avid contester and great audio accessory for any Ham Shack FFATURES

perior natural voice quality Micro-processor controlled 32 seconds of message time PTT/VOX operation

- Selectable audio compressor Sealed membrane keyboard 4 independent voice memories Positive/negative keyed PTT ESD/EMURFI shielding Selectable end of transmission tone generator
- DAYTON **BOOTH #2**

SEE US AT

122

PTT/VOX operation Dynamic/condensor mic input Selectable monitor amplifier with preset level controls The sound of the future is here today. Contact your local Amateur Radio dealer or NTL for further information

\$24900 SUGGESTED NET AMATEUR PRICE


DEALER INQUIRIES INVITED



LOW BAND DX-ING COMPUTER PROGRAMS by John Devoldere, ON4UN for Apple IIe/c, MS-DOS, Commodore C-128 Apple Macintosh and Kaypro CPM Computers

Here's a collection of 30 super programs written by ON4UN. Just about every interest or need is covered—from antenna design and optimization to general operating programs. Antenna programs include: shunt and series input L network design, feedline transformer, shunt network design, SWR calculation, plus 11 more! General Ham programs include: sunrise/sunset, great circle distances, grayline, vertical antenna design program, sunrise calendar plus 9 more! Phew. When you sit down to use these programs you'll be amazed at what you have. Super value at a super low price. The best value in computer software available today. © 1986.

continue aranabie todaji e ieco.	
UN-Apple IIe/c	\$19.95
UN-MS (MS-DOS)	\$19.95
UN-CPM/Kaypro	\$19.95
UN-C-128 (COMMODORE)	\$19.95
UN-MAC (MACINTOSH)	\$24.95
VISA Please enclose \$3.50 for shipping and handling	
ham	TODE
radio BOOK	SIUKE
GREENVILLE, NH 03048 6	03-878-1441

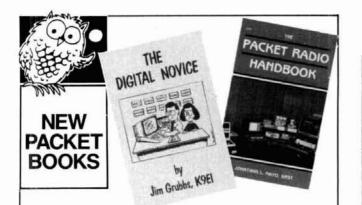

THE DIGITAL NOVICE by Jim Grubbs, K9EI

Now that novices have digital privileges, there are thousands of new Amateurs anxiously awaiting to get on-the-air. Who's going to answer their questions, however? Jim Grubbs' new book, The Digital Novice, is written with beginner's needs in mind. Each of the popular digital modes is fully covered with a brief history and full description of how it works. Hardware and software are covered in clear, concise terms. The book finishes with a look toward the future. Four appendixes cover; Morse, Baudot, AMTOP and ASCII Codes and has a glossary full of commonly used but misunderstood terms. Great for beginners and experts alike. ©1987 1st edition

JG-DN

Softbound \$9.95

THE PACKET RADIO HANDBOOK

by Jonathan Mayo, KR3T

Packet radio is the fastest growing mode in Amateur operation today. No wonder - it combines the power of today's microcomputer with worldwide digital communications. Newcomers will find this book to be full of helpful tips, tricks and information that will help get them on Packet as guickly as possible. Providing you first with packet basics, this book progresses through the inner workings and operational aspects of packet to a look at future technology still in developmental stages. Also includes: using bulletin boards, traffic handling on packet, modulation methods and networking principles, protocols (both AX.25 and VADCG) and a thorough discussion of the various TNCs and accessories available. ©1987 1st Edition 218 pages.

□T-2722

Softbound \$14.95

Please enclose \$3.50 to cover shipping and handling.



wear heavy gloves! As you push the mast up, you'll find that by pushing the section to one side a bit, it will bind enough so that you'll have a momentary respite and will be able to change the position of your hands.


Remember those marks you made on the mast sections for later reference? Now they'll prove their value. When you get the top section fully extended, clamp it off securely. If you're using the guy ring at this position, be sure to attach the wires to it before you raise it out of reach. If you have doubts about the efficacy of your clamp, you may even want to drill through the overlap between the two mast sections and secure them with a 1/4-inch bolt, flat washers, and a lock washer.

The higher you raise the mast, the less secure it will seem. *Don't worry*. Even though what you're lifting does indeed get heavier (because there's an extra section of mast each time, and the lower sections are larger and therefore heavier than the upper ones), you'll find that the load is well within your capacity. Of course, if you want to be doubly sure, ask a friend to hold the mast while you take a breather, search around for the pliers or wrench you've dropped, or just stand back and admire what you've wrought.

final precautions

One last thought: if you live in an area where the climate is less benign than it is here in Southern California, you may want to consider some sort of protection for the bearing assembly *before* you mount the mast to the nipple. The protective device will likely need to be attached, in some fashion, to the lowest section of the mast. Some sort of clamp or machine screws, with holes suitably drilled and tapped, can be used to secure it to the mast.

ham radio

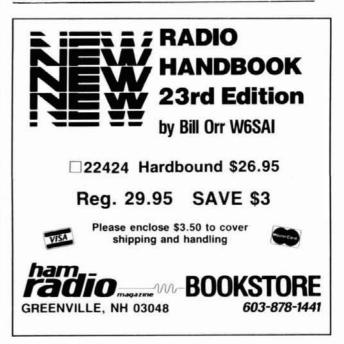

ANIRAGE /KLM

ANTENNA POLARITY SWITCHER MODEL APS-1

The APS-1 is a self-contained control head designed to allow remote polarity switching of circular antennas such as the Mirage/KLM range of crossed yagis.



The APS-1 may be powered by the power adaptor (included) or may alternately be powered from a vehicle or other 13-17 VDC source.

In addition to switchable outputs for two antennas, the APS-1 also contains a 6-13 volt regulated DC power supply. This feature is designed for powering items such as preamplifiers, VHF/UHF converters, etc., but may also be used whenever a low-current stabilized variable voltage source is required.

SPECIFICATIONS:

Power Requirement (AC)	
Power Requirement (DC)	

Total output current 500 mA with AC transformer that is included, 1 amp with optional high current transformer or external DC supply. This unit has our popular five (5) year warranty.

P.O. BOX 1000

MORGAN HILL, CALIFORNIA 95037

⊭ 124 (408) 779-7363



The MEADOWLAKE Corp.

DEPT. UV. P.O. Box 497

Northport, New York 11768

5 East Upshaw Temple, Texas 76501 (817) 771-1188

J 127

✓ 126

125

815 E. Hudson Street


Columbus, Ohio 43211

(614) 261-8871

SEE US AT DAYTON BOOTHS 237 & 238

Yagi triangular array

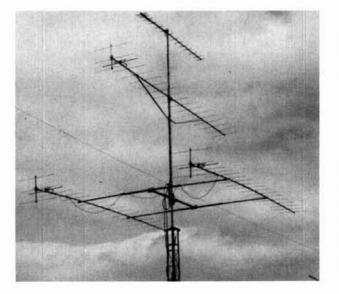Somewhat unconventional stack performs well mechanically and electrically



Inspired by recent articles on stacking Yagis, I decided to improve my 2-meter antenna system, which consisted of a single 19-element, horizontally polarized Yagi. Before long, I had installed another 19-element antenna above it — and with great anticipation, began making comparative checks with the new system.

Because my primary interest is in terrestrial communications, the 2.5- to 3-dB increase in gain didn't overly impress me. With a 2 x 2 array in mind, I bought two more antennas and started designing an H-frame structure. Very quickly, however, I realized how large and heavy the completed array would be. I weighed the possibilities: a tilt-over tower, with block and tackle, would allow access to the array, but would probably be unfeasible because of the antennas' size and weight. After much soul searching, I decided that a stack of four antennas, with the required H-frame, would be out of the question.

alternate stacking methods

I have, from time to time, heard mention of the diamond stacking configuration and claims of improved performance when compared with conventional rectangular stacking. Assuming reports on the diamond's performance to be correct, and seeing a triangle as half of a diamond, I concluded that a triangle would be likely to offer better performance than an inline stacked array.

Unfortunately, oddball stacking geometry such as the triangle or diamond has received little or no publicity; I've yet to find informative literature on anything but the inline stacking methods. (It would almost seem that the numeral 3 simply doesn't exist in the world of antennas. Instead, the philosophy of "double or nothing" seems to prevail.) Nevertheless, after due consideration of weight distribution on the mast and tower, I concluded that a triangle stack configuration — with two horizontally stacked antennas located at the lower level of the mast and a third Yagi mounted at the top of the mast — would best suit my needs.

Theoretically, three Yagis would provide an additional 1.75-dB gain over a pair. Subtracting the phasing harness loss from the theoretical value, a realistic gain of 4.5 dB over a single antenna should be possible. What was more important to me at this time, however, was what the plotted antenna pattern would be. How would it differ from a rectangular stack of four antennas?² The only way to find out would be to build the triangular array and compare the results with published articles on a four-antenna array.

optimum stacking distances


The first problem was to determine the optimum spacing required between antennas. Available stacking data apply only to a pair of antennas stacked in either of two unique locations with respect to each other. Both antennas must be located on the axis of either the E or H plane. Polarization and phasing of both must also be the same.^{1,2} With triangular stacking, the two lower antennas would satisfy the above con-


John C. Cichowski, W2IKP, 167 Emeline Drive, Hawthorne, New Jersey 07506 ditions. However, the upper antenna is offset, and its H plane axis does not fall upon that of either of the two below. Consequently, the spacing from it to either of the two below will differ from dimensions found in previous studies.^{1,2} After a little head scratching, it became apparent that non-standard H plane stacking dimensions were still useful.


Visualize, as in **fig.1**, a pair of vertically stacked Yagis evolving through positions into a horizontal stack. For example, by keeping the lower antenna location and polarization fixed, and swinging the upper one through an arc (which defines a locus), while maintaining the same polarization as the lower one, one ends up with a horizontal stack. Each and every point along the locus will locate the movable antenna at an *optimal* distance from the fixed antenna. Also, at some point along the locus, the antenna will be equidistant to either of the two lower antenna positions (see **fig. 1**).


E and H optimum spacing differs

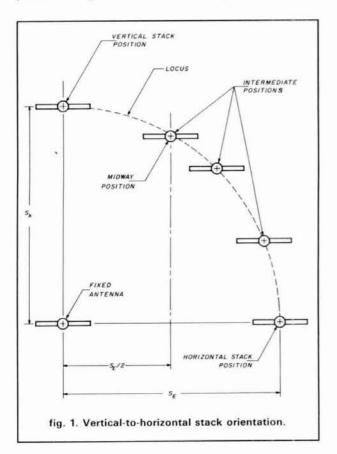If optimum spacing for E and H plane were identical, the locus would be a 90-degree arc of a circle, with its radius equal to the optimum spacing dimension. However, the E and H plane optimum values are *not* equal, and studies have shown that optimum spacing, in a particular plane, depends on beamwidth in that plane. The greater the beamwidth, the closer the



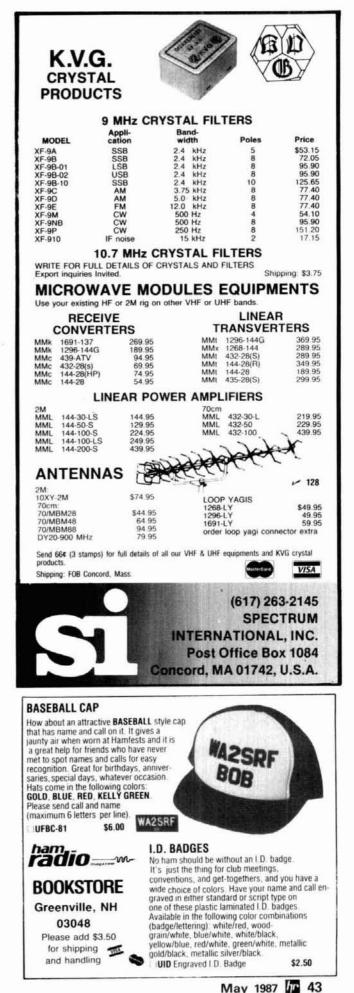

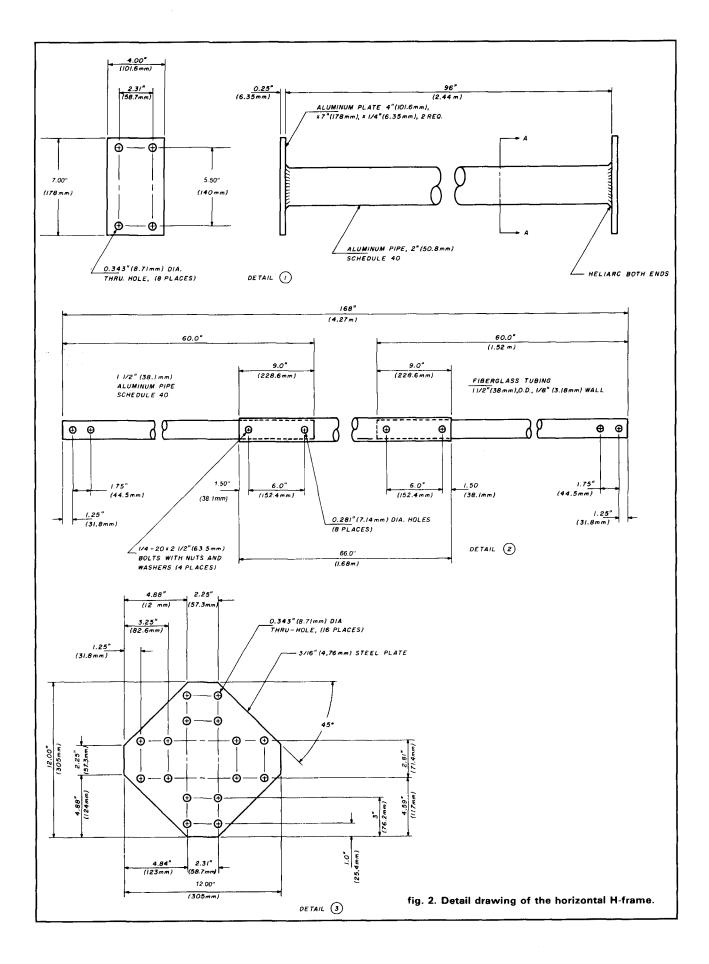

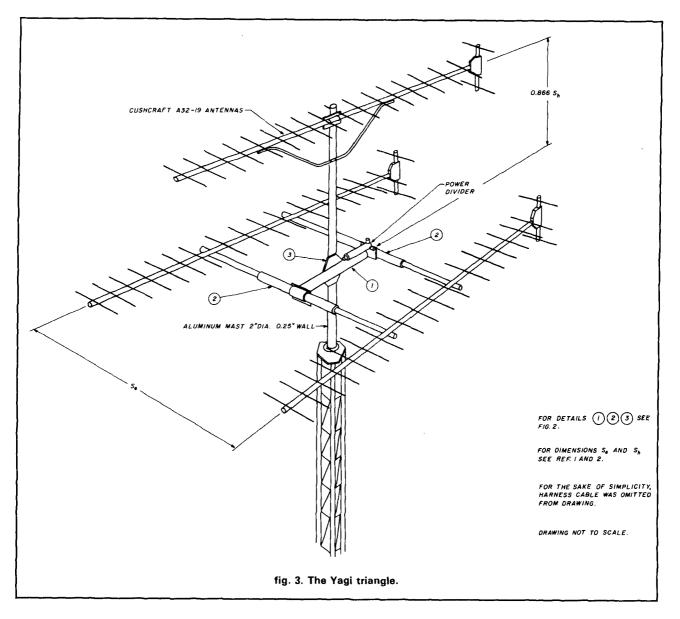

spacing.¹ The one feature all Yagis seem to have in common is greater beamwidth in the H plane than in the E plane. Consequently, H plane spacing will be less than the E plane's. The locus in this case is an arc of an ellipse. (To visualize an ellipse, picture a hoop rotated about its diameter and viewed at an angle.) Put into usable terms, E plane spacing is the value recommended by Joe Reisert, W1JR¹ and Steve Powlishen, K1FO.² Their tabulated data includes the most popular antennas in use today. The vertical stacking dimension is 86.6 percent of the optimum H plane dimension or S = 0.866 S_H where S_H is the optimum H plane stacking dimension recommended for inline stacking.^{1,2}

horizontal H-frame construction

Horizontal stacking of horizontally polarized antennas requires the use of dielectric material in the

immediate vicinity of the Yagi elements. A minimum distance of 1/2 wavelength of metal-free structure is recommended, or 1/4 wavelength beyond the active element tips.³ Detail drawings for the structural parts used to assemble the H-frame are shown in **fig. 2**. The Cushcraft A32-19 antennas used in the Yagi triangle normally require boom supports supplied by the manufacturer; these are not necessary when mounted on this horizontal H-frame. The upper antenna, however, must be mounted in accordance with the manufacturer's recommendations (see **fig. 3**). Within reasonable limits, variations in frame design are certainly permissible.

If antennas other than those shown are used, changes in the overall length of items 1 and 2 might be required. Should it be necessary to make such adjustments, remember that the fiberglass support arms of the H-frame must be located midway between

PAC-COMM TNC-220 HF / VHF Terminal Node Controller

\$129.95 KIT

The TNC-220 is a new, low-cost Packet Terminal Node Controller evolved from the Pac-Comm TNC-200 (TAPR TNC-2). It uses more large scale integrated circuits and fewer components to provide greater functionality, reliability and sensitivity with reduced size and cost. The single-chip modem used for both 300 baud HF and 1200 baud VHF operation has two radio ports. Switching between ports is done entirely in software and no cable changing, no switch setting and no retuning is required! The HF port has an active bandpass filter and provides either FSK or AFSK keying. An optional tuning indicator slides inside the cabinet. A standard modem disconnect header will connect accessory high-speed or satellite modems.



- Two radio ports
- 7910 single-chip modem
- 300 and 1200 bauds
- Enhanced command set
- Multi-color status LED's
- Supports RS-232 and TTL computers
- Active HF bandpass filter
- Tuning indicator option
- 12 volt DC operation
- Premium quality case
- 6″ w x 2″ h x 7″ d

\$159.95 ASSEMBLED

The TNC-220 has the familiar TAPR command set and AX.25 Level 2 Version 2 protocol running on a Z-80 processor with 32k bytes of EPROM and 16k bytes of battery-backed RAM. A Zilog 8530 SCC performs all packet HDLC in hardware. The terminal port can select either RS-232 or TTL for your C-64/128, VIC-20 or other TTL computer. Five large, color-coded LED's clearly indicate status at a glance. The power switch is now located on the front panel. The TNC-220 is enclosed in a rugged extruded aluminum cabinet with an attractive two-tone blue front panel. All indicators and controls have large, clear labels.

> Tech Line (813) 874-2980 Write For Free Packet Catalog

"GO-ANYWHERE

Quality, shirt pocket, digital multimeter

tests electrical equipment-at home, in

your car, on your job, and even in the

4.5"Hx3"Wx 1/2" thick. Measure up to

case. Satisfaction guaranteed. 30 day money-

Call TOLL FREE: 1-800-221-5749

In CT: 203-877-4417

Mon-Fri, 9-5:30, EST.

VISA

back woods! Case folds to approx.

ONLY \$35., includes probes and carrying

back return. ONE YEAR WARRANTY.

500V ac/dc and 20 megohms.

eaglestone

plus \$2. each for shipping and handling. CT residents add 71/2% sales tax.

ZIP

Send

Charge:

NAME

ADDRESS CITY_____ STATE____

Acct No

Exp / Signature

84 RESEARCH DRIVE . MILFORD, CT 06460

My check or money order is enclosed.

VISA®


_ DM1000 pocket meter(s) at \$35. each

ORDER DIRECT 800-223-3511 FREE UPS BROWN

Pac-Comm Packet Radio Systems, 3652 West Cypress St., Tampa, FL 33607 - 129

DX on 160, 80 and SECRET WEAPON

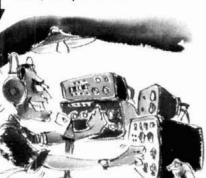Alpha Delta's new DX-A Twin Sloper Antenna combines the tremendous power of the quarter wave sloper with the wide bandwidth of a half wave dipole. Easy to install, simple to tune.




"DX is a snap with my secret weapon!"

- 160 and 40 m leg approx. 55' long. 80 meter leg 67' long. Installs just like an inverted V. Fed with single 50Ω feedline
- Current lobe up high for maximum radiation. Can be installed between 25 and 40 feet
- Broad band performance. Although bandwidth is determined by your installation, tests have shown 85 kHz on 160 m, 200 kHz on 80 m, and full coverage of 40 m. Tuner usually not required.
- No lossy traps. A single "ISO-RES," isolator/resonator coil is used to tune 40 and 160 meters
- Rated at 1.5 KW output
- Quality hardware and UV protected coil. Stainless steel ensures excellent all weather performance.




131

 

HRM4

MasterCard®

Only 1/2" thick

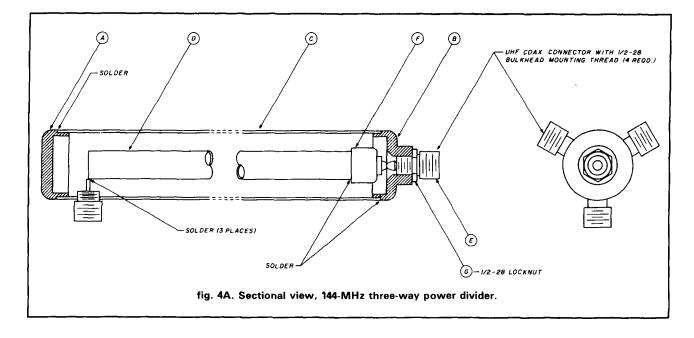

the director elements of the antennas as shown in fig. 3.

material sources

I made use of readily available material. A local metal fence supply dealer stocked aluminum pipe and was also equipped with Heliarc welding facilities, which became very useful while constructing the H-frame. The 1-1/2 inch diameter fiberglass tubing, available in 5-foot lengths and used for satellite antenna work, was purchased from my local Amateur Radio dealer.

Because the inside diameter of the 1-1/2 inch aluminum pipe measures slightly more than 1-1/2 inches, it was necessary to shim the fiberglass tubing with glass filament tape to achieve a tight fit. The assembled frame and the three Yagis mounted on top of the tower are shown in **fig. 3**. All that remained at this point was choosing a feedline and deciding on a power divider method. A 50-ohm impedance, 7/8-inch hardline had already been installed with the previous array. The phasing harness and feedline around the rotator used more flexible RG-8U.

Use good quality cable for the harness. Each leg must be cut to equal electrical lengths, preferably from the same run of cable. Each antenna must be parallel to the others — elements as well as booms — and the most forward director element of all three Yagis must be located within the same vertical plane. Otherwise, the wavefront launched by any one individual antenna will be out of phase with the others, resulting in lower gain, greater sidelobes, and possible multipath propagation. Phasing lines, besides being equal in length, should be kept as short as possible, especially at higher frequencies. Mounting the power divider as shown in **fig. 3** allows shorter harness leads.

three-way power divider

Obtaining a three-way power divider meant building one from scratch, because I couldn't locate any commerical units. So I went back to the books and set off on a thorough search of local supply houses⁴ for appropriate hardware.

To my knowledge, two methods for power splitting are commonly used. Most popular is the transformation of impedance by the use of a single 1/4 wavelength of coaxial transmission line. A common input port is located at one end and the required number of output ports at the other end. The characteristic surge impedance is determined as the mean value between transmitter output impedance and the parallel combined load impedance presented by the three antennas. Manufacturers of communications equipment have standardized their products for use with 50-ohm coaxial line. This simplifies the mathematics to determine power divider impedance when using more than one Yagi. Reduced to its simplest form, the equation for characteristic surge impedance for the above power divider becomes:4-8

$$Z = \frac{Z_o}{\sqrt{n}} = \frac{50}{\sqrt{n}} \tag{1}$$

where n = number of antennas in array, $Z_o = impedance$ of each antenna and equals the transmitter output impedance of 50 ohms.

Using eqn. 1, the characteristic impedance is:


$$Z = \frac{50}{\sqrt{3}} = 28.9 \text{ ohms}$$

To determine the proper diameter ratio for coaxial line



Send this ad along with your order to:

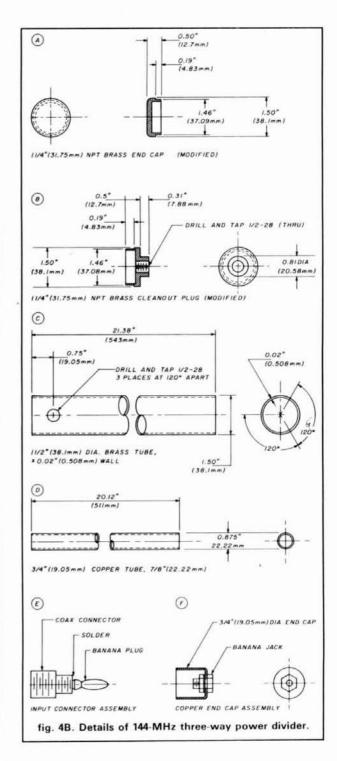STV®/OnSat® P.O. Box 2384—Dept. HR • Shelby, NC 28151-2384 SUBSCRIPTION CALLS ONLY TOLL FREE 1-800-438-2020



with the above impedance, the following relationship is used:

$$a/b = antilog \frac{Z}{138} = 1.62$$
 (2)

a = Inside diameter of outer conductor

b = Outside diameter of inner conductor

Z = Characteristic surge impedance of coaxial line in the power divider.

The above diameter ratio (a/b) can be closely satisfied by using standard 3/4-inch diameter copper plumbing tubing (which actually measures 7/8 inch diameter) and 1-1/2 inch diameter brass tubing with 0.02-inch wall, normally used for kitchen sink drains. It can be purchased without the usual nickel plating at most plumbing supply stores.

To cap each end of the 1/4-wavelength line, it's necessary to machine 1-1/4 inch NPT brass cleanout plugs and end caps to the dimensions shown in the detail and assembly drawing for the three-way power divider (fig. 4).

Suitable connectors for this application are the familiar UHF type with 1/2-28 thread mounting capability. Amphenol 83-875 or equivalent can be used. By removing the snap ring, the connector can be dismantled and soldered to the body of the divider. Otherwise, excessive heat will destroy the insulator insert. To simplify assembly, it was necessary to include what at first would seem to be two unnecessary steps: first, the addition of a banana plug and jack at the input end of the line, to allow for adjusting the position of the inner conductor when you're soldering to output ports; and second, the drilling of three tapped holes (1/2-28) at the output end to hold coax connectors in place while you solder them to the 1-1/2 inch diameter brass tubing.

The power divider shown in **figs**. **5** and **6** is the 432 MHz version of the above. Also, a scaled-down H-frame for a 432-MHz Yagi triangle is shown in **fig**. **7**. (Although the antennas shown aren't representative of 144-MHz proportions, the reader may find the photos helpful nevertheless.) For further harness detail, see **fig**. **8A**. The alternate power divider method (**fig**. **8B**) requires 86.7-ohm impedance transformation sections of coaxial line in each leg of harness to the antennas.

$$Z = Z_0 \sqrt{n}$$
(3)

A 1/4 wavelength of RG-62/U cable whose impedance is 93 ohms should work well. However, transmitter power must be limited to a couple of hundred watts. With higher power, use of RG-63/U is recommended. The velocity factor for both cables is 86 percent, which makes the overall length (including connectors) of the 1/4-wavelength sections 17 inches.

A three-way "T" junction must be used at the feed point. A weathertight metal junction box with closely spaced coaxial connectors will easily satisfy the short junction lead lengths required at the distribution point. A variation of the above division method is shown in **fig. 8C**. The three 1/4-wavelength sections as well as the three 50-ohm harness cables are replaced with equal lengths of RG-62/U. The three lengths, however, must be odd multiples of 1/4 wavelength each.

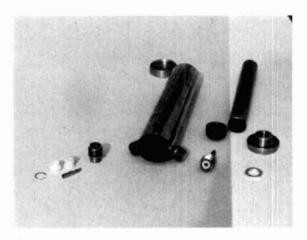


fig. 5A. Three-way power divider before assembly.



fig. 5B. Three-way power divider output ports.

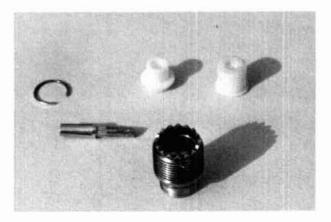


fig. 5C. Dismantled Amphenol coax connector.

Before connecting the harness to the power divider, best results will be obtained if each antenna is separately adjusted for best SWR using that leg (i.e, the same length) of feedline intended for the harness.

After adjustments have been made, connect the power divider to the antennas and feedline. Measure the SWR of the assembled array. In some cases, the

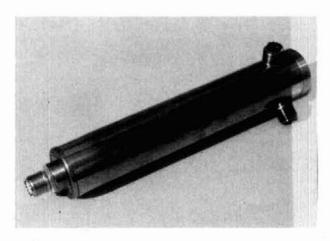


fig. 6. Assembled three-way power divider.


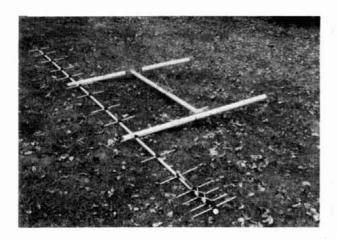



fig. 7. Horizontal H-frame for 432-MHz Yagi triangle.

final SWR measurement will appear to be better than that of the individual Yagis. Offhand this would seem to indicate an improvement to the system; however, this may not necessarily be so since the SWR measurements, other than 1:1, simply indicate the presence of a reactive load. The reactance, which can be either inductive or capacitive, depends upon how far the operating frequency is from the center frequency of the antenna and on the adjustment of the matching device at the individual antennas.⁴ The inductive reactance of one antenna can cancel out, in part or completely, the capacitive reactance of another so that the resulting sum can be less than that of the individual antenna. Other than becoming more broadband (i.e., having lower Q), this does not imply that gain performance of the stacked array will be enhanced in any way. The SWR, as previously measured at the individual antennas, still exists and should be adjusted for the lowest ratio attainable or the maximum forward gain will be degraded accordingly. Once assured that the individual as well as the overall system SWR measurements are satisfactory, the Yagi triangle is ready for use.

E plane plot

The E plane plot shown in **fig. 9** indicates a halfpower, 15-degree beamwidth. This was determined by the 48.5-percent method described by Gunther Hoch, DL6WU.² A comparison of the E plane plot of four stacked NBS-17 antennas with that of the Yagi triangle shows very little variation.² In fact, the frontto-back response seems to be better with the triangle. This might be attributed to the trigon reflectors on the Cushcraft A32-19 antennas used in the Yagi triangle.

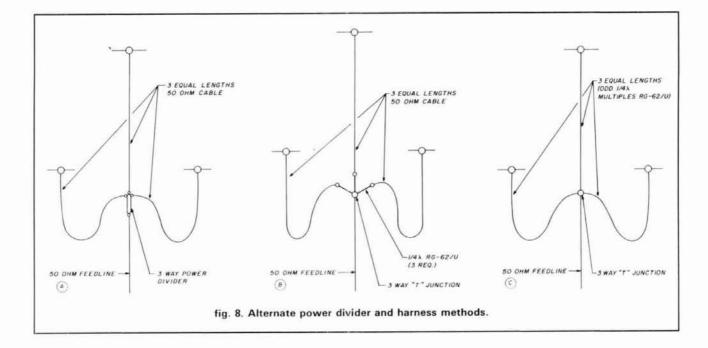

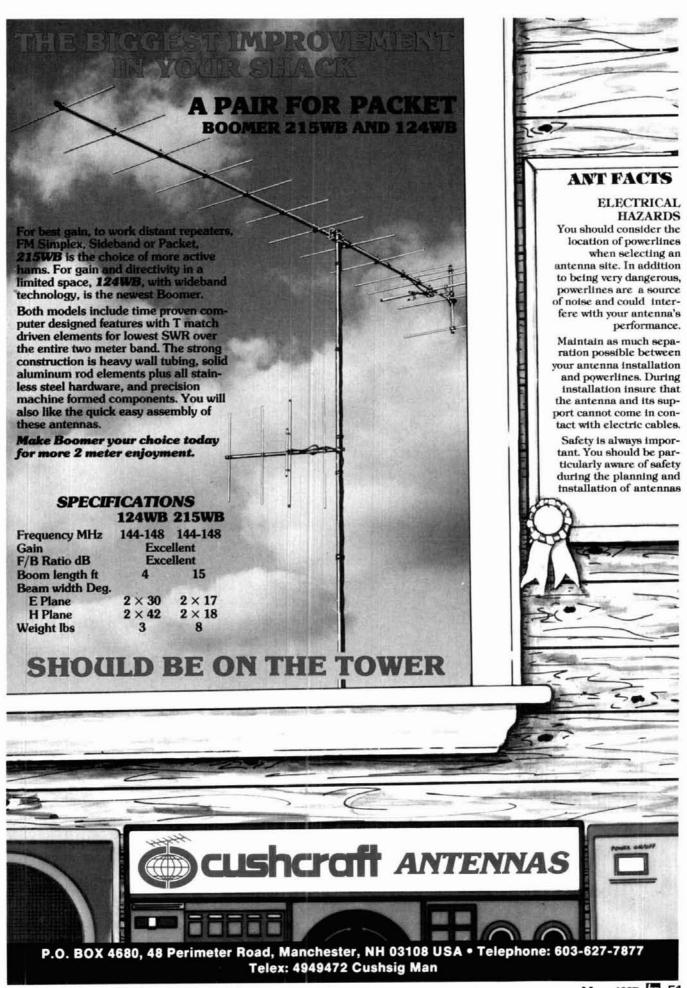

PERFORMANCE AND VALUE WITHOUT COMPROMISE

Word is spreading fast-

KRP-5000 REPEATER

2 meters - 220 - 440

"Nothing matches the KRP-5000 for total performance and value. Not GE, not even Motorola."

in tough repeater environments, so the KRP-5000 receiver gives you 7 helical resonators, 12-poles of IF filtering, and a precise Schmitt trigger squelch with automatic threshold switching. The transmitter gives you clean TMOS FET power.

> SEE US AT DAYTON BOOTH 106, 107 & 108



with PA-100 Amplifier

RF performance really counts Enjoy high performance operation with: remote programmability, sequential tone paging, autopatch, reverse autopatch, 200-number autodial, remote squelch setting, status inputs, control outputs, and fieldprogrammable Morse messages

Call or write for the full performance story ... and the super value price!

Micro Control Specialties 23 Elm Park, Groveland, MA 01834 (617) 372-3442 TELEX: 4932256 Kendecom FAX: 6173737304

The first choice in Transmitters - Receivers Repeaters Repeater Controllers Power Amplifiers Voice Mail Systems


136



HERE'S A NEAT GIFT IDEA

When we first saw the Casio PQ-40U Portable World Time Clock, we knew instantly that Ham Radio Bookstore customers would love this one.

This time piece is more than a simple clock. Besides all the standard features, alarm, snooze, lightweight portable design and digital readout, this clock gives you time at 21 different locations around the world at the twist of a dial. DX'ers will delight at being able to get rid of their cumbersome manual time calculators: determining band and path to use will be greatly simplified. Contesters can simultaneously display both local and UTC times for logging purposes. In fact, every Amateur will find at least a dozen uses for this nifty clock. You can take it with you when you go on vacation-business trips-set the alarm and get out of meetings early-anywhere you need a clock, the PQ-40U can go with you. Get a couple of them and give them as gifts, one for the house, car, office, just about anywhere you need a clock, the PQ-40U can go with you. Quantities are limited-order now and avoid disappointment.

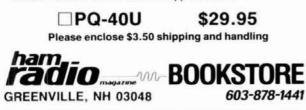

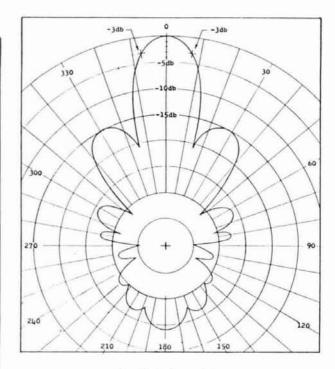


fig. 9. E plane plot.

No attempt was made to plot the H plane pattern, since no facilities to do so were available. It's my guess that the pattern would very much resemble that of two vertically stacked A32-19 antennas. Since I expect to duplicate the Yagi triangle at higher frequencies in the near future, a smaller array will be more manageable for the setup required to make H plane measurements.

antenna rotators and resolution

As the gain of a beam antenna system is increased, the beamwidth gets smaller until the point at which the resolving capability of the rotating system reaches a practical limit.

Most rotators available for Amateur use are geared to rotate at 1 rpm. The indicator on the control unit is graduated in divisions of 5 degrees. This means that rotation occurs at a rate of 6 degrees per second, or to put it in more dramatic terms, less than one second per division. A 15-degree segment (three divisions) will be scanned in 2.5 seconds.

To fix a beam heading, the antenna rotation between first nulls on either side of the main lobe shouldn't take less than 5 to 6 seconds. A main lobe with 15-degree beamwidth will have approximately 30 degrees between first nulls. Therefore, 1-rpm rotators will perform at the limit of their resolution capability. Antennas with beamwidths less than 15 degrees should be rotated with slower-speed devices. Aircraft prop-pitch motors are often used for this purpose. Manufacturers of one or two commercial rotators available for Amateur use claim dual speed, but the load capability of these units isn't sufficient for the size

of the 144-MHz antenna array that would require the lower speed.

Used with 1-rpm rotators, antennas with less than 15-degree beamwidth require rocking the rotation back and forth several times to attain true beam heading. The problem is further compounded because of play (backlash) inherent in all such devices.

Still another resolution gremlin is the inertia that builds up during antenna rotation, causing long-boom Yagis to whip laterally when rotation is suddenly stopped. Many of these antennas have boom braces to keep them from sagging. However, the brace does little or nothing for the side motion. Heavy gusts of wind will also cause lateral flexing with these antennas. Though the two lower antennas of the Yagi triangle aren't prone to this problem because of the H-frame construction, the upper antenna does occasionally do a little dancing. Polypropylene guys from the upper antenna to the H-frame should remedy this problem.

Rotation at 1 rpm seems like a long enough period of time for a complete 360-degree turn of the antenna, and many of us - myself included - wouldn't relish the thought of extending the time. Therefore, antenna arrays with beamwidths of 15 degrees, or perhaps by stretching a point or two, even 14 degrees, should satisfy the resolution capability limits of 1-rpm rotators. This Yagi triangle is such an antenna.

performance

The triangle-stacked Cushcraft A32-19 antennas certainly perform better than the original dual stack. The theoretical 1.75-dB increase in signal seems to mock the theoretical 3 dB originally obtained while using the dual stack. QRP signals, unheard before, are now Q5 copy. Reports on my signal are almost always complimentary.

Raising or lowering the tower with the triangle stack is a one-man operation. Repeated inquiries about the triangle stack seem to indicate that others would like to give it a try. Anyone interested in a totally different approach for stacking Yagis will find building the Yagi triangle a worthy and rewarding effort.

references

1. Joe Reisert, W1JR, "VHF/UHF World: Stacking Antennas - Parts 1 and 2," ham radio, April and May, 1985.

2. Steve Powlishen, K1FO, "Stacking Yagis is a Science," ham radio, May, 1985

3. American Radio Relay League, The ARRL Antenna Book, 13th Edition, pages 75, 129, and 245.

4. William I. Orr, W6SAI, Radio Handbook, 17th Edition, page 459.

5. W. M. Meyer Jr., W6GGV, "Transmission Line Circuit Design," ham radio, January, 1981

6. Frederick E. Terman, Radio Engineers Handbook, First Edition, page 174. 7. Jim Pruitt, KL7HIT, "Easy Matching Sections," ham radio, March, 1982. 8. Frank A. Regier, OD5CG, "Series Section Transmission Line Impedance Matching," OST, July, 1978.

ham radio

HIGH PERFORM ECTOR-

The solution to most interference, intermod, and desense problems in AMATEUR and COMMERCIAL systems. · 40 to 1000 Mhz - tuned to your frequency



Typical rejection:

±5

600 Khz@144 Mhz:

±1.6 Mhz@220 Mhz: -40dB

- 28dB

-50dB

· Low noise - High overload resistance 8 dB gain - ultimate rejection > 80 dB 10 to 15 volts DC operation Size - 1.6 x 2.6 x 4.75" exc. connectors

5 large helical resonators

 FANTASTIC REJECTION! Price - CALL bipolar w/RCA jacks Connector options: BCN \$5, UHF \$6,

N \$10 SUPER HOT! GaAs Fet option \$20

Mhz@450 Mhz: ID-2 iD-· For transceivers and repeaters - AMATEUR and COMMERCIAL Automatic operation - adjustable speed and amplitud
 Small size - easy installation - 7 to 15 volts DC 8 selectable, reprogrammable messages - each up to 2 min. long · Wired, tested, and programmed with your message(s) SEE US AT Model ID-1 - \$49.95 Model ID-2 w/2 to 10 minute timer - \$69.95 DAYTO **BOOTH 318** We offer a complete line of transmitter and receiver strips and synthesizers for amateur and commercial use. Request our free catalog. Allow \$2 for UPS shipping - Mastercard and VISA welcome GLB ELE(IKON

Dept H. 151 Commerce Pkwy., Buffalo, NY 14224 716-675-6740 9 to 4

- 134

TORING

TIMES

Subscribe Today To The World's Leading Magazine For Shortwave & Scanner Listeners!

- International Broadcasting
- **Utility Monitoring**
- Scanners
- Shortwave and Longwave
- Satellites
- Electronic Projects Listening Tips
- Frequency Lists
- Equipment Reviews
- News-breaking Articles
- Feature Articles
- Exclusive Interviews
- · Insights by the Experts
- New Products

Each month MONITORING TIMES, the first widespectrum listener's publication and still the best, brings you 64 giant tabloid pages of late-breaking information on every aspect of monitoring the radio spectrum.

Fast-paced and information-packed, MONITORING TIMES consistently scoops the publishing industry.

ORDER YOUR SUBSCRIPTION TODAY before another issue goes by: only \$15 per year (U.S. and Canada), \$22 per year (foreign) or send \$1 for a sample issue (foreign send 2 IRCs).



May 1987 1 53





brother- the 735 OSYet for the ICOM IC-735! Both units are deluxe frequency-entry keypads containing their own preprogrammed microprocessor, audio speaker and power supply. In operation, they allow immediate switching to any frequency


138

in the transceiver's range, while the rig retains absolutely all of its operator's controls. They install in seconds, connecting to the rig's data terminal and power supply output. Their durable metal enclosures are painted classic metallic gray and black.

\$89.50 plus \$2.50 shipping and handling, and 4% sales tax for GA residents. MasterCard and Visa customers please send name, card number, expiration date, and signature, or call us at 404-879-0241. 10 day money-back guarantee

In Canada, call Atlantic Ham Radio, Ltd., at 416-636-3636 Stone Mountain Engineering Co.

Box 1573 • Stone Mtn., GA 30086

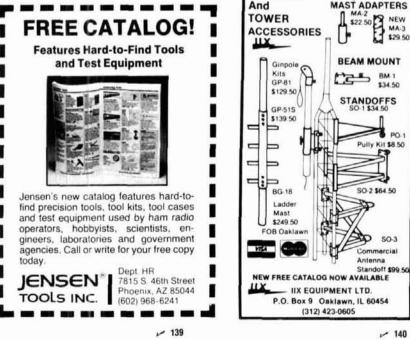



ham radio techniques


In the northern areas, winter is almost over and signs of spring are in the air. It's a good time to think about antenna systems. A lot of interesting antenna concepts have just been waiting for some good weather to set in! Here are some interesting projects for you to consider . . .

inexpensive base station antenna for 2 meters

I think Fred Dietrich, NM6J, has come up with a winning 144-MHz antenna that has decent gain and a low SWR, and costs very little to construct. Shown in fig. 1, this vertical, omnidirectional array is only about 6 feet tall. The antenna structure is made of a length of 3/4-inch Schedule 40 (thick wall) PVC water pipe. The overall pipe length is long enough so that the antenna can be supported by clamps at the base end. For this particular installation, an 8-foot length of PVC was selected. The top of the pipe is closed with a PVC cap cemented in place using the liquid sealer that applies to such material.

The radiating portion of the antenna is a No. 12 copper wire 51.75 inches long. Enough extra wire is added to this length to allow it to be attached to the cap with PVC cement and to form a solder connection to the coax line at the base of the antenna.

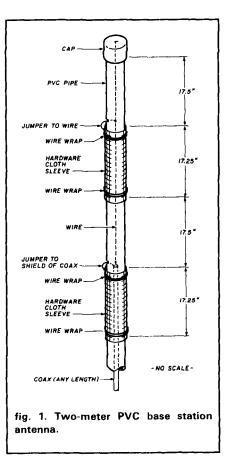Two phasing sleeves are used. They're made of galvanized hardware cloth folded around the PVC pipe and wrapped with wire to hold them in place. Each sleeve is 17.25 inches long. The retaining wires are soldered to the hardware cloth at several points around the circumference.*



A short jumper wire joins the top of the upper screen to the antenna wire running inside the PVC tubing. It is suggested that this wire be soldered to the antenna wire and then fished out through a small hole drilled in the PVC wall. If this and the following step are done before the top PVC cap is fastened in place, the assembly will proceed smoothly.

A second phasing sleeve is affixed to the structure below the first, as shown in **fig. 1**. This sleeve is connected to the outer shield of the coax line by means of a short length of wire inserted through a second hole after the antenna wire has been passed within the PVC pipe. After assembly, the holes are filled with cement to make the assembly waterproof.

The antenna is mounted in a vertical position and the coax line is brought down directly below the antenna. A VSWR plot representative of the antenna's performance is shown in **fig. 2**.

a "rubber duckie" for 160 meters

The ham who lives on a small, treeless lot faces a real problem when contemplating 160-meter operation. One solution to this problem is a vertical antenna. But a guarter-wave vertical antenna on "top band" is over 130 feet high. Joe Moraski, KY3F, has a solution to the problem. He recommends a helix antenna operating in the normal mode -- that is, a coil with a small diameter compared to the operating wavelength. Maximum radiation is normal to the axis, hence the name. This is the same mode of operation as that of the 2-meter "rubber duckie" antennas used on handhelds.

^{*}Though more expensive copper-based hardware cloth would maintain its electrical properties longer. - Ed.

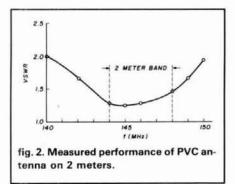




Photo 1. Base assembly of the KY3F vertical antenna for 160 meters. Final frequency adjustment is made by varying number of turns at the bottom of the helix.


There are no hard and fast rules about the length or diameter of the helix. The rule of thumb is that about a half-wavelength of wire is used to make the helix.

Antenna size is a matter of tradeoffs. The shorter and thinner the helix, the narrower the bandwidth. The longer and thicker it is, the harder it is to build and keep up in the air! A shorter helix is less efficient — consequently, the longer the better.

Since the helix bandwidth is narrow,

a top hat is added to reduce antenna Q and add capacitance at the high voltage point. The resulting reduction in circuit Q causes the feedpoint impedance at the antenna base to vary less rapidly with frequency change than the unloaded antenna. This means that the antenna can be used over a larger portion of the band than would otherwise be possible.

By experiment Joe found that a

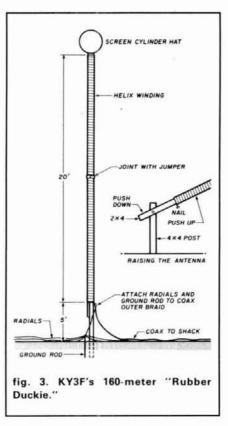


20-foot antenna was a good operating compromise. Accordingly, he used two 12-foot sections of 4-inch diameter PVC water pipe cemented together to make a 24-foot mast. He wound No. 18 insulated hookup wire on it at ten turns-per-inch spacing. This helix, in combination with a screen wire capacitance hat on top, resonated in the 160-meter band when operated against a ground rod and quarter-wave counterpoise wire run around the backyard. Four 30-foot radials were added. A sketch of the antenna is shown in **fig. 3**.

The construction is simple if done in the proper sequence. The first step is to drill holes for the end tie bolts that terminate the winding. The holes are 10 feet apart. Galvanized bolts are used, with washers on each side of the PVC pipe. With a tape measure and felt-tip pen, make small marks at 1-inch intervals between the bolts.

Next, fasten an eye-lug to one end of a 140-foot length of No. 18 insulated wire. Fasten the lug to one bolt and wind the coil on the PVC pipe, using the pen marks as a guide — one turn per mark. Use tape to hold the coil in place as you progress along the form.

Wind the wire as tightly as you can and when you reach the second terminating bolt, cut the wire and place an eye-lug on the end that will fit over the bolt.

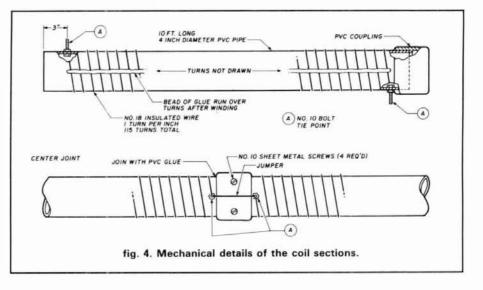With the winding properly spaced, run a bead of RTV along the length of





ICOM extends congratulations to privilege-enhanced Novices, and invites everyone to extend their horizons with ICOM!

ICOM is the only amateur radio manufacturer hosting a full product line especially geared toward privilege-enhanced Novices (and Technicians joining 10-meter activity). Whether your interests include 1.2GHz, 220MHz, HF bands, FM, CW, or SSB, choosing ICOM gear means going First Class!

Explore 1.2GHz DX attractions and local activities with pacesetting ICOM gear. The all mode IC-1271A base station transceiver includes numerous deluxe features and is expandable with your future interests. FM mobiling pleasures begin with ICOM's **new 10 watt IC-1200** which is easy to install and operate. Every amateur enjoys handheld portable operations, and ICOM's deluxe **IC-12AT** handheld is ready to go.

Experience 220MHz activities using top quality ICOM equipment. For your multi-mode interests is the **new IC-375A** 25-watt base station transceiver: a true masterpiece of modern technology. ICOM's ultra slim IC-37A and compact IC-38A are ideal 25-watt mobile units. For a versatile and rugged handheld, choose the deluxe IC-03AT or the everpopular IC-3AT. Enjoy HF QSOs worldwide and depend on ICOM transceivers for top communications performance. The **exciting new IC-761** offers you superb "everything in one cabinet" operation. Or there's the ICOM deluxe midsize transceivers, the IC-751A and IC-745. The IC-735 is today's most popular fixed/ mobile rig. Also, friends, all ICOM HF transceivers include a full one-year warranty.

ICOM Accessories are interchangeable. Use them with ICOM's 2-meter and 440MHz gear when you upgrade!

Get on the Air with ICOM and explore 1.2GHz, experience 220MHz, and enjoy HF QSOs.



ICOM America, Inc., 2380-116th Ave. N.E., Bellevue, WA 98004 Customer Service Hotline (206) 454-7619 3150 Premier Drive, Suite 126, Irving, TX 75063 / 1777 Phoenix Parkway, Suite 201, Atlanta, GA 30349 ICOM CANADA, A Division of ICOM America, Inc., 3071 - #5 Road, Unit 9, Richmond, B.C. V6X 2T4 Canada All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. NH387

Professional Meter for Amateur Radio.



The standard of the electronics industry is setting a new standard for amateur radio use as well.

The Fluke 77 multimeter is ideal for testing and repairing any amateur radio gear. It's inexpensive, easy to use, and filled with professional features. Plus a full line of accessories let you measure high frequency, high voltage and current, and temperature. Made in the U.S.A. and backed by a 3-year warranty, the new Fluke 77 is the world's first handheld meter to combine analog and digital displays.

For a free brochure or the distributor nearest you, call toll-free **1-800-227-3800**, ext. 229. Or write John Fluke Mfg. Co., Inc., P.O. Box C9090, Everett, WA 98206. Distributor programs available.

FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.


FLUKE 73	FLUKE 75	FLUKE 77
\$791	\$109†	\$145†
Analog/digital display	Analog/digital display	Analog/digital display
Volts, ohms, 10A, diode test	Volts, ohms, 10A, mA, diode lest	Volts, ohms, 10A, mA, diode test
Autorange	Audible continuity	Audible continuity
0.7% hasic dc accuracy	Autorange/range hold	Touch-Hold
2000 + hour battery life	0.5% basic dc accuracy	Autorange/range hold
3-year warranty	2000 + hour battery life	0.3% basic dc accuracy
	3-year warranty	2000 + hour battery life
		3-year warranty
		Multipurpose holster




✓ 143

pipe over the coil turns to lock them in place.

You have now completed half the antenna. Now, wind a second similar coil on the second section of PVC pipe, making sure that both coils are wound in the same direction (left- or right-hand turns, but be sure they're both the same).

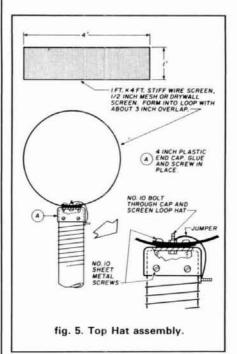

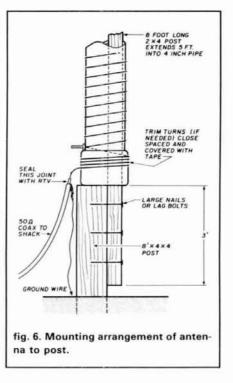

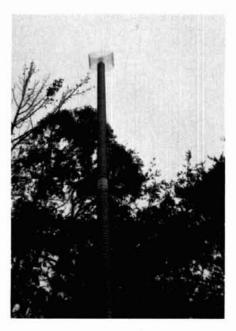


Photo 2. View of winding and capacitance hat on KY3F helix antenna.

The two pipe sections are now joined with a plastic pipe splice section and PVC cement. Align them quickly and let the joint dry (**fig. 4**). Some PVC pipes have a built-in coupling joint — nice if you can locate one. For added strength, run four No. 10 self-tapping sheet metal screws through the joints where the PVC pipes and splice section overlap. Finally, connect a wire jumper between the two coils to form one 20-foot coil.

The next step is to make the "top hat." A section of 1/2-inch mesh chicken wire or drywall screen can be used. Wrap it into a cylinder about 1 foot in diameter and 4 feet long. Solder the overlapping wires. Drill the cap piece of the antenna for a No. 10 bolt, which is bolted through the overlap portion of the top hat. Use large washers on each side of the screen to enhance stability. Then run four No. 18 sheet metal screws through the screen and cap to keep the screen from turning or buffeting in the wind (see **fig. 5**).


The final step is to attach the top hat to the top of the helix with a jumper wire. Glue the top hat in place and pass four sheet metal screws through the hat to hold it securely to the PVC pipe.

Eureka!

We just struck gold with a miniature, high quality and very reliable DTMF decoder at a rock bottom price of \$59.95. Our DTD-1 will decode 5040, 4 digit codes with the security of wrong digit reset. It contains a crystal controlled, single chip DTMF decoder that works great in bad signal to noise environments and provides latched and momentary outputs. Why carry that heavy gear when its size is only 1.25 x 2.0 x .4 inches and it comes with our etched in stone, legendary, one year warranty.

Instead of sifting through the field...searching, use our super quick one day delivery and cash in on a rare find.



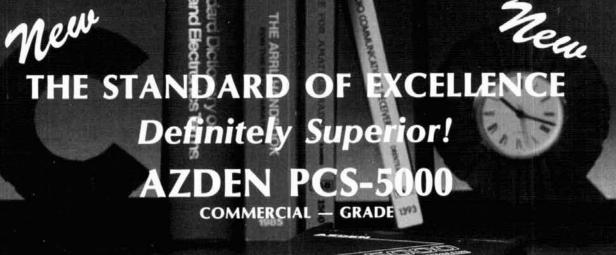

AZDEN I

550

UNPRECEDENTED WIDE FREQUENCY RANGE: Covers 140.000-153.000 MHz in steps that can be set to any multiple of 5 kHz up to 50 kHz.

CAP/MARS/NAVY MARS, BUILT IN: The wide frequency range facilitates use of CAP and ALL MARS FREQUENCIES including NAVY MARS. COMPARE!

TINY SIZE: Only 2 inches high, 5½ inches wide and 7¼ inches deep!

MICROCOMPUTER CONTROL: Gives you the most advanced operating features available.

UP TO 11 NONSTANDARD SPLITS: COMPARE this with other units!

20 CHANNELS OF MEMORY IN TWO SEPARATE BANKS: Retains frequency, offset information, PL tone frequency.

DUAL MEMORY SCAN: Scan memory banks separately or together. **ALL** memory channels are tunable independently. **COMPARE!**

MEMORY SCAN LOCKOUT: Allows you to skip over channels you don't want to scan.

TWO RANGES OF PROGRAMMABLE BAND SCANNING: Limits are quickly reset. Scan ranges separately or together with independently selective steps in each range. COMPARE!

BUSY SCAN AND DELAY SCAN: Busy scan stops on an occupied channel. Delay scan provides automatic auto-resume.

DISCRIMINATOR CENTERING (AZDEN EXCLUSIVE PATENT): Always stops on frequency desired when scanning.

PRIORITY MEMORY AND ALERT: Unit constantly monitors one memory channel for signals, alerting you when channel is occupied.

LITHIUM BATTERY BACKUP: Memory information can be stored for up to 5 years even if power is removed.

FREQUENCY REVERSE: Allows you to listen to repeater input frequency.

ILLUMINATED KEYBOARD WITH ACQUISITION TONE: Keys are easily seen in the dark, and actuation is positively verified audibly. CRISP, BACKLIGHTED LCD DISPLAY: Easily read no matter what the lighting conditions!

DIGITAL S/RF METER: Shows incoming signal strength and relative transmitter power.

MULTI-FUNCTION INDICATOR: Shows a variety of operating parameters on the display.

FULL 16-KEY TOUCHTONE PAD: Keyboard functions as autopatch when transmitting.

MICROPHONE CONTROLS: Up/down frequency control and priority channel recall.

PL TONE GENERATOR BUILT IN: Instantly program any of the standard PL frequencies into the microcomputer. COMPARE! TRUE FM, NOT PHASE MODULATION: Unsurpassed intelligibility and audio fidelity. COMPARE!

HIGH/LOW POWER: Select 25 watts or 5 watts output — fully adjustable.

SUPERIOR RECEIVER: Sensitivity is better than 0.15 microvolt for 20-db quieting. Commercial-grade design assures optimum dynamic range and noise suppression. COMPARE!

DIRECT FREQUENCY ENTRY: Streamlines channel selection and programming.

OTHER FEATURES: Rugged dynamic microphone, built-in speaker, mobile mounting bracket, remote speaker jack, and all cords, plugs, fuses and hardware are included.

EXCLUSIVE DISTRIBUTOR: DEALER INQUIRIES INVITED FOR YOUR NEAREST DEALER OR TO ORDER: AMATEUR-WHOLESALE ELECTRONICS TOLL FREE...800-327-3102 46 Greensboro Highway, Watkinsville, Georgia 30677 Telephone (404) 769-8706 Telex: 4930709 ITT




MANUFACTURER: JAPAN PIEZO CO., LTD. 1-12-17 Kamirenjaku, Mitaka, Tokyo, 181 Japan

Telex: 781-2822452



Photo 3. Joe, KY3F, standing beside his 160-meter "Rubber Duckie."

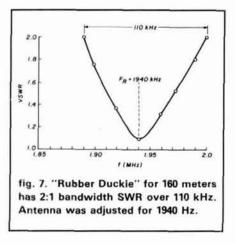


Dig a 3-foot hole for the mounting post. Wrap the portion of the post that will be beneath the surface of the ground with heavy kitchen-type aluminum foil. A double wrapping held in place with plastic tape will protect the post from ground water. After the sides and bottom of the post have been wrapped, place the antenna in the hole and drive a ground rod into a corner of the hole, as far down as possible. Fill the hole with concrete, using a level to make sure the post is vertical. To make the pivot joint, insert a section of 2x4 lumber within the PVC tubing. Fasten this extension to the 4x4 ground post with one lag bolt, used as a pivot. (See **fig. 6** for details.) Bolt the 2x4 and 4x4 together, with the 2x4 in a vertical position. Then raise the antenna to a vertical position and drop it down over the 2x4 section. When the antenna is in the final position, it will sit atop the 4x4 post with the 2x4 section acting as a positioning guide. Various views of the installation are shown in the accompanying photographs.

When completed, the radials and outer shield of the coax line are connected together and the inner conductor is connected to the helix by a short length of wire. The open end of the coax is taped and covered with RTV to keep water out.

As shown, the antenna is resonant at the top end of the 160-meter band. Four close-spaced turns were added at the bottom of the antenna to bring the resonant frequency down to 1.94 MHz. By picking the part of the band you wish to use most and adjusting the extra turns at the antenna base, you can resonate the antenna at any spot in the band you wish. SWR plots of Joe's antenna are shown in **fig. 7**.

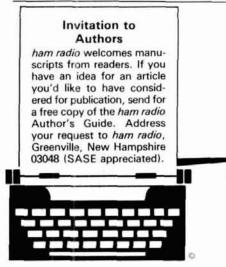Joe says the helix seems stable without any guy ropes, but recommends that ropes be added if the antenna is in an exposed, windy location. Light nylon guys would do the job. ham radio





11903 Alief Clodine Rd #500 Houston, Texas 77082 713-879-7764 telex 166872 MCON UT (MC/VISA/COD)


J 145

COMMODORE 64 LADDER NETWORK ANALYSIS PROGRAM "ALADYN-64"

This program is a menu-driven design tool with a built-in circuit file editor, fast calculations and graphic output to either the screen or printer. Useable for circuits which operate from VLF through Microwave. Circuit elements include R's, L's, C's, transmission lines, transistors and FET's. Output format rectangular or Smith chart.

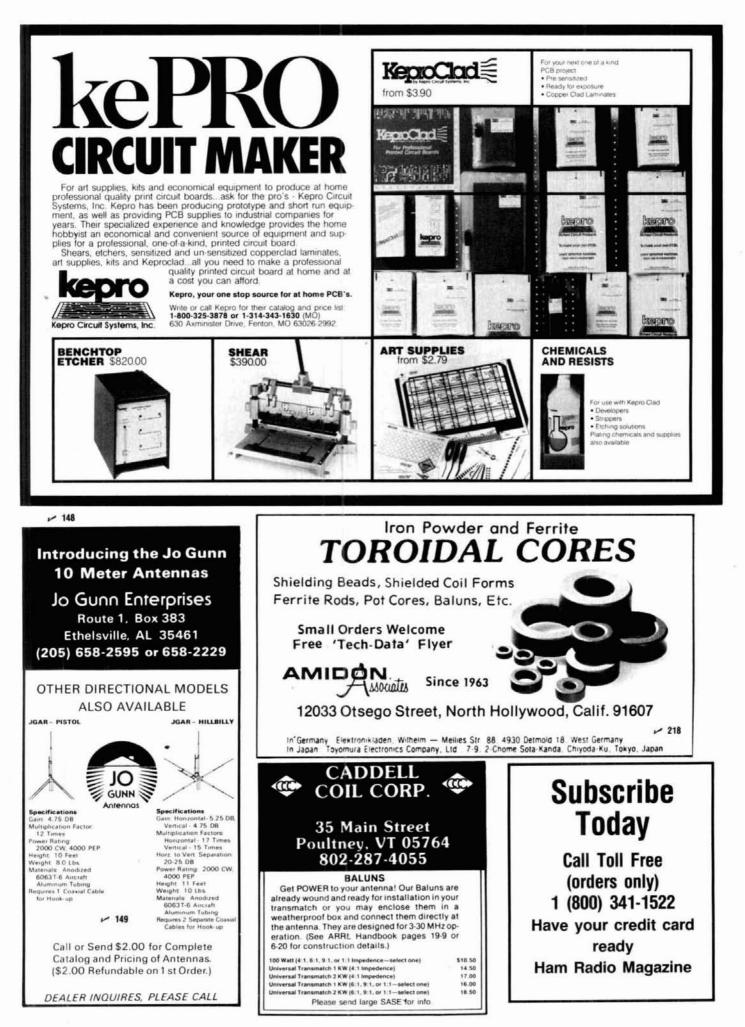\$59.95 PPD. Check or M.O. INTERCEPTOR ELECTRONICS INC. ROUTE 1, BOX 439, ROUND HILL, VA 22141-9307 PHONE (703) 338-4905







a 2-meter halo antenna

After obtaining a 2-meter multimode radio and operating it mobile for a short time, I came to a conclusion: 2-1/2 watts output and a 5/8-wave vertical wasn't good enough.


I decided to improve the antenna first; I could install my small 80-watt amplifier later for long trips. I decided to build a 2-meter halo since I'd worked several mobile stations who were using them, and they seemed to do a good job.


construction

The halo is a half-wave dipole bent into a circle (**fig. 1**). To make the insulator mounting block (**fig 2**), cut a piece of 1/2-inch thick plastic into a 2-1/2 by 3-inch rectangle. Cut a slot and drill the holes as shown in **fig. 2**.

The driven element or dipole is made from a 38-inch long, 3/8-inch diameter piece of copper tubing. Mark the center of the piece of tubing and bend it into a hoop measuring 12 inches in diameter. Drill a 9/64-inch hole at the top of the center mark on the dipole element. Secure the dipole element to the mounting block by inserting a screw through the dipole element and mounting block. Fasten with a lockwasher and nut. Insert a small piece of 5/16-inch diameter wood dowel into the ends of the halo element, leaving a 1-1/2 inch gap between the tubing ends. This completes the main element of the halo (see fig. 1).

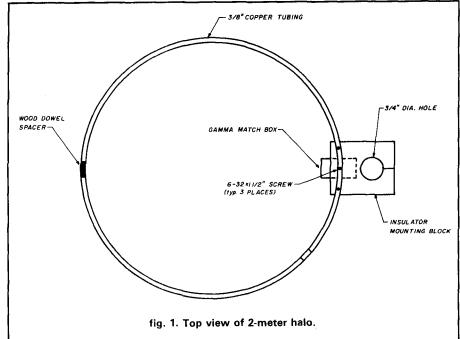To assemble the rest of the halo, refer to **fig. 3**. Mount the small plastic



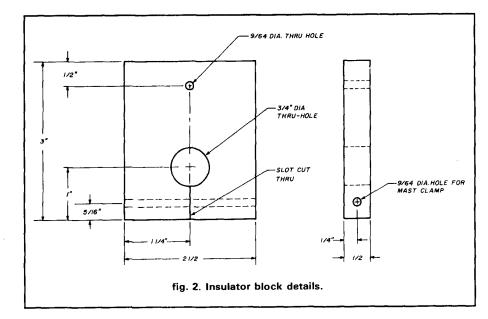

(not metal!) box under the insulator mounting block.

Following the details shown in **fig. 3**, drill the holes in the box and install the coax connector and gamma match capacitor. A variable capacitor of about 35 pF will work fine.

A 6-inch length of 3/8-inch diameter copper tubing is used for the gamma rod. Bend it around the halo's element to form it into a slight circle. Make a shorting bar now so you can secure the gamma rod to the halo antenna. (Any kind of easily bendable metal will work.) Be careful to keep the spacing between the gamma rod and dipole element to about 1-3/4 inch.

Insert one end of the gamma rod into the gamma match box and install the shorting bar on the other end.

Lay the halo on its side, with the open end of the gamma box facing up. Apply some 5-minute epoxy around the gamma rod and let it dry. Your halo is now finished and needs only to be tuned. $\longrightarrow \mathcal{M} \longrightarrow$

1987 CALLBOOKS



The "Flying Horse" sets the standards

Continuing a 66 year tradition, there are three new Callbooks for 1987.

The North American Callbook lists the calls, names, and address information for licensed amateurs in all countries from Canada to Panama including Greenland, Bermuda, and the Caribbean islands plus Hawail and the U.S. possessions.


The International Callbook lists the amateurs in countries outside North America. Coverage includes South America, Europe, Africa, Asia, and the Pacific area.

The 1987 Callbook Supplement is a new idea in Callbook updates; it lists the activity in both the North American and International Callbooks. Published June 1, 1987, this Supplement will include all the new licenses, address changes, and call sign changes for the preceding 6 months.

Publication date for the 1987 Callbooks is December 1, 1986. See your dealer or order now directly from the publisher.

	-
DNorth American Callbook	
incl. shipping within USA	\$28.00
incl. shipping to foreign countries	30.00
International Callbook	170215-0202
incl. shipping within USA	\$28.00
incl, shipping to foreign countries	30.00
Callbook Supplement, published J	
incl. shipping within USA	\$13.00
incl, shipping to foreign countries	14.00
SPECIAL OFFER	
Both N.A. & International Callboo	ks
incl. shipping within USA	\$53.00
incl, shipping to foreign countries	58.00

Illinois residents please add 6½% All payments must be in U.S. fu	
	С.
Dept. F	
925 Sherwood Dr., B	ox 247
Lake Bluff, IL 60044	, USA
Tel: (212) 224 6600 VISA	Manfercaro
Tel: (312) 234-6600	
	~ 1
CA 100 NA	- 10

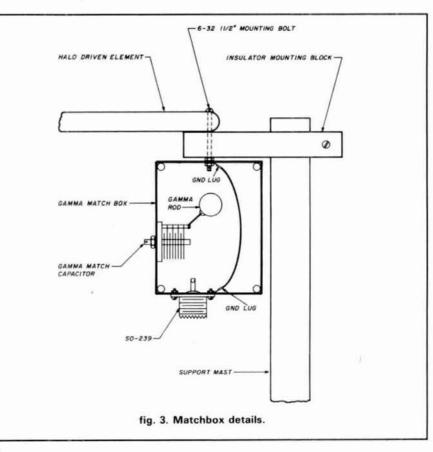

tuning

Mount the halo 5 to 6 feet above the ground or temporarily attach it to your car. Adjust the spacing on the driven element for minimum reflected-power indication. (Mine was lowest at an 11/16-inch spacing.) Do the same for the shorting bar, sliding it back and forth along the gamma rod. (My lowest SWR was 1 inch from the end of the gamma rod.) The final adjustment is made by tuning the gamma-match capacitor for minimum reflected power. My final SWR is 1.2:1 on the halo.

Remove the halo and seal the gamma match box. Plug the end of the gamma rod with RTV or epoxy. Coat the wood dowel spacer on the driven element with epoxy; this will waterproof it and keep it from slipping. The last step is to spray paint the assembly with a nonlead-based paint.

The 2-meter halo has increased my range significantly. While on vacation in Oklahoma, I worked West Virginia, New Jersey, and Maryland during an E opening. (My normal range is 50 to 100 miles with only 2-1/2 watts.) One final word of caution: if you build and mount the halo, be prepared for lots of stange stares and questions. You'll get plenty of them.

> Jerry Felts, NR5A ham radio

short circuit MMIC multiplier chains

In fig. 5 of N6JH's article, "MMIC Multiplier Chains for the 902-MHz Band" (February, 1987, page 72), all values indicated as "µF" should be corrected to read "pF." Note too that coil L1, which can be seen just to the left of the crystal and directly above the partially meshed plates of the variable capacitor (fig. 7), is not the same as the coils in the multiplier. L1, which is five turns of No. 24 (AWG), is airwound with an interior diameter of about 0.2 inches - this dimension is not critical because only broad resonance is needed to select the correct crystal overtone.

64 May 1987

AAIRAGE/KLM

The **BEST** is still

"made in U.S.A."

American made RF Amplifiers and Watt/SWR Meters of exceptional value and performance.

•5 year warranty • prompt U.S. service and assistance

RF AMPLIFIERS

E101

2 METERS-ALL MODE

B23 2W in = 30W out (useable in: 100 mW-5W)

B108 10W in =80W out (1W = 15W, 2W = 30W) RX preamp

B1016 10W in = 160W out (1W = 35W, 2W = 90W) RX preamp

B3016 30W in = 160W out (useable in: 15-45W) RX preamp (10W = 100W)

220 MHz ALL MODE

C106 10W in = 60W out (1W=15W, 2W=30W) RX preamp

C1012 10W in = 120W out (2W = 45W, 5W = 90W) RX preamp

C22 2W in = 20W out (useable in: 200mW-5W)

RC-1 AMPLIFIER REMOTE CONTROL Duplicates all switches, 18' cable

WATT/SWR METERS

• peak or average reading • direct SWR reading MP-1 (HF) 1.8-30 MHz MP-2 (VHF) 50-200 MHz

430-450 MHz ALL MODE D24 2W in=40W out

(1W = 25W) D1010 10W in = 100W out

(1W = 25W, 2W = 50W)

Available at local dealers throughout the world.

✓ 152



16890 Church St., Morgan Hill, CA 95037. (408) 779-7363





More Details? CHECK-OFF Page 130

May 1987 🚾 67

New PK-232 Breakthrough

Six Digital Modes - Including Weather FAX



\$379.95 AEA RETAIL

Your home computer (or even a simple terminal) can be used for radio data communication in six different modes. Any RS-232 compatible computer or terminal can be connected directly to the PK-232, which interfaces with your transceiver. The only program needed is a simple terminal program, like those used with telephone modems, allowing the computer to be used as a data terminal. All signal processing, protocol, and decoding software is in ROM in the PK-232.

The PK-232 also includes a no compromise VHF/HF/CW modem with an eight pole bandpass filter, four pole discriminator, and 5 pole post detection low pass filter. Experienced HF Packeteers are reporting the PK-232 to have the best Packet modem available.

Operation of the PK-232 is a breeze, with twenty-one front panel indicators for constant status and mode indication. The 240 page manual includes a "quick start" section for easy connection and complete documentation including schematics. Two identical back panel radio ports mean either your VHF or HF radio can be selected with a front panel switch. Other back panel connections include external modem disconnect, FSK and Scope Outputs, CW keying jacks, and RS-232 terminal interface.

The RS-232 connector is also used for attaching any Epson graphics compatible parallel printer for printing Weather Fax. Weather maps and satellite photos, like the one in this ad, can be printed in your shack.

Contact your local AEA dealer today for more information about the one unit that gives you six modes for one low price, the PK-232.



2006-196th St. SW Lynnwood, WA 98036 (206) 775-7373

a no-compromise, multiband, low-VSWR dipole

Back-to-basics design uses capacitor divider/balun for high-efficiency operation

In searching for an effective, balanced feed system for a dipole, I developed an antenna that's efficient, exhibits low VSWR across several bands at the same time, and meets my original objectives. Patented under the title, "Dipole of Delight," its design is based on the use of a capacitive balun at the center of the dipole.^{1,2,3}

The use of capacitors at the midpoint of the dipole allows the resonance currents in the dipole to reach larger amplitudes than are possible when the 50-ohm cable impedance is present as a series resistance. Apart from the copper loss, the principal limitation of resonant currents is the radiation loss. For this reason the capacitor dipole is highly efficient and has a very wide bandwidth.

Before studying the details, one should review the problems associated with the traditional half-wave dipole (see **fig. 1**), which are chiefly:

an unbalance that causes an undesirable current on the outside of the shield results in higher levels of electrical noise from local sources on receive, and on transmit provokes annoying rf voltages at the transceiver (i.e., microphone feedback or finger burns); and
matching problems between free-space impedance (377 ohms), a typical traveling wave on a wire dipole (800 ohms), and the feedpoint impedance of a halfwave dipole, said to be 73 + j 42 ohms.⁴

The first problem experienced with the conventional dipole has traditionally been solved by using a balanced feedline or a transformer balun. Unfortunately, use of a transformer brings its own problems: increased weight; the possibility of saturation and harmonic generation; or introduction of even more inductive reactance, from its leakage reactance, which necessitates shortening the antenna more than the customary 5 percent to achieve resonance.

The next step involves replacing the dipole with its equivalent (resonant) circuit as seen at its center where the voltage is least and the current is maximum. See **figs. 1, 2,** and **3**.

The magnitude of the various components are:

$$Z_o = \sqrt{\frac{L}{C}}$$

where Z_o = traveling wave impedance where L = inductance per meter and C = capacitance per meter traveling wave velocity

$$v = \frac{l}{\sqrt{LC}}$$

Rearranging terms, the impedance exhibited by a wire can be expressed in terms of velocity and capacitance as:


$$Z_o = \frac{1}{vC}$$


Because the velocity of a traveling wave on a wire in air is almost equal to its free-space velocity $(3 \times 10^8 \text{ m/s})$ and the capacitance per meter of a 2-mm (0.08 inch) diameter wire is approximately 4.17 pF, then this same 2-mm diameter wire impedance is:


$$Z_o = \frac{1}{3 \times 10^8 \times 4.17 \times 10^{-12}} = 800 \text{ ohms}$$

The circuit can be considered to consist of two equal and opposite sign reactances (800 ohms) that correspond to two oppositely traveling waves, and a shunt

Maurice C. Hately, GM3HAT, 1 Kenfield Place, Aberdeen AB1 7UW, Scotland, UK.

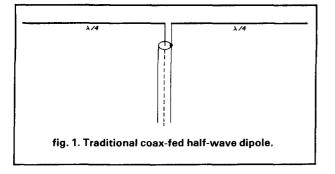

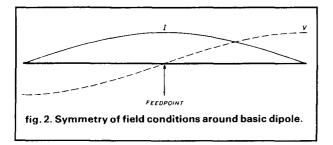

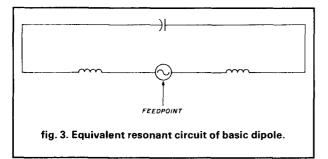



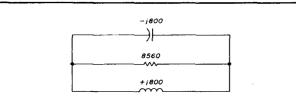



fig. 4. Parallel resonant circuit equivalent to practical dipole.

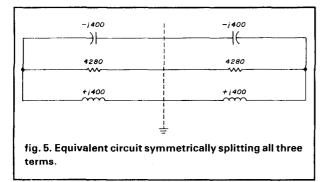



resistance that represents total losses (mainly attributable, one would hope, to radiation into space). The half-power bandwidth of a half-wave dipole is 9.3 percent of the nominal resonance frequency.⁵ Q is the reciprocal of the percentage bandwidth or equal to 1/0.093 = 10.7 (for a length-to-diameter (L/D) ratio of 10,000 and a height above ground of $\lambda/4$). The shunt loss resistance value (i.e., radiated power) in parallel resonance is reactance times Q or 800 x 10.7 = 8.56 k. On the other hand, the series equivalent "loss" resistance (series resonance) is 800/10.7, or approximately 73 ohms. Figure 4 shows the complete parallel equivalent circuit. Figure 5 shows the next progression, developed by splitting all three terms, which enables one to place at this location a virtual ground or balance point. Next, fig. 6 shows the actual induction field couplings which exist from end to end. M shows the magnetic field and E shows the antiphase electric field coupling. (The electric field has two 180-degree out-of-phase components that are at the same time out of phase with the current maxima and magnetic field. In other words, the energy stored in the resonant system of the antenna has either most of its energy in the electric field, or a quarter of a cycle later in time, in the magnetic field.) These are not small effects - in fact. they are considerable and must therefore always be taken into account.


If Kraus had drawn the half-wave dipole in this way, he would have shown it as it appears in fig. 7.4 The extra -j42 ohms required for resonance, and the necessity for some balun in order to properly feed the coaxial cable, led me to decide to put in series two equal-value capacitors of -j21 ohms reactance and to feed the power across one of them as shown in fig. 8. The coaxial shield is now connected to the electric field center of the antenna. When first tried, this arrangement immediately showed promise in the removal of most of the local hash from machines, TV sets, and computers. But the VSWR on the feeder could not be reduced below 2:1 no matter what value capacitors were tried, or at which length or frequency the antenna was operated. Some of the problems must have been attributable to the unwarranted connection

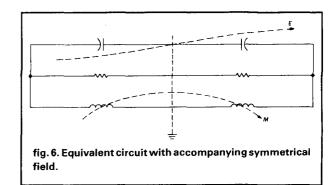

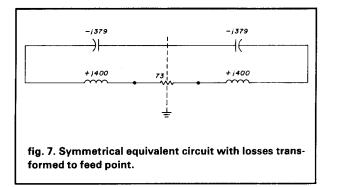

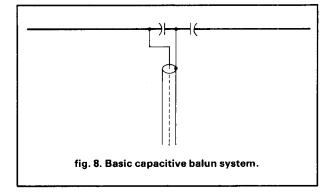


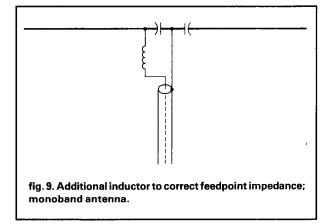


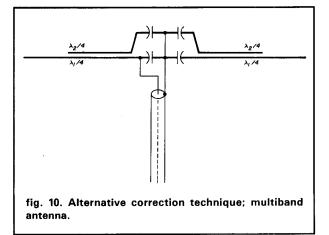

of a capacitor of only 21 ohms across a 50-ohm feeder. It turns out that there are two solutions to this problem: you can install a series inductor before the capacitor (see **fig. 9**) or use a second resonant circuit, thereby making the antenna a dual-band radiator (see **fig. 10**). This approach extended its operating on two, three, four, or even five bands with low SWR, while still providing a balanced structure — hence the name, "Dipole of Delight," under which these capacitor dipoles are sold.

The additional reactance needed in the capacitive balun of the monoband dipole helped match the transmission line (50 ohms) to 800-ohm characteristic impedance of the antenna wires. It turns out that the optimum capacitive reactance is -j50 ohms (see fig. 11). If this is redrawn as a single-ended equivalent, all the components must be scaled down by a factor of $1/\sqrt{2}$ (This is due to the sharing of the load in the two halves and the doubling of the impedance on return to a dual, or balanced form (fig. 12). After slight rearrangement (fig. 13), the two capacitors are seen

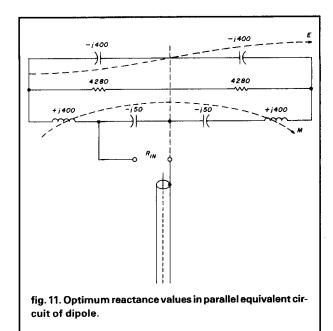


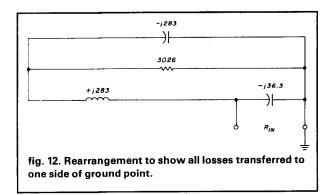



as a capacitive autotransformer that works efficiently because of the considerable circulating current **I**. The equivalent inductive autotransformer is shown in **fig. 14**. The input resistance seen by the source is


$$3026 \ x \ \left(\frac{36.3}{283}\right)^2 = 49.7 \ ohms$$


Figure 15 shows a series inductive reactance of almost j50 ohms. This is needed to cancel out the equal

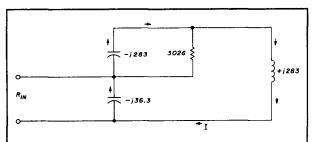

 

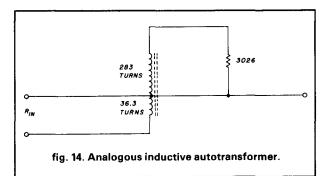

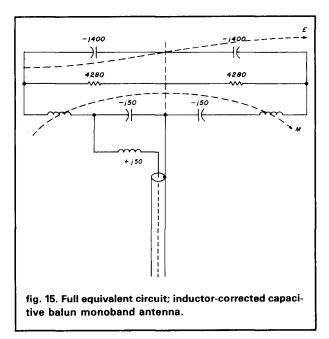

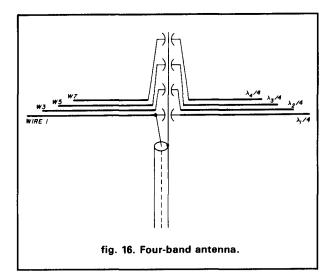

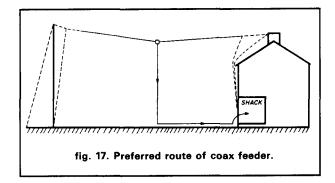


Table 1. Input impedance is a genuine 50 ohms for a con-	
siderable bandwidth.	

Frequency (MHz)	VSWR	
13.7	1.45	
13.8	1.25	
13.9	1.14	
14.0	1.08	
14.1	1.03	
14.2	1.02	
14.3	1.07	
14.4	1.13	
14.5	1.22	
14.6	1.30	
14.7	1.40	
14.8	1.50	

and opposite capacitive reactance of 50 ohms, leaving a pure resistive termination of approximately 50 ohms. The Q of this resonant circuit is 1, and consequently does not affect the overall bandwidth of the system. The antenna bandwidth is determined by the Q of the dipole (10.7). As **table 1** shows, the input impedance is a genuine 50 ohms over a considerable bandwidth.



The excellent sensitivity of the 1200H makes it ideal for use with the telescoping RF pick-up antenna; accurately and easily measure transmit frequencies from handheld, fixed, or mobile radios such as: Police, firefighters, Ham, taxi, car telephone, aircraft, marine, etc. May be used for counter surveillance, locating hidden "bug" transmitters. Use with grid dip oscillator when designing and tuning antennas. May be used with a probe for measuring clock frequencies in computers, various digital circuitry or oscillators. Can be built into transmitters, signal generators and other devices to accurately monitor frequency.

The size, price and performance of these new instruments make them indispensible for technicians, engineers, schools, Hams, CBers, electronic hobbyists, short wave listeners, law enforcement personnel and many others.

STOCK NO:

#1200HKC	Model 1200H in kit form, 1-1200 MHz counter complete including all parts, cabinet, Ni-Cad batteries, AC adapter-battery charger and instructions \$ 99.95
#1200HC	Model 1200H factory assembled 1-1200 MHz counter, tested and calibrated, complete including Ni-Cad batteries and AC adapter/battery charger \$137.50
#1300HC	Model 1300H factory assembled 1-1300 MHz counter, tested and calibrated, complete including Ni-Cad batteries and AC adapter/battery charger \$150.00
ACCESSOR	NES:
#TA-1005	Telescoping RF pick-up antenna with BNC connector \$12.00
#P-100	Probe, direct connection 50 ohm, BNC connector \$18.00
이가 프로그램 등 등	

CC-70	Carrying case, black vinyl with zipper opening. Will hold a counter and					
	accessories	00				
4 4879						

FLA (305) 771-2050





OPTOelectronics inc 5821 N.E. 14th Avenue Ft. Lauderdale, Florida 33334

Orders to US and Canada add 5% of total (\$2 min., \$10 max) Florida residents add 5% sales tax. COD fee \$2.

1.3 GHZ

13007548


AVAILABLE NOW!

SEE US AT DAYTON BOOTH #49

MasterCard


VISA

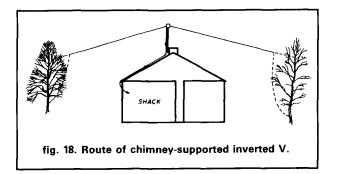This second solution - i.e., the addition of a second, third, or fourth resonant system with voltage dividing capacitors, as shown in **figs. 10** and **16** - works by inducing current in the resistive components by inductive coupling from left-hand-traveling current



in wire 1 to right-hand-traveling current in wire 2 into capacitor 2, and so on. **Table 2** gives the measured SWR values for a four-band antenna for the older hf Amateur bands. The system is not harmonic-dependent however, as can be seen in **table 3**, which lists data for a production version for the WARC Amateur bands.

Figure 19 shows the Smith chart display of the input impedance of a four-band Dipole of Delight when fed through approximately 50 feet of transmission line. The dot at the exact center of the chart represents exactly 50 ohms. Notice how closely the curve approaches this point for the 40, 20, 15, and 10-meter Amateur bands. **Figure 20** illustrates the effect with the feeder length canceled out. The equipment used for these experiments was a Hewlett-Packard Network Analyzer Model 8407A sweeping from 1 to 33 MHz.

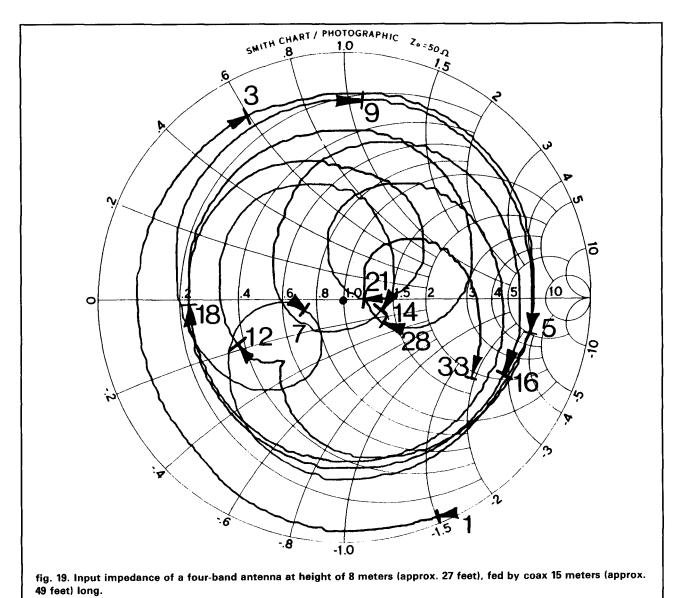

74 May 1987



A DIVISION OF TREVOSE ELECTRONICS 4033 BROWNSVILLE RD., TREVOSE, PA 19047 (215) 357-1400

-

SPECIAL PRICES

Join AMSAT...Today

Amateur Radio Satellite OSCAR 10 provides:

• A New Worldwide DX Ham Band open 10 hours a day.

• **Rag Chew With Rare DX Stations** in an uncrowded, gentlemanly fashion.

• **Popular Modes In Use:** SSB, CW, RTTY, SSTV, Packet

• Full Operating Privileges open to Technician Class licensee or higher.

Other AMSAT Membership Benefits:

Newsletter Subscription: Dependable technical articles, satellite news, orbital elements, product reviews, DX news, and more.

> Satellite Tracking Software Available for most popular PCs.

QSL Bureau, AMSAT Nets, Area Coordinator Support, Forum Talks

Construction of Future Satellites For Your Enjoyment!

AMSAT Membership is \$24 a year, \$26 outside North America. VISA and MC accepted.

AMSAT P.O. Box 27 Washington, DC 20044

301 589-6062

🗸 159

Table 2. Measured SWR values for a four-band antenna for the older hf Amateur bands.

Frequency	VSWR	
(MHz)		
7.00	1.3	
7.05	1.2	
7.10	1.3	
7.15	1.4	
7.20	1.6	
14.0	1.32	
14.1	1.15	
14.2	1.20	
14.3	1.30	
14.35	1.45	
21.0	1.3	
21.1	1.15	
21.2	1.15	
21.3	1.25	
21.4	1.37	
28.0	1.62	
28.2	1.45	
28.4	1.22	
28.6	1.05	
28.8	1.35	
29.0	1.55	

Table 3. Measured SWR values for a production version for the WARC Amateur bands.

Frequency (MHz)	VSWR	
9.9	1.45	
10.0	1.3	
10.1	1.18	
10.2	1.25	
18.0	1.25	
18.1	1.15	
18.2	1.20	
18.3	1.32	
24.8	1.38	
24.9	1.12	
25.0	1.08	
25.1	1.22	

capacitor construction

The capacitors consist of etched double-sided epoxy-glass-fiber circuit board. One side is not etched at all and is connected to the coaxial cable shield. The other side is etched, leaving copper patches (in pairs) of sufficient size to provide the needed capacitance for each wire. The glass fiber acts as the dielectric of the capacitor. In this way a lightweight capacitor balun without too much wind-catching area and usable at a kilowatt PEP level can be made from single-layer pc board. The only reported failures have been thought to be due to lightning flashover across the unconnected right-side wires to the shield. A solution to this problem is presently being investigated. For medium powers — up to 100 watts of rf power output lumped silver mica capacitors are used. These are easily concealed in a small center connector assembly which presents a negligible wind load. **Photo A** shows the center card and UHF connector and cable hanging from the water-shedding cowl.

ATU not needed

Since the VSWR is so close to 1:1 on 40 through 10, there's no need for an ATU between the transmitter and the antenna. This feature provides the freedom to QSY rapidly in a competitive situation without wasting time retuning. For blind or handicapped operators, it offers considerably simplified operation. For


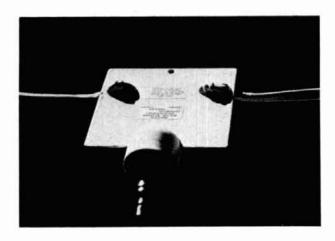


Photo A. Capacitor card of a three-band Dipole of Delight for 14, 21, and 26 MHz.

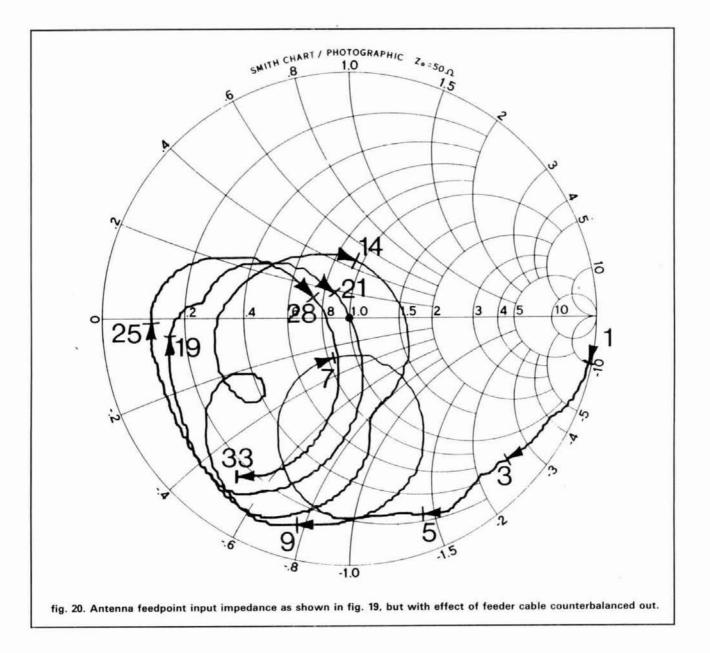



The monthly magazine with a natural blending of two popular hobbies --- Ham Radio and Computers

- * Articles on Ham Radio & Most Personal Computers
 - ★ Hardware & Software Reviews
 - ★ Various Computer Languages
 - + Construction Articles
 - 🛧 Much Much More

Your #1 Source for PACKET Info

"...received my moneys worth with just one issue..."

-J. Trenbick

"...always stop to read CTM, even though most other magazines I receive (and write for) only get cursory examination..."

—Fred Blechman, K6UGT

U.S.A	\$18.00 for 1 year
Mexico, Canada	\$32.00
Foreign	\$43.00(land)-\$68.00(air)
(U.S. funds only)	
Permanent (U.S S	Subscription)\$150.00
Sample Copy	\$3.50



Circulation Manager 1704 Sam Drive



use with a no-tune semiconductor PA or linear, no antenna system could be more appropriate. The VFO is the only control that has to be moved!

Electrically, it's advantageous to have the shield of the coaxial cable at the rf zero potential right down to the shack. It should be emphasized that in order to preserve the balance, the cable should come away from the dipole at right angles until the feeder gets to an object such as the ground beneath the antenna, a tree, or a garage roof, for example, where it may then be turned to run to the shack along the same earth boundary (see figs. 17 and 18). This helps reduce VSWR. Observe SWR as shown in fig. 17, then pull the feedline to the side and watch the SWR rise from 1.02:1 and go up to 1.3:1. With the thorough balance of the Dipole of Delight it's never necessary to ground the case of the transceiver. There's a complete absence of rf feedback to the microphone and electronic keyer, and never any sign of "hand capacitance."

Because the feedline is at rf zero voltage right to the center balun unit, the Dipole of Delight works well as an inverted V. The support can be metal or any other material and there will be no effect on VSWR or radiation pattern.

helps TVI

Since no current flows down the outside of the feedline, no vertical polarization rf currents are induced into the downleads of nearby TV antennas. One disabled GM operator for whom ham radio is his main daytime activity (he tells me he is on 40 and 80 meters for 8 to 10 hours every day and likes to use his linear all the time) has found that a dual-band Dipole of Delight has not only cured TVI and BCI next door, but has also cured interference to an electronic organ at a church across the street. Now he can operate on Sunday mornings as well! We don't promise purchasers that TVI will be less than they've had with other antennas; in fact, the ground plane versions of these antennas^{1,3} are definitely not recommended where TVI is a problem, though they are nevertheless useful for low-angle radiation, of course.

references

1. M. C. Hately, GM3HAT, "Multiband Dipole and Ground Plane Antennas," Patent Application No. 81 27439, September 10, 1981. (Granted UK Patent No. 2 112 579 and USA No. 4,518,968 from this priority date.)

2. M. C. Hately, GM3HAT, Lecture at Scottish Amateur Radio Convention, "Multiband Dipole and Ground Plane Antennas," Glenrothes, September 12, 1981.


3. M. C. Hately, "Multiband Dipole and Ground Plane Antennas," IEE Conference Proceedings No. 245, pages 102-106. (Lecture to IEE International Conference on HF Communications Systems and Techniques, February, 1985.)

4. J. D. Kraus, W8JK, Antennas, McGraw-Hill, 1948. (See Equation 10.59.)
5. L. A. Moxon, *HF Antennas for All Locations*, Radio Society of Great Britain, 1982, page 122.

6. National Research Development Corporation, British Technology Group, 101 Newington Causeway, London SE1 6BU.

ham radio



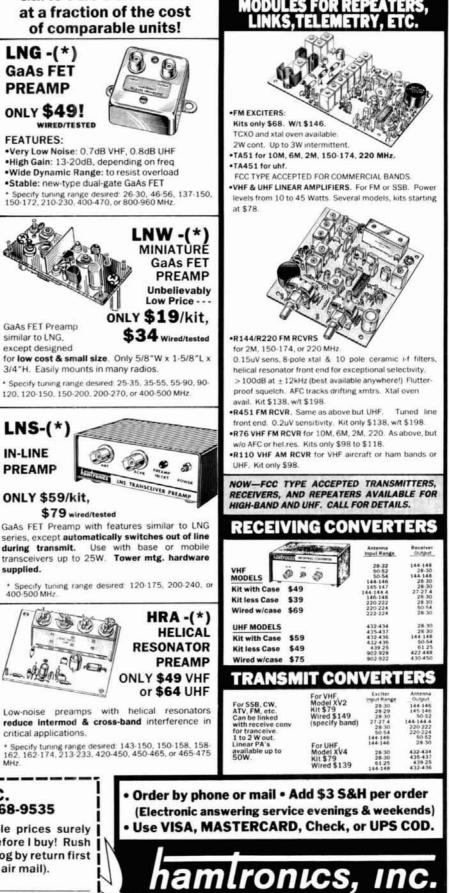

O 65-E MOUL ROAD+HILTON NY 14468-9535 Phone: 716-392-9430 Hamtronics* is a registered trademark

BY J. FERRELL

(Advertisement)



New Receivers. New Showrooms.

If you want to own the newest receiver around, then you'd better take a good look at the **Kenwood R-5000.** GILFER SHORTWAVE has them in stock – walk in and try it out in our new showroom – 210 sq. ft. of shortwave heaven. All the receivers and antennas operational.

You'll also see the best portable around, the **Sony 2010**. Why buy the copy when the original is at its lowest price ever!

New Book Offers.

Gilfer has a fascinating new book for utility buffs. Entitled **Utility Address Handbook**, authored by Reinhard Klein-Arendt, this compilation of UTE station addresses has the majority of world addresses and they're 99% up-to-date! Countries are listed in alpha order with stations listed by type. Address divisions are Post, telephone & telegraph, maritime, aeradio, airlines, meteorological, military, relief groups (Red Cross etc.) diplomatic, police, press, scientific, U.S. MARS, etc. This is the easiest way to get UTE addresses and the least costly, 140 pp just \$12.95 (+ \$2). For DXers interested in the subrosa broadcasts of the world, Gilfer publishes **Confidential Frequency List**, a 304 pp compendium of fixed, FAX, military, aeronautical, embassy, INTERPOL, VOLMET, press, coastal and hundreds of RTTY stations plus mystery stations etc. Covers 4 – 26 MHz by frequency and gives broadcast modes and hours. Chapters include an Introduction by Tommy Kneitel, a Primer on RTTY, About Cyrillic, etc. Now in its 6th edition. \$15.95 (+ \$2).

Save with this Combo Offer. Order both the Utility Address Handbook and the Confidential Frequency List and save \$6.95. Both for just \$24.95 postpaid!




The Best in Listening Aids.

This **Datong FL-3** Automatic Audio Filter, exclusive with Gilfer, gives you six different ways to dig out the weak SSB DX, hear CW you didn't know was there, pull RTTY out of noise, remove whistles and heterodynes. Has two notch filters, one manual, one automatic; variable high and low pass filtering. Easy between-receiverand-speaker connection. \$229.95 (+\$4).

Dayton Booth 446




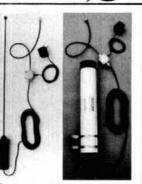

Gilfer exclusive – **Dressler** Active Receiving Antennas. They're perfect for limited antenna space – perform like they were outdoor full size jobs, but they fit anywhere. Two models: **ara 30** is ideal for SWL, covering 200 kHz to 30 MHz optimum, up to 100 MHz reduced performance. 10 dB gain. \$159.95 (+ \$4); model **ara 500** is perfect for VHF-UHF scanner receivers, covering 50 MHz – 650 MHz optimum, up to 900 MHz reduced performance. Up to 16 dB gain. \$169.95 (+ \$4).

Order service ph. 1-800-GILFER-1 For Flyer, send SASE GILFER SHORTWAVE 52 Park Ave, Park Ridge, NJ 07656 1-800-445-3371 • In NJ 201/391-7887

✓ 160

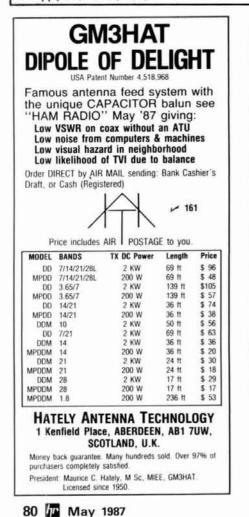



vaila	ble i m Un N	cation is n microfor liversity ficrofilms internation	
Name Company/In Address	stitution	ation about these titles:	
Name Company/In Address Gity	stitution		
Name Company/In Address Gity	stitution		

✓ 162



grounding, shielding, and isolating: part 2


Last month we discussed the problems of keeping outside interference from adversely affecting our equipment and preventing cross-interference between equipment in the same system.

Grounding problems affect not only single circuits, but collections of equipment as well. In **fig. 1A**, we see a prescription for disaster: the equipment grounds are daisy-chained together and grounded to earth at a point close to only one piece of equipment, identified as *D*. Typically, the ground lines are small-diameter sections of wire not particularly appropriate for the purpose.

One way to correct this problem the star ground - is illustrated in fig. 1B. Ground conductors from all four pieces of equipment are brought together at a common point, which is then grounded. Although it's difficult to achieve the exact configuration shown in fig. 1B in an actual Amateur station, we can approximate it using the arrangement shown in fig. 2. Keep in mind that our goal is to radiate as much of the available power as possible, while keeping spurious radiations (mostly harmonics) at home. Given the nature of most radio communications situations, if we have to sacrifice a little power at the fundamental operating frequency in order to lower the level of harmonics, then it's to our advantage to do so.

The signal flow logic for an hf sta-

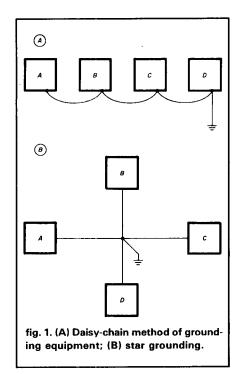tion is shown in the inset in fig. 2. The output circuit, a low-pass filter and an antenna matching network, surprises



few Amateurs. The low-pass filter for hf usually has a cutoff frequency above the 10-meter band, but below 6 meters (36 and 42 MHz are often quoted in the advertisements). Above that frequency, attenuation is quite high.

The antenna matcher is seen in many Amateur stations today because solid-state final amplifiers aren't tolerant of high VSWR loads. Such rigs include shut-down circuitry that reduces output power sharply when a VSWR greater than 1:1 is encountered. Previously, many Amateurs didn't use matching networks because tube-type finals used pi networks that could match a wide variety of antenna impedances. Many years ago, former ARRL President Vic Clark (W4KFC) told me that he recommended antenna matching networks even on wellmatched antennas because they add another stage of relatively high-*Q* tuned circuitry between the transmitter and the antenna . . . and thus reduce TVI-producing harmonics.

What may come as a surprise to many readers is the low-pass filter at the input of the linear amplifier. Because the exciter/transmitter output signal isn't perfectly clean, and will contain harmonic energy, we should attenuate those signals prior to amplifying them in a 1500-watt amplifier! Use of a low-pass filter helps that situation tremendously.

There is one problem with using a low-pass filter on some solid-state equipment. Many linear amplifiers, especially grounded-grid designs, either don't have a 50-ohm input impedance or have a widely varying input impedance that is frequency dependent. The characteristics of LC low-pass filters are guaranteed only when the correct load impedance is presented to the filter (in our case normally 50 ohms, resistive). If the linear amplifier input impedance varies, then filter performance is adversely affected. In addition, the impedance reflected to the filter input will also vary. This

	A STREET					le de la	Eta das	
		Lan 120						
		The second				Muter © \$50	912 Mills	
	000	000	000 0	0		000		
							PAL	
T						50	Hz to 51	2 MHz 5% X 5 X 1%
	10.4	10 MHz Ove	en Oscillator	X 8½ X	3%	1	PPM ACCL	
1	1011	E to The Grie .						
Optie	A Monthly and the		YEAR WARRAN		ie in the second	VISA	master charge	FOR DEALER LOCATIONS OR PHONE ORDERS
			MAX INSTR			20		800-854-1566 8560 Production Avenue San Diego, CA 92121
		FREQUENCY	ACCURACY OVER	READ		IVITY TYP.	POWER	California Call 619-578-7171 Telex #697120-DATAMAX-103
MODEL	PRICE	RANGE	TEMPERATURE	OUTS	50 Hz-25 MHz	25 MHz-450 MHz	REQ.	EXPORT AGENT: MAGNUS
and the second	\$149.95	50 Hz-512 MHz	1 PPM 17*-35*C TCXO	8	15 to 50 MV	20 to 50 MV to 450 MHz	8-15 VDC 300 MA	3500 Devon Avenue
D500	and the second second		TIME BASE			50 to 100 MV to 1 GHz	AC-12 REO. FOR	Chicago, IL 60659 312-679-6070
D510	\$179.95	50 Hz-1.0 GHz				2 to 20 MV	110 VAC	Telex #253503 MAGNUS CGO
and the second	\$179.95 \$259.95 \$299.95	50 Hz-1.2 GHz	0.1 PPM 20"-40"C PROPORTIONAL 10 MHz OVEN	9	15 to 50 MV 15 to 50 MV	to 450 MHz 20 to 30 MV to 1 GHz	8-15 VDC 500 MA	Telex #255505 MIAGNUS COO

New 6- & 8-Pole Crystal Filters For ICOM, Kenwood & Yaesu Radios

 ICOM 730/735/740/745/751/R70/R71A SSB 2.1kHz, 8-Pole – Exact replacement for FL-44A. Model IR455H1.05X-\$99
 ICOM IC-271/471/1271/ CW 400Hz, 8-Pole – Great for DXing or EME.

Model IR10.7H400C-\$115 • Kenwood TS-930/940/830/R-2000 CW Super Selective 250Hz 8-Pole 455 kHz Filter – Comes mounted on high-quality glass PC board for the TS-930 and TS-940, drops into the TS-830.

Model IR455H125C-\$125 • TS-940/930/830 Super Selective CW Switch Kit – This new kit allows you to add another CW bandwidth. For example, on the 930/940/830, if you already have 400Hz or 500Hz filters installed, you can now select a set of IR1250Hz filters. Our 250Hz matched set allows for a lower noise floor for super quiet DXing.

 9mHz 8-Pole Crystal Filters for Experi-All 8-Pole Filters-\$60 menters-All 6-Pole Filters-\$50 For SSB For FM A. 2.4kHz @ 6dB A. 1.5kHz @ 6dB B. 2.1kHz @ 6dB B. 30kHz @ 6 dB 1.8kHz @ 6dB For CW C D. 2.2kHz @ 6dB A. 600Hz @ 6dB ★ B. 600Hz @ 6dB ★ E. 2.2kHz @ 6dB For AM * (6-pole) A. 60kHz @ 6dB \$5.00 shipping and ★ B. 6.0kHz @ 6dB handling on all orders. YEA -

For more information, call International Radio, Inc. 747 So. Macedo Blvd. Port St. Lucie, FL 33452 Send S.A.S.E. (396) for latest catalog. (305) 879-6868

82 May 1987

164




ALL	BAND 1	RAP
"SLOP	ER" ANT	ENNAS!
Ave a HI-Power Ments. Rest I	JLL COVERAGEI ALL CS SELECTION with PF aled Traps - 16 Ga ROUND MOUNT SLO edeel Ground 1, 2014, 9 edeel Ground 1, 2014, 9 MY angle from Straight callent "SLOPER" I not it anywhere you n P Input, max. Perma Stalls In 10 minutes. MOST INVISABLE - DX Antenna. Ideal For RICTED AREAS - Pre- tands (axcept 80-160 CVER, COMPLETELY cas feedline and PL21 * ready to hookup	IOVEN Westherproof Copperweid Wirel IPERS - No Radiais - Nouse watter faucett luildings, Poles, etc at up to 60 degrees for 2X. Antenns Gain or ead to! 2000 watt inent or portable Use SMALL - NEAT - No one will know you r COND'OR APART- -tuned for 2-1 or iss -300kc) No adjust- ASSEMBLED, with 50 connector - Built
TIONSI No. 10805 - 80- No. 10405 40- No. 10205	40-20-15-10 — 1 trap 0-20-15-10 — 1 trap 20-15-10 — 1 trap -80-40-20-15-10 - 2 tr 60-40-20-15-10 - 2 tr 61c) or order using 1 atc) or order using 1 Number Ex Date. P	49 ft. 559.95 26 ft. 558.95 13 ft. 558.95 13 ft. 589.95 SA (Canada is \$5.00 VISA, MASCARD - 1-308-236-5333
1 yr - 10 day mor Dept. AH	WESTERN ELECT	

✓ 166

Sub Problem? Contact Sue. She'll fix it for you! (603) 878-1441


Ham Radio Greenville, N. H. 03048

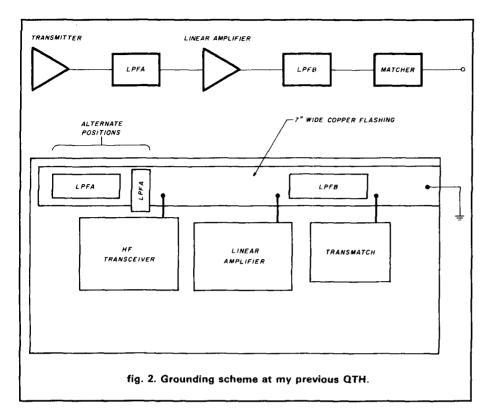

difficulty will cause a high VSWR to be seen at the transmitter output, causing it to fold back.

I experienced this problem using a Drake low-pass filter between a Kenwood TS-120 transmitter and a Heath SB-220 linear amplifier. There are two possible solutions. First, we can place a 50-ohm attenuator pad between the filter output and the linear amplifier input. The pad swamps out the impedance variations, although at the loss of some power. The attenuator pad method is recommended only where suitable resistors are available, and there's plenty of power to drive the linear and accommodate a 1- to 3-dB power loss. Second, we can either replace the low-pass filter with a variable matching network or add an antenna matcher to the circuit between the filter and amplifier. When I owned the TS-120, my solution was to use a Drake MN-4 matcher in place of LPF A (see fig. 2).

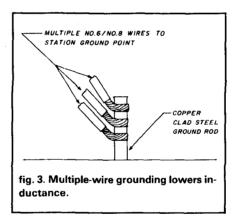Note the configuration of the operating position in **fig. 2**. The equipment was mounted on a door converted into a table. The grounding system consisted of a piece of 7-inch wide copper



roofing flashing along the back of the table. Though you probably won't find copper flashing at your local hardware store, it should be available from metal distributors and professional roofing supply outlets. (I found mine at a metal distributor after asking a neighbor, a contractor, where he bought his copper roofing supplies.)

Although the cost per foot (or per pound, as some sell it) for the amount that you need will probably be relatively low, the distributor may want a \$50 to \$100 minimum purchase. Joining with other Amateurs in a group order, therefore, might be wise. Copper flashing, or similar copper stock, is sometimes available through artists' supply outlets in areas where copper bas relief engraving and smithing is popular. The stock he showed me was only about half as thick as roofing flashing, but should work just as well.

The copper flashing on my desk is grounded at one end with a ground rod. In the station where I used this system, the building was a well-constructed (i.e., heated and air-conditioned) shed in the backyard. I was able to drop the copper foil through a break between the wall and the floor, then sweat-solder it directly to a ground rod driven into the earth. In other cases, it's necessary to use a heavy ground wire between the desk and the ground rod.

ground wires

A ground wire must be short and nonresonant, and possess low inductance. As a result, it's usually best to use a piece of heavy flat braid rather than circular wire. You'll find braid for sale at some outlets, but it's often quite expensive. I've found it cheaper to strip the shield carefully from an appropriate length of RG-8 or RG-11 coaxial cable.

Low inductance is achieved by using a wide, short conductor. The braid mentioned above possesses this property. It's also possible to cut some of the copper flashing into slices thinner than 7 inches and use it for a ground conductor. In other cases, it's possible to approximate the ideal by using ordinary circular wire conductors, but be sure to use multiple lengths of conductor in parallel (**fig. 3**). Automotive parts stores are often the best sources for such wire stock. Use either No. 6 or No. 8 "primary wire" or copper battery cable wire.

The conductors can be either clamped to the ground pipe (or rod) or sweat-soldered. Because of the heat sinking capacity of the pipe and ground, it's usually necessary to use a torch for sweat-soldering. Either a propane torch, one of the home "brazing" torches sold in hardware stores, or a jeweler's torch will suffice for this

800-882-	134	3
	OM	
Ö. 11		Juns
IC-735 Gen. Cvg. Xcvr IC-761A w/Antenna Tuner	\$999.00	Call \$
R7000 Gen. Cvg. Rcvr. R71A Gen. Cvg. Rcvr.	1099.00 949.00	Call \$ Call \$
IC-27A/H FM Mobile 25w/45w	429/459	Call \$
IC-28A/H FM Mobile 25w/45w IC-37A FM Mobile 25w	429/459 499.00	Call \$ Call \$
IC-47A 440 Mobile 25w	549.00	Call \$
IC-04AT UHF HT IC-48A UHF 45w	449.00 459.00	Call \$ Call \$
IC-38A FM Mobile 25w IC-02AT FM HT	459.00 399.00	Call \$ Call \$
IC-µ2AT Micro HT	329.00	Call \$
KENWC	00	D
	0.0	1
	\sim \circ	1
TS-440S/A	<u>.</u>	
TS-940SAT Gen. Cvg. Xcvr	\$2249.95	Call \$
TS-430S Gen. Cvg. Xcvr TS-711A All Mode Base 25w	819.95 899.95	Call \$ Call \$
TR-751A All Mode Mobile 25w		Call \$
TM-201B FM Mobile 45w TM-2530A FM Mobile 25w	369.95 429.95	Call \$ Call \$
TM-2550A FM Mobile 25w	469.95	Call \$
TM-2570A FM Mobile 70w TH-205 AT, NEW 2m HT	559.95 259.95	Call \$ Call \$
TH-215A, 2m HT Has It All	349.95	Call \$
TH21BT 2M HT TH31BT 220 HT	259.95 269.95	Call \$ Call \$
TH41BT 440 HT	269.95	Call \$
YAES	BU	
THITTE		4
		5
FT 757GX		
FT-757 GX Gen. Cvg. Xcvr	995.00	Call \$
FT-767 4 Band New FT-270RH FM Mobile 45w	1895.00 439.95	Call \$ Call \$
FT-290R All Mode Portable	579.95	Call \$
FT-23 R/TT Mini HT FT-209RH RM Handheld 5w	299.95 359.95	Call \$ Call \$
FT-726R All Mode Xcvr	1095.95	Call \$
FT-727R 2M/70CM HT FT2700RH 2M/70CM 25w	479.95 599.95	Call \$ Call \$
	1	
JUN'S	N	
ZELECT	RON	CS
	-11	
1-t-1	1	
3919 Sepulveda		
Culver City, CA 213-390-800		

84 May 1987

job. Choose your solder carefully, however. Some of the solder used for this purpose, and sold in local hardware stores, is acid-core. Also, some solders don't have the right metals mix. You want either resin core or coreless solder with resin flux, lead/tin solder of 50/50 or 60/40 mix.

Finally, make sure that the ground wire isn't resonant on either the fundamental frequency or one of the low order harmonics (e.g., second and third). Try to avoid even 1/8 or 1/4 wavelengths, even though this requirement may be difficult to achieve in practice on 80- to 10-meter antennas.

ground rods

The goal in a station ground system is to reduce the resistance between the radio and the earth. In most cases, this requirement translates to surface area in contact with the ground — and our job is to maximize that area. Several different options are available to us regarding ground rods.

First, we could do what a friend of mine did 20 years ago: he found an old copper bathtub in his grandfather's garage and buried it in an 8-foot deep hole. Considering the amount of work involved in burying a bathtub 8 feet underground, I'd prefer to sell the bathtub either for its metal content or its antique value . . . and use the proceeds to buy a truckload of proper ground rods!

Second, we could build a ground matrix grid on our property. When I was in high school, a local Amateur built a new home nearby. He arranged for several "custom extras" to the house. First, a concrete pedestal for the 60-foot tower was installed. Around the base of the tower was a series of eight or ten 8-foot copperclad steel around rods. He then constructed a grid of No. 12 solid copper wire (bare) over the entire 150 x 175-foot lot. At each crossover point on the grid the conductors were soldered together. He also added several more ground rods at nodes around the lot. The grid was clamped and soldered to the tower grounding system, then attached to a rather massive 3-inch copper pipe coming through the wall of the house from the intended operating position. After this extensive ground system was installed, sod was brought in by the builder, who was clearly bewildered by the seemingly odd behavior of his eccentric client.


Third, we can use copperclad steel ground rod, available in several lengths from electrical supply outlets. Although this type is preferred for Amateur applications, surprisingly few Amateur outlets sell these rods in the proper lengths. The non-copperclad type, though less useful for Amateur applications, is also available.


Copperclad steel rods are normally sold in 4-, 6-, and 8-foot lengths. Tenfoot lengths, used by some power companies, are also occasionally available. Of these, the 8-foot length is probably the best, and may be the only one legal in your area. (Your local electrical inspector may have an enforceable opinion regarding your choice of ground rod. In many jurisdictions, electrical codes specify the 6- or 8-foot minimum length for towers and sometimes even Amateur stations.)

The 4-foot types, typically used by TV antenna installers, are the most common. But because they're less effective for both radio grounding and lightning protection, they should be avoided — except, perhaps, where multiple rods are used.

Another alternative is shown in fig. 4. This ground system, which uses a copper plumbing pipe, is especially useful for areas with hard clay-rich soil. The top end of the pipe is fitted with a "Tee" connector and short pipe sections to be used as a handle. One end of the handle is closed off with an end cap, while the other is fitted with a spigot nipple of the sort used to connect a garden hose. The bottom end of the 1-inch x 8-foot pipe is beveled to a point with a hacksaw. Drive the pointed end into the ground and apply water pressure. Although a bit messy, this method will allow you to work the pipe down into the soil with relative ease.

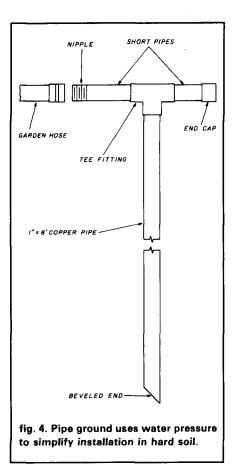When you finish driving the copper pipe into the ground you will discover



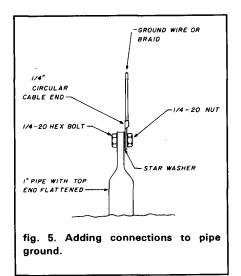

one of the advantages of this system. With conventional ground rods you must either sweat-solder the ground wire (which is sometimes difficult), or use a clamp (which easily comes loose). The pipe end can be flattened with a heavy pair of pliers, hammer (with a 2 x 4 backstop used as an "anvil"), or other means. You can then drill

one or more 1/4-inch holes in the flattened end to accept a nut and bolt to hold the ground wire (see fig. 5).

A word of caution is needed for those who are going to drive ground lines into the earth. Find out where the gas, water, sewer, and power lines are on your property. Although you can usually make intelligent guesses, some configurations are hard to determine. For example, at my old QTH, the gas line ran in a dog-leg path from the shutoff valve on the street to the meter on the back of the house. Unless you knew that the gas company was trying to serve two dwellings with the least amount of pipe, you wouldn't easily guess its path. Information on utility service run locations is often recorded on your survey plate, or in the local building inspector or engineer's office, or can be obtained from the utility involved. An 8-foot ground rod can disrupt these utilities - and that's always expensive and sometimes dangerous.

a warning on some defibrillator capacitors

In an earlier column I mentioned using medical defibrillator capacitors in high-power, high-voltage dc power supply filters. While that advice is still valid, a reader pointed out one possible pitfall. Some manufacturers of these machines depend upon the fact that defibrillator capacitors are charged for only a few minutes to de-rate some capacitors. As a result, in 7000-volt circuits they use capacitors with as little as 2000-WVDC dielectric strength. The small size of these capacitors enhances the portability of the product.

The capacitors to which I referred are high quality units manufactured by well-respected companies such as CDE and Sangamo; marked for 7500-WVDC or 10,000-WVDC, they're oil-filled and quite large. My reference capacitors came from American Optical and Hewlett-Packard (Model 7802) machines. No one has miniaturized those highvoltage capacitors significantly, so if a surplus defibrillator capacitor seems too small to be a 7 kV unit, then it probably isn't what it seems to be.

ham radio

		RF	Se Dayton	e us at Booth 360
TR/	٨N		STO	RS
		MHz 12V		
<i>P/N</i> MRF412./A		Rating 80W	Net Ea. \$18.00	Match Pr. \$45.00
MRF412,/A	۵	100W	22.50	51.00
MRF422* MRF426,/A*		150W 25W	38.00 18.00	82.00 42.00
MRF428,7A		12.5W	12.00	30.00
MRF449,/A MRF450./A	0 0	30W 50W	12.50 14.00	30.00 31.00
MRF453,/A	Q	60W	15.00	35.00
MRF454,/A MRF455,/A	a a	80W 60W	15.00 12.00	34.00 28.00
MRF458	-	80W	20.00	46.00
MRF475 MRF476		12W 3W	3.00 2.75	9.00 8.00
MRF477		40W	11.00	25.00
MRF479 MRF485*		15W 15W	10.00 6.00	23.00 15.00
MRF492	٩	90W	16.75	37.50
SRF2072 SRF3662	0 0	65W 110W	13.00 25.00	30.00 54.00
SRF3775	ä	75W	14.00	32.00
SRF3795 3800	Q Q	90W 100W	16.50 18.75	37.00 41.00
2SC2290	-	80W	19.75	45.50
2SC2879 <i>Q</i> = Select	Q ed Hiah	100W Gain Mat	25.00 ched Quads	56.00 Available
	-	HF TRAN		
R	ating	MHz	Net Ea.	Match Pr.
MRF224 MRF237	40W 4W	136-174 136-174	13.50 3.00	32.00
MRF238	30W	136-174	13.00	30.00
MRF239 MRF240,/A	30W 40W	136-174 136-174	15.00 18.00	35.00 41.00
MRF245	80W	136-174	28.00	65.00
MRF247 MRF607 1	75W .75W	138-174 136-174	27.00 3.00	63.00
MRF641	15W	407-512	22.00	49.00
MRF644 MRF646	25₩ 40₩	407-512 407-512	24.00 26.50	54.00 59.00
MRF648	60W	407-512	33.00	69.00
	150W	136-174 136-174	74.50 32.50	170.00 78.00
2N5591	25W	136-174	13.50	34.00
2N6080 2N6081	4W 15W	136-174 136-174	7.75 9.00	-
2N6082	25W	136-174	10.50	-
2N6083 2N6084	30W 40W	136-174 136-174	11.50 13.00	24.00 31.00
MRF134	516.		S & MODULE MRF497	.5 14.25
MRF136	21.		2N1522	10.50
MRF136Y MRF137	70. 24.		2N3866 2N4048	1.25 10.50
MRF138	35.	00	2N4427	1.25
MRF140 MRF148	89. 35.		2N5590 2N5642	10.00 13.75
MRF150 MRF172	89.	50	2N5643 2N5646	15.00 18.00
MRF174	62. 80.		2N5846 2N5945	10.00
MRF208 MRF212	11. 16.		2N5946 2SC2097	13.00 29.50
MRF221	10.	00	2SC2237	13.50
MRF260 MRF261		00 00	2SC1969 S10-12	3.00 13.50
MRF262	9.	00	SAV6	34.50
MRF284 MRF406	13. 14.		SAV7 SC1019	34.50 59.90
MRF428	55.	00	SC1027	47.50
NE41137	3.	50	M57737	47.50
Selected, ma				
cross-referen	Kenwood, Cubic, TWC, etc. Technical assistance and cross-reference on CD, PT, SD, SRF and 2SC P/Ns.			
			-call for quo C.O.D./V	
			Venty Dollari	
		9) 744		
	FA	X: (619) 74	4-1943	
			PAF	
Manul			6 Grand Av arcos, CA 9	

May 1987 12 85



CALL LONG DISTANCE ON YOUR HANDHELD

The Model 335A will deliver 35 watts of power using the latest state-of-the-art circuitry. The amplifier will operate SSB or

FM and is compatible with most handheld transceivers, including the TR2400, TR2500, IC-2AT, Yaesu, Santec, and Ten-Tec. Only 300 mw input will deliver 5 watts out; 3 watts in will deliver 35 watts out. Maximum input drive level is 5 watts.

VISA





gamma matching programs for the C-64/128

Simplify antenna matching with WBØIKN's handy program

WBØIKN's article, "Basic Gamma Matching" provided a useful program for the Apple II + computer. Because I needed gamma matching data for a homebrew project but have a C-64, I decided to convert the program. (If you own a Commodore 128, simply set the computer to 64 mode and you're ready to calculate.)

Figure 1 lists the revised program. The most significant modifications appear in the calculation lines. These changes were made to avoid exceeding the C-64's maximum input of 80 characters per statement.

I renumbered and compacted the program, adding an Option Menu from which you may choose to print hard copy, start new calculations, or end the program.

The final results were also truncated to two decimals; for practical purposes, this number of significant digits should be sufficient. The last three inputs of **line 10** change the screen/border/letter colors. If you prefer the standard blue, omit all POKE statements and colons in **line 10**.

design examples and program notes

To demonstrate the conversion program, and to allow you to check operation as well as the correctness of your data entry, I've used WBØIKN's design examples. I suggest you read his article; for convenience — or in case you don't have a copy of the January, 1985, issue — I've summarized details below. The hardest part will be determining the driven element impedance. Fortunately, the feedpoint characteristics of most common antennas are sufficiently documented to provide good data. Use your impedance meter or noise bridge, if no published data are available. You must know the diameter of your driven element and gamma rod. Then select an arbitrary gamma rod spacing. Use common sense, as in any homebrew project.

Load and run the program. Input the requested data when prompted. The computer will then calculate and display the results in the format shown in **figs. 3** and **4**.

If the values aren't acceptable, select Menu Option 2 ("all new calculations"). By trying a different gamma rod spacing or diameter, or varying the feedpoint impedance by slightly changing the length of the driven element, you can find the best combination with reasonable mechanical and electrical parameters. If the antenna isn't suitable for gamma rod matching, you'll learn this quickly, without tedious experimentation.

Figure 2 shows the screen display on a run for a computer-generated six-element, 20-meter Yagi design by Lawson.² The calculated feedpoint impedance of the antenna is 20 + j7.5 ohms. In this example, the assumptions are a 1.5-inch diameter element, a gamma rod diameter of 0.25 inch, and a gamma rod spacing of 3 inches.

additional designs

The results of two additional gamma match designs for the Yagi antenna are shown in fig. 3. In fig. 3(A) the gamma rod spacing has been increased to 6 inches; in fig. 3(B) the gamma rod diameter has been increased to 0.5 inch.

Figure 4 shows the results for a monopole approximately 1/4 wavelength high. In this case the

Fred A. Sontag, NØCAO, Lake Farm, Boute 1, Box 86, Tebbetts, Missouri 65080

```
10 PRINTCHR$(19)CHR$(147): POKE53280, 9: POKE53281, 0: POKE646, 5
20 REM***********
30 PRINT "GAMMA MATCH DESIGN"
40 PRINT "BY RICHARD A. NELSON - WBØIKN"
50 PRINT"FOR APPLE II+ COMPUTER"
60 REM*****
70 PRINT: PRINT "ADAPTED & CUSTOMIZED FOR C64 WITH"
80 PRINT"OPTIONS FOR PRINT/NEW CALCS.& END"
90 PRINT"BY - FRED A.SONTAG, P.E. - NOCAO
100 REM******
110 PRINT"* VERSION 1.3 *":PRINT
120 DEF FN CSH(X)=LOG(X+SQR(X*X-1))
130 PRINT"ENTER <M> FOR MONOPOLE": OPEN1,0
140 PRINT"ENTER <D> FOR DIPOLE > ";: INPUT#1, DM$: PRINT
150 IF DM$="D" OR DM$="M" THEN GOT0170
160 GOT0130
170 PRINT "ENTER FREQ IN MHZ > ";: INPUT#1, F: PRINT
180 PRINT"ENTER FEEDPOINT RESISTANCE > ";:INPUT#1,RA:PRINT:IFDMS="D"THENRA=RA/2
190 PRINT"ENTER FEEDPOINT REACTANCE > ";:INPUT#1,XA:PRINT:IFDMS="D"THENXA=XA/2
200 PRINT "ENTER FEEDLINE RESISTANCE > ";:INPUT#1,RO:PRINT
210 PRINT: PRINT: PRINT *** THE FOLLOWING ARE IN INCHES **"
220 PRINT:PRINT"ENTER DRIVEN ELEMENT DIAMETER > ";:INPUT#1,K:PRINT
230 PRINT "ENTER GAMMA ROD DIAMETER > ";:INPUT#1,B:PRINT
240 PRINT "ENTER GAMMA ROD SPACING > ";:INPUT#1,S:PRINT:CLOSE1
250 H=(1+((FNCSH((4*S*S-K*K+B*B)/(4*S*B)))/(FNCSH((4*S*S+K*K-B*B)/(4*S*K)))))*2
260 20=60*FN CSH((4*S*S-K*K-B*B)/(2*K*B)):T=H/ZO:A=((RO*XA)/(H*RA-RD))
270 W=(RD*((RA)+2+(XA)+2))/(H*RA-RD):Q=A+SQR(A*A+W)
280 XS=H*((RD*XA+SQR((RD*XA)+2+RD*(H*RA-RD)*((RA)+2+(XA)+2)))/(H*RA-RD))
290 LDGA=ATN(Q*T):LDG=(LDGA*360)/(2*3.14159)
300 E=(R0/RA)*(((RA)+2+(XA)+2)/Q):G=(R0/RA)*XA
310 CR=1000000/(2*3.14159*(E+G)*F): PRINTCHR$(147)
320 IF DM$="D" THEN RA=RA*2:IF DM$="D" THENXA=XA*2:PRINT
330 IFDMS="D" THENPRINT"DIPOLE ANTENNA"
340 IFDMS="M" THENPRINT"MONOPOLE ANTENNA"
350 PRINT: PRINT"FREQUENCY <MH2> = ";F
360 PRINT"DRIVEN ELEMENT DIAM = ";K:PRINT"GAMMA ROD DIAM = ";B
370 PRINT"GAMMA ROD SPACING = ";S:PRINT"DRIVEN ELEMENT RESISTANCE = ";RA
380 PRINT"DRIVEN ELEMENT REACTANCE = ";XA:PRINT"FEEDLINE RESISTANCE = ";RO
390 PRINT: N=LDG: GOSUB550
400 PRINT"GAMMA LENGTH <DEGREES> = ";U$:FT-(949/F)*(LDG/360):N-FT:GOSUB550
410 PRINT "GAMMA LENGTH <FEET> = ";U$: IN=FT*12:N=IN: GOSUB550
420 PRINT "GAMMA LENGTH <IN> = ";U$:CM=IN*2.54:N=CM:GOSUB550
430 PRINT"GAMMA LENGTH <CM> = ";U$:N=CR:GOSUB550
440 PRINT"GAMMA CAP IN PF = ";U$
450 PRINT: PRINTTAB(13)CHR$(18) "OPTION MENU"CHR$(146): PRINT
460 PRINT"1. HARDCOPY"
470 PRINT"2. ALL NEW CALCULATIONS"
480 PRINT"3. END"
490 OPEN1, 0: PRINT "PRESS OPTION NO.- THEN PRESS RETURN "; : INPUT#1, X: PRINT
500 IFX=1THENCLOSE1,0:GOT0530
510 IFX=2THENCLOSE1,0:GOTO10
520 IFX=3THENCLOSE1, 0: PRINTCHR$(147): END
530 OPEN3, 3: OPEN4, 4: PRINTCHR$(19); : FORI=0T0679: GOT0540
540 GET#3, AS: PRINT#4, AS; : NEXT: CLOSE3: CLOSE4: PRINTCHR$(147): GOTD470
550 US-STR$(N):L-LEN(US):PD-0:FOR I = 1 TO L:IF MID$(U$,I,1)-"."THEN PD-I
560 NEXT I: IF L <= (PD+2)THENRETURN
570 R$=MID$(U$,(PD+3),1):U$=LEFT$(U$,(PD+2)):IF R$<"S"THENRETURN
580 U=ABS(VAL(U$))+.01:U$=STR$(U*SGN(N)):RETURN
READY.
```

```
fig. 1. Gamma matching program listing for the C-64/128.
```

GAMMA MATCH DESIGN BY RICHARD A. NELSON - WBØIKN FOR APPLE II+ COMPUTER

ADAPTED & CUSTOMIZED FOR C64 WITH OPTIONS FOR PRINT/NEW CALCS.& END BY - FRED A.SONTAG, P.E. - NØCAO * VERSION 1.3 *

ENTER <M> FOR MONOPOLE ENTER <D> FOR DIPOLE > D ENTER FREQ IN MHZ > 14.200 ENTER FEEDPOINT RESISTANCE > 20.0 ENTER FEEDPOINT REACTANCE > +7.5 ENTER FEEDLINE RESISTANCE > 50

** THE FOLLOWING ARE IN INCHES **

ENTER DRIVEN ELEMENT DIAMETER > 1.5 ENTER GAMMA ROD DIAMETER > .25 ENTER GAMMA ROD SPACING > 3.0

DIPOLE ANTENNA

FREQUENCY <MH2> = 14.2 DRIVEN ELEMENT DIAM = 1.5 GAMMA ROD DIAM = .25 GAMMA ROD SPACING = 3 DRIVEN ELEMENT RESISTANCE = 20 DRIVEN ELEMENT REACTANCE = 7.5 FEEDLINE RESISTANCE = 50

GAMMA LENGTH <DEGREES> = 28.8 GAMMA LENGTH <FEET> = 5.34 GAMMA LENGTH <IN> = 64.09 GAMMA LENGTH <CM> = 162.78 GAMMA CAP IN PF = 188.92

UFICON MENU

1. HARDCOPY 2. ALL NEW CALCULATIONS 3. END PRESS OPTION NO.- THEN PRESS RETURN

fig. 2. Screen display for a sample run showing the sequence of data entry and output. (See text for 20-meter Yagi description.)

gamma rod is a length of No. 10 wire (approximate diameter = 0.1 inch). Figure 4(A) is for a 60-foot tower used as a vertical radiator on 3.8 MHz. (WB0IKN's computer analysis shows its impedance to be approximately 33 + j1.3 ohms. Figure 4(B) is for a 55-foot tower operated on the same frequency. The results show how a smaller gamma capacitor may be used if the radiator is made capacitively reactive by reducing its overall height.



May 1987 🌆 89

DIPOLE ANTENNA

FREQUENCY <MH2> = 14.2 DRIVEN ELEMENT DIAM = 1.5 GAMMA ROD DIAM = .25 GAMMA ROD SPACING = 6 DRIVEN ELEMENT RESISTANCE = 20 DRIVEN ELEMENT REACTANCE = 7.5 FEEDLINE RESISTANCE = 50

GAMMA LENGTH <DEGREES> = 25.32 GAMMA LENGTH <FEET> = 4.7 GAMMA LENGTH <IN> = 56.34 GAMMA LENGTH <CM> = 143.12 GAMMA CAP IN PF = 241.89

fig. 3A. Calculated results for additional run on the antenna described in fig. 2, showing gamma rod spacing increased to 6 inches.

DIPOLE ANTENNA

FREQUENCY <MHZ> = 14.2 DRIVEN ELEMENT DIAM = 1.5 GAMMA ROD DIAM = .5 GAMMA ROD SPACING = 3 DRIVEN ELEMENT RESISTANCE = 20 DRIVEN ELEMENT REACTANCE = 7.5 FEEDLINE RESISTANCE = 50

GAMMA LENGTH <DEGREES> = 38.34 GAMMA LENGTH <FEET> = 7.11 GAMMA LENGTH <IN> = 85.32 GAMMA LENGTH <CM> = 216.72 GAMMA CAP IN PF = 262.10

fig. 3B. Calculated results for additional run on the antenna described in fig. 2, showing gamma rod diameter increased to 0.5 inch.

As stated previously, I strongly recommend that you read WBØIKN's article and also the publications dealing with gamma matching design and construction referenced therein.

MONOPOLE ANTENNA

FREQUENCY <MHZ> = 3.8 DRIVEN ELEMENT DIAM = 12 GAMMA ROD DIAM = .1 GAMMA ROD SPACING = 12 DRIVEN ELEMENT RESISTANCE = 33 DRIVEN ELEMENT REACTANCE = 1.3 FEEDLINE RESISTANCE = 50

GAMMA LENGTH <DEGREES> = 44.82 GAMMA LENGTH <FEET> = 31.06 GAMMA LENGTH <IN> = 372.69 GAMMA LENGTH <CM> = 946.64 GAMMA CAP IN PF = 122.62

fig. 4A. Results of run for a 75-meter vertical monopole antenna on 3.8 MHz, (60-foot tower).

MONOPOLE ANTENNA

FREQUENCY <MH2> = 3.8 DRIVEN ELEMENT DIAM = 12 GAMMA ROD DIAM = .1 GAMMA ROD SPACING = 12 DRIVEN ELEMENT RESISTANCE = 25 DRIVEN ELEMENT REACTANCE = -38 FEEDLINE RESISTANCE = 50

GAMMA LENGTH <DEGREES> = 53.73 GAMMA LENGTH <FEET> = 37.24 GAMMA LENGTH <IN> = 446.82 GAMMA LENGTH <CM> = 1134.92 GAMMA CAP IN PF = 76.99

fig. 4B. Results of run for 75-meter vertical on 3.8 MHz, (55-foot tower).

references

1. Richard A. Nelson, WBØIKN, "Basic Gamma Matching," ham radio, January, 1985, page 29.

2. James L. Lawson, W2PV, "Yagi Antenna Design", harn radio, July, 1980, page 19.

ham radio





VHF/UHF WORLD for Keiser

optimized 2- and 6-meter yagis

Several years ago I decided to take a different approach to 2-meter EME. The idea was to build an array of eight small Yagis mounted on a short tower. The stacking frame would be attached to a single boom not exceeding 30 feet. Such a system could be mounted conveniently in my back yard with minimum interference to existing structures and would be easily transportable for EME DXpeditions.

It seemed reasonable that a physically small Yagi with a clean radiation pattern and high gain-per-unit boomlength could be designed.¹ Small Yagis require only short, low-loss phasing lines. If this approach was successful on 2 meters, I concluded, the design could later be scaled to 70 cm (432 MHz), where the individual Yagis could be rear-mounted and possibly rotated in polarity for EME operation.²

I decided that a 12-foot boom, 144-MHz Yagi might be the ideal answer for the individual antenna; 12-foot boom material is readily available, and short Yagis can be mounted on towers that are only 12 to 15 feet high.

Several designs emerged for both 2 and 6 meters. While some of the results of this study were unexpected, they do answer several frequently asked questions.

where to begin

I started by designing a 2-meter Yagi on a 12-foot boom. Obviously, the boomlength could not exceed 142 inches — which, at 144 MHz, is approximately 1.75 wavelengths. I wanted the sidelobes to be as low as possible, at least 16 to 18 dB in the E plane, and a minimum of 13 dB in the H plane. If improved performance was possible, so much the better.

I studied but quickly discarded the NBS Yagis because the only designs near my requirements, 1.2 or 2.2 wavelengths, were either too short or too long.³ Then I considered the Greenblum designs.⁴ Unfortunately, design information was incomplete; furthermore, previous Yagi designs using the Greenblum tables didn't produce very clean radiation patterns, especially in the H or vertical plane.

Several articles in the *IEEE Proceed-ings* discussed a method of optimizing Yagi performance through the use of nonequally spaced and nonuniform length elements.^{5,6} They started with an initial six-element design using equal spacing and director lengths. The elements were 0.0067 wavelengths in diameter on a 1.49 wavelength boom. The reflector was 0.51 wavelengths long and spaced 0.25 wavelength behind the driven. All directors were equally spaced at 0.31 wavelength and were 0.43 wavelengths long.

They ran a program similar to that used by Morris⁷ — the forerunner of the one used by W2PV⁸ — on a large IBM computer. It calculated the gain of this antenna at 11.2 dBi, with relatively high first sidelobes.

Maintaining the same reflector length and spacing, believed to be near optimum, the director spacings were mathematically iterated (adjusted in small steps) for maximum gain. This step increased the Yagi gain by 1.65 dB to 12.85 dBi. However, the boomlength had increased to 1.70 wavelengths, and all director spacings were now unequal. The pattern was definitely cleaner, but not terrific. The next step involved adjusting the reflector length and spacing, but very little improvement resulted.


A further improvement in the computer program through the use of larger matrices allowed for the simultaneous iteration of element spacing and length. The results were quite gratifying. After several optimizations, a new Yagi design with approximately the same boomlength (1.69 wavelengths with a gain of over 13.4 dBi) emerged, showing an improvement of 2.2 dB over the original constant length and spacing design and a cleaner radiation pattern.

Some preliminary conclusions can be drawn as a result of this study. With a fixed number of elements, there is a particular boomlength for optimum gain. Furthermore, gain and pattern aren't optimum when constant director length and spacing are used. For best Yagi performance, the boomlength and all element spacings and lengths must be individually optimized.

implementing the design

Limited practical information was, however, available for the "optimized" Yagi design. No element diameter scaling information was available to me at that time (in the mid-1970s) and the diameters recommended were rather impractical — over 0.5 inch at 2 meters! Therefore I decided to scale my own design by overlaying the element lengths on an NBS-type of scaling graph.³ I designed a 144-MHz Yagi using 3/16-inch diameter rod (0.0023 wavelength diameter at 144 MHz).

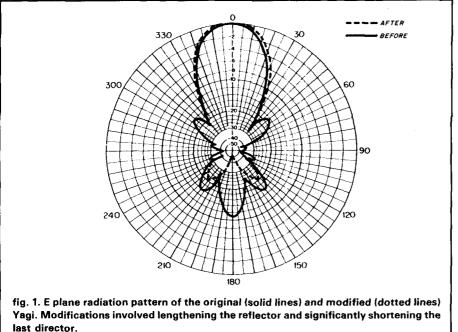I built this antenna and tested it on a commercial antenna range. The gain was as predicted. However, the bandwidth for maximum gain was very nar-



row, only about 1.0 MHz at the -1 dB points, and gain peaked near 146 MHz. Back to the drawing board!

Based on the data taken on the antenna range, I was able to correct my scaling graph. I then scaled the design to 50.1 MHz. It worked like a champ. The lengths and spacings chosen are shown in the first and second columns of **table 1**. A typical antenna radiation pattern is shown in **fig. 1**.

Upon close inspection of the radiation pattern, however, the f/b ratio wasn't worth writing home about. Dave Olean, K1WHS, figured that he could trade gain, if necessary, for a better f/b ratio. He left the element spacings constant, but shortened the last director by almost 10 inches; by lengthening the reflector a few inches. he was able to obtain a nearly infinite f/b ratio, though over only a very narrow bandwidth. The cost was about 1 dB in forward gain. The pattern of the modified Yagi is superimposed on the original design in fig. 1. The final element lengths chosen are shown in column 3 of table 1.

A close inspection of the patterns illustrated in **fig. 1** shows that the sidelobes aren't as good as my original design goals. Also, the improved f/b design had lower gain than desired. With the help of John Kenny, W1RR, a computer optimization was conducted on a similar six-element Yagi design scaled to 2 meters.* The results were similar to those reported in references 5 and 6. Either maximum gain or reasonable f/b ratio *could* be achieved, *but not simultaneously!*

I decided to make another search and again reviewed the Greenblum designs.⁴ Using his designs, I found that eight elements were required for a 1.75-wavelength boom. I quickly calculated a 144-MHz design and W1RR computed the radiation pattern with his program. The gain was right on the money, but as previously speculated, the radiation pattern had very high sidelobes.

Next John ran an optimization routine on my new eight-element design. The input design parameters were maximum gain with all side and rear lobes at least 18 to 20 dB down in the E plane, with the overall boomlength fixed at 1.734 wavelengths (142 inches at 144 MHz).

After many computer iterations, a new design emerged. The pattern looked too good to be true. The gain penalty for a clean radiation pattern was only a few tenths of a dB, not a big compromise for over 13 dBi gain! The bandwidth of the design was also very good — several MHz at the -1dB points.


I hurriedly ran out and built the optimized design using leftover materials from Cushcraft 2-meter beams. Cushcraft uses above-the-boom element mounting, which requires a 0.312-inch element extension when mounted on a 1.0-inch diameter boom. A T match with a 4:1 half-wave balun completed the design. Construction details on the final design are shown in **fig. 2**.

Soon afterwards, the improved design was measured on a commercial antenna test range and was found to be satisfactory. A typical radiation pattern is shown in **fig. 3**. All side and rear lobes were about 20 dB down, and the gain was only 0.75 dB less than the NBS 2.2-wavelength design that used a trigonal reflector. Not bad for a design with a lot less hardware, six fewer elements and a 36-inch shorter boom!

Seven more copies were built along with the necessary phasing lines. They were assembled into a "quick and dirty" 2-meter EME array consisting of a 30-foot irrigation tube for the main boom, four 12-foot vertical masts, and a 12-foot portable tower. The spacing was 8-1/2 feet horizontally and 8 feet vertically. The VSWR of the entire array was fine. A photo of the completed array is shown in **fig. 4**.

The rest is history. On October 17, 1981 — even before making a single QSO — we broke it down and immediately set off for Rhode Island, where we fired it up for the first time on EME. In two nights of activity, we worked 25 stations in 16 states off the moon. Several stations completed a 2-meter WAS; only two stations scheduled were missed, but they turned out to be no-shows. Not bad performance for a small transportable array with only 64 elements!

^{*}Yagi analysis programs for computing gain and patterns of specific Yagi designs are readily available.⁸⁻¹¹ However, the programs used to *optimize* Yagi designs are much more complex and not available for distribution. They're experimental, use proprietary software, and usually require a large mainframe computer. Therefore, I'd urge you *not* to contact persons doing such work until their programs are suitable for distribution.

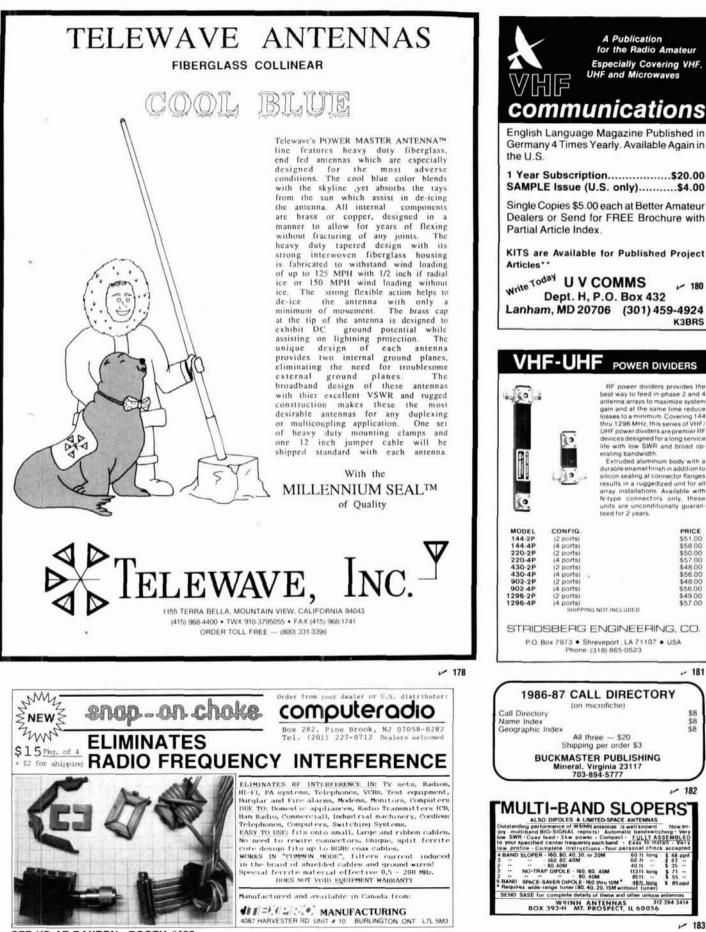

SEE US AT DAYTON BOOTH #430

× 182

ALSO DIPOLES & LIMITED SPAce performance of WBINN principals in well knownt and BIO-SIGNAL reports Automatic bandswitching · Very Coas feed - 3 we power - Compact - FULLY ASSEMILE OF For the Irequincy each band · Early for Initial · Very trequincy each band · Early for Initial · Very Assemble - Your personal check soccepted CA ti long § 48 ppd band - Easy To Instant - y Your personal check acce 60 ft long \$ 48 60 ft - \$ 43 40 ft - \$ 35 M 113 ft long \$ 71 85 ft - \$ 55 \$ 48 ppd \$ 35 \$ 71 \$ 55 \$ 85; SPACE-SAVER DIPOLE - 160 thru 10M * wide range luner (80, 40, 20, 15M wi 46ft. long SE for complete details of these and other unique antennas W91NN ANTENNAS 312 394 3414 BOX 393-H MT. PROSPECT, IL 60056 ✓ 183

A Publication for the Radio Amateur Especially Covering VHF, UHF and Microwaves

Dept. H, P.O. Box 432

10

CONFIG

(2 ports) (4 ports)

(4 ports) (2 ports) (4 ports) (2 ports) (4 ports) (2 ports) (4 ports) (4 ports) (4 ports) (4 ports) (4 ports)

ING NOT INCLUDED

(on microfiche)

All three - \$20

Shipping per order \$3

BUCKMASTER PUBLISHING

Mineral, Virginia 23117 703-894-5777

✓ 180

KIBRS

PRICE

\$51.00

\$58.00 \$50.00 \$57.00 \$48.00 \$56.00 \$48.00 \$56.00 \$49.00 \$57.00

- 181

\$8

\$8

\$8

POWER DIVIDERS

HI power dividers provides the best way to feed in-phase 2 and 4 antenna arrays to maximize system gain and at the same time reduce losses to a minimum. Covering 144 thru 1296 MHz, this series of VHF/ UHF power dividers are premier RF

devices designed for a long service life with low SWR and broad operating bandwidth. Extruded aluminum body with a durable enamel finish in addition to silicon sealing at connector flanges

since searing at connector hanges results in a ruggedized unit for all array installations. Available with Nitype connectors only, these units are unconditionally guaran-teed for 2 years.

dividers provides the

別厚

insulated element mounting

Since the original Yagi was constructed, insulated through-the-boom element mounting has become quite popular.9 Fortunately, the same dimensions as those shown in fig. 2 can be used, since the correction factor for through-the-boom with insulated elements is about the same as the one used in the original design. Just maintain a 1.0-inch diameter boom and 3/16-inch element diameters with insulators and keepers as described in reference 9. However, the driven element length and/or the lengths and spacings of the T match will probably have to be optimized if low (1.2:1 maximum) VSWR is to be maintained.

I've used the eight-Yagi, 2-meter array on EME for several years. WAC was accomplished with less than 600 watts of output in the shack. Several European stations are using this Yagi on tropo and meteor scatter. Several local Amateurs and I have also used it to put rare grids on the air, since it's so compact and uncluttered.

This Yagi design is highly recommended where a small, simple, highgain antenna with excellent sidelobe suppression is preferred. It's easily duplicated and can be used singly or as part of an array. Despite its size, four of these Yagis stacked 8-1/2 feet horizontally and 8 feet vertically make a good beginner's 2-meter EME array. Eight are better for the more serious EMEer, yet still affordable.

A secondary benefit of this 2-meter array hasn't previously been discussed, but may be worth mentioning. Because of space limitations, I can't fit both a 2-meter and a 135-cm (220 MHz) EME array in my back yard at the same time. But fortunately, if you use the 4.2-wavelength NBS Yagi designs on 135 cm, the mechanical spacings used on 2 meters just happen to be the same as the optimum mechanical spacing for 135 cm.3 In my case, when I change bands I just swap out the Yagis, reconnect the same phasing lines, change the power dividers, and presto! For just an hour or so of changeover effort, I'm on 135-cm EME. (A photo of this array on a 1984 expedition to New Hampshire, using the same tower and stacking frame, is shown in reference 10).

6-meter Yagi

Shortly after this 2-meter Yagi design was completed, several Amateurs who needed a high-performance, high-

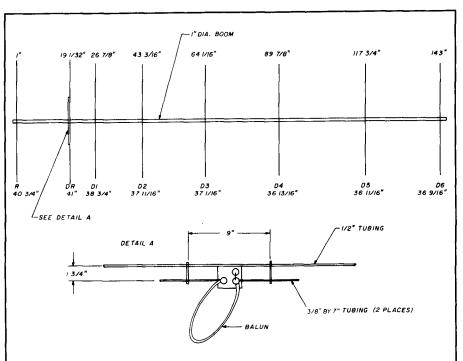


fig. 2. Optimized eight-element, 2-meter Yagi construction details. The reflector and directors are 3/16-inch rod. Element location is referenced from rear of boom to avoid tolerance buildup. A 4:1 half-wave type balun made from RG11 75-ohm coax is used. Overall length of the balun including connectors is 25 inches.

Element	Spacing (inches)	Element length {inches}*	Element length (inches)**
R	59.0	113.75	117.0
DR	68.0	113.0	113.0
D1	95.5	104.75	104.75
D2	75.5	103.88	103.88
D3	100.0	104.25	104.25
D4		103.88	93.88


*Maximum gain model.

Optimized for best f/b ratio. A 2-inch diameter, 33-1/2 foot boom is used. The elements are 3/4-inch diameter, and are attached to the boom with U-bolt mounting as shown in **fig. 5C. A 0.625-inch element lengthening correction is included for this method of boom mounting.

gain 6-meter Yagi with clean radiation patterns — one that would also be usable on EME — approached me. Their requirements seemed to call for a frequency-scaled copy of the 2-meter design. At 6 meters, this would require a boomlength of about 35 feet.

Several mechanical configurations were evaluated. It appeared that a boom diameter of at least 2 inches was in order. "Through-the-boom" element mounting (fig. 5A), either directly in contact with or insulated from the boom, was immediately discarded since it would severely degrade the mechanical strength of the boom. Insulated elements mounted above the boom are advisable, but require special materials (see fig. 5B).

Several commercial element mounting methods were also evaluated. Cushcraft uses large diameter (3/4

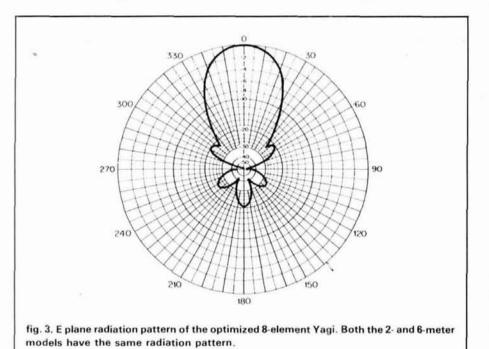

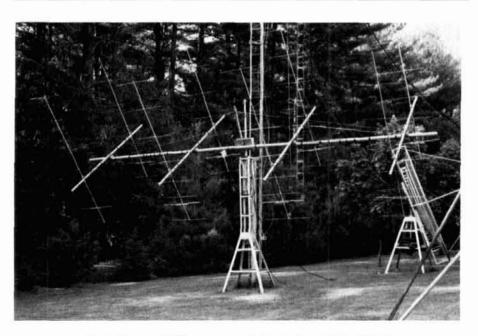


fig. 4. 2-meter EME array uses eight of the optimized Yagis.

inch) elements on its 6-meter "Boomer"™ and places a U-bolt directly through the element with a stiffening half-diameter element above and below the element (**fig. 5C**). Wilson antennas (now out of production) used a different mounting method that doesn't pierce the element (**fig. 5D**). Finally, with the help of Don Cook, K1DPP, a homebrew nonpiercing above-the-boom mounting was also fabricated (**fig. 5E**.)

The final element mounting scheme chosen was that shown in **fig. 5D**, since many of the older Wilson eightelement antennas are still available and easily modified for the new design. However, any of the above-the-boom mounting schemes shown will work satisfactorily. If you don't have an old Wilson beam to modify, I recommend the element mounting scheme shown in **fig. 5E**. More on this shortly.

Based on the use of an obsolete Wilson eight-element Yagi, the 2-meter design was scaled to 50.1 MHz. This design uses a 4-foot section of 5/8-inch diameter tubing for the inner portion of the elements and 1/2inch diameter tubing for the outer portion of the elements. Construction details are shown in **fig. 6**.

Several 6-meter Amateurs have used this design. Each has used a slightly different set of tubing for the driven element matching, so the sizes shown for the driven element matching assembly may need some final adjustment. Either the length of the driven element and/or the length and spacing of the matching section may have to be changed slightly to suit your individual design.

If you build your own from scratch, the element mounting schemes shown in figs. 5C, D or E are recommended. The elements used may be either 1/2-, 5/8-, or 3/4-inch diameter tubing, or you can use graduated tubing as shown in fig. 6, since the difference in tuning is negligible (less than 100 kHz). If you use insulated mounted elements as shown in fig. 5B, each of the elements should be shortened approximately by 5/8 inch.

If you're building from scratch, I

recommend the use of a 30-foot length of irrigation pipe measuring 2 inches in diameter. This is available in farming supply stores. To obtain the required 35-1/2 foot length, a 1-7/8 inch outside diameter tube can be telescoped into the end of the tubing near the last director. Suitable tubing can be obtained from WD4BUM.**

Any boom this length and size should be supported from above. Two suggested methods are shown in **fig. 7**. This beam is large and has a high wind load, so any short cuts can turn into an expensive disaster.

If you decide to build your own, use the element mounting method shown in **fig. 5E.** A 2-inch wide aluminum channel measuring 1/2 inch thick and 5 to 6 inches long is recommended. It's easy to file out a semicircular groove in the channel to match the boom curvature. Don't file too deeply; the strength of the channel will be diminished if you go all the way down to the base plate.

The elements are held to the channel with short pieces of aluminum straps approximately 1/2 inch wide, 1/16 inch thick, and 2-1/2 inches long. These straps are held in place with stainless steel screws, nuts, and washers. For best element alignment, each channel should be attached to the boom using two U-bolts. Suitable stainless steel U-bolts can be purchased from suppliers such as WB9IPG*** or homebrewed.

At the suggestion of K1DPP, I made my own U-bolts using 3/16-inch diameter stainless steel welding rods available from a local welding supply house. All that was required was a 10-32 die, a die handle, and some patience. If you'd like to try this, First de-burr the edges of the rod and then cut the required length of threads on both ends. Next, place a 2-inch diameter tube upright in a bench vise. Place about a 6-inch piece of suitable diameter tubing over each threaded end of the rod. Then carefully bend the

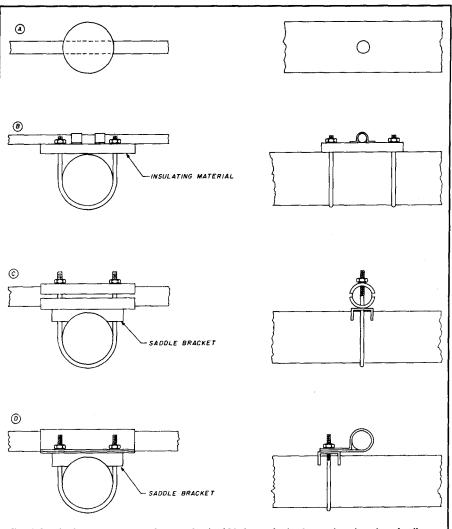


fig. 5. Typical element mounting methods: (A) through-the-boom insulated, or in direct contact with the boom; (B) insulated above the boom; (C) element held in contact with the boom by a U bolt; (D) element held by special bracket. (Because of last-minute production problems, fig. 5E will appear next month. — Ed.)

rod around the 2-inch diameter tube until the desired U-shape is obtained.

6-meter results

The performance of the 6-meter Yagi design has been gratifying to all who built one. Some Amateurs used it in contests to set high scores. Compared with most other designs, the pattern is very clean, and the gain definitely matches or exceeds that of any other 6-meter Yagi designs, even those with more elements or longer boomlengths.


Ray, WA4NJP, who's been active on 6 meters for many years and has used several different Yagi designs, recently built a large array for 6-meter EME. After finding his results only marginal, he asked for my recommendation.

I gave him the details shown in **fig. 6**, and he built four of the 6-meter Yagis, stacking them 28-1/2 feet in the E plane and 24 feet in the H plane. He started hearing EME echoes on 50 MHz immediately. Recent tests have yielded EME echoes regardless of where the moon is in the sky; previously, he could use the moon only when it was at low elevations to obtain horizon gain. Echoes more than 10 dB above the noise are now quite common off the moon — even on SSB!

^{**}George Shira, WD4BUM, Route 7, Box 258, Anderson, South Carolina 29624.

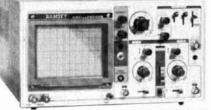^{***}H. C. Van Valzah Company (WB9IPG), 1140 Hickory Trail, Downers Grove, Illinois 60515.





\$369.95* INCLUDES 2 HOOK-ON PROBES **20 MHz DUAL TRACE**

Features component testing circuit for resistors, capacitors, digital circuits and diodes—TV sync filter—high sensitivity-Zaxis-XY mode-built-in calibrator-5X horizontal magnifier

0 -10

\$499.95* **INCLUDES 2 HOOK-ON PROBES** 35 MHz DUAL TRACE

wide frequency bandwidth—optimal sensitivity —delayed triggering sweep—hold off—ALT trigger—single sweep TV sync 5X magnification—XY or XYZ operation— HF/LF noise reduction

CT-90 9 DIGIT 600 MHz



NEW \$449.95 **INCLUDES 2 HOOK-ON PROBES 15 MHz DUAL TRACE PORTABLE**

Field/bench applications—built-in charger and battery pack —up to 2 hours operation per charge—5X horizontal magnification—high brightness CRT—front panel trace rotator

MAXIMUM

RAMS	FYO	SCIL	OSC	DPES
17:11/E	LIU	JUILI	-000	

All Ramsey oscilloscopes feature unsurpassed quality at an unbeatable price. Of heavy duty construction, they are suitable for hobby, service and production applications

	MODEL	BARD WIDTH	IT INAGES	GHI OILL	achaitivitti	Thisrney	DANOTIDIT
T	2200	20 MHz	(2)	8x10CM	5 mV per div	35 MHz	30 MHz
T	2500	15 MHz	(2)	3.5 inch	2 mV per div	30 MHz	25 MHz
t	3500 -	35 MHz	(2)	8x10CM	1 mV per div	50 MHz	60 MHz

*Add an additional \$10.00 for each unit for shipping. **MINI-100 COUNTER CT-707 DIGIT 525 MHz**



FREQ RANGE

1-500 MHz

20 Hz-550 MHz

10 Hz-600 MHz

5 Hz-600 MHz

10 Hz-1.25 GHz

10 Hz-600 MHz

DIGITAL

\$2495

test leads and

battery inclu



1 PP1

1 PPN

1 PPM

0.1 PPI

10mv To 150 MHz 150mv To 600 MHz

LESS THAN 25 my

25mv @ 50 MHz 15mv @ 500 MHz

< 100 my @ 800 MHz

< 10mv To 150 MHz < 150mv To 600 MHz

ACY	DIGITS	RESOLUTION	PRICE
1	7	100 Hz, 1 KHz	119.95
1	7	1Hz, 10Hz, 100Hz	139.95
1	9	0.1Hz, 1Hz, 10Hz	169.95
1	8	1Hz, 10Hz	189.95
4	9	0.1Hz, 1Hz, 10Hz	189.95
м	9	0.1Hz, 1Hz, 10Hz	229.90

RAMSEY D-5100

AUTORANGING

\$49.95

Includes Probes 1 Year Warranty

METER

\$169.95 WIRED INCLUDES



\$189.95 WIRED INCLUDES

08168 DOCTOR DOCTOR

CT-125 9 DIGIT 1.2 GHz

USFARIE MAXIMU

\$189.95 WIRED INCLUDES

RAMSEY FREQUENCY COUNTERS

VERTICAL

Ramsey Electronics has been manufacturing electronic test gear for over 10 years and is recognized for lab quality products at breakthrough prices. Our frequency counters have features and capabilities of counters costing twice as much. BP-4 Nicad battery pack for CT-70, - 184 CT-90 and CT-125 Frequency Counters. \$8.95.



MODE

MINI-100

CT-70

CT-90

CT.50

CT-125

CT-90 WITH OV-1 OPTION

Compact sized reliability and accuracy. This LCD digital multitester easily fits in your pocket, you can take it anywhere. It features full overload protection • 3% digit LCD readout . recessed input jacks safety probes

 diode check function

· 2000 hours battery life

Tilt bail, for CT-70, 90, 125.



3.95

Has TOUCH-HOLD feature to allow readings to be logged or referred to before making the next reading. Up to 10 AMP current capability and a continuity function which beeps on zero Ohms.





\$8995

wired includes AC adapter

\$4495 The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for sniffing RF • ideal wired includes AC adapter

receiver/TV preamp PR-2 kit \$39.95

PR-2 COUNTER PREAMP


PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies Up in frequency • great for PL tone measurements • multiples by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner

PS-10B1 GHz PRESCALER

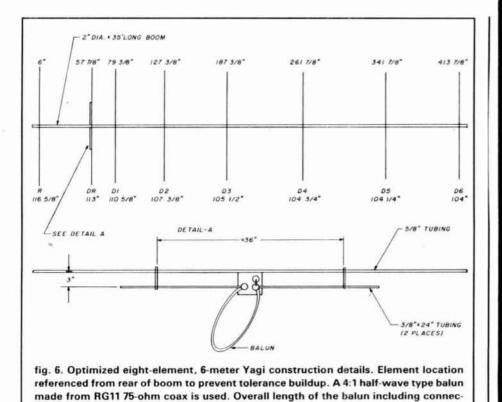Extends the range of your present counter to 1 GHz • 2 stage preamp • divide by 1000 cir-cuitry • super sensitive (50 mV typical) • BNC connectors • 1 GHz in, 1 MHz out • drives any counter





tors is 78 inches. Coax can be coiled up in a 6- to 9-inch diameter and taped to boom.

summary

Since these Yagis were originally designed, additional data has indicated that optimum boomlengths exist for Yagi antennas, especially those shorter than 4 wavelengths.1 The optimum boomlength for short Yagi designs seems to be an odd multiple of guarterwavelengths (i.e., 0.25, 0.75, 1.25, and 1.75 wavelengths). If these boomlengths are used with the proper number of elements, optimum gain and pattern can often occur simultaneously. According to my analysis, the optimum number of elements for any specific boomlength seems to follow those recommended by Greenblum.⁴ Furthermore, the use of a T match with a built-in 4:1 half-wave type balun, as shown in figs. 2 and 6, is strongly suggested.

This month's column was primarily aimed at the design of shorter boomlength Yagis. Emphasis was on performance, with high gain-per-unit boomlengths and clean radiation patterns. Several designs for 2 and 6 meters that meet the criteria specified above were discussed. These designs should be just the ticket for those who want high performance with an antenna they can modify or build for themselves.

acknowledgements

Any project this size requires plenty of help. I'd especially like to thank John Kenny, W1RR, for his work on optimizing the designs. Thanks also to Dave Olean, K1WHS, for his assistance with measurements and the optimization of the f/b ratio on the six-element 6-meter design. Stan Jaffin, WB3BGU, has been particularly helpful in analyzing my results and comparing notes on this and other designs. Thanks also go to Don Cook, K1DPP, for his help with the 6-meter antenna mounting brackets and hardware. Finally, thanks to Ray Rector, WA4NJP, for trusting my designs enough to build his large 6-meter EME array that works so well. I hope I didn't forget anyone!

new records

In last month's column I predicted

B & W PRESENTS A WINNING COMBINATION



MODEL PT2500A LINEAR AMPLIFIER

The Barker & Williamson PT2500A Linear Amplifier is a completely self-contained table-top unit designed for continuous SSB, CW, RTY, AM or ATV operation. Intended for coverage of all amateur bands between 1.8 MHz and 21 MHz, it can be readily modified for frequencies outside the amateur bands for commercial or military application. Two type 3-5002 glass envelope triodes provide reliability and rapid turn-on time.

FEATURES INCLUDE:

- Full 1500 watt output
- PI-network input for maximum drive
- Pressurized plenum cooling system
- DC antenna relay for hum-free operation
- Illuminated SWR and power meters
 Vernier tuning for accurate settings
- PI-L output for greater harmonic attenuation

Ruggedly constructed of proven design, this amplifier reflects the manufacturer's critical attention to details- such as the silver-plated tank coil for maximum efficiency. Cathode zener fuse and internal/external cooling are among the protective and safety devices employed. Input and output impedances are 50 ohms.

Dimensions: 17" wide x 19" deep x 8"1/2 high Weight: 80 lbs. (shipped in 3 cartons to meet UPS requirements)

Price: \$2175.00 FOB factory. Price

includes one year limited warranty. Call or write factory for complete specifications.



MODEL VS1500A ANTENNA COUPLER

The Barker & Williamson VS1500A antenna coupler is designed to match virtually any receiver, transmitter or transceiver in the 160 to 10 meter range (1.8 to 30 MHz) with up to 1500 watts RF power to almost any antenna, including dipoles, inverted vees, verticals, mobile whips, beams, random wires and others, fed by coax cable, balanced lines or a single wire. A 1:4 balun is built in for connection to balanced lines.

FEATURES INCLUDE:

- Series parallel capacitor connection
- for greater harmonic attenuation. In-circuit wattmeter for continuous
- monitoring
- Vernier tuning for easy adjustment.

Front panel switching allows rapid selection of antennas, or to an external dummy load, or permits bypassing the tuner.

Dimension (Approx.): 11" wide x 13" deep x 6" high

Weight: 6½ lbs.

Price: \$499.00 FOB Factory. Fully warranted for one year.





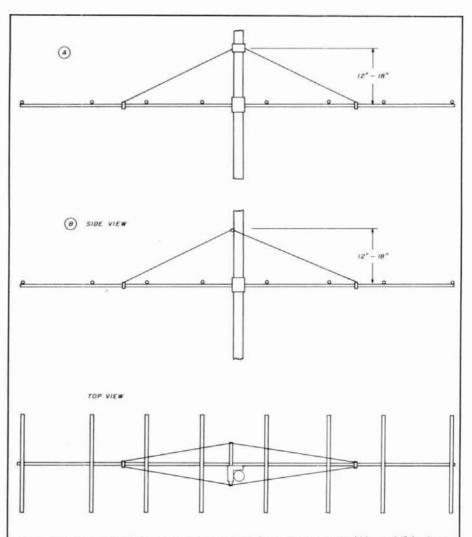


fig. 7. Recommended boom mounting method for extra strength: (A) use 1/2-inch or larger diameter tubing approximately 10 feet long mounted about 18 inches above the boom at the center. Flatten tubing ends and attach to mast and boom with U bolts. (B) Use Phillystran[™] or equivalent cable mounted as shown to prevent swaying (side and top views).

that before the April issue was printed, the 33-cm (903 MHz) record would again be broken.¹² On Christmas Eve, 1986, another unexpected Midwest tropo opening occurred; this time, Sam, W2PGC (FN02OR), completed a two-way QSO with Gary, K3SIW/9 (EN52WA), for a record-shattering distance of 478 miles (769 km). Both stations were using modest setups, 10 and 70 watts, respectively, and singleloop Yagi antennas. Signals were S9 each way, and the contact was completed on two-way SSB. Congratulations to Sam and Gary.

East Coast VHF Society

One of the first of its kind, the East Coast VHF Society is now being reactivated by president Russ Pillsbury, K2TXB, vice-president Roger Amidon, K2SMN, secretary Allen Katz, K2UYH, and treasurer Tom Kirk, KA2VAD. There are plans for a newsletter and an annual flea market, as well as antenna and noise figure measuring contests in July. Equipment loan and activity to various rare grids are also planned. Contact K2UYH for further information.

MININEC 3 is available

From time to time I've mentioned computer-aided antenna modeling programs. Till now, these computer programs were either difficult to obtain, not generally available, or suitable only for mainframe or other large computers.

All that has changed. MININEC 3 is now available for general distribution for use on IBM and IBM-compatible personal computer systems. This program is faster than its predecessor and has more available options. To obtain your copy, send an MS DOS-formatted, double-sided, double-density disk with sufficient return postage and a note requesting a copy of MININEC 3 to Jim Logan, Code 822, Naval Ocean Systems Center, 271 Catalina Boulevard, San Diego, California 95152-5000.

important VHF/UHF events

May 2-3	West Coast VHF Conference (contact WB6GFJ)
May 5	Predicted peak of the Eta Aguarids
indy o	meteor shower at 1300 UTC
May 8	ARRL 902-MHz Spring Sprint Contest (Friday evening)
May 9	2304 EME special by WA2WEB (con- tact K2UYH for skeds)
May 14	ARRL 1296-MHz Spring Sprint Con- test (Thursday evening)
May 15	EME perigee
May 15-17	13th Annual Eastern VHF/UHF Con-
	ference, Nashua, New Hampshire
	(contact W1EJ)
May 23-24	ARRL 50-MHz Spring Sprint Contest (Saturday evening)
June 7	Predicted peak of the daytime
	Arietids meteor shower at 1900 UTC
June 10	Predicted peak of the Zeta Perseids meteor shower at 0400 UTC
June 13	EME perigee
June 13-15	ARRL June VHF QSO Party
June 20-21	SMIRK 6-Meter QSO Party Contest
	(contact KA0NNO)
June 21	±1 month. Peak of Sporadic E propagation
	propagation

references

 Joe Reisert, W1JR, "VHF/UHF World: Yagi Facts and Fallacies," *ham radio*, May, 1986, page 103.
 Joseph H. Reisert, Jr., W6FZJ/1, "VHF Antenna Arrays for High Performance," *OST*, December, 1974, page 38.

 Joseph H. Reisert, Jr., W1JR, "How to Design Yagi Antennas," *ham radio*, August, 1977, page 22.
 Carl Greenblum, "Notes on the Development of Yagi

Arrays," *QST*, August, 1956, page 11.

 David K. Cheng and C. A. Chen, "Optimum Element Spacings for Yagi-Uda Arrays," *IEEE Transactions on Antennas and Propagation*, September, 1973, page 615.


6. C. A. Chen and David K. Cheng, "Optimum Element Lengths for Yagi-Uda Arrays," *IEEE Transactions on Antennas and Propagation, January, 1975, page 6.* 7. I. Larry Morris, "Optimization of the Yagi Array, 1," PhD Thesis, Harvard University, October, 1964.

8. James L. Lawson, W2PV, "Yagi Antenna Design: Performance Calculations," ham radio, January, 1980, page 22.

9. Joe Reisert, W1JR, "VHF/UHF World: A High-Gain 70-CM Yagi," *ham radio*, December, 1986, page 75. 10. Joe Reisert, W1JR, "VHF/UHF World: 220-MHz EME Requirements," *ham radio*, September, 1984, page 45.

11. Stanley Jaffin, WB3BGU, "Applied Yagi Antenna Design," Part 6, *ham radio*, October, 1984, page 89. 12. Joe Reisert, W1JR, "VHF/UHF World: 33-CM Update," *ham radio*, April, 1987 page 00.

ham radio

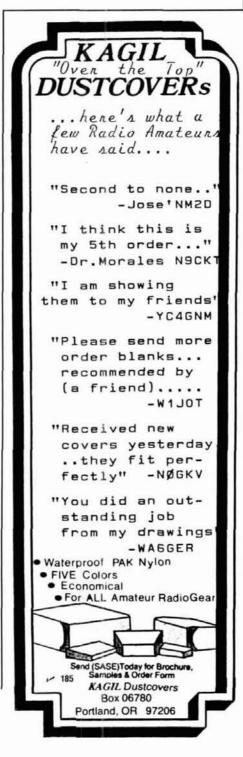


Step up

to the world's mostadvanced antenna system!

WITH NOT A SINGLE WATT WASTED IN LOSSY TRAPS! (There aren't any!)

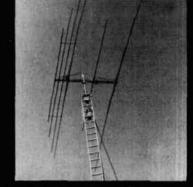Hams in over 50 DXCC countries have done so already!



The DJ2UT-Multiband-Systems offer:

- Maximum gain plus F/B ratio with low VSWR across each band
- 2 kW CW output power
- 10/15/20/(30) 40-meter bands with up to 7 band coverage incl. WARC bands with self-supporting "TWIN-BOOM" and boomlegths from 8 to 20 ft
- Air-core teflon dielectric coaxbalun and stainless-steel hardware at no extra cost
- traditional Blackforest craftsmanship

The DJ2UT-MULTIBANDERS provide the superior full-size monoband-beam performance required during the present sunspot minimum.

For further information contact:



H.J. Theiler Corp. P.O. Box 5369 Spartanburg, SC 29304 (803) 576-5566 or our distributor in Canada: Dollard's Radio West P.O. Box 58236 762 S.W. Marine Drive Vancouver, B.C. V6P 6E3

Selected dealerships available.





2345 LY 45el loop Yagi 1296 MHz 20dBi \$93 1345 LY 45el loop Yagi 2304 MHz 20dBi \$80 3333 LY 33el loop Yagi 902 MHz 18.5dBi \$93 Above antennas assembled and tested. Kits available. All Aluminum and Stainless Construction. Add \$8 UPS SiH, \$11 West of the Mississippi. 2316 PA Linear Amp 1W in 18W out 1296 MHz 13.5V. \$245 ppd. 2335 PA Linear Amp 10W in 35W out 1296 MHz 12.5V. \$295 ppd. **NEW! MICROWAVE TRANSVERTERS** BY LMW ELECTRONICS 1296TRV6D 6W, GaAsFET, T/R Sequencer, Output Meter \$489 2304TRV2D 2W, GaAsFET, T/R Sequencer, Output Meter \$589 Add \$6 for shipping UPS/48 Stripped down version, kits also available Write For FREE Catalog VISA DOWN EAST MICROWAVE 6 Bill Olson, W3HQT Box 1655A RFD #1, Burnham, ME 04922 U.S.A. (207) 948-3741 192

DOPPLER SYSTEMS, INC. P.O. Box 31819

Phoenix, AZ 85046

(602) 488-9755

HF Equipment IC-735 HF transceiver/SW rcvr/mic † PS-55 External power supply AT-150 Automatic antenna tuner FL-32 500 Hz CW filter EX-243 Electronic keyer unit UT-30 Tone encoder	199.00 179 ⁹⁵
50 - () 500 50 - 500	
IC-745 9-band xcvr w/.1-30 MHz rcvr PS-35 Internal power supply EX-241 Marker unit EX-242 FM unit EX-243 Electronic keyer unit FL-45 500 Hz CW filter (1st IF) FL-54 270 Hz CW filter (1st IF) FL-52A 500 Hz CW filter (2nd IF) FL-53A 250 Hz CW filter (2nd IF) FL-44A SSB filter (2nd IF)	199.00 179 ⁵⁵ 22.50 44.00 56.00 66.50 53.00 108.00 99 ⁵⁵ 108.00 99 ⁵⁵
IC-751A 9-band xcvr/.1-30 MHz rcvr PS-35 Internal power supply FL-32 500 Hz CW filter (1st IF)	1649.00 1399 199.00 179 ⁹⁵ 66.50
FL-63 250 Hz CW filter (1st IF) FL-52A 500 Hz CW filter (2nd IF) FL-53A 250 Hz CW filter (2nd IF) FL-53A Mf filter FL FL-70 2.8 kHz wide SSB filter FL RC-10 External frequency controller	108.00 99 ^{%5} 35.25 52.00 39.25
Other Accessories: IC-2KL 160-15m solid state amp w/ps PS-15 20A external power supply PS-30 Systems p/s w/cord, 6-pin plug OPC Opt. cord, specify 2, 4 or 6-pin MB Mobile mount, 735/745/751A	Regular SALE 1999.00 1699 169.00 154 ³⁵ 299.00 269 ³⁵ 10.00 24.50 61.00
SP-3 External speaker SP-7 Small external speaker CR-64 High stab. ref. xtal (745/751) PP-1 Speaker/patch SM-6 Desk microphone	49.00 63.00 159.25 149 ⁹⁵ 44.95
SM-8 Desk mic - two cables, Scan SM-10 Compressor/graph EQ, 8 pin mic AT-100 100W 8-band auto antenna tuner AT-500 500W 9-band auto antenna tuner AH-2 8-band tuner w/mount & whip	78.50 136.25 124 ³⁵ 445.00 389 ³⁵ 559.00 489 ³⁵ 625.00 549 ³⁵
AH-2A Antenna tuner system, only	495.00 429 ³⁵

ICOM
Other Accessories - continued: Regular SALE GC-5 World clock
6-meter VHF Portable Regular SALE IC-505 3/10W 6m SSB/CW portable 549.00 489% EX-248 FM unit 55.50 55.50 39.50
VHF/UHF base multi-modes Regular SALE IC-551D 80W 6-meter SSB/CW 799.00 719*5 EX-106 FM option 140.00 126*5 BC-10A Memory back-up 9.50 IC-271A* 25W 2 meters CLOSEOUT 859.00 699*5 AG-20* Internal preamplifier 64.00 10 10.271H 100W 2m FM/SSB/CW 1099.00 969*5 AG-25 Mast mounted preamplifier 95.00 10.275A 25W 2m FM/SSB/CW w/ss 1199.00 1049
IC-471A [*] 25W 430-450 CLOSEOUT 979.00 769 ³⁵ AG-1 [*] Mast mounted preamplifier 99.50 IC-471H [*] 75W 430-450 CLOSEOUT 1399.00 999 ³⁵ AG-35 [*] Mast mounted preamplifier 95.00
*Preamp \$995 with 271A/471A/471H Purchase
Accessories common to 271A/H and 471A/H PS-25 Internal power supply for (A) 115.00 104 ⁹⁵ PS-35 Internal power supply for (H) 199.00 179 ⁹⁵ SM-6 Desk microphone
VHF/UHF mobile multi-modes Regular SALE IC-290H 25W 2m SSB/FM, TTP mic 639.00 569% IC-490A 10W 430-440 SSB/FM/CW 699.00 599%
VHF/UHF/1.2 GHz FM Regular SALE IC-27A Compact 25W 2m FM w/TIP mic 429.00 369% 10.27H 20.00 369% 10.27H 20.00 329% 10.27H 20.00 129% 10.00
IC-28A 25W 2m FM, TTP mic 459.00 399 ³⁵ IC-28H 45W 2m FM, TTP mic 489.00 429 ³⁵ IC-38A 25W 20 FM, TTP mic 489.00 429 ³⁵ IC-48A 25W 440-450 FM, TTP mic 489.00 429 ³⁵ IC-48A 25W 440-450 FM, TTP mic 55.50 55.50 UT-28 Digital code squelch 37.50 37.50 UT-29 Tone squelch decoder 43.00 43.00
HM-16 Speaker/microphone 34.00 IC-3200A 25W 2m/440 FM w/TTP 599.00 529 ³⁵ UT-23 Voice synthesizer 34.99 AH-32 2m/440 Dual Band antenna 37.00
AHB-32 Trunk-lip mount 34.00 Larsen PO-K Roof mount 20.00 Larsen PO-TLM Trunk-lip mount 20.18 Larsen PO-MM Magnetic mount 19.63 RP-3010 440 MHz, 10W FM, xtal cont. 1229.00 1089 IC-120 1W 1.2 GHz FM Mobile 579.00 399*5 IC-1271A 10W 1.2 GHz SB/CW Base 1229.00 1069 AG-1200 Mast mounted preamplifier 105.00 PS-25 Internal power supply 115.00 104*5
EX-310 Voice synthesizer





More Details? CHECK-OFF Page 130

THRULINE WATTMETER

0.45-2300 MHz 0.1-10,000 watts

Ask for model 43 Bulletin

BIRD Electronic Corporation 30303 Aurora Rd., Cleveland (Solon), Ohio 44139 216-248-1200 TLX: 98-5298 Cable: BIRDELEC



1986 propagation review

Now that most of the geophysical and propagation data for 1986 is in and has been analyzed, let's review the significant events so you can compare them with your DX operating log.

There were only four major geomagnetic-ionospheric disturbances (i.e., those with a geomagnetic A index greater than 40) during the year and eight large ones (i.e., those with an A index greater than 30). Surprisingly, April was the quietest month. The four major disturbances occurred in February, May, September, and November; with the exception of the September disturbance, these occurred as the 27-day solar flux cycle was decreasing. The February event (from February 5 to February 10) was so extraordinary that it warranted special coverage in the July, 1986, column.

The next major solar event, which occurred from May 1 through May 4, included a geomagnetic-ionospheric disturbance (to K7) at 1200 UT on May 2. On May 3, an old-cycle solar flare at 2017 UT (with signal attenuation in the United States and in the Pacific area) produced protons at the polar regions at 1255 UT on the following day, with the next geomagnetic-ionospheric disturbance (to K6) about 2100 UT on May 5. A decrease of as much as 22 percent in mid-latitude maximum usable frequencies (MUF) occurred on east-west paths, which included QSB.

On September 11 at 1837 UTC, the next major event occurred during a period of relatively constant solar flux. Possibly attributable to a small newcycle flare, it produced a sudden-commencement geomagnetic-ionospheric disturbance. As a result of a favorable sun-earth equatorial alignment, an A of 49 and a K of 7 were registered, with an aurora visible as far south as Albuquerque, New Mexico, and Columbia, Missouri. MUFs decreased 25 percent on September 12, with considerable fading and weak signals occurring on east-west paths. There must have been good transequatorial openings to southern areas on this one, but I didn't hear of them.

The last of the four events took place in early November, as the solar flux decreased from its October 23 peak. The driving forces for this event were probably several small old-cycle flares and numerous solar flux bursts. the largest of which occurred on October 31 at 2249 UT. A sudden-commencement geomagnetic-ionospheric disturbance (to K6) started on the November 3 at 2354 UT and ended at 1500 UT on the 5th. A decrease of 20 percent in the MUF during the early part of the 4th was experienced on east-west paths to Europe from this short disturbance. This MUF decrease is related to equatorward extension of the lower F laver electron density of the auroral Atlantic trough situated between 60 to 70 degrees north latitude. Signal levels on the normal great circle paths are lower and QSB is experienced. However, perhaps other less common paths were useful and resulted in some interesting DX in your log.

new forecasting tool --via computer BBS

In October 1978 the Institute for Telecommunication Science of the Department of Commerce in Boulder, Colorado, stopped providing radio propagation quality information to the public via mailed weekly bulletins and WWV broadcasts of "N7's" at 14 minutes after the hour. These were replaced with solar flux and geomagnetic A and K data included with the geophysical alert announcements at 18 minutes after the hour. With the help of articles by Ted Cohen, N3AT, George Jacobs, W3ASK, and others of us, hams became their own fore-casters.

Now the Space Environment Services Center (SESC) in Boulder has resumed radio quality reporting with an expanded, worldwide version of the "N7" report/forecast system. They've divided the northern hemisphere into a grid of four longitude quadrants, 0 to 90 and 180 degrees east and west, and five latitude zones, 0-10-30-55-70-90 degrees north. A two-digit code (such as N7) appears in each grid space. The letter (W, U, or N) represents conditions for the current 6-hour period; the number (1 through 9) indicates the forecast for the next 6-hour period. The primary forecast is at 0600 UT daily with 6-hour updates.

You can use your computer terminal to obtain these forecasts from SESC's "bulletin board" service. Call (303) 497-5000 with the usual 300/ 1200-baud, 8-bit (1 stop bit, no priority) conventional protocol of bulletin board systems. An simple menu will allow copying data for up to 5 minutes. Registration (entering your name and intended use) will give you a user number and extend available data-copying time to 15 minutes. User acceptance of the experimental service will assure permanence and menu expansion.

last-minute forecast

The higher frequency bands, 10 through 30 meters, are expected to be favorable for DX openings the first and last weeks of the month, when the possibility of higher solar flux is greatest. Short-skip sporadic-E openings are also possible during the last week or so. On the lower bands, the middle weeks should be best, with higher daytime and nighttime signal strengths. Atmospheric noise (thunderstorms) may be building up generally now, but not significantly — so enjoy these bands while you can.

Of interest to moonbounce DXers, the lunar perigee occurs on the 15th with a full moon occurring on the 13th. The Aquarid meteor shower, of interest to meteor-burst DXers, peaks be-

MADISON SPRING FLING

New rigs and old favorites, plus the best essential accessories for the amateur.

3621 FANNIN ST HOUSTON, TX 77004-3913 CALL FOR ORDERS 1-713-520-7300 OR 1-713-520-0550 TEXAS ORDERS CALL COLLECT

ULECT

ALL ITEMS ARE GUARANTEED OR SALES PRICE REFUNDED

EQUIPMENT

Kenwood TH205AT Trade in your old H1 Kenwood TS 440 Call for trade Icom T7000 25-2000 MHz	EQUIPMENT	
Icom I(C735 849.00 Fen.Tec 2510 (Easy OSCAR) 439.00 KDK FM 240 NT 279.00 Mirağe Amps 15%0 OFF Tokyo Hy-Power HL 1K AMP, no 4CX250B 699.00 New Kenwood TM-221A, 45W, mobile Cal VJ Amplifier, VHF, built in England, 1 in-100 out 3-100, 5-100 (ea.) 269.00 25 in-160 out 219.00 229.00 229.00 ALI models include preamp 10.01 319.00 Lunar 2M4-40P 109.00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Stock Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (tor the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soon Astatic SilverEagle & Base 66.00 Cen-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/th 9237 RG8 39c/th 824 RG8 Foam 45c/th 8258 RG62A/U 16a 6a 18 Ga	Kenwood TH205AT	Trade in your old HT
Icom I(C735 849.00 Fen.Tec 2510 (Easy OSCAR) 439.00 KDK FM 240 NT 279.00 Mirağe Amps 15%0 OFF Tokyo Hy-Power HL 1K AMP, no 4CX250B 699.00 New Kenwood TM-221A, 45W, mobile Cal VJ Amplifier, VHF, built in England, 1 in-100 out 3-100, 5-100 (ea.) 269.00 25 in-160 out 219.00 229.00 229.00 ALI models include preamp 10.01 319.00 Lunar 2M4-40P 109.00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Stock Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (tor the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soon Astatic SilverEagle & Base 66.00 Cen-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/th 9237 RG8 39c/th 824 RG8 Foam 45c/th 8258 RG62A/U 16a 6a 18 Ga	Kenwood TS 440	Call for trade
KDK FM 240 NT 279.00 Mirağe Amps. 15% OFF Tokyo Hy Power HL 1K AMP, no 4CX250B 699.00 New Kenwood TM 221A, 45W, mobile Cal VJ Amplifier, VHF, built in England, 1 in-100 out, 29.00 25 in +160 out. 219.00 All models include preamp 109.00 Lunar 2M4-40P 109.00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (tor the big boys!) 529.00 Soorn Soorn New Tokyo HC 200A 115.00 Astatic SilverEagle & Base 66.00 Cen-Tec Nobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51cH 8237 RG8 39cH 8248 Ronductor rotor cable 33cH 8267 RG213 S	Icom R7000 25-2000 MHz	
KDK FM 240 NT 279.00 Mirağe Amps. 15% OFF Tokyo Hy Power HL 1K AMP, no 4CX250B 699.00 New Kenwood TM 221A, 45W, mobile Cal VJ Amplifier, VHF, built in England, 1 in-100 out, 29.00 25 in +160 out. 219.00 All models include preamp 109.00 Lunar 2M4-40P 109.00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (tor the big boys!) 529.00 Soorn Soorn New Tokyo HC 200A 115.00 Astatic SilverEagle & Base 66.00 Cen-Tec Nobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51cH 8237 RG8 39cH 8248 Ronductor rotor cable 33cH 8267 RG213 S	Icom IC735	
Miraĝe Amps 15%0 OFF Tokyo Hy-Power HL 1K AMP, no 4CX250B 699 00 New Kenwood TM-221A, 45W, mobile Cal VJ Amplifier, VHF, built in England, 1 in-100 out, 3-100, 5-100 3-100, 5-100 (ea) 269 00 25 in-160 out. 319,00 All models include preamp 109,00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89,95 Heil HC4/HC5 Stock Heil BN 00 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189,00 Daiwa NS660A 30/300/30000 watts 135,00 Alinco ELH 230D- Excellent buy 88,00 Nye MB5-A (tor the big boys) 529,00 Shure 444D 54,95 Ameco PT-3 Soor New Tokyo HC 200A 115,00 Net-Tech Labs Digital Voice Keyer DVK 100,335,00 345atic SilverEagle & Base 66 00 Ten-Tec Mobile Switch 30001 17,00 BELDEN 9913 low loss, solid center, foil/braid shield 51cfft 8267 RG213 Socitt 33cfft 8267 RG213 Socitt 33cfft <t< td=""><td>Ten-Tec 2510 (Easy OSCAR)</td><td>439.00</td></t<>	Ten-Tec 2510 (Easy OSCAR)	439.00
New Kenwood TM-221A, 45W, mobile Cal VJ Amplifier, VHF, built in England, 1 in-100 out, 3-100, 5-100 (ea.) 269 00 25 in-160 out. 219 00 229 00 25 in-160 out. 319 00 All models include preamp Lunar 2M4-40P 109 00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HCA/HCS Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189 00 Daiwa NS660A 30/300/3000 watts 135 00 Daiwa NS660A 30/300/3000 watts 135 00 New Tokyo HC 200A 115 00 Net-Tech Labs Digital Voice Keyer DVK 100 335 00 Astatic SilverEagle & Base 66 00 Ten-Tec Mobile Switch 30001 17:00 BELDEN 9913 low loss, solid center, foil/braid shield 51c/h 8267 RG213 Socht 827 RG8 39c/h 8267 RG213 Socht 8268 RG8x 20c/h 8267 RG213 Socht 8268 RG8x 20c/h 8268 RG8x 20c/h	KDK FM 240 NT	
New Kenwood TM-221A, 45W, mobile Cal VJ Amplifier, VHF, built in England, 1 in-100 out, 3-100, 5-100 (ea.) 269 00 25 in-160 out. 219 00 229 00 25 in-160 out. 319 00 All models include preamp Lunar 2M4-40P 109 00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HCA/HCS Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189 00 Daiwa NS660A 30/300/3000 watts 135 00 Daiwa NS660A 30/300/3000 watts 135 00 New Tokyo HC 200A 115 00 Net-Tech Labs Digital Voice Keyer DVK 100 335 00 Astatic SilverEagle & Base 66 00 Ten-Tec Mobile Switch 30001 17:00 BELDEN 9913 low loss, solid center, foil/braid shield 51c/h 8267 RG213 Socht 827 RG8 39c/h 8267 RG213 Socht 8268 RG8x 20c/h 8267 RG213 Socht 8268 RG8x 20c/h 8268 RG8x 20c/h	Mirage Amps	15% OFF
VJ Amplifier, VHF, built in England, 1 in-100 out, 3:100, 5:100 (ea) 269:00 10 in-100 out, 229:00 25 160 out, 319:00 All models include preamp 109:00 ACCESSORIES 84W VIEWSTAR ANTENNA TUNER 89:95 Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189:00 Daiwa NS660A 30/300/3000 watts 135:00 Alinco ELH 230D- Excellent buy 88:00 Nye MB5-A (for the big boys!) 529:00 Shure 444D 54:95 Ameco FT-3 Soor Soor New Tokyo HC 200A 115:00 New Tokyo HC 200A 115:00 Tri-H 5000B Remote Rever DVK 100 336:00 Astatic SitverEagle & Base 66:00 Ten-Tec Mobile Switch 30001 17:00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ft 8000 14 Ga stranded copper ant. wire 13c/ft 9405 Heavy duty 2:16 Ga 6:18 Ga 56c/ft 9258 RG6x 20c/ft 20c/ft 9405 Heavy duty 2:16 Ga 6:18 Ga 56c/ft 9258 RG6x 20c/ft 20c/ft 9405 Heavy duty 2:16 Ga 6:18 Ga 56c/ft 9258 RG6x 20c/ft 5	Tokyo Hy-Power HL 1K AMP, no 4	CX250B699.00
3-100, 5-100 (ea) 269 00 10 in -100 out 229 00 25 in -160 out 319 00 All models include preamp 109 00 Lunar 2M4-40P 109 00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89 95 B&W VIEWSTAR ANTENNA TUNER 89 95 Heil HCA/HCS Stock Daiwa NS660A 30/300/3000 watts 135.00 Daiwa NS660A 30/300/3000 watts 135.00 Daiwa NS660A 30/300/3000 watts 135.00 Nye MB5-A (for the big boys!) 529 00 Shure 444D 54 95 Ameco PT-3 Scoon New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335 00 Astatic SilverEagle & Base 66 00 Ten Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ht 9237 RG8 39c/ht 8267 RG213 5c/ht 8267 RG213 5c/ht 9269 RG-62A/U 16 Ga 6-18 Ga 9269 RG-62A/U 16 Ga 6-18 Ga 9269		
10 in-100 out 229 00 25 in-160 out 319 00 All models include preamp 109 00 Lunar 2M4-40P 109 00 ACCESSORIES 88 W1EWSTAR ANTENNA TUNER 89.95 Heil HG4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soorn New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/h 8267 RG213 55c/h 8000 14 Ga stranded copper ant. wire 13c/h 9405 Heazy duty 2: 16 Ga 6-18 Ga 56c/h 9258 RG8x 20c/h 9258 RG8x 20c/h 9268 R-62A/U 16c	VJ Amplifier, VHF, built in England,	1 in-100 out,
25 in 160 out. 319 00 All models include preamp 109 00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soon New Tokyo HC 200A 115.00 Astatic SilverEagle & Base 66.00 Cen-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/h 8237 R68 39c/h 8267 RG213 55c/h 8267 RG213 55c/h 9013 Wic Cable, 3 condctr & shield 45c/h 9269 RG62A/U 16c/h 9403 Mic Cable, 3 condctr & shield 45c/h 9269 RG62A/U 16c/h 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 30 831J Double Female UHF 2.00 82-61 N Male 3.00 82-716 "tinned copper braid <td>3.100, 5.100</td> <td>(ea.) 269.00</td>	3.100, 5.100	(ea.) 269.00
All models include preamp 109.00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Allinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soon New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ft 8267 RG213 Socitt 33c/ft 8267 RG213 Socitt 33c/ft 848 & conductor rotor cable 33c/ft 9269 RG 62A/U 16c/ft 9268 RG8x 20c/ft 9269 RG 62A/U 16c/ft 9269 RG 62A/U 16c/ft 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 30 831J Double Female UHF 20 </td <td>10 in-100 out</td> <td></td>	10 in-100 out	
All models include preamp 109.00 ACCESSORIES B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Allinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soon New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ft 8267 RG213 Socitt 33c/ft 8267 RG213 Socitt 33c/ft 848 & conductor rotor cable 33c/ft 9269 RG 62A/U 16c/ft 9268 RG8x 20c/ft 9269 RG 62A/U 16c/ft 9269 RG 62A/U 16c/ft 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 30 831J Double Female UHF 20 </td <td>25 in-160 out</td> <td></td>	25 in-160 out	
ACCESSORIES B& VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco FT-3 Soon New Tokyo HC 200A 115.00 Net Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ht 8237 RG8 39c/ht 8267 RG213 55c/ht 8000 14 Ga stranded copper ant. wire 13c/ht 9405 Heavy duty 2.16 Ga 6-18 Ga 56c/ht 9258 RG8x 20c/ht 9268 RG-62A/U 16c/ht 8408 Mica Cable, 3 condert & shield 45c/ht 100 feet 8214 w/ends installed 54.00 8669 7/16" tinned copper braid 100/ht MPHENOL	All models include preamp	
ACCESSORIES B& VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco FT-3 Soon New Tokyo HC 200A 115.00 Net Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ht 8237 RG8 39c/ht 8267 RG213 55c/ht 8000 14 Ga stranded copper ant. wire 13c/ht 9405 Heavy duty 2.16 Ga 6-18 Ga 56c/ht 9258 RG8x 20c/ht 9268 RG-62A/U 16c/ht 8408 Mica Cable, 3 condert & shield 45c/ht 100 feet 8214 w/ends installed 54.00 8669 7/16" tinned copper braid 100/ht MPHENOL	Lunar 2M4-40P	109.00
B&W VIEWSTAR ANTENNA TUNER 89.95 Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco FT-3 Soor New Tokyo HC 200A 115.00 Net Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ht 8237 RG8 39c/ht 8267 RG213 55c/ht 8000 14 Ga stranded copper ant. wire 13c/ht 9405 Heavy duty 2.16 Ga 6-18 Ga 56c/ht 9258 RG8x 20c/ht 9268 RG-62A/U 16c/ht 8193.P-PL259 Silverplate 122 9268 RG-62A/U 16c/ht 813 Double Fermale UHF 200 8268 7/16" tinned copper braid 100/ht <td< td=""><td></td><td></td></td<>		
Heil HC4/HC5 Stock Heil BM10 Boom Mike headset CALL Tri-H 5000A Remote Phone \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy \$88.00 Nye MB5-A (tor the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soor New Tokye HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/tt 8237 R68 39c/tt 8237 R68 39c/tt 9405 Heavy duty 2-16 Ga 6-18 Ga 56c/tt 9405 Heavy duty 2-16 Ga 6-18 Ga 56c/tt 9269 R6 62A/U 16c/tt 8403 Mic Cable, 3 condctr & shield 45c/tt 9269 RG 62A/U 16c/tt 8403 Mic Cable, 3 condctr & shield 30.00 82-61 Niale 30.00 82-61 Niale 30.00 831SP-PL259 Silverplate 1.25 U	ACCESSORIES	
Tri-H 5000A Remote Phone. \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco FT-3 Soon New Tokyo HC 200A 115.00 Nel Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SitverEagle & Base. 66.00 Ten Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, fol/braid shield 51c/ht 8237 RG8 39c/ht 8267 RG213 55c/ht 8000 14 Ga stranded copper ant. wire 13c/ht 9258 RG8x 20c/ht 9268 RG-62A/U 16c/ht 8408 K conductor rotor cable 33c/ht 9268 RG-62A/U 16c/ht 8313 Double Female UHF 200 9268 RG-62A/U 16c/ht 8314 Double Female UHF 200 8313 Double Female UHF 200 8314 Double Female UHF 200 9269 RG-62A/U 300 8313 Double Female UHF 200 9312 10 uoble Female UHF 200 <td>B&W VIEWSTAR ANTENNA TUNE</td> <td>R</td>	B&W VIEWSTAR ANTENNA TUNE	R
Tri-H 5000A Remote Phone. \$189.00 Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco FT-3 Soon New Tokyo HC 200A 115.00 Nel Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SitverEagle & Base. 66.00 Ten Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, fol/braid shield 51c/ht 8237 RG8 39c/ht 8267 RG213 55c/ht 8000 14 Ga stranded copper ant. wire 13c/ht 9258 RG8x 20c/ht 9268 RG-62A/U 16c/ht 8408 K conductor rotor cable 33c/ht 9268 RG-62A/U 16c/ht 8313 Double Female UHF 200 9268 RG-62A/U 16c/ht 8314 Double Female UHF 200 8313 Double Female UHF 200 8314 Double Female UHF 200 9269 RG-62A/U 300 8313 Double Female UHF 200 9312 10 uoble Female UHF 200 <td>Heil HC4/HC5</td> <td>Stock</td>	Heil HC4/HC5	Stock
Daiwa NS660A 30/300/3000 watts 135.00 Alinco ELH 230D- Excellent buy 88.00 Nye MBS-A (tor the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soon New Tokyo HC 200A 115.00 Astatic SilverE agle & Base 66.00 Cren-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/h 8237 R68 39c/h 8237 R68 39c/h 8237 R68 39c/h 9405 Heavy duty 2-16 Ga 6-18 Ga 55c/h 9405 Heavy duty 2-16 Ga 6-18 Ga 55c/h 9405 Heavy duty 2-16 Ga 6-18 Ga 55c/h 9269 R6-62A/U 16c/h 8403 Mic Cable, 3 condctr & shield 45c/h 9269 R6-62A/U 16c/h 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 30 831J Double Female UHF 2.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31.2 Double Female UHF 9.00	Heil BM10 Boom Mike headset	CALL
Alinco ELH 2300- Excellent buy 88 00 Nye MB5-A (tor the big boys) 529 00 Shure 444D 54 95 Ameco PT-3 Soor New Tokyo HC 200A 115 00 Net-Tech Labs Digital Voice Keyer DVK 100 335 00 Astatic SilverEagle & Base 66 00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ft 9213 Tow loss, solid center, foll/braid shield 51c/ft 8267 RG213 55c/ft 8267 RG213 55c/ft 848 8 conductor rotor cable 33c/ft 9405 Heavy duty 216 Ga 6-18 Ga 56c/ft 9269 RG-62A/U 16c/ft 848 8 conductor rotor cable 33c/ft 9405 Heavy duty 216 Ga 6-18 Ga 56c/ft 9269 RG-62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 45c/ft 804 00 feet 8214 w/ends installed 54 00 831SP-PL259 Silverplate 125 9269 R Heav 30 82-97 N Female Bulkhead 30 82-97 N Female Bulkhead 30	Tri-H 5000A Remote Phone	\$189.00
Nye MB5-A (for the big boys!) 529.00 Shure 444D 54.95 Ameco PT-3 Soon New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ft 8237 RG8 39c/ft 8200 14 Ga stranded copper ant, wire 13c/ft 848 8 conductor rotor cable 33c/ft 9405 Heavy duty 2.16 Ga 6-18 Ga 56c/ft 9258 RG68 20c/ft 9258 RG68 20c/ft 9258 RG68 20c/ft 9269 RC-62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 54.01 9258 RG68 20c/ft 9269 RG-62A/U 16c/ft 8310 Double Female UHF 20 9258 RG68 300 9258 RG68 300 931.216 UG201 A/U N Male-BNC Female 300 82-97 N Female Bulkhead 300 931.22 BNC-RG59 150	Daiwa NS660A 30/300/3000 watts.	
Shure 444D 54.95 Ameco PT-3 Soon New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ht 9237 RG8 39c/ht 8247 RG8 39c/ht 8267 RG213 55c/tt 8200 14 Ga stranded copper ant. wire 13c/ft 9405 Heavy duty 2-16 Ga 6-18 Ga 36c/ht 9269 RG62A/U 16c/ht 8403 Mic Cable, 3 condctr & shield 45c/ht 9269 RG62A/U 16c/ht 8403 Mic Cable, 3 condctr & shield 100/ht AMPHENOL 831SP-PL259 Silverplate 1.25 931 Jouloub Female UHF 2.00 831 SP-PL259 Silverplate 1.25 931 Jouloub Female N 4.00 82-63 Inline Female UHF 2.00 831 SP-PL259 Silverplate 2.05 31.210 Duble Female N 4.00 82-98 N ebow 9.00 <td< td=""><td>Alinco ELH 230D- Excellent buy</td><td></td></td<>	Alinco ELH 230D- Excellent buy	
Ameco PT-3. Soon New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ht 8247 RG8 39c/ht 8257 RG81 39c/ht 8267 RG213 55c/ft 8000 14 Ga stranded copper ant, wire 13c/ht 9405 Heavy duty 2.16 Ga 6-18 Ga 56c/ht 9269 RG-62A/U 16c/ht 9269 RG-62A/U 16c/ht 9403 Mic Cable, 3 condctr & shield 45c/ht 9269 RG-62A/U 16c/ht 9269 RG-62A/U 16c/ht 9269 RG-62A/U 16c/ht 9269 RG-62A/U 100/ht AMPHENOL 831SP-PL259 Silverplate 1.25 9261 N Male 3.00 82-97 N Female Bulkhead 3.00 82-97 N Female Bulkhead 3.00 82-97 N Female Bulkhead 3.00 31-212 BNC-RG59 1.55 31-216 UG201 A/U N Male-BNC Femal	Nye MB5-A (for the big boys!)	
New Tokyo HC 200A 115.00 Nel-Tech Labs Digital Voice Keyer DVK 100 335.00 Astatic SilverEagle & Base 66.00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ft 8214 RG8 Foam 45c/ft 8237 RG8 39c/ft 8200 14 Ga stranded copper ant. wire 13c/ft 848 8 conductor rotor cable 33c/ft 9405 Heavy duty 2.16 Ga 6-18 Ga 56c/ft 9269 RG-62A/U 16c/ft 9243 RG86x 20c/ft 9258 RG6x 20c/ft 9258 RG68x 20c/ft 9258 RG68x 20c/ft 9258 RG68x 20c/ft 931 L00 teet 8214 w/ends installed 54.00 831.D Double Female UHF 2.00 831.J Double Female UHF 2.00 82-63 Inline Female UHF 2.00 82-63 Inline Female N 4.00 82-97 N Female Bulkhead 3.00 31.216 UG201 A/U N Male-BNC Female 2.00 31.22 BNC-RG58 3.00 31.22 BNC-RG58	Shure 444D	
Astatic SilverEagle & Base 66 00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, fol/braid shield 51c/h. 8217 RG8 39c/h. 8237 RG8 39c/h. 8267 RG213 55c/h. 8267 RG213 55c/h. 8488 & conductor rotor cable 33c/h. 9405 Heavy duty 216 Ga 6-18 Ga 56c/h. 9269 RG-62A/U 16c/h. 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 36 831J Double Female UHF 2.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.55 34125 N Female UHF male 9.00 312 BNC-RG58 1.55 34125 N Female UHF male 9.00 3128 BNC Female-PL259 <	Ameco PT-3	Soon
Astatic SilverEagle & Base 66 00 Ten-Tec Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, fol/braid shield 51c/h. 8217 RG8 39c/h. 8237 RG8 39c/h. 8267 RG213 55c/h. 8267 RG213 55c/h. 8488 & conductor rotor cable 33c/h. 9405 Heavy duty 216 Ga 6-18 Ga 56c/h. 9269 RG-62A/U 16c/h. 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 36 831J Double Female UHF 2.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.55 34125 N Female UHF male 9.00 312 BNC-RG58 1.55 34125 N Female UHF male 9.00 3128 BNC Female-PL259 <	New Tokyo HC 200A	115.00
Ten-Tec: Mobile Switch 30001 17.00 BELDEN 9913 low loss, solid center, foll/braid shield 51c/ft 8214 RG8 Foam 45c/ft 8217 RG8 39c/ft 8267 RG213 55c/ft 8000 14 Ga stranded copper ant, wire 13c/ft 848 8 conductor rotor cable 33c/ft 9405 Heavy duty 2:16 Ga 6-18 Ga 56c/ft 9269 RG-62A/U 16c/ft 9269 RG-62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 54 of 9269 RG-62A/U 16c/ft 8310 Double Female UHF 200 8311 Double Female UHF 200 8311 Double Female UHF 200 82-63 Inline Female UHF 300 82-63 Inline Female N 400 82-97 N Female Bulkhead 300 81-212 BNC-RG59 150 31-216 UG201 A/U N Male-BNC Female 200 31-28 BNC Female PL259 300 34125 N Male, RG58 300 31-28 BNC Female PL259 300 31-216 UG201 A/U N Male-BNC Female 200 31-28 BNC Female PL259 300 3128 BNC Female PL259	Nel-Tech Labs Digital Voice Keyer I	DVK 100
BELDEN 9913 low loss, solid center, foll/braid shield 51c/ht 8214 RG8 Foam 45c/ht 8237 RG8 39c/ht 8267 RG213 55c/ht 8200 14 Ga stranded copper ant, wire 13c/ht 9405 Heavy duty 2-16 Ga 6-18 Ga 56c/ht 9269 RG62A/U 16c/ht 9269 RG62A/U 16c/ht 9403 Mic Cable, 3 condctr & shield 45c/ht 9269 RG62A/U 16c/ht 931 SP-PL259 Silverplate 1.00/ht AMPHENOL 831SP-PL259 Silverplate 1.25 931 Double Female UHF 2.00 82-63 Inline Female UHF 2.00 82-63 Inline Female UHF 2.00 82-63 Inline Female N 4.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-218 BNC-RG58 3.00 31-218 BNC-RG59 1.50 31-218 BNC Female PL259 3.00 3124 BNC Female	Astatic SilverEagle & Base	
9913 low loss, solid center, foll/braid shield 51c/ft 8217 RG8 39c/ft 8237 RG8 39c/ft 8247 RG8 39c/ft 8267 RG213 55c/ft 8000 14 Ga stranded copper ant wire 13c/ft 9405 Heavy duty 2-16 Ga 6-18 Ga 36c/ft 9269 RG62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 45c/ft 9269 RG62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 45c/ft 100 feet 8214 w/ends installed 54.00 8699 7/16" tinned copper braid 1.00/ft AMPHENOL 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 30 831J Double Female UHF 2.00 82-61 In Male 3.00 82-91 N Female Bulkhead 3.00 82-63 Inline Female UHF 2.00 31-216 UG201 A/U N Male-BNC Female 2.00 31-218 BNC Female PL259 3.00 31-218 DNC RG58 1.50 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 3128 BNC Female PL259 </td <td>Ten-Tec Mobile Switch 30001</td> <td></td>	Ten-Tec Mobile Switch 30001	
9913 low loss, solid center, foll/braid shield 51c/ft 8217 RG8 39c/ft 8237 RG8 39c/ft 8247 RG8 39c/ft 8267 RG213 55c/ft 8000 14 Ga stranded copper ant wire 13c/ft 9405 Heavy duty 2-16 Ga 6-18 Ga 36c/ft 9269 RG62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 45c/ft 9269 RG62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 45c/ft 100 feet 8214 w/ends installed 54.00 8699 7/16" tinned copper braid 1.00/ft AMPHENOL 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 30 831J Double Female UHF 2.00 82-61 In Male 3.00 82-91 N Female Bulkhead 3.00 82-63 Inline Female UHF 2.00 31-216 UG201 A/U N Male-BNC Female 2.00 31-218 BNC Female PL259 3.00 31-218 DNC RG58 1.50 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 3128 BNC Female PL259 </td <td>REL'DEN</td> <td></td>	REL'DEN	
8214 RG8 Foam 45c/ft 8237 RG8 39c/ft 8267 RG213 55c/ft 8000 14 Ga stranded copper ant, wire 13c/ft 848 8 conductor rotor cable 33c/ft 9405 Heavy duty 2:16 Ga 6-18 Ga 56c/ft 9258 RG8x 20c/ft 9269 RG-62A/U 16c/ft 9403 Mic Cable, 3 condctr & shield 45c/ft 100 feet 8214 w/ends installed 54 00 8669 7/16" tinned copper braid 1.00/ft AMPHENOL 831SP-PL259 Silverplate 1.25 UG176 reducer RG8X 36 8313 Double Female UHF 2.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.55 31-216 UG201 A/U N Male-BNC Female 2.00 312 BNC-RG58 1.55 34125 N Female UHF male 9.00 3128 BNC Female PL259 3.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 <tr< td=""><td>0012 low loss colid center foll/brai</td><td>dehield 51c/H</td></tr<>	0012 low loss colid center foll/brai	dehield 51c/H
8237 RG8	9914 DC9 Ecom	45c/#
8267 RG213 55c/tt 8000 14 Ga stranded copper ant. wire 13c/tt 8448 8 conductor rotor cable 33c/tt 9405 Heavy duty 2-16 Ga 6-18 Ga 56c/tt 9258 RG8x 20c/tt 9269 RG-62A/U 16c/tt 8403 Mic Cable, 3 condctr & shield 45c/tt 9269 RG-62A/U 16c/tt 8403 Mic Cable, 3 condctr & shield 45c/tt 9269 RG-62A/U 16c/tt 8468 7/16" tinned copper braid 1.00/tt AMPHENOL 831SP-PL259 Silverplate 1.25 931J Double Female UHF 2.00 82-61 N Male 3.00 82-37 N Female Bulkhead 3.00 82-63 Inline Female N 4.00 82-98 N elbow 9.00 31-216 UG201 A/U N Male-BNC Female 2.00 21-21 BNC-RG58 1.50 3122 BNC-RG58 3.00 3128 BNC Female UHF male 9.00 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 </td <td>0214 NG0 F0d10</td> <td>20o/tt</td>	0214 NG0 F0d10	20o/tt
8448 8 conductor rotor cable 33c/ft 9405 Heavy duty 2-16 Ga 6-18 Ga 56c/ft 9258 RG6x 20c/ft 9269 RG 62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 45c/ft 100 feet 8214 w/ends installed 54.0 8669 7/16" tinned copper braid 1.00/ft AMPHENOL 8315P-PL259 Silverplate 1.25 UG176 reducer RG8X 33 831J Double Female UHF 2.00 82-63 Inline Female Bulkhead 3.00 82-63 Inline Female N 4.00 82-63 Inline Female RN 9.00 31-216 UG201 A/U N Mate-BNC Female 2.00 31-218 DC-RG58 1.50 31-216 UG201 A/U N Mate-BNC Female 2.00 31-218 DC-RG58 1.50 31-218 DC-RG58 1.50 31-218 DC-RG58 1.50 3128 BNC Female UHF male 9.00 3129	0007 00010	55c/ft
8448 8 conductor rotor cable 33c/ft 9405 Heavy duty 2-16 Ga 6-18 Ga 56c/ft 9258 RG6x 20c/ft 9269 RG 62A/U 16c/ft 8403 Mic Cable, 3 condctr & shield 45c/ft 100 feet 8214 w/ends installed 54.0 8669 7/16" tinned copper braid 1.00/ft AMPHENOL 8315P-PL259 Silverplate 1.25 UG176 reducer RG8X 33 831J Double Female UHF 2.00 82-63 Inline Female Bulkhead 3.00 82-63 Inline Female N 4.00 82-63 Inline Female RN 9.00 31-216 UG201 A/U N Mate-BNC Female 2.00 31-218 DC-RG58 1.50 31-216 UG201 A/U N Mate-BNC Female 2.00 31-218 DC-RG58 1.50 31-218 DC-RG58 1.50 31-218 DC-RG58 1.50 3128 BNC Female UHF male 9.00 3129	8267 HG213	
9405 Heavy duty 2-16 Ga 6-18 Ga	8000 14 Ga stranded copper ant. w	are 130/11
9258 RG6x 20c/ft 9269 RG-62A/U 16c/ft 9403 Mic Cable, 3 condctr & shield 45c/ft 100 feet 8214 w/ends installed 54.00 8669 7/16" tinned copper braid 1.00/ft AMPHENOL 8315P-PL259 Silverplate 1.25 WG 176 reducer RG8X 36 831J Double Female UHF 2.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-216 UG201 A/U N Male-BNC Female 2.00 32-98 N elbow 9.00 31-216 UG201 A/U N Male-BNC Female 2.00 312 BNC-RG58 1.50 34125 N Female UHF male 9.00 3128 BNC Female-ULF 9.00 3128 BNC Female-ULF 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF 1.95 25A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or .001/20KV 1.95 365pF cap 1.95	8448 8 conductor rotor cable	33C/II
9269 RG-62A/U 16C/II 8403 Mic Cable, 3 condctr & shield 45C/II 100 feet 8214 w/ends installed 54.00 8669 7/16" tinned copper braid 1.00/It AMPHENOL 331.7 8315P-PL259 Silverplate 1.25 UG176 reducer RG8X 33 831.J Double Female UHF 2.00 82-63 Inline Female Bulkhead 3.00 82-63 Inline Female R 4.00 82-63 Inline Female R 4.00 82-63 Inline Female R 4.00 82-63 Inline Female R 9.00 31.216 UG201 A/U N Mate-BNC Female 2.00 31.218 DC-RG58 1.50 31.218 DG S0 3.00 3.00 31.218 DG S0 3.00 3.00 31.218 DG Female UHF male 9.00 31.28 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female VL259 3.00 34125 N Fample/00V full wave bridge rectilier 1.95 1.5 Ampl400V full wave bridge rectilier 1.95 30201 .95 25A/1000PIV Epoxy diode 29	9405 Heavy duty 2-16 Ga 6-18 Ga.	
8403 Mic Cable, 3 condert & shield 45c/ft 100 feet 8214 w/ends installed 54.00 8669 7/16" tinned copper braid 1.00/ft AMPHENOL 831SP-PL259 Silverplate. 1.25 831J Double Female UHF 2.00 831J Double Female UHF 2.00 82-61 N Male 3.00 82-63 Inime Female N 4.00 82-98 N elbow 9.00 31-216 UG201 A/U N Male-BNC Female 2.00 31-2 BNC-RG58 1.50 31-28 BNC Female NHF male 9.00 31-216 UG201 A/U N Male-BNC Female 2.00 31-28 BNC Female UHF male 9.00 31-28 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 4400 N Male-50 239 7.00 PARTS 1.5 Amp/400V full wave bridge rectifier 1.95 365pF cap 1.95 365pF cap 1.95 365pF cap 1.95 3.00 1/8.14. watt carborn resistors 0.5 each Meters 0.3000 VDC 2½" Square 0-1 Amp DC 9.95 3.00 1.95 </td <td>9258 RG8x</td> <td>20C/IL</td>	9258 RG8x	20C/IL
100 feet 8214 w/ends installed 54.00 8669 7/16" tinned copper braid 1.00/ft AMPHENOL 8315P-PL259 Silverplate 1.25 UG 176 reducer RG8X 30 8315P-PL259 Silverplate 1.25 UG 176 reducer RG8X 30 831J Double Female UHF 2.00 82-61 N Male 3.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-216 UG201 A/U N Male-BNC Female 2.00 31-218 DNC-RG58 3.00 34125 N Female UHF male 9.00 3128 BNC Female-UL59 3.00 3128 BNC	9269 HG-62A/U	160/11
8669 7/16" tinned copper braid 1.00/ft AMPHENOL 831SP-PL259 Silverplate. 1.25 UG176 reducer RG8X 30 831J Double Female UHF 2.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-63 Inline Female UHF 2.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31-216 UG201 A/U N Male-BNC Female 2.00 31-218 DKC-RG58 1.50 34025 N Male, RG58 3.00 3425 N Female UHF male 9.00 31425 N Female UHF male 9.00 315 Amp/400V full wave bridge rectilier 1.95 365pf cap 1.95 Sanyo AAA AN Nicads witabs 2.00	8403 Mic Cable, 3 condctr & shield	450/1
AMPHENOL 125 831SP-PL259 Silverplate 125 UG176 reducer RG8X 30 831J, Double Female UHF 200 82-61 N Male 300 82-61 N Male 300 82-61 N Male 300 82-61 N Male 300 82-63 Inline Female N 400 82-98 N elbow 900 31-216 UG201 A/U N Male-BNC Female 200 31-216 UG201 A/U N Male-BNC Female 200 31-28 BNC Female UHF male 900 3128 BNC Female UHF male 900 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 3128 BNC Female PL259 3.00 3120 D00FIV Epoxy diode 29 each or 19.00/100 0015/10KV or 001/20KV 1.95 each 3N201 .95 365pF cap 1.95 365pF cap 1.95 3000 VDC 2Var Square 0-1 Amp DC 9.95 01/8.14.4 watt carborn resistors .05 each Meters 0.3000 VDC 2Var Square 0-1 Amp DC 9.95 Drake— Collins mike plug	100 feet 8214 w/ends installed	54.00
831SP-PL259 Silverplate 1.25 UG176 reducer RG8X .30 831J, Double Female UHF 2.00 82-61 N Male .300 82-61 N Male .300 82-61 N Male .300 82-63 N Inione Female N .400 82-63 Inione Female N .400 82-98 N elbow .900 31-216 UG201 A/U N Male-BNC Female .200 31-216 UG201 A/U N Male-BNC Female .200 31-28 BNC-RG58 .150 3126 BNC Female UHF male .900 3128 BNC Female UHF male .900 3128 BNC Female PL259 .300 4400 N Male-50 239 .700 PARTS 1.5 Amp/400V full wave bridge rectifier .195 1.5 Amp/400V full wave bridge rectifier .195 .302 3120 D001/20KV .195 each .195 365pF cap .195 .300 .195 365pF cap .195 .300 .184 .14, watt carborn resistors .05 each .200 .24, 56, 8 pin mic plugs .300 .200	8669 //16" tinned copper braid	1.00/11.
831SP-PL259 Silverplate 1.25 UG176 reducer RG8X .30 831J, Double Female UHF 2.00 82-61 N Male .300 82-61 N Male .300 82-61 N Male .300 82-63 N Inione Female N .400 82-63 Inione Female N .400 82-98 N elbow .900 31-216 UG201 A/U N Male-BNC Female .200 31-216 UG201 A/U N Male-BNC Female .200 31-28 BNC-RG58 .150 3126 BNC Female UHF male .900 3128 BNC Female UHF male .900 3128 BNC Female PL259 .300 4400 N Male-50 239 .700 PARTS 1.5 Amp/400V full wave bridge rectifier .195 1.5 Amp/400V full wave bridge rectifier .195 .302 3120 D001/20KV .195 each .195 365pF cap .195 .300 .195 365pF cap .195 .300 .184 .14, watt carborn resistors .05 each .200 .24, 56, 8 pin mic plugs .300 .200	AMPHENOL	
UG176 reducer RG8X 36 831J Double Female UHF 200 82-61 N Male 3.00 82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-216 UG201 A/U N Male-BNC Female 2.00 31-216 UG201 A/U N Male-BNC Female 2.00 31-216 UG201 A/U N Male-BNC Female 2.00 31-218 DKC-RG58 1.55 34025 N Male, RG58 3.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF 1.95 5 A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or .001/20KV 1.95 each 3N201 .95 2.5 A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or .001/20KV 1.95 each 3N201 .95 2.4 5.6 B pin mic plugs 3.00 1/8, 1/4, watt carbon resistors .05 each <tr< td=""><td>831SP-PL259 Silverplate</td><td>1.25</td></tr<>	831SP-PL259 Silverplate	1.25
82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-63 Inline Female N 4.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-216 UG201 A/U N Male-BNC Female 2.00 31-28 BNC-RG58 1.50 34025 N Male, RG58 3.00 34125 N Female UHF male 9.00 3128 BNC Female PL259 3.00 34128 NF Female UHF male 9.00 3128 BNC Female PL259 3.00 34126 N Female UHF male 9.00 3128 BNC Female VLS9 3.00 4400 N Male-50 239 7.00 PARTS 1.5 Amp/400V full wave bridge rectilier 1.95 1.5 Amp/400V full wave bridge rectilier 1.95 3.00 3N201 .95 5.31 .90 3N201 .95 .90 .90 24.5 6.8 pin mic plugs .300 .00 .18 365pF cap .95 .99 .90 .95 Sarko AAA, AA Nicads w/tabs .200 .24,5 6.8 pin mic plugs .300 .00	UG176 reducer RG8X	30
82-61 N Male 3.00 82-97 N Female Bulkhead 3.00 82-63 Inline Female N 4.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-216 UG201 A/U N Male-BNC Female 2.00 31-28 BNC-RG58 1.50 34025 N Male, RG58 3.00 34125 N Female UHF male 9.00 3128 BNC Female PL259 3.00 34128 NF Female UHF male 9.00 3128 BNC Female PL259 3.00 34126 N Female UHF male 9.00 3128 BNC Female VLS9 3.00 4400 N Male-50 239 7.00 PARTS 1.5 Amp/400V full wave bridge rectilier 1.95 1.5 Amp/400V full wave bridge rectilier 1.95 3.00 3N201 .95 5.31 .90 3N201 .95 .90 .90 24.5 6.8 pin mic plugs .300 .00 .18 365pF cap .95 .99 .90 .95 Sarko AAA, AA Nicads w/tabs .200 .24,5 6.8 pin mic plugs .300 .00	831J Double Female UHF	2.00
82-97 N Female Bulkhead 3.00 82-98 N elbow 9.00 82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-216 UG201 A/U N Male-BNC Female 2.00 31-2176 UG201 A/U N Male-BNC Female 2.00 31-218 DNC-RG58 1.55 34025 N Male, RG58 3.00 312 BNC-RG58 3.00 312 BNC-RG58 3.00 312 BNC-RG58 3.00 312 BNC-RG58 3.00 312 BNC-Female UHF male 9.00 3128 BNC-Female PL259 3.00 4400 N Male-50 239 7.00 PARTS 1.5 Amp/400V full wave bridge rectilier 1.95 2.5A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or .001/20KV 1.95 each 3N201	82-61 N Male	3.00
82-63 Inline Female N 4.00 82-98 N elbow 9.00 31-218 BIC-RG59 1.55 31-218 DIC-RG58 1.50 31-218 DIC-RG58 1.50 34025 N Male, RG58 3.00 34125 N Female UHF male 9.00 3128 BINC Female PL259 3.00 34025 N Male, RG58 3.00 34125 N Female UHF male 9.00 3128 BINC Female PL259 3.00 4400 N Male-50 239 7.00 PARTS 1.5 Ampl400V full wave bridge rectilier 1.95 2.5A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or.001/20KV 1.95 365pF cap 1.95 3.00 1.95 3.00 3121 NA AA Nicads witabs 2.00 1.8 1.95 365pF cap 1.95 3.00 1.8 1.95 365pF cap 1.95 3.00 1.8 1.95 Sanyo AAA AA Nicads witabs 2.00 1.00 1.95 3.00 1/8.1/4. watt carbon resistors .05 <each< td=""> .05<each< td=""> 1.95</each<></each<>	82-97 N Female Bulkhead	3.00
82-98 N elbow 9.00 31-212 BNC-RG59 1.50 31-216 UG201 A/U N Male-BNC Female 2.00 31-28 NC-RG58 1.50 34025 N Male, RG58 3.00 34125 N Male, RG58 3.00 34125 N Male, RG58 3.00 3128 BNC Female UHF male 9.00 3128 BNC Female PL259 3.00 700 PARTS 1.5 Amp/400V full wave bridge rectilier 1.95 25A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or .001/20KV 1.95 each 3N201 .95 24,56,8 pin mic plugs 3.00 24,56,8 pin mic plugs 3.00 1/8, 1/4, watt carbon resistors .05 each Meters 0.3000 VDC 2V2* Square 0-1 Amp DC 9.95 Drake - Collins mike plug 2.00 Thousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time .24 We may have what you're looking for. .29 Duracell 9 Volt Battery - 2 Pak MN1604 3.42	82-63 Inline Female N	4.00
31-212 BNC FG659 1 50 31-216 UG201 A/U N Male-BNC Female 2 00 31-2 BNC FG58 1 50 312 BNC Female UHF male 9 00 3128 BNC Female UHF male 9 00 3128 BNC Female UHF male 9 00 3128 BNC Female PL259 3 00 4400 N Male 50 239 7 00 PARTS 1 5 Amp/400V full wave bridge rectilier 1 95 2 5A/1000PIV Epoxy diode 29 each or 19 00/100 0015/10KV or .001/20KV 1 95 each 3N201 .95 365pF cap 1 95 365pF cap 1 95 2 4 5 6 8 pin mic plugs 3 00 1 95 300 1 98 3 14, watt carbon resistors 05 each 9 95 50 rake - Collins mike plug 2 00 2 4 5 6 8 pin mic plugs 3 00 ud/18, 1/4, watt carbon resistors 05 each 9 95 Drake - Collins mike plug 2 00 2 00 1 00 4/3KV 5 00 others CALL Close out on rigs & accessories. All the time Call We may have what you're looking for. 29 Duraced 9 Vott Battery - 2 Pak MN1604 3 42 34 34	82-98 N elbow	9.00
31.216 UG201 A/U N Male-BNC Female 2.00 31.2 BNC-RG58 1.50 34025 N Male, RG58 3.00 34125 N Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female PL259 3.00 4400 N Male 50 239 7.00 PARTS 1.5 Ampl400V full wave bridge rectifier 1.95 2.5A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or.001/20KV 1.95 each 3N201 .95 3.000 1.95 3.65,67 cap 1.95 Sanyo AAA AA Nicads witabs 2.00 2.4,5,6,8 pin mic plugs 3.00 1.85 1/4. watt carbon resistors .05 each .05 0.00 1.95 Drake-Collins mike plug 2.00 Thousands of panel meters 3.95 up CALL .00 MICA Cap.0004/3KV 5.00 others CALL .00 .00 .00 .00 MiCA Cap.0004/3KV 5.00 others CALL .00 .00 .29 .00 MiCA Cap.0004/3KV .00 .00 .00	31-212 BNC-RG59	1.50
31-2 BNC-RG58 1 5C 34025 N Male, RG58 3 00 34125 N Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 3128 BNC Female UHF male 9.00 9RRTS 3.00 1 5 Amp/400V full wave bridge rectifier 1.95 2 5A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or .001/20KV .95 each 3N201 .95 3anyo AAA AA Nicads w/tabs 2.00 2.4,5,6,8 pin mic plugs .3.00 1/8, 1/4, watt carbon resistors .05 each Meters 0.3000 VDC 2V ₂ " Square 0-1 Amp DC .9 95 Drake — Collins mike plug .200 Thousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV 500 others CALL Close out on rigs & accessories. All the time .24 We may have what you're looking for. .29 Duracell 9 Vott Battery - 2 Pak MN1604 .3.42	31,216 LIG201 A/LLN Male-BNC Fr	emale 2.00
34125 N Female UHF male 9.00 3128 BNC Female PL259 3.00 4400 N Male-50 239 7.00 PARTS 1.5 Amp/400V full wave bridge rectifier 1.95 2.5A/1000PIV Epoxy diode .29 each or 19.00/100 0015/10KV or .001/20KV .1.95 each 38201 .95 4 inch ferrite rod .1.95 365pF cap .1.95 365pF cap .1.95 3000 VDC 2Vs/ Square 0.1 Amp DC .9.95 Drake-Collins mike plug .200 Thousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV .500 others CALL Close out on rigs & accessories. All the time .Cal We may have what you're looking for. .29 Diodes 3A/1000 PIV .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3.42	21.2 BNC RG58	1.50
34125 N Female UHF male 9.00 3128 BNC Female PL259 3.00 4400 N Male-50 239 7.00 PARTS 1.5 Amp/400V full wave bridge rectifier 1.95 2.5A/1000PIV Epoxy diode .29 each or 19.00/100 0015/10KV or .001/20KV .1.95 each 38201 .95 4 inch ferrite rod .1.95 365pF cap .1.95 365pF cap .1.95 3000 VDC 2Vs/ Square 0.1 Amp DC .9.95 Drake-Collins mike plug .200 Thousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV .500 others CALL Close out on rigs & accessories. All the time .Cal We may have what you're looking for. .29 Diodes 3A/1000 PIV .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3.42	34025 N Male BG58	3.00
3128 BNC Female-PL259 3.00 4400 N Male-50 239 7.00 PARTS 7.00 1.5 Amp/400V full wave bridge rectifier 1.95 2.5A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or.001/20KV 1.95 each 3N201 .95 4 inch ferrite rod 1.95 365pF cap 1.95 365pF cap 1.95 Sanyo AAA AA Nicads w/tabs 2.00 2.4,5,6,8 pin mic plugs 3.00 1/8.1/4. watt carbon resistors .05 each Meters 0.3000 VDC 2½° Square 0-1 Amp DC 9.95 Drake-Collins mike plug 2.00 Close out on rigs & accessories. All the time Call We may have what you're looking for. 29 Diodes 3A/1000 PIV .20 Duracell 9 Volt Battery - 2 Pak MN1604 3.42	34125 N Female LIHE male	9.00
4400 N Male 50 239 7.00 PARTS 1.5 Amp/400V full wave bridge rectilier 1.95 2.5A/1000PIV Epoxy diode 29 each or 19.00/100 0015/10KV or .001/20KV 1.95 each 3N201 .95 365pF cap 1.95 365pF cap 1.95 2.4, 56, 8 pin mic plugs 3.00 1/8, 1/4, watt carbon resistors .05 each Meters 0.3000 VDC 2Vall Square 0-1 Amp DC 9.95 Drake - Collins mike plug 2.00 2.002 Chins mike plug 2.002 Chousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time Call We may have what you're looking for. .29 Duracell 9 Volt Battery - 2 Pak MN1604 3.42	3128 BNC Female PI 259	3.00
PARTS 1.5 Amp/400V full wave bridge rectifier 1.95 2.5A/1000PIV Epoxy diode .29 each or 19.00/100 .0010000000000000000000000000000000000	4400 N Mala 50 220	7.00
1.5 Amp/400V full wave bridge rectilier 1.95 2.5A/1000PIV Epoxy diode .29 each or 19.00/100 0015/10KV or .001/20KV .195 each 3N201 .95 4 inch ferrite rod .195 365pF cap .195 2.4,5,6,8 pin mic plugs .300 1.8, 1/4, watt carbon resistors .056 each Meters 0.3000 VDC 2Vs/" Square 0-1 Amp DC .955 Drake—Collins mike plug .200 Thousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV 500 others CALL Close out on rigs & accessories. All the time .24 Diodes 3A/1000 PIV .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3.42	4400 N Male 50 255	
2:5A/1000PIV Epoxy diode .29 each or 19:00/100 0015/10KV or .001/20KV .195 each 3N201 .95 4 inch ferrite rod .195 365pF cap .195 Sanyo AAA AA Nicads w/tabs .200 2:4,5.6,8 pin mic plugs .300 1/8:1/4, watt carbon resistors .05 each Meters 0:3000 VDC 2½° Square 0:1 Amp DC .95 Drake-Collins mike plug .200 Thousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV 500 others CALL Close out on rigs & accessories. All the time .21 We may have what you're looking for. .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3.42	PARTS	
2:5A/1000PIV Epoxy diode .29 each or 19:00/100 0015/10KV or .001/20KV .195 each 3N201 .95 4 inch ferrite rod .195 365pF cap .195 Sanyo AAA AA Nicads w/tabs .200 2:4,5.6,8 pin mic plugs .300 1/8:1/4, watt carbon resistors .05 each Meters 0:3000 VDC 2½° Square 0:1 Amp DC .95 Drake-Collins mike plug .200 Thousands of panel meters .3.95 up CALL MICA Cap. 0004/3KV 500 others CALL Close out on rigs & accessories. All the time .21 We may have what you're looking for. .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3.42	1.5 Amp/400V full wave bridge rect	tifier
0015/10KV or .001/20KV 1.95 each 3N201 .95 4 inch ferrite rod .95 365pF cap .95 Sanyo AAA, AA Nicads w/tabs .200 2.4,5,6,8 pin mic plugs .300 1/8, 1/4, watt carbon resistors .05 each Meters 0.3000 VDC 2½" Square 0-1 Amp DC .9 95 Drake—Collins mike plug .200 Close out on rigs & accessories. All the time .04 We may have what you're looking for. .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3 42	2 5A/1000PIV Epoxy diode 2	9 each or 19.00/100
3N201 .95 4 inch ferrite rod .195 365pF cap .195 Sanyo AAA, AA Nicads w/tabs .200 2,4,5,6,8 pin mic plugs .300 1/8, 1/4, watt carbon resistors .05 each Meters 0:3000 VDC 2½° Square 0:1 Amp DC .95 Drake—Collins mike plug .200 Thousands of panel meters .395 up CALL MICA Cap. 0004/3KV .500 others CALL Close out on rigs & accessories. All the time .Cal We may have what you're looking for. .29 Diodes 3A/1000 PIV .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3.48	0015/10KV or .001/20KV	
4 inch ferrite rod 1.95 365pF cap 1.95 Sanyo AAA, AA Nicads w/tabs 2.00 2,4,5,6,8 pin mic plugs 3.00 1/8, 1/4, watt carbon resistors .05 each Meters 0.3000 VDC 2Va's Square 0.1 Amp DC 9.95 Drake—Collins mike plug 2.00 Thousands of panel meters 3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time Cal We may have what you're looking for. 29 Diodes 3A/1000 PIV .29 Duracell 9 Volt Battery - 2 Pak MN1604 3.42		
365pF cap 195 Sanyo AAA, AA Nicads w/tabs 2.00 2.4, 5, 6, 8 pin mic plugs 3.00 1/8, 1/4, watt carbon resistors 0.5 each Meters 0-3000 VDC 2½" Square 0-1 Amp DC 9.95 Drake—Collins mike plug 2.00 Chousands of panel meters 3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time Cal We may have what you're looking for. 29 Duracell 9 Volt Battery - 2 Pak MN1604 3.42		
Sanyo AAA, AA Nicads witabs 2.00 2.4,5,6,8 pin mic plugs 3.00 1/8, 1/4, watt carbon resistors .05 each Meters 0:3000 VDC 2½° Square 0-1 Amp DC 9.95 Drake—Collins mike plug 2.00 Thousands 01 panel meters .3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time .Cal We may have what you're looking for. .29 Diodes 3A/1000 PIV .29 Duracell 9 Volt Battery - 2 Pak MN1604 .3.49		1.95
2,4,5,6,8 pin mic plugs 3,00 1/8, 1/4, watt carbon resistors 0.56 each Meters 0.3000 VDC 2½° Square 0.1 Amp DC 9,95 Drake—Collins mike plug 2,00 Thousands of panel meters 3.95 up CALL MICA Cap. 0004/3KV 500 others CALL Close out on rigs & accessories. All the time Cal We may have what you're looking for Diodes 3A/1000 PIV 29 Duracell 9 Volt Battery - 2 Pak MN1604 3.42	Sanyo AAA.AA Nicads w/tabs	2.00
Meters 0-3000 VDC 2½" Square 0-1 Amp DC 9.95 Drake—Collins mike plug 2.00 Thousands of panel meters 3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time Cal We may have what you're looking for. 29 Diodes 3A/1000 PIV 29 Duracell 9 Volt Battery - 2 Pak MN1604 3.45	2,4,5,6,8 pin mic plugs	3.00
Meters 0-3000 VDC 2½" Square 0-1 Amp DC 9.95 Drake—Collins mike plug 2.00 Thousands of panel meters 3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time Cal We may have what you're looking for. 29 Diodes 3A/1000 PIV 29 Duracell 9 Volt Battery - 2 Pak MN1604 3.45	1/8, 1/4, walt carbon resistors	
Drake—Collins mike plug 2.00 Thousands of panel meters 3.95 up CALL MICA Cap. 0004/3KV 5.00 others CALL Close out on rigs & accessories. All the time Cal We may have what you're looking for. Diodes 3A/1000 PIV Divacell 9 Volt Battery - 2 Pak MN1604 3.48	Meters 0-3000 VDC 21/2" Square 0-	-1 Amp DC
Close out on rigs & accessories. All the time Cal We may have what you're looking for. Diodes 3A/1000 PIV 29 Duracell 9 Volt Battery - 2 Pak MN1604 3.49	Drake-Collins mike plug	2.00
Close out on rigs & accessories. All the time Cal We may have what you're looking for. Diodes 3A/1000 PIV 29 Duracell 9 Volt Battery - 2 Pak MN1604 3.49	Thousands of panel meters	3.95 up CALL
Close out on rigs & accessories. All the time Cal We may have what you're looking for. Diodes 3A/1000 PIV 29 Duracell 9 Volt Battery - 2 Pak MN1604 3.49	MICA Cap 0004/3KV	5.00 others CALL
We may have what you're looking for. Diodes 3A/1000 PIV	Close out on rigs & accessories All	the time Call
Diodes 3A/1000 PIV 29 Duracell 9 Volt Battery - 2 Pak MN1604 3 49	We may have what you're looking f	or
Duracell 9 Volt Battery - 2 Pak MN1604 3 49 DC Fan 3½" Sq. × 1" 9 95	Diodes 3A/1000 PIV	29
DC Fan 3½" Sq. × 1"	Duracell 9 Volt Battery - 2 Pak MN1	604 3.49
NEW CONTRACTOR AND	DC Fan 31/2" Sq. x 1"	9.95
CINCH 12 nin conn fitz (Drake etc.) female 3.00	CINCH 12 pin conn fitz (Drake atc.)	temale 3.00

ICOM



ANTENNAS	
Isopole 144 MHz	44 95
AOP-1, Complete Oscar Antenna	140.05
Butternut HF6V, 80-10 vertical	
HF2V, 80 & 40 vertical	119.00
HF4B	
Hustler G7-144	119.95
Hustler 6BTV KLM HF World Class Series Antennas	139.00
KLM HF World Class Series Antennas	Call Don
ALPHA Delta DX-DD	63.00
Coax Seal	2 00/rol
B&W Dipoles	Loss 100%
KLM KT-34A	399.00
W2AU, W2DU NEW KLM 1,2-44LBX	Now Available
NEW KLM 1,2-44LBX	129.00
1296 Power Divider	Soon
Create CD-78 + BS 80 75/80 rotatable dip	ole
GS-RV	
OTHER ANTENNAS	
Diamond D-130 Discone 25-1300 MHz	
Larsen Kulduck	17.00
Larsen 2M ½wave telescope ant	25.00
Avanti AP151 3G on Glass Antenna	
Anteco 2M, 5/8, Mag. Mount, Comp	
Orion 2M 1/2 wave Handy Antenna	
Van Gordon SLA-1 160-80-40 Sloper	
Valor AB-5 Mobile	79.95
Stoner DA100 D Active Rx Antenna	190.00
DC 'Tenna Hitch 3/8-24 Thread Fits 3/4" trailer hitches	
	29.95
KEYS	1
Bencher & Vibroplex Bencher is now improved. Screws & sprin	Less 10%
steel and outer band collability	go, an atan noo.
steel and extra hand polishing. Nye ESK-001 Keyer	58.00
TUBES Collins & Drake Replacement tubes	Di
GE 6146B	
3-500Z	109.95
GE Industrial Tubes	Cal
GE 12BY7A	7.00
GE 6JS6C	12 94
GE 8950	16 0
12JB6 Sylvania	
Hard to find Tubes 50-90% off list	
6JB6A	9.95
6.IE6C/6LO6	9.94
6.IE6C/6LO6	.9.95
6JE6C/6LQ6 572B	
6JE6C/6LQ6 5728 6KD6	
6JE6C/6LQ6 5728 6KD6 BOOKS	
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am	69.00 10.95 eco Radio
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am	69.00 10.95 eco Radio
6JE6C/6LQ6 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna	69.00 10.95 eco Radio Cal ational SW
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews	69.00 10.95 eco Radio Cal ational SW
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER	69.00 10.95 eco Radio Cal ational SW 12.95
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232	69.00 10.95 eco Radio
6JE6C/6L.Q6 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronice Packet II	69.00 10.95 eco Radio Cal ational SW 12.95 299.00 149.00
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270	69.00 10.95 eco Radio Cal ational SW 12.95 299.00 149.00 125.00
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1274	69.00 10.95 eco Radio Cal ational SW 12.95 299.00 149.00 125.00 149.00
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1274	69.00 10.95 eco Radio Cal ational SW 12.95 299.00 149.00 125.00 149.00
6JE6C/6L 06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1270 MFJ 1274 AEA PM-1	69 00 10.95 eco Radio .Cal ational SW 12.95 299 00 149 00 125 00 149 00 149 00 149 00 149 00
6JE6C/6L Q6 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1274 AEA PM-1 New AEA UDC-232 Firmware, No moder	69 00 10.95 eco Radio Cal ational SW 12.95 299.00 149.00 125.00 149.00 149.00 n,
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1270 MFJ 1274 AEA PM-1 New AEA UDC-232 Firmware, No moder List 279.00	69.00 10.95 eco Radio Cal ational SW 12.95 299.00 149.00 149.00 149.00 n, 249.00
6JE6C/6L 06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1274 AEA PM-1 New AEA UDC-232 Firmware, No moder List 279.00 New Kantronics KAM SERVICES	69.00 10.95 eco Radio Aatonal SW 12.95 299.00 149.00 149.00 149.00 n, 299.00
6JE6C/6L.06 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1274 AEA PM-1 New AEA UDC-232 Firmware, No moder List 279.00 New Kantronics KAM SERVICES	69.00 10.95 eco Radio Aatonal SW 12.95 299.00 149.00 149.00 149.00 n, 299.00
6JE6C/6L O6 572B 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1274 AEA PM-1 New AEA UDC-232 Firmware, No moder List 279.00 New Kantronics KAM	69 00 10.95 eco Radio Cal ational SW 299 00 149 000
6JE6C/6L Q6 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270 MFJ 1270 MFJ 1274 AEA PM-1 New AEA UDC-232 Firmware, No moder List 279.00 New Kantronics KAM SERVICES Complete KWM 2 Retube Flat fee Collins rebuild	69 00 10.95 eco Radio Cal ational SW 299 00 149 000
6JE6C/6L.06. 5728 6KD6 BOOKS We stock SAMS, TAB, ARRL, RSGB, Am Pubs New 1987 Radio Database Book - Interna plus reviews PACKET POWER AEA PK-232 Kantronics Packet II MFJ 1270. MFJ 1274 AEA PM-1 New AEA UDC-232 Firmware, No moder List 279.00 New Kantronics KAM SERVICES Complete KWM 2 Retube	69 00 10.95 eco Radio Cal ational SW 299 00 149 00 149 00 149 00 149 00 149 00 149 00 149 00 149 00 149 00 299 00 299 00 299 00 290 00 200 200 00 200 00000000

day trial. Six months full trade against new equipment. Sale price refunded if not satisfied Call for latest used gear list

(800) 231-3057

TOWER ACCESSORIES

1/4" E H S Guy cable. Rohn US. 1000 ft.	250.00
3/16" E H S cable. Rohn US. 1000 ft.	210.00
1/4" Guy Cable. 6100 #7 × 7 strand, import	18c/ft.
3/16" Guy Cable, 3700 #7 × 7 strand, import	15c/ft.
3/8" × 6 E&J Turnbuckle	7.95
3/16" Wire Rope Clips	
1/4" wire clips	
Porcelain 500D Guy Insulator (3/16)	1.99
Porcelain 502 Guy Insulators (1/4)	

POLICIES


Minimum order \$10.00. Mastercard, VISA, or C.O.D. All prices FOB Houston, except as noted. Prices subject to change without notice Items subject to prior sale. Call anytime to check the status of your order. Texas residents add sales tax. All items full factory warranty plus Madison warranty.

NEW AMPLIFIER LINE

Coming soon. How to buy a portable transceiver. The factors in order are: size, features, reliability, parts availability outside USA. Call for information.

DON'S CORNER

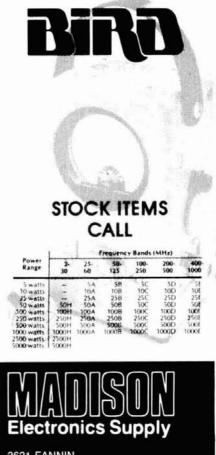We will be glad to do your Kenwood Warranty repair, even if you did not purchase from us. Send your rig, copy of your receipt and return address. 2-3 weeks turnaround.




3621 FANNIN HOUSTON, TEXAS 77004 1-713-520-7300 OR 1-713-520-0550

Call on the IC-761

106 May 1987

	2300	2200	2100	2000	1900	ŝ	1700	1800	1500	1400	1300	1200	1100	1000	0900	0800	0700	0600	0500	0400	0300	0200	0100	0000	GMT	
MAY	8	3:00	2:00		12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	POT	
ASIA FAR EAST	20	20	20	20	30	20	20	20	20	20	20	20	20	30	20	20	20	20	20	20*	15	15	15	20	-+ z	
EUROPE	20	20	20	20	15	15	15	15	15	15	20	20	20	20	30	30	20	20	20	30	30	30	30	30	Z	
S. AFRICA	20	20	15	15	12	12	10	10	10	12	12	15	20	20	20	20	15	15	20	30	20	20	20	20	↓ m	Ň
S. AMERICA	10	10	10	12	12	12	12	12	12	15	20	20	20	30	20	20	20	20	20	20	15	15	12	12	S≣ ∕	WEST
ANTARCTICA	15	15	15 5	15	20	20	20	40	40	40	40	40	ω 0	30 0	30	30 0	30	30	30 0	20	20	20	15	15	• • •	ERN
NEW ZEALAND	12	12	12	12	12	15	20	20	20	20	20	20	20	20	20*	15	15	12	12	10	10	10	10	12	S¥	USA
OCEANIA AUSTRALIA	10	12	12	15	20	30	30	30	30	20	20	20	20	20	20	20 *	15	12	10	10	10	10	10	10	† ₹	
JAPAN	15	20	20	20	20	20	30	30	30	20	30	30	30	20	20	20	2.0	20	15	15	15	15	15	15	/ ₹	
	L	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8	7:00	6:00	5.0	*	3:00	2:00	1:	12:00	11:00	.10:00	9	8:00	7:00	6:00	MDT	
 Asia	5:00	8	8	8	8 [w	8 w	8	8	8	8	8	8	8	8	2	8	ё ч	8	8	8	8	8	8	8		
FAR EAST	20 2	20 2	20 2	202	30 2	30 1	01	01	0 1	0 1	0 2	0 2	0 2	0 2	0 2	0 3	10 3	03	0 2	0*	σ ω	0 3	03	0 2	> Z	
EUROPE	20 2	20 2	0 1	0	0	5	51	5	5	5	20 1	0	0 1	0 2	0 2	0 2	0 2	0 2	0 2	0 	0 2	0 2	0 2	0 2	M R	
S, AFRIÇA	0 1	0	5	5	21	21	01	0	01	2 1	2 1	2 2	52	0 2	0 3	0 2	0 2	0 2	0 2	0 2	0 1	0 1	0 1	0 1		S
S. AMERICA	2 1	01	01	0 2	0 2	22	222	2 4	2 4	2 4	54	04	0 4	0 4	0 4	0 3	0 3	0 3	0	0 2	52	N	2 1	21	SE .	MID US,
ANTARCTICA	5 1	5	51	0	0	01	0 2	0 2	0 2	0 2	0 2	0	0	0		0	0	0	0			0	5	5	• · · ·	SA
NEW ZEALAND	0	2	2	2	2	2	0	0	0	0	0					0	5	5	~	2			0		Š	
AUSTRALIA	10	12	12	15	20	30	30	30	30	30	20	20	20	20	20	20	15	15	12	12	10	10 1	10 1	10 1	₹ 1 7	
JAPAN	15	5	20	20	20	20	30	30	30	30	20	20	20	30	30	30	20	20	20	20	20	ິ ເກ	ဟ T	5	2	
	6: 00	5:00	4: 8	3:00	2:08		12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	8	3:00	2:00	:: 8	12:00	11:00	10:00	9:00	8:00	7:00	CDT	
	7:00	6:00	5:00	4:00	3:00	2:00		12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8:00	EDT	فيكتبو
ASIA FAR EAST	20	20	30	30	30	20	20	20	20	20	15	15	20*	2	20	20	20	20	20	20	20	20	20	20	> z	
EUROPE	20	20	20	20	20	15	15	15	15	20	20	20	20	20	20	20	30	30	30	3	ω	30	20	20	M	
S. AFRICA	20	20	15	15	12	12	10	10	10	10	12	12	12	1-3 5	20	20	20	20	0 20	0 30	0 20	20	20	20	1 m	EA
CARIBBEAN S. AMERICA		11		12		1			1	1	1	15	20	20	30	20	20	20	0 20	20	20		112	12	SE SE	STE
ANTARCTICA	2 20	2 20	0 20	0 20	0 20	0 20	2 20	2 40	2 40	5 40	5 40	40) 40	40	40	40	30	30	30) 30	30	20	20	20	• 0	ASTERN USA
NEW ZEALAND	0 10	12	12	0 15	15	15	20	20	20) 20	20	<u> </u>	20) 20	20) 20	20*		15) 15) 12	12	10	10	S¥	USA
OCEANIA AUSTRALIA	10	12	12	15	15	30	30	30	30	30	20	╉────	20	20	20	20	20	15	15	12	12	10	10	10	∮ ₹	-
JAPAN	15	15	20	20	20	20	30	30	30	20	20	20	20	20	20	20	20	20	20	20	20	20	15	15	12	

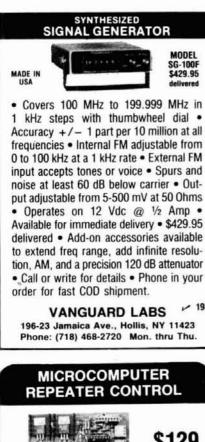The italicized numbers signify the bands to try during the transition and early morning hours, while the standard type provides MUF during "normal" hours. *Look at next **higher** band for possible openings.



r 198




Want to Advertise in HAM RADIO?

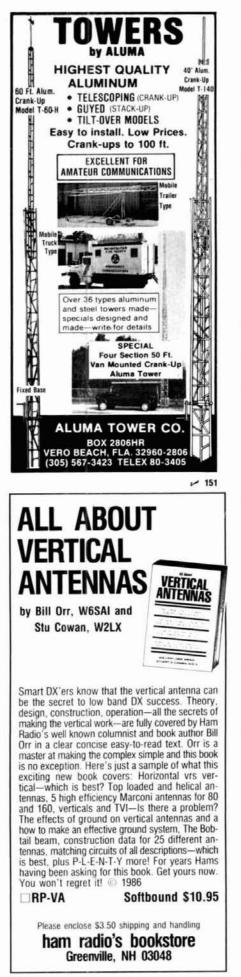(612) 484-9176 7pm-10pm evenings CALL OR WRITE FOR FREE CATALOG AND SPECIFICATIONS

VISA

Call Rally Dennis (603) 878-1441 today for more information




tween May 4 and 6, with rates of 10 to 25 per hour for the northern and southern hemispheres, respectively.

band-by-band summary

Ten, twelve, fifteen, and twenty meters will support DX propagation from most areas of the world during daylight and into the evening, with long-skip out to 2000 miles (3500 km) per hop. Signals on the upper three bands arrive mainly from the southern countries and occur near noontime. Sporadic-E short-skip will be available on some days toward the end of the month near local noon. The direction of propagation will follow the sun across the sky: morning to the east, south at midday, and west in the evening.

Thirty, forty, eighty, and one-sixty meters are the nighttime DXers' bands. Because of low solar flux in midmonth, daytime DX - particularly in the early mornings - may be worthwhile. The direction of propagation follows the darkness path across the sky: evening to the east, south and north around midnight, and toward the west in the predawn hours. Distances will decrease to 1000 miles (1600 km) generally, for skip on these bands. Sporadic-E openings will be observed most frequently around sunrise and sunset toward the end of the month. ham radio



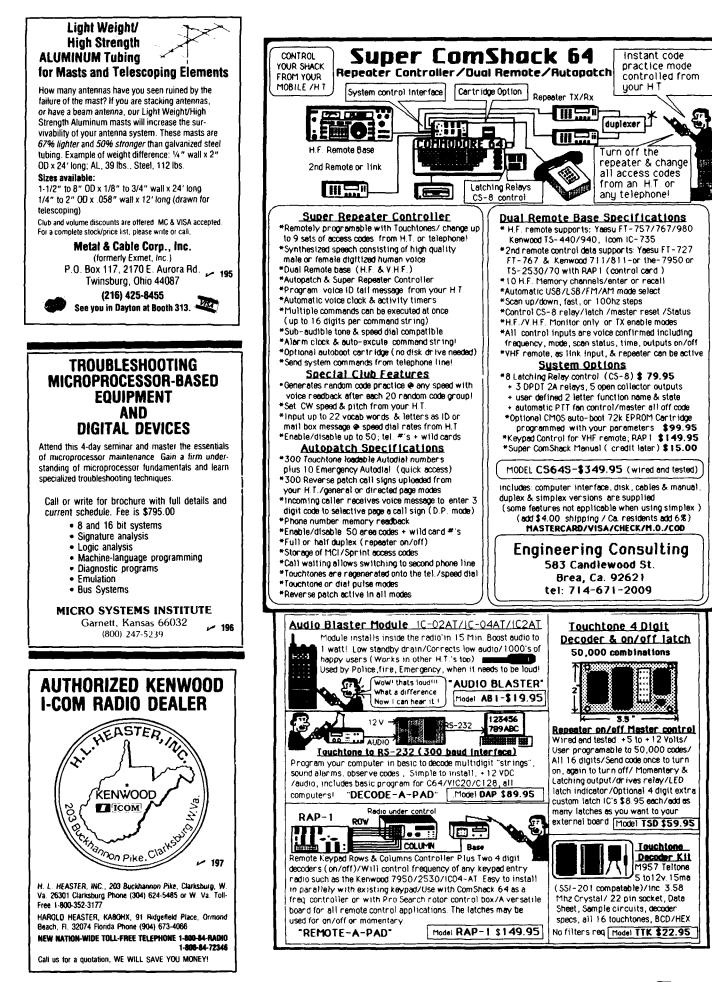

California

JUN'S ELECTRONICS 3919 SEPULVEDA BLVD. CULVER CITY, CA 90230 213-390-8003 800-882-1343 Trades Habla Espanol

Colorado

COLORADO COMM CENTER 525 EAST 70th AVE. SUITE ONE WEST DENVER, CO 80229 (303) 288-7373 (800) 227-7373 Stocking all major lines Kenwood Yaesu, Encomm, ICOM

Connecticut

HATRY ELECTRONICS 500 LEDYARD ST. (SOUTH) HARTFORD, CT 06114 203-527-1881 Call today. Friendly one-stop shopping at prices you can afford.

Delaware

AMATEUR & ADVANCED COMMUNI-CATIONS 3208 CONCORD PIKE WILMINGTON, DE 19803 (302) 478-2757 Delaware's Friendliest Ham Store.

DELAWARE AMATEUR SUPPLY

71 MEADOW ROAD NEW CASTLE, DE 19720 302-328-7728 800-441-7008 Icom, Ten-Tec, Microlog, Yaesu, Kenwood, Santec, KDK, and more. One mile off I-95, no sales tax.

Florida

AMATEUR ELECTRONIC SUPPLY 1898 DREW STREET CLEARWATER, FL 33575 813-461-4267 Clearwater Branch West Coast's only full service Amateur Radio Store. Hours M-F 9-5:30, Sat. 9-3

Ham Radio's guide to help you find your local

AMATEUR ELECTRONIC SUPPLY 621 COMMONWEALTH AVE. ORLANDO, FL 32803 305-894-3238 Fla. Wats: 1 (800) 432-9424 Outside Fla: 1 (800) 327-1917 Hours M-F 9-5:30, Sat. 9-3

Georgia

DOC'S COMMUNICATIONS 702 CHICKAMAUGA AVENUE ROSSVILLE, GA 30741 (404) 866-2302 / 861-5610 ICOM, Yaesu, Kenwood, Bird... 9AM-5:30PM We service what we sell.

Hawaii

HONOLULU ELECTRONICS 819 KEEAUMOKU STREET HONOLULU, HI 96814 (808) 949-5564 Kenwood, ICOM, Yaesu, Hy-Gain, Cushcraft, AEA, KLM, Tri-Ex Towers, Fluke, Belden, Astron, etc.

Idaho

ROSS DISTRIBUTING COMPANY 78 SOUTH STATE STREET PRESTON, ID 83263 (208) 852-0830 M 9-2; T-F 9-6; S 9-2 Stock All Major Brands Over 7000 Ham Related Items on Hand

Illinois

ERICKSON COMMUNICATIONS, INC. 5456 N. MILWAUKEE AVE. CHICAGO, IL 60630 312-631-5181 Hours: 9:30-5:30 Mon, Tu, Wed & Fri; 9:30-8:00 Thurs; 9:00-3:00 Sat.

Indiana

THE HAM STATION 220 N. FULTON AVE. EVANSVILLE, IN 47710 812-422-0231 Discount prices on Ten-Tec, Cubic, Hy-Gain, MFJ, Azden, Kantronics, Santec and others. SASE for New & Used Equipment List.

Maryland

MARYLAND RADIO CENTER 8576 LAURELDALE DRIVE LAUREL, MD 20707 301-725-1212 Kenwood, Ten-Tec, Alinco, Azden. Full service dealer. T-F 10-7 SAT 9-5

Massachusetts

TEL-COM, INC. 675 GREAT ROAD, RTE. 119 LITTLETON, MA 01460 617-486-3400 617-486-3040 The Ham Store of New England You Can Rely On.

Michigan

ENCON PHOTOVOLTAICS Complete Photovoltaic Systems 27600 Schoolcraft Rd. Livonia, Michigan 48150 313-523-1850 Amateur Radio, Repeaters, Satellite, Computer applications. Call Paul WD8AHO

Minnesota

TNT RADIO SALES 4124 WEST BROADWAY ROBBINSDALE, MN 55422 (MPLS/ST. PAUL) TOLL FREE: (800) 328-0250 In Minn: (612) 535-5050 M-F 9 AM-6 PM Sat 9 AM-5 PM Ameritron, Bencher, Butternut, ICOM, Kenwood

Missouri

MISSOURI RADIO CENTER 102 NW BUSINESS PARK LANE KANSAS CITY, MO 64150 (800) 821-7323 Missouri: (816) 741-8118 ICOM, Kenwood, Yaesu Same day service, low prices.

Nevada

AMATEUR ELECTRONIC SUPPLY 1072 N. RANCHO DRIVE LAS VEGAS, NV 89106 702-647-3114 Dale Porray "Squeak," AD7K Outside Nev: 1 (800) 634-6227 Hours M-F 9-5:30, Sat. 9-3

Dealers: YOU SHOULD BE HERE TOO! Contact Ham Radio now for complete details.

Amateur Radio Dealer

New Hampshire

RIVENDELL ELECTRONICS 8 LONDONDERRY ROAD DERRY, N. H. 03038 603-434-5371 Hours M-S 10-5; THURS 10-9 **Closed Sun/Holidays**

New Jersey

ABARIS SYSTEMS

276 ORIENTAL PLACE LYNDHURST, NJ 07071 201-939-0015 Don WB2GPU Azden, Larsen, KLM, Mirage, Newmar, Vocom, W1JC, many others. M-F 10 am-9 pm SAT 9 am-7 pm VISA/MC

KJI ELECTRONICS

66 SKYTOP ROAD CEDAR GROVE, NJ 07009 (301) 239-4389 Gene K2KJI Maryann K2RVH Distributor of: KLM, Mirage, ICOM, Larsen, Lunar, Astron. Wholesale - retail.

QEP's

110-4 ROUTE 10 EAST HANOVER, N. J. 07936 201-887-6424 In N.J. 1-800-USA-9913 **Bill KA2QEP** Jim N2GKW VISA/Mastercard **Belden Coaxial Cable** Amphenol Connectors Hours: 9:30 am-7:00 pm

New York

BARRY ELECTRONICS 512 BROADWAY NEW YORK, NY 10012 212-925-7000 New York City's Largest Full Service Ham and Commercial Radio Store.

VHF COMMUNICATIONS 915 NORTH MAIN STREET JAMESTOWN, NY 14701 716-664-6345 Call after 7 PM and save! Supplying all of your Amateur needs. Featuring ICOM "The World System." Western New York's finest Amateur dealer.

North Carolina

F & M ELECTRONICS 3520 Rockingham Road Greensboro, NC 27407 1-919-299-3437 9AM to 7PM Closed Monday ICOM our specialty - Sales & Service

Ohio

AMATEUR ELECTRONIC SUPPLY 28940 EUCLID AVE. WICKLIFFE, OH44092(Cleveland Area) 216-585-7388 Ohio Wats: 1 (800) 362-0290 Outside Ohio: 1 (800) 321-3594 Hours M-F 9-5:30, Sat. 9-3

DEBCO ELECTRONICS, INC.

3931 EDWARDS RD. CINCINNATI, OHIO 45209 (513) 531-4499 Mon-Sat 10AM-9PM Sun 12-6PM We buy and sell all types of electronic parts.

UNIVERSAL AMATEUR RADIO, INC. 1280 AIDA DRIVE **REYNOLDSBURG (COLUMBUS), OH** 43068

614-866-4267 Featuring Kenwood, Yaesu, Icom, and other fine gear. Factory authorized sales and service. Shortwave specialists. Near I-270 and airport.

Pennsylvania

HAMTRONICS, **DIV. OF TREVOSE ELECTRONICS** 4033 BROWNSVILLE ROAD TREVOSE, PA 19047 215-357-1400 Same Location for over 30 Years

LaRUE ELECTRONICS 1112 GRANDVIEW STREET SCRANTON, PENNSYLVANIA 18509 717-343-2124 ICOM, Bird, Cushcraft, Beckman, Larsen, Amphenol, Astron, Belden, Antenna Specialists, W2AU/W2VS, Tokyo Hy-Power Labs, WELZ, Daiwa, Sony, Saxton, Vibroplex, Weller.

Tennessee

MEMPHIS AMATEUR ELECTRONICS 1465 WELLS STATION ROAD MEMPHIS, TN 38108 Call Toll Free: 1-800-238-6168 M-F 9-5: Sat 9-12 Kenwood, ICOM, Ten-Tec, Cushcraft, Hv-Gain, Hustler, Larsen, AEA, Mirage, Ameritron, etc.

Texas

MADISON ELECTRONICS SUPPLY 3621 FANNIN HOUSTON, TX 77004 713-520-7300 Christmas?? Now??

KENNEDY ASSOCIATES AMATEUR RADIO DIVISION 5707A MOBUD SAN ANTONIO, TX 78238 Stocking all major lines. San Antonio's Ham Store. Great Prices - Great Service, Factory authorized sales and service

Hours: M-F 10-6; SAT 9-3

MISSION COMMUNICATIONS 11903 ALEIF CLODINE SUITE 500 (CORNER HARWIN & KIRKWOOD) HOUSTON, TEXAS 77082 (713) 879-7764 Now in Southwest Houston-full line of equipment. All the essentials and extras for the "ham."

Wisconsin

AMATEUR ELECTRONIC SUPPLY 4828 W. FOND DU LAC AVE. MILWAUKEE, WI 53216 414-442-4200 Wisc. Wats: 1 (800) 242-5195 Outside Wisc: 1 (800) 558-0411 M-F 9-5:30 Sat 9-3

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria Karin Ueber Posttach 2454 D-7850 Loerrach West Germany Ham Radio Belgium Sterephouse

Canada Canada Send orders to Ham Radio Magazine Greenville, NH 03048 USA Prices in Canadian funds 1 yr. \$41.85, 2 yrs \$74.25 3 yrs. \$99.90

Brusselsesteenweg 416 B-9218 Gent Belgium

Ham Radio Holland Postbus 413 NL-7800 Ar Emmen Holland

Ham Radio Europe Box 2084 S-194 02 Upplands Vasby Sweden

Ham Radio France SM Electronic 20 bis, Ave des Clarions F-89000 Auxerre

Ham Radio Germany Karin Ueber Postfach 2454 D-7850 Loerrach West Germany

Ham Radio Italy Via Maniago 15 I-20134 Milano

Ham Radio Switzerland Karin Ueber Postlach 2454 D-7850 Loerrach West Germany

Ham Radio England c/o R.S.G.B. Alma House Cranborne Road Potters Bar Hens EN6 3JW England



RATES Noncommercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing) on a space available basis only. Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (**not** all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N. H. 03048.

HOT/NEW PACKET PROGRAMS FOR YOUR IBM PC. Several telecommunications programs to choose from, especially written to interface your packet controller with your PC or compatible/clone. Features like Full Screen, Line Screen editing, Split Screens, ASCII, Binary, X-Modern or user defined file transfers, DOS shell, Macro Keys, Command Files, many types of time/date/oper. ID. Multi-page brochures explain them all. Software Support. Write for new information and pricing. KALT & ASSOCIATES, 2440 E. Tudor Rd, Suite 138, Anchorage, AK 99507. (907) 248-0133. Charge Cards accepted.

HOMEBREW PROJECTS LIST SASE. WB2EUF, Box 708, East Hampton, NY 11937.

FOR SALE: Tower, Rotator, Antenna Package – Tri-Ex W-67 Tower, motorized extension from 22' (nested) to 67' plus mast height. Hand winch operated tilt-over feature. CDE Ham III Rotator. Wilson DB-33 (10/15 meter beam). Cushcraft 20 meter beam. Very good condition. Package price \$1250 firm. WA1USO, Fred Moller, Old Fitzwilliam Rd, Jaffrey, NH 03452. (603) 532-7635.

PERFORATED ENCLOSURES 17 x 8.5 x 7.5 deep with grey paint and 17 x 8.5 x 11 deep with iridite finish. Unpainted blank front panel. Approximately 50 each. \$10 and \$15 respectively. Quantity discount available. Don Reed, K0IFO, 911 North Lynn, Independence, MO 64050. (816) 252-9436

DISCOVER "THE RADIO WORKS". See what we are doing with high performance HF and VHF antennas, parts, and accessories. Unusual 48 page discount catalog. 22 cents SASE. The RADIO WORKS, HRAPR, Box 6159, Portsmouth, VA 23703 (804) 484-0140.

R-390A RECEIVER: \$195 check; \$115 reparable. Parts, tubes, sections. Info SASE. Mint military-spec pull-out 12AT7, 6AG5: \$15/dozen. CPRC-26 six meter transceiver (see Ham Radio, March 1985) \$17.50 apiece. \$32.50 pair (add \$4.50/unit shipping). Baytronics, Box 591, Sandusky, OH 44870. (419) 627-0460 evenings.

VHS VIDEO CASSETTES \$29.50 total price for a box of 10 delivered anywhere in continental U.S. Call for 24-hour order information. KB6MT (714) 990-9622.

WANTED TO BUY zip code and directory published before 1980 publication No. 65. Bernard Fair, 19455 Houghton, Detroit, MI 48219.

S.S.B. CRYSTAL FILTERS. 9.0 MHz, 2.2 kHz bandwidth, six pole, with data \$20.00 postpaid. OEM quantity available. ICL7117 D.V.M. I.C.'s direct drive 3-1/2 digit LED same as 7107 plus hold, with data; \$6.00. 2/\$10.00 postpaid. Dentron Scout C.A.P. transceiver, 4 MHz, 100 watts, new; \$250.00. A.C.P.S. \$75.00 postpaid. George Misic, 14481 Watt, Novelty, Ohio 44072.

DC to 400 MHz Spectrum Analyzer Kit. For info SASE to: A & A ENGINEERING, 2521 W. La Palma Ave, #K, Anaheim, CA 92801. (714) 952-2114.

MOTOROLA C-34MSY MOTRAN 402-420 UHF Base Stations. Sold by individual strips only: RX, TX, TCN-10-58A control chassis w/squelch gate and station logic cards, and TLN-8204A meter panels. No channel elements. \$25,00 ea strip including postage, add \$3,00 for Air Parcel Post. Also 2 C.34RCB MICOR base stations---make offer. Greg Westrup, WA9BWZ, 202 C Avenue, Apt D, Kodiak, AK 99615. (907) 487-2476.

FOR SALE: TR-7950, 25 watt 2 meter transceiver with mobile mount. \$275.00 FOB. (401) 789-1817. W1CPI.

LEARN MORSE CODE IN 1 HOUR. Amazing new easy technique. Moneyback guarantee. \$10. Bahr, 2549H Temple, Palmbay, FL 32905.

SUPERFAST MORSE CODE SUPEREASY. Subliminal cassette. Moneyback guarantee. \$10. Bahr, 2549H Temple, Palmbay, FL 32905.

ANALOG AND RF CONSULTING for the San Francisco Bay area. James Long, Ph.D N6YB (408) 733-8329.

TEN-TEC now shipping new-boxed USA made latest 1987 factory models Corsair II, Century 22, Argosy II transceivers. Titan linear amplifier 229A 2kw antenna tuner plus accessories, antenna. For the best Ten-Tec deal write or phone Bill Slep (704) 524-7519, SLEP ELECTRONICS COMPANY, Highway 441, Otto, NC 28763.

WANTED Schematic for Bearcat 100 Electra, Model BC-100 Scanner. Please contact Ralph E. Smith, 857 Rougemont, St. Foy, Quebec City, Canada.

HEATH Deluxe antenna tuner Model SA2060 – a beauty – best offer, (401) 789-1817 FOB.

CHASSIS, CABINET KITS. SASE. K3IWK, 5120 Harmony Grove Road, Dover, PA 17315.

COLLINS KWM-380. Fully updated. Excellent condition. Full service manual. Write or call. W3IRE, 9436 Howes Road, Dunkirk, MD 20754. (301) 257-3041.

BACK ISSUES OF HAM RADIO Magazine from March 1968 to June 1974. Complete your collection. Individual issues \$4.00 each. KX9P (319) 377-3563.

IBM/APPLE COMPUTER program "Hamlog". 18 modules logs auto-sorts 7-band WAS/DXCC, Full feature. Also CP/M. Apple \$19.95, IBM \$24.95. HR-KA1AWH, PB 2015, Peabody, MA 01960.

BOUND VOLUMES CQ 1958/69, 73 1963/72, Audio 1957/68, Radio Electronics 1950/69, Radio News (Electronics World) 1950/69, Electronics 1953/73, 55 per year plus shipping. Also some later individual issues. K4QQK, 307 Old Fort, Tullahoma, TN 37388.

IBM-PC SOFTWARE: CW Keyer, COM sends CW from RS232 port, any speed, using type ahead buffer, memory or disk. \$29.50. ELEC. EXE solves most common electronic equations, \$19.50. Bill Feldmann, 6677 Charing St, Simi, Calif. 93063, or SASE for details.

TELEVISION SETS made before 1946, early TV parts, literature wanted for substantial cash. Especially interested in "mirror in the lid" and spinning disc tv's. Finder's fee paid for leads. Arnold Chase, 9 Rushleigh Road, West Hartford, Conn. 06117. (203) 521-5280.

WANTED: EIMAC 8873 tube for Heath SB-230. Please contact G2DRT, F.S.G. Rose, 84 Cock Lane, High Wycombe, Bucks HP 13 7 EA England.

ENGINEERS request free catalog of Electronics Software. Circuit analysis, filter design, graphics, etc. BV Engineering, 2200 Business Way, Suite 207, Riverside, CA 92501 (714) 781-0252.

NJ-NJ-NJ-NJ-NJ-NJ-NJ-A Full-Service Ham-SWL-CB-Scanner store in NJ. Discount Grand Opening Prices. Top performing radio systems for every budget. New 10 meter and VHF/UHF rigs. ARRL, Amphenol, Astatic, Astron, Azden, BeW, Bilal Belden 9913, Butternut, Clear Channel, KLM, Larsen, MFJ, Mirage, Mil Spec Cables, much more. Open M-F 10 AM-9PM. Sat 10 AM-7 PM. Buy and sell used gear and have qualified repair facility. ABARIS SYSTEMS, 276 Oriental PI, Lyndhurst, NJ 07071 (201) 939-0015.

LO COST Sensitive-Selective HF receiver system. Ideal/1st station set. Enhanced Novice 10/15/40/80m coverage. Send 2 stamps for free info. I. Megeff, KD2EF, 729 Lori Drive #101, Palm Springs, FL 33461.

HOBBY, EDUCATIONAL, INDUSTRIAL PRODUCTS. 70 kits. Amplifier, FM transistor, VU meter, door bell, alarm system, power supply. Send \$3.00 to HOBBY ELECTRONIC, PO Box 1339, Claremont, NH 03743 or call (603) 543-0033.

COLLECTORS: Have Karl Pierson KP-81 communications receiver for sale. Complete system- receiver, speaker cabinet and book. Open to offers. Cal, KL7HEM, 10300 Silver Knolls, Reno, NV 89506.

IBM-PC RTTY/CW. New CompRtty II is the complete RTTY/CW program for IBM-PC's and compatibles. Now with larger buffers, better support for packet units, pictures, much more. Virtually any speed ASCII, BAUDOT, CW. Text entry via built-in screen editor! Adjustable split screen display. Instant mode/speed change. Hardcopy, diskcopy, break-in buffer, select calling, text file transfer, customizable full screen logging, 24 programmable 1000 character messages. Ideal for MARS and traffic handling. Requires 256k PC or AT compatible, serial port, RS 2320 CTU, \$65. Send call letters (including MARS) with order. David A. Rice, KC2HO, 25 Village View Bluff, Ballston Lake, NY 12019. TRS80 4P/KANTRONICS UTU RTTY. Split-screen, 10 user keys, file transfer. Runs in Mod 4 (80 char) mode. \$30 to COMMPRO RTTY, c/o KB6IC, 3711 Gayle Avenue, Omaha, NE 68123.

COMPUTERS COMMODORE 64 and XT repair. ABS (201) 758-6673.

CODE PROGRAMS. Apple/C-64. 31 modes, graphics, menus, wordprocessor, etc. LARESCO, POB 2018, 1200 Ring Road, Calumet City, IL 60409. (312) 891-3279.

SOLAR ELECTRIC PANELS and System Components. 1st quality for home or repeaters. Lowest prices in country. KA8DSS, RADIANT DISTRIBUTORS, 3900 Dursum, Ada, MI 43301. (616) 874-8899.

WA9GFR RF SOFTWARE \$15.00 disk contains HF/VHF/UHF/LBAND propagation and Smith Chart impedance matching programs. Specify Commodore-64 or MS-DOS BASIC. Lynn Gerig, 6417 Morgan RD, Monroeville, IN 46773.

REMEMBER TROLLEY CARS? Trolley Treasures: The Wartime Years in New Jersey (1939-1947), a 4-volume photodocumentary history, includes 1600 unpublished, original photographs plus extensive historical notes. Volume 1, The Compromise Roof Cars of Public Service Coordinated Transpart, ready now. SASE for details. To order, contact Trolley Themes, A.W. Mankoff, 2237-3 Woodside Lane, Sacramento, CA 95825. (\$14.95 plus \$1.50 SGH).

UHF PARTS. GaAs Fets, MMICs, trimmers, chip caps, teflon pcb, and other builder parts. SASE brings list. MICROWAVE COMPONENTS, 11216 Cape Cod, Taylor, MI 48180.

\$\$\$\$\$\$SUPER SAVINGS on electronic parts, components, supplies and computer accessories. Free 40-page catalog for SASE. Get on our mailing list. BCD ELECTRO, PO Box 830119, Richardson, TX 75083 or call (214) 690-1102.

SHOW IT IN STYLE Full color OSL's by Smith Printing. From your prints/slides. Sample packet. SASE. 20420 Calhaven Drive, Saugus, CA 91350 (805) 251-7211.

WANTED: For Drake 4C the noise blanker 4NB (dead or alive). H. Schroefer, Dorfstr. 14, 3131 Gollau/Luechow, West Germany.

ANTIQUE RADIOS, schematics, tubes and literature. Send SASE to VRS (HR), 376 Cilley Rd, Manchester, NH 03103 for large list.

HAM MONITOR SCOPE Millen 90932 \$85, audio signal generator HP200-CD \$125, Precision E-200-C AM/FM signal generator \$45, Yaesu FRG-7 general coverage receiver \$125, Johnson phone patch \$25, trade for TR-9000. K6KZT, 2255 Alexander, Los Osos, CA 93402

YAESU OWNERS: Hundreds of modifications and improvements for your rig. Select the best from fourteen years of genuine top-rated Fox-Tango Newsletters by using our new 32-page Cumulative Index. Only \$5 postpaid (cash or check) with \$4 Rebate Certificate creditable toward Newsletter purchases. Includes famous Fox-Tango Filter and Accessories Lists. Milt Lowens, N4ML (Editor). Box 15944, W. Palm Beach, FL 33416. Telephone (305) 683-9587.

RTTY JOURNAL—Now in our 35th year. Join the circle of RTTY friends from all over the world. Year's subscription to RTTY JOURNAL, \$10.00, foreign \$15.00. Send to: RTTY JOUR-NAL, 9085 La Casita Ave., Fountain Valley, CA 92708.

IMRA International Mission Radio Association helps missionaries. Equipment Ioaned. Weekday net, 14.280 MHz, 2-3 PM Eastern. Eight hundred Amateurs in 40 countries. Brother Frey, 1 Pryer Manor Road, Larchmont, New York 10538.

RUBBER STAMPS: 3 lines \$4.50 PPD. Send check or MO to G.L. Pierce, 5521 Birkdale Way, San Diego, CA 92117. SASE brings information.

ELECTRON TUBES: Receiving, transmitting, microwave... all types available. Large stock. Next day delivery, most cases. DAILY ELECTRONICS, PO Box 5029, Compton, CA 90224. (213) 774-1255.

CUSTOM MADE EMBROIDERED PATCHES. Any size, shape, colors. Five patch minimum. Free sample, prices and ordering information. HEIN SPECIALTIES, Inc., Dept 301, 4202 N. Drake, Chicago, IL 60618.

RECONDITIONED TEST EQUIPMENT \$1.25 for catalog. Walter, 2697 Nickel, San Pablo, CA 94806.

COMING EVENTS Activities — "Places to go . . . "

SPECIAL REQUEST TO ALL AMATEUR RADIO PUBLICI-TY COORDINATORS: Please indicate in your announcements whether or not your Hamfest location, classes, exams, meetings, flea markets, etc, are wheelchair accessible. This information would be greatly appreciated by our brother/sister hams with limited physical ability.

MASSACHUSETTS: April 19. Spring Flea at MIT. Sponsored by the MIT Electronics Research Society and W1XM/R. 10-4 PM. Albany and Main Streets, Cambridge. Buyers admission \$1.50. Sellers \$5. per space. Talk in on 146.52, 449.2 W1XM/R. NEW YORK: June 14. The Hall of Science ARC Hamfest, New NEW YORK: June 14. The Hail of Science ARC Hamilest, New York Hall of Science parking lot, Flushing Meadow Park, 47-01-111 Street, Queens. 9 AM to 3 PM. Donations—buyers \$4,00; seliens \$6,00 per space. Taik in on 144.300 simplex link 223.600 repeat and 445.225 repeat. For information call Steve Greenbaum, WB2KDG (718) 898-5599 or Arnie Schiffman, WB2YXB (718) 343-0172 evenings.

LOUISIANA: May 2 and 3° The Baton Rouge ARC Hamfest 50 and LA State Convention, Gym Armory, campus of LSU, Ba-ton Rouge. Sat 8 AM – 3 PM. Sun. 8 AM – 2 PM. Free admis-sion. Forums, ARRL speakers, Advanced swap tables reservations accepted. Dealers, tours, VE exams both days 9 AM. SASE, 610, check for \$4.00 payable to ARRL/VEC to Ge-orge Perry, W5LVX, 17424 Lady Constance, Greenwell Springs, LA 70739. Talk in on 146.19/79. For more info SASE to Rick Pourciau, NV5A, 879 Castle Kirk Dr, Baton Rouge, LA 70808. There will be Cajun food and entertainment Saturday nite. Come nass a nood time! pass a good time!

PENNSYLVANIA: May 17. The Warminster ARC's 13th annu-al Hamfest, Middletown Grange Fairgrounds, Penns Park Rd, Wrightstown. Gates open 7 AM. 6 AM for Vendors. Donation \$3.00. Non-hams and kids free. 8' indoor tables/power \$5.00 by pre-registration only. Unlimited outdoor 8' space \$5.00. Talk in on 147.69/09 and 146.52. For info and pre-registration con-tact Frank Charlton, KA3FBP, 1479 Kingsley Drive, Warminster, PA 18974. (215) 675-2549. PENNSYLVANIA: May 17. The Warminster ARC's 13th annu-

MARYLAND: May 24. Maryland FM Association's annual Ham-fest, Howard County Fairgrounds, West Friendship, 30 miles west of Baltimore. Gates open 8 Am to 3 PM. Advance inside tables \$7.00. At the door \$10. Donation \$3. Talk in on 146.16/76, 222.16/223.76 or 449.1/444.1 MHz. For tables or information: Jim Clifford, N3FBV, 7461 Terry Street, Ft. Meade, MD 20755. (201674.4752) (301)674-4752

COLORADO: May 16. Pikes Peak Radio Amateur Association 1987 Swapfest, Rustic Hills Mall, Palmer Park and Academy Blvd, Colorado Springs, 8:30 AM. Free admission. Tables \$8.00 advance; \$10.00 at door. VE testing. Talk in on 146.37/97. For information or reservations: AI, NOCMW (303) 4731660 or write PPRAA Swapfest, POB 1652, Colorado Springs, CO 80935.

ARIZONA: May 1-3. The Cochise Amateru Radio Association (CARA) will hold its 1987 Hamfest, club training facility, South Moson Road, Sierra Vista. Free tailgating. Talk in on 14y.52 or 146.16/.76. For information: Don Morgain, W7ACI, (602) 458-5293 or CARA, POB 1855, Sierra Vista, AZ 85636.

MISSOURI: May 17. The Western Illinois ARC will hold its 2nd annual Tri-State Swapfest, Haerr Field, Taylor, Tailgate flea mar-ket, aircraft exhibits, plane rides and VEC exams. Flea market setup 8 AM. General admission:9 AM. Talk in on 147.03 repeater. For information: Western Illinois ARC, POB 3132, Quincy, IL 62301

NEW HAMPSHIRE: May 15-17. The 13th annual Eastern VHF/UHF Conference, Rivier College, Nashua. For information contact Lewis D. Collins, W1GXT, Publicity Chairman, Eastern VHF/UHF/SHF conference, 10 Marshall Terrace, Wayland, MA 01778. (617) 358-2854 (6 to 10 PM EST)

NEW YORK: May 17. LIMARC will sponsor the ARRL Long Is-land Hamfair, New York Institute of Technology, Rt 25A, North-ern Blvd, Old Westbury, NY, Sellers 7:30 AM. Buyers 9 AM. Outdoor tailgating. Sellers car space \$5.00, General admission \$3.00, Non-hams and kids admitted free. Talk in on 146.85. For information call Hank Wener, WB2ALW (516) 484-4322 eveptions evenings.

PENNSYLVANIA: June 7. The 33rd annual Breeze Shooters Hamfest, White Swan Amusement Park, Rt 60, near Pittsburgh International Airport. Free admission and Flee Market, family amusement park, 9 Am to 4 PM. For information and table reser-vations Bud Faulhaber, N3DOS, 1059 Balmoral Drive, Pittsburgh, National Alaba and Faulhaber, N3DOS, 1059 Balmoral Drive, Pittsburgh, PA 15237 (412) 366-5097.

OKLAHOMA: May 15-17. Green Country Hamfest, sponsored by the Broken Arrow and Tulsa ARCs, Vo. Tech SE Campus, 4600 S. Olive, Broken Arrow. Friday night mixer 6-10 PM at the Travelodge. Flea market and dealers open 9-5 Saturday and 9-01 Sunday. ARRL FCC exams. Children's room. Non-ham pro-grams. Family BBQ dinner. For information contact Ron gamel, NSWX, (918) 663-0385 or write Green CountryHamfest, POB 4970, Tulsa, OK 74159.

MICHIGAN: May 16. Teh Wexaukee ARA's 27th annual Swap Shop, Wexford civic Arena, US 131 and 13th Street, Cadillac. 9 Am to 2 PM. Admission \$3.00. Reefreshments available. Talk in on 146.97. For table reservations and more info call John Crad-dock, (616) 797-5491 or write Wexaukee ARA, POB 163, Cadillac, MI 49601

OHIO: May 17. TheAthens County ARA's 8th annual Hamfest, City Recreation Center, East State Street, Athens. 8 AM to 3 PM. Admission \$4.00. License exams. Send Form 610 and \$4.35 check payable to ARRI/VEC to John Cornwell, NC8V, 101 Coventry Lane, Athens, OH 45701. Free paved outdoor flea mar-ket space. Bring your own tables. No reservations. Indoor space by advance registration. Contact Wall Jones, N8DDL, 17 Berk-ley Dr, Athens, OH 45701 (614) 593-7871. For general informa-tion Carl Denbow, KA8JXG, 63 Morris Ave, Athens, OH 45701.

PENNSYLVANIA: May 24. The Ephrata Area Repeater Socie-ty's 2nd annual Hamfest. Walk in VEC exams. Packet and ATV demos.

MICHIGAN: May 30. The Central Michigan Amateur Repeater Association (CMARA) 13th annual Hamfest, Midland Comuni-ty Center, Midland. 8 AM to 1 PM. Admission \$3. Food availa-ble. Dealers welcome. Packet radio, new/used Amateur electronics and equipment. License exams. Talk in on 147.00/60 Midland. For information CMARA Hamfest, POB 67, Midland, MI 48640. Please SASE. (517) 631-9228 evenings and weekends.

ILLINOIS: May 17. The Knox County Radio Club's annual Ham-Rest, Knox County Failure Knox County hadro Gub Sanhual halm fest, Knox County Failurgrounds, Knoxville, Li, Gates open 7 AM. Building open 8 AM. Free flea market spaces available. ARRL/VE testing. For table reservations, pre-registration for testing and advanced tickets write Keith L. Watson, WB9KHL, 119 South Cherry Street #3, Galesburg, IL 61401-4527 or call (309) 342-3885 evenings.

NEW YORK: May 30. First Skaneateles Ham and Computer Fest, Allyn Arena, Jordan and Austin Streets. 8 AM to 5 PM. Vendors, ham gear and computer displays, exhibits. VE license exams. For reservations, info, motel list, contact Hank Bryant (315) 685-7658 or write Skaneateles Hamfest, 49 Elizabeth Street, Skaneateles, NY 13152.

ILLINOIS: May 17. The Chicago Amateur Radio Club's annual Mini-Hamfest, North Park Village, 5801 N. Pulaski, Chicago. 9 AM to 3 PM. Admission \$1. Half table \$3. Full table \$5. Admits one seller. For info call 545-3622.

NEW JERSEY: May 9. The Cherryville Repeater Association's annual Hamfest, Hunterdon Central High School, Flemington. 8 AM to 4 PM. Indoor tables plus tailgating. FCC exams, forums displays and more. Talk in on 146 52, 147 975./ 375. For further information or reservations call Bill Inkrote. K2NJ (201) 788-4080 or Don Mazak, NR2H (201) 782-1114.

COLORADO: June 20. The Grand Mesa Repeater Society will hold its 8th annual Western Slope Amateur Radio and Computer Swapfest, 9 AM to 4 PM, National Guard Armory, 482-28 Road, Grand Junction. Free admission. Swap tables \$5.00 each. Indors wapfest, Amateur Radio examis, auction and refreshments. Talk in on 146;22/32 and 449:20. For tables or information SASE to Les Scott, NVOF, 2105 Yellowstone Rd, Grand Junction, CO 81503 or call (303) 242-5296.

CALIFORNIA: May 1, 2, and 3: The Fresno Amateur Radio Club will hold its 45th annual Hamfest, Fresno Airport Holiday Inn. Air conditioned dealer spaces and swap tables. FCC exams. Good programs and parking. Demonstrations and forums. Talk in on 146.34-94. For information: Glen T. Caine, Fresno ARC, PO Box 783, Fresno, CA 93712 or (209) 292-4611.

NEW YORK: May 3. The Suffolk County Radio Club's in-door/outdoor flea miarket, 8 AM to 2 PM, Republic Lodge No. 1987, 585 Broadhollow Road, Rt. 110, Melville, L.I. General ad mission \$3.00. Spouse and kids under 12 free. Indoor tables \$10. each. Outdoor spaces \$7.00 each. Includes one free admission. Talk in on 144.61/145.21 and 146.52 simplex. For information: Bill Sullivan, N2ETG (516) 689-9871 evenings.

NEW JERSEY: May 3. The Tri-County Radio Association's an-nual Indoor Hamfest / Flea Market, Passaic Township Commu-nity Center, Stirling. 9 AM to 3 PM. Donations 43.00. Tables \$8.00; w/power \$10.00. Reserved tailgating. Refreshments. Talk in on 147.855 / 255, 146.52 and 444.975/449.975. For informa-tion: Dick Franklin, W2EUF, POB 182, Westfield, NJ 07090. (201) 232-5955.

ARKANSAS: May 2. The Northwest Arkansas ARC will hold its 7th annual Hamfest, Rogers Youth Center, 315 West Olive Street, Rogers 8 AM to 4 PM. Doors open 6 AM for exhibi-tors. General admission and parking free. Nearby recreational areas and parking for RV's and campers. Talk in on 16/76 or 03/63. For information: Roy Milliene, AFSW, 2014 S. 16th Street, Rogers, AR 72756 (501) 636-6750.

VIRGINIA: May 3. The Lynchburg ARC will hold its annual Swapfest, Brookville High School grounds, Route 460 West, just outside Lynchburg, Rain or shine. Starts 9 AM. Admission \$1.00. Tailgaters pay general admission plus \$2.00. VE exams beginning 1 PM. Please pre-register. For more information write Lynchburg ARC, PO Box 4242, Lynchburg, VA 24502.

RHODE ISLAND: May 16. The RI Amateur FM Repeater Serv-ice will hold their annual Spring Flea Market and Auction, Ameri-can Legion Fairmount Post 85, 870 River Street, Woonsocket, Flea market opens 9 AM and spaces are \$5.00 each. Auction from noon to 5 PM. Free admission. Food and beverages avail-able. Talk in on 34/94 and 52 simplex. For information: Rick Fair-weather, K1KYI, Box 591, Harrisville, RI 02830 or call (401) 56:8-0566, 7-9 PM.

CONNECTICUT: May 31. The Newington Amateur Radio League will hold its fourth annual Flea Market, Newington High School, Willard Avenue, Newington. 9 AM to 2 PM. New/used ham gear, computer equipment. Admission \$2.00 at the door. Indoor tables 88:50, \$10 after May 23. Taligaters \$5. Guided tours of ARRL Hg. Amateur Radio exams. Talk in on 146.52 and W1AW/R, 144.85/145.45 and 223.24/242.48. For exam infor-mation or table reservations: Les Andrew, KA1KRP, 23 Grove St, West Hartford, CT 06110. (203) 523-0453. Please SASE.

ILLINOIS: May 17. The Kankakee Area Radio Society's annual Hamfest, Kankakee County Fairgrounds, 8 AM to 4 PM. Ad-mission \$2.50 advance; \$3.00 at the door. FCC and ARRL booths.Free flear market tables. Free parking. Talk in on 146.34/94. For information: KARS c/o Frank DalCanton, KA9FWV, RR 1, Box 361, Chebanse, JL 60922, (815) 932-6703 after 5 PM CST or (815) 937-2452 before 5 PM.

MINNESOTA: May 9. The Arrowhead Radio Amateur Club's Swapfest '87, First United Methodist Church, 230 East Skyline Parkway, Duluth. 10 AM to 3 PM. Admission \$4.00. 4' tables \$5.00. License exams 9 AM. For Amateur exams contact Eddy Lonnstrom, N9DHG, 2026 Baxter Ave, Superior, WI 54880 (715) 392:2415. General information: Ron Carlson, K0BR, 5128 Wyo-ming Street, Duluth, MN 55804 (218) 525-6860.

SOUTH CAROLINA: May 2 and 3. The Blue Ridge Amateur South CAROLINA: May 2 and 3. The Blue Ridge Anateur Radio Society's 48th annual Greenville Hamfest and Electronic Flea Market, American Legion Fairgrounds, Greenville. Satur-day 8 AM to 5 PM. Sunday 8 AM to 3 PM. Admission \$3.50 advance and \$5.00 at gate. Indoor/outdoor flea market, license exams, free parking, food. For tickets or information SASE to Blue Ridge ARA, PO Box 6751, Greenville, SC 29606. NEW HAMPSHIRE: May 9. New England's favorite — The Hoss-traders Spring Tailgate Swapfest, Deerfield Fairgrounds. Ad-mission \$2.00 per person including sellers and commercial dealers. Friday night camping at nominal fee only after 4 PM. Profits benefit Shriners' Burns Hospital. Last year's gift over \$13,500! For map, SASE to WA1IVB, RFD Box 57, West Bald-win MF (0401 win, ME 04091

PENNSYLVANIA: May 3. The Delaware County ARA is spon-soring their 8th annual Hamfest, Drexel Hill Middle School, State Road and Penn Avenue, Drexel Hill. Doors open 8 AM. Setup 7 AM. Admission \$3. Reserved indoor tables/elec. available for \$3.00 per space. License exams. Refreshments available. Talk in on 147.96/36, 224.5 and 146.52. For registration and infor-mation write Hamfest, DCARA, PO Bkox 236, Springfield, PA 19064 or call Barbara, N3DLG (215) 535-1616.

1987 "BLOSSOMLAND BLAST" Sunday, September 20, 1987. Write "BLAST" PO Box 175, St. Joseph, MI 49085.

VIRGINIA: June 7. The Ole Virginia Hams present the Annual Manassas Hamfest, Prince William County Fairgrounds. 8 AM to 4 PM. General admission \$4.00, Children under 12 free. Tail-gating \$5.00/space, Dealers, ARRL booth, CW proficiency award. Talk in on 146.37/97, 146.52. For information write: Ole Virginia Hams ARC, POB 1255, Manassa, VA 22110. John Gun-sett, KI4VP (703) 361-5255 or Gene Roberts, N4HFW (703) 361-3987 361-3983

NEW JERSEY: May 17. OBRA Annual Festival. Old Bridge Civic Center Arena, Cottrel Road and Hwy 516, Old Bridge. Sellers 6 AM \$12.00. Buyers 8 AM, \$5.00. Tailgating \$8.00. FCC ex-ams, pre-registration suggested. Walks in 9 AM. Testing 10 AM. Talk in on 7.12/7.72. For information N2DHN.

NORTH CAROLINA: May 23. The Durham FM Association's annual Hamfest, Lower rear deck South Square Mall, Durham. 8 Am to 4 PM. FCC exams, vendors and free tailgating. Talk in on 147.825/.225, WA4WTX.

MICHIGAN: June 7. The Chelsea Swap and Shop, Chelsea Fair-grounds, Chelsea. Sellers 5 AM. Buyers 8 AM to 1 PM. Dona-tion \$2.50 advance and \$3.00 at the gate. Children under 12 and non-ham spouses free. Talk in on Chelsea Repeater 146.980. For information: Robert Schantz, 416 Wilkinson St, Chelsea, MI 48118. (313) 475-1795.

WISCONSIN: May 2. The Ozaukee Radio Club will sponsor its Bith annual Cedarburg Swaptest, Circle B Recreation Center, Highway 60 and County I, Cedarburg. 8 Am to 1 PM. Admis-sion \$2.00 advance, \$3.00 at the door. 4' tables \$3.00 each, Food and refreshments available. For tickets, reservations or informa-tion SASE to 1987 ORC Swapfest, 101 E. Clay Street, Sauk-ville, WI 53080 or phone (414) 284-3271.

NEW JERSEY May 17. The Bergen County ARA is sponsoring its Spring Hamfest, Bergen Community College, 400 Paramus Road, Paramus. 8 to 4 PM. Rain or shine. Buyers free. Sellers \$5 per space, tailgate only. License exams. Talk in on 146.19/79 and .520 simplex. Forfurther information: Jim, KK2U (201) 445-2855, 444 Berkshire Rd, Ridgewood, NJ 07450.

OPERATING EVENTS

"Things to do . . .

May 2. The Louisville A.R.T.S. will operate "Run For The Roses" under the call W4CN. 2400 to 0500 May 1 and 1300 to 1700 May 2. For a commemorative certificate send QSL and 39 cents SASE to ARTS Club, W4CN, POB 7391, Louisville, KY 40207

May 9. The Laurel ARC will operate special event station W3GFS from 1400Z to 2000Z to help celebrate the 4th annual Main Street Festival in Historic Laurel, MD. SASE for 8x11 certificate. QSL to LARC, POB 1436, Laurel, MD 20707.

May 23: The Old Barney ARC os Southern Ocean County, New Jersey announces a special event Arnateur Radio operation commemorating the 75th anniversary of the start of construction of the Tuckerton Wireless Tower. 00001Z May 23 thru 2359Z May 24. For information contact Bob Schenck, N2DO. Publicity Manager, OBARC. (609) 296-0307


May 23, 24, 30. The Carroll County ARC will operate K3PZN in celebration of Carroll County's Sesquicentennial. For 8x11 cer-tificate send QSL and SASE to Carroll County ARC, POB 2099, Westminster, MD 21157.

ARMED FORCES DAY May 16 1987. In recognition of the 38th anniversary of this event, ARS W40DR aboard NAS Memphis, Millington, Tennessee will be operated by sailors and marines from 13002 to 23002. For additional information Station Custo dian, Senior Chief Petty Officer Bob Donan, KA4FAL, (901) 872.2007 872-2007

May 16. The Charleston Amateur Radio Society will operate May 16. The Charleston Amateur Hadio Society will operate Special Event Station from the deck of the aircraft carrier USS Yorktown CV-10 located in Charleston, SC. Callsign WA4USN. 10002 to 22002. For a special OSL card with photo of the ship to confirmed contacts) SASE to Special Event Station, 346 Parkdale Dr, Charleston, SC 29407.

THE FOUNDATION FOR AMATEUR RADIO, INC. plans to ITE FUNIVATION FOR AMATEUR RADIO, INC. plans to award 26 scholarships for academic year 1987-88 to assist licensed Radio Amateurs who plan to pursue a full-time course of studies beyond high school and are enrolled or have been accepted by an accredited university, college or technical school. For further information write FAR Scholarships, 6903 Rhode Is-land Avenue, College Park, MD 20740 prior to May 31, 1987.

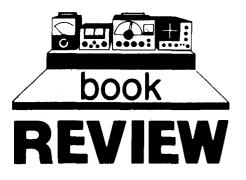ARMED FORCES DAY 1987 May 16. The 38th annual Armed Forces Day Communication Test. Traditional military-to-Amateur cross band operation and broadcast of the Secretary of Defense message are the featured highlights and include operations in CW, SSB and RTTY




the digital novice

The man who helped thousands of Amateurs Get ***Connected to Packet Radio has done it again. In The Digital Novice, author Jim Grubbs, K9EI, explains the fundamentals of digital communications with authority, clarity, simplicity, and wit.

Warning: This is a very basic book that covers, rather lightly — but in detail sufficient for most beginners — the whole range of Amateur digital communications, from what Jim calls "cavedweller digital" to spread spectrum and transmission, via packet radio, of *animated* visual images.

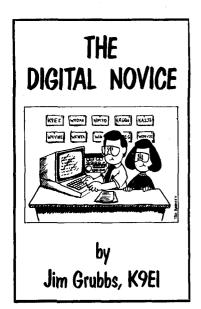Why are we recommending it to readers of ham radio with enthusiasm? Well, for one thing, we know that some readers are dyed-in-the-wool analog types to whom digital technology is something of a mystery. Others understand the technology, but want to acquire an overview of



New from QSKY, *The Digital Novice* introduces beginners – regardless of license class – to digital communications.

equipment available, with an eye toward becoming active in one digital mode or another.

But there's a better reason to read this book. There are some 80,000 Novices out there, and the new Novice enhancement regulations (which Jim spells out in comprehensive, up-to-theminute detail) will certainly bring in more. Now these people will no doubt expect you, with your higher class of license, to know *everything*. What's more, they're going to be looking to you not only to know it all, but to explain it, too in terms they can understand — or at least direct them toward appropriate sources of information.




"Cave Dweller Digital" was earliest form of digital communications.

The Digital Novice helps you answer questions like "What exactly is AMTOR?", "How is packet different from earlier digital techniques like RTTY and ASCII?", and "What interface should I buy?" without having your face turn red or getting your tongue all tied up in embarrassing knots — and without confounding the questioner. No doubt you can answer all sorts of questions about digital techniques, even roused from a deep sleep after driving home from Dayton for two days straight. But wouldn't it be convenient to just point to The Digital Novice, roll over, and go back to sleep?

This isn't another book about packet radio, by the way, or a book about computers, though there's enough about computers to form a solid basis for understanding the material. It isn't "a computer book." It is a book you can give without reservation to any interested beginner, regardless of age. Though it's written for adults, I wouldn't hesitate to give it to a bright, highly motivated eighth-grader. There's no question about it: Jim is a born communicator, a writer who knows his audience and speaks to them in language they understand, simplifying complex subjects without ever "talking down." What might cause us to be rendered essentially inarticulate (as a function of knowing either too much or too little), he explains with refreshing simplicity. As Jim points out, technically knowledgable people aren't necessarily the best "missionaries for the new technologies." Not convinced? Quick: explain spread spectrum in language a Novice can understand.

Describing equipment available, Jim names names and comments, with candor, on every piece of hardware about which Novices need to know, citing advantages and disadvantages of each. Though addresses are not included, they're all here: AEA, GLB, MFJ, Kantronics, Packeterm — and, of course, TAPR and Vancouver as well.


The text is supplemented with an ample glossary plus appendices listing the various digital codes (Morse, Baudot, AMTOR, ASCII). There's a clever little bonus at the end, too: to give readers an opportunity to check how well they've retained what they've read, Jim has included a 33-question test covering topics discussed in the book. Answers are included, plus references to page numbers where subjects covered by questions can be found. Score 80 or better (on your honor), send Jim an SASE, and — just for fun — he'll send you a certificate attesting to your status as an official "Digital Novice."

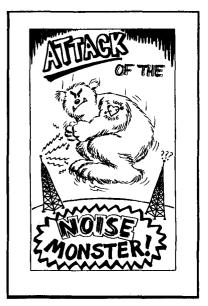

"Noise Monster" substantiates author's assertion that noise is the natural enemy of digital communications.

Ted Barney's cartoons go a long way toward lightening up *The Digital Novice*. I was pleased, too, by Jim's conscious (but never self-conscious or heavy-handed) effort to ensure gender fairness throughout the text; his deft use of pronouns may help women entering Amateur Radio through the digital modes feel more welcome.

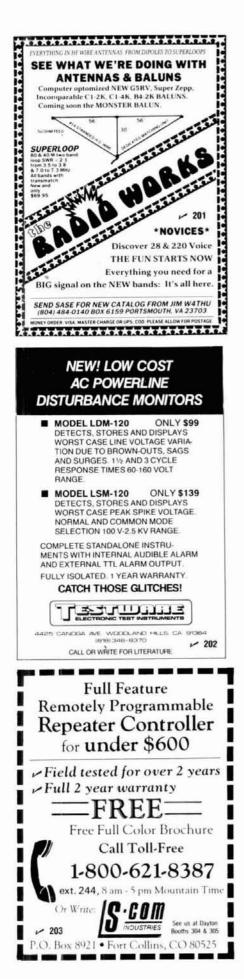The Digital Novice will be released at this year's Dayton Hamvention[®], you can meet the author at his booth (QSKY Publishing, No. 358) if you're there. You can also catch his presentation on Sunday morning at 9:30 AM. Whether or not you make it to Dayton this year, you can order your copy of *The Digital Novice* from Ham Radio's Bookstore Store for \$9.95 plus \$3.50 shipping and handling.





solid-state linear amplifier

The latest addition to the Yaesu product line — the new FL-7000 Solid State Linear Amplifier for the 160 through 15 meter bands — features an automatic antenna tuner with automatic band-switching when used with the Yaesu FT-757GX, FT-767GX, or FT-980 transceivers. Antenna switching is also automatic when using the FAS-1-4R remote antenna selector. Power output is 1200 watts, for approximately 70 watts input. A protection circuit prohibits operation with high SWR until the antenna tuner completes matching process. Thermostatically controlled dual fans run even when the amplifier is turned off, if needed for dissipation of heat.



For details, contact Yaesu U.S.A. Amateur Products Division, 17210 Edwards Road, Cerritos, California 90701.

Circle #312 on Reader Service Card.

new dual-port tnc, personal mailbox upgrade

The new KPC-4 Dual Port Communicator from Kantronics features two fully-functional VHF packet ports, digipeating on each port, VHF gateway between ports, and an RS-232 computer port. Digipeating and gateway operations occur simultaneously while you're connected on one or both ports. You can bridge two frequencies on one band and operate crossbands.

The KPC-4's RS-232/TTL terminal interfacing provides universal compatibility to all computers, including Commodores and PC compatibles. Stream switching provides for access to both radio ports, each of which supports AX.25.

Priced at \$329.00, the KPC-4 contains the popular Personal Packet Mailbox[™] feature (optional on all other Kantronics Packet Communicators), a 256K EPROM that allows you (and others) to leave and collect messages on

MU	LTI BAND	TR	AP A	NTEN	NAS
•		-8			
TRAP Model D-42 D-52 D-56 D-66	DIPOLES: 8ands 10/15/20/40 10/15/20/40/80 10/15/20/40/80 10/15/20/40/80/160	Traps 2 2 6	Longth 55' 105' 82' 163'	Price \$59.95 64.95 109.95 129.95	X
TRAP VS-41 VS-52 VS-53 VS-64	VERTICALS - ' 10/15/20/40 10/15/20/40/80 10/15/20/40/80 10/15/20/40/80/160	SLO	PERS''	* 44 95 59 95 59 95 89 95	H
	used without radials e can be buried if desire	đ	1.	Permanent or Por	table Use

ALL TRAP ANTENNAS are Ready to use - Factory assembled -Commercial Quality -Handle full power - Comes complete with: Deluxe Traps, Deluxe center connector, 14 ga Stranded CopperWeld ant, wire and End Insulators. Automatic Band Switching - Tuner usually never required - For all Transmitters, Receivers & Transceivers - For all class amateurs - One feedline works all bands - Instructions included - 10 day money back guarantee!

SINGLE BAND DIPOLES (Kit form): Media Band Langth Price D15 15 22 18 95 D20 20 33' 19 95 040 40 66' 22 95

80 includes assembly instructions. Deluxe center connector, 14 ga Stranded CopperWeld Antenna wire and End insulators COAX CABLE: (includes PL-259 connector on each end) 88.00 Separately \$11.95 DELUXE CENTER CONNECTOR NO RUST Brass Termin NG Jumper Wires Used ND Soldering ning A aled. Weath CE-1 Easy Ele \$8.95 DELUXE ANTENNA TRAPS: Completely sealed & weatherproof -Solid brass terminals - Handles Full Power - NO jumpers - NO Soldering Instructions included For 4-band Dipole Ant. 40/20/15/10 \$36.00/pr For 5-band Dipole Ant 80/40/20/15/10 \$38.00/pr ORDER DIRECT FROM FACTORY. All orders shipped US Postpaid. VISA/MC - give card #, Exp. date, Signature SPI-RO MANUFACTURING, INC. Dept. 103, P.O. Box 1538 Hendersonville, NC 28793

Dealer Inquiries Invited

- 204



▶ 205









your system. All other functions of your packet unit continue to be available at the same time. Established and operated from your keyboard, the mailbox uses familiar commands such as SEND, LIST, READ, KILL, and BYE. The number of messages is limited only by the amount of RAM available in your packet unit.

The Personal Packet Mailbox option is currently available for the KAM (Kantronics All Mode), the PKC-1, the KPC-2, and the KPC-2400. To add the Personal Packet Mailbox option to your Kantronics packet unit, contact Kantronics or an authorized Kantronics dealer. The option retails for \$39.95 (plus \$2.50 for shipping if ordering through Kantronics), and includes a replacement plug-in EPROM and an installation/operations manual.

For further information, contact Kantronics, Inc., 1202 E. 23 Street, Lawrence, Kansas 66046. Circle #315 on Reader Service Card.


new Radio Handbook

The 23rd Edition of Bill Orr, W6SAI's, *Radio* Handbook has just been released by Howard W. Sams & Company.

Completely revised and updated, this edition contains new material reflecting the latest developments in technology, covering everything from HF-VHF amplifier design to interference reduction for VCRs and video disc players.

Readers will find schematics, photos, construction diagrams, tables, and charts right at their fingertips, for expert guidance and instant reference. Specific topics addressed include an introduction to Amateur Radio communications; fundamental of communications receivers; fm and repeaters; mobile, portable, and marine equipment; radio and television interference; equipment design, components, and controls; VHF and UHF antennas; and transmission lines and matching systems.

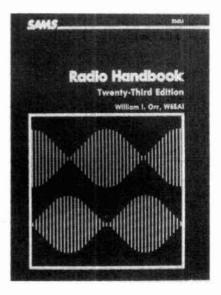Licensed as a radio amateur in 1934, Bill has authored or co-authored many books. Editor of the *Radio Handbook* since 1955, he's written



hundreds of technical articles, including a monthly column in ham radio.

Bill Orr's *Radio Handbook*, 23rd Edition, (640 pages, hardbound) retails for \$26.95 and is available from Ham Radio's Bookstore, Greenville, New Hampshire 03048. Add \$3.50 for shipping and handling.

new 900-MHz antennas

Two new 900-MHz antennas available from NCG are specifically designed for operation in the 902-928 MHz band.

The anodized black Model CMW-202N mobile antenna, a 5-dB gain antenna capable of a maximum of 30 watts of drive power, uses a magnetic mount with a double coil whip. The 900-MHz base/repeater antenna, model CFC7-71, is a collinear fiberglass antenna with a gain of 7.14 dB and maximum power capability of 50 watts. Mast mounting brackets and hardware is included.

For information, contact NCG Company, 1275 N. Grove Street, Anaheim, California 92806.

Circle #310 on Reader Service Card.

new hf amplifier

Tokyo Hy-Power Labs' HL-2K/A is a compact hf amplifier utilizing the popular 3-500Z transmitting tubes. Similar to their HL-1K/A, it features a built-in power supply with a heavy-duty transformer that permits continuous key-down operation. The amplifier is equipped with two large panel meters: one monitors plate current, and the other can be switched to read plate voltage, grid current, or power output. A delayed cooling fan system protects the tubes for a timed period after the power has been turned off.



THE MOST POPULAR HAM RADIO ACCESSORIES are available from WELZ. WELZ brand easyto-read power and VSWR meters and other high quality station accessories are used world-wide. WELZ, good enough to be the best.

SANTEC

PORTABLES

COMPACT MOBILES MAKE FULL DUPLEX POSSIBLE KDK mobile radios are so small, TWO of them will fit in the space normally accomodating one full size mobile radio. This allows for full duplex cross band operation with 32 memory capacity, plus many other advantages. Check out the FM-240 (VHF) and the FM-740 (UHF) today.



ROTORS • ACCESSORIES

WHEN YOU TURN YOUR ANTENNA, DO IT WITH KENPRO antenna aiming devices and accessories. From light to heavy-duty there's a KENPRO for you. NEW Satellite tracking AZ-EL units with external computer controller interface.

PERFORMANCE add-on accessory VHF/UHF

amplifiers, antenna couplers

and now HF LINEARS too.

When power out is

your problem, stop

in for the THL

brand solution.

LOOK CLOSELY AND YOU WILL CHOOSE SANTEC. Santec hand-helds are truly the BEST value + quality + performance combination available today. A Full 5 Watts output, Multi-mode Scan, 10 Memories and AUTO-DIALER make the SANTEC a fantastic hand-held radio. Try one yourself at your next trip to your favorite Ham Radio Shop.

FUCONN

\$ WITE

1506 CAPITAL AVENUE, PLANO, TEXAS 75074 PHONE · 214-423-0024 GIII FAX · 214-423-0081 NATIONAL DISTRIBUTION FOR SANTEC · KDK · KENPRO · THL · WELZ · DIAMOND



210

NEMAL ELECTRONICS

escription /2" Aluminum Black Jacket /2" Corr. Copper Blk. Ikt. /8" Corr. Copper		Per FL 89		Description		
/2" Corr. Copper Blk. Jkt. /8" Corr. Copper			40.100			Each
/8" Corr. Copper			NE 720	Type N for Belden 9913		4.25
		1.59	NE723	N Female Belden 9913		4 75
Carterio de la construcción de la c		3 92	PL258AM		100000	1.45
Conn., 172" Alum. (Male or Female		22.00	PL259	Standard Plug for RG8, 213	10/5 90 or	.65
Conn., 1/2" Copper (Male or Femal		22.00	PL259AM		10/7 90 or	89
		54.00	PL259TS			1.59
COAVIAL CARLES			UG21D	Type N for RG8, 213, 214		3 00
		Second Second				6.50
	100 Ft.	Per Ft.				1 25
	28.00	.32		S0239 to Male N	10000	6.50
	30.00	32			10/2 00 or	22
	15 00	17				3.75
	34 00	.36	KA51-18			4.35
	155.00	165				8.95
elden 9913 Low Loss	46.00	50				89
G142B/U Teflon/Silver	140.00	1.50			RAID	
G217/U 5/8" 50 ohm Dbl. Shield	80.00	85				Per Ft
	80.00	85	GS38	3/8" Tinned Copper		30
G174 95% Shielded Mil. Spec.	12.00	.14		1/2" Tinned Copper		40
OTOR CABLE - 8 CO	ND.		GS316	3/16" Tinned Copper		15
scription	100 Ft.	Per FL		Search and the search of the s		32
18 Ga . 6-22 Ga	19 00	21			ANDED	
16 Ga., 6-20 Ga. Heavy Duty	34.00	36				Per Ft.
			HW06	6 Ga. insulated stranded		35
GGGGGGGGGGGGGGGGGGGGGGGGGGGGGGGGGGGGGG	Conn. 7/8" Copper (Male or Femal COAXIAL CABLES scription 8 95% Shielded Mil. Spec 8 95% Shielded Foam 38 95% Shielded foam 38 95% Shielded Mil. Spec 213/U Mil. Spec. 95% Shield 214/U Mil. Spec. Jobl. Shield 223/U Mil. Spec. Dobl. Shield 223/U Mil. Spec. Dbl. Shield 233/U Mil. Spec. Dbl. Shield 234/U Mil. Spec. Dbl. Shield	Conn. 7/8" Copper (Male or Female) COAXIAL CABLES corpation 100 FL serigition 30 00 38 95% Shielded Mill Spec 28 00 38 95% Shielded Foam 30 00 38 95% Shield (mini 8) 15 00 213/J Will Spec 95% Shield (mini 8) 15 00 34 00 214/J Will Spec 95% Shield (mini 8) 15 00 34 00 1242/U Telfon/Silver 140 00 30 00 323/J Will Spec. Dbl. Silver 160 00 123/J Will Spec. Dbl. Silver 160 00 30 00 30 00 323/J Will Spec. Dbl. Silver 12 00 COTOR CABLE 8 COND. 12 00 100 FL 8 0.0 12 00 COTOR CABLE 8 COND. 100 FL 8 0.0 19 00 6 5.0 6 5.2 Ca 19 00 6 5.6 6 5.2 Ca 19 00 5 5.3 0.0 10 00 FL 3 0.0 13 00 13 00 13 00 13 00 13 00 13 00 13 00 13 00 13 00 13 00 13 00 13 00 14 00 13 00 14 00 1	Conn. 7/8" Copper (Male or Female) 54.00 COAXIAL CABLES scription 100 Ft. Per Ft. servisition 28.00 32 32 s9.5% Shielded Mil. Spec 28.00 32 28.95% Shielded Foam 30.00 32 28.95% Shielded Foam 30.00 32 21.37.041 Spec 95% Shield 30.00 32 21.37.041 Spec 55.00 1.65 1.65 10428/U Felfon/Shiver 140.00 50 1.1428/U Felfon/Shiver 140.00 1217/UNI. Spec. Dbl. Shiver 140.00 1.50 1.65 12428/U Felfon/Shiver 140.00 1.50 1217/US/8".50 ohm Dbl. Shivel 80.00 85 223/U Mil. Spec. Dbl. Silver 80.00 85 12495% Shielded Mid. Spec. 12.00 14 OTOR CABLE — 8 COND. 86 15.00 21 66.36, 622 Ga 19.00 21 66 22.00 36 67.300 - 100 Ft. / Conn. \$3.00 / C 0.0. \$2.00 36 30.0 - 100 Ft. / Conn. \$3.00 / C 0.0. \$2.00 3	Conn. 7/8" Copper (Male or Female) 54.00 PL2591S COAXIAL CABLES UG21D UG33B scription 100 FL Per FL UG38 8 95% Shelded Mil. Spec 28.00 32 UG175/6 1237/J Mil. Spec. 96% Sheld 30.00 32 UG175/6 1217/J Mil. Spec. 96% Sheld 30.00 36 KA51-18 12142/J Telfor/Sileer 140.00 55 S0239AM 1217/J JJ. Shelded Mil. Spec. 12.00 150 S0239AM 12147/U.Mil. Spec. Dbl. Silver 140.00 85 GS38 2237/J Mil. Spec. Dbl. Silver 12.00 150 S0239AM 1217/J J5/8" Shelded Mil. Spec. 12.00 14 GS12 COTOR CABLE — 8 COND. 6S316 GS316 GS316 GS316 GS326 GS316 GS316 GS316 GS3.6.20 Ga. Heary Duft 34.00 36 Hemail No. Kription 100 FL Per FL. G GS316 GS3.6.20 Ga. Heary Duft 30.00 20 Hemail No. <td>Conn. 7/8" Copper (Male or Female) 54.00 PL2591S PL259 Tetion/Silver cookarial constraints 100 FL Per FL UG21D Type N for R68, 213, 214 B 95% Shielded Mil. Spec 28.00 32 UG880 BNc R658 UG175/6 Adapter for RC58/59 (specify) UG255 S0239 to Male N UG175/6 Adapter for RC58/59 (specify) UG255 S0239 to BNC Amphenol 213/U Mil Spec. 96% Shield 300 36 AM9501-1 SMA RG142B 1242/U Tetino/Silver 1400 50 S0239 to BNC Amphenol S0239 1217/U Mil Spec. Dbl. Silver 14000 85 S0239 to BNC Amphenol S0239 1217/U JS/8" 50 ohm Dbl. Sheld 8000 85 S0239 to BNC Amphenol S0239 1217/U JS/8" 50 ohm Dbl. Sheld 8000 85 S0239 to BNC Amphenol S0239 GROUND STRAP — E 1214 95% Shelded Mil Spec 12 00 14 DEscription GS16 3/16" Tinned Copper GS16 3/16" Silver Plated GROUND WIRE — STR Remail No. Description GROUND WIRE — STR 6 Ga, 6-20 Ga<</td> <td>Comm. 7/8 Copper (Male of Female) 54.00 COAXIAL CABLES 54.00 Type N for RG8, 213, 214 Borgition 100 FL Per FL 88 95% Shielded Mil. Spec 28.00 32 UG328 95% Shielded foam 30.00 3213/U Mil. Spec. 96% Shield 36 213/U Mil. Spec. 96% Shield 36 2124/U Holl Silver 155.00 165 36 2124/U Mil. Spec. 96% Shield 36 2124/U Mil. Spec. 910 150 2121/U Mil. Spec. Dbl. Silver 1400 OTOR CABLE — 8 COND. 14 Crock Cable — 8 COND. 14 Crock 22 Ga 19.00 63, 6-20 Ga. Heavy Duty 34.00 63, 6-20 Ga. Heavy Duty 34.00</td>	Conn. 7/8" Copper (Male or Female) 54.00 PL2591S PL259 Tetion/Silver cookarial constraints 100 FL Per FL UG21D Type N for R68, 213, 214 B 95% Shielded Mil. Spec 28.00 32 UG880 BNc R658 UG175/6 Adapter for RC58/59 (specify) UG255 S0239 to Male N UG175/6 Adapter for RC58/59 (specify) UG255 S0239 to BNC Amphenol 213/U Mil Spec. 96% Shield 300 36 AM9501-1 SMA RG142B 1242/U Tetino/Silver 1400 50 S0239 to BNC Amphenol S0239 1217/U Mil Spec. Dbl. Silver 14000 85 S0239 to BNC Amphenol S0239 1217/U JS/8" 50 ohm Dbl. Sheld 8000 85 S0239 to BNC Amphenol S0239 1217/U JS/8" 50 ohm Dbl. Sheld 8000 85 S0239 to BNC Amphenol S0239 GROUND STRAP — E 1214 95% Shelded Mil Spec 12 00 14 DEscription GS16 3/16" Tinned Copper GS16 3/16" Silver Plated GROUND WIRE — STR Remail No. Description GROUND WIRE — STR 6 Ga, 6-20 Ga<	Comm. 7/8 Copper (Male of Female) 54.00 COAXIAL CABLES 54.00 Type N for RG8, 213, 214 Borgition 100 FL Per FL 88 95% Shielded Mil. Spec 28.00 32 UG328 95% Shielded foam 30.00 3213/U Mil. Spec. 96% Shield 36 213/U Mil. Spec. 96% Shield 36 2124/U Holl Silver 155.00 165 36 2124/U Mil. Spec. 96% Shield 36 2124/U Mil. Spec. 910 150 2121/U Mil. Spec. Dbl. Silver 1400 OTOR CABLE — 8 COND. 14 Crock Cable — 8 COND. 14 Crock 22 Ga 19.00 63, 6-20 Ga. Heavy Duty 34.00 63, 6-20 Ga. Heavy Duty 34.00

r 211





The price of the HL-2K/A is \$1695. For details, contact ENCOMM, Inc., 1506 Capital, Plano, Texas 75074.

Circle #309 on Reader Service Card.

Lunar returns to market

Lunar Industries, Inc., of San Diego has reentered the Amateur Radio market with its wellknown line of VHF and UHF preamps and VHF power amps, and has introduced a new line of products scheduled for production early this year. Glenn Rattmann, K6NA, heads the marketing effort.

Lunar recently moved into larger facilities in order to accommodate expanded production of Amateur and commercial communications and television equipment. A network of select dealers is being established and inquiries are encouraged. For details, contact K6NA at Lunar Industries, Inc., 7930 Arjons Drive, San Diego, California 92126.

Circle #308 on Reader Service Card.

cordless tool for soldering, welding, heat shrinking

The Ultratorch, available now from Jensen Tools, is a compact, cordless combination soldering iron, flameless heat tool, and torch. The Ultratorch burns ordinary butane lighter fuel to generate infra-red and ultra infra-red heat by means of a catalytic combustion system. Temperature can be adjusted from 394 degrees to 2372 degrees. Normal settings range from 394 degrees to 932 degrees F for soldering; to 1292 degrees for heat shrinking; and to 2372 degrees for blazing, welding, and other high-heat applications. Soldering /heat ejector, torch ejector, tapered needle soldering tip, heat tip, solder



The RC-850 controller offers your group the most advanced repeater control technology available anywhere. Through ongoing hardware and software enhancements, even our first customers enjoy new features that keep it ahead of the pack.

With the '850, your repeater becomes fully remotely programmable. From command codes to the repeater's operating schedule, virtually everything can be easily changed. Touch-Tone programming from your radio or the phone with synthesized voice readback, or programming from your home computer via modem or packet.

The autopatch supports local and radio-linked remote phone lines, extending your patch coverage to match your RF coverage. You don't even need a phone line at your site! The 250



"The RC-850 Repeater Controller ... still the leader of the pack!"

autodial slots meet everyone's needs, with up to 35 digit storage for personal MCI/Sprint codes.

The easy-to-use mailbox lets you include phone numbers, times, or frequencies in messages. The controller is so smart, it'll leave you a message if you miss a reverse patch or an alarm.

Selective call capabilities range from CTCSS and two-tone to display paging, so you can always be available without having to listen. Voice response telemetry lets you remotely meter your site. Its continuous measurements with storage of updated min and max readings let you find out how cold it gets, how high the reflected power reads . . . and when.

Individual user access codes, with callsign ID, offer secure access to selected functions to completely prevent horseplay.

The industry's top-of-the-line controller, now better than ever, for *your* repeater.

2356 Walsh Avenue, Santa Clara, California 95051 (408) 727-3330



Toroid Cores. Iron Powder & Ferrite. Ferrite Beads. Ferrite Rods.

Free catalog and winding chart on request.



CIRCUIT ANALYSIS COMMODORE 64

212

ADVANCED LNCAP64 V4.1

RF and Microwave Circuit Analysis can easily be performed using LNCAP64. Design and analyze RF circuits containing S,Z,Y and ABCD-parameters; R,L,C's, transmission lines, coupled lines, stubs and many other element blocks. Includes parallel and series branching and network combining; sensitivity and full optimization. Performs complete stability analysis for active networks. Also includes filter and matching network design program. Print results to screen, disk or printer. Includes file editor with instructions and examples.

> V4.1 ONLY \$36.95 plus \$2.50 for S&H (up grades \$15.00)


> > BMA software 1234 Rousseau Drive Sunnyvale, CA 94087 (408 732-9475) N.O. or Check Accepted.

> > > 214







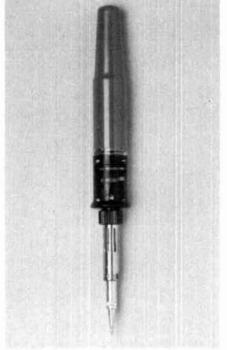

sponge, tip cleaner and spanner wrench are all included.


For more information and free catalog, contact Jensen Tools, Inc., 7815 S. 46th Street, Phoenix, Arizona 85044.

Circle #307 on Reader Service Card.

new mic

Shure Brothers Inc. has introduced the Shure Prologue 2L, an economical dynamic microphone for gooseneck applications.

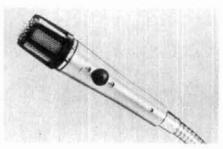Priced at \$40, the Prologue 2L provides a widerange frequency response with a low-end rolloff and high-end presence boost for intelligibility and clarity. Other features include a long-life, easy-



access momentary push-to-talk switch, a tight cardioid polar pattern for effective rejection of feedback and background noise and chromeplated metal casing.

For information, contact Shure Brothers Inc., Customer Services Department, 222 Hartrey Avenue, Evanston, Illinois 60202-3696.


Circle #306 on Reader Service Card.

two new Kulglass™ antennas

Larsen Electronics has added two new models to its line of patented Kulglass antennas: the KG-440 and the KG-900. The two new antennas offer the same features as the earlier KG-450 and KG-825, but extend Kulglass[™] convenience and performance to the 440-450 and 902-928 MHz bands.

The Kulglass tuning assembly is placed on the outside surface of the glass — a car windshield, for example. This allows a low-impedance power transfer through the glass.

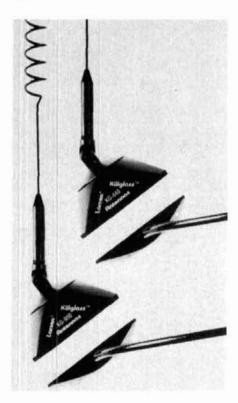The KG-440 is based on a single half-wave design that offers unity gain performance without a ground plane and up to 2.4-dB gain in a typical vehicle installation.



The antennas are fully adjustable to vertical for practically any window angle. This permits their resonant design to attain a low VSWR, a low radiation angle, and maximum ornnidirectional range without a ground plane. This is especially important with the KG-900 because



Barry Electronics Commercial Radio Dept. offers the Best in two-way communications for Businesses, Municipalities, Civil Defense, Broadcasting Companies, Hospitals, etc. Sales and Service for all brands: Maxon, Yaesu, Icon, Tad, Octagon, Regency/Wilson, Midland, Standard, Uniden, Shinway, Fujitus, Seas, Spillsbury, Neutec, etc. Call or write for information, 212-925-7000.







of the multipath signals and low power used in this band.

Both antennas feature a removable whip (which can come in handy in zero clearance situations, such as at the car wash) and Larsen's exclusive Kulrod T[™] plating. The antenna kits include 14 feet of premium RG-58 A/U dualshield, low-loss coax and choice of connectors.

For further information, contact Larsen Electronics, P.O. Box 1799, Vancouver, Washington 98668.

Circle #305 on Reader Service Card.

HF/VHF packet radio controller with tuning indicator

MFJ Enterprises' latest TAPR TNC-2 clone, the MFJ-1274, (\$169.95) works not only for VHF but also for HF, OSCAR, and other non-fm packet. MFJ has made the 1274 modem-selectable for both VHF and HF operation, added their precision 20-segment LED tuning indicator, a TTL serial port, an easily replaceable lithium battery for memory back-up, and a new cabinet.

All you need to enjoy packet radio is an MFJ-1274, your rig, and any home computer with an RS-232 or TTL serial port and terminal program.

If you have a Commodore 64, 128 or VIC-20 you can use MFJ's optional Starter Pack to get on the air immediately. The Starter Pack includes interfacing cable, terminal software on disk or tape and complete instructions . . . everything you need to get on packet radio. The MFJ-1282 (disk) and the MFJ-1283 (tape) are \$19.95 each.


With the MFJ-1274, you'll never have to worry about your TNC's becoming obsolete because you change computers or because packet radio standards change. You can use any computer with an RS-232 serial port with an appropriate terminal program. If packet radio standards change, software updates will be made available as TAPR releases them.

With the addition of a suitable external modem, speeds in excess of 56 kilobaud are possible.

The MFJ 1274 features AX.25 Level 2 Version 2 software, hardware HDLC for full duplex, true Data Carrier Detect for HF, multiple connects, 256K EPROM, 16K RAM (expandable to 32K with optional EPROM), simple operation, and socketed ICs.

You get an easy-to-read manual, a cable to connect your transceiver (you have to add a connector for your particular radio), a connector for

(Sele	1.1.1.1	a lean	
•		LT 73 S	D :
SSB ELEC	TRONIC TRANSVERT	ERS & PREAMP	LIFIERS
LT 2S LT33S LT23S	144/28 XVRTR 20W 902/144 Xvrtr 20W 1295/144 Xvrtr 10W 2304/144 XVRTR 0.5	GaAstet DBM GaAstet GaAstet SW GaAstet W GaAstet stet preamps froi GaAstet preamp	TBA \$549 \$549 \$429 \$599 m\$129 m\$129 ps\$199
TRANSVE	RTERS UNLIMITED		
T220/28 T144/28 PA23200 PA23150 PA1325 HF400 RK500	144 Hhz Xvrtr 28 or 1296 Mhz 2 tube PA	50 IF, 25 W , 200W + + W - W w at 144 Mhz	\$199 \$299 \$449 \$429 \$129
Call or wr	rite for catalogue.		▶ 222
BOX 6286	RTERS UNLIMITED STATION A ONTARIO M5W 1P3	HANS PETER (416) 759-55	

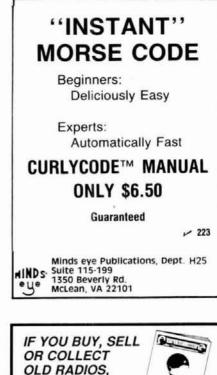



ALL NEW! DUAL BAND ANTENNAS FOR ULTIMATE PERFORMANCE!!

Model	Description		Sug. List
2X4Z	Base/Repeater 20	0 Watt	\$168.95
Gain 146	MHz 8.2dB, 446 MHz 1	1.5dB	
2X4SR	Mobile with Mag. M	1t. 150 Watt	71.90
Gain 146	MHx 3.8dB, 446 MHz 6.	.2dB	
2X4SDY	Mobile with Mag. M	ft. 100 Watt	65.95
Gain 146	MHz 2.15 dB, 446 MHz	3.8dB	
HT 702	146/446 MHz Hand	d Held BNC 50 Watt	29.95
C7-71	Base/Repeater 92	0 MHz	\$115.95
	50 Watt 7.14 dB Ga	ain	
C202N	Mobile 920 MHz w	ith Mag. Mt.	72.95
	5 dB Gain 50 Watt		
1234E	Base/Repeater 20	0 Watt	\$178.95
Gain 446	MHz 8.5dB, 1.2 GHz 10	.1dB	
124X	Mobile with Mag. M	1t. 100 Watt	104.95
Gain 446	MHz 2.5dB, 1.2 GHz 3.5	5dB	
1221S	1.2 GHz Base/Rep	eater 100 Watt	\$158.95
Gain 15.	5dB, 21 Step colinear		
1210M	1.2 GHz Mobile wit	h Mag. Mt. 50 Watt	76.95
Gain 8.8	dB		
415M	High power duplex	er 146 MHz 400 Watt	59.95
	446 MHz 250 Wat	t	
412N	UHF/GHz Duplexe	r 446/1400MHz	68.95
	Max. 70 Watt		
NOA 00	1275 NORTH GROVE ST.		- 226
	ANAHEIM, CALIF. 92806		es may be
NCG	(714) 630-4541 CABLE: NATCOLGLZ		nt than list.
	FAX (714) 630-7024	Prices and specifications change without notice or	





MISA"

× 227



the TTL serial port and a power supply for 110 VAC operation (you can use 12 VDC for portable, remote or mobile operation).

The MFJ-1274 comes with a double guarantee. If ordered directly from MFJ, it may be returned within 30 days for a prompt refund, less shipping. The MFJ-1274 is also covered by MFJ's one-year unconditional guarantee.

For more information, contact MFJ Enterprises, Inc., P.O. Box 494, Mississippi State, Mississippi 39762.

Circle #311 on Reader Service Card.

computer control of rf monitoring

The CR 202, a sophisticated new receiver distributed by Ace Communications, allows monitoring of any frequency from 25 to 550 MHz, plus 800 to 1300 MHz.

With both narrow and wide band reception modes in fm and also a-m, the receiver, priced at \$445, is excellent for general monitoring and surveillance reception of a wide variety of services.

Uses for the unit include general off-air monitoring, spot frequency monitoring and stength measurement, selective multi-frequency analysis, spectrum surveillance, and detection of unwanted transmissions.

An optional digital control accessory permits the user to interface the receiver to any computer equipped with a standard RS-232C port. The resulting computer control permits virtually unlimited channel monitoring and activity analysis with normal communications, text editing, and data base software. A dedicated menu driver software package and a full line of accessories are available.

For information, contact Ace Communications, Monitor Division, 10707 East 106th Street, Indianapolis, Indiana 46256.

Circle #304 on Reader Service Card.

new battery packs

Two new battery packs for King Radio Corporation products are available from Centurion International Inc. No. KR0105 is a 9.6-volt, 800 MAH nickel-cadmium rechargeable battery pack; No. AL0514 is a 13.5-volt, 2100 MAH throwaway alkaline pack. For prices and details, contact Centurion International, Inc., P.O. Box 82846, Lincoln, Nebraska 68501.

Circle #303 on Reader Service Card.

Credit Card Orders (5% added)

introducing a new dimension ...

FROM PRO-SEARCH®


NEW DIGITAL CONVERSION

- For All 8 Wire CDE Rotors
- North & South Center
- Continuous 1° Readout For Full 360°
- Bright ½ x 1½" Display



ONLY \$59.95 PLUS SHIPPING

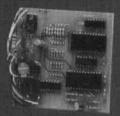- Made In USA
- Easy To Install
- Quality Material
- Designed For Years Of Service



FOR JUST A FEW DOLLARS MORE YOU CAN HAVE THE CONTROLLER OF THE FUTURE TODAY!

introducing a new LOW COST MODEL THE PSE-1K PRICED AT \$189.95 plus shipping

PRI-SFART

Reaching The Worl

For Contesters, DX'ers, Handicapped Operators and General Purpose Ham Operators:

The Most Advanced Antenna Control Available

- The Only Computerized Unit
- The Only Talking Unit
- The Only Scanning Unit
- The Only Programmable Unit
- The Only Automatic Braking Unit

Now Three Models of Our Computerized-Digital Antenna Control Priced From \$189.95 to \$469.95

PSE-1K Series PSE-1A Series PSE-1 Series



Pro-Search Is Adaptable To Many Systems, Simple To Install.

No modifications are necessary.

Disconnect your present antenna control system and connect ours.

Pro-Search is used with HAM-M, HAM-II, III, IV, and TX². Other models are available to work with the HDR-300, etc.

To Order:

1-800-325-4016 1-314-994-7872 (Missouri)

Or write:

Pro-Search Electronics 1350 Baur Blvd. St. Louis, MO 63132

GREAT TRAVELING COMPANIONS

REPEAT

THE ARRL 1987-1988 REPEATER DIRECTORY! OVER 12,000 LISTINGS

Novices will find the 220 and 1270 MHz listings a must. For those interested in packet radio and other modes there are almost 1,000 digipeaters and specialized repeaters listed. You'll find much other useful information including a CTCSS (PL) Tone Frequency Chart, addresses of members of both the ARRL VHF-UHF and Repeater Advisory committees, band plans, information on how to operate through repeaters, compilations of frequency coordinators and ARRL Special Service Clubs. Available in the handy pocket-size (3¼ x 5¼ in.) that was introduced last year. 16th Edition, copyright 1987, \$4.00. Shipping and handling \$2.50 (\$3.50 for UPS). Off the press in late April. Purchase at your dealer or directly from:

The American Radio Relay League, Inc. 225 Main Street, Newington, CT 06111



Super ComShack 64[™]

On January 1, 1987, Engineering Consulting shipped the first Super Com Shacks 64's to previous purchasers of the Com Shack 64 Duplex/Simplex ham shack and repeater controllers. The first units shipped were designed to upgrade existing systems to allow the features found in the new "Super" version.

New features of the "Super" version include a unique code practice mode, speed dial data entry of command strings consisting of multiple commands, and nine complete sets of access codes which can be changed at any time remotely from an HT or telephone, allowing instant repeater access code changes, which can reduce unauthorized use of repeater functions. The system autopatch supports up to 310 stored telephone numbers; ten emergency numbers may be accessed instantly with two digit commands. The balance of the 300 numbers may be stored via touchtone and recalled at any time.

Three hundred callsigns can be programmed into the new Super ComShack. In the "directed page mode," an unlicensed person can call the repeater telephone line and receive a voice message identifying the repeater and requesting input of a three-digit code. A valid code will voice-page the selected callsign over the repeater. If the page message is answered by the Amateur with the proper answer code, the calling party is then put "on the repeater" and a normal conversation can take place. If a control operator needs to gain access to the repeater, it can be done via telephone or touchtones from an HT.

The Super ComShack system offers dual remote base capability, which allows both UHF and HF radios to be input or linked to the main repeater. Total control of the link radio is provided through the use of serial data. Software is included to control the Yaesu FT-757, FT767, FT980, and FT-727; the Kenwood TS440 and TS940; the TM711/811; and Icom's IC735 transceivers. New radios are being added as manufacturers provide samples for serial data programs to be tested.

A new system — dubbed the "Ultra" — is currently under development. Compatible with the "Super," the "Ultra" will link several systems together, allow for Packet input, and incorporate other advanced features.

The Super ComShack is available from Engineering Consulting, 583 Candlewood Street, Brea, California 92621.

solder 14 different metals – with a match

Quick Silver is a new silver-bearing bonding paste that flows at 430 degrees F using a match, butane lighter, or soldering gun — not 1200 to 1300 degrees F, as in conventional silver soldering. Quick Silver has a tensile strength of 18,000 to 22,000 psi compared to only lead solder's 3,000 psi.

Quick Silver is furnished in a syringe-type applicator that enables the user to apply the paste first and then hold and apply heat. Suitable for electrical work where high conductivity and strength are required, it conforms to pure food laws (i.e. contains no lead, zinc, cadmium or antimony) and provides a good color match to stainless steel. It won't darken or tarnish.



Quick Silver can be used on brass, bronze, chrome-plated steel, chrome-plated copper, copper, gold-filled and gold-plated materials, molybdenum, nickel silver, silver, stainless steel, steel, sterling silver, 800 silver, tin, and zinc. Priced at \$9.95 plus \$2.00 postage and handling, it's available from E.L. Jones Company, P.O. Box 849, Sanford, North Carolina 27330.

Circle #302 on Reader Service Card.

DX nets, beam headings

DX Net List Around the World provides full information about all active DX nets and updates the DX Net List for 1987. Previous editions of the list — with information about DX Nets that might be reactivated as conditions allow — are still available.

DX Beam Headings Around the World shows bearing, distance in miles and kilometers, and reverse bearing for your QSO partner), for both shortpath and longpath, for more than 450 locations throughout the world. Special care has been taken for the Antarctic, USA, USSR, the Peoples Republic of China, and the Pacific Ocean.

For information, contact Ing. Christian Hohenwallner, OE2CHN, Gneisfeldstrasse 5, A-5020 Salzburg, Austria or Dieter Konrad, OE2DYL, Bessarabierstrasse 39, A-5020 Salzburg, Austria.

SATELLITE TV BOO-4-SATMAN BOO-4-SATMAN NEW 24 Page Buver's Guide

Buyer's Guide With Guaranteed Lowest Prices

• Explains all about FREE 100 channel Satellite TV and how to shop for an earth station!

.

.

.

- Lists GUARANTEED LOWEST PRICES...we will not be undersold, save 30-50% over local dealer prices!
- Tells how to easily and quickly Install-Your-Own earth station and save \$400 or more!
- Shows how to demonstrate and sell earth stations from your home and earn extra money!

uniden	Panasonic
BALCOA	CHAPARRAL
	HAmpitoo, Inc.

The new SATMAN Buyer's Guide is a *necessity* for any prospective or current earth station owner who wants to save big money on name brand satellite products and also earn some extra money. Buy direct, Do-It-Yourself, and save with SATMAN. Toll free ordering, no sales (ax (IL only), major credit cards accepted, huge in-stock inventories available, and fast UPS shipping anywhere in U.S. Check with SATMAN before you buy....*We will not be undersold! Call now* for your free 24 page SATMAN Buyer's Guide.



MISSOURI RADIO CENTER

00

HYGAIN

1-800-821-7323



KANTRONICS





ADVERTISER'S INDEX AND READER SERVICE NUMBERS

Listed below are the page number and reader service number for each company advertising in this issue. To get more information on their advertised products, use the bind-in card found elsewhere in this issue, select the correct reader service number from either the ad or this listing, check off the numbers, fill in your name and address, affix a postage stamp and return to us. We will promptly forward your request to the advertiser and your requested information should arrive shortly. If the card is missing, send all the pertinent information on a separate sheet of paper to: *ham radio* magazine, Attn: Reader Service, Greenville, NH 03048.

F

PAGE #

A. C.	SERVICE # PA	GE #
119 -	Ace Communications	33
212 -	Advanced Computer Controls	
	Advanced Receiver Research	
	AEA	
	All Electronics Corp	
	Alpha Delta Communications	
	Aluma Tower Co	
	Amateur Electronic Supply	100
144	Amateur Wholesale Electronics	-103
144	Amateur Wholesale Electronics	
	American Reliance, Inc.	
	Amidon Associates	
159 -	AMSAT	76
_209 ·	Antennas Etc	.116
176 -	Antique Electronic Supply	
224 -	Antique Radio Classified	.122
168 -	Arnold Co	
123 -	ARRL	126
219 -	Astron Corp	34
118 -	Avcom	
	Barker & Williamson	
	Barrett Elec	
	Barry Electronics	
175 -	Bilal Company	00
193 .	Bird Electronic Corporation	104
	BMA Software	
177	BMA Software Buckmaster Publishing	119
	Buckmaster Publishing	
- 15	Butternut Electronics	
- 31	С.О.М.В.	130
-	Caddell Coil Corp	
186 -	California Packet Concepts	.100
_210	Coaxial Dynamics, Inc	118
169 -	Communication Concepts, Inc.	
142 -	Communications Specialists	
179 -	Computer Radio	94
	Creative Design /Orion Hi-Tech	24
	Cushcraft	
	CTM	
	Digitrex	
	Digimax Instruments Corp	
	Doppler Systems, Inc	
	Down East Microwave	
	Eaglestone	
235 -	EGE, Inc	131
200 -	Encomm, Inc	117
-	Engineering Consulting	109
_205 -	Fair Radio Sales	115
143 -	Fluke Manufacturing Co	58
	Fox Tango Corp	108
· · ·	Gem Quad Products Ltd	.86
160 -	Gilfer Shortwave	.80
134 -	GLB Electronics	.53
	H.L. Heaster, Inc	
112 -	HAL Communications Corp	23
117 -1	Hal-Tronix	20
125 -1	Hall Electronics	41
16.0	Ham Radio Magazine	100
104	Ham Padia Outlet	120
104 -1	Ham Radio Outlet 66 Ham Radio's Bookstore 29, 40, 43, 52,	100
- 12	The Ham Station	
	Hamtronics, NY	. 79
	Hamtronics, PA	.75
	famfronics, PA	122
161 -	Hately Antenna Technology	.80
	Hildreth Engineering	
	COM America, Inc	
141 -1	COM America, Inc.	.57
		54
146 -1	nterceptor Electronics. Inc	
164 -1	nternational Radio	82
	lensen Tools, Inc.	
149	lo Gunn Enterprises	62
	lun's Electronics	
103 -1	(agil	101
	Cantronics	
173 -	Cennedy Associates	.91
	rio-Kenwood Communications2, 5, 7, 15,	
	Cepro	
	Gron Corporation	61
	Madison Electronics Supply	
101 5	Elaine Martin, Inc	102
191 - 6		
	Slen Martin Engineering, Inc.	

READER SERVICE #

*Please contact this advertiser directly.	*Please	contact	this ad	vertiser	directly.	
---	---------	---------	---------	----------	-----------	--

Please use before June 30, 1987.

108 136 196 223 124 152 144 152 174 234 135 174 226 122 211 211 177 157 111 157 111 129 233 213 199	Metal & Cable Corp. MEJ Enterprises Micro Control Specialties Micro Systems Institute Midland Technologies Minds Eye Publications Mirage Communications Missouri Radio Center Monitoring Times. Notron Electronics Note Volts OPTOelectronics Pac-Comm Packet Radio Systems, It Pacific Rim Communications Padomar Engineers Proc-Search The PX Shack Radio Amateur Callbook	13 52 52 109 102 122 41 65 53 53 91 123 39 91 123 39 91 123 20 nc 46 20 nc 46 129 19 108 20 129 108 125 120 20 20 20 20 20 20 20 20 20 20 20 20 2
108 136 196 223 124 152 144 152 174 234 135 174 226 122 211 211 177 157 111 157 111 129 233 213 199	MFJ Enterprises Micro Control Specialties Micro Control Specialties Micro Systems Institute Midland Technologies Minds Eye Publications Mirage Communications Mirage Network Motron Electronics Not Sevent Labs, Inc Nenal Electronics Nuts & Volts OPTOelectronics Pac-Comm Packet Radio Systems, It Pacific Rim Communications Palomar Engineers Procsearch The PX Shack Radio Amateur Callbook	13 52 52 109 102 122 41 65 53 53 91 123 39 91 123 23 91 123 23 91 123 20 nc 46 129 129 108 125 120 120 120 120 120 120 120 120 120 120
136 196 196 223 124 152 110 145 234 136 174 226 122 211 171 157 111 157 111 129 232 213 199	Micro Control Specialties Micro Systems Institute Micland Technologies Mirage Communications Montron Electronics NetFech Labs, Inc Nenal Electronics Nuts & Volts OPTOelectronics Pac-Celectronics Pacific Rim Communications Palomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook	52 109 102 122 41 85 53 91 128 53 91 123 39 118 89 73 39 118 89 73 39 118 89 73 39 118 89 120 20 nc 46 129 109 119 102 120 120 120 120 120 120 120 120 120
196 190 223 124 152 110 145 234 135 174 226 211 171 157 111 157 232 213 213 199	Micro Systems Institute Midland Technologies Minds Eye Publications Minds Eye Publications Mirage Communications Mirage Communications Mirage Communications Mirage Communications Missouri Radio Center Montoring Times Morron Electronics Net Tech Labs, Inc Nemal Electronics Nuts & Volts OPTOelectronics Pacific Rim Communications Pacific Rim Communications Processor Concepts Procesarch The PX Shack Radio Amateur Callbook Radio Amateur Callbook	109 102 122 121 125 18 18 53 53 91 123 123 123 123 123 123 123 123 123 12
223 124 152 110 145 234 174 226 122 211 171 157 111 157 111 157 232 213 199		122 41 65 18 61 128 91 123 91 123 39 118 89 73 39 118 89 73 39 118 89 73 20 nc 46 129 119 108 125 120
124 152 110 145 234 135 174 226 122 211 171 157 111 129 232 213 199	Mirage Communications Mirage Communications Mirage Communications Mirage Communications Mission Communications Mission Communications Mission Communications Morron Electronics Nord Neral Electronics Net Tech Labs, Inc Nemal Electronics Nots & Volts OPTOelectronics Pac-Comm Packet Radio Systems, In Pacific Rim Communications Pacific Rim Communications Pacommunications Pacommunications Pacommunications Pacommunications Pacommunications Pacommunications Pacommunications Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook	41 65 18 61 128 53 91 123 39 118 89 73 20 nc 46 20 129 119 108 2125 120
152 110 145 234 135 174 226 122 211 171 157 157 157 157 157 157 157 157 1	Mirage Communications Mirage Communications Mirage Communications Mission Communications Missouri Radio Center Motioning Times Motron Electronics Notal Electronics Net Tech Labs, Inc Net Tech Labs, Inc Net all Electronics Notal S Volts OPTOelectronics Pac-Comm Packet Radio Systems, In Pacific Rim Communications Patiomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radio Amateur Callbook	65 18 61 128 53 91 123 39 18 89 118 89 73 20 20 0nc 46 129 119 108 125 120
110 145 234 135 174 226 122 211 171 157 111 157 232 213 199	Mirage Communications Mirage Communications Missouri Radio Center Monitoring Times. Montron Electronics Noto Ned. Net-Tech Labs, Inc. Nemal Electronics Notos Volts OPTOelectronics Pac. Celectronics Pac. Comm Packet Radio Systems, In Pacific Rim Communications Palomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radio Amateur Callbook	18 61 128 53 91 123 39 18 89 73 73 73 73 73 73 73 73 73 10 8 9 119 108 125 120
145 234 135 174 226 122 211 171 157 111 129 232 213 199	Mission Communications Missouri Radio Center Morisouri Radio Center Morino Electronics Nord Neral Electronics Net Tech Labs, Inc Nemal Electronics Nuts & Volts OPTOelectronics P. C. Electronics Pac-Comm Packet Radio Systems, fit Pacific Rim Communications Palomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radio Amateur Callbook	61 128 53 91 123 39 118 89 73 20 nc 46 129 119 108 125 120
234 135 174 226 122 211 171 157 111 157 111 129 232 213 199	Missouri Radio Center Monitoring Times Monitoring Times Notion Electronics NCG Net-Tech Labs, Inc Nemal Electronics Nots & Volts OPTOelectronics Pac-Comm Packet Radio Systems, In Pacific Rim Communications Patiomar Engineers Processor Concepts Proc-Search The PX Shack Radio Amateur Callbook Radiokit.	128 53 91 123 39 118 89 73 20 20 nc 46 129 119 108 125 120
135 174 226 122 211 171 157 111 129 232 213 199	Monitoring Times. Motron Electronics Notoron Electronics Noto Ned-Tech Labs, Inc. Nemal Electronics Noto & Volts. OPTOelectronics Pac. Celectronics Pac. Celectronics Pacific Rim Communications Palomar Engineers Processor Concepts. Processor Concepts. Pro PX Shack Radio Amateur Callbook Radio kit.	53 91 123 39 118 89 73 73 73 20 nc 46 129 119 108 125 120
174 226 122 211 171 157 111 129 232 213 199	Motron Electronics NGC Net Tech Labs, Inc Nemal Electronics Nuts & Volls OPTOPEctronics P.C Electronics P.C Electronics Pacific Rim Communications Padomar Engineers Processor Concepts Processor Concepts Pro PX Shack Radio Amateur Callbook Radiokit.	91 123 39 118 89 73 200 nc 46 129 119 108 125 120
226 122 211 171 157 111 129 232 213 199	- NCG - Net-Tech Labs, Inc - Net-Tech Labs, Inc - Nemal Electronics - Nuts & Volts - OPTOelectronics - P.C. Electronics - Pac-Gomm Packet Radio Systems, In Pacific Rim Communications Palomar Engineers - Processor Concepts - Pro-Search - The PX Shack - Radio Amateur Callbook - Radio Amateur Callbook	123 39 118 89 73 20 nc 46 129 119 108 125 120
122 211 171 157 111 129 232 213 199	NetTech Labs, Inc. Nemal Electronics Nuts & Volts OPTOelectronics P.C. Electronics Pac-Comm Packet Radio Systems, In Pacific Rim Communications Patiomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radiokit.	39 118 89 73 20 nc 46 129 119 108 125 125 120
211 171 157 111 129 232 213 199	Nemal Electronics Nuts & Volts OPTOelectronics P.C. Electronics P.C. Electronics Pac-Comm Packet Radio Systems, Il Pacific Rim Communications Pacific Rim Communications Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radio Kit.	118 89 73 20 nc 46 129 119 108 125 120
171 157 111 129 232 213 199	Nuts & Volts. OPTOelectronics P.C. Electronics Pac-Comm Packet Radio Systems, It Pacific Rim Communications Palomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radiokit.	89 73 20 nc 46 129 119 108 125 120
157 111 129 232 213 199	OPTOelectronics P.C. Electronics Pac-Comm Packet Radio Systems, II Pacialman Packet Radio Systems, II Pacific Rim Communications Pationar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radiokit.	73 20 nc 46 129 119 108 125 120
111 129 232 213 199	P.C. Electronics Pac.Comm Packet Radio Systems, It Pacific Rim Communications Palomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radiokit.	20 nc 46 129 119 108 125 120
129 232 213 199	Pac-Comm Packet Radio Systems, In Pacific Rim Communications. Palomar Engineers. Processor Concepts. Pro-Search. The PX Shack. Radio Amateur Callbook. Radiokit.	nc 46 129 119 108 125 120
232 213 199	Pacific Rim Communications Patomar Engineers Processor Concepts Pro-Search The PX Shack Radio Amateur Callbook Radiokit.	129 119 108 125 120
213	Palomar Engineers Processor Concepts Pro-Search The PX Shack Shack Radio Amateur Callbook Radio Amateur Callbook	119 108 125 120
199	Processor Concepts Pro-Search The PX Shack Ando Amateur Callbook Radiokit	108 125 120
	5 - Pro-Search 7 - The PX Shack 8 - Radio Amateur Callbook 7 - Radiokit	125
225	7 - The PX Shack 3 - Radio Amateur Callbook 7 - Radiokit	
	3 - Radio Amateur Callbook 7 - Radiokit	
217	7 - Radiokit	
	7 - Radiokit	
227		
121	- Radiosporting	
	- Radio Works	
	4 - Ramsey Electronics, Inc.	
	* - RF Parts	
) - RF Products	
	7 - Robot Research, Inc.	
221	1 - Roensch Microwave	
215	- Rutland Arrays	
203	3 - S-Com	
230) - Satman	
120) - Sias Engineering Co	
187	7 · Sommer	
_	Spec-Com Spectrum International Spi-Ro Manufacturing Co	
125	3 - Spectrum International	
204	I - Spi-Ro Manutacturing Co	115
	3 - Stone Mountain Engineering Co	
	 Stridsburg Engineering Co. 	
132	2 - STV/OnSat	
	2 - Synthetic Textiles, Inc.	
13/	7 - Tel-Com 3 - Telewave, Inc	
	2 - Testware	
	7 - Texas Radio Products 3 - Thermax Corp	
110	- Thermax Corp	29
	 Torontel Technology Systems Ltd. Total Electronic Concepts 	
100	5 - Transleteronic, Inc. 2 - Transverters Unlimited	122
	3 - Unity Electronics	
23	Onity Electronics Onity Electronics Oniversity Microfilm Int	129
	- University Microfilm Int	
	3 - UV Comms 3 - Vanguard Labs	
	9 - Varian	
	3 - W9INN Antennas	
	2 Webster Communications	
	Western Electronics	
	5 - Yaesu Electronics Corp - E.H. Yost Co.	

PRODUCT REVIEW/NEW PRODUCTS

304 - Ace Communications	124
303 - Centurion International, Inc	
309 - Encomm, Inc.	
Engineering Consulting	
* - Ham Radio's Bookstore	
307 - Jensen Tools, Inc.	
302 - E L Jones Company	127
315 - Kantronics	
305 - Larsen Electronics	
308 - Lunar Industries, Inc	118
311 - MFJ Enterprises	122
310 - NCG	
· OE2CHN, OE2DYL	
306 - Shure Brothers, Inc	
312 - Yaesu USA Amateur Products Division	

Limit 15 inquiries per request.



130 In May 1987






YOU ALREADY OWN 75% OF A COLOR VIDEO STATION

It's true. With your transceiver, antenna, television set and audio tape recorder, you already have 75% of what's required to receive and send

color video world-wide!

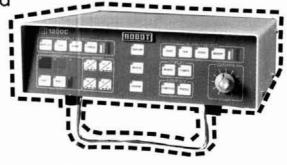

Add a **ROBOT** Video Transceiver and your station is complete.

Thousands of amateur video operators around the world are exchanging beautiful color images every day. Whether your favorite mode is SSB or FM or AM—direct, via repeater or

17

satellite—you can join in the high-tech fun without modifying your present equipment. Just add a Robot to your station!

	Please send me the follow disatisfied for any reason,	ing Robot equipment. I understand that if I I can return the unit and receive a full refur
ROBOT	 ☐ 1200C high resolution ☐ 450C standard resoluti ☐ 400C upgrade kit \$395 ☐ More Information 	on \$795
	Name	Call
ROBOT RESEARCH, INC.	Address	
7591 Convoy Court San Diego, California 92111 Phone (619) 279-9430	City	Zip
	Enclosed check or mo	ney order \$
		Exp. Date:

See us in Dayton Booth #472 & 473.

× 237

HF performance you can have a real field day with.

With Yaesu's FT-757GX/II, you can enjoy full-featured HF performance just about anywhere.

On vacation. During field day. On the road. Or in your shack.

Because the FT-757GX/II packs all its HF performance into one highly compact, actionready case. A case so small, it even fits under airplane seats.

Of course, you've probably noticed a similarity to its predecessor, the FT-757GX. That's purely intentional. And now its performance is even better.

With new features like memory storage of operating mode. Slow/fast tuning selection. Automatic step-change according to mode. IF notch filter. 10 memories. And VFO to VFO scan.

Plus you get an iambic electronic keyer. Woodpecker noise blanker. 600-Hz CW filter. AM and FM modes. AF speech processor. And 25-kHz marker generator. All at no extra charge.

Three microprocessors. Dual VFOs. Single-button VFO/ memory swap. Receive coverage from 500 kHz to 30 MHz. Transmit coverage from 10 to 160 meters, including WARC bands. All-mode coverage (LSB, USB, CW, AM and FM). 100-watt RF output.


QSK operation. Massive heatsink and duct-flow cooling system for continuous RTTY operation for up to 30 minutes.

Computer Aided Transceiver (CAT) System for computer control via optional interface (software is available from your Yaesu dealer).

Of course, the FT-757GX/II offers the kinds of options you'd expect from Yaesu, too. Including standard and heavyduty power supplies, automatic antenna tuner, and more.

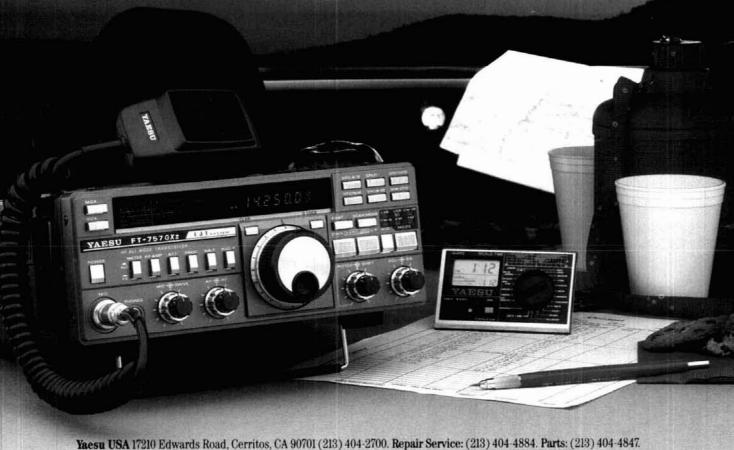So no matter where you work the DX, take along Yaesu's FT-757GX/II. The full-featured HF rig you'll have a real field day with.





Yaesu USA 17210 Edwards Road, Cerritos, CA 90701 (213) 404-2700. Repair Service: (213) 404-4884. Parts: (213) 404-4847 Yaesu Cincinnati Service Center 9070 Gold Park Drive, Hamilton, OH 45011 (513) 874-3100.

KENWOOD

... pacesetter in Amateur radio

First Again!

TW-4100A 2 m/70 cm FM Dual Bander

A Kenwood original just got better! Kenwood was the first to develop a 2 m/70 cm mobile radio in a single, compact package. Since then, other companies have imitated the concept, but still have not done it the "Kenwood way." The all-new TW-4100A is more compact, more powerful, and packed with more features than ever before! With many new features and accessories, and backed by Kenwood's experience, the all-new Kenwood Dual Bander is light years ahead of the rest!

- Selectable full duplex cross band ("telephone style") operation.
 Remote base or cross band repeater function possible (a control operator is needed for remote or repeater operation*).
- 45 watts on 2 m. 35 watts on 70 cm. 5 watts (adjustable) low.
- Frequency coverage: 142-149 MHz (allows operation on certain MARS and CAP frequencies) and 440-449.995 MHz.



- New compact size! Only 5.9" W x 1.97" H x 7.87" D and weighs less than 4 pounds!
- Proven high performance Kenwood GaAs FET front end receiver.
- Easy to operate! Only 3 knobs and 8 keys on the front panel.
- Separate antenna ports for VHF and UHF. Minimizes loss and increases reliability and performance!
- 10 memory channels. Lithium battery backs up memory. Store frequency, offset, subtone. Two channels store the transmit and receive frequencies independently for odd split or cross band operation.
- Front panel-selectable CTCSS tone (when optional TU-7 is installed.)

- Non-volatile operating system.
 Even after memory back up cell dies, all operating features remain intact!
 No re-programming or "boardswapping" necessary!
- Programmable band scan and memory scan with memory channel lock-out.
- Large, illuminated LCD display and main knob. For excellent visibility in direct sunlight or darkness.
- Selectable frequency step for quick and easy QSY.
- Voice synthesizer VS-2 option.
- Optional accessories:

 PS-50/PS-430 DC power supplies
 MU-1 DCL modem unit * TU-7 CTCSS encoder * VS-2 Voice synthesizer * SW-100B SWR/Power/Volt meter 140-450 MHz for mobile use * SW-200B SWR/Power meter for base station use 140-450 MHz. 0-200 W in 2 ranges * SWT-1/SWT-2 2 m and 70 cm antenna tuner * SP-40 Compact speaker * SP-50B Mobile speaker * PG-2N Extra DC cable * PG-3B DC noise filter * MC-60A, MC-80, MC-85 Base station mics. * MC-55 (8-pin) Mobile microphone * MA- 4000



Dual band mobile antenna with duplexer (mount not included) * **MB-11** Extra mobile mount



*Please check FCC regulations on repeater operation

Minor modification necessary for repeater operation

Specifications and prices subject to change without notice or obligation

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories.