
AUGUST 1987 / \$2.50

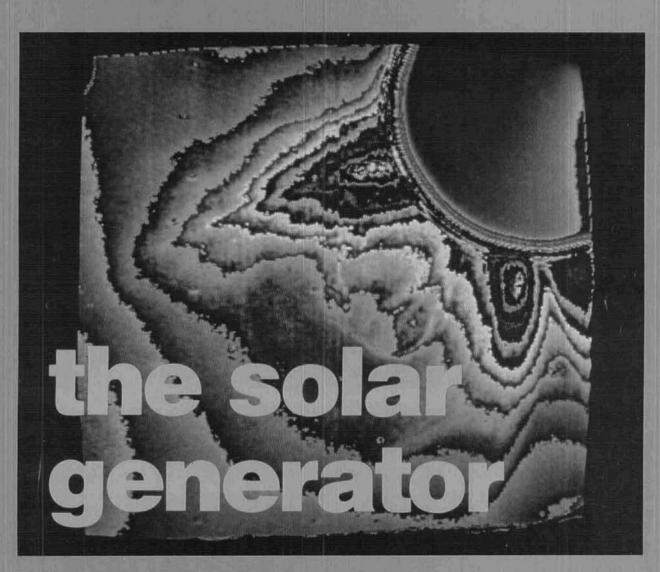



focus on communications technology



UF

VOL/PWR

VFO

DOWN

- Compact Size
- Simple to Operate
- Large LCD Readout
- 25 Watt IC-28A
- 45 Watt IC-28H
- Packet Compatible
- 21 Memory Channels

The IC-28H has all the features you need for carefree 2-meter mobile operation. The only thing it doesn't have is a big price.

45 Watts. The IC-28H provides a full 45 watts of powerful output. The **IC-28A** 25-watt version is also available. Both units have a selectable low power.

Large LCD readout. A wide-view LCD readout can be easily read even in bright sunlight. An automatic dimmer circuit reduces the brightness for evening operation. Wideband Coverage. The IC-28H performs from 138–174MHz (specifications guaranteed from 144.00–148MHz) and includes weather channels. Ideal for MARS and CAP operation.

Compact Size. The IC-28H measures only 2 inches high by $5\frac{1}{2}$ inches wide by $7\frac{1}{4}$ inches deep (IC-28A is $5\frac{1}{4}$



The IC-27H 45 watt and IC-27A 25 watt ultra compact 2-meter mobiles continue to be available.

inches deep). Great for mobile installations where space is limited.

ICOM

21 Memory Channels. Store 21 frequencies into memory, or lock out certain memory channels. All memories are backed up with a lithium battery.

Scanning. Scan the entire band or the memory channels from the provided HM-12 mic.

Easy to Operate. With only 11 front panel controls, the IC-28H is simple to operate.

Available Options. IC-HM14 DTMF mic, PS-45 13.8V 8A power supply, UT-29 tone squelch unit, SP-10 external speaker, IC-HM16 speaker mic and HS-15/HS-15SB flexible boom mic and PTT switchbox.



ICOM America, Inc., 2380-116th Ave NE, Bellevue, WA 98004 Customer Service Hotline (206) 454-7619 3150 Premier Drive, Suite 126, Irving, TX 75063 ICOM CANADA, A Division of ICOM America, Inc., 3071 - #5 Road, Unit 9, Richmond, B.C. V6X 2T4 Canada

IGOM CANADA, A Division of ICOM America, Inc., 3071 – #5 Road, Unit 9, Hichmond, B.C. V6X 214 Canada All stated specifications are approximate and subject to change without notice or obligation. All radios significantly exceed FCC regulations limiting spurious emissions 28H986

Work VHF or HF Packet On Any Computer With Kantronics Complete Packet Communicator KPC-2

From IBM to C-64, or any computer with an asynchronous serial port, you can now work packet on VHF or HF with one TNC, the KPC-2! Extra cost options are unnecessary. KCP-2 is packed full of features and backed by our full-time customer support departments. KPC-2 has totally new hardware and software, Kantronics designed. For more information contact Kantronics or a Kantronics dealer.

Suggested Retail \$-219.00 \$169

KPC-2 PACKET COMMUNICATOR II

Features

- AX.25 Version 2.0 software
- Supports multiple connects, up to 26
- RS232 or TTL compatible (C-64 too!)
- HF modem included! (both U.S. and European tones)
- Carrier Detect, and software squelch operation
- FCC Part 15 Certified
- Kantronics industry standard extruded aluminum case
- Power supply and cabling included
- All EPROM software is Kantronics sourced and copyrighted

- 128K EPROM, 16K RAM expandable to 32K, 4K EEPROM.
- Advanced software HDLC routines, eliminating costly out-ofdate chips

Customer Support

- Extensive dealer network
- In-house programmers/engineers
- In-house service representatives
- Periodic software updates (like 2.0!)

Want more information on Packet? Contact us about our new PACKET VIDEO. \$ 25.00 (shipping included), VHS or BETA format.

RF Data Communications Specialists 1202 E. 23 Street Lawrence, Kansas 66046 (913) 842-7745

KENWOOD

... pacesetter in Amateur radio

DX-cellence!"

The new TS-940S is a serious radio for the serious operator. Superb interference reduction circuits and high dynamic range receiver combine with superior transmitter design to give you no-nonsense, no compromise performance that gets your signals through! The exclusive multi-function LCD sub display graphically illustrates VBT, SSB slope, and other features.

- 100% duty cycle transmitter. Super efficient cooling system using special air ducting works with the internal heavy-duty power supply to allow continuous transmission at full power output for periods exceeding one hour.
- . High stability, dual digital VFOs. An optical encoder and the flywheel VFO knob give the TS-940S a positive tuning "feel."
- Graphic display of operating features.

Exclusive multi-function LCD sub-

display panel shows CW VBT, SSB slope tuning, as well as frequency, time, and AT- 940 antenna tuner status.

- Low distortion transmitter. Kenwood's unique transmitter design delivers top "guality Kenwood" sound.
- Keyboard entry frequency selection. Operating frequencies may be directly entered into the TS-940S without using the VFO knob.
- QRM-fighting features. Remove "rotten QRM" with the SSB slope tuning, CW VBT, notch filter, AF tune, and CW pitch controls.
- · Built-in FM, plus SSB, CW, AM, FSK.
- Semi or full break-in (QSK) CW. 40 memory channels. Mode and frequency may be stored in 4 groups of 10 channels each.
- Programmable scanning. General coverage receiver.
- Tunes from 150 kHz to 30 MHz. I yr. limited warranty
- Another Kenwood First!

Optional accessories: AT-940 full range (160-10m) automatic antenna tuner = SP-940 external



Pated

speaker with audio filtering . YG-455C-1 (500 Hz), YG-455CN-1 (250 Hz), YK-88C-1 (500 Hz) CW filters; YK-88A-1 (6 kHz) AM filter = VS-1 voice synthesizer SO-1 temperature compensated crystal oscillator = MC-43S UP/DOWN hand mic. • MC-60A, MC-80, MC-85 deluxe base station mics. . PC-1A phone patch = TL- 922A linear amplifier SM-220 station monitor

 BS-8 pan
 BS-8 pan

 display = SW-200A and SW-2000 SWR and power meters.



Complete service manuals are available for all Kenwood transceivers and most accessories

Specifications and prices are subject to change without notice or obligation



from authorized Kenwood dealers.

KENWOOD U.S.A. CORPORATION

2201E. Dominguez St., Long Beach, CA 90810 P.O. Box 22745, Long Beach, CA 90801-5745



contents

- 8 solar activity and the earth's magnetosphere Bradley Wells, KR7L
- 21 better frequency stability for the Drake TR7 Urs Hadorn, HB9ABO
- 32 BASIC program analyzes simple ladder networks Ed Wetherhold, W3NQN
- 39 VHF/UHF world: minimum requirements for 2-meter EME — part 1 Joe Reisert, W1JR
- 53 ham radio techniques Bill Orr, W6SAI
- 60 designing trap antennas: a new approach Yardley Beers, W0JF
- 73 practically speaking: battery problems – part 2 Joe Carr, K4IPV
- 79 convert a \$25 CB HT for 6 meters Peter Bertini, K1ZJH
- 91 Elmer's notebook Tom McMullen, W1SL
- 98 advertisers index and reader service
 6 comments
 82 DX forecaster
 90 flea market
 - 88 ham mart 84 new products 4 reflections 41,95 short circuits

AUGUST 1987

volume 20, number 8

T. H. Tenney, Jr., W1NLB publisher

> Rich Rosen, K2RR editor-in-chief and associate publisher

Dorothy Rosa, KA1LBO managing editor

> Tom McMullen, W1SL Joseph J. Schroeder, W9JUV Alfred Wilson, W6NIF associate editors Susan Shorrock editorial production

editorial review board

Peter Bertini, K1ZJH Forrest Gehrke, K2BT Michael Gruchalla, P.E. Bob Lewis, W2EBS Mason Logan, K4MT Vern Ripportella, WA2LQQ Ed Wetherhold, W3NQN

publishing staff J. Craig Clark, Jr., N1ACH assistant publisher

Rally Dennis, KA1JWF director of advertising sales

Dorothy Sargent, KA1ZK advertising production manager Susan Shorrock

circulation manager Therese Bourgault circulation

National Center for Atmospheric Research/NASA cover

ham radio magazine is published monthly by Communications Technology, Inc. Greenville, New Hampshire 03048-0498 Telephone: 603 878-1441

subscription rates

United States: one year, \$22.95; two years, \$38.95; three years, \$49.95 Canada and other countries (via surface mail): one year, \$31.00; two years, \$55.00; three years, \$74.00

All subscription orders payable in U.S. funds, via international postal money order or check drawn on U.S. bank

international subscription agents: page 89

Microfilm copies are available from University Microfilms, International Ann Arbor, Michigan 48106 Order publication number 3076 Cassette tapes of selected articles from hain radio are available to the blind and physically handicapped

from Recorded Periodicals, 919 Walnut Street, Philadelphia, Pennsylvania 19107

Copyright 1987 by Communications Technology, Inc. Title registered at U.S. Patent Office

Second-class postage paid at Greenville, New Hampshire 03048-0498 and at additional mailing offices ISSN 0148-5989

ηΡ_w

Send change of address to *ham radio* Greenville, New Hampshire 03048-0498

August 1987 🌆 3



evolution

In September, 1983, we published a survey soliciting your opinion on a number of subjects. In that survey, we asked about your use of computers, including any that you owned or had access to. In your responses, 50 percent of you answered affirmatively. Many of you — even those who were "computerized" — indicated clearly that you did not wish to see *ham radio* turn into yet another "computer book."

Since that time, however, the complexion of Radio Amateurs has changed. What used to be packet freckles can now be likened to a full tan after basking in the warmth of this useful and entertaining mode of communication. Most who predicted the yearly growth rate of this digital phenomenon were wrong, erring on the low side. *ham radio*, for its part, published articles that emphasized some of the more technical aspects of packet radio, such as TEXNET's recent three-part series on packet networking (March, April, and June, 1987).

Concurrently, even though statistics indicated a higher median and mean age of Radio Amateurs, some of the faces started to look younger, with Novice Enhancement bringing in a welcome influx of youth.

One concern raised by many readers responding to the survey brings new wrinkles to the face of Amateur Radio; many voiced and continue to voice the opinion that no one's building any more. Does anybody build any more? Well, it depends on how you define building. Yes, it's true that far fewer of us design and build our own receivers and transmitters nowadays, but this is quite understandable in light of the abundance of high performance and versatile commercial units available. With few exceptions, there's simply no need to build equipment today; without running a cost analysis, I'd almost be willing to bet that on a percentage basis the cost of a present-day rig eats up less of your earned income than a state-of-the-art rig would have consumed 10, 20, or 30 years ago.

From what I see in the manuscripts that arrive here, it appears that there's been a redirection or refocusing of attention to the more sophisticated technologies and techniques. A trend seen years ago in the Aerospace industries a "systems" approach to construction — is now evident in Amateur projects. Recognizing that "soup-to-nuts" designs were no longer cost-effective, aerospace industries turned to modular construction, letting those individuals or companies who could build a better mixer, for example, supply that component. This same trend, I believe, has permeated Amateur Radio; it's just not cost-effective to build a 2-meter station when, for a few hundred dollars, you can buy a multi-function miniaturized unit. Personally, I'll still repair them . . . but try to compete on a design/construction basis? No way! I don't know how you value your time, but I can assure you that the price tag I'd put on a similar unit that I'd built would have to be a lot higher than the one you'd find on any off-the-shelf unit.

There's an inherent danger lurking in this path of reasoning, however: we don't want to become jacks of all trades and masters of none. I reconcile this dilemma by reading more, zeroing in on several specific areas of technical interest, and using computers more than ever before. Sometimes I just have to sit back and laugh at the amount of time I spent preparing a 24-hour propagation forecast by hand for just one point-to-point path a few years ago. It took hours. This process is now reduced to seconds with affordable computers . . . which is my next point: we're still constructors — but what we're "building," in many cases, are computer routines instead of hardware. I don't think it's fair to say which is more related to Amateur Radio. Like everything else, Amateur Radio is evolving through a logical sequence of events.

All I ask of you is to provide me with a glimpse of your new interests, regardless of the form (i.e., hardware or computer programs) they take. Let us help in the evolutionary process by sharpening the focus and providing a few more details.

Rich Rosen, K2RR Editor-in-Chief

KENWOOD

... pacesetter in Amateur Radio



Here's One for You! TM-221A/321A/421A

2 m and 70 cm FM compact • TM-221A receives from 138mobile transceivers • TM-221A receives from 138-173.995 MHz. This includes to

The all-new TM-221A, TM-321A and TM-421A FM transceivers represent the "New Generation" in Amateur radio equipment. The superior Kenwood GaAs FET front end receiver; reliable and clean RF amplifier circuits, and new features all add up to an outstanding value for mobile FM stations! The optional RC-10 handset/control unit is an exciting new accessory that will increase your mobile operating enjoyment!

- TM-221A provides 45 W, TM-321A, 25 W. The TM-421A is the first 35 W 70 cm mobile! All three models have adjustable 5 W low power.
- Selectable frequency steps for quick and easy OSY.

- TM-221A receives from 138-173.995 MHz. This includes the weather channels! Transmit range is 144-148 MHz. Modifiable for MARS and CAP operation. (MARS or CAP permit required.) (Specifications guaranteed for Amateur band use only.)
- TM-321A covers 220-224.995 MHz. The TM-421A covers 438-449.995 MHz.
- Built-in front panel selection of 38 CTCSS tones. TSU-5 programmable decoder optional.
- Simplified front panel controls makes operating a snap!
- 16 key DTMF hand mic., mic. hook, mounting bracket, and DC power cable included.
- Kenwood non-volatile operating system. All functions remain intact even when lithium battery

back-up fails. (Lithium cell

est. life 5 yrs.)

POWER

IOW

memory back-up-

Packet radio compatible!

- 14 full-function memory channels store frequency, repeater offset, sub-tone frequencies, and repeater reverse information. Repeater offset on 2 m is automatically selected. There are two channels for "odd split" operation.
- Programmable band scanning.
- Memory scan with memory channel lock-out.
- Super compact:
- approx. 1-1/2"Hx5-1/2"Wx7"D.
- New amber LCD display.
- Microphone test function on low power.
- High quality, top-mounted speaker.
- Rugged die-cast chassis and heat sink.

RC-10 Remote Controller For TM-221A/321A/421A. Optional telephone-style handset remote controller RC-10 is specially designed for mobile convenience and safety. All front panel controls (except DC power and RF output selection) are controllable from the RC-10. One RC-10 can be attached to two transceivers with the optional PG-4G cable. When both transceivers are connected to the RC-10, cross band, full duplex repeater

operation is possible. (A control operator is needed for repeater operation.)



KENWOOD U.S.A. CORPORATION

2201 E. Dominguez St., Long Beach, CA 90810 P.O. Box 22745, Long Beach, CA 90801-5745

M.IN MHZ KENWOOD 144MHz FM TRANSCEIVER TM-221A

SCAN

Optional Accessories:

VEO/M

 RC-10 Multi-function handset remote controller
 PG-4G Extra control cable, allows TM-221A/ TM-421A full duplex operation * PS-50/PS-430
 DC power supplies * TSU-5 Programmable CTCSS
 decoder * SW-100A Compact SWR/power/volt meter (18-150 MHz) * SW-100B Compact SWR/ power/volt meter (140-450 MHz) * SW-200A SWR/ power meter (18-150 MHz) * SW-200B SWR/power meter (140-450 MHz) * SWT-1 Compact 2 m

antenna tuner (200 W PEP) * SWT-2 Compact 70 cm antenna tuner (200 W PEP) * SP-40 Compact mobile speaker * SP-50B Mobile speaker • PG-2N Extra DC cable * PG-3B DC line noise filter * MC-60A, MC-80, MC-85 Base station mics. • MC-55 (8-pin) Mobile mic, with gooseneck and time-out timer * MA-4000 Dual band antenna with duplexer (mount not supplied) * MB-201 Extra mobile mount

Specifications and prices subject to change without notice or obligation Complete service manuals are available for all Kenwood transceivers and most accessories.



improving writing skills

Dear HR:

I'm writing this letter in response to conversations I had at the recent Dayton Hamvention[™] with you [Rich Rosen, K2RR], Bob Grove (editor of *Monitoring Times*), and several others of us who write for radio communications journals. There was considerable interest expressed by these persons in the possibility of organizing a meeting at next year's Hamvention that would be oriented toward those who write or would like to write — for radio communications journals.

The program could present several speakers who would cover various areas of interest. The first speaker, probably an editor from one of our popular journals, could address the question of what beginning writers need to know in order to begin writing for the journals. Another speaker, or perhaps better yet, a panel of speakers, could offer ideas for alreadypublished writers who want to improve their skills. Thirdly, a well-known, successful writer such as Joe Carr, K4IPV, Ed Noll, W3FQJ, or Bill Orr, W6SAI, might offer words of wisdom to aspiring writers who want to move up the ladder of professionalism in writing on the subject of radio technology.

As far as I know, there is no organized way for radio communications writers to contact one another, exchange information, or share ideas. In addition to being useful in its own right, the meeting proposed above might present a good opportunity for the founding of a writer's group or writer's newsletter for those of us who write for radio communications journals.

I hope that writers — both published and potential — who are interested in

any of these ideas will contact me with lists of the kind of information they'd like to see covered in such a program, and which writers and editors they would like to hear speak. If the feedback is sufficiently positive, perhaps I could approach the appropriate committee to see if such a program could actually be arranged for next year's Hamvention.

> W. Clem Small, KR6A Salisbury, Vermont 05769

grounding, shielding

Dear HR:

I enjoyed reading K4IPV's column, "Practically Speaking: Grounding, Shielding, and Isolating — Part 2," in the May issue of *ham radio*. However, I felt a few comments might be in order.

First, I think that readers would be more satisfied with the performance of one-inch, or even half-inch, copper strap in place of the suggested braid. Braid becomes increasingly inductive faster than strap or even heavy wire at the TVI frequencies the author is concerned with.

Second, I would strongly suggest that if brazing is inconvenient, silver solder should be used for all soldering that may be exposed to the elements. Regular solder seems to "decompose" when exposed to weather, leaving a joint that is electrically and often visually similar to a cold solder joint.

I hope these suggestions will improve someone's hamshack.

Gary D. Sharpe, KA8DKT Beaumont, Pennsylvania 18618

continuous phase tones

Dear HR:

Richard Ferranti's article, "Amateur FSK: A Spectral Analysis" (December, 1986, page 42) clearly makes the case for continuous phase tones for radio modems. This theme is even more pertinent if we directly modulate coherently the radio frequency carrier instead of using tones.

Modems were evolved for cables and telephone lines in order to make

data look like a sound spectrum. Their purpose was to overcome the inductance and capacitance of cables, and though the same technique will work on a radio channel, we have a much more linear system with a wider useful bandwidth.

I feel we should be using our data signals to shift the radio frequency carrier directly - i.e. without the use of audio tones.

Had the author extended his discussion from fm to SSB, he would have found that an on-the-air signal would be more or less two separate frequencies separated by the difference in the tones and the advantages of phase coherence would be very marked. However, the SSB method is complex and wasteful of power, and to apply the data in the generation of the carrier is simpler and cheaper. All that's required is to switch a small capacitor across the crystal — but beware of the effect of the synthesizer, which may turn the square waves into triangular ones.

Another way of generating coherent phase fm is to impress the data as ripple on the supply to a free-running oscillator. Work is going on along these lines for a radio link between computers and peripherals in an effort to overcome interference and security problems.

> R.J. Redding, G3VMR Maidenhead, Berks, SL63EL

modifying the MLA-2500 amp

Dear HR:

A lot of us still have Dentron MLA-2500 amps, which use the Eimac 8875s. You know what they cost to replace.

How about an article on modifying this amp to use less expensive tubes? I've had mine since 1978, and it's still OK, but when the 8875s go, I doubt if it will be worth \$700 or so for new ones.

Thanks for your fine magazine and keep up the good work!

Joe W. Williamson, KB5YA Killeen, Texas 76541

Ideas, anybody? -- Ed.



MFJ-9628 \$229.95

Run up to 1.5KW PEP and match any feedline continuously from 1.8 to 30 MHz: coax, balanced line or random wire.

Lighted Cross-needle Meter reads SWR, forward and reflected power in one glance. Has 200 and 2000 watt ranges. 6 position antenna switch handles 2 coax lines, random wire and balanced lines. 4:1 balun. 250 pf, 6 kv variable capacitors. 12 position ceramic Inductor switch. Smaller size matches new rigs: 103/4 x 41/2 x 14 7/8 inches. Flip stand for easy viewing. Requires 12V for light.

MFJ RANDOM WIRE TUNER

MFJ-16010 \$39.95 MFJ's ultra compact 200 watt random wire tuner lets you

operate all bands anywhere with any transceiver using a random wire. Great for apartment, motel,

camping. Tunes 1.8-30 MHz. 2x3x4 inches. ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO **OBLIGATION. IF NOT SATISFIED RETURN WITHIN 30** DAYS FOR A PROMPT REFUND (less shipping).

 One year unconditional guarantee
 Add \$5.00 each shipping/handling . Call or write for free catalog, over 100 products.

push buttons select three power ranges that give you QRP to full legal limit power readings. Reads 20/200/2000 W forward, 5/50/500 W reflected

and 1:1 to 1:5 SWR on easy-to-read two color scale. Lighted meter needs 12 V. ±10% full scale accuracy. 61/2x31/4x41/2 inches.

COMPACT SPEAKER MFJ-280 \$18.95

Mobile speaker. Tilt bracket on magnetic base. 31/2 mm phone plug. Use with 8 and 4 ohm impedances. Handles 3 watts audio

HANDHELD TELESCOPING

ANTENNAS WITH BNC MFJ-1710, \$9.95, 3/8 wave 2 meter. Pocket clip. 5³/4" · 24¹/2". MFJ-1712, \$14.95, 1/4 wave 2 meter; 5/8 wave 440 MHz, 71/4" - 19". MFJ-1714, \$16.95, 1/2 wave 2 meter. End-fed halfwave dipole. Shorter, lighter, more gain, less stress than 5/8 wave mounted on handheld. When collapsed it performs like rubber duck.



MFJ ENTERPRISES, INC. Box 494, Miss. State, MS 39762 MFJ . . . making quality affordable





Reader Service CHECK-OFF Page 98

August 1987 br 7

solar activity and the earth's magnetosphere

A close look at the energy source responsible for worldwide communications

Although Amateurs have been aware of a relationship between solar activity and ionospheric conditions since the earliest days of radio, concentrated studies in these areas did not begin until after the end of World War II. While many questions remain unanswered, we now have a large body of knowledge about solar activity and its effects on the Earth's magnetosphere, the region of charged trapped particles above the Earth controlled by our magnetic field. This information allows us to predict, with some degree of certainty, ionospheric activity and its effects on the parameters of hf radio propagation.

Such knowledge can provide some measure of solace to the intrepid DXer who, with an hour to spare from family obligations, has discovered that a Sudden lonospheric Disturbance is in progress or that Polar Cap Absorption has wiped out the short path to Europe. These disruptions are the result of changes within the ionosphere, brought about by earlier flares and eruptive prominences on the surface of the Sun; this activity, in turn, results from still earlier processes originating deep within the Sun's interior.

historical perspective

Our understanding of solar activity began when physicists calculated and tried to explain the enormous output of energy from the Sun. In 1871, Hermann von Helmholtz calculated its energy production as the equivalent of burning 1500 pounds of coal per hour on each square foot of the solar surface. Since ordinary chemical reactions cannot produce these energy levels, scientists realized that solar energy could not be explained in terms of conventional chemistry.

Some years later, Lord Kelvin proposed a solution to the problem, suggesting that solar energy could be attributed to the energy released from gravitational contraction; even if the solar surface contracted by 100 feet per year, the Sun could shine for 30 million years. However, geologists soon produced evidence that the Earth had existed for much longer than 30 million years, and astronomers were then compelled to devise new theories of solar energy.

nuclear energy

In the 1920s, scientists realized that nuclear reactions could provide the necessary vehicle for energy production. Chemical reactions involve interactions only between the electron structures of various atoms. Nuclear reactions - whether by fission or fusion involve the release of energy through the restructuring of an atom's nucleus. Nuclear fusion reactions, they found, do two things within a star: they provide a tremendous amount of energy and, over long periods of time, change its composition. In a dwarf star such as our Sun, the primary reaction is believed to be the proton-proton cycle, in which hydrogen nuclei fuse into helium nuclei. However, studies done in recent years question this supposition, asserting that the proton-proton cycle involves the release of neutrinos (neutral, massless, high-energy particles) as part of the reaction. Fewer neutrinos than expected, however, have been detected, and it's not known whether this is the result of experimental error, prediction error, or stellar core inactivity.

In larger stars, with their higher core temperatures, the CNO (carbon-nitrogen-oxygen) cycle is dominant. Either fusion process liberates energy by changing a small amount of mass into energy. In the protonproton cycle, about 0.007 grams of matter are converted to energy for each gram of hydrogen processed into helium. Every second, the Sun converts 4 million

By Bradley Wells, KR7L, 1290 Puget Drive East, Port Orchard, Washington 98366 tons of solar matter into 400 trillion trillion watts of energy and radiates it into space.

30,000-year trip

Most of the energy generated within the core of the Sun heats its photosphere, the bright surface layer of gas that radiates the visible light of the Sun. The energy that heats the photosphere today, however, was generated eons ago.

The gas within the Sun's core, compressed to a density 150 times that of water, prevents radiation from traveling directly to the Sun's surface. The movements of photons within the Sun's interior move in a highly erratic motion known as "random walk" (rather than straight-line free flight). The thermal radiation associated with the 15 million degrees Kelvin temperature of the solar core is hard* X-rays, which move an average of only half a centimeter before they crash into a material particle and are absorbed or scattered in a completely different direction. Through this process, these X-rays are gradually degraded into optical photons with lower energy levels. Consequently, it takes 30,000 years for a photon to "walk" out of the Sun; a photon in free flight, on the other hand, would be freed in 2 seconds. Thus, the current appearance and activities of the photosphere were determined by the core conditions some 30 millennia ago.

The temperature of the photosphere can be determined from the following relationship:

$$T = \frac{0.290}{W} \tag{1}$$

where W = wavelength in cm, and T = temperature in degrees K.

Since the wavelength of maximum radiation in the solar spectrum is 5.1 \times 10⁻⁵ cm, this corresponds to a temperature of 5700 degrees Kelvin.

The apparent sharply defined surface of the Sun is attributable to changes in the opacity of its surface gas. The gas at the bottom of the photosphere has a high proportion of negative hydrogen ions that obstruct light, causing high opacity. A few hundred kilometers above this layer, near the top of the photosphere, negative hydrogen ions are fewer; this renders the gas clearer and less opaque. Most of the Sun's light comes from this layer. This layer — where photons make the transition from "walking" to flying is very thin, measuring only 0.1 percent of the Sun's radius. Because it's thin, and because of its abrupt changes in opacity, it appears as a sharply defined surface, just as cumulus clouds in the sky appear to be solid. The gases of the Sun and solar atmosphere comprise a plasma, often referred to as the fourth state of matter. Relatively rare on Earth, plasma normally exists only in regions of extreme temperatures and is composed of positive ions and free electrons, although it's electrically neutral in bulk composition. In the magnetic fields of the Sun, these ions and electrons cannot move freely, but must stream in directions dictated by magnetic lines of force. For this reason, much of the solar atmosphere moves in particular patterns following twisted and intricate magnetic fields.

Photographs of the solar surface show a pronounced granulation. Each of these "grains" is a convection cell measuring 1000-2000 km across, rising at a vertical rate of 2 to 3 km/sec, and lasting only a few minutes. The dark areas between grains mark the regions where cooled gas descends again into the Sun. Large-scale patterning of individual granules is called supergranulation; this involves areas some 30,000 km in diameter, with gas flowing horizontally toward the outer edge of each cell. Surging motions, with wavelengths of 5000 km and periods of 5 minutes, have been observed within these areas.

Between these areas of supergranulation are spicules, small needle-like structures that form the lower half of chromospheric loops and are best seen on the limb of the Sun, where they appear in emission. Since the temperature is too high or the density is too low to scatter much light in the upper part of the loop, these portions tend to remain invisible. Consequently, what is seen of this gas are flames that erupt and fade in periods lasting from 2 to 5 minutes. They form a transition from the photosphere to the overlying chromosphere, the lower layer of the solar atmosphere. Visible to the naked eve during a total eclipse as a ring of small, intense red flames encircling the Sun, the chromosphere is about 2500 km thick, and the temperature in its upper regions exceeds 10,000 degrees Kelvin.

the corona

Above the chromosphere is the solar corona, a pale glowing halo of gas surrounding the Sun. Gas density here is very low, having dropped by a factor of 10,000 from the photosphere to the chromosphere and again by 10,000 between the chromosphere and the lower corona. Like the chromosphere, the corona is normally visible to the naked eye only during a total eclipse. This region emits only one millionth the amount of light produced by the photosphere, yet its temperature is 1 to 2 million degrees Kelvin.

When gases are heated, they become ionized, losing one or more electrons. In the corona, hydrogen and helium are essentially bare nuclei, while the electron shells of heavier elements are severely depleted. This

^{*} X-rays have wavelengths $(10^{-7} \text{ to } 10^{-10} \text{ cm})$ which are considerably shorter than visible light. Hard X-rays are at the short wavelength end of that 1000:1 spectrum. -- Ed.

Wide Dynamic Range and Low Distortion – The Key to Superior HF Data Communications

- Dynamic Range > 75 dB
- 400 to 4000 Hz
- BW Matched to Baud Rate
- BER < 1 X 10^{-5} for S / N = 0 dB
- 10 to 1200 Baud
- Linear Phase Filters



ST-8000 HF Modem

Real HF radio teleprinter signals exhibit heavy

fading and distortion, requirements that cannot be measured by standard constant amplitude BER and distortion test procedures. In designing the ST-8000, HAL has gone the extra step beyond traditional test and design. Our noise floor is at -65 dBm, not at -30 dBm as on other units, an extra 35 dB gain margin to handle fading. Filters in the ST-8000 are all of linear-phase design to give minimum pulse

- 8 Programmable Memories
- Set frequencies in 1Hz steps
- Adjustable Print Squelch
- Phase-continuous TX Tones
- Split or Transceive TX/RX
- CRTTuning Indicator
- RS-232C, MIL-188C, or TTL Data
 Mark or Space-Only Detection
- 8,600, or 10K Audio Input
- Signal Regeneration
- Variable Threshold Diversity
- RS-232 Remote Control I/O
- 100-130/200-250 VAC, 44-440 Hz 8 or 600 Ohm Audio Output
- AM or FM Signal Processing
- 32 steps of M/S filter BW
- Diaital Multipath Correction
- · FDX or HDX with Echo
- Spectra-Tune and X-Y Display
- Transmitter PTT Relay

distortion, not sharp-skirted filters with high phase distortion. All signal processing is done at the input

tone frequency; heterodyning is NOT used. This avoids distortion due to frequency conversion or

introduced by abnormally high or low filter Q's. Bandwidths of the input, Mark/Space channels, and

standard features of the ST-8000 include:

post-detection filters are all computed and set for

the baud rate you select, from 10 to 1200 baud. Other

- Code and Speed Conversion
- Signal Amplitude Squelch
- Receive Clock Recovery
- 3.5" High Rack Mounting

Write or call for complete ST-8000 specifications.



HAL Communications Corp.

Government Products Division Post Office Box 365 Urbana, Illinois 61801 (217) 367-7373 TWX 910-245-0784 high degree of ionization is one characteristic of extremely high temperatures.

These high temperatures were deduced from early spectroscopic studies. For a number of years, however, this evidence was discounted because it apparently violated the second law of thermodynamics, which states that heat cannot spontaneously flow from a cool object (the photosphere at 5700 degrees Kelvin) to a hotter one (the corona at 1 to 2 million degrees Kelvin). So fundamental was this objection that for several decades physicists refused to accept spectroscopic analysis at face value. Finally, in the 1940s, the idea of a truly hot corona was accepted and progress was made in coming to terms with this apparent contradiction. It now appears that magnetic effects and shock waves from subsurface convection are responsible for the transfer of large amounts of energy to the corona.

Early photgraphs of the corona taken during total eclipses showed it as a bland sphere of gas whose shape was dependent upon the phase of the solar cycle. During the years of high solar activity, it completely surrounded the Sun. In years of minimal activity, it was concentrated along the equator, with little gas visible in the polar regions. More recent studies conducted at a variety of wavelengths, particulary ultraviolet and X-ray, confirm this phenomenon and also show that the corona is not static, but rather an area of complex activity and turbulent motion.

Transient features of the corona include loops, streamers, and holes that seem so prevalent that some astronomers believe there may be no such thing as a "quiet" corona. Coronal features may be even more transient than once believed. Multiple photographs taken during any solar eclipse provide some evidence of movement in these features even during this very short period of time.

magnetic field has major influence

Individual loops and streamers suggest the patterns formed when iron filings are sprinkled near a magnet. The structure of the Sun's magnetic field imposes itself on the coronal gas. The interaction of this gas and the Sun's magnetic field is governed by the basic laws of electromagnetism. A charged particle in a magnetic field is subjected to a force that depends on its charge, its velocity, and the strength of the magnetic field. Only components of the particle's motion that are at right angles to the field are affected, with the net result that charged particles move in helical paths around the magnetic lines of force. Put another way, a particle is free to move in the direction of the field, but if it's pushed at right angles to the field, it moves in a circle rather than in a straight line. Thus, charged paticles in a magnetic field are said to be "frozen" to

the field, and free to move only in the direction of the field's lines of force.

Since the coronal plasma is highly ionized, the corona is an excellent electrical conductor and can sustain large electric currents. These currents, in turn, give rise to magnetic fields that modify the original magnetic fields. This two-way interaction gives the corona a complexity that is simply unavailable in a non-conducting gas.

Studies have indicated that transient events, such as coronal loops, may be uplifted by magnetic buoyancy. Regions with strong magnetic fields are buoyed up by the surrounding gas within the corona. These loops may suddenly become unstable and rise rapidly through the corona. Causes of this instability may be the random motion of photospheric gas at the base of a magnetic loop or the response to a violent photospheric event such as a solar flare.

generation of solar wind

Since magnetic loops are bound to the solar surface at both ends, there's no way for the coronal gas in these loops to escape into interplanetary space. However, in the regions where the Sun's magnetic lines of force stretch infinitely outward, the solar wind can escape along these field lines. It's now believed that much of the solar wind material, especially the high-speed streams, originates within these coronal holes.


Coronal transient events may provide another avenue for escape of material into space. If a closed loop becomes unstable, it can rise and expand to the point at which its field lines open up, ejecting material from the Sun. Observations have also revealed the existence of coronal "bullets" — knots of cool, dense material that are accelerated through the corona and may contribute to this outflow from the Sun.

sunspots

Sunspots are the Sun's most obvious surface feature. Very large groups may be visible to the naked eye, particularly when the solar disk is obscured by thin clouds or fog.

A sunspot is essentially a broad, shallow depression in the photosphere. The umbra, or central floor of the depression, appears dark because its temperature is 1700 degrees Kelvin below the temperature of the surrounding photosphere. At this lower temperature, it emits only one-quarter the light of the surrounding gases. It's believed that the lower temperatures associated with the umbra are due, in part, to intense magnetic fields, first discovered by observation of Zeeman splitting in spectral emission lines.* Individual

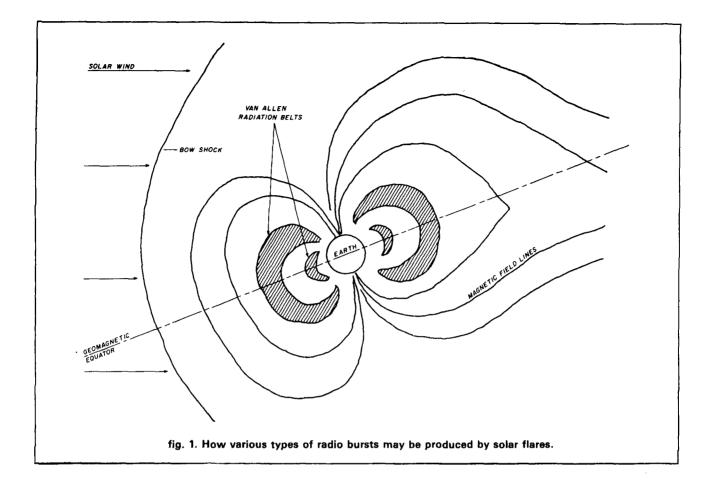 $^{^{\}ast}$ Splitting of the line spectrum of a light source by the influence of a magnetic field. — Ed.



magnetic fields, centered in the umbra, have a typical intensity of 3000 gauss* and are confined and compressed by the surrounding gases. Magnetic fields of this strength can be duplicated on a small scale within a laboratory environment. It's interesting to note that in such a field it's nearly impossible to maintain your grip on a metallic object; a wrench or screwdriver will literally tear itself out of your hand and slam up against one pole of the magnet.

The sunspot umbra is surrounded by the penumbra, a gray striated border of material that slopes up and outward from the umbra to the surrounding photosphere. The magnetic field emerging from the umbra spreads out across the penumbra. At some distant point, this field is again compressed and reenters the solar surface, often in a neighboring sunspot of opposite magnetic polarity. As the magnetic lines of force arch up between the two sunspots, a "moat" — an area outside the sunspot, beneath the magnetic arch, that is essentially free of any magnetic influence sometimes forms.

Sunspots are normally found in bipolar groups with opposite magnetic polarities. Their magnetic fields nor-


mally run east and west and are of opposite polarities on either side of the solar equator. The differential rotation of the Sun is the mechanism thought responsible for this. Because the Sun behaves as a fluid rather than solid sphere, surface rotational velocities vary with distance from its equator. The time required for one complete rotation ranges from 27 days in equatorial regions to 33 days near the poles. This unequal movement drags the entrapped magnetic lines of force around, under the solar surface, winding them tighter and tighter. The formation of sunspots, with their associated disturbances, begins to disrupt these fields. They become increasingly chaotic and, eventually, are neutralized as a new cycle of opposite polarity begins.

sunspot cycle

Individual sunspot groups may last from a few weeks to several months. The first spots in a new 11-year cycle appear in a broad band centered around the 40-degree north and south latitudes. As the cycle progresses, succeeding new spots migrate toward the equator. The regions of sunspot formation die out as they approach the equator and, simultaneously, sunspots of a new cycle appear at midlatitudes.

Huge clouds of gas called prominences are ejected from these sunspot regions. There are two types:

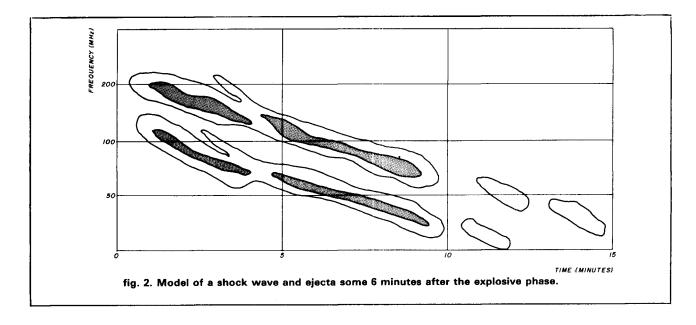^{*} Compare this to the considerably smaller magnetic field surrounding the Earth. - Ed.



eruptive and quiescent. Eruptive prominences move outward from the photosphere with velocities of 1000 km/sec. Quiescent prominences are masses of flowing gas held in relatively fixed positions above the Sun for hours or days by constraining magnetic fields.

flares

The largest blasts of energy and material on the surface of the Sun are flares. A single large solar flare may release the explosive power of 100 million hydrogen bombs, each with a yield of 100 megatons. Flares are normally observed in the light of hydrogen or ionized calcium. The largest, called "white-light" flares, are visible to the naked eye. All involve the highspeed ejection of material from the surface of the Sun. Not visible to optical telescopes is the cloud of electrons ejected by a flare, which is detectable only by radio telescope.

The regions of the Sun where flare energy is released are probed most directly by observation of centimeter radio emissions (listen to WWV at 18 minutes after the hour for the solar flux — 10.7 cm numbers) and the detection of hard X-rays. Continued observations at these wavelengths has led to some understanding of pre-flare conditions and flare activity. Pre-flare buildup is observed at centimeter wavelengths as small areas of increased brightness that exhibit shifts in polarization. At times, these regions show polarization increases of 100 percent and brightness temperatures of 10 million degrees (a measure of radio intensity rather than actual temperature).

Three types of flare models, each with their own distinctive magnetic structure (**fig. 1**), have been proposed. In one type, currents run along field lines arranged in isolated loops to form a sheared magnetic field capable of producing instabilities. The second

type involves current sheets at the interface of two loops having opposite magnetic polarities. The third type offers large-scale current sheets between open magnetic field lines. The variation of radio wave polarization with time indicates the primary release of energy occurring by magnetic reconnection in very localized areas. This energy release is rapid, being distributed throughout the magnetic loop in less than 10 seconds. In every case, the size and shape of the magnetic field undergoes major transformations an hour or so before a flare, with the primary release of energy occurring in the upper portions of isolated loops.

The progress of a flare (fig. 2) may be divided into two phases. In the first, the visually observable flare appears with strong emissions in the hydrogen (Balmer) alpha line (6560 Å units, red light) and is accompanied by the ejection of an electron jet at velocities up to half the speed of light. As they recede from the Sun, these particles are slowed through interactions with the solar magnetic field and the surrounding solar atmosphere. During this initial phase, X-rays and centimeter radio waves are generated in the region of the optical flare. As the flare moves upward through the layers of the solar atmosphere, radio energy is detected at progressively longer wavelengths. This "synchrotron" radio emission originates as these relativistic electrons spiral in the magnetic fields. The initial radio energy from a flare is designated as a Type Il radio burst; it serves as the chief diagnostic tool for investigation of flare activity and the solar corona. Type II bursts (fig. 3) are characterized by narrow bands of intense radio emission that drift slowly toward lower frequencies. Generally composed of a fundamental frequency and second harmonic, this dual-frequency emission is characteristic of oscillations within a plasma.



Cards and plaque courtesy W6TC

EIMAC's new DX champion! The 3CX800A7.


Varian EIMAC continues to commit its development of reliable tubes for HAM radio.

The new, rugged 3CX800A7 power triode provides 2 kW PEP input for voice service or 1 kW cw rating up to 30 MHz. Two tubes will meet the new, higher power ratings authorized by the FCC.

Designed for today's low profile, compact linear amplifiers, the 3CX800A7 powerhouse is only 21/2 inches (6.35 cm) high. Cooling requirements are modest and a matching socket, air chimney and anode clamp are available.

A data sheet and more information is available from Varian EIMAC. Or the nearest Electron Device Group sales office. Call or write today.

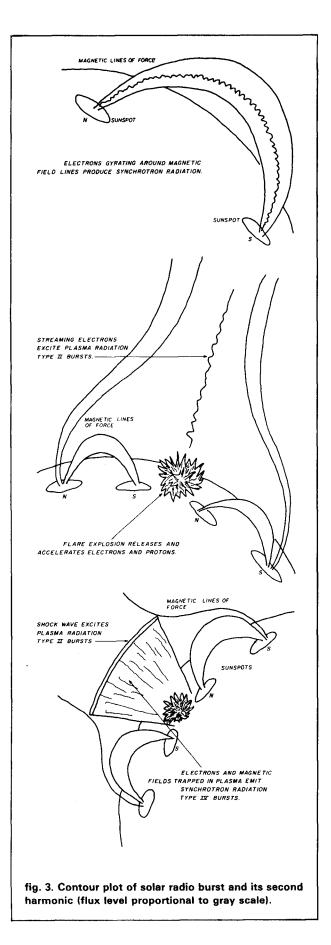Varian EIMAC 301 Industrial Way San Carlos, California 94270 Telephone: 415+592-1221



The natural vibration frequency of a plasma is directly related to its electron density. Density decreases with altitude above the Sun's surface; therefore, the lower the frequency, the greater the height of origination above the photosphere. The velocity of a shock wave can be determined by its frequency drift; shock wave velocities up to 3000 km/sec have been observed.

The shock front formed by a solar flare is believed to be quite thin, averaging only 1000 km from front to back. As such, it will move through a given point in the solar atmosphere in less than a second. Shock fronts form only when the wave velocity exceeds a critical value called the Alfven velocity, which is to magnetic waves what the speed of sound is to acoustic waves. It is determined by the strength of a region's magnetic field and electron density.

In the second phase of flare activity, a gas cloud moves up behind the electron jet, but at a much lower velocity. If this material is expelled at a speed greater than 500 km/sec, it will also generate a shock wave that expands outward ahead of it. Since the solar atmosphere has a relatively low density and strong magnetic field, this shock wave becomes a fastmoving magnetic disturbance rather than the more familiar pressure wave. Rising through the corona, it generates radio emission at the leading edge of the cloud as it pushes through the tenuous solar atmosphere. The ejection of this material is also accompanied by a Type IV radio flare, which takes the form of broadband emission over a wide range of frequencies.

During a solar flare, the total visible radiation changes by much less than 1 percent; however, ultraviolet and X-ray radiation may increase a hundredfold. When this radiation strikes the ionosphere, it changes the amount and distribution of free electrons. These shifts in electron density, in turn, affect the refractive characteristics of the ionosphere.*


Although the radio output of the Sun is very small in comparison to its output at visible wavelengths, radio output is highly variable and tends to follow the 11-year solar cycle. During a large flare, the radio energy of the Sun may increase a millionfold for short periods.


In spite of this increased activity outside the visible spectrum, the radiative output of the Sun remains relatively constant, with short-term variations of less than 1 percent. This energy amounts to 1400 watts per square meter at the distance of the Earth. Small-scale, long-term variations in this "solar constant" follow the 11-year sunspot cycle and other, longer, less easily determined cycles.

delay effects of solar "bombardment"

Solar particles ejected from the Sun travel much

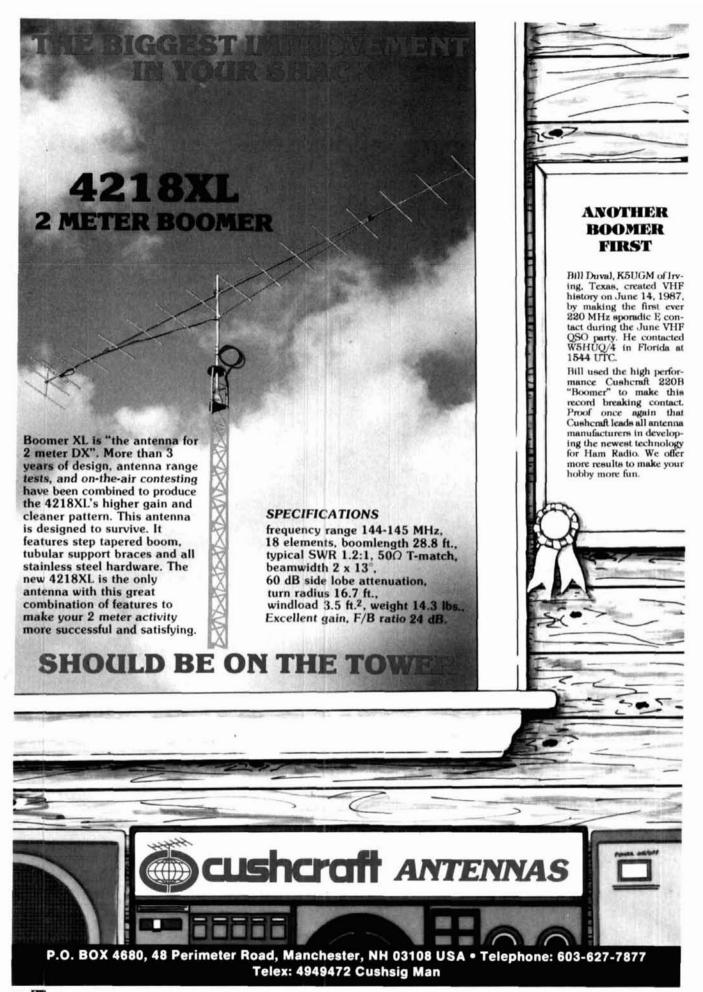* Which, of course, is the main focus of our attention. - Ed.



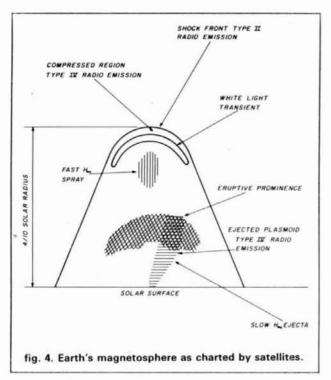


more slowly than its electromagnetic radiation. It takes some 24 to 36 hours after an event before they impinge on the upper atmosphere, changing its chemistry and creating aurorae.* These colored, swirling patterns of light are visible around the Earth's north and south magnetic poles.

Magnetic fields from the surface of the Sun are frozen into the solar wind and drawn out by the flow. The magnetized plasma of the solar wind cannot easily penetrate the closed magnetic field of the Earth. Consequently, as the solar wind encounters the Earth's magnetosphere, a shock wave (fig. 4) develops. This bow shock, formed 60,000 km on the "upwind" side of the Earth, is analogous to the shock wave that forms in front of an aircraft moving at supersonic speeds. However, the Earth's bow shock isn't fixed in position, but moves back and forth in response to pulses of energetic particles streaming out of the Sun. Beyond this wave, the solar wind plasma flows much more slowly around the Earth's magnetic field.

the Van Allen belt


If captured by the Earth's magnetic field, particles from the Sun form two doughnut-shaped belts or rings around the Earth. These were discovered in 1958 by James Van Allen, using particle counters aboard Explorer 1, the first United States satellite. The inner Van Allen belt is about 2500 km and the outer Van Allen ring is about 15000 km above the Earth's magnetic equator. Particles temporarily stored in these

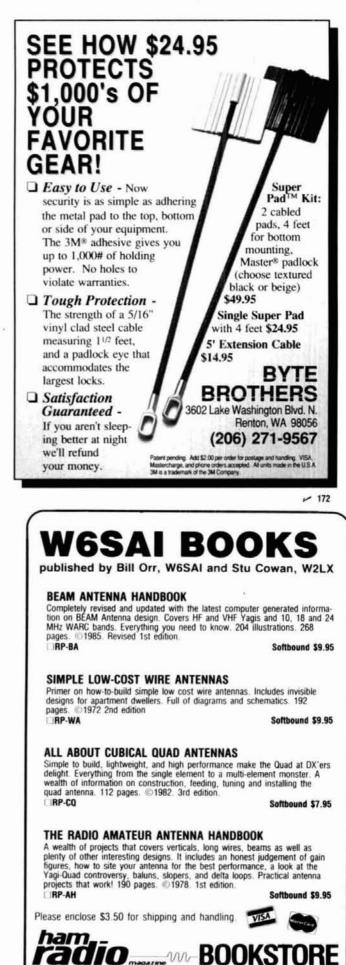 This helps explain short-term F2 layer enhancement followed a day or two later by higher absorption — as experienced on 80 meters, for example. — Ed.



GREENVILLE, NH 03048

(603) 878-14

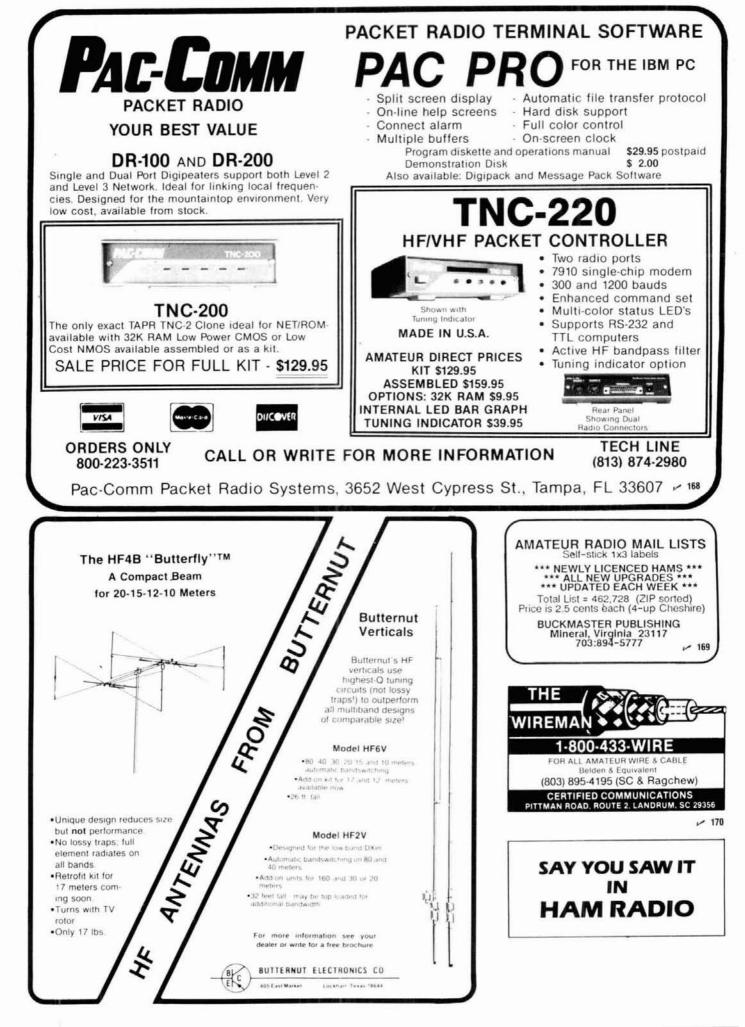

belts oscillate back and forth along the lines of force of the Earth's magnetic field. Eventually they leak out the ends of these magnetic "bottles" and into the Earth's atmosphere. Here, these ions collide with upper atmosphere air molecules, causing spectral emission lines whose color is determined by the elements and collision energies involved.

The Van Allen belts are one manifestation of the interaction of the Earth's magnetosphere with the solar wind. The supply of ions and electrons forming the Van Allen belts is continuously replenished by the solar wind. By the time it reaches the Earth, this wind has a density of 5 ions per cubic centimeter and moves with an average velocity of 500 km/sec (about a million miles per hour). These values increase dramatically during periods of intense solar activity.

The electrons circulating in the Van Allen belts also generate an enormous amount of radio energy. This synchrotron radio emission may reach power levels of 1 billion watts at frequencies between 100 and 300 kHz. Fortunately, the ionosphere forms a normally effective barrier preventing radio energy with wavelengths greater than 100 meters from reaching the Earth's surface. It's interesting to note that Grote Reber, the amateur radio astronomy pioneer, constructed a large dipole array in Tasmania which can "see" through the ionosphere at a wavelength of 300 meters on the occasional nights when the electron density of the ionosphere falls to abnormally low values.

The ability of the various layers within the ionosphere to refract radio energy is determined by a number of factors. The time of day, season of year, phase of the sunspot cycle, transient solar events, and the Sun's core conditions 30,000 years ago all affect hf radio communications at this moment. The continued study of the Earth's magnetosphere and the Sun's atmosphere may eventually allow us to forecast, with increasing certainty, the hourly state of the ionosphere and its impact on hf communications.

bibliography

1. Briggs, John, "Shortwave Detection of Solar Flares," Sky and Telescope, November, 1984, page 452.

 Foukal, Peter, "Magnetic Loops in the Sun's Atmosphere," Sky and Telescope, December, 1981, page 547.

3. Hartmann, William K., Astronomy: The Cosmic Journey, Wadsworth Publishing Company, Belmont, California, 1978.

 Kraus, John, Our Cosmic Universe, Cygnus-Quasar Books, Powell, Ohio, 1980.

5. Kundu, M.R., "Probing The Radio Sun," Sky and Telescope, July, 1982, page 6.

6. Maffie, Paolo, Beyond The Moon, The MIT Press, Cambridge, Massachusetts, 1979.

7. Maran, Stephen, "The Sun's Violent Flares," Popular Science, June, 1981, page 66.

 Maxwell, Alan, "Solar Flares and Shock Waves," Sky and Telescope, October, 1983, page 285.

 Moore, Patrick, The Rand McNally New Concise Atlas of the Universe, Rand McNally and Company, New York, New York, 1978.

10. Parker, E.N., "The Sun," Scientific American, September, 1975, page 43.

11. Shields, John, "Backyard Radio Astronomy," Astronomy, March, 1982, page 75.

12. Shu, Frank H., *The Physical Universe*, University Science Books, Mill Valley, California, 1982.


Stafford, Edward, Sun, Earth and Man, NASA, Washington, D.C., 1982.
 Van Allen, James, "Interplanetary Particles and Fields," Scientific American, September, 1975, page 161.

15. Wild, J.P., "Radio Waves From the Sun," *Scientific American*, June, 1955, page 40.

16. Wolfson, Richard, "The Active Solar Corona," Scientific American, February, 1983, page 104.

ham radio

K.V.G. CRYSTAL PRODUCT		1		D B
MODEL A XF-9A G XF-9B S XF-9B-01 L XF-9B-02 L XF-9B-10 S XF-9C XF-9C XF-9D XF-9C XF-9E XF-9D XF-9E XF-9D	AM AM FM 1 CW	Band- width 2.4 kHz 2.4 kHz 2.4 kHz 2.4 kHz 2.4 kHz 2.4 kHz 2.4 kHz 3.75 kHz 5.0 kHz 2.0 kHz 500 Hz	Poles 5 8 8 8 10 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8	Price \$61.00 83.00 110.00 145.00 89.00 89.00 62.00 127.00
XF-9P XF-910 IF			8 2 TERS	175.00 21.00 ping: \$3.75
MICROWA Use your existing HF RECEIVE	or 2M rig on oth	er VHF or UHF	bands.	1
CONVERTE MMk 1691-137 MMk 1296-144G MMc 439-ATV MMc 432-28(s) MMc 144-28(HP) MMc 144-28	270.00 190.00 99.00 70.00 73.00 60.00	MMt 1 MMx 1 MMt 4 MMt 1 MMt 1	ANSVER 296-144G 268-144 32-28(S) 44-28(R) 44-28 35-28(S)	TERS 370.00 290.00 280.00 400.00 200.00 300.00
LIN 2M MML 144-30-LS MML 144-50-S MML 144-100-S MML 144-100-LS MML 144-200-S	EAR POWE 145.00 160.00 225.00 250.00 500.00	70cm MML MML	FIERS	245.00 220.00 450.00
ANTENNA	s 🛞	and a	Gear	- 171 - 171
2M: 10XY-2M 70cm: 70/MBM28 70/MBM48 70/MBM88 DY20-900 MHz	\$80.00 \$50.00 70.00 115.00 80.00	LOOP \ 1268-LY 1296-LY 1691-LY order lo		55.00 55.00 65.00 ector extra
Send 66¢ (3 stamps) for products. Shipping: FOB Concord, 1		ur VHF & UHF eq	uipments and K	VG crystal
	Harris anger	NTERNA	ffice Box	TRUM ., INC. . 1084

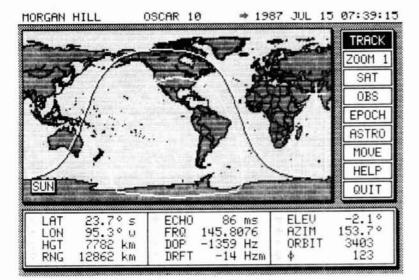

FEATURES INCLUDE:

SWITCH SELECTABLE — ELEVATION FROM 0° - 90° AND 0° - 180°

- " ELEVATION SCALING X1 OR X2
- •
- NORTHERN OR SOUTHERN HEMISPHERE — MANUAL OR AUTOMATIC MODE
- " BAUD RATE (300 2400)
- 100 PAGE DETAILED MANUAL
- CABLE FOR KENPRO'S[™] "A" SERIES CONTROLLER




P.O. BOX 1000 MORGAN HILL, CA 95037 (408) 779-7363 (800) 538-2140 (outside CA)

440-6X

ELECTRICAL:	
BANDWIDTH	
GAIN	8.9 dBd
VSWR	
F/B	20 dB
BEAMWIDTH	60°
FEED IMP	
BALUN	4:1 coax
MECHANICAL:	
ELEMENT LENGTH	
BOOM LENGTH	
TURN RADIUS	
WINDLOAD	
WEIGHT	
MAST	
MOUNT	Rear

440-10X

ELECTRICAL:	
BANDWIDTH	420-460 MHz
GAIN	11.2 dBd
VSWR	
F/B	
BEAMWIDTH	
FEED IMP	
BALUN	4:1 coax
MECHANICAL:	
ELEMENT LENGTH	131/2" max.
BOOM LENGTH	
TURN RADIUS	
WINDLOAD	
WEIGHT	
MAST	
MOUNT	Rear

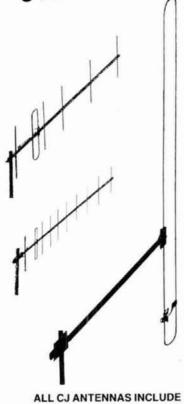

ALL CJ ANTENNAS INCLUDE INSULATED SUPPORT MAST



P.O. BOX 1000 MORGAN HILL, CA 95037

MIRAGE TRACKING INTERFACE

"MTI" IS THE ONLY SMART INTER-FACE BOX THAT WORKS WITH SILI-CONE SOLUTIONS™ SOFTWARE.

"MTI" OFFERS AUTOMATIC TRACK-ING OF ANY ORBITING BODY.

"MTI" KEEPS ANTENNAS AIMED CORRECTLY AT ALL TIMES.

"MTI" COMES WITH A ONE YEAR WARRANTY FROM MIRAGE/KLM.

"MTI" OFFERS ONE YEAR SOFT-WARE SUPPORT TO REGISTERED OWNERS.

"MTI" IS AVAILABLE FROM MIRAGE/KLM ONLY. CALL FOR MORE DETAILS ...

(408) 779-7363 or outside CA, (800) 538-2140

CALL YOUR DEALER TO ORDER ONE NOW!

CJ2M

ELECTRICAL:	
BANDWIDTH	
GAIN	1.8 dBd
VSWR	
FEED IMP	
NO GROUND PLA	NE REQUIRED
MECHANICAL:	
HEIGHT	61"
WEIGHT	
MAST	

CJ220

ELECTRICAL:	
BANDWIDTH	
GAIN	1.8 dBd
VSWR	
FEED IMP	
NO GROUND PLA	NE REQUIRED

HEIGHT		
WEIGHT 2 I		*
WEIGHT	2 lbs	ŝ
MAST11/2" 0.	1½" o.d	ĺ.

CJ440

N

ELECTRICAL:	
BANDWIDTH	
	1.8 dBd
VSWR	
FEED IMP	
NO GROUND PL	ANE REQUIRED

MECHANICAL:	
HEIGHT	
WEIGHT	1 lb.
MAST	

20 Ir August 1987



167

better frequency stability for the Drake TR7

Adding a circuit board improves performance without affecting appearance

Although the TR7 has a rather stable VFO, it can still be improved. With this modification, its stability becomes comparable to that of synthesized frequency generators; consequently, it becomes more useful in the following ways:

• If you're operating on AMTOR, retuning is not necessary.

 Your operating frequency is stable within a second or so after switch-on, even in a cold shack.

• The frequency setting remains stable for an indefinite length of time, making the rig usable for remotely controlled installations such as AMTOR repeaters.

Improved frequency stability is achieved by means of a Digital Automatic Frequency Control (DAFC) circuit. A frequency counter with a crystal-controlled reference measures the frequency to be stabilized. If the count is above or below a defined fixed value, a dc voltage controlling a varicap within the VFO is altered so as to counteract any frequency deviation. The divider ratios used in this design produce a series of stable frequencies which are separated from each other by 30.5 Hz. Actually, the frequency slowly varies about the *nearest* 30.5-Hz point. This is because the output is either too low or too high, but never exactly on. That's why the control voltage continues to hunt.

These fluctuations are generally not noticed when operating in CW, SSB, AMTOR, or RTTY. If you connect a frequency counter, you can see that the VFO frequency excursions amount to not more than \pm 10 Hz. PA0KSB has designed a circuit that can be incorporated into existing VFOs; he describes the

theory behind this kind of frequency control in detail in reference 1.

The present circuit provides VFO frequency control by applying the correcting voltage to the RIT-line. This also enables a possibly connected external VFO to be frequency controlled when switched on.


The reference frequency used is the TR7's 500-kHz signal drived from the 40-MHz main crystal reference, thereby eliminating the need for a separate crystal oscillator. PA0KSB's circuit uses a pointer instrument to indicate the tuning voltage and an UP/DOWN switch for manual control of this voltage.

I wanted to find a way to avoid drilling holes into the front panel of the transceiver for additional switches and a meter. The TR7 already has UP/-DOWN keys; when you depress the STORE key, the UP/DOWN keys are assigned to the DAFC circuit for as long as the STORE key is held down. The rest of the time the UP/DOWN keys perform their usual functions. This means that the initial function of the STORE key can no longer be used — a sacrifice which is more than justified by the advantages of the DAFC circuit. But I couldn't find a way to have the S-meter indicate the DAFC control voltage; instead I adopted an idea proposed by K6EHV.² Two lamps indicating the upper and the lower limit of the control voltage are sufficient to display this information. The FIXED lamp (the *upper* one) indicates that the control voltage has exceeded its upper limit. The SET BAND lamp (the lower one) shows that the control voltage has gone below its lower limit. Besides being DAFC indicators, both lamps still serve their traditional purpose; in normal operation the control voltage does not reach either limit, so the double use of the lamps presents no problem.

circuit description

The circuit for this modification is shown in fig. 1.

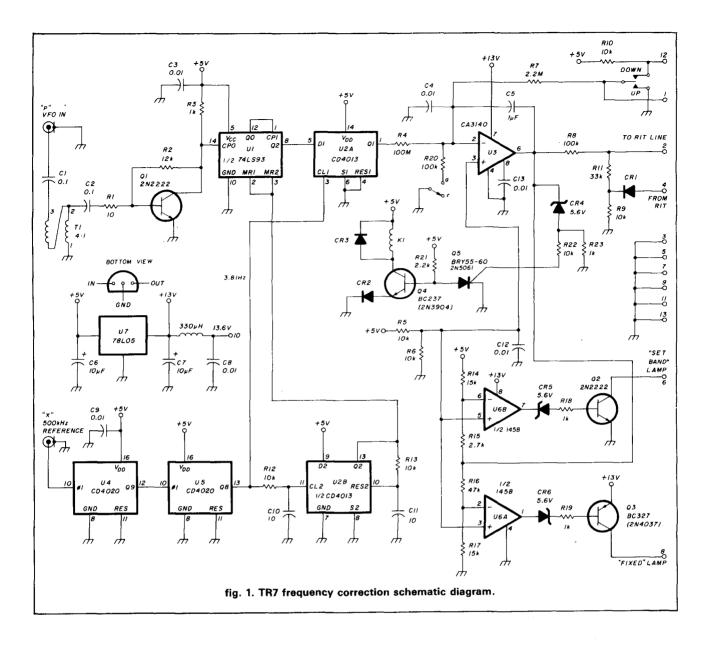By Urs Hadorn, HB9ABO, Im Riedtli 1, CH-8154 Oberglatt, Switzerland



The VFO signal enters the DAFC circuit at terminal P. A broadband autotransformer, T1, steps down the signal to match it to the low impedance input of Q1, where it is amplified to TTL level to enable it to drive the frequency counter chip U1. U1 divides the VFO frequency by 8. After each counting period, the count (1 bit) is stored in U2A and the counter is reset to zero. The binary counters U4 and U5 divide the 500-kHz reference by 217, thus establishing the counting period of 262 ms. A short time (determined by R12, C10) after the rising edge of the counter clock, U2B generates the reset pulse for the counter. The reset pulse width is given by R13, C11. The integrator U3 transforms the 1-bit count result into a slowly rising and falling dc voltage which is used to control the VFO frequency. The integrator time constant is established by R4 and C5. This control voltage and the former RIT voltage

entering the circuit at terminal 4 are combined via R8 and R11. The resulting dc voltage is put onto the RIT line at terminal 2 for the VFO in use (internal or external). CR1 and R9 reduce the original RIT voltage so that the combined voltage looks like the former RIT voltage when RIT and DAFC voltages are at midrange. The integrator output voltage, and with it the VFO frequency, can be raised or lowered manually by applying either +5 volts or 0 volts via R7 to the integrator input.

The circuit associated with thyristor Q5 ensures that the integrator output voltage starts at mid-range at power-up. After switch-on, Q4 conducts, thereby pulling the integrator input down via R20 and the relay contact to ground. U3's output voltage rises at a rate determined by R20 and C5. As soon as it reaches approximately 6 volts, SCR Q5 fires and cuts off the relay driver Q4, which releases the integrator input by floating R20. This mechanism is not repeatable because Q5 remains on (i.e., conducting) via R21 until the power is turned off.

The two op amps of U6 are used as comparators. The upper comparator drives Q2 into saturation when the integrator output voltage drops below the lower limit of about 2 volts. Q2 turns on the SET BAND lamp. The lower op amp drives Q3 and with it the FIXED lamp when the output voltage rises above the upper limit of about 10.5 volts.

construction

Component layout is not critical. I have built several versions of this circuit mostly using Veroboard. Follow sound rf construction techniques in the area of T1, Q1, and U1: provide a low impedance common ground, keep leads short, and pay attention to shielding. The components used are easy to obtain and low in cost. Impedance transformer T1 is wound on a ferrite toroid core (Philips Part No. 4322 020 97170) with an OD of approximately 0.37 inch and an ID of approximately 0.22 inch. There is no reason why other suitable types — for example, an Amidon FT37-63 or FT37-67 — could not be used.

The winding consists of ten turns of a twisted transmission line you can make yourself. Stretch out a 23.6-inch length of enameled copper wire with a diameter of about 0.016 inch (AWG 26) to smooth out any bends, then cut it in half. Using a hand drill, twist the two pieces to obtain about five turns per inch. Wind ten turns of this transmission line on the toroidal core, taking care that the windings are equally spaced on the circumference. Then connect one end of one wire with the opposite end of the other wire. This connection is the low impedance port (2) of the transformer. The other two ends form the high impedance input (3) and the ground end (1), respectively. They may be interchanged without any effect because the transformer is symmetrical.

The relay may be replaced by a 12-volt type, in which case it has to be connected to the 13.6-volt bus. The capacitor at C5 should be a polystyrene or similar type. Electrolytic or tantalum capacitors would exhibit too much leakage at this point of extremely high resistance. To keep the height of the pc board low, we used three 0.33- μ F capacitors instead of one 1- μ F capacitor. The voltage divider chain for the comparators (R14, R15, R16, R17) should be selected to be within 2 percent of nominal value to define the range limits of the control voltage accurately.

initial tests

The completed circuit board should be tested before it's incorporated into the transceiver. The following hints assume that there are no leads and signals connected, except for the 13.6-volt supply and those mentioned. When removing and replacing ICs, be sure to disconnect the power supply first.

power supply

Remove all ICs except regulator U7. Verify that there is + 5 volts at the regulator output. Check whether there is 2.5 volts at pins 3 and 5 of U6. The current drain from the 13.6-volt supply should be around 10 mA. Insert all ICs. The current drain should now be around 30 mA.

integrator

Remove U2. After power is connected, the relay should actuate momentarily and drop out immediately. The output voltage at pin 6 of U3 should be in the vicinity of 6 volts. Connect terminal No. 1 of the board to ground (corresponding to a depressed UP switch). The output voltage of U3 should rise within a few seconds to 11 volts. Connect terminal 1 with terminal 12, (corresponding to a closed DOWN circuit). The output voltage of U3 should decrease within a few seconds to about 0.1 volts.

comparators

The following maneuvers are performed by manipulating the UP and DOWN contacts as described above. Lower the integrator output voltage, starting from 6 volts. When the 2-volt level is crossed, output pin 7 of U6 should jump from 2 volts to about 12 volts.

Raise the integrator output voltage, starting from 6 volts. When the 10.5-volt level is crossed, output pin 1 of U6 should jump from 12 volts to about 2 volts.

time base

Remove U2. Apply the 500-kHz signal to terminal X. (You may use either the 500-kHz signal from the TR7 or a signal from another source. In any case, it should be a square wave of 4 to 5 V_{pp} .) At pin 13 of U5 there should be a square wave of 3.81 Hz.

frequency counter


Remove U2, grounding pins 2 and 3 of U1. Connect the VFO signal (from the main board of the TR7) to terminal P. At pin 8 of U1, you should now detect a square wave measuring one-eighth of the VFO frequency. You can verify this by connecting the DAFC terminal P to the VFO line of the main board; doing this should cause just a minor drop of the VFO (PTO) voltage in the TR7.

installation

The DAFC circuit board is mounted to the lower side of the main board as shown in **fig. 2**. Insert a sheet of flexible pressure-resistant insulating material between the two soldered sides. The circuit board and



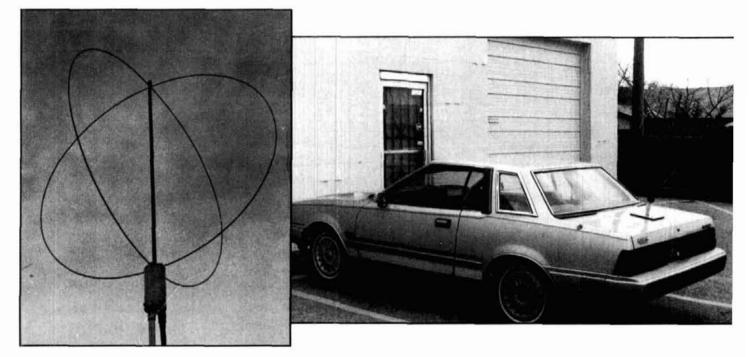MOBILE OMNI-DIRECTIONAL HORIZONTAL EGGBEATER ANTENNA



Polarity

Val Comm Inc. offers an exciting New Mobile Antenna for 2 meter operations for the SSB/FM mode. The original antenna, designed by Mike Staal in conjunction with Val Comm Inc. was to produce a mobile antenna in the VHF band for government satellite communication networks. Its outstanding performance is now offered to the amateur operator for mobile or fixed communications.

Orientation of the Eggbeater is unimportant as it produces an omnidirectional horizontally polarized pattern. As an omni-directional satellite antenna, the Eggbeater is very effective as it produces a right hand circular polarization off the top. When placed 1/8 wavelength over a metallic surface, such as a vehicle roof top, the signal level off the top portion of the antenna increases by as much as 6 dB. No rotation or steering is necessary. Circularity is optimized in the 144 to 146 MHz region, ellipticity will increase either side of that range but the antenna is still effective from 135 to 150 MHz.

Base station, contest and field day use of the Eggbeater will allow rapid fire communications in all directions with other horizontally polarized stations. While the Eggbeater won't replace a good directional antenna, it is certainly a valuable addition to any mobile or fixed station.

EGG BEATER SPECIFICATIONS:

Spec. Freq. Range Usable Freq. Range Impedance VSWR Max. Pattern 144 to 148 MHz 135 to 150 MHz 50 OHMS 1.5:1 Omni-directional at horizontal, circular off the top.



Power Handling Max 1 kilowatt Mounting Requires 3/8-24 male thread Connector SO-239 Size 34" high x 28" wide Wind Speed Max 100 MPH Materials: Loops 17-7 stainless Loop Support 3/8" fiberglass Body Delrin & anodized alum Hardware Stainless & brass VC Eggbeater Price \$119.95 Options: Magnetic Mounts 39.95 Spring Coil 9.95 15.95 **Bumper Mounts** 54" Bumper Mount 22.95 Extension Folding Extension 29.95


Horizontal

Warranty: This product is guaranteed for a period of one year from date of purchase against defective workmanship and materials. It is the option of Val Comm Inc. or M2 Enterprises to repair or replace the defective part. This specialty antenna product has been carefully manufactured by M2 Enterprises, (408) 683-2067, and serviced and marketed thru Val Comm Inc.

Val Comm Inc. is a small business, woman-owned corporation specializing in design and fabrication of prototype special applications communications systems in RF links, video transmitters, data communications and security communications.

- 166

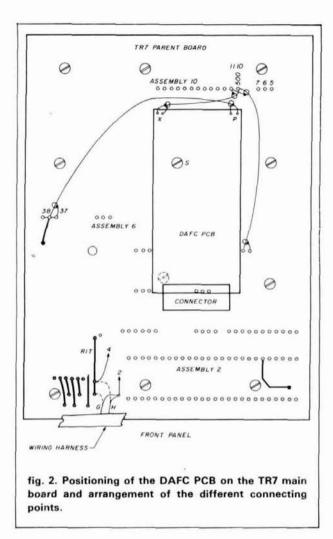"Let us help you meet your requirements."



the insulating sheet are fixed to the main board by means of a screw (S in fig. 2) and two insulating spacers, each about 0.08 inch thick. To be on the safe side, insulate the bottom cover of the TR7 with insulating tape or sheet. The connection of the board to the TR7 is via a 13-pin connector and two small-diameter coaxial cables. (See **photo B**.)

switch wiring

Label all applicable wires before modifying (see fig. 3). After identifying wires A through F, unsolder all connections from the three switches and remove the spring hook from the STORE switch so that it can no longer lock when depressed. The new wiring of the switches is shown in fig. 4 and fig. 5. Wire F of the former STORE function is no longer used. Insulate its dead end and bend it into a safe place. The two wires from D2a and S2m are dressed together with the wire from the FIXED RCV switch towards the bottom side of the main board. The various connections to the DAFC board are shown in the figures, with their respective connector numbers circled.


Parts list for di	gital AFC:
C1.C2	0.1µF
C3.C4.C8.C9.	0.14
C12.C13	0.01µF
C5	1 µF (or three 0.33µF)
C6.C7	10 µF 16 V
C10,C11	10 pF
CR1.CR2.CR3	1N4148
CR4,CR5,CR6	5.6-volt Zener 1N708A or 1N4626
K1	Reed relay
L1	330 µH ferrite choke
Q1.Q2	2N2222
Q3	BC327 or 2N4037
Q4	BC237 or 2N3904
Q5	BRY55-60 = 2N5061
R1	10 ohms
R2	12 k
R3.R18.R19	1 k
R4	100 megohms
R5, R6, R9, R10.	
R12,R13,R22	10 k
R7	2.2 megohms
R8,R20	100 k
R11	33 k
R14.R17	15 k
R16	51 k
R21	2.2 k
U1	74LS93
U2	CD4013BE
U3	CA3140
U4,U5	CD4020BE
U6	CA1458
U7	LM78L05



GLB ELECTRONK

151 Commerce Pkwy., Buffalo, NY 14224 716-675-6740 9 to 4

PORTABLE ANTENNA

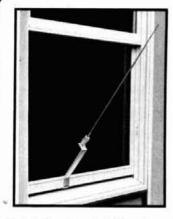

MODEL AP-10

Designed for APARTMENTS MOTELS VACATIONS

^{\$5195}

Add \$3.00 Shipping and Handling

Guick Simple Installation. Operates on 2, 6, 10, 15, 20, 30 and 40 meters. All coils supplied. Only 22-1/2 inches long. Weighs less than 2 lbs. Supplied with 10 ft. RG 58 coax and counter poise. Whip extends to 57 inches. Handles up to 300 watts.

VSWR-1.1:1 when tuned write for more details and other B&W products





HERE'S A NEAT GIFT IDEA

When we first saw the Casio PQ-40U Portable World Time Clock, we knew instantly that Ham Radio Bookstore customers would love this one.

This time piece is more than a simple clock. Besides all the standard features, alarm, snooze, lightweight portable design and digital readout, this clock gives you time at 21 different locations around the world at the twist of a dial. DX'ers will delight at being able to get rid of their cumbersome manual time calculators: determining band and path to use will be greatly simplified. Contesters can simultaneously display both local and UTC times for logging purposes. In fact, every Amateur will find at least a dozen uses for this nifty clock. You can take it with you when you go on vacation-business trips-set the alarm and get out of meetings early-anywhere you need a clock, the PQ-40U can go with you. Get a couple of them and give them as gifts, one for the house, car, office, just about anywhere you need a clock, the PQ-40U can go with you. Quantities are limited-order now and avoid disappointment.

PQ-40U \$29.95 Please enclose \$3.50 shipping and handling ham BOOKSTORE

GREENVILLE, NH 03048

603-878-1441

Join AMSAT...Today

Amateur Radio Satellite OSCAR 10 provides:

• A New Worldwide DX Ham Band open 10 hours a day.

• Rag Chew With Rare DX Stations in an uncrowded, gentlemanly fashion.

• Popular Modes In Use: SSB, CW, RTTY, SSTV, Packet

• Full Operating Privileges open to Technician Class licensee or higher.

Other AMSAT Membership Benefits:

Newsletter Subscription: Dependable technical articles, satellite news, orbital elements, product reviews, DX news, and more.

> Satellite Tracking Software Available for most popular PCs.

QSL Bureau, AMSAT Nets, Area Coordinator Support, Forum Talks

Construction of Future Satellites For Your Enjoyment!

AMSAT Membership is \$24 a year, \$26 outside North America. VISA and MC accepted.

AMSAT P.O. Box 27 Washington, DC 20044

301 589-6062

164

connections on the main board

Figure 2 shows the bottom side of the TR7 main board. The connecting points which are used to install the DAFC board are labeled with assembly and pin numbers according to the TR7 service manual. The power supply board is not part of the main board; it is located to the left of the main board between the PA radiator and the rf and a-f gain controls. The 13.6-volt supply voltage is picked up from pin 9 (counted from the left) of the power supply board. The RIT control voltage is available on the conductor labeled RIT in **fig. 2**. In the original wiring the RIT voltage is run from this conductor to the internal and external VFOs with one wire each.


Two wires (labeled G and H) have to be removed from the RIT conductor and connected instead to the DAFC connector, pin 2. The RIT conductor is connected to DAFC connector, pin 4. This completes the installation. It might now be necessary to realign the RIT control center setting according to the service manual (section 3.16).

To gain confidence in this modification, zero-beat

a strong a-m broadcast station. Switch on the passband tuning at its center position to allow for maximum response at the carrier center frequency. Try the best zero-beat setting you can obtain; it will be somewhere between 0 and 15 Hz. Don't worry if you hear a rather unsteady beat note. The fluctuations are in the order of a few Hz — less than you will ever notice in one of the stability-sensitive operating modes. If you leave the rig untouched and check in after hours or even days, the beat note will still be moving back and forth, but will be near the same 30.5 Hz point — and by the same few Hz!

operation

This DAFC circuit controls any undesirable frequency excursions under 2 kHz. If the drift exceeds this range, one of the two lamps — either FIXED (upper limit) or SET BAND (lower limit) — will light to announce that the DAFC cannot compensate for any further drift. It is obvious that with the inherent stability of the TR7 VFO, this condition is not very likely to occur. Holding down STORE momentarily DOWN

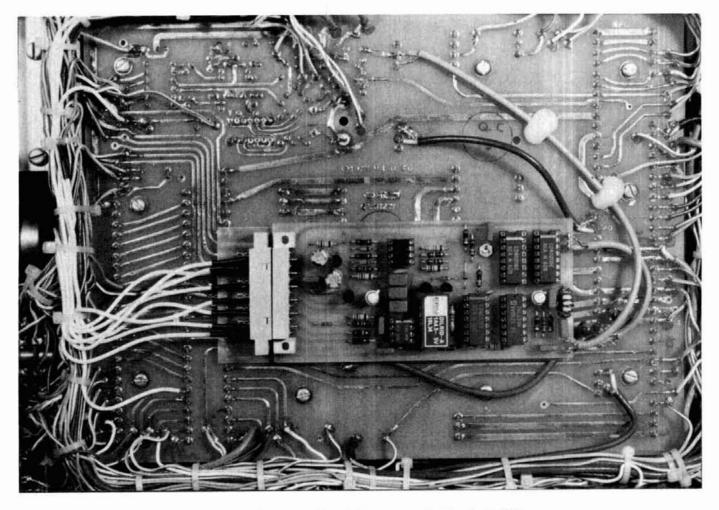

Closeup shows new board placement and wiring in the TR7.

AMATEUR TELEVISION

HAMS SHOULD BE SEEN

AS WELL AS HEARD!

TVC-4G 70cm ATV Downconverter Now only \$99 Delivered UPS surface in cont. USA



Tom (W6ORG)

Maryann (WB6YSS)

- See live action color & sound like broadcast TV
- Many areas have ATV Repeaters (call us or see the 87/88 ARRL Repeater Directory pg. 328 for your area)
- Most ATVers use home cameras and VCRs to show the shack, projects, home video tapes, public service events like parades, races, etc.
- Some repeaters also have weather radar, Space Shuttle video, BBS, & computer video

It's easy to start watching: 70cm antenna, a TVC-4G and any TV set tuned to ch2, 3 or 4. Our TVC-4G tunes the whole 420-450 mHz band & includes GaAsfet preamp & mixer, AC/12vdc wall plug, attractive shielded 4x2.5x7 cabinet. We also have wired & tested boards for the builder starting at \$39. See ARRL Hbk chapter 20. When you are ready to try transmitting, we have transmitters, transceivers, antennas, and all your ATV needs for the 70, 33 & 23cm bands.

Hams, Call or Write for our full catalog of ATV gear!

(818) 447-4565 m-f 8am-5:30pm pst. P.C. ELECTRONICS

2522 Paxson Ln Arcadia CA 91006



A magazine dedicated to quality and sportsmanship in amateur radio operating. Fresh, timely, practical and down to earth reading for little pistols and big guns. Written by the world's best in their fields: ON4UN, SMØAGD, LZ2CJ, VE3BMV, KH6BZF, DJ9ZB, ZS6BRZ, W1WY, N2AU, K7GCO, K4ZN, W4GF, VE3JTO, WB4ZNH, WB9TBU, K02M, NS6X, W3FG, KA3B, K1PLR, N7CKD, VE3XN, ABØX, JE1CKA and others.

Includes DX News, QSL Info, 160m, 80m, 10m, 6m columns, DXpeditioning, Propagation, Awards, Contest rules and results, Traffic - Emergency, FCC News, New Products, Antennas, Technical news and articles, equipment reviews and modifications, computer programs, Radio Funnies, Club Life, RTTY, VHF/UHF, Mail Box, Classified Ads and much more in a magazine format with the speed of a bulletin.

RADIOSPORTING sponsors DX Century Award, Contest Hall of Fame and World Radio Championship contest.

"Your publication is superb! Keep it up!" Joe Reisert, WIJR

"Your W2PV articles are priceless. Your magazine is super!" Rush Drake, W7RM


"Let me congratulate you on a very impressive magazine. Just what I've been looking for as a DXer and Contester!"


Dick Moen, N7RO "RADIOSPORTING, once received, cannot be tossed aside until it is read from cover to cover. Then reviewed again and

again." Chas Browning, W4PKA Subscription rates: 1 year USA \$18, Canada CDN\$26, Overseas

US\$23; 2 years \$33, \$48, \$42 respectively. Single issue \$2. USA First Class Mail add \$8/year, DX Air Mail add \$15/year.

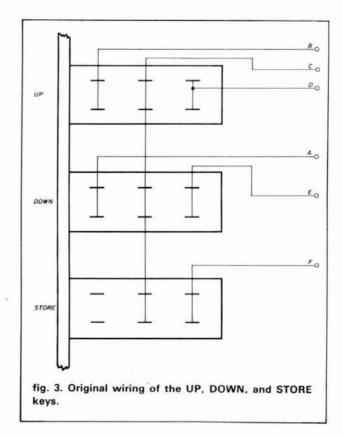TRY US! SUBSCRIBE OR SEND \$1 FOR YOUR SAMPLE COPY. RADIOSPORTING Magazine PO Box 282, Pine Brook, NJ 07058, USA



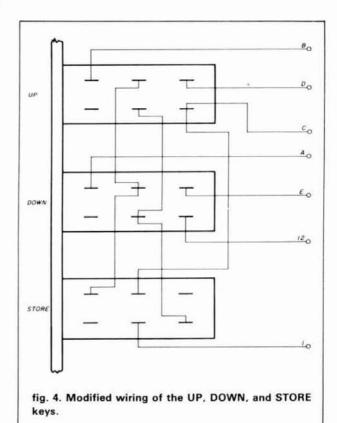



163

or UP, as is appropriate, brings the DAFC voltage back into its operating range. (UP and DOWN can also be used as a fine tuning, but I think the main tuning knob does a better job.) After several months of operation with more than one modified TR7, the range limits were never reached. It is therefore left to the reader to decide whether to build the circuit with or without the comparator stage and with or without making the connections to the lamps and switches. Tuning behavior and the traditional functions of the UP and DOWN keys are not impaired at all by the DAFC.

limitations

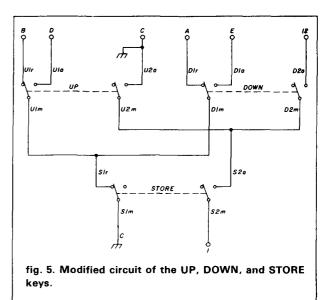When operating with RIT switched on, you have to take into account that after an RX/TX/RX transition it is not necessarily true that the frequency will be on the same 30.5-Hz spot as it was before. The DAFC has no means of remembering previous voltage/fre-



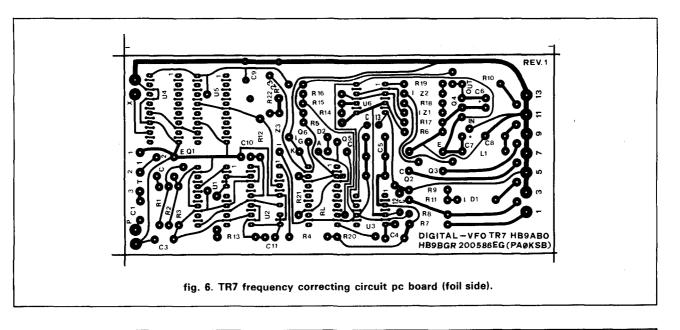

designation on DAFC board	connector	Destination within TR7
	pin number	
VFO (PTO) signal (P)	-	assembly No. 06, pin 38
braid (coax VFO)	-	assembly No. 06, pin 37
500-kHz reference (X)		assembly No. 10, pin 10
braid — 500 kHz	-	assembly No. 10, pin 11
13.6-volt supply	10	assembly No. 21, pin 9
		(power supply board)
RIT voltage from RIT circuitry	4	conductor labeled RIT
RIT output voltage	2	to wires G and H
+ 5 volts via R10	12	DOWN switch lug D2a
integrator input via R7	1	STORE switch lug S2m
SET BAND lamp	6	assembly No. 02, pin 6
FIXED lamp	8	FIXED RCV key
ground	3, 5, 7, 9,	ground solder lug near
-	11, 13	assembly No. 21



The monthly magazine with a natural blending of two popular hobbies -- Ham Radio and Computers * Articles on Ham Radio & Most Personal Computers

- * Hardware & Software Reviews
 - * Various Computer Languages
 - * Construction Articles
 - * Much Much More

Your #1 Source for PACKET Info

"...received my moneys worth with just one issue..."

-J. Trenbick

"...always stop to read CTM, even though most other magazines I receive (and write for) only get cursory examination..."

—Fred Blechman, K6UGT


U.S.A	\$18.00 for 1 year
Mexico,	Canada\$32.00
Foreign	\$43.00(land)-\$68.00(air)
(U.S. fun	ids only)
Perman	nent (U.S Subscription)\$150.00
Sample	e Copy\$3.50



Circulation Manager 1704 Sam Drive Birmingham, Alabama 35235

Phone 205/854-0271

Name	
Call Sign	
Address	
City	State
Zip	Phone
Date	
Signature	

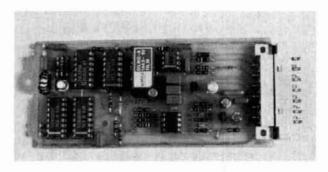

Frequency correcting circuit improves TR7 stability.

quency conditions once the controlling voltage has been changed externally. (That's what happens when RIT is in operation.)

After the power is turned on, you might occasionally hear a short chirp. This is caused by the control voltage being driven into mid-range. Because there are spurious responses at 21266.7 and 28050.0 kHz due to harmonics of the VFO frequency generated by the nonlinear amplifier at Q1, it is important to use good shielding at that stage.

conclusion

Working with the modified TR7 is very rewarding: no longer is there any need to warm up before a sked. Just switch your rig on and tune in. Should a frequency difference arise during a QSO, you can be confident that it's caused by the other station's equipment!

Although this modification isn't difficult, it's a good idea to review references 1 and 2 as well as the TR7 service manual. Doing so will help you understand what you're doing at every step along the way.

Materials for this project can be obtained from HB9BGR (Charlie Egli, HB9BGR, Rümelbachstrasse 9, CH-8153 Rümlang, Switzerland). A list of available items, with prices (U.S. currency, air mail delivery included), follows.

Printed circuit board, undrilled	\$12.00
Drilled circuit board	\$15.00
Kit with all components and undrilled	
PCB	\$61.00
Kit with all components and drilled PCB	\$64.00
Assembled and tested unit	\$92.00

For those who wish to etch their own full-size printed circuit board, artwork is provided in **fig. 6**. Follow the foil side labels and detail shown in the photos for parts placement.

references

1. "Drift Correction Circuit for Free-Running Oscillators," Klaas Spaargaren, PA0KSB, ham radio, December, 1977.

2. "AFC Circuit for VFOs," by Read Easton, K6EHV, ham radio, June, 1979.

ham radio



9 Autry Irvine, CA 92718 (714) 458-7277

CORPORATION	(714) 458-7277				▶ 160
INSIDE VIEW — RS-12A	AST - HEAVY D SPECIAL FEATURES - SOLID STATE ELECTRONICALLY RE - FOLD-BACK CURRENT LIMITING PF from excessive current & continuou - CROWBAR OVER VOLTAGE PROTEC • Scept RS-3A, RS-4A, RS-5A. - MAINTAIN REGULATION & LOW RIF Voltage - HEAVY DUTY HEAT SINK - CHASSI - THREE CONDUCTOR POWER CORD - ONE YEAR WARRANTY - MADE IN	GULATED otects Power Supply is shorted output CTION on all Models PPLE at low line input S MOUNT FUSE	 (Internally Adjustable: 11-15 VDC) RIPPLE Less than 5mv peak to peak (full load & low line) 		
MODEL RS-50A		DEL RS-50M		MODEL	/S-50M
RM SERIES	$19'' imes 5^{1\!\!/_{\!\!4}}$ rack mount power supplies				
	MODEL RM-12A RM-35A RM-50A • Separate Volt and Amp Meters RM-12M	Continuous Duty (Amps) 9 25 37 9	ICS* (Amps) 12 35 50 12	$\begin{array}{c} \text{Size (IN)} \\ \text{H} \times \text{W} \times \text{D} \\ 5\% \times 19 \times 8\% \\ 5\% \times 19 \times 12\% \\ 5\% \times 19 \times 12\% \\ 5\% \times 19 \times 12\% \end{array}$	Shipping Wt. (lbs.) 16 38 50 16
MODEL RM-35M	RM-35M RM-50M	25 37	35 50	5¼ × 19 × 12½ 5¼ × 19 × 12½	38 50 Shipping
RS-A SERIES	MODEL RS-3A RS-4A RS-5A RS-7A RS-7B RS-10A RS-12A RS-12A RS-12B RS-20A RS-35A RS-50A	Continuous Duty (Amps) 2.5 3 4 5 7.5 9 9 9 16 25 37	(Amps) 3 4 5 7 10 12 12 12 20 35 50	Size (1N) H × W × D $3 \times 4^{3} \times 5^{5} \times 3^{3}$ $3^{3} \times 6^{5} \times 9$ $3^{5} \times 6^{5} \times 9$ $4 \times 7^{5} \times 10^{3}$ $4 \times 7^{5} \times 10^{3}$ $4^{5} \times 9 \times 10^{3}$ $4^{5} \times 9 \times 10^{3}$ $5 \times 9 \times 10^{5}$ $5 \times 11 \times 11$ $6 \times 13^{3} \times 11$	WI. [ibs.] 4 5 7 9 10 11 13 13 13 18 27 46
RS-M SERIES	MODEL	Continuous Duty (Amps)	ICS" (Amps)	Size (IN) H × W × D	Shipping W1. (lbs.)
MODEL RS-35M	 Switchable volt and Amp meter RS-12M Separate volt and Amp meters RS-20M RS-35M RS-50M 	9 16 25 37	12 20 35 50	$\begin{array}{c} 4^{1/_2} \times 8 \times 9 \\ 5 \times 9 \times 10^{1/_2} \\ 5 \times 11 \times 11 \\ 6 \times 13^{1/_4} \times 11 \end{array}$	13 18 27 46
VS-M AND VRM-M SERIES	MODEL	Continuous Juty (Amps) C @10VDC @5VDC 5 2 9 4 15 7 22 10	IC (Am @1; 1 2 3		om 1.5 amps Shipping Wt. (lbs.) 13 20 29 46 38 50
RS-S SERIES MODEL RS-12S	Built in speaker MODEL RS-7S RS-10S RS-12S RS-20S	Continuous Duty (Amps) 5 7,5 9 16	ICS* Amps 7 10 12 20		Shipping Wl. (Ibs.) 10 12 13 13

the second state of the second state of the second se

MODEL RS-12S

BASIC program analyzes simple ladder networks

BASIC or PASCAL — which is best for you?

This article is written in response to a recent article discussing a compiled PASCAL network analysis program.¹ The author of the PASCAL program contended that a network analysis program written in an interpreted language such as BASIC would result in unacceptably long execution times; he also claimed that BASIC doesn't lend itself to structured programming techniques. The intent of this article is to offer an alternative viewpoint and to demonstrate a simple and useful BASIC network analysis program.

The main fault with the BASIC language - from the programming teacher's point of view - is that BASIC lends itself to unstructured programming techniques, and consequently, self-taught programmers (most of us) tend to start writing code without having worked out the overall structure of the program. This is not a fault of the BASIC language, but of the programmer. A BASIC program can be just as well structured as a PASCAL program, but this is seldom so because one can start writing BASIC code without worrying about how it will finally end! In fact, that is why Dr. Niklaus Wirth developed the PASCAL language --- to force the programming student to use good structuring techniques. However, this forced method of programming is of little interest to the Radio Amateur wanting to learn only enough about programming to perform some network analysis on relatively simple ladder circuits.

The contention that BASIC programs have unacceptably long execution times is subjective and relative; that is, if you are required to analyze circuits on a daily basis, a reduction in calculation time of more than half is very important. If you want to analyze only a few circuits with some minor modifications now and then — and if a tabular output instead of a graphical output is sufficient — then it doesn't matter too much whether the calculations take 5 seconds or 20 seconds per run. Consequently, a slower, non-compiled BASIC network analysis program may be quite satisfactory. The BASIC network program discussed in the following article will permit *ham radio* readers to decide which network approach they prefer.

simple vs. complex BASIC programs: - which do you need?

Although many powerful and versatile BASIC network analysis programs have been published in the electronics trade journals, the length and complexity of these programs make them unattractive.^{2,3,4,5} (nstead of considering these more complex programs, why not first try the following simple BASIC program to see if it meets your requirements?

short BASIC program solves simple ladder networks

Computer analysis of a proposed circuit is preferable because many circuit variations can be more quickly and conveniently evaluated by computer than by actual circuit construction and measurement. The BASIC program discussed in this article permits you to evaluate networks consisting of alternating singleelement shunt and series branches, such as Chebyshev high-pass or low-pass filters. By using "null" branches, the program can also evaluate more complex networks with series-tuned series branches or parallel-tuned shunt branches. You can specify the actual measured component values and Ω s so you can be assured that your circuit, when properly assembled, will perform the same as your computer model.

BASIC listing

Figure 1 is a listing of a BASIC network analysis program that requires less than 3K of memory and is short enough to be entered into your computer at one sitting. Because of its simplicity, the program can't analyze networks having a parallel-tuned circuit in a series branch or a series-tuned circuit in a shunt branch. Elliptic low-pass and high-pass filters are examples of the circuits this program cannot analyze.

Ed Wetherhold, W3NQN, Honeywell Inc., Signal Analysis Center, P.O. Box 391, Annapolis, Maryland 21401

10 REM Written by W3NQN on SANYO MBC-550 computer using MS-DOS BASIC, Ver. 1.1. For publication in HAM RADIO. 20 REM Program gives filter Atten (dB) vs. Freq (MHz) for simple ladder networks with equal source & load resistances. 30 REM RL≈Load resistance. List first branch starting at load end with shunt element or a null shunt branch. 40 REM List in Data Statements TYPE (1=R, 2=L, 3=C), VALUE (ohms, uH or pF) and Element Q (1E10 = no loss). 50 DIM M(15), X(15), P(15) : PI=3.14159 : RL=50 : FU=1E+06 : LU=.000001 : CU=1E-12 : REM Max.branches = 14. 40 DATA -3,1100,1E10 : REM Negative sign indicates prior null shunt branch in filter network shown in Figure 2. 70 DATA 2, 1.75, 1E10 80 DATA 3, 560, 1E10 90 DATA 2, 1.75, 1E10 100 DATA 3, 1100, 1E10 110 DATA ~1, 50, 1E10 : REM Negative sign indicates a null branch prior to resistor. For a resistor, 1E10 does : REM not refer to Q. The iE10 is used only to maintain a proper data READ order. 120 DATA 0, 0, 0 130 INPUT "ENTER FREQUENCY START (MHz), STEP (MHz), NO. STEPS"; FS, ST, NS 140 FOR N=1 TO 15 : READ M(N), X(N), P(N) : IF M(N)=0 THEN 160 150 P(N) = 1/P(N) : NEXT N160 PRINT "Output data in Pairs" : PRINT "Freq (MHz) Atten. (dB)" 170 FOR FX=FS TO FS+(NS*ST) STEP ST : REM Selected range of test freqs (MHz) and start of FOR/NEXT loop. 180 OM=2*PI*FX*FU : BR=1 : BI=0 : DR=0 : DI=0 : CR=RL : CI≈0 : K=0 : N=0 : F1=0 190 K=K+1 : N=N+1 : MK = M(N) : IF F1>0 THEN MK = ~MK 200 F1 = 0210 GOSUB 360 220 IF K=1 THEN V1 = AR : REM AR = Real (Resistance). 230 IF K=1 THEN V2 = AI : REM AI = Imaginary (Reactance). 240 IF MK= 0 THEN 370 250 IF MK< 0 THEN 280 260 ON MK GOSUB 290, 310, 330 270 GOTO 190 280 CR=0 : CI=0 : N=N-1 : F1=1 : GOTO 190 : REM Null Branch. 290 CR=X(N) : CI =0 : IF K =INT(K/2)*2 THEN RETURN : REM Resistor. 300 CR = 1/CR : RETURN 310 CI = OM*X(N)*LU : CR = CI*P(N) : IF K=INT(K/2)*2 THEN RETURN : REM Inductor 320 DD = P(N)*P(N)+i : CR =P(N)/DD/CI : CI = -i/DD/CI : RETURN 330 CI = OM*X(N)*CU : CR = CI*P(N) : IF K=INT(K/2)*2 THEN 320 : REM Capacitor 340 RETURN 350 REM Complex Linear Update -360 AR=BR*CR-BI*CI+DR : AI=BI*CR+BR*CI+DI : DR=BR : DI=BI : BR=AR : BI=AI : RETURN 370 IF K=INT(K/2)*2 THEN 390 380 AR=BR : AI=BI : BR=DR : BI=DI : DR=AR : DI=AI 390 DEM= V1^2 + V2^2 : RNUM= DR*V1 + DI*V2 : REM Following calculations for Freq (MHz) vs. Atten (dB). 400 INUM = DI*V1-DR*V2 : RTXF = RNUM/DEM : ITXF = INUM/DEM 410 MTXF = 1/(SQR(RTXF^2 + ITXF^2)) : ATXF = -2*ATN(ITXF/(MTXF + RTXF)) 420 AA = -20*(LOG(2)/LOG(10)) - 20*LOG(MTXF)/LOG(10) : REM Filter Atten (corrected for source resis V-drop). 430 PRINT USING "####.## "; FX; : IF AA>1 THEN 450 : REM Prints Freq (MHz) to two decimal places. 440 PRINT USING ".#### "; AA : GOTO 460 : REM Formats output for Atten less than one dB. 450 PRINT USING " ###.# "; AA : REM Formats output for Atten greater than one dB. 460 NEXT FX : END : REM Program ENDS after completion of FOR/NEXT loop. fig. 1. Listing of BASIC network analysis program for attenuation vs. frequency.

However, the program can analyze all networks consisting of alternating shunt and series branches composed of single elements, or those networks that can be configured to simulate alternating single-element shunt and series branches by the insertion of null branches. The BASIC program was derived from a listing found in reference 6.

using the program

Starting at the load end of the network and progressing towards the voltage source, the coding for each component TYPE, VALUE, and *Q* is entered

in separate program DATA statements in the same order the components appear in the network. The coding of all DATA statements starts with a number indicating the component type (1 = resistor, 2 = inductor, or 3 = capacitor), followed by a second number indicating the component value (ohms, μ H, or pF) and concluding with a third number indicating the component *Q*.


This program always expects to start with a shunt branch across the load. Consequently, the coding in the first DATA statement must be for a shunt branch. However, if your circuit has no shunt branch across the load, then a negative sign must immediately precede the coding of the first series branch TYPE number to indicate to the program that there is a prior null shunt branch. Whenever there is a prior null branch (either series or shunt), a negative sign must be placed before the next component TYPE number.

The next-to-last DATA statement is the coding for the source resistance, and it must have the same value as the load resistance. For this program listing, a 50-ohm load and source resistance is used, but you may change this value by changing RL in **line 50** and the source resistance in the DATA statement. The DATA statements conclude with 0,0,0 to indicate to the program that all data entries are completed. An example will demonstrate the coding of the network components and the running of the program.

design application and network analysis example

Assume we want to protect an 80-meter directconversion receiver from overload caused by a nearby 1-MHz broadcast transmitter. Measurements showed that an attenuation of 50 dB at 1 MHz eliminates the receiver overload. A five-element Chebyshev standard-value capacitor (SVC) high-pass filter with a cutoff frequency of 3.37 MHz is selected from table 16 of reference 7. The schematic diagram of this filter (design No. 54) and the frequencies at the 3-, 20-, and 40-dB attenuation levels are shown in **fig. 2**. We will use the network analysis program to find the expected attenuation at 1 MHz to see if this filter design is suitable.

The analysis program shown in fig. 1 requires that the network branches be listed in the DATA statements starting with a shunt element at the load end, but because this high-pass filter configuration does not have a shunt element across the load, we must simulate in the DATA coding the null branch indicated by the dashed box in fig. 2. The first branch coding entered in the DATA statement is for a 1100-pF capacitor. The first number in the coding is a negative 3 to indicate to the program that a prior null branch exists, and that the following series branch is a capacitor. The 1100 indicates the capacitance in pF and the 1E10 indicates no loss. This completes the coding for the first DATA statement. For this first example, we will assume all components have no loss. The coding for the remaining components is entered into the DATA statements in a similar manner, concluding with the series source resistance (with a negative sign because the previous shunt branch was a null). A DATA statement with three zeroes indicates to the program that it has worked back to the network's voltage source and that the input element (the source resistance) has been processed. Note that this program considers the source resistance to be part of the network being

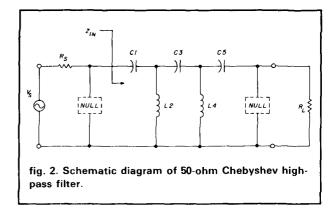

analyzed. See **lines 60** to **120** in **fig. 1** for the coding of the network illustrated in **fig. 2**.

After the DATA statements are completed, the program is run and the responses to the prompts for FREQUENCY START and STEP (both in MHz) and NUMBER OF STEPS are entered. For our evaluation, we start at 1 MHz with steps of 0.2 MHz, and enough steps will be used to provide frequency and attenuation data to 4.2 MHz. The output for this run is shown in **fig. 3A**. The filter attenuates the broadcast transmitter signal at 1 MHz by 52.9 dB, but this was for perfect components. Let's see if the filter attenuation at 1 MHz is still adequate when we assign typical *Q*s of 1000 and 150 to the capacitors and inductors, respectively.

After the *Q* values are changed in the DATA statements, the program is run again; the output is shown in **fig. 3B**. We see there is less than 0.4 dB change in attenuation between 1 and 4 MHz (between the filters that use ideal rather than real components) and therefore the filter should provide the required attenuation when built with real components.

Note that the validity of the program's operation is confirmed by checking the frequency and attenuation output values of the program against the published frequencies at the 3-, 20-, and 40-dB attenuation levels shown in **fig. 2**. This was done with frequency increments of 0.01 MHz and component *Q*s of 1E10. **Figure 3C** shows the results of runs covering the frequencies corresponding to the 3-, 20-, and 40-dB attenuation levels. Because the program's calculated frequency and attenuation data (for no-loss components) are essentially identical to the data in **fig. 2**, it means that the network analysis program is functioning correctly, and it may be used with confidence.

additions and refinements

The program listing in **fig. 1** gives only attenuation vs. frequency data; however, input impedance (Z-input) vs. frequency of the filter network is also often desired. To obtain Z-input vs. frequency, the program in **fig. 1** is modified by adding **line 470** and by chang-

THE LARGEST AND MOST SPECTACULAR SATELLITE SEMINAR/TRADE SHOWS IN THE WORLD HAPPEN WITH SBCA/STTI! COME TO NASHVILLE FOR THE BEST OF SATELLITE TVRO OPRYLAND HOTEL SEPTEMBER 7-8-9, 1987!

Over 500 Exhibit Booths! Hundreds of Operating Antennas! Major Manufacturers & Programmers! Satellite Seminar Training! Marketing! Sales Opportunities! Fun in the Music Capital! FOR DETAILS: Call STTI at 1-800-654-9276 or 702-367-1471 or Write STTI, 4970 S. Arville, Suite 108, Las Vegas, Nevada 89118

output da	ata in pairs			output dat	a in pairs
freq (MHz) atten (dB)			freq (MHz)	atten (dB)
1.00	52.9			1.00	52.9
1.20	44.5			1.20	44.5
1.40	37.2			1.40	37.2
1.60	30.8			1.60	30.8
1.80	24.8			1.80	24.9
2.00	19.3			2.00	19.4
2.20	14.2			2.20	14.3
2.40	9.4			2.40	9.5
2.60	5.2			2.60	5.4
2.80	2.2			2.80	2.5
3.00	0.6974			3.00	0.9274
3.20	0.1490			3.20	0.3432
3.40	0.0136			3.40	0.1743
3.60	0.0011			3.60	0.1375
3.80	0.0118			3.80	0.1316
4.00	0.0199			4.00	0.1280
4.20	0.0217			4.20	0.1212
freq (MHz)	atten (dB)	freq (MHz)	atten (dB)	freq (MHz)	atten (dB)
2.72	3.2	1.96	20.4	1.30	40.7
2.73	3.1	1.97	20.1	1.31	40.4
2.74	3.0	1.98	19.9	1.32	40.0
2.75	2.8	1.99	19.6	1.33	39.7

fig. 3. Program outputs for five frequency scans. (A) Both the inductors and capacitors are considered lossless. The run time is 25 seconds. (B) A capacitor Ω of 1000 and an inductor Ω of 150 are assumed. (C) Closer response examination around 2.74 MHz. (D) Closer response examination around 1.97 MHz. (E) Closer response examination around 1.32 MHz.

160 PRINT " Freq. Z-Input Phase R-Input X-Input":PRINT " (MHz) (ohms) (deg) ----- (ohms) ----"
390 AI=BR*BR + BI*BI : AR=(DR*BR + DI*BI)/AI : AI=(DI*BR - DR*BI)/AI : REM Sub-routine for Z-input.
400 AR=AR-RL : REM Removes source resistance from Z-in calculation.
410 PRINT USING " ####.## ";FX; : REM Frequency (MHz).
430 PRINT USING " ####.##"; SQR(AR^2 + AI^2) ;: REM Z-input magnitude (ohms).
440 PRINT USING " #####.#"; ATN(AI/AR)*180/PI; : REM Phase angle (degrees).
450 PRINT USING " #####.#"; AR ; : REM Real part (ohms).
460 PRINT USING " #######"; AI : REM Imaginary part (ohms).
470 NEXT FX : END

fig. 4. Listing of changes to fig. 1 program to get Z-input vs. frequency.

ing lines 160 and 390 to 460, as shown in fig. 4. Figure 5 shows an output run using this Z-input subroutine. In addition to the input impedance magnitude, the impedance phase and the resistive and reactive components of the impedance are calculated and tabulated. (Those wishing to calculate both the attenuation and Z-input of the network should combine the appropriate lines for the two subroutines within the analysis program.)

The program in **fig. 1** can be used to analyze filters in the audio-frequency range if the inductance and capacitance units in **line 40** and in the DATA statements are changed to millihenries and nanofarads, and if the frequency unit "MHz" is changed to "kHz" in lines 20, 130, 160, 170, 390, and 430. If these changes are made to the program, the DATA statements are correct for a 50-ohm, 3.37-kHz high-pass filter, and the same attenuation vs. frequency data listed in **fig. 3A** applies to this filter, except the frequency unit in the table heading is kHz, not MHz.

The output statements of the programs shown in figs. 1 and 4 direct the calculated results to the CRT

Freq.	Z-Input	Phase	R-Input	X-Input
(MHz)	(ohms)	(deg)	(oh	ms)
1.00	133.2	-90.0	0.0	-133.2
1.20	106.5	-90.0	0.1	-106.5
1.40	86.6	-90.0	0.1	-86.6
1.60	70.6	-90.0	0.0	-70.6
1.80	57.2	-89.9	0.1	-57.2
2.00	45.2	-89.7	0.3	-45.2
2.20	33.9	-88.8	0.7	-33.8
2.40	22.5	-85.3	1.8	-22.4
2.60	11.3	-65.6	4.7	-10.3
2.80	11.5	11.1	11.2	2.2
3.00	26.6	23.5	23.8	11.8
3.20	41.0	17.6	39.1	12.4
3.40	48.6	6.2	48.3	5.2
3.60	50.0	-1.8	50.0	-1.6
3.80	49.0	-5.8	48.7	-5.0
4.00	47.6	-7.2	47.2	-6.0
4.20	46.6	-7.0	46.2	-5.7
fig. 5. Z	input vs. freq	uency for th	e same test c	onditions
used in	fig. 3A.			

monitor; however, if hard copy is preferred, the user should modify all PRINT statements to cause the table headings and outputs to be directed to the printer. See your printer manual for the proper coding.

precautions to observe when copying the program

When copying the program into your computer, be



LOW BAND DX-ING COMPUTER PROGRAMS by John Devoldere, ON4UN, for Apple Ile/c, MS-DOS, Commodore C-128 Apple Macintosh and Kaypro CPM Computers

Here's a collection of 30 super programs written by ON4UN. Just about every interest or need is covered—from antenna design and optimization to general operating programs. Antenna programs include: shunt and series input L network design, feedline transformer, shunt network design, SWR calculation, plus 11 more! General Ham programs include: sunrise/sunset, great circle distances, grayline, vertical antenna design program, sunrise calendar plus 9 more! Phew. When you sit down to use these programs you'll be amazed at what you have. The best value in computer software available today. © 1986. UIUN-Apple \$19.95

□UN-Apple □UN-MS (MS-DOS) □UN-CPM/Kaypro □UN-C-128 (COMMODORE) □UN-MAC (MACINTOSH)

SAVE \$5

BUY'EM BOTH

\$19.95

\$19.95

\$19.95

\$24.95

\$24.90

SPECIAL OFFER

LAR-UN

LOW BAND DX'ING

by John Devoldere ON4UN

1987 2nd Edition 200 pages

Book & Software Reg. \$29.90 (\$34.96 for Mac) Just \$24.90 (\$29.90 for Mac)

UN-SO (specify computer)

UUN-MSO Macintosh Special

ham radio BOOKSTORE GREENVILLE, NH 03048 603-878-1441

careful not to confuse the number 1 with the letter I or the number 0 with the letter O. After the transfer is completed, be sure to SAVE the program to disk or tape before attempting to RUN it. If you don't save the program, and the program crashes on the first run, you may have to reset your computer and the program will be wiped out. After saving the program, make a trial run for attenuation vs. frequency by duplicating the input parameters shown in **fig. 3A**. If your data output is the same as shown, you have copied the program correctly and it is ready for use. Test the Z-input subroutine the same way if you plan to use it later.

acknowledgment

The author gratefully acknowledges the assistance of Matt Fivash of Honeywell in providing the attenuation vs. frequency program subroutine and for reviewing the manuscript.

references

1. J. A. Koehler, "Top-down Filter Design," ham radio, January, 1987, page 41.

E. Niemeyer, "Network-Analysis Program Runs on Small Computer Systems," (written in HPL for the H-P 9825 computer), *EDN*, February 4, 1981.
 R. Steincross, "BASIC Program Performs Circuit Analysis," *EDN*, September, 1982.

4. K. D. Wyatt, "A Ladder Network Analysis Program," *rf design*, November, 1986.

5. B. K. Erickson, "Network Analysis on the Personal Computer," *rf Design*, December, 1986.

6. T. R. Cuthbert, Jr., *Circuit Design Using Personal Computers*, John Wiley & Sons, Inc., 1983, Program B4-1, page 434.

7. *The 1987 ARRL Handbok for the Radio Amateur*, 64th Edition, Table 16, page 2-48. Published annually by the American Radio Relay League, Newington, Connecticut.

Now Available! The new, 2nd edition of the definitive book on Low Band DX'ing. Based upon years of practical on-the-

air experience, learn the secrets of how ON4UN has been

given to transmit and receive antennas with clear concise

explanations and plenty of illustrations-dipoles, inverted

V's, slopers, phased arrays and Beverages-they're all in

receivers, operating, software and an extensive Low Band

Please enclose \$3.50 shipping & handling

bibliography. Going to be a best seller! Get yours today. ©

this book. Also covered: propagation, transmitters,

so successful on the low bands. Extensive coverage is

ham radio

Softbound \$9.95

\$29.90

THE STANDARDS OF EXCELLENCE SUPERIOR WEAK SIGNAL PERFORMANCE COMMERCIAL MODEM **COMPARE** with <u>ANY</u> unit at <u>ANY</u> Price Now Available With PACKET RADIO THE WORLD OF VHF/HF PACKET*. CW. RTTY. ASCII AND NEW DUAL AMTOR** IS AS CLOSE AS YOUR FINGERTIPS WITH THE BRILLIANTLY **INNOVATIVE STATE-OF-THE-ART** MICRO-COMPUTER CONTROLLED EXL-5000E. SPECIAL SALE SHOWN WITH OPTIONAL KANTRONICS KPC2400 AND MFJ-1270 TNC-2 \$795 Everything built in — nothing else to buy! AUTOMATIC SEND/RECEIVE—ANY SPEED ANY SHIFT • BUILT IN COMPUTER GRADE 5" MONITOR • EXTERNAL MONITOR JACK • TIME CLOCK ON SCREEN • TIMED TRANSMISSION AND RECEIVING • SELCAL • CRYSTAL CONTROLLED AFSK MODULATOR • PHOTOCOUPLER CW, FSK KEYER • ASCII KEY ARRANGEMENT • 15 CHANNEL BATTERY BACK-UP MEMORY • 1,280 CHARACTER DISPLAY MEMORY • SPLIT SCREEN TYPE-AHEAD BUFFER • FUNCTION SCREEN DISPLAY • PARALLEL PRINTER INTERFACE • SPEEDS: CW 5-100 WPM (AUTOTRACK), 12-300 BAUD (ASCII AND BAUDOT); 12-600 BAUD TTL: 100 BAUD ARQ/FEC AMTOR • ATC • RUB-OUT FUNCTION • AUTOMATIC CR/LF • WORD MODE • LINE MODE • WORD WRAP AROUND • ECHO • TEXT CURSOR CONTROL • USOS • DIDDLE • TEST MESSAGES (RY AND OBF) • MARK AND BREAK (SPACE AND BREAK) SYSTEM • VARIABLE CW WEIGHTS • AUDIO MONITOR CRICUIT BUILT IN • CW PRACTICE FUNCTION • CW RANDOM GENERATOR • BARGRAPH LED METER FOR TUNING • OSCILLOSCOPE OUTPUTS • BUILT IN 100-120 / 220-240 VAC 50/60HZ AND 13.8VDC POWER SUPPLIES • AND MUCH. MUCH MORE • SIZE: 14W x 14D x 5H · FOR YOUR NEAREST DEALER OR TO ORDER DEALER INQUIRIES INVITED EXCLUSIVE DISTRIBUTOR: asterCarc TOLL FREE...800-327-3102 AMATEUR-WHOLESALE ELECTRONICS 46 Greensboro Highway, Watkinsville, Georgia 30677 Telephone (404) 769-8706 Telex: 4930709 ITT MANUFACTURER TONO CORPORATION VISA 98 Motosoja Machi, Maebashi-Shi, 371, Japan *PLEASE CALL FOR DETAILS **Dual Amtor: Commercial guality, the EXL-5000E incorporates two completely separate modems to fully support the amateur Amtor codes and all of the CCIR recommendations 476-2 for commercial requirements. Specifications Subject to Change. 159 CADDELL We've Got Books (11) (11) COIL CORP. RFI KIT Plenty of Books Use ferrite beads and toroids 35 Main Street to keep RF out of your Poultney, VT 05764 802-287-4055 TV, stereo, Send SASE for free flyer

BALUNS

Get POWER to your antenna! Our Baluns are already wound and ready for installation in your

transmatch or you may enclose them in a

weatherproof box and connect them directly at the antenna. They are designed for 3-30 MHz operation. (See ARRL Handbook pages 19-9 or

Please send large SASE for info

-select o

\$10.50

17.00

16.00

6-20 for construction details.)

Universal Transmatch 1 KW (4:1 Impedence) Universal Transmatch 2 KW (4:1 Impedence)

Universal Transmatch 1 KW (6:1, 9:1, or 1:1-select one) Universal Transmatch 2 KW (5:1, 9:1, or 1:1-select one)

100 Watt (4:1, 5:1, 9:1, or 1:1 Impedence

Ham Radio's Bookstore Greenville, N. H. 03048



telephone.

9

Free catalog and interference tip sheet on request.

Box 455, Escondido, CA 92025

Phone: (619) 747-3343

etc.

VHF/UHF WORLD Joe Reiser

minimum requirements for 2-meter EME: part 1

First postulated in the early 1930s in Short Wave Craft, edited by Hugo Gernsbeck,1 the concept of Earth-Moon-Earth (EME) communications has been around for over 50 years. However, it wasn't until March, 1946, that authenticated echoes were heard off the moon. This was accomplished with a commercial radar operating at approximately 112 MHz.² Amateurs weren't successful at using the EME path until 1950, when W3GKP first heard W4AO off the moon on 144 MHz.³ The first Amateur two-way EME QSO didn't occur until ten vears later, when W1BU contacted W6HB on 1296 MHz on September 12, 19604; four years after that, OH1NL and W6DNG completed the first 2-meter EME QSO, on April 12, 1964.5

EME communications differs from conventional propagation in one major way: the time it takes the signal to reach the other station. In conventional terrestrial propagation, if a signal circumscribes the Earth (such as on the long path) and returns to the point of origin, it will do so in less than 140 milliseconds or one-seventh of a second (excluding, of course, the mysterious long delay echoes, or LDE). Since this is a relatively short time period, it's difficult for the average Amateur to determine whether the signal transmitted ever arrived at the desired destination. (This is the so-called "dead band" or "black hole" syndrome - was the band open, or was there just no one listening in Tibet?)

Because the distance to the moon is always greater than 221,450 miles (356,375 km) from the Earth, a radio signal traveling from the Earth to the moon and back will always take at least 2.38 seconds to complete the trip! Therefore, if you listen and hear your echo return from the moon, you can be sure your equipment is functional, propagation is favorable, and you are definitely completing the desired path.

EME communications is maturing rapidly. Only a decade ago it took a sizable commitment in time, money, and effort to be successful on EME. That is no longer true for the following reasons:

• Suitable equipment — either homebrew or commercial — is now readily available.

• On August 29, 1983, the FCC raised the USA Amateur power limit to 1500 watts output (versus 1000 watts dc input); this represents a potential 3- to 4-dB improvement.

• Improved antennas and antenna systems are now available.

• Many so-called "super stations" are now active.

I still receive many questions about EME and am often asked what band I recommend. Naturally, I'd like to recommend 70 cm (432 MHz), since that's where I began and still continue most of my EME work. However, it's definitely easier to get on 2 meters, where there's a higher concentration of super stations, all states are available, and over 50 DXCC countries have been active. Two meters is a good place to start your EME career, especially if larger antenna systems don't frighten you!

With the first weekend of the ARRL EME contest just around the corner (October 17-18, 1987) I decided to devote this and next month's column to 2-meter EME. This month's column will be primarily an introduction into EME background information and jargon. Next month's will address the minimum requirements for successful 2-meter EME communications as well as the various pieces of equipment required. By the time this material appears, you should be able to set up your own 2-meter EME station with little or no assistance.

terminology

It would be foolish to jump into EME communications headfirst without knowing and understanding the jargon. Some of the more common terms are listed in **table 1**.

Probably the most common one, *hearing echoes*, means that you can hear your own signal returning from the moon (fig. 1). As mentioned, the round-trip time on the EME path is greater than 2.38 seconds. There's plenty of time to send at least one or two letters or numbers on CW or a full call sign on SSB and then listen for your echo.


A related term, *self-test*, involves listening for your echoes. Whenever you change equipment, you can quickly evaluate the effect of that change on your system by listening to the strength of your echoes. If you can adjust and measure your output power level accurately, you can reduce your transmitter power until your echoes are barely perceptible; you'll now have a reference point for any future changes.


Measuring approximately 2160 miles in diameter, the moon travels around the Earth in a slightly elliptical orbit with an eccentricity of 0.0549. When the moon is closest to the Earth, it is said to be at **perigee**. At minimum this distance is about 221,450 miles.⁶ Perigee occurs once every 25 to 29 days throughout the year,⁷ at all phases of the moon during any one-year period, not just at the full-moon phase.

Table 1. Common EME terms (see text). Echo Self-test Periaee Apogee Semi-diameter (S.D.) Finding the moon Greenwich hour angle (GHA) Declination Right ascension Local azimuth Local elevation EME window See the moon Common window Rising or setting moon European, North American, and Asian EME window Faraday rotation Cross polarized Doppler shift Libration fading Scintillation Ground, sky, and sun noise Cold sky Hot spot Horizon shot Ground gain

Since the moon orbits the Earth in a sinusoidal manner, it stays fairly close to perigee for five to seven days at a time. Then the moon rapidly moves away from the Earth, almost like a pendulum, until it reaches apogee, its furthest distance from the Earth. At maximum this distance is approximately 252.736 miles (406,720 km), where the moon also stays for five to seven days. The average distance between perigee and apogee is 25 to 30,000 miles (40 to 48,000 km). Because of this property, EME signals at maximum apogee are attenuated by an additional 1.12 dB on each path direction, or overall about 2.25 dB more than at minimum perigee.

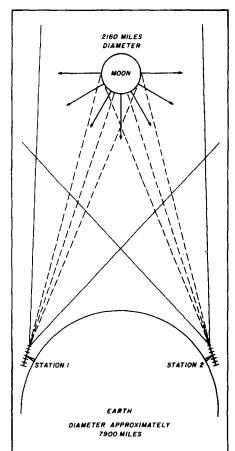Astronomers often refer to apogee and perigee by the term **semidiameter**, or S.D; this is the apparent half-width of the moon as viewed from the Earth in minutes of arc. The daily S.D. is shown at the foot of the pages in "The Nautical Almanac."^{8,9} Perigee varies greatly throughout the year; typically, it occurs with an S.D. of 16.1 to 16.7, which indicates an apparent



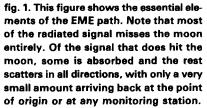

arc of 32.2 to 33.4 minutes, or just over half a degree of angular width as viewed from the Earth. Apogee is much more uniform throughout the year, with a typical S.D. of 14.6 to 14.8.

I first published a graph showing the relationship between S.D., perigee, and apogee in the Eimac EME notes.¹⁰ It was later published in reference 9 and has been reproduced in reference 11. **Figure 2** shows a recently revised version.

finding the moon

The moon's position is generally referred to in terms of *Greenwich Hour Angle* (GHA) and *declination*. GHA is the Earth's longitude over which the moon appears to be hovering, referenced to the Greenwich Meridian. The GHA of the moon varies a slight bit less than the rotation of the Earth, or just under 15 degrees per hour.

The moon's declination is referenced to the Earth's equator. Therefore, the declination of the moon represents the angular number of degrees the moon is north or south of the Earth's equator (this is the same as the Earth's latitude). The declination of the moon varies in a sinusoidal manner. Every 25 to 29 days, the moon reaches maximum northerly or southerly declination for five to seven days at a time. Declination changes slowly, seldom varying more than a degree per day at maximum, but with large variations - up to several degrees per day - when going from northerly to southerly declination and vice versa.

The moon's maximum declination is a slow, smooth function of its location with respect to the 18- to 19-year lunar cycle and varies between about 18 and 28 degrees. In the years from 1986 through 1989, we have been and will continue to be near maximum declination. Minimum declination of 18 degrees last occurred between 1977 and 1979 and will occur again between 1995 and 1998.⁷

Sometimes the moon's position may be defined in terms of right ascension and declination. This is another astronomical coordinate system which locates the apparent position of the moon with respect to the number of degrees east of the vernal equinox and the declination as previously discussed. Right ascension can be expressed in degrees, but is usually expressed in terms of hours and minutes, with one hour representing 15 degrees. Right ascension is often used to determine which portion of the sky or constellation is behind the moon as viewed from the Earth (more on that shortly).

In the good old days, we EMEers used to find the moon either by looking up at the sky and aiming our antennas accordingly or by using the hourly GHA and declination values shown in *The Nautical Almanac* with the tabular method described in reference 9. For example, if the moon's position was at GHA 66 degrees with a north declination of 18 degrees, 26.5 minutes, we knew it would appear directly overhead in San Juan, Puerto Rico. This was a tedious procedure; sometimes we'd goof, but that was part of the challenge on EME communications.

Later some fortunate EMEers with access to large mainframe computers and moon orbital prediction programs could print out a year's worth of data showing the local azimuth and elevation angles of the moon every 10 or 15 minutes of the day. With personal computers, that's changed; accurate moon position programs are now available even for the least expensive PCs. One of the most popular is the one written by Lance Collister, WA1JXN. Just input your latitude and longitude and the program displays or prints out your local azimuth and elevation to the moon as well as the GHA, declination, and right ascension for any day, time, or increment of time desired.* Figure 3 shows a sample printout; other output data shown will be discussed shortly.

the EME window

For successful EME echoes, the moon must be above your horizon. You don't actually have to be able to *see the moon* for successful EME operation; you just have to be sure that you'd be able to see it if the skies were clear. The moon isn't usually visible to the naked eye — especially in daylight — when it's within one to two days of its new moon phase, but this may still be acceptable for EME operation.

Most EMEers know their local antenna azimuth and elevation limits based on the size of the antenna structure and any local obstructions. They translate these local parameters into GHA and declination limits. If you have a few different days of EME printout,

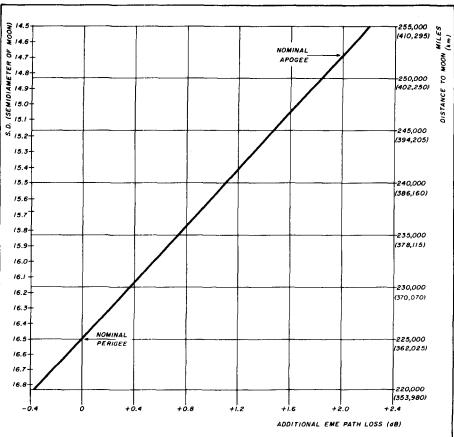


fig. 2. This graph shows the variations in EME path loss versus the distance to the moon. S.D. is the semidiameter, as explained in the text. To find additional attentuation to the moon, draw a line horizontally from either the S.D. or distance side to the pivot line and drop down to the additional path loss.

typically one at maximum northerly, one at maximum southerly, and another at zero moon declination, you can easily determine your EME window. Then it's just a simple matter of comparing your window with the window of the station you want to reach to see whether you have a *common window* at the desired schedule time. If you do, contacts at distances greater than 10 to 11,000 miles (16 to 18,000 km) are possible.

When 2-meter EME operation took off in the early 1970s, there were many stations using large tropo antenna arrays that were rotatable only in azimuth. Therefore, they could operate EME only when the moon was low on the horizon — usually referred to as a *rising or setting moon* — typically below 10 degrees of elevation.

short circuits HW-101 readout

In fig. 2 (top board schematic) of NU4F's article, "A True-Frequency Digital Readout for the HW 101" (January, 1987, page 8), the connection between the 600-ohm resistor and the 1.0-MHz timing crystal, which goes to pin 6, U5, is also shown connected to the run from pins 1, 2, 4, 5, and 8. This connection should go only to pin 6, U5.

U13 through U16 were omitted from the parts list on page 12; these are 74LS00 Quad NAND gates.

2-meter Yagi

In **fig. 2** of W1JR's May column (see page 95), the spacing of the first director is shown as 26 7/8 inches. This should have been indicated as 26 7/16 inches. According to the author, this discrepancy would probably not affect performance.

^{*}For a copy of this program suitable for IBM compatibles or the Apple Macintosh, send a double-sided, double-density diskette with sufficient return postage to Gene Shea, KB7Q, 417 Staudaher Street, Bozeman, Montana 59715.

WELCOME-NOVICES Call for Special Prices on 220 MHz Radios & Antennas

MA.



NEW ENGLAND'S FACTORY-AUTHORIZED SALES & SERVICE FOR

Also displaying the popular accessories needed to complete a HAM STATION . . .

KFN

OPEN SIX DAYS A WEEK

ARRL PUBLICATIONS • AEA PRODUCTS • AMPHENOL

- ALPHA DELTA ASTRON AUSTIN ANTENNAS AVANTI
 - BELDEN BENCHER B & W DAIWA ALINCO
 - HUSTLER KLM LARSEN MIRAGE ROHN
 - TELEX/HY-GAIN TOKYO HY-POWER LABS
 - TRAC KEYERS VIBROPLEX WELZ ETC.

KENWOOD SPECIALS

TR-3600A w/extra battery pack (70 cm) \$284.00

TM-401B (70 cm) \$318.00

TM-411A (70 cm) \$345.00

TW-4000A Dual Band 2m & 70 cm \$449.00

Cash Prices Plus Shipping Limited Stock — Order Early

Telephone 617/486-3400, 3040 675 Great Rd., (Rte. 119) Littleton, MA 01460 1³/₄ miles from Rte. 495 (Exit 31) toward Groton, Mass.

CONGRATULATIONS SWEEPSTAKES WINNERS

GRAND PRIZE KB4IP CALLBOOKS N4BPX AD9S NM6U N7GQT W1GYI JAMES HANSON K6HAZ W5PSA W9TBZ W7DCD W9DUT WB4GHY W8CTN W1JNX W9SVE W2ADK WB8VSU **BILL BROWN WD0FTS** WA8CEW K3TKW KB400J WB4EHB WD7QLD WE4R WB5FBC N4LXB W7ISV W1ULF WA2PHH WB2SIH NT8R WODYL KA9JST WB9ZMC **WB3IMW** K4VDY WA5ZIB WA9KKX K4JVT W8PIK W9DPO **WOEPB** K4TO KL7GRG DK9RU N6OA KA1Z **WB00WG** K9LL



J 156

-		ATT A CARLEND
Ċ.		LT (2) 1 THEN I MANNET TO STATE STATE
LT 2S LT33S LT23S	144/28 XVRTR 20W 902/144 Xvrtr 20W 1296/144 Xvrtr 10W 2304/144 XVRTR 0 10368/144 XVRTR 0 series low noise Ga series mast mount	State PREAMPLIFIERS / GaAstet DBM \$549 GaAstet \$559 V GaAstet \$549 /5W GaAstet \$549 /5W GaAstet \$529 Aster preamps from \$129 \$3646 ft preamps \$199 stelt DBM from \$129
TRANSVER	220 MHz Xvrtr 28 o	r 50 IF, 20 W. \$220
T144/28 PA33200 PA23150 PA1325 HF400 RK500	902 MHz 2 tube PA 1296 2tube PA, 150 2304 1tube PA, 25 High power relay 2	50 IF, 25 W\$199 200W + \$499) + W \$449 + W \$429 (w at 144 MHz \$129 y 1KW at 144 MHz \$69
Call or wri	te for catalogue.	
BOX 6286		TRANSVERTERS UNLIMITED (US) P. 0. BOX 178 NEW BOSTON, NH 03070
	~	157

ICOM

154



.....



Small enough to fit into a shirt pocket, our new 1.2 GHz and 1.3 GHz, 8 digit frequency counters are not toys! They can actually out perform units many times their size and price! Included are rechargeable Ni-Cad batteries installed inside the unit for hours of portable, cordless operation. The batteries are easily recharged using the AC adapter/charger supplied with the unit.

The excellent sensitivity of the 1200H makes it ideal for use with the telescoping RF pick-up antenna; accurately and easily measure transmit frequencies from handheld, fixed, or mobile radios such as: Police, firefighters, Ham, taxi, car telephone, aircraft, marine, etc. May be used for counter surveillance, locating hidden "bug" transmitters. Use with grid dip oscillator when designing and tuning antennas. May be used with a probe for measuring clock frequencies in computers, various digital circuitry or oscillators. Can be built into transmitters, signal generators and other devices to accurately monitor frequency.

The size, price and performance of these new instruments make them indispensible for technicians, engineers, schools, Hams, CBers, electronic hobbyists, short wave listeners, law enforcement personnel and many others.

STOCK NO:

ACCESSO	RIES: Telescopies PE pick-up antenna with RNC connector \$12.00
#1300HC	Model 1300H factory assembled 1-1300 MHz counter, tested and calibrated, complete including Ni-Cad batteries and AC adapter/battery charger \$150.00
#1200HC	Model 1200H factory assembled 1-1200 MHz counter, tested and calibrated, complete including Ni-Cad batteries and AC adapter/battery charger
#1200HKC	Model 1200H in kit form, 1-1200 MHz counter complete including all parts, cabinet, Ni-Cad batteries, AC adapter-battery charger and instructions \$ 99.95

#TA-1005	Telescoping RF pick-up antenna with BNC connector
#P-100	Probe, direct connection 50 ohm, BNC connector
#CC-70	Carrying case, black vinyl with zipper opening. Will hold a counter and accessories \$10.00
158	

FLA (305) 771-2050

ORDER FACTORY DIRECT 1-800-327-5912



OPTOelectronics inc

5821 N.E. 14th Avenue Ft. Lauderdale, Florida 33334

Orders to US and Canada add 5% of total (S2 min., S10 max) Florida residents add 5% sales tax. COD fee \$2.

MasterCard

VISA

1.3 GHZ

13007548

AVAILABLE NOW!

ISDOH

W6PO.¹²⁻¹⁴ Three windows, the *European, North American, and Asian EME windows* were defined. All three required the moon to be at any positive (north) declination.

The start of the European EME window is two hours before the moon sets in Frankfurt, West Germany. The Asian EME window begins when the moon rises above the horizon in Kurume, Japan and ends two hours later. The North American EME window is sandwiched between the European and Asian EME window. Hence, it starts immediately after the European EME window and ends when the Asian window opens. It is centered on a GHA of 116 degrees, which can also be described as the 116-degree west longitude meridian which passes just to the west of Las Vegas, Nevada.

This may all seem confusing and difficult to remember. However, the WA1JXN moon locator program un-

complicates it by incorporating all these windows in the printout. If you look at **fig. 3**, you'll see the letters E, N, and A alongside the printout between 1500 and 2145 UTC. These letters indicate, respectively, the times when you're in the European, North American, and Asian EME window. Simple enough?

path anomalies

So far I've mentioned only the anomalies attributable to the difference in path attenuation. Many others affect not only the returned signal strength, but its quality; these include *Faraday rotation, doppler shift, libration fading, scintillation*, and *noise*.

On 2-meter EME, *Faraday rotation* is probably the biggest problem. Whenever a linearly polarized electromagnetic wave passes through an ionized region such as the ionosphere, its polarity is shifted or rotated. On EME this is a double problem because signals pass through the ionosphere twice, once on the way to the moon and again on the return. Dick Turrin, W2IMU, has suggested the following rule-of-thumb equation for maximum Faraday rotation one way on 100 MHz and above:¹⁵

$\Theta \approx 200/f^2$

where Θ is the maximum number of degrees of Faraday rotation one-way and *f* is frequency in GHz. For example, the maximum one-way Faraday rotation on 144 MHz can reach 9645 degrees!

Faraday rotation is usually minimal for a station operating on the equator with the moon directly overhead because the magnetic field in the direction of propagation is virtually zero. Polar stations will be most severely affected since they have to operate at low antenna elevation angles. Hence

Apr 26, Sunday JD: 244				42D 347 71D 227 (QTH: 1							-	83,997 km ays 15.56 ´S[
									144 I	MHz	432	MHz
GMT	Notes	W	Az	Elev	GHA	DEC	RT	ASCN	DK	DB	DK	DB
0915			82.6	0.9	338.6	6.3	0H	55M	275	2.5	20	1.3
0930			85.1	3. 8	342.3	6.3	OH	56M	276	2.5	20	1.3
0945			87.5	6.5	345.9	6.3	OH	56M	276	2.5	20	1.3
1000			89.9	9.2	349.5	6.3	OH	57M	276	2.5	20	1.3
ş			ş	ş	ş	ş	ş	ş	§	§	ş	
1430			152.3	51.6	55.0	7.6	1 H	6M	282	2.7	20	1.3
1445			158.0	52.7	58.6	7.6	1H	6M	282	2.7	20	1.3
1500		Е	164.0	53.6	62.2	7.6	1H	7M	282	2.7	20	1.3
1515		Е	170.2	54.2	65.8	7.6	1H	7M	283	2.7	20	1.3
§		ş	§	§	ş	5	5	ş	ş	§	5	
1630		Е	201.9	53.1	84.0	8.0	1H	10M	284	2.7	20	1.4
1645		ε	208.0	52.2	87.7	8.3	1H	10M	284	2.7	20	1.4
1700		Ν	213.5	50.8	91.4	8.3	1H	11M	284	2.7	20	1.4
1715		N	218.7	49.3	95.0	8.3	1H	11 M	285	2.7	20	1.4
ş			§	ş	ş	ş	ş	5	ş	5	ş	ş
1930		Ν	253.5	29 .7	127.7	8.9	1H	16M	287	2.7	20	1.4
1945		N	256.4	27.1	131.3	8.9	1H	16M	288	2.8	20	1.4
2000		Α	259.1	24.5	134.9	8.9	1H	17M	288	2.8	20	1.4
2015		Α	261.8	21.9	138.5	8.9	1H	17M	288	2.8	20	1.4
ş			§	ş	ş	ş	§	ş	ş	ş	ş	5
2130		Α	274.6	8.6	156.7	9.2	1H	20M	290	2.8	21	1.4
2145		Α	277.3	6.0	160.5	9.5	1H	20M	290	2.8	21	1.4
2200			279.7	3.3	164.1	9.5	1H	21M	290	2.8	21	1.4
2215			282.1	0.5	167.7	9.5	1H	21M	290	2.8	21	1.4

Note: § indicates data omitted.

fig. 3. Sample printout of the WA1JXN EME program as described in the text. Note: Deletions have been made in the interest of brevity. This should not affect the example given in the text.

the direction of travel of radio signals is often parallel to the magnetic field and with a greater path through the ionosphere. Likewise, even stations at the equator and midlatitudes will experience significant Faraday rotation when the moon is at low local elevation angles.

Fortunately, the number of degrees of Faraday rotation are often less, perhaps only 10 percent of the maximum value shown above. The least amount of Faraday rotation occurs late at night, during the winter, and when the ionosphere has low ionization, such as during times when solar activity is at a minimum (1984 to 1986). The polarity of 2-meter EME signals during these times will usually remain constant for up to several hours.

Faraday rotation is most troublesome during daytime and summertime, especially near sunrise when drastic ionization changes take place, and during periods of high solar activity, such as the solar cycle 22 maximum predicted for 1989 to 1992. During these times, 90- to 180-degree polarity changes can sometimes occur as often as every 15 to 30 minutes. Remember that Faraday rotation occurs each time a signal passes through the ionosphere, so at any one station it's double the one-way value.

For example, if Faraday rotation is only one-tenth the maximum value (945 degrees) going toward the moon, it will probably be 1890 degrees when the signal returns from the moon to the point of origin. This just happens to be 5.25 complete polarity rotations (1890/360), and hence the signal arriving at your antenna is now 90 degrees out of phase or **cross-polarized**, so the chances of hearing echoes at this time are almost nil!

Furthermore, Faraday rotation is nonreciprocal. As a result, the station scheduled may have a different phase shift, which may cause the polarity of the signal to be optimum at one location but not at the other station at the same time. You have to be patient and wait for the polarity to shift back to optimum. (This will be discussed in next month's column.)

There are ways to beat Faraday rotation, but they're all complicated, especially on 2 meters. The most obvious fix is to use circular polarization. However, when a circularly polarized radio signal hits a surface such as the moon, its sense is reversed. Hence a signal transmitted using right-hand sense will return from the moon in lefthand sense and vice versa, thus being cancelled out at the antenna! Furthermore, a station using circular polarization will be penalized 3 dB when receiving or transmitting to a linearly polarized station. The only partial solution is to use linear polarization and devise a scheme to rotate your antenna polarity manually - a difficult job at best. This will also be discussed further in next month's column.

Doppler shift is another EME problem, but not a big one at 144 MHz. As viewed from any one location, when the moon is east of your local longitude, signals have an apparent positive frequency shift with a maximum at moonrise. When the moon is approximately due south (passing over your same longitude), doppler will be minimum to nonexistent and will shift negative as the moon travels westerly, with another maximum at moonset. Maximum doppler shift seldom exceeds about 500 Hz at 144 MHz. Remember that if the longitude of the station scheduled differs from yours, its doppler will also differ. Some tuning may be required to compensate for this change.

Libration fading is a minor problem on 2-meter EME. Basically speaking, the moon appears to rock slightly with respect to an observer on the Earth. Libration is worst when the moon is near apogee and perigee and diurnally when the moon is directly south or crossing your local longitude. If libration fading is severe, it can actually cause fades of up to 20 dB in very short periods of time, sometimes even during a single letter on CW. However, libration fading is more pronounced on higher (e.g., 70 cm) frequency bands.

Scintillation is another sporadic 2-meter EME problem somewhat simi-

lar to libration fading. Caused by patches or blobs of ionization in the ionosphere that focus or defocus the signals, it causes fading — especially during winter nighttime and while geomagnetic storms are in progress. At times it can even enhance reception by a few dB for short periods of time. Scintillation decreases with frequency and is seldom observed on 70 cm.

Several types of noise affect EME operation — for example, *man-made*, *ground*, *sky*, *and sun noise*. Manmade noise is sometimes a problem on 2 meters. If you do encounter manmade noise, it can often be decreased or eliminated with an effective automatic noise blanker on your EME receiver (or i-f if applicable) or by moving your antenna position slightly to null it out.

One of the reasons that EME is so effective on 144 MHz and above is that the local ambient noise is low. At hf, ambient noise is often 10 to 20 dB above that of a receiver looking into a shielded 50-ohm resistor. This can easily be observed. Terminate the antenna input connector on your hf receiver with a shielded 50-ohm resistor and observe the receiver noise. Now disconnect the termination and replace it with an outdoor antenna and observe the increase in noise level. It's not necessary to strive for the lowest noise figure in hf receivers because the local noise would mask internally generated noise. Repeat this same test on 2 meters or above and you may see little or no change indicating low ambient noise.

Noise can be converted to an equivalent temperature. The reference for noise is generally considered to be a temperature of absolute zero, 0.0 degrees Kelvin or -273.16 degrees Celsius (one degree change on the Kelvin scale is equal to one degree change in Celsius). The Earth's temperature is generally considered to be about 290 degrees Kelvin or approximately 17 degrees Celsius.

At 144 MHz, the *cold sky*, that portion of the galaxy that contributes the least amount of galactic or sky noise, is typically less than 200 degrees Kel-

AAI	RA	G	Ξ	KLM
	114/1	G	三	/KLM

NEW PRICE!

ANTENNA POLARITY SWITCHER MODEL APS-1

The APS-1 is a self-contained control head designed to allow remote polarity switching of circular antennas such as the Mirage/KLM range of crossed yagis.

The APS-1 may be powered by the power adaptor (included) or may alternately be powered from a vehicle or other 13-17 VDC source.

In addition to switchable outputs for two antennas, the APS-1 also contains a 6-13 volt regulated DC power supply. This feature is designed for powering items such as preamplifiers, VHF/UHF converters, etc., but may also be used whenever a low-current stabilized variable voltage source is required.

SPECIFICATIONS:

Power Requirement (AC)......117V ± 10% AC 50/60 Hz 15 Watt Power Requirement (DC)......11-16 VDC 500 mA

Outputs......Two 12 VDC unregulated, switched (antenna relay supply). One 6-13 VDC variable regulated auxiliary supply.

Total output current 500 mA with AC transformer that is included, 1 amp with optional high current transformer or external DC supply. This unit has our popular five (5) year warranty.

P.O. BOX 1000

MORGAN HILL, CALIFORNIA 95037 OUTSIDE CA

NIA 95037 (408) 779-7363 OUTSIDE CALIF. (800) 538-2140

✓ 150

FACTORY

DIRECT

HERE NOW! 1987-88 ARRL Repeater Directory

\$5.00 postpaid from ham radio Bookstore Greenville, NH 03048 (603) 878-1441

KENNEDY ASSOCIATES

Stocking all major lines. San Antonio's Ham Store. Great Prices—Great Service. Factory authorized sales and service. Hours: M-F 10-6; SAT 9-3



/ 151



152

COMMODORE 64 LADDER NETWORK ANALYSIS PROGRAM "ALADYN-64"

This program is a menu-driven design tool with a built-in circuit file editor, fast calculations and graphic output to either the screen or printer. Useable for circuits which operate from VLF through Microwave. Circuit elements include R's, L's, C's, transmission lines, transistors and FET's. Output format rectangular or Smith chart.

\$59.95 PPD. Check or M.O. INTERCEPTOR ELECTRONICS INC. ROUTE 1, BOX 439, ROUND HILL, VA 22141-9307 PHONE (703) 338-4905

- 153



vin, 98 degrees Celsius below room temperature, or about -73 degrees Celsius. Therefore, if you first aim your 2-meter EME antenna a few degrees below the horizon, note the receiver output noise level and then elevate your antenna to point at one of the colder portions of the sky, all other things being equal, you'll notice a decrease in receiver noise.

Radio astronomers have measured and mapped galactic noise in terms of equivalent noise temperature at several different frequencies using very narrow beamwidth antennas.¹⁶ These maps are now widely available; the 136- and 400-MHz versions were reproduced in one of the Eimac EME notes.¹⁷

Using these maps, you can find hot spots, areas that have an equivalent noise temperature of over 3000 degrees Kelvin! Aim your antenna at the center of the galaxy in the Milky Way (between the constellations of Sagittarius and Scorpius), and you'll find that your antenna noise temperature will increase significantly. Because the moon moves across the sky once every 28 days, it sometimes passes directly between the Earth and one of these hot spots. C.R. Somerlock, W3WCP, showed a method of calculating your system's degradation based on the sky temperature behind the moon.18

Fortunately the hottest spots in the galaxy are very narrow and mostly in the southern hemisphere (southerly or negative declinations), which is not used as much by 2-meter EMEers. Since 2-meter EMEers feel that the noise in these areas significantly degrades performance, they usually avoid making schedules when the moon passes through the higher temperature portions of the sky.

Sky noise maps are usually referenced to right ascension and declination and are therefore cumbersome to use with the normal parameters of GHA and declination. However, Derwin King, W5LUU, and Lance Collister, WA1JXN, have devised tables and incorporated sky noise temperature information into the WA1JXN EME program described earlier. If you look at the sample printout in **fig. 3**, you'll note that the right ascension (RT ASCN) is shown along with the sky temperature in degrees Kelvin at both 144 and 432 MHz for each position of the moon along with potential degradation in dB. This really simplifies calculations.

Sun noise is another minor problem on EME. On a good EME system, your receiver output with a typical EME antenna will increase 6 to 10 dB when your antenna is aimed directly at the sun. Consequently, EMEers don't make schedules when the moon is within about one day of new moon.

Despite its noise, the sun is still an excellent source for antenna and system tests. Generally speaking, the more sun noise you see, the higher the gain of your antenna. To do a sun noise test, first reference your receiver noise output by aiming your antenna at a cold spot in the sky. Then aim your antenna at the sun and measure the increase in noise. One note of caution: sun noise is a function of solar activity, so if you get a very high reading, test at another time when the sun is less active.

You can check your antenna's pointing accuracy at the same time you test for sun noise. Calculate the position of the sun just as you calculated the position of the moon. Sun locator programs are also available; one is included on the WA1JXN moon locator program diskette.

horizon shot

As mentioned before, it's sometimes inconvenient for 2-meter EMEers to elevate their large tropo antenna arrays, but they still want to make EME contacts. So these operators keep schedules with the larger stations at their local moonrise or moonset, whichever is applicable.

Horizon schedules are much less reliable because ground noise may limit signal levels. Nevertheless, many EME contacts have been made in this manner. All that's necessary is to set up a schedule when the moon is at less than about 10 degrees of elevation at your location. If you're very lucky on a horizon schedule, you may get *ground gain*, which is somewhat analogous to the enhancement reflection you occasionally experience if you observe sunrise or sunset across a body of water. Six to 12 dB (round trip) of enhancement is theoretically possible; this can improve your chance of success significantly. Give it a try. Many stations are willing to run such schedules.

summary

This month's column was essentially a primer on EME communications, with the emphasis on 2 meters. Several techniques for locating the moon were discussed, as well as some of the terminology involved with EME communcations. Next month's column will discuss the minimum requirements and equipment required for 2-meter EME communications. With this information, you can join the fun on the cutting edge of communications technology.

new records

I'm happy to announce that the first Amateur two-way EME contact above 2320 MHz was made on April 7, 1987. Dave Hallidy, KD5RO (EM12KV), operating from Rick Fogle, WA5TNY's QTH, completed a two-way EME QSO on 9 cm (3456.1 MHz) with Les (Lucky) Whitaker, W7CNK/5 (EM15FI), for a distance of 174 miles (280 km). Then WA5TNY joined in to work W7CNK. Three- and 5-meter dishes with relatively low power (100 watts maximum) were used. Congratulations to Dave, Rick, and Lucky, who have been working very hard on this project for some time. Now that the 9-cm band has been scaled, I'll bet this record won't last long!


technical notes available

Dick Turrin, W2IMU, has recently updated the classic *Technical Reports* from The Crawford Hill VHF Club. Primarily devoted to 1296-MHz EME, it includes 20 separate notes dealing with subjects such as system considerations, transmitters, receivers, and antennas for EME. These notes are in-



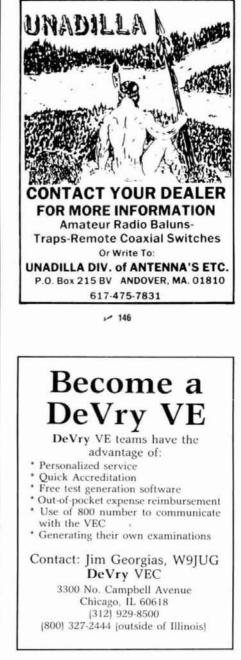Barry Electronics Commercial Radio Dept. offers the Best in two-way communications for Businesses, Municipalities, Civil Defense, Broadcasting Companies, Hospitals, etc. Sales and Service for all brands: Maxon, Yaesu, Icon, Tad, Octagon, Regency/Wilson, Midland, Standard, Uniden, Shinway, Fujitus, Seas, Spillsbury, Neutec, etc. Call or write for information. 212-925-7000.





87 CALL DIRECTORY	
All three — \$20	\$8 \$8 \$8
Shipping per order \$3 KMASTER PUBLISHING Mineral, Virginia 23117	
	(on microfiche) ex All three — \$20 Shipping per order \$3 KMASTER PUBLISHING

Jun 147

valuable for the serious UHF and VHF EMEer as well as the microwave specialist. A check for \$24.00 (\$26.00 outside the United States) made out to Dick Turrin at P.O. Box 65, Colts Neck, New Jersey 07722, will bring a copy by return mail. Because of the high cost of cashing them, no foreign bank drafts can be accepted.

important VHF/UHF events

August 1-2	ARRL UHF Contest
August 1-3	SWOT (Sidewinders On Two)
	Open QSO Party (contact
16.221 16.1	K5IS)
Aŭgust 8	EME Perigee
August 12	Predicted peak of the Perseids meteor shower at 1300 UTC.
August 22-23	ARRL 10-GHz Cumulative Contest, first weekend.
September 5-6	International Region 1 VHF Contest, 2 meters only
September 6	EME perigee
September	
10-13	Microwave Update '87 Confer- ence, Estes Park, Colorado (contact W0PW)
September	
12-14	ARRL September VHF QSO Party
September 21	Optimum time for TE propaga- tion (±2 weeks).
September	
19-20	ARRL 10-GHz Cumulative
	Contest, second weekend.

references

 Bill Orr, W6SAI, "Ham Radio Techniques: Diana to EME in 20 Years," *ham radio*, February, 1981, page 40.
 Herbert Kauffman, W2OQU, "A DX Record: To the Moon and Back," *QST*, May, 1946, page 65. 3. Edward P. Tilton, W1HDQ, "Lunar DX on 144 MHz!", QS7, March, 1953, page 11.

 Edward P. Tilton, W1HDQ, "Coast to Coast Via the Moon on 1296 mc!" *QST*, September, 1960, page 10.
 Sam Harris, W1FZJ, "U.S. to Europe on Two Meters,"*QST*, June, 1964, page 95.

 Jean Meeus, "Extreme Perigees and Apogees of the Moon," Sky and Telescope, August, 1981, page 11.
 Berenice L. Morrison, "Perigee and Apogee of the Moon 1959-1999," United States Observatory Circular No. 130, April 19, 1971.

8. The Nautical Almanac, 1987, United States Government Printing Office, \$11.00.

 Joseph H. Reisert, Jr., W6FZJ/1, "EME Scheduling, When and Where," *OST*, July, 1974, page 25.
 Joe Reisert, W6FZJ, "An EME Path Loss Nomogram," *Eimac Amateur Service Note 49-2: Moonbounce Operating Aids*, Varian Eimac, Inc., 301 Industrial Way, San Carlos, California 94070.

11. The ARRL Handbook, 1987 edition, Chapter 23, "Space Communications"; available from Ham Radio's Bookstore for \$18.00 plus \$3.50 shipping and handling. 12. Robert I. Sutherland, W6PO, "Universal EME Window for USA and Europe," *Eimac Amateur Service Note* 49-2: *Moonbounce Operating Aids*, Varian Eimac, Inc., 301 Industrial Way, San Carlos, California 94070. 13. Ken Tentarelli, W1FZA, "Proposal for a Universal EME Moonbounce Window," *Eimac Amateur Service Note* 49-3: *More on the Moonbounce Universal Window for 144 MHz*, Varian Eimac, Inc., 301 Industrial Way, San Carlos, California 94070.

 Robert I. Sutherland, W6PO, "Recommendations for Moonbounce Universal Window," *Eimac Amateur Service Note 49-12: Additional Moonbounce Operating Aids*, Varian Eimac, Inc., 301 Industrial Way, San Carlos, California 94070.

 The Crawford Hill VHF Club W2NFA, "Polarization Standardization for 1296 mc EME," *Technical Report* May, 1968 (see technical notes available, above).
 Ko, "The Distribution of Cosmic Radio Background Radiation," *Proceedings of the IRE*, January, 1958, page 208.

17. Radio Sky Maps, Eimac Amateur Service Note 49-25.

18. C. R. Somerlock, W3WCP, "Sky Temperature Behind the Moon," *QST*, October, 1964, page 38.

ham radio



DOWN E	AST N	ICROW	AVE	
معمد المعالم المعالية المعالم المعالية المعالية المعالية المعالية المعالية المعالية المعالية المعالية المعالية معمد المعالية	Ĩ		TRANSI	-
MICROWAVE AN • Loop Yagis • Power Di Arrays • Microwave Tran • TROPO • EME • Weak • 2304 • 2400 • 3456 MH	viders sverter Signal z	Linear Amp • GaAsFE • OSCAR • 1	T Preamp 02 + 1260	complete • • 1296
1345 LY 45el loo	p Yagi		20dBi 20dBi	\$93 \$80
Above antennas assemb			18.5dBi available.	\$93
All Aluminum and Stainle Add \$8 UPS S/H, \$11 Wes			i.	
2316 PA Linear Amp 1W 2335 PA Linear Amp 10W NEW! MICRON BY LMW	WAVE	out 1296 Mi	VERTE	295 ppd.
Stripped down	T, T/R : for shi versio	Sequencer, pping UPS n, kits also	Output M /48 o availab	nter \$589
VISA DOWN E	AST	EE Catalog		
Box 1655A RFD .			04922 U.	S.A.
				r 14
VHF-U	HF	POWE	R DIVI	DERS
40.	-	RF power (best way to fountenna array pain and at th osses to a mi	eed in-pha is to maxim he same to	use 2 and 4 nize system ime reduce

best way to feed in phase 2 and 4 antenna arrays to maximize system gain and at the same time reduce losses to a minimum. Covering 144 thru 1296 MHz, this series of VHF/ UHF power dividers are premier RF devices designed for a long service life with low SWR and broad operating bandwidth.

Extruded aluminum body with a durable enamel finish in addition to silicon sealing at connector flanges results in a ruggedized unit for all array installations. Available with N-type connectors only, these units are unconditionally guaranteed for 2 years.

MODEL	CONFIG.	PRICE
144-2P	(2 ports)	\$51.00
144-4P	(4 ports)	\$58.00
220-2P	(2 ports)	\$50.00
220-4P	(4 ports)	\$57.00
430-2P	(2 ports)	\$48.00
430-4P	(4 ports)	\$56.00
902-2P	(2 ports)	\$48.00
902-4P	(4 ports)	\$56.00
1296-2P	(2 ports)	\$49.00
1296-4P	(4 ports)	\$57.00
	SHIPPING NOT INCLUDE	

STRIDSBERG ENGINEERING, CO. P.O. Box 7973 • Shreveport, LA 71107 • USA Phone: (318) 865-0523

- 149

(MRM)	Microwave Research & Mfg
wave Engine MRM is a fast wave oscillato assemblies to wave market	ng for some self-motivated Micro- ers and Microwave Technicians. moving company supplying micro- ors, amplifiers and integrated hybrid the military and commercial micro- place. We offer excellent salary
EESOF, AUT or oscillator d	to our team members. If you know OCAD, chip & wire techniques and/ esigns; and can get things done— Send resumes to D. Mitchell, K8UR.
EESOF, AUT or oscillator d we want you.	OCAD, chip & wire techniques and/ esigns; and can get things done—
EESOF, AUTo or oscillator d we want you.	OCAD, chip & wire techniques and/ esigns; and can get things done— Send resumes to D. Mitchell, K8UR.



50 🌆 August 1987



Reader Service CHECK-OFF Page 98

August 1987 🛺 51





BY0AA revisited


There it is! The QSL card from BY0AA — the station located in the far western province of China, an area that had been void of Amateur Radio activity until now. But where is the town where BY0AA is located? *Wulumuqi* wasn't even on the large wall map of China a friend of mine brought back recently from Peking!

My good friend Ned Jacoby, NG6W, solved the riddle with the aid of the large Times Atlas of the World, which explained the variations in spelling Chinese place names. According to that source, the old English Conventional spelling had gone through various convolutions, to be followed by the Wade-Giles translations of place names, which had in turn given way to the newer Pinyin spelling. In the English Conventional system, the name of BY0AA's town was spelled Urumchi; in the Wade-Giles system, it was spelled Wulumuchi; in the Pinyin system, it's Urumqui. BY0AA's OSL card, on the other hand, spells it Wulumuqi.

In passing, NG6W pointed out that what we knew as Sinkiang Province is now Xinjiang Uygur Zizhiqu. Tibet is now Xizang Zihiqu! Lhasa seems to have remained Lhasa. Is it all clear now? (NG6W also suggests that when the pile-ups on BY0AA get too huge, you can always direct-dial them on the telephone via a satellite link!)

do you have AMI?

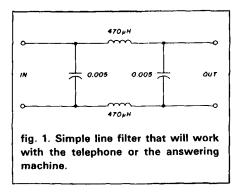More and more Amateurs are having problems with AMI (Answering Machine Interference). What next? Some




of these little demons seem to have rf sensitivity comparable to that of a good communications receiver. Luckily, the machine I have seems to be rfproof. But my next-door neighbor has one that turned into a public address system every time I went on the air! The usual cures of wrapping the line cord around a ferrite toroid and placing a telephone type Z-100 filter in the phone line didn't make any difference in the level of interference.


Not wishing to dig into my neighbor's answering machine, I enjoyed the luxury of indecision until an Amateur friend who had gone through this ordeal a few months earlier came up with a solution that worked for me. His opinion was that the phone company's Z-100 filter was designed mainly to filter out nearby broadcast stations and was therefore relatively ineffective at 14 MHz. He suggested wrapping the power cord of the answering machine around a "lossy" ferrite rod* and then placing a simple rf filter in the answering machine at the point where the telephone line entered the machine (see fig. 1). I had no option but to dig into the machine and insert the filter, which turned out to be a simple task. The gamble was worth it. The combination of a lossy line filter for the power cord and the little network filter in the phone line did the job. Keep this scheme in mind if you're unlucky enough to have AMI.


the "computerized" Yagi beam antenna

Great advances in Yagi antenna design have been accomplished in the last decade, thanks to the versatility of the computer. A number of programs for antennas such as the W2PV design and others have been generated; all seem to have been derived from an original program done by I.L. Morris for a PhD thesis at Harvard in 1965. The resulting offspring yield good Yagi

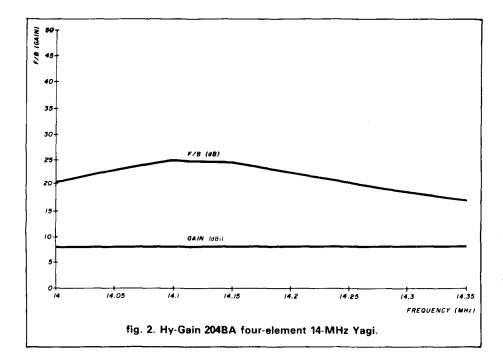^{*}The ferrite rod measures 7.5 inches long by 0.5 inches in diameter; manufactured by Amidon (No. R33-050-0750), with $\mu = 800$ (type 33 material).



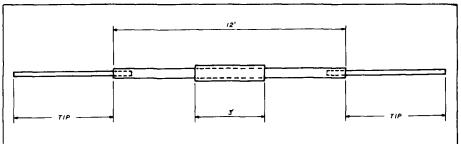

 

struction details are illustrated in fig. 3.				
Element	Tip lengths	Spacing		
Ref	136.4 inches (346.46 cm)	122.9 inches (312.17 cm		
DE	126.9 inches (322.33 cm)	88.8 inches (225.55 cm		
D1	116.7 inches (296.42 cm)	95.6 inches (242.82 cm		
D2	112.6 inches (286.00 cm)			

data — but unfortunately, all initial conditions don't always converge to the same antenna! The taper data provided by W2PV brought these programs into greater uniformity.

Wayne Hillenbrand, N2FB, working with others, has come up with some computer-aided antenna designs that provide good gain and excellent frontto-back ratio. The data was presented at the 1986 Dayton Harnvention. The first N2FB design involves a four-element, 14-MHz beam derived from a Hy-Gain 204BA. The gain and front-to-back ratio of the revised antenna are shown in **fig. 2**. Construction details are provided in **fig. 3**; dimensions are given in **table 1**. Each element is made up of a 3-foot length of 1.25-inch diameter sleeve which is slipped over a 12-foot length of 1.125-inch diameter tubing. The tip

sections are made of 12-foot lengths of 1-inch diameter tubing.

The driven element appears to be shorter than normal, and this is correct. The length shown provides better SWR bandwidth across the entire band, but doesn't change the antenna pattern.

Details for a modification of the Hy-Gain 205BA-S are provided in **table 2** (see **fig. 3** for element assembly details). Antenna gain remains substantially the same as with the original dimensions, but the front-to-back ratio at the design frequency rises from about 15 dB to nearly 35 dB. Minimum front-to-back ratio (at the band edges) is better than 21 dB with the revised dimensions.

Data for an optimized six-element, 14-MHz beam is shown in **table 3**. The boom length is 54 feet; the boom is made of heavy-wall aluminum tubing measuring 3 inches O.D. All elements are insulated from the boom with a plastic plate. The front-to-back ratio is better than 26 dB across the band.

All beams employ a gamma match feed system. A 4-foot rod is used, with some RG-8/U center conductor fed into the tube for the capacitance adjustment. The end of the tube is crimped to keep water out.

Wayne tells me that 10-meter versions of these antennas have been built by simply scaling down the dimensions. The boom length is slightly altered to allow the use of 12-foot lengths of standard 2-inch diameter industrial tubing. Dimensions for these antennas are given in **table 4** and **table 5**; construction details are shown in **fig. 4**.

Wayne makes the interesting observation that if the driven element is removed, the remaining elements are almost equally spaced. Equal spacing of all parasitic elements produces a high front-to-back ratio, but only for a narrow bandwidth. Wayne is working on a program that compares a Yagi to an LC filter. With that, he expects he'll be able to design for very high *Q* and narrow bandwidth or lower *Q* (i.e., poorer front-to-back ratio) but wider bandwidth.

Obviously, great advances are being made in understanding the operation of the Yagi antenna, and it's now possible to custom-design a Yagi for a particular degree of gain, bandwidth, or front-to-back ratio. This demolishes the old W6SAI theory of Yagi design: "Cut the director short, the reflector long, and let 'er rip!"

a toggle-switch box for changing antennas

Use toggle switches for changing antennas? Cliff Klinert, WB6BIH, has tried it at the 100-watt level in the hf region and reports that it works well. He's taken a small aluminum box and mounted two coax receptacles on it, plus four DPDT center-off toggle switches on the face of the box (see **fig. 5**). With this arrangement, he can hook either his transmitter or receiver to any one of four antennas. The box can also be used with two transceivers.

A less obvious use of the "toggle box" is to connect two or more antennas in parallel. Cliff says that his 20-meter Yagi and his 80-meter vertical antenna, when switched in parallel, provide a low enough value of SWR to work well on 15 meters! He's found that for general coverage listening, some combination is always optimum for any frequency.

The center-off switch was chosen so that two radios can be used with minimum danger of transmitting into a receiver. To prevent confusion, all switches should be clearly labeled. The only danger is the possibility of accidentally transmitting when all toggle switches are in the center-off position, which would make any transmitter very unhappy.

75-80 meter helical antenna

Bob Walton, W6CYL, sent me information about this interesting antenna, which was developed by Gene Koenig, W6HVR. The simplified version of his design, shown in **fig. 6**, requires a space of about 40 feet.

The helix is wound from a 110-foot length of No. 15 copper-enamel (or formvar) wire. It's close-wound on a 3/16-inch diameter aluminum rod used as a temporary form.

If you don't have access to a coilwinding machine but know how to operate a lathe, you can do the job that way. You'll need an assistant to track the wire so that it doesn't kink or snarl. Once the coil is wound, the hard part of the job is over.

The helix is supported on a heavy-


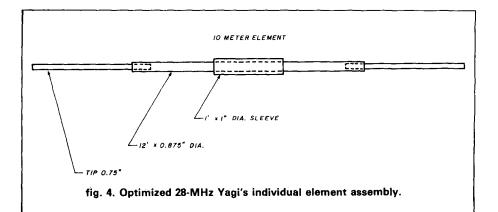


Table 2. Dimensions of modified 14-MHz Hy-Gain Yagi (No. 205BA). See fig. 3 for assembly details.

Element	Half-length	Spacing
	(inches)	(inches)
Reflector	213.23	65.2
Driven Element	198.68	64.8
Director 1	198.21	124.1
Director 2	188.55	153.7
Director 3	181.52	

Table 3. Dimensions of six-element, 14-MHz optimized Yagi on 0.75 wavelength boom (maximum gain = 10.71 dBI). See fig. 3 for construction details.

Element	Tip	Spacing
Reflector	139 inches (353 cm)	86.4 inches (219.5 cm
Driven Element	124.5 inches (316.2 cm)	77.7 inches (197.4 cm
Director 1	126.6 inches (321.6 cm)	157.5 inches (400 cm)
Director 2	121.9 inches (309.6 cm)	142.9 inches (362.9 cm
Director 3	121.9 inches (309.6 cm)	142.9 inches (362.9 cm
Director 4	113.5 inches (288.3 cm)	

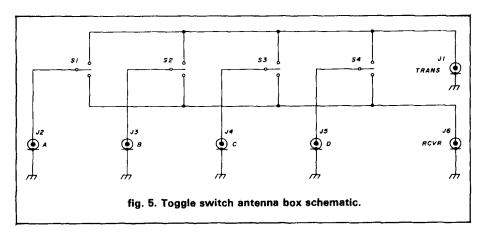



AMECO, AMERITRON, AMP SUPPLY, ANTENNA SPECIALISTS, ASTRON, BENCHER, BUTTERNUT, B & W, CSI, CALLBOOK, CUSHCRAFT, DAIWA, DIAMOND, ENCOMM, HAL, HEIL, HUSTLER, ICOM, KDK, KANTRONICS, KENPRO, LARSEN, MFJ, MICROLOG, MIRAGE/KLM, NYE, PALOMAR, RF CONCEPTS, ROHN, SANTEC, SHURE, TE SYSTEMS, TELEX/HYGAIN, TEN-TEC, TOKYO HY-POWER, VIBROPLEX, W2AU BALUNS, WELZ, YAESU

For Orders and Price Checks Call 800-523-7731

Indiana and Information Call 1-812-422-0231

	HARDLINE - 50 C	HM		11	C	ONNECTORS - MAD	FINUS	4
Namal No.	Description	rim.	Per Ft.	1		Description	E IN 0.5.	Each
FXA12	1/2" Aluminum Black Jacket		89	4	NE720	Type N for Belden 9913		4.25
FLC12	1/2" Corr. Copper Blk Jkt.		1 59		NE723	N Female Belden 9913		4.75
FLC78	7/8" Corr Copper		3 92	14	PL258AM	Amphenol Barrel		1.45
NM 12AL	N Conn. 1/2" Alum (Male or Female	63	22.00	1	PL259	Standard Plug for RG8, 213	10/5 90 or	65
NM12CC	N Conn. 1/2" Copper (Male or Fema		22 00		PL259AM		10/7 90 0/	89
NM 78CC	N Conn. 778" Copper (Male or Ferna		54 00	3	PL259TS	PL259 Tetion/Silver		1.59
THE FOUL	Second and the second second		94.00	1	UG21D	Type N for RG8, 213, 214		3.00
	COAXIAL CABLES			1	UG83B	N Female to PL259		6 50
Nemai No.	Description	100 Ft.	Per FL		UG88C	BNC RG58		1.25
1100	RG 8 95% Shielded Mil Spec	28 00	32		UG146	S0239 to Male N		6 50
1102	RG8 95% Shielded Foam	30.00	32		UG175/6	Adapter for RG58/59 (specify)	10/2 00 of	22
1110	RG8X 95% Shield (mini 8)	15.00	17		UG255	S0239 to BNC Amphenol		3.75
1130	RG213/U Mil Spec 96% Shield	34 00	36		KA51-18	TNC RG58		4.35
1140	RG214/U Mil Spec - Dbl Silver	155.00	1.65		AM 9501-1	SMA RG1428		8.95
1180	Belden 9913 Low Loss	46 00	50		S0239AM	Amphenol S0239		89
1705	RG142B/U Tetion/Silver	140.00	1 50		S.2010.000	GROUND STRAP - E	BRAID	
1310	RG217/U 5/8" 50 ohm Dbl. Shield	80.00	85			Description		Per Ft
470	RG223/U Mil. Spec. Dbl. Silver	80.00	85		GS38	3/8" Tinned Copper		30
1450	RG174 95% Shielded Mil. Spec.	12 00	14		GS12	1/2" Tinned Copper		40
	ROTOR CABLE - 8 CC	ALD.			G\$316	3/16 Tinned Copper		15
		10070			G\$3165	3/16" Silver Plated		35
	Description	100 Ft.	Per Ft.		G	ROUND WIRE - STR	ANDED	
C1822 C1620	2-18 Ga 6-22 Ga 2-16 Ga 6-20 Ga Heavy Duty	19.00	21 36			Description		Per Ft
	ping \$3.00 - 100 Ft. / Conn. \$3.00 /				HW06	6 Ga insulated stranded		35
Call c	or write for complete prin	ce list.	Nema					
is av	ailable at no charge with	n orde	rs of \$5	0.00	or more.	, or at a cost of \$4.00 i	ndividual	y.
NE	MAL ELECTRO	DNI	CS,	INC).	(305) 893—3924 • Te	lex 69753	77
1	2240 N.E. 14 Ave., No. M	liami, I	FL 331	61		24-Hr. FAX (305) 8	95-8178	
	2240 N.L. 14 AVE., NO. N	nann,	FL 331			24111.1 AX (303) 0	35-0170	

This publication is available in microform from University from University Microfilms International. Please send information about these titles: Name Company/Institution Address City State Zip Phone [__] Coll toll-free 800-521 3044. In Michigan.


56 🕼 August 1987

Call toll-free 800-521-3044. In Michigan, Alaska and Huwan call collect 313-761-4700. Or mail inquiry to: University Microfilms International, 300 North Zeeb Road, Ann Arbor, MI 48106. Table 4. Optimized 28-MHz Yagi: six-element, 24-foot boom, 10-meter Yagi dimensions (see fig. 4 for construction details).

Element	Tip lengths	Spacing
Ref	33.48 inches	35.19 inches
DE	26.25 inches	35.86 inches
D1	27.32 inches	75.75 inches
D2	25.19 inches	68.43 inches
D3	24.95 inches	86.77 inches
D4	20.77 inches	

 Table 5. Optimized 28-MHz Yagi: four-element, 12-foot boom, 10-meter Yagi dimensions (see fig. 4 for construction details).

Element	Tip lengths	Spacing
Ref	31.70 inches	57.55 inches
DE	26.25 inches	40.38 inches
D1	21.84 inches	43.82 inches
D2	19.82 inches	

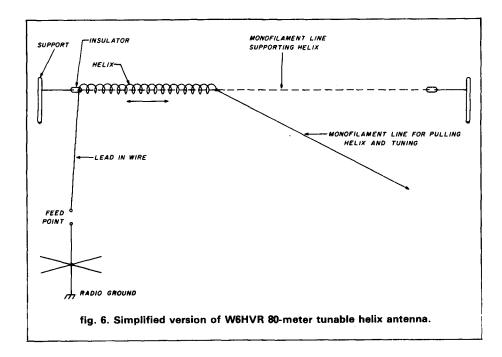

duty monofilament fishing line — the type used for ocean fishing. The helix is carefully laid out on the ground, still close-wound. A length of the nylon monofilament line is fished through the center of the helix, using an aluminum welding rod as a guide or needle. One end of the nylon line is then run to an insulator. A second length of nylon line is attached to the far end of the helix to permit expansion and compression of the coil. This line is left dangling, and the far end of the assembly is hoisted to the top of the support structure. The opposite end of the helix is attached to the feed wire. The nylon center rope is then used to pull the helix into the final position.

As an end-fed antenna, it requires a good ground system. A ground rod, plus quarter-wave radials laid on the ground, are recommended.


The antenna is capable of operation across the 80-meter band. To resonate the antenna, the helix is pulled out with the nylon cord. Bob recommends the use of a noise bridge and the station receiver for the initial adjustments. The antenna can be then be fine-tuned with the aid of an SWR meter and a little transmitter power.

Although this antenna is only about 40 feet long, its bandwidth response is quite good. It's possible to bring the nylon cord back to the operating room and tune the antenna to any portion of the 80-meter band by adjusting tension on the cord. With the use of a tuner, it will operate on the higher frequency Amateur bands.

new EME directories

A new supply of the popular "144 MHz EME Directory" has been printed. This lists many of the moonbounce stations and operators, giving the name, call, address, phone number (where applicable), and equipment. To obtain your copy, send five first-class stamps (or five IRCs) to me at EIMAC, 301 Industrial Way, San Carlos, California 94070.


ham radio

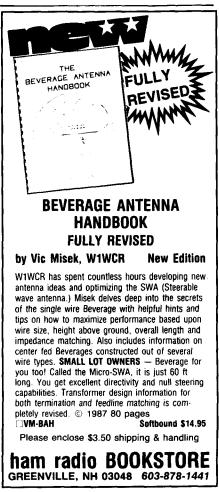

Put More Punch in Your Packet

Outstanding mechanical design makes the IsoPole the only logical choice for a VHF base station, especially for Packet operation. All Isopole antennas yield the maximum gain attainable for their respective lengths and a maximum signal on the horizon. Exceptional decoupling from the feed line results in simple tuning and a significant reduction in TVI potential. The IsoPole antennas are all impedance matched in the factory so that no field tuning is required. The IsoPoles have the broadest frequency coverage of any comparable VHF base station antenna. This means no loss of power output from one end of the band to the other, when used with SWR protected solid state tranceivers. Typical SWR is 1.4 to 1 or better across the entire band.

A standard 50 Ohm SO-239 connector is recessed within the base sleeve (fully weather protected). With the IsoPole you will not experience aggravating deviation in SWR with changes in weather. The impedance matching network is weather sealed and designed for maximum legal power. The aerodynamic cones are the only appreciable wind load and are attached directly to the support (a standard TV mast which is not supplied).

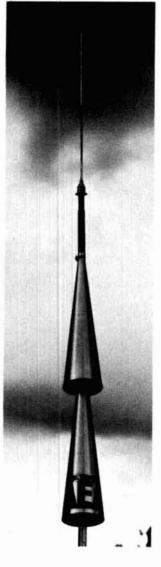

High Performance Hand-Held Antenna — The Hot Rod

The Hot Rod antenna can be expected to make the same improvement to hand-held communications that the IsoPole antennas have made to base station operation. Achieve 1 or 2 db gain over ANY 5/8 wave two meter telescopic antenna. The factory tuned HR-1 is 20% shorter, lighter and places far less stress on your handheld connector and case. It will easily handle over 25 watts of power, making it an excellent emergency base or mobile antenna. In the collapsed position, the Hot Rod antenna will perform like a helical guarter wave. Three Hot Rods are available; HR-1 1/2 wave 2M Ant., HR-2 for 220 Mhz, and HR-4 for 440 Mhz. Amateur Net Price on all Hot Rods is \$19.95.

For either base station or hand-held operation AEA has the perfect VHF/UHF antenna. Put more punch in your Packet station with an AEA IsoPole or Hot Rod antenna. To order your new antenna contact your favorite Amateur Radio Distributor. For more information contact Advanced Electronic Applications, P.O. Box C-2160, Lynnwood, WA 98036, or call 206-775-7373.

IsoPole Specifications

Model Freq. Coverage (Mhz) 2.1 VSWR bandwidth Power Rating Gain** Radiating Element Length Amateur Net Price

144	220	440
135-160	210-230	415-465
)12Mhz @ 146Mhz)15Mhz @ 220Mhz)22Mhz @ 435Mhz
1 kw	1 kw	1 kw
3 dbd	3 dbd	3 dbd
125.5" (3.2m)	79.25" (2m)	46'' (1.2m)
\$49.95	\$49.95	\$69.95

**dbd - db gain over a dipole in free space

Prices and Specifications subject to change without notice or obligation.

AEA Brings you the Breakthrough!



138



TRANSMISSION LINE TRANSFORMERS A new ARRL Publication by Dr. Jerry Sevick, W2FMI

COMING SOON!

Despite the popularity of transmission line transformers in both commercial and amateur applications, little practical design information has been published concerning these devices. The lack of data was made abundantly clear to Jerry Sevick, W2FMI when he began designing matching transformers for the short vertical antennas that are the subject of his classic series of articles that appeared in *QST*. In order to fill in the gaps of available knowledge, Jerry decided to study the subject of transmission line transformers in depth and the results of his findings are contained in this new ARRL publication!

Transmission Line Transformers covers types of windings, core materials, fractional-ratio windings, efficiencies, multiwinding and series transformers, baluns, and limitations at high impedance levels. There is also a chapter on practical test equipment. This book is must reading for everyone interested in antenna and transmission line theory. Copyright 1987, 128 pages \$10 hardcover only.

The American Radio Relay League, Inc 225 Main St., Newington, CT 06111 / 140

designing trap antennas: a new approach

Symmetrical design increases gain and directivity

Most Amateurs don't realize that the original design of a trap antenna^{1,2,3,4} represents just one particular case, and is not the best possible choice of the many designs available. According to the references, a dipole designed to resonate at two frequencies, f1 and f2, contains parallel RLC circuits - or traps that are resonant at the upper frequency, f2, and physically separated by a half wavelength (at f2). This approach I call the "classic" design. At f2 these circuits offer a very high impedance and, in effect, disconnect the outer portions of the antenna. The inner portion acts as a half-wave dipole. With the total antenna length made equal to one half wavelength at the lower design frequency, f1, the antenna would resonate at this frequency if the traps presented a short circuit. In practice, however, the traps introduce an inductive reactance at all frequencies lower than f2. To compensate, the total length of the antenna is slightly shortened in order to be resonant at f1.

Treatments of this subject in reference books usually ignore other existing designs and imply incorrectly that this description applies to all trapped antennas.

Extending this design approach to three bands (10, 15, and 20 meters) would require the two sets of traps to resonate at 21 and 28 MHz and be separated by approximately 3 feet (on each half-dipole element). Some of the first commercially manufactured triband antennas actually did use separated traps, but those generally available today have such pairs of traps built into a single assembly.

A vertical trap antenna, just slightly longer than a quarter wavelength at the upper frequency f2, was discussed in an earlier article; the principle upon which that antenna was based can be applied to dipoles as well.⁵ In this case, the trap is placed at the base of the antenna and its parameters are selected to produce the correct inductive reactance for resonance at the lower frequency f1. At f2 the antenna is slightly longer than a quarter wavelength, and the trap provides the necessary *capacitive* reactance for resonance to be achieved.

To lower the resonant frequency of a fixed-length dipole, inductance must be added. Conversely, capacitance must be added to raise its frequency. A parallel RLC circuit can provide the required reactances at f1 and f2. (A series RLC circuit, which has à capacitive reactance at low frequencies and inductive reactance at high frequencies, cannot be used in this application.)

There's wide variation in the positioning of the traps, which affects the properties of the antenna (directivity, bandwidth, efficiency, and trap resonant frequencies). Mathematically speaking, the design of a trapped antenna is over-determined since there are *four* parameters to be adjusted in order to meet the *two* resonance conditions at f1 and f2: total length; trap position; trap resonant frequency, f0 (when removed from the antenna) and the value of the capacitance, C.

Without further information, it's impossible to say how these parameters are to be selected in order to obtain the best performance. The classic design isn't optimum because the outer portions of the dipole have little current at the upper frequency, f2. A design that causes a significant current to flow in these outer portions can improve directivity.

In addition, minimum loss reactances should be used. The capacitive loading required by a single-band antenna longer than a half wavelength can usually be supplied with negligible loss. However, inductive loading required for a single-band short dipole usually adds

By Yardley Beers, WØJF, 740 Willowbrook Road, Boulder, Colorado 80302

some losses. With a two-band trap antenna, the losses are usually greater at both frequencies than if singleband loading is used. Because losses tend to be greater if the trap resonance is near one of the operating frequencies, I'll discuss a design in which f0 is as far removed from the operating frequencies, f1 and f2, as possible, and in which the traps have equal impedances at these two frequencies. For this to occur, the trap resonant frequency, f0, must be equal to the geometrical average of f1 and f2 — that is, equal to the square root of their product. The reactances at the two design frequencies are equal in magnitude but different in sign, and the resistances are equal. I call this approach the "symmetrical" design.

a dual-band antenna

To illustrate this principle, two separate two-band trap dipoles were built: the first for 18.1 and 24.9 MHz. and the second for the 14- and 21-MHz bands. Actually, I have built two of the former; the first had minimum SWRs of 1.5 in the 18.1-MHz band and 1.4 in the 24.9-MHz band. After I had dismantled it, I improved my computer programs for designing these antennas and built the 14/21-MHz antenna, with which I obtained minimum SWRs of 1.1 on both bands. I reworked the calculations for the 18.1/24.9-MHz antenna and got slightly different values. I decided that although the original antenna was still useful, I hadn't trimmed it to best advantage. I built the second antenna with significantly different dimensions and, as shown in fig. 1, it has minimum SWR of 1.1 on both bands.

18.1/24.9-MHz dual-band antenna

Both antennas were developed for design frequencies of 18.118 and 24.94 MHz with a trap design frequency of 21.257 MHz, using nominal trap capacitances of 50 pF. After the second version of the dual-bander was built, the trap capacitances were measured at 51.6 pF. The trap resonances measured, on the average, 21.27 MHz. The inductors consisted of 13 turns of No. 18 plastic-coated wire wound on 1/2-inch diameter plastic rod. Since I operate at low power (about 100 watts) I was able to use No. 18 wire. but I advise those readers who intend to operate at higher power to build inductors with heavier wire. I didn't measure the Qs of the coils, but I assume that 200 is a reasonable value. (Resonance is independent of the Q.) Using these values and eqns. 8, 10, and 11 (see appendix 1), I found the magnitude of the reactances and the resistances to be 449 and 7.0 ohms, respectively.

The total antenna length is 20.0 feet. The traps are 13.8 feet apart, symmetrically placed about the center feedpoint. The earlier antenna, with similar traps, had dimensions of 20.7 feet (length) and 15.3 feet (trap

separation). For comparison, the (unloaded) lengths of half-wave dipoles for these design frequencies, as given by **eqn. 6** (see **appendix 1**), are, respectively, 25.9 feet and 18.8 feet. The wire is No. 14 gauge. Standing wave measurements relative to a 50-ohm transmission line, with the antenna 20 feet above ground, are shown in **fig. 1**. The measurements take line losses into account.

Before building the second antenna, I followed the mathematical procedure discussed in **appendix 2**, which gave the following results: for S1 (the distance from the center feedpoint to one trap), 6.90 feet; for S2 (the distance from a trap to the end), 3.88 feet. With these dimensions, the SWR pattern at 24.94 MHz wasn't very different from that shown in **fig. 1**, but the f1 SWR minimum of 1.2 was at 17.4 MHz, about 5 percent too low in frequency. I tried trimming both S1 and S2. Finally I retained the original value of S1, but I reduced S2 by 0.8 feet (9.5 inches) for a final value of 3.08 feet. These dimensions apply to **fig. 1**.

Moxon gives a method for estimating the efficiency of trapped antennas.⁶ It's necessary to measure or assume values for the radiation resistance. The minimum SWR at both frequencies is 1.1, which implies that the total resistance at the drivepoint is between the limits 50/1.1 = 45.5 ohms and $50 \times 1.1 = 55$ ohms. Because the radiation resistance is larger for dipoles greater than one half wavelength and less for those less than one half wavelength, I assumed the lower (resistance) value for f1 and the upper one for f2.

The power radiated is the current at the center multiplied by the square of the current at the center. The power lost in the traps is their resistance multiplied by the square of the current at the traps, which is smaller than at the center. The total resistances of the traps is actually 14 ohms, but a calculation shows that the losses are as though the trap resistances were at the center and had the values of 5.8 and 2.0 ohms, respectively, at f₁ and f₂. After subtracting off these transformed loss resistances, 1 obtain estimates for the radiation resistances at the two frequencies as 45 - 5.8 = 39.2 and 55 - 2.0 = 53 ohms, respectively. The efficiencies are then respectively 39.2/45 = 87% and 53/55 = 96%.

However, since the radiation resistance of a halfwave dipole is about 72 ohms, one would expect the radiation resistances to be slightly higher than the estimates given above; consequently, working with the same trap resistances, efficiency should actually be higher.

15/20-meter dual-band antenna

The design frequencies for this antenna are, respectively, f1 = 14.15, f2 = 21.2, and f0 = 17.32 MHz. The trap capacitors have measured values of 52 pF, on the average. The inductors are seven and a half

NEW COMPUTER BOOKS

YOUR COMMODORE 64: A GUIDE TO THE C-64 COMPUTER YOUR COMMODORE 128: A GUIDE TO THE

C-128 COMPUTER

These books cover in great detail the best selling Com-modore C-64 and C-128 home computers. You get a complete introduction to the operating sytems used, BAS-IC tutorials, graphics, sound and much more. Also discussed are hardware and peripheral considerations. The 128 book covers C-64 emulation, extended memory, CP/M mode, mouse, ram disk, printers and modems. Excellent source books for beginners and experts alike. © 1985 1st Edition

005-C64 464 pages	Softbound \$14.95
0S-C128 480 pages	Softbound \$14.95
Ruy'em Both Sner	ial Ren \$29.90

OS-C Save \$4.95

MS-DOS USER'S GUIDE

by Chris DeVoney

MS-DOS computer users will find this handbook to be essential addition to their computer library. Includes a full explanation of MS-DOS commands in clear, con-cise language and examples of command syntax. Hints on command usage and explanations of the hierarchial directory and I/O redirection will enable you to get maximum benefit from your computer investment. For novice and expert users. © 1987 2nd Edition 330 pages. Softbound \$21.95 **COUE-061**

PC SECRETS: TIPS FOR POWER PERFORMANCE

by James Kelly

Here's one of those unheralded gems we stumbled upon recently. This nifty book is jam-packed with ideas and suggestions on how to get more out of your PC-DOS or MS-DOS computer. Not a tutorial; more for the intermediate user who is looking to get more speed and efficien-(c) Improve your keyboard, enhance your display, organize your files, and manage your printer better than ever before. You'll be amazed at what this book can add to your PC. Also covers Lotus 1-2-3 and Wordstar. (©) 1985 1st Edition 224 pages IOS-PCS

Softbound \$16.95

\$24.95

APPLE II USER'S GUIDE, Apple Plus and II series

by Poole, McNuff and Cook

All time Apple II best seller! Now available in updated third edition. Learn from the experts how to get the most from your Apple home computer and peripherals. You also get a complete explanation on how to use DOS 3.3 and Pro-DOS. Easy-to-use tutorial explanation of BASIC programming will teach you how to use all the sound and graphics capabilities as well as the Apple IIe high resolution graphics. This book is worth it's weight in gold! 1985 1st Edition 512 pages IOS-UG

Softbound \$18.95

We're really proud of the next two books! Doug was Jim Fisk's right hand man during the early seventiles. His first computer book, The introduc-tion to TURBO Pascal, quickly went best seller. The TURBO Library is an invaluable addition to TURDO user's theories. TURBO user's libraries.

INTRODUCTION TO TURBO PASCAL by Doug Stivison WA1KWJ (ex Ham Radio assistant editor)

Thousands have learned Pascal programming with this popular best seller. As a tutorial this book enhances the unique aspects of Turbo Pascal by concentrating on the extended applications capabilities offered. Includes graph ics, look-up tables, word processor to typesetting equip-ment conversion tables, TTS to ASCII conversion and fast sort/search routines. © 1985 1st Edition 268 pages Softbound \$14.95 SY-269

TURBO PASCAL LIBRARY by Doug Stivison WA1KWJ

Perfect compliment to the Turbo Pascal Introduction book listed above. Stivison shares his extensive collection of proven programs and will save experienced programmers time and illustrate to beginners good programming techniques and Turbo versions of standard algorithims. Includes games, systems utilities, and routines for business and engineering applications. © 1986 1st Edition 350 pages

JŠY-330 Softbound \$14.95 Please Enclose \$350 to cover shipping and handling BOOKSTORE adio Greenville, NH 03048




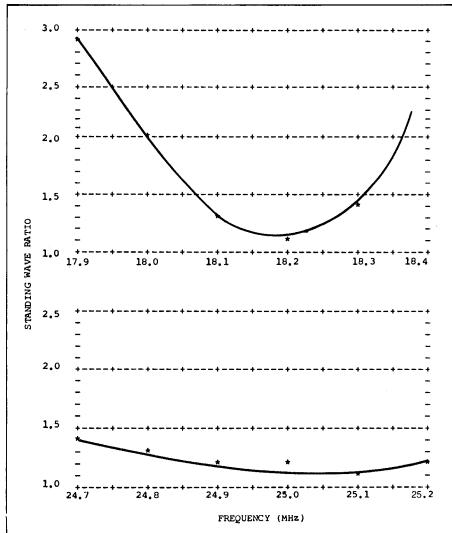


fig. 1. SWR vs. frequency for trapped dipole for use in 18.068-18.168 MHz and 24.890 -24.990 MHz bands. The antenna is 20 feet, 10 inches long and has traps placed 15 feet, 2 inches apart, equidistant from the center feedpoint. The traps use 50-pF capacitors and are self-resonant at 21.2 MHz.

LIN	EAR TRANSVERTERS		WER AMPLIFIERS	
		BUILT-IN PREAM	PLIFIERS	
MMT 50/28S MMT 50/144S MMT 144/28 MMT 144/28R MMT 220/28S MMT 220/28S MMT 1296/144G MMX 1268/144	50 MHz 20 Warts \$359 50 MHz 20 Warts \$359 144 MHz 10 Warts \$198 144 MHz GASFET 25 Warts 220 MHz 15 Warts \$242 432/435 MHz 10 Warts \$299 1296 MHz GASFET 2 Warts 0SCAR MODE-L 2 WARTS	MML 144/30LS MML 144/100LS MML 144/200S MML 432/30L MML 432/100 MML 432/50 MML 1296/15	30 WATT - 1,3W INPUT 100 WATT - 1,3W INPUT 200 WATT GAÅSFET PREAMP 30 WATT - 1,3W INPUT 100 WATT ATV/SSB/FM/RPT 50 WATT - 10 INPUT 15 WATT - 1,3W INPUT	\$13 \$24 \$45 \$24 \$24 \$45 \$21 \$21
	CONVERTERS	PREA	MPLIFIERS GaAsFET	
MMC 50/28 MMC 144/28HP MMC 432/28S	50 MHZ RCV CONVERTER \$ 59 2m GAASFET RCV CONVERTER \$ 79 432/435 MHZ RCV CONVERTER\$ 91	MMG 144V MMG 1296 MMG 1691	144MHZ RF Sw 100 WATTS 1296 MHZ GAASFET 1691 MHZ GAASFET ATV	\$ 7 \$11 \$20
MMK 1296/144 MMC 1691/137.5 PRICES SUBJECT TO VISA/MASTERCARD AG	1691/137.5 WX RCV CONV. \$239 CHANGE WITHOUT ADVANCE NOTICE.	MMC 435/600 MTV 435	432 TO 600MHZ BLOCK CONV 20 Watt Video Xmtr-70cm	\$ 6 \$31

и 135

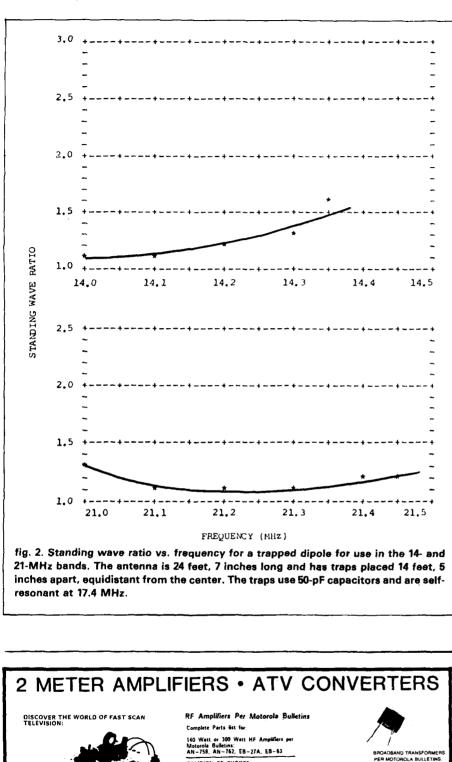



Qit∕

SPECIALIZED

CAMBION RF CHOKES BL. Bal. Mixer. DBL. Bal. Mixe

FERROXCUBE DEVICE

8 49.95 Ki

AMATEUR TELEVISION CONVERTERS

n. Kit ar Assembled/Teste

VISA

ATV-3 420-450 MHz GaAs-Fet ATV-4 902-928 MHz GaAs-Fet

Add \$ 2.00 For Shipping and Handling

POWER SPLITTER/COMBINER 2-30 MHz 600 Wates (2 Part of 4 Part)

Communication Concepts Inc. 121 Brown Street * Dayton,Ohio 45402 * (513) 220-9677

8 5 30

KEMET CHIP CAPACITORS METALCLAD MICA CAPACITORS SEMICONDUCTORS RF POWER TRANSISTORS For detailed information, please call or write for our free catalog 136

We Also Stock Hard-To-Find Parts:

turns of No. 18 plastic-coated wire on 1-inch plastic pill bottles. The wire spacing was varied to adjust the resonant frequencies of the traps. During coil construction, the half turn was left slack for fine tuning. The average measured resonant frequency was 17.41 MHz. The wire used in the antenna is No. 12 gauge.

Appendix 2 provides a detailed discussion of calculations which suggested the initial dimensions S1 = 7.69 feet and S2 = 5.41 feet. After I trimmed them experimentally to S1 = 7.36 feet and S2 = 5.24 feet, I obtained the standing wave pattern shown in **fig. 2**.

As the length of a loaded dipole, measured in wavelengths, increases, the bandwidth increases. Although a wider bandwidth is expected at f2 than at f1, I can't explan why bandwidths I've observed at f2 are very much wider than those at f1. These different bandwidths showed considerable sensitivity to changes in length while trimming; in each of the three cases I've dealt with, the standing wave pattern at f2 has changed hardly at all when I changed the dimensions, but a change of only a few inches made a significant change in the f1 resonance frequency. It's likely that the f1 resonance is very susceptible to changes in antenna location.

theory of the symmetrical design

The selection of a trap antenna's dimensions can be made almost entirely by experiment. The only mathematics one needs to build a two-band antenna using the symmetrical design is to calculate f0 by taking the square root of the product of f1 and f2. After installing the traps and adjusting the antenna length and trap location, a working antenna is produced. The mathematical details can usually save the designer some time by providing at least a "starting point."

In designing a trap antenna, the following conditions must be satisfied: it must resonate at f1; it must resonate at f2; the trap resonant frequency must be the geometric average of f1 and f2. The trap resistances at f1 and f2 are equal, and the reactances are equal in magnitude but opposite in sign. Arbitrarily, I chose 50 pF as a convenient value for the trap capacitances. (The effect of using other values is also considered.) The required value of the trap inductances, L, can then be determined by **eqn. 7**.

Most of the necessary formulas are listed in **appendix 1**, with detailed examples provided in **appendix 2**. The condition for resonance is that the total reactance as referred to any point on the antenna is zero. It is axiomatic that if the total reactance at *any* one point is zero, then it is zero at all other points. For convenience, I chose the trap location as a reference point and considered only half the dipole at a time.

The antenna and the ground can be thought of as forming a transmission line. Although the center is connected to the feedline, I assume that its input impedance, as viewed at the location of the trap, is the same (positive) reactance, X1, as it would be if the center were connected to ground. Calculate this with **eqn. 15**. Similarly, I consider the part between the trap and the end as a section of open-circuited transmission. Its impedance is given by the (negative) reactance, X2, in **eqn. 17**.

If S1, the distance from the center to the trap, and if S2, the distance from the trap to the open end, are a quarter wavelength long, then X1 + X2 = 0, *independent of the value of S1*. This configuration is well known as a resonator.

For resonance using arbitrary lengths of S1 and S2, it's necessary to introduce a reactance X such that:

$$X + XI + X2 = 0$$
 (1)

Various values of S1 and S2 are tried until the equation is satisfied at both f1 and f2. (See **appendix 2**.)

As a simplification, a characteristic impedance of 575 ohms was calculated for a transmission line consisting of a horizontal 12-gauge wire parallel to and 20 feet above a perfectly conducting groundplane (**eqn. 14**). Though good for a transmission line, this formula neglects the effect of radiation, and, of course, radiation is the primary purpose of the antenna.

The calculation of characteristic impedances of radiating antennas is more complicated.⁷

parallel RLC circuit properties

A complete understanding of the design of trap antennas requires a knowledge of parallel RLC circuits. Graphs of impedance, series resistance, and series reactance are shown as a function of frequency f in **fig. 3**. These normalized curves require that quantities plotted on the vertical scale be multiplied by the value of R, and the frequency shift measured from the resonant frequency be given in units of D, where


$$D = f0/2Q \tag{2}$$

Losses in the inductor and capacitor are represented by a resistance, R, where:

$$R = \frac{500,000Q}{\pi C f 0} ohms$$
(3)

and *C* is the capacitance in picofarads, and *f0* is the resonant frequency in MHz.

To apply these ideas to the traps in the 18.1/24.9-MHz antenna, fO = 21.257 MHz, C = 51.6 pF, R = 29,002 ohms, and D = 0.053 MHz (53 kHz). The reactance has small positive values at low frequencies and increases to a maximum of 0.5 R = 14,501 ohms at a normalized value of -1 (21.204 MHz), after which it decreases to zero at resonance. Then it decreases to a negative maximum -0.5 R = -14,001 ohms, at +1 (21.310 MHz) and approaches zero at very large frequencies.

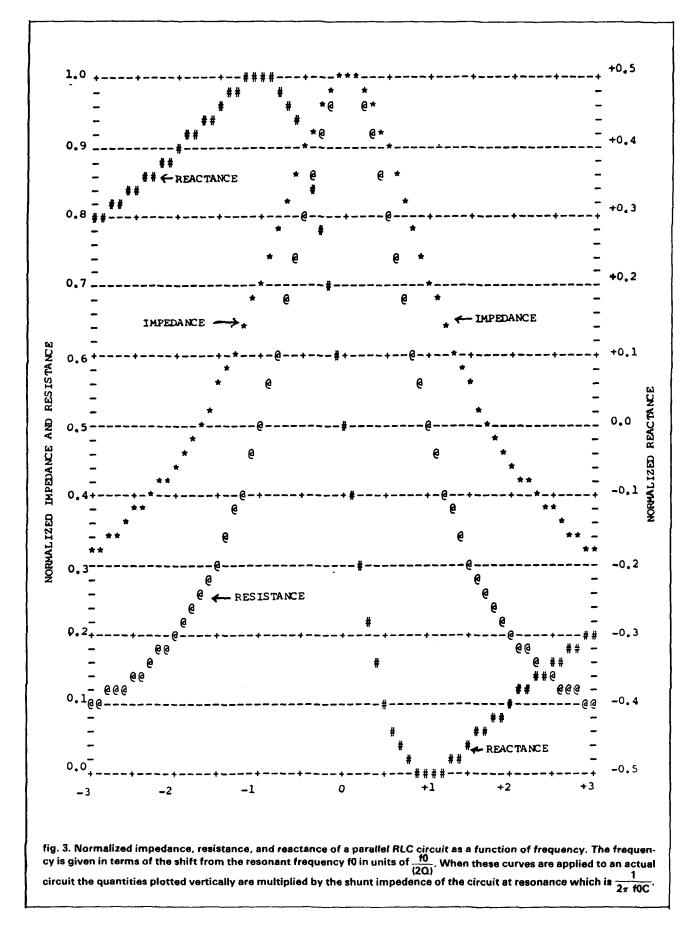

here is the next generation Repeater

MARK 4CR

The only repeaters and controllers with REAL SPEECH!

No other repeaters or controllers match Mark 4 in capability and features. That's why Mark 4 is the performance leader at amateur and commercial repeater sites around the world. Only Mark 4 gives you Message Mastertm real speech • voice readout of received signal strength, deviation, and frequency error • 4channel receiver voting • clock time announcements and function control • 7helical filter receiver • extensive phone patch functions. Unlike others, Mark 4 even includes power supply and a handsome cabinet.

Call or write for specifications on the repeater, controller, and receiver winners.


Create messages just by talking. Speak any phrases or words in any languages or dialect and *your own voice* is stored instantly in solid-state memory. Perfect for emergency warnings, club news bulletins, and DX alerts. Create unique ID and tail messages, and the ultimate in a real speech user mailbox — only with a Mark 4.





MICRO CONTROL SPECIALTIES

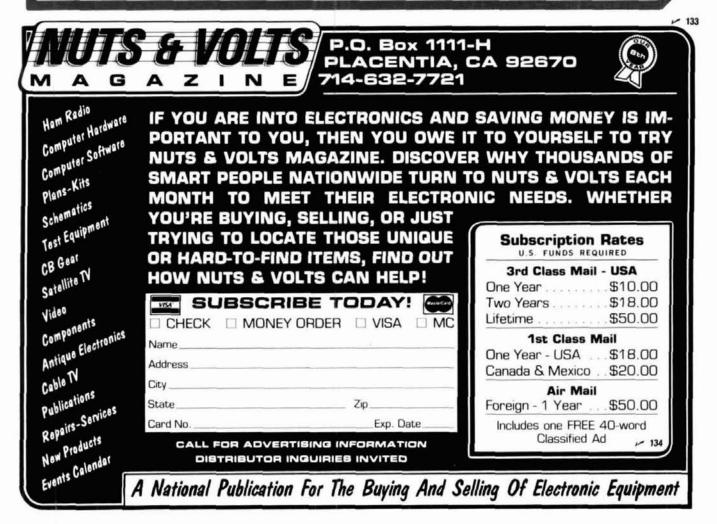Division of Kendecom Inc. 23 Elm Park, Groveland, MA 01834 (617) 372-3442



The design frequencies, f1 and f2, correspond respectively to -70.6 and +58.4, and lie very far off the graph in fig. 3. The values of the impedances, resistances, and reactances cannot be obtained from the graph and must be calculated by formulas such as those shown in **appendix 1**. The reactances, as stated previously, are ± 449 ohms and the resistances are 7.0 ohms. Consequently, the circuit can be considered as a low-loss reactance.

Since the reactance goes through zero at resonance, there are two other frequencies — very close (about 10 kHz) — at which the desired reactance of \pm 449 ohms can be obtained. There the resistance is very close to its maximum value. Such a reactance would hardly be considered low-loss! This is the situation encountered when such a circuit is used as a trap at f2 in the classical design. In such a situation the RLC circuit becomes a "trap" in another sense of the word: as an absorber of power.

The curves shown in fig. 3 assume that Q is at least 10 and preferably much larger, as is likely to be the case in practice. The errors resulting from this assumption are then negligible. This assumption simplifies the math. When Q is small, it is necessary to draw individual curves. Equations 8, 9, 10, and 11 don't have this limitation.

Another assumption is that the losses in the circuit are represented by a resistor, R, whose value is given by **eqn. 3**, and that its value is independent of frequency. Strictly speaking, this assumption is unrealistic. Most of the losses are in the inductor, and they depend upon frequency in a complicated way because of skin effect and distributed capacitance.

For physical reasons, air (dielectric) capacitors often aren't practical to use in antenna traps - but they are low-loss. The losses in solid dielectric capacitors are generally lower than those in the *inductors*, but they (the losses) mustn't be overlooked. While an air-core inductor has the shape to dissipate heat, a solid-state capacitor does not; a small amount of power dissipated in it causes its temperature to rise and its capacitance to change. If the effect is large, the antenna is detuned when the power level is raised. Thus, a solidstate capacitor has a current limitation as well as a voltage limitation. Usually one that has a high voltage rating can also pass a lot of current, but this isn't always true. Capacitors with thin pigtails, even with high voltage ratings, must be avoided. Sometimes it's necessary to use more than one capacitor in series or parallel to get sufficient current carrying capability.

conclusion

The main purpose of this article is to review the principles of design of trapped antennas and to show that there are alternative designs that are superior to the classic one. I've illustrated the principles by showing the design of practical antennas for the 18.1- and 24.9-MHz bands, and for the 14- and 21-MHz bands.

A central point of the discussion is that the operating and trap frequencies should not coincide. Equation 12 shows that with far-off resonance the series resistance decreases with the square of the difference between the operating and trap resonant frequencies. A further argument for keeping the trap resonant frequency remote from the operating frequency is the fact that the same RLC circuits used in the 18.1/24.9-MHz antenna could be used as traps in a 14/21-MHz dual-band antenna of classic design. The total trap resistance at the new f2 (21 MHz) is about 58,000 ohms. In considering such an antenna, Moxon⁶ estimates that the radiation resistance, when transformed to the trap location, is about 32,000 ohms. Therefore, the efficiency is about (32/60) = 53 percent, whereas the efficiency with the symmetrical design at $f^2 = 24.94$ MHz is 96 percent. Furthermore, with the symmetrical design there is significant current in the outer portions, and the directivity is greater. Therefore, at the upper frequency, f2, there is a significant advantage of the symmetrical over the classic design. With the classic design, the lower frequency, f1, is further from resonance than with the symmetrical design, and therefore the loss resistance is lower and the efficiency is higher. With the symmetrical design, it is already very good - 87 percent - so this advantage is not important.

I haven't tried to optimize the value of the trap capacitances. **Equation 13** shows that the resistances of the traps' far-off resonance are inversely proportional to the product of the capacitance and the Q of the traps. With the present values of 50 pF and a Q of 200, they're about the largest acceptable. If the capacitances were lowered to 25 pF, the resistances would be double and would cause a significant reduction in efficiency at both operating frequencies. If they were made 100 pF, there would be an insignificant improvement in the efficiency.

The principle of symmetrical design should be applicable to a 14/21/28-MHz triband dipole. The traps should be resonant in the vicinity of 17 MHz and 24 MHz, respectively. Efficiency and directivity would be greater. However, there would be a problem in extending the design to many bands; the radiation resistance would be different on the lowest and highest frequency bands, and an elaborate impedance matching network would be required to get a good match to the transmission line for all bands.

This article has dealt only with a single dipole. This approach can be applied to multi-element antennas with both driven and parasitic elements.

acknowledgments

I wish to thank Les Moxon, G6XN, Francis M.

New rigs and old favorites, plus the best essential accessories for the amateur.

CALL FOR ORDERS 1 (800) 231-3057 1-713-520-7300 OR 1-713-520-0550 TEXAS ORDERS CALL COLLECT ALL ITEMS ARE GUARANTEED OR SALES PRICE REFUNDED

EQUIPMENT	
Manufactor IC 704	Trades wanted
Kenwood TH205AT Kenwood TS 440S/AT	Trade in your old HT
Kenwood TS 440S/AT	Call for trade
Icom R7000 25-2000 MHz	949.00
Icom IC735	849 00
KDK FM 240, 220 MHz, 25w KDK FM 240 NT Mirage Amps Tokyo Hy-Power HL 1K AMP, no	
KDK FM 240 NT	2/9.00
Mirage Amps	15% UFF
New Kenwood TM-221A, 45W, m	40A250B 699.00
VJ Amplifier, VHF, built in England	d 1 in-100 out
3 100, 5-100	
10 m ² 100 out	229 00
10 in 100 out 25 in 160 out	
All models include preamp Lunar 2M4-40P	
Lunar 2M4-40P	109.00
ACCESSORIES	
B&W VIEWSTAR ANTENNA TUR	
Heil HC4/HC5	Stock
Heil BM10 Boom Mike headset.	
Tri-H 5000A Remote Phone.	
Daiwa NS660A 30/300/3000 wat	135.00
Alinco ELH 230D- Excellent buy. Nye MB5-A (for the big boys!)	529.00
Shure 444D	54.95
Ameco PT-3	Soon
Ameco PT-3 New Tokyo HC 200A	115.00
Astatic SilverEagle & Base	66.00
Ten-Tec Mobile Switch 3001	17.00
ANTENNAS	
Isopole 144 MHz	44.95
Isopole 440 MHz	59.95
Cushcraft 124-WB (146 MHz)	33.00
Butternut HF6V, 80-10 vertical	
HF2V, 80 & 40 vertical	
HF4B	189.00
Hustler G7-144	119.95
Hustler 6BTV KLM HF World Class Series Anter	139.00
KLM HF World Class Series Anter	nnas
ALPHA Delta DX-DD	63.00
Coax Seal	2.00/roll
B&W Dipoles	Less 10%
KLM KT-34A W2AU, W2DU	May Available
NEW KLM 1,2-44LBX	129.00
1296 Power Divider	69.00
Create CD-78 + BS 80 75/80 rotal	table dipole 385.00
G5-RV	44 00
OTHER ANTENNAS Diamond D-130 Discone 25-1300	MUa 70.00
Larsen Kulduck	17 00
Larsen 2M 1/2 wave telescope ant	25.00
Avanti AP151 3G on Glass Anten	36.00
Anteco 2M, 5/8, Mag. Mount, Col	mp 25.00
Van Gordon ND-4, 4 band Novice	e dipole 45.00
Valor AB-5 Mobile	79 95
Stoner DA100 D Active Rx Anteni	na 190.00
DC 'Tenna Hitch 3/8-24 Thread Fits 3/4" trailer hitches	
Fits 3/4" trailer hitches	29.95
PARTS	
	ctitier 1.95
1.5 Amp/400V full wave bridge re 2.5A/1000PIV Epoxy diode	29 each or 19.00/100
.0015/10KV or .001/20KV	1.95 each
3N201	95
4 inch ferrite rod	1.95
365pF cap Sanyo AAA,AA Nicads w/tabs	1.95
Sanyo AAA, AA Nicads w/tabs	
2,4,5,6,8 pin mic plugs	3.00
1/8, 1/4, watt carbon resistors Meter 0-3000 VDC 0-1 Amp DC 2	11/2" Square
with shunt	19.95
Drake—Collins mike plug Thousands of panel meters MICA Cap_0004/3KV	2.00
Thousands of panel meters	3.95 up CALL
MICA Cap 0004/3KV	5.00 others CALL
Diodes 3A/1000 PIV	11604 2.40
Diodes 3A/1000 PIV Duracell 9 Volt Battery - 2 Pak MN DC Fan 3½" Sq × 1"	0.05
DC Fan 3½" Sq. x 1" CINCH 12 pin conn fitz (Drake etc) female 3.00
Aerovox 1000 pf/500 V feedthrou	inh cups 195
Mallory 6 volt, 4 prong Vibrator Pl	

USED EQUIPMENT

All equipment, used, clean, with 90 day warranty and 30 day trial. Six months full trade against new equipment. Sale price refunded if not satisfied. Call for latest used gear list

(800) 231-3057

AMPHENOL

831SP-PL259 Silverplate	1.25
UG176 reducer RG8X	
831J Double Female UHF	
82-61 N Male	
82-97 N Female Bulkhead	3.00
82-63 Inline Female N	4 00
82-98 N elbow	9.00
82-202-1006 N Male for 9913.	4.50
31-212 BNC-RG59	1.50
31-216 UG201 A/U N Male-BNC Female	
31-2 BNC-RG58	1.50
34025 N Male, RG58	3.00
34125 N Female UHF male	9.00
3128 BNC Female-PL259	
4400 N Male-S0 239	7.00

ICOM



ICOM 28H/TTM	399.00
TUBES	
Collins & Drake Replacement tubes	Stock
GE 6146B	12.95
3-500Z	109.95
GE Industrial Tubes	Call
GE 12BY7A	7.00
GE 6JS6C	12.95
GE 8950	16.00
12JB6 Sylvania	6.00
Hard to find Tubes 50-90% off list	
6JB6A	9.95
6JE6C/6LQ6	9.95
572B	.69.00
6KD6	
PACKET POWER	
AEA PK-232 with new WX FAX	299.00
Kantronics KPC II	149.00
MFJ 1270	119.00
MFJ 1274	149.00
New Kantronics KAM	
SERVICES	
Complete KWM 2 Retube	179.00
Flat fee Collins rebuild	
TOWER ACCESSORIES	

1/4" E H S Guy cable Rohn US 1000 ft.	250.00
3/16" E H S cable. Rohn US, 1000 ft	210.00
1/4" Guy Cable. 6100 #7 x 7 strand, import	18c/ft
3/16" Guy Cable, 3700 #7 x 7 strand, import	15c/ft
3/8" x 6 E&J Turnbuckle	7.95
3/16" Wire Rope Clips	.40
1/4" wire clips	
1/4 Thimbles	45
Porcelain 500D Guy Insulator (3/16)	1.99
Porcelain 502 Guy Insulators (1/4)	3 39

POLICIES

todav

Call

products in stock

Belden

Bird and

Minimum order \$10.00. Mastercard, VISA, or C.O.D. All prices FOB Houston, except as noted. Prices subject to change without notice. Items subject to prior sale. Call anytime to check the status of your order. Texas residents add sales tax. All items full factory warranty plus Madison warranty

DON'S CORNER

New! "World Radio Report" for SWL & Hams. Full of info. \$2.50/month. Try 30 meters? N5JJ Houston has 101 countries. Have more? Contact Don at Madison - 130





× 129





Dukat, K6NL, and Oswald G. Villard, Jr., W6QYT, for their valuable suggestions.

appendix 1

basic equations

The formulas have been used for calculations discussed in the text. The wavelength

....

$$\lambda = 299.8/f \text{ in meters} \tag{4}$$

$$= 983.6/f$$
 in feet, with the frequency f in MHz. (5)

The length of a half-wave dipole is

$$G = 468/f \text{ in feet.}$$
 (6)

Equation 6 gives a length which is 95 percent of a half wavelength as given by **eqn. 5** because of corrections for end effects. This simplification valid for hf wire antennas depends on the ratio of conductor diameter to wavelength. At VHF, where the ratio is usually smaller, the correction is larger.

The inductance L (in μ H) required to resonate with a capacitor C (in pF) at a frequency f0 (in MHz) is

$$L = \frac{l}{4\pi^2 C (f_0)^2}$$
(7)

It is convenient to define a new quantity, t

$$t = Q \cdot \frac{f^2 - f_0^2}{f \cdot f_0}$$
(8)

where f0 is the resonant frequency of the RLC circuit and f is any arbitrary frequency. The impedance is given by

$$Z = \frac{R}{\sqrt{I + t^2}} \tag{9}$$

The series resistance is given by

$$R_s = \frac{R}{l+t^2} \tag{10}$$

and the reactance is given by

$$X_s = \frac{R t}{l + t^2} \tag{11}$$

To understand the behavior of traps far from resonance, it is desirable to derive approximate expressions for the resistance and reactance.

$$R_s = \frac{f_0}{8\pi \ CQ \ (f - f_0)^2}$$
(12)

The resistance is inversely proportional to the square of the frequency shift.

The reactance far-off resonance is given approximately by

$$X_{s} = \frac{1}{4\pi C (f_{0} - f)}$$
(13)

Because reactance far from resonance is independent of Q, it isn't necessary to have values of the Qs of the traps to make calculations involving resonance conditions.

A transmission line consisting of a wire of diameter d parallel to and at a distance H from a conducting plane has a characteristic impedance of

$$Z_0 = 138 \ LOG_{10} \ (4H/d) \ ohms$$
 (14)

H and d can be in any similar units.

A section of lossless transmission line of length S1 short-circuited at the far end has an input reactance of

$$X_I = Z_0 TANA \tag{15}$$

where

$$A = \frac{360 \cdot SI}{\lambda} \tag{16}$$

A is the length S1 expressed as an angle in degrees.

A section of transmission line of length S2 open-circuited at the far end has an input reactance of

$$X_2 = \frac{-Z_0}{TANB}$$
(17)

$$B = \frac{360 \cdot S2}{\lambda} \tag{18}$$

is an angle corresponding to the length S2.

Equation 1 gives the condition for resonance at a single frequency. It is necessary to derive from it an equation giving the condition for resonance at the two frequencies f1 and f2. Note from eqns. **16** and **18** that angles A and B are inversely proportional to wavelength. Therefore they are, for fixed lengths S1 and S2, proportional to the frequency. Hence, if we now use A and B to denote the angles at the upper frequency f2, at f1 they are reduced by the factor f1/f2. Since the design is based on the assumption that the trap reactances at these two frequencies are equal in magnitude but opposite in sign, it follows from eqn. **1** that:


$$-TAN \quad \frac{AfI}{f2} + \frac{I}{TAN \quad \frac{BfI}{f2}} =$$
(19)
$$TANA - \frac{I}{TANB}$$

The characteristic impedance Z_0 has cancelled out.

This equation cannot be solved exactly. It has to be solved

Trial	Angle A (Degrees)	Angle B (Degrees)	Residual U	S1 (feet)	S2 (feet)	Reactance (ohms)
2		33	- 0.922	_		
3		37	- 0.412	-		_
4		41	+ 0.0072	_	-	
5		40.8	- 0.012	—	_	
7		40.9	- 0.002	8.38	5.27	569
10	60	47	-0.00014	7.73	6.06	459
16	60.3	46.65	+ 0.00035	7.77	6.01	465
23	59.7	47.35	- 0.00054	7.69	6.10	454



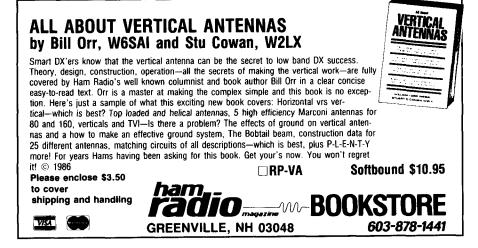





numerically by trial and error. For this purpose it is convenient to define a quantity U_{r} called the residual, as follows:

$$U = TAN \frac{AfI}{f^2} +$$

$$TAN A - \frac{I}{TAN \frac{BfI}{f^2}} - \frac{I}{TAN B}$$
(20)

If the left side of eqn. 19 is transposed to the right, the result is identical to the right side of eqn. 20, but on the left is U instead of 0. It is solved by trying values of A and B, which ideally make U equal to zero. In practice it is impossible to obtain zero exactly. The practical method is to choose a value of A and then find two values of B that are close together, one of which gives a small positive value to U and the other of which gives a small negative value to it. Then, one or the other, or some intermediate value can be taken as the desired value of B. This method is illustrated below.

appendix 2

designing a 14/21-MHz antenna

First select the design operating frequencies. In this example f1 = 14.15 MHz and f2 = 21.2 MHz. Next calculate the trap resonance frequency f0 = 17.32 MHz by taking the square root of the product of f1 and f2. As a starting point, assume a value of trap capacitance of 50 pF. **Equation 7** can then be used to calculate the inductance needed for resonance, 1.69 μ H. Assuming a *Q* of 200, **eqns. 8**, **10**, and **11** can then be used to calculate the reactance and resistance at the design operating frequencies. These turned out to be \pm 451 and 5.55 ohms, respectively.

By repetitively substituting best length "guesstimates" into eqn. 20 the final correct values for resonance are found. (See table 1.) The first guess was for an angular length, A, of 65 degrees and Bof 35 degrees, which gave a large residual U of -0.654. Then, using the fixed value A = 65 degrees, I used B = 33 degrees as a second guess to obtain U = -0.922, which of course, is still further from zero. Therefore, it was obvious that it was necessary to increase B rather than to decrease it. B was gradually increased until U had the value +0.0072, which I considered reasonably close to zero. Next, eqns. 5, 16 and 18 are used to determine distances S1 and S2 in feet and reactance magnitude. In the reactance calculation I assumed a value of 575 ohms for the characteristic impedance. The first value determined for reactance was 569 ohms which is significantly different from the trap reactance 451 ohms. Therefore it was necessary to repeat the process using other values of A.

For the other values of A in **table 1** I have given only the results for the final trial values of B. A reactance of 454 ohms in the last line was considered close enough to the calculated trap reactance of 451 ohms to start building the antenna.

Nevertheless S2 still had to be corrected for end effects. Half-wave wire dipoles, as suggested by **eqn. 4**, have physical lengths of 95 percent of the free space half wavelength. I assumed that a similar correction must be made to a trap antenna. In principle, the correction is slightly different at each of the operating frequencies. As a simplifying approximation, I assumed that it is the same as it would be for a half-wave dipole at f0 = 17.32 MHz, which I found to be 0.69 feet. Therefore, I reduced the computed value of S2 from 6.10 feet to 5.41 feet.

The entire calculation, starting with the calculation of *f0* and ending with the end correction, took less than 20 minutes with the use of the programs I had written for my Commodore 64 computer.* These calculations can also be performed with any hand calculator that features trigonometric functions.

The traps were then built and measured; average resonant frequency was 17.2 MHz. Using the dimensions S1 = 7.69 feet and S2 = 5.41 feet, a minimum SWR of 1.1 occurred at 13.75 MHz and 1.2 at 20.7 MHz. These frequencies are about 3 percent lower than the design ones. This observation suggests that the dimensions

*Copies of these programs are available; send a self-addressed business-sized envelope with two first-class stamps, plus one loose first-class stamp to cover the cost of photocopying. should be reduced about 3 percent, or each S1 and each S2 should be shortened by 2 inches. When I made this change, the SWR was 1.2 at 14.0 MHz and 1.3 at 21.0 MHz, and in both bands it increased with frequency with the implication that the minima were at the low edges or outside the low edges. I then removed 2 more inches from each S1. Then, with the final dimensions S1 = 7.36 feet and S2 = 5.24 feet, I obtained the standing wave pattern shown in fig. 2.

Thus the final dimensions differed from the calculated ones by only a few percent. In view of the uncertainties that are present, the agreement between theory and experiment is as good or better than can be expected. The biggest uncertainty is the value of the characteristic impedance. The end correction is another. Then there are experimental sources of error due to the length of the leads on the traps and due to the wires wound on the insulators. At the same time, the theoretical calculation provided a useful guide which probably reduced the experimental adjustment by hours. Trial and error can be done much more rapidly by computer than by experiment!

references

 Terman² gives the following reference as the original work on trapped antennas: Howard K. Morgan, "A Multifrequency Tuned Antenna System," *Electronics*, August, 1940, page 42. (When I looked in this publication, I failed to find this paper there: I have been unable to locate it elsewhere.)

2. F. E. Terman, Radio Engineers' Handbook, McGraw-Hill Book Co., New York 1943 page 854

 Chester L. Buchanan, W3DZZ, "Duo Band Antenna," Radio and Television News, December, 1950, page 66.

 Chester L. Buchanan, W3DZZ, "The Multimatch Antenna System," QST, March, 1955, page 22.

 Yardley Beers, "Short Antennas for the Lower Frequencies – Part 1," QST, August, 1970, page 26.

 L. A. Moxon, G6XN, HF Antennas for All Locations, Radio Society of Great Britain, London, 1982, page 109.

 Sée, for example, S.A. Schelkunoff and H. T. Friis, Antennas: Theory and Practice, John Wiley and Sons, New York 1952, section 13.4.

ham radio



THE PACKET RADIO HANDBOOK PACKET BADIO

by Jonathan Mayo, KR3T

Packet radio is the fastest growing mode in Amateur operation today. No wonder - it combines the power of today's microcomputer with worldwide digital communications. New-



comers will find this book to be full of helpful tips, tricks and information that will help get them on Packet as guickly as possible. Providing you first with packet basics, this book progresses through the inner workings and operational aspects of packet to a look at future technology still in developmental stages. Also includes: using bulletin boards, traffic handling on packet, modulation methods and networking principles, protocols (both AX.25 and VADCG) and a thorough discussion of the various TNCs and accessories available. ©1987 1st Edition 218 pages.

T-2722

Softbound \$14.95

603-878-1441

THE

DIGITAL NOVICE

Jim Grubbs, K9E

Please enclose \$3.50 shipping & handling

ham_ radio BOOKSTORE **GREENVILLE, NH 03048**

THE DIGITAL NOVICE by Jim Grubbs, K9EI

Now that novices have digital privileges, there are thousands of new Amateurs anxiously awaiting to get on-the-air. Who's going to answer their questions, however? Jim Grubbs'

new book, The Digital Novice, is written with beginner's needs in mind. Each of the popular digital modes is fully covered with a brief history and full description of how it works. Hardware and software are covered in clear, concise terms. The book finishes with a look toward the future. Four appendixes cover Morse, Baudot, AMTOR and ASCII Codes and has a glossary full of commonly used but misunderstood terms. Great for beginners and experts alike. © 1987 1st edition

Softbound \$9.95 JG-DN Please enclose \$3.50 to cover shipping and handling.





Only \$19.95 per year (12 monthly issues)

\$1.00 for sample copy



Scheduled Channels ★Weekly Updated Listings ★Magazine Format ★Complete Movie Listing ★All Sports Specials ★Prime Time Highlights ★Specials Listing and + Programming Updates!

- Only \$45.00 per year (52 weekly issues)
- 2 Years \$79.00 (104 weekly issues)
- \$1.00 for sample copy

Visa® and MasterCard® accepted (subscription orders only). All prices in US funds. Write for foreign rates.

Send this ad along with your order to:

STV®/OnSat®

P.O. Box 2384—Dept. HR • Shelby, NC 28151-2384 SUBSCRIPTION CALLS ONLY TOLL FREE 1-800-438-2020

PRACTICALLY SPEAKING ...) E CAN KAIPU

battery problems: part 2

Last month we discussed NiCd batteries; this month we'll take a look at charging systems for NiCds, as well as lead acid and gel cel batteries.

charging NiCds

There are two basic forms of charger for NiCd batteries: constant-current (CI) and constant-voltage (CV). Regardless of the type, it's important to use a charging current no greater than A-H/10 unless specifically instructed to do so by the battery manufacturer (not the equipment maker, by the way). The A-H/10 rate is one-tenth of the ampere-hour rating. For a 500-mAH AA cell, for example, a 50-mA charging current is used. Similarly, 200 mA should be used for a 2 A-H C cell, and 400 mA for the 4 A-H D cell. (Be careful not to overcharge batteries using other A-H ratings.)

Figure 1 shows the basic circuit for a low-cost constant current charger of simple design. The transformer secondary voltage should be 2.5 or more times the cell or battery voltage. The resistor in series with the rectifier limits the output current under short-circuit conditions to the A-H/10 charging rate.

Figure 2 shows two electronic Cl chargers based on three-terminal IC voltage regulators. The variable circuit shown in fig. 2A is based on the LM-317 (up to 1 ampere) and LM-338 (up to 5 amperes). Both circuits require a filtered dc input voltage several volts higher than the battery or cell potential. The actual value isn't critical as long as it's high enough to turn on the circuit (in general, V_{in}) is greater than (V_B + 3 volts). We can adjust the


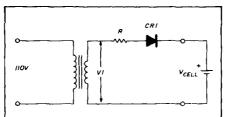


fig. 1. Simple constant-current battery charger.

charge current by setting the value of resistor R. For example, for a 400-mA charger for 4 A-H D cells, we would use a resistor value of 1.2/1 = 1.2/0.4 = 3 ohms. Charging currents down to 10 mA can be accommodated by the circuit shown in **fig. 2A**, so both regular and trickle chargers can be designed.

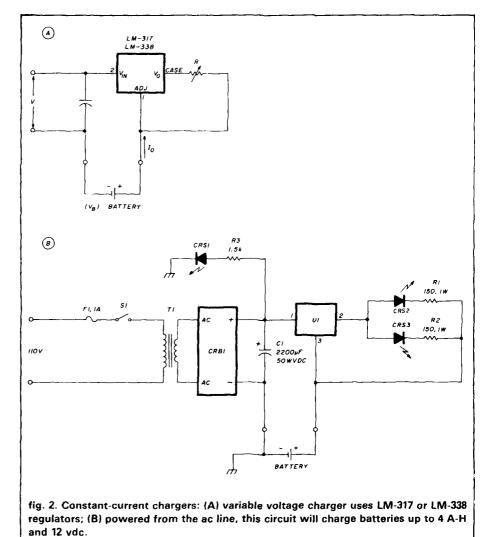The circuit shown in fig. 2B will charge batteries up to 4 A-H with ter-



minal voltages up to 12 Vdc. Similar to the circuit shown in **fig. 2A**, it is based on 5-volt fixed regulators such as the LM-309, LM-340-05, or 7805 devices.

A constant-voltage charger is shown in **fig. 3**. The output voltage of the charger is set by the ratio of R1 and R2, and is determined by the equation:

$$V_o = 1.26 \left(\frac{R2}{Rl} + l \right)$$

A series resistor, R3, is chosen to limit the short-circuit current to a maximum of A-H/10. The required charger output impedance is the resistance equivalent of V_o / I_{MAX}, where V_o is the open-terminal battery voltage and I_{MAX} is the maximum permissible charging current. For a 12-volt, 4 A-H battery, for example, the required impedance is 12/(4/10) = 12/0.4 = 30 ohms. We can solve the equation in the figure for R3 and place that resistance in series with the output of the regulator. The power rating of the resistor must be V_o × I_{MAX}.


using bench power supplies

A bench power supply shouldn't be used to charge NiCd batteries unless it has both a variable output voltage control and a current-limiting control. Set the output voltage to exactly the full terminal voltage of the NiCd battery and adjust the current limiter for a short-circuit current equal to the A-H/10 value. Disconnect the output short from the power supply and connect the supply across the battery.

multiple-cell batteries

A large number of multiple-cell batteries are used in electronic equipment. Most are typically 6, 12, or 24-volt models. In most cases, these batteries are made up of individual AA, C, D, or F cells. I found it possible to take apart these battery packs and replace individual cells to restore the battery to normal operation. Some packs are put together with screws or snaps, while others are glued together.

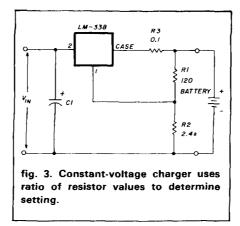My friend who uses a transcutaneous electronic nerve stimulator (TENS) unit for pain control (see last month's column) paid \$90 each for the battery



packs to power his device. One afternoon we took apart one of the packs he'd decided was bad, using a razor knife and lots of care. We found that the pack consisted of three AA cells connected in series. We went to a store that sold commercial solder-tab AA NiCd cells and returned with \$18 worth of cells to make a "new" battery. I showed him how to solder them in, and then re-glued the plastic package; the pack lasted nearly 18 months.

If you don't know how to find a local source of commercial (as opposed to consumer) grade NiCd cells, then try calling the chief engineer at a local TV station. The portable video cameras used by TV news crews are powered by NiCd cells. It's a sure bet that the engineer will know a good source of fully rated cells.

When selecting cells for replacement, keep in mind several factors. First, of course, is the right size (AA, C, D, F) and the right A-H rating (as I said last month, not all C and D cells are created equal). Also keep in mind whether regular cells or solder-tab cells are needed. I've found that some consumer NiCd cells are in nonstandard packages. One brand of AA cells is a millimeter or so shorter than standard AA cells; as a result, intermittent operation is sometimes experienced. To avoid solder-shimming these cells or re-tensioning the contact spring, I simply avoid buying this brand and use standard-size batteries instead.

other batteries


Several other types of batteries are

used in communications equipment. For mobile and some portable applications, for example, there's the lead acid automobile battery. These are the familiar batteries used to start automobile engines; though they're very heavy and quite dangerous because of their contents, they're popular because they're generally well behaved and easily available. In addition, many Amateur Radio sets are designed to operate from the nominal 13.6 Vdc produced by the typical automobile battery.

In addition to the 13.6-volt (nee "12 volt") battery, there are also 6, 24, 28, and 32-volt lead acid batteries on the market. Some of these are marine batteries, others are military batteries (28 Vdc), and still others are truck batteries. The terminal voltage can be increased by connecting batteries in series, while current availability is increased by connecting batteries in parallel.

Mobile operation is usually carried out with the regular vehicle battery. But in certain cases, it's wise to have a separate battery for the radio communications equipment in order to have battery power in the event of a main vehicle power supply failure. Boaters, four-wheel drive "boondockers," hunters, and others may want to consider the type of system shown in fig. 4. This system, common in recreational vehicles, powers the creature comforts separately from the vehicle battery. The point is to keep your communications capability, even if you accidentally discharge the vehicle battery by leaving the lights on or suffer some other problem. The backup battery could then be used to start the vehicle or summon help, depending upon the situation.

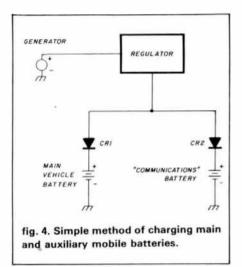The charger will be a generator or alternator installed in the vehicle. Although the ideal system would be to have separate charging and regulating systems, that ideal isn't always achievable for certain practical reasons. Thus, we have a single charger and voltage regulator for two or more batteries. Isolation between the batteries is provided by a pair of large-current



silicon diodes (CR1 and CR2). The rating of these diodes should be at least 1.5 times the maximum charge rate of the charger. In most cases, large studmounted diodes are used for CR1 and CR2, and they're mounted on a finned heat sink. In vehicular installations, keep in mind that ambient temperature is high in some locations, and will affect diode reliability.

For portable operations, some means must be provided to charge the lead acid battery. In most cases, a small gasoline or kerosene engine-powered generator is used to provide battery power. In some cases, an automotive type battery charger is needed to convert the ac output from the generator to dc for the battery. It's increasingly common, however, to find small 500to 2000-watt generators that include a "12-volt" output that provides from 6 to 35 amperes for purposes of powering radio equipment or charging batteries.

Other forms of chargers are also used. Some people use wind power, while others use falling water (which is somewhat easier in isolated locations than you might think possible), and still others use sunlight. I once met a Swedish Pentecostal missionary who worked in the deserts of Sudan. In the area of Africa to which he was sent, the roads are littered with the corpses of dead animals — even camels which should give you an idea of just how dreadful the place is. His organization doesn't allow him to set up camp without a 6-MHz Stoner Communications transceiver and an Amateur Radio transceiver (he uses a Kenwood TS-120). One thing that's plentiful in those latitudes is sunshine, so a set of solar panels (intended originally for boaters) was procured to charge the lead acid batteries. A 6-ampere charging system cost him about \$2300 at the time it was purchased several years ago, but it's probably cheaper now.

Regular maintenance of lead acid batteries is relatively easy and absolutely essential. The water level in each cell must be checked periodically; those whose need for the battery is critical should check the level weekly. Although it's best to fill the cells with distilled water (because of the lack of additional chemicals), ordinary tap water will also work. The vents in the caps that cover the cells mustn't be blocked; if dirt obscures the opening, replace the cap or clean it.

Warning: lead acid batteries produce hydrogen as a normal byproduct. If you fail to observe proper procedures, this hydrogen may cause the battery to explode, causing serious injury to people and damage to equipment.

Never allow the battery to become overcharged. Turn off all circuits connected to the battery - especially the charger - before disconnecting the wires to the battery. If current is flowing in those circuits, then a spark will occur . . . and that spark can create an explosion. This is not a hypothetical possibility, but a real danger. I've seen it happen twice in my career, and one time it darn near cost a fellow two-way radio technician his eyesight. He made the mistake of disconnecting the wires from a battery charger before turning off the charger and all peripheral circuits.

gel cell batteries

Another form of battery popular in portable radio equipment is the gel cell. I've seen these batteries in commercial, medical, and Amateur Radio equipment. Several years ago I worked with





Receive Only	Freq. Range (MHz)	N.F. (dB)	Gain (dB)	1 dB Comp. (dBm)	Device Type	Price	
P28VD P50VD P50VDG P144VD P144VDA P144VDG P220VD P220VDA P220VDG P432VDG P432VDA P432VDG	28-30 50-54 144-148 144-148 144-148 220-225 220-225 220-225 420-450 420-450	<1.1 <1.3 <0.5 <1.0 <0.5 <1.8 <1.2 <0.5 <1.8 <1.1 <0.5	15 24 15 24 15 24 15 20 15 20 15 7 16	0 + 12 0 + 12 0 + 12 - 20 + 12 + 12	DGFET DGFET DGFET DGFET DGFET DGFET GaAsFET Bipolar Bipolar GaAsFET	\$29.95 \$29.95 \$29.95 \$37.95 \$37.95 \$37.95 \$37.95 \$79.95 \$32.95 \$49.95 \$79.95	
Inline (rf swit							
SP28VD SP50VD SP50VDG SP144VDA SP144VDA SP144VDG SP220VD SP220VDA SP220VDA SP220VDG SP432VDA SP432VDA SP432VDA SP432VDG	28-30 50-54 144-148 144-148 144-148 220-225 220-225 220-225 220-225 420-450 420-450	<1.2 <1.4 <0.55 <1.6 <1.1 <0.55 <1.9 <1.2 <0.55 <1.9 <1.2 <0.55	15 24 15 24 15 24 15 20 15 17 16	0 + 12 0 + 12 0 + 12 - 20 + 12 - 20 + 12	DGFET DGFET DGFET DGFET DGFET DGFET GaAsFET Bipolar GaAsFET	\$59.95 \$59.95 \$59.95 \$59.95 \$67.95 \$59.95 \$59.95 \$67.95 \$109.95 \$109.95 \$79.95 \$109.95	


Every preamplifier is precision aligned on ARR's Hewlett Packard HP8970A/HP346A state-of-the-art noise figure meter. RX only preamplifiers are for receive applications only. Inline preamplifiers are rf switched (for use with transceivers) and handle 25 watts transmitter power. Mount Inline preamplifiers between transceiver and power amplifier for high power applications. Other amateur, commercial and special preamplifiers available in the 1-1000 MHz range. Please include \$2 shipping in U.S. and Canada. Connecticut residents add 7-1% % sales tax. Co.D. orders add \$2. Air mail to foreign coun-tries add 10%. Order your ARR Rx only or Inline preamplifier today and start hearing like never before



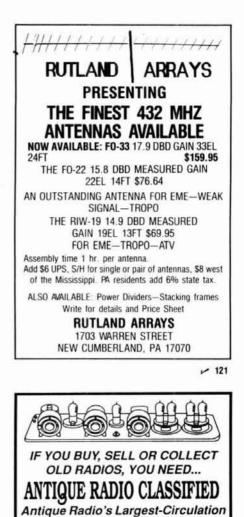Box 1242 • Burlington, CT 06013 • 203 582-9409








Monthly Magazine Articles - Classifieds - Ads for Parts & Services Also: Early TV, Ham Equip., Books, Telegraph, 40's & 50's Radios & more ... Free 20-word ad each month. Don't miss out! Sample - Free, 6-Month Trial - \$10. 1-Year: \$18 (\$24 by 1st Class). Foreign - Write. A.R.C., P.O. Box 2-A3, Carlisle, MA 01741

122

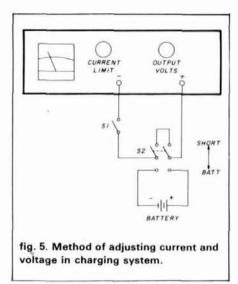ative Design Co., Ltd. **ROOF TOWERS!** A size to fit your needs 6, 10, or 15 ft. 10 FT CR-30 ILLUST 800-255-7020 **Excluding California Galvanized Steel Bracing and Hardware** 123 Dist. by **ORION HI-TECH** P.O. Box 8771. Calabasas, CA. 91302 (213) 663-2541



a piece of equipment that kept failing because of "premature" battery failure. The equipment manufacturer sent us a newly designed internal battery charger, but it too was deficient. All our battery chargers were high-tech models that depended upon sensing small variations in terminal voltage to determine a charge or discharge state. Unfortunately, the analog sensing circuitry had enough dc drift to produce bad results. In desperation, the engineer in our laboratory called the battery manufacturer - instead of the manufacturer of the device - and asked him. The manufacturer's applications engineer asked if we'd ever heard of Kirchoff's Voltage Law. Allowing that we'd heard that one before, we let the applications engineer quide us to a solution (see fig. 5).

The circuit shown in fig. 5 shows a simple method of charging gel cells (and other forms of batteries). The charger power supply must have two features: a precisely controlled output voltage and a current-limit control. With switch S1 open, set the output voltage to exactly the value of the fully charged voltage of the battery, or perhaps a small amount higher (100 to 200 mV). Place S2 in the shorting position and then close S1. Adjust the current-limit control for a short-circuit current equal to the maximum permitted charge current of the battery (A-H/10 for many batteries). After the

current and voltage are set, place switch S2 in the BATT position and charge the battery. When the battery voltage is less than the power supply output voltage, current flows into the battery. But when the battery voltage equals the power supply voltage, current flow ceases.

conclusion

Batteries can provide freedom of operation for electronic equipment. But they can also be a nuisance if not maintained correctly. Proper maintenance of the battery will provide long and reliable life.







- Controls. Ear Plug and Vinyl Case Incl.
- Compact. Just 1"H x 5%"W x 3%"D.
 90-Day Limited Factory Warranty.







\$369.95* **INCLUDES 2 HOOK-ON PROBES 20 MHz DUAL TRACE**

Features component testing circuit for resistors, capacitors, digital circuits and diodes—TV sync filter—high sensitivity-Zaxis-XY mode-built-in calibrator-5X horizontal magnifier

0 -10

\$499.95* **INCLUDES 2 HOOK-ON PROBES 35 MHz DUAL TRACE**

\$169.95 WIRED INCLUDES

RESOLUTION

100 Hz, 1 KHz

0.1Hz, 1Hz, 10Hz

1H7: 10H2

0 1Hz, 1Hz, 10Hz

0 1Hz 1Hz 10Hz

Hz 10Hz 100Hz

wide frequency bandwidth—optimal sensitivity —delayed triggering sweep—hold off—ALT trigger—single sweep TV sync 5X magnification—XY or XYZ operation— HF/LF noise reduction



NEW \$449.95* **INCLUDES 2 HOOK-ON PROBES** 15 MHz DUAL TRACE PORTABLE

Field/bench applications—built-in charger and battery pack —up to 2 hours operation per charge—5X horizontal magnification—high brightness CRT—front panel trace rotator

All Ramsey oscilloscopes feature unsurpassed quality at an unbeatable price. Of heavy duty construction, they are suitable for hobby, service and production applications.

MODEL	BAND WIDTH	# TRACES	CRT SIZE	VERTICAL SENSITIVITY	MAXIMUM TRIG FREQ	BANDWIDTH
2200	20 MHz	(2)	8x10CM	5 mV per div	35 MHz	30 MHz
2500	15 MHz	(2)	3.5 inch	2 mV per div	30 MHz	25 MHz
3500 ,	35 MHz	(2)	8x10CM	1 mV per div	50 MHz	60 MHz

*Add an additional \$10.00 for each unit for shipping.

MINI-100 COUNTER

600 AUM

s119.95

MODEL

MINI-100

CT-70

CT-90

CT-50

CT-125

CT-90 WITH OV-1 OPTION

110 CHARGER, NICAS BATTERIES. AC ADAPTER INCLUDED

FRED RANGE

1-500 MHz

20 Hz-550 MH;

10 Hz-600 MHz

5 Hz-600 MHz

10 Hz-1 25 GHz

10 Hz-600 MHz

COMPACT

\$2495

lest leads and battery included

DIGITAL

CT-70 7 DIGIT 525 MHz CT-90 9 DIGIT 600 MHz CT-508 DIGIT 600 MHz

PRICE

119.95

139.95

169.95

189.95

189.95

229.90



and pass

CT-125 9 DIGIT 1.2 GHz

USFARIE

\$189.95 WIRED INCLUDES

RAMSEY FREQUENCY COUNTERS

Ramsey Electronics has been manufacturing electronic test gear for over 10 years and is recognized for lab qual-ity products at breakthrough prices. Our frequency counters have features and capabilities of counters costing twice as much. BP-4 Nicad battery pack for CT-70, 118 CT-90 and CT-125 Frequency Counters. \$8.95

RAMSEY ELECTRONICS, INC. 2575 Baird Ave.—Dept. HR Penfield, N.Y. 14526



Compact sized reliability and accuracy. This LCD digital multitester easily fits in your pocket, you can take it anywhere. It features full overload protection • 3% digit LCD readout • recessed input jacks safety probes • diode check function
 2000 hours battery life

RAMSEY D-4100 RAMSEY D-5100 MULTITESTER

16.95

13.95

3.95

00000

\$139.95 WIRED. INCLUDES

SENSITIVITY

50mv To 150 MHz

10mv To 150 MHz 150mv To 600 MHz

25mv @ 50 MHz 15mv @ 500 MHz 100 mv @ 800 MHz

LESS THAN 25 my

< 10mv To 150 MHz < 150mv To 600 MHz

Less than 250

- Th

16

ACCURACY

1 PPM

PPM

1.PPM

1 PPN

1 PPM

0.1 PPM

DIGITS

8

a

Has TOUCH-HOLD feature to allow readings to be logged or referred to before making the next reading. Up to 10 AMP current capability and a continuity function which beeps on zero Ohms





(0)

TWO IST

\$8995

wired includes AC adapter

PR-2 COUNTER PREAMP \$4495 wired includes AC adapter

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for sniffing RF • ideal receiver/TV preamp

PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies Up in frequency • great for PL tone measurements multiples by 10 or 100 • 0.01 Hz resolution
 & built-in signal preamp/conditioner

PS-10B1 GHz PRESCALER

Extends the range of your present counter to 1 GHz • 2 stage preamp • divide by 1000 cir-cuitry • super sensitive (50 mV typical) • BNC connectors • 1 GHz in, 1 MHz out • drives any counter

MINI KITS—EASY TO ASSEMBLE—FUN TO USE--FOR BEGINNERS, STUDENTS AND PROS NEN COLOR ORGAN VIDEO MODULATOR M WIRELESS 100 C C01 \$7.95 stable, funable over ch 4-6. Runs on 5-15V rent lights flicker SUPER e decoder a single PC board. Fe with music One light each for, high, mid-range and lows. Each individu-ally adjustable and ts std. video signal. Best unit on the (CRORDS SLEUTH C board. Features: 400-5 le range via 20 turn pot v on, 567 IC. Useful for tou efection. FSK, etc. Can al market! Complete kit. VD-400-5000 MAD BLASTER Produces LOUD ear shat-tering and attention get-ting siren like sound. Car supply up to 15 watts of oppositions audio Buns s up to 300 1 Trans A Super se ative amp **FM MINI** drives up to 300 W runs in 110VAC any FM broadcast radio e regulation LED BLINKY KIT which will pick up a drop at 15 feet! Great MIKE uses any type of mike Runs on 310 9V. Type FM-2 has added sensitive **FM RECEIVEN** for monitoring baby's room or as general pur-pose amplifier. Full 2W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker Iternately flashes: mbo LEDs. Use for ame badges, butto be used as a stable to on 5 to 12 volts. \$8.95 or hobby experiment tion. Full fledged sug uper high perfo ML-1Kit. TELEPHONE FM wireless mike kit! hike preamp stage RANSMITTER \$5.95 Complete kit, TD-1 Transmits a stable signal up to 300 yards with ns on 3 to 15 Low cost with prote sional performance wresinclude; self p on 6-15 VDC \$3.95 **VOICE ACTIVATED** FM-1Kit up to 300 yards with exceptional audio quality, by means of its built in efectret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is \$4.95 microvolt sensitivity, 10.7 MHz /F Integrated Circuit detector, 50 mw audia amplifier, 9V external power source, operation on standard FM broadcast band as well as large portions o each side, compact (6° square). for bug detec-tion or reception \$2.95 ance Fes SWITCH BL-1KIT MALTER SDRAKE \$4.95 FM-2Kit ce activated switch 40 WATT 2 mtr \$5.95 WHISPER LIGHT voice activated switch kit provides switched output with current ca-pability up to 100 mA Can drive relays, lights, LED or even a tape recorder motor. Runs on over UNIVERSAL TIMER BN-9Kit inable te powered, tunat om 76 to 100 MHz, Provides the basic parts and PC board required to provide a source of pre-cision timing and pulse An interesting kit, sma mike picks up sounds and converts them to light. The louder the sound, the brighter the light includes mike, cou trals are PWR AMP Simple Class C power amp leatures 8 times power gain 1 W in for 8 out, 2 W in for 15 out, 5 W in for 400 wort. Max outpu of 50 W, incredible value, complete with all parts, less case and T-R relay ergo proroduces upward and downward wail. 5W peak audio output, runs on 3-55 volts, uses 3-45 ohm speaker. SIREN 60 Hz TIME BASE Huns on 5-15 VDC polarity antisensitive. compact size (%* x 1%*) cision timing and pulse generation. Uses 555 timer IC and includes a ow current (25ma) easily installs anywher on the phone line or naide the instrument FM-3Kit \$14.95 min/month accuracy PA-1, 40 W pwr amp kit \$22.95 9 VDC. VS-1 KIT range of parts for most trols up to 300 W, runs on 119 VAC 18-6Kit \$5.50 square), for tion or reces FM-3 Wired and Tests lete kit, SM-3 timing needs TR-1. RF sensed T-R relay kit 6.95 \$6.95 \$2.95 \$14.95 \$5.95 \$6.95 18-6 Assy \$9.95 FR-1KIT \$14.95 19.95 UL5KI WL-1Kit TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for retund • and 6% for shipping and insurance to a maximum of 310.00 • loreign add 15% for surface mail • COD add 22.50 1000 In USA only) • orders under 515.00 add 15.6 • NY residents add 7% sates tax • 90 day parts warranty on all kits • 1 year parts & labor MAMSEV & LECTORULES ACCESSORIES FOR RAMSEY COUNTERS PHONE ORDERS CALL Telescopic whip antenna—BNC plug \$ 8.95 VISA 586-39 51 AasterCord

TELEX 466735 RAMSEY CI

FAX 716-586-4754

convert a \$25 CB HT for 6 meters

New crystals, alignment put you on the air

Radio Shack's new TRC-501 is intended for unlicensed 49-MHz CB operation. While most units sold for this band commonly use a-m and super-regenerative receivers, this unit is a unique full-fledged fm transceiver aimed at the semi-professional user who needs inexpensive, very local communications. At its low price (about \$25), this unit obviously can't be compared with commercial quality HTs — but it still represents a surprising value for Amateur experimenters. This article shows how to convert this transceiver for the 6-meter Amateur band.

The schematic supplied with the transceiver is unfortunately very tiny and impossible to read. (I did try enlarging the print to produce a more legible copy, but the optical limitations of my copying machine produced only larger, even more illegible prints.) Since very little other useful technical information accompanies the transceiver, I'll provide a quick description of the circuits used in this frugally engineered package.

receiver

The rf amplifier is a common-base stage. Most of the front-end selectivity is provided by L2, the interstage coupling transformer between the rf amplifier and mixer. Another bipolar transistor serves as the mixer stage. The first of two ceramic filters, an inexpensive wideband 10.7-MHz type commonly found in fm broadcast i-f stages, follows the mixer. A thirdovertone crystal oscillator provides LO injection. The heart of the receiver is a Motorola MC1355 integrated circuit. This chip provides all of the i-f functions, including the second LO oscillator and mixer, fm detection and audio squelch circuits. The second i-f is on 455 kHz. The ultimate receiver selectivity is determined by the 455-kHz ceramic filter. An LM386 audio amplifier delivers surprisingly good audio.

transmitter

The transmitter signal starts with a 16-MHz oscillator, triples, and finally ends up in a low-power amplifier stage. Direct fm — via a varicap modulator is applied to the 16-MHz oscillator. A deviation control (RV1) is included in the audio chain. The internal electret mic element produces good quality audio.

order crystals

The first thing to do is order the crystals for the desired receiver and transmitter channels. The transmitter crystal operates at one-third the actual transmitting frequency. For example, for 52.525-MHz (the national simplex channel), order a crystal for 17.508333 MHz.

The receiver crystal operates 10.7 MHz below the desired receive frequency. Again, using 52.25 MHz as an example, the crystal would be on 41.825 MHz. Specify a third-overtone series-resonant cut when ordering.

Most crystal companies will gladly, and without cost, correlate new crystals against customer samples. For best results I suggest carefully removing the crys-

By Peter Bertini, K1ZJH, 20 Patsun Road, Somers, Connecticut 06071

tals from the TRC-501 and sending them along with your order. They'll be returned undamaged. Since I chose to order my crystals before the TRC-501 was available, I gambled and guessed that a 20-pF load capacitance was correct for the transmit crystals. I was wrong, and the transmitter was nearly 25 kHz low in frequency. By inserting a 22-pF capacitor in series with the crystal, I was able to persuade the crystal to oscillate on the proper frequency. This involved cutting a run on the bottom of the board. I strongly recommend sending the 49-MHz crystals to the crystal company for proper correlation on the new frequencies. Mention that these crystals are for 49.830-MHz operation. Otherwise, I'd suggest ordering crystals about 8.333 kHz higher in frequency than calculated to correct for my errors. (For 52.525 MHz, the crystal would be at 17.516666 MHz instead of 17.508333 MHz when specified for 20-pF load capacitance, fundamental cut.) Also be sure that the new wire lead crystals are physically no larger than the ones supplied with the TRC-501; if they're larger, you'll find (as I did) that you won't be able to fit the radio back into its case without expending considerable effort in repositioning the crystals. Most crystal manufacturers will have no problem in supplying a crystal package equal to or smaller than those supplied with the TRC-501.

disassembly

Opening the TRC-501 is somewhat of a challenge. Start by removing the belt clip from the rear of the radio and the battery compartment cover. This will expose a single phillips-head screw which must be removed. The front and rear covers are clamshelled together; looking into the battery compartment reveals two of the four plastic clips locking the pieces together. Try to pry the case open carefully while working on one of the small exposed hooks with a pick or small screwdriver. Once the case pops open, be careful not to misplace the call button or push-to-talk bar. The call button must be reinstalled exactly as removed upon reassembly — the button's switch shaft-hole is not symmetrically oriented.

Once the pc board is exposed, remove the phillips screw located at the top of the board. The board may be lifted and laid to one side of the front of the case, but be careful not to stress the speaker or mike leads unduly. Note that the component part numbers, referenced to the schematic, are silkscreened on the component side of the board. Remove the solder from the leads mounting crystals X2 and X3 carefully. Once the holes are completely clear of solder and the leads are free, remove the crystals.

transmitter alignment

When the new crystals arrive, install the transmit crystal at X3 and the receive crystal at X2. Receiver

alignment requires an adjustable level signal source. Transmitter alignment requires a field-strength meter and some means of setting the frequency; either a counter or receiver equipped with a zero discriminator meter will be useful.

I found it easiest to tune the transmitter using a fieldstrength meter. Coils L6, L5, and L1 are peaked for maximum field strength with the antenna fully extended. These three coils are clustered together in the lower right-hand section of the pc board, below crystal X3. Repeak the coils several times until no further improvement is noted. Transmitter frequency is adjusted by coil L7, directly above X3. The coil wax should be removed before the coil is adjusted. Heat the wax with a small iron and use tissue paper to wick away the wax when it's molten. The coils might tend to peak with cores almost fully removed from the forms. By going further into the forms (i.e., clockwise, rather than upwards) there's more adjustment for raising frequency.

The transmitter deviation is controlled by RV1, located above X3. The audio sensitivity is very good, and the deviation limiting is excellent, as is the modulation symmetry and quality.

receiver alignment

When crystal X2 is installed, a strong local signal should be audible. If not, the crystal may not be oscillating, and a slight readjustment of L4 may be needed. Remove the coil wax from L4 before adjusting. Coil L4 is below X2 in the bottom left-hand corner of the board. Receiver alignment is done by setting coils L4 and L2 for best quieting on a weak signal. Coil L2 is located near center at the board bottom. If the audio sounds slightly distorted, adjusting coil L4 will clear up the problem. (Although the factory setting is just fine, coil L3 may be adjusted for best recovered audio.)


performance

Because I had some difficulty finding a true 50-ohm termination point in this transceiver, the actual performance specs may be better than those I've measured, and certainly no worse. The manufacturer specifies 0.5- μ V sensitivity for 20 dB-s/n; I measured about 2 μ V. Transmitter power is rated at 10,000 μ V/M at 3 meters, the maximum allowed by the FCC for unlicensed 49-MHz operation. Actual power, with a fresh alkaline battery, was measured at +11 dBm (roughly 10 mW).

There's a dearth of 6-meter fm activity here in Connecticut, and I've converted only one of these units so far, so I can't boast about great DX contacts made with the TRC-501. For local line-of-sight communications, I suspect the TRC-501 will be hard to beat.



Reader Service CHECK-OFF Page 98

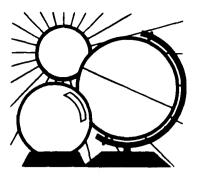

DX FORECASTER Garth Stonehocker, KØRYW

summertime DX

You've probably noticed some changes in operating conditions between this spring and summer's DX season. One obvious difference is that the daytime bands are open for more hours, from early morning till late evening. This translates to more hours for DXing during your summer leisure time.

Even though the 15- and 20-meter bands are open for long skip, the 10and 12-meter bands don't open often, and when they do, they're not open for very long. Signal levels also appear to be down. All these effects are attributable to the fact that the sun is in the northern hemisphere. During the daytime, the sun's ultraviolet light generates a thicker, more dense ionosphere over a larger area. Because this increase in ion production occurs in the D, E, and lower F regions of the ionosphere (i.e., 48 to 100 miles above the surface of the earth), it's more difficult for ions to diffuse and drift upward to the higher F2 layer, about 180 miles above the Earth. Consequently, the maximum usable frequencies (MUFs) don't build up as high in summer as they do during the other seasons of the year. The lower MUF signal loses more of its energy as it travels through the thicker, more dense D, E, and lower F regions. The loss can be up to 7 dB on 20 meters in the mid-latitudes. As a result, summertime long-skip conditions on 10 and 12 meters include shorter openings — if the bands are open at all and weaker signal levels. Thunderstorm noise is also prevalent.

So what can we say that's positive about this season? Well, there are sporadic E short-skip openings. The upper bands retain their MUFs longer, and the MUFs are higher and nearly constant over the north polar regions because of the continuous daylight there. The sporadic E openings (up to 1200 miles and multiples) produce signal levels that are sometimes 25 dB greater than those received during long skip; they also account for 6meter (and lower) band openings for a few hours nearly every day. You can also expect an improvement in 20 meters, with long-skip paths increasing in duration and available in more northern latitudes. This opportunity may provide contacts you haven't thought of working before. So the summer season is good for some decent DX after all!

last-minute forecast

The month opens with the lower bands favored in spite of the high probability of thunderstorm QRN in the late afternoon and evening. Solar flux levels are expected to be low during the first and second weeks; work DX from early morning till noon. A typical day might start with a mix of short-skip propagation from Sporadic E openings around sunrise and long-skip paths from the darkness periods traveling from the west but shifting to the east. As the sun rises - and with it, the ionospheric layer and consequent signal absorption - expect short-skip conditions to reoccur. If the signals weaken too much, move up to 15 or 20 for awhile. Look for E_S openings closer to noontime. Try the higher bands for Es also. These higher frequencies are expected to be best around August 20. Don't expect many transequatorial one-long-hop openings this summer, but look for the ES openings to the south. Geomagnetic disturbances may be experienced around

August 4, 17, 22, and 28. These disturbances will affect the nighttime bands the most.

For the VHF/UHF enthusiast, the moon's perigee will occur on the 8th, with the full moon on the 9th. The Perseids meteor shower will occur from the 10th to the 14th, with a maximum rate of better than 50 meteors per hour expected on the 11th and 12th. This is an excellent shower to work with.

band-by-band summary

Six-meter sporadic E short-skip conditions will occur for 30 minutes to a couple of hours around local noon on some days, for this last good month of this summer's E_S season. Expect about 1000 miles per hop.

Ten, twelve, and fifteen meters will experience quite a few short-skip E_S openings and some long-skip openings during the 27-day solar flux peaks to southern areas of the world during daylight hours. Fifteen meters will be best for only an hour or two as the maximum usable frequency decreases during the late afternoon.

Twenty, thirty, and forty meters will be useful for DX communications to most eastern, western, and northern areas of the world during daylight hours and into the evening almost every day, via long skip to 2000 miles per hop or by means of short-skip E_S , with 1000-mile hops. The period of daylight is still relatively long, but will be noticeably shorter by the end of the month.

Thirty, forty, eighty, and one-sixty meters are all good for nighttime DX, even though the background noise is severe in the evenings. The direction of the openings will rotate around from the east to the south and then westward toward the morning. If you want to avoid thunderstorm QRN, Sporadic E propagation may be helpful in the early evening toward the east and south. Try the early morning hours for communication paths to the west and monitor WWV or WWVH on 2.5 and 5 MHz as beacons.

	2300	2200	2100	2000	1900	1800	1700	1600	1500	Ĩ	1300	1200	1100	1000	3060	0000	0700	9800 0000	0500	0400	0300	0200	0100	800	GMT	
AUGUST	4:00	3:00	2:00	1:08	12:00	11:00	10:00	9:00	8:00	7:00	6:00	5:00	4:8	3:00	2:00	1:00	12:00	11:00	10:00	9;00 00	8:00	7:00	8:00	5:00	PDT	
ASIA FAR EAST	30	30	30	40	30	30	30	30	20	20	20	30	40	30	30	30	30	20	20	20	20	20	20	20	- > Z	
EUROPE	20	20	20	20	20	20	20	20	20	20	20	20	20	30	30	30	30	30	20	20	30	30	30	30	Z	
S. AFRICA	20	20	15	15	12	12	10	10	12	12	15	15	20	30*	20	20	20	20	20	30	20	20	20	20	 m	٤
S. AMERICA	10	10	10	12	12	12	12	12	15	15	20	20	20	30	20	20	20	20	20	20	5	15	12	12	SE .	WESTERN
ANTARCTICA	15	15	15	15	20	2	20	ω ω	40	40	40	40	40	30	30	30	30	30	30	20	20	20	5	15	- 0	ERN
NEW ZEALAND	12	12	12	15	15	20	20	30	20	20	220	20	20	20	20	15	15	12	12	12	10	10	10	12	SX	I USA
OCEANIA AUSTRALIA	12*		12	15	20	30	30	30	20	20	20	20	20	20	20	15	15		12	12	6	10	10	10	1 2	Þ
JAPAN	20	20	20	20	20	30	40	30	30	30	40	30	30	30	30	20	20	20	20	20	20	15	15	15	1 Z Z	
	5	4	ω	N		12	=	1	6	00		6	o,		ω	~~~~		12	=	đ	6]			3	
	5.08	8	30	8	8	12:00	1.08	8	9:00	8	8	8	8	8	8	8	8	12:00	11:08	10:00	8:00	2	7:08	8:00 2	9	
ASIA FAR EAST	20	30	40	30	30	30	30 	30 	20	20	20	20	20		30	30	30	30	30 3				<u>þ</u>	203	> Z	
EUROPE	20	20	20 1	20	20	20	20	20	15	20 1	20 1	20 1	20 2	30 2	30	30	30 2	30 2	30 2	0	30	30	30 2	30 2	Ž	
S. AFRICA	20	20	5	5	12	5	6	2	12	ე	5	5	ŏ	0	30	20	õ	0	0	30		20	0	Õ	• •	Ζ
S. AMERICA	12	10	10		12	5		5	1-1 5	15	н 5	20	20	30	30	20	20	20	20	20	20	10	15	12	SE SE	MIDL
	15	15	15	20	20	20	20	20	<u>ω</u>	40	40	40	40	40	40	30	30	30	30	20	20	20	20	15	ۍ ـــ	USA
NEW ZEALAND	12	12	12	15	15	20	30	20	20	20	20	20	20	20	20	20	15	15	12	12		12*	10	10	SW SW	
OCEANIA AUSTRALIA	12*	12	15	5	20	20 0	30	30	20	20	20	20	20	20	20	15	15	15	12	12		10	10	10	₹	
JAPAN	20	20	20	20	20	30	30	30	30	30	20	20	30	30	30	30	30	30	20	20		20	20	20	/ ž	
	6:00	5:00	4:00	3:00	2:08		12:00	11-08	10:00	9:00	8:00	7:00	6:00	5:00	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9 8	8:00	7:00	COT	
	7:00	6:00	5:00	4:00	3:00	2:00	1:00	12:00	11:00	10:0	9:00	8:00	7:00	6:00	5.00	4:00	3:00	2:00	1:00	12:00	11:00	10:00	9:00	8:00	EOT	
 ASIA	120	30	4	ι <u>ο</u> ω	ι <u>α</u> Ιω		ω	l° N	N	2	$\frac{1}{2}$	2	<u> </u> 2	1	2	2	о З	3	3		ω ω	2	2	2	+ z	
EUROPE	ω	2	10 2	0 2	0 2	6 2	2 2		0	0 2	0 2	0 2	0 2	<u>p</u> _	0 2	0 3	0 4	10 3	03	80 4	0 3	0 ω	03	0 3	Zm	
S. AFRICA	80 2	0 2	0	0 1	Ď.	Ď	Ď	<u>5</u>	<u>ர</u> ப	0	0	0		<u>p</u> _	0 2	0 	0 2	0 2	2	0	0 2	0 2	0 2	0 2	ът 1 т	Ū
CARIBBEAN	0 1	0	5	5					N*	21	2	5 2	52	0 2	03	0 2	0 2	0 2	02		0	0 1	01	0 1	SE	AST
S. AMERICA	2	0 2	0 2	0 2	2	2	2	2	2 ω	5 4	5	04	0 4	0 4	0 4	0 4	03	03	03	0 3	2	5 2	52	2 2	• • •	ERN
NEW ZEALAND	0	0	0	0		6 	0	6	0 2	0 2	0 2	0 2	0 2	0 2	02	0 2	0 2	0 2	0 1	0 1	~	0 1:	0 1	0 1 0	SW	ASTERN USA
OCEANIA	2 1	21	21	<u> </u>	5-2	ۍ ا	6 	30-3	03	0 2	0 2	0 2	03	02	0 2	0 2	0 2	0 2	5 1	1		21:	0 10	0 10		Þ
AUSTRALIA JAPAN	N	2 2	2 21	5 2	0	2013	0	03	03	03	0 3(0 20	0 20	N	0 30	0 30	0 30	0 30	5 30	3	2 20	2 20	0 20	0 2 0	T ₹ N¥	
	0	2	0	0	<u>р</u>	<u>P</u> _	30	Þ	0	0	0	0	0	<u> </u>	0	0	0	0	0		0	Ľ	Ľ		/ 2	_

The italicized numbers signify the bands to try during the transition and early morning hours, while the standard type provides MUF during "normal" hours.

*Look at next higher band for possible openings.

ham radio




universal temperature probe

The 80T-150U Universal Temperature Probe from the John Fluke Manufacturing Company, Inc[®], is a measurement accessory that converts any digital multimeter into a thermometer. The 80T-150U uses a P-N junction temperature sensor housed in a low thermal mass tip to provide fast, highly accurate readings.

Switch-selectable for readouts in F or C, the 80T-140U can make temperature measurements of live circuits, with 350-volt peak ac standoff capability. Small components can be accurately measured without cooling caused by the mass of the probe tip.

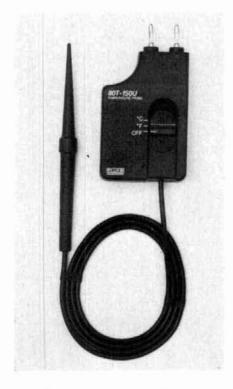The 80T-150U has a range of -58 to +302degrees F (-50 C to +150 C). Its basic accuracy is \pm 1.8 degrees F (1 C) from 32 to 212 degrees F (0 to 100 C), thereby providing more accurate readings than most thermocouple de-



vices. The unit uses a standard 9-volt battery, with a built-in battery check feature using the external DMM. Average battery life is 1600 hours. The 80T-150U has a suggested U.S. list price of \$129.

For more information, contact John Fluke Manufacturing Company, Inc., P.O. Box C9090, Everett, Washington 89206.

Circle #301 on Reader Service Card.

new tuning indicator

MFJ Enterprises, Inc. has released a new tuning indicator for users of TAPR TNC-1s, TNC-2s, and clones such as the MFJ-1270.

The MFJ-1273 (\$49.95) lets you tune in hf,



OSCAR and other non-fm packet stations fast because it shows you in which direction to tune your radio. Just center a single LED and you're precisely tuned in to within 10 Hz.

Twenty high-resolution LEDs and wide frequency coverage make tuning easy.

The MFJ-1273 tuning indicator plugs into the MFJ-1270 and all TNC-1s, TNC-2s, and clones that have the TAPR tuning indicator connection.

This MFJ product comes with a double guarantee. If ordered directly from MFJ, it may be returned within 30 days for a prompt refund (less shipping). It's also covered by MFJ's one-year unconditional guarantee.


For more information, contact MFJ Enterprises, Inc., P.O. Box 494, Mississippi State, Mississippi 39762.

Circle #302 on Reader Service Card.

ATV exciter/modulator for 33 cm

P. C. Electronics' Model TXA5-33 1-watt ATV exciter/modulator board for the 33-cm (902-928 MHz) band allows Amateurs of Technician class license or higher to transmit live-action color or black and white composite video from cameras, VCRs, or computers to other hams.

Most ATV activity has been on the 70-cm (420-450 MHz) band up until now. By also having a 33-cm ATV station, hams can now run full duplex video and audio crossband with another station on 70 cm. The TXA5-33 board should also make putting up a short-distance video link, crossband ATV repeater, bulletin board video repeater, and public service applications such as Space Shuttle video and weather radar video easy — without tying up one or both of the usual 70-cm ATV channels.

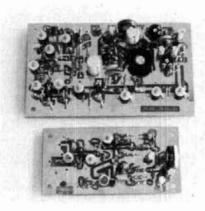

The 3 x 5-inch wired and tested TXA5-33 board accepts the standard 1-volt peak-to-peak composite video from any source. For sound, the P.C. Electronics FMA5 or XFMA5 Sound Subcarrier board is connected to the 4.5-MHz input pad of the TXA5-33 modulator circuit. The board takes 12 to 14 Vdc. At 13.8 Vdc, the board draws about 400 mA and puts out over 1 watt PEP into 50 ohms on the sync tip.

Using the 1-watt TXA5-33 and 23-element Tonna 20923 beams (16.2 dBd), the snow-free line-of-sight video range is 10 miles. This distance assumes a 4.2-dB loss in 100 feet of Columbia 1180C or Belden 9913 coax and the P.C. Electronics TVC-9G GaAsFET Downconverter ahead of any good TV set tuned to channel 3. Distance will be greater with shorter coax length or by mounting the antenna on the downconverter (every 6 dB doubles the distance).

Video quality is about as good as what you'd see fromyour own camera on your home VCR. The TV set's i-f bandwidth is the major limitation on resolution. Since ATV uses the same standards as broadcast TV, receiving is as easy as connecting a downconverter and antenna for Amateur frequencies to your TV set or VCR tuner set for channel 2, 3, or 4, depending on which one is unused in your area.

The TXA5-33 transmitter board is priced at \$139; the TVC-9 GaAsFET downconverter board at \$69; and the TVC-9G downconverter — ready to go in a cabinet with power supply — is \$109. The Tonna 20923 23-element Yagi is \$59. All prices include UPS surface shipping in the contiguous USA.

For a complete catalog of product information, contact P.C. Electronics, 2522 Paxson Lane, Arcadia, California 91006.

Circle #303 on Reader Service Card.

1.2-GHz transceiver

ICOM has announced the release of its compact new IC-1200, a 1.2-GHz transceiver for mobile or base operation that covers 1240-1300 MHz.

Featuring a simple-to-use front panel and a large LCD readout with an automatic dimmer circuit, the IC-1200 has 21 memory channels, 10 watts output power (including a low-power position for Novices), and memory scan. All subaudible tones are built-in.

The IC-1200 incorporates ICOM's AFC (Automatic Frequency Control) function, which automatically adjusts the receive frequency to the frequency of the transmitting station.

Two new options for the IC-1200 are the UT-28 digital code squelch unit, which incorporates a system of digital coding and decoding, and the UT-29 tone squelch unit, which encodes and decodes subaudible tones.



For further information, contact ICOM America Inc., 2380 116 Avenue N.E., P.O. Box C-90029, Bellevue, Washington 98009-9029.

Circle #304 on Reader Service Card.

packet radio handbook

In the new Packet Radio Handbook from TAB, Jonathan Mayo, KR3T, covers just about everything a beginner needs to know to put a packet radio station on the air. In addition, he discusses the history and development of packet radio; the people and organizations who introduced it to Amateurs; using packet with other modes for emergency communications and traffic handling, and more.

For newcomers, the book serves as a comprehensive introduction to packet radio theory and operation. Experienced operators will find a thorough review of basic techniques, along with more detailed technical information about modulation methods and networking principles, the use of protocols such as AX.25 and VADCG, an explanation of how TNCs work, and a discussion of bulletin board operation.

Also included are a complete glossary of common packet radio terms, listings of available equipment, and names and addresses of packet manufacturers, clubs, and newsletters.

The Packet Radio Handbook can be ordered from Ham Radio's Bookstore for \$14.95, plus \$3.50 shipping and handling.

software for Novices

Heathkit's updated computer-assisted instruction (CAI) software offers FCC-approved questions for all five Amateur Radio examination elements, including the latest Novice, Technician, and General class examinations. Menu-

Measure Up With Coaxial Dynamics Model 7510 Frequency Counter/Wattmeter

This 2-in-1 laboratory/portable, compact, dual function digital frequency counter/wattmeter makes frequency and power readings easy. The optional battery pack converts Model 7510 to a portable field service instrument. The frequency counter measuring range is 10 Hz to 1.25 GHz. The wattmeter power measuring range is 100 mW to 5 kW over 2 to 1,000 MHz, determined by standard elements ordered separately. Contact us for your nearest authorized Coaxial Dynamics

00000

authorized Coaxial Dynamic representative or distributor in our world-wide



sales network.


15210 Industrial Parkway Cleveland, Ohio 44135 216-267-2233 1-800-COAXIAL Telex: 98-0630

Service and Dependability...A Part of Every Product

J 117

X-ANNES

38-

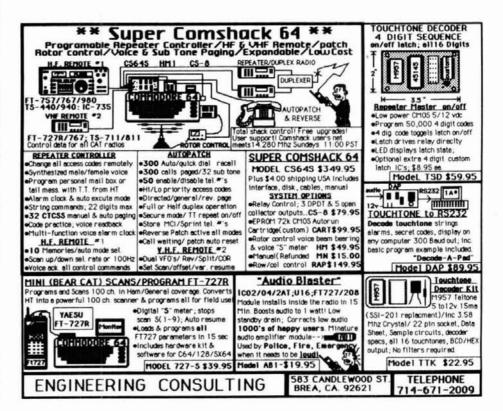



driven programs on disk feature all nine subelements plus the entire data base of FCCapproved questions. Users can create sample tests with multiple-choice questions and a CW practice program.

The software can be used with Heathkit, Zenith Data Systems, IBM, and other PCcompatible computers.

For information, contact Heath Company, Department 150-905, Benton Harbor, Michigan 40922. (In Canada, contact Heath Company, 1020 Islington Avenue, Department 3100, Toronto, Ontario M8Z 523.)

Circle #305 on Reader Service Card.

new terminal program for C-64, 128

Kantronics has introduced a comprehensive terminal program written for use with the Commodore 64 and 128 computers. Offering split screen display, message buffers, disk storage, a type-ahead buffer, and other features, the C-128 program runs in 128 mode and provides for 80-character lines. It be used with almost all the Kantronics "smart" modems, including the KPC-1, KPC-2, KPC-4, KPC-2400, KAM, and UTU-XT/(P). Kanterm 64 and 128 are included on a single diskette. The suggested retail price is \$29.95.

For details, contact Kantronics, 1202 E. 23rd Street, Lawrence, Kansas 66046.

Circle #306 on Reader Service Card.

.

compact VHF amplifier

The HL-160V25A is the compact version of the HL-160V25 VHF amplifier. The HL-160V25A has all the performance of the original, with a simplified control panel to reduce costs without sacrificing quality.

Multi-mode operation for FM, SSB, and CW plus a new GaAsFET type internal pre-amplifier make the HL-160V25A the best choice for high-power mobile or base operation with today's 25-watt output radios. The HL-160V25A produces 160 watts output from 25 watts drive across the entire 2-meter band. The amplifer can be keyed by a remote contact or by the rf signal from the transceiver or transmitter.

Currently in stock at local Encomm, Inc. dealers, its suggested retail price is \$269.95. For details, contact Encomm, Inc., 1506 Capital, Plano, Texas 7507.

Circle #307 on Reader Service Card.

new dual-band antenna coupler

Larsen Electronics, Inc. has introduced its new AD-2/70 Dual-Band Antenna Coupler, which allows simultaneous operation in both VHF and UHF bands with a common dual-band antenna.

The AD-2/70 will connect separate VHF and UHF radios with a common dual-band antenna, such as one from the Larsen 2/70 series, or allow separate VHF and UHF antennas to be used with a single-port dual-band radio.

The Dual-Band Coupler, designed for operation in Amateur 2-meter and 70-centimeter bands, can be used for commercial VHF and UHF applications as well. Crossband isolation is suppressed to -50 dB or more, permitting interference-free simultaneous transmission or reception. Maximum power rating is 200 watts PEP composite VHF/UHF power.

For additional information, contact Larsen Electronics, Inc., P.O. Box 1799, Vancouver, Washington 98668.

Circle #312 on Reader Service Card.

weather satellite converter

Hamtronics, Inc. recently announced a new receiving converter for reception of weather fax pictures transmitted from satellites operating in the 137-MHz band. Basically a modified version of the CA144 2-meter Amateur converter, the CA137-28 Converter translates all signals received in the 136-138 MHz satellite band for reception on tunable 28-30 MHz wideband fm receivers. To make the conversion in dial frequency, simply subtract 108.000 from the frequency you want to receive. The receiver uses a low-noise front end to provide sensitivity of less than $0.2 \mu V$. It operates on + 13.6 Vdc at 30 mA.

The CA137-28 Converter is available in three versions: wired and tested in the 4 x 4 x 2-inch cabinet shown at \$69; in kit form at \$49; and a kit for just the pc board module (less case) at \$39. Shipping and handling is \$3.

GaAsFET preamps of various types are also available for this band for those who'd like to take advantage of reduced cable loss by mounting a preamp at the antenna. An LNG-144 GaAs-FET preamp enclosed in a 2 x 2-inch metal case is \$49 wired and tested. An LNW-144 Preamp, which is the same basic circuit without a case, is available for \$34 wired and tested or \$19 in kit form. All three have a noise figure less than 1 dB. By using one of these preamps, the sensitivity of the converter can be made as low as 0.1 μ V.

Other Hamtronics products include VHF and UHF transmitter and receiver modules and complete repeaters, "202"-type fsk modulators and demodulators for digital data interface, low-noise GaAsFET receiver preamps, 806-MHz scanner converters, transmitting and receiving converters for various amateur bands, VHF and UHF am receivers, repeater COR and CWID units, simplex and repeater autopatches and DTMF decoders, and many other products related to VHF and UHF fm systems.

For a complete 40-page catalog of Hamtronics[™] products by return first-class mail, please send \$1 (\$2 for overseas mailing) to Hamtronics, Inc., 65-F Moul Road, Hilton, New York 14468-9535.

new interference suppression device

Computeradio has announced the availability of a new rfi suppression device, the TEXPRO Snap-On-Choke, which simplifies the application of an anti-interference technique that has long been appreciated by experts. Useful for minimizing interference to radios, TV sets, VCRs, TV converters, computers, digital data cables, telephones, process control and telecommunications systems, The TEXPRO Snap-On-Choke consists of a two-piece ferrite core and a plastic clamp. Its performance is similar to the toroidal ferrite cores, and is effective within a 0.5 to 200 MHz range. The choke can be clamped onto cables of a diameter up to 10 mm (0.4 inch) or can take



many turns of a thinner cable that will fit in the opening (9.9 x 21.6 mm). Installation does not require the removal of connectors or the unsoldering of connections — and doesn't void the warranty on equipment. A number of chokes can be snapped together if necessary.

The TEXPRO Snap-On-Choke is a "commonmode" choke that reduces radiation from the currents associated with cables — even shielded cables — acting as transmitting or receiving antennas. They can be used in place of a balun at the antenna feedpoint.

Single chokes are priced at \$4.00 each. A package of four costs \$15.00 plus \$2.00 for shipping. Chokes come with a specification sheet and installation instructions. If you're not satisfied, you can return them within 30 days for a refund (less shipping).

For more information, contact COMPU-TERADIO, Box 282, Pine Brook, New Jersey 07058.

Circle #308 on Reader Service Card.

computer-aided design

RF Notes No. 1, Version 3.0, aids in the design of resonant circuits, filters, basic stripline and microstrip projects, as well as cross-product and VSWR analysis. Version 3.0 incorporates improved schematic and graphics, in addition to allowing on-screen "what if" calculations. Priced at \$85, the fully menu-driven program is easy to use and includes tutorial sections.

For details, contact Etron RF Enterprises, P.O. Box 4042, Diamond Bar, California 91765.

Circle #309 on Reader Service Card.

five new antennas

Mirage has announced the release of five new antennas, including three omnidirectional antennas of a "closed J" design and two upgraded designs for 440 MHz designed with through-theboom elements rather than molded-on elements, for greater durability. ATV users will be especially interested in the 440-10X and 440-6X models, which were designed to replace the 440-6 and the 440-14.

Mirage will continue to replace parts and service older models. For details, contact Mirage/ KLM Communications Equipment, Inc., P.O. Box 1000, Morgan Hill, California 95037. Circle #310 on Reader Service Card.

novice "quick course"

In his new 21-day code and theory course, consisting of two long-play, stereo code cassettes and a fully illustrated Novice voice-class license preparation manual, Gordon West covers learning the code in a humorous and educational manner. The cassette code learning course is designed for students with absolutely no background in code copy.

Written by West and Fred Maia, W5YI, the accompanying manual includes every Novice class exam question, plus a thorough explanation of each as well as a discussion of each of the right and wrong answers. Several other chapters cover a detailed introduction to the Amateur Radio service.

Both the tapes and the book contain sections specifically for hams preparing administer the Novice test. An FCC Form 610 as well as a sample examination are included, as is a full-color ICOM frequency-band chart.



The course is available through local dealers or directly from Gordon West Radio School, 2414 College Drive, Costa Mesa, California 92626 for a total cost of \$19.95 plus \$2.00 for postage and handling.

Circle #311 on Reader Service Card.



AEA	BELDEN	ICOM.	NYE
ALINEO	BENCHER	JSC	PALOMAR
AMERITRON	BIRD	KANTRONICS	RADIO CALLBOOK
AMPHENOL	BUTTERNUT	KDK	RITRON
AMP SUPPLY	CENTURION	KLM	ROHN
ANTEN	CES.	LARSEN	TELEX/HYGAIN
ANTENNA	CUSHCRAFT	MFJ	TEN-TEC
SPECIALISTS	DIAWA	MINI-PRODUCTS	TRIO-KENWOOD
ASTRON	ENCORT/1	MIRAGE	UNADILLA/REYCO
B&W	HUSTLER	MOSELEY	YAESU

Write today for our latest Bulletin/Used Equipment List.

- 116

VISA

P.O. Box 73

182 North Maple Street

Watertown, SD 57201

PAKRATT - Model PK-232

AEA'S FINEST

CALL OR WRITE FOR SPECIAL QUOTE

Now Available - Especially For You!

California

A-TECH ELECTRONICS 1033 HOLLYWOOD WAY BURBANK, CA 91505 (818) 845-9203 New Ham Store and Ready to Make a Deal!

JUN'S ELECTRONICS

3919 SEPULVEDA BLVD. CULVER CITY, CA 90230 213-390-8003 800-882-1343 Trades Habla Espanol

Colorado

COLORADO COMM CENTER 525 EAST 70th AVE. SUITE ONE WEST DENVER, CO 80229 (303) 288-7373 (800) 227-7373 Stocking all major lines Kenwood Yaesu, Encomm, ICOM

Connecticut

HATRY ELECTRONICS 500 LEDYARD ST. (SOUTH) HARTFORD, CT 06114 203-527-1881 Call today. Friendly one-stop shopping at prices you can afford.

Delaware

AMATEUR & ADVANCED COMMUNI-CATIONS 3208 CONCORD PIKE WILMINGTON, DE 19803 (302) 478-2757 Delaware's Friendliest Ham Store.

DELAWARE AMATEUR SUPPLY 71 MEADOW ROAD NEW CASTLE, DE 19720 302-328-7728 800-441-7008 Icom, Ten-Tec, Microlog, Yaesu, Kenwood, Santec, KDK, and more. One mile off I-95, no sales tax.

Florida

AMATEUR ELECTRONIC SUPPLY 1898 DREW STREET CLEARWATER, FL 33575 813-461-4267 Clearwater Branch West Coast's only full service Amateur Radio Store. Hours M-F 9-5:30, Sat. 9-3

Ham Radio's guide to help you find your local AMATEUR ELECTRONIC SUPPLY 621 COMMONWEALTH AVE. **ORLANDO, FL 32803** 305-894-3238

Fla. Wats: 1 (800) 432-9424 Outside Fla: 1 (800) 327-1917 Hours M-F 9-5:30, Sat. 9-3

Georgia

DOC'S COMMUNICATIONS 702 CHICKAMAUGA AVENUE ROSSVILLE, GA 30741 (404) 866-2302 / 861-5610 ICOM, Yaesu, Kenwood, Bird... 9AM-5:30PM We service what we sell.

Hawaii

HONOLULU ELECTRONICS **819 KEEAUMOKU STREET** HONOLULU, HI 96814 (808) 949-5564 Kenwood, ICOM, Yaesu, Hy-Gain, Cushcraft, AEA, KLM, Tri-Ex Towers, Fluke, Belden, Astron, etc.

Idaho

ROSS DISTRIBUTING COMPANY 78 SOUTH STATE STREET PRESTON, ID 83263 (208) 852-0830 M 9-2; T-F 9-6; S 9-2 Stock All Major Brands Over 7000 Ham Related Items on Hand

Illinois

ERICKSON COMMUNICATIONS, INC. 5456 N. MILWAUKEE AVE. CHICAGO, IL 60630 312-631-5181 Hours: 9:30-5:30 Mon, Tu, Wed & Fri; 9:30-8:00 Thurs; 9:00-3:00 Sat.

Indiana

THE HAM STATION 220 N. FULTON AVE. EVANSVILLE, IN 47710 812-422-0231 Discount prices on Ten-Tec, Cubic, Hy-Gain, MFJ, Azden, Kantronics, Santec and others. SASE for New & Used Equipment List.

Maryland

MARYLAND RADIO CENTER 8576 LAURELDALE DRIVE LAUREL, MD 20707 301-725-1212 Kenwood, Ten-Tec, Alinco, Azden. Full service dealer. SAT 9-5 M-F 10-7

Massachusetts

TEL-COM, INC. 675 GREAT ROAD, RTE. 119 LITTLETON, MA 01460 617-486-3400 617-486-3040 The Ham Store of New England You Can Rely On.

Michigan

ATLANTIC SOLAR POWER/ENCON (SINCE 1979) 37677 W. SIX MILE RD. LIVONIA, MI 48152 (313) 591-7745 Solar Electric Power for Repeaters, Ham Shacks, Packet Radio. Call Paul, WD8AHO

Minnesota

TNT RADIO SALES 4124 WEST BROADWAY ROBBINSDALE, MN 55422 (MPLS/ST. PAUL) TOLL FREE: (800) 328-0250 In Minn: (612) 535-5050 M-F 9 AM-6 PM Sat 9 AM-5 PM Ameritron, Bencher, Butternut, ICOM, Kenwood

Missouri

MISSOURI RADIO CENTER 102 NW BUSINESS PARK LANE KANSAS CITY, MO 64150 (800) 821-7323 Missouri: (816) 741-8118 ICOM, Kenwood, Yaesu Same day service, low prices.

Nevada

AMATEUR ELECTRONIC SUPPLY 1072 N. RANCHO DRIVE LAS VEGAS, NV 89106 702-647-3114 Dale Porray "Squeak," AD7K Outside Nev: 1 (800) 634-6227 Hours M-F 9-5:30, Sat. 9-3

Dealers: YOU SHOULD BE HERE TOO! Contact Ham Radio now for complete details.

Imateur Radio Dealer

New Hampshire

RIVENDELL ELECTRONICS 8 LONDONDERRY ROAD DERRY, N. H. 03038 603-434-5371 Hours M-S 10-5; THURS 10-7 Closed Sun/Holidays

New Jersey

ABARIS SYSTEMS

276 ORIENTAL PLACE LYNDHURST, NJ 07071 201-939-0015 Don WB2GPU Astatic, Azden, B&W, Butternut, Larsen, Mirage/KLM, Kenpro, Nye, Santec, THL, and many others. M-F 10 am-9 pm SAT 9 am-7 pm VISA/MC

KJI ELECTRONICS

66 SKYTOP ROAD CEDAR GROVE, NJ 07009 (201) 239-4389 Gene K2KJI Maryann K2RVH Distributor of: KLM, Mirage, ICOM, Larsen, Lunar, Astron. Wholesale - retail.

New York

BARRY ELECTRONICS 512 BROADWAY NEW YORK, NY 10012 212-925-7000 New York City's Largest Full Service Ham and Commercial Radio Store.

VHF COMMUNICATIONS

915 NORTH MAIN STREET JAMESTOWN, NY 14701 716-664-6345 Call after 7 PM and save! Supplying all of your Amateur needs. Featuring ICOM "The World System." Western New York's finest Amateur dealer.

North Carolina

F & M ELECTRONICS 3520 Rockingham Road Greensboro, NC 27407 1-919-299-3437 9AM to 7PM Closed Monday ICOM our specialty — Sales & Service

Ohio

AMATEUR ELECTRONIC SUPPLY 28940 EUCLID AVE.

WICKLIFFE, OH 44092 (Cleveland Area) 216-585-7388 Ohio Wats: 1 (800) 362-0290 Outside Ohio: 1 (800) 321-3594 Hours M-F 9-5:30, Sat. 9-3

DEBCO ELECTRONICS, INC.

3931 EDWARDS RD. CINCINNATI, OHIO 45209 (513) 531-4499 Mon-Sat 10AM-9PM Sun 12-6PM We buy and sell all types of electronic parts. UNIVERSAL AMATEUR RADIO, INC. 1280 AIDA DRIVE

REYNOLDSBURG (COLUMBUS), OH 43068 614-866-4267 Featuring Kenwood, Yaesu, Icom, and other fine gear. Factory authorized sales and service. Shortwave specialists. Near I-270 and airport.

Pennsylvania

HAMTRONICS, DIV. OF TREVOSE ELECTRONICS 4033 BROWNSVILLE ROAD TREVOSE, PA 19047 215-357-1400 Same Location for over 30 Years

LaRUE ELECTRONICS 1112 GRANDVIEW STREET SCRANTON, PENNSYLVANIA 18509 717-343-2124 ICOM, Bird, Cushcraft, Beckman, Larsen, Amphenol, Astron, Belden, Antenna Specialists, W2AU/W2VS, Tokyo Hy-Power Labs, WELZ, Daiwa, Sony, Saxton, Vibroplex, Weller.

Tennessee

MEMPHIS AMATEUR ELECTRONICS 1465 WELLS STATION ROAD MEMPHIS, TN 38108 Call Toll Free: 1-800-238-6168 M-F 9-5; Sat 9-12 Kenwood, ICOM, Ten-Tec, Cushcraft, Hy-Gain, Hustler, Larsen, AEA, Mirage, Ameritron, etc.

Texas

MADISON ELECTRONICS SUPPLY 3621 FANNIN HOUSTON, TX 77004 713-520-7300 Christmas?? Now??

KENNEDY ASSOCIATES

AMATEUR RADIO DIVISION 5707A MOBUD SAN ANTONIO, TX 78238 512-680-6110 Stocking all major lines. San Antonio's Ham Store. Great Prices — Great Service. Factory authorized sales and service. Hours: M-F 10-6; SAT 9-3

MISSION COMMUNICATIONS 11903 ALEIF CLODINE SUITE 500 (CORNER HARWIN & KIRKWOOD) HOUSTON, TEXAS 77082 (713) 879-7764 Now in Southwest Houston—full line of equipment. All the essentials and extras for the "ham."

Wisconsin

AMATEUR ELECTRONIC SUPPLY 4828 W. FOND DU LAC AVE. MILWAUKEE, WI 53216 414-442-4200 Wisc. Wats: 1 (800) 242-5195 Outside Wisc: 1 (800) 558-0411 M-F 9-5:30 Sat 9-3

Invitation to Authors

ham radio welcomes manuscripts from readers. If you have an idea for an article you'd like to have considered for publication, send for a free copy of the ham radio Author's Guide. Address your request to ham radio, Greenville, New Hampshire 03048 (SASE appreciated).

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria Kann Ueber Posttach 2454 D.7850 Loerrach West Germany Ham Radio Belgium Stereohouse Brussetsesteenweg 416 B-9218 Gent Referent

Belgium Ham Radio Holland Postbus 413 NL-7800 Ar Emmen Holland

Ham Radio Europe Box 2084 S 194 02 Upplands Vasby Sweden Ham Radio France SM Electronic

SM Electronic 20 bis, Ave des Clarions F-89000 Auxerre France Ham Badio Germany

Ham Radio Germany Katin Ueber Postfach 2454 D-7850 Loerrach West Germany Canada Send orders to Ham Radio Magazine Greenville, NH 03048 USA Prices in Canadian funds 1 yr \$41 85, 2 yrs \$74.25 3 yrs \$99.90

Ham Radio Italy Via Maniago 15 I-20134 Milano Italy

Ham Radio Switzerland Karin Ueber Postfach 2454 D-7850 Loerrach West Germany

Ham Radio England c/o R S G B Lambda House Cranborne Road Potters Bar Herts EN6 3JW England



RATES Noncommercial ads 10¢ per word; commercial ads 60¢ per word **both payable in advance**. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing) on a space available basis only. Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (**not** all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N. H. 03048.

THE ORIGINAL HAM SACK. Deluxe soft padded case for all popular handhelds with battery packs. Three zippered compartments for radio, antenna and accessories including spare battery pack. Belt loops and detachable shoulder strap. Tough Dupont Cordura¹myNon. We are harms and we "know" you will like this case. Full refund guarantee. \$12.50 includes shipping. Frank & Linda Reed, KCIDM & NIEUR, 15A Daniel Webster Drive, Hudson, NH 03051.

AMPLIFIER BREAKTHROUGH The current amplifier drives loads push-pull without internal voltage gain. Fastest, quietest circuit in transistor electronics. Plans for quieter audio amplifiers, ideal for home builders, all wattages, \$15. Amplifiers Unlimited, Rt. 2, Box 139, Highmore, SD 57345.

HAM LICENSES SUPEREASY. Cut exam preps 50%. All classes. Free catalog. SASE. Bahr, 2549-H4 Temple, Palmbay, FL 32905.

SMART BATTERY CHARGER for gell-cells or lead acid batteries, by Warren Dion, W1BBH. See June '87 QST Magazine for circuit details. Complete kit, nothing else to buy, only \$49.95 plus \$3.50 s/h. Order #150-KIT. A & A ENGINEERING, 2521 W. LaPalma, Unit K, Anaheim, CA 92801. (714) 952-2114.

SELL: Amazing Mizuho SSB-CW Handheld. Mint \$125. Argosy. calibarator, crystal and audio filters, noise blanker. Mint \$325. KLM Echo II, 432 MHz SSB/CW factory preamp very fine \$185. MFJ Digi-Dial (counter becomes digital readout). New \$20. Century 21 Calibrator and circuit breaker with meter \$30. All guaranteed and UPS prepaid. WANT: Mocom-10, TIL 306, 308 readouts. Morsematic SSB squelch. WA6GER, 3241 Eastwood Road, Sacramento, CA 95821.

WANTED: WW2 Transceiver BC-654 (SCR 284) and PE-103 dynamotor. Also 1947/48 issues of Radio Craft and Radio & TV News magazines. E. Bircher, 108 Troy Drive, Slidell, LA 70461 (540) 649 7425.

COMPLETE STATION FOR SALE: Hammarlund HQ170A-VHF receiver, Hammarlund HX-50A transmitter, Mosley TA-33 Tri-Band antenna, Tri Ex MW-35 crank-up tower 135' extended), Shure 444 station mike, Ham-M-CDR rotor (needs minor repair) and Heathkit cantenna dummy RF load. Make offer for all or separate items; you ship. Call 301-948 0035 and leave name and number.

2M/1.25M/70CM MOBILE ANTENNA. The Austin Metro mobile provides tri-band operation with single 15" antenna atop car. \$62.45. (\$4.50 PH) including magnet mount. Ed Noll, W3GQJ, Sales Rep., PO Box 75, Chalfont, PA 18914. FULL NTS TRAFFIC MESSAGE FORMS FOR PACKET OR RTTY on your IBM PC. MESSAGE-PAC works with any communications program to give you full Message Forms and formatted script/macro command files, ready to transmit. This is the one you've been waiting for. With user defined Pop-Up Helg & Selection System that no one else offers. Can Pre-Load forms from disk. Only \$29.95. DEMO DISK for \$2.00. Write for information. Kalt and Associates, 2440 E. Tudor Rd, Suite 138, Anchorage, AK 99507. 907-248-0133. Charge Cards accepted.

WEST COAST SWAP SHEETS: Special introductory offer. SASE. WD6AFC, Bill, 4076 No. Hammel, Fresno, CA 93727.

ELITE + CODE PROGRAMS. Apple II + /c/e/GS. C-64/128. 37 modes. Graphics, wordprocessor, menus, lessons, speed techniques, dill, practice, print, teach, view modes; 1-100 WPM, variable sound, character, word spacing, and more. \$49,95. Check/MO. COD's add \$2. Other versions (\$14,95–\$44,95). \$3.50 demo disk gives \$2 off next purchase. Write: LARESCO, POB 2018, 1200 Ring Road, Calument City, IL 60409. 1-312-881-3279

ANALOG AND RF CONSULTING for the San Francisco Bay area. James Long, Ph.D N6YB (408) 733-8329.

APPLE COMPUTER p.d. Ham programs. Six disk sides: CW, OSCAR, logs, calcs, etc. \$9.00 pp. Cashier's check/m.o. WA7ZYQ, 238 Tenth, St. Maries, ID 83861.

TEST EQUIPMENT WANTED. Don't wait -- we'll pay cash for LATE MODEL HP, Tek, etc. Call Glenn, N7EPK, at Skagitronics Co. (800) 356-TRON.

auto-logs, sorts 7-band WAS/DXCC. Full features. Apple \$19.95, IBM or CP/M \$24.95. KA1AWH, POB 2015, Peabody, MA 01960.

RV OPERATORS are invited to check in Sun 2 PMC, 14.240 ± 5 . Tues, Thurs 8 PMC 3.880 ± 5 . Good Sam RV Net. Info SASE KJ4RO.

CHASSIS, CABINET KITS. SASE. K3/WK, 5120 Harmony Grove Road, Dover, PA 17315.

TELEVISION SETS made before 1946, early TV parts, literature wanted for substantial cash. Especially interested in "mirror in the lid" and spinning disc tv's. Finder's fee paid for leads. Arnold Chase, 9 Rushleigh Road, West Hartford, Conn. 06117. (203) 521-5280.

ENGINEERS request free catalog of Electronics Software. Circuit analysis, filter design, graphics, etc. BV Engineering, 2200 Business Way, Suite 207, Riverside, CA 92501 (714) 781-0252.

NJ-NJ-NJ-NJ-NJ-NJ-NJ-NJ A Full-Service Ham-SWL-CB-Scanner store in NJ. Discount Grand Opening Prices. Top performing radio systems for every budget. New 10 meter and VHF/UHF rigs. ARRL, Amphenol, Astatic, Astron, Azden, BW, Bilal Belden 9913, Butternut, Clear Channel, KLM, Larsen, MFJ, Mirage, Mil Spec Cables, much more. Open M-F 10 AM-9PM. Sat 10 AM-7 PM. Buy and self used gear and have qualified repair facility. ABARIS SYSTEMS, 276 Oriental PI, Lyndhurst, NJ 07071 (201) 939-0015.

IBM-PC RTTY/CW. New CompRtty II is the complete RTTY/CW program for IBM-PC's and compatibles. Now with larger buffers, better support for packet units, pictures, much more. Virtually any speed ASCII, BAUDOT, CW. Text entry via built-in screen editor! Adjustable split screen display. Instant mode/speed change. Hardcopy, diskcopy, break-in buffer, select calling, text file transfer, customizable full screen logging, 24 programmable 1000 character messages. Ideal for MARS and traffic handling. Requires 256k PC or AT compatible, serial port, RS-232C TU. \$65. Send call letters (including MARS) with or der. David A. Rice, KC2HO, 25 Village View Bluff, Ballston Lake, NY 12019.

REMEMBER TROLLEY CARS? Trolley Treasures: The Wartime Years in New Jersey (1939-1947), a 4-volume photodocumentary history, includes 1600 unpublished, original photographs plus extensive historical notes. Volume I, The Compromise Roof Cars of Public Service Coordinated Transport, ready now. SASE for details. To order, contact Trolley Themes, A.W. Mankoff, 2237-3 Woodside Lane, Sacramento, CA 95825. (\$14.95 plus \$1.50 S&H).

SSSSSUPER SAVINGS on electronic parts, components, sup plies and computer accessories. Free 40-page catalog for SASE. Get on our mailing list. BCD ELECTRO, PO Box 830119, Richardson, TX 75083 or call (214) 690-1102.

RTTY JOURNAL—Now in our 35th year. Join the circle of RTTY friends from all over the world. Year's subscription to RTTY JOURNAL, \$10.00, foreign \$15.00. Send to: RTTY JOUR-NAL, 9085 La Casita Ave., Fountain Valley, CA 92708.

NEED YAESU READOUTS: Texas Instruments TiL-306, TIL-308. R110 GRC Schematic. Want ICOM DV-21 VFO. Wagger, 3241 Eastwood Rd, Sacramento, CA 95821.

IMRA International Mission Radio Association helps missionaries. Equipment Ioaned. Weekday net, 14.280 MHz, 2-3 PM Eastern. Eight hundred Amateurs in 40 countries. Brother Frey, 1 Pryer Manor Road, Larchmont, New York 10538.

ANTENNAS G5RV Kit \$29.95, KT5BA Multi-Band Ant. 160M-10M only \$49.95, Antenna accessories, roller inductors, bal-Feed line, coaxial cable weather boot kit \$9.50 and MUCH MOREI To order call (805) 646-9645, For catalog write Kilo-Tec, Box 1001, Oak View, CA 93022. HOMEBREW PROJECTS LISTS. SASE, WB2EUF, Box 708, East Hampton, NY 11937.

FOR SALE: All new RCA 6816, RCA 8072, Eimac 8560A, Sucket, Berylium oxide block, heat sink. 2- 4CX250B screen rings and ceramic chimneys. Richard Stevens, POB 118, Ashuelot, NH 03441, 16031 239-6079.

RUBBER STAMPS: 3 lines \$4.50 PPD. Send check or M0 to G.L. Pierce, 5521 Birkdale Way, San Diego, CA 92117. SASE brings information.

ELECTRON TUBES: Receiving, transmitting, microwave... all types available. Large stock. Next day delivery, most cases. DAILY ELECTRONICS, PO Box 5029, Compton, CA 90224. (213) 774-1255.

CUSTOM MADE EMBROIDERED PATCHES. Any size, shape, colors. Five patch minimum. Free sample, prices and ordering information. HEIN SPECIALTIES, Inc., Dept 301, 4202 N. Drake, Chicago, IL 60618.

RECONDITIONED TEST EQUIPMENT \$1.25 for catalog. Walter, 2697 Nickel, San Pablo, CA 94806.

COMING EVENTS Activities — "Places to go"

SPECIAL REQUEST TO ALL AMATEUR RADIO PUBLICI-TY COORDINATORS: Please indicate in your announcements whether or not your Hamfest location, classes, exams, meetings, flea markets, etc, are wheelchair accessible. This information would be greatly appreciated by our brother/sister hams with limited physical ability.

MAINE: September 12. Windsor Hamfest, sponsored by the Augusta Emergency Arnateur Radio Unit. Southern Kennebec Agricultural Society Fairgrounds, Windsor. Flea Market, outdoor spaces free, indoor tables available. Forums, distributors, Saturday night homebaked beans and casseroles. Gate donation \$2.00. Overnight camping \$3/night or \$5/two nights. Talk in on W1TLC 146.22/82 repeater. For information: Phil and Dot Young, W2JTH and W1TGY, 47 Longwood Avenue, Augusta, ME 04330. Telephone (207) 622-1385.

TENNESSEE: August 30. The Lebanon Hamfest sponsored by the Short Mountain Repeater Club, Cedars of Lebanon State Park, US 231, 7 miles south of Lebanon. All outdoors. Bring your own tables. Food and drinks available. For further information contact Mary Alice Fanning, KA4GSB, 4936 Danby Drive, Nashville, TN 37211.

INDIANA: August 16. The Lafayette Hamfest, Tippecanoe Co. Fairgrounds, on Indiana 25 in Lafayette. Indoor setup 5 PM to 8:30 PM EST Saturday night. No overnight camping on fairgrounds. Outdoor setup 5 AM.

OHIO: September 27. The Cleveland Hamfest Association's annual Hamfest and Computer Show, Cuyahoga County Fairgrounds, Berea. Doors open 8 AM to 4 PM. Early setup 6 AM. VE exams 9 AM. Tech forums and non-ham activities all day. Talk in on 146.52. Admission 33.50 advance; \$4.00 at the gate. Inside tables \$10. Outside flea market \$4.00. Saturday night banquet. For more information write C.H.A., POB 81252, Cleveland, OH 44181-0252.


COLORADO: August 8. The Ski Country ARC will host its 6th annual Hamfest in conjunction with the Colorado Council of ARC summer meeting, CMC Building, 1402 Blake Avenue, Glenwood Springs. 9 AM to 3 PM. Admission free. Tables \$5. Refreshments and lunch available. VE exams 9 AM. Videotapes, packet and AMSAT demos. For information contact Bob Ludtke, K9MWM, 406 Yale Circle, Glenwood Springs, CO 81601. (33) 945-8722.

ALABAMA: August 15 and 16. The Huntsville Hamfest and ARRL State Convention, Von Braun Civic Center, 700 Monroe Street, Huntsville. 9 AM to 5 PM Saturday. 9 AM to 3 PM Sunday. Amateur exams August 15 by CAVEC. Walk ins welcome. Flea market, dealers/distributors and non-ham activities. All airconditioned. No admission fee. Light refreshments available. Talk in on .34/.94. For further information contact Gwin Givens (205) 883.2760 or Don Tunstill (205) 536-3904.

OHIO: September 13. The Findlay Hamfest, Hancock County Fairgrounds, Findlay. Doors open 8 AM. Admission prior to 9/1 \$3.00. After 9/1 \$4.00. Flea market spaces \$4.00 at door. Reserved indoor tables \$6.00. For tickets and table reservations send check and SASE to FRC Hamfest, POB 587, Findlay, OH 48839.

WASHINGTON: August 22-23. The Radio Club of Tacoma presents Hamfair '87 and the ARRL Northwestern Division Convention, Pacific Lutheran University, Tacoma, Friday evening entertainment. Doors open 9 AM August 22. Registration 55.00 til August 12. \$6.00 at the door. Banquet \$10.00 by August 12. RV spaces 20.00. No hookups. Technical seminars, forums. Ifea market (tables \$18/6') non-ham activities, VE exams all classes. For reservations and/or flea market tables write AI Wittich, KA7SBJ, 3832 Gay Rd E. Tacoma, WA 98443 or call Bill Morgan, W7GRP (206) 531-3821 or Marion O'Neal, WB7SQU (206) 838-3126.

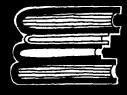MISSOURI: September 13. The Ozarks Amateur Radio Society will hold its 6th annual Ozarks Club Congress and Swapfest, City Park in Monett. Tailgating starts 9 AM. Potluck dinner (continued on page 92)



ELMER'S NOTEBOOK

oops!

Thanks to K4TG for pointing out an error, Please see the "short circuit" at the end of this month's column.

outguessing the ionosphere

From what I've been hearing on the bands and reading in newsletters and magazines, the 10-meter band ushered in the era of Novice Enhancement with an impressive demonstration of the fun it can provide. Reports abound of Novices working some terrific DX, and the enthusiasm shown by the lucky operators has been truly contagious. This is a perfect time for you Novices to get acquainted with Garth Stonehocker's "DX Forecaster" column in this magazine and make some notes about what you've heard or worked. You can then check against the column to build up a "prediction data base" for your location. Many an old hand at the Amateur game considers the thrill of outguessing the ionosphere to be as gratifying as collecting the QSL cards from the DX they've worked.

We'll continue last month's discussion of digital communications next month; in this column, we'll take a look at 220 MHz, a band that's sure to provide plenty of exciting local communications.

220 MHz: background

Years ago, Amateurs had a band known as 2-1/4 meters, or 112 MHz. A natural offshoot of this was another experimental band at 224 MHz - I say "natural" because the common practice was to use harmonics of lower frequencies to generate output on the VHF and UHF bands. Later, the 2-1/4 meter band was changed to 2 meters (144 MHz), but 224 remained unchanged, and the harmonic relationship obviously fell apart.

At the time, only true experimenters were willing to invest the time and money necessary to build separate stations for the 220-225 MHz "orphan." The appearance of surplus commercially made fm equipment on the 2-meter band encouraged manufacturers to produce equipment that would lead to our present crop of compact, solid-state, VHF-fm and all-mode rigs: the 220-MHz band, however, remained of little interest to most manufacturers - partly because of its very low occupancy, which was brought on by repeated attempts by government and commercial interests to grab all or part of the band for their use.

These attempts are still being made and fought off. There's an important difference, however, in that there's immensely greater occupancy now, and there will be more activity as Novices learn to use this part of the spectrum to its full potential. Consequently, finding equipment for 220 MHz won't be a problem.

equipment

A visit to any Amateur equipment dealer or a scan through Amateur publications will show that there are plenty of rigs to choose from. Among the most obvious are Kenwood's TM-3530A mobile and TH-31BT/31A handheld; Icom's IC-375A base station,

Tom McMullen, W1SL

IC-37A and IC-38A mobile units, plus their IC-03AT and IC-3AT hand-helds; and Yaesu's FT-109RH hand-held. There will undoubtedly be more models available soon — perhaps even before you read this. Repeaters, too, are being manufactured for Amateur 220 MHz use.

While I'm talking about equipment, let me point out that a rig advertised as a mobile unit can be used as a base station too. A good (i.e., well filtered) power supply that provides the required 12 volts dc at sufficient current will afford many hours of home use. In fact, many operators get double duty out of their rigs by operating them both at home and in their cars. Some have done as I have -i.e., installed a newer mobile rig with more bells and whistles in the car, then put the older one to work at home.

antennas

Every major manufacturer of Amateur antennas offers models for the 220-MHz band. They're available in the form of beam (Yagi) antennas, groundplane antennas, magnet-mount and fixed-mount mobile whips of various sizes, and the ubiquitous "rubberduckie" that's so useful for portable and hand-held use.

Making your own antennas is always fun, however, and the size of the elements required for 220 MHz makes doing so much easier. Anything from new aluminum rod or tubing to salvaged TV antenna parts can be used to produce high-performance antennas that will let you extend your 220-MHz contacts to ever-expanding distances. You can find directions and 12:30. Special activities throughout the day. Free coffee and soft drinks provided by the Club Talk in on 146 37/97 Free admission

INDIANA: August 2. The Porter County ARC presents the Northwest Indiana Hamfest and Computer Fair, 49 er Drive-In Theater, Rt. 49, north of Valparaiso. Gates open 7 AM. 6 AM for vendors. Admission 83.00. Children under 12 free. VE test-ing, food available. Free parking. Many beautiful area attrac-tons. Talk in on 146.775/175 and 145.45/144.950. For further information: Rich Stahl, K9LBO, POB 1782, Valparaiso, IN 45992 46383

WASHINGTON: August 22 and 23. The Radio Club of Tacoma presents Hamfair '87 and the ARRL N.W. Division Convention, Pacific Lutheran University, Tacoma. Friday evening entertain-ment for early arrivers. Doors open 9 AM on 8/22. Flea Market, commercial exhibits, VE testing, all classes. Registration 55.00 until August 12. \$6.00/door. Banquet \$10.00 by August 12. Flea market tables \$18/6' includes one reservation. For reservations and/or flea market table write Al Whitch, KA75BJ. 3832 Gay Road, E, Tacoma, WA 98443 or call Bill Morgan, W7GRP (206) 531.3821 or Marion O'Neal, WB7SQU (206) 838-03126.

IOWA: August 1 and 2. Summerfest '87 sponsored by the Ce-dar Valley ARC, Five Seasons Center, downtown Cedar Rapids. 8 AM to 5 PM Saturday and 8 AM to 3 PM Sunday. Admission 55 adult; 33 student advance. \$6 adult, \$4 student at the door. Seminars, FCC exams, vendors, flea market and non-ham activ-ities. For information/reservations Duane Rinderknecht, 2825 – 23 Avenue, Marion, Iowa 52302. (319) 277-2761 days. (319) 377-2761 nights.

TEXAS: August 7-9. Austin SummerFest, sponsored by the Austin ARC and Austin Repeater Organization, Villa Capri Mo-tor Hotel, 2400 North Interstate 35 near center of Austin, Intor Hotel, 2400 North Interstate 3b near center of Austin. In-door flea market, ARRL forum, tech program transmitter hunt and VE exams for all license classes. Saturday evening barbeque and Midnight Wouff Hong ceremony. Non-ham arts and crafts and Austin Agua Festival available during convention. General registration \$5 advance; \$7/door. Children 15 and under free. To register write Austin SummerFest, PO Box 13473, Austin, 7x 78711. TX 78711

MISSOURI: August 23. The St. Charles ARC will sponsor Ham-fest 87 at Blanchette Park, St. Charles. 6:30 AM to 3:30 PM. Free admission and parking including handicapped spaces. 92. donation requested for tailgate flea market. Food available. Forums and FCC license exams at 10 AM. Taik in on 146.07/67 repeater and 146.52 simplex. Contact Firc Koch, NF00, 2805 Westminister, St. Charles, MD 63301 (314) 946-0948.

ONTARIO: September 19. The Hex-9 Group of the Barrie Ama-teur Radio Club is holding its third PACKET RADIO SYMPOSI-UM co-sponsored by and held at Georgian College, Barrie. Talks for beginners at 9:30 AM. Main discussions start 1 PM. Regis-tration \$5.00. Inquire Hex-9 Group, Box 254. Barrie, Ontario, L4M 4T2. Pre-register via packet VE3FJB-1.

OHIO: August 23. The 11th annual Marysville Hamfest and Com-OHIO: August 23. The 11th annual Marysville Hamtest and Com-puter Show, Marysville Fairground. Admission \$3.00 advance: \$4.00 at the gate. Giant flea market. Free overnight camping available on grounds. Free entertainment Saturday night plus good food and lots of fun. For further information or tickets write Gene Kirby, W8BJN, 13613 US 36, Marysville, OH 43040 (513) 644-0468

KENTUCKY: August 9. The Central Kentucky ARRL Hamfest sponsored by the Bluegrass Amateur Radio Society, Scott Coun-ty High School, Longlick Road and US 25, Georgetown. 8 AM to 4 PM. Tech forums, license exams, awards and commercial exhibits in air conditioned facilities. Free outdoor flea market space with paid admission. Tickets \$5/advance; \$6/gate. Talk in on 146.16/76 repeater. For information or tickets SASE to Bill DeVore, N4DIT, 112 Brigadoon Parkway. Lexington, KY Ansna 40503

TEXAS: August 8-9. The Panhandle Amateur Radio Club's 13th annual PARC-Golden Spread Hamfest, Inn of Amarillo, 601 Amarillo Blvd West, Amarillo. Stars 9 AM both days. Pre-registration \$5 Admission at door \$6. Distributors, dealers, flea market tables \$5. VE testing, walk ins only, both days. For more information write PARC Hamfest, Box 10221, Amarillo, TX

1987 "BLOSSOMLAND BLAST" Sunday, September 20, 1987. Write "BLAST" PO Box 175, St. Joseph, MI 49085.



OPERATING EVENTS "Things to do . . .'

August 2: The South Hills Brasspounders and Modulators will operate W3PIQ to commemorate their 50th Hamfest and 200th anniversary of Allegheny County. 20, 15 and 10 meter General phone bands. For certificate QSL and SASE to Bill Gardiner, N3DXE, 4756 Child Drive, Pittsburgh, PA 15236.


August 16: The Arapahoe Radio Club will operate from sever-al of Colorado's 14,000-ft mountain peaks. 1000-12000 MDT (1600-1800 UTC). SSB on 14.285 MHz. CW 14.060 MHz. A cer-tificate will be available tisting all Colorado Fourteeners Opera-tions with checkoff of all stations worked. A special memento will be sent to any station working all Fourteener stations. Send OSL and legal SASE to K9AY, 7277 S. Clermont Drive, Little-ton, CO 80122.

September 6: The Schaumburg Amateur Radio Club will oper-ate WB9TXO from the Schaumburg Septemberfest site from 1500-20002. Suggested frequencies 7.250, 14.250 and 28.400 MHz. For a confirming certificate send QSL to SARC, POB 68251, Schaumburg, IL 60168-0251.

August 1-23. Special event station W9PAX (W9 Pan Ameri-August 1-23. Special event station WPAA (W9 PAA Met) can Ten) will operate during the 10th Pan American Games be-ing held in Indianapolis, August 7-23. For additional information contact Cornelius M. Head, WB3ZOE, 9046 Mercury Drive, In-dianapolis, IN 46229. (317) 263-5281 (0) (317) 898-2792 (H).

September 5. The Old Pueblo Radio Club of Tucson will spon-September 5. The Old Pueblo Radio Club of Tucson will spon-sor the 6th annual Labor Day Special Event Station W7GV from the OK Corral in Tombstone, Arizona, site of the famous shootout between the Earps and the Clantons in 1881. On new Novice/Tech 10 meter SSB frequencies. 00002 September 5 to 2002 September 7. For more information contact Bill Croghan, WB0KSW, 1854 W. Dominy Street, Tucson, A2 85713. (602) 622-1535 622-1535

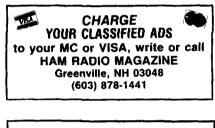August 29: The Antietam Radio Association will operate spe-cial event station W3CWC to celebrate the 25th anniversary of the club. 80,40,20,15 and 10 meters phone, CW and RTTV. For a commemorative certificate send OSL and legal SASE to Spe-cial Events Station W3CWC, Antietam Radio Association, Inc., POP 52 Homestraw, MD, 21741 POB 52, Hagerstown, MD 21741.



HAM DATA C-64 Software

SUPER LOG

Super log gives you all the advantages of a com-puterized data base without significantly changing the traditional log format. For contesters, Super Log can be configured to either manually or automatically enter contact number as well as time of contact. Make an error and you can easily go back and edit the entry. Super Log also allows you to print out either selected contents or the whole log. Will print **OSLs**

\$19.95

LIHD-SL (For C-64)

CONTEST LOG

This disk contains four different contest programs; ARRL Sweepstakes, Field Day, Universal WW Contest log, plus a dupe checking routine. Each program is designed for real time use. It automatically enters date, time, band and serial number for each contact. A 24-hour clock is displayed at the top of cach contact. Screen. When the contest is over, the program will print your results listing all duped and scored con-tacts in serial sequence with all the necessary infor-mation as well as completed score at the bottom of the page. \$24.95

HD-CL (For C-64)

MASTER LOG

Over three years of development went into this pro-gram. It creates a file of 2100 individual records with up to 13 different entries per record. Master Log can do a search and select based upon time, parameters. It keeps track of DXCC and WAS status, prints QSL labels and can search its whole file in less than 5 seconds! Complete documentation is included to help you learn and use this truely stateof-the-art logging program. \$28.95 HD-ML (For C-64)

The Please enclose \$3.50 for shipping



ew Books

ARRL OPERATING MANUAL

This book has been completely revised and up-dated! Over 600 pages are crammed full of the information every ham should have at their fingertips. In addition to message handling, emergency operating, repeaters and contesting, this book includes sections written by noted DX'ers W9KNI and WB4ZNH, a new section on packet radio and over 60 pages in full color describing operating awards from around the world. © 1987 688 pages.

AR-06

Softbound \$14.95

TRANSMISSION LINE TRANSFORMERS by Jerry Sevick, W2FMI

Contains a complete explanation and discussion of transmission line transformers and how to use them. Written by one of the experts in the field-this book is full of helpful information. ---- 1987 1st Edition 144 pages AR-TLX

Saftbound \$9.95

THE BUYER'S GUIDE TO AMATEUR RADIO by Angus McKenzie, G3QSS

All currently available radios are reviewed. This new book from the RSGB is an invaluable aid in evaluating which radio best suits your personal operating needs. Author McKenzie spent hundreds of hours testing and measuring each radio's operating para-meters—over 10,000 measurements and 500 analyzer plots were made. Equipment was also subjected to many hours of on-the-air testing by hams throughout the UK and around the world. There are more than 100 full equipment reviews and nearly 100 more products with brief reviews. (c) 1986 472 pages. RS-BG

Solibound \$11.95

TUNE IN THE WORLD WITH HAM RA-**DIO** by ARRL staff

NOW INCLUDES TWO C-90 CODE STUDY TAPES! This package has been revised to cover new digital & voice Novice requirements and contains THE goodies needed by the beginner to get started in Amateur Radio. Assuming that you have no prior knowledge of radio, the reader is taught how to pass the Novice exam, both code and theory, and how to set up a station. Unique code study method makes learning the Morse code easy as 1-2-3. And it's full of illustrations to help clarify difficult technical points, 160 pages © 1987 7th edition. AR-HR

Softbound \$14.95

1987-88 ARRL REPEATER DIRECTORY

- Fits in your shirt pocket 3¼" x 5¼"
 Over 12,000 listings from 28 MHz to 10 GHz
- · Latest info on all repeaters

 Now includes digipeaters Also includes CTCSS (PL) tone chart, VHF/UHF and Repeater Advisory committee addresses, special mode repeaters (packet and ATV) band plans, repeater operating practices. ARRL Frequency Co-ordinators, and Special Service Clubs. AB-BD87

Softbound \$4.00

MORSE CODE TRAINER (for the Apple II) by David Fahnestock

This new program turns your Apple II into a com-plete 5-25 wpm code trainer. You can configure the program to generate random code groups, transmit letters from the keyboard in learning mode and output to either the computer's speaker or to a cassette tape recorder. Elegant in its simplicity and a great value to either students or new hams looking to improve their code proficiency. © 1986.


HR-MCT (Apple II) Introductory price \$9.95

ENGLISH SHORTWAVE BROADCASTS (MS-DOS) by Tom Sundstrom, W2XQ

Here's a new two disk MS-DOS program and database that provides you with one of the most thorough listings of English shortwave broadcasts available Allows you to search by time, frequency or by country and print your findings. A quarterly up date is available from the author for just S6 includ-ing shipping. Super value to SWL's and Harris alike. Should sell for many times more what is being charged Up-dated regularly-latest version will be shipped \$19.95 TS-SWL (MS-DOS)

Please enclose \$3.50 shipping & handling

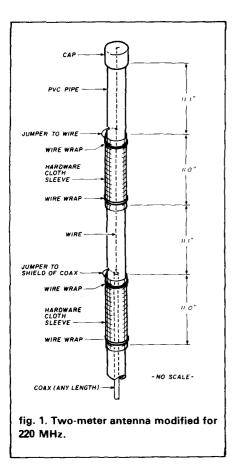ham radio BOOKSTORE GREENVILLE, NH 03048 603-878-1441



formulas for building antennas in many handbooks; just drop a note or postcard to *ham radio's* Bookstore and ask for a catalog.

An increase in coverage that's especially useful for simplex operation can be obtained by using an antenna that's larger in terms of wavelength; a halfwave 220-MHz antenna is only seven inches longer than a quarter-wave whip for 144 MHz, and has more gain and a better angle of radiation from a car-top location. A 5/8-wave antenna element for 223 MHz is approximately 33 inches long, compared with 50 inches for 146 MHz. This difference in size isn't visible in most mobile antennas because a loading coil in the base of the antenna allows a shorter 2-meter radiator to perform as if it were 5/8wavelength; it will be apparent, however, in home-station antennas such as multi-section verticals or ground-plane types with 5/8-wave vertical radiators.

A neat 2-meter antenna was described in Bill Orr's column in the

May, 1987 issue of ham radio (see page 55). A few minutes with a calculator produced some dimensions that will let you adapt the 2-meter design for 220 MHz; see fig. 1. Note that neither version has elements that are exactly one-quarter or one-half of a free-space wavelength. A quarterwave in space at 144 MHz is approximately 20 inches; at 223 MHz, it's approximately 13.2 inches. When you allow for the capacitive loading at the end of the elements, the coupling to the wire mesh "sleeves," and the dielectric effects of the PVC tubing, the element dimensions get shorter.

distances

The normal operating range of stations on the 220-MHz band is amazingly close to what can be expected on 2 meters. Well-located repeaters with good antennas can provide coverage that's virtually identical to 144 MHz. And because of the short space a wavelength occupies, peaks and nulls in signal strength experienced by stations in motion in urban or weak-signal areas aren't as bothersome at 220 as they might be at 144 MHz. There's also more "fill" of shadowed areas because of the slightly increased reflectivity of many materials at 220 MHz - but by the same token, many materials absorb 220 MHz more readily, thus causing some signal loss.

the ins and outs of repeaters

Band plans allow orderly occupancy of our sometimes crowded VHF spectrum and provide a basis for compatibility among various makes of fm transceivers and the repeaters through which they work. There's been a band plan for 220 ever since repeaters began appearing in VHF circles. Rather than use a lot of space to reproduce the entire 220-MHz band plan here, I'll just make a few comments about it.

The separation between a 220-MHz repeater's input and output frequencies is 1.6 MHz. When you transmit on 223.10 MHz from your mobile or handheld rig, the repeater retransmits your signal on 224.70 MHz; this higher frequency is where your receiver is listening. Don't worry about 224.70 being out of the Novice "band"; this type of operation is authorized by the FCC. At 223.10, your transmitter is operating within the limits of the Novice subband, which is what counts. (Novices beware: be sure that you never transmit "direct" on the repeater's output frequency. Never use the "reverse" or "inverted" mode of operation that's available on many current rigs.)

The band plan allows for 20 kHz between each repeater input; for example, 223.02, 223.04, 223.06, and so on. Each input has its corresponding output 1.6 MHz higher. There are a few "gotcha's," though. In some areas, 223.4 is designated as an input frequency. But if you add 1.6 to 223.4, you get 225.0. Obviously, you can't have a repeater output on the very edge of the band, so watch out for that one. In some areas, repeater input and output frequencies are reversed by local agreement; this usually means that the input is somewhere near the current input range, but the output of the repeater is 1.6 MHz lower.

Many simplex frequencies have been agreed upon, starting at 223.40 or 223.42 MHz and occurring every 20 kHz up to 223.88 or 223.90 MHz. Many stations use 223.50 MHz as a calling frequency to establish initial contact, then move to another simplex channel for a QSO.

This arrangement of repeater frequencies and simplex channels could change, however. Novices will no doubt want to use other modes such as CW, SSB, or packet in their segment of 220 MHz, and some changes will have to be worked out to accommodate them. I'll keep you abreast of changes in this column. For a listing of current repeaters and band plans on 220 MHz (and others), try *The ARRL Repeater Directory* — a neat, pocketsized little guide that's been a bestseller everywhere. Again, ham radio's Bookstore has it.

For any of you who'd like to exercise your computer, **fig. 2** shows a short program that will generate a printout of common repeater and simplex



5 LPRINT "REPEATER AND SIMPLEX FREQUENCIES"
10 LPRINT "IN THE 220-MHz BAND"
15 LPRINT
20 A≈222.28
30 B=224.98
40 =0
50 FOR I=1 TO 150 STEP 1
60 A = A + .02
65 A≈INT(A*100)/100
70 IF A<223.4 THEN PRINT A;"INPUT":LPRINT A;"INPUT"
75 IF A<223.9 AND A=>223.4 THEN PRINT A;"SIMPLEX":LPRINT A;"SIMPLEX"
80 IF A=<225 AND A=>223.9 THEN PRINT A;"OUTPUT":LPRINT A;"OUTPUT"
85 IF A=B THEN 100
90 NEXT
100 END
fig. 2. This short program generates a printout of common repeater and simplex fre- quencies on 220 MHz.

frequencies on 220 MHz. I've found that it works without line 65 on the Radio Shack TRS-80[®] Model III and their PC-5 Pocket Scientific Computer. When used on an IBM PC® or compatible, however, the algorithm used in the computer causes it to "round up," which adds two extra decimal places! Line 65 takes care of that glitch. I haven't tried it on other computers, but it's a simple BASIC program that should be easy to translate. The printout will be approximately 2-1/2 pages long.

ham radio

short circuit novice privileges

Because of a profusion of announcements early in the Novice Enhancement program, I used information about Novice privileges on the 10meter band from a bulletin that was erroneous and missed a later correction. As a result, the information depicted in fig. 1 of the June, 1987 column (page 95) is incorrect.

The correct Novice 10-meter modes and segments are: CW and digital, 28,1 to 28.3 MHz; CW and voice, 28.3 to 28.5 MHz. - W1SL



CALL FOR FREE BROCHURE OF MORE COMPUTER SUPPLIES (305) 551-4023 HOURS: 10 AM - 7 PM EST Mail to: World Data Enterprises P.O. Box 652737, Miami, FL 33265

.62

25

40

– PRICE PER DISK –

BULK DISKS 5.25" DSDD-RH

LIBRARY CASE -HOLDS 10 DISKS 1.99

QVS FILE BOX -HOLDS 75 DISKS 8.50

FLIP-N-FILE BOX -HOLDS 100 DISKS ... 15.95

.58

50-400

.38

.55

425-1000

.37

Uncle Bill's Commodore C-64 Computer Software by Bill Clarke WA4BLC

magazine M

CODE COURSE

This computer program is broken into three user friendly parts. Part one introduces to the beginner the different morse characters. The student simply presses a key and the character is sent and displayed on the screen. Part two generates the morse character and the student is required to press the correct key on the computer. If the student answers incorrectly, the character is automatically resent. Part three sends morse characters in random groups of five. The student can tailor what is sent to their particular needs; numbers only, letters only or a combination of both. Speeds are from 5 to 20 groups per minute. The computer can also be configured to send the Farnsworth method (high speed/ slow spacing code.) V 2.2 UB-CC (For C-64) \$9.95 **KODE MASTER** (for Novice, General or Extra Class students) Prepare for your next code exam

using computer generated QSOs. Each QSO contains callsigns, names, OTH's equipment info plus many of the other exchanges commonly found in Ham QSO's. QSO's can be displayed on the screen by one character at a time, by each sentence or after the completion of the QSO for checking. With a printer you can print out a hard copy Available in 5 wpm for Novices, 13 wpm for Generals and 20 wpm for Extra class students.

UB-KN Novice Class (for C-64)\$14.95 \$14.95 UB-KG (for C-64) UB-KE Extra Class (for C-64) \$14.95

ANTENNA SYSTEM


This nifty antenna modeling and development program will help you get the most from your antenna projects while eliminating much of the drudgery of antenna calculations. Part one covers standard design antennasdipoles, verticals and Yagi designs. Part two designs shortened dipole antennas for space limited nams. Great for shortened 160/80 meter antennas. All dimensions are listed. At this price it's not an engineering program but a neat program to have around. UUB-AS (for C-64)

XIDEX

DSDD


\$9.95

RADIO AMATEUR CALLBOOK SUPPLEMENT

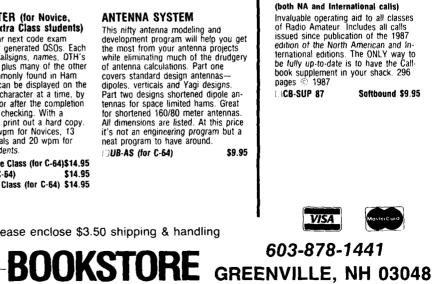

Please enclose \$3.50 shipping & handling

ACCURACY	DIGIMAX	PERFORMANCE

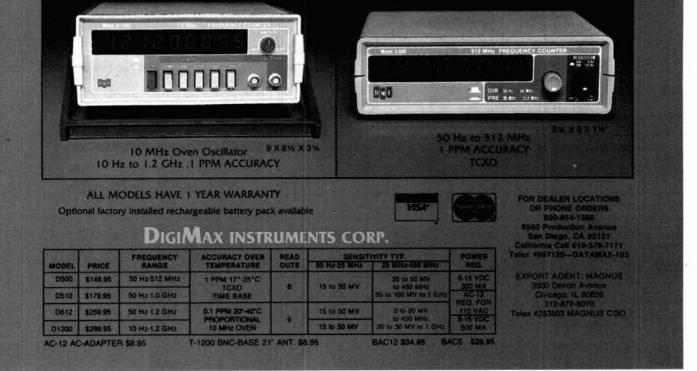

✓ 106

USA



delivered


Covers 100 MHz to 199.999 MHz in 1 kHz steps with thumbwheel dial • Accuracy +/- 1 part per 10 million at all frequencies • Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate • External FM input accepts tones or voice • Spurs and noise at least 60 dB below carrier • Output adjustable from 5-500 mV at 50 Ohms
Operates on 12 Vdc @ ½ Amp • Available for immediate delivery • \$429.95 delivered • Add-on accessories available to extend freq range, add infinite resolution, AM, and a precision 120 dB attenuator • Call or write for details • Phone in your order for fast COD shipment.

VANGUARD LABS


196-23 Jamaica Ave., Hollis, NY 11423 Phone: (718) 468-2720 Mon. thru Thu.

J 107



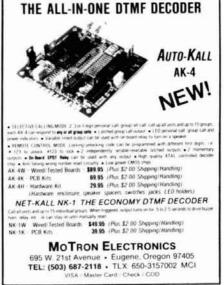

► 109

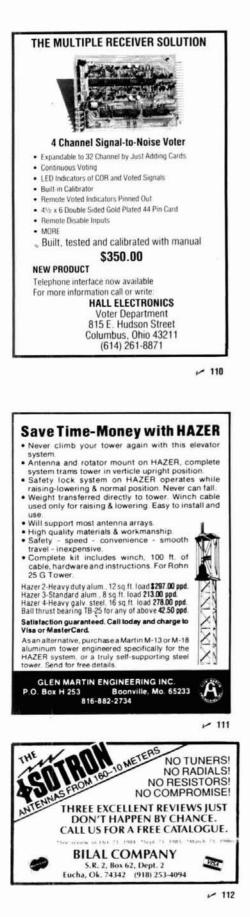





1 YR - \$22.95 2YRS - \$38.95

3 YRS - \$49.95 Prices U.S. only





DATATEL 800"

800-341-1522

Weekdays 8 AM - 9 PM EST • Saturdays 9 AM - 5 PM EST IN MAINE CALL COLLECT (207) 236-2896

OUR 800 NUMBER IS FOR SUBSCRIPTION ORDERS ONLY!

For Errors or Change of Address CALL ham radio direct at (603) 878-1441 8-5 EST

VISA

ADVERTISER'S INDEX AND READER SERVICE NUMBERS

Listed below are the page and reader service number for each advertiser in this issue. For more information on their products, select the appropriate reader service number make a check mark in the space provided. Mail this form to ham radio Reader Service, I.C.A., P.O. Box 2558, Woburn, MA 01801.

READER SERVICE #

Call Name Address ____

State

City

*Please contact this advertiser directly.

PAGE # READER SERVICE # 170 - Certified Communications 18 _165 - GLB Electronics _____25 * - Ham Radio's Bookstore ... 17, 26, 48, 52, 57, 62, 63 _179 - ICOM America, Inc.....Cll ____132 · IIX Equipment Ltd......68 ____178 - Kantronics......1 * - Microwave Research & Mfg.......49

____168 - Pac-Comm Packet Radio Systems, Inc.____18 _144 - Processor Concepts _____149 - Stridsburg Engineering Co._____49 ____139 - Unity Electronics _____59 ____107 - Vanguard Labs _____96 ____108 - E.H. Yost Co._____96 PRODUCT REVIEW/NEW PRODUCTS

Zip

Please use before September 30, 1987.

PAGE #

	· · · · · · · · · · · · · · · · · · ·	
_	308 - Computeradio	
_	307 - Encomm, Inc	
	309 - Etron RF Enterprises	
_	301 - John Fluke Mfg. Company, Inc	84
_	311 - Gordon West Radio School	
	• - Ham Radio's Bookstore	
	Hamtronics, NY	86
_	305 - Heath Company	
	304 - ICOM America, Inc	
	306 - Kantronics.	
_	312 - Larsen Electronics	
_	302 - MFJ Enterprises	
	310 - Mirage/KLM Communications	
	303 - P.C. Electronics	

2x4Z BASE REPEATER ANTENNA

THE HIGHEST GAIN DUAL BAND BASE/REPEATER ANTENNA

HIGH POWER 200 WATTS

FREQUENCY: BROAD BAND 140-170 MHz 410-470 MHz

GAIN: VHF - 8.2dB UHF - 11.5dB VSWR - 1.-1.2 or less

CONNECTOR: N TYPE FEMALE

LIGHTNING PROTECTION GROUNDED DIRECT

LENGTH: 16 FT. WEIGHT: 5 LBS. 3 OZ. WIND LOAD: 90 MPH MOUNTING: UP TO 2 IN. MAST CAN SIMULCAST ON BOTH BANDS

WATERPROOF CONNECTING JOINTS

UPS SHIPPABLE


AMATEUR SPECIAL



1275 NORTH GROVE ST. ANAHEIM, CALIF. 92806 (714) 630-4541 CABLE: NATCOLGLZ FAX (714) 630-7024

98 August 1987

104

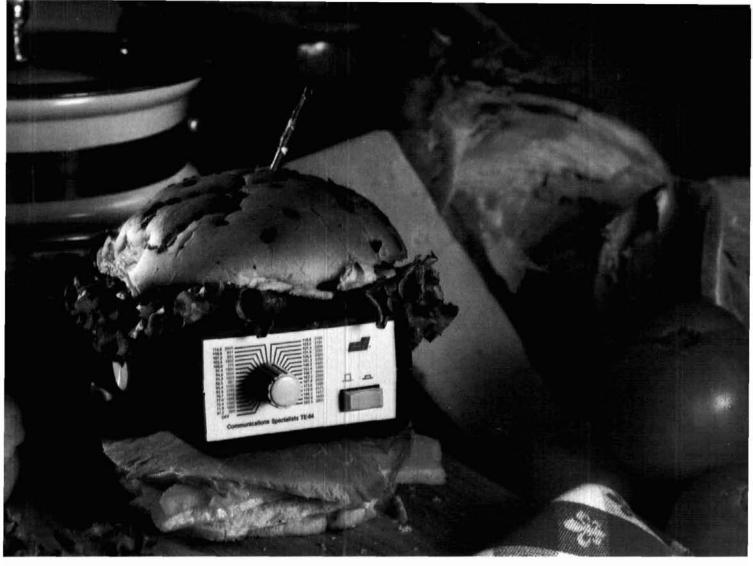

Food for thought.

Our new Universal Tone Encoder lends its versatility to all tastes. The menu includes all CTCSS, as well as Burst Tones, Touch Tones, and Test Tones. No counter or test equipment required to set frequencyjust dial it in. While traveling, use it on your Amateur transceiver to access tone operated systems, or in your service van to check out your customers' repeaters; also, as a piece of test equipment to modulate your Service Monitor or signal generator. It can even operate off an internal nine volt battery, and is available for one day delivery, backed by our one year warranty.

- · All tones in Group A and Group B are included.
- · Output level flat to within 1.5db over entire range selected.
- Separate level adjust pots and output connections for each tone Group.
- Immune to RF
- Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak
- · Instant start-up.
- Off position for no tone output.
- · Reverse polarity protection built-in.

Group A

67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
77.0 XB	100.0 1Z	131.8 3B	173.8 6A
79.7 SP	103.5 1A	136.5 4Z	179.9 6B
82.5 YZ	107.2 1B	141.34A	186.2 72
85.4 YA	110.9 2Z	146.2 4B	192.8 7A
88.5 YB	114.8 2A	151.4 5Z	203.5 MI

Frequency accuracy, ± .1 Hz maximum - 40°C to + 85°C

· Frequencies to 250 Hz available on special order

· Continuous tone

Group B

TEST-TONES:	TOUCH	-TONES:	E	URST	TONES	5:
600	697	1209	1600	1850	2150	2400
1000	770	1336	1650	1900	2200	2450
1500	852	1477	1700	1950	2250	2500
2175	941	1633	1750	2000	2300	2550
2805		1044408	1800	2100	2350	

- Frequency accuracy, ± 1 Hz maximum 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

Model TE-64 \$79.95

COMMUNICATIONS SPECIALISTS

426 West Taft Avenue, Orange, California 92667 (800) 854-0547/ California: (714) 998-3021



✓ 105



Introducing the next logical step. Yaesu's Dual Band Handie.

Two affordable radios in one—that's exciting.

Yaesu's dual-band FT-727R packs our best HT know-how into one compact design. At a price that's in step with your ham budget.

Hit hard-to-reach repeaters with a powerful 5 watts on both 2 meters and 440 MHz.

Work the bands quickly and easily with a wealth of microprocessor-controlled commands:

Jump between the separate VHF and UHF VFO registers. Program each of the ten memories for instant recall of repeater input and output frequencies, odd splits, and tone encode/decode.

Scan the memory channels, the entire band, or a band segment. And return to any special frequency with the priority feature.

Use link repeaters by programming TX on one band and RX on another.

Conserve power with the battery saver. It lets you monitor silently



while drawing negligible current. And measure your battery level with the digital battery voltmeter. There's even a "Low Battery" LED.

Finally, your operation is rounded out with features like VOX capability. A one-touch repeater reverse switch. An LCD readout with illumination lamp. A high/low power switch. Remote computer control capability. An optional CTCSS module. And Yaesu's full line of optional accessories.

So step up your operating capability now with the logical choice in HT operation.

Yaesu's dual-band FT-727R.



Yaesu USA

17210 Edwards Road, Cerritos, CA 90701 (213) 404-2700 Repair Service: (213) 404-4884 Parts: (213) 404-4847

Yaesu Cincinnati Service Center 9070 Gold Park Drive, Hamilton, OH 45011 (513) 874-3100

Prices and specifications subject to change without notice.

✓ 102

KENWOOD

... pacesetter in Amateur radio

This HT Has it TH-215A/315A/415A Full-featured Hand-held Transceivers

Kenwood brings you the greatest hand-held transceiver ever! More than just "big rig performance," the new TH-215A for 2 m and TH-415A for 70 cm pack the most features and the best performance in a handy size. And our full line of accessories will let you go from hamshack to portable to mobile with the greatest of ease!


- · Wide receiver frequency range. Receives from 141-163 MHz Includes the weather channels! Transmit from 144-148 MHz. Modifiable to cover 141-151 MHz (MARS or CAP permit required). TH-415A covers 440
- 449.995 MHz
- . 5, 2.5, or 1.5 W output, depending on the power source. Supplied battery pack (PB-2) provides 2.5 W output. Optional NiCd packs for extended operation or higher RF output available.
- · CTCSS encoder built-in. TSU-4 CTCSS decoder optional.
- 10 memory channels store any offset, in 100-kHz steps. Each memory channel can store frequency, frequency step, offset, reverse switch position, and CTCSS frequency.
- Nine types of scanning! Including new "seek scan" and priority alert.
- Intelligent 2-way battery saver circuit extends battery life. Two battery-saver modes to choose, with power save ratio selection.
- Easy memory recall. Simply press the channel number!
- 12 VDC input terminal for direct mobile or base station supply operation. When 12 volts is applied. RF output is 5 W!
- New Twist-Lok Positive-Connect locking battery case.
- · Frequency entry by keyboard or UP/DWN keys
- · Priority alert function.
- · Monitor switch to defeat squelch. Used to check the frequency when CTCSS encode/decode is used or when squelch is on.

. Large, easy-to-read multifunction LCD display with night light

DC IN

 \mathbf{O}

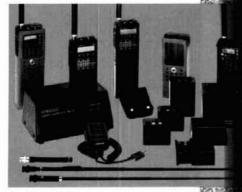
- · Audible beeper to confirm keypad operation. The beeper has a unique tone for each key. DTMF monitor also included.
- Supplied accessories: Belt hook, rubber flex antenna, PB-2 standard NiCd battery pack (for 2.5 W operation), wall charger, dust caps.



Optional Accessories:

· PB-1: 12 V, 800 mAH NiCd pack for 5 W output * PB-2: 8.4 V, 500 mAH NiCd pack (2.5 W output) * PB-3: 7.2 V, 800 mAH NiCd pack (1.5 W output) - PB-4, 7.2 V. 1600 mAH NiCd pack (1.5 W output) BT-5 AA cell manganese/alkaline battery case - BC-7 rapid charger for PB-1, 2, 3, or 4 - BC-8 Compact battery charger SMC-30 speaker microphone - SC-12, 13 soft cases - RA-3, 5 telescoping antennas - RA-8B StubbyDuk antenna - TSU-4 CTCSS decode unit - VB-2530: 2m, 25 W amplifier + LH-4, 5 leather cases · MB-4 mobile bracket · BH-5 swivel mount PG-2V DC cable - PG-3C cigarette lighter. cord with filter

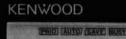Complete service manuals are available for all. Kenwood transceivers and most accessories Specifications and prices are subject to change without notice or obligation





VHF

SAVE

LAMP R/TONE



TH-215A

