



FOR COMPACT HIGH FIDELITY EQUIPMENT Ultra compact, lightweight, these UTC audio units are ideal

for remote control amplifier and similar small equipment. New design methods provide high fidelity in all individual 20,000 cycles. There is no need to resonate one unit in an amplifier to com-Units, the frequency response being ±2 DB from 30 to pensate for the drop of another unit. All units, except those carrying DC in Pensaie for the arop or anomer unit. All units, except mose carrying ut in a collaboration with a combined with a high conductivity outer case, effects good inductive shielding. Maximum operating level + 10 DB. Weight - 5 ½ ounces. Dimensions - 1 ½ " wide x 11/2" deep x 2" high.



actual size. 6V6 tube shown for comparison



FOR IMMEDIATE DELIVER

From Your Distributor

List

Price

ULTRA COMPACT HIGH FIDELITY AUDIO UNITS ± 2 DB from

	OTIVA C.	Primary Impedance	Impedance	30-20,000	\$15.00
Type	Application	50, 125, 200, 250, 333,	50,000 ohms	50-10,000	16.00
No. A-10	Low impedance mike, pickup, or multiple line to grid	500 ohms 50, 200, 500 ohms	50,000 ohms	multiple alloy shield for extremely low	
A-1.1	Low impedance mike, pickup, or line to 1 or 2 grids			hum pickup	15.00
		50, 125, 200, 250, 333,	80,000 ohms overall in two sections		14.00
	Low impedance mike, pickup,	500 ohms	orall	30-20,000	
A-12	or multiple title	8,000 to 15,000 ohms	80,000 ohms overall, 2.3:1 turn ratio overall	30-20,000	15.00
A-18	Single plate to two grids	8,000 to 15,000 ohms	50, 125, 200, 250, 333, 500 ohms	50-12,000	14.00
A-24	Single plate to multiple line	8,000 to 15,000 ohms	50, 125, 200, 250, 333, 500 ohms	20,000	15.00
A-2	Single plate to multiple line 8 MA unbalanced D.C.		50, 125, 200, 250, 333 500 ohms	D.C., inductance	1.0.00
A-2	- h null low level plates	each side 2 MA 6000 ohms D.C., 75 h	nenrys @ 4 MA 1300 on		
Α-	30 Audio choke, 300 henrys with no D.C. 450 henrys	licting includes only	a few of the many Ultra		

The above listing includes only a few of the many Ultra Compact Audio Units available . . . write for more details.

United Transformer (
SO VARICK STREET NEW YORK 13, N. Y.

EXPORT DIVISION 13 EAST 40th STREET. NEW YORK 16, N. Y... CABLES: "ARLAB"

electronics



NOVEMBER • 1948

MERCHANT-MARINE RADAR
THE PROSPECTS FOR UHF TELEVISION
INTERNATIONAL BROADCASTING, by John H. Battison
ULTRASONIC THICKNESS INDICATOR, by Benson Carlin
HERMETICALLY SEALED COMPONENTS, by W. J. Leiss, G. R. Moltrup, J. H. Slaton and A. H. Waynick 80 Sealed plug-in components provide humidity and moisture protection
ROAD-TESTING GASOLINE, by R. R. Proctor
COMPOSITE AMPLITUDE AND PHASE MODULATION, by Oswald G. Villard, Jr
REGULATOR FOR 400-CYCLE INVERTER, by Carl A. Helber
SONIC NAVIGATION SYSTEM, by Stanley R. Rich and A. H. Rosen
LOW-DISTORTION CROSSOVER NETWORK, by Paul W. Klipsch
LIGHT-FLASH GENERATOR, by R. G. Roush and Ferdinand Hamburger, Jr
MOBILE SELECTIVE CALLING, by E. H. B. Bartelink
MICROPHONE CALIBRATOR, by D. H. Bastin
DESIGN OF A NAVAL COMMUNICATION STATION, by David Baker
STABILIZING SERVOMECHANISMS, by Donald McDonald
F-M AND TELEVISION RECEIVING ANTENNAS, by George P. Kearse
BUSINESS BRIEFS 64 ELECTRON ART 124 NEW BOOKS CROSSTALK 67 NEW PRODUCTS 128 BACKTALK TUBES AT WORK 120 NEWS OF THE INDUSTRY 132 INDEX TO ADVERTISERS

DONALD G. FINK, Editor; W. W. MacDONALD, Managing Editor; John Markus, Vin Zeluff, Frank H. Rockett, A. A. McKenzie, Associate Editors; William P. O'Brien, Assistant Editor; Hal Adams, Editorial Assistant; Gladys T. Montgomery, Washington Editor; Harry Phillips, Art Director; Eleanor Luke, Art Assistant; R. S. Quint, Directory Manager; John Chapman, World News Director; Dexter Keezer, Director Economics Department

KEITH HENNEY, Consulting Editor

H. W. MATEER, Publisher; WALLACE B. BLOOD, Manager; D. H. Miller, H. R. Denmead, Jr., New York; Wm. S. Hodgkinson, New England; F. P. Coyle, Warren W. Shew, Philadelphia; C. D. Wardner, Chicago; J. L. Phillips, Cleveland; J. W. Otterson, San Francisco; Carl W. Dysinger, Los Angeles; Ralph C. Maultsby, Atlanta; Paul West, London, England; J. E. Blackburn, Jr., Director of Circulation

Contents Copyright 1948, by McGraw-Hill Publishing Company, Inc. All Rights Reserved. McGRAW-HILL PUBLISHING COMPANY, INCORPORATED, JAMES H. McGRAW (1860-1948), Founder • PUBLICATION OFFICE 99-129 North Broadway, Albany 1, N. Y., U. S. A. EDITORIAL AND EXECUTIVE OFFICES, 330 West 42nd St., New York 18, N. Y., U. S. A.—Member A. B. P. Member A. B. C.

James H. McGraw, Jr., President: Curtis W. McGraw, Vice-President and Treasurer: Eugene Duffield, Executive Assistant for Publications; Nelson Bond, Director of Advertising: James A. Gerardi, Secretary; and J. E. Blackburn, Jr., Director of Circulation.

LECTRONIO No. November 1948, Vol 21: No. 11, Published monthly, with a additional issue in June, price 75c a copy for U. S. and possessions, and Canada; \$1.00 for Latin America; \$1.50 for all other foreign countries. Directory issue \$2.00. Allow at least ten days for change of address. All communications about subscriptions should be addressed to the Director of Circulation. Subscription rates—United States and possessions, \$5.00 a year, \$9.00 two years, \$12.00 for three years. Canada (Canadian funds accepted), \$7.00 a year, \$11.00 for two years, \$14.00 for three years. Latin American countries \$10.00 for one year, \$16.00 for two years, \$20.00 for three years. All other countries \$15.50 for one year, \$30.00 for three years. Please Indicate position and company connections on all subscription orders. Entered as Second Class matter August 29, 1936, at Post Office, Albany, New York, under the Act of March 3, 1879, BRANCH OFFICES: \$20 North Michigan Avenue, Chicago II. III.; 68 Post Street, San Francisco 4; Aldwych, London, W.C. 2; Wannington, D. C. 4; Philadelphia 3; Cleveland 15; Detroit 26; St. Louis 8; Boston 16; Atlanta 3, Ga.: 621 So, Hope St., Los Angeles 14; 738-9 Oliver Building, Pittsburgh 22, ELECTRONICS is indexed regularly in The Engineering Index.

better components build better REPUTATIONS

... specify El-Menco

No product is better than its weakest component. This is why more and more manufacturers now use EL-MENCO mica capacitors. Rather than risk their reputations on inferior components they automatically specify El-Menco—the mica capacitor with the kind of performance that always gives customer satisfaction and builds better reputations.

CM 15 MINIATURE CAPACITOR

9/32" x 1/2" x 3/16"

For Radio, Television and Other Electronic Applications

2 to 420 mmf. capacity at 500 v DCA

2 to 525 mmf. capacity at 300 v DCA Temp. Co-efficient ± 50 parts per mil-

lion per degree C for most capacity values

6-dot standard color coded

CM 2Q CAPACITOR

Available in "A", "B", "C" and "D" characteristics

2 to 1500 mmf. in tolerances down to ± 1%* or
.5 mmf. at 500 D.C. working voltage

6-dot color coded

*Whichever is greater

CM 35 CAPACITOR

Available in "A'll "B", "C", "D" and "E" characteristics

Minimum tolerance 1%
500 D.C. working yoltage
6-dot color coded

THE ELECTRO MOTIVE MFG. CO., INC. WILLIMANTIC CONNECTICUT

lillenc

APACITORS



MICA TRIMMER

municate direct with our Export Dept. at Willimantic, Conn. for information

Foreign Radio and Electronic Manufacturers com-

ARCO ELECTRONICS, INC.

135 Liberty St., New York, N. Y.

Sole agent for Jobbers and
Distributors in U. S. and Canada

MOLDED MICA

LIOS new, better BLACK line prints

DRY DEVELOPED


Here are positive line working prints that are amazingly clear and easy to read. Every detail on the original pencil drawing is reproduced in crisp, dense black lines that stand out in sharp contrast against the white background.

It has been the goal of K&E in developing Heliost, to bring you a better, more dependable line of dry diazo reproduction materials than had ever been made before. To achieve this, K&E established a new, modern plant for the manufacture of Helios materials exclusively. We not only make the finished products -but we manufacture, to our own exacting standards, the required color-forming components. You see the results whenever you make prints on Helios papers, cloths or films—for their consistently high quality is due to the fact that, from


partners in creating

start to finish, Helios materials are made with the skill, care and vigilance characteristic of K&E throughout 81 years of making drafting and reproduction materials and equipment.

You can make positive line working prints on black line, blue line or maroon line opaque Helios papers or cloth directly from original drawings, layouts, letters, documents, forms. Or you can save your originals and reproduce positive line working prints directly from positive line intermediate originals on Helios transparent papers, cloth or films. For samples, write Keuffel & Esser Co., Hoboken, N. J., or ask your K&E Dealer or K&E Branch for a demonstration. Remember . . .

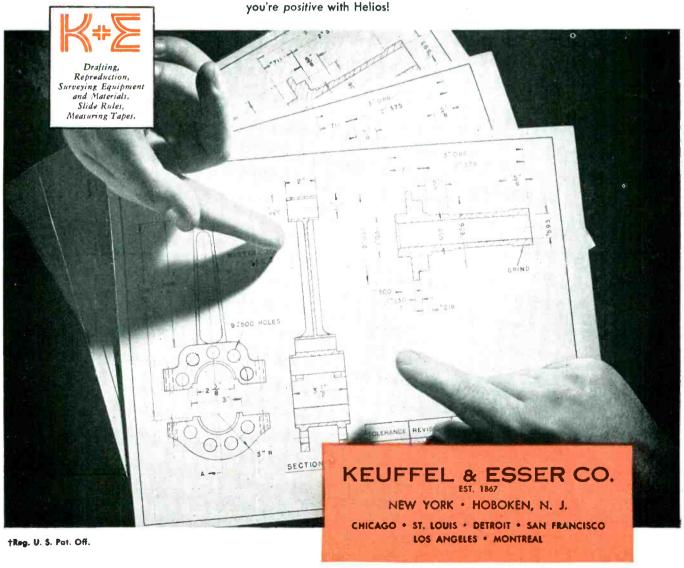

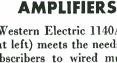Build quality into your wired music systems ... with these dependable components





The Western Electric 1140A Amplifier (at left) meets the needs of 85% of subscribers to wired music programs. Operates on a-c or d-c, delivering 10 watts from a-c source; 6 from d-c. Connects directly to telephone wires-needs no separate isolating

For higher power requirements, use the 124H (at right) or the 124J, a-c amplifiers rated at 12-20 watts.



LOUDSPEAKERS



The compact 8-inch 755A direct radiator has 8-watt capacity-ample for most uses. For higher power, use the 20-watt 756A or the 30-watt 728B. All give the same high quality, the same true reproduction.




AUTOTRANSFORMERS

These units are specifically designed for easy matching of multiple loudspeakers in wired program and sound distribution systems. Three power ratings: 25A, 4 watts; 26A, 16 watts; 27A, 64 watts.

MICROPHONES



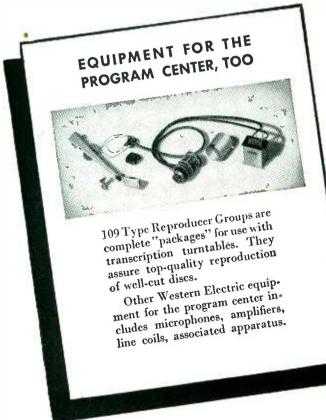With a 633A Microphone, subscribers can use their wired music systems for announcements or paging-or can pick up programs originating on their own premises. 639 Type Cardioids also available.



THE TWO major wired music program THE TWO major when made restautions put the most into their discs with Western Electric recording equipment. Be sure to get the most out of these discs . . . with Western Electric reproducing equipment!

The completeness of Western Electric's line simplifies the planning of a peak-performance system to meet any requirements. You can get full details from your local Graybar Representative-or write Graybar Electric Company, 420 Lexington Avenue, New York 17, N. Y.


-QUALITY COUNTS-



Distributed by Grayba Richard Company Line Legal Electric Distributors: in the u.s. a.—Grayba Electric Co. In Canada and new Foundland—

Northern Electric Company, Ltd.



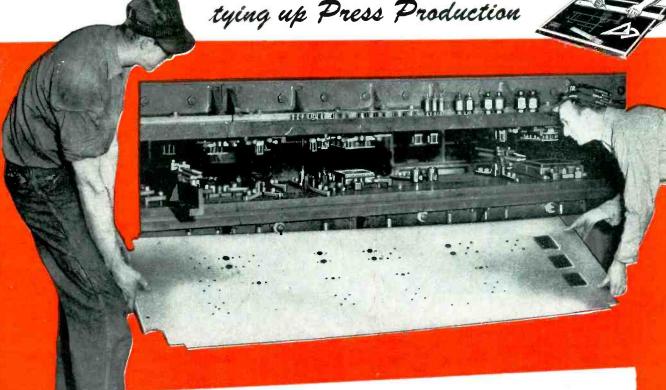

ADJUSTABLE PERFORATING DIES

quickly and easily rearranged







Change orders from the engineer. ing department usually cause plenty of headaches in production...particularly where die piercing operations are involved.

But...if you're using Whistler Adjustable Dies, there is no lost time—no waiting—no extra die expense. The same dies are easy to rearrange to the new design. Add units from stock, or delete sizes and shapes no longer required. Arrange the new set-up right on the press. set-up right on the press.

Consider the savings in production time alone. Then think how continued re-use of the same dies in sub-sequent jobs writes off first cost.

Whistler Dies can be used in practically any press. All parts are interchangeable. Precision is assured on long or short runs. Closer centers permit fewer press operations.

Deliveries are quick...little or no waiting. Standard round punches and dies up to 3" are available from stock. Ovals, squares, rectangles and special shapes can be made up in a few days. Write for the Whistler Catalogs today and get all the facts.

S. B. WHISTLER & SONS, INC.

742 MILITARY ROAD

BUFFALO 17, NEW YORK

See us at Booth 1502 National Metal Exposition October 25 to 29—Convention Hall—Philadelphia




What's your problem?

Fine Wire?

Tungsten?

Molybdenum?

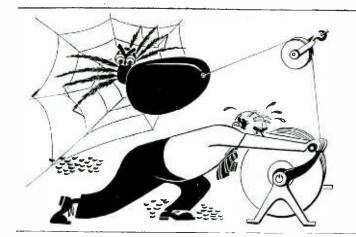

Problem 1

The firm of AL LOYS & AL UMINUM were in urgent need of fine aluminum and aluminum alloy wire for a delicate production job. Fine Wire Headquarters assured them that it was no problem at all. The order was placed, the Fine Wire delivered, and it performed to the complete satisfaction of all concerned.

Problem 2

Mr. Hi Hott needed molybdenum sheets for forming into parts. High hot strength and good ductility were required. North American Philips supplied him with Elmet Molybdenum sheets that met his specifications exactly.



Problem 3

Mr. N. O. Emission, II, required plated grid wires. He solved his problem with a call to Fine Wire Headquarters. We shipped him some gold plated tungsten and molybdenum wires. Result: no secondary emission.

the answer

WHY not call Fine Wire Headquarters when you have a question about fine wire? We can't do the impossible, but we can do lots of things that can bring you the right fine wire for the job.

So—when you have a problem on Fine Wire, Tungsten or Molybdenum—wire, phone or write to North American Philips, makers of NORELCO Fine Wires, and ELMET Tungsten and Molybdenum products.

NORTH AMERICAN PHILIPS COMPANY, INC.

Dept. XT-11, 100 East 42nd Street, New York 17, N.Y.

Export Representative • Philips Export Corporation • 100 East 42nd Street, New York 17, N.Y.

Baird

Associates

Incorporated



Sorensen

electronic

voltage

regulation



Shown above is the Infrared Gas Analyzer. Baird Associates, Incorporated, manufacturers of precision optical instruments for

production and research analytical control use a Sorensen Model 250 A.C. line voltage regulator with their Infrared Gas Analyzer. Only Sorensen units provide the degree of line voltage stabilization necessary to
increase the sensitivity of the Analyzer readings. SIX IMPORTANT SORENSEN FEATURES: • Precise regulation
accuracy; • Excellent wave form; • Output regulation over wide input voltage range; • Fast recovery time; • Adjustable output voltage, that once set, remains constant; • Insensitivity to line frequency fluctuations between 50 and 60 cycles.

If you calibrate meters, need quality control on test lines, work with X-ray equipment, or are a research physicist
or chemist, there is a standard Sorensen AC or DC unit to solve your voltage problem. The Sorensen Catalog
contains complete specifications on standard Voltage Regulators and Nobatrons. It will be sent to you upon request.

THE FIRST LINE OF STANDARD ELECTRONIC VOLTAGE REGULATORS.



SORENSEN & Company, Inc.

Stamford, Connecticut

Represented in all principal cities.

hp Presents...

COMPLETE FMI TEST EQUIPMENT

For Broadcast Stations

Here is a complete transmitter maintenance group — providing every measurement necessary for top-flight operation from microphone to antenna! Three fast, accurate precision instruments in one compact whole — specifically designed for years of trouble-free performance — proven in service in radio stations throughout America.

These are the -bp- instruments that comprise this group.

- -hp- 335B Frequency and Modulation Meter.
 Continuous measurement of carrier frequency and modulation swing. Low distortion audio output for measuring and monitoring.
- 2. -hp- 206A Audio Signal Generator.

 Provides continuously variable audio frequency voltage having a total wave form distortion of less than 0.1% from 50 cps to 20 kc.
- 3. -hp- 330C Noise and Distortion Analyzer.


 Measures harmonic distortion and noise level from demodulated carrier or audio channels. Built-in-vacuum-tube-voltmeter measures audio level, frequency response and gain.

All instruments have identical panel sizes for convenient mounting in relay racks. Can be delivered in colors and finishes to match your equipment.

GET FULL INFORMATION...WRITE TODAY

HEWLETT-PACKARD COMPANY

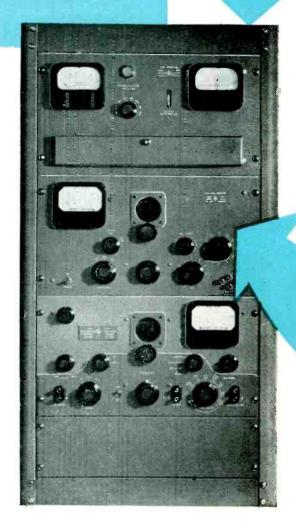1481A PAGE MILL ROAD . PALO ALTO, CALIFORNIA



This-hp-Maintenance Group Makes These Essential FM BROADCAST MEASUREMENTS

Carrier Frequency: Continuously monitored with accuracy well within F.C.C. limits.

Modulation Swing: Continuously measured at instrument installation and at control console.

Modulation Limit: Alarm lamp flashes on instrument and console when pre-set level is exceeded. Aurel Monitor: Demodulated signal provides listening check for operator.

Harmonic Distortion: Measured from r-f carrier or audio channel.

Noise: Measured accurately from FM carrier or audio channel.

Frequency Response: Overall response, microphone to antenna, of individual units in transmitter set-up. Audio Transmission: Accurately measures gain of audio channels.

Audio Level: Measured over range from +50 db to -60 db at 600 ohm level.

Equalizer Circuits: Characteristics of circuits and lines can be checked accurately, swiftly.

Oscilloscope Connections: Facilitates visual study of noise and distortion.



-hp-335B FM Monitor

Accurate, Stable, Easy to Operate

BRIEF SPECIFICATIONS

Frequency Range: Any single frequency, 88 to 108 mc.

Deviation Range: +3 kc to -3 kc.

Accuracy: Better than ± 1000 cps.

Modulation Range: Modulation swing 100 kc. Scale calibrated 100% at 75 kc.

Audio Output: Supplied with 75 microsecond de-emphasis circuit, flat within 1/2 db of standard curve, 20 cps to 20 kc.

Monitoring Output: 1 milliwatt into 600 ohms, balanced, at 100% modulation.

Size: Panel 101/2"x 19". Depth 13".

Precision accuracy, unique stability, new convenience and compact size—those are but a few of the reasons why this -bp- 335B is the finest instrument ever developed for FM broadcast monitoring. Here are additional advantages that help make this new -bp- instrument an ideal component of the -bp- FM group.

Simple to Operate. No adjustments required during operation.

Independent of Signal Level. Readings of frequency or modulation meter are unaffected by variations in transmitter level.

Unusual Stability. Low temperature coefficient crystal in temperature-controlled oven combined with specially developed

electronic linear counter circuits provides accuracy far beyond that required. Measurements do not depend on accuracy of conventional discriminator circuits.

Remote Modulation Meter. Modulation may be monitored at control console or other remote point.

Low Distortion. Audio output for measuring purposes has less than .25% residual distortion.

Low Noise Level. Residual noise and hum in audio output are at least 75 db below 100% modulation.

Meets F.C.C. Requirements.

This instrument is small in size, easy to install, suitable for cabinet or rack panel mounting. Can be furnished to match your transmitter color scheme.



-hp-206A Audio Signal Generator

Distortion Less Than 0.1%

BRIEF SPECIFICATIONS

Frequency Range: 20 cps to 20 kc, 3 bands,

Output: +15 dbm to matched resistive loads. 10 volts available for open

Output Impedance: 50, 150, 600 ohms center-tapped and balonced. 600 ohms single-ended.

Frequency Response: Better than 0.2 db beyond output meter at all levels.

Distortion: Less than 0.1% above 50 cps. Less than 0.25% from 20 cps to 50 cps.

Hum Level: At least 70 db below output signal, or more than 100 db below 0 level, whichever is larger.

Size: Panel 101/2"x 19". Depth 13".

The -hp- 206A Audio Signal Generator provides a source of continuously variable audio frequency voltage having a total distortion of less than 0.1%. This feature, combined with high stability, flat frequency response, and great accuracy of output voltage, makes it an ideal component for FM station maintenance. Here are some of this instrument's unusual advantages:

Distortion less than 0.1% between 50 cps and 20 kc.

Continuously variable frequency range, covered in 3 bands, micro-controlled dial,

effective scale length 47", ball-bearing smoothness for tuning ease.

Output meter monitors output voltage signal with accuracy of at least 0.2 db.

Special low temperature co-efficient frequency determining elements provide high stability and excellent accuracy over long periods of time.

Precision attenuators vary output signal level in 0.1 db steps over 111 db range.

This new -hp- generator is convenient to use, compact in size. It can be provided for rack or cabinet mounting, in colors matching your installation.

148





When an aircraft magneto is rotated at low RPM while the aircraft engine is functioning, a small triple unit starting coil introduces a high tension spark into the magneto circuit, resulting in increased temperatures within the unit. Proper insulation is necessary during this period to insure against low voltages.

Extra

This is why you find BH Extra Flexible Fiberglas Sleeving used on the triple unit starting coil of the booster section of the Bendix-Scintilla ignition system. The system is installed on the Pratt Whitney R-4360 Wasp Major engine.

This is what Bendix-Scintilla engineers

"BH Extra Flexible Sleeving is used as added insulation against low voltages. BH Fiberglas Sleeving is required rather than ordinary varnished tubing because temperatures up to 400 F. are encountered. Its remarkable flexibility and non-fraying qualities are added advantages. Results have been completely satisfactory."


If you have a tough insulation problem in your product or plant where extreme temperatures, excessive current loads, grease or moisture are causing iusulation breakdowns, then specify BH Fiberglas Mrite today.

BENTLEY, HARRIS MFG. CO., CONSHOHOCKEN, PA.

USE COUPON NOW	
Bentley, Harris Mfg. Co., Dept. E-28, Conshohocken, Pa.	1
I am interested in BH Non-Fraying Fiberglas Sleeving for	
(product)	Send samples, pamphlet and prices
operating at temperatures of°F. at volts. Send samples so I can see for myself how	on other BH Products as follows:
BH Non-Fraying Fiberglas Sleeving stays flexible as string, will not crack or split when bent.	☐ Cotton-base Sleeving and Tubing
NAMECOMPANY	☐ Ben-Har Special Treated Fiberglas Tubing
ADDRESS	Tublig

for mobile two-way radio

ALLIED'S NEW CO-AXIAL RELAY

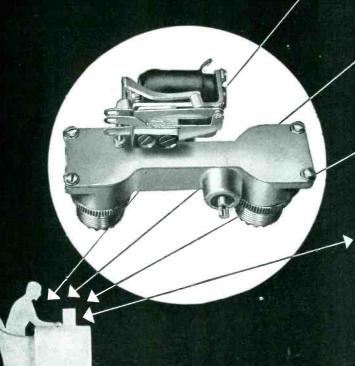



The new Allied "RA" relay transfers 52 ohm antenna transmission line (type RG-8U Cable) from receiving to transmitting position. It is now used in police car radios and is highly recommended for both mobile and stationary applications.

This new relay is equipped with two Co-Axial cable fittings and one insulated transmitter line terminal. Co-Axial fittings for antenna and receiver connection are die cast as part of the metal housing. They will accommodate Signal Corps cable connector PL-259. Auxiliary double-pole, double-throw contacts can be supplied when specified.



ALLIED CONTROL COMPANY, INC.
2 EAST END AVENUE, NEW YORK 21, N. Y.


ENGINEERING FEATURES OF THE ALLIED TYPE "RA" RELAY

Contact Rating: Antenna transfer contacts will handle a maxi num of 75 watts of radio frequency up to 150 megocycles when inserted in a properly terminated 52 ohm line. Auxiliary contacts have a non-inductive rating of 1 ampere at 24 volts D.C. or 115 volts A.C. Coil Rating: Up to 110 volts D.C. and 115 volts A.C. 60 cycles.


Coil	D.C.	D.C.	D.C.
No.	Volts	Current	Resistance
31	6.	.46	13.
34	12.	.22	54.
38	26.5	.083	320.
40	48.	.060	800.
43	110.	.026	4100.

(This table is based on an average power rating of 2.5 watts. Minimum operating voltages are 80% of voltages shown above.)

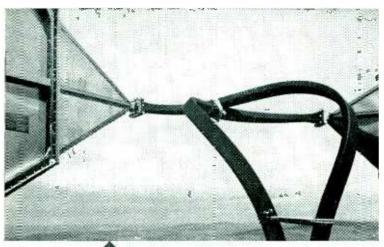
Dimensions: 2"x21/8" x13/4". Weight: 4 oz.



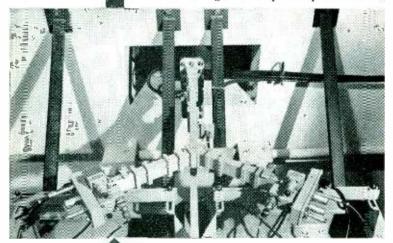The waveguide connects with antennas, which are oriented in azimuth with antennas at next station. At right is complete repeater station,



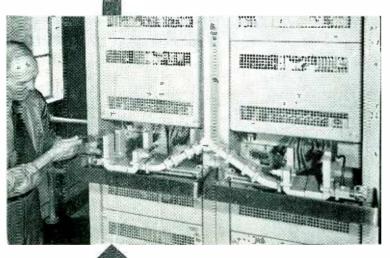The waveguide continues upward through the roof of the station toward the antennas.



Base of a waveguide circuit in a repeater station of the New York-Boston radio relay system.



Pipe Circuits

UNLIKE radio broadcast waves, microwaves are too short to be handled effectively in wire circuits. So, for carrying microwaves to and from antennas, Bell Laboratories scientists have developed circuits in "pipes," or waveguides.

Although the waves travel in the space within the waveguides, still they are influenced by those characteristics which are common to wire circuits, such as capacitance and inductance. A screw through the guide wall acts like a capacitor; a rod across the inside, like an inductance coil. Thus transformers, wave filters, resonant circuits — all have their counterpart in waveguide fittings. Such fittings, together with the connection sections of waveguide, constitute a waveguide circuit.

From Bell Laboratories research came the waveguide circuits which carry radio waves between apparatus and antennas of the New York-Boston radio relay system. As in long distance wire communication, the aim is to transmit wide frequency bands with high efficiency — band widths which some day can be expanded to carry thousands of telephone conversations and many television pictures.

Practical aspects of waveguides were demonstrated by Bell Telephone Laboratories back in 1932. Steady exploration in new fields, years ahead of commercial use, continues to keep your telephone system the most advanced in the world.

BELL TELEPHONE, LABORATORIES

EXPLORING AND INVENTING, DEVISING AND PERFECTING FOR CONTINUED IMPROVEMENTS AND ECONOMIES IN TELEPHONE SERVICE.





Control panel for use with cascade rectifiers.

This cascade rectifier, 42 inches high, delivers 70 kv, 15 ma d-c. Consists of two basic Kenotron-tube rectifier units.

SMALL RECTIFIERS VOLTAGES up to 135 KV

New, within the last year, is this small cascade-type rectifier for generating smooth high d-c voltages. Suitable for laboratory and factory for testing and as power supply. Features: versatility, reliability, reasonable price and long tube life with much lower cost of replacement tubes. The rectifiers can be furnished for singlephase operation from 115- or 230-volt, 50- or 60-cycle power supply.

Basic unit is a 35 kv, 32 ma (continuous) rectifier, with necessary transformers mounted in an oil-filled steel tank. Each unit is 34" wide, 25" deep and 21" high. Up to four units can be stacked, giving d-c voltages up to 135 kv. Output voltage ripple, peak to peak, will not exceed 0.1% per milli-

A CONTROL PANEL can be supplied which will provide smooth output voltage control over the complete range from zero to maximum. Accuracy of output voltage, with this panel, is ± 5 per cent of full scale; accuracy of current indication, ± 2 per cent. Overcurrent protection is included.

SUITABLE FOR INTEGRAL MOUNTING. Because of its small size, this rectifier can often be mounted within the enclosure housing your own product. Such integral mounting is usually preferable from all standpointslowers cost, saves space, and improves appearance of the entire assembly.

STANDARD UNITS, IN REGULAR PRO-DUCTION. These cascade rectifiers are built up of standard units that are in regular production. They can be shipped on shorter schedules than are normal for this general class of equip-


For prices and specific information, address inquiries to our nearest office, or to General Electric Company, Transformer Sales Division, 16-215, Pittsfield, Mass.

GENERAL




ELECTRIC

Centralab reports to

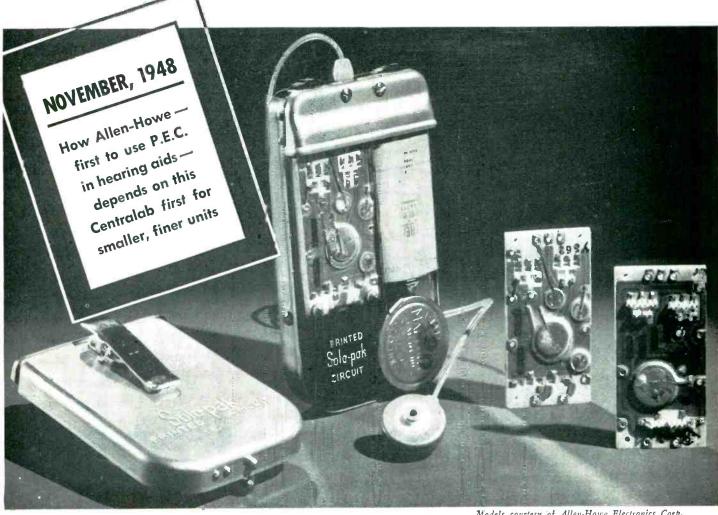


Models courtesy of Allen-Howe Electronics Corp.

Size and weight are vital to Allen-Howe, hearing aid manufacturer. That's why this firm's engineers chose Centralab's Printed Electronic Circuit to help them design and build smaller, lighter, more efficient units. Months of actual experience using P.E.C. have proved to them how very rugged these miniature audioamplifiers are . . . just how well they resist humidity and moisture. That's why they continue to use Centralab's revolutionary P.E.C. Write for Bulletin 973.

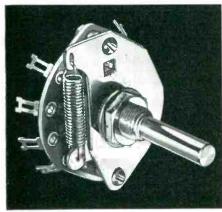


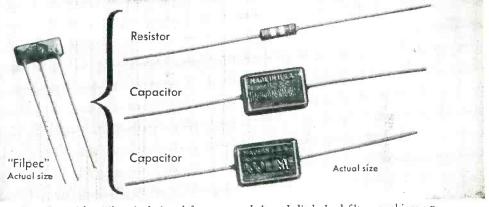
Great step forward in switching is CRL's new Rotary Coil and Cam Index Switch. Its coil spring gives you smoother action, positive indexing, longer life.




Centralab's Filpec is designed for use as a balanced diode lead filter, combines up to three major components into one tiny unit, lighter and smaller than one ordinary capacitor. Capacitor values available from 50 to 200 mmf. Resistor values from 5 ohms to 5 megohns. For complete information, write for Bulletin 976.


Electronic Industry

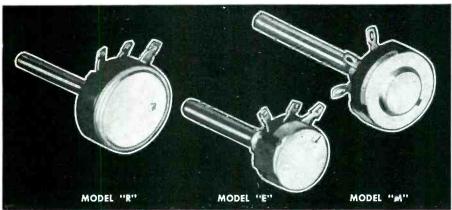

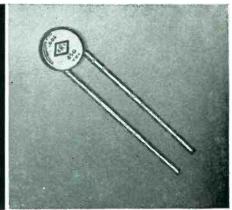

- Let Centralab's complete Radiohm line take care of your special needs. Wide range of variations: Model "R" wire wound, 3 watts; or composition type, 1 watt. Model "E" composition type, 1/4 watt. Direct contact, 6 resistance tapers, Model "M" composition type, 1/2 watt. Send for Bulletin 697.
- For utmost reliability in small physical size, low mass weight, use CRL Hi-Kaps miniature ceramic disc capacitors. Write for Bulletin 933.

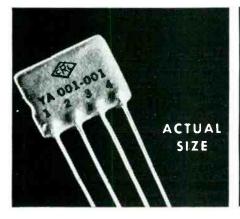

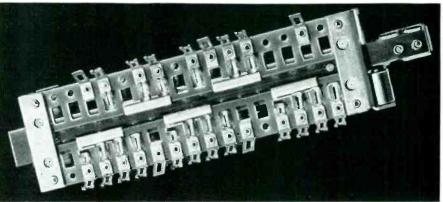

- CRL's Couplate consists of a plate lead resistor, grid resistor, plate by pass capacitor and coupling capacitor. Write for Bulletin 943.
- Centralab's development of a revolutionary, new Slide Switch promises improved AM and FM performance! Flat, horizontal design saves valuable space, allows short leads, convenient location to coils, reduced lead inductances for increased efficiency in low and high frequencies. Rugged, efficient. Write for Bulletin 953.

LOOK TO CENTRALAB IN 1948! First in component research that means lower costs for the electronic industry. If you're planning new equipment, let Centralab's sales and engineering service work with you. Get in touch with Centralab!



DIVISION OF GLOBE-UNION INC., MILWAUKEE, WIS.

ONE OF THESE 5 WILL BEST FILL YOUR V.O.M. REQUIREMENTS



MODEL 630. Outstanding Features: (1) The new Triplett Molded Selector Switch with contacts fully enclosed . . . (2) Has Unit Construction with Resistor Shunts, Rectifier Batteries in molded base . . . (3) Provides direct connections without cabling . . . no chance for shorts . . . (4) Big easily read cabling . . . no chance for shorts . . . (4 51/2" Red • Dot Lifetime Guaranteed Meter.

D.C. VOLTS: 0.3-12-60.300-1200.6000, at 20,000 Ohms/Volt A.C. VOLTS: 0.3-12-60-300-1200.6000, at 5,000 Ohms/Volt D.C. MICROAMPERES: 0-60, at 250 Millivolts D.C. MILLIAMPERES: 0-12-12-120, at 250 Millivolts D.C. AMPERES: 0-12, at 250 Millivolts D.C. AMPERES: 0-12, at 250 Millivolts OHMS: 0-1000-10,000; 4.4 Ohms at center scale on 1000 scale; 44 Ohms center scale on 10,000 range.
MEGOHMS: 0-1-100 (4400-440,000 at center scale).
DECIBELS: -30 to -4, -16, -30, -44, -56, -70.
OUTPUT: Condenser in series with A.C. Volt ranges.

. U.S.A. Dealer net price. Leather Carrying Case, \$5.75. . . Adapter Probe for TV and High Voltage Extra.

MODEL 666-HH. This is a pocket-size tester that is a marvel of compactness and provides a complete miniature laboratory for D.C. and A.C. voltages, Direct Current and Resistance analyses. Equally at home in the laboratory, on the work bench or in the field . . . its versatility has labeled it the tester with a thousand uses . . . housed in molded case . . .

TECH DATA

D.C. VOLTS: 0-10-50-250-1000-5000, at 1,000 Ohms/Volt A.C. VOLTS: 0-10-50-250-1000-5000, at 1,000 Ohms/Volt D.C. MILLIAMPERES: 0-10-100-500, at 250 Millivolts OHMS: 0-2,000-400,000, (12-2400 at center scale)

MODEL 666-HH.... U.S.A. Dealer Net Price....\$22.00 Leather Carrying Case, \$4.75.

MODEL 625-NA. This is the widest range laboratory-type instrument with long 5.6" mirrored scale to reduce parallax. Special film resistors provide greater stability on all ranges. Completely insulated molded case. Built by Triplett over a long period of time, it has thoroughly proved itself in laboratories all over the world.

TECH DATA

SIX D.C. VOLTS: 0-1.25.5-25-125-500-2500, at 20,000 Ohms/Volt SIX D.C. VOLTS: 0-2.5-10.50-250-1000-5000, at 10,000 Ohms/Volt SIX A.C. VOLTS: 0-2.5-10.50-250-1000-5000, at 10,000 Ohms/Volt D.C. MICROAMPERES: 0-50, at 250 Millivolts D.C. MILLIAMPERES: 0-10-100-1000, at 250 Millivolts D.C. AMPERES: 0-10: at 250 Millivolts

OHMS: 0-2000-200,000, (12-1200 at center scale)
MEGOHMS: 0-40, (240,000 at center scale)
SIX DECIBELS RANGES: -30 +3.0, +15, +29, +43, +55, +69.
(Reference level "O" DB at 1.73 V. on 500-Ohm line.)
Six Output on A.C. Volts ranges.

U.S.A. Dealer Net Price ... \$45.00 MODEL 625-NA. Carrying Case, \$5.50. Accessories available on special order for extending ranges.

MODEL 2405-A. This instrument combines ultra sensitivity with a large 53/4" scale meter and is housed in a rugged metal . . It is furnished with hinged cover so that it can be used for service bench work or for portable field service. Gives A.C. Amperes readings to 10 Amps.

TECH DATA

D.C. VOLTS: 0-10-50-250-500-1000, at 20,000 Ohms/Volt D.C. AMPERES: 0-10, at 250 Millivolts D.C. MILLIAMPERES: 0-1-10-50-250, at 250 Millivolts D.C. MICROAMPERES: 0-50, at 250 Millivolts A.C. VOLTS: 0-10-50-250-500-1000 at 1000 Ohms/Volt A.C. AMPERES: 0-0.5-1-5-10, at 1 Volt-Ampere OHM-MEGOHMS: 0-4000-40,000 ohms—0-4-40 megohms (self-contained batteries) OHM-MEGOHMS: 0-4000-40,000 ohms—0-4-40 megonms (seir-contained batteries)
OUTPUT: Condenser in series with A.C. Volts ranges
DECIBELS: -10 to +15, +29, +43, +49, +55. (Reference level "O" DB at 1 73 V. on 500-ohm line.)
CONDENSER TEST: Capacity check of paper condensers is possible by following data in instruction book. MODEL 2405-A.... U.S.A. Dealer Net Price.... \$59.75

to use in complicated testing . . . A must in F.M. and TV work in any sensitive circuit when work in any sensitive circuit where low current drain is a factor . . . TECH DATA

D.C.-A.C.-A.F. VOLTS: 0.2.5-10-50-250-500-1000
R.F. VOLTS; 0.2.5-10-50
D.C. MILLIAMPERES: 0.2.5-10-50-250-500-1000
OHMS: 0.1K-10K-100K
MEGOHMS: 0.1-10-100
INPUT IMPEDANCE: 11 Megohms on D.C. Volts.
4.8 Megohms on A.C.-R.F. Volts


MODEL 2451. U.S.A. Dealer Net Price External high-voltage probe available on special order. See the Triplett V.O.M. line at your local Radio Parts Distributor or write

TRIPLETT ELECTRICAL INSTRUMENT COMPANY · BLUFFTON, OHIO, U.S.A.

In Canada: Triplett Instruments of Canada, Georgetown, Ontario




JAN TON

 

It is a combination of chemical, electrical, physical, and mechanical properties which makes Synthane laminated plastics valuable in so many applications. Synthane is moisture and corrosion resistant, easily machined and weighs only about half as much as aluminum. One of the best electrical insulators known, Synthane is hard, dense, strong and has excellent anti-frictional qualities. Synthane is also the set plastic . . . not affected by wide variations in temperature.

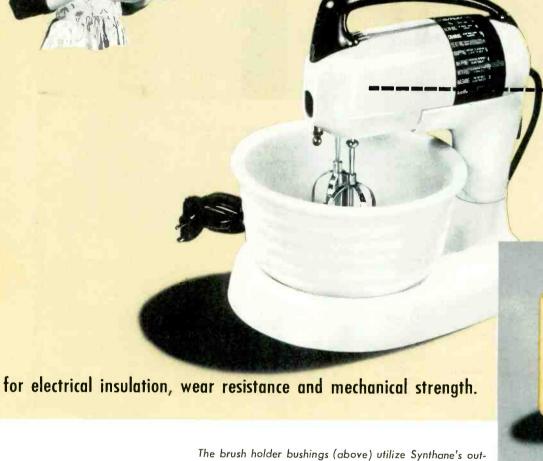Among the more domestic occupations of our type of plastics are these bushings used in Dormeyer Food Mixers.



standing electrical qualities—high dielectric strength, low moisture absorption, high dielectric constant—to insulate the brush mechanism. In addition, Synthane's unusual mechanical strength helps them render long and useful service without need of replacement. These and other hard-working properties also fit Synthane for use in fans, refrigerators, washing machines, vacuum cleaners, ironers, sewing machines and many other electrical appliances.

If there's a use for Synthane in your product, let us help you with design, materials or completely fabricated parts. Write for your free copy of our complete catalog of Synthane plastics today! Synthane Corporation, 6 River Road, Oaks, Pa.



where Synthane belongs

DESIGN • MATERIALS • FABRICATION • SHEETS • RODS • TUBES
FABRICATED PARTS • MOLDED-MACERATED • MOLDED-LAMINATED



You can match the characteristics of most transcriptions and recordings...

...with the 109 Type Reproducer Group



Recording characteristics vary widely from one company's recordings to another. But... when you use the Western Electric 109 Type Reproducer Group, with its 7-position Equalizer, you can correct for practically any of the more commonly used recording characteristics.

Note in the adjoining panel how closely the 109 Type Group equalizes not only for the NAB and Orthacoustic curves, but also for commercial records and lateral transcriptions. In fact, you can match within close tolerances all vertical and most lateral transcriptions and 90% of phonograph records.

That's one factor in the high-quality performance of the 109 Type Group. Another is the exceptionally low intermodulation distortion of the 9 Type Reproducer. Hear the Group for yourself — note how this feature reduces "hash" at the higher frequencies.

The 109 Type Group consists of reproducer arm, your choice of 9A or 9B Reproducer, equalizer and cable assembly, and repeating coil. You can easily mount this top-performance group on your present turntables—and you can get it from stock!

Place your order with your local Graybar Representative — or write Graybar Electric Co., 420 Lexington Ave., New York 17, N. Y.



- QUALITY -


DISTRIBUTORS: IN THE U. S. A. — Grayhar Electric Company. IN CANADA AND NEWFOUNDLAND—Northern Electric Co., Ltd.

Western Electric


See how closely the 109 duplicates all of these recording curves

Recording Characteristic

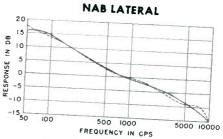
109 Type Reproducer Group (using average production reproducer)




Equalizer Curve B, Pos. L2

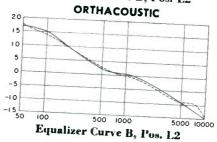

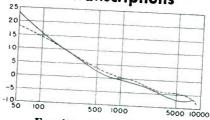
Typical curves for commercial records and transcriptions




Equalizer Curve B, Pos. L2

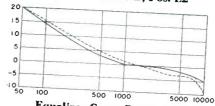

Equalizer Curve B, Pos. L1

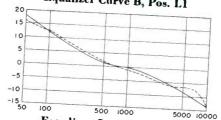


Equalizer Curve B, Pos. L1

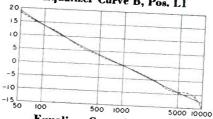

Equalizer Curve B, Pos. L2

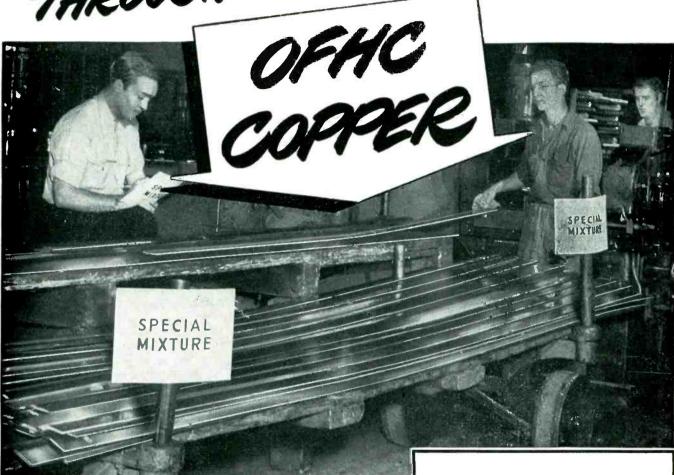PERSONALLY CONDUCTED THEOUGH THE REVERE MILLS



BECAUSE OFFIC Copper looks like any other copper, Revere takes great pains to identify it throughout processing, to see it is not lost track of or mixed up with other types. The obvious thing is to mark each piece, which is done, but markings are obliterated by operations such as rolling, and so Revere goes to the length of assigning special personnel to follow each lot of OFFIC Copper from one operation to another, watching carefully to be sure each load is kept intact.

In addition, Revere takes full cognizance of the fact that OFHC Copper for radio purposes must have special qualities. In making anodes, it must be deep drawn, and for the feather-edge seal, it must be capable of being rolled or machined down to .002"/.010". By carefully controlling mill processing, grain size is kept at or below permissible limits. Freedom from oxygen, and from voids, is guaranteed by the method of casting the bars from which we roll the forms required. In addition, there is an operation which results in Revere OFHC Copper being not just commercially free but nearly absolutely free of internal and external defects. This great care in producing copper for radio and radar purposes probably accounts for the fact that Revere is a preferred source of supply.

REVERE PRODUCTS AND SERVICES

All Revere Metals are processed with the care and attention required to assure that they meet all metallurgical and physical specifications. Revere supplies mill products in non-ferrous metals and alloys, and also electric welded and lockseam steel tube. An important part of our service to industry is the Revere Technical Advisory Service, which will gladly collaborate with you on specifications and fabrication methods.

REVERE

COPPER AND BRASS INCORPORATED

Founded by Paul Revere in 1801 230 Park Avenue, New York 17, New York

Mills: Baltimore, Md.; Chicago, Ill.; Detroit, Mich.; New Bedford, Mass.; Rome, N. Y. Sales Offices in Principal Cities, Distributors Everywhere

November, 1948 — ELECTRONICS

HI-Q

TUBULAR CERAMIC CAPACITORS





ELECTRICAL REACTANCE CORPORATION

GENERAL OFFICES:

• FRANKLINVILLE, N. Y.

SALES OFFICES:
• IN ALL PRINCIPAL CITIES

No Service is too Rugged for FEDERAL...



You can specify Federal Mobile Radiotelephone with confidence—and be sure of the finest performance under the toughest operating conditions. At the factory, every Federal Mobile Radiotelephone has to operate at peak efficiency under "engineered" conditions that far exceed those encountered normally in police, fire, taxi, utility, bus, truck, forestry or any other kind of duty.

Every Federal Mobile Radiotelephone undergoes a test even more severe than that given to military tank and aircraft equipment—the Federal "shock test." The unit is vibrated, with-

cut shock mounts, at 5 G's—which is the force of an impact equivalent to 5 times its own weight. This rigorous test continues for 10 minutes while the equipment is in actual operation.

This is only one of the thorough tests which every Federal Mobile Radiotelephone must pass

- and pass with flying colors - before it is shipped. You will find it profitable to get the facts on Federal . . . the shock-tested Mobile Radiotelephone. Write to Department I-716.



Federal's Mobile Transmitter-Receiver Unit



Federal Telephone and Radio Corporation

100 KINGSLAND ROAD, CLIFTON, NEW JERSEY

In Canada: Federal Electric Manufacturing Company, Ltd., Montreol, P. Q. Export Distributors: —International Standard Electric Corp. 67 Broad St., N.Y.

November, 1948 -- ELECTRONICS

PROGRESS REPORT ON C.*

How Microtone uses


twelve Printed Electronic Circuit units

to save space and simplify


production of fine hearing aids!



Models courtesy of The Microtone Co.

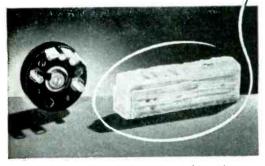

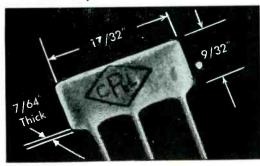MODEL No. 1 RADIOHM (above, left) and ten "Filpecs" molded into a single amplifying unit (above, right) help Microtone build hearing aids that are smaller, more efficient and easily serviced. "Filpec" is shown below.



*Centralab's "Printed Electronic Circuit" — Industry's newest method for improving design and manufacturing efficiency!

Hearing and performance is better... absolutely unaffected by moisture and humidity. Centralab's amazing Printed Electronic Circuit is an important reason and the Microtone hearing aid is important proof. When Microtone engineers switched to P.E.C. "Filpec," here's what they found. Centralab's Filpec cuts down size and weight by reducing the number of components needed. It makes increased production possible by eliminating many assembling operations. It improves performance by minimizing the chance of broken or loose connections.

Integral Ceramic Construction: Each Printed Electronic Circuit is an integral assembly of "Hi-Kap" capacitors and resistors closely bonded to a steatite ceramic plate and mutually connected by means of metallic silver paths "printed" on the base plate.

You'll want to see and test this exciting new electronic develop-

You'll want to see and test this exciting new electronic development. For complete information about "Filpec" as well as other CRL Printed Electronic Circuits, see your nearest Centralab Representative, or write for Bulletin 976.

LOOK TO Centralab IN 1948!

Division of GLOBE-UNION INC., Milwaukee

This NEW Du Mont Type 248-A does the work of 2 oscillographs

WITH THE TYPE 5RP-A CATHODE-RAY TUBE AT 4000 VOLTS ACCELERATING POTENTIAL

The new Du Mont Type 248-A, which replaces the former Type 248 in the medium-voltage field, now employs the Type 5RP-A Cathode-ray Tube at an accelerating potential of 4000 volts. As a wide-band oscillograph (5mc) for studies of pulses and other signals containing high-frequency components, the Type 248-A still provides all the desirable features of the discontinued Type 248. In addition, it may be used immediately as a high-voltage oscillograph simply by plugging in a suitable power supply. No modification is necessary.

Thus the new Type 248-A can take the place of two instruments -a medium-voltage and a highvoltage cathode-ray oscillograph. And, best of all, production economies allow the new Type 248-A to be sold at the same low price of the former Type 248.

Now, more than ever, the Type 248-A excels any instrument in its class!



Du Mont Type 248-A Cat. No. 1244-E, with 5RP2-A \$1870.00

AND FOR OPERATION AT 14,000 VOLTS ACCELERATING POTENTIAL, JUST PLUG IN THE TYPE 263-B HIGH-VOLTAGE POWER SUPPLY

The requirements of modern oscillography frequently demand relatively high accelerating potentials for the investigation and photo-recording of high-speed transients and pulses of extremely low repetition-rates. 14,000 volts accelerating potential is immediately available for these studies, with the Type 248-A, by simply plugging in a power supply such as the new Du Mont Type 263-B. No modification is necessary.

ALLEN D. DU MONT LABORATORIES, INC.

With the power supply and the Type 2088 Projection Lens, the Type 248-A becomes also a projection oscillograph.

The facility with which the range and versatility of the Type 248-A are thus increased, together with the availability of such Du Mont accessories as projection lenses, power supplies and oscillograph record cameras, is further evidence that in oscillography, Du Mont is always your best buy.

Du Mont Type 263-B High-Voltage Power Supply Cat. No. 1208-E \$142.50

Technical details on request



new alesigns ENSURING GREATER EFFICIENCY


in R.F. HEATERS and TRANSMITTERS

Special silver layer gives low-loss high conductivity electrode surfaces.

Special triple mounting allows passage of air along outside of body, and is specially designed for banks of capacitors on extra high R.F. loads.


Ceramic body of special transmitter low-loss ceramic.

TRIPLE MOUNTING TYPE

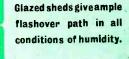

Aerodynamic shape gives improved cooling, particularly with forced draught.

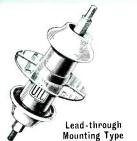Heavy rod connection with double spider mounting gives reliable heavy current connection to inside silver laver.





SAMPLES FROM THE RANGE OF 24 TYPES

TYPE	HLS2033	HLT2024	HLT2 0 23	HLC2013	HLC2013
Capacitance	200	430	500	820	1250
Max. R.F. Load	70	50	50	25	25
Peak Voltage	7.5KV	7.5KV	7.5KV	7.5KV	7.5KV
Max. R.F. Current	30 Amps.	30 Amps.	30 Amps.	30 Amps.	30 Amps.
Body Dimensions	18"×31"	13"×3½"	1 §" × 3 ½ °	$1\frac{3}{4}$ $\times 3\frac{1}{2}$	1音"×3量

★ Lead-through type, all other examples triple mounting type




U.I.C. of England, pioneers in the manufacture of Ceramic Transmitter Capacitors, are foremost in the development of special ceramic bodies for Transmitter Capacitors. These special lowloss ceramic bodies, together with the aerodynamic shape of the capacitor, have made it possible to pack heavy R.F. ratings into small dimensions. U.I.C. "Hi-Load" Capacitors are of rugged construction, electrically stable, and will not deteriorate. Further details furnished on request. All orders and enquiries to:

LTD INSULATOR CO. UNITED

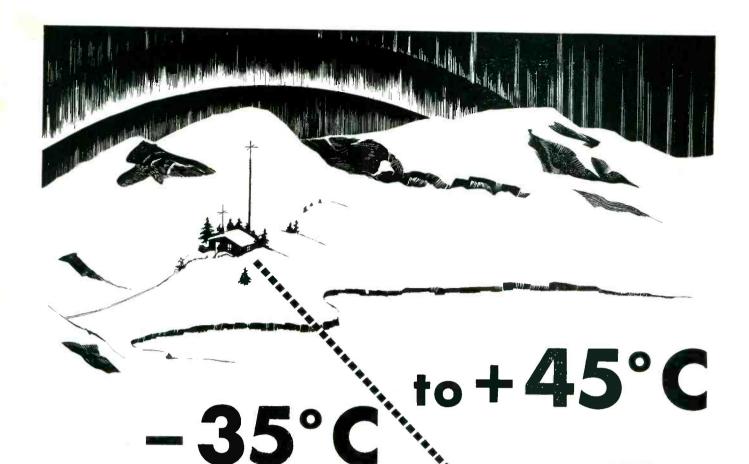TOLWORTH, SURBITON, SURREY, ENGLAND . Cables: CALANEL, SURBITON, SURREY





Aerocom's new V. H. frequency AM radiotelephone transmitter is designed and built to operate amid ice and snow or steaming jungles, and what's more, this fine transmitter will give long trouble free efficient service with low maintenance and operating costs. Built in two models VH-200 and VH-50 to meet your communications needs.

Model VH-200


The model illustrated (VH-200) operates on one Crystal Controlled frequency (plus one closely spaced frequency) anywhere in the range 118-132 Mcs. or 132-165 Mcs., A-2 (with accessory unit) or A-3 AM. Nominal carrier power 200 watts up to 132 Mcs., reduced power up to 165 Mcs. Low temperature operation using gas filled rectifiers. Normal temperature operation using mercury vapor rectifiers. Relative humidity up to 95%. Model VH-50 has similar characteristics except nominal carrier power is 50 watts. Complete technical data on both models on request. Aerocom builds other radiotelegraph and telephone transmitters with accessories, and invites your inquiry if you have a communications problem.

CONSULTANTS, DESIGNERS AND MANUFACTURERS OF STANDARD OR SPECIAL ELECTRONIC, METEOROLOGICAL AND COMMUNICATIONS EQUIPMENT



AERONAUTICAL COMMUNICATIONS EQUIPMENT, INC.
3090 Douglas Road, Miami 33, Florida

DEALERS: Equipeletro Ltda., Caixa Postal 1925, Rio de Janeiro, Brasil * Henry Neuman Jr., Apartado Aéreo 138, Barranquilla, Colombia

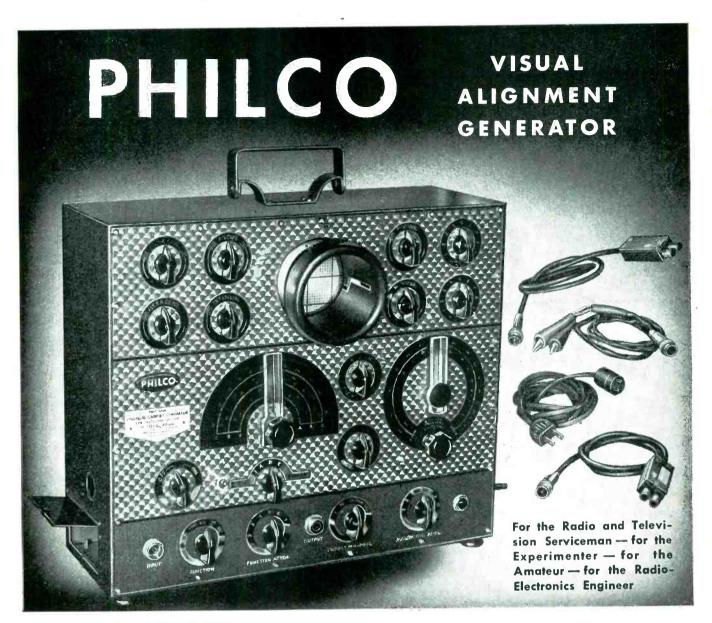

PHILCO 7008

The only completely self-contained and moderately priced instrument for aligning television and FM receivers. Includes 5 different signal generators with their associated controls; a complete oscilloscope with centering, gain, focus, intensity, phasing and blanking controls, and power supplies; separate RF probe for measurements of sensitive circuits without disturbance. Removable crosshatch screen for ultra-short 3" cathode-ray tube. Compartment for cables and RF probe.

WRITE FOR TECHNICAL LITERATURE

Philco Corporation, Philadelphia 34, Pa.

No. 7008 Philco Visual Alignment Generator

No. 7001 Philco Electronic Circuit
Master

No. 7070 Philco RF Signal Generator

No. 5072 Philco Crosshatch Generator

No. 7030 Philo Dynamic Tester

No. 7019 Philco Junior Scope

COMPLETE PHILCO TEST EQUIPMENT LINE

Primarily, to provide for the needs of radio's largest, best informed group of service technicians—the 25,000 members of Philco Service—Philco engineers have created this complete line of precision instruments for radio measurements, in compact, portable, inexpensive form. The unique, practical advantages of Philco equipment are widely known today, wherever electronic devices are used—in communications, laboratories, and industrial plants. If you use, or plan to use, electronics in your work, get the facts now about Philco Test Equipment.

PHILCO CORPORATION · Philadelphia 34, Pa.



RADIO "TRAFFIC COP" with a good heart!

Operating where audio frequencies crowd the thoroughfares, variable attenuators assure precision volume control in speech input equipment for radio consoles, sound motion pictures, public address systems, and television.

With a "traffic cop" of this type in each microphone circuit of a multimicrophone set-up, input volume of one unit can be gradually faded out while that of another is increased; close-up and background program effects can be reproduced with whatever degree of contrast is desired; and the resultant mixing of all microphone inputs can be precisely and smoothly handled, through a master gain control, to meet all variations in program tonal intensity.

Since impedance of a circuit is kept constant while volume is changed, uniform performance is obtained without sacrifice of quality.

To assure topnotch results, the maker -Daven Company of Newark, N. J .specifies that all its resistors, "standards in the industry", be wound with wire drawn from Driver-Harris electrical heat and corrosion-resisting alloys: Nichrome*V, Nichrome*, Advance*, D-H Manganin and the newly developed 331 Alloy which has very high specific resistance and a very low temperature coefficient of resistance.

If you require electrical resistance wire of outstanding uniformity, high stability, and long life, be guided by the example of Daven, whose products are used the world over, and have Driver-Harris supply your needs. For D-H alloys are the very heart of good electrical equipment of all kinds. Send us your specifications.





Nichrome is Manufactured only by

Driver-Harris Company HARRISON, NEW JERSEY

BRANCHES: Chicago, Detroit, Cleveland, Los Angeles, San Francisco, Seattle Manufactured and sold in Canada by The B. GREENING WIRE COMPANY, LTD., Hamilton, Ontario, Canada

*T.M. Reg. U. S. Pat. Off.

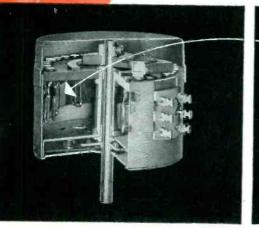


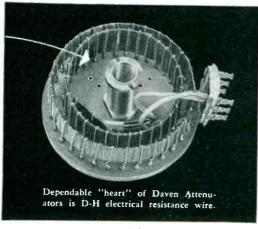




Notably compact, Daven Rotary-type Variable Attenuators are made in sizes from 13/4" to 23/4" outside diameter. Standard units, giving up to 45 steps of attenuation, are available with built-in cueing control, enabling recordings, transcriptions, temote or network programs to be cued without necessity for auxiliary switching mechanism. Accuracy of resistance: from 0.1% up.

THEY'RE BETTER BECAUSE ...

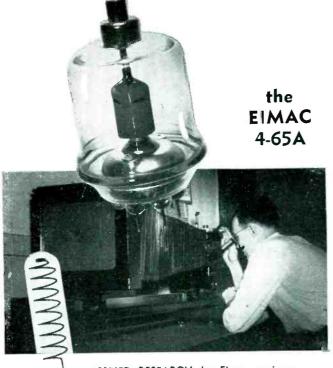

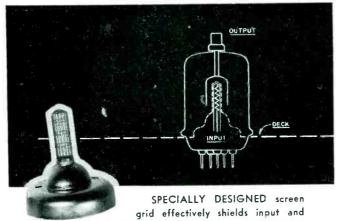APPLIED RESEARCH by Eimac engineers has produced a thoriated tungsten filament with ample reserve emission. Its instant heating characteristics make the 4-65A well adapted to mobile application.




output circuits, within the tube, without excessive screen power. All internal structures are self supporting without the aid of insulating hardware.


These are but some of the features that combine to make the Eimac 4-65A a better tetrode. It is unexcelled in its category as a power amplifier, oscillator or modulator. For example, in typical operation as a power amplifier or oscillator (class-C telegraphy or FM telephony) one tube with 1500 plate volts will supply 170 watts of output power with less than 3 watts of driving power. A complete comprehensive data sheet on the 4-65A has just been released. Write for your copy today.

EITEL-McCULLOUGH, INC. 204 San Mateo Ave., San Bruno, California

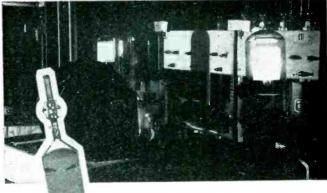
Export Agents: Frazer & Hansen, 310 Clay Street, San Francisco II, California



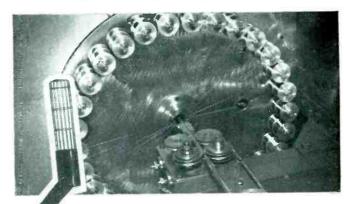PYROVAC* PLATES, the revolutionary Eimac development, withstand excessive abuse. Manufactured by an advanced technique, these plates can handle momentary overloads in excess of 1000%, consequently they contribute appreciably to the tube's life.



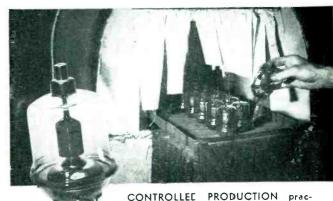EIMAC PROCESSED GRIDS, manufactured by an exclusive technique, impart a high degree of operational stability. Both primary and secondary emission are controlled.




tices include a slow oven-anneal to remove the last vestige of residual strains, and four to eight hours of testing under severe VHF conditions.

*Trade Mark Reg. U. S. Pat. Off.



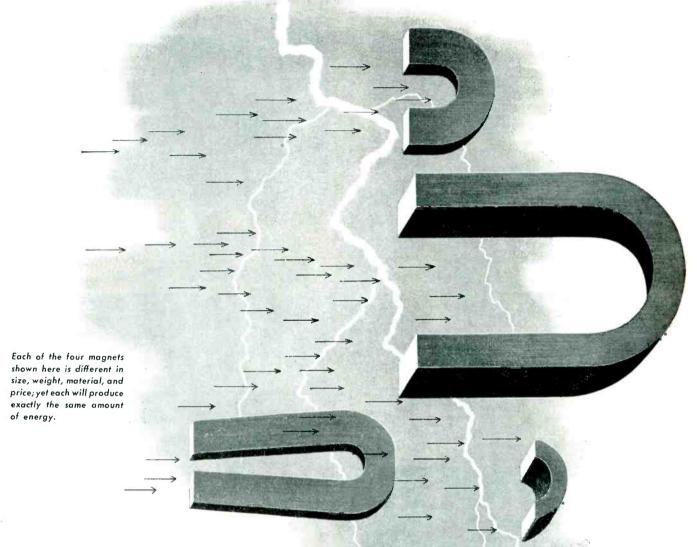INDIANA PERMANENT MAGNETS MAY BE YOUR ANSWER, TOO



"PACKAGED ENERGY" SAVES SPACE, CUTS COSTS

INDIANA permanent magnets fit your need like a doctor's prescription-the right material, the right design, the right magnets to do your job best.

When you buy Indiana permanent magnets, you buy product improvement . . . new and higher efficiency . . . new versatility . . new economy. Today, Indiana magnets are performing operations that were impractical only a few years ago-actually replacing many mechanical and electrical devices-and with less weight, less bulk, lower cost.

For example, certain radar magnets of Alnico originally weighed 14 pounds. Through redesign by Indiana, their size was reduced materially and their weight cut to 3½ pounds. Both were of identical material; both produced the same energy. The substantial savings in weight and cost were accomplished wholly by a change in design. Consultation with our engineers may result in similar savings for you.



NEW! BOOKLET NO. 4-E11-TELLS ALL ABOUT PERMA-NENT MAGNETS. A NOTE ON YOUR COMPANY LETTER-HEAD WILL BRING YOU A FREE COPY.

Indiana is the only manufacturer of all types of commercially used permanent magnet alloys. Continuous research and production control assure top quality and uniformity of all your Indiana permanent magnets, regardless of size or quantity. Call on our Special Design Service in solving your problems.



THE INDIANA STEEL PRODUCTS COMPANY

PRODUCERS OF "PACKAGED ENERGY" 6 NORTH MICHIGAN AVENUE - CHICAGO 2, ILL. SPECIALISTS IN PERMANENT MAGNETS SINCE 1908

PLANTS: VALPARAISO, INDIANA; CHAUNCEY, N. Y.

FREED for Quality & Performance Use





FREED HERMETICALLY SEALED CLASS A GRADE 1 COM-PONENTS ARE APPROVED for JAN-T-27 SPECIFICATIONS.

POWER TRANSFORMERS FILTER REACTORS **AUDIO TRANSFORMERS** SUPERSONIC TRANSFORMER'S WAVE FILTERS HI-Q COILS **DISCRIMINATORS** SATURABLE REACTORS **PULSE TRANSFORMERS** CHARGING CHOKES




TRANSFORMER CO., INC. Dept. NE 72-78 Spring Street New York 12, N. Y.

Special **CAPACITORS**

... engineered by AEROVOX

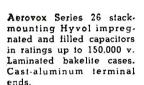Aerovox Series 20 Hyvol impregnated and filled capacitors in ratings up to 50,000 v. in hermetically sealed welded steel cases.



• For those extra-severe-service applications on the largest capacitors, as well as others, Aerovox units have the extra stamina that makes them last. Decades of specialization pro. vide an experience background second to none in solving all kinds of capacitor prob. lems; unexcelled production facilities assure QUAL-ITY as well as quantity. Aerovox capacitors are iberally engineered for

their individual applications. Special multi-layer capacitor tissues ... long-life, non-inflammable Hyvol impregnant and fill... constant filtration and testing of impregnant as regular production routine ... thorough evacuation and impregnation ... Positive hermetic sealingthese facts of Aerovox crafts. manship spell long, trouble. free service.

Aerovox capacitors in daily use speak for themselves. No finer capacitors are built. Aerovox engineers stand ready to meet your most severe require. ments.

Submit your capacitor problem. The tougher the better! Write for literature.



AEROVOX CORPORATION, NEW BEDFORD, MASS., U.S.A.

SALES OFFICES IN ALL PRINCIPAL CITIES . Export: 13 E. 40th St., New York 16, H. Y.

Cable: 'ARLAB' . In Canada: AEROVOX CANADA LTD., HAMILTON, ONT.

lo value equal

Model 260 Volt-Ohm-Milliammeter

There's good reason why this is the world's most por ular high sensitivity volt-ohm-n illiammeter. In every part, from smallest componet to overall design, no competing instrument can show superiority. It outselfs because it outranks every similar instrument. And in the Simpson patented Roll Top safety case, shown here, it brings you important and exclusive pro-

tection and convenience.

. in staying accuracy . in functional design in useful ranges
in sensitivity
in ruggedness in precision

Sub-Panel Assembly—Strong, Simple, Accessible

over resistor pockets remo to show design

The ruggedness, the simplicity of design, and the consequent accessibility of components are shown here. Molded of sturdiest bakeste, the sub-panel provides separate packets for resistors. This separation makes for orderly assembly, highest possible accessibility, and added insulation for preventing shorts. All connections are short and direct. Cable wiring is eliminated. Each batter, has its own com-



The New Simpson Switch Merhanism. You will find no other switch mechanism on the market like this Simpson switch. It is built of molded bakelite discs. Unusually sturdy contacts, of heavy stamped brass, silver-plated for superior conductivity are molded permanently into each disc. They can never come loose, never get out of position. When the discs are assembled into the complete switch, these contacts are self-enclosed against dust. Danger of shorts is automatically eliminates. As the switch is rotated from range to range, the contact is always positive and unvarying.

A ball-and-spring mechanism positions the switch at the selected range by a 3-poist pressure. Switch is thus held securely in place, ye smoothly re-positions to each new range. This mechanism is also self-enclosed against dust in a bakelite housing.




Ask your jobber or write for complete descriptive literature.

RANGES

SIMPSON ELECTRIC COMPANY 5200-5218 W. Kinzie St., Chicago 44, III.

In Canada: Bach-Simpson, Ltd., London, Ont.

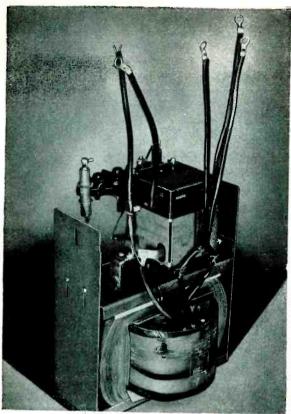A flick of the finger opens or closes the Roll Top front.



This interior view of the Kuhlman 5kva, 4160-120/240 volt, single phase, Oil Immersed Self Cooled distribution transformer shows secondary breaker, protective links, and Bl Core Construction. Secondary breaker mechanism normally closes a signal lamp circuit at a coil temperature of 105° C, and trips the breaker at 125° C. Protective links between primary winding and each line terminal disconnect the transformer from the line in the event of transformer failure. Bl Core Construction, introduced by Kuhlman, pioneered use of low loss steel in distribution transformers. Leads are insulated and protected by Natvar 400 Extruded Vinyl Tubing.



- Varnished cambric—straight cut and bias
- Varnished cable tape
- Varnished canvas
- Varnished duck
- Varnished silk
- Varnished special rayon
- Varnished Fiberglas cloth
- Silicone coated Fiberglas
- Varnished papers
- Varnished tubings and sleevings
- Varnished identification markers
- Lacquered tubings and sleevings
- Extruded vinyl tubing and tape
- Extruded vinyl identification markers

Ask for Catalog No. 21

KUHLMAN OISC TRANSFORMER LEADS

are protected with

NATVAR 400

Distribution transformers are now more vital links in the distribution system than ever before. Not only has power consumption reached a new peak, but the load itself is more widely distributed.

Completely Self-Protecting transformers manufactured by Kuhlman Electric Company, Bay City, Michigan, combine sound design with proven accessories. The result is a self-contained unit.

Natvar 400 Extruded Vinyl Tubing, approved for 105° C is used to insulate and protect the leads because it meets operating temperature requirements, and in addition, has uniformly superior resistance to oil.

Prompt deliveries can be made either from a nearby wholesaler's stock or direct from our own. Full Underwriters' report on request.

THE NATIONAL VARNISHE


TELEPHONE RAHWAY 7-2171 CABLE ADDRESS
NATVAR: RAHWAY, N. J.

PRODUCTS Corporation

201 RANDOLPH AVENUE

.

WOODBRIDGE NEW JERSEY

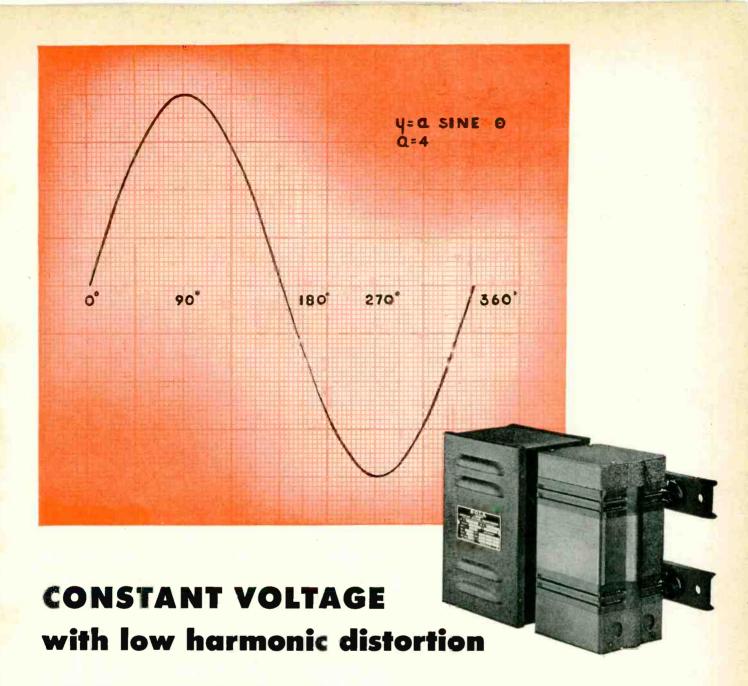

TYPE CVH, an important newcomer in a famous line—a Sola Constant Voltage Transformer designed for use with equipment that requires a source of undistorted voltage. These new transformers, available in 250, 500 and 1,000 VA capacities, provide all of the voltage stabilizing characteristics of the standard Sola Constant Voltage Transformer, with less than 3% harmonic distortion of the output voltage wave.

Since the output voltage wave is essentially sinusoidal, these transformers may be used for the most exacting applications such as general laboratory work, instrument calibration, precision electronic equipment or other equipment having elements which are sensitive to

power frequencies harmonically related to the fundamental

As in all Sola Constant Voltage Transformers the regulation is automatic and instantaneous. There are no moving parts, no manual adjustments and every unit is self-protecting against short circuit.

Type CVH represents an outstanding advance in automatic voltage regulation and an important contribution to precise electronic equipment.

WRITE FOR THESE BULLETINS

DCVH-138—complete electrical and mechanical characteristics of the new Type CVH Constant Voltage Transformers.

DCV-102 — complete engineering handbook and catalog of standard Constant Voltage Transformers available for remedial or built-in applications.

SOLA Constant Voltage TRANSFORMERS

Transformers for: Constant Voltage • Cold Cathode Lighting • Airport Lighting • Series Lighting • Fluorescent Lighting • Luminous Tube Signs
Oil Burner Ignition • X-Ray • Power • Controls • Signal Systems • etc. • SOLA ELECTRIC COMPANY, 4633 W. 16th Street, Chicage 50, Illinois

Manufactured under license by: ENDURANCE ELECTRIC CO., Concord West, N. S. W., Australia • ADVANCE COMPONENTS LTD., Walthamstow, E., England UCOA RADIO S.A., Buenos Aires, Argentina • M. C. B. & VERITABLE ALTER, Courbevoie (Seine), France

BIG RUNS (large or small PARTS)

are everyday business

SILL CAP FOR RAILWAY CARS

at RICHARDSON Manufacturers of

Molded INSUROK R.T.M.

Capacity for big runs is only one of the advantages offered in custom molding by The Richardson Company. A blend of long experience, able engineering, plant capacity and all-around production efficiency helps give you a quality job at a price that's Perhaps you can use these advantages to your advantage.

The RICHARDSON COMPANY

Sales Headquarters: MELROSE PARK, ILLINOIS

here's on-the-job proof of Westinghouse Instrument Performance where reliabilit

Westinghouse instrument specialists are available in the field for consultation on your instrument problems. Call your nearest Westinghouse office, or write Westinghouse Electric Corporation, P. O. Box 868, Pittsburgh 30, Pa.

Send for Booklet B-2209-A, Communication Instrument Booklet

and readability

B-3283, or Switchboard Instrument Booklet B-3363.

Radio stations can take no chances on "outages"—time off the air is costly. For split-second timing, efficiency, and continuity, all vital operating information must be readily available to the control engineer at a glance.

For these reasons, instruments of unfailing performance and quick readability are a must. The Westinghouse instruments at KMOX solved these problems. They also provide co-ordinated styling and smart appearance.

What are YOUR electrical measuring problems?


Would they include—reliable performance . . . styling . . . size . . . readability or different types of service . . . portable ... switchboard ... panel ... recording?

The vast lines of Westinghouse electrical measuring instruments provide you with the answers to all of these problems. Every Westinghouse instrument is backed up by more than 60 years of skill, "know-how", and experience in every field of industry.

Westinghouse Instruments Also Provide You With

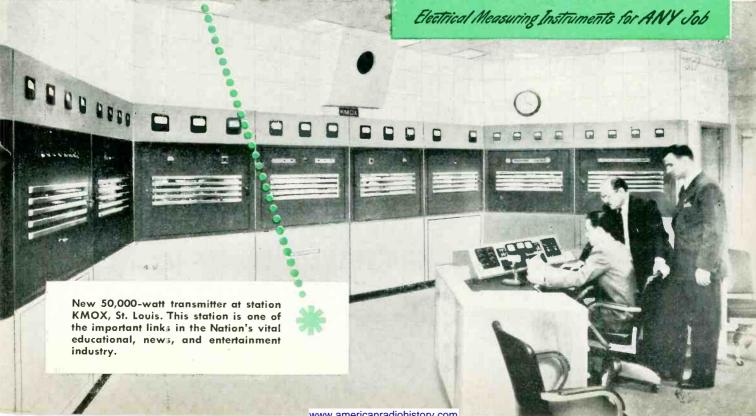- Dials that stay white under all conditions
- Magnets that stay perma-
- Pivots with high shock capacity and low friction
- Springs that remain constant for life
- Quick delivery of more different ratings and types
- Complete Nationwide Serv-





PROBLEMS IS OLD MITCHELL-RAND



With our background of 59 years experience in solving the WAX and COMPOUND problems of the electrical industry, we no longer think it strange that there are so many different and unique specifications and requirements for a WAX and COMPOUND to meet. In these 59 years, more than 3500 WAXES and COMPOUNDS were developed . . . and almost daily a new condition arises calling for a special formula. It was just such a challenge that enabled us to produce the latest in Mitchell-Rand's large line of WAXES and COMPOUNDS-#1366EX: here is a CAPACITOR END SEAL with characteristics, most unusual-check them and see if your electrical apparatus won't benefit from its use.

... and no matter how difficult or involved your insulating and impregnating wax or compound problems are . . . bring them to Mitchell-Rand, the Electrical Insulation Headquarters since 1889.

136 CAPACITOR	6EX END SEAL
Cold Flow	238/243° F
S. P. (R&B)	250/255° F
Pouring Temp.	350/400° F
Color	Tan
Adhesion	Satisfactory
Penetration 77/100/5	o
Chloride Free	Yes
Spec. Grav.	1.55
Flash Point	450° F

FREE FOR THE ASKING...

YOUR'S FOR THE ASKING ..

is this COMPOUND DATA BOOK. The latest work of its kind, it is a comprehensive manual containing all the data, facts and figures, physical characteristics, test methods, active formulas and general applications for Mitchell-Rand's exten-

sive line of Compounds, Waxes, etc. It's free upon written request.



M-R WAXES

PENETRATE fibre . . . floss . . . bakelite . . . paper and cloth. HAVE low viscosity . . . high surface tension . . . good electrical characteristics.

M-R COMPOUNDS

RESIST high voltage breakdown . . salt spray atmosphere . . . humidity . . . cracking or flaking ... acids and alkalis.

HAVE excellent flexibility and adhesive qualities . . . high cold flow and good thermal conductivity MORE THAN 3500 FORMULAS

MITCHELL-RAND INSULATION CO. Inc.


51 MURRAY STREET . COrtlandt 7-9264 . NEW YORK 7, N. Y.

A PARTIAL LIST OF M-R PRODUCTS: FIBERGLAS VARNISHED TUBING, TAPE AND CLOTH . INSULATING PAPERS AND TWINES . CABLE FILLING AND POTHEAD COMPOUNDS . FRICTION TAPE AND SPLICE . TRANSFORMER COA POUNDS . FIBERGLAS SATURATED SLEEVING . ASBESTOS SLEEVING AND TAPE . VARNISHED CAMBRIC CLOTH AND TAPE - MICA PLATE, TAPE, PAPER, CLOTH, TUBING - FIBERGLAS BRAIDED SLEEVING - COTTON TAPES, WEBBINGS AND SLEEVINGS - IMPREGNATED VARNISH TUBING - INSULATED VARNISHES OF ALL TYPES - EXTRUDED PLASTIC TUBING

M-R THE

ELECTRICAL


NSULATION

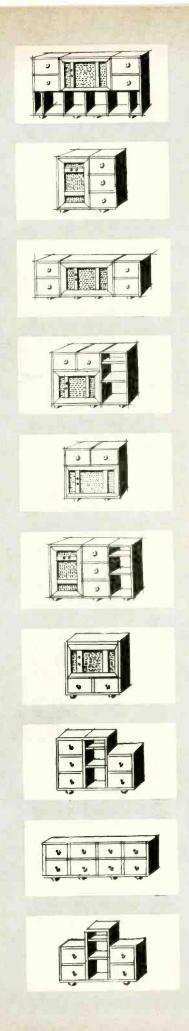

Customode

Customode is the answer to the ever expanding requirements of audiovideo equipment. Today, you may install a 15" speaker, communications receiver, tuner, and a record changer. Tomorrow, you can add a television set, a pick-up for Micro-groove records, and a record cabinet. The illustrations show only a few of hundreds of cabinet variations for Home Entertainment Centers. Designed by leading furniture stylists and electronics engineers, Customode's "building block" versatility enables you to create your own layouts as you wish, when you wish.

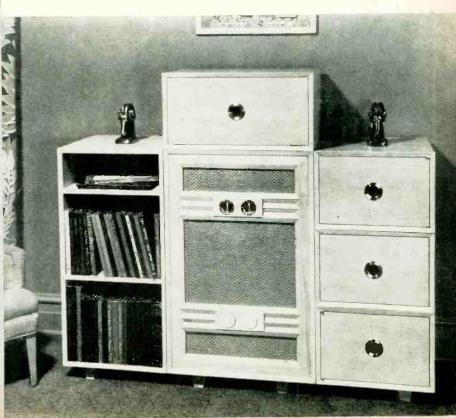
Write today for literature and scale cut-up illustrations. Jensen Manufacturing Company, 6607 S. Laramie Ave., Chicago 38, Illinois.



www.americanradiohistory.com

NOW! Specify KENYON



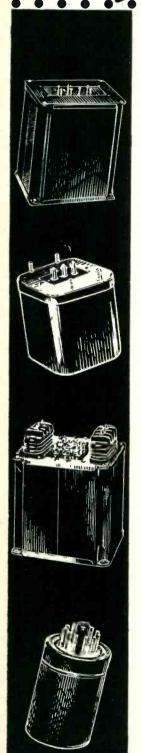

KENYON one of the oldest names in transformers, offers high quality specification transformers custom-built to your requirements. For over 20 years the KENYON "K" has been a sign of skillful engineering, progressive design and sound construction.

KENYON now serves many leading companies including: Times Facsimile Corporation, Western Electric Co., General Electric Co., Schulmerich Electronics, Sperry Gyroscope Co., Inc.

Yes, electronification of modern industrial machinery and methods has been achieved by KENYON'S engineered, efficient and conservatively rated transformers.

For all high quality sound applications, for small transmitters, broadcast units, radar equipment, amplifiers and power supplies — Specify KENYON! Inquire today for information about our JAN approved transformers.

Check Your Requirements

"T" LINE TRANSFORMERS HERMETICALLY SEALED TRANSFORMERS "A" LINE TRANSFORMERS

- PLATE TRANSFORMERS
- FILAMENT TRANSFORMERS
- **REACTORS**
- **∠** CHOKES
- MODULATION TRANSFORMERS
- INTERSTAGE TRANSFORMERS
- INPUT & OUTPUT TRANSFORMERS
- SPECIAL FREQUENCY TRANSFORMERS
- ISOLATION TRANSFORMERS
- ✓ AUDIO TRANSFORMERS
- HUMBUCKING TRANSFORMERS
- AUTO TRANSFORMERS

Now — for the first time in any transformer catalog, KENYON'S new modified edition tells the full complete story about specific ratings on all transformers. Our standard line saves you time and expense. Send for the latest edition of our catalog now!


SEND FOR OUR CATALOG NOW!

KENYON Transformer Co., Inc. 840 Barry Street, New York 59, N. Y.

Send me the latest edition of your new catalog without obligation

Names Address

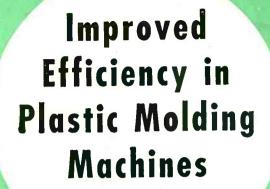KENYON TRANSFORMER CO., Inc. 840 BARRY STREET NEW YORK 59, N.Y.



Rockford's Prize Winning Design uses a **Vibration Control** System

HE outstanding design features of the Rockford Hy-Jector Automatic Molding Machine won one of the five equal awards in an annual product design contest.

A Lord Vibration Control System is an important part of Rockford's design. Here's

what Rockford says:

"In attempting to incorporate the maximum possible tube life and protection for the other components of the High Frequency R. F. Generator used in the Rockford Hy-Jector Automatic Molding Machine for Thermosetting Materials, we chose the Lord Mountings because of their superiority in the field of Vibration Control. They have proven themselves in our application."


This is another example of improved product performance with a Lord Vibration Control

System.

Bulletin 900 is a complete outline of Lord products and services. Write for it today.

LORD MANUFACTURING CO., ERIE, PA.

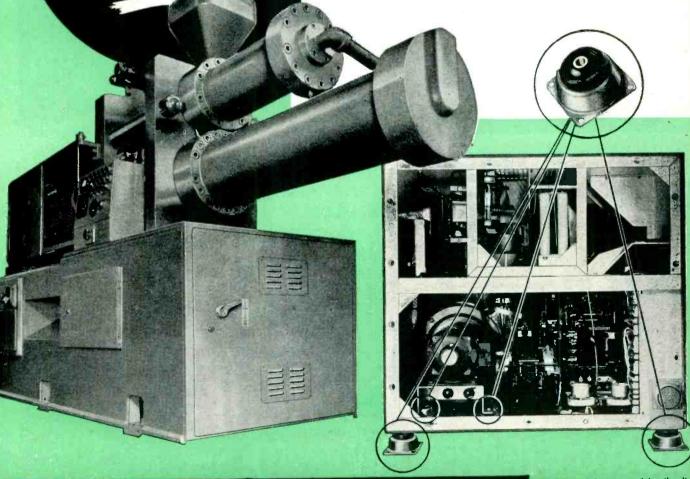Canadian Representative: Railway & Power Engineering Corp., Ltd.



LORD Vibration Control Systems

The entire cabinet containing the dielectric heating unit is mounted on Lord Holder Type Plate Form Mountings, and the blower within the cabinet is separately mounted on smaller mountings of the same type.



When it comes to fitting Budgets as well as Circuits . . .



you can't beat the effectiveness of STRUTHERS-DUNN'S 5,348 RELAY TYPES

HERE ARE RELAYS FOR ALMOST EVERY CONTROL APPLICATION -Data Bulletins available on any of these general types

SMALL RELAYS

POWER RELAYS

SENSITIVE RELAYS

Midget—General Purpose—Vending Machine Large Power—Mercury Swing Mercury Clapper—Nutcracker (D-C)—High Voltage

Low Power-Snap Action

INSTRUMENT-CONTROLLED RELAYS

MEMORY RELAYS (Mechanical Latch) Industrial Types -- Vibration-Resistant Types

SEQUENCE RELAYS Ratchet Types-Multipole Types

Lamp Control—Polarized—Close
Differential—Overload Motor Reversing—Telephone Signalling

SPECIAL-PURPOSE RELAYS

TIMING RELAYS Inertia - Thermal Motor-Operated With 5,348 standard types to choose from . . .

With each type subject to many electrical and mechanical adaptations . . .

Struthers-Dunn can readily match the relay requirements of both your circuit and your budget. Prices are well in line-and, by way of good measure, you get all of the advantages of well designed sturdily constructed relays that are specifically "tailored" for your particular application.

STRUTHERS-DUNM, INC., 150 N. 13th St., Philadelphia 7, Pa.

STRUTHERS-DUNN



..AT 5,000 MEGACYCLES?

.. AT 25,000 MEGACYCLES?

0

Features:

METALLIZED-GLASS
ATTENUATING ELEMENTS

PRECISE AND PERMANENT

CALIBRATION

BROADBAND

CHARACTERISTICS

NEGLIGIBLE INSERTION LOSS

BACKLASH-FREE

VERNIER DRIVE

LOW REFLECTION

WELL SHIELDED CASING

PRECISION VARIABLE ATTENUATORS

These attenuators, utilizing metallic-film-on-glass resistive elements, are of the most advanced design now available. Broadband matching, minimum frequency sensitivity, and constancy of attenuation with time, are but a few of the advantages which this technique affords. Casing designs available cover requirements from that of a simple power control attenuator to that of a precisely calibrated secondary standard.

Metallized glass attenuators are an important type of microwave measurement component in the complete PRD line. Available also are precision slotted sections and probes, impedance matching devices, frequency meters and standard cavities, and all of the other items which make up a complete measurements bench. An illustrated catalog and price list may be obtained by writing to Department E-7, on company letterhead.

66 COURT STREET BROOKLYN 2, N. Y.





With CT's Famous Sealed in Steel Construction

The clean, streamlined appearance and compactness of CT's new Sealed in Steel construction contribute immeasurably to the trim, precision-like effect of any electronic equipment. In addition, CT Transformers provide "steel wall" pro-

In addition, CT Transformers provide "steel wall" protection against atmospheric moisture, efficient magnetic and electro-static shielding, unsurpassed strength and rigidity to withstand shock and vibration, and unusual convenience of mounting.

Two base styles are available for most of the units in this catalog line, one with clearly identified solder lugs in a phenolic terminal board, the other with RMA color coded leads, stripped and tinned for easy soldering.

The design of these new power transformers assures maximum performance with minimum physical size and minimum temperature rise in accordance with RMA standards.

The wide range of carefully selected ratings achieves maximum flexibility of application, close matching with today's preferred types of tubes, and conformance with all industry standards.

Write direct for catalog illustrating, describing and listing the complete line, or contact your nearest radio parts jobber at once.

PLATE AND FILAMENT SUPPLY TRANSFORMERS

Primary 117 Valts, 50-60 Cycles

	777770				,-		
	For CA	PACIT	OR IN	PUT	SYST	TEMS	
	HIGH VOLTAGE SECONDARY		FILAMENTS				
Catalog Number	A.C. Volts	D.C. Ma.			ifier Amps.	No. 1 Volts Amps.	No. 2 Volts Amps,
PC-55 PC-70 PC-85 PC-105 PC-120 PC-150 PC-200	270-0-270 335-0-335 330-0-330 345-0-345 375-0-375 370-0-370 385-0-385	55 70 85 105 120 150 200	260 320 320 320 380 390 390	5 5 5 5 5 5 5	2 2 2 2 3 3 3 3	6.3CT 2 6.3CT 3 6.3CT 3.5 6.3CT 4 6.3CT 4 6.3CT 4.5	6.3CT 1 6.3CT 1
For REACTOR INPUT SYSTEMS							
PR-55 PR-70 PR-85 PR-105 PR-120 PR-150 PR-200	350-0-350 425-0-425 440-0-440 445-0-445 500-0-500 505-0-505 520-0-520 550-370-75-0		260 320 325 325 400 400 410	5 5 5 5 5 5 5 5	2 2 2 2 3 3 3 6	6.3CT 2 6.3CT 3 6.3CT 3 6.3CT 3.5 6.3CT 4 6.3CT 4 6.3CT 4.5	6.3CT 1 6.3CT 1

Also available in the Sealed in Steel constructions:
FILTER REACTORS with current ratings to match power transformers above.
FILAMENT TRANSFORMERS to meet a wide range of modern tube requirements.

requirements.

AUDIO TRANSFORMERS — Input, Output, Driver, and Modulation — that provide uniformly high fidelity response in three frequency ranges: 30-15,000 cycles, 50-10,000 cycles, and 200-3,500 cycles.

CHICAGO TRANSFORMER

DIVISION OF ESSEX WIRE CORPORATION

3501 ADDISON STREET . CHICAGO 18, ILLINOIS



Age-Resistant
Wire Keeps Your
Products Young
... and Keeps
Your Customers
SOLD!



Let's suppose you make a television set, a range, a waffle iron or some other electrical product . . . and Mrs. Jones buys one.



Her friends like its smooth modern design, dependable operation . . and enthuse over its novel features.



But after awhile wire-trouble rears its ugly head, performance goes haywire, again . . . and again.



Then Mrs. and Mr. Jones tell all their friends, and you can say goodby to a customer . . . and a lot of prospects.



1. Magnet Wire. 2. Firewall Hookup Wire. 3. Appliance Lead Wire. 4. A.V.C. Switchboard Wire. 5. Thermostat Control Wire.

TOUGH BREAK?

Maybe . . . but it could have been prevented with wire designed for years of dependable operation under even the most severe conditions. For many products that means permanently insulated Rockbestos wires, cables and cords.

Rockbestos wires, cables and cords—insulated with impregnated felted asbestos and other enduring materials— are the best insurance you can buy against wire-failure caused by heat, flame, fumes, grease, oil ... and age.

WRITE TODAY — for your copy of the new No. 10-F Catalog, sectioned for easy reference to Appliance, Aircraft, Electronic, Fixture, Lighting and Magnet Wires; Apparatus Wires and Cables; Power and Control Cables.

ROCKBESTOS PRODUCTS CORP.

New York Pittsburgh 465 NICOLL ST., NEW HAVEN 4, CONN.
Cleveland Detroit


Chicago Oakland, Calif.

ROCKBESTOS



THE WIRE WITH PERMANENT INSULATION


See How Springs Stay Springy

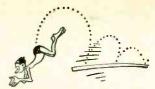

... despite high HEAT and active CORROSION when made of INCO NICKEL ALLOYS



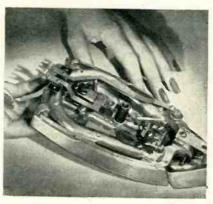G. E. Automatic Toaster uses five Inco Nickel Alloy springs to insure long-time operation. Temperatures up to 500° F.



Yale & Towne "Tip Toe" Automatic Iron uses Inconel coil spring for the flexing arm of the sole plate. Corrosive steam here from damp clothes.



Westinghouse Sun Lamp uses "Z" Nickel springs to support quartz tube inside the lamp. Temperatures up to 750°.


Look at these well-known appliances, and consider the user-benefits they offer the consumer

How to provide for long-time strength and resiliency at elevated temperatures, particularly in the presence of corrosives, poses a problem. The springs in the appliances shown above withstand temperatures ranging from 500° to 750° F. Two operate in the presence of moisture. The springs in the fuse cutout switch shown here maintain their excellent spring properties even when subjected to salt and sulphurous atmospheres in heavy industrial areas.

Inco Nickel Alloy springs are particularly useful in applications where corrosion or high temperatures are present. Their fatigue-resistant properties are often of prime value, but most apparent where corrosion and heat are factors.

For example, consider the G. E. Automatic Toaster: The pop-up spring has to retain spring

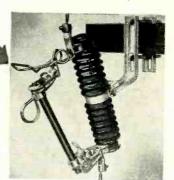properties after long exposure to temperatures up to 500° F. This and three similar springs subject to 400° F. are all made of Monel. The main switch spring, subject to only 300° F. requires close tolerances. If too thick, it might take a set. If too thin it would lack sufficient contact pressure. Full hard Inconel strip .012" x $\frac{3}{8}$ " solves this problem.



The flat "K" Monel spring on the top casting of this fuse cutout holds the fuse under constant pressure against the upper
coating. A coil spring, also "K"
Monel, trips the fuse tube when
the fuse blows. According to
James R. Kearney Corporation
"K" Monel springs "are well
adapted to applications in
heavy industrial areas subjected to a salt and sulphurous atmosphere."


For a more complete discussion of the valuable spring properties of various Inco Nickel Alloys, write for 66 Practical Ideas for Metal Problems in Electrical Products. Address, please,



THE INTERNATIONAL NICKEL COMPANY, INC., 67 Wall Street, New York 5, N. Y.

MONEL* • "K" MONEL • "S" MONEL • "R" MONEL • "KR" MONEL • INCONEL* • NICKEL • "L" NICKEL • "Z" NICKEL

Reg. U.S Pat. Off

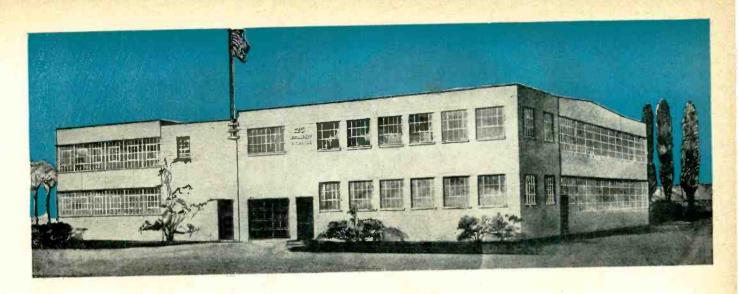


PRESS WIRELESS MANUFACTURING COMPANY, INC.

(Combining Press Wireless Manufacturing Corporation and Milliken Machine Company)

Designer and Manufacturer of Communications, Microwave and Electro-Mechanical Equipment

ANNOUNCES

A NEW 5 KILOWATT TRANSMITTER

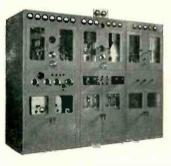


- To augment its already extensive line of Transmitters (ranging from 100 watts to 50 kilowatts) Press Wireless announces a new 5 kilowatt Transmitter, Model T5CM-1, illustrated here.
- This versatile, precision unit, housed in one compact cabinet, is a medium-power, frequency shift radiotelegraph-radiotelephone Transmitter combin-

ing ruggedness and adaptability.

- Press Wireless was first to develop complete "Packaged" Radio Communications Systems—transmitting, receiving and terminal equipment, including everything from the powerline switch to the antenna tower. The PW "Package" purchaser gets not only the most advanced communications equipment available, but he also benefits materially from having everything supplied by the one expert organization.
- Inquiries are invited on communications systems and equipment of any power to meet any requirements.



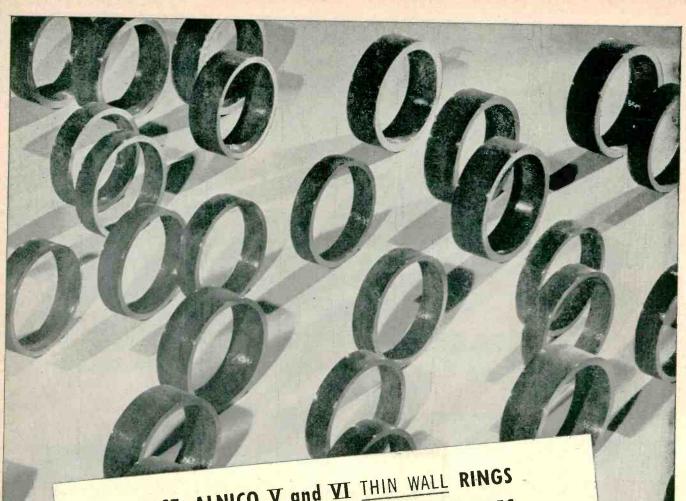

CAST ALNICO Y and VI THIN WALL RINGS FOR MAGNETIC FOCUSING ASSEMBLIES

Quality and Quantity-NO PROBLEM!

In TELEVISION SETS, magnetic focusing eliminates blur; gives clear, sharp reception even during warm-up, or line voltage fluctuations; and the first focusing adjustment is the last. The thin ring-type permanent magnets of Alnico V and VI produced by Arnold for this use (several sizes are pictured here) are cast, not sintered, in order to save on first cost. It's a difficult job, but Arnold's advanced methods produce these rings in the desired quality and any quantity, without trouble. -No matter what the application, in any grade of Alnico or other materials, you can depend on Arnold Permanent Magnets. We'll welcome your inquiries.





THE ARNOLD ENGINEERING COMPANY



Subsidiary of

ALLEGHENY LUDLUM STEEL CORPORATION

147 East Ontario Street, Chicago 11, Illinois

Specialists and Leaders in the Design, Engineering and Manufacture of PERMANENT MAGNETS



STANDARD SPECIFICATIONS

OPERATION:

Automatic (self-interrupting) or remote controlled.

WIPERS:

One to ten, traversing individual contact levels.

INTERRUPTER SPRINGS:

Form 1B (to open the operating circuit at the end of each step). Contacts are single platinum-iridium.

OPERATE SPEED:

Remote controlled operation: maximum 30 steps per second. Self cycling operation: average 60 steps per second, with 48-volt power supply.

FINISH:

Framework and armature: cadmium; Bank contacts and wipers: phosphor bronze.

MOUNTING:

Frame drilled and tapped at each end to accomodate No. 8-32 mounting screw.

DIMENSIONS:

Overall length: 6-9/16 in.; width: 2-3/8 in.; height: 4-5/8 in.

NET WEIGHT:

27 oz., approximately.

SHIPPING WEIGHT:

4 lbs., approximately.

Write for Clare Bulletin 101 on complete details.

For Selection - Sequence Control - Counting - Totalizing

Selection of any channel or circuit path from a total of 26 or 52 circuits is provided by this new CLARE Stepping Switch.

This selection may be at the rate of 30 steps per second on remote control—up to 60 steps per second on self-cycling operations. Operating at these speeds, the switch gives a minimum life of 5 million half-revolutions or 130 million stepping operations.

Each of the ten levels possible for the Type 26 Switch, or the five levels of the Type 52 Switch, is unit-molded in Bakelite. Hand positioning of individual contacts is thus eliminated, and each bank level is easily replaced if a contact becomes damaged in service.

In operation, a pair of double-ended wiper springs is stepped over each bank level of 180 degrees. One end of the wipers is engaged with the bank contact at all times, one end is always free of the bank. The stepping magnet may be remotely controlled or wipers may be stepped automatically by interrupting the magnet circuit through a pair of interrupter springs. As many as eight auxiliary interrupter springs may be provided for other control or signal functions.

Like many other CLARE developments, this new stepping switch was designed to meet a specific requirement . . . has provided an answer to others. Whatever your relay problem, it will pay you to submit it to CLARE. Sales engineers are located in principal cities for your convenience. Look in your classified telephone directory . . . or write to C. P. Clare & Co., 4719 West Sunnyside Ave., Chicago 30, Illinois. In Canada: Canadian Line Materials Ltd., Toronto 13. Cable address: CLARELAY.

CLARE RELAYS

First in the Industrial Field

www.americanradiohistory.com

ELECTRONICS



Designers



A panel instrument for every need

These general-purpose panel instruments are particularly suitable for use in radio equipment and industrial applications where accuracy and quality are required and space is at a premium. Many of the instruments have been newly styled

for better readability and for the smooth, modern appearance that will help give your panels a well-engineered look.

Thermocouple-type instruments, for measurements of high-frequency alternating current in radio or other electronic circuits, are available. There is also a complete line of rectifier types (a-f), for measuring alternating current or voltage at high frequencies or where the source is not sufficient to operate conventional a-c instruments. Typical applications include television transmitters, radar wave meters, testing equipment for electronic circuits. For a full story of G-E instruments, send for Bulletin GEC-227.

GENERAL & ELECTRIC

Digest

TIMELY HIGHLIGHTS ON G-E COMPONENTS



CAGED FOR PROTECTION

Suitable for wall or panel mounting, these cage-type, enameled resistor units employ a strong, high-heat-resisting silicate-compound body which withstands sudden and extreme temperature changes without weakening or in any



way being injured. The resistance wire has a low temperature coefficient so that the resistance remains nearly constant as the temperature increases. Ample protection to the units is provided by the perforated metal case. Each unit is rated at 85 watts and is available in resistance values from 0.5 to 100,000 ohms; one to four units in a cage. For more complete information please contact your G-E representative.

NEED A "LOW VA" VOLTAGE STABILIZER?

General Electric's latest additions to its line of automatic voltage stabilizers are three 115-volt, 60-cycle designs in 15-, 25-, and 50-va ratings. Check the low prices—you may now be able to utilize the advantages of an automatic voltage control for your application. The price consideration plus the low case height and small size will make these units especially applicable to radio chassis and other shallow-depth installations. Other features include totally insulated design, which is necessary where isolation is required between primary and secondary circuits, and universal lead

construction which makes these units adaptable to various wiring and mounting arrangements. If you have an application problem, contact your G-E representative, or check bulletin GEA-3634B.

SOMETHING NEW IN CIRCUIT CONTROL DEVICES

Simplify your circuit designs by replacing complicated and costly components with simple, economical G-E Thermistors. These electronic semiconductors are unique in that the resistance changes rapidly with slight variations in temperature—electrical resistance decreases as temperature rises, and increases as temperature falls. G-E Ther-



mistors give you these five advantages: flexible in application, small in size, available in various shapes, indefinitely stable, and they are economical. These new circuit devices are especially adaptable as sensitive elements in flow meters, liquid-level gages, time-delay relays, vacuum gages, switching devices, and modulating thermostatic circuits. Check coupon for technical report CDM-9.

HERMETIC SEAL ELIMINATES MOISTURE PROBLEMS

The new cast-glass bushings with their sealed-in metal hardware can be readily welded, soldered, or brazed directly to the apparatus, thus eliminating gaskets and providing a better seal than ever before. The small, compact structure of the bushings often makes it possible to



reduce the overall size and weight of the electric apparatus. Bushings are practically unaffected by weathering, microorganisms, and thermal shock. Their great mechanical strength makes them well suited for use in airplanes, etc., where they are subject to continual vibration. Available in ratings up to 8.6 kv and for currents to 1200 amperes. Check bulletin GEA-5093.

MORE SOLDERING WITH LESS POWER

G.E.'s midget soldering iron can do a big job for you with only one-fourth the wattage usually used. This handy 6-volt, 25-watt iron is only 8 inches long (with 1/8" or 1/4" tips) and weighs but 1 3/4 ounces. It was especially designed for close-quarter, pin-point precision soldering. The "midget" offers you all these advantages: low-cost soldering; "fingertip" operation; quick, continuous heat; easy renewal; long life; low maintenance. The iron is a real aid in manufacturing radios, instruments, meters, electric appliances, and many other products requiring precision soldering. Irons and specially designed 115/6-volt transformers are available from stock. Check bulletin GES-3488.



GENERAL ELECTRIC COMPANY, Se Apparatus Department, Schenectady, Please send me the following bulletins	N. Y.
GEC-227 Instruments	GEA-5093 Cast-Glass Bushings
☐ GES-3488 Midget Soldering Iron	CDM-9 Thermistors
☐ GEA-3634B Voltage Stabilizer	/
Name	
ddress	
ty	State

TURN TO PLAX FOR PLASTICS

Plax supplies materials be- low in forms as checked. They are available in a full color range.	SHEET	ROD	TUBE	FIBER	BLOWN WARE	MACHINE PARTS
Cellulose Acetate	V	/	~		W	1
Cellulose Acetate Butyrate	/	/	/	~	~	~
Ethyl Cellulose	~	~	~	~	~	
Methacrylate		~	V	~		~
Polyethylene	V	V	~	~	V	V
Polystyrene			V	/	V	

Vinyls, Cerex, Styraloy, Plexene, and certain special copolymers are also available from Plax, as are special extruded shapes in most materials.

Plax is a leading source of plastics in sheet, rod, tube, and fiber blown forms - also machined parts. This ability of Plax to supply a wide variety of plastics in a wide variety of forms simplifies your task of obtaining the best type of material for your product. Plax of-

fers you many unique plastics develop-

ments, such as the tough and flexible

Polyflex* Sheet, Laminated Polyflex,

PACIFIC COAST REPRESENTATIVE, GLENN H. TAYLOR CO., LOS ANGELES

and Polyflex fiber forms of polystyrene.

At your disposal, too, is expert advice on plastics applications by Plax engineers and a comprehensive library of technical data (see list of literature). These advantages point convincingly to the wisdom of turning to Plax for your plastics requirements — for both materials and the guidance you may need in their application.

*T.M. Reg. U.S. Pat. Off.

WRITE FOR THIS POLYSTYRENE DATA

How to Machine Plax Polystyrene Products.

How to Use Coolants with Plax Polystyrene Products.

How to Cement Plax Polystyrene Products.

How to Polish Plax Polystyrene Products.

Notes on Design and Assembly of Plax Polystyrene Products.

Die-cut Parts from Plax Polystyrene. How to Form Plax Polystyrene Rod.

AND THIS PRODUCT INFORMATION


Data Sheets on Plax Cellulose Acetate, Cellulose Acetate Butyrate, Methacrylate, Polyethylene, Polystyrene and Ethyl Cellulose Products. Article on Plax's Blown Products.

New special plastic shapes by Plax.



P. O. BOX 1019 HARTFORD 1. CONNECTICUT * In Canada — Canadian Industries, Ltd., Montreal The new Collins 737A 5 kw FM transmitter

The most economical way...

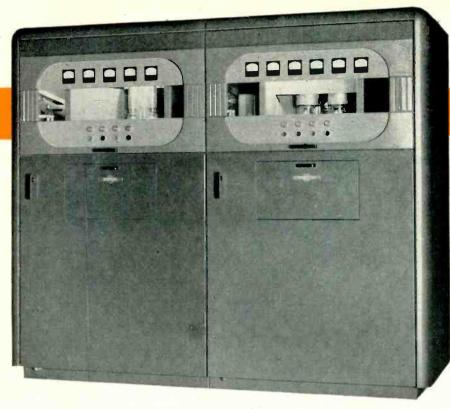

to radiate 20 to 40 kilowatts

Those who hold FM grants for 20 to 40 kw radiated power have found themselves confronted with something of a problem.

Neither a 3 kw transmitter and very high gain antenna, nor a 10 kw transmitter and low gain antenna, is the ideal combination. The first is risky because of transmission line loss, and the second calls for an unduly expensive transmitter.

A better and far more economical balance is found in the combination of the new Collins 737A 5 kw FM transmitter and a Collins four to eight bay 37M FM ring antenna. This transmitter delivers plenty of power to overcome transmission losses to the antenna, and the savings in costs in obtaining 20 to 40 kilowatts of radiated power are very substantial.

The 737A costs much less than a 10 kw transmitter to buy, ship and install. It requires less than 66 square feet of floor space with all doors

open; its external plate transformer approximately 6 square feet. The power demand is only 11.5 kw, 90% power factor at maximum rated transmitter output. The 737A's complement of 29 tubes includes but 10 tube types, minimizing the number of maintenance spares.

You also save in antenna cost. A large transmission line is not required; standard 1 1/8" line will handle the load. Thus windloading is reduced and, especially with the Collins 37M series top or side mounting FM ring antennas, lighter structures may be used.

Economy is an increasingly important factor in the successful conduct of a broadcasting business. Whatever power you intend to put on the air, call us in for consultation. The Collins line of FM transmitters ranges from 250 to 50,000 watts, and includes the only 5 kw FM transmitter on the market!

FOR THE BEST IN FM, IT'S ...

COLLINS RADIO COMPANY, Cedar Rapids, Iowa

11 W. 42nd St., New York 18, N. Y.



YOU, TOO, will be interested

in this advertisement — currently appearing in radio amateur journals — because it contains information of interest also to radio engineers.








Most complete characteristics sheet for a transmitting triode; typical operation data for 8 plate potentials. Also class B Interchangeability Chart demonstrating comparatively the 5514's superiority over other triodes. Write for



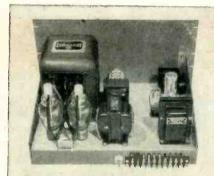WIPEK's complete 350-w, 3.5-to-28-mc, 'phone/c-w transmitter uses 4 Hytran 5514's—class B and C— and only 7 cubic feet of space. QST for Sept., 1947, pp. 37-46.



Two 5514's class B deliver 300 w at 1250 plate v, zero bias. (At 1500 plate v, -4.5 v bias, 5514's will give 400 w class B.) RADIO HAND-BOOK, 11th Ed., pp. 336–337.



WIIVU/6's half-kw rig on single chassis. Economical zero bias throughout. All Hytron: 2E25 osc., 5514 driver, 5514 push-pull final. CQ for Oct., 1947, pp. 32–35.

Tube data sheets are helpful. Those for the Hytron 5514, unusually so. But seeing how the other fellow has put the 5514 to work is even better. The articles describing the illustrated transmitters bristle with "hot" ideas. It will pay you to review them. Write also for both of the 5514 data sheets. Discover for yourself why the Hytron 5514 is so popular: Low internal tube drop and consequent high efficiency at plate potentials from 400 to 1500 volts. Generous output, low drive. Ready interchangeability with other triodes. In short, an economical, all-purpose ham tube designed for hams. Plan to put the 5514

to work in your rig, too. See it - buy it at your



Simple, economical, 3-stage, 3.5-to-28-mc out-fit. Single 5514 gives 43 to 200 w output at 400-1500 plate v. THE RADIO AMATEUR'S HANDBOOK, 25th Ed., pp. 184-187.

SPECIALISTS IN RADIO RECEIVING TUBES SINCE 1921

AND

Hytron jobber's.

GOT TVI TROUBLES?

Two 5514's in properly balanced Closs B R-F-1500 v at 350 ma plote, -4.5 v bias, 6.5 w grid driving power-deliver400 w.c. woutput essentially harmonic-free. See National od p. 85, July QST.

MAKE IT

HOVE

with


alliance MOTORS

Alliance Motors operate automatic controls, valves, switches, fans and blowers, air circulators, motion displays, phonograph turntables, record changers, air conditioning units, room heaters, automobile heaters, electric fans, magnetic disc tape and wire recorders, radio tuning, automatic television tuning, toys, business machines, hair dryers and numerous other devices.


Horse power ratings range all the way from 1/400th up to 1/30th h.p. Alliance Motors are light-weight, compact, and are mass-produced at low cost—made in both shaded pole induction and split-phase resistor type. Designed for particular jobs, some are uni-directional, others are reversible. Alliance makes motors for both continuous and intermittent duty. Wherever designs call for more motion—automatic action—remember, there is an Alliance Motor for the job!

Model in type will up to 1/1

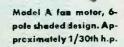Model K shaded pole induction type will develop upto1/100th h.p.



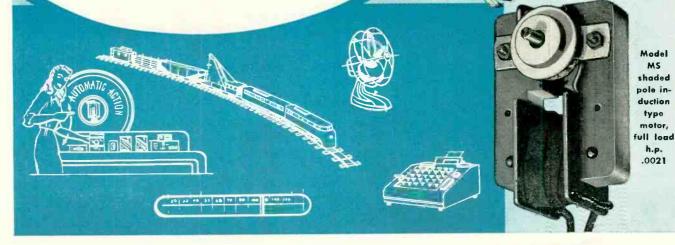Model B—forfans and recorders. Approximately 1/30th h.p. 4-pole shaded pole motor.



WHEN YOU DESIGN-KEEP

MOTORS IN MIND


ALLIANCE MANUFACTURING COMPANY • ALLIANCE, OHIO Export Department: 401 Broadway, New York 13, N. Y., U. S. A.



Frequency Standards



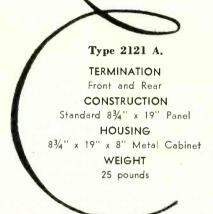GUARANTEED **ACCURACY** 1 part in 100,000 (.001%)



Uses

Time bases, rate indicators, clock systems, chronographs, geo-physical prospecting, control devices and for running small synchronous motors.

features

1. Bimetallic, temperature-compensated fork, no heating or heat-up time is required.

2. Fork is hermetically sealed, no barometric effects on frequency.

3. Precision type, non-ageing, low coefficient resistors used where advantageous.

4. Non-linear negative feedback for constant amplitude control.

- 5. No multi-vibrators used.
- 6. Synchronous clock simplifies checking with time signal.

Specifications

Accuracy—1 part in 100,000 (.001%).

Temperature coefficient—1 part in 1,000,000 per degree centigrade (or better).

Outputs-

1. 60 cycles, sine wave, 0-110 volts at 0 to 10 watts (adjustable).

2. 120 cycle pulses, 30 volts negative.

3. 240 cycle pulses, 30 volts positive and negative. Pulse duration, 100 micro-seconds.

product of

Name..... Company..... Address City.....State

Please send descriptive folder, No. 2121A.

American Time Products, Inc.,

Gentlemen:

580 Fifth Ave., New York 19, N. Y.

AMERICAN TIME PRODUCTS 580 Fifth Avenue INC. New York 19, N. Y.

Operating under patents of the Western Electric Company



flexible insulation you need...

FOR HIGH HEAT PPLICATIONS

UNDERWRITERS' APPROVED FOR

105°C

THE NEW TURBO

35/10%

FEATURING:

- * PERMANENT
 - FLEXIBILITY
- * EXTREME HEAT RESISTANCE
- * NON-COMBUSTIBLE
- * MOISTURE ABSORPTION LESS THAN 1%
- * HIGH DIELECTRIC STRENGTH
- * SMOOTH WALL FINISH
- * EXPANDED RANGE OF WALL THICKNESSES

THERMO PLASTIC TUBING

REL 16-A is the new heat-resistant TURBO Thermo-plastic Tubing that provides an economical and dependable solution to most electric insulating problems involving high temperature. Approved by the Underwriters' Laboratories for continuous operation at 105° Centigrade, REL 16-A safely withstands even higher temperatures intermittently, without deterioration of mechanical or electrical characteristics. In addition to complete stability under high heat, REL 16-A tubing provides permanent flexibility—maintained under


severe temperature conditions, high dielectric strength, negligible moisture absorption (less than 1%). Typical applications in which this tubing offers important advantages over ordinary tubing include the insulation of coils and wiring where baking, potting or soldering is required; equipment with high thermal rise; enclosed units such as motors, generators, transformers, etc. Write today for complete laboratory test results, including UL reports, on TURBO REL 16-A. Samples on request.



WILLIAM BRAND & COMPANY

276 4th Ave., New York 10, N.Y. - 325 W. Huron St., Chicago 10, III.

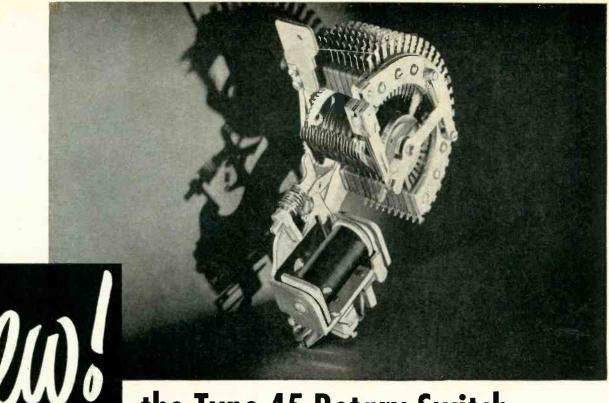Wanufacturers of TURBO FLEXIBLE VARNISHED SLEEVING, FIBROUS GLASS TUBING, PLASTIC INSULATED WIRE, MICA AND MICA PRODUCTS, VARNISHED CAMBRICS, INSULATING PAPER and TAPES, WIRE MARKERS



the Type 45 Rotary Switch

70 Steps a Second Speed Up to 10 (or more) Bank Levels Only 1 Field Adjustment

For all the features you want . . . in any remote-control application . . . look to Automatic Electric's Type 45 Rotary Switch!

SPEED... it's faster! It carries 10 wipers at 70 steps a second on 46 volts d.c. self-interrupted, or at 35 steps a second, externally interrupted.

CAPACITY... it's greater! Ten or more 25-point bank levels can be accommodated on the same frame, and single ended wipers can be provided for 50-point operation.

ADJUSTMENT . . . it's simpler! A rare readjustment of the interrupter springs is all that's normally required.

OPERATION...it's smoother! With an even load on *all* contacts, the Type 45 runs without galloping; there's no chatter or bounce.

ADAPTABILITY... it's more useful! With more levels, faster speed and 25- or 50-point operation, it's suitable for a wider variety of control applications.

For complete information on this switch that's new and better, write for our new circular.



the Type 57 Relay

Here's a new relay, too, that can be used for ordinary relay serviceopening, closing or switching circuits—and for extremely highspeed operation. Independently operating twin contacts assure perfect contact operation. Contact points are dome-shaped to maintain uniformly low contact resistance. They may be arranged in one or two pile-ups with a maximum of 16 contacts on 13 springs in each pile.

See it in Action!

AUTOMATIC AL ELECTRIC

Distributors in U. S. and Possessions:
Automatic Electric Sales Corporation
1033 West Van Buren Street, Chicago 7, Illinois
In Canada: Automatic Electric (Canada) Limited, Toronto

... at the National Electronics Conference


November 1, 2, 3



OW-PRICED because of large production . . . due to ✓ large demand! Shown here are representative G-E power tubes with a nation-wide name for reliability. Specify General Electric tubes in that new transmitter you're designing, to get the biggest dollar-value . . . to get the right tubes (G.E., from its wide list of types, can match precisely your circuit requirements) . . . to enhance your product's standing in the eyes of qualityconscious buyers. A phone-call to your nearby G-E electronics office will bring helpful counsel from tube engineers glad to focus their experience on your problems. Act today!

General Electric economy tubes!

If you operate a broadcast station, you're interested in fast replacement service. Time off the air is money out-of-pocket. General Electric tubes score again . . . there's a G-E distributor or dealer right in your area, with ample stocks on hand, waiting for your request to rush new tubes to you. You get the types you want, when you want them-built right, priced right, sold right with the solid backing of General Electric's tube warranty! Electronics Department, General Electric Company, Schenectady 5, New York.

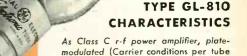

of 1.0).

Filament voltage current Max ratings (CCS): 1,600 v --500 v d-c plate voltage
d-c grid voltage
d-c plate current
d-c grld current (approx) 210 ma 70 ma 335 w plate input

for use with a max modulation factor

plate dissipation 85 w Typical operation d-c plate voltage
d-c grid voltage
d-c plate current
d-c grid current (approx)
driving power (approx)
plate power output 1,600 v



GL-810 TRIODE


GL-828 BEAM POWER TUBE



As Class AB₁ a-f power amplifier and modulator

Filament voltage	10 v
current	3.25 amp
Max ratings (CCS):	
d-c plate voltage	1,750 v
d-c suppressor voltage	100 v
d-c screen voltage	750 v
*max signal d-c plate current	150 ma
*max signal d-c plate input	225 w
*screen input	16 w
*plate dissipation	70 w
Typical operation (CCS), 2 tubes:	
d-c plate voltage	1.700 v
d-c suppressor voltage	60 v
d o suppressed the same	750

*max signal d-c plate current	150 ma
*max signal d-c plate input	225 w
*screen input	16 w
*plate dissipation	70 w
Typical operation (CCS), 2 tubes: d-c plate voltage d-c suppressor voltage d-c screen voltage d-c grid voltage peak a-f grid-lo-grid voltage zero signal d-c plate current max signal d-c plate current	1,700 v 60 v 750 v —120 v 240 v 50 ma 248 ma
d-c suppressor current	9 ma
zero signal d-c screen current	4 ma
max signal d-c screen current	43 ma
effective load, plate-to-plate	16,200 ohms
**max signal plate power output	300 w

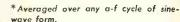

** Distortion only 1 per cent with 20 db of feedback to grid of driver.




ERIE TRIMMERS

for easy assembly and dependable performance at reasonable cost

ERE are six popular ERIE Resistor trimmers, all notable for their fidelity to specifications, their rugged stability, and their straight-line capacity change throughout the total range.

The new miniature style Tubular Trimmers and Styles 554 and 557 open up many design possibilities for added efficiency in chassis layout.

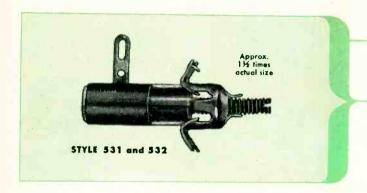General specifications are given below. Samples will be sent to interested manufacturers on request.




STYLES 531 and 532

Capacity Ranges: 0.5-5 MMF & 1-8 MMF

Working Voltage: 500 V.D.C. Max. Temperature: 75°C

Q Factor @ 1 MC .: 1,000 min.

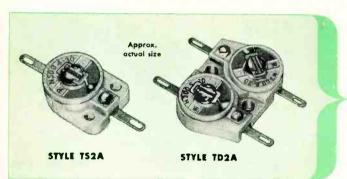Initial Leakage Resistance: 10,000 megohms min. Styles: 531 for panels .015" to .039"; 532 for .040" to .065"



STYLES TS2A and TD2A


Capacity Ranges:

Zero Temp. Coeff. 1.5-7 MMF & 3-12 MMF N300 Temp. Coeff. 3-13 MMF & 5-20 MMF N500 Temp. Coeff. 4-30 MMF & 7-45 MMF

Working Voltage: 500 V.D.C. Q Factor @ 1 MC .: 500 min.

Initial Leakage Resistance: 10,000 megohms min.

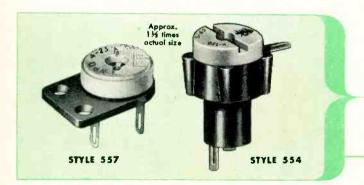Styles: TS2A, Single Condenser; TD2A, Dual Condenser



STYLES 554 and 557

Capacity Ranges:

Zero Temp. Coeff. 3-12 MMF & 5-25 MMF N750 Temp. Coeff. 5-30 MMF & 8-50 MMF

Working Voltage: 350 V.D.C. Q Factor @ 1 MC.: 500 min.

Initial Leakage Resistance: 10,000 megohms min.

Styles: 554 Mounted with Spring-Clip; 557 for

Sub-panel or Bracket Mounting

Electronics Division ERIE RESISTOR CORP., ERIE, PA.
LONDON, ENGLAND . . . TORONTO, CANADA





as high as 50%.

SALES STARCHED UP! Unburred American Phillips Screwheads mean that coin-laundry customers can't snag the clothes they put into machines. And these stay-tight screws mean, too, that washers are less often down for repair. Find out what double-edged production and sales-spurs American Phillips Screws can apply to your product. Write.


AMERICAN SCREW COMPANY, PROVIDENCE 1, RHODE ISLAND

Detroit 2: 502 Stephenson Building



4-WINGED DRIVER CAN'T SLIP OUT

OF PHILLIPS TAPERED RECESS

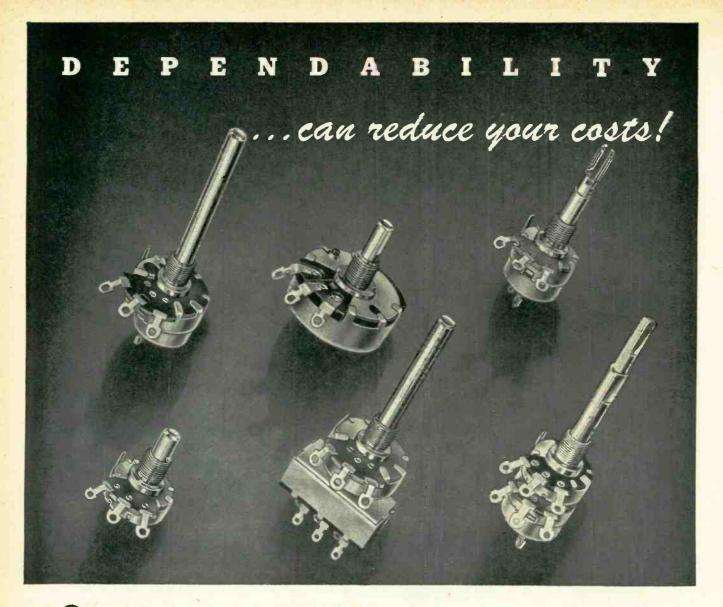

ou can depend on Stackpole controls. Carefully supervised production means that you can depend on each unit to operate satisfactorily after it has been soldered into the circuit — and Stackpole facilities are such that you can depend, too, on quantity deliveries to meet your needs.

In both fixed and variable resistors, Stackpole is a major supplier to an important segment of the radio and electronic industries. If you are not already checking Stackpole regularly as your production releases and design requirements come up, we welcome the opportunity to cooperate on your next assignment. Write for Stackpole Control Engineering Bulletin RC-7D. The Complete Stackpole Electronic Components Catalog is also available on request.

STACKPOLE CARBON COMPANY . ST. MARYS, PA.

STACKPOLE

RESISTORS · CONTROLS · SWITCHES · IRON CORES

G Leads Again



mechanism is both simple and positive in operation.

with 7WO rim drive

DUAL SPEED PHONOMOTORS

for BOTH 331/3 and 78 R.P.M. Records

The new long-playing microgroove records are here. Their enthusiastic reception proves that your 1949 customers will want, and demand, dual speed phonographs—operating at 331/3 R.P.M. for the new records, and at 78 R.P.M. for their existing record collections.

Only General Industries gives you a choice of TWO great new rim drive dual speed phonomotors to meet this profitable market. Built with the same precision that distinguishes all GI products, these dependable rim drive dual speed motors have been thoroughly tested under all operating conditions.

NOW is the time to get complete information about prices and delivery of GI phonomotors, engineered and designed expressly for this newest development in the record industry. Write today to:

MODEL DM—Compact low cost 2 pole, shaded pole motor designed for portables, table models and other instruments in which space is an important factor. Simple speed change mechanism incorporates a special long-lasting molded neoprene belt.

fi.



The GENERAL INDUSTRIES Co.

DEPT. B . ELYRIA, OHIO



ADVERTISING CAMPAIGN IN .

FOR MANUFACTURERS OF ELECTRONIC AND

The 12 monthly issues of electronics and the

Editorially, the 12 monthly issues of ELECTRONICS bring to its more than 30,000 subscribers authentic and complete reviews of technical developments and applications vital to all whose interests lie in any phase of the vast aspects of the electronic industry. Because this technical coverage is so complete and timely - because ELECTRONICS has been outstanding in its field for better than a decade and a half, design engineers of all types, and management, consider it essential to their work.


Manufacturers have learned, either by observation or through conversation with their own engineers, of the industry-wide acceptance and coverage of ELECTRONICS. To them, as well as to engineers, its leadership has been, and is an accepted, proven fact.

It follows, therefore, that there is no better place for a manufacturer to tell his product story - each month - than in the publication read by users of his products. Manufacturers are certain of reaching old customers and prospects or developing new ones. Inquiries from ELECTRONICS' advertising develop new applications and new markets in industries other than are presently utilizing a manufacturer's products. Advertising is certain of careful readership—where it will do the most good in terms of eventual sales. The reason, therefore, that more manufacturers names, both big and small, are regularly seen in the advertising pages of ELECTRONICS.



electronics - First in RECOGNITION -

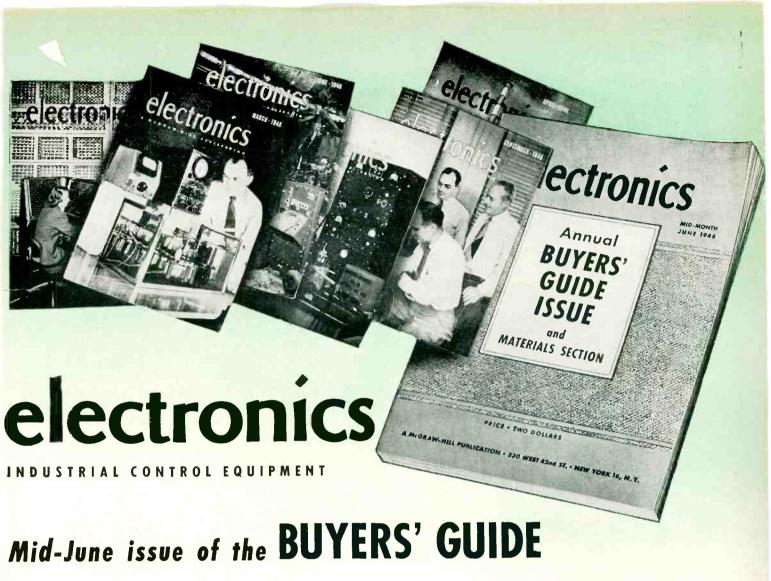A McGRAW-HILL PUBLICATION 330 WEST 42nd ST. NEW YORK 18, NEW YORK



bool

FOR THE 1949

Budget NOW

13

ISSUES OF

electronics

The Buyers' Guide serves several distinctly different functions than those of the month-ly issues of ELECTRONICS. First: It is accepted and used as the only complete reference book in the industry. Secondly: It includes a "where-to-buy-it" function in the carefully compiled Directory Section. Thirdly: Its catalogue-type of advertising provides design engineers with technical data on ALL of the manufacturers' products. In this respect it serves as a condensed summary of the advertising in the 12 monthly issues and permits a manufacturer to catalogue his entire line in one issue. Lastly: It saves valuable time for the busy engineer in locating data on a particular component he is designing into some equipment.

These are only a few of the many exclusive features of this recognized reference book.

They are, however, the basic reasons for the long and important list of Buyers Guide advertisers and its wide use by both management and engineers.

Plan now to use it in any campaign designed to sell electronic and industrial control equipment manufacturers. Keep in mind that this one issue is used throughout the year—that it is the only complete reterence book on product data and product source. As conclusive proof a manufacturer can quickly determine its wide and valuable use by simply questioning his own engineering staff.

First in IMPORTANCE — First in PREFERENCE






electronics edition

November 1948

FOR TELEVISION RECEIVERS

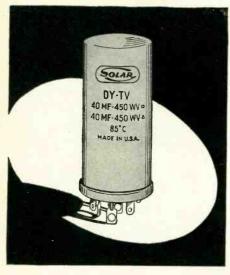

Solar's new Type DY-TV series of dry electrolytic capacitors assures dependable operation under the severest conditions found in television receivers.

An especially developed Solar processing technique makes possible small yet sturdy capacitors designed for high temperature operation with no sacrifice in long life or electrical characteristics.

Because of the remarkable film stability of Solar's DY-TV series of electrolytics, there is but an extremely small change in power factor and leakage current from room temperature to 85° C.

Type DY-TV capacitors, with their special film formation, do not "run away" when voltage is applied after idling under no-voltage conditions at 85° C. These characteristics are retained even after extended shelf life.

Investigate this remarkable achievement in capacitor design today! Write today for catalog.

Solar Manufacturing Corporation 1445 Hudson Blvd., North Bergen, N. J.



BUSINESS BRIEFS

By W. W. MacDONALD

Mobilization Of Industry to meet any possible international contingency is a major concern in Washington and it is known that the powers-that-be are currently studying at least one plan prepared by people in our field. While it would be inadvisable on many counts to disclose the details of such plans, even if they were known, it may be that random thoughts on the subject, picked up by an editor in his travels, will be helpful. . . .

It seems obvious that the ability of any industry to quickly contribute to a war effort would depend to a great extent upon its health at the time such an emergency arose. Thus the number of manufacturers doing a profitable peacetime business in, for example, television apparatus, might be a major factor.

Experience in the last war indicates that while it is in the main desirable to utilize companies having complete engineering as well as production know-how and facilities to head up major projects the number of companies employed as prime contractors should be materially increased.

Despite the obvious wastefulness and risk of design obsolescence involved when government agencies place pilot orders in advance of an actual emergency it seems apparent that no amount of paper planning is such good insurance in a field involving complicated development and manufacturing machinery as cash from the public till.

In particular, it should be remembered that highly specialized component parts not ordinarily employed in commercial gear constituted a major bottleneck in the production of all kinds of electronic apparatus in the last war and that in this branch of the industry at least advance stockpiling or something comparable to it will inevitably be necessary.

More later on this extremely com-

plex problem as the situation develops.

Exhibitors at the Third National Instrument Conference down in Philadelphia (excluding Associations, publishers and other nonmanufacturing groups) totalled 150 firms. Ferreting around the booths, we determined that 66 of them employ tubes or other components inherently electronic in nature in the construction of their products and we'll bet that many of the others have something of like nature on the drawing boards back home.


This is a high percentage when compared with what we remember about the first and second shows, and very gratifying when it is considered that the attendance consisted largely of members of the Instrument Society of America, the Industrial Instruments & Regulators Division of the American Society of Mechanical Engineers, the American Institute of Physics, the Joint Subcommittee on Electronic Instruments of the American Institute of Electrical Engineers and the Scientific Apparatus Makers Association.

A Washington Engineer has devised a neat chassis for use by men who spend a lot of time experimenting with breadboard layouts. It comprises a piece of metal bent into a shape that accommodates tube sockets and other parts required in the average small piece of electronic gear, has half-adozen parallel busbars supported on insulated terminal strips built in and is used with clever little connectors and clips that permit the bars to be used for most wiring.

We understand the gizmo will shortly be available in commercial form

Mixed Blessing to componentpart manufacturers is the growing popularity of television, largely at

PRESENT THINKING ON RESISTORS IS

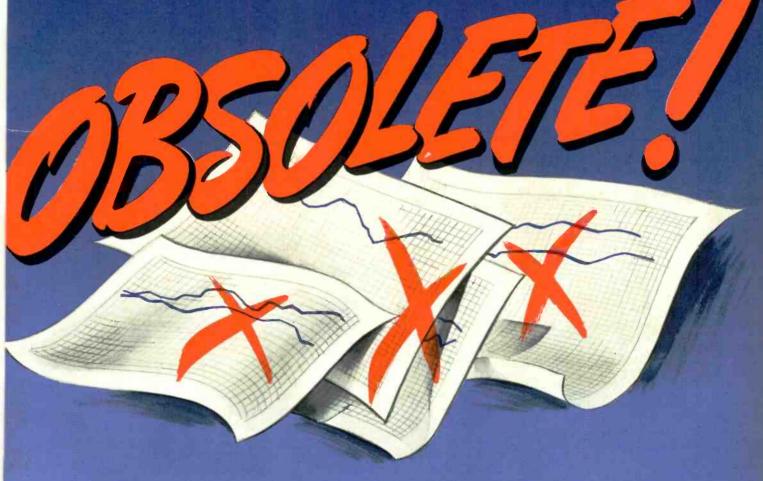

discard your current standards of performance for fixed composition resistors



ANNOUNCES A NEW ADVANCED RESISTOR

Read the following pages carefully, they will affect your planning for years to come.

NEW IRC BT RESISTORS obsolete all present standards

Review your resistor reSURPASSES quirements in the light
SURPASSES quirements in the light
SURPASSES quirements in the light

New red



TYPE

BTR . . . unexcelled at 1/3 watt

BTA unexcelled at 1 watt


RT-2 unexcelled at 2 watts

Test Results for ½ watt Type BTS—equally outstanding performance of ⅓, 1 and 2 watt types is shown in Catalog Bulletin B-1.

BT means Better Technically

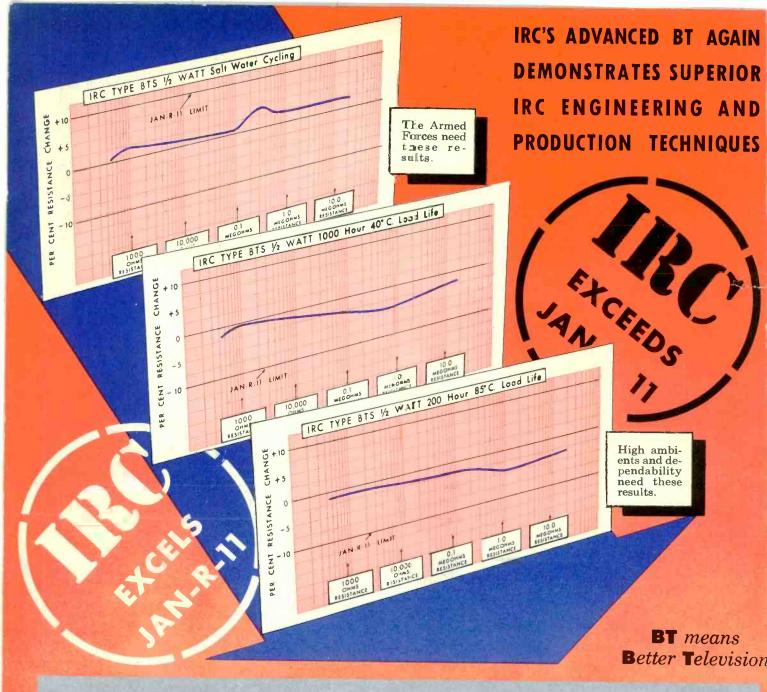compare this ADVANCED resistor to JAN-R-11 SPECS





There is no blue sky surrounding this advanced resistor. Performance of this new Type BT has been proved by independent testing agencies. It is in production now . . . hundreds of thousands are coming off production lines daily. Its outstanding characteristics are particularly evident in high ambient temperatures, and it easily performs the rigorous requirements of television.

Standards for resistor performance set by this new IRC

resistor are so advanced, you need complete information on its characteristics. Although Test Results shown here are only for ½ watt Type BTS, comparable data is available for BTR, BTA and BT-2... Technical Data Bulletin B-1 gives you the full story. We shall be glad to rush it to your desk or drawing board... or to have our representative review your requirements in the light of this advanced resistor. Use the handy coupon below.

International Resistance Co.
401 N. Broad St., Phila. 8, Pa.

I want to know more about IRC's advanced BT Resistor:

Send me Technical Data Bulletin B-1
Have your representative call—no obligation.

Name.

Title

Company

Address



POWER RESISTORS •
PRECISIONS • INSULATED
COMPOSITION RESISTORS •
LOW WATTAGE WIRE
WOUNDS • RHEOSTATS
• CONTROLS • VOLTMETER
MULTIPLIERS • VOLTAGE
DIVIDERS • HF AND HIGH
VOLTAGE RESISTORS

INTERNATIONAL RESISTANCE CO., 401 N. Broad St., Philadelphia 8, Pa.
IN CANADA: International Resistance Company, Ltd., Toronto, Licensee

PREPARED BY

In Important Sale at AUCTION

OF THE VALUABLE

ELECTRONIC COMPONENTS AND MANUFACTURING MATERIALS SURPLUS TO THE PEACETIME REQUIREMENTS

OF THE SUBMARINE SIGNAL COMPANY

7-11 SEARS ST., BOSTON, MASS.

ON THE PREMISES

M.A 00:01 to 8481 (A108 vol , ypbasuT nO

THE PROPERTY TO BE SOLD CONSISTS OF LARGE STOCKS OF COMPONENTS BOUGHT TO HIGHEST QUALITY STANDARDS FROM THE COUNTRY'S BEST KNOWN MANUFACTURERS

Some of the more important items are indicated below:

METERS, Hundreds, all types, by Weston, G.E., Triplett, etc., in substantial lots.

SOLDER, quantity in excess of 2,000 lbs. Kester Solder in 5 lb. spools.

SWITCHES, Thousands—Cutler Hammer, Mallory, H & H, Micro, in all styles, Push, Toggle, Gang, etc.

RELAYS, Thousands—Edison, Ward Leonard, Struthers

Dunn, in all types,

BEARINGS, Ball, Roller, many types & sizes by SKF, New Departure, Fafnir and others.

FUSES, quantity in excess of 200,000, Fuse Links, Fuse Blocks, Fuse Clips.

PLUGS, Receptacles, Connectors, Socket, quantity in excess of 50,000 by Amphenol, Cannon, Jones, etc.

SPEAKERS and Headsets by Jensen, Western Electric, etc.

SPEAKERS and Headsets by Jensen, Western Electric, etc.

Mallory, all types and sizes,

LUGS, Terminals, Spaghetti, Winding Tapes, Potting Compounds, Waxes and many other manufacturing supplies.

Space does not permit the listing of more than a few representation—WRITE OR WIRE FOR YOUR COPY TODAY. To any one interested in obtaining bulk quantities of Electronic Materials, this sale offers a very exceptional opportunity.

XHIBITION

liems to be sold may be examined from Nov. 22d to Nov. 29, inc. (Sunday & Holiday excepted) between the hours of 9:30 A.M. and 3:00 P.M.

TRANSFORMERS, quantity in excess of 10,000, Plate and Filament, Power, Audio, by Raytheon, G.E., UTC, Westinghouse, etc., also Chokes.

Mostly tractional HP. some Selsyns, Autosyns, Gear

Mostly fractional HP. some Selsyns, Autosyns, Gear Reduction Types.

ACUUM TUBES, quantity in excess of 20,000 include—

VACUUM TUBES, quantity in excess of 20,000 include— RECEIVING TYPES 2A3, 6L6, 6H6, 6V6, 6AC7, 6AK5, 6SC7, 6SH7, 2X2, 76 etc.

CATHODE RAY TYPES 5CP1, 5BP1, 5FP7, etc.
Voltage Regulators, Rectiffiers, Crystals, Thyratrons,
Magnetrons.

LAMPS, Miniature, quantity in excess of 80,000 including Mazda 51, 53, 52, 55, 8-6 many others.

MAGNET WIRE, quantity in excess of 10,000 lbs. in Plain Enamel, Single Cotton, Double Cotton, Single Silk, Includes considerable Litz.

HOOKUP WIRE, #16—#18—#20 Guage Shielded and

CABLE, Quantity in excess of 200,000 Ft. Co-ax, R.F., Microphone, Power, etc., single and multi-conductor, many shielded and armored for Marine use.

CAPACITORS, quantity in excess of 20,000 Fixed-Postage, Tubular, Bathtub, Receiving and Transmitting types all well known makes represented.

CONDENSERS, Variable, National, Cardwell, Millen, Etc.,

RESISTORS, quantity in excess of 100,000 Composition, Wire Wound, Fixed and Variable, all types and makes represented.

BOSTON, MASS. OWNER SUBMARINE SIGNAL COMPANY
SUBMARINE SIGNAL COMPANY
SALE IS BY ORDER OF

SAMUEL T. FREEMAN & CO.

27 William St. New York, 5, New York ROSTON, 10, MASS. 80 FEDERAL ST.

1808-10 Chestnut St. Philadelphia, 3, Pa.

INDEX TO ADVERTISERS

161 '0 802 802 802 802 801 192 801 191 191 191 191 191 191 191 191 191 1	FR. 6 T. 7. 100. T.	Laboratories, Co. Time de Co. Time. Time. Time. Co. M. d. Mille (Sill Books, H. Co. M. d. Mille (Sill Books). L. Corporation becaused the Co. M. d. Mille (Sill Books). Mille (Sill Books). L. Corporation on the Co. M. d. Mille (Sill Books). Mille (Sill Books). Mille (Corporation on the Corporation on the Co. M. d. Mille (Sill Books). Mille (Corporation on the Corporation on the Corporation on the Co. M. d.	taghdagh xovanyak xovanyak xovanyak a yoligh a yoligh yo
162 881 142 261 142 122	Inc	Lahoratories, to receive to rateries to receive to the to the to the total total to the total total total to the total tot	Lampkin Lavoie L. Legri S L. Leland, II. Lenkurt B Lewis Litte Linde Air
251 161 160 160 160 160 161 161 161 161 16	.00., Inc. 0., Inc.	fineering Co. al Products ransformer C der Co. der Co. der Co. o., asser Co.	End elda Hann Hann Tonynah Tonynah Hannah Tonynah Tangan Tangan
282 243 183	B., Cinch Mit	CO. E. F.	Jensen Mf Johnson C Jones Dir Gores, Groot
Pt9 10 11 15 15 15 15 15 15 15 15 15 15 15 15	h	Tracding Clot feel Product Timer Corp. I Resistors of Manufacture Manufacture I Mechine I Mechine I Mechine I Resistan	Listagent 2 sensibnt 2 sensibnt 1 sistagent 2 sensibnt 2 sensibnt 2 sensibnt 2 sensibnt 2 sensibnt 2 sensibnt 2 sensibnt
982 983 981 981 981 981 983 983 983 983 983	co.	Harman Harman II Harman Go., Inc for, John Inc Instrument Inc., Inc.	Handy and Harvey He Hashaway Harydon M Heineman Heineman Heineman Heinett-P
961 777 961 19 987 987	o. 117 159, 202, 228 57, 159, 202, 228 0rp orp	Deptics Deptics Deptidustries Coidustries Coidustring Metallizing C	Chemical Electron General Ha Gorhard M Graphite I Gray Rese
822 . 02 62 782 . 782 .	Instrument Corp. Endio Corp. Inc. ies	amera and lengther and lengther Co., selection and lengther Co., training training training and lengther length	Fairchild (Federal Traf Freed Traf Freed Traf Fugle-Mille
61 622 632 632 632 632 632 632 632 632 632	orp. The Jing- satories its Co.	Reactance C gineering Wo oducts Laboi ce, Inc. The Corp. or Corp.	Electrical Electro Eng Electro-No Electro-Vo Electronic Electronic Electronic Eric Regist

118 517 540 540 128 128	er Co., X. S. Harden Lines, Inc. M. S. Harden Laboratories, Inc. Hered W. Harden Line. Harden Line. Harden Works, Inc. harden Works, Inc.
883	inno, Ltd.
99	dio Devices, Inc.
131	dio Devices, Inc.
012	dio Development Co.
883	atic Company
7 9 I	and standard of the
117	nold Engineering Co. row Electronies, Inc. Wire and Stamping Co.
218	orl anigorbald wor
91	Section of principal blog
27I 96I	aconda Wire & Cable Co.
100	nerican Screw Co. nerican Television and Radio Co. nerican Time Products, Inc.
88T	orien Television and Kadio Co
69	terican serew co.
29T	nerican Gas Accumulator Co. nerican Lava Corp. nerican Phenolic Corporation
69T	егісан Ілауа Согр.
96I	terican Gas Accumulator Co
003	bed Radio Corporation bits Metalls, fac. ce Lausing Corp. certean Electrical Heater Co.
TIT	ee Lansing Corp
t61	ha Metals, Inc
677	ied Radio Corporation nied Bai
11	
63	en-Bradley Co. en Co., Inc., L. B. iance Manufacturing Co.
192	en Co., Inc., L. B.
121	en-Bradley Co.
003	ovox Corporation craft Radio Corp.
80	nent, Inc.
t 3	deplay communication maintena
	on Co., Inc., H. W.
122	o Transformer Mfg. Co., Graham Div.
148	

91	Burnell and Co	
83	Burlington Instrument Co	
52	Browning Laboratories, Inc. Buck Engineering Co., Inc.	
81	Browning Laboratories, Inc.	
22	Brown-Bridge Mills, Inc.	
g	Brand and Co., Wm.	
22	Bradley Laboratories, Inc.	
178	Boland and Boyce, Inc., Publishers	
33 T2	Billey Electric Co	
83	Istwax Corporation	
83	Bird Electronic Corp.	
13	Beta Electronics Co	
T	Bentley, Harris Mfg. Co.	
18	Bendix Ariation Corp., Pacific Div	
T_	earnoter to the first spirit is a spirit spirit in the spi	
4T	Barry Corp. Works, Inc.	
13 83	Barker and Williamson, Inc.	
160	Barber Labs., Alfred W.	
120	Ballantine Laboratories, Inc.	
83	Ballantine Laboratories, Inc.	

126	11 03 8304
91	ornell-Dubilier Electric Corp.
PPI	continental Screw Co.
312	Continental Electric Co
ĩŧĩ	Ousondated Monded Products Corp.
212	onn, Ltd., C. G. Sonsolidated Products Corp
181	Condenser Products Co
182	ollins Radio Co.
19	Olips Radio Co
912	Corp., Signand
75T	leveland Container Co.
112	larostat Mfg. Co., Inc.
677	Jark Crystal Co.
4.1	lark Crystal Co.
LII	dio a manufacturing corp.
34	Wire Corp.
	thiengo Transformer, Div. of Essex
CF2	hieago Condenser Corp.
Ĩž	centralab, Div. Globe-Union, Inc. 14, 15.
617	arter Motor Co. inc.
112	SAFER MOIOF CO.
CCI	or borundum Co
188	apitol Radio Engineering Institute
	annon Electric Development Co
81T	
	allite Tungsten Corp.
203	gro'd gatawarr atille

881	•	õ	ã										1	I	τ	Iê	1	IV		٠.,) u	I	•	• - 1	84	1	ß,	I	4	u	Ю	ш	111	O
212	٠			٠	٠	٠	٠	٠	•		٠	٠	•	•				ď	1	O.)	o i	ļ.i	1	J	ð	Į5	Ŧ	ļ	u	0	ш	a	a
98	*			٠	•	٠	٠	٠	٠		٠	•		٠						•	0)		S	ij.	ı.	ı	3	1	٠.	19	Λ	ij	a
68T	•		0	,	,	٠	٠	٠	٠	•	•	•	•	٠	•	•	•	B		ı	10	Ш	Ų	11		•	.(),)		Į,	Α	į.i	a
212	٠	٠		٠	٠	٠	٠	٠	٠	٠	•	٠		ι	C	ij	31	1.5	D	L	O	Э		2	31	ij	u	ы	0	э		A	W	e
813					٠	٠	٠		•	•	•	٠	•	•	1	B.	Þį	19	u	u \	y	į	0	•	o	э	1	μ	[.7	į	Ί	I	Bi	O
LOL	90	ì	y	13	1	35													+	• •	٠.	٠.	٠)				L Ei	

٠			•	٠	•			•		. ე	u	1	•	0	Э	u	O i	μı	31	u	31	П		18	,)	iч	4.	ıΘ
																o		10	11	30	Į)	ρŧ	ıΙ		Э	i٦	40	160
٠			٠	٠	٠	٠	٠		•						. 5	ŭj		ʻu	3	n	οį	п	10	Ю	L	Ū	16	91
40	22	12	× .								•	·o	u	T	***	2	- 2	tu	IJ	0	ð	11	28	u!	H		63	[5]
	•		•			i								٠٠	7	sv	ш	oı	i.		٠	٠.,	u	ı Ì	•	u	06	ID



.. make them faster, with EASY-FLO with EASY-FLO and solutions.

These two low-temperature silver brazing alloys provide every property essential to both current-carrying connections and structural joints in electrical work.

High strength and ductility, high electrical conductivity, strong resistance to oxidization and corrosion — you get them all when you braze with EASY-FLO and SIL-FOS.

And the combination of low working temperature, extreme fluidity and silver content exclusive with both alloys, give you these results with substantial savings in time, labor and cost.

BULLETINS 12-A AND 15 give you full details. Write for copies today.



(continued)

the expense of radio. There are, roughly, ten times as many parts such as resistors and capacitors in the average television set as in the average radio receiver, so makers of these components are feeling little pain. On the other hand, television receivers still use only one component such as a loud-speaker, so unless and until unit sales become comparable with those achieved in the radio business in recent years some component-part manufacturers will be unhappy.

Television will eventually be a bonanza to all of these boys but temporarily it may cause something of a revolution in the parts business.

It Seems To Us that during the war everybody and his brother ground crystals. Now they are winding coils.

Receiver Sales by RCA licensees during the first half of 1948 totalled 8,606,057 units, worth \$328,413,690. Here's the way the total broke down:

		- "
Type	Units	Dollars
Electric		
Table (under \$12.50 billing price)	g	
price)	1,415,531	\$13,256,747
Table (over \$12.50 billing	g	
price)	-	
A-M	. 2,286,923	42,569,939
A-M/F-M	152,720	5,731,705
F-M (including conventers)		1,211,081
Consoles	,	
A-M	53,855	3,542,348
A-M/F-M		793,121
Table-Radio-Phonos	. 0,040	7,00,122
A-M	352,313	16,354,665
A-M/F-M		573,467
Console-Radio-Phonos	. 0,001	0101201
	373,873	35,376,577
A-M		54,514,481
	. 500,911	04,014,401
Battery	. 1,253,492	23,047,960
Portable A-C/D-C		
Table		4,576,992
Consoles		10,653
Auto	1,654,854	52,950,657
Television		
Converters		05 455 044
Radio Table Models		35,477,011
Radio Consoles		
Direct Viewing		10,294,232
Projection	6,795	4,090,976
Radio Phonos		
Direct Viewing	43,850	17,476,145
Projection	1,356	1,002,756
Phonographs		
Phono Only	. 141,998	2,897,059
With Radio Attachment	3,645	191,711
Without Cabinets		
A-M	30,873	1,201,113
A-M/F-M		1,073,207
Television		209,087
2000		
TOTAL	8,606,057	\$328,413,690
IOIMBALL	,,,	T, 2, 0

Transmitter Makers will want to sharpen their pencils on this one: There are approximately 300 f-m broadcast station construction permits on the FCC's books. It is a good bet that most of these

people have already selected their gear. Less than 100 new applications are on file.

By contrast, a more liberal attitude on the part of the Commission toward new a-m station applicants, and a flock of applications for permission to increase a-m power, is swelling this market. And applications for television licenses are, as is well known, jamming clerical and other facilities.

Still more important: orders for transmitters for purposes other broadcasting, particularly f-m transmitters, are pouring into most plants.


Just To Prove (if proof is necessary) that this columnist is not infallible note that in August the following brash statement was made: "In Australia 45 firms make radios but only one makes tubes." This we hasten to amend (after being jogged by our friend E. W. Burnett of Philips Electrical Industries of Australia Pty. Limited) to read: "In Australia 45 firms make radios but only two make tubes."

Sidelight on the GE story featured in October ELECTRONICS is the difficulty we had determining the precise location of 'Electronics Park" with respect to the center of Syracuse. The boys up there said it was north and slightly east (as well they might since at least one company circular says so in uncompromising black and white) while a map, straightedge and our own keen eye said it was north and a gnat's eyebrow west.

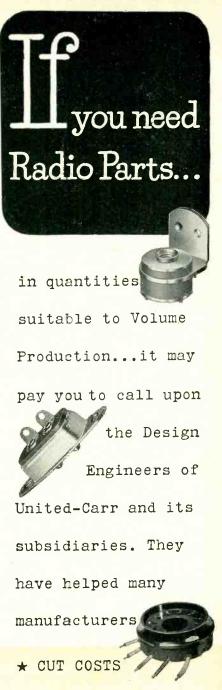Exercising our usual editorial judgement in the face of what could easily become a crisis, we have decided that for us henceforward the Park is just plain *north*.


Latest Example of unconscious humor on the part of our drafting department was a slip in the letter ing on a block diagram, which we fortunately caught before making a cut. The original drawing called for the words Repetition-Rate Multivibrator. This came out Reputation-Rate Multivibrator.

A handy device, no doubt, but not one for which we can suggest a practical design approach.



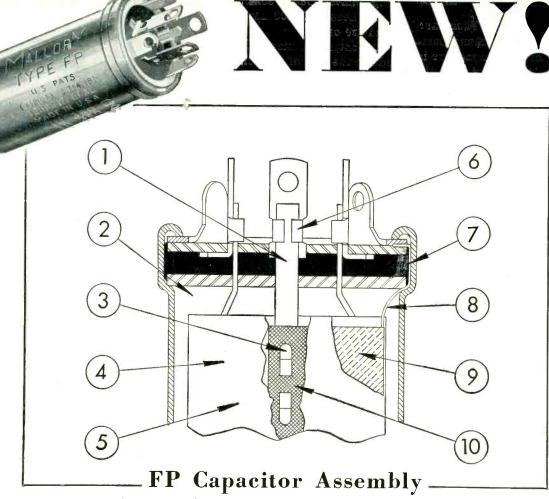- * SPEED PRODUCTION
- * TURN OUT FINER
 FINISHED PRODUCTS





For the past ten years Mallory FP Capacitors have set new standards of dependability.

Now new improvements make them more reliable than ever.

- 1 New design anode tabs cannot break from vibration.
- (2) Ample air space retained for gas expansion at elevated temperatures.
- (3) New staking method between anode and tab permits higher discharge currents.
- (4) Improved high surge separator material better at high temperatures.
- (5) Unique processing improvements provide still better performance at 85°C. No voltage derating required by Mallory FP capacitors at this temperature. (Including the 450V rating.)

- (6) Lower tab to terminal contact resistance for sensitive circuits.
- Textra heavy rubber seal for high temperature and ripple conditions with venting feature preserved.
- (8) Heavier cathode tab for better tab to ring weld, lower resistance and more rugged mechanical construction.
- ⑤ Special etched cathode (all voltages) reduces loss of capacity under high ripple conditions, lowers RF impedance and remarkably reduces intersection coupling.
- (1) Increased FP anode ratio of 12 to 1 at 450V and 15 to 1 at 150V provides better design factors.

Still cost no more. Mallory FP capacitors have given exceptional performance at prices comparable to ordinary capacitors. These new improvements have all been accomplished without extra cost to the user.



Yours for the asking!

Send for the Mallory Capacitor Catalog, which contains useful data on all types of Mallory Capacitors—sizes, electrical characteristics, test measurements, mounting hardware.

MALLORY CAPACITORS
(ELECTROLYTIC, OIL and WAX)

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



CROSS TALK

- ► STRATOPIX . . . The argument for Stratovision has taken a new turn in the discussion now centering on the expansion of television into the frequencies above 475 mc. As proposed for use in the present commercial channels, airborne transmissions were open to objection on two grounds: First, Stratovision produces a uniform field strength which would provide rural service, but probably could not overcome the high noise levels in outlying cities. Second, one Stratovision station would put off the air a score of ground-based stations on the same channel and thus would foster monopoly. But television on uhf is a different story. The uhf noise level in cities is not so high, so more uniform coverage would be obtainable. Second, it looks as though a groundbased uhf station would have so limited a range (see p 68, this issue) that it would be difficult to cover suburban areas, let alone rural districts. Thus the question of monopoly is overshadowed to a large extent by technical considerations. A comprehensive field test is in order to test Stratovision's capabilities in the uhf band.
- ► ARGUMENT... We thought Jeremiah Courtney's "What's Wrong with U. S. Frequency Allocations?" (p 73, August) would start something. It brought a rejoinder from A. L. MacIntosh of the FCC, published in this month's Backtalk column (p 240). We recommend a careful reading of both sides of the argument.
- ▶ ANDB... The Air Navigation Development Board is an agency deserving every support of the electronic industry. Its purpose is to guide and support the development of a system of air navigation and traffic control, the so-called "common system" which will assure safe all-weather flight in military and civil aircraft. Administered jointly by the Secretaries of Defense and Commerce, it will bring together the requirements of the Navy, Air Force and the civil airlines, lay out specifications for equipment and let contracts for development of some 30 items of electronic equipment ranging from ground radar to auto-

pilots. In approximately ten years ANDB plans to spend 80 million dollars on research and development, and Congress has looked favorably on its plans. When the final system is proved in, the amount spent for production of the equipment will run into many hundreds of millions of dollars. This huge program is essential to the future expansion of aviation, which is now stymied by its inability to meet heavy schedules in bad weather. Aviation and electronics have wrestled with this problem for ten years or more. The all-out effort to solve it looms big; it should keep a large segment of our industry busy for the next decade.

▶ PARTICLES . . . Time was when the electron and proton sufficed to describe the structure of our material world. Then came the positron. Then, a decade ago, it became impossible to ignore the neutron. For a while these four particles held the stage to themselves. The neutrino was suggested but, being virtually impossible to detect, it has remained a figment, a dream particle. But lately the cosmic-ray physicists have bumped into the meson, and the flood gates are down. We have positive mesons and negative mesons, mesons of several different masses, all transitory, living long enough only to leave a track in a cloud chamber. Most lately we have the "heavy component" of cosmic rays.

Understandably, the discoverers of these latter-day particles have tended to label them "fundamental." But other physicists, clinging to the hope that nature has a simple core, say it is only a matter of time before mesons will be found to consist of aggregations of electrons and positrons. We hope so too. Things are tough enough without multiple-valued mesons cluttering up the landscape.

Whatever the future may hold, there is some comfort in the fact that, since electronics began, only two types of particle have amounted to anything in practical electron tubes, electrons and ions. If we add the absence of an electron, the "hole" of the transistor, we have the lot, so far as practical electronic engineering goes.

The PROSPECTS

JTAC reports to FCC that service on 475-890 mc is possible only with high field strengths, and predicts megawatts must be radiated by ground-based stations to give results comparable with present service. Suggests study of Stratovision, satellites

HERE to find additional spectrum space for the burgeoning television broadcasting industry is one of the most perplexing questions now facing the FCC. To explore the prospects of expansion into the uhf band from 475 to 890 mc, the Commission held a hearing late in September and invited the Joint Technical Advisory Committee (JTAC) to present evidence. The JTAC report, a 200-page document, contained an analysis based on information collected by IRE and RMA committees.

The conclusion reached by JTAC is that television on 475-890 mc cannot hope to provide the same grade of coverage over as wide an area as the present channels from 54 to 216 mc offer unless a radically different form of broadcasting, such as Stratovision or satellite stations, is adopted. This sweeping conclusion is based on the propagation characteristics of the uhf band, coupled with performance characteristics of the uhf band and uhf equipment.

The first point made by JTAC is that high field strengths will be required for uhf service. The FCC rules establish a field of 500 microvolts per meter as adequate for residential-rural service on the 54-216 mc channels. The report shows that a field strength ten times as great, or 5,000 microvolts per meter. will probably be required for the same grade of service in the 475-890 mc band. This increase is based on the fact that the effective heights of uhf antennas are smaller, the transmission-line losses substantially greater, and the noise inherent in uhf receiver circuits considerably greater than on the presently-used vhf channels. Thus 2.650 microvolts per meter would be required to produce a 30 db signalto-noise ratio at the viewing screen, using a dipole at 475 mc, 50 feet of 300-ohm twin-lead cable, and a receiver with a 13-db noise figure.

This figure applies to 6-mc blackand-white service comparable to the present commercial practice. A wideband color-television service at the opposite end of the band (890 mc) would require 20,000 microvolts per meter, even if a directive antenna having a voltage gain of 4 were used. The report indicates that there is much room for improvement in antennas, transmission lines and receivers.

In city districts, the FCC rules provide a field strength ten times that for residential districts, to overcome man-made noise on whf channels. On uhf channels such man-made noise is not so prominent, so the same increase in field strength may not be required. But a value between 5,000 and 50,000 microvolts per meter would be required for city service on uhf channels.

Coverage Problems

The remaining question is whether such high field strengths can be established at any great distance from the transmitter, using presently available power levels. The answer is definitely in the negative. The RMA Television Transmitter Committee reported to JTAC that the maximum power available from existing tubes, over a 6-mc channel, is 2,000 watts at 475 mc and 500 watts at 890 mc. An antenna power gain of 10 is immediately available, so the effective radiated power ranges from 5 to 20 kw, depending on the position in the band in which the transmitter operates. Such low power levels cannot produce a 5,000 microvoltper-meter field at a distance of 20 miles, let alone at the 40-mile range typical of present performance on vhf channels.

These conclusions are based on the Norton propagation formula

HOW TO EXPAND?

Television broadcasting today presents a troublesome paradox. In late September, of the 124 television stations authorized by the FCC, less than 40 were on the air. Yet the industry already sees a shortage of channels. Over 300 additional applications for television station licenses await action, and in many heavily populated districts the supply of channels is exhausted. All this, despite the fact that no television station is today meeting its expenses.

To find room for more stations, the FCC is considering the uhf band now reserved for experimentation with color and high-definition monochrome service. The pros and cons of uhf operation were analyzed by JTAC at the Commission's request, with the results here described. Whatever the outcome, to secure maximum service from the proposed new channels, many new techniques must be explored

for UHF TELEVISION

and on measurements of field strength made from an experimental transmitter on the Empire State Building, which operated on 510 and 910 mc. Along one radial, the 5,000 microvolt-per-meter contour was found to fall at 15 miles, despite the fact that the antenna height was 1,060 feet and the figures were converted to an effective radiated power of 100 kw. Along other radials the required field strength was propagated out 30 miles, but fell far short of the 50 miles predicted by the Norton formula.

Even assuming that the Norton formula is applicable to the uhf band, and using the nominal value of 500 feet for transmitting antenna height, the report shows that 5,000 microvolts-per-meter can be delivered to 40 miles only if 214 kw of effective power is radiated. This power is at least 10 times that available from existing experimental equipment. In contrast, the Norton formula predicts, and experience verifies, that 50 kw radiated from a 500-foot antenna at 65 mc will radiate the 500 microvoltsper-meter required for vhf service to 42 miles.

Perhaps most surprising is the fact that when the experimental results from the Empire State transmitter are averaged and substituted for the Norton formulation, similar performance could be obtained (5,000 microvolts-permeter at 40 miles) only if the effective radiated power is in the range from 5 to 20 megawatts. As the report states, this is more power than has ever been radiated in any broadcast service in any region of the spectrum, and beyond foreseeable attainment of the future.

The report concludes from this evidence that conventional ground-based transmitters may not be suitable for uhf television service and suggests the possibilities of airborne transmitters and satellite

stations be investigated as alternatives.

System standards (number of lines and frames, bandwidth, type of sync signals, modulation, etc) are necessary before uhf television service can be instituted. An investigation conducted by an RMA subcommittee revealed that the present commercial standards (6mc, 525-line, 30-frame picture) are technically feasible for use in the uhf service and if adopted would permit existing vhf receivers to receive the new service with the addition of a frequency converter and a uhf antenna. Since one objective of the study was to find ways of expanding the present service, such compatibility with existing equipment is evidently a basic requirement. But it is possible that modifications of the existing standards, and possibly wholly new standards, could be set up to provide a superior service, while still permitting existing equipment to receive the serv-JTAC recommends that this possibility be carefully studied, in the immediate future, before adopting system standards for uhf tests.

The need for development of a color-television service must not be forgotten in the expansion of monochrome service, the report warns. It recommends that the FCC continue to reserve space in the uhf spectrum for the experimental development of color and high-definition monochrome service. No system standards for such wideband services are proposed, however, since JTAC considers that these systems are not yet ready for commercial operation.

Equipment Availability

Investigations by IRE and RMA committees revealed that no commercial equipment for transmission or reception of uhf television is now available, and indications are that from 1 to 3 years will be required to develop such equipment to the


point of commercial production. One encouraging report was that a new water-cooled tube, capable of producing 10 kw of power at 890 mc, is under development and may be proved in by next year.

Further measurements of propagation effects (especially tropospheric propagation which may cause serious interference far bethe normal interference vond range) are required before an allocations plan can be set up. JTAC recommends that such measurements be made during the 1 to 3 year period required for the production of transmitters and receivers suitable for the band. study should include a detailed field test of the field strengths required for residential and city service, the interference protection ratios required for co-channel and adjacentchannel stations, and the coverage attainable with available transmitter power. Moreover, the special capabilities or limitations of airborne and satellite stations in these respects should be investigated.

Plan for Future Hearing

The JTAC report concludes with a recommendation that another hearing be set by the FCC in approximately six months to receive additional evidence on propagation and coverage. At this hearing, and in the light of additional information, definite systems standards (either the existing standards or variations of them compatible with existing receivers) should be decided upon. The number of channels in the uhf spectrum and the portion of the spectrum to be used should also be decided at this time.

Acting on this information, the industry can then proceed to develop equipment and transmission methods best adapted to uhf service and the service can be instituted commercially as soon thereafter as the propagation studies are completed.—D.G.F.

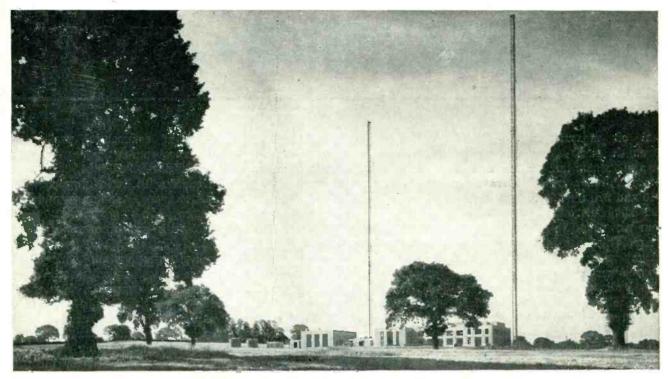

BBC 200-kw station at Droitwich, England, operating on 200 kc

INTERNATIONAL

A review of world-wide practices indicates the international character of all European radio broadcasting and the extent of wire-network public-address systems used in many countries. Despite exploitation of radio as a propaganda medium, the potentialities of broadcasting as known in the U. S. and Canada have barely touched much of Europe


Y ITS VERY NATURE, broadcast-Bing is international. Yet few engineers seem to have either the time, or the inclination, to regard it as such. Stuck away in offices working a slide rule, or watching meters at the transmitter, the broadcast engineer too often sees only the domestic side of the picture. For him, the FCC is the god to be appeased, and the creator of the rules under which he operates. NARBA is a word which comes into the conversation when the going gets really technical, but not many stop to think what it means or how it affects their bread and butter.

Yet without it the conditions of the North American ether would be chaotic, and within a very short time many stations would be forced to close down owing to excessive interference. The Standards of Good Engineering Practice and the Rules and Regulations of the FCC are not the composition of only that body, but reflect the contractual obligations proposed by the North American Radio Broadcasting Agreement, which is adhered to by the U. S., Canada, Cuba, Mexico, Newfoundland, the Bahamas and Bermuda.


The system of allocating radio

frequencies to the countries of the world requires much more space to give even a brief description than is available here. Moreover, to do justice to the great amount of work and thought which these conferences and conventions entail, the history of their growth would have to be included.

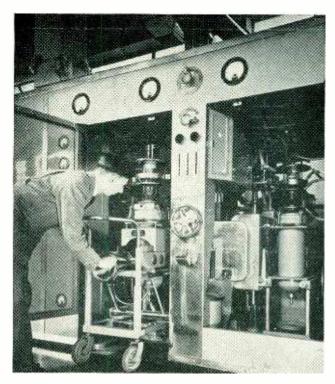As far as domestic and North American region operations are concerned the most vital controls and regulations spring directly from NARBA, and indirectly from the International Telecommunications Conventions which are held periodically. The most recent one



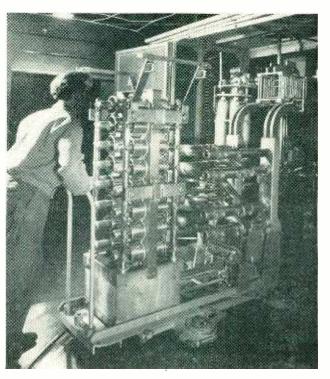Changing a 50-kw tube in EBC final amplifier. Dolly speeds work and avoids damage to equipment



One of several pretuned final tanks used at Skelton, England being wheeled into position

BROADCASTING

Table I—License Fees for Private Canadian Broadcasting Stations

By JOHN H. BATTISON

Allocations Engineer American Broadcasting Co. New York, N. Y.

concerning the broadcast engineer was the Atlantic City Convention. Up until October 2, 1947, the convention of Madrid, 1932, had governed the radio transmissions of most countries of the world. On January 1, 1949, the operations of 72 countries will be affected by the changes made in the International Union of Telecommunications.

The actual allocating of frequencies and recording of requests is the job of the International Frequency Registration Board, which is composed of eleven members and is charged with the equitable allocations of frequencies and supervision

Class, and Power of Station in Watts	Service Radius in Miles	Population in Service Radius	License Fee
Class A			
100 or less	18	Under 25,0000	\$ 50 100 250 400 500
Class B			
250	24	(Under 25,000	100
$\begin{smallmatrix} 500 \\ 1,000 \end{smallmatrix}$	31 37	25,000 and under 50,000	200 300
1,000	31	50,000 and under 150,000	500 700
Class C			
5,000	61	(Under 100,000	500
10,000	72	{ Under 100,000	$\frac{1,000}{4,000}$
Class D		(Over 500,000,	1,000
15,000	77	Under 500,000	3,000 4,000
Class E			1,000
20,000	82	Under 500,000	5,000
25,000	87	Over 500,000	7,000
Class F			
50,000	100	Under 1,000,000	8,000 10,000
Class G		(0,00 1,000,000,	10,000
50,001 and over	Fee det	ermined by Order in Council	

Table II—Facilities of Major Countries

Country	Operation	Freq and Max Power in kw	Number of Stations	Number of Receivers	Notes
Afghanistan China	Government Government	h-f 20 m-f 100 h-f 35	62 16		Planned for all to commence in 1948
England	Government	l-f 200 m-f 200	1 53	11,233,500 includes 43,500 tele licenses as	This does not include tele or f-Synchronized operations, 10 statio from 1 to 60 kw in one group, several groups all told, mostly groups of
		h-f 100	31	of Feb. 1948	stations. One group consists of to 100-kw stations. Separate license r quired for car radio
France	Government. Also commercial prewar. Final policy not yet definite	m-f 100	47	8,000,000 approx includes estimated 2,000,000	French stations suffered extensive datage when the Germans retreated, be reconstruction progress has been go
Germany (American Zone)		m-f 100 h-f 1	6 3	unregistered 8,789,008 Nov. 1947. These are	Western Allies plans are for eventure of operations to German These exclude occupation recreation
(British Zone)		m-f 100 h-f 25	6	approx figures	networks. License fees of 2 mar monthly are imposed
French Zone)		m-f 50 h-f 1	5 1 -		
U. S. S. R. Zone)		m-f 100 h-f 12	9		
Holland	Final postwar policy un- decided. Prewar adver- tising was allowed	l-f 100 m-f 60 h-f 40	1 7 6	1,424,318 includes 492,046 relay subscribers	
celand	Government, but about 30 min of time daily is sold at 1 kroner per word, for advertising	l-f 100 m-f 1 h-f 1	1 1 1	34,692	Government obtains about one third its income from advertising, also h full powers to curb interference a assists rural districts in radio upkeep
taly <mark>ap</mark> an	Advertising 2.89% of total programs Government and com-	m-f 100 h-f 50 h-f —	29 7 New plans	1,900,000 Oct. 1947	At present there are 3 networks: The Red, Blue, and Short-wave Final allocation plans now being
uxembourg	mercial, similar to Aus- tralia and Canada Commercial	l-f 150 h-f	call for 108 1 1	42,468	worked out License fee 72 francs (Belgian) collected annually by postoffice. Use
Norway	Government company	m-f 100 h-f 100	16	566,000	for anti-interference work License fees average 20 kroner ann ally; where reception is poor reduced
			5		5 kroner, plus tax when buying receivers. Until 1940 advertising we carried. The company assists listeneby providing wind chargers when
Polan d			-	675,000 Dec. 1947	electric power is not available
outh Africa	Government	m-f 10 h-f 2	16 11		Includes Transvaal, Cape Division, ar Natal Division. Programs in Engli- and Afrikaans
pain	Government	m-f 200 h-f 40	25 2		
witzerland	No advertising. Transmitters run by one organization, studios and programs by another—	m-f 100 h-f 100	6 16	922,959 47	License fee is 20 francs. Operation the radio systems is in accordance wi the free spirit of the people of Switze land
ugoslavia	both semifederal Government, no adver- tising	m-f 20	12	200,000	5 federated republics support the individual stations by license fee
	eromg	h-f	2		Propaganda use to all parts of the world except China and Japan.
		l-f 50	10		America beam completed by 1951

to ensure that they are used to the best advantage. All the documents of the IFRB are written in English, French, Chinese, Russian, and Spanish, with French as the official language. The Provisional Frequency Committee (CPF) is the direct result of the Atlantic City Convention, and met at Geneva in January 1948 to prepare a new

international list of frequencies for the use of IFRB. In spite of these agreements, countries have been known to use more power than that authorized, or to jump frequencies. Fortunately such happenings are relatively rare.

The Canadian system of broadcasting is very similar to that of the United States in that it allows private commercial broadcasting, but it also has its own government network system working in competition with the private broadcasters. The Department of Transport is the regulatory body in this instance, although the CBC actually passes on the applicants, thus, in effect, controlling its own competi-A fact which may have escaped the notice of a large number of U.S. broadcasters is the license fee which has to be paid for the privilege of operating a commercial broadcast station. This fee ranges from \$50 for a 100-watt station to \$10,000 for a 50-kw station, as seen in Table I. Plans are afoot to increase these fees. The listener also has to pay a fee of \$2.50, even in areas where reception of CBC stations is impossible.

The United States side will be familiar to all readers, but perhaps the European aspect may not be. In fact the writer has often been amazed by the many times engineers have asked what body exists in England and Europe similar to the FCC. In each case the answer is none; and as we shall proceed to show, the need for a similar regulatory body does not exist, owing entirely to the different approach towards broadcasting.

Human nature being what it is, and engineers being, by virtue of their common interest, of a similar type, it is only natural to expect, and to find, that radio has progressed along very similar lines in most countries. An advance in one phase in one country is matched by an advance in the same field in the next, and so on. Although individual differences may cause slight changes in equipment operation and layout, the principles of construction follow somewhat similar lines, as may be seen in some of the illustrations.

Operational Procedures

As a result of engineering parallels one might expect the business procedures and principles of the various nations to be similar. They are not. The U.S. and Canada

have somewhat similar operation, but there are not many countries that allow commercial broadcasting by private companies; although wherever the U.S. influence is felt, a trend towards commercial operation is noticed. In most nations of the world radio is the voice of the government, and is used as a propaganda tool by the party in power.

In general it will be noticed that the majority of countries do not permit sponsored or commercial broadcasting. However, a few favor limited commercial broadcasting along somewhat similar lines to the Canadian system. Generally speaking, where this type of operation is allowed, the government runs the broadcasting system and collects the revenue from it. Receiver license fees are collected even where sponsored broadcasting is the rule. As far as the writer has been able to ascertain, such is the practice in every country except the United States of America. In countries where commercial broadcasting is allowed, or advertising is accepted, the license fees are sometimes used for improvement of the service to listeners.

A large number of foreign countries have strict laws concerning the use of apparatus which causes interference to radio reception. And in these countries the authorities are empowered to trace it down, and cause the owners of the offending equipment to modify it at their own expense. As television becomes more and more general in this country, it appears that a similar measure may have to be invoked.

The incidence of relay exchanges, and "wire broadcasting", in Europe and other countries, is much greater than is generally realized. A number of factors contribute to this, among them being the extremely poor conductivities in many of the mountainous countries of the continent, the lack of facilities for the domestic construction of receivers, the lack of money, either by the government or the listeners themselves for providing equipment, and the extremely poor reception conditions obtaining in many places. An example is the Gold Coast of West Africa, where for five shillings a

month (\$1) a loudspeaker may be leased together with a wire connection to the local relay exchange. This is an ideal provision for the inhabitants and well within their means. In many parts of Europe high and medium-frequency carrier-current systems are used over power and telephone lines. Some of these relays provide only the program of the national station; others also act as local stations and provide programs from local studies in addition. Of course, the great disadvantage of all these systems is the dependency on a physical connection. In the event of war a large part of the population could be denied broadcast intelligence by a few skillful saboteurs. This possibility is particularly true of Russia and many of the eastern states of Europe. In some of the villages in these areas only one loudspeaker and receiver is available for perhaps 500 people.

The very nature of the terrain in so many parts of Europe is an added handicap. A glance at any map will show large areas of mountainous country where reception is extremely poor. In view of these handicaps, it is interesting to reflect on the large number of highpower stations in Europe. High power is considered to be 60 to 500 kw. In the writer's opinion there is no doubt that the European answer to the coverage problem is large-scale synchronized operation of high-power stations, thus providing a nationwide groundwave signal from nationally operated transmitters. Either by accident or design, the local station and program, such as are known in this country, are virtually nonexistent. Possibly it is by design, for single sources of high-intensity groundwave service can be used more effectively with one propaganda program to influence a country than a number of small stations with varying ideas of program content.

In this respect, the Balkan countries are the worst situated. Conditions of low income per capita and scattered population combine with extremely mountainous terrain to present a very difficult problem. Very rapid attenuation of groundwave is experienced in these small countries and they are usually too

small to utilize skywave for night

In certain countries where commercial and government broadcasting is allowed, operation is along rather similar lines to that of the CBC and the private broadcasters in Canada. For example in prewar days, Radio Luxembourg on 232 kc with 150 kw, provided an excellent day and night signal to more than 50 percent of Great Britain. This station carried limited commercial programs in English, as well as programs addressed in the national tongue of Luxembourg. Other stations such as Radio Paris, Radio Lyons, Toulouse, Radio Normandie, and Hilversum on the medium-frequency band, carried sponsored programs for both home and overseas, that is, British Isles consumption. These stations enjoyed a popularity equal to or greater than that of the BBC stations, especially among the younger people who were more receptive to the dance and light music which formed the major part of the programs. The International Broadcasting Company programmed some of these stations, with operation by nationals of the countries in which they were located.

It is simpler to list those countries where receiver licenses are not required than to list those requiring one! America is the shining example of free listening, although the principality of Monaco with its three stations is likewise untaxed. As a result of this almost universal imposition of license fees, a fairly accurate check can be maintained of the number of listeners throughout the world. It is not difficult to evaluate illegal operations. In 1942, it was estimated that there were 400,000,000 listeners. This world total can be broken down to show 29,393,000 radio homes in the U.S.A., against 51,986,000 in the whole of Europe and Russia. The terrific impact of radio in Europe is only now commencing to be felt and as more sets become available great mass reactions may be expected.

A problem peculiar to a number of European countries, and one with which the United States is not faced, is the provision of programs and radio services to colonies, dominions, and protectorates. Sometimes this service is achieved by high-frequency transmission from the mother country for direct reception, relying on these broadcasts to combat adjacent country propaganda interference. An alternative is to build local stations and program them locally, supplemented by relays from home. The latter is better, for it insures a service not dependent on the ionosphere layer, and not requiring different frequencies for different times of day.

Practically every European country operates at least one low frequency transmitter between 150 and 285 kc together with high power up to 200 kw. This combination usually results in a large part of the population receiving a fairly reliable single program service. However, secondary service has to be depended upon to a much greater extent than it is in America, and as a result relay exchanges are numerous and extremely popular.

Table II presents a brief summary of conditions in a number of countries. A breakdown of U. S. broadcast operations is given in Table III.

European Problems

In France in 1944 there were approximately 34 stations under government and private control. At the end of the war there were only five of any considerable power remaining. At present, there are two countrywide networks known as the National and the Paris networks. Recently, a third program heard only in Paris and the suburbs has been added. This program may

Table III—Broadcast Stations in the U.S.

	July 1.		In-
	1947	1948	crease
A-M	1,795	2,034	239
F-M	918	1,020	102
Television	66	109	43
Television (experi- mental)	81	124	43
Educational	38	46	8
Inter- national	37	37	0
Remote Pickup	583	571	(-12)
Other -	33	26	(-7)
Totals	3.551	3.967	416


later develop into a third network so that the combination will prove similar to the three BBC program services. Thirteen transmitters in the National network cover about 80 percent of the population and ten in the Paris network provide coverage of 66 percent. Some areas hear only one service.

In July 1947, a new coaxial cable was put into operation between Paris and Toulouse. This span of approximately 490 miles requires the use of 42 repeater stations. Unfortunately, no details are yet available concerning its frequency response. A new transmitter with a power of 100 kw operating on 895 kc went on the air September, 1947, at Lyons-Tramoyes, and it is believed this is the first new one to be built since the war.

Before the war, Italy maintained three networks consisting of 40 stations in the m-f-band varying up to 100 kw. Nine short-wave transmitters used power up to 100 kw for broadcasts to Italian-dominated territories.

Belgium provides a good example of the dual language problem. Before the war the state operated two 15-kw transmitters at Brussels providing programs for the Walloons and Flemings, in French and Flemish; and 16 small privately-owned stations carried sponsored programs for local and regional consumption. Today, Belgium is rapidly rebuilding a first-class system out of the ruin left by the war. A 1-kw f-m transmitter on 100.1 mc is operating at Brussels, with two or more planned for Antwerp and Liege. It is suggested that an f-m network may be set up at a later date. However, this does not affect in any way the instant plans for a complete a-m network providing nationwide primary service.

Czechoslovakian broadcasting is governed by the law of March 23, 1923, and the decree of February 8, 1925. These reserved to the State the right to grant concessions to the use of the ether. The Ministry of Post may grant to individuals the right to operate a station, but there have never been any such grants. The Czechoslovakian Broadcasting Company, in which the government holds most of the shares, is the only source of broadcasting in the coun-

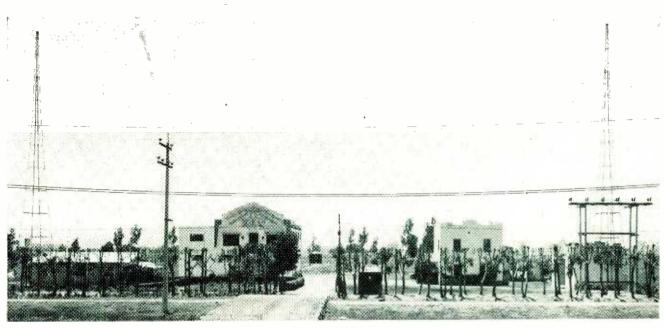

Mexican stations XEW and XEWW, showing a flat-top transmitting antenna (RCA photo)

try. Although nominally a private company, the State virtually controls its operations. About 1,600 people are employed and the organization is administered by a board of three members in Bohemia, five in Slovakia and the Ministry of Information. There are approximately 2,000,000 licensed listeners in the country.

Before the war, the Czechoslovakian radio system was one of the best in Europe. It operated eight stations, ranging up to 120 kw at Prague I. A number of these were destroyed during the war, but they are being replaced and in last December a new one of 100 kw on 1,204 kc was brought into operation near Presov. Incidentally, it is a European custom to identify stations by their location rather than call letters, and to carry it a step further, when two or more are located in the same town, they are labeled Prague I, Prague II, and so on. (This would be a little unwieldy in New York!)

At the time of writing, Poland operates nine medium-frequency transmitters and one low-frequency transmitter. The most powerful of these is Warsaw I with 50 kw on 758 kc. Licensing is employed as a means of raising money, but here it is rather illuminating to note that imprisonment is not provided as a penalty for failing to register, as in most countries, but a fine equal to six months' license fee is im-The normal license fee is paid monthly, and is graded according to the size of the receiver, and the class of the owner, peasants, workers, clerks, pensioners, and military paying from half to twothirds less than "other persons."

Polskie Radio, the official name of the organization, maintains a technical section which assists listeners in assembling or installing receivers. At the end of 1947 there were about 600,000 subscribers to wire broadcasting service. Special importance is attached to these installations in mining areas and it is intended thus to service ten large industrial centers in Silesia, where reception conditions are extremely poor.

Radio in Russia is, of course, a government service. The existence of two hundred different peoples in the Union, the extreme poverty of a large part of the population, and enormous areas to be covered all serve to direct radio towards grouplistening practices. There were approximately 90 stations, one more than there were a-m stations in New York State, and 39 less than in California, at the end of 1947. The principal station, Moscow-Komintern, has a power of 500 kw; eleven others have 100 kw each. The exact number of shortwave stations for the Asiatic regions of the U.S.S.R. is not known since reports vary, but well over 50 frequencies are used.


Radio reception in this tremendous area varies from place to place, but on the whole, conductivity is on the low side. To assist dissemination of programs a system of relay exchanges distributing the national program by wire was set up. In 1937 there were 7,000 of these exchanges, and by now there must be many more. They are similar in effect to United States local stations, except that they carry oneparty propaganda only, and on a public-address basis.

Whenever radio men from different countries get together the conversation eventually turns to sponsored versus government radio. Without considering the merits of the case, the popularity of the American system is attested by the fact that last year a British company offered 300,000 crowns to the Danish Government to be allowed to put a transmitting station on the Faroe Islands. When this offer was turned down, the offer was increased to a figure of half their annual profits. So far as the author is aware, a decision has not yet been reached.

BIBLIOGRAPHY

- (1) BBC Yearbook. (2) BBC Quarterly
- (3) International Broadcasting Organization Bulletin.
 (4) Arno G. Huth, "International Broadcasting." (5) O. Lund Johansen, "World Radio Handbook," Denmark.
 (6) Le Radio Monde.


ULTRASONIC

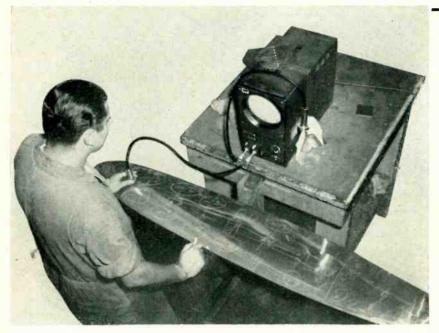

Wall thickness readings chalked in at various points on surface of hollow propeller

By BENSON CARLIN

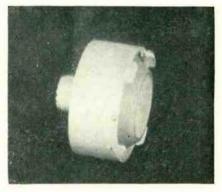Product Research Supervisor Sperry Products, Inc. Danbury, Conn.



Crystal transducer searching unit

LTRASONIC METHODS are being successfully applied to the testing of materials, using various instruments. One of these is the Reflectogage, based upon the principles used in the Sonigage originally developed by General Motors.

This device utilizes electronic methods of generating and receiving ultrasonic waves which are transmitted through the article under test. These waves are reflected within the material either by its opposite side or by a flaw or discontinuity, so that the thickness of most parts can be measured or the presence of flaws indicated. The accuracy of measurement can be made almost as great as the operator desires but in an ordinary commercial instrument such as the one

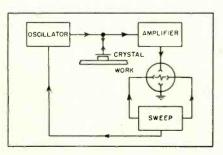


FIG. 1-Block diagram of equipment

described it is approximately 2 percent of the thickness of the part, regardless of what the thickness may be.

Parts ranging from a few thousandths of an inch to four inches thick can be measured by variations of the basic method. The present commercial instrument reads directly in the range from 0.025 to 0.300 inch in steel and measures up to 4 inches by harmonic methods. It measures the thickness of material forming pipes, tanks, and vessels which can only be reached from one side of the wall. Such measurements were formerly made by drilling a hole and reading the thickness by mechanical means.

Not only metals but glasses and certain plastics can be measured. The use of the instrument is particularly valuable in cases where the material is formed into a closed vessel or long tube. For example, hollow propeller blades are being widely tested at present. It was formerly impossible to measure these sections by any known means. Lack of bond between similar or different materials can also be indicated either by changes in the amplitude or in the location of the

indications on the instrument. Eccentricity of bore can also be measured quickly and easily. Other applications are the testing of knife blades made of several sections bonded together, and of shell cases for separations within their wall sections.

Ultrasonic Principles

Ultrasonic waves commonly used in testing or gaging can be defined as sound or vibrational waves of very high frequency ranging between 100 kilocycles and 10 megacycles. For purposes of measurement, they may be considered to travel through a material with a fixed velocity that depends in a complex way upon the density and elasticity of the material.

The tables give experimental velocities and wavelengths for ultrasonic waves. Such waves are strongly reflected by an interface and will ordinarily return toward the source which produces them. Standing wave patterns are set up in the manner of electrical waves; the patterns are determined by the dimensions of the medium of travel and by frequency. The ultrasonic gage indicates the frequencies at

THICKNESS INDICATOR

Nondestructive testing and gaging device gives visual display. Equipment comprises motor-driven variable frequency oscillator, contactor-initiated R-C sweep, crystal transducer, and cathode-ray tube. Graduated screens provide direct readings

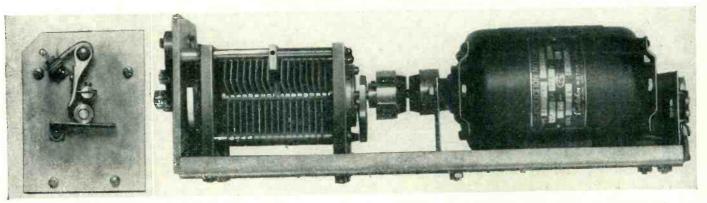


FIG. 2—Motor-driven capacitor for variable-frequency oscillator. Contactor for initiating sweep is shown in detail at left

which resonances take place. Because the velocity of travel is fixed, this action is equivalent to measuring the thickness of the medium, and the instrument may therefore be directly calibrated in thickness.

The operation of the instrument depends upon the fact that the amount of energy required to drive a system varies with its dimensions,—that is, resonances occur when ultrasonic wavelength has a specific relation to the thickness of the part and at this point there is a great increase in the vibration of the wall being measured. As a result, the plate current in the driving oscillator increases sharply. Any part can be put into such resonance depending on its dimensions, elastic characteristics, and density.

The lowest frequency at which resonance occurs is called the fundamental; and subsequent ones, harmonics. The frequency deviation between any two consecutive harmonic frequencies is equal to the fundamental. Therefore, when either the fundamental or the difference between two consecutive harmonics is known, the thickness (T, in inches) is determined by the relation T = S/f

where S is half the velocity of sound in inches per second, and f is the frequency in cycles per second. For steel this becomes

T = 121,000/f

Harmonic indications can be directly used to calculate thickness from the relation

 $T \equiv R_1 R_2 / (R_2 - R_1)$

where R_1 and R_2 are thickness readings of any two successive indications and R_2 is thicker than R_1 .

It should be noted that the thickness is read over a small area directly under the crystal. When the thickness varies sharply within that section, readings cannot be obtained. However, satisfactory results can be obtained even where a liquid or solid is contained against the reflecting surface.

Most materials transmit ultrasonic waves well³ and can therefore be measured. However, this is not true for materials which have very high internal damping or absorption. Most metals are in the first class, and each different material requires a separate calibration screen for use with the instrument. Alloys in which velocities vary greatly also require separate screens.

In cases where the medium under test is not electrically conducting, a metallic face must be placed over the front of the crystal search unit so that a suitable ground return can be made to the instrument. The interface between the crystal and work will interrupt the passage of ultrasonic waves unless it is filled in with some form of couplant such as transformer oil.

It is also important that the sur-

Table I—Velocities in Common
Materials

Material	Velocity in cm per sec × 10 ⁵
Air Alcohol Aluminum Bakelite Brass Copper Glass Lead Magnesium Mercury Nickel Polystyrene Quartz Steel Transformer oil Water	

face of the part be fairly smooth. In general, most metallic surfaces are satisfactory or can be made so with a hand grinder. The back or reflecting surface must be smooth for if it is very badly pitted, the energy is scattered and it becomes difficult to make satisfactory readings. However, measurement can sometimes be made even when the reflecting surface is pitted by limiting the crystal to a small area.

The thickness of curved sections can also be measured. When the curvature is not great, flat crystals will give satisfactory indications. In other cases, crystals ground to fit the curved surface are necessary.

Electronic Principles

In a simple instrument of the resonance type, an oscillator with a milliammeter in its plate circuit might be used. A manually tuned variable capacitor can be slowly turned and the meter watched for changes in plate current. The thickness of a known part is calibrated against current dips and calibrations marked on a suitable tuning knob. Unknown parts can then be checked and the thickness read directly from the knob. This type of device would prove inconvenient because each successive test requires a laborious readjustment of the instrument before a reading can be taken.

A block diagram of the Reflectogage is shown in Fig. 1. It is an entirely automatic instrument, comprising a variable-frequency oscilla-

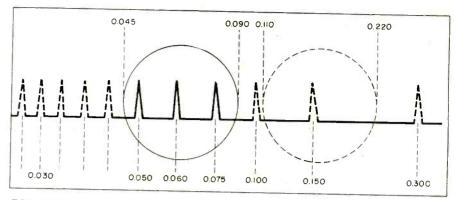


FIG. 3—Harmonic spectrum for steel piece 0.300-inch thick. Dashed and solid circles show indications for two different modes of operation

tor whose frequency is swept by means of a motor-driven capacitor, a sweep generator, an electronic sweep amplifier and signal amplifier, an indicator in the form of a cathode-ray tube, and a searching unit.

The oscillator produces electrical variations that are impressed across the crystal search unit. The rotation of the tuning capacitor continually changes the frequency of oscillation throughout an optional tuning range. The same mechanical device also contains a contactor or switch unit for producing a sweep voltage by discharging a capacitor through a resistor. This contactor, shown at the left of Fig. 2, is so adjusted that it fires the cathoderay sweep at the beginning of each successive variation in frequency, that is, at the high-frequency end of the range, and the cathode-ray beam is swept horizontally across

the screen once for each revolution of the capacitor. As a result, each point along the beam corresponds to a particular frequency of oscillation. The scale is then calibrated in thickness for the parts under test, increasing from left to right. As energy is returned from the part, variations in the voltage across the crystal and across the amplifier cause the beam to be deflected vertically. These pips are the thickness indications.

If the oscillator were adjusted so that it operated over a very wide range the indications received would look like those in Fig. 3. However, in ordinary use it is convenient to limit the range so that only one marker or pip is received. This pip indicates a resonance in the material and although it may not be a fundamental, the range is ordinarily chosen so that it is. The instrument can be operated at almost

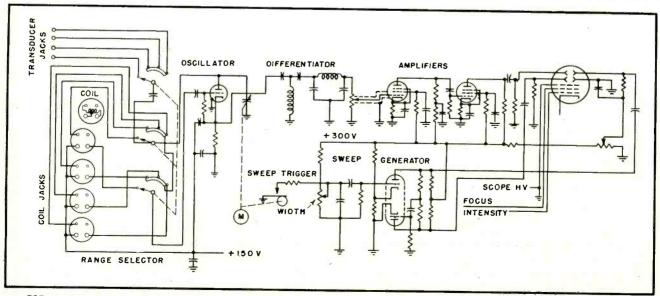


FIG. 4—Schematic circuit diagram of the Reflectogage. Conventional power supplies for plates and scope have been omitted

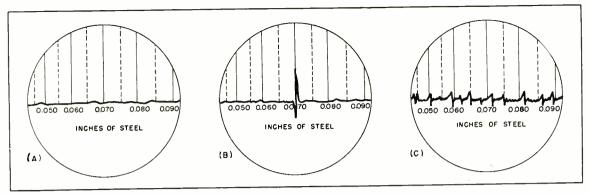


FIG. 5—Typical visual displays: (A) sweep without thickness indication; (B) fundamental thickness indication; (C) harmonic indications

any convenient frequency by substituting plug-in coils, but it is basically a 4-range unit. Range 1 is 0.025 to 0.050 in., Range 2 is 0.045 to 0.090 in., Range 3 is 0.080 to 0.160 in., and Range 4 is 0.150 to 0.300 in. A total frequency range from 400 kc to 5 mc is required.

Crystal Transducer

The energy produced by the electronic oscillator is impressed across the X-cut quartz crystal, illustrated, which transforms the electrical voltage into longitudinal physical vibrations. This crystal is usually either ½ or 1 inch in diameter and mounted in a spring holder so that it is always supported at a fixed pressure against the work. The ultrasonic waves then travel perpendicular to the face of the crystal and are essentially limited in their crosssectional coverage to a projection of the crystal face. The part of the work tested is therefore only that directly under the crystal and the instrument does not in any way integrate thickness readings over considerable areas.

The crystal resonance frequency is chosen to be somewhat greater than the highest frequency of electrical oscillation employed in that range so that the output is essentially constant and spurious crystal resonances do not appear as indications on the sweep.

Circuit Details

The oscillator output is connected to a vacuum-tube amplifier as shown in Fig. 4. The variations in plate current are separated, amplified, and finally displayed on the cathoderay tube. The actual variations in plate current range from 2 to ap-

Table II—Wavelengths in Centimeters in Common Materials

]	Frequency in	megacycles	
Material	0.5	1	2.25	5
Air	1.244 0.518 0.886 0.924 1.040 0.426 0.284 0.534 1.150 1.162 0.278	0.0344 0.622 0.259 0.443 0.462 0.520 0.213 0.142 0.575 0.575 0.581 0.139 0.145	0.0153 0.277 0.115 0.196 0.206 0.231 0.0947 0.0632 0.119 0.255 0.259 0.0618 0.0645	0.00688 0.124 0.0518 0.0886 0.0924 0.104 0.0426 0.0284 0.0534 0.115 0.116 0.0278 0.0290

proximately 25 percent. The pips produced may be from ½ inch to 3 or 4 inches in height but the instrument is ordinarily operated with the markers about ½ inch high to give a clean base line and sharp vertical indications.

The general shape of the voltage variation in the plate circuit is that of a resonance curve and is therefore not so sharp as is desirable for indicating purposes. The signal is therefore differentiated by a series of filters and appears on the face of the tube as a sharp increase followed by an equally sharp decrease of voltage. The point at which the changeover from increase to decrease occurs is the one at which thickness is ordinarily calibrated.

Calibration is carried out by placing over the face of the cathode-ray tube a transparent plastic screen on which vertical lines are inscribed for various thicknesses. A different screen must be used for each material and also for each range of frequencies. Additional screens could be made for operating at harmonic frequencies.

The appearance of the final signal may be more completely visualized from Fig. 5, in which the cathoderay trace without resonance signal is shown at A; B is the trace with a single fundamental indication; and C illustrates the appearance of the trace with several harmonic indications. In B the thickness of the part is within the range of frequencies for which the instrument produces fundamental oscillations. At C the thickness of the part is much greater than the maximum fundamental possible on that range.

Work connected with the instrument was carried out with the aid of W. Doniger and T. C. Nehrbas.

REFERENCES

(1) Norman G. Branson, Portable Ultrasonic Thickness Gage, ELECTRONICS, January 1948.

(2) Wesley S. Erwin, The Sonigage, A Supersonic Contact Instrument for Thickness Measurement. Paper presented at the S.A.E. Meeting at Los Angeles, Calif., October 1944.

(3) B. Carlin, Supersonic Westerness.

(3) B. Carlin, Supersonic Wave Penetration into Materials, Product Engineering, October 1947.

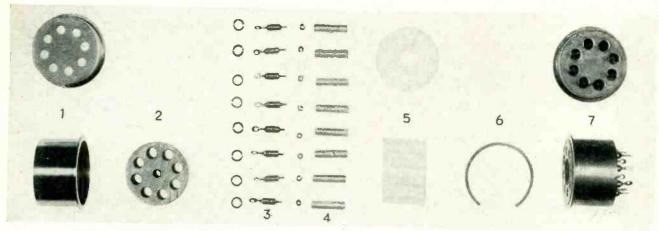


FIG. 1—Component parts (1, 3, 4, 5, 6, 7) and metal assembly jig (2) of a hermetically sealed octal socket

Hermetically Sealed Electronic Components

By W. J. LEISS, G. R. MOLTRUP, J. H. SLATON and A. H. WAYNICK

Ordnance Research Laboratory, School of Engineering The Pennsylvania State College, State College, Penna.

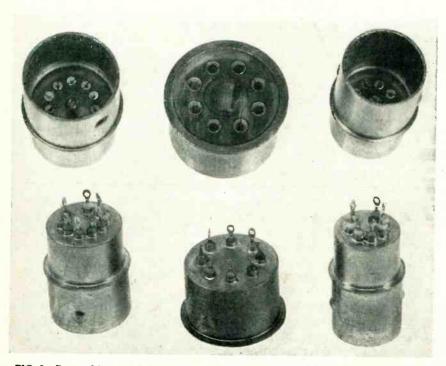


FIG. 2—Top and bottom views of assembled nine-pin, octal and seven-pin hermetically sealed sockets

ONSIDERABLE EFFORT has been expended during and since the end of the war by numerous laboratories attempting to devise means of protecting electronic equipment in use against numerous deleterious environmental factors such as high humidity, fungus growth and salt water spray. The Ordnance Research Laboratory of the Pennsylvania State College, which is interested in electronic developments for the U. S. Navy, has designed hermetically sealed plug-in units, assemblies and complete devices.

By utilizing the components and techniques to be described it has been found possible to seal hermetically an entire electronic chassis as well as subassemblies and components. By so doing, the major problems of protection of electronic equipment during storage, shipment and use against high humidity, fungus growth and salt-water spray have been solved. The servicing problem has been greatly alleviated by the use of hermetically sealed plug-in components. In the case of more complex devices, the servicing problem has been further simplified by the use of hermetically sealed



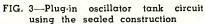




FIG. 4—Two-tube sealed subassembly that plugs into a larger chassis

Sealed plug-in units such as tubes and sockets, transformers, relays, capacitors and tuned circuits are utilized in construction of subassemblies and complete chassis that are also hermetically sealed to provide protection against high humidity, salt-water spray and fungus growth

plug-in subassemblies which, in themselves, may generally be so constructed as to be simple to test.

For relatively simple electronic devices all of the critical or high impedance circuits have been placed in one chassis, the entire chassis then being hermetically sealed. More complex devices have been broken into subassemblies which are in themselves constructed in plug-in type hermetically sealed containers. In either case the maintenance and/or servicing procedure, aside from replacement of tubes, transformers, relays and other standard hermetically sealed components, involves the replacement of the entire hermetically sealed chassis or subassembly in case of electrical or mechanical failure. By utilizing this construction, the problems of protection against humidity, fungus growth and salt-water spray may also be satisfactorily taken care of by proper choice of materials.

Sealed Sockets

Hermetically sealed tube sockets for octal and seven and nine-pin miniature types are made up from the components shown in Fig. 1, and examples of the resulting sockets appear in Fig. 2. Use of these sockets results in a gas and vapor seal of the chassis interior relative to its exterior. The sealing is accomplished by means of glass and metal surfaces, with all materials exposed to the exterior so chosen as to avoid surface condensation leakage paths when exposed to humid atmospheres.

In mounting, a hole which is just large enough to permit entry of the socket body is punched in the chassis. The latter must be hot tin dipped to permit soldering. The socket is then placed in the hole and is supported therein by a protuberance at the top of the octal socket and near the center of the miniature sockets. The socket is then soldered into place with a solder ring and, if desired, by cylindrical soldering irons designed for this purpose. The portions of the miniature socket shells above the chassis surface fit standard

As shown in Fig. 1, the socket body is a hot tin dipped brass shell, item 1. The feed-through insulators, 3, are a standard commercial

item. Pin receptacles, 4, are made from beryllium-copper rod which has been drilled, slit and silverplated.

In assembly, the metal insert, 2, is placed in the shell to locate the terminals while they are being soldered to the shell. Items 3 and 4 are assembled and inserted into items 1 and 2 along with the appropriate solder rings as shown.

The entire assembly, 7, is preheated and then immersed, with the aid of appropriate jigs, in a bath of Crisco for approximately 30 seconds at a temperature of 550 F.

The socket terminals are sufficiently flexible to account for pin location variations from tube to tube. This is accomplished by slitting the terminal and by using a flexible lead-through insulator. The magnitude of the connector displacement is limited by the polystyrene spacer, 5. In assembly, the split ring, 6, is held tightly in the groove around the circumference of the spacer. The spacer and ring are inserted in the socket and, when seated, the ring expands into a groove in the shell.

The miniature sockets are assembled similarly except for a center shield pin screwed into the shell.

Plug-in Components

Certain electronic circuits and devices are most usefully constructed in the form of separate, hermetically sealed components which may be plugged into larger assemblies. Figure 3 illustrates a hermetically sealed plug-in oscillator tuner circuit. This circuit is plugged into a hermetically sealed octal socket so that it may be removed from the larger unit without affecting its seal. The components of the tuned circuit are vacuum potted in a can with a hermetically sealed header. The potting process is used primarily for mechanical strength since potting, by itself, does not form a satisfactory hermetic seal. The assembly is fastened to the larger units by screws through the two lugs. The screws fit into sealed studs.

Figure 4 shows an entire electronic subassembly which, in turn, is plugged into a larger unit which may or may not be hermetically sealed. Coil assemblies, tubes and

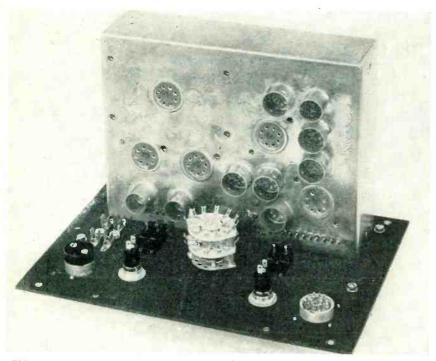


FIG. 5—Complete chassis before wiring. Connections to all major components are made through octal sockets

other sealed components which may require replacement are connected to the subassembly by means of the hermetically sealed sockets. The assembly is connected to the main unit through an hermetically sealed connector.

In case of failure, aside from tubes, coil assemblies, or similar plug-in units, the entire subassembly is replaced by a new unit. Thus, special packaging of spare units is avoided, and the circuit in the subassembly can usually be tested by relatively simple, perhaps plug-in, test equipment.

Hygrometer Indicator

It has been found desirable to incorporate an electric hygrometer in large assemblies involving many solder seals. It is also useful for preproduction tests of smaller subassemblies.

The hygrometer unit is installed inside the assembly to be sealed. One of its terminals is connected to the chassis ground while the other is connected to a lead-through sealed terminal. The hygrometer is used to check the drying process and, in larger units, further permits easy checking of the seal during the life of the assembly.

A relative humidity of six percent, measured at 130 F, results in satisfactory operation of most electronic equipment, as far as condensed moisture is concerned, when the equipment is operated at temperatures as low as -60 F. Consequently, commercial hygrometers have been chosen to operate over the relative humidity range of five to ten percent.

An electronic chassis comprising a test set for other electronic equipment will be described to illustrate the use of hermetically sealed components in a large assembly. All components except low-impedance circuits and power 'switches are mounted in a standard chassis box which is hermetically sealed.

With all top components removed from the chassis (Fig. 5), it is evident that construction is quite different from usual. The transformer leads are fed through an hermetically sealed octal socket and the transformer is fastened to the chassis with the aid of screws and hermetically sealed studs. Similar mountings are used for the relay. the electrolytic capacitor and the tuned circuits. Low-impedance and power leads are fed through the sealed lead-through terminals. The remaining sockets are for tubes and are also hermetically sealed.

All components are soldered into place before final assembly by solder rings and cylindrical soldering irons.

Resistor boards are fastened to the walls of the main assembly and held in place by rivets which are peened so as to fill an indentation in the assembly wall around the rivet hole. The rivet is soldered to the assembly wall so that a smooth exterior assembly wall surface is obtained. A hygrometer unit is permanently mounted in a corner of the chassis. Final sealing, except for two 1/32-inch diameter holes in the side walls of the chassis, is accomplished by placing a flat metal plate over the bottom of the chassis and flowing solder around its edge in contact with the chassis lip.

Sealing Procedure

As would be expected, it is necessary to dry out the interior of the chassis before making the final seal. The metallic surfaces, and some component surfaces, are covered by an adsorbed layer of water vapor which must also be removed.

In drying a chassis before final sealing, the entire chassis is placed in a heater where it is maintained at a temperature of 130 F for about thirty minutes. Dry air from a commercial air-drying unit is then forced into the chassis through one of the 1/32-inch holes left in the chassis sidewalls. This flushing process is continued until the hygrometer has indicated a relative humidity of six percent or less for at least one-half hour. At this time the two 1/32-inch holes are solder closed while the chassis remains in the drying oven. The sealing process is then complete.

This type of construction should be of use in geophysical prospecting, airborne and many other services where electronic devices are subjected to humid atmospheres, fungus growth and other deleterious conditions.

We wish to acknowledge the assistance rendered in this work by Dr. F. W. Dunmore of the National Bureau of Standards who so kindly furnished information concerning the procurement of suitable hygrometers. Professor E. R. Queer of the Pennsylvania State College Engineering Experiment Station contributed many helpful suggestions concerning proper methods of hermetic sealing and dehumidifying.

Road-Testing Gasoline

Electronic spark-advance indicator and tachometer provide a method of rating gasoline throughout the entire speed range, instead of at two speeds as is usually done in octane number determination

By R. R. PROCTOR

Research & Development Laboratories The Pure Oil Company Northfield, Illinois

THE OCTANE NUMBER or octane rating of automotive fuels has for years been determined on what is known as the CFR (Cooperative Fuel Research) engine, a single-cylinder variable-compression-ratio engine running at a slow speed, 600 rpm for the so-called Research Method and 900 rpm for the Motor Method. While this procedure is still standard in all laboratories, it does not give a complete picture of the fuel since rating is determined at only two points or speeds.

About 1936 or 1937 a supplementary procedure known as the Borderline Method of fuel rating was developed by means of which the octane rating of a fuel throughout the entire speed range could be determined. Briefly, the fuel rating is determined by plotting a framework of reference fuels and superimposing the unknown fuel on the framework to determine its octane rating at any speed.

All fuels are used in a test car in which the distributor governor and vacuum advance have been locked out and a manual control installed. The distributor is first set so that ignition occurs at a known point somewhere near top-dead-center of the piston stroke. With the car in high gear and running at 8 to 10 mph on a level road, it is accelerated at wide-open throttle and the speed of the engine at which the knock fades out is recorded. At least two check runs are made, or more if nec-

essary, until the same fade-out speed is agreed upon by two observers. The spark is then advanced two degrees and the procedure repeated, then two more degrees, and so on, until a complete curve has been plotted for speeds up to 70 miles per hour.


A graph consisting of a framework of five or six standard-reference fuels of known octane numbers is thus prepared and the curve of the unknown fuel can be plotted. From a comparison of curves the octane number of the unknown fuel at any speed can be obtained.

Some sort of instrumentation is required to determine the spark advance each time it is changed, or conversely, to set the spark at any given poin accurately and easily. Also, since it is easier to work with engine rpm than with miles per hour, and since the standard speed-

ometer is not ordinarily accurate enough for this type of work anyway, an engine-rpm indicator is desirable.

It is necessary to know how far from top-dead-center the spark plugs fire, in degrees of crankshaft movement, and arbitrary limits of 60-degrees advance and 10-degrees retard can be assumed. A stroboscopic light can be used as an indicator but this is rather inconvenient when the driver or observer in the test car must know the spark-advance setting accurately while speeding down the road on a fuel test. Therefore, to bring the indication to the driver's seat, electronics is employed.

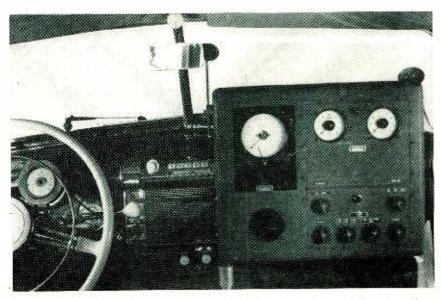To get a reference point electrically, a magnetic pickup is fixed on the engine in such a position that small metal studs on the flywheel pass close to it and produce voltage



Mounted with other instruments in the test car, the electronic unit indicates engine speed and spark advance

pulses in the pickup coil two or three times per revolution. The arrangement is shown in Fig. 1. The pickup is a small reluctance generator consisting essentially of an Alnico magnet in a structure containing a ris-inch air gap, and a 1,000 to 1,500-ohm coil. The signal from the pickup is conducted to the interior of the car by a shielded wire.

The variable parameter in this problem is the ignition impulse and this is obtained from the ignition primary on the distributor. For a constant engine speed, therefore, two minute pulses of voltage are available in the car, the time interval between which varies as the ignition is advanced or retarded. These voltages are both amplified to give 3 to 4-volt pulses at the output.

A thyratron, A, is set up as in Fig. 2, so that when it passes current it will indicate on a meter in its cathode circuit. The circuit constants are adjusted so that the tube is cut off and no current passes unless the grid is made a volt or two positive. The output pulse from the pickup amplifier tube then permits thyratron A to fire. Since the plate supply for the thyratron is d-c, the grid loses control after firing and current passes continuously through the meter. The only practical way it can be stopped is by reducing the plate voltage to less than about 15

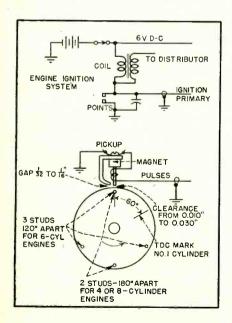


FIG. 1—Location of flywheel pickup-studs for 4, 6 and 8-cylinder engines, and electrical circuits used to actuate the electronic equipment

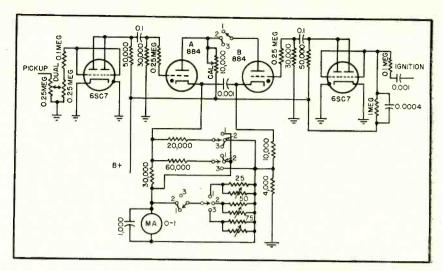


FIG. 2—Circuit for showing how far from top-dead-center the plugs fire

volts with respect to the cathode. To do this another thyratron, B, which draws plate current through the same plate resistor as thyratron A, is fired by the amplified voltage pulse from the ignition primary.

As thyratron B fires, the voltage drop across the common plate resistor increases suddenly, thus greatly reducing the plate voltage of thyratron A. At the same time, by means of a small capacitor connected between A and B cathodes. the cathode of A is given a positive pulse when thyratron B fires and becomes momentarily positive with respect to the plate. The tube is therefore extinguished and only the thyratron B passes current, which does not flow through the meter. Since the meter is no longer passing current, its needle drops back toward the left. And since the grid of thyratron B no longer controls, this tube continues to pass current to ground until the next impulse from the pickup amplifier trips thyratron A again. This extinguishes thyratron B by the process just explained, and current again starts to flow in the meter circuit.

Thus the meter receives current intermittently, and, with a capacitor across it, will indicate average current which is dependent in value on the ratio of the on-time to the off-time of thyratron A. This ratio is constant at any speed of the engine flywheel as long as the ignition timing or spark-advance setting is constant.

When the spark setting changes, the ratio changes accordingly.

Hence, the magnetic pickup is installed in such a way that a flywheel stud passes it and produces a pulse 60 degrees before top-dead-center on the No. 1 cylinder. Theoretically, spark advance from plus 60 to minus 60 degrees can be indicated on a meter with a zero-center scale. When the ignition is advanced to 60 degrees before top-dead-center, the ratio of on-time to off-time is theoretically one over infinity, or zero, and both thyratrons fire almost simultaneously. Thyratron A cannot remain ignited for more than an instant and hence it will pass practically no current. The metertherefore, indicates almost zerocurrent, so the bottom of the scale is marked 60-DEGREES ADVANCE.

Since we seldom are interested in more than 10-degrees retard, 10 DE-GREES RETARD is made the top point on the scale and the meter is caused to read full current for this setting by juggling the series and shunt resistors. Now, using one pin on the flywheel, and with the ignition at say, 40 degrees before top-deadcenter, the ratio of on-time to offtime is 40 degrees out of 360 degrees or 1 to 8, the pickup thyratron fires 60 minus 40 or 20 degrees before the ignition primary thyratron and the meter passes current for a. certain period. The pulses are averaged and this average current point is marked 40-Degrees Advance. At top-dead-center, for example, theratio of on-time to off-time is 60 degrees out of 360 degrees or 1 to-5, the meter reads still higher and this point is marked ZERO DEGREES. Thus the meter is calibrated from

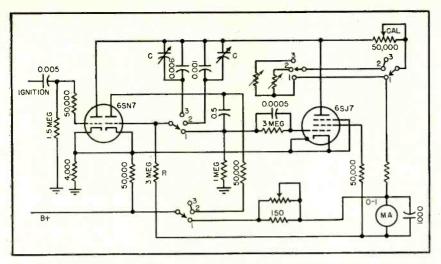


FIG. 3-Tachometer circuit for measuring engine speed

minus 10 degrees on the right to plus 60 degrees on the left, and the spark setting at any time can be read instantaneously on this meter.

With a constant voltage source for the plates, obtained from a vibrator and rectifier system operating on the 6-volt car supply, the instrument described indicates the spark setting at all times, inside the car.

Speed Measurement

Additional tubes integrate the ignition primary impulses and indicate them as average current on another meter calibrated in rpm to provide an electronic tachometer. The tachometer circuit is shown in Fig. 3.

The ignition impulse applied to the grid of one triode of the 6SN7 causes that triode to draw current through the meter and its series resistors. This applies a negative pulse to the grid of the other triode through one of the mica coupling capacitors, the capacitance of which determines the range. (Two scales are sometimes used, 0-1,000 and 0-5,000 rpm.) This pulse is amplified and applied to the grid of the 6SJ7, causing this tube also to draw current through the meter and its series resistors. The action is cumulative, resulting in a final current in the 6SJ7 limited only by the series resistors in the meter circuit. This current flows without change until the charge leaks off the mica coupling capacitor and the circuit returns to its original state with the 6SJ7 cut off. At this time, the second half of the 6SN7 is again drawing full plate current.

The meter reads average current, which is quantity-per-unit-of-time, or engine speed. Resistor R and the mica coupling capacitors, with their adjusting trimmers C, determine the time of flow, which must be less than the time between impulses at the highest speed to be measured. For this circuit the time of current flow is approximately 0.7 RC second.

The complete instrument requires but two wires to a battery and two wires to the engine to give all the information needed in the test. Calibration can be made accurate to plus or minus 1 percent in speed and plus or minus 1 degree in spark advance at any speed or spark setting and under battery-voltage variations from 5.5 to 7.5 volts.

Other Details

On a 6-cylinder engine, 3 pickup studs on the flywheel provide three pickup impulses per revolution. This tripling of the current impulses to the meter allows decreasing the instantaneous load on the B supply and reducing the size of the capacitor across the meter. On an 8-cylinder car, four ignition impulses per revolution are obtained. Theoretically four studs on the flywheel could be used since the 70degree range is less than 360/4 or 90 degrees, but practically it is rather difficult to get four pins exactly 90 degrees apart on the flywheel. Hence 2 pins 180 degrees apart are used. In this case there is provided a pickup impulse, then 2 ignition impulses, before the next pickup pulse. The second ignition

pulse has no effect, however, as thyratron B is already passing current, having been tripped by the first impulse.

The total current through the meter is less than in the case of 3-stud 6-cylinder operation, so the resistor network in the meter circuit must be changed. A selector switch is incorporated in the panel which changes circuit conditions to allow one or two-stud 4-cylinder operation, 3-stud 6-cylinder operation or 2-stud 8-cylinder operation. This same switch also changes the resistors in the tachometer circuit.

A calibrating circuit is also incorporated to allow setting the meter to a definite point (zero degrees on the scale) at any time to compensate for tube aging and other factors. A gain control on the pickup line, and a check position on the calibrating switch permit setting the gain to a standard point without flicking the meter needle to one end or the other.

The B voltage for the instrument is obtained from a vibrator power supply which incorporates a T-4½ neon lamp, a 6SJ7 and a 6V6 connected in the usual voltage-regulator circuit. The load on the unit is very nearly constant and the input voltage is the main variable. The output voltage supplied to the tubes is nominally held to less than one-percent change for 20 percent or more change in input voltage.

The original circuits were designed around 1-ma-fan-shaped meters. Several instruments have been built recently, however, using 2-ma or 5-ma concentric-scale meters, such as shown in the photograph. The basic circuits have necessarily been changed somewhat to accommodate the higher current, but the advantages of the longer easier-to-read scales more than offset the circuit complications involved.

BIBLIOGRAPHY

Sidney Oldberg, Gilbert Way and J. B. Macauley, A Spark Advance Indicator and Knock-Rating Observations, SAE Transactions, p 521, 1937.

R. J. Greenshields and L. E. Hebl, Additional Service Data on Effect of Ignition Timing, SAE Transactions (Discussion), p 148, 1937.

W. E. Drinkard and J. B. Macauley,

148, 1937.
W. E. Drinkard and J. B. Macauley,
Spark Advance and Octane Number—A
Road Test Technique, Jour. Soc. Auto.
Enar. 436, p 43, 1938.
C. R. Wagner, W. B. Ross, L. M. Henderson and T. H. Risk, Improved Motor
Fuels through Selective Blending, presented 22nd Annual Meeting API, Nov.
1941, San Francisco.

Composite Amplitude

High transmitter efficiency is combined with reduced bandwidth. The signal to one modulator is shifted 90 degrees. This, plus the inherent 90-degree phase difference between sidebands from p-m and a-m, cancels one set of sidebands

By OSWALD G. VILLARD, JR.

Acting Assistant Professor Electrical Engineering Dept. Stanford University Stanford, Calif.

SYSTEM OF CARRIER MODULA-A TION having several unique advantages compared with conventional double-sideband amplitude modulation has been developed. Although this new method produces substantially a single-sideband with carrier, the signal can be demodulated with negligible distortion in conventional receivers employing linear diode detectors. The bandwidth required for transmission is approximately half that of the double-sideband method. The maximum amplitude modulation required for communication, equally effective to that obtained with 100percent double-sideband a-m, is 81.5 percent, resulting in a saving of 33 percent in audio power when plate modulation is used.

The system can be added to existing phase or amplitude modulated transmitters with very little trouble, and appears to be the simplest way to achieve the advantages of single-sideband transmission from the standpoint of simplicity in installation, adjustment and maintenance. The sole disadvantage of the system is the presence of an appreciable secondorder sideband that is beyond the primary sideband and is capable of causing adjacent-channel interference comparable to that arising from a badly adjusted conventional transmitter. It should, therefore, be particularly interesting for lowpower mobile and point-to-point communication where moderate adjacent-channel interference can be tolerated, as in Fig. 1.

Basically, the system consists of combined amplitude and phase modulation with a 90-degree phase shift between the two audio modulating voltages. Because a-m and first order p-m sidebands are in radio-frequency quadrature, this arrangement can be made to cancel either the two upper or the two lower sidebands, as in the phase-rotation system of single-sideband modulation.

Sideband Structure

Operation of the composite system will be more readily understood after a description of its sideband structure for a single-frequency modulating voltage. The first problem is to select the degree of modulation for which the composite system will have a communication effectiveness equal to that of a carrier wave 100 percent amplitude modulated. It is necessary that the uncancelled first-order sidebands have a combined amplitude seventenths that of the reference carrier. This requirement arises because the receiver bandwidth is halved with the new system, hence the noise power received is halved. Because the two sidebands in a-m add directly, so far as detection is concerned, removing one has the same effect as cutting the sideband power to one-quarter its former value. Thus, for the remaining sideband power to be halved (that is, reduced as much as is the noise power when the receiver bandwidth is halved), the remaining sideband must have 0.707 times the reference carrier amplitude.

In the composite system, half of this sideband (35 percent) is con-

tributed by a-m, and half by p-m. Assume that 3,000-cycle p-m alone is acting on the carrier; an index of 0.75 radian is sufficient to give first-order sidebands of 0.35 times the reference amplitude. The resulting spectrum (amplitude vs frequency) is illustrated in Fig. 2A. If this phase-modulated radio wave is simultaneously amplitude-modulated 81.5 percent by a 300-cycle tone, the spectrum becomes that of Fig. 2B. It will be observed that a pair of a-m sidebands (shown with dotted lines for clarity) is generated about each component of the original p-m spectrum. The low frequency of the second modulation helps to make the situation clear. Note that the entire wave must be amplitude-modulated 81.5 percent in order to generate two sidebands on either side of the reduced carrier of 0.35, or the same amplitude as the first-order p-m sidebands.

Components Combine

We may now re-examine the spectrum when the a-m frequency becomes relatively high, say 2,900 cycles, illustrated in Fig. 2C. This representation of the sidebands shows what happens when the frequencies producing the a-m and the p-m become the same. The groups of sidebands merge, and the resultant sideband at each 3,000-cycle interval can be found by combining the components, taking the various phase relationships of each component into account.

Figure 2D shows the original p-m spectrum but with the relative phases of the components indicated by the direction of the vectors, for the instant at which the modulating voltage passes through a maximum.

and Phase Modulation



FIG. 1—Mobile single-sideband transmitter used by author to test dependability of unconventional modulation system that produces a signal which is easily demodulated by a conventional receiver

Figure 2E shows this spectrum with the addition of a-m sidebands corresponding to an audio voltage 90 degrees out of phase with that producing the p-m; however, for the sake of clarity these sidebands have been shown displaced from their correct position in the frequency spectrum. In Fig. 2F, the sidebands are given their correct position and phase, so that their resultant can be found. The final spectrum, phases once more disregarded, appears in Fig. 2G.

It will be seen that the first-order sidebands on one side of the carrier are nearly cancelled (cancellation can be made complete by a slight reduction in the percent a-m), while those on the other side add directly. Of particular interest is the relatively strong second-order sideband (0.22) on the same side of the carrier. The remaining higher order sidebands are negligible, being 20 db or more below the desired first-order sideband.

Modulation Distortion

The existence of a strong secondorder sideband in the composite modulating system is not surprising when it is remembered that the envelope must necessarily be sinusoidal when all frequency components are taken into account. This must be the case since the shape of the envelope is solely due to the a-m portion of the composite modulation. If the carrier and the firstorder sideband were taken by themselves, their envelope would be distorted, rather than a pure sinusoid. (For example, if carrier and sideband were equal in strength, their envelope would resemble the output of a full-wave rectifier.) It follows that the strong secondorder sideband has the effect of removing a large portion of the envelope distortion which would otherwise be present. Because the other sideband components are 10 db or more weaker than the strong second-order sideband, it seems safe to assume that the envelope will be very nearly sinusoidal even when these components are neglected.

It is interesting to observe that when a true carrier-plus-single-sideband signal in which the ratio of sideband to carrier is 0.7 to 0.86, as in the situation under discussion, is rectified in a linear detector, the second harmonic distortion in the output is 18 percent. This is of the same order of magnitude as

the audio signal which would be produced by the rectification of a carrier of 0.86 and a second-order sideband of 0.22.

It therefore appears that when, in the composite system, only the carrier, first-order sideband and strong second-order sideband are accepted by a selective receiver or band-pass filter, the resulting signal will have an envelope substantially free from distortion.

Furthermore the distortion will be low at all modulation levels. While the p-m portion of the second-order sidebands will decrease faster than the modulation level, thus tending to remove the difference between these sidebands at low signal levels, at the same time the distortion accompanying linear detection of a single firstorder sideband tends to decrease as the modulation depth decreases. Thus the distortion (and the level of the spurious higher-order sidebands as well) will never exceed the full modulation situation illustrated in Fig. 2G.

We may now consider a typical example. Assume a voice communication system having a maximum modulating frequency of 3,000 cycles. A receiver having a 3,000cycle bandwidth and a linear diode detector can be tuned so that the carrier falls at the proper edge of the passband. For all modulating frequencies below 1,500 cycles, the strong second-order sideband falls within the receiver passband, and detection is substantially distor-For modulating frequencies between 1,500 and 3,000 cycles, the second-order sideband will fall outside the receiver passband, and detection will be accompanied by roughly 18-percent dis-

As far as adjacent-channel interference is concerned, there will be a band of frequencies 3,000 cycles wide outside the 3,000-cycle bandwidth of the system in which spurious sidebands will be heard of an amplitude equal to that which would be present if the radio wave were amplitude-modulated in the

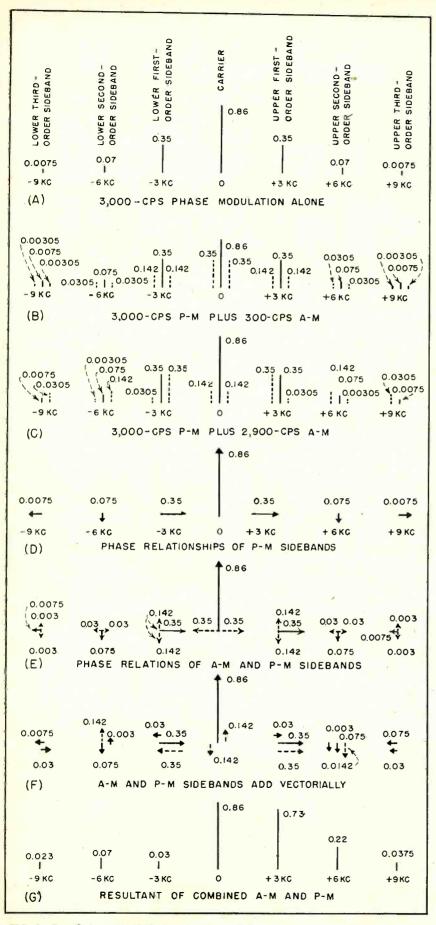


FIG. 2—Type of transmitted signal produced by composite modulation can be visualized from the sidebands produced by it. Signals shown are not to scale

conventional way with a signal containing approximately 45-percent second-harmonic distortion. In estimating the practical effect of this interference, it should be remembered that the strongest and most often-occurring frequency components in speech or music are in the range below 1,500 cycles, where the sidebands fall within the assigned channel and negligible distortion occurs in reception.

Adjusting the Modulators

The combined modulation system has been tried both in the laboratory and in several experimental transmitters. Its installation involves one unusual feature, which is a phase-equalizing network. The purpose of this network is to make the frequency response of the phase modulator, and of any associated amplifiers, identical to that of the amplitude modulator and its associated amplifiers. This is essential if the 90-degree phase shift existing at the output terminals of the phase-shift network is to be preserved through to the voltages which actually perform the phase and the amplitude modulation. Any difference between the shapes of the frequency response curves of the two modulator channels will introduce a spurious phase shift which must be avoided. In most cases it will be found that the frequency response of the amplitude modulator is worse than that of the phase modulator, owing to the presence in the former of driver and modulation transformers.

The required equalization can then be obtained by inserting simple single-section R-C high-pass and low-pass filters in the audio line to the phase modulator. It is convenient to make the resistances variable and to find the correct values experimentally with the aid of an oscilloscope connected to show the phase shift between the voltages actually performing the phase and the amplitude modulation. The leads normally connected to the two outputs of the 90-degree phaseshift network are connected in parallel and to the terminals of an audio oscillator. If the 45-degree line on the oscilloscope opens into an ellipse at any frequency, undesired phase shift is present. The

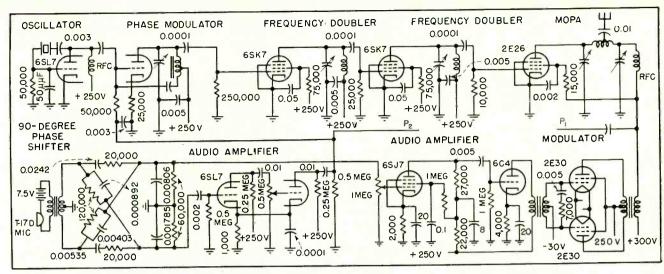


FIG. 3—Principal circuits of mobile transmitter using composite modulation. Values of unlabeled parts depend on carrier frequency

correct adjustment of the equalizing network is surprisingly easy to find in practice, even when widely different phase and amplitude modulators are used. It is theoretically possible that filters having two or more sections with differing time constants might be needed if the amplitude modulator has many stages compared with the phase modulator. In the cases tried so far, single-section filters have been sufficient.

The phase modulation index for optimum sideband cancellation is readily found with the aid of a selective receiver, preferably one having a crystal filter. A sine wave in the 2,000- to 3,000-cycle range is applied to the amplitude modulator, and the percent modulation adjusted to 81.5. The receiver is then tuned to the unwanted sideband and the gain of the phase modulator adjusted until cancellation occurs.

Note that only one adjustment (relative phase modulator gain) is required. There is no simultaneous radio-frequency phase setting to be made, nor are there any balanced modulators whose characteristics must be equalized, as in other phase-rotation single-sideband systems.

Cancellation of the undesired sideband with the composite system is readily detectable in practice, even with a fairly unselective receiver. Receiving operators are seldom aware of the nature of the incoming signal, since it sounds like any other; they automatically tune slightly to one side of the incoming

carrier to make the modulation sound the loudest. Reversal of the phase of the voltage fed to one modulator will cause the opposite sideband to be cancelled: the receiving operator then finds he must tune to the opposite side of the carrier for loudest modulation. Another interesting demonstration is to ask the receiving operator to narrow his bandwidth and tune in the composite signal for best reception. If the phase modulator is then disabled, the receiving operator will report a noticeable drop in the strength of the modulation.

Circuit Details

To illustrate the stability and reliability of the composite system, the author installed a mobile single-sideband transmitter in the trunk compartment of his car. After 4,000 miles of vacation driving, some of it over unpaved roads in national parks, the transmitter was checked and found to be in perfect adjustment, having given satisfactory performance throughout the trip.

A simplified circuit diagram of this transmitter is shown in Fig. 3, and a photograph of the installation appears at the beginning of this article. The 90-degree audio phase shift is obtained from a network driven directly by a surplus T-17D carbon microphone. This microphone also serves very conveniently as a band-pass filter, its output being restricted to those frequencies (300-3,000 cycles) for which the phase-shift network is

effective. The stepup transformer between the microphone and the network should not have too high a turns ratio; the conventional variety will not maintain a 180-degree phase shift between halves of the secondary at all frequencies, owing to the finite input impedance of the network. Small power-output transformers of the type designed to match push-pull tubes (20,000-ohms plate-to-plate) to a 200-ohm line have been found to be satisfactory.

The transmitter itself consists of a commercial phase-modulated unit which has been modified for simultaneous amplitude modulation. The final stage was rewired to permit simultaneous plate and screen modulation, and a smaller screen bypass capacitor inserted. No other changes were needed. The amplitude modulator is conventional. In this particular arrangement, the only phase equalization found to be necessary was the 0.002-uf capacitor in series with the line to the phase modulator audio input. This was determined by connecting an oscilloscope to the points marked P_1 and P_2 and following the procedure outlined earlier.

Research, the result of which is described in this paper, was an outgrowth of Project W-28-099-Ac-131 between Stanford University and the Watson Laboratories of the Air Materiel Command. The author wishes to thank the Watson Laboratories for their cooperation and for permission to publish this paper.

Regulator for

By CARL A. HELBER

Jack and Heintz Precision Industries, Bedford, Ohio

UMEROUS methods have been used for regulation of aircraft inverters. Among them are the carbon pile, Tirrill vibrating contact, Brown-Bovari, Silverstat and others. In each of these systems there are some moving parts which are subject to mechanical wear.


The electronic regulator to be described compares favorably with the previously mentioned regulators in regard to size, weight, accuracy, reliability and other factors. While the regulator which was developed for use on a 250 voltampere machine is somewhat heavier (1.7 lb compared to about 1.1 lb) than the carbon pile regulator, it has the advantage of having no moving parts.

In laboratory tests the unit appeared to be quite reliable for any of the conditions it was designed to meet. The electronic regulator is capable of providing about 40 watts of d-c power to the exciter field in the inverter and maintains the output voltage of the inverter within ± 1.0 volt from no load to full load.

Inverter Operation

As shown in the diagram, the inverter is supplied with 28 volts d-c from the aircraft battery and generator. The exciter field current is supplied partly by the 28-volt d-c source to help the machine build up and partly by the rectified a-c from the output of the inverter. Without a-c excitation, the 28-volt supply provides about 30 volts at the output terminals of the inverter at no load.

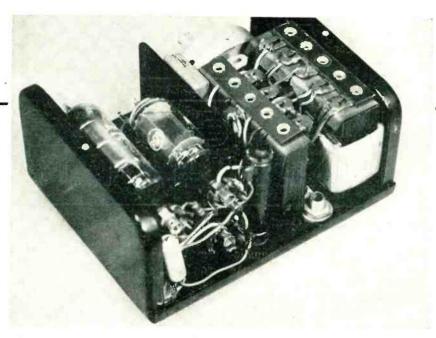The field current is governed by the saturable reactor SR. As the current through the d-c winding of SR is increased, the reactance de-



The entire regulator is packaged to fit into a space of $4\frac{1}{4}$ by $3\frac{1}{2}$ by 2 inches high

creases. This action increases the amount of excitation provided to the machine. By adjusting this current to the proper value, the output of the machine can be maintained within narrow limits for a wide range of load conditions.

Tube Circuit

Most voltage-sensitive circuits provide a rapidly increasing current with a small increase in voltage above some given reference level; this being just the opposite of the characteristic which is desired by the saturating coil of the reactor. It is therefore necessary to provide a fixed maximum current through the saturating coil of the reactor, this current being bucked by the current provided by the voltage-sensitive circuit. The fixed current is made high enough to provide full output from the regulator when the voltage reference circuit is not supplying any bucking current. The major portion of this current is bucked out by the voltage reference circuit under the condition of lowest field requirement (no load).

The voltage-sensitive circuit, 2D21 and OB2, is designed to provide a sharply increasing current

for a slight increase in output voltage. This characteristic is obtained by triggering a thyratron with the voltage drop across a resistor in series with a VR tube. The thyratron is normally a-c biased to a point sufficient to prevent firing. When the voltage drop across resistor R_1 is great enough to overcome the necessary portion of the bias, the thyratron will fire. With the circuit arrangement used, firing occurs at approximately the peak value of the output voltage and therefore the thyratron conducts for about one quarter of a cycle.

Because of the relatively high inductance of the polarizing winding on the saturable core reactor, the pulses of thyratron current are smoothed considerably. The number of these pulses provided to the polarizing coil per second determines the average current flowing in the polarizing coil of the saturable core reactor.

In typical operation, the number of pulses per second may range anywhere from one to four hundred. This current opposes the fixed current provided by resistor R_2 . Thus the polarizing coil current may have any average value between the maximum current as provided

400-Cycle Inverter

Voltage output of an aircraft inverter is maintained within plus or minus one volt from no load to full load by a two-tube electronic regulator having no moving parts. Operation remains substantially constant down to — 55 centigrade

by the battery and a value of zero.

Resistors R_3 and R_4 are used to provide the a-c bias for the 2D21. For economy, resistor R_3 is a potentiometer which is used to adjust the level of the regulator voltage. It was found that the d-c voltage drop across the polarizing coil of the reactor was at times sufficient to fire the 2D21 before the bias had gained sufficient amplitude on the positive half cycle of the a-c voltage. In other words at the instant when the a-c voltage is zero going from the negative half cycle to the positive half cycle, the bias is also zero. Since the voltage drop across the polarizing winding may be about 10 volts, some 2D21's will fire at this potential.

Capacitor C_1 is used to shift the bias a few degrees ahead of the anode voltage in order that the d-c voltage across the polarizing coil will not fire the thyratron. It should be noted that with the constants in the circuit the VR tube fires on the positive half of every cycle.

The thyratron may or may not fire on the positive half of each cycle depending upon the magnitude of the peak voltage drop across R_1 . This feature makes the firing of the thyratron dependent upon the conduction characteristics of the VR tube rather than upon the striking characteristics.


Since the regulator works on the peaks of the voltage which it is regulating, it is important to maintain a fairly sinusoidal wave form for the output of the machine. Another specification for these machines requires that the waveform be quite good any way so that the regulator does not actually impose any additional hardship on the designer of the machine.

The current supplied to the exciter field ranges from about 70 ma at 105 volts for no load to 150 ma at 225 volts for an output of 250 voltamperes at a power factor of 0.9 lagging.

The regulator is used on a 3-phase inverter which is designed to

provide 250 va of 3-phase power continuously with conservative ratings or 250 va of single-phase power from terminals A and B with the machine running just within ratings. Checks have been made on the operation of the regulator at -55 C and the results indicate that the difference in voltage between this temperature and room temperature is not more than about one volt. Compensation for the variation in exciter field resistance had to be made, however, because of the fact that the field resistance, which is about 1,400 ohms at room temperature, is about 900 ohms at -55 C. A thermistor shunted with the proper value of resistance provides compensation and results in a regulator which is quite satisfactory. Tests at full load were run for 500 hours followed by 150 hours of cycling tests during which the load was changed abruptly from full load to no load in 5-second intervals. The output voltage remained within ± 1.5 volts for this entire period. The regulator was still operating satisfactorily when the test was shut down.

It was found necessary to shock mount the regulator to obtain suitable life from the 2D21 thyratron. When mounted directly on an inverter running at 12,000 rpm, the thyratron would last for about 100 hours after which enough cathode material had been broken loose to make the tube characteristics change considerably. It was suspected that the high (200 cps and above) vibration frequencies were responsible for this effect. Proper vibration isolation solved this problem. Regulators based on the same principle have been built for machines up to 2,500 volt-amperes capacity and undoubtedly could be made for much larger machines.

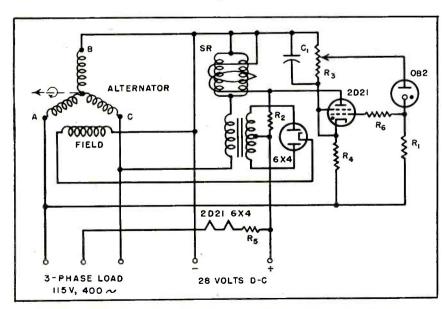

Complete circuit of voltage regulator for a 400-cycle, 250-va aircraft inverter

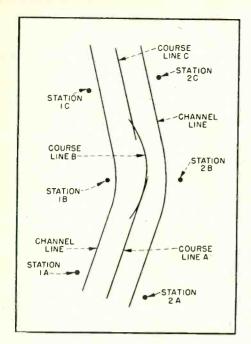


FIG. 1—Transmitter locations along a channel

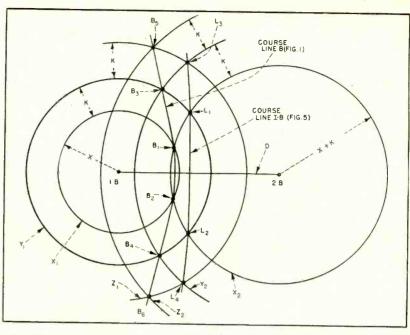


FIG. 2—Construction shows how straight and curved course lines are generated

Sonic Navigation

A new hyperbolic underwater-sound navigation system for harbors and channels uses pairs of transmitters pulsed at audible frequencies. A ship on course receives the two tones simultaneously. Aural monitoring assures position within 50 yards while lesser deviations are possible when meter indications are used

ONVENTIONAL METHODS harbor navigation require the following of floating buoys in order to keep ships in the proper traffic lanes as well as in channels of safe navigable depth. Pilotage by buoys becomes extremely difficult in fog when neither the buoy nor the light with which it may be equipped is visible for any appreciable distance. Whistling and bell buoys can be followed at best only at a slow rate of speed and then only if all other conditions are quiet. As a result most ships are still forced to wait out a fog rather than risk entering or leaving a fog-bound harbor.

The Hysonav system described below employs underwater sound to mark channels and traffic lanes which can be followed by any vessel having only the simplest listening equipment, independent of weather conditions.

System Elements

The system consists of one or more pairs of underwater sound generators located at spaced positions along a channel or traffic lane, one member of the pair (illustrated) on each side of the channel. In each pair the members are pulsed at intervals, and the pulse from each member has a distinguishing frequency characteristic. A person on a vessel sailing between a pair is in a position to hear both generators with a simple listening or hydrophone arrangement. Pulse lengths as short as 30 milliseconds are used. so that the listener can ascertain his position within fifty yards.

In accordance with the basic con-

cepts of a hyperbolic system, the listener navigates the path on which he receives a single note, indicating that first-arrival signals from both generators are being received simultaneously. This path is made to be a straight line or a curve, depending on channel shape and other harbor requirements. Where it is a straight line, two generators are pulsed simultaneously, so that the locus of points where the first arrival pulses are available simultaneously is a straight line which is the perpendicular bisector of the line between the generators. provide a curved path, the two generators are pulsed in sequence, and, as explained below, the isotime locus generated is a hyperbola, which is made to fit a particular channel by adjusting the time interval between

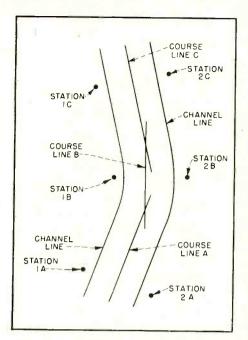


FIG. 3-Curved channel-straight courses

System

By STANLEY R. RICH


Design Coordinator

and

A. H. ROSEN

Patent Attorney

Submarine Signal Co. Boston, Mass.

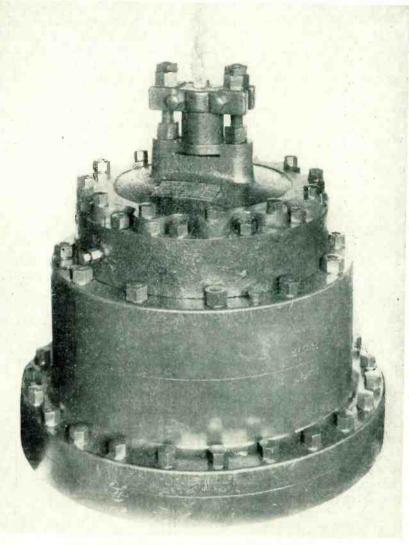

Oscillator transducer used at transmitter stations

the pulses. If the navigator is not on the predetermined path or course, he will hear first one and then the other pulse, and he tells them apart by the difference in audible pitch. In this way he knows which way to turn to regain his course. This information may be used to enable the navigator to keep to one side of a predetermined center line for two-way traffic.

Referring to Fig. 1, a ship channel is illustrated, as delineated by a pair of channel lines. It is desired to provide a system that will guide a vessel along the center line of this channel. A number of pairs of sound generators are located along the channel, the members of each pair being located one on each side. Thus Stations 1A and 2A comprise one pair, 1B and 2B a second pair,

and 1C and 2C are a third pair. Stations 1A and 2A are on a straight section of the channel. They are pulsed simultaneously at intervals which, for convenience, are regular. The stations of a pair are distinguished by a difference in the pitch of the respective signals; that is, the frequency of sound emitted by Station 1A is different from that of Station 2A. For example, 1A may oscillate at 600 cycles per second when pulsed, while 2A may oscillate at 900 cycles per second. The stations are so located with respect to the channel that the perpendicular bisector straight line drawn between them coincides to a satisfactory degree with the center line of the channel in the region of these stations.

This perpendicular bisector is

designed as course line A. It is the locus of points which are equidistant from both stations for sound travelling through the water, so that a person on a vessel which is navigated along this line is in a position to hear a single sound, which is a mixture of 600 and 900 cycles per second, whenever the stations are simultaneously pulsed. Thus, a navigator who is provided with only simple underwater listening equipment needs merely to steer the path along which he hears this single mixed signal to remain in the channel and on course line A in even the deepest fog. If he steers or drifts too far to one side or the other, he will hear a sequence of two pulse signals, either a low and then a higher frequency, or vice versa, each time the two stations are

pulsed, and will know that he is closer to the station that emits the first frequency he hears. Navigators would, of course, be furnished with the necessary information from which they can mark the locations of the stations and the frequencies of their signals on a chart of the channel, so that one may know which way to turn to sail along course line A. The course line can be regarded as a highway center-line, and, when it is desired to navigate to either side, it is useful that the signals are received successively rather than simultaneously.

Curved Channels

After passing along course line A, the channel curves to the left. in the region of stations 1B and 2B. Stations 1B and 2B are pulsed in such a fashion that the locus of all points at which the emitted pulses will be heard simultaneously is a curved line which follows the curve in the channel to a satisfactory de-This line is designated as course line B in Fig. 1. Course line B is curved by pulsing one station of the pair before the other. The direction of curvature is determined by the order of pulsing, and the degree of curvature by the amount of time difference between the pulsing of the first and second stations. In Fig. 1, course line B is curved to the left by pulsing station 2B prior to station 1B.

Station 1B emits signals having the same sound frequency as those of 1A, while 2B emits signals having the same sound frequency as those of 2A. As the navigator leaves Stations 1A and 2A behind and approaches 1B and 2B, the signals from the former fade and those from the latter become louder. Where the two paths cross, both pairs of stations will be heard, and a choice of paths may be presented to the navigator. Before he has gone far, the signals from Station A will become weak enough and those from Station B strong enough that there will be no doubt by which to be guided. The signal strengths of the pairs of stations are so adjusted that there is not a strong set of signals tending to guide the navigator out of the channel; that is, course line A fades out in the listening equipment long before the navigator can be guided out of the channel, while course line B becomes comparatively so strong that he will make no other choice than to follow it. Also, the signals from the nearest pair will be heard first. From course line B the navigator proceeds to another straight course line C, which is produced by the third pair of stations 1C and 2C in the same fashion as course line A.

The signals that are heard by the navigator consist of first arrivals plus reverberation signals. The first arrivals are the signals by which the navigator is guided, the reverberations being ignored. Since the first arrival signals are much louder than the reverberations, that is not difficult. Also the pulse repetition frequency of the generators is made deliberately low (ten seconds between pulses). This per-

mits ample time for reverberations to die out prior to the successive pulsing of the generators. The pulsing of the various pairs of stations need have no definite interrelation, but as will be shown a sequence can be provided which further reduces the chances of confusion.

Timing the Pulses

Consideration of the problem of planning and laying out course lines in a channel in the system reveals that there are four ways in which a pair of sound generators may be treated that are of interest. These four cases are:

Case 1. They may be pulsed simultaneously, and the locus of points of simultaneous arrival is a straight line which is the perpendicular bisector of the line between them (course line A).

Case 2. They may be pulsed in

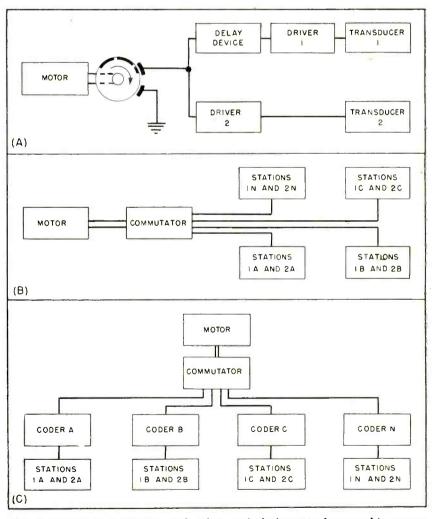


FIG. 4—Development of keying and coding methods from simple motor-driven commutator. Delay device shown in A is used to generate curved-channel signals

sequence, and the locus of points of simultaneous arrival is that line of which each point is X lineal units from the second station pulsed and X+K lineal units from the first station pulsed, where K is a constant equal to ct, c being the speed of sound in water, and t the time difference between pulses in a given pair.

Case 3. They may be pulsed simultaneously, and the locus of points of fixed differential time (t') of arrival is that line in which each point is T seconds from the first station heard, and T+t' seconds from the second station heard. Here T is analogous to X above, and T+t' is analogous to X+K.

Case 4. They may be pulsed in sequence and the locus of points of fixed differential time (t') of arrival is that line in which each point is T seconds from one of the stations, and T+t+t' seconds from the other station, where both t' and t are constants. Again T is analogous to X and T+t+t' is analogous to X+K.

Referring now to Fig. 2, Stations 1B and 2B are shown with a straight line D drawn between them. The actual shape of course line B depends not only on X and X + K as developed above, but also on the length of D, which is apparent from Fig. 2. If we assume that Station 2B is pulsed before Station 1B, then in accordance with Case 2 above, the locus of points of simultaneous arrival of the first arrival signals from both stations is that line which is everywhere Xlineal units from Station 1B and X + K lineal units from Station 2B. This locus can be determined as shown in Fig. 2, using one of the standard methods by which hyperbolas are constructed in elementary descriptive geometry. The distance D being fixed, the amount of curvature of the hyperbola drawn is governed by the value of the constant K, which is to say, by the fixed amount of time delay between pulsing of the two generators 1B and 2B, since c is the same for sound from both stations. It will be recognized that the constant K represents an identical elapsed time in the travel of both signals to the observer. It will likewise be appre-

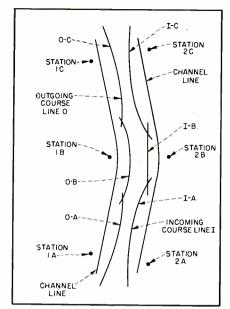


FIG. 5—Incoming and outgoing channels can be indicated by observing time differences

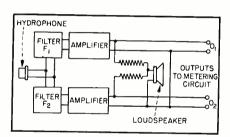


FIG. 6—Time difference indicator

ciated that the foregoing discussion applies equally well to Cases 3 and 4 mentioned above, being understood that K includes also the fixed differential time of arrival.

When the bend in a channel is slight, it is not always necessary to curve the course line to fit, but, depending on the width of the channel, the conditions to either side of it, and the traffic problem, it may often be satisfactory merely to employ a series of straight course lines having different respective directions. Such an arrangement is that of Fig. 3, which is otherwise the same as that of Fig. 1.

Receiving Equipment

As stated, a vessel need be equipped with only the simplest kind of listening apparatus in order to take some advantage of the system. Such an apparatus might comprise a hydrophone connected to a suitable amplifier, which furnishes output signals to a loudspeaker. The hy-

drophone is omnidirectional in construction and installation. An even simpler arrangement, a stethoscopelike listening arrangement known as a sea tube can be employed. Or, in a more elaborate electronic equipment the two pulses can be separately amplified and compared, as in the arrangement shown in Fig. 6. The hydrophone then feeds into two filters in parallel, each of which passes only the frequency of one of the stations. One filter is set for f_1 (600 cps) and the other filter is set for f_2 (900 cps). Each filter feeds into an amplifier which provides two separate output signals at O_1 and O_2 , respectively. The loudspeaker is provided with the output of both amplifiers simultaneously by a bridging or isolating circuit arrangement. The output signals have sufficiently high level for use in an automatic electronic time comparison circuit. Such a circuit is shown in Fig. 7.

Keying the Transmitters

The signal generating equipment is composed of conventional parts, as in Fig. 4A. A keying device or coder controls the output of two transducers, one for each station of a pair. The coder generally comprises a pair of switch contacts and a motor-driven commutator. The commutator has a group of switch segments each of which is successively closed. One segment, in this instance, is of a given length, and the other two are longer so that when the commutator is rotated in the direction indicated by the arrow. the code letter W is generated. The coder keys two drivers, one for each of the two transducers, respectively. The keying signal to one of the drivers is fed through a device that serves to delay the output from one transducer with respect to that from the other transducer. Thus, if these transducers are the sound producers for Stations 1B and 2B of Fig. 1 respectively, the system of Fig. 4A can be set up to emit, for each keying operation of the coder, a pulse from Station 2B and thereafter a pulse from Station 1B, the time between these pulses being controlled by the delay device. The delay device can be omitted where a straight path (Stations A or C) is desired, or placed in the line to the

other driver if the curvature of the path is to be reversed.

The possibility of confusion when the navigator is transferring his observations from one pair of stations to the next pair along his path has already been noted. The arrangements shown in Fig. 4 are provided to eliminate such confusion completely, and are particularly valuable in crowded harbors or in channels where the region to either side is dangerous. To enable a navigator to distinguish between sets of stations, the various pairs may be provided with characteristic codes. Thus, the A stations may be pulsed with a dash, while the B stations may be pulsed with two dots, and the C stations with a dot and a dash.

Confusion between adjacent pairs of stations can be minimized also with the system shown in Fig. 4B. There each of the pairs of stations is brought to a commutator switch driven by a motor. The switch functions in the usual manner to key the pairs of stations in succession, one pair at a time. Keying is maintained at a low repetition rate so that a navigator will not hear the signals of two pairs of stations together. This arrangement also permits reverberations to die out between the keying of adjacent stations. The arrangement of Fig. 4B also enables a navigator to pick out the signals of the next pair of stations that he is going to use before he begins actually to use them.

In Fig. 4C the coding arrangement of 4A is incorporated into the system of 4B by placing individual coders in the lines between the commutator and the pairs of stations, thereby keying the respective pairs of stations through their own individual coders.

Multichannel Navigation

Now, by arbitrarily choosing two sets of particular fixed time differences and orders of arrival for each pair of stations, two separate marked paths can be provided for incoming and outgoing traffic. Figure 5 illustrates how an incoming course line I and an outgoing course line O are provided in the same channel, so that two-way traffic can be handled. The incoming course line I is made up of sec-

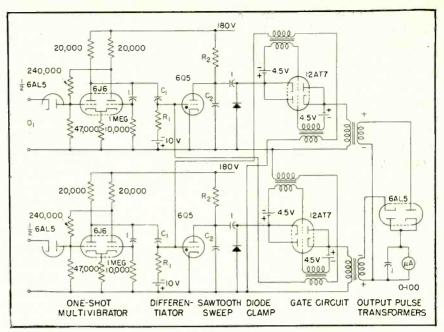


FIG. 7—Circuit diagram of metering circuit used with time difference indicator

tion I-A for stations 1A and 2A, section I-B for Stations 1B and 2B, and section I-C for Stations 1C and 2C. Similarly, the outgoing course line is made up of sections O-C, O-B, and O-A. Each section of each course line has a predetermined fixed time difference and order of arrival for the pulses from its pair of stations.

Where the channel is straight or nearly so, the stations of a pair are pulsed simultaneously, as in Case 3. Such stations are the A stations and the C stations. A navigator negotiating the incoming course line I is then in a position to hear the No. 2 member of each of these pairs first, while on the outgoing course line O he will be in a position to hear the No. 1 member first. Where the channel curves to an appreciable degree, the two B stations are pulsed in sequence (as in Fig. 1). Then Case 4 applies, and the navigator on the incoming course line negotiates a path that is nearer to the No. 2 station than to the No. 1 station; even nearer than is the corresponding course section B in Fig. 1. As a result, the signal from Station 2B not only starts first, but also arrives first. Referring again to Fig. 2, it is recalled that circles X_1 and X_2 exist simultaneously, while Y_1 and Y_2 exist simultaneously, and the same is true of Z_1 and Z_2 . However, if the navigator is to occupy a position such

that the wavefront represented by circle X_2 passes him first, and then, a fixed time later the wavefront represented by circle Y₁ passes, which is the condition when he negotiates incoming course section I-B, then the line that determines section I-B is the locus of points L_1 , L_2 , L_3 and L_4 , which has considerably less curvature than line B. This is to be expected, for the curvature that is imparted to line B by starting the pulse from 2B prior to 1B and receiving them simultaneously is changed in Fig. 5 by receiving the pulse from 2B prior to the pulse from 1B. For the same reasons, the outgoing course section O-B has a more pronounced curvature than line B in Fig. 1, for here the pulse from 2B is not only started earlier than the 1B pulse, but it is also received later. From the navigator's point of view, the effect is the same as on the straight stretches of the channel; on the incoming course the Station 2B pulse arrives first, and on the outgoing course the 1B pulse arrives first.

Thus the navigator may regard the course line in Fig. 1 as the center-line of a highway, and by keeping the pulses of one pitch coming in before the pulses of another pitch, he keeps to the right of the center line. From his charts, he can determine exactly what the time difference should be for each pair

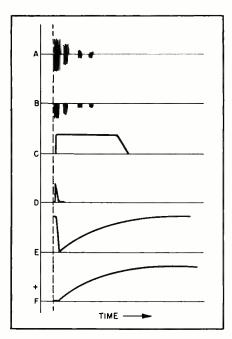


FIG. 8—Waveform oscillograms in time difference circuit

of stations to keep himself in the best path to the right of center. The time differences that he must observe for each line for each pair of stations will be furnished to the navigator in advance as part of his instructions for conduct while entering and leaving the harbor. He may employ the arrangement shown in Fig. 6 for determining that he is on a proper course line section. Such an arrangement is particularly valuable in that it tends to reject extraneous noise signals, such as propeller noises from other ships. With this apparatus, the ear alone can be depended upon to recognize and maintain a small time difference between two signals of a pair of stations, making possible safe navigation with very simple listening apparatus. For accurate measurement of the time difference, however, the navigator can employ the indicator shown in Fig. 7.

This time difference indicator employs two identical channels, one connected to output O_1 and the other to output O_2 of Fig. 6, in each of which there is generated a single voltage pulse trigger in response to the first arrival signal from the corresponding station of the pair under observation. Each pulse trigger initiates a sawtooth voltage wave in its own channel and controls a normally open gate stage in the other channel. The output of the

sawtooth voltage stage of each channel is momentarily made available, through the gate circuit of that channel, to a meter into which both channels feed, and which indicates the amount and sense of the time difference. Since both signal channels are identical, only one need be described.

Channel Indicator Circuit

Each signal channel includes a one-shot multivibrator, a differentiating circuit, a sawtooth sweep generator, a gate circuit, and an output pulse transformer. The multivibrator is set up so that the first triode is normally conducting in the absence of signals. A diode is provided in the input circuit of the one-shot multivibrator and connected so that negative voltages only appear on the control grid of the normally conducting triode in response to signals from the station under observation. As shown in Fig. 8, at A, the signal from a station consists of a first arrival wave train of comparatively large amplitude, plus reverberations. The negative portion of this signal, shown at B, appears on the grid of the triode. This signal initiates the action of the one-shot multivibrator whose time constants are set up to be long enough to prevent reversal until all reverberations and other signals have disappeared. The differentiating circuit has a time constant C_1R_1 of the order of 1 millisecond, and produces a short positive pulse across R_1 marking the leading edge of the multivibrator reversal (C). This pulse is shown at D.

The sweep generator is an RC circuit (R_2C_2) triggered by a thyratron. The control grid of the thyratron is triggered by the differentiating circuit R_1C_1 . Thus, a semisawtooth voltage wave is provided as shown at E. The sawtooth voltage wave is sampled by a gate circuit.

A diode clamp is connected across the output of the sweep generator on the isolated side of the channel. The sweep voltage that is available to the gate circuit is shown at F. This sweep voltage starts at the zero level because of the diode clamp.

The gate circuit is a conventional back-to-back triode gate. Each sec-

tion is biased to cutoff, as shown, and is provided with a grid-input-control pulse transformer. The O_1 channel gate is connected to the differentiating circuit of the O_2 channel, and the O_2 channel gate is connected to the differentiating circuit of the O_1 channel. Thus the O_1 channel gate is controlled by the positive pulse from the O_2 channel, and the O_2 channel gate is controlled by the O_1 channel.

The secondary windings of the output pulse transformers of the O_1 and O_2 channels respectively are connected to a normally centered meter which is deflected to one side or the other depending on the magnitude and direction of the output signal. The two secondary windings are so phased that their output signals deflect the meter needle in opposite directions, and each is connected to the meter through a suitable rectifier.

If the two first arrival signals from a pair of stations are picked up in sequence, one is fed through O_1 to one channel, while the other is fed through O_2 to the other channel. The pulse trigger (Fig. 8D) which corresponds to the first signal opens the gate in the second channel, but since the second channel has not yet received any signal, there is no sweep voltage to be sampled through the opened gate. This same pulse, however, starts the sawtooth wave in its own signal channel. Thereafter, the trigger pulse from the second channel opens the gate in the first channel and a pulse having a peak voltage determined by the instantaneous level of the sawtooth voltage in the first channel is applied to the output circuit. Thus, the sampled output of only one of the sweeps is applied to the meter, namely, that which comes from the signal channel carrying the first signal received, and the voltage level at which it is applied is determined by the time difference between the two signals. If the two signals are received simultaneously, both trigger pulses occur simultaneously and the meter will not deflect. The loudspeaker will at all times furnish the information that the signals are being received, so that an operator need refer to the meter only at intervals to secure an accurate measurement of the time difference.

Low-Distortion

RANSFORMERS are recognizable as sources of distortion due to the nonlinearity of the inductance, which gives rise to an exciting current that contains components other than the fundamental. The same nonlinearity also produces intermodulation distortion.

The crossover network can be used to reduce transformer distortion by placing at least part of the low-pass filter between the power source and the low-frequency output transformer, instead of between the output transformer and the load.

Consider an output transformer operating between a high-impedance tube source and a 5,000-ohm load (referred to the primary side). Assume the primary inductance to be 26 henrys. At 30 cycles $\omega=190$ and $\omega L=5,000$. The shunt reactive load, equal to the resistive load, would produce a response which is 3 db down at 30 cycles. This is considered good response.

Next consider that the exciting current contains a considerable harmonic content. At ordinary power levels the third harmonic would typically be about one-third the amount of the fundamental current. This harmonic current, flowing in the generator impedance, produces a distortion voltage which is then fed to some other load, such as a high-frequency channel.

Evidently, a much higher primary inductance is required for reasonable distortion than would be required merely to give a flat response.

The circuit of Fig. 1A is an approximate equivalent of a tube source G_1 having a tube impedance R_r , feeding a transformer having a winding resistance R_r and primary inductance L. The distortion components are considered as being produced by generator G_2 . This added generator produces harmonic voltages and intermodulation products.

The crossover network arrangement of Fig. 1B accomplishes two major purposes. First, the low-pass filter $L_1 - C_1$ attenuates high frequencies propagating in either direction. Voltages produced by G_2 are attenuated before reaching tube impedance R_P , so that relatively less distortion voltage is available at R_P for transmission to the high-pass channel.

Second, $L_1 - C_1$ attenuates high frequencies from G_1 propagating to the transformer, so that a narrow range of frequencies is received by T_1 . The modulation products generated in T_1 (represented by G_2) are therefore of lower order than would be the case if the transformer were required to handle the entire spectrum. Furthermore, such modulation products from G_2

By PAUL W. KLIPSCH

Klipsch and Associates Hope, Arkansas

are again attenuated in their transmission back to the impedance of the tubes.

Obviously, both these effects reduce the distortion which can be fed to the high-frequency channel. The most annoying distortion generally appears as a form of high-frequency noise, and reduction of transmission of low-channel distortion to the high channel reduces this form of distortion.

This network system, by limiting the distortion produced by the nonlinear exciting current of the lowfrequency output transformer and by limiting the transmission of such distortion back into the rest of the system, offers a double-dose cure for over-all distortion.

The network of Fig. 2 has already been described in some detail.¹ This circuit was originally developed primarily for purposes of economy. Since the original publication, some of the reasons for the superior performance have been studied, with the result that the advantage of lower distortion is now recognized as of greater importance than the reduced cost.

Numerical Example

For the conventional tube output circuit one may set up transformer requirements. Taking the exciting current as composed of a fundamental component $I_1 = E/\omega L$ and a third harmonic content $I_2 = (1/3)$ I_3 , consider a tube source with R_P of 2,000 ohms working into a load of 5,000 ohms, and consider a low-end cutoff of 31 cycles. Assume we want to limit third harmonic distortion to 0.5 percent or 0.005 per-unit of the fundamental.

The inductance can be determined from

 $L = R_P/3\omega_1 D$ (1) where L is the primary inductance of the transformer, R_P is the plate

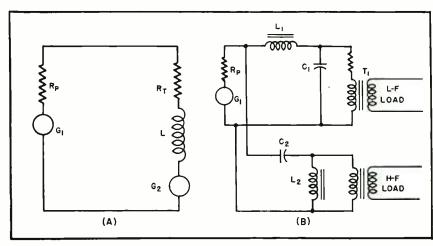


FIG. 1—Equivalent circuit of output tube, and recommended crossover network arrangement for reducing distortion due to inductance of output transformer

November, 1948 — ELECTRONICS

Crossover Network

If placed between the output stage and the low-frequency output transformer, an audio crossover network for woofer-tweeter loudspeakers reduces distortion due to nonlinearity of transformer inductance and makes special transformer designs unnecessary

impedance, ω_1 is the angular velocity of the lowest frequency, and D is the per-unit distortion. (Distortion D is the product of the harmonic component of exciting current times the tube impedance, divided by the fundamental voltage. The exciting current (fundamental) was $I_1 = E/\omega_1 L$. I_3 is taken as $I_1/3$, so $I_3 = E/3\omega_1 L$. $I_3R_P = DE$ so $D = 1/3\omega_1 L$ or $L = 1/3\omega_1 D$.)

Putting in numerical values, $L=2.000/3\times200\times0.005=667$ henrys. This is a difficult value to achieve, doubly so if the leakage inductance is to be held to a minimum dictated by a top limit of transmission of say 15,000 cycles.

If the transformer is required to transmit only the lower part of the total spectrum the leakage inductance limitation is removed and a transformer with realizable ratio of primary-to-leakage inductance can be designed. Therefore, placing the low-pass filter ahead of the transformer relaxes its design requirements relative to maximum primary-to-leakage inductance ratio.

Placing the filter ahead of the transformer also reduces the required primary inductance for a stipulated distortion. First, the filter attenuates in each direction, so that harmonics and other distortion products arising in the transformer are attenuated before getting back to the generator where they can be transmitted to the high channel. Second, the higher frequencies are attenuated in a forward direction so that the distortion products arising in the transformer are of low order.

Thus, conventional transformers with primary inductance values of the order of 100 to 200 henrys can be used, instead of special designs with values like 667 henrys. Further, since the transformer is re-

quired to transmit only up to the crossover frequency, say 500 cycles, the leakage inductance is not a severe design requirement and the transformer may be a relatively low-priced unit.

Appendix

An examination of Eq. 1 and its derivation indicates the desirability of keeping the plate impedance low. Triodes, with or without feedback, and the more efficient beam tubes with voltage feedback, both offer the desirable low impedance. Either can be designed for any desired characteristics. It should be noted, however, that reducing the driver stage impedance to zero would still leave the transformer winding resistance, so a loudspeaker would never look back into zero impedance.

In the numerical example, the figures chosen would apply either to a pair of 2A3 (6B4G) tubes in push-pull without feedback, or to a pair of 6L6 tubes with about 15 db of voltage feedback.

To reduce the plate impedance to zero or near zero values might appear to be highly desirable. However, the characteristics of the driven loudspeakers are such that some source impedance is desirable. Even in highly developed horn loudspeakers, the efficiency and impedance vary, and the source impedance tends to smooth out the resulting response. In the case of direct radiators with the 20 to 1 variations in impedance a constant-voltage source is not the best.

Thus, feedback to reduce output impedance would appear capable of being carried too far. Feedback for distortion reduction can be applied simultaneously as voltage feedback which tends to reduce the tube impedance (make it constant voltage) and current feedback which tends to increase the impedance (make

the source constant current). A happy combination of the two might prove to be the best overall.

Here one is faced with the desirability of an optimum impedance for operation of the loudspeakers, and a minimum impedance from the standpoint of distortion in the transformers. The crossover arrangement discussed here offers the possibility of minimizing transformer distortion while maintaining the tube impedance at optimum levels from the standpoint of loudspeaker operation and distortion.

Either voltage or current feedback reduces distortion in the tube system (and both together reduce distortion to the same extent as would the same amount of total feedback of either type by itself). A combination of both affords any desired impedance, so it appears that the designer is free to design the amplifier for optimum loud-speaker performance, relying on the described crossover to hold the distortion from reasonably good transformers within tolerable levels.

In the numerical example, a low cutoff of 31 cycles was chosen. There are very few loudspeakers that will reproduce a 30-cycle fundamental. If one is dealing with direct radiators of moderate size cutting off around 70 to 90 cycles, the improvements afforded by the present crossover will be slightly noticeable. But if one starts working with organ reproduction or generation where low-C performance is demanded, some very annoying distortions crop up. It is particularly for the users of reproducers capable of 30-cycle perthat this article is formance² written.

REFERENCES

(1) P. W. Klipsch, Crossover Network, ELECTRONICS, Nov. 1945.
(2) P. W. Klisch, Design of Compact Two-Horn Loudspeaker, ELECTRONICS, Feb. 1946.

Light-Flash Generator

Flash repetition rate may be continuously varied between 12 per minute and 150 per second. Flash duration is continuously variable from 400 microseconds to 2 seconds. Either of two light sources may be made to precede the other

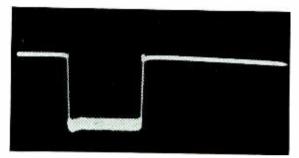


FIG. 1-Waveform of 400-microsecond light flash

By R. G. ROUSH

Electronic Design Engineer, Systems Research The Johns Hopkins University

and FERDINAND HAMBURGER, Jr.

Professor of Electrical Engineering The Johns Hopkins University Baltimore, Maryland

In Many fields of visual research, a convenient method of generating controllable light flashes is desired. For example, studies of flicker can be greatly simplified if a system is available for the production of a repetitive light flash which can be varied in duty cycle without changing its rate of presentation.

The problem of producing such a flash by mechanical means is a difficult one if flexibility of adjustment is required. To overcome many of the problems associated with a system of this nature, an electronic flash system has been developed and is described in detail in this paper.

General Description

The equipment was designed to permit presentation of one or two light-flash sources. These light-flash sources may be presented at repetition rates continuously variable from one flash in five seconds to 150 flashes per second. The duration of each flash is continuously variable from a minimum value of 400 microseconds to a maximum of 90 percent of the period of presentation, or about 2 seconds. Either of the two flash sources may be delayed in time of presentation with respect

to the other from a minimum value of 1 millisecond to a maximum of two seconds, the maximum available delay time being limited at all times to the difference between the period of repetition and the duration of the flash

The light flashes are produced by exciting a facsimile recording light source of the glow-modulator type, such as the Sylvania R1131, with a voltage of rectangular waveform and of the desired duration. The tubes are of the hollow-cathode or crater type which produce a high ionization density when excited. They are designed in such a manner that this discharge is viewed in depth, thus giving a resultant flash of high intensity having spectral characteristics determined mainly by the type of gas employed and the ionizing current. In this application, the tubes are operated so that a considerable portion of the output energy lies in the visible spectrum.

Examination of the flash under dynamic conditions has indicated that there is no apparent shift in spectral characteristics during the flash period. Measurements were made by viewing the flash with a spectrally selective photometer¹ and examining the electrical output of the photometer on the screen of a cathode-ray tube. A typical waveform obtained by this method is shown in Fig. 1. The minimum pulse length of 400 microseconds was purposely chosen to illustrate the rapid build up and decay time of the flash.

Basic Operation

To demonstrate the basic operation of the individual timing circuits a functional block diagram of the equipment is given in Fig. 2. The voltage waveforms appearing at various points in this diagram are represented by Roman numerals. The numbers also appear frequently throughout the paper and refer to the correspondingly numbered waveforms given on the timing chart in Fig. 3.

The repetition-rate multivibrator shown in the functional block diagram provides an adjustable-frequency square wave (waveform I) from which a reference timing-trig-

This work was carried out in the Electrical Engineering Laboratories of The Johns Hopkins University under Task Order No. 1 of Contract N5-ori-166 between Special Devices Center, Office of Naval Research, and The John Hopkins University.

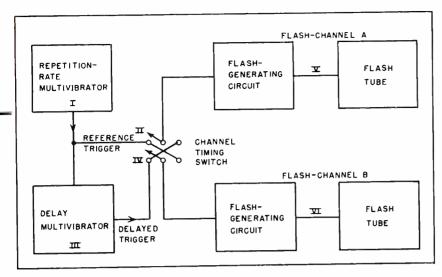


FIG. 2—Functional block diagram of light-flash generator

ger pulse (waveform II) is obtained for the system. This voltage is connected to the upper left terminal of the reversing switch labeled Channel Timing Switch and also is applied to the delay multivibrator as shown. In the latter circuit the reference trigger is delayed to provide a second timing pulse waveform IV similar in every respect to the timing trigger pulse but occurring at a subsequent time, t_d . The delayed trigger is connected to the lower left terminal of the channel timing switch and the output terminals of the switch are connected to the flash-generating circuits in the manner shown in the diagram.

Each of the flash-generator circuits consists of a single-cycle square-wave generator which is cycled by the timing trigger appearing on its input line. The output voltage of each of these circuits is developed across the flash tube in sufficient amplitude to permit the desired light intensity level to be realized. Since the flashes in each channel are initiated by the trigger pulses connected to their respective inputs, it can be seen that when the channel timing switch is in the lefthand position, the flash in channel A (waveform V) is cycled by the reference trigger (waveform II) and thus occurs at t_o . The flash in channel B is initiated by the delayed trigger and therefore occurs at t_d . When the switch is in the righthand position the flashes are reversed in order of presentation

(channel A has waveform VI), thereby providing an extremely useful device for temporal discrimination studies.

Reference And Triggers

The circuits of the reference and delayed-trigger sources are shown schematically in Fig. 4.


The period of the reference trigger is established by a cathodecoupled free-running multivibrator, V_{i} , whose period is determined by the R-C time-constant of its grid cifcuit. Coarse adjustments of repetition rate can be made in five steps by means of the capacitor selector switch S_1 , and fine adjustments by means of the linear potentiometer R_2 . The value of R_1 was so chosen as to limit the ratio of maximum to minimum period on any range setting to a value of six. This value represents the approximate limit of the ratio for continuously adjustable periods without introducing amplitude distortion of the multivibrator output voltage.

The output of V_{1B} (waveform I) is differentiated and negatively clipped by the combined action of C_0 , $R_{\rm s}$, $R_{\rm r}$, and the series-diode clipper $V_{2\lambda}$. Additional clipping action is provided by the inverted diode V_{2B} , so that the absence of any negative voltage at the grid of V_{3A} is assured. The voltage appearing at the cathode of V_{2B} is therefore a positive trigger (waveform II) which serves as a reference timing voltage for the system, The synchronizing

trigger voltage is applied to the FIG. 3-Waveforms at various circuit points

single-cycle delay multivibrator, V_3 . The components of this circuit were selected so that $V_{\rm SB}$ is normally conducting and V_{8A} normally cut off. When the synchronizing trigger arrives at the grid of V_{3A} these conditions are abruptly reversed by the combined action of the feedback paths supplied by R_0 and the selected capacitor in the bank controlled by S_2 . Tube V_{3A} is therefore conducting and V_{3B} cut off, a condition which is maintained until the grid potential of V_{3B} rises above the cutoff level. When this occurs, the conditions are again abruptly reversed, thus returning the circuit to its original state.

During the operating cycle, the current through the common cathode resistor R_{θ} is less than the normal quiescent current, since the tubes V_{3A} and V_{3B} are operated with different circuit components and under different bias conditions. The voltage appearing at the cathode of V_{3} (waveform III) is therefore a negative square wave with leading edge coincident with the reference trigger (t_o) and trailing edge occurring at t_d , the time $t_d - t_o$ being established by the multivibrator cycle duration. In order that this delay time be realized in useful form, the square wave is differentiated and negatively clipped by C_{12} , R_{13} , R_{14} , and V_4 , thereby creating a second positive trigger (waveform IV) delayed with respect to the Variations in reference trigger. the multivibrator cycle duration thereby produce corresponding variations in the time spacing of the two synchronizing triggers. Since this time is determined by the exponential decay of the grid potential

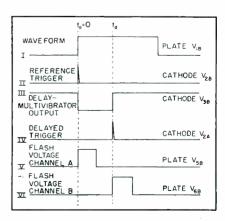

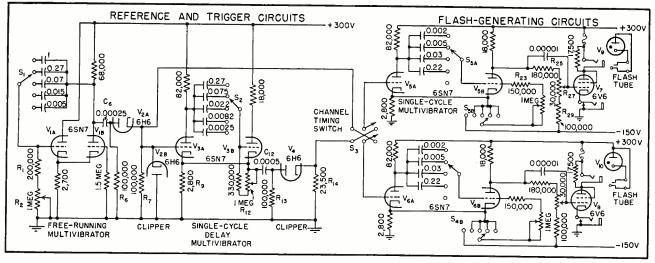


FIG. 4—Schematic of complete light-flash generator, less power supply

of V_{sB} , adjustments of the R-C time constant in this circuit produce direct variations of delay time. These adjustments can be made in five overlapping ranges by means of the capacitor selector switch S_2 and the linear potentiometer R_{12} , the combination providing continuous control of delay time in the available range.

Flash Circuits

The two trigger sources are connected to the two flash-generating circuits, included in Fig. 4, through the double-pole reversing switch S₃. Since both channels operate identically in every respect, the circuit description to follow will be confined to channel I, the channel shown in the upper-right portion of the diagram. The twin triode V_5 , and its associated circuit elements constitute another single-cycle multivibrator whose operation is identical to that of the previously described delay multivibrator V_s . The output of this circuit, however, is obtained from the plate of the normally-conducting tube $V_{\rm sB}$. Cycling of the circuit by the application of a positive trigger of sufficient amplitude will therefore initiate a positive-going rectangular wave at the plate of this tube (waveform V), the duration of the cycle being dependent upon the R-C time-constant in the grid circuit of V_{68} .

The output voltage of $V_{\rm sn}$ is applied to one terminal of a voltage-divider network composed of $R_{\rm zn}$, and $R_{\rm zn}$, the opposite end being returned to the negative 150-volt

supply. The variable tap on R_{27} is connected to the control grid of V_{τ} , a triode-connected beam-power tube whose plate load impedance consists of the glow-modulator flash tube. V_{p} . Continuous excitation of this tube is prevented by adjusting R_{zz} in such a manner that the grid bias on V_{τ} is well beyond that required for plate current cutoff during the quiescent period of V_s . When the latter is cycled, the positive gate voltage appearing at the control grid of V_7 drives this tube into the region of conduction, thereby exciting the flash tube.

Coarse adjustment of flash duration can be made by means of S_{s} and fine adjustments by R_{23} , the combination permitting continuous control of flash durations ranging from a minimum of 400 microseconds to a maximum of approximately 2 seconds. When S_s is in switch-position 5, the gridleak resistor of V_{5B} is returned to the 150volt negative supply, thus placing the flash-duration multivibrator in a continuous-cycle condition permitting adjustment of the flashtube intensity to the desired level. The intensity level obtained by this method will be the value to which the flash tube will be excited under dynamic conditions, since the intensity is a function of tube current only.

Calibration

The timing calibrations were obtained through the use of an audio oscillator and a cathode-ray oscilloscope of the type permitting

beam-intensity modulation. The rectangular waveform to be calibrated is presented on the screen of the oscilloscope as a vertical deflection and the calibrating signal from the audio oscillator is superimposed upon this pattern as an intensity variation of the trace. To prevent drift of the intensity modulation of the trace across the pattern, the repetition frequency of the square wave must be a submultiple of the calibrating sine wave. This condition can be obtained by connecting the calibrating sine wave to the control grid of V_{1B} , thereby synchronizing the repetition-rate multivibrator with the timing signal.


By counting the number of spots present on the deflected portion of the trace, and multiplying this number by the period of the calibrating signal, the delay or duration time can be readily evaluated. The calibration of pulse lengths longer than 70 or 80 milliseconds by the above method becomes virtually impossible since the repetition rate of an 80-millisecond pulse must be less than $1/80 \times 10^{-8}$ or 12.5 pulses per second, at which frequency flicker effects are objectionable. For these and greater pulse durations a highspeed synchronous clock circuit has been successfully used for calibration.

REFERENCES

(1) Ferdinand Hamburger, Jr. and Ellwood J. King, A Recording Photometer and Its Use in Studies of Cathode Ray Screen Displays, Jour. Opt. Soc. Amer., in press.

Screen Displays, Jour. Opt. Soc. Amer., in press.

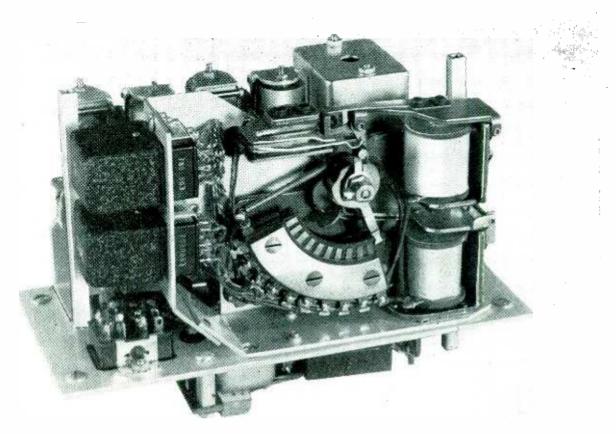(2) R. G. Roush and Ferdinand Hamburger, Jr., Electronic Chronograph for Measurement of Voice Reaction Time. Amer. Jour. Psych., October 1946.



Stepping switch in center is controlled by incoming pulses and prewired connections of plugs at left. Audio peaking amplifier is on other side of partition. The whole unit can be plugged into a mobile receiver

Mobile Selective Calling

Mobile radiotelephone service for connection to wire telephone networks generally requires individual signal for each subscriber. A new low-cost decoder for dial-impulse selective calling can be used in areas now served by two-tone systems. A 2,600-cycle tone generator is added at the central office

tems used by police and similar services generally employ a loudspeaker in the mobile unit to monitor all transmissions. Thus the operator of the vehicle must listen to all the traffic in the system and be on the alert to answer whenever his name, number, or code is called.

While such an operation is satisfactory to some groups there are other miscellaneous users, among the general public, for whom the constant monitoring of the channel is unacceptable. They prefer a bell or other signal only when a call is specifically meant for their mobile unit and, in addition, often want a permanent signal such as a light,

By E. H. B. BARTELINK

Radio Engineer General Telephone Service Corp. New York, N. Y.

to appear when such a call has been received while they are absent from the vehicle. In such cases, a selective calling or signaling system is needed.

One type of service offered by the telephone companies provides connection to the wire network and enables the mobile user to communicate with anyone that he could ordinarily reach from a wire telephone. Selector systems for this general service, using the dual-tone principle, have already been developed and are in use. The new selec-

tive calling system described here was specifically designed to be low in cost yet usable in a general service system. It is, moreover, equally useful in other types of service requiring selective calling.

System Requirements

Two types of general service are presently being provided. One is the highway service, which is designed to cover arterial highways and surrounding territory; the other is the urban service for vehicles chiefly engaged in local operations. For the former service, which generally requires somewhat larger ranges, frequency assignments have been made in the 30 to

40-mc range, while the urban service has been assigned to the 152 to 162-mc band.

In the highway frequencies, it was found necessary to introduce a zoning plan of frequency assignments in order to avoid long-range interference. On the basis of the number of systems expected in each zone and the mobile units expected in each system, the present computations indicate that the number of mobile units, using the same channel or pair of frequencies in each zone, may be in the order of 1,500. To differentiate among all mobile units on the same pair of highway frequencies, a selector must be able to provide a corresponding number of different combinations.

An urban system, operating far removed from other cities, could be operated with a selector system which provides a number of combinations equal to the maximum number of mobile units that can be served by the system. According to present experience, this would require somewhere between 50 and 150 combinations, depending on the traffic conditions in the particular system. Wherever cities are located close together, so that cars frequently travel from the coverage of one mobile system into that of another, a much larger number of combinations is again necessary. Such conditions exist, for example, in the northeastern Atlantic coast region.

To give the subscriber satisfactory service, at least three conditions must be met. A comprehensive regional plan must be worked out by all the telephone companies involved so that the necessary coverage is obtained without causing excessive overlaps. Arrangements must be worked out by the telephone companies so that a customer of one telephone company will receive service no matter whether he travels in the coverage of a system operated by the company to which he is a subscriber or that of another company. Finally, sufficient uniformity in equipment must exist so that a customer can have uninterrupted access to the service as he travels through the service area of different mobile-radio systems. The first two requirements have been met by the cooperative efforts of

the different telephone companies confronted with these problems. Regarding the equipment, the standardization of the radio equipment is such that units made by different manufacturers can, in general, be used interchangeably provided that they are all adjusted to operate on the same channel.

In a local or urban system, far enough removed from other cities to minimize the chance of visits by outside units, any kind of selector system can be used provided it fits in with the general routine of traffic handling and does not require any other special treatment. For highway systems where the through customers already have dual-tone selectors and for urban systems adjacent to others using such selectors, it is still possible to use a different signaling system for the local customers provided the system meets the above requirements and that equipment at the central office can be arranged to signal to customers having either type of selector. Furthermore the additional provisions required at the central office should not result in any major cost differentials.

Fundamentals of Operation

The new selector system uses a single signaling tone in which the dial pulses that actuate the stepping mechanism of a multicontact switch are transmitted as interruptions of the tone. This tone is applied prior to the time that the operator starts dialing and is kept on for a short period after the dial-

ing is completed. The selector returns to the idle or starting position whenever the dial tone is interrupted for any period materially in excess of the dial pulse duration. Thus the selector is self-resetting and does not require any special clearing pulses to reset it to zero. Such clearing signals are needed in systems where noise might activate the selector and leave it set in some intermediate position.

The fundamental circuit of the receiver unit is shown in Fig. 1. In the idle positions, all relays except the release control relay, RC, and the release magnet, RM, are deenergized, and the off-normal contact, ONC, is in the position shown. The pulse relay, P, is operated by the rectified audio-frequency voltages appearing across a circuit tuned to the dialing frequency. If a steady dial tone is applied. P energizes and in turn operates the slow-release relay, SR, which deenergizes the release magnet, RM, prepares the circuit for the stepping magnet, SM, and thus readies the stepping switch for operation. Subsequent interruption of the dial tone will operate the stepping magnet and cause the switch to step under control of the dial pulses.

As soon as the switch arm has left the first contact, the off-normal contact, *ONC*, is operated. This removes one ground from the *RC* relay which, being of the slow-release type, is now held operated by the pulsations of the *P* relay contact. The *SR* relay is likewise held


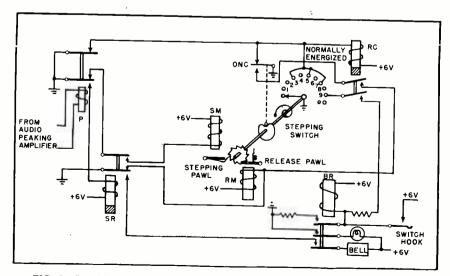


FIG. 1—Simplified schematic diagram of the decoder relay and stepping circuits

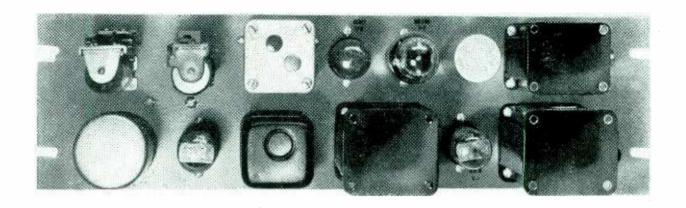

Tone generator and supervisory relays installed at central office

operated during these pulsations. At the end of a pulse series, the RC relay will release and, by operating the release magnet, return the selector to zero unless this pulse series left the switch on one of the specially selected contacts which are connected to the RC relay. If it comes to rest on one of these special contacts, the arm of the switch will provide ground for the RC relay which then remains energized. The release magnet is not energized: thus the switch will remain in this position and be ready to receive another series of pulses. The selection of these special switch contacts therefore determines the series of digits which must be dialed if the switch is to advance without setbacks.

The energizing circuit for the bell-ringing relay, BR, is connected to one of the latter contacts, for instance contacts 7, 8, or 9, on the switch; and the switch contacts beyond this point are left unconnected. If at the end of the last pulse series the switch comes to rest on one of these contacts, RC will release, as they are not connected, and thus cannot complete the circuit for RC. If the switch comes to rest on the contact to which BR is connected, RC will, when it releases, energize BR, which in turn will close a holding circuit through its own contacts. A very short time after this, RM pulls up and returns the switch to zero. Another contact on BR closes the circuit to the bell through a contact on SR. Thus the bell will ring until the SR relay is released by the interruption of the dial tone, which occurs shortly after the completion of the dialing operation. Another contact on the BR relay energizes a signal lamp, which remains lighted until the subscriber removes his handset. This operates the hook-switch, and releases BR by shorting its winding.

In the actual selector, the BRrelay is replaced by a decade-switching relay DS which is energized in the same way as the BR relay and which holds itself over a contact on the SR relay. This relay transfers the holding circuits which were connected between the RC relay and the special switch contacts to a second set of contacts on the switch. In the meantime, the switch has returned to zero and has energized RC. It is thus ready for a new series of impulses; and, if the proper code is again dialed, it will then operate the BR relay which is connected in the second set of contacts in the same manner as described before. It is this utilization of two sets or banks of contacts on the stepping switch which provides the much larger number of combinations.

In addition to providing a large number of different possible combinations (about 1,500), the new selector also permits group calling. If both the decade-switching relay and the BR relays are connected to contact 9, then the dialing of 99 will call all cars. If in some cars the DS relay is connected to contact 9 and in others to 8, and if the same holds for the BR relay, then the subscribers may be divided into four groups having group calling codes of 99, 98, 89, and 88 respec-


tively. Thus, for instance, the police department, the fire department, doctors, and the general public could be given group calls. If contact 7 is also similarly used, the number of possible group calls increases to seven.

Coding combinations are easily arranged by the insertion of two properly wired multicontact plugs into the mobile unit, one for each bank of contacts. This feature facilitates maintenance whenever all or part of the mobile equipment is removed from the vehicle. The code plugs are simply reinserted in a spare unit to give it the correct dial-response characteristics for the subscriber.

The decoder was built by Hammarlund Manufacturing Co., and was designed to be physically replaceable for the Fleet Control unit (described by J. K. Kulansky in ELECTRONICS, June 1946) for which provision has been made in several commercial models of mobile radio receiver chassis.

System Tie-In

Besides making provision for simple modification of existing Western Electric control units, without disturbing the original function, equipment has also been designed for central office use. A tone generator for 2,600 cycles and necessary relays for keying it in and out of service permit central-office signaling with either the new system or the existing two-tone system. A coded number assigned to the subscriber informs the operator which system she must use to complete the call.

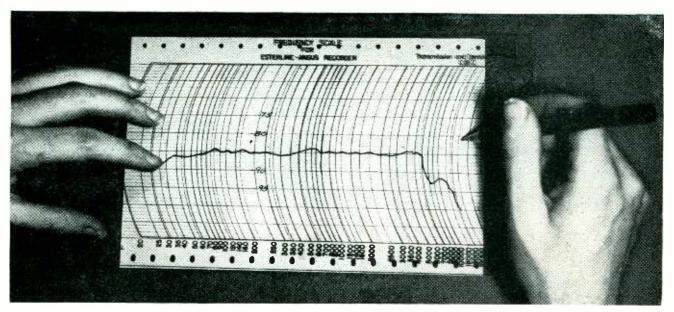

Transparent frequency scale is held over response curve produced on chart paper of recorder

Microphone Calibrator

By D. H. BASTIN

Transmission & Development Department Canadian Broadcasting Corporation Montreal, Canada

THE FIELD CALIBRATION of a microphone requires that the microphone be placed in a plane sound field of known intensity. This type of calibration differs from a pressure calibration in that the effect of diffraction around the microphone is charged up as part of the response of the microphone. It is therefore the most useful type of calibration for microphones used in broadcasting.

Inexpensive Dead Room

Obtaining the required sound field indoors is a matter of some difficulty because reflections build up standing waves to give a nonuniform sound field. The usual method of obtaining the sound field by the use of free-field or anechoic chambers was felt to be too expensive for the present project, so two less expensive devices are used to obtain the required field, one operating from 30 to 1,000 cycles and the

other unit operating from 1,000 to 15,000 cycles.

The two measuring techniques involved, outlined below, were developed for use on all microphones used in CBC studios across Canada. In both, the microphone being tested is compared against a standard microphone by a two-channel logarithmic voltmeter that automatically plots the response in decibels against frequency. The

system can also be used for recording loudspeaker response and polar diagrams.

Low-Frequency Chamber

The frequency response from 30 to 1,000 cycles is measured by placing the microphone three feet from the end of a wooden tube 30 feet long and 11 by 11 inches in cross section. A drawing of the tube is shown in Fig. 1. At the end of the


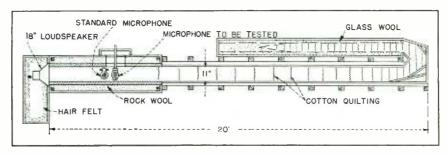


FIG. 1—Cross-section of 11-inch-square hollow wood tube used to absorb sound energy below 1,000 cycles from loudspeaker and thereby prevent reflection back to microphone being tested

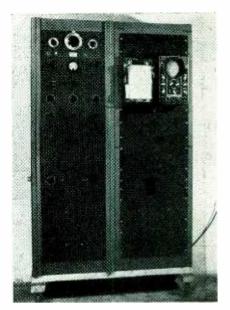

Microphone calibration rack, designed to plug into a-c wall outlet

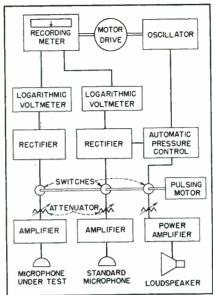


FIG. 2—Block diagram of microphone calibration rack used in CBC laboratories

Simple, rapid and reasonably accurate method of measuring sensitivity, frequency response and polar response without a costly free-field anechoic chamber. Below 1,000 cycles a long wood tube absorbs unwanted sound. Higher frequencies are pulsed and recording is done before reflected sound returns to microphone

tube near the microphone is a loudspeaker. That part of the tube on the far side of the microphone contains curtains of cotton quilting hung across the tube in increasing amounts to form an acoustic resistance to absorb the energy of the sound passing from the loudspeaker. The treatment is adjusted until the acoustic impedance looking into the tube is approximately that of open air, or 40 acoustic ohms per square centimeter.

With the source of sound located symmetrically on the axis of such a tube no standing waves exist across the tube for frequencies below 1,000 cycles, and the acoustic treatment effectively absorbs reflections from the end of the tube; the result is a plane wave flowing past the microphone. The tube can be used only below 1,000 cycles, because above this frequency standing waves exist across the tube.

Mounted beside the microphone

being tested is a small standard microphone, having flat response over the 30 to 1,000-cycle range, and of known sensitivity. The outputs of the two microphones are fed to the measuring rack and as the frequency of the loudspeaker signal is slowly changed the response curve is automatically plotted.

High-Frequency Pulse System

Over the range above 1,000 cycles a pulsing system is used to obtain effective free-field conditions. The microphone to be tested and a small loudspeaker are set up about three feet apart in a studio or small room. Midway between the microphone and loudspeaker is placed a small standard microphone.

A short pulse of sound at the desired frequency is transmitted from the loudspeaker, and the resulting output from the microphone is measured before enough time has elapsed for reflected sound from the

nearest wall to arrive back at the microphone. The pulse is repeated at intervals long enough to allow reflections to die out between pulses. During the pulsing the frequency of the oscillator driving the loud-speaker is slowly changed and the response curve is automatically plotted by a logarithmic recording voltmeter. By rotating the microphone undergoing test a polar diagram of the response at any frequency can be plotted.

Pulse Length

The length of the pulse that is used is 10 milliseconds and the pulse is repeated 10 times every second. With a pulse of 10 milliseconds length and a sound velocity of 1,100 feet per second the sound path before the first reflection can reach the microphone is 11 feet. This means that the microphone can be half this distance or within 5½ feet of the nearest wall, hence a comparatively small room is suitable for the measurement.

At 1,000 cycles a pulse of 10 milliseconds consists of only 10 cycles, of which the first and last few eycles are obscured by transients, so that 1,000 cycles is about the low-frequency limit of this pulsing system. In a larger room a longer pulse could be used, and consequently a lower frequency could be reached. On the microphone channels the beginning and end of the pulses are clipped to remove transients from the pulses before comparing the two signals.

No special treatment is required on the walls of the room used for this part of the test, for the repetition rate of 10 per second allows sufficient time between pulses for reflected sound to drop to a negligible value before the next pulse is transmitted.

The sound source used for the high-frequency test is a small dynamic loudspeaker that was found to have adequate output up to 15 kc. As will be noted later, the response of the source is not critical in this method.

Standard Microphone

The standard microphone is a small type M101 crystal unit § by 15/16 inch in size, manufactured by Massa Laboratories.¹ The pre-

amplifier housing supports the standard microphone in the position for minimum diffraction effect, with the end of the crystal unit parallel to the sound axis. In this position the diffraction effect is negligible below 10 kc, and the response can be considered flat. A reciprocity calibration on this unit gave a value of sensitivity in good agreement with the value stated by the manufacturer.

The preamplifier housing contains a 9002 tube connected as a cathode follower, acting as an impedance changer between the high impedance of the crystal and the low-impedance output. Terminals are provided on the preamplifier for injecting a signal in series with the crystal for making overall electrical calibration of the associated equipment.

Tests have shown that at the testing distances used, 15 inches to the standard microphone and 30 inches to the other microphone, neither microphone has appreciable influence on the sound intensity at the other, and for the period of the pulse each microphone is in a progressive sound wave, the pressure at the nearer microphone being twice that at the other. In the low-frequency tube an inexpensive crystal microphone is used as the standard, and is checked at intervals against the Massa standard.

The absolute accuracy of the measurements depends upon the standard microphone, but the type of crystal microphone used appears to be stable, and a reciprocity calibration can be made upon it at any time if required.

Rack Equipment

Both parts of the calibration method require the comparison of the outputs of the two microphones. This comparison is carried out in the rack of equipment shown in the block diagram in Fig. 2.

The rack contains amplifiers for the two microphone channels, a logarithmic voltmeter which compares the outputs of the two microphones, a recording meter, an audio oscillator with a motor drive on the frequency dial, a power amplifier to drive a loudspeaker, an automatic pressure control, pulsing switches and a cathode-ray oscil-

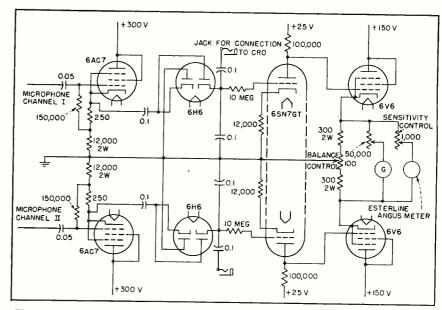


FIG. 3—Circuit of voltmeter providing logarithmic amplification over range of 46 db as required for plotting response curves in db

loscope for waveform examination.

The two microphone channels are similar, each consisting of an amplifier, attenuator, rectifier and logarithmic stage. The attenuator controls are marked directly in decibels on the front panel. Each amplifier is followed by a cathode follower, using a 6AC7 as shown in Fig. 3 to provide a low-impedance source and so avoid peak clipping by the rectifier action. The 6H6 rectifiers are connected as voltage doublers. The maximum undistorted signal available from the cathode follower is about 100 volts, hence the peak d-c output from the rectifier is about 200 volts, or 46 db above the minimum usable output of 1 volt. Below 1 volt the initial current from the diodes becomes important, introducing nonlinearity.

Since only the amplitudes of the pulses are compared, the rectifier circuit has a short charge time constant, in order that the amplitude of the signal can rise to full value during the first millisecond of pulse. The discharge time constant is long, however, in order that the rectified level does not fall appreciably during the tenth second between pulses.

Logarithmic Action

Logarithmic action is obtained by applying the positive voltage from the rectifier through a 10-megohm resistor to the grid of a 6SN7GT triode section operating with 25

volts plate supply. Because the emission velocities of the electrons given off by a hot cathode follow a Maxwellian distribution, the grid current which flows bears a logarithmic relation to the applied voltage. This logarithmic change in grid current produces a corresponding change in grid-to-cathode voltage, which is amplified and appears as a change in plate potential. The circuit as developed by Walter Ives2 is accurately logarithmic over about 46 db, the limitations lying not in the log tube but in the rectifier and amplifier ahead of the log tube.

The direct-current output of the two logarithmic stages is further amplified by direct-coupled 6V6 tubes connected as cathode followers and fed to the recording milliammeter, which is a standard 5-ma Esterline-Angus meter. potentiometer at the midpoint of the cathode resistors of the 6V6 tubes enables the two channels to be balanced so that equal signals on the two channels give center-scale deflection of the meter. This meter responds to the difference between the output of the two channels, and so is equivalent to the difference of the logarithms of the two microphone signals, and hence to the ratio of the two microphone responses. Since the response of the standard microphone is known to be flat, the result is the response curve of the unknown microphone plotted in db

against frequency on the recording meter chart.

Recording Method

A sensitivity control in series with the meter can be set so that one division of the chart paper represents one db. The absolute sensitivity represented by the center line on the chart is found by subtracting the difference in gain of the two microphone channels, easily read off the two panel attenuators, from the sensitivity of the standard mi-The two-channel concrophone. struction tends to balance out effects of line voltage variation. In addition, electronic regulation is used on the plate supply for the logarithmic stage and directcoupled amplifier. The stability of the gear is sufficient so that measurements remain accurate to within one db over long periods.

A small motor synchronized with the paper drive on the recording meter slowly changes the frequency of the oscillator driving the loudspeaker. The speed at which the oscillator frequency can be varied is dependent on the time constant of the rectifiers, which is relatively long. Even with this restriction, however, it only takes three minutes to traverse the frequency range from 30 to 15,000 cycles.

The curved coordinates produced by the meter are not as convenient to use as rectangular coordinates, but when a transparent scale marked in frequency is laid over the chart the sensitivity at any frequency can readily be read off.

For the low-frequency test in the tube no pulsing is used. The oscillator frequency is simply varied slowly as the response is plotted. For the high-frequency test the loudspeaker signal must be pulsed. This is done by a motor-driven commutator-type switch which shorts the oscillator signal except for the period of the pulse. Other commutators mounted on the same shaft short the microphone channels for a slightly longer period, clipping the transients from the beginning and end of the loudspeaker pulse. These commutators have to be phased on the shaft to allow for the time interval taken by the sound in travelling from the loudspeaker to each microphone.

It is difficult to find a loudspeaker or any sound source that has an output independent of frequency, but since this method compares the outputs of two microphones it does not greatly matter what variations occur in the sound output of the loudspeaker. However, to maintain approximately constant sound level at the microphone and to insure that the 46-db range of the voltmeter is not exceeded, a portion of the output of the standard flat-response microphone is fed to the automatic pressure control, a variable-gain amplifier in the loudspeaker circuit. Here it controls the signal fed to the loudspeaker, increasing the output when the loudspeaker response drops, and decreasing the output when it tends to increase.

The cathode-ray oscilloscope mounted in the rack is useful for visual checks on wave form. It quickly shows up, for example, the characteristic distortion produced in a velocity microphone when the ribbon strikes a pole piece during part of a cycle. The picture of the pulse received by a microphone will show up excessive distortion if present, but unfortunately the pulsing system is not easily adapted for distortion checks, although very satisfactory for response measurements. When checking loudspeakers the shape of the pulse is very useful for giving a qualitative measure of the transient response.

Polar Response Curves

For normal tests the microphone is terminated at the input of the rack in a resistive load of 500 ohms. corresponding to the input impedance of standard speech equipment. The response curve then includes the loading effect of the termination on the internal impedance of the microphone, an effect which in most microphones reduces the sensitivity at the higher frequencies. If desired, other terminations may be selected by a panel switch. The stand carrying the microphone under test can be rotated by a small motor for the automatic plotting of polar response curves.

Besides measuring the response of microphones, the equipment using the pulsing system can be used

to measure the response and polar distribution of loudspeakers above 1,000 cycles. For this test the standard microphone is placed in front of the loudspeaker to be tested, and a portion of the voltage applied to the voice coil is fed to one of the microphone channels in the rack. The curve plotted is the acoustic output of the loudspeaker for constant voltage on the voice coil, corresponding to the response that would be obtained if the loudspeaker were fed from a source having zero internal impedance. The response curve for other source impedances can be calculated from impedance measurements, quickly plotted by placing the desired impedance in series with the voice coil after the point at which the comparison voltage is picked off.

Conclusion

The equipment described has been in routine use for almost a Since the calibration proyear. cedure is rapid and almost automatic the effects of adjustments on the microphones can be quickly seen and the best adjustment readily

The equipment has also been used to check new models of microphones, to measure the response and directional pattern of monitor loudspeakers, and for miscellaneous measurements, such as finding the transmission loss of loudspeaker grille cloth. If in the future a freefield room should become available the equipment can be used as it stands, simply by not using the pulsing switches. The equipment can also be readily adapted for more general laboratory purposes,. such as measuring and plotting the response of filters or pickups.

Editor's Note—This paper was completed shortly before the death of the author, and was forwarded to Electronics by William G. Richardson, Transmission and Development Engineer with Canadian Broadcasting Corporation in Montreal.


REFERENCES

(1) Frank Massa, Working Standard for Sound Pressure Measurements, Journal of the Acoustical Society of America, vol 17, p 29, 1945.
(2) Walter Ives, A Logarithmic Indicating Instrument for the Measurement of Itadio, Noise Voltages, Master's Thesis at McGill University, Sept. 1946.

By DAVID BAKER

Architect
Electronics Division
Bureau of Ships
U. S. Navy
Washington, D. C.

Design of a

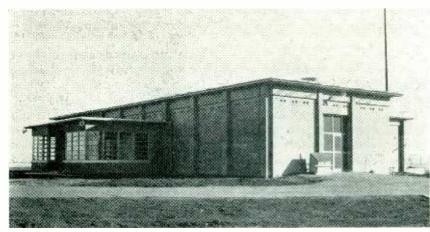

Exterior of Dixon, California station. Holes under cornice are for feeders

Naval Communication

New unit planned for pleasing appearance, operation by minimum of personnel, and capable of rational expansion stands at hub of rhombic array system. Deterioration of reinforced concrete structure is inhibited by novel method of bonding the rods

o SET the best possible example in its postwar construction, the Office of the Assistant Chief of the Bureau of Ships for Electronics, in cooperation with the Bureau of Yards and Docks, has attempted to evolve a basic layout for the United States Naval Radio Transmitting Station at Dixon, California, which will function with a minimum number of personnel, provide low maintenance cost, and solve all probable expansions in the future.

The building expresses a definite architectural character rather than a box-like interpretation, by locating the columns which support the roof loads on the outside of the exterior wall, on centers of about 13 by 40 feet. This arrangement provides for a clear wall surface on the interior of the building and allows for ease of cleaning and lowered maintenance cost. It provides unobstructed maximum working area around the transmitters, and makes possible the running of transmission lines without any obstructions whatsoever within the transmitting room.

In order to obtain a flexible

arrangement for routing incoming transmission lines to the various transmitters, seventy-five pairs of entering insulators are located beneath the protecting cornice of the building. Thus, a line can be pulled tight and held fast on the transmission line anchor, then looped under the cornice and into the feed-through insulator.

Internal Wiring


Cableways are used for cable, conduit, bus bars, piping, and the like, in lieu of an alternate design which would have necessitated that the transmission room be on a second floor, with access to cables arranged in continuous hangers from the ceiling below. Low cost in installing cable is made possible by the ease with which it can be rolled off reels over the main cableways without moving any equipment to do so. The equipment is installed directly over an adjacent system of small feeder trenches.

The floor material finish is terrazzo, ground smooth and divided into squares. The brass strips ordinarily used for dividing terrazzo could prove electrically dangerous to the personnel in the transmitter room, so plastic strips are used instead. Contrasted with a painted concrete surface, battleship linoleum, or asphalt tile, terrazzo fully meets the need of a good wearing surface capable of resisting heavy loads, and is easily maintained and kept clean.

Trucks for carrying equipment for the initial installation or any emergency find easy access through large aluminum sliding end doors. An overhead rail for supporting a hoist is utilized over the end bays of the transmitter room. Thus, equipment is lifted from a truck by means of the hoist to a hand-steered electric-powered transporter.

Air Conditioning

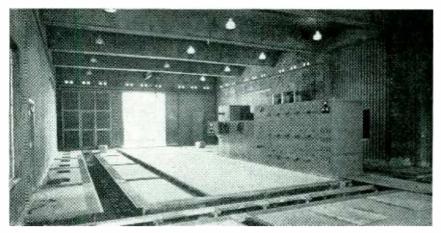This windowless building, save for the administrative portion and the lavatory, is ideal for air conditioning. In addition, it keeps the building insect-proof, a vital consideration, because bugs have a tendency to work their way into transmitter equipment. The out-



Interior showing main switchgear, main and branch cable runways with covers removed


Station

side wall acts as a blast-resisting surface and the inside face provides a good light-reflecting surface.

In the normal course of operation, sufficient heat is generated by the transmitters to heat the building. This warm air is therefore recirculated and utilized for heating, being tempered by cool fresh air. A cooling system for warm weather utilizes the same duct system. The air in the ducts is maintained at a constant 70 to 75 degrees in the summer and winter. In the event of a transmitter shutdown, a boiler is provided as an auxiliary source of heat. Controls provide for automatic operation.

Designed for construction when future commitments so require is a whf and shf tower which will be located over the loading platform at the rear. The cantilever floor of the tower provides a 360-degree area for spacing line-of-sight link antennas of the parabolic-reflector type.

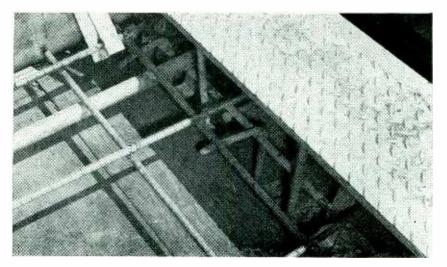Antenna switching will be accomplished by a system of hand-wheel switches that may later be remote controlled. The completed unit will be suspended from cross members framed into sidewall angles or channels in lieu of suspending the units from the ceiling or concrete girders.



Detail of brazed bonds between reinforcing rods, structural members and conduit

The antenna arrangement consists of a number of rhombic transmitting antennas erected circularly from the transmitter building. The antennas are oriented in the specific direction in which the maximum signal is desired. The transmission lines run directly from the antenna to the antenna switching system. so that any transmitter can be connected to any transmission line. The transmission lines are 600-ohm open-wire type. The transmissionline anchors form an integral part of the building cornice design and, together with the antenna feedthrough insulator, give the radio transmitting station its definite character.

Some previously erected reinforced concrete transmitting buildings have suffered partial disintegration owing to expansion of reinforcing rods at a rate faster than that of the concrete surrounding them. This heating was caused by absorption of stray radio-frequency energy. Appreciable energy can be picked up by rods that are resonant at full, half, or quarter wavelengths. Negligible energy is picked up at an eighth wave or less.

Grounding

Since the shortest wave at which appreciable power is to be radiated at the station is 12 meters, only ungrounded rods above 5 feet in length needed special treatment. Accordingly, all steel reinforcing rods are rigidly and continuously bonded to ground by arc welding or brazing. In addition, bonding wires are provided to ground as a precaution against breakage of the rod junctions during the vibrating of the concrete in the molds. Metal doors, window frames, and the like are bonded to the reinforcing steel. Conduit is tied in at least every 20 feet. All mechanical equipment is grounded separately with No. 6 or larger copper wire. The grounding system in the cableways consists of a network of $\frac{1}{8} \times 2$ -inch copper bars. Ground rods are $\S \times 10$ -foot copper-covered steel with No. 2/0 stranded copper cable for connection to the reinforcing steel. This system is then tied in with the external underground network surrounding the station, and used with the antenna systems.

DEVELOPMENT of new techniques for improving the response of servomechanisms has made it possible to apply them to an ever increasing number of uses. These techniques are based upon: (1) improved methods of analysis which show the factors that limit servomechanism response, and (2) the design, or redesign, of components which improve the response.

This article describes a new and simple method for designing stabilization circuits which may be used to improve servomechanism response, and offers a new approach to the design of stabilization circuits in general. The design of these stabilization circuits is based upon the principle that a circuit. having a transfer function which is the inverse of the transfer function of the servomechanism, can be used as a stabilization network, and that this circuit can be approximated by a feedback amplifier having in its feedback path a network with a transfer function proportional to that of the servomechanism.


Consequently the first step in obtaining such a stabilization circuit is to design a circuit having a transfer function proportional to the transfer function of the unimproved servomechanism. This latter circuit will be referred to as the equivalent servomechanism circuit or the equivalent circuit.

Obtaining Equivalent Circuit

The first step in designing the equivalent circuit is to set up the general form of the equivalent network. The second step is then to determine the parameters of this network. These two steps are illustrated by the examples of Fig. 1.

In Fig. 1A is shown the schematic of a simple servomechanism, using a motor-generator set as a power control component of the servomechanism. Figure 1B is the approximate electromechanical equivalent of Fig. 1A. Transfer functions of the system are expressed by the equations. This approximation is justifiable for the operating range of interest because, in general, the armature circuit time constant is short compared to the rotor time constant.

Figure 1C shows the general form of an electrical network hav-

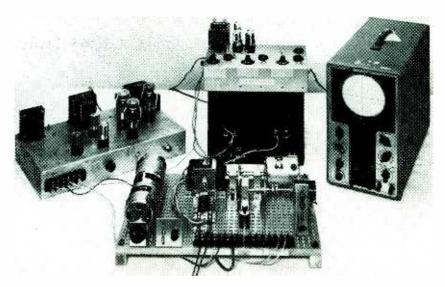

Laboratory equipment used in determining feedback constants includes the uncompensated servo (foreground), its amplifier (left), the adjustable feedback circuit whose parameters are to be found (background), and an oscilloscope

Stabilizing Servomechanisms

By this laboratory technique, constants of feedback stabilization circuits for servomechanisms can be quickly determined without resorting to mathematical computations. thus making it feasible to design and adjust servos for heretofore impracticable applications

By DONALD McDONALD

Head of Controls Group Acronautical Research Center, University of Michigan Willow Run Airport, Ypsilanti, Mich.

ing a transfer function of the same type as the velocity transfer function of the servomechanism. Comparison of the analytical expressions for the transfer function of the equivalent circuit of Fig. 1C, and for the servomechanism, demonstrates the equivalence of the network. The approximation in Fig. 1B was made so that the circuit of Fig. 1C could be composed only of R-C networks, thus simplifying the

adjustment of the circuit of Fig. 1D.

Figure 1D is a schematic of the setup used in determining the values of the parameters of the equivalent circuit. This setup consists of the unimproved open-cycle servo-mechanism, the equivalent circuit, a variable-frequency sinusoidal-voltage source, a d-c tachometer, and an oscilloscope having d-c amplifiers to drive its deflection plates.

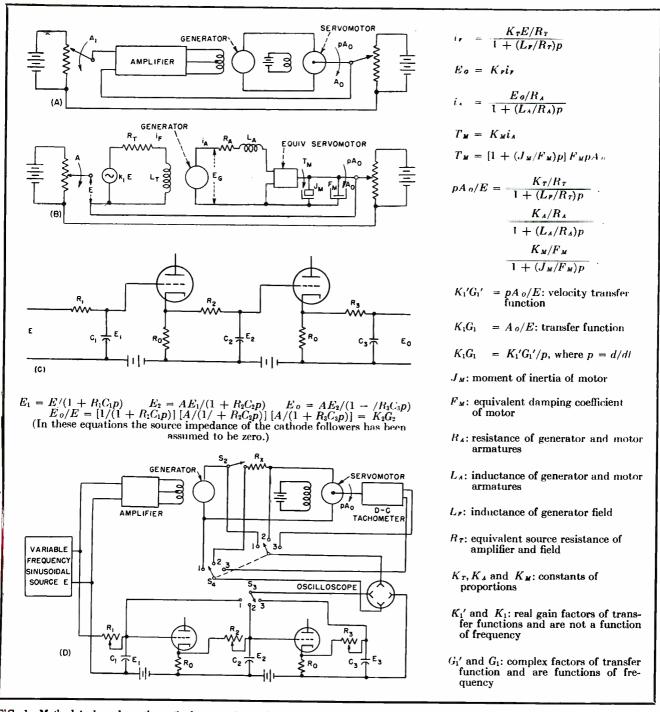


FIG. 1—Method is based on theoretical comparison of servo (A) and (B) with feedback circuit (C). By adjusting the responses of the two systems to be the same (D) proper compensation is obtained

(This setup, in a simplified form, was first developed by the author in 1945 while a member of the MIT Servomechanisms Laboratory.)

With switch S_2 open, the selector switches S_3 and S_4 in position 1, the voltage E_1 of the equivalent circuit and the open-circuit output-voltage E_c of the generator are placed across the deflection plates of the oscilloscope. By adjusting resistor $R_{\rm h}$, it is possible to reduce the elliptical figure on the oscilloscope screen to a straight line. Then the first factors of the velocity transfer functions of the actual servomechanism and of the equivalent circuit are the same.

In essence, when the ellipse becomes a straight line, the phase shift of the first stage of the equivalent circuit has been made equal to the phase shift of the first stage of the actual servomechanism. Therefore, the first factors of the velocity transfer functions of the actual servomechanism and of the equivalent circuit are the same because the servomechanism contains only minimum phase networks.

The frequency of the variable-frequency sinusoidal-voltage source should be varied over a large frequency range to insure that the first factors of the velocity transfer

functions of the actual servomechanism and of the equivalent circuit are the same for all frequencies. Nonlinearities in the servomechanism may make it impossible to obtain one value of R_1 which reduces the elliptical figure to a straight line for all frequencies. If this occurs, then that value of R_1 which minimizes the width of the ellipse over the frequency range of interest should be chosen.

With switch S_2 closed, selector switches S_3 and S_4 in position 2, and with the rotor of the servo motor locked, the voltage E_2 of the equivalent circuit and a voltage proportional to the current i_A of Fig. 1B are placed across the deflection plates of the oscilloscope. By adjusting resistor R_2 it is possible to reduce the elliptical figure to a straight line, whereupon the second factors of the velocity transfer functions of the actual servomechanism and of the equivalent circuit are the same.

In a similar fashion, with switch S_2 closed and selector switches S_3 and S_4 in position 3, the voltage E_3 of the equivalent circuit and a voltage proportional to pA_0 of the servo

motor are placed across the deflection plates of the oscilloscope. By proper adjustment of the resistor $R_{\rm s}$ it is again possible to minimize the width of the ellipse and make the third factors of the velocity transfer functions of the actual servomechanism and of the equivalent circuit the same.

Upon conclusion of these three steps, the transfer function of the equivalent circuit is proportional to the velocity transfer function of the unimproved servomechanism. As mentioned before, nonlinearities in the servomechanism may make it necessary to choose values of R_1 , R_2 , and R_3 which tend to minimize the width of the ellipse over the frequency range of interest.

From simple network considerations of the equivalent circuit, it is possible to determine what factors in the unimproved servomechanism limit its response. If these factors cannot be removed by redesign, then a stabilization network must be used.

Stabilization Network

The schematic diagram of Fig. 2A shows how the equivalent cir-

cuit can be incorporated into a feedback amplifier and thus create a stabilization network. The resulting feedback amplifier will be referred to as the stabilization feedback amplifier.

In Fig. 2A the unimproved opencycle servomechanism, represented by the transfer function K_1G_1 of Fig. 1, is cascaded with the stabilization feedback amplifier having a transfer function K_1G_2 . The stabilization feedback amplifier has a constant gain amplifier K_3 in its forward branch, and the equivalent circuit of Fig. 1C in its feedback.

The expressions of Fig. 2A demonstrate that if K_3 is large enough, K_4G_4 approaches $1/K_2G_2$. It is further shown that the overall transfer function K_5G_5 reduces to 1/Bp and A_0/A_1 to 1/(1 + Bp).

Thus by combining the equivalent circuit of the velocity transfer function of a servomechanism with an amplifier, it is possible to obtain a stabilization network which tends to reduce both the transfer function of the compensated servomechanism to 1/Bp, and the output-to-input ratio to 1/(1 + Bp).

If the output-to-input ratio

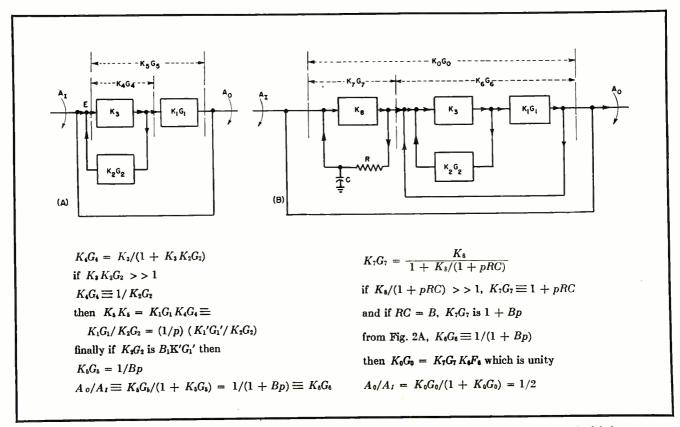


FIG. 2—When necessary, additional feedback loops can be added by the basic technique. The experimental method helps to assure that the circuit parameters of the multiloop system will not produce oscillation

 $A_{\circ}/A_{\scriptscriptstyle f}$ of the compensated servomechanism of Fig. 2A is considered to be a transfer function $K_{\circ}G_{\circ}$, it is possible to design an equivalent network for this transfer function. This equivalent network may be obtained by comparing $K_{\circ}G_{\circ}$ to a single R-C stage in a manner similar to that demonstrated in Fig. 1D.

This single stage equivalent R-C network can be used as the feedback branch of a stabilization feedback amplifier and the resulting feedback amplifier cascaded with K_6G_6 , as shown in Fig. 2B. If this is done, the expressions of Fig. 2B show that K_7G_7 , the transfer function of this stabilization feedback amplifier, approaches 1+Bp, and the overall transfer function K_0G_0 of the twice-compensated servomechanism approaches unity. Therefore, in the limit, A_{\bullet} becomes directly proportional to A_i . Although not shown schematically in Fig. 2, the gain of the system can be increased with the application of the principle outlined above.

In the examples of Fig. 2, it was assumed that the transfer function $K_{\bullet}G_{\bullet}$ approached 1/(1+Bp) and that, therefore, the R-C product of the equivalent circuit of $K_{\bullet}G_{\bullet}$ should equal B. In general, it may not be possible to reduce $K_{\bullet}G_{\bullet}$ to exactly 1/Bp, and therefore $K_{\bullet}G_{\bullet}$ will be slightly more complex than 1/(1+Bp). Consequently, when comparing the equivalent R-C network to $K_{\bullet}G_{\bullet}$, a value of R should be chosen which tends to minimize the width of the ellipse over the frequency range of interest.

Figure 2 shows that it is possible to enhance the stability of a servomechanism by first cascading the open-cycle servomechanism with a stabilization feedback amplifier containing the equivalent circuit of its transfer function, and then by closing the servo feedback loop around these two cascaded components. This procedure may be repeated successively until the desired improvement in the response of the servomechanism has been achieved.

Practical Considerations

In any servomechanism it may not be necessary to compensate for every time delay or its equivalent. Consequently, the equivalent circuit used in the stabilization feedback amplifier need not always contain all of the terms of the complete velocity transfer function. In fact, it may be more practical not only to reduce the number of terms in the equivalent transfer function, but also to approximate the remaining ones.

Following this philosophy, an approximate equivalent circuit can be designed which is composed of only one or two R-C networks or an RLC network. With the setup of Fig. 1D these R-C or RLC networks can be made equivalent for only those frequencies where the maximum phase shift and resonance in the servomechanism response has been observed. Then an approximate stabilization feedback amplifier can be constructed, and the procedure of Fig. 2A gollowed. The remaining uncompensated factors which limit the response of the servomechanism can either be neglected, or removed, by another approximate equivalent circuit and stabilization feedback amplifier, as was done in Fig. 2B.

The number of cathode followers used in the equivalent circuit may be reduced if the impedance of one R-C network is several times greater than the impedance of the preceding network, thus making it unnecessary to isolate these two networks.

In some cases the inertia of the d-c tachometer of Fig. 1D, might be comparable to the inertia of the servomotor which would change the effective characteristics of the servomotor. If this condition arises, the d-c tachometer should be coupled to the motor through a gear reduction. This gearing down usually can be accomplished by coupling the d-c tachometer into the output gear train at some convenient gear mesh.

It is a worthwhile precaution, when combining the equivalent circuit with an amplifier, to form a stabilization feedback amplifier to use no more than two time constants, or their equivalent, in one feedback branch. Otherwise the possibility exists that the stabilization feedback amplifier may oscillate itself. If there are more than two time constants, or their equivalent, in an equivalent circuit, then

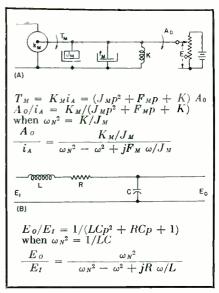


FIG. 3—Spring loaded servos can be compensated by an additional step in the method

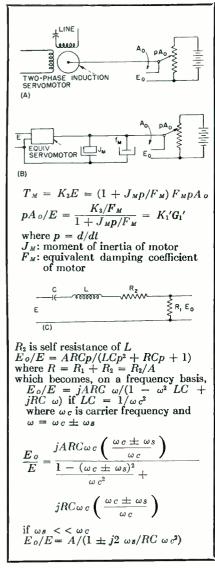


FIG. 4—Alternating-current servomechanisms can be handled similarly to d-c ones, but see Fig. 5

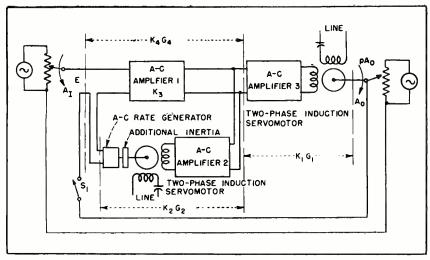


FIG. 5—Stabilizing a-c servos can be simplified if a motor-generator set is used in the feedback path instead of a passive network

several stabilization feedback amplifiers should be used.

Good results can be obtained from a stabilization feedback amplifier with a value of K_s , in Fig. 2A, of only 7 to 10. The overall gain K_* of the stabilization feedback amplifier can be made any value desired by proper choice of the value of K_s of the equivalent circuit. It is worth noting that the amplifier K_s does not have to be an additional amplifier, but may be a stage of K_s .

Case of Spring Loading

In many applications the output motion of the servomotor is restrained by a spring, as in the case of a torque servomotor actuating the pilot valve of a hydraulic system. Figure 3A shows the electromechanical circuit of a servomotor restrained by a spring of stiffness K, and Fig. 3B shows its equivalent circuit. In this example the servomechanism amplifier stages are not shown, and the servomotor is assumed to operate on d-c.

The output voltage E_o of the equivalent circuit may be made proportional to the output voltage E_o of the physical system in a manner similar to that demonstrated in Fig. 1D. In this case it is not possible to subdivide the equivalent circuit or the electromechanical circuit so that only one variable may be adjusted, or compared, at a time. This difficulty may be overcome by noting that at high frequencies the voltage E_o is primarily a function

of the L-C product, and that at low frequencies it is primarily a function of the R-C product. Therefore, with the frequency of the variablefrequency sinusoidal-voltage source high, C should be adjusted until the width of the ellipse has been minimized. Then the frequency should be reduced until the width of the ellipse is quite large. At this frequency the value of R should be adjusted until the width of the ellipse has again been minimized. Estimate of approximate value of L and C may be obtained by visual observation of natural frequency of unexcited servomotor and spring.

So far, the servomechanisms described have been d-c types. Figure 4A shows part of a two-phase induction motor servomechanism and Fig. 4B its electromechanical equivalent. The amplifier components have not been considered because, in general, straightforward amplification stages act upon the sidebands of the modulated suppressedcarrier signals and therefore produce only very small time delays. On the other hand, the servomotor essentially demodulates the modulated suppressed-carrier signal and acts only upon the envelope or modulating signal, and thus may produce large time delays.

Compensating A-C Servos

Figure 4C is a schematic of the equivalent circuit of the two-phase induction servomotor. As will be noted from the analytical expressions of Fig. 4C, the equivalence of

this circuit holds only over a limited region of the modulating signal frequencies. This situation is generally true of any a-c network containing only linear elements.


The parameters of this equivalent circuit may be determined by the procedure demonstrated in Fig. 1D. As there are two variables, L and R to be adjusted together, tuning L and C so that they resonate at the carrier frequency leaves only R to be adjusted.

As mentioned before, the a-c servomotor demodulates the modulated suppressed-carrier signal, and, therefore, it is difficult with linear elements to synthesize a network which is the equivalent of the a-c servomotor. This factor makes it quite difficult to obtain as much stabilization from linear a-c networks as from linear d-c ones. It is, therefore, suggested that a small two-phase motor, directly coupled to a small a-c rate generator, be used as the equivalent circuit for an a-c servomechanism. This small two-phase motor and generator combination can then be used as the feedback branch of a stabilization feedback amplifier, and the resulting amplifier will serve as a stabilization network for two-phase servomechanisms. Figure 5 demonstrates the method by which this may be accomplished.

The a-c amplifier No. 2 of Fig. 5 does not need to be a separate amplifier, but may be a stage from either K_s or a-c amplifier No. 3. A velocity signal proportional to the signal developed by an a-c rate generator can be obtained from the control phase of the small two-phase motor and thus eliminate the a-c rate generator from the circuit (see Fig. 5).

In review, the response of a servomechanism can be improved with the aid of an approximate stabilization feedback amplifier (Fig. 1D). Furthermore, if the response is not sufficiently improved after the use of a single stabilization network, additional networks may be added. The design of these additional networks usually is simplified by the use of a minor feedback loop around the first stabilization network and the unimproved servomechanism which are in cascade. This effect is demonstrated in Fig. 2B.

CINCH SOCKETS ARE STANDARD

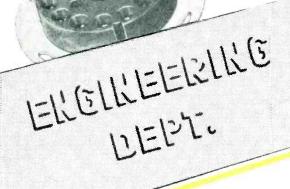



A LONG LINE OF FIRSTS"



... testifies to the confidence of the electronics manufacturer in Cinch. Behind "locked doors" the experimental engineers work on your design

problems, exploiting the broad electrical experience that has contributed so much in the development of electronics and related products. In the Cinch designing room many of radio's most serviceable features, represented by small metal plastics parts, were created and perfected. For example: The sub-miniature and the grip-pin type socket. Cinch offers a complete metal plastic service for small and intricate assemblies.

AVAILABLE AT LEADING ELECTRONIC JOBBERS . . .

everywhere

PATENTS PENDING



Sub-miniature for "printed electronic circuits," No. 54A13124



Grip-pin type miniature socket, 1" mtg. center, No. 56F12865

MANUFACTURING CORPORATION
2335 WEST VAN BUREN STREET CHICAGO 12, ILLINOIS

Subsidiary of United-Carr Fastener Corporation - Cambridge \$2, Massachusetts

www.americanradiohistory.com


F-M and Television Receiving Antennas

By GEORGE P. KEARSE Senior Engineer, American Phenolic Corp., Chicago

Type of Antenna; Length in Feet Approxi- Radiation Pattern			Gain over Dipole			
$\Lambda = \frac{468}{f_{me}} B = \frac{492}{f_{me}} C = \frac{246}{f_{me}}$	mate Terminal Impedance in Ohms	Electric, in Line with Radiator	Magnetic, Right Angles to Radiator	Power	Decibels	Recommended Feed Line, Application and Remarks
DIPOLE PLAIN FOLDED A	72	Figure of eight, bidirectional broadside to elements	Circular	Unity	Zero	PLAIN—75-ohm coaxial. FOLDED—300-ohm twin-lead. Use of twin-lead to feed plain dipole gives broadband operation but extreme loss in gain; not recommended General two-direction coverage for receiving in areas of moderate signal strength. Folded dipole slightly more broadbanded than plain. If 306-ohm twin-lead is used as radiator, do not shorten length A for propagation factor
DIPOLE AND REFLECTOR PLAIN B C C FOLDED	250	Uni- directional broadside to radiator	Half of figure of eight	2 to 2½ times	3 to 4 db	PLAIN—50-ohm or 75-ohm coaxial; 75-ohm cable is more broadbanded. FOLDED—300-ohm twin-lead Single-direction coverage, high front-to-back ratio and high gain. Recommended for use in areas of low signal strength and where single-direction radiation pattern is desired. Folded radiator slightly increases bandwidth. If array is to be used over narrow band, calculate length B at lowest frequency desired. Reducing C to 0.15 λ (in air) gives higher gain but lowers impedance and reduces bandwidth
DIPOLE, REFLECTOR, AND DIRECTOR PLAIN C + C + C + D = 450 FOLDED FOLDED D 450 D 450 MC	20 to 30 80 to 120	Uni- directional broadside to radiator	Half of figure of eight	to t times	4 to 6 db	PLAIN—50-ohm coaxial. If better impedance match is desired, use quarter-wave matching transformer; impedance of transformer should be square root of product of line and antenna impedances. FOLDED—75-ohm coaxial or 95-ohm twin coaxial Single-direction coverage, high front-to-back ratio and high gain. Very frequency-sensitive. Narrow bandwidth. Recommended for use in areas of very low signal strength and for one frequency only. Spacing is $\lambda/4$; reducing C to 0.15 λ for reflector and 0.1 λ for director (in air) increases gain but reduces impedance to 8 to 10 ohms for plain and 30 to 40 ohms for folded dipole
STACKED DIPOLES PLAIN B FOLDED A	35 to 40	Figure of eight, bidirectional broadside to elements	Figure of cight, bidirectional broadside to elements	2 to 2½ times	3 to 4 db	PLAIN—50-ohm coaxial. FOLDED—150-ohm twin-lead. Quarter-wave matching transformer may be used for 300-ohm twin-lead if desired, but will be frequency-sensitive High-gain array for use in areas of low signal strength and where two-direction coverage is needed. Useful over moderate frequency hand. Value of B may be reduced to λ/8 (in air) if desired, with a reduction in gain
STACKED DIPOLES AND REFLECTORS PLAIN B A D 10 10 10 10 10 10 10 10 10 10 10 10 10	25 10 30, -	Uni- directional broadside to elements	Uni- directional broadside to elements	to 5 times	6 to 7 db	PLAIN—50-ohm coaxial cable. Quarter-wave matching transformer may be used for better impedance match but will be frequency-sensitive. FOLDED—95-ohm twin coaxial cable or 150-ohm twin-lead High-gain array for use in areas of low signal strength and where single-direction coverage is desired. Useful over relatively narrow band. Value of C may be reduced to 0.15 λ (in air) with an increase in gain. Value of impedance will be lower and array will be more frequency-sensitive. Value of D may be reduced to λ/8 (in air) if desired, with a reduction in gain
TURNSTILE PLAIN A A FOLDED	35 to 40	Circular. Radiation pattern changes with frequency	Figure of eight	0.7 of a dipole	-1½ db	PLAIN—50-ohm coaxial cable. FOLDED—150-ohm twin-lead Omnidirectional coverage for use in areas of high signal strength. Low gain. Very frequency-sensitive; radiation pattern approximates dipole pattern rotated 45° from axis of either dipole when operated off frequency. With this array, two dipoles are connected together with a quarter-wave phasing section of 75-ohm coaxial cable for plain dipoles and 300-ohm twin-lead for folded dipoles. Length of phasing section must be corrected for propagation constant of line used

ELECTRONICS REFERENCE SHEET

A New, Better LEVER ACTION SWITCH!

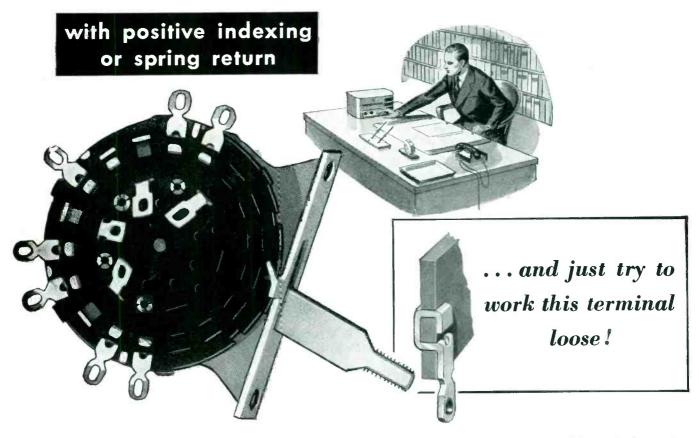


Although only recently developed and placed on the market, this lever action switch is in big demand. No wonder! It is ideally suited to intercommunications, centralized radio, sound distribution and public address equipment. It gives you a choice of positive indexing or spring return. It is as dependable as the leaf spring telephone type switch, yet available at much lower cost.

Consider some of the other "plus" features that set this switch apart: Self-holding terminals of exclusive design are securely clinched to the stator without rivets or eyelets (just try to pull them loose!). All terminals, contacts and ground rings are silver plated for low contact resistance. Constant tension of rotor contact members provides a dependable, self-cleaning action. Insulation is of the highest-grade phenolic.

Positive indexing types of this switch have 48 standard circuit combinations, 24 shorting and 24 positive non-

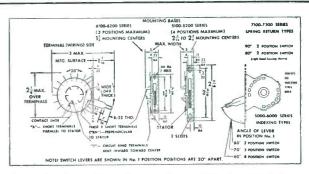shorting. Spring return types have 17 standard shorting and 17 positive non-shorting circuit combinations. Write for engineering data folder or see your nearest Mallory distributor.



Send for Engineering Data Folder

The Engineering Data Folder for the new Mallory Lever Action Switch contains complete specifications, available circuit combinations with respective terminal locations, dimensional drawings—everything the engineer needs to assist in selection of the particular Mallory Lever Action Switch to best handle the application.

MALLORY SWITCHE

(ELECTRONIC, INDUSTRIAL and APPLIANCE)

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

TUBES AT WORK

Including INDUSTRIAL CONTROL


Edited by VIN ZELUFF

Automatic Rat-Catcher Circuit	120
Pulsed Underwater Acoustic Measurements	120
Electronic Fuse	136
Improving Performance of Milliwatt Relays	140
Camera Shutter Timer	140
Telecontrolled Clocks	150
Sound Flashlight for the Blind	102
Doma Trading to the Dinter	196

Automatic Rat-Catcher Circuit

AUTOMATIC electrocution of rats and other rodents is accomplished by the machine illustrated in the accompanying photograph. It is designed to be placed on a rat runway in a factory building in the food or other industry having a general sanitation problem.

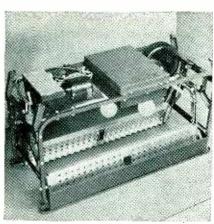The unit illustrated is normally contained inside a metal case that is open at each bottom end to provide the rat runway. When a rodent enters the runway he intercepts a beam of light from a projec-




View of the rat catcher with metal case removed to show the electronic and mechanical features

tion lamp that shines into a phototube on the other side of the runway. The phototube triggers a 2050 thyratron, shown in the circuit diagram, which fires and energizes a relay that connects the line voltage to a solenoid. This in turn trips two metal grids having pointed projections and the grids snap together and hold the rat firmly.

The grids are maintained at the

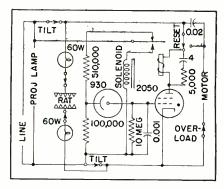voltage of the power line (through the series 60-watt lamps) and the potential is applied to the rat for a lethal period of about 120 seconds. When electrocution is completed, the rat is lifted, still held by the grids, to a door at the side of the metal case which opens to allow ejection. A motor-driven mechanism carries out this ejection and resetting cycle in 30 seconds. At the



Circuit of the rodent electrocution machine

end of the cycle, the grids return to the ready or arming position and the ejection door closes.

During ejection, the plate voltage is removed from the 2050 thyratron and when the cycle is completed this connection is restored so that the tube is ready to be triggered by another pulse from the phototube, in turn caused by another rat. The technique is said to cause the rodent no pain, mutilation or freightened struggle by the manufacturers of the machine, LFC Corporation, Rochester, N. Y.

Pulsed Underwater Acoustic Measurements

BY GEORGE F. BREITWIESER

Acoustics Laboratory Massachusetts Institute of Technology Cambridge, Massachusetts


UNDERWATER acoustic measurements in laboratory tanks are sometimes complicated by interfering waves reflected from the walls. Unless the tank is lined with highly absorbing material, steady state measurements are difficult to make, because standing waves of significant amplitude are almost always present.

This difficulty can be avoided' however, if measurements are made by a pulse technique in the short time interval before unwanted reflections can reach the receiver. Such measurement of reflections from a steel plate is illustrated in Fig. 1.

A burst of acoustic power is projected into the tank. Echoes are formed when this burst strikes the plate and the walls and before long these echoes fill the tank with complex wave patterns. The condition required for measurements is

shown in Fig. 1B. Here the outgoing burst has entirely passed, the echoes reflected from the walls have not yet reached the receiver, and the middle of the wave packet reflected from the plate is just at the receiver.

Figure 2 is a block layout of a reliable circuit which has been developed for making this kind of measurement. Only the useful middle section of the received signal is shown on an oscilloscope allowing the study of phase, amplitude, and wave shape of the reflected wave. The measurement cycle is repeated at a frequency which leaves time for reverberation to die out between bursts. Pulses formed at 60 cps from the a-c line actuate a submultiple generator which in turn delivers pulses at 10 to 60 per second. These pulses initiate the measurement cycle by controlling the transmitting and re-

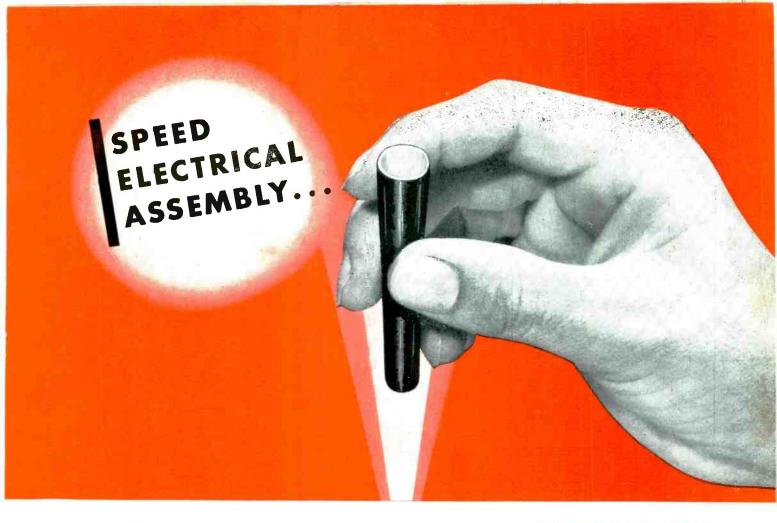

with smooth inside bore of DIEFLEX



Your product assembly will be quicker and easier if you use top-quality Dieflex products. Every one has smooth inside bore that makes it easy to use. It slips over bent wire, around corners, and into crowded places quickly, because wire ends won't catch on the smooth inside surfaces.

The many inherent advantages of Dieflex Tubing Products, including the smooth inside bore, extreme flexibility, thorough impregnation with oleoresinous baking-type insulating varnish, and the many other desirable features found in every piece, are reasons for the widespread use of Dieflex Varnished Tubing Products. Get these advantages for your own product. Dieflex is available with either a cotton or glass fiber base to meet your insulating requirements. Call your nearest representative for details.

DIEFLEX PRODUCTS LIST

MADE WITH BRAIDED COTTON SLEEVING BASE

VTA Grade A-1 Magneto Grade Varnished Tubings VTA Grade B-1 Standard Grade Varnished Tubings VTA Grades C-1 and C-2 Heavily Coated Saturated Sleevings VTA Grade C-3 Lightly Coated Saturated Sleevings Heavy Wall Varnished Tubings and Saturated Sleevings

MADE WITH BRAIDED GLASS SLEEVING BASE

VTA Grade A-1 Magneto Grade Varnished Fiberglas Tubings VTA Grade C-1 Extra Heavily Saturated Fiberglas Sleevings VTA Grade C-2 Heavily Saturated Fiberglas Sleevings VTA Grade C-3 Lightly Saturated Fiberglas Sleevings Silicone-Treated Fiberglas Varnished Tubings and Sleevings

MANUFACTURERS CORPORATION *CHICAGO 6 . 565 W. Washington Blvd.

MILWAUKEE 2 312 E. Wisconsin Ave DETROIT 2 15 Lawrence Ave.

*Local Stocks Available

*CLEVELAND 14 1231 Superior Ave., N. E. DAYTON 2

IMC Representatives

W. C. JOHNSON - PEORIA 5 - 101 Heinz Court H. A. HOLDEN - MINNEAPOLIS 3 - 1208 Harmon Place H. R. BRETHEN - DETROIT 2 - 15 Lawrence Ave.

Authorized Distributors

INSULATION and WIRES INCORPORATED

St. Louis 3, Mo. • Atlanta, Ga. • Boston 20, Mass. Detroit 2, Mich. • Houston 2, 1ex. • New York 7, N. Y.

TRI-STATE SUPPLY CORPORATIONS

Los Angeles 13, Cal. • San Francisco 7, Cal. • Seattle 4, Wash.

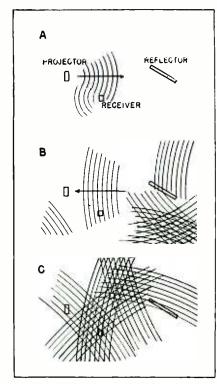


FIG. 1—Acoustic measurements incorporating the pulse technique are made only during interval (B) when only the desired reflected wayes are at the receiver

ceiving systems and synchronizing the oscilloscope sweep circuit.

An initiating pulse acting on the oscillator control circuit creates a longer control pulse which actuates the oscillator. While on, the oscillator delivers a burst of power at its characteristic frequency. This burst, amplified in a conventional transmitting amplifier, is delivered to a transducer which then projects a sound pulse into the water.

After passing through the acoustic system, the wave packet is picked up by a hydrophone receiver, which feeds a signal into the receiver amplifier. A gate circuit is interposed between the output of this amplifier and the input of the oscilloscope. A delayed gate pulse is applied to the receiver gate circuit when the acoustic pattern in the tank has developed to the The gate pulse proper degree. allows the receiver to become operative only long enough to pass the desired section of the received signal.

It will be evident that full use has been made here of the pulse techniques used during the war in radar and sonar systems. From a practical point of view, phase and wave shape observations which were out of the question in previous acoustic pulsing equipment using electronic switch tubes can now be made, because variable switching transients and lack of phase synchronization have been eliminated.

The detailed schematic circuit is shown in Fig. 3. Except for the pulsed oscillator,² which is somewhat unusual, each section is a conventional circuit with constants adjusted for this application. These circuits are given in standard texts³ and can be redesigned by well known methods^{3,4,5} to fit other applications.

With circuit constants shown in the schematic diagram, burst repetition rates of 60, 30, 20, 15, 12, and 10 per second are possible. The burst duration is adjustable from 1

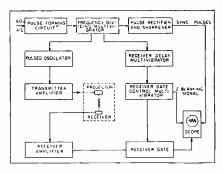


FIG. 2—Block diagram of acoustic pulse measurement equipment

to 90 milliseconds, while the receiver gate pass duration is variable between 0.1 to 9 milliseconds. Acoustic frequencies from 17 kc to 50 kc are available, and the receiver gate time delay may be varied from 1 to 90 milliseconds. Any of these (continued on p 136)


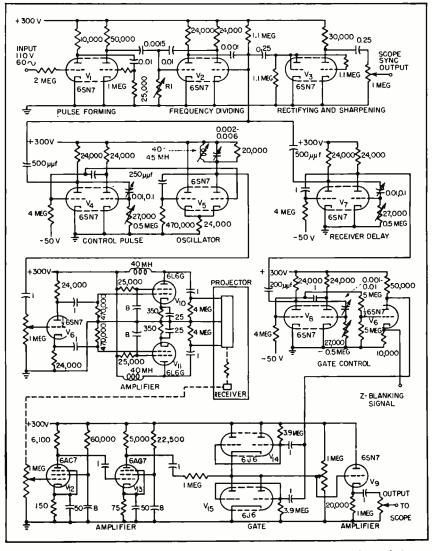


FIG. 3—Schematic diagram of acoustic measurement circuit using the pulse technique. Resistor R_1 is variable in steps of 0.75, 1.5, 2, 2.7, 4 and 5 megohms for selection of pulse repetition rates

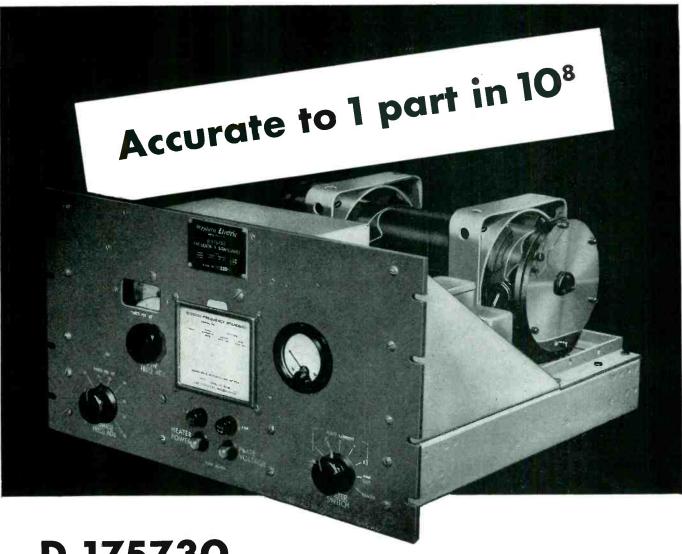

D-175730 Primary Frequency Standard

Here is a 100 kc frequency source of the highest precision—yer rugged enough to be used in semi-portable service.

The frequency of the Western Electric Primary Frequency Standard D-175730 is maintained to within one part in 108, measured over a period of one day, regardless of moderate changes in ambient temperature, humidity and air pressure.

Heart of this high-precision instrument is a GT-cut crystal, suspended by wires inside an evacuated glass envelope. Crystal is cut and ground for

extremely low temperature coefficient (less than 10.5 parts per 10^8 per degree F) and is enclosed in an oven that maintains constant crystal temperature within 1/100 of a degree.

If you are making time-frequency measurements—or operating two or more independent systems in synchronism—you will want to investigate the Western Electric Primary Frequency Standard. For further information, call your nearest Graybar Representative, or write Graybar Electric Company, 420 Lexington Avenue, New York 17, N. Y.

Western Electric

-QUALITY COUNTS-



DISTRIBUTORS: IN THE U. S. A. — Graybar Electric Company. IN CANADA AND NEW FOUNDLAND — Northern Electric Co., Ltd.


THE ELECTRON ART

Edited by FRANK ROCKETT

Radio-Frequency Mass Spectrometer	124
Noise in Vacuum Phototubes at High Current Levels	
Detecting Displacement	168
Reducing Hum in Pentodes	170
Survey of New Techniques	178

Radio-Frequency Mass Spectrometer

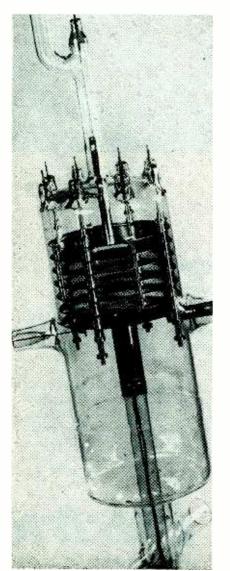A NEW TYPE ELECTRONIC TUBE, which provides a greatly simplified and flexible mass spectrometer, has been designed by W. H. Bennett of the National Bureau of Standards. The new spectrometer provides



New electronic tube makes practical the investigation of negative ions and simplifies equipment for studying positive ions

means of exploring the little-known fundamentals of negative atomic ions and a simple method for studying positive ions. The accompanying photograph shows the construction of a single-stage tube, which requires low direct biasing voltages and a radio-frequency voltage that can be varied from about 100 kc to 3 mc for its operation. In experiments with negative ions, a magnetic field of the order of 100 gauss parallel to the grids of the tube is also required.

Formation of Negative Ions

Development of the new tube was necessitated by attempts to investigate conditions leading to the formation of negative atomic ions of the heavier elements. Detecting, separating, identifying and measuring such ions is one of the neglected fields of research in pure physics. These negative ions, consisting of atoms with extra electrons, have very low energies of formation; their study has been difficult because of their rapid dissociation in very short distances, before they reach a measuring electrode.

Since their discovery about 40 years ago, negative ions have been detected for only a few elements, although theory indicates that many elements should have such ions. Previous experiments at NBS indicated that negative ions might exist in many familiar forms of electronic tubes, but that they would not be detected if the discharge path within the tube was longer than about an inch.

Operation of Spectrometer

The radio-frequency mass spectrometer tube consists of a cathode,


CURE FOR RESIDUAL RIPPLE

Ripple introduced into high-gain balanced low-frequency amplifiers from the alternating heater currents can be removed by demagnetizing the tubes. In setting up hundreds of biological amplifiers at the Burden Neurological Institute (England), it was observed that although ripple could be reduced in some cases by using tubes with screened heaters or operating the heaters at reduced voltage, ripple from the magnetic component of the heater current remained in some tubes. Inasmuch as selection of tubes was impractical, some method for removing this source of ripple was sought. The investigation showed that this residual magnetic source of ripple could be removed by demagnetizing the tubes in a decreasing a-c field. (Electronic Engineer, p 235, July 1948)

near which positive or negative ions are formed, several grids and a plate. If negative ions are to be studied, a small magnetic field is required to confine the electrons to the space inside the first grid to prevent formation of positive ions in other parts of the tube.

Ions arising at the cathode are accelerated through the first grid into the alternating field of the second grid, to which the r-f voltage is applied. Those ions that enter this field at the proper phase, and which have a mass and velocity related to the frequency of the field, pass through the second grid as the r-f potential changes polarity. Thus these ions are accelerated while traveling from the first to the third grid. A blocking potential, nearly equal to the maximum energy with which ions of the proper mass emerge from the r-f field, is applied to the fourth grid and the current to the plate is observed, thus indicating the rate at which ions of a particular type are being formed.

The method can be extended to two cascaded stages as shown in the following picture, thus obtaining a high order of mass resolution. In its more advanced form, this double-stage spectrometer can be used for measuring positive or negative ions. The equipment consists essentially of a multigrid tube in which the adjustable radio frequency is applied to two grids, one in each of the two stages, while all

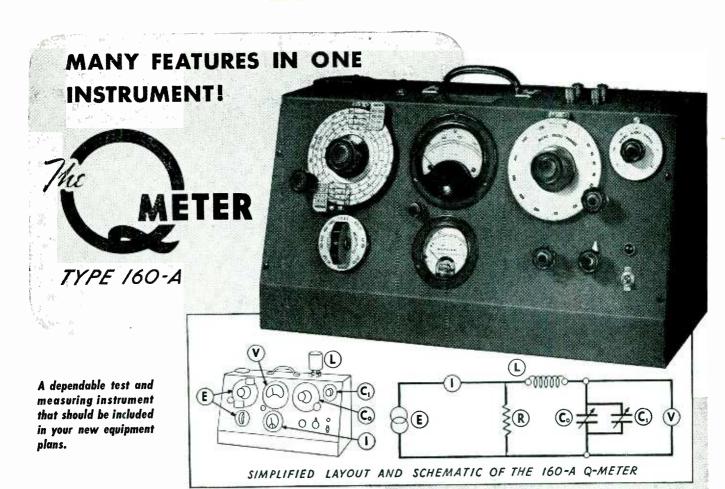

For many years the Q-Meter has been an outstanding contribution to the field of radio frequency measuring equipment. It is an indispensible instrument to engineers, manufacturers, research laboratories and to the whole radio and electronics industry. Because of its simplicity and ease of operation, it replaces many costly pieces of apparatus with which the radio laboratory is customarily equipped. More than one radio engineer has told us that "The Q-Meter is the most valuable instrument that we have in our laboratory".

A FEW USES FOR THE 160-A Q-METER

Q and inductance measurement of coils.

Q and capacitance measurement of capacitors.

Dielectric and power factor measurements of ceramics, plastics and other insulating materials.

Measurement of circuit losses.

Interelectrode capacitance measurements.

Measurement of input impedance of vacuum tubes.

Measurement of coefficient of coupling of R. F. Transformers.

Measurement of transmission line characteristics.

The measurement of frequency with negligible loading on circuit under test (50kc.—75 mc.).

Write for catalog "F" describing our complete line of electronic laboratory measuring equipment.

BOONTON RADIO BOONTON N.J. U.S.A. Orporation

THE BASIC METHOD OF MEASUREMENT EMPLOYED IN THE 160-A Q-METER

An 8 range R.F. oscillator (E) supplies a heavy current (I) to an extremely low resistance load (R), the value of which is accurately known. The calibrated voltage thus developed across the load resistance (R) is coupled to a series circuit consisting of the inductance under test (L) and a calibrated variable air capacitor (C_0), having a vernier section (C_1). When this series circuit is tuned to resonance by means of the capacitor ($C_0 + C_1$), the "Q" of the inductance under test is indicated directly by the vacuum tube voltmeter (V). Variations of this basic method of measurement are used to measure inductance, capacitance and resistance.

SPECIFICATIONS

Oscillator Frequency Rasge: 50 kc. to 75 mc. in 8 ranges.

Oscillator Frequency Accuracy: $\frac{1}{2}$ 1%, 50 kc. — 50 mc. $\frac{1}{2}$ 3%, 50 mc. — 75 mc.

Q-Measurement Range: Directly calibrated in Q, 20–250: "Multiply-Q-By" Meter (I) calibrated in tenths from x1 to x2, and also at x2.5; extending Q range to 625.

Q-Measurement Accuracy: Approximately 5% for direct reading measurement, for frequencies up to 30 mc. Accuracy less at higher frequencies.

Capacitance Calibration Range: Main capacitor section (Co) 30–450 mmf accuracy 1% or 1 mmf whichever is greater. Vernier capacitor section (C₁) \pm 3 mmf, zero, \pm 3 mmf, calibrated in 0.1 mmf steps. Accuracy \pm 0.1 mmf.




DESIGNERS AND MANUFACTURERS OF THE "Q" METER . . . QX-CHECKER . . . FREQUENCY MODULATED SIGNAL GENERATOR . . . BEAT FREQUENCY GENERATOR . . . AND OTHER DIRECT READING TEST INSTRUMENTS

the other electrodes are held at appropriate direct potentials. As in the single stage unit, the ion current is measured at the plate. The exacting requirements of negative-ion separation require the use of a small magnetic field produced with external coils, but no magnetic field is required if positive ions are being separated.

Because large electromagnets or tubes containing electrodes with elaborate systems of slits are not required in the r-f mass spectrometer, this new instrument should find wide application where its resolution is sufficient. One of the principal limitations upon the resolution possible with ordinary mass spectrometers using magnetic deflection of beams is the spread in energies of the ions at the source. The percentage spread can be reduced by increasing the voltage applied to the ions before they are magnetically resolved, but the extent to which they can be accelerated is limited by the magnetic field strength that can be produced within the tube.

In the r-f mass spectrometer, this difficulty is eliminated so that the voltage applied to the ions can be pushed easily to at least an additional order of magnitude. The frequencies that are required are then increased by an amount equal to the square root of the factor by which the voltage is increased. Increasing the voltage reduces the percentage spread of the measured mass line, which is due to the velocity spread in the ion source, by the same percentage that the accelerating voltage is increased.

The large number of grids (seven) in the double-stage spectrometer would be impractical if it were not that a knitted wire fabric, which has more than 95-percent open area and with which this type of tube can readily be constructed. is now available. The simplicity and low cost of the r-f mass spectrometer should make it attractive in those applications in which its special characteristics make it superior to other kinds of mass spectrometers. Although the full possibilities of the new tube have not yet been explored, preliminary experimentation with it suggests that it will have wide application.

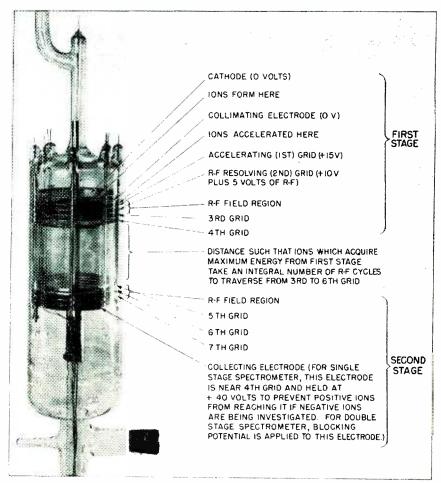

Radio-frequency fields in two-stage mass spectrometer separate ions by passing only those whose initial mass and velocity give them a transit time comparable to r-f period

Noise in Vacuum Phototubes at High Current Levels

By R. F. Morrison National Bureau of Standards Washington, D. C.

MEASUREMENTS of the output noise from phototubes were made and compared to the theoretical noise due solely to shot effect. The good agreement between measured and computed values indicates that, at cathode currents from as low as 50 microamperes to as high as 1.0 milliampere, shot effect is the only important source of noise.

Sources of Noise


The flow of electrons from cathode to anode of a phototube under steady illumination is not perfectly uniform. Although the average current is constant, there are small fluctuations due to the

random nature of photoelectric emission. These fluctuations produce noise that limits the percent modulation which may be used in optical systems having phototube detectors. Knowledge of the amount of noise generated in phototubes is essential to the design of precision optical equipment. Several investigators have measured shot effect noise at low frequencies, approximately 1,000 cps, with phototube currents of the order of a microampere or less^{1,2}.

The mean relative fluctuation δ in number of emitted electrons can be deduced from the theory of

(continued on p 162)

A MAGNET WIRE

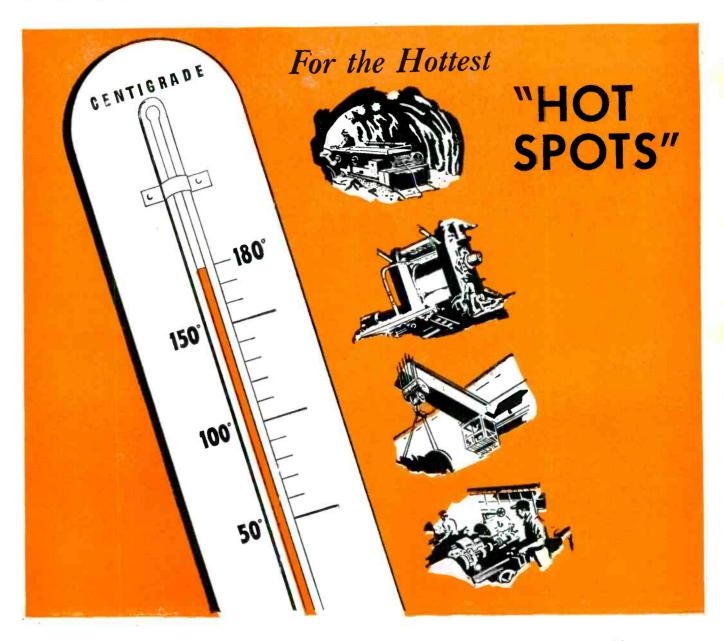

H OW CAN MAGNET WIRE, even Silotex*, withstand continuous operation at extreme high temperatures?

The answer is in war-developed silicones, now brought to the magnet wire field by Anaconda in amazing glass insulated Silotexbonded with silicone varnish. Such insulation qualifies for the new A.I.E.E. high-temperature rating of "Class H"...180°...a 140° rise in temperature over an ambient 40° C!

Even at operating temperatures around 180° C, here's what Silotex offers: Greater life expectancy, greater over-load protection, immunity to ambient temperature, greater moisture resistance, reduction in fire hazard. For complete information on the properties of Silotex, write to Anaconda Wire and Cable Company, 20 N. Wacker Drive, Chicago 6, Ill.

Anaconda SILICONE BONDED SILICONE BONDED SILICONE BONDED




NEW PRODUCTS

Edited by A. A. McKENZIE

New equipment, components, tubes, testing apparatus and products closely allied to the electronics field. A review of catalogs, handbooks, technical bulletins and other manufacturers' literature

Subminiature Tubes

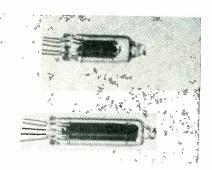
SONOTONE CORP., Elmsford, N. Y., announces a new line of T-2 subminiature filamentary type tubes. The line includes a pentode voltage amplifier and pentode power-output



tube. Both types are produced in three filament current ratings: 20, 15, and 10 milliamperes. Normal filament voltage across the voltage amplifier is 0.6 volt; across the power amplifier, 1.2 volt. With battery supplies of about 20 v and a typical hearing-aid circuit, the amplifier has a voltage gain per stage of about 75. The power tube delivers 2 milliwatts with a battery drain of 10 milliwatts.

Beat-Frequency Oscillator

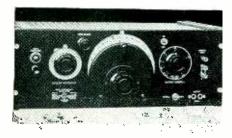
GENERAL RADIO Co., 275 Massachusetts Ave., Cambridge 39, Mass. Type 1304-A beat-frequency oscillator supersedes the older type 913-C. Although it is identical in



overall size and frequency range the new oscillator has greater accuracy, better stability, and lower distortion. Frequency range is 20 cycles to 20 kc with accuracy of \pm (1 percent + 0.5 cycle) after the dial zero has been set in terms of the a-c line frequency. Output impedance is 600 ohms; normal maximum output is 0.3 watt with total distortion of less than 0.25 percent over most of the range.

Television Equipment

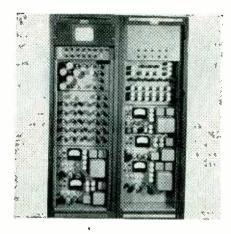
TELEQUIP RADIO Co., 1901 South Washtenaw Ave., Chicago 8, Ill.



The television picture generator illustrated is representative of a line of equipment for studio rehearsal or broadcast use. The TMG-100A monoscope picture generator and distribution panel are also available.

Subminiature Battery

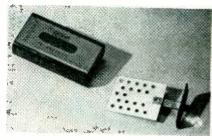
NATIONAL CARBON Co., 30 East 42nd St., New York 17, N. Y. A new hearing aid A battery with life



of 80 hours (4.25 ampere-hours under ASA test conditions) is only the size of a dual penlite-type battery. Zinc electrode is in the center and carbon strips on the outside of the plastic case act as depolarizers.

Sensitive D-C Scope

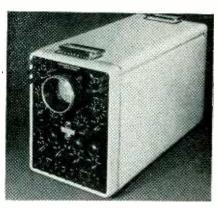
AMERICAN BRITISH TECHNOLOGY, Inc., 57 Park Ave., New York 16, N. Y., distributors for Furzehill Labs. Model 1684K is a new high-




sensitivity version of the Model D scope and has a gain of about 10,000 times. Sensitivity of the d-c amplifiers for both axes is 1 millivolt per inch. Frequency range up to 300 kc

Step Attenuator

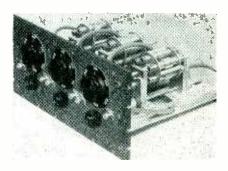WEINSCHEL ENGINEERING Co., 123 William St., New York 7, N. Y. A new step attenuator can be used in the frequency range from 0 to 1,000 mc, or by heterodyne methods its



November, 1948 — ELECTRONICS

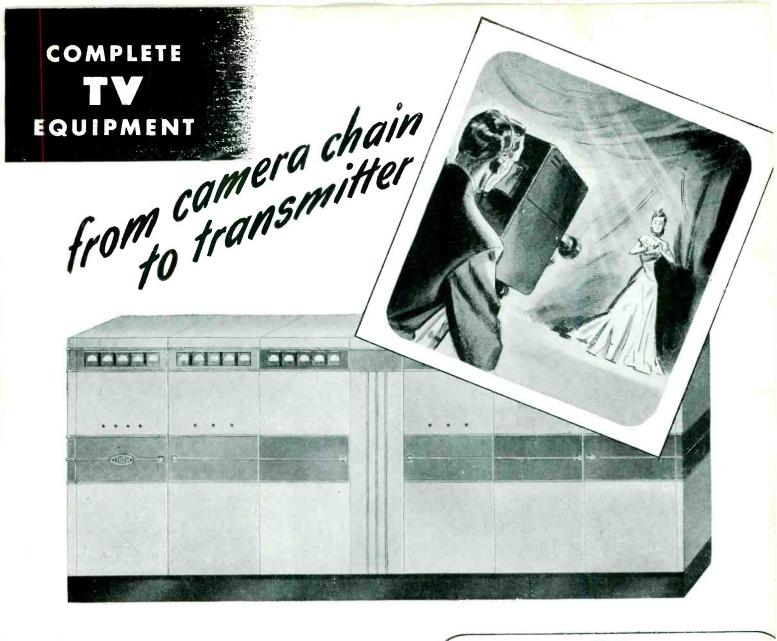

LOOK TO RAYTHEON FOR ALL YOUR NEEDS

RAYTHEON is prepared to furnish complete equipment for television stations. Through this one dependable and reliable source of supply you can obtain any single item or an entire installation ranging from camera chains to antenna and associated equipment ...including 50 watt microwave equipment for remote pickup, STL, or point-to-point relay. Raytheon stands ready to provide you with prompt and intelligent service at all times.



NEW ENGLAND

Albert Keleher, Jr.
Raytheon Manufacturing Co.
Waltham 54, Mass.
WA. 5-5860, Ex. 422

CHATTANOOGA, TENNESSEE

W. B. Taylor Signal Mountain 8-2487

CHICAGO 6, ILLINOIS

Warren Cozzens Ben Farmer 222 West Adams Street Ran. 7457

DALLAS 8, TEXAS

Howard D. Crissey 414 East 10th Street Yale 2-1904

NEW YORK 17, NEW YORK

Henry J. Geist 60 East 42nd Street MU. 7-1550

SAN FRANCISCO, California

E. J. Rome 49 California Street Sutter 1-0475

SEATTLE, WASHINGTON

Adrian VanSanten 135 Harvard North Minor 3537

WASHINGTON 4, D. C.

Raytheon Manufacturing Co. 739 Munsey Building Republic 5897

WILMINGTON, CALIFORNIA

J. L. Lovett

404 North Avalon Blvd., Terminal 4-1721



RAYTHEON MANUFACTURING COMPANY


Industrial and Commercial Electronic Equipment, FM, AM and TV Broadcast Equipment, Tubes and Accessories

WALTHAM 54, MASSACHUSETTS

range can be effectively extended to 3,000 mc. It is useful for impedance measurements, taking antenna characteristics, calibrating voltmeters, and checking receiver gain. Attenuation is 0 to 60 db.

Electronic Counters

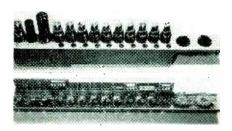TECHNITROL ENGINEERING Co., INC., 3212 Market St., Philadelphia 4, Pa. The basic decade electronic



counter illustrated is combined with switching circuits for counting and timing circuits that involve speeds exceeding 150,000 counts per second. Predetermined counting, measurement of elapsed time to less than 7 microseconds, and various other features are included.

Loudspeaker


KLIPSCH AND ASSOCIATES, Hope, Arkansas. The new Style 5 high-fidelity loudspeaker is complete



with cabinet. Each loudspeaker comprises a high-frequency tweeter and new K-3-C woofer with response down to nearly 35 cycles. Equipment is distributed through Brociner Electronics Lab., 1546 Second Ave., New York 28, N. Y.

Tone Arm

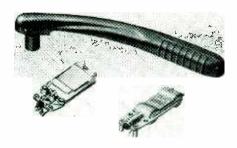WEBSTER ELECTRIC Co., Racine, Wisconsin, has announced the



Featheride tone arm and two new crystal cartridges for reproduction of long-playing microgroove records. The unit is balanced to maintain 7-gram tracking pressure. Model F12 cartridge is for long-playing records only, and model F11 plays either microgroove or standard records.

Television Test Device


RADIO CORP. OF AMERICA, Camden, N. J. Type WA-21A video sweep generator, when used with suitable



detector and oscilloscope, facilitates rapid testing of television i-f frequency systems with visual observation of the frequency response characteristic through a range of 100 kc to 10 mc.

Microgroove Cartridge

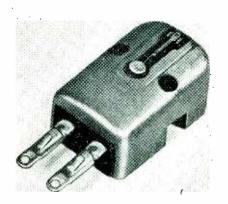
GENERAL ELECTRIC Co., Syracuse, N. Y. A new variable reluctance



cartridge designed for long-playing microgroove records has a sapphire stylus, 1 mil in diameter. One-third smaller than previous models, its shape makes it adaptable to various tone arms and gives more clearance for record changers.

F-M Radio Link

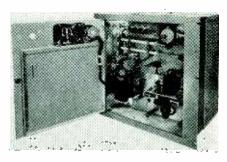FEDERAL TELEPHONE AND RADIO CORP., Clifton, N. J. The FTL-11-A is a high-fidelity studio-to-transmitter radio link for f-m broadcasting. It operates in the 940 to 952-mc



band and permits program transmission up to line-of-sight ranges of approximately 30 miles. Distortion is less than 0.5 percent between 50 and 15,000 cycles, with the noise level 65 db below 100-percent modulation. The transmitter illustrated here has a power output of about 3 watts.

Subminiature 6AK5

RAYTHEON MFG. Co., Newton, Mass. The new subminiature type CK-5702/CK605CX tube is now avail-



able. Aside from a small difference in heater current, the tube is electrically interchangeable with the type 6AK5. Sockets for the new tube are also available.

Tuned-Ribbon Reproducers

AUDAK Co., 500 Fifth Ave., New York 18, N. Y. The LM series of Tuned-Ribbon reproducers was designed for use with long-playing records. They operate with a point (Continued on p 182)

130

November, 1948 — ELECTRONICS

FOR FINER ALL-WEATHER RECORDING



Now audiodisc* lacquer provides permanent resistance to humidity

Excessive humidity has long been one of the industry's major problems—both to the manufacturer and to the recordist. Humid conditions in factories have frequently held up production and caused excessive spoilage. Also, discs which have absorbed too much moisture make poor recordings. The noise level increases progressively while recording and the cut gets greyer and greyer.

Air conditioning has been tried by several producers, but this does not prevent moisture absorption during transportation and storage. The real solution lies in the formulation of a lacquer which will provide permanent resistance to humidity. This has now been successfully accomplished by our research laboratory. Here are the facts:

- 1. THE IMPROVED AUDIODISC FORMULATION has eliminated all production difficulties due to excessive humidity. During the past summer no trouble was encountered, even with humidity as high as 90%.
- 2. Countless Tests in our "weather room" have proved the new Audiodiscs to be remarkably resistant to moisture absorption. Discs subjected to a temperature of 90° at 80% to 90% humidity for many weeks show no increase in noise level while recording. Ordinary discs, under the same conditions, show a noise level increase of from 15 to 25 db. The most conclusive proof of all, however, has come from the field—for during the past summer, one of the most humid on record, our customers have reported no difficulties in recording or reproduction due to humid conditions.
- 3. This "Weather-Proof" Feature has been achieved without any basic change in our lacquer formulation. Recordists will therefore continue to note the outstanding qualities in recording, playback and processing which have made for Audiodisc leadership.

This improved humidity-resistant lacquer is now used on all Audiodiscs. It is your assurance of finer, all-weather recording—with the same consistent, uniform quality which has characterized Audiodiscs for a decade.

*Reg. U. S. Pat. Off.

Audiodiscs are manufactured in the U.S.A. under exclusive license from PYRAL, S.A.R.L., Paris.

Audio Devices, Inc., 444 Madison Ave., N.Y.C.

EXPORT DEPT: ROCKE INTERNATIONAL, 13 EAST 40TH STREET, NEW YORK 16, N. Y.

they speak for themselves audiodiscs

NEWS OF THE INDUSTRY

Edited by JOHN MARKUS

Radio Parts Show; IRE fellowships announced; midwest television networks; National Electronics Conference program

Television Application Freeze Announced by FCC

RECENT ACTION by the FCC temporarily halted any further authorization of new television stations. Chairman Wayne Coy announced that the freeze would remain in effect long enough for the Commission to decide whether certain changes should be made in engineering standards for the avoidance of interference between television sta-


tions in adjacent cities. This investigation would probably take about six months.

The freeze order applies only to stations for which applications are pending. Stations previously authorized, including the thirty-seven now on the air and the eighty-six now under construction, are not affected.

Coolidge Lab Dedicated

GROWING DEMAND for specialized industrial and medical applications for x-ray led to the foundation of the world's largest x-ray development laboratory, by General Electric X-Ray Corp. at Milwaukee,

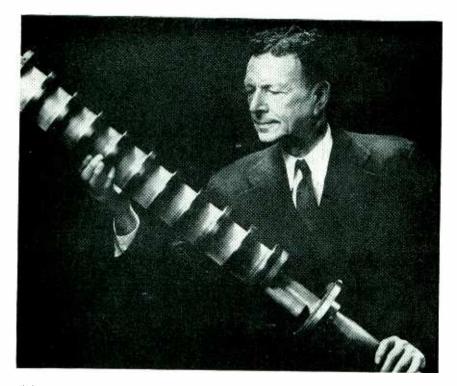Wisconsin. The \$750,000 research center will be known as Coolidge Laboratory, in honor of William D. Coolidge, x-ray pioneer and director emeritus of the GE Research Lab, Schenectady, N. Y. Dedication



William D. Coolidge, father of modern x-ray tube, examines a million-volt x-ray tube

ceremonies, attended by 200 radiologists, 1,100 employees, and 200 industrial leaders, physicists and research scientists, were highlighted by the addresses of Charles E. Wilson, president of General Electric, and Dr. William D. Coolidge, the guest of honor.

Since GE's expansion program began a year ago, seven major pieces of equipment have been developed by the Coolidge Laboratory: the Cardioscribe, a new direct-writing electrocardiograph that eliminates developing a film to read the heart's action: a directrecording x-ray diffraction machine, which opens broad fields for the application of diffraction and facilitates analysis of unknown materials; the Maximar 100, a 100, 000-volt machine designed especially for treating skin diseases; the Maxiscope 500, a new type of robot x-ray apparatus equipped for highvoltage radiography to provide better x-rays of heavy body sections; a new type Inductotherm, not yet ready for announcement; a special fluoroscope used by shoe manufacturers to find unwanted nails in shoes: and a new line of x-ray film illuminators using circular fluorescent lamps.

New IRE Section

OVER FORTY PEOPLE attended a recent organizational meeting of the IRE, held in Omaha, Nebraska, and signed a petition asking the national board of directors of IRE to form an Omaha-Lincoln Section. Papers were read, a collection was taken up to help finance the activity, and temporary officers were elected.

The meeting was presided over by George Hixenbaugh, chairman of the Cedar Rapids Section. An address outlining the place of the IRE in the local situation was given by T. A. Hunter, regional director. John A. Green, secretary-treasurer of Region 5, assisted with the organizational activity for the new section.

Rochester Fall Meeting

TENTATIVE PROGRAM of the Rochester Fall Meeting of members of the IRE and RMA Engineering Department, to be held at the Sheraton

UHF EQUIPMENT

DEVELOPED · DESIGNED · PRODUCED

7. DEVELOPMENT . . from concept of idea to working model

2. DESIGN by thoroughly experienced UHF engineers

3. MANUFACTURE .. using methods especial. ly suited to UHF work

Specialized UHF knowledge, experience and shop practice enable Lavoie Laboratories to handle every phase of electronic production efficiently and economically.

Precision work and low unit cost are based on these factors developed through years of prac-

tical specialization in this field.

• LAVOIE PRODUCTS: Frequency Meters - Frequency Standards - Receivers Transmitters Antennas and Mounts.



Detailed information and estimates of LAVOIE service are available promptly without cost or obligation.

Larvie Laboratories

RADIO ENGINEERS AND MANUFACTURERS MORGANVILLE, N. J.

Specialists in the Development and Manufacture of UHF Equipment

Hotel, Rochester, N. Y., November 8, 9 and 10, 1948, is as follows:

Monday, Nov. 8

9:30 A. M.—Technical Session—B. E. Shackelford presiding:
A Television Station Selector Using Die Stamped Inductances, by A. D. Sobel of A. W. Franklin Mfg. Corp.
A discussion of Image Sharpness in Photography and Television, by O. II. Schade of RCA.
Application of Subminiature Tubes, by R. K. McClintock of Sylvania.
2:00 P. M.—Technical Session—D. B. Smith presiding:
The Transitrol, an Experimental AFC Tube, by J. Kurshan of RCA Laboratories, A New Low-Noise, Low-Microphoric Miniature Tube, by C. R. Knight and A. P. Haase of GE.
4:00 P. M.—Committee Meetings
8:15 P. M.—General Session—E. F. Carter presiding:
What's When in America by Konneth S.15 P. M.—General Session—E. F. Carter presiding:
What's When in America, by Kennet's
W. Jarvis, consulting engineer.
9:15 P. M.—Stag Party, courtesy of
American Lava Corp.
9:00 A. M.—Technical Session—S. L.
Bailey, presiding:
Report of RMA Safety Committee, by
William Vassar of Emerson.
Developments in Germanium Crystals.
by Stuart T. Martin and Harold Heins
of Sylvania.
A Television Distribution System for
Laboratory Use, by Joseph Fisher of
Philoo.

2:00 P. M.—Technical Session I. Israel presiding:
A Direct-Coupled Video and AGC System for Television Receivers, by H. R. Shaw of Colonial Radio Corp.
A Pulse-Cross Generator for Television Receiver Production, by R. P. Burr of Hazaltine.

-Technical Session-D. D.

Phileo. 2:00 P. M.

Receiver Production, by R. P. Burr of Hazeltine.
4:00 P. M.—Committee Meetings
6:30 P. M.—Stag Banquet—E. DeForest Bayly, toastmaster
Wednesday, Nov. 10
9:30 A. M.—Technical Session—O. L. Angevine, Jr. presiding:
Lightweight Pickup Design for Microgroove Record Playing, by B. P. Haines, Elmo Voegtlin, C. D. O'Neill and R. S. Cranmer of Philloo.
Symposium—What Constitutes High Fidelity, by Harvey P. Fletcher of Bell Telephone Laboratories, John K. Hilliard of Altec Lansing Corp. and C. J. LeBel. consultant.
High-Quality Audio System for Radio

consultant.

High-Quality Audio System for Radio Receivers, by R. S. Anderson and B. E. Atwood of Stromberg-Carlson Co. 2:00 P. M.—Technical Session—K. J. Gardner presiding:

Front Ends of Television Receivers, by J. O. Silvey of GE.

A Picture-And-Sound-Modulated Generator for Television Receiver Production, by W. R. Stone of Hazeltine.

4:00 P. M.—Committee Meetings 8:00 P. M.—Photographic Session—A. L. Schoen presiding.

Audio Engineers Compare Loudspeakers

A RECENT MEETING of the San Francisco Section of Audio Engineering Society featured a listening test of twenty different commercial loudspeakers and a demonstration of a new tweeter-tweeter speaker. Groups of high-fidelity speakers were cross-compared, driven from the output of a pair of push-pull 211's operating essentially as a zero-impedance source. Audio was derived from an Ampex tape recorder.

The session concluded with a description and demonstration of a new h-f speaker developed by Bob Smith and Water Selsted, San Fran-

MEETINGS

Oct. 25-29: 64th semiannual convention, Society of Motion Picture Engineers, Hotel Statler, Washington, D. C.

Oct. 27-28: Annual Convention, Society for Non-Destructive Testing, Hotel Adelphia, Philadelphia.

Nov. 4-6: National Electronics Conference, Edgewater Beach Hotel, Chicago.

Nov. 8-10: Twentieth Rochester Fall Meeting of members of IRE and RMA Engineering Dept., Sheraton Hotel, Rochester, N. Y.

Nov. 29-Dec. 1: Conference on electronic instrumentation in nucleonics and medicine, sponsored by IRE and AIEE, Engineering Societies Building, New York City. Nov. 29-Dec. 4: 18th National Exposition of Power and Mechanical Engineering, Grand Central Palace, New York.

DEC. 10-11: Southwestern IRE Conference, Baker Dallas, Texas.

Symposium 10-12: on high-frequency measurements, held by Instruments and Measurements Committee jointly with the IRE and National Bureau of Standards, at Washington, D. C.

April 11-15: Sixth Western Metal Congress and Exposi-tion, Shrine Auditorium, Los Angeles, Calif.

May 16-20: Radio Parts Industry Trade Show and RMA Silver Anniversary Convention, Hotel Stevens, Chicago.

cisco audio engineers. The new speaker serves the range from 5.000 to 20,000 cps, operating above an ordinary tweeter, and is essentially nondirectional in both horizontal and vertical planes. It features a moving system of only 142 milligrams.

Navy Training by Television

EVALUATION and test of television as a vehicle for mass training of military personnel with a minimum of instructors is now under way at the Navy's Special Devices Center near Port Washington, Long Island. Weekly television lectures on naval science subjects are being telecast

eight miles to classrooms at the Merchant Marine Academy, Kings Point, N. Y., where one-fifth of the third-year c'ass will be taught two subjects by television. Other students will receive standard instruction, and results will be evaluated by the Psychology Department of Fordham University.

Plans call for a tryout of network television training before the end of the year, with lectures going out from Special Devices Center over existing and new coaxial lines and microwave relay facilities to Naval Air Reserve Stations at Squantum, Floyd Bennett, Willow Grove and Anacostia. In all these tests, tele-

(continued on p 212)




Newly-elected officers of the San Francisco Section of Audio Engineering Society are, left to right: Myron Stolaroff, Ampex Electric Corp.; Jack Mullen, Bing Crosby Enterprises; Harold Lindsay and Frank Lennart, Ampex; Don E. Lincoln, Audiophone; I. R. Ganic, Audiophone (chairman); Walter T. Selsted, Pacific Broadcasting; Dick Beck, C. C. Brown and Ross H. Snyder, KJBS-FM

MAGNETIC CIRCUIT BREAKERS

electro

Therefore they carry up to full rated current under all conditions.

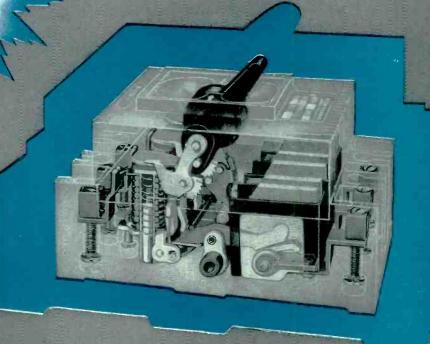They are manufactured with instantaneous trip or time delay.



Because they are entirely electromagnetic in action and do not depend on any thermal unit, HEINEMANN CIRCUIT BREAKERS will not trip before the current reaches the trip point specified. Whatever the surrounding temperature, the breaker will trip only on a load in excess of its rating.



HEINEMANN ELECTRIC COMPANY

97 PLUM ST.

TRENTON, NEW JERSEY

A lot of speaker in a little space



Western Electric 755A

TRY listening to the 755A first...then look at its size! You'll be amazed that so much performance can be packed into so little space.

Covering the frequency range from 70 to 13,000 cycles, the 755A gives brilliant tonal quality, faithful reproduction. Its 8-watt continuous capacity is ample for the general run of applications. And you ample for the general run of applications. And you get all this in a speaker only 83%" in diameter—only 434 pounds in weight!

Only 4-74 Poulles III 11-28.

Use the 755A in broadcast stations, wired music, program and sound distribution systems, home radios and record players.

You can get 755A's from stock in quantity. Call your nearest Graybar Representative—or write to Graybar Electric Co., 420 Lexington Ave., New York 17, N.Y.

-QUALITY COUNTS-



DISTRIBUTORS: IN THE U.S.A.

Graybar Electric Company. IN
CANADA AND NEWFOUNDLAND

Northern Electric Company, Ltd.

TUBES AT WORK (continued from p 122)

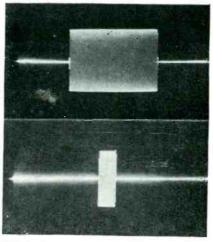


FIG. 4—Long exposure oscillograms showing signal pulse and gated response

parameters may be adjusted independently.

This circuit is sufficiently stable for close comparison of amplitudes, wave shapes and phase angles. Oscillator frequency drift is small enough to permit accurate measurements extending over 15 minutes or more. Operation of the receiver gate can be adjusted within a few microseconds. Figure 4 illustrates the quality of the transmitted wave packet and the gated receiver signal.

This work was supported in part by the Navy Department, Bureau of Ships, under Contract NObs-25391, Task No. 1.

REFERENCES

 E. L. Carstensen, Self-Reciprocity Calibration of Electroacoustic Transducers, J. Acous. Soc. Am. 19, p 961, 1947.
 F. Butler, Cathode-Coupled Oscillator, Wireless Engineer, 21, p 521, Nov. 1944.

(3) M.I.T. Radar School Staff, "Principles of Radar", Second Edition, McGraw-Hill Book Company, Inc., New York, 1946.

McGraw-Hill Book Company, Inc., New York, 1946. (4) M. V. Kiebert and A. F. Inglis, Multivibrator Circuits, Proc IRE, 33, p 534. Aug., 1945. (5) B. E. Phelps, Dual-Triode Trigger Circuits, Electronics 18, p 110, June, 1945.

1945.

(6) E. R. Shenk, Multivibrator; Applied Theory and Design, ELECTRONICS 17, p 136, Jan., Feb., and Mar., 1944.

Electronic Fuse


OCCASIONALLY situations arise in which it may be necessary to fuse a circuit when the current passing through the fuse does not exceed the normal current. A circuit which provides heat control by turning off and on a heating element may provide just such a situation. In case of failure of the control mechanism or of the contactor which opens and closes the

FOR RF HEATING— BETTER PERFORMANCE LONGER LIFE

ML-5668

(REPLACES TYPE 892 FOR ELECTRONIC HEATING)

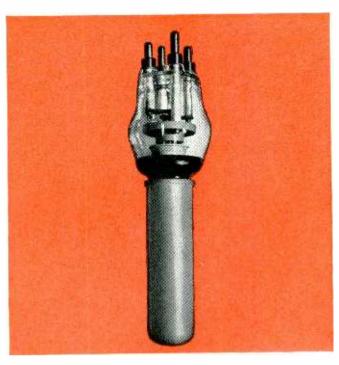AND UNIQUE MACHLETT AUTOMATIC SEAL WATER JACKET*



ML-5668—Water-cooled RF Heating Triode. With Machiett Automatic Seal Water Jacket is directly interchangeable with Type 892. Max. Input—28 kw. Max. Plate Dissipation—20 kw. For equivalent anode dissipation requires less than ½ water flow needed by the 892.



MACHLETT AUTOMATIC SEAL WATER JACKET. No tools needed to open and close this new jacket. No worry about tube breakage or water leakage. Jacket cannot be opened unless water pressure is off, nor closed unless tube is properly seated. Your hand opens and closes a perfectly safe seal with just a single twist.

THE new Machlett ML-5668 is of special and direct interest to every operator of electronic heating equipment using the 892 type of tube. The ML-5668, in combination with the Machlett Automatic Seal Water Jacket, is directly interchangeable with the 892 and its jacket, and, since it is designed specifically for this type of service, will provide greater effectiveness and increased economy on both induction and dielectric heating applications. RF heating requires the very best in tube design, construction, and processing, and the ML-5668, with its extra-heavy and uniquely-processed anode, its mechanically-sturdier grid, cathode and

terminal construction, truly meets the need. This tube, and those who use it, benefit fully from Machlett's advanced techniques of design and manufacture. For better, more consistent performance—for lower operating costs—for longer tube life—replace the 892 with the ML-5668.

The advantages offered by ML-5668 are also available to manufacturers and users of equipment employing other communication-type tubes, such as the 889A and 880, through the *new* Machlett Types ML-5604, ML-5619, ML-5666 and ML-5658. These RF heating tubes were designed, built and rated for electronic heating service, without compromise with the needs of other applications. For the complete story

of the improved performance and lower costs offered by these tubes, write Machlett Laboratories, Inc., Springdale, Connecticut.




Over 50 Years of Electron Tube Experience

MACHLETT LABORATORIES, INC.

Springdale, Connecticut




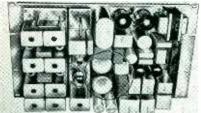

Common Carrier Terminal Chassis



Subscriber Coupling Unit

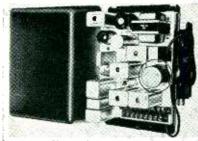

Subscriber Terminal Equipment

The Western Electric M1 Power Line Carrier Telephone System permits telephone service in thousands of farm houses having electric power service but no telephone wire line connections. It will help raise living standards in many rural areas.

Sigma Relays are used for three functions in this equipment, two of which are unusually exacting. By careful cooperative study of each application Sigma was able to work out solutions using highly refined but none the less conventional sensitive relays of standard Sigma design — available at comparatively low cost.

From vending machines to V-Bombs specialized relay design plus facility at solving problems involving circuit, relay and function enable Sigma to render valuable service.

SIGMA RELAY TYPES

A.C. - D.C. - POLAR
SENSITIVE - PRECISION - KEYING
SINGLE OR MULTIPLE CIRCUIT
From 686 to \$25.00 each!

Sigma Instruments, INC.

ensitive RELAYS
62 CEYLON ST., BOSTON 21, MASS.

circuit, the heating element will continue to raise the temperature above that desired, and may constitute a fire hazard.

An ordinary fuse will not provide protection against this hazard, since the current in the heating element has not changed appreciably from its normal value. Temperature sensitive devices may be too expensive or may not be desirable for other reasons.

In one electric blanket, a feeler wire is placed through the blanket that responds to temperature change, and this response serves as the basis for a control voltage. The control opens or closes a contactor to maintain the proper heating in the blanket. If the contactor fails to open at the proper time, some means must be provided to open the circuit to prevent excessive overheating.

Both the desired protection and comfort are obtained with a thyratron. The current carried by the tube when it is conducting is limited by the impedance in series with the tube, which need not necessarily affect the operation of the circuit to be fused.

When two cathode connections are provided in a thyratron tube, one side of the voltage supply can be connected to one of the cathode connections, and the other cathode terminal connected to the circuit, thereby making a lead inside the tube actually a part of the supply line to the circuit. The anode of the thyratron is connected to the other side of the supply voltage, the tube normally not conducting current and therefore not affecting the operation of the circuit.


The grid circuit of the thyratron is connected to the control circuit in such a way that as a fault occurs which would cause overheating of the element, the negative grid voltage on the thyratron is reduced to a point where the tube conducts. The tube current will be far in excess of the circuit current and will be sufficient to burn out one of the cathode connections, thereby opening the supply line to the heating element. Like any other fuse, the tube is rendered useless and must be replaced when the circuit fault has been corrected.

The GL-1367, a General Electric

Photomicrographics are only part of the story...

EVERY KNOWN TEST QUALIFIES WILBUR B. DRIVER ALLOYS FOR SUPERIOR INSTRUMENTATION!

Photomicrographic checking of grain size and quality of metals is only one of the exhaustive tests which Wilbur B. Driver resistance alloys are subjected to throughout production. There are many others including ASTM life, tensile strength, yield point, hardness, micrometer and thorough testing for resistance. These constant checks plus industry-old experience, are the reasons you can depend on all Wilbur B. Driver alloys to perform as specified. The alloys listed are so produced, and are especially recommended for instrumentation.

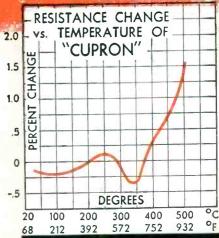

CUPRON:

FOR CONTROLS RHEOSTATS, ETC. LOW TEMPERATURE COEFFICIENT OVER A WIDE RANGE OF TEMPERATURE.

MANGANIN:


FOR METER AND INSTRUMENT SHUNTS.
LOW TEMPERATURE COEFFICIENT. LOW
THERMAL EMF AGAINST COPPER.





WILBUR B. DRIVER CO.

150 RIVERSIDE AVE., NEWARK 4, NEW JERSEY

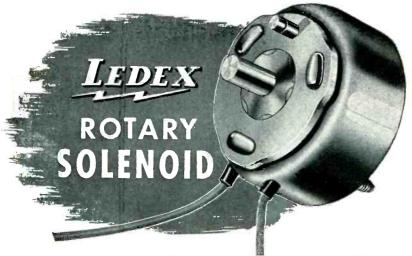

... solves remote control problems

he many production uses of Ledex Rotary Solenoids vary from actuating bomb releases in military aircraft to controlling hydraulic valves in heavy duty industrial material handling equipment.

Five Ledex Rotary Solenoid models are manufactured. Diameters range from 11/8 to 33/8 inches. Predetermined rotation up to 95°, either right or left, can be engineered to suit your production requirements. Starting torques for 45° of rotation range from 1/4 to 50 pound-inches.

Precision manufacture to exacting specifications and individual operating tests are your assurance of dependable, long-life service under severe operating conditions.

G.H. Seland INC.

Magnetic action moves the armature along the solenoid axis. This action is converted into a rotary motion by means of ball bearings on inclined races.



					MC	М
		_	10	Man	0)//	Di
42	Took .	Sol	69/1	10		To
(09)			PI	PI	1	LE
				1		W
2	5	6	7	8 =	A PERSONAL PROPERTY.	

MODEL No.	2	5	6	7	8
Diameter	1 1/8"	17/8"	21/4"	23/4"	33/8"
Torque LbInches	1/4	5	10	25	50
Weight Lbs.	1/6	1/2	1	21/4	41/4

G. H. LELAND, INC. 118 Webster Street, Dayton 2, Ohio	FILL IN
Send descriptive literature on the Ledex Rotary Solenoid. The Ledex Rotary Solenoid may be applicable to our	COUPON FOR
Product	FOLDER GIVING
Name(Please Print)	COMPLETE INFORMATION
Company	
Street Address	-

development, is designed specifically for such use. Two cathode connections are provided so that the series connection can be made in the circuit supply line, and the tube is designed to burn out this connection when the tube is operated directly across a 110-volt source. The cathode connections normally carry about 1.5 ampere.

Improving Performance of Milliwatt Relays

BY GENE HALPERIN Sands Point, N. Y.

Many relays of the sensitive polarized type operating on as little as one-half milliwatt have contact characteristics which make operation in aircraft or other mobile applications difficult. The causes for unsatisfactory operation are generally inherent in the physical design or a function of the high sensitivity of the relay.

Several milliwatt relays investigated for use in an airborne temperature control exhibited al-

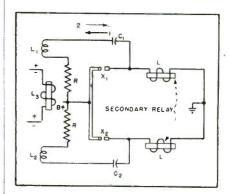


FIG. 1—Operation is improved by addition of coils L_1 and L_2

most a linear relationship between input current to the coil and contact-arm motion. Where the input signal is a slowly varying function, such as in a temperature control, this linearity can cause the moving contact to hover a few ten-thousandths of an inch away from the fixed contact.

Under these conditions any small vibration or variation in line voltage can cause a momentary closure of the contacts, but since there is not yet enough input to develop contact pressure, the moving arm when relieved of the disturbing force (vibration or voltage variation)

PLASTIC METAL

together, as stead-fast a team as

DAMON **PYTHIAS**

Below . . . A Clarostat Wire-wound Potentiometer and Rheostat Product shown thru courtesy of CLAROSTAT MANUFACTURING CO., INC.



CLAROSTAT CONTROLS SOLVE RESISTANCE PROBLEMS

In fact, as Clarostat states it, "Clarostat is interested solely in resistance. This specialization is reflected in the personnel and material engaged in Clarostat production. Every worker, machine, operation represents the end result of over a quarter-century spent in learning how to make quality resistors at mass-production prices.

Consolidated as a plastics production source, holds this company's precision requirements in highest regard ... for we, too, after many years of service have built our custom-molding reputation upon quality. For your products, too, some plastic may help metal components to behave best — perform best! We'd be glad for the opportunity to discuss the possibilities with you. Inquiries invited!

When Metal Controls are Anchored

Plastic maintains a strong - and goodlyinfluence over Metal . . . especially when designed as base structures for complex circuit assemblies.

in Plastic .- They Stay Put!

Modern mold development encourages product designers to specify in plastic the most involved arrangement of levels, channels, holes, slots and recesses . . . each precisionpositioned so that when the metal components are assembled, thereto, they fit like a glove!

NOTE PHOTOS HEREWITH

They indicate what proven molding techniques can accomplish in small space. Both bases shown actual size. Featured reference to letters "A" identify specially recessed channels for permanently positioning and accurately anchoring multiples of metal terminals ... Final assemblies are pictured at top of page.

Gonsolidated

MOLDED PRODUCTS Corporal 309 CHERRY STREET. SCRANTON 2, PA



PRODUCT DEVELOPMENT . MOLD DESIGN . MOLD CONSTRUCTION . PLUNGER MOLDING . TRANSFER MOLDING . INJECTION MOLDING . COMPRESSION MOLDING

ches: NEW YORK, 1790 Broadway . CHICAGO, 549 W. Randolph St. . DETROIT, 550 Maccabees Bldg. . CLEVELAND, 4614 Prospect Av. . BRIDGEPORT, 211 State Street.

MODEL

SPECIFICATIONS:

CARRIER FREQUENCY

RANGE: Continuously variable from 20 to 250 megacycles, in eight ranges.

ACCURACY: Crystal frequency standard permits setting to .01%. Dial scale may be set to 0.1%.

STABILITY: Warm-up drift less than .05%. LEAKAGE: Less than 10 microvolts.

MODULATION

Continuously variable from zero to 100%. ENVELOPE: Sinusoidal, or composite television. Bandwidth to 3 db is 4 Mc. Rise time from 10% to 90% modulation 0.15 microsecond. Overshoot less than 5%. Slope less than 5% on 60 cycle square wave.

INPUT IMPEDANCE: 75 ohms ± 10% (RMA Standard).

INPUT LEVEL: 1.5 volts peak to peak minimum level for 100% modulation. Black negative polarity.

MODULATION PERCENTAGE: Zero to 110%; plate modulation.

OUTPUT

LEVEL: Continuously variable from 0.3 microvolt to 0.1 volt balanced to ground (measured at 100% modulation-level). IMPEDANCE: (a) 107 ohms line to line (balanced)

- (b) 53.5 ohms line to ground (unbalanced).
- (c) Suitable pads may be employed to alter these impedances.

DIMENSIONS

MANUFACTURERS OF

Standard Signal Generators

Pulse Generators FM Signal Generators

Square Wave Generators

Vacuum Tube Voltmeters

UHF Radio Noise & Field Strength Meters

Capacity Bridges

Megohm Meters

Phase Sequence Indicators

OVERALL: Height-583/4"; Width-281/4"; Depth-251/2".

WEIGHT: Model 90-302 pounds. External Voltage Regulator 92 pounds. POWER SUPPLY: 117 voits, 60 cycles.


dental frequency modulation. Features: A self-contained crystal calibrator

frequency settings to a high degree of accuracy. A built-in video modulator with manual or automatic dc inserter, designed to operate from a standard RMA composite signal. Continuous monitoring is provided by built-in oscilloscope.

This signal generator meets the most exacting standards required for high definition television use.

ADDITIONAL DATA ON REQUEST



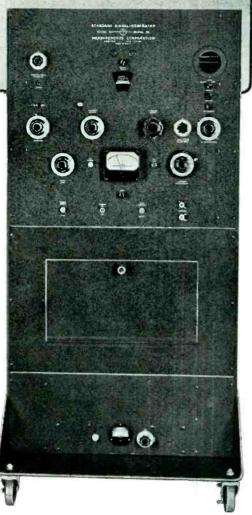

THE FIRST COMMERCIAL WIDE-BAND, WIDE-RANGE SIGNAL GENERATOR EVER TO BE DEVELOPED

The Model 90 employs a master oscillator, buffer amplifier and modulated power amplifier. The push-pull buffer eliminates inci-

and individually calibrated dial scales permit

TUBES AT WORK

(continued)

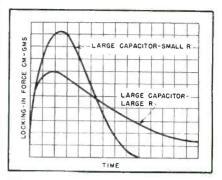


FIG. 2-Locking force as a function of RC

leaves the fixed contact drawing a small arc in the process. This arc maintains itself until the input is sufficiently high to develop contact pressure or until the arc causes welding of the contacts.

These arcs are of small, almost microscopic size and the welds would not be serious in a power relay. However, in sensitive relays, the arc generally passes enough current to cause chattering of the secondary relays with attendant intermittent operation of the control or indicating mechanism. In addition the welds cause shifts of the drop-out point. Some improvement may be effected by R-C suppressors used across the milliwatt relay contacts, but severe vibration will still cause unstable contact operation.

Figure 1 shows modifications made to a milliwatt relay, to make it more satisfactory for applications involving slowly changing quantities and severe vibration. The main winding of the sensitive relay is shown at L₃ connected to any source of d-c of reversible polarity, such as a resistance bridge.

Closing of Contacts

The movable armature carrying the two contacts X_1 and X_2 is connected to a source of voltage which operates the secondary relays when X_1 or X_2 make contact with their respective fixed surfaces. Coils L_1 and L_2 have been added to the relay and are located at the bottom of the coil form, underneath the main winding L_3 . The turns ratio of auxiliary to main winding was chosen as 1 to 10, but can be made greater or less in accordance with the individual requirements of the application.

While contacts X_1 are open, capacitor C_1 is across the d-c line

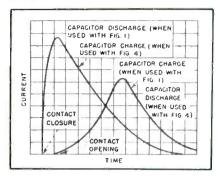


FIG. 3—Difference in charge and discharge action caused by secondary relay

through resistor R, auxiliary winding L_1 and the coil of the secondary relay L. It therefore assumes the potential of the voltage source. The first momentary contact between the surfaces of X_1 (even of a transient nature) allows the capacitor to initiate a discharge through the auxiliary winding L_1 , resistor Rand the closed contacts. The discharge has a current flow in the direction of arrow 1 and a magnitude fixed by the capacitance of C_1 , the emf of the voltage source, resistance R and the d-c resistance of the auxiliary winding. If winding L_1 is phased so that current in the direction shown by arrow 1 generates ampere-turns additive to those of the main winding, a transient locking impulse is achieved. The armature is immediately subjected to an additional mechanical force due to the increased ampere-turns and locks in tightly to its fixed contact.

The magnitude of the locking impulse and its duration are determined by the magnetic circuit and the nature of the typical exponential discharge of the R-C combination. By suitable selection of the three variables the transient mechanical force on the armature can be adjusted through a wide range.

Figure 2 shows various methods of operation based on variations of R and C and the resultant variations in transient locking force. It also shows that, for any fixed number of turns in each auxiliary winding, it is possible to get a large locking impulse for a short time or a lesser locking impulse for a long time.

The choice of variable will be dictated by the specific application but the chosen parameters should allow the exponential locking impulse to






WARD LEONARD ELECTRIC COMPANY RESISTORS - RHEOSTATS - RELAYS - CONTROL DEVICES

The Life of Your Product Hangs by a Thread!

Yes, your product's length of life in consumer service is determined to a large extent by the precision and strength of threads—the threads of screws, bolts, nuts and allied threaded fastenings used in its assembly.

The old adage "a chain is as strong as its weakest link" applies perfectly to the assembly of your product. Obviously, it can be only as strong, precise, efficient and enduring as its fastenings.

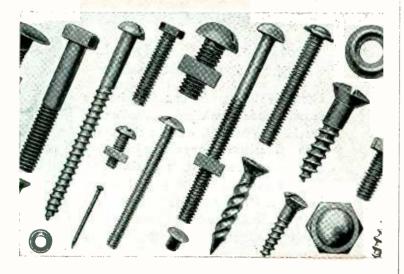HOLTITE Engineered Fastenings are precision-made to resist the loosening effects of vibration. Scientific processing and heat-treating of laboratory-selected materials assure strength far beyond ordinary demands. Under vigilant, skillful supervision these qualities of strength and precision are combined to produce fastenings that effect economies in application and permanance in performance.



The HOLTITE line comprises a complete range of dependable fastenings in all standard styles, sizes, finishes and heat treatments. Furnished with HOLTITE-Phillips Recessed Heads or slotted heads. SPECIALS made to order exact to your specifications, blue prints or samples.



fall to at least 10 percent of its initial value before it is time for the contacts to open. In other words, the shortest period of contact closure to be expected in any particular application will determine the maximum decay time of the transient impulse. This limitation is obviously necessary in order that the drop-out characteristics of the relay be unaffected by the presence of the additional transient ampere-turns.

Opening of Contacts

If the maximum decay time is made shorter than the smallest period of contact closure, the capacitor will always be in a substantially discharged condition by the time contacts X_1 break the circuit. Capacitor C_1 , resistor R and winding L_1 will again be subjected to the supply voltage and a charging current will flow in the direction of arrow 2. Without mechanical switching, a reversal of current flow has been achieved in auxiliary winding L_1 and a negative or kickout impulse will be applied to the armature.

The capacitor discharges exponentially on closure of X_1 but does not charge in the same manner because of the presence in the charging circuit of the highly inductive secondary relay coil. This action is illustrated in Fig. 3 where the discharge current rises almost as a step function (limited in rate of rise only by small inductances in the capacitor, wiring and coil L_1) and then falls exponentially to zero, while the charging current rises much more slowly to a maximum and then tapers off to zero.

Time Delay

A by-product of the circuit operation as described above is a finite amount of time delay in the opening of secondary relay L due to the charging current of capacitor C_1 which passes through the secondary relay coil L in the same direction as its normal closing current. This small delay in the opening of the secondary contacts is of considerable advantage in achieving stability in certain applications. Unfortunately, it is not always possible to achieve the desired amount of time delay when parameters are



for TELEVISION'S exacting applications

Designed for dependable operation up to 450 volts at 85°C. these new Sprague electrolytics are a good match for television's severest capacitor assignments. An extremely high stability characteristic is assured, even after extended shelf life, thanks to a special Sprague processing technique. Greatly increased manufacturing facilities are now available.

Your inquiries concerning these new units are invited.

DEPENDABILITY
TO MATCH THESE
NEW ELECTROLYTICS!
SPRAGUE PHENOLIC
MOLDED TUBULARS...

Highly heat- and moisture-resistant—
Non-inflammable—Moderately priced
Tonservatively rated for 40°C.
Operation—Small in size
cally rugged—Thoroughly field-tested
Write for Engineering Bulletin 210A

SPRAGUE ELECTRIC COMPANY . NORTH ADAMS, MASS.

SPRAGUE

Capacitors
Koolohm Resistors

PIONEERS OF

*T. M. Reg. U. S. Pat. Off.

ELECTRIC AND ELECTRONIC PROGRESS

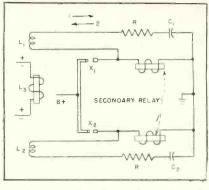


FIG. 4—Alternate circuit in which the charge and discharge actions are reversed from that of Fig. 1

chosen on the basis of locking and kick-out forces, but where such delay is beneficial and necessary, a compromise between locking force, duration and secondary time delay can usually be achieved.

The combination of R and C_1 constitutes a spark suppressor to reduce the arc across the contacts X_1 and X_2 , in addition to its other functions.

Alternative Circuit

Figure 4 illustrates an arrangement which can be used in extreme cases of inadequate relay operation. It enables auxiliary winding L_1 to utilize to full advantage the discharge of C_1 without any attenuating effects from the opposite side of the circuit. The auxiliary winding circuits are connected across the secondary relay coils. The action. of the transient network is now reversed from that shown in Fig. 1, since C_1 is discharged during the time that contacts X_1 are open and charges when they are closed, due to the line voltage which appears across the secondary relay coil.

The system operates as follows: When contacts X_1 close, the line voltage appears across the secondary relay coil. The rise of relay current lags due to inductance in the coil, but the voltage appears as a step-function. This causes a charging current to flow through winding L_1 , capacitor C_1 and resistor R in the direction shown by arrow 1. The fact that the rise of current lags in the relay coil does not delay the charging of C_1 since the capacitor draws its charging power from the line. As the capacitor reaches line voltage, current 1 is reduced to zero and remains



GRADE G-7-830 Phenolite combines high heat, flame and arc resistance. It is recommended for exacting low loss electrical applications and for insulation in transformers, motors, electric toasters and other applications subjected to elevated temperatures.

For full details call or write

NATIONAL VULCANIZED FIBRE CO.

WILMINGTON 99, DELAWARE
Offices in the Principal Cities





Columbus equipment reaches fires <u>faster</u> sped by 2-way *Motorola* Radio and Sylvania Lock-In Tubes

Those first few minutes are vital in fighting a fire!


That's why the Columbus (Ohio) Fire Department counts on Motorola 2-way FM to maintain constant touch between the dispatcher's office and 24 radio-equipped vehicles. Equipment returning to the firehouse can be instantly diverted en route—dispatched to the scene of a new alarm.

And where fires are potentially big enough to call for additional equipment to bring them under control, a radio message from the scene to the dispatcher's office has the extra vehicles under way within seconds!

For requirements like this, Motorola counts on Sylvania Lock-In Tubes to help maintain uninterrupted, efficient performance of its mobile units. These tubes stay firmly in place through jolting and jarring. They have few welded joints, no soldered ones. No warping of weaving of elements. Low loss, low leakage. See Sylvania Distributors, or write Radio Tube Division, Emporium, Pa.

SYLVANIAFELECTRIC

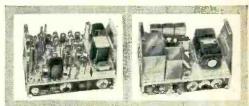Dispatcher's affice is in constant communication with vehicles at all times, directing them to the scene, checking on progress in bringing fire under control.



Mobile FM transmitting and receiving units built by Motorola, Inc., Chicago, and used in 24 vehicles of the Columbus Fire Department.

Superior mechanical and electrical features of Sylvania Electric's famous Lock-In Tube make it ideal for equipment on the road, in the air, on the rails—for marine radar, FM and selevition.



RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS

Whether MICROPHONE or SPECIAL AMPLIFIER

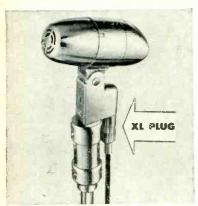


Photo Courtesy Electro-Voice, Inc.

Model No. 645 Broadcast Microphone made by Electro-Voice, Inc., Buchanan, Mich. used an XL Plug as standard disconnect equipment. This is only one of the several Electro-Voice microphones "XL"-equipped.



Photo Courtesy Brown Geophysical

Special amplifier used in oilfield geophysical exploration and survey by Brown Geophysical Co. of Houston, Texas uses K connectors for the circuits on this Amplifier equipment.

TYPE "K" Series is made in several

shell types, including the "RK", and

approximately 190 insert arrange-

ments among the 8 shell sizes for a

wide variety of wire sizes, including

zero until contacts X_1 open. The voltage across the relay coil decreases as its field collapses and the capacitor discharges with current flow 2.

The discharge current is in the same direction as the normal flow of relay current and can be made large enough to provide some delay in the drop-out time of the secondary relay where this is desirable. This arrangement is particularly advantageous in keeping the two halves of the circuit electrically isolated from each other. The charge and discharge of C_1 on contact closure and on contact opening is shown in Fig. 3.

Camera Shutter Timer

BY HUBERT SEAR

Mount Airy Road Croton-on-Hudson, N. Y.

Most of the existing camera shutter timing devices make use of the moving-film or the ballistic galvanometer principle. In the development of the instrument described here, however, these ideas were avoided because of their relative expense, the time element with the former, and the difficulty in construction of the latter.

This instrument requires no critical set-up procedure. A light placed behind the camera lens and the length of the flash transmitted when the shutter is snapped is measured. A photocell transforms this flash into an electric impulse which develops a voltage across the resistor R_1 as shown in the accompanying circuit diagram. This voltage is high enough to fire the neon bulb, which acts as a switch to the circuit $R_{\rm s}$, $R_{\rm s}$, developing a voltage across $R_{\rm s}$. One half of the 6SN7 is thus biased to a predetermined value making it conduct a constant known current.

When the light on the photocell is extinguished by the closing of the camera shutter, the firing voltage for the neon bulb is removed and it goes out. This interrupts the current in the bias resistor R_3 and the triode section is returned to a nonconducting condition. This arrangement eliminates the necessity of a light source of regulated intensity.

Once the neon light switch is

Plug-in with CANNON PLUGS



TYPE "XL" Series is two plugs and several receptacle types, with two insert variations of 3 and 4 contacts, 10 and 15-amp. Latchlock type connection.



For a survey of Cannon Plugs, write for the C-47 Condensed General Catalog, covering the 13 major type series and electrical specialties. . . Details on Type "K" are found in the K-945 Bulletin. Address Department K-120.

coaxials.





3209 HUMBOLDT ST., LOS ANGELES 31, CALIF.

WORLD EXPORT (excepting British Empire):
FRAZAR & HANSEN, 301 CLAY STREET
SAN FRANCISCO 11, CALIFORNIA

IN CANADA & BRITISH EMPIRE:
CANNON ELECTRIC COMPANY, LTD.
TORONTO 13, ONTARIO

November, 1948 — ELECTRONICS

NEW



with a range of TEN BILLION to ONE

Higher Accuracy

- Greater Sensitivity
- More Operating Conveniences

For Measuring Electrolytic Condensers • Testing Dissipation Factor of Transformer Bushings and Insulators • Measuring Dissipation Factor and Dielectric Constant of Solid and Liquid Dielectric Materials • General Electrical Machinery Insulation Testing • Product Control and Uniformity Production Checks on Materials Sensitive to Variable Electrical Properties

This new Type 1611-A Capacitance Test Bridge has many circuit and operating conveniences which make it highly adaptable to all sorts of capacitance and dissipation-factor measurements. Its enormous range of 1 micromicrofarad to 11,000 microfarads is achieved with the unusually good accuracy of $\pm (1\% + 1$ micromicrofarad) over the whole range. For dissipation factor measurements the range is 0 to 60% at 60 cycles, with an accuracy of $\pm (2\%$ of dial reading $\pm 0.05\%$ dissipation factor).

The bridge detector is composed of a single stage amplifier and an electronray visual null indicator. The detector is designed to be very sensitive when the bridge is at or near balance, but relatively insensitive when off balance.

A new zero-compensating circuit has been developed to provide marked improvement over previous bridges of this general type when making measurements below 1000 micromicrofarads.

For measurements on electrolytic condensers, a polarizing voltage, up to 500 volts, may be applied, from a grounded power supply if desired. Terminal capacitances of the power supply do not affect the accuracy of the bridge.

The bridge and its accuracy are unaffected by temperature and humidity variations over normal room conditions (65 deg. F. and 0 to 90% RH).

The ac-voltage applied to the capacitance under test varies from approximately 125 volts at 100 micromicrofarads to less than 3 volts at 10,000 microfarads.

This bridge combines all of the principal operating features of our popular Type 740-B and Type 740-BG bridges but improves the performance of each in most of their important characteristics.

TYPE 1611-A Capacitance Test Bridge...\$375.00
WRITE FOR COMPLETE INFORMATION

GENERAL RADIO COMPANY

Cambridge 39, Massachusetts

90 West St., New York 6

920 S. Michigan Ave., Chicago 5

950 N. Highland Ave., Los Angeles 38



efficient than any rosin flux-yet NON-CORROSIVE • NON-CONDUCTIVE



ACTIVITY "Resin-Five" will solder zinc, brass, nickel silver, nickel-plate, copper and ferrous alloys

STABILITY Under the most extreme soldering temperatures the Flux still does the soldering job.

MOBILITY The unusual activity and stability of "Resin-Five" give it complete mobility.



KESTER "RESIN-FIVE"

The most important development in Cored Solder within the last ten years. "Resin-Five" has virtually no odor even at extreme temperatures. Available in 5 core sizes; varying percentages of flux content. Diameters ranging from .010" to .250". All practical alloys.

KESTER SOLDER COMPANY


4204 Wrightwood Ave., Chicago 39, Ill. Factories Also At

Newark, New Jersey . Brantford, Canada

KESTER SOLDER

A COMPLETE TECHNICAL SERVICE

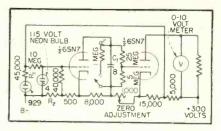Any soldering problems? Consult our Technical Department. No obligation to you.




Schematic diagram for electronic shutter timer. The 0-10 voltmeter shows shutter time directly in seconds


closed, a constant bias is applied to the triode regardless of the size of the photocell current. Therefore the magnitude of the plate current is constant for as long as it is permitted to flow by the light flash. The voltage drop across the plate resistor charges capacitor C. This charging proceeds slowly because of the long time constant of this R-C circuit. In usual operation the capacitor is never completely charged. When the plate current is extinguished, the capacitor slowly discharges through the plate resistor causing a voltage to appear across it, proportional to the charge. Since the charge depends on the duration of the charging pulse, the voltage across the capacitor is proportional to the duration of that pulse, or the duration of shutter opening. This discharge voltage is taken from part of the plate resistor and applied to the grid of the second half of the 6SN7 used as a d-c amplifier. A voltmeter in this plate circuit indicates shutter speed directly in seconds.

The grid voltage for this last stage is not taken across the whole plate resistor since such a high resistance in the grid circuit would cause appreciable drifting due to the grid current. If adjusted correctly with the values shown, sufficient voltage may be obtained across part of this resistor without appreciable grid current effect. Grid current in the first stage prevents the use of this R-C circuit in its grid. Three selenium rectifiers are used in a voltage tripler circuit to furnish the high voltage (about 300 volts) which is necessary for proper biasing of the d-c amplifier. An ordinary gooseneck desk lamp has been used satisfactorily with the unit described.

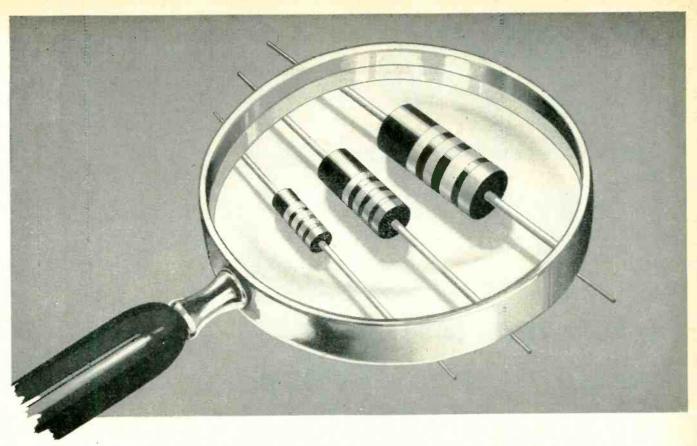Because of tube variables and other changes common with d-c



BRADLEYUNITS

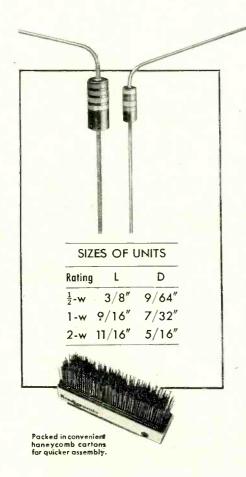

½ WATT • 1 WATT • 2 WATT Small in Size • Big in Wattage

Bradleyunits are so small for their ratings that we can't picture their exceptional capacity... without magnifying them. So here they are... available in all standard R.M.A. values, as follows:

½-watt rating—10.0 ohms to 22 megohms

1-watt rating — 2.7 ohms to 22 megohms

2-watt rating - 10.0 ohms to 22 megohms

Bradleyunits will operate at full rating for 1000 hours at 70 C ambient temperature with a resistance change of less than 5%. They require no wax impregnation to pass salt-water immersion tests and have high mechanical strength and permanent characteristics. Let us send you a complete Allen-Bradley resistor chart.

Allen-Bradley Co., 110 W. Greenfield Ave., Milwaukee 4, Wis.





AMERICAN PHENOLIC CORPORATION
1830 SOUTH 54TH AVENUE, CHICAGO 50, ILLINOIS
COAXIAL CABLES AND CONNECTORS • INDUSTRIAL CONNECTORS, FITTINGS AND
CONDUIT • ANTENNAS • RADIO COMPONENTS • PLASTIC FOR ELECTRONICS

amplifiers, the zero point must be reset about once a day. A low resistance R_L is also included to be switched in parallel with the high resistance of the R-C circuit so that the meter needle may be returned to zero more quickly than the natural discharge would allow. A type 929 photocell is used in preference to the higher output gas types because the speed of response is better.

Although the accuracy of the device is good enough for shop work, the difficulties inherent in d-c devices using vacuum tubes make it inadvisable for more exacting applications. Furthermore, due to the dependance on an R-C combination, the range is limited. Shorter time constants would cause the meter to move too fast to be read. The combination shown may be used from about 1/10 to 1/350 second.

A more versatile device now under consideration has an extended range and is an a-c instrument and therefore not subject to the inaccuracy of a d-c amplifier and hence is more suitable for the laboratory. It is, however, less suitable for a repair shop because it is also more expensive. An r-f oscillator suitably isolated and crystal stabilized, feeds its output to a scaling circuit through a gating tube. The impulses are gated by the photocell voltage. The number of impulses passed is a function of the time the light is passing the opened shutter. They are counted and scaled down by the scaler and may be indicated in any suitable The range of speeds manner. measurable is limited on one hand by the frequency of the oscillator, and on the other by the capacity of the scaler. Both may be extended almost indefinitely with circuits now available.

Telecontrolled Clocks

CLOCKS connected directly to the 60-cycle line are self-regulated electronically without special clock wiring in a development by International Business Machines Corporation. Each clock is checked individually and automatically once an hour for uniformity with the system time. Should any of the clocks be out of step, owing to a current interruption, they will be corrected



-better readability


D-C AMPERES GENERAL 🍘 ELECTRIC

MPROVED SCALE DESIGN

ON NEW THIN PANEL INSTRUMENTS

The new General Electric thin panel instruments have been designed especially for easy reading. Arc lines have been eliminated to make scale divisions stand out by themselves. New lance-type pointer gives precise indications. Restyled figures are bigger, and shaped for maximum legibility. A mask covers distracting mechanism at base of pointer. And, notice the scale as a whole. All extraneous printing has been removed. You can be sure of quicker, more accurate readings with these new Type DO-71 instruments, as proved by tests before large audiences.

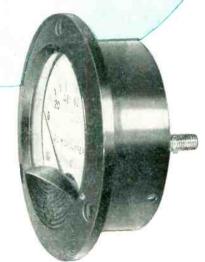Greater sturdiness, more reliable operation, and longer life are assured by the internal-pivot construction, temperature compensation, and other features described more fully in Bulletin GEA-5102. Write for your copy today. Apparatus Department, General Electric Company, Schenectady 5, N.Y.




Also available as a-c ammeter, a-c wattmeter, d-c voltmeter, d-c ammeter, temperature indicator, power-factor meter, synchroscope, and frequency meter.

GENERAL (\$



ELECTRIC

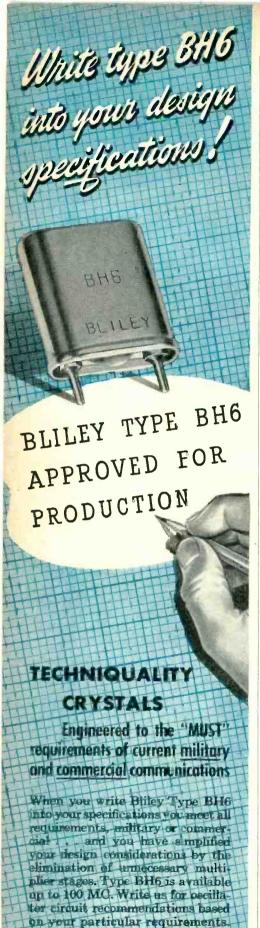


LILEY ELECTRIC COMPANY

UNION STATION BIDG. ERIE PA

TUBES AT WORK

(continued)

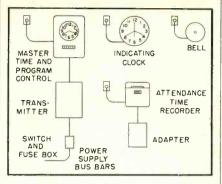

Electronic system for synchronizing clocks, signal units, time stamps and recorders

once an hour up to 59 minutes slow and 55 seconds fast.

The new system would be a convenience to industrial concerns, schools, and hospitals.

In the new system, a master time control is installed and operated from the same alternating current to which the indicating clocks are connected. This control is the director of the entire system and keeps all units in agreement with it. Every hour electronic tube action in a transmitter at the control sends a supervisory impulse out over the power lines. A simple electronic receiver in each indicating clock accepts the impulse. If the clock is slower or faster than the master time control, it corrects itself once each hour automatically. If the clock is in agreement to the second to the master control, it continues to function as an independent clock. Thus, without special wiring, all clocks in a building show the same time.

This IBM system also permits automatic signaling, sounding of bells, horns, buzzers, gongs, or chimes, through the program unit of the master control, without special signal wiring. These signals are also fed to the line to actuate the electronic receivers when an impulse is released to them. Three different schedules of signals may be sounded without special wiring. Self-regulating minute impulse units, attendance time recorders, job cost recorders and time stamps, are operated by the system through use of an adapter. This adapter is connected to the line to receive the hourly corrective impulse sent out by the transmitter. After verifying its own agreement with the time of the master time control, the



RAILWAY EXPRESS offers you a complete transportation package. Around its nation-wide facilities is built a convenient, economical shipping service including door-to-door pick-up and delivery in all principal cities and towns at no extra cost. It is designed to meet every one of your business or personal shipping requirements.

Your shipments are carried swiftly over America's railroads and scheduled airlines—providing an all-inclusive service for a single charge. Consistent improvement in equipment and methods is your assurance of a continued, dependable, coordinated shipping service to you, your community and the nation.




November, 1948 — ELECTRONICS

HOW Resistance-Voltage Characteristics are altered by Resistor Design

Here are negative resistance-voltage curves plotted for two GLOBAR type BNR RESISTORS. Both resistors are voltage sensitive. However, the two curves coincide at one point only, namely, 30 volts. But, of more importance, observe how the difference in resistor design drastically alters its characteristics. Note the effect a change in the shape of the resistor has on the slope of its resistance-voltage curve. Fundamentally, this change in characteristics is accomplished by altering the specific resistance of the resistor.

Graphically presented here, this variance in characteristics—caused by resistor design points up an important factor in specifying and ordering GLOBAR resistors to meet exact needs of specific applications. It is a good reason why GLOBAR resistors are not carried in stock, but are quickly made to your requirements.

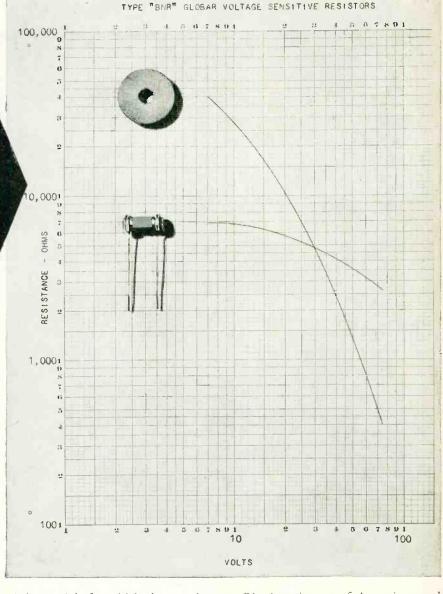To save time and trouble in producing for you voltage sensitive resistors that



will do the job for which they are intended, we ask only that you furnish a few simple facts. Briefly tabulated, this necessary information is:

- 1 Type of apparatus in which the resistors are to be used.
- 2 Method of mounting and space limitations.
- 3 Normal operating voltage and peak voltage if available.
- **4** Resistance and inductance of the circuit if available.

- 5 Ohmic resistance of the resistor and allowable plus and minus tolerance.
- 6 Maximum voltage applied continuously or intermittently.
- 7 Duration of load and elapse of time between its application.

For your engineering tests, we can furnish samples in a hurry. For any information that may be helpful in working out your resistor problems, write Dept. V-108, The Carborundum Company, GLOBAR Division, Niagara Falls, N.Y.



GLOBAR Ceramic Resistors BY CARBORUNDUM

"Carborundum" and "Globar" are registered trademarks which indicate manufacture by The Carborundum Company

adapter then proceeds to verify the agreement of the minute impulse units with itself and to correct any variations from accurate time which might have occurred in them during the preceding hour.

Sound Flashlight for the Blind

BY VICTOR TWERSKY


Technical Adviser, Guidance Device Project
Biology Department
Gity College of New York
New York

VARIOUS obstacle-detecting devices to aid the blind in foot travel are being studied by research laboratories. A group of students from the City College of New York have developed a relatively simple "sound flashlight" which has proved successful in aiding sightless persons to detect and avoid objects in walking which might otherwise be discovered by collision.

Similar in size and shape to a large flashlight, the unit is carried by the blind person with a scanning motion. Sound waves projected from the unit in a narrow beam are reflected by solid objects, and the reflected sound warns the user of the object's presence.

The heart of the unit is a single-tube oscillator powered by hearing-aid batteries. The circuit is shown in the accompanying schematic diagram. A headphone unit was chosen for the transducer, and its inductance in conjunction with the 0.002- μ f capacitor form a resonant circuit for the desired frequency range between 8 kc and 15 kc.

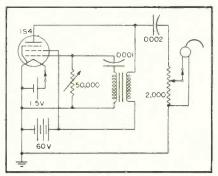The choice of this range of frequencies was guided by the consideration of reflection and interference from ambient noises which might be encountered out of doors. It was found advisable to make the frequency adjustable to allow



Complete circuit of the obstacle-detecting oscillator



SPECIFICATIONS

BALLANTINE MODEL 300 ELECTRONIC VOLTMETER

RANGE: .001 to 100 Volts, r.m.s. (.00001 to 10,000 Volts, with accessories)

ACCURACY: ±2% at any point on the scale.

FREQUENCY: 10 cycles to 150,000 cycles.

STABILITY: Permanent calibration unaffected by variation in line voltage, tubes, etc.

METER: Logarithmic Voltage scale and uniform decibel scale.

AC OPERATION: Will operate on 105-125 Volts, 50-60 cycles. (Battery operated models also available)





MODEL 220 DECADE AMPLIFIER



MODEL 402 MULTIPLIER

The Model 300 Voltmeter is a valuable tool for measurements in communication and "weak current" engineering. Its unusual sensitivity, accuracy and stability make it ideal for work in the audio, carrier, and supersonic ranges. Logarithmic meter indication assures uniform accuracy of reading over the whole scale while permitting range switching in decade steps. There is but one scale to read for all ranges. Output jack and output

since 1935

the only VOLTMETER

featuring a simplified

LOGARITHMIC

SCALE

MODEL 300

ELECTRONIC

VOLTMETER

gain stable amplifier,
Accessories include Model 220
Decade Amplifier, which supplies
standardized gains of 10x and
100x, and the Model 402 Multipliers which supply additional
ranges of 1,000 and 10,000 Volts.

control are provided so that the voltmeter can be used as a high-

Descriptive Bulletin No. 12 Available

BALLANTINE LABORATORIES, INC.

BOONTON, NEW JERSEY, U. S. A.



ELECTRONICS - November, 1948



Fishing reel gears must operate smoothly at a speed of 3000 revolutions per minute or more, when a cast is executed. These gears must also withstand the strain of hauling in a fighting fish of unpredictable size and strength, thus rendering a dual purpose: speed and velvety smoothness in one direction—strength and durability in the other.

Instruments and machines have individual gear problems. For over a quarter of a century, Quaker City Gear Works has solved thousands of them and produced millions of gears of every description up to 60" in diameter for manufacturers in many diversified industries.

Aircraft controls, dental drills, electric clocks, gauges, indicators, heat controls, machine tools, radar, radios, washing machines and motion picture projectors are but a few of the many conveniences of modern progress which depend upon the heartbeat of Quaker City Gears. Your gear problem is our business, our large productive capacity is at your service.

YOUR INQUIRIES WILL RECEIVE PROMPT ATTENTION

The heart of the Outdoorsman Castomatic reel illustrated above is but one of many gear trains developed by our engineers and produced in our fully equipped plant.

uaker City Gear Works

1910 N. Front Street, Philadelphia 22, Pa.



In appearance, the sound flashlight resembles the conventional type

changes for different conditions and for relief of ear fatigue. Experimenters noticed that sound at frequencies below 10 kc attracted considerable undesired attention from bystanders.

Beam widths between 12 and 30 degrees (depending on frequency) are possible with the reflector which is 4 inches in axial length and 4 inches in diameter at the mouth. The reflector is made of spun aluminum covered with papier maché.

The headphone transducer is mounted at the focal point of the reflector. It is insulated from the metallic reflector by a layer of sponge rubber and held in place by rubber cement and papier maché. A male plug is embedded in the rear of the horn for connection of the extension cord from the oscillator which is carried in a pocket.

To reduce the intensity of the sound reaching the user caused by leakage around the rim, baffles of cotton and sponge rubber are used with only slight reduction in the intensity of the main lobe.

Although the sound flashlight was designed primarily as an obstacle detector, skilled operators


SPECIFY THIS TUBE for h-f heating equipment to do these jobs—

Seal, stitch, and join plastics and various other substances

Braze—quick-solder—set glues by heat conduction

Surface-harden or anneal small metal parts

Defrost and cook foods electronically

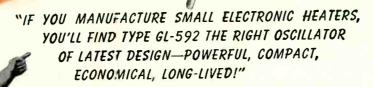

Naturally you want to profit from the zooming demand for electronic heaters for high-speed repeti-

tive work. And knowing it's the oscillator tube that makes or mars performance, you intend to be extra-careful about tube high frequency—ample capacity in watts—reliability that users can bank on—availability you can bank on!

These qualities are packaged in Type GL-592. The tube already is in service, helping to speed plant output. Stocks are on hand to meet your requirements, and sockets, grid connectors, finned anode connectors, all are available. Specify and install... there'll be no lag between the two!

That high frequency ceiling (150 mc at full ratings) means Type GL-592 will handle easily the up-to-70-mc requirements of bench dielectric heaters, not to

mention lower-frequency induction work: The tube carries substantial plate ratings, and if still more power is desired, a pair or two pairs may be employed without prohibitive increase in cost or size of the equipment. Conversion efficiencies above 70 percent are routine for the GL-592 in properly designed circuits. Cooling calls for merely an 8-inch household-type fan, or a small and inexpensive pressure blower.

The tube is sturdy—cathode, grid, and anode are solidly mounted and braced. All leads are short. Fernico metal-to-glass seals mean (1) no cemented caps or bases with the dielectric losses these entail, (2) no soft-soldered leads or terminals to come loose.

Get further facts about this modern, efficient, tough triode—including the favorable price—from your nearby G-E electronics office! Or wire or write Electronics Department, General Electric Company, Schenectady 5, New York.



GL-592 Power Triode

Ratings, Class C Power Amplifier and Oscillator

ana Oscillator				
Filament voltage	10 v			
current		5 amp		
Max ratings:	CCS	ICAS		
d-c plate voltage	3,500 v	3,500 v		
d-c grid voltage	_500 v	_500 v		
d-c plate current	250 ma	350 ma		
d-c grid current	50 ma	100 ma		
plate input	670 w	1,000 w		
plate dissipation	200 w	300 w		
Type of cooling forced-air				
Frequency at max ro	150 mc			

The G-E line of power triodes for electronic heating is complete, covering every need and application. Tube types range in max plate voltage from 2,000 v to 20,000 v—max current, from 250 ma to 10 amp—max dissipation, from 125 w to 100 kw. Prices and details on any or all types will be supplied at your request.

GENERAL



ELECTRIC

FIRST AND GREATEST NAME IN ELECTRONICS



MOSINE

"More than Paper"


In the field of electronics and the electrical goods industry, MOSINEE stands for paper-base processing materials with scientifically controlled chemical and physical properties, high quality standards and dependable uniformity... with good dielectric strength, high tensile or tear strength; proper softness or stiffness; creped with controlled stretch or flexibility; specified pH for maximum-minimum acidity or alkalinity; accurate caliper, density, liquid repellency or absorbency... or other technical characteristics vital to your quality standards and production requirements.

MOSINEE PAPER MILLS COMPANY · MOSINEE, WIS. "Essential Paper Manufacturers"


have been able to detect slight depressions by directing the beam so that it makes an angle of about 60 degrees with the ground. The device is most successful, however, in detecting such obstructions as trees, lamp posts, parked vehicles, hedges, flights of stairs leading up, and open doorways.

Preliminary tests showed that detection was possible at distances up to and greater than 30 feet, depending on the number of obstacles present, the prevailing acoustical conditions and the user's experience and proficiency.

RADAR-EQUIPPED LINER BERTHS IN FOG

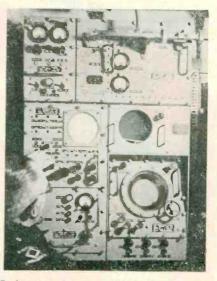

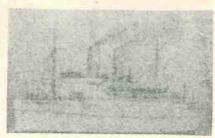Radar installation in iron hutch atop navigation bridge of 20.000-ton Canadian Pacific line's "Empress of Canada" with plan position indicator screen just above operator's head. Repeater tube is located on navigation bridge for use by captain and pilot, who keep in contact with the trained radar operator by telephone when interpretation of complex patterns is required



View of "Empress of Canada" running into fog in the Mersey. This ship recently came into Liverpool harbor in total fog and reached her berth entirely by radar. The landing stage could be seen by the crew only after they had gone half-way down the gangplank. The ship is fitted with British Admiralty type 268 radar



We've got our eye on your assembly line

... to help you speed production

When we build cabinets, housings or enclosures for you, we plan and work with the objective of saving you time, labor and extra operations on your production line.

Karp-constructed units are handsome and streamlined, but their beauty is more than skin deep. The extra value our work affords is a degree of quality, accuracy and precision that will speed up your assembling operations.

You will find all units completely uniform in every detail, all measurements exact, all holes the right size

and cleanly drilled, all openings precisely spaced, all welding skillfully done with finest equipment.

As a result, in your assembling, all functional parts, instruments and controls will fit correctly and easily into place Installation operations will be smooth and speedy. You will encounter no delays for any completion details. This saving of time and labor will cut your costs. Your completed assemblies will have added market value, too. In short, Karp custom craftsmanship will prove less expensive in the long run.



KARP METAL PRODUCTS CO., INC.

215-63rct STREET, BROOKLYN 32, NEW YORK

Custom Craftsmen in Sheet Metal



as Zuickly as Simply

change Cartridges in Astatic's FL-33 PICKUP to switch from Microgroove to 78 RPM RECORDS

No tools needed . . No changing of needle pressure . . Nothing else to do!



UNPARALLELED quality of reproduction of Columbia Microgroove Records is not the only advantage of Astatic's FL-33 Pickup. This new achievement of Astatic precision manufacture offers superior utility and convenience as well. Produced to Columbia's own specifications, its LP-33 Crystal Cartridge is easily, instantly replaceable with the new LP-78 Cartridge for playing conventional 78 RPM Records. No tools are needed, no adjusting of needle pressure, there is nothing else to be done. Identical in appearance, the cartridges are designed for insertion in the FL Arm on the same slip-in principle with which the modern fountain pen secures itself in its cap. The LP-78 Cartridge has a permanent sapphire needle with .003-inch tip radius, as compared with the .001-inch tip of the LP-33. Check the accompanying detailed features. Write for further information.


FEATURES OF ASTATIC'S FL-33 PICKUP

- 1. Five-Gram Needle Pressure.
- 2. Permanent Sapphire Needle with .001" Tip Radius.
- 3. Approximately One-Half Volt Output.
- 4. Frequency Range 30 to 10,000 c. p. s.
- 5. Novel Design at Base Eliminates Tone Arm Resonances and Assures Perfect Tracking.
- LP-33 Cartridge for Microgroove instantly replace-able in FL Arm with LP-78 Cartridge having .003 radius needle for playing 78 RPM Records. Both simply slip into position, no tools needed, NO CHANGING OF NEEDLE PRESSURE.



THE ELECTRON ART

(continued from p 126)

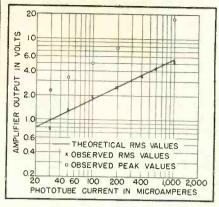

Agreement of observed and theoretical rms noise voltages indicates that, over the measured range, shot effect is the only important contribution to the noise output of vacuum phototubes

statistics, which gives $\delta = N_0^{-1/2}$ where N_o is the average number of electrons emitted in the interval T seconds. The mean fluctuation A is equal to the product of the mean relative fluctuation and the average number of electrons emitted during the interval, or $\Delta = N_0^{1/2}$. This result implies that the random variation in phototube current (noise) is proportional to the square root of the phototube current, if every electron that is emitted by the cathode reaches the anode.

When a phototube provides the input signal to an amplifier, the output of the amplifier consists of the shot noise from the phototube and the thermal noise from the input resistance of the amplifier, assuming that subsequent stages in the amplifier contribute relatively negligible noise. If the characteristics of the amplifier are known, the noise contribution of the phototube can be calculated from the measured noise output.

Effect of Amplifier

The mean-square voltage across the output terminals of an amplifier is given by3

$$V_{\scriptscriptstyle N}{}^{\scriptscriptstyle 2}=\,2ei\,\int_{\scriptscriptstyle 0}^{\scriptscriptstyle \infty}\,Z^{\scriptscriptstyle 2}G^{\scriptscriptstyle 2}df$$

in which V_N is the rms noise voltage, e the change on an electron $(1.59 \times 10^{-19} \text{ coulomb}), i \text{ the photo-}$ tube current in amperes, Z the phototube coupling impedance in ohms, G the voltage gain of the amplifier, and f is frequency in cycles per second. Inasmuch as G is a function of frequency, this

STUPAKOFF KOVAR-GLASS TERMINALS

Give Permanent....

Hermetic....Pressure-tight Seals

Stupakoff hermetic seals are the answer where proucts must have permanently vacuum- and pressuretight insulated electrical lead-ins. They seal against atmosphere, dirt, dust, fungus, and other foreign substances that normally cause failures.


Available from stock or specially made to suit your needs, Stupakoff metal-glass seals can be supplied with single or multiple, hollow or solid electrodes.

The metal Kovar is available in sheets, rod, wire, thing and special shapes for manufacturers having working facilities.

We will gladly send literature, recommendations and prices on your hermetic seal requirements. Write today.



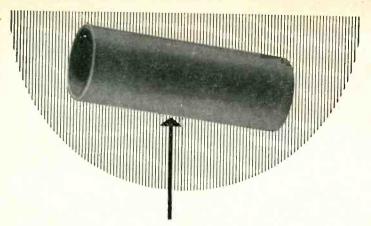LATROBE, PENNSYLVANIA Cable Address: Stupakoff, Latrobe, Pa.



WANT TO MAKE SOMETHING OF IT?

Pictured above is a tube of Taylor Laminated Phenol Fibre, just as it comes from our production line.


Pictured below is a coil form . . . quickly fabricated from this same tube, Note the precision of the punching and threading.

Sheets, rods, and tubes of Taylor Laminated Plastics possess so many properties, physical and electrical, of interest to industry . . . and adapt themselves to such a variety of fabrication processes . . . that their usefulness grows and grows and grows.

If you want a dependable source of supply for Phenol Fibre, Vulcanized Fibre, or special laminates . . . or if you're interested in having completed parts or sub-assemblies delivered on schedule at your plant . . . get in touch with Taylor. Send a sketch or blueprint, if you will, and we'll tell you exactly what we can do for you. Expect plenty; you won't be disappointed.

TAYLOR FIBRE COMPANY

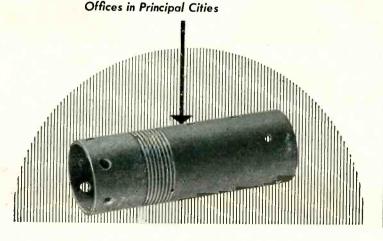LAMINATED PLASTICS: PHENOL FIBRE - VULCANIZED FIBRE - Sheets, Rods, Tubes, and Fabricated Parts
NORRISTOWN, PENNA.
Pacific Coast Plant: LA VERNE, CAL.



equation indicates that the noise output is proportional to the square root of the amplifier bandwidth. The noise due to the amplifier can

Effective Noise Bandwidth of Tuned Amplifiers		
Number	Bandwidth	
of stages	factor	
1	1.57	
2	1.22	
3	1.15	
4	1.13	
5	1.11	
6	1.10	
infinity 1.06		

Effective noise bandwidth of an amplifier consisting of cascaded, independent, identical, single-tuned pentode stages is the product of the overall half-power bandwidth of the amplifier and the above bandwidth factor for the appropriate number of stages


therefore be reduced by making the pass band of the amplifier as narrow as other design considerations permit.


Usually in computing the noise contribution of an amplifier, the bandpass characteristic, including the skirts out to -6 db of the midband transmission, is measured and the frequency-gain area corresponding to a rectangular bandpass obtained to simplify the calculation. A rigorous approach' shows that the noise bandwidth equals the overall half-power bandwidth of the amplifier times a factor which is a function of the number of stages, as given in the table. This bandwidth factor accounts for the skirt shape and indicates that increasing the number of identical stages, up to about three stages, produces an appreciable reduction in equivalent noise bandwidth for circuits of fixed selectivity. On these considerations an amplifier consisting of three tuned stages with a cathode follower output was built. A peak gain of approximately $9 \times 10^{\circ}$ at 395 kc was obtained.


Experimental Method

The input circuit to the amplifier consisted of the phototube and its load resistor in parallel with the amplifier input impedance. The coupling impedance Z was measured to be 21,000 ohms to within 5

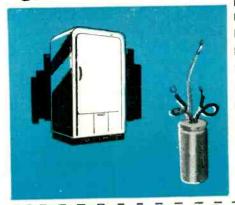
YOUR PRODUCT, TOO CAN BE RADIO NOISE-PROOFED WITH C-D Quietones REG. U.S. Pal. Off.




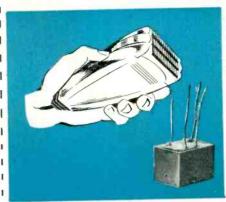

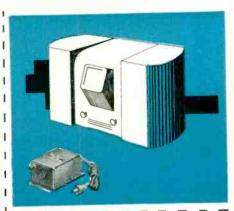



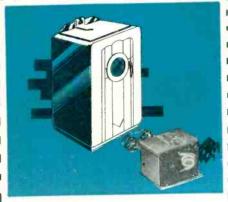

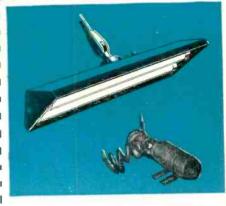

When we say Radio Noise-Proofed-we mean Radio Noise-Proofed. It's no trick at all to build a filter with high attenuation at 150 kc or 100 mc . . . but to build one which filters at 150 kc and 100 mc-as well as all points in between-is a horse of a different color. We know because we've done it. It is only one of hundreds of available types of C-D Quietones designed for all standard requirements.

Among these stock types there may be one which will bring the interference level of your product down to the level of a rabbit's bark. If not, we invite you to make full use of our Radio noiseproofing laboratory and our engineers for the development of a unit designed for your specific needs.

Your inquiries are cordially invited. Address: Cornell-Dubilier Electric Corporation, Dept.K-11, South Plainfield, N. J. Other large plants in New Bedford, Worcester and Brookline, Mass., and Providence, R. I.

> Make Your Product More Saleable With C-D Quietone Radio Noise Filters and Spark Suppressors



1948

. ELECTROLYTIC





An Electrical Relay, whatever its style or type, responds to a changing condition in one electrical circuit to cause a change in another electrical circuit.

Wherever electrical energy is used as a controlling agent, SIGNAL ENGINEERING Relays can be applied in a wide variety of uses.

Perhaps you have an electronic circuit where a change in voltage or current requires the switching of several other circuits. The SENSITIVE MULTIPLE CONTACT PLUG-TYPE RELAY, illustrated at right, is

designed to meet just such a condition and

offers up to 6 pole, double throw, with a 20 point plug. A.C. or D.C. Ask for Bulletin 50-6.

OR

A keying circuit or pulsing circuit where rapid response and low current drain are required characteristics. The SERIES

10 AND SERIES 20 RELAYS are fast, sensitive, shockproof and are adaptable to many contact arrangements. Bulletin KR1-6.

OR

The need for a small, rugged, POWER RELAY, double pole, double throw, without pigtails, for operation of bells, horns, lamps, small motors, etc. Write for Catalog 6-6.

OR

An application requiring a high frequency COAXIAL CABLE RELAY, with correctly designed, low loss circuit, available with A.C. or D.C. actuating coils. Bulletin CR1-6.



154 WEST 14th ST.

NEW YORK 11, N. Y.

THE ELECTRON ART

(continued)

percent; this impedance can be considered constant over bandwidth.

The phototube used in these measurements was a GE 1P24. Several tubes were tested and little difference between them was found.

The output voltage from the amplifier was measured by two methods: a vacuum thermocouple with a 3,000-ohm resistor in series indicated the rms value of the output, while a vacuum-tube voltmeter was used to measure peak voltage. (The vtvm was a peak reading instrument calibrated in rms value of a sine wave, which is 0.707 of the peak. Therefore the actual meter readings were multiplied by 1.414 to obtain peak values.) The thermocouple output is fed to a galvanometer. The combination was calibrated at 395 kc and checked at 300 and 500 kc, at which frequencies the calibration was little changed from the center-frequency value.

Theoretical values of the noise output of the amplifier were obtained from the foregoing equation using the measured value of Z. The expression

 $\int_0^\infty G^2 df$


was evaluated by numerical integration of the measured response of the amplifier, with squared ordinates. Substituting the numerical values in the equation for noise gave $V_{\rm N}{}^2=3.0\times10^4i$ square volts, where i is the phototube current.

Theoretical and observed values for $V_{\scriptscriptstyle N}$ are shown in the graph. Observed values were corrected for residual amplifier noise by means of the relationship


 $V_N = (V_0^2 - V_R^2)^{1/2}$

where V_o is the measured amplifier output voltage with noise signal from the phototube applied and V_R is the residual noise with no applied signal. The residual noise amounted to about 0.3 rms volt. The close agreement between theoretical and observed values indicates that other sources of noise contribute very little to the noise output.

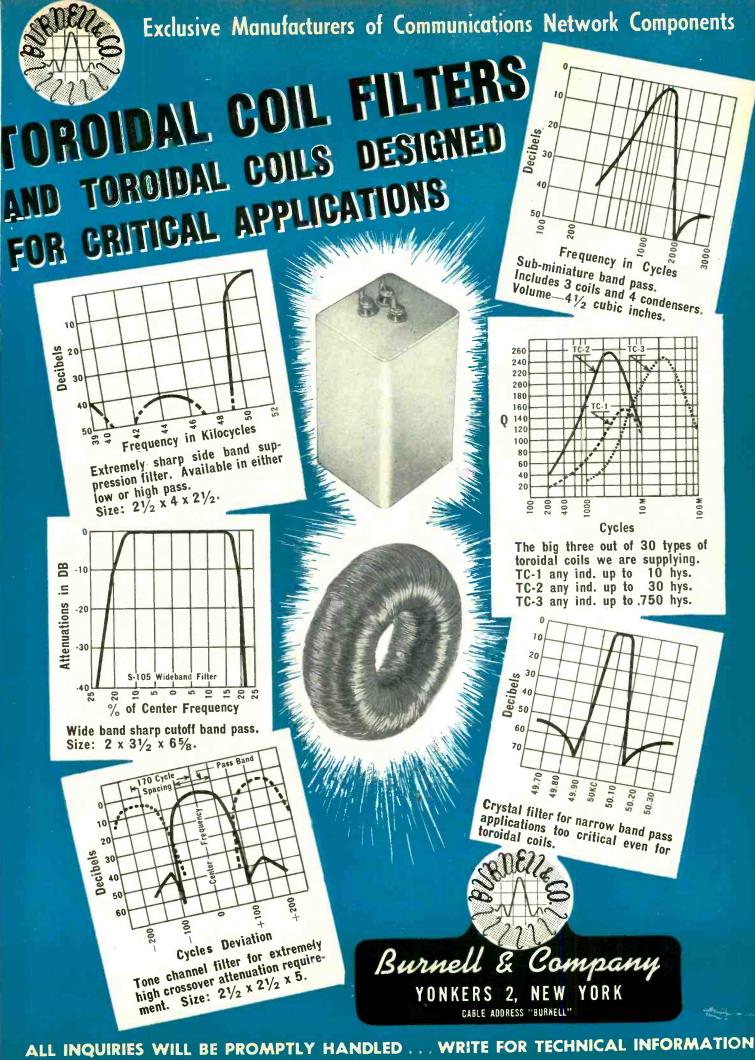Observed peak values are also plotted on the graph. The peak voltage is about three times the rms value. This represents considerable departure from sinusoidal waveshape for which the peak value is 1.414 times the rms value. (Something about the impulse waveform



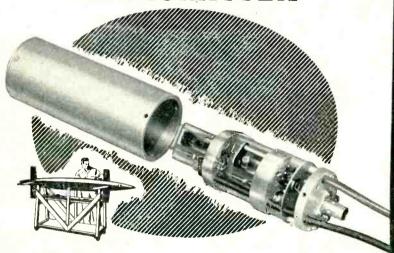Bendix Pacific **MODEL TXV-2A** TRANSMITTER



The Bendix Model TXV-2A Transmitter is a VHF direct FM transmitter developed to supplement a complete line of telemetering components designed for use in the FM/FM subminiature telemetering system.

Complete telemetering facilities are available at Bendix Pacific including not only the manufacture and supply of components, but also installation and application engineering, field operations, data reduction and engineering consultation.

SPECIFICATIONS

Frequency range: 209 mc to 227 mc


Modulation: to ± 125 kc

Power required: 135 volts at 40 ma and 6 volts at 0.45 amp.

Nominal output: 0.5 watt into 51.5 ohms

Weight: .875 pounds

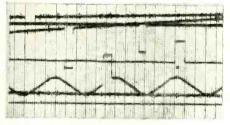Case Dimensions: 2 inches in diameter-51/8 inches long (excluding connectors)



Additional information on the TXV-2A Transmitter or other telemetering components or services is available upon request from qualified companies.

DATA REDUCTION



Aviation Corporation NORTH HOLLYWOOD, CALIF.

East Coast Offices: 475 Fifth Ave., New York 17, N.Y.

(continued)

of the noise could be inferred from this factor of three, but would have little significance without further measurements.)

Conclusions

From these observations it is concluded that the noise output from vacuum phototubes is almost entirely due to shot effect for currents up to at least one milliampere. and can be calculated simply and accurately. The fact that the peak to rms ratio is higher for the noise signal than for a sinewave is important in applications where the response to peak voltage is being

REFERENCES

(1) A. L. Hughes and L. A. DuBridge, "Photoelectric Phenomena," p 34, McGraw-Hill Book Co., 1932.

(2) B. A. Kingsbury, The Shot Effect in Photoelectric Currents, Physical Review, 38, p 1458, 1931.

(3) J. B. Johnson and F. B. Llewellyn, Limits to Amplification, Electrical Engineering, 53, p 1449, 1934.

neering, 53, p 1449, 1934.


(4) Henry Wallman, Stagger-Tuned I-F Amplifiers, MIT Rad. Lab. Report No. 524. (The factors for 1, 2, 3, and 4 stages were independently determined by I. Rotkin and P. R. Karr of NBS and reported by them at the October 1947 meeting of URSI in Washington.)

Detecting Displacement

SENSITIVE variable-resistance helical spring transducers are being studied by W. A. Wildhack and his associates at the National Bureau of Standards. The device consists of a gold-coated nickel-allov wire spring that is wound with high initial tension and so that its elastic constant varies slightly along its length (by varying the winding tension, angle of feed or spring radius). Thus, when the spring is slowly loaded, the turns pull apart one by one rather than simultaneously. When the spring is entirely closed, it has a low electrical resistance from end to end because of the low contact resistance of the gold plating; as it is loaded, the recontinuously increases. The percentage change in resistance can be hundreds of times greater than the percentage change in length. Displacements of 0.0001 inch can be measured without electrical amplification by this highly sensitive and versatile method that is applicable to strain gages, pres-

GLSINGS TRADE MARK REGISTERED US PATENT OFFICE

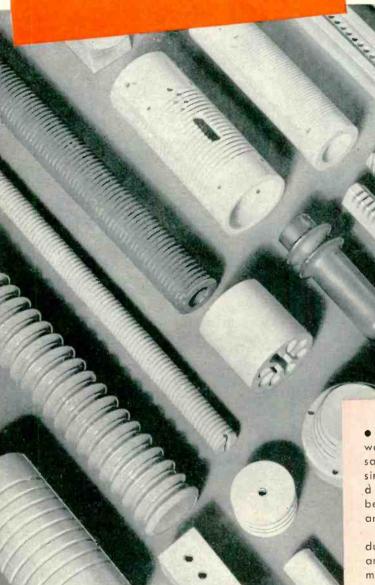a superior, low cost alternate for many commonly used materials



Example: A manufocturer replaced a machined port which cost him 33 cents each with an improved AlSiMag component which cost 14 cents each. AlSiMag engineers cooperated in redesigning this component for maximum usefulness to the customer and minimum production cost—That same engineering cooperation is available to you on request.

• Engineers are often surprised to find that metal, plastic or wood parts can be replaced with AlSiMag components at a saving in cost. At the same time they usually gain highly desirable advantages in product performance. It is natural that a product with the many superior advantages of AlSiMag would be expected to be expensive. The basic materials in AlSiMag are costly.

Automatic and efficient manufacture permits quantity production of AlSiMag parts at low prices. Thus, AlSiMag prices are frequently lower than prices of similar parts in cheaper materials which are more expensive to fabricate.

AlSiMag technical ceramic components are custom made for the individual requirement. AlSiMag is the trade name of a large number of ceramic compositions. The physical characteristics of the various compositions are clearly and accurately listed in the AlSiMag Property Chart, sent free on request.

Our engineers will be glad to submit suggestions on design and give you information on cost if you will submit details of your requirements.


47TH YEAR OF CERAMIC LEADERSHIP

AMERICAN LAVA CORPORATION

CHATTANOOGA 5, TENNESSEE

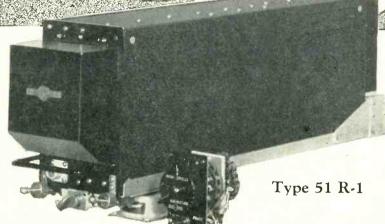SALES OFFICES: ST. LOUIS, MO., 1123 Washington Ave., Tel: Garfield 4959 • NEWARK, N. J., 671 Broad St., Tel: Mitchell 2-8159 • CAMBRIDGE, Mass., 38-B Brattle St., Tel: Kirkland 4498 • CHICAGO, 9 S. Clinton St., Tel: Central 1721 • LOS ANGELES, 324 N. San Pedro St., Tel: Mutual 9079 • PHILADELPHIA, 1649 N. Broad St.





PROBLEM

To build a receiver intended for airline and military service in the vhf navigation and communication bands. Compactness and elimination of extra weight dictated use of a crystal that is light in weight, hermetically sealed and highly stable.

SOLUTION

STANDARD'S Crystal-Type 20



REASONS

(as stated by Collins Engineering Department)

- (1) Standard's Type 20 meets ±.005 % stability requirement over -55°C to +90°C range and is hermetically sealed in dry nitrogen.
- (2) Low price for required performance.
- (3) Best volume and shape factor.
- (4) Standard's Type 20 proved consistently superior in stability and activity.


Let us send you our FREE catalog showing the STANDARD line of frequency control units. For special problems, our engineering department is at your service. There's no obligation involved.

(We manufacture quality super-sonic and ultra-sonic crystals.)

STANDARD PIEZO COMPANY

Office and Development Laboratories

CARLISLE - PENNSYLVANIA

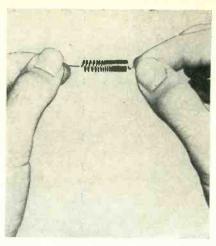

Basis of sensitive mechanoelectrical transducer is progressive separation of turns under increasing tension. Unloaded resistance is that of a solid cylinder because of low contact resistance between gold plating on coils and high average initial tension of the spring

sure elements, accelerometers, weighing devices, temperature controllers, and other measurements involving changes in dimensions. The preferable construction for a transducer using such springs is a four-arm bridge in which a displacement elongates one pair and shortens the other pair of springs. Measurements with this circuit are reproducible to one percent.

Reducing Hum in Pentodes


By IMRE ZAKARIAS

Picofarad Elektromos Meroberendezesek Budapest, Hungary

USING SCREEN-GRID TUBES for amplifying low-level signals of the order of ten microvolts having frequency components in the band from 0.5 to 200 cycles per second, as in equipment for electrocardiography and electroencephalography, is troublesome because of the residual hum from the alternating current used in the heaters, despite screening, filtering, and grounding of the cathode. show that this heater hum varies with tube type and between individual tubes of the same type. To find means for counteracting this source of hum, measurements were made which showed the effectiveness of the several alternatives.

Sources and Measurement of Hum

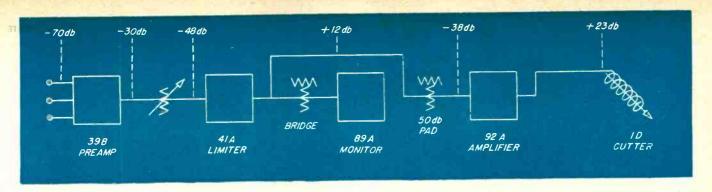
If there is a potential difference between cathode and heater, as in



You're sure

WHEN IT'S 100% PRESTO



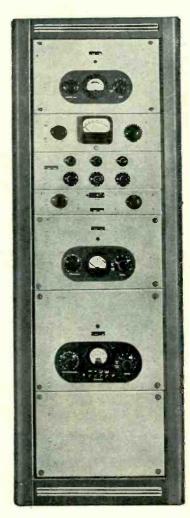


Pictured here is an all-Presto single channel recording system. Above is the block diagram, worked out for this equipment by Presto engineers.

When you need recording or transcription equipment you can't go wrong if you make the complete system 100% Presto.

For Presto is the world's foremost manufacturer of recording and transcription equipment and discs. And Presto's experience with countless installations, including all the big ones, will aid you in achieving greater efficiency and trouble-free operation.


The recorder is the 8DG with direct gear drive. The amplifiers are the 39-B three channel preamp, the 41-A limiter, the 92-A 60 watt recording amplifier, and the 89-A monitor.

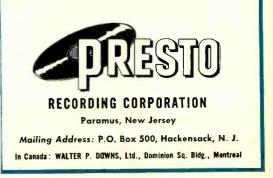Multiple channel installations consist of as many duplications of the basic channel as are needed with the addition of switch or patching facilities. When you think of recording, think of PRESTO.



WORLD'S LARGEST MANUFACTURER OF INSTANTANEOUS SOUND RECORDING EQUIPMENT AND DISCS

SHURE "900MG"

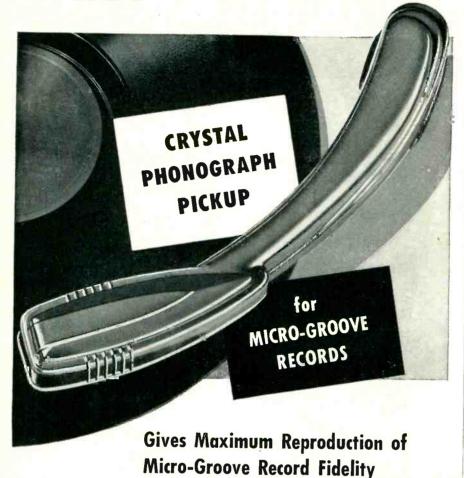

The Shure "900MG" Pickup is an ideal instrument for tracking on the new micro-groove records. It tracks at 6 grams . . . uses a special offset osmium-tipped needle with a point radius of only .001" . . . and has an output of 1 volt! The Shure lever system has been adapted in the development of this new pickup—providing a high needle compliance. Listen to it—you will be thrilled with the results!

Model "900MG"

Code: RUZUZ

Shure Patents Issued and Pending. Licensed under the Patents of the Brush Development Co.



SHURE BROTHERS, Inc.

Microphones and Acoustic Devices

225 W. HURON ST., CHICAGO 10, ILL. . CABLE ADDRESS: SHUREMICRO


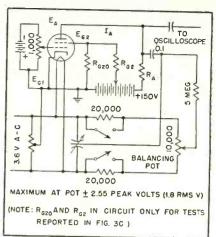


FIG. 1—Experimental circuit for measuring hum produced by heater current

self-biased circuits and in which case the cathode is not grounded, a portion of the hum can arise from leakage currents between heater and cathode. But usually the hum results from the fluctuations of the current distribution between screen grid and plate caused by the deflection effect of the alternating magnetic field of the heater current. Tests in which the tube was heated by direct current and an auxiliary alternating potential of six volts was applied between heater and cathode, with the cathode grounded, showed no hum. Also, the hum disappeared when the screen was connected directly to the plate, with a-c heating. Furthermore, the hum was found to be up to 40 fold greater in a variable-mu tube such as an AF 3 (comparable to a 58) compared to a sharp cutoff tube such as the AF 7 (like a 57). It was also observed that the hum varies with the operating point so that varying the control or screen bias can cause the hum to pass through zero, and that an unbypassed screen biasing resistor tends to increase hum whereas an unbypassed cathode resistor tends to decrease

In making these measurements of power line hum, the compensating method was used. A voltage, derived from the heater circuit by means of a wired potentiometer, for controlling magnitude, and a differential capacitor, for adjusting phase, was impressed on the plate of the tube under test. The normal operating voltages for the tube were obtained from batteries; Fig. 1

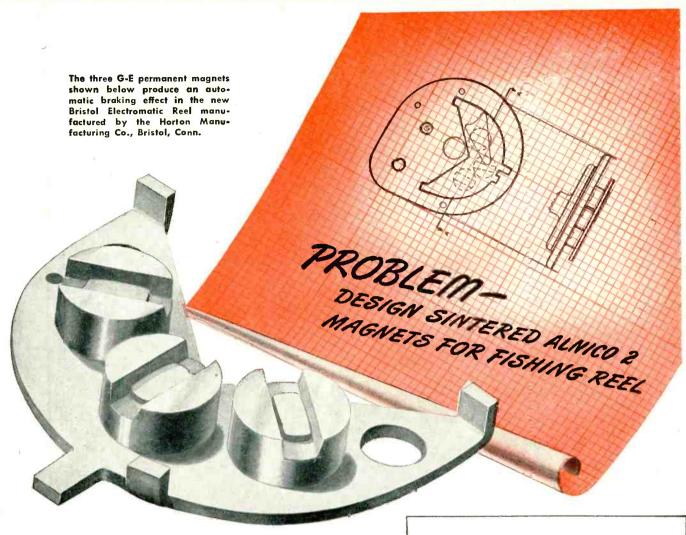YOU GET QUALITY PLUS ENGINEERING SERVICE WITH G-E PERMANENT MAGNETS



The magnets that brake your reel

Now it's G-E permanent magnets for greater accuracy in casting. The permanent magnets shown above develop a non-friction braking action directly in proportion to the speed of the plug. Maximum braking is applied at the start of the cast and, as the spool is slowing down, the braking effect decreases automatically.

G-E permanent magnets are continually finding wide application in many fields. The magnetic reel is but one example of the adaptation of an industrial magnet engineering

principle to an entirely different field.

Perhaps there's a use for G-E permanent magnets in your product. Or, you may wish to improve your present magnet design for greater efficiency. Our engineers will be glad to work with you to improve your product. For details and your free copy of CDM-1, G-E PERMANENT MAGNETS, write Metallurgy Division, Section CM-11, Chemical Department, General Electric Company, Pittsfield, Mass.





Smooth casting action with the **Bristol Electromatic Reel**

Three G-E Sintered Alnico magnets are mounted on a non-magnetic plate having adjustable air gap. A bi-metallic disc of copper and steel mounted on the end of the spool cuts the lines of force of the permanent magnets. The eddy currents induced set up electromagnetic poles which repel the permanent magnet poles producing a drag on the speed of the spool. Since the strength of the electromagnetic poles depends on the speed of rotation of the spool, this braking effect is automatically applied at all times in just the right amount. Outstanding advantages of this new reel are smooth casting action, greater accuracy, and freedom from backlash.


GENERAL (%)



ELECTRIC

Professional TAPE RECORDING

with FM QUALITY and EASY PORTABILITY

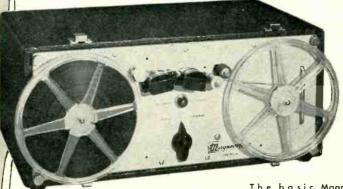

The basic Magnecorder recorder mechanism (PT6·A)

The New 3 Element

MAGNECORDER

The Magnecorder meets the highest broadcast standards, and it costs you less. You buy and combine only the units you need:

Magnecorder (PT6-A) — Basic recorder mechanism.

Portable Mixer-Amplifier (PT6-P) — Recording and reproducing portable field amplifier. Can be used as high-quality remote amplifier. Mixes three low-level microphones.

Rack Mount Amplifier (PT6-R) — Recording and reproducing amplifier for studio rack mounting. With PT6-A makes complete studio recorder-reproducer.

It's Portable! It's Flexible!

Weight - PT6-A, 23 pounds; PT6-P, 29 pounds.

Wow and Flutter - .2%

Frequency Response - 40 to 15,000 cycles; + or - 2 db. Tape Speed - 15 inches or $7\frac{1}{2}$ inches per second (Interchangeable).

Motor - Synchronous 1/50 HP.

Single Control

Rewind - 45 seconds.

Reels - Standard 7-inch 8MM film reels.

Current failure never throws tape. Instantly interchangeable from portable to rack mounting.

Write today for detailed specifications

Magnecord

360 N. Michigan Ave.

Dept. E

Chicago 1

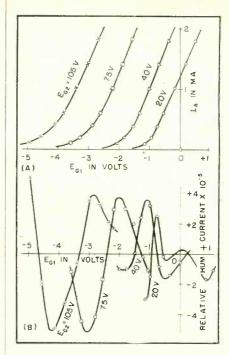


FIG. 2—Characteristics (A) and relative hum current in plate circuit (B) of a sharp cutoff pentode


shows the circuit. Balance in the plate circuit was indicated by a cathode-ray oscilloscope.

Experimental Method and Results

So that absolute values could be obtained, the deflection sensitivity of the oscilloscope and the volts per scale division of the balancing potentiometer were determined. Knowing these factors, the hum can be expressed in terms of alternating current in the plate circuit. or as the ratio of hum current to steady plate current. Shorting the two 0.02-meg resistors in series with the balancing potentiometer increased the compensating voltage by a factor of five. Although the differential capacitor was found necessary to eliminate minor phase shifts, it was observed that, in general, the hum was in phase with the heater voltage.

The results are presented in the form of curves. Figure 2A is the measured characteristic of the AF 7 tube used in the tests. Figure 2B shows the ratio of hum to steady plate current as a function of control grid voltage for four values of screen-grid voltage. Figure 3A shows the same measurements plotted as a function of plate current. In interpreting the effects shown in these last two families of curves,

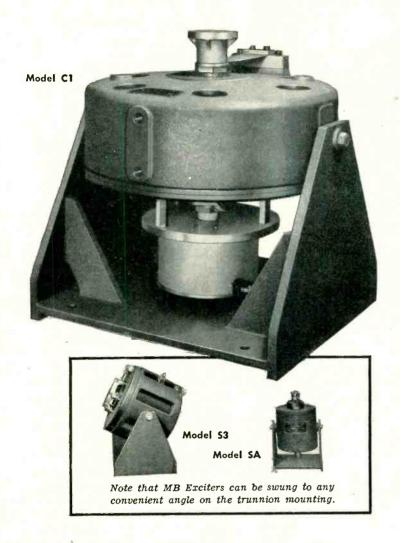Product faults found in minutes with MB vibration exciters!



SOME TIME AGO, a large automotive manufacturer was attempting to learn whether gas tanks could be strengthened.

They first used a mechanical shaker on a test tank in an attempt to discover possible trouble—but days went by without signs of failure. However, when an MB Exciter was attached, the tank was vibrated to destruction in a matter of minutes! A repeat test produced a similar failure. Based on the visual evidence, which eliminated the need for any dynamic computations, the tank was redesigned, and it was made not only stronger, but materially lighter—cutting costs as well as saving steel.

In another case, where one manufacturer's headlight bulbs were failing in great numbers, an MB Exciter fixed the blame at once—on the filament supporting arm, which was resonating at a frequency within the operating range of the car.

These cases illustrate a technique of testing that you'll find increasingly valuable as experience shows you new applications for this product improver. MB vibration exciters are now being used by many of the country's largest companies—for fatigue testing, for location of noise sources, for determining the vibratory response of products—and the corrective measures.

Would you like to know more about how to use this shaker in your own work? An MB engineer will be glad to give you the benefits of our specialized vibration experience.

If your product has any vibration at all—this MB VIBRATION PICKUP will detect it!

There's no practical lower limit on the amplitude of vibration you can detect with the MB Vibration Pickup—it's that sensitive! And there's no engine it can't be used on — it's that durable under high-powered pulsations!

It is a velocity-type pickup, electri-


cally damped, with a range of 5 to 1000 c.p.s. and usable in any position. When the pickup's electrical output is fed to standard voltage measuring equipment, it can be used to check products for operating smoothness and for quality-control.



WRITE FOR FREE BULLETINS

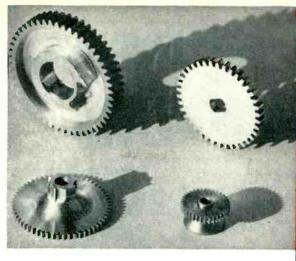Ask for bulletin "Vibration Testing Technique" which describes how MB Exciters are used. And Bulletin 124A will give you more details on Pickup. Write Dep't. D5.





GEARS WITH OUADEO

Special Shapes and Features? ... Tolerances within .0005"... Let our experience in supplying precision small and medium sized gears with such features solve these production problems for you... Ask for quotation on your job specifications. Circular on Request.

MEMEER OF

. SPUR

- . WORM
- . SPLINE
- . HELICAL
- SPROCKET
- . STRAIGHT BEVEL
- . GROUND THREADS



MODEL 204A POWER SUPPLY

0-500 VOLTS D.C. AT 300 MA. WITH POSITIVE OR NEGATIVE GROUND

The Model 204A Regulated Power Supply will provide from 0-500 volts of well regulated and well filtered D.C. The output voltage is continuously variable without switching and either positive or negative side may be grounded.



SPECIFICATIONS:

OUTPUT VOLTAGE

High Voltage: 0-500 Volts D.C. continuously variable (Without switching).
Current: 300 Ma.

Low A.C. Voltage: 6.3 Volts A.C. at 6 amps. center-tapped, unregulated

REGULATION

Within 1% for voltage between 30-500 volts, from no load to full load.

Within 1% for line voltage variations from 105 to 125 volts at full load current for any voltage between 30-500 volts and within 2% at 10 volts.

HUM VOLTAGE

Within 10 Millivolts at any voltage or load within ratings.

LINE INPUT 105-125 Volts A.C. 50-60 cycles.

OUTPUT TERMINATIONS

High and low voltage outputs available from front and rear of unit. Positive or negative terminal of high voltage output may be grounded as desired.

Detailed specifications will be forwarded upon request without obligation.



RED BANK . NEW JERSEY

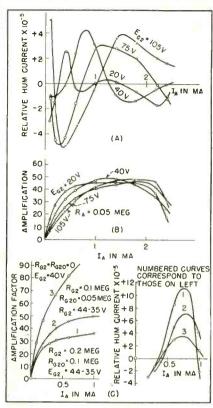


FIG. 3—Results obtained for sharp cutoff tube AF 7 (comparable to a 57)

it is necessary to take into consideration the change in gain produced by the change in grid bias (or plate current). This change is shown as a function of plate current, for use with Fig. 3A, in Fig. 3B. The effect of resistance in the screen circuit is shown by the two sets of curves in Fig. 3C; those to the left show change in gain, those to the right show relative hum, both as functions of plate current.

Comparing Fig. 2A and 2B it can be found that the equivalent hum amplification factor of the screen grid is 34 compared to 27 for the anode current amplification factor. This greater amplification factor for the hum is also evident from Fig. 3A. Figure 3C shows that, as the unbypassed screen resistance is increased, the hum increases and the gain decreases. The screen-grid voltage varies somewhat with plate current therefore the curves are not fully comparable. At plate currents below 0.4 ma the amplification factor is small so that the screen degeneration is negligible and the curves are therefore identical.

Figure 4 shows measurements on an AF 3; Fig. 4A shows the hum, Fig. 4B shows the gain. From Fig.

Where cables can't go



SHARING MULTIPLEX Can

Natural hazards are no longer obstacles to the telephone engineer. Standard Time-sharing Multiplex can provide a thoroughly reliable trunk system which is easy to install and maintain in the most difficult terrain.

Each equipment deals with up to 24 channels, handling any kind of A.F. traffic in the 300-3400 c/s range, including teleprinter and automatic telephone signals. Time-sharing Multiplex ensures low crosstalk and noise levels, and fading does not affect speech levels.

A UHF carrier is used, and the normal line-of-sight range can be extended by automatic repeaters.

Complete terminal equipment occupies a double cabinet 7' wide x 2'4'' deep x 6'6'' high, and aerials may be up to 100' from the main equipment.

Write for Bulletin No. 511 which gives further facts and figures.

Standard Telephones and Cables Limited Radio Division

OAKLEIGH ROAD, NEW SOUTHGATE, LONDON, N.11, ENGLAND

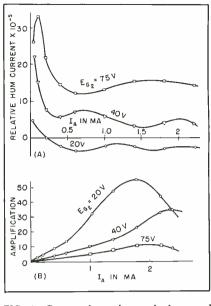


FIG. 4—Curves show change in hum and gain of variable-mu tube like a 58

4A one can infer that at some screen voltage between 20 and 40 volts there should be a hum curve having several zeros. From these measurements, as summarized in the introduction and as elaborated in these curves, it can be seen that the operating condition of a tube affects the relative hum current appearing in the plate circuit. Under special favorable conditions this hum current can be made to vary about zero magnitude.

In conclusion, I express my thanks to Mr. Nandor Szabo, chief of the Company Erdely and Szabo, for making the instruments, and to Mr. Henry Tabori for his help in the tests, which were completed in September 1944.

SURVEY OF NEW TECHNIQUES

STEREOSCOPIC SCREENS for motion picture or television projection before large audiences have been experimentally developed by E. G. Beard of the Philips Company in Sydney, Australia. In its simplest form the screen consists of a polished metal sheet engraved with over-lapping sets of concentric circular grooves of semicircular cross-section. The grooves act as concave mirrors that reflect the two images projected onto the screen to the observers at the correct angles. The



DO YOU CUT DISCS' OR DOLLARS'



Two years ago Soundcraft introduced the 'Broadcaster', a premium quality instantaneous recording disc. The "super" blank record costs more to make, is worth more to the broadcast engineer.

Representing but a small portion of the cost of a recorded program or record release, the blank disc is yet the heart of any recording project. No platter can be more expensive than one that loses a program or originates doubtful pressings. Soundcraft knew that key engineers appreciated these facts.

Soundcraft's judgment in offering the high-reliability 'Broadcasters' (master-selected discs in standard sizes) and the wax-like 'Maestros' (oversize discs for processing) has been vindicated by widespread acceptance on the part of makers of the best off-the-line recordings, transcriptions, and phonograph records.

For real economy don't cut your disc budget, cut the best disc!

Clip the coupon today for the story of how Soundcraft discs are made, the list of Soundcraft distributors, and your sample 'Broadcaster'.

For real economy don't cut your disc budget, cut the best disc!

REEVES COUNTACTACT CORP.

10 EAST 52nd STREET • NEW YORK 22, N.Y.

Export Address
REEVINTER, N.Y.

The Broadcaster' The Playback' The 'Audition' The 'Maestro

ALBANY: Fort Orange Radio Distributing Co. **BALTIMORE: Radio Electric Service Co. BOSTON: The Radio Shack Corp. BUFFALO:** Radio Equipment Corp. CHICAGO: Walker-Jimieson Inc. CINCINNATI: United Radio Inc. **CLEVELAND: Radio & Electronic** Parts Corp. **DETROIT: Radio Specialties Co.** HOUSTON: Geophysical Supply Co. INDIANAPOLIS: Phillip E. Graham Co. LOS ANGELES: Leo J. Meyberg Co. MILWAUKEE: Radio Parts Co. Inc. NASHVILLE: Electra Distributing Co. NEWARK: Aaron Lippman & Co. Parr Electric Co. NEW ORLEANS: Radio Parts, Inc. NEW YORK: E. B. Latham & Co. NORFOLK: Radio Supply Co. PHILADELPHIA: Rumsey Electric Co. PITTSBURGH: Cameradio Co. ST. LOUIS: Van Sickle Radio Co. SAN FRANCISCO: Leo J. Meyberg Co. ELECTRONS INCORPORATED 127 SUSSEX AVENUE In stock near you GRID CONTROL RECTIFIERS RECTIFIERS

principle can also be applied to transparent screens by using refracting circular elements instead of reflecting ones. Stereoscopic motion pictures have been successfully shown with the screen. Experiments will next be made to project stereoscopic television pictures in which the two views are transmitted with the interlacing, thus requiring no additional bandwidth.

Noise has been put to good use by two physicists, Drs. J. V. Garrison and A. W. Dawson. By using the increase in thermal noise with temperature as an indication of temperature, they have devised a method of measurement that operates from absolute zero to about 5,000 F and is more accurate over this range than other means.


STATIC CHARGES can be dissipated as formed, thus preventing the possibility of abrupt discharges that produce interference, by placing minute amounts of polonium in the vicinity. Radiations from the rare radioactive element that are harmless to humans are, nevertheless, sufficient to ionize the surrounding air so that charges can be dissipated. Polonium can be plated easily onto other metals.

RESISTANCES from 10° to 1012 ohms, for use with phototubes, electrometers and other high-impedance devices, have been developed that consist of platinum evaporated on glass and sealed within a vacuum. Such resistors obey Ohm's law within about one percent from 0.1 to 300 volts, and are stable with time to within a few percent, unaffected by humidity, and are small, being about 2 inches long and 0.25 inch in diameter. A particularly interesting property of these resistors is that the magnitude of the noise produced by them equals that theoretically expected from the value of their resistance. Patented by D. Vodar, Laboratorie de Physique Enseignement, Sorbonne, Paris, the resistors are commercially produced by Etablissement Beaudouin (3 Rue Rataum, Paris).

Two NEW Plasticon Developments

TS CAPACITORS - are used in -

(operate from -80° to $+400^{\circ}$ F)

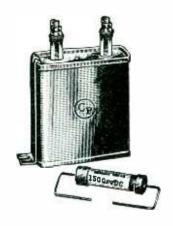


The dielectric combination in Type TS capacitors consists of "Teflon" film and "Silicone" fluid. Both materials are unusually temperature-stable and have extremely low dielectric losses. Properly engineered and processed, Type TS capacitors have remarkable characteristics.

A typical example is Type TSG103-3. This is an .01 mfd. 3000VDC capacitor in a Glassmike style container 29/32" OD x 21/4" long. The DC resistance is in excess of 100,000 megohms at 150°C. The dissipation factor at one megacycle is .0005 at 70°C and .001 at 150°C. At 60 cycles, the dissipation factor is as low as .0002 - .0003.

The temperature coefficient of Type TS is negative, 300-400 parts per million per degree Centi-

We recommend Type TS capacitors for ultra high temperature DC applications and for RF bypassing and coupling duty.

PLASTICON PULSE FORMING **NETWORKS**

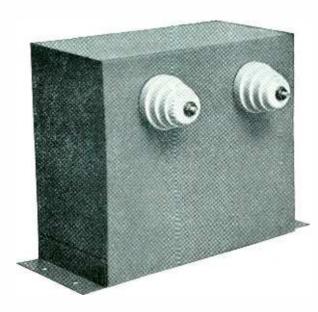

Type TS capacitors properly designed for pulse operation have many advantages over paper and mica capacitors. Type TS can operate at much higher ambient temperatures (150°C and up) but have much lower losses. The Type TS dielectric combination does not fatigue under pulse duty. PLASTI-CON networks are smaller and lighter.

Plasticon TS Pulse Forming Networks are designed to meet your specifications.

Condenser Products Company

1375 NORTH BRANCH STREET . CHICAGO 22, ILLINOIS



Sault Hinder

We look for trouble in our coils — before they're built! Before a Wheeler coil is started, its component parts must be checked, tested, proved to be faultless.

The wire wound into Wheeler coils is no exception. It is closely inspected by experts — micrometer checks are made regularly to insure its uniformity. Only by following engineering practices proved over a long period of time can we be sure our coils will give the service and performance expected of them.

Wheeler coils — wound with Wheeler Magnet Wire — are rapidly becoming standard for the electrical industry. Investigate them today. They may be the answer to your electrical coil problems.

THE WHEELER INSULATED WIRE CO., INC.



DIVISION OF THE SPERRY CORPORATION

1011 WASHINGTON AVENUE BRIDGEPORT 4, CONNECTICUT

MAGNET WIRE . COILS . COMMUNICATIONS EQUIPMENT

NEW PRODUCTS (continued from p 130)



pressure of about 6 grams and cover a range from 40 cycles to over 10 kc.

Fidelity Pickup

SHURE BROTHERS, INC., 225 W. Huron St., Chicago 10, Ill. The 900MG crystal phonograph pickup for microgroove records provides high-fidelity reproduction. It tracks at 7 grams, has a needle force of



9 grams, uses an offset osmiumtipped needle with a 0.001-inch point radius and has an output of 1 volt.

High-Q Chokes

CHICAGO TRANSFORMER, 3501 W. Addison Blvd., Chicago, Ill. Designed specifically for use in dynamic noise suppressor circuits, the NSI-1 and NSI-2 reactors can be used in any tuned circuits requiring the given inductances. Induct-



November, 1948 — ELECTRONICS



Indeed, the Type 5SP- is an unique cathode-ray tube since it embodies two complete and independent electron guns and deflection plate assemblies for the production of two entirely separate electron

ferent screen phosphors.

And please remember this: The Du Mont Type 5SP- is the only dual-gun cathode-ray tube registered with the Radio Manufacturers Association.

Details on request.



ALLEN B. DU MONT LABORATORIES, INC., PASSAIC, N. J. CABLE ADDRESS: ALBEEDU, NEW YORK, N. Y., U.S.A.

ALLEN B. DU MONT LABORATORIES, INC.



QUESTION MARKS

... were put to work!

by the successful design and production of Elinco instrument-type fractional h.p. motors and generators that met special needs.

Yes, every finished Elinco motor or generator was born of a question mark. There was a job to be done . . . could Elinco engineer and produce a special unit to do the job? The answer is in the over 100,000 special Elinco units, successfully designed to the most exacting specifications, and now serving in practically every type and branch of industry. Special design is our business . . not low-cost, mass-production motors . . but special high-precision instruments demanding the highest engineering ability, and exceptional manufacturing skill and care.

there are over 400

Basic Models of Elinco Fractional H. P. Instrument-Type Motors and Generators


Units are produced to order, either by the design of a new model to meet your exact requirements, or by the adaptation of one of our over 300 basic units in order to meet your needs, either electrically or physically

ELECTRIC INDICATOR CO. PARKER AVENUE, STAMFORD, CONN.

ance values, 2.4 and 0.8 henrys respectively, are accurate within ± 5 percent with up to 15 ma d-c. Units have a minimum Q of 20.

Servo Tester

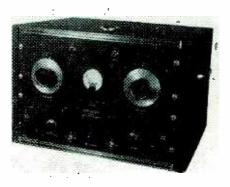SERVO CORP. OF AMERICA, 2020 Jericho Turnpike, New Hyde Park, N. Y. The Servoscope is the first of



a line of design instrument aids for the servomechanisms engineer. It furnishes continuous performance data so that frequency response can be plotted and transient characteristics deduced in a few minutes. Rapid measurements are furnished of frequency-versus-amplitude attenuation and phase shift.

Audio-Frequency Meter


GENERAL RADIO Co., 275 Massachusetts Ave., Cambridge 39, Mass. Discontinued during the war years,



type 1141-A audio-frequency meter is again available. Using a null method, accuracy of the bridge is 0.5 percent. Because it uses a Wien bridge circuit, the instrument can be used as an adjustable-frequency filter over its range from 20 to 20,000 cycles.

Tripod Dolly

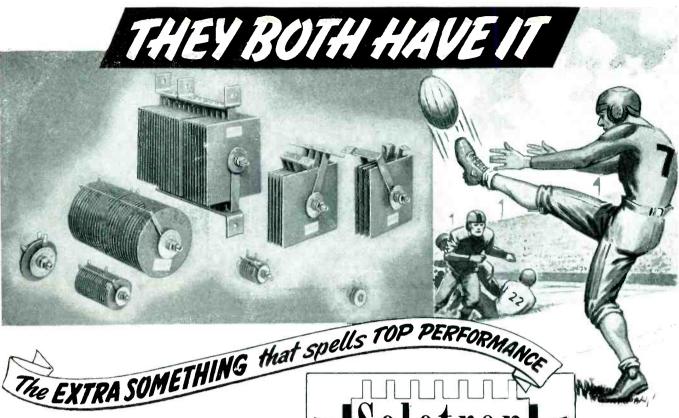RADIO CORP. OF AMERICA, Camden, N. J. Type MI-26042 portable chrome-finished dolly may be used



THE football star who eludes the players of the rival team and sends the pigskins hurtling down the field to a goal has "the extra something that spells top performance."

For outstanding service in every rectifier application specify Seletron Selenium Rectifiers. They have the "extra something" that spells top performance.

From the large power stacks to the miniature units for radio and television, Seletron uniformity and precision methods of manufacture, insures user satisfaction. Efficientdependable, durable under the severest service conditions.

Furnished in a wide variety of voltages and currents to meet the individual requirements.



SELENIUM RECTIFIERS



SPECIFY SELETRON MINIATURE SELENIUM RECTIFIERS FOR RADIO AND TELEVISION APPLICATIONS

The complete family of miniature Seletron Rectifiers is designed for use on a nominal 115 A-C line, to provide direct current for radio, television sets, amplifiers, and other low power applications. Instant starting, small size, long life and simplicity of installation are a few of many features of the Seletron Family.

CODE NUMBER 51.1 5M1 5P1 5R1 Current Rating 75 ma. 100 ma. 150 ma. 200 ma. 250 ma. 7/8" 11/2" 11/2" Plate Height Plate Width

Write today for catalog. Address Dept. ES-11



Laboratory and Research Instruments ENGINEERED FOR ENGINEERS

SWEEP CALIBRATOR

Model GL-22


This versatile source of timing markers provides these requisites for accurate time and frequency measure-ments with an oscilloscope:



Positive and negative markers at 0.1, 0.5, 1.0. 10, and 100 microseconds • Marker amplitude variable to 50 volts • Gate having variable width and amplitude for blanking or timing • Trigger generator with positive and negative outputs.

Further details in Bulletin MC-811

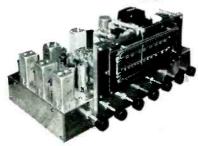High-fidelity RADIO RECEPTION WITH THE Browning Tuner



This is the new Model RJ-20 FM-AM Tuner . . . designed for high-fidelity reception on both FM and AM, and built to meet your highest performance requirements. Its features include:

- Armstrong FM circuit for maximum noise reduction and full frequency response to 15,000 cycles.
- Separate RF and IF systems for FM and AM . . . no coil switching.
- Variable bandwidth IF gives AM bandwidths from 9 kc. to
- Two-stage audio system allows 20 db. boost in bass or treble range.
- New 6AL7 tuning eye for precise tuning on strong or weak FM stations.
- Self-contained power supply.

See, hear, and handle this new Browning Tuner . . . and enjoy new satisfaction in your radio and music reproduction.

> Write today for Data Sheet MT-811



OSCILLOSYNCHROSCOPE Model OL-15B


Provides a variety of time bases, triggers, phasing and delay cirtriggers. pnasing and delay circuits, and extended-range amplifiers in combination with all standard oscilloscope functions.


Extended-range amplifiers: vertical, flat within 3 db 5 cycles to 6 meracuales beri


within 3 db 5 cycles to 6 megacycles; horizontal, flat within 1 db 5 cycles to 0 megacycles; norrzontal, flat within 1 db 5 cycles to 1 megacycle • High sensitivity: vertical, 0.05 RMS volts per inch; horizontal 0.1 RMS volts per inch • Single-sweep-triggered time base permits observation of transients or irregularly recurring phenomena • Variable data; circuit rockle with av • Variable delay circuit usable with external or internal trigger or separate from scope • Sawtooth sweep range covers 5 cycles to 500 kilocycles per second • 4,000-volt acceleration gives superior intensity and definition. Request Bulletin MO-811

HERE'S PERFORMANCE to satisfy the man who knows radio . . . provable by both instrument and listening tests.

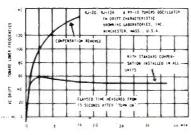CHECK THESE CURVES and you'll see why Browning Tuners are chosen by those who insist upon the best.




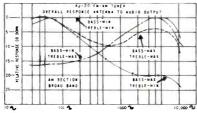

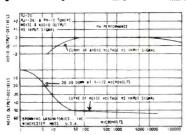

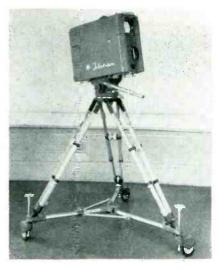To feed a separate high-fidelity audio system, use the Browning RJ-12A for FM/AM or the Browning RV-10 for straight FM. They're all "tops" in the high-fidelity field.





both for field-type and studio television tripods. It can be locked in a fixed position by means of springloaded stop-feet.

Cabinet Racks

ECLIPSE MFG. Co. INC., 294 East 137th St., New York 54, N. Y. A new line of six cabinet racks is available with panel heights rang-



ing from 83 to 35 inches. Mounting holes are tapped for 10-32 screws with standard or amateur hole spacing.

Mobile Equipment

COMMUNICATIONS Co., INC., 300 Greco Ave., Coral Gables, Florida. Model 275-C radiotelephone equipment is designed for mobile applications in the emergency services operating in the 152 to 162-mc f-m

You know more about advertising than you think!

IF YOU UNDERSTAND the basic principles of mass production —

If you're on familiar ground when it comes to time-motion studies, obsolescence curves, and assembly-line techniques —

If you regard every operation in your plant as a challenge to further reduce your manufacturing cost-permit—

Then you know a lot more about advertising than you think. Yes, advertising!

For basically, advertising is the application of assembly-line techniques

to the manufacture of a sale. And how are sales manufactured? Like any other commodity, by sequence of "processing operations." In this case they include —

- 1. Seeking out prospects
- 2. Arousing their interest
- 3. Creating a preference for your product
- 4. Making a specific proposal
- 5. Closing the order

Couldn't your salesmen handle this entire sequence? Certainly — if you had *enough* salesmen, and weren't concerned about the cost. But no

salesman should have to spend his valuable time on missionary work. Not when those first three steps can be mechanized for him — not when they can be handled so much more economically — through the efficient use of business paper advertising.

Why business papers? Because nowhere does your advertising work more efficiently than in the business publications which reach your best prospects. Nowhere else can "mechanized selling" contribute so much toward reducing the cost of manufacturing a sale!



ELECTRONICS

is a member of The Associated Business Papers, who have published an interesting folder entitled, "10 ways to measure advertising effectiveness." We'll be glad to send you a copy. And if you'd like reprints of this advertisement (or the entire series) to pass along to others in your organization, just say the word.






For Inverting D. C. to A. C. . . .

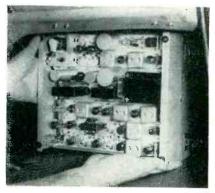Specially Designed for operating A. C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D. C. Districts.






band and is also available for other f-m services operating above 30 mc. The unit weighs 20 pounds, has a transmitter power output of 8 to 10 watts, a battery drain of 6 amperes standby, and 13 amperes when transmitting. Audio output from receiver is over 1 watt.

Deflection Cores

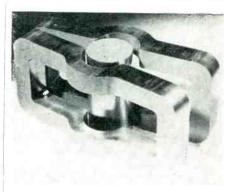HENRY L. CROWLEY & Co., INC., 1 Central Ave., West Orange, N. J. A two-piece frame and center slug



assembly of powdered iron is being made for television receiver deflection transformers. Effective a-c permeabilities in the order of 40 to 230 are attainable. Hum noise is low as compared with that produced in laminated core structures.

Bridge Amplifier

RUGE-DE FOREST, 76 Massachusetts Ave., Cambridge, Mass. The new deflection-type amplifier is designed for use with resistance



November, 1948 - ELECTRONICS

Tellpot. demark of the HELIcal POTentiometer!

THE REVOLUTIONARY Potentiometer that Gives You $46\frac{1}{2}$ " of Slide Wire in a Panel Space $1\frac{1}{2}$ " in Diameter!

> Throughout the electronic industry — wherever quality electronic instruments are designed, manufactured or used—the big news is HELIPOT, the helical potentiometer-rheostat that is making possible entirely new standards of accuracy, convenience and compactness in modern electronic equipment. Briefly, here's what makes the Helipot so unique . . .

> Instead of a single partial turn of slide wire as found in the conventional potentiometer, the Helipot has many full turns of slide wire coiled into a compact helix requiring no more panel space than the ordinary potentiometer. The sliding contact follows the long helical path of the slide wires from end to end when a single knob is rotated. Thus, the Helipot requires the same panel space—the same single control knob—as a conventional potentiometer . . . yet it provides the wide range control and accuracy of a slide wire approximately twelve times as long.*

> In other words, whereas the conventional rheostat gives approximately 300° of rotation, the 10turn Helipot gives 3600° of rotation in the same panel space. Think what this important advancement can mean in simplifying the control, increasing the convenience and improving the accuracy of your electronic equipment. Helipots are already being used in a wide range of devices—depth sounding equipment, flight control instruments, electrical computors, strain-gage circuits, oscilloscopes and other indicating and measuring apparatus, and a great variety of other electronic applications. Let our engineering staff study your control problem and show you how Helipots can increase the accuracy, utility and simplicity of your equipment. There's no obligation, of course.

* For the standard 10 turn, $1\frac{1}{2}$ " unit. Other sizes proportional. We are also equipped to supply other types of potentiometer-rheostats. Send us your requirements. we are al

Send for Helipot booklet!



A SIZE FOR EVERY APPLICATION!

Cutaway

View

Helipots are available in a wide range of sizes and types to meet varying application requirements. Standard Helipots include the following . . .

Model A—Case diameter—1.8" Number of turns—10; Slide wire length—46½"; Rotation—3600°; Power rating—5 watts; Resistance ratings—10 to 100,000 ohms

Model B—Case diameter—3.3": Number of turns—15; Slide wire length—140½"; Rotation—5400°; Power rating—10 watts; Resistance ratings—50 to 300,000 ohms

Model C—Case diameter—1.8" Number of turns— 3 | Slide wire length—13½" Rotation—1080° | Power rating—3 watts; Resistance ratings— Power rating-5 to 30,000 ohms.

In addition, special models of Helipots in production include

Model D—Case diameter—3.3"; Number of turns—25; Slide wire length—234"; Rotation—9000° Power rating—15 watts; Resistance ratings—100 to 500,000 ohms.

Model E—Case diameter—3.3"; Number of turns—40; Slide wire length—373"; Rotation—14, 400°; Power rating—20 watts; Resistance ratings—150 to 800,000 ohms.

Write for data on the

DUODIAL

. . . the ideal turns-indicating dial for use with the Helipot. Compact, simple and fool-proof, here's a dial that requires no more panel space than conventional dials. Yet it contain TWO concentric dials—a PRIMARY dial that indicates rotational position of the slider — and a position properly dial that shows number SECONDARY dial that shows number of complete revolutions of the Primary of dial. Available in a wide range of turns-ratios for all sizes of Helipots—and for other helical applications.



Send for descriptive details!

T CORPORATION, SOUTH PASADENA 2, CALIFORNIA




THE LOW-LOSS, HIGH FREQUENCY INSULATION

for every electrical and mechanical requirement


MYCALEX, a most versatile, low-loss insulation material, possesses unusual characteristics that ideally suit it for use in ultra high-frequency applications. It can be molded, or machined to very close tolerances—it is impervious to water, oil or humidity; has dimen-

sional stability, high dielectric strength and will not carbonize. Metal inserts can be molded into the material giving it an almost endless number of applications in the field of electronics. It is available in the three following types:

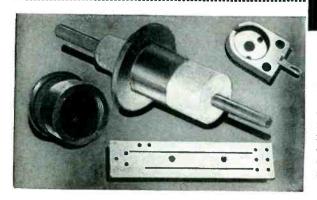

MYCALEX 410

This injection-molded form of Mycalex is useful in 4 cases: 1. When shape is too intricate to permit fabrication by machine. 2. When quantities necessitate high production and low cost. 3. When great dimensional stability is essential. (Mycalex 410 can be molded to very close tolerances.) 4. When metal inserts must be incorporated into the insulator. These inserts may be made of any common metal that can withstand temperatures of about 1200° F and that has a coefficient of thermal expansion of the order of 100 to 175 x 10⁻⁷ per degree C. Mycalex metal seals can withstand pressure of 90 psi.

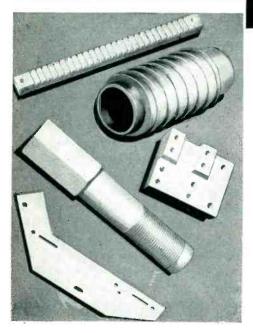

MYCALEX 400

Compression molded for high-frequency applications. Its loss factor is well within requirements for operation in this portion of the electromagnetic spectrum. An outstanding characteristic is the long frequency range over which the loss factor is a minimum. Tropical climates do not impair its electrical and physical properties. It is, therefore, used for insulation in radio transmitters, radio receivers, communication panels, switchboard panels, are shields in high tension switches, brush holders, relay contact supports, etc. Available in sheets 14 by 18 in.; thickness of ½ to 1 in. Rods 18 in. long, diameter ¼ to 1 in.

MYCALEX K series

Dielectrics. Many ceramic materials offer low power factor, negligible moisture absorption, high dielectric strength, lack of cold flow, ability to withstand high temperatures. Few, however, include a dielectric constant greater than 7 or 8 at radio frequencies. Few are available with flat surfaces of large dimensions that don't warp, or close tolerances in rods. Mycalex K capacitor dielectrics combine all of them and is available in practically any form. Power factor varies from 0.002 to 0.004 at 1 mc.

MYCALEX FABRICATING SERVICE

Mycalex can be machined to customers' exact specifications in our new plant at Clifton, N. J. This plant is especially tooled for large volume machining of Mycalex in a wide variety of forms. This service offers the following advantages . . . PRECISION WORKMANSHIP: specialized equipment that assures remarkable precision and super-

vision by skilled engineers. REDUCED COSTS: substantial savings effected by efficient performance on a quantity basis. RELIEF TO PLANT BOTTLENECKS. PROMPT DELIVERIES. Consult our engineering staff for advice on the application of Mycalex to your insulating problems.

MYCALEX CORPORATION OF AMERICA

"Owners of 'MYCALEX' Patents"

Plant and General Offices CLIFTON, N. J.

Executive Offices, 30 ROCKEFELLER PLAZA, NEW YORK 20, N.Y.

bridges ranging in impedance from 100 to 500 ohms and having a full-scale output as small as 25 microvolts per volt of input to the bridge, or as large as 5 millivolts per volt. Output is 18 volts across an external 1500-ohm load with a linearity of 0.5 percent. Frequency response is flat to ± 2 percent from 0 to 50 cycles when working into a resistive load.

Electrical Insulation

JOHNS-MANVILLE, 22 E 40th St., New York 16, N. Y. An asbestosbase, completely inorganic electrical



insulation, Quinterra was designed for use where high temperatures are encountered since it retains its dielectric strength of over 250 volts per mil. It has already been used as wire insulation in transformers.

Equalizer

BROCINER ELECTRONICS LABORATORY, 1546 Second Ave., New York 28, N. Y. Model A65 amplifier and



companion model P6-300 d-c power supply provide a means of compensating magnetic phonograph pickups to various recording characteristics. Turnover frequencies of 300, 500, and 800 cycles are accommodated.

F-M Transceiver

Doolittle Radio, Inc., 7421 South Loomis Blvd., Chicago 36, Ill. The PJZ-1 portable f-m transmitter and receiver with quarterwave telescopic antenna is designed for operation on a single frequency in the

An Important Statement

by

MYCALEX CORPORATION OF AMERICA

An explanation of the properties and advantages of Mycalex (glass bonded mica) 410, Mycalex 400, and Mycalex K are given on the opposite page.

Your attention is also called to the Mycalex 410 advertisement which appeared on pages 54 and 55 of the October 1948 issue of Electronics.

Constant research, improved technics, advances in the art, new, modern plant expansion, improved engineering, more efficient manufacturing equipment—now permit us to make available in increased quantities—Mycalex 410—molded—at prices comparable to other less efficient molded insulations.

MYCALEX 410 is now priced to meet rigid economy requirements

Any interest evidenced on your part in Mycalex products and services—will receive the prompt, courteous and intelligent attention of a competent Mycalex sales engineer. He will receive the fullest backing and cooperation from other factory executives—to serve you promptly—with a quality

product and at an economical and fair price.





Adaptability is a prime advantage you gain by using S.S.White flexible shafts to couple variable elements to their control knobs or dials.

The example above shows why. The flexible shaft coupling permits you to position both the condenser and its control knob independently of each other. Likewise, the flexible shaft that transmits the movement of the tuning control shaft through a worm gear to the indicating dial makes it possible to place the dial where desired.

This adaptability of parts provided by S.S.White flexible shafts greatly simplifies the problem of satisfying such design requirements as circuit efficiency, easy assembly, wiring and servicing.

S.S.White remote control flexible shafts come in α wide range of sizes and characteristics and can be supplied in any required length. Specially designed for remote control they are positive, sensitive and jump-free in operation.

GET DETAILS IN THIS FLEXIBLE SHAFT HANDBOOK

You can get a free copy of this informative 260-page book on flexible shaft application and selection by writing to us on your business letterhead and mentioning your position.



FLEXIBLE SHAPTS - FLEXIBLE SHAPT TOOLS - AIRCRAFT ACCESSORIES
SMALL CUTTING AND GRINDING TOOLS - SPECIAL FORMULA RUBBLES
MOLDED RESISTORS - PLASTIC SPECIALTIES - CONTRACT PLASTICS MOLDING

One of America's AAAA Industrial Enterprises



30 to 44-mc band. Power output of the transmitter is $\frac{1}{2}$ watt, obtained from two 2-volt storage batteries. The receiver has a $1\frac{1}{2}$ - μ v sensitivity for 20-db silencing, and selectivity is 85 db down at 100 kc and 40 db down at 40 kc.

Colorimeter

BROCINER-MASS INSTRUMENTS, INC., 1546 Second Ave., New York 28, N. Y. The Clinical Analyzer is a



photoelectric colorimeter calibrated for 60 clinical determinations. The instrument uses test tubes 17 and 11 mm in diameter. Five filters in a revolving disc permit quick selection.

Klystron Oscillators

RADIO CORP. OF AMERICA, Harrison, N. J., announces the 2K26 (illustrated) and 2K56 klystron oscillators of the single-resonator, reflex type intended primarily for use as local oscillators in microwave receivers. The 2K26 is designed for operation in the 6,250 to 7,060-mc



Nagnavox produces over 100 different speaker models exclusively for the manufacturing trade. From start to finish they are researched, designed and produced by engineers whose sole business is the making of better loud speakers... whose complete plant facilities are constructed specially for the quickest, most efficient manufacture of quality loud speakers!

The modern 2½-acre Magnavox Paducah factory is a model of engineering achievement. Everything from the building itself to the equipment and

method of line assembly used is new and different. And the innovations measure up! World-famous Magnavox speakers now are coming off the line at a greatly accelerated pace.

All the skill and experience Magnavox has amassed in thirty-three years of service to the radio industry combine with a complete line of quality speakers to make this modern new plant loud speaker headquarters! Write for catalog today.

The Magnavox Company, Sales and Engineering Offices, Components Division, Ft. Wayne 4, Indiana.

Magnavox is the oldest and largest producer of quality loud speakers

Magnavox

has served the radio industry for over 33 years

SPEAKERS . CAPACITORS . SOLENOIDS . ELECTRONIC EQUIPMENT

ALPHA TRI-CORE Rosin-filled

faster · more economical · more efficient

Alpha Tri-Core rosin-filled solder—with 3 cores instead of 1—gives you three times the "performance insurance" you get from ordinary solder. The simple facts are: You get more for your money with Alpha Tri-Core rosin-filled solder - more speed! More operations per pound! More operations per hour! In addition, Tri-Core permits the use of lower-tin-content alloys with superior soldering results to that obtained from ordinary solders with 5-15% more tin. Can you—can any manufacturer—afford to overlook such outright savings these days? Write for samples or trial order and put Alpha through your own tests in your own shop. It is the accepted solder by over 70% of electronic equipment manufacturers.



MORE FOR YOUR MONEY WITH ALPHA TRI-CORE ROSIN-FILLED SOLDER



SOLDER SPECIALISTS FOR OVER 58 YEARS

- 3 cores of flux instead of 1—at no extra cost!
- Even distribution of flux throughout . . . no fluxless areas!
- 22% more joints per pound of solder!
- 25% more joints per hour of soldering time!
- No high-resistance joints! No inspection rejects! No returns!
- 99.9% pure, water-white rosin used exclusively!
- No toxic fumes! Preferred by solderers everywhere!
- Absolutely non-corrosive; non-hydroscopic flux residue is glass-like in hardness and non-conductive!

other ALPHA PRODUCTS include:

TRI-CORE"ENERGIZED"ROSIN-FILLED SOLDER; TRI-CORE "LEAK-PRUF" ACID-FILLED SOLDER, SOLID SOLDER WIRE; PREFORMS (rosin and acid-filled); BAR SOLDER, ANODES AND FOIL.

PHA METALS, INC., 371 HUDSON AVENUE, BROOKLYN 1, NEW YORK

(continued)



range, and the 2K56 in the range from 3,840 to 4,460 mc. Both have a useful power output in the order of 100 milliwatts.

Remote Amplifier


RADIO CORP. OF AMERICA, Camden, N. J., has announced a lightweight, portable remote amplifier designed




to provide high-fidelity audio pickup for a-m and f-m broadcasts. The 3-channel amplifier, type BN-2A, has built-in power supply for use with standard 115-volt, 60-cycle outlets, but may also be batteryoperated. Each channel offers an overall gain of 92.5 db.

Electrolytic Capacitors

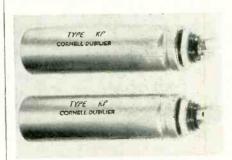CORNELL-DUBILIER ELECTRIC CORP., South Plainfield, N. J. Type KP



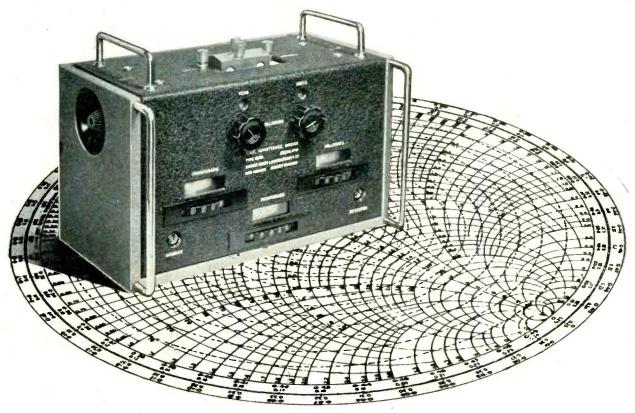A New Type of Bridge Makes Balanced Measurements at V.H.F.



HE use of tape-wound transformers on toroidal cores has made possible the development of a new type of high frequency bridge. The technique was originated in the Research Dept. of the B.B.C., who found it necessary to provide a more rapid and accurate means of measuring antennae, feeders and cables. Subsequent development by Wayne Kerr has considerably extended the field of application by

increasing the useful frequency range to above 100 Mc/s. The same principle is employed in a multi-ratio instrument having a wide range of application and high accuracy. The two bridges described are now in production and both offer the advantage that balanced and unbalanced measurements can be

V.H.F. BRIDGE Type B801 (Above) 1 Mc/s. to 100 Mc/s.

Ranges-Conductance: 0-100 m/mhos. Susceptance: Corresponding to +250 pfds.
General accuracy: 2%. R.F. BRIDGE Type B601

15 Kc/s.—5 Mc/s. Capacity: 0.1 pfds.—20,000 pfds. Resistance: 10 ohms.—10 megohms. Inductance: Values resonating above capacities between 15 Kc/s. and 5 Mc/s. General accuracy: 1% to 3 Mc/s.-2% to 5 Mc/s.





THE WAYNE KERR LABORATORIES LIMITED, NEW MALDEN, SURREY, ENGLAND

IF YOU NEED TIME DELAY ...



YOU NEED AGASTAT

Made in two types for direct current operation, and two corresponding types for alternating current operation:—


- 1. Time delay starts when coil is energized.
- 2. Time delay starts when coil is de-energized.

Time delay from .1 second to 5 or more minutes. Complete data from

A'G'A

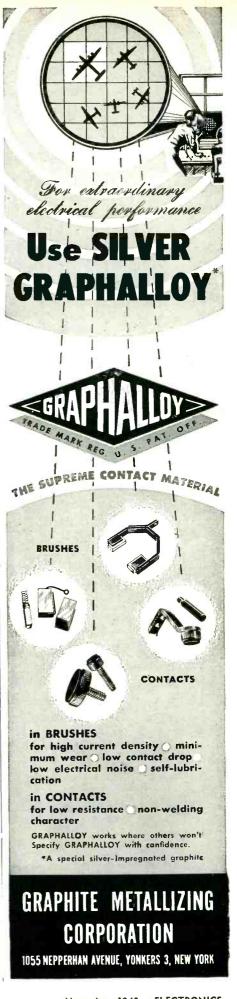AMERICAN GAS ACCUMULATOR COMPANY
1029 Newark Avenue • Elizabeth 3, New Jersey





electrolytic capacitors designed for electronic and communications equipment are available in two and three-lug terminal assemblies. Two-lug units can be had from 15 microfarads at 100 working volts to 80 microfarads at 450 working volts; three-lug terminals are suitable for either dual or triple capacitance units. Write for bulletin 123.

T-F Analyzer

FAIRCHILD CAMERA AND INSTRU-MENT CORP., 88-06 Van Wyck Blvd., Jamaica 1, N. Y. The transfer func-




tion analyzer has been designed for measuring the performance characteristics of servo systems. By means of the equipment, amplitude and phase of servos using signal frequencies between 50 and 800 cycles can be checked. It can also be modified for use with d-c systems.

Laboratory Power Supply

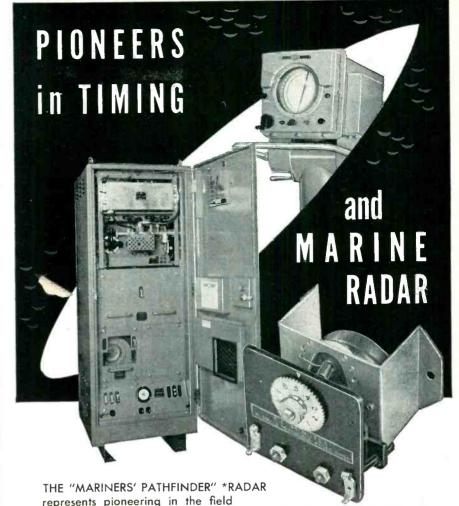W. GREEN ELECTRIC Co., INC., 130 Cedar St., New York 6, N. Y. The MR1 Multi-Rectifier power supply was produced to meet the need for a high-amperage laboratory unit. It





of navigation by the Raytheon Manufacturing Co. and in the field of timing by Haydon Manufacturing. The development of equipment components enabling today's ships to sail safely and on schedule in all weather is typical of Haydon's pioneering in the science of timing. Knowing that any equipment is only as good as its components, Raytheon relies on the quality of Haydon timers for dependable radar operation. In one model, a 5901 series time delay relay protects a magnetron tube by providing a 3 minute interval for tube warm-up prior to application of plate voltage. In another a Haydon timer provides a 5 second delay to allow a motor generator to attain operating speed. A third delays operation of rectifier tubes 45 seconds. In each instance engineering by Haydon and Raytheon is coupled to insure dependable operation.

For thoroughly reliable timing devices, take time to talk time with Haydon. See the Haydon insert in Sweet's File for Product Designers, or write for your own copy of the complete Engineering Catalog. An experienced field representative will be pleased to discuss your requirements and demonstrate Haydon timing at your desk.

* "Mariners' Pathfinder" is the trademark of Raytheon Manufacturing Co., denoting its commercial search radar.

WRITE 2411 ELM STREET, TORRINGTON, CONNECTICUT



MANUFACTURING COMPANY, INC

TORRINGTON

HARNESS TIME TO

CONNECTICUT

YOUR PRODUCTS

SUBSIDIARY OF GENERAL TIME INSTRUMENTS CORPORATION

Only AIR EXPRESS gives you all these advantages

A combination you don't get with other air-shipping methods

Special pick-up and delivery at no extra cost. Your shipments are picked up promptly when you call; fast delivery to consignee's door.

You get a receipt for every shipment, and delivery is proved by signature of consignee. One-carrier responsibility. Complete security.

Assured protection, too—valuation coverage up to \$50 without extra charge; 10 cents for each additional \$100 or fraction thereof.

These advantages, plus 21 others, make Air Express the best and fastest way to ship. Your shipments go on every flight of the Scheduled Airlines—repair parts, equipment, finished items keep moving to where they're needed. Reach any U.S. point in hours. Phone local Air Express Division, Railway Express Agency, for fast shipping action. Specify "Air Express" on orders for quickest delivery.

FACTS on low Air Express rates

22 lbs. machine parts goes 700 miles for \$4.73.
10 lbs. printed matter goes 1000 miles for \$3.31.
30-lb. carton of new fashions goes 500 miles for \$4.61.
Same day delivery in all these cases if you ship early.



AIR EXPRESS, A SERVICE OF RAILWAY EXPRESS AGENCY AND THE

SCHEDULED AIRLINES OF THE U.S.

is designed for operation from 220 or 440 volt, three-phase a-c, and has a flexible d-c output. Output voltage ripple content is about 5 percent.

Studio-Type Ribbon Mike

AMPERITE Co., INC., 561 Broadway, New York 12, N. Y. Frequency range of the new studio ribbon mi-



crophone models R80L & R80H is 40 to 14,000 cps; output is -56 db; harmonic distortion, less than 1 percent; discrimination with angle is 60 to 10,000 cycles. The unit is available in 200 ohms output, also in high impedance.

D-C Amplifier

MILLIVAC INSTRUMENTS, Box 3027, New Haven, Conn. Model DCA-1025 d-c amplifier has a 0 to 10 millivolt d-c input and 25 v, 1-milli-




ampere or 5-volt 3-milliampere d-c output. Its applications are the same as those of the model MV-17.A device but it can be used with either delicate or coarse output meters. Adjustable gain is included. A brochure gives further details.

Selenium Cell

INTERNATIONAL RECTIFIER CORP., 6809 South Victoria Ave., Los Angeles 43, Calif. The new type H selenium cells illustrated have a

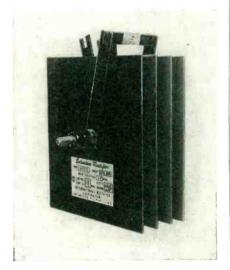maximum reverse voltage of 24 v rms with current ratings from 6 to 20 amperes depending upon the type of connection. Forward drop is about 1 volt. A brochure is available.




Miniature Controls

DAVEN Co., 191 Central Ave., Newark, N. J. A new line of attenuators with decreased dimensions is now in production. They are designed for use in equipment in which mounting space is limited and have the same mechanical and electrical construction as former units.

Speech Clipper

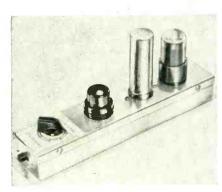ELECTRO-VOICE, INC., Buchanan, Mich. Model 1000 Speech Clipper




is a peak limiting preamplifier that clips the tops and bottoms from speech frequencies which rise above a preset amplitude, to provide higher articulation for communication services. Frequency response of the unit is from 200 to 3,000 cycles. Clipping is from 3 to 20 db.

Fidelity Speaker

RACON ELECTRIC Co., INC., 52 East 19th St., New York, N. Y. The Cel-

Shallcross

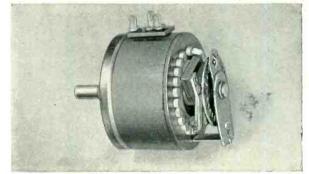

BRIDGED 'T' ATTENUATOR Type 410-481


10 steps, 4 db/step. Linear attenuation with detent. 21/6" diameter, 21/6" depth.

\$11.50

BRIDGED 'T' ATTENUATOR Type 420-2B2

20 steps, 2 db/step. Linear attenuation with off position and detent. 21/8" diameter, 21/16" depth.

> \$16.00 LIST PRICE

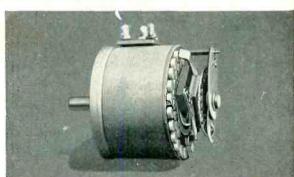

POTENTIOMETER Type C720-2A3

20 steps, 2 db/step, tapered on last three steps to off, composition resistors. 1 3/4" diameter, 1 3/4" depth.

\$8.00

These Shallcross Features Mean Better Performance— Better Value!

Off position attenuation well in excess of 100 db.

25% to 50% fewer soldered joints. Noise level ratings that are factual. (130 db. or more below zero level.)

Non-inductive Shallcross precision resistors used throughout assure flat attenuation to and beyond 30 kc.

Types and sizes engineered for all needs. Attenuation accuracies of 1%, Resistor accuracies of 0.1%, on special order.

SHALLCROSS ATTENUATORS

Shallcross variable attenuators have proved their remarkable quietness and service-ability in dozens of applications for leading users in all parts of the world. Such important details as the use of spring-temper silver alloy wiper arms, silver alloy collector rings and contacts, non-inductive precision resistors, and sturdy, substantial mounting plates have made possible the high standard of performance attributed to Shallcross.


Standard types include ladder and bridged T mixer controls, bridged T and straight T master gain controls and V.U. meter multipliers, wirewound and composition potentiometers for grid control. Cueing attenuators, and fixed pads, both composition and wirewound, in all circuit configurations are also available.

Write for Catalog and Attenuator Specification Sheet

SHALLCROSS MANUFACTURING COMPANY

Department E-118, Collingdale, Pa.



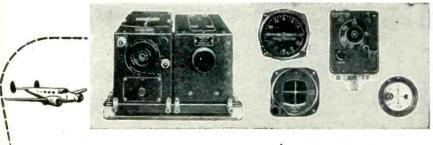

The Magic of VHF

Airborne Equipment for;

OMNI-DIRECTIONAL RANGES
RUNWAY LOCALIZERS
VISUAL-AURAL RANGES
SIMULTANEOUS VOICE
GCA VOICE RECEPTION

The Type 15A VHF Navigational Receiving Equipment (illustrated) provides for reception on the new Omni-Directional Ranges as well as operation on both types of VHF Runway Localizers, and the VHF Visual-Aural Airways Ranges. Simultaneous voice feature is included on these ranges. The tunable A.R.C. Receiver permits selection of any VHF aircraft frequency.

The A.R.C. Type 17 or A.R.C. Type 18 is the companion communication equipment normally associated with the Type 15A. The Type 17 VHF Communication Equipment adds independent two-way VHF communication facilities. The Type 18 adds VHF Transmitting Equipment only. All Type 17 and 18 units are type-certificated by the CAA.

The dependability and performance of these VHF Communication and Navigation Systems spells increased safety in flight. Specify A.R.C. for your next installation.



Aircraft Radio Corporation

DEPENDABLE ELECTRONIC EQUIPMENT SINCE 192



lular Grand has a new type cellular horn with horizontal distribution angle of 120 degrees and vertical distribution of 60 degrees. A resistive-capacitive filter network is included. Frequency range is 50 to 12,000 cycles.

Street Lighting Control


FISHER-PIERCE Co., INC., Boston 21, Mass. announces the series 63300



photoelectric street lighting control with a capacity of 3,000 watts of incandescent lamp load. Models are available for both 120 and 230 volts, 50-60 cycles. Standard turnon adjustment is 0.5 foot-candle with turn-off at 1.25 foot-candles.

Interval Timer

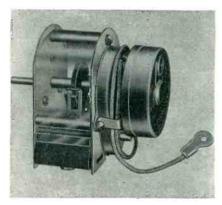HAYDON MFG. Co., INC., Torrington, Conn. A new multipurpose interval



timer is now available in the 8006 series. Several different models in the series are used for varying applications such as multiple sequence switching.

Portable Picture Monitor

POLARAD ELECTRONICS Co., 9 Ferry St., New York 7, N. Y. Model 102-






- Specifically designed for the new long playing records...low mass stylus assembly
- Equipped with 1 mil tip radius sapphire stylus
- Can be used with standard G-E preamplifiersPlace your order today!

General Electric Company, Electronics Park, Syracuse, New York

168-G10A



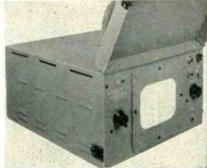

MPS portable television picture monitor has a maximum resolution in excess of 500 lines and employs a 7-inch electromagnetic deflection picture tube. The equipment operates with a minimum video input signal 1 volt peak-to-peak.

Line Match Indicator

AERONAUTICAL COMMUNICATIONS EQUIPMENT, INC., 3090 Douglas Road, Miami, Florida. Model LMI-




500 illustrated is a device for aiding adjustment of load for optimum line match at frequencies from 0.2 to 2 mc, or 2 to 20 mc. Model LMI-72 is used for coaxial lines at frequencies between 0.2 and 10 mc.

Rotary Beam Calculator

GORDON SPECIALTIES Co., 542 S. Dearborn St., Chicago 5, Ill. Dimensions for various types of beam antennas to operate in the region between 10 and 30 megacycles can be found quickly with a new calculator. Values for capacitance and inductance required for resonance between 5 and 60 mc are given, along with other information such as length of supporting boom required for various arrays. Price direct is \$1.60 which includes postage.

Cable Reel

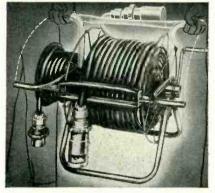
INDUSTRIAL ELECTRICAL WORKS, 1509 Chicago St., Omaha 2, Ne-



braska. With a capacity of 300 feet of \(^3\)-inch four-conductor cable, or equivalent, the Powereel illustrated can be used for all types of cables. Each reel has either three or four collector rings of beryllium copper with double contact copper brushes.

Transducers

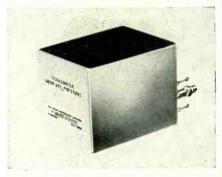KOLLSMAN INSTRUMENT DIVISION, 80-08 45th Ave., Elmhurst, N. Y. Important in flight testing and con-



trol applications for pilotless aircraft the new, small transducers, one of which is illustrated, provide means of obtaining electrical signals that are functions of air speed, altitude, differential pressure, and gage pressure.

Dynamic Micrometer

ELECTRO PRODUCTS LABORATORIES, INC., 549 W. Randolph St., Chicago 6, Ill., has developed a dynamic mi-





Callite Tungsten Corporation
544 Thirty-ninth St., Union City, N. J.

*Manufactured by the well-known Radiation Counter Laboratories, Inc. of Chicago. Hard glass leads, welds, tungsten and molybdenum, wire, rod, sheet, formed parts, and other materials for incandescent lamps and electronic tubes.

GRAY TRANSCRIPTION ARMS and EQUALIZERS



The GRAY TRANSCRIPTION ARM 103-LP, with Selected GE Variable Reductance Cartridge with 1 mil Diamond Stylus, has been especially designed for use with the new LP Micro-Groove Records. Due to such features as adjustable stylus pressure, frictionless motion, self-leveling base and the accommodation of any standard cartridge, arm obsolescence is precluded. Arm, with 1 mil Diamond Stylus Cartridge, \$77.95.

The GRAY #601 4-position EQUALIZER for GE Cartridge, finest performance and workmanship, ideal response curves. Adopted by radio networks. Matches pickup to microphone channel. Complete, \$49.50.

Inquiries invited for development and manufacturing.

GRAY RESEARCH & DEVELOPMENT COMPANY, Inc.

16 ARBOR STREET

HARTFORD 1, CONN.



3½ KW
VACUUM TUBE
BOMBARDER

or
INDUCTION
HEATING UNIT




Only \$975

Never before a value like this $3\frac{1}{2}$ KW bombarder or high frequency induction heater . . . for saving time and money in surface hardening, brazing, soldering, annealing and many other heat treating operations. Is

Portable . . . mounted on four rubber coasters. Width 14½"; depth 27"; height 42½"; weight 300#.

Operates from 220 volt line. Complete with foot switch and one heating coil made to customer's requirements. Send samples of work wanted. We will advise time cycle required for your particular job. Cost, complete, only \$975. Immediate delivery.

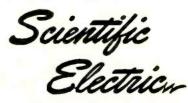Scientific Electric Electronic Heaters are made in the following ranges of power: 1-2-3-5-7 $\frac{1}{2}$ -10-12 $\frac{1}{2}$ -15-18-25-40-60-80-100-250. KW.



Division of

"S" CORRUGATED QUENCHED GAP CO.

105 - 119 Monroe St., Garfield, N. J.

crometer for measuring movement. radial displacement, or vibration of any part made of ferrous material. Displacement is read in tenths of a thousandth of an inch and accuracy is the same for a static condition as for a dynamic condition corresponding to speeds up to 200,-000 rpm. Total weight is 27 pounds.

Wavemeter

SIMPSON ELECTRIC Co., 5218 West Kinzie St., Chicago 44, Ill. Model



380 wavemeter is a pocket-size instrument for use by amateurs, ships, police radio, and similar services. Provision is also made for checking percentage of modulation. Separate coils are provided for the 10 to 80-meter amateur bands. A 2-foot antenna is furnished to be plugged into a jack on the instrument. Frequencies as high as 420 megacycles can be checked.

Flexible Waveguide

AIRTRON, INC., 650 Bloomingdale Road, Staten Island, N. Y. A new type of convoluted bellows electro-



ELECTRONICS - November, 1948



On every count the new Turner Model 20X has won the vote of users. Response to voice and music pickups is smooth and even over a desired range of frequencies. Output level is remarkably high. Engineered for dependable service indoors or out with high quality moisture sealed crystal circuit. Light in weight, natural to hold, and most convenient to use. It is equipped with hook ring for hanging. Attractive case is finished in rich baked brown enamel. And the price, complete with 7 ft. cable is exceptionally low.

Write for Complete Microphone Literature

COMPANY TURNER THE Cedar Rapids, Iowa


905 17th Street N. E.

Crystals licensed under patents of the Brush Development Co

Microphones BY TURNER



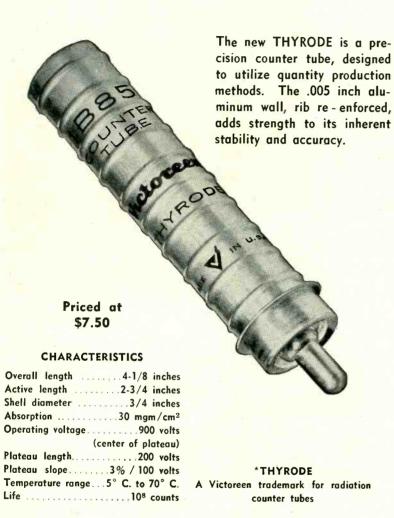The G.M. counter tube reaches maturity in the new all metal *THYRODE 1885



Victoreen radiation measuring instruments for laboratory and field determinations together with such components as the VX series subminiature electrometer tubes, vacuum sealed hi-meg resistors and G-M counter tubes have made notable contributions to the present refinement of radiation instrumentation.

Victoreen 5806 Hough Avenue Cleveland 3, Ohio

plated flexible waveguide is now available having an electrical impedance matching that of rigid waveguide. Sizes down to that required for 1 cm can be supplied.

Alpha Counter


INSTRUMENT DEVELOPMENT LABORATORIES, INC., 223 West Erie St., Chicago 10, Ill. Model 117 alpha



counter will count alpha particles in the presence of a strong beta background. Unit consists of a methane flow proportional counter, high-gain amplifier, scaler (256 to 1), impulse recorder, and variable high-voltage supply.

Phone Plug

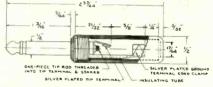
SWITCHCRAFT, INC., 1328 N. Halsted St., Chicago 22, Ill. The Little-



Plug illustrated features a sleeve terminal that can be clamped over the metal braid of shielded wire cables to form both mechanical anchor and electrical connection. If the terminal is used only for mechanical anchorage an extra lug can be used for connection to the sleeve of the plug.

Blowers

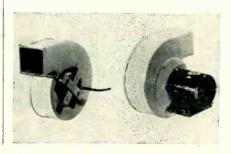
JOHNSON FAN & BLOWER CORP., 1319 W. Lake St., Chicago 7, Ill. Type 5CB centrifugal fans have a



wheel diameter of 5 inches. Various sizes of motors and different fan combinations can be furnished for many applications in cooling electrical and electronic equipment.

Multiple Control Unit

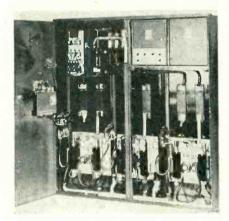WELTRONIC Co., 19446 W. Eight Mile Road, Detroit 19, Mich. Model 312KS2, a 3-phase multiple control combination, has a remote control



relay timer which provides a variety of multiple welding sequences with independent dial adjustment of weld time on each phase. Automatic control circuit protection is incorporated. Write for detailed information on standard and supplementary equipment.

Plug-Tip Soldering Iron

HEXACON ELECTRIC Co., 130 W. Clay Ave., Roselle Park, N. J.



Model P212 electric soldering iron is rated at 200 watts with a halfinch diameter tip.

Literature_

Allen B. C-R Tube Primer. DuMont Labs., Inc., 1000 Main Ave., Clifton, N. J. A 63-page manual presents an excellent nontechnical discussion of the cathode-ray tube and its functions. The book is available without cost to anyone professionally engaged in electronics or teaching the sub-



THE problem of meeting new power and frequency requirements in communications systems, with minimum obsolescence, is solved by the Telepak line of transmitting equipment, the latest achievement in this field by Radio Receptor.

Telepak consists of a basic frame supporting a series of separately and easily

removable units or cells of standard construction, varying in height according to power requirements. These unit assemblies are housed in standard cabinets, as illustrated. Any cell may be easily removed to permit servicing or replacement

by a new unit of different function or frequency. This adaptability offers another advantage as it permits the combination of units of all ratings in a single installation. Units are available in power output ratings varying from 500 watts to 3 kilowatts.

Remote control elements are also on the unit cell basis, and are capable of expansion along with other elements in the system.

It will pay you to look into the many exclusive features of Telepak, Radio Receptor's new transmitting system that enables you to keep in step with Progress.

Write for the new Telepak Handbook containing information of value to every engineer. Address Department C-10



Communications Division RADIO RECEPTOR COMPANY, INC. (P)

Since 1922 in Radio and Electronics

251 WEST 19th STREET • NEW YORK 11, N. Y.





THE NO. 92105

Single Sideband Selector

The No. 92105 is designed to permit Single Sideband Selection with existing receivers. Full technical details in April 1948 QST. Produced in co-operation and under exclusive U. S. patent license (2,364,863 and others) with the J. L. A. McLaughlin Research Laboratories.

MFG. CO., INC.

MAIN OFFICE AND FACTORY

MALDEN

MASSACHUSETTS



NEW PRODUCTS

(continued)

ject, and others may obtain it at 50 cents per copy, or at \$2.50 in lots of a dozen.

Data Handling Systems. Teleregister Laboratories, 157 Chambers St., New York 7, N. Y. The engineering services available for teleregister systems covering everything from parimutual totalizers to inventory and production control are described and representative equipment is illustrated in a 24-page booklet.


Motor Speed Control. Servomechanisms Inc., Mineola, N. Y. The new motor speed control SC104 provides a speed range of 40 to 1 for armature output of 5,000 rpm maximum. Torqueversus-speed curves are given in a page descriptive sheet.

Connector Catalog. American Phenolic Corp., Chicago 50, Ill. Catalog A-1 on AN connectors and fittings for power, signal, and control circuits, lists thousands of sizes and graphically illustrates the different types of shells and insert arrangements available for each. Dimensions and electrical data are shown in detail.

Magnetic Tape Recorders. Ampex Electric Corp., 681 Fifth Ave., New York 22, N. Y. An 8-page booklet describes and illustrates chief features of the model 200-A magnetic tape recorder. The unit has already been tested on continuous commercial network operation.

Tube Information. Radio Corp. of America, Harrison, N. J. Technical data on types 6BA7 and 12BA7 pentagrid converters has been published, as well as application notes on receiver sensitivity measurements at high frequencies, and a brochure on improved arrangement of base pin connections in new miniatures.

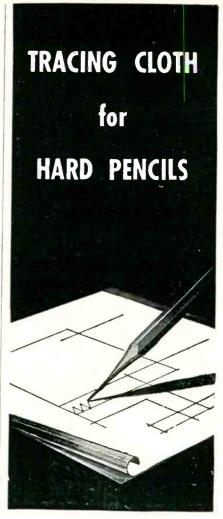
Attenuator Pad. Weinschel Engineering Co., 123 William St., New York 7, N. Y., has issued a folder describing the model 50-L/p-x coaxial attenuator pad with atten-



• Imperial Pencil Tracing Cloth has the same superbly uniform cloth foundation and transparency as the world famous Imperial Tracing Cloth. But it is distinguished by its special dull drawing surface, on which hard pencils can be used, giving clean, sharp, opaque, non-smudging lines.

Erasures are made easily, without damage. It gives sharp, contrasting prints of the finest lines. It resists the effects of time and wear, and does not become brittle or opaque.

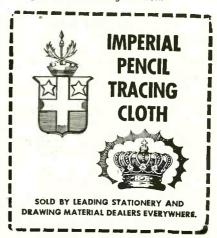Imperial Pencil Tracing Cloth is right for ink drawings as well.



November, 1948 - ELECTRONICS

(continued)

uation between 5 and 25 db and a 50-ohm characteristic impedance. Specifications are included.

Tube Data. General Electronics, Inc., 101 Hazel St., Paterson, N. J. A recently issued folder gives technical data for a large line of transmitting tubes, rectifiers and vacuum capacitors. Prices are also listed.

Recording Wire. Fidelitone Inc., 1616 Devon Ave., Chicago 26, Ill. Bulletin No. 9 gives informative and semitechnical data comparing the 0.004 and 0.0036-inch diameter wire for magnetic wire recording.

Electrical Insulation. Insulation Manufacturers Corp., 565 West Washington Blvd., Chicago 6, Ill. Outstanding features of the Dieflex varnished tubings or sleevings are set forth on two sides of a sheet. A variety of grades and sizes of the products may be obtained.

Radio Link Equipment. Federal Telecommunication Laboratories, Inc., 67 Broad St., New York 4, N. Y. Special features, illustration and general description, and technical characteristics of a variety of radio link equipment, a monitor, and dummy load are treated in five loose-leaf folders now available.

Quartz Crystals. Reeves-Hoffman Corp., Carlisle, Pa. Bulletin RHC-X covers an assortment of crystal units ranging from 50 kc to 100 mc. Ordering instructions are included.

Automatic Controls. Leeds & Northrup Co., 4934 Stenton Ave., Philadelphia 44, Pa., has issued a newly-revised, 40-page catalog on position-adjusting and electrically-actuated control equipment. Both Micromax and Speedomax instruments are listed. Ask for catalog ND4A(1).

Tube Catalog. Amperex Electronic Corp., 25 Washington St., Brooklyn 1, N. Y. The new 296-page

Investigate COPPER ARMORED SISALKRAFT

Reinforced with tough

Sisal Fibres

for electrostatic shielding of

TELEVISION AND RADIO STUDIOS, TESTING ROOMS, INDUSTRIAL LABORATORIES, AND DIATHERMY, RADAR AND ELECTRONIC EQUIPMENT

The success of COPPER ARMORED SISALKRAFT for shielding during the past decade suggests that you might find this reinforced "electro sheet copper" product practical for rooms and large enclosures or equipment requiring electrostatic shielding.

SISALKRAFT engineers do not presume to be authorities on this complex subject. We shall be glad to cooperate, however, on the basis of experience gained in such installations as:

Steinmetz Hall, New York • Hollywood Television Studio of Don Lee WBKB Radio Station, Chicago • Sentinel Television Testing Rooms Corn Products Company's Argo Laboratory • Delco Radio Sets CBS Radio Testing Laboratories

... and other applications that indicate the merit of COPPER ARMORED SISALKRAFT in these and allied fields.

COPPER ARMORED SISALKRAFT is available in 1-oz., 2-oz., and 3-oz. weights, in rolls 4" to 60" wide. Reasonable cost . . . as low as \$9.75 per 100 square feet. Send for samples.

COPPER ARMORED SISALKRAFT

	FT CO., Chicago 6 • New York 17 • San Francisco
Please send samples of	, 205 W. Wacker Drive, Dept.E-2, Chicago 6, III. One-Ounce; Two-Ounce; Three-Ounce COPPER he use I contemplate involves (describe briefly)
0.000,000000000000000000000000000000000	
Name	



Greater Strength
& Rigidity!
Less Corrosion!
Better Contacts!
Longer Life!

The new streamlined design of ADC Jacks uses heavier gauge metal for greater strength. The frame is die-formed and press-welded for utmost rigidity and dimensional accuracy.

Silver-alloy contacts and genuine Nickel Silver springs guarantee corrosion resistance, even under the most humid conditions.

All the way through, the new ADC is a better jack! If you require top quality and precision-made components, ADC Jacks merit your *first* consideration.

See Your Jobber or write today for ADC CATALOG



catalog covers a line of electronic tubes for communications, industrial, amateur, and electromedical uses. Contents are grouped under four headings: air-cooled power tubes, water and forced-air cooled power tubes, rectifier tubes, and vacuum capacitors. Full data are given on each tube. A formal request to Amperex will bring your copy to you.


Magnetic Sub-Assemblies. General Electric Co., Chemical Dept., Pittsfield, Mass. Booklet CDM-16 describes and illustrates a line of permanent magnet sub-assemblies for engineering and production economy. Ordering instructions are included.

Sound Products Catalog. Radio Corp. of America, Engineering Products Department, Camden, N. J. Catalog 218P lists in 84 pages a complete line of sound equipment. Concise descriptions of each model include such information as special features, uses, specifications, photographs and diagrams.

Electrical Tapes. Minnesota Mining & Mfg. Co., 900 Fauquier Ave., St. Paul 6, Minn., announces a new 24-page two-color catalog describing 39 Scotch brand electrical tapes. Tape properties are listed and eighty-six applications illustrated.

Radioteletype Converter. George J. Maki, Radiotelegraph Engineering, Moraga, Calif. Description, block and circuit diagrams, and specifications of the model RC-55 frequency-shift radioteletype converter may be found in a new booklet.

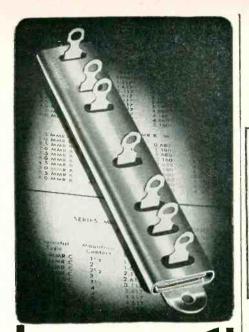Vacuum Measurement. George E. Fredericks Co., Bethayres, Pa., has available a new 28-page booklet on vacuum measurement. Written in nontechnical language, it is intended for the layman interested in the proper selection and use of vacuum gages for industrial processes.



VOLTAGE VOLTAGE DIVIDERS

★ Clarostat Series MMR bakeliteinsulated metal-clad resistors run definitely COOLER than any other similar types, SIZE FOR SIZE. Or putting it another way, these strip resistors will DISSIPATE MORE POWER for the same temperature rise, SIZE FOR SIZE.

Hundreds of thousands in daily use!They tell their own story!

Resistance values from fraction of ohm to 15,000 ohms per winding inch. In standard, inverted and vertical mounting types. Any number of intermediate taps within reason. 5 watts per winding inch mounted on metal radiating surface; 2½ watts in free air.



Engineering Bulletin 109 on request.
Let us quote.




CLAROSTAT MFG. CO., Inc - - - DOVER, N. H.

in Canada: CANADIAN MARCONI CO., Ltd.
Montreal, P.Q., and branches

GIVE YOUR FAMILY THIS GIFT OF A LIFETIME AN ALTEC LANSING

home music system

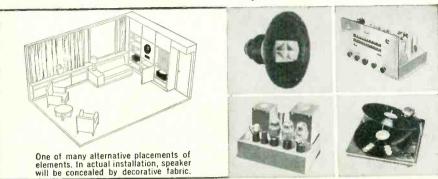

As an engineer with professional knowledge of the science of audio reproduction, you can appreciate more thoroughly than any layman the incredible life-like reproduction of voice and music of which this magnificent Altec Lansing Home Music System is capable. Added to the lifetime enjoyment which this system will provide is the pleasure of installing it yourself. Full instructions are included. This system transcends the inherent limitations of commercial radio-

161 Sixth Avenue, New York 13, N. Y. 1161 N. Vine Street, Hollywood 38, Calif.



phonographs, yet costs are favorable to this system. The system includes the famous Altec Lansing Duplex speaker, a special Altec Lansing amplifier, a newly designed TRF Altec Lansing tuner, and the Webster 70 changer. Built-in Altec Lansing Daylight Television can also be included.


A brochure will be sent on request.


ALTEC

LANSING

custom-in-built

bome music system

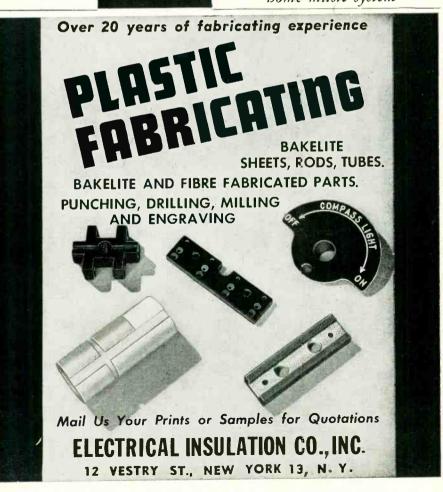

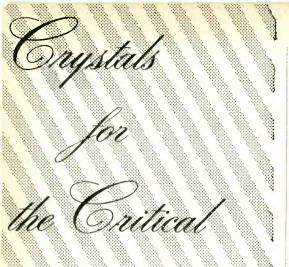

STABILIZED CRYSTALS TO MEET EVERY NEED

Whatever your crystal needs, James Knights Co. is equipped to satisfy them quickly and economically.

To effect greater savings for you on short runs, a special production system has been established.

We are also equipped to quickly build "Stabilized" crystals to your exact specifications. In addition, James Knights Co. fabricates a complete line of "Stabilized" crystals to meet every ordinary need—precision built by the most modern methods and equipment.

For quality—speed—economy, contact the James Knights Co. You'll be glad you did!

New James Knights Catalog On Request



A university physicist wanted a 2" supersonic X-cut crystal. The James Knights Company made it promptly, and has since delivered many other special crystals for the same university.


74e James Knights Co.

SANDWICH, ILLINOIS



NEWS OF THE INDUSTRY

(continued from p 134)

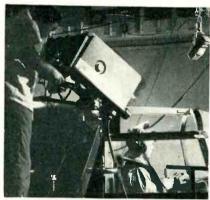

Televising cockpit mockup of P2V Neptune during Navy flight training lecture. Studio has two GE cameras like this and two DuMont cameras


vision receivers of various types will be used under a variety of conditions and with screen sizes ranging from that of a 10-inch tube on up to that projected onto a 9 by 12-foot screen. Also under investigation will be methods of instruction best adapted to the television medium and the design of the ideal television classroom. Tryouts of talkback circuits are contemplated, so that students anywhere in widely scattered classrooms can ask questions of the instructor during or after a lecture.

Advantages of Television

With television, lectures by the Navy's best instructors can be presented to as many students as desirable, all at one time. During emergencies or accelerated wartime training programs, increased utilization of top notch men would justify holding them for training purposes, where they can do more good than on combat assignments.

Lectures and demonstrations of newly developed devices can be presented immediately by television, with no passing on of training from one instructor to another. If necessary, the pilot model itself can be used for demonstration. Since only one demonstration device is needed more money can be spent on its development and construction. Security can be maintained by guarding coaxial terminal points and by scrambling the r-f signal, where necessary.

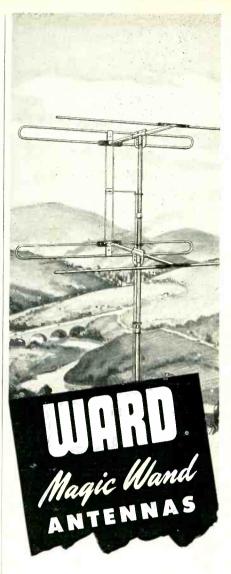Television training gives every student a front-row seat, where he can see every movement of the in-



THE ONLY BROAD BANDED, HIGH GAIN, STACKED ARRAY ON THE MARKET

Many times more sensitive for TV reception in fringe areas and poor signal locations, the WARD TVS-6 STACKED ARRAY achieves maximum forward gain by stacking two high gain folded dipoles and reflectors with effective 1/2 wave spacing rather than the ordinary 1/8 or 1/4 wave which materially reduces sensitivity. THE ONLY STACKED ARRAY ON THE MARKET THAT IS BROAD BANDED, it will give excellent results with MANY CHANNELS where others are too selective. The advanced engineering and PRE-ASSEMBLED design of the WARD TVS-6 is only one of the reasons why WARD is the largest exclusive manufacturer of antennas in the world, See any leading parts distributor or write for catalog.

THE WARD PRODUCTS
CORPORATION

1523 E. 45TH STREET, CLEVELAND 3, OHIO.

November, 1948 - ELECTRONICS

Save Time...Speed Assembly with CTC ALL-SET Boards!



On the assembly line and in the laboratory, CTC ALL-SET Boards are valuable time-savers.

With Type 1558 Turret Lugs, a new board now offers mounting for miniature components. 1 1/16" wide, 3/32" thick, only. (Type X1401E.)

With Type 1724 Turret Lugs, boards come in four widths: $\frac{1}{2}$ ", 2", $\frac{21}{2}$ ", 3"— in $\frac{3}{32}$ ", $\frac{1}{8}$ ", $\frac{3}{16}$ " thicknesses.

With the addition of the new miniature board, CTC ALL-SET Boards now cover the entire range of components.

All boards are of laminated phenolic, in five-section units, scribed for easy separation. Each section drilled for 14 lugs. Lugs solidly swaged into precise position ... whole board ready for your assembly line.

SPECIAL PROBLEMS

Custom-built boards are a specialty with CTC. We're equipped to handle many types of materials including the latest types of glass laminates... many types of jobs requiring special tools... and all types of work to government specifications. Why not drop us a line about your problem? No obligation, of course.



CAMBRIDGE THERMIONIC CORPORATION

437 Concord Avenue, Cambridge 38, Mass.



PILOT LIGHT ASSEMBLIES

PLN SERIES—Designed for NE-51 Neon Lamp

Features

- THE MULTI-VUE CAP
- BUILT-IN RESISTOR
- 110 or 220 VOLTS
- EXTREME RUGGEDNESS
- VERY LOW CURRENT

Write for descriptive booklet


The DIAL LIGHT CO. of AMERICA

FOREMOST MANUFACTURER OF PILOT LIGHTS

900 BROADWAY, NEW YORK 3, N. Y.

Telephone-SPring 7-1300




 

(continued)

structor clearly. The television camera scales demonstration models up or down to proper size for most effective training.

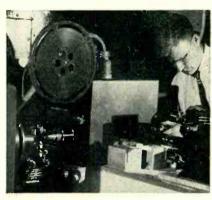With television, usable portions of obsolete motion picture training film can be salvaged and brought up to date by combining with personal demonstrations. Students lose interest in films showing obsolete planes, for instance, yet basic prin-



Two 35-mm slide-strip film projectors and a 16-mm sound film projector here feed into a GE film camera located under the control room of the Navy's television studio at Sands Point, Long Island. Two full-silvered front-surface mirrors make possible permanent mounting of all three sources, any of which can be cut into a studio program at will

ciples involved remain the same. Unparallelled flexibility in choice of instruction material is another advantage. The lecturer can change at will from models to artwork, maps, diagrams, motion pictures, film strips, slides, demonstration devices, training devices and actual service gear.

Though television offers promise of better instruction, it does not eliminate all instructors. Rather, it permits use of local laboratory instructors and assists them with the best of lecture help. It is not intended for teaching all subjects; introduction sessions to courses and the more difficult sessions offer greatest promise. Whether television will actually reduce learning time through use of new and more effective techniques is not yet known.

Radio Parts Show and RMA Silver Anniversary

PLANS HAVE BEEN made for a gala radio industry celebration in Chicago during the week of May 15, 1949, combining the RMA Silver



NEW BARRY CATALOG Describing Equipment and Methods Used in Shock and Vibration Control Many Designers and Engineers will use

WINDING LABORATORIES

9 ALBERMARLE AVE., TRENTON 3, N. J.

this Barry Catalog as a reference book. It contains Fundamental Vibration Charts, describes basic problems in shock and vibration control.

The new catalog illustrates and describes Barrymounts and their applicafions.

BARRYMOUNTS Control VIBRATION and IMPACT

We offer a complete line of highly engineered Vibration and Impact isolators for commercial, industrial, and military applications . . . also an engineering consulting service on special problems.

> Send for **NEW CATALOG**

Name	
Company	itle
Street	
City S	itate

THE BARRY CORPORATION

of and Vibration Control


179 SIDNEY STREET .. CAMBRIDGE 39, MASS

THE	BARRY CORPORATION
*	Formerly L. N. BARRY CO., INC. 177 SIDNEY STREET CAMBRIDGE, MASS.



HUNDREDS OF AUTHORS

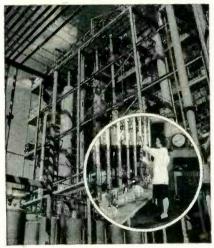Thanks to the cooperative efforts of hundreds of scientists and engineers in almost every field of industry, we have been able to compile a comprehensive new booklet about DC 200 Fluids.



In early 1943 glass distillation columns supplied the demand for silicone products. By 1944, we had completed a multi-million dollor plant to supply wor time requirements. During the past four years plant capacity has been tripled to supply the domestic and foreign markets.

We had been producing DC 200 Fluids for less than a year when we published a 4-page leaflet describing these remarkably stable silicone fluids. Our newest publication is a 32-page booklet describing some of the more typical applications and giving data on the more significant properties of the DC 200 Fluids.

This volume of information is evidence of a unique and useful combination of properties in the fluids themselves. It is proof of the ready acceptance given to these basically new materials by scientists, engineers and technicians in almost every industry. They have improved the performance of all sorts of devices by capitalizing on the properties of DC 200 Fluids. We, in turn, have gained knowledge and experience by giving technical assistance.


The benefits of our years of research and experience in producing DC 200 Fluids and in adapting them to many different applications are made available in booklet No. N-C-13. We hope that you will call on the technical representatives assigned to each of our branch offices for any additional information or assistance.

DOW CORNING CORPORATION MIDLAND, MICHIGAN

In Canada: Fiberglas Canada, Ltd., Toronto In England: Albright and Wilson, Ltd., London



you Manufacture...

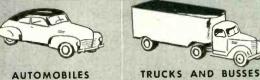

TRUCKS AND BUSSES







YOU CAN SAVE 3 Ways

WITH ESSEX "PACKAGED" WIRING HARNESS.....

1 Engineering

2 First Cost

Installation

Scores of users have found that they save time, trouble and money by turning their electrical wiring harness problems over to Essex specialists.

Essex One-Source service handles the intricate job of producing lighting, ignition and control harness assemblies custom-built to your exact specifications and complete with all manual and electrical control devices for quick, efficient installation.

Through intensive specialization in wiring harness assemblies, Essex has developed line production methods of manufacturing, assembly and inspection, for economical production of high grade, individually tested, specially engineered assemblies.

INVESTIGATE ESSEX "ONE-SOURCE" SERVICE TODAY!



CORPORATION

MBLY AND CORD SET DIVISION SALES DEPARTMENT

MONTICELLO, INDIANA

Sales Offices: Chicago, Ill.; Cleveland, Ohio; Dayton, Ohio; Dettoit, Mich.; Kansas
City, Mo.; Los Angeles, Calif.; Milwaukee, Wis.; Newark, N. J.; Philadelphia, Pa.;
San Francisco, Calif.; St. Louis, Mo.



GENEVA, ILLINOIS

HAS THE TOPS

FM TRANSLATOR General Electric Model XFM-1



ross-war version of the old G.E. J.F.M-90 Translator which was used and enjoyed by tens of thousands of discriminating radio listeners.

Covers 88-108 mc range, dial 12 inches long, uses guillotine tuning for highest efficiency, high stability. Designed for export, has power inputs for 110 to 250 volts, 50/60 cy. Used in conjunction with good audio section or separate amplifier will provide best FM listening you ever heard. In attractive natural walnut cabinet — 10¾" high x 15¾" wide x 11¾" deep, complete with 8 tubes. Iropic-proof construction. Quantity limited.

Special Price \$49.50 TECHMASTER TV KIT



LS-3 SPEAKER



Signal Corps model, 6" PM s p e a k e r, weather resistant, in rugged crackle finish steel case. Complete with self-contained transformer to match 4000-ahm load. Voice coil im-

pedance 6-8 ohms. Ideal for many uses.

Harvey Special\$4.95

All prices Net, F.O.B., N.Y.C. Subject to Change Without Notice



NEWS OF THE INDUSTRY

Anniversary convention and the annual Radio Parts Industry Trade Show. Events will be climaxed by a banquet on Thursday, May 19, at the Stevens Hotel.

(continued)

The Parts Show management also decided to broaden the eligibility rule for exhibits by parts and components manufacturers to give limited exhibition privileges in the 1949 show to parts manufacturers selling to set manufacturers or other industrial outlets, in addition to manufacturers selling to jobbers, heretofore admitted.

IRE Fellowships

At the September meeting of the IRE board of directors, the following members of the Institute were elected to the grade of Fellow:

elected to the grade of Fellow:


H. A. Affel of Bell Telephone Laboratories, New York, N. Y., K. C. Black of Aircraft Radio Corp., Boonton, N. J.; J. E. Brown of Zenith Radio Corp., Chicago, Ill.; Cledo Brunetti of National Bureau of Standards, Washington, D. C.; W. L. Carlson of RCA Laboratories, Princeton, N. J.; P. S. Carter of RCA Labs, Rocky Point, N. Y.; F. E. d'Humy of Western Union Telegraph Co., New York, N. Y.; John N. Dyer of Airborne Instruments Laboratory, Mineola, N. Y.; L. A. Gebhard of Naval Research Laboratory, Washington, D. C.; T. T. Goldsmith, Jr. of Allen B. DuMont Laboratories, Passaic, N. J.; F. W. Grover of Union College, Schenectady, N. Y.; E. A. Guillemin of MIT. Cambridge, Mass.: Ross Gunn of U. S. Weather Bureau, Washington, D. C.; A. V. Haeff of Naval Research Laboratory, Washington, D. C.; L. C. Holmes of Stromberg-Carlson Co., Rochester, N. Y.; J. Kelly Johnson, consulting engineer, New York, N. Y.; S. R. Kantebet of the Government of India Overseas Communication Service, Bombay, India; W. B. Lodge of Columbia Broadcasting System, New York, N. Y.; K. A. MacKinnon, consulting engineer, Ottawa, Ontario, Canada; H. F. Olson of RCA Laboratories, Princeton, N. J.; G. D. O'Neill of Sylvania Electric Products, Inc., Flushing N. Y.; L. S. Payne of Canadian Marconi Co., Ltd., Montreal, Canada; L. M. Price of Radio Valve Co. of Canada, Toronto, Canada; H. J. Reich of Yale University, New Haven, Conn.; J. D. Reid of Crosley Division of Avco Mfg. Corp., Cincinnati, Ohio; Karl Spangenberg of Stanford University, Calif.; George Sterling of the PCC, Washington, D. C.; C. E. Strong of Standard Telephones and Cables, Ltd., New Southgate, London, England; Franz Tank, Institut fur Hochfrequenz Technik, Zurich F. Switzerland; W. N. Tuttle of General Radio Co., Cambridge, Mass.: I.

It was also announced by the board that the Institute's Medal of Honor would be awarded to Ralph Bown, director of research at Bell Telephone Laboratories and member of the Joint Technical Advisory Committee of the RMA and IRE.

Midwest Television Networks

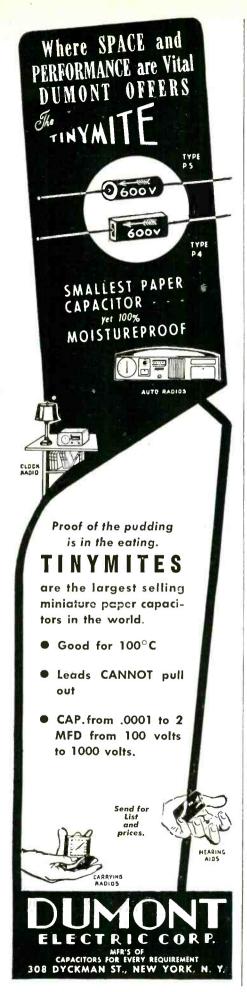FIVE TELEVISION affiliates of NBC are now linked in a new midwestern coaxial cable network. Participating stations are WBEN-TV, Buffalo, N. Y., WSPD-TV, Toledo, O.;







JULIUS KORANY

Leading authority on tube production and design, whose association with Arcturus dates back to the QUICK HEATING BLUE TUBES is in charge of our Tube Division.

Constant research and improvement in manufacturing techniques, under the supervision of Mr. Korany, have resulted in a line of tubes unsurpassed for dependability and high quality performance.

Write for the Arcturus Tube Data Chart



STANDARD ARCTURUS CORPORATION

54 CLARK STREET . NEWARK 4, NEW JERSEY

HUmboldt 2-2400



Used effectively in leading laboratories, such as: Harvard University, Bell Aircraft Corp., and Hamilton Standard Propellers... for measuring natural frequencies or speed of rotating objects, checking or calibrating tachometers, oscillators, impulse generators, similar equipment.

C. G. CONN LTD., DEPT. 1112 ELKHART, IND.



Write for Free Folder



Please send free Stroboconn folder containing information about operation and application of this new precision instrument. I understand this places me under no obl

strument. I understand this places me under no ob gation.

Name

Position

Ciry	Zone	State
Address		
Company		



PARTS OFF" MANY MATERIALS All hot and cold

rolled rods Stainless steel Chrome Molybdenum Aluminum Brass Copper Bi-metals Many types of plastics Fibre Rubber Wood

This newest member of the DI-ACRO "DIE-LESS DUPLICATING" family of Machines brings you accuracy, speed, capacity range and ease of operation fully up to the standards of DI-ACRO Benders, Brakes, Shears.

Do you require precision?—The DI-ACRO Rod Parter holds tolerance to .001" on duplicated cuts. The ends are square. and roundness is maintained.

Do you want speed? - The Rod Parter exceeds output of other methods with equal accuracy, on rods and bars up Torrington Roller Bearings incorporated in an exclusive multiple leverage arrangement provide remarkable ease of operation in both heavy and light materials.

GET "DIE-LESS DUPLICATING" CATALOGI

Shows parts produced without die expense by DI-ACRO Benders. Brakes, Shears, Rod Parters, Notchers, Punches. Send for your free copy.

Pronounced "DIE-ACK-RO" 321 EIGHTH AVENUE LAKE CITY, MINNESOTA

ADVANCE - AMPHENOL - AEROVOX - ASTATIC

ALTEC-LANSING

FOR YOUR CONVENIENCE

W-BUD

BACH

BURGES

CENTRALAB - CIN AUDAGRAPH - CORNELL - DUBLIER

EIMAC-ELECTROVOICE-GE-JFD-IRC-JENSEN

MALLORY - LITTLEFUSE - MEISSNER - MILLEN

MILLER - NATIONAL - OHMITE - RCA - SANGAMO

SHURE - UTAH - STEVENS - STANCOR - WELLER

DMXVERSITY — SYLVANIA — THORDARSON — WEBSTER

PICKERING ICA - PRECISION - UNITED ELECT.

CALL JACK KIRSCHBAUM

DIGBY 9-4714

BRUSH

BROWNING

CARDWELL DRAKE


CORTLANDT STREET, NEW YORK 7, N.Y. NEWS OF THE INDUSTRY

(continued)

WWJ-TV, Detroit, Mich.; WTMJ-TV, Milwaukee, Wis.; and KSD-TV, St. Louis, Mo.

The pioneer NBC group listed above will soon be expanded to other cities in the area, including WNBQ. Chicago and WNBK, Cleveland. It is expected that by January 1 the midwestern net will be linked with the NBC television network now spanning the eastern seaboard.

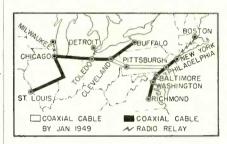Also in operation for telecasting of presidential election returns was ABC's six-station midwestern television network, comprising KSO-



TV in St. Louis, WTMJ-TV in Milwaukee, WSPD-TV in Toledo, WXYZ-TV in Detroit, WEWS in Cleveland and WBEN-TV in Buffalo. As this lineup indicates, midwestern television stations are in some instances joining two networks

National Electronics Conference Program

Two outstanding features of the 1948 National Electronics Conference at the Edgewater Beach Hotel, Chicago, November 4, 5, and 6, will be the banquet in the Marine Dining Room on Thursday evening, November 4, and a large-screen television demonstration by RCA in the Crystal Ballroom on Friday at 8:00 p.m.

The technical program is as follows:

Thursday, November 4

9:00 a.m.—Registration, Edgewater Beach Hotel, Chicago 10:00 a.m.—Session 1: NEW MATE-TERIALS

TERIALS
Properties of CbN at Radio Frequencies, by J. V. Lebacqz and Donald H. Andrews of Johns Hopkins University.
Development and Properties of Some Ceramic Dielectrics, by G. R. Shelton, E. N. Bunting and A. S. Creamer of National Bureau of Standards.
The Transistor—Its Properties and Characteristics, by Walter H. Brattain of Bell Labs.

Characteristics, by Walter H. Brattam of Bell Labs.

10:00 a.m.—Session 2: SOUND MEAS-UREMENT—RECORDING
Application of Miniature-Circuit Techniques to the Sound Level Meter, by H. H. Scott of Hermon Hosmer Scott, Inc.
An Evaluation of the Application of New and Old Techniques to the Improvement of Magnetic Recording Systems by

ment of Magnetic Recording Systems, by



BAR & DOT GENERATOR

A precise means for adjusting horizontal and vertical sweep linearity of television receivers when used in conjunction with Standard Synchronizing Signal and Monoscope Generator or other pattern or picture signal generator. Requires only 51/4" of standard rack space. Five convenient push-buttons allow instantaneous selection of: • Standard blanking • Vertical bars only • Horizontal bars only • Vertical and horizontal bars • Complete dot pattern. Has phasing control for adjustment of vertical bar position. Self contained regulated power supply.



CRYSTAL CONTROLLED **MULTI-FREQUENCY GENERATOR**

A 10 frequency, 400 cps modulated crystal controlled oscillator, ideal for production line adjustment of stagger tuned I.F. amplifiers in television sets. Available with crystals ranging from 4.5 to 40 mc. provided to exact frequency and in sequence specified by customer. Each frequency is immediately selectable by means of a push button. Output attenuator range .5 V to 500 microvolts. Self contained regulated power supply.

Write for bulletins 2000 & 1900

Rutherford, New Jersey RUtherford 2-9



Eliminate time-consuming manual solder operations in your assembly processes. Pre-formed rings, washers, discs, pellets, squares, etc., complete with flux, save time, trim labor costs, insure cleaner, more uniform, sturdier bonds. We meet your specifications in the widest variety of solder alloys. Consult with us on any solder or brazing problem.

(Literature on Request).

Soldering Specialties

Dept. C, Summit, N. J.



A BRADLEY! RECTIEIERS

HIGH VOLTAGE SELENIUM RECTIFIERS



Hermetically sealed in 1/2" diameter glass tubes, Bradley SE6M high voltage selenium rectifiers are rated up to 5 ma. D.C. They are polarized for fuse clip-type mounting. Available from 1,000 to 15,000 volts peak inverse. Bradley engineers can quickly specify the right type of selenium or copper oxide rectifier for your need.

PHOTO CELLS

SIMPLIFY PHOTO CELL CONTROL



Luxtron* photo cells convert light into electrical energy. No external voltage is required to operate meters and meter relays directly from Bradley photo cells, improving control over your processes, reducing your costs. Housed model shown. Many different sizes and shapes, mounted and unmounted.

*T. M. REG. U. S. PAT. OFF.

Our engineers will select or develop rectifiers or photo cells to meet your needs exactly. Write for BRADLEY LINE showing basic

BRADLEY

LABORATORIES, INC. 82 Meadow St. New Haven 10, Conn. NEWS OF THE INDUSTRY

(continued)

Lynn C. Holmes of Stromberg-Carlson Co.
Magnetic Records for Home Entertainment, by Marvin Camras of Armour Research Foundation.
10:00 a.m.—Session 3: SERVOMECHAN-ISMS

ISMS
Electronic Circuits for Control of Clutch
Type Servomechanisms, by F. E. Edwards,
Jr. of Buehler and Co.
Signal Generators for Servo System
Measurements, by Charles F. White of
Navai Research Laboratory.
Evaluating Servomechanisms Performance, by George M. Attura of Servomechanisms, Inc.
12:15 p.m.—Luncheon Meeting; Science,
Industry and the Future of Man, by Anton
J. Carlson of Univ. of Chicago.
2:00 p.m.—Session 4: COMMUNICATIONS
Corona Interference with Radio Recept-

Corona Interference with Radio Reception in Aircraft, by M. M. Newman of Lightning and Transients Research Insti-

Lightning and Transients Research Institute.

The Effect of Air Speed Upon Precipitation Charging of an Airplane, by Homer J. Dana of Washington State College.

Extraction of Weak Signals from Noise by Integration, by Harry Stockman of Cambridge Field Station, Watson Labs., Cambridge, Mass.

Optimum Selectivity in Superregenerators, by Donald Richman of Hazeltine.

Terminal Equipment for Pulse-Time Multiplex, by A. M. Levine and D. D. Grieg of Federal Telecommunication Laboratories, Inc.

2:00 p.m.—Session 5: ELECTRONIC INSTRUMENTATION—I

A Square-Law Power-Level Recorder, by W. R. Clark and A. J. Williams, Jr. of Leeds and Northrup, and W. R. Turner of Naval Ordnance Laboratory.

The Development of a High-Speed Recording Anemometer, by John M. Cage of Purdue Univ.

A Precision Electronic pH Control, by L. Research Caup

cording Anemometer, by John M. Cage of Purdue Univ.

A Precision Electronic pH Control, by J. E. Breeze of National Research Council, Canada.

Electronic Methods for Measurement of Pressure and Displacement, by A. Crossley and D. L. Elam of Electro Products Laboratories, Inc., Chicago, Ill.

Application of a D-C Negative Feedback Amplifier to Compensate for the Thermal Lag of a Hot-wire Anemometer, by Philip G. Hubbard of State Univ. of Iowa.

2:00 p.m.—Session 6: NEW TUBE DE-VELOPMENTS

Alkali-Metal Alloys for Cathodes of Power Electronic Tubes, by J. A. M. Lyon of Northwestern Univ. and C. E. Williams of Standard Oil Co. of Whiting, Ind.

Mass Production Techniques for Television Kinescopes, by D. Y. Smith of RCA, Camden, N. J.

The Surge Testing of High Vacuum Tubes, by H. J. Dailey of Westinghouse.

A New Subminiature Electrometer Tube, by H. F. Starke of Raytheon.

Design Considerations for Dual Control Grid Pentode, by Roger W. Slinkman of Sylvania.

Sylvania.
7:00 p.m.—Banquet; Marine Dining Room; Edgewater Beach Floor Show and Dancing.

Friday, November 5

9:00 a.m.—Session 7: MICROWAVES
The Dynotron Tube as a Very HighFrequency Oscillator, by R. A. Dehn of GE.
A New Type of Slotted Line Section, by
W. Bruce Wholey and W. Noel Eldred of
Hewlett-Packard Co.
Microwave Slotted Sections, by Stanley
A. Johnson of Polytechnic Research and
Development Co.
Tunable Waveguide Cavity Resonators
for Broadband Operation of Reflex Klystrons, by W. W. Harman of Stanford
Univ.

A Periodic Waveguide Travelling Wave Amplifier for Medium Powers at Micro-waves, by G. C. Dewey of Federal Tele-communication Laboratories. 9:00 a.m.—Session 8: ANALYSIS AIDS-COMPUTERS

9:00 a.m.—Session 8: ANALYSIS AIDS-COMPUTERS
Root-Solver for Tenth Degree Algebraic Equations, by G. H. Singer, Jr., and J. F. Calvert of Northwestern Univ.
Analysis of Rototrol Voltage Regulators by Electrical Analogy, by James T. Carleton of Westinghouse.
A Polar Vector Indicator, by A. H. Waynick, P. G. Sulzer, and E. A. Walker of Pennsylvania State College.
Automatic Number Storage System, by T. Kite Sharpless of Technitrol Engineering Company, Inc.
Design and Operation of the IBM Selective Sequence Electronic Calculator, by Robert Rex Seeber, Jr. of International Business Machines Corp.

- **MATERIALS**
- MAN-HOURS
- MONEY



Select exactly the right semitubular, split rivet, or coldheaded fastener from Milford's complete line. You'll find it






Then use the right rivet setting machine for your application. One of Milford's 15 basic machines is sure to solve your particular problem . . . and slash your production costs!



PHILADELPHIA 33, PENN.

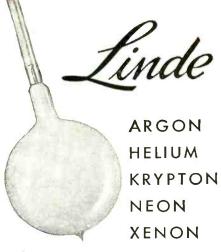

and Standard or Special

MIXTURES

LINDE rare gases are spectroscopically pure—argon, helium, neon, and standard mixtures are available in one- and two-liter glass bulbs and in cylinders; xenon and krypton are available in liter and fractional-liter bulbs.

The word "Linde" is a trade-mark of

THE LINDE AIR PRODUCTS COMPANY
Unit of Union Carbide and Carbon Carporation
30 East 42nd St. New York 17, N. Y.



SPECIALTY DRY BATTERY

for your special need



If you are looking for hardto-get or special dry batteries, write us. We design, create and manufacture to your requirements.



SPECIALTY BATTERY COMPANY

OF THE RAY-O-VAC COMPANY

MADISON 4, WISCONSIN



PRECISION BOBBINS

Precision provides the strength, the insulation, the dependability by the most thorough specialized engineering, exactly to your specifications.

Spiral winding of the tube—heavy heat-treated compression—swaged tube ends securely locked—impregnation of the complete assembly are factors of Precision's exceptional service. Lightest of all coil bases. Permit larger gauge, or more wire of same gauge in winding area.

Let us make up samples for your requirements

Also mfrs. of dielectric tubes, round, square, rectangular, any length, ID or OD; coil forms; spools; dust caps and thread protectors.



2041 W. CHARLESTON ST. Plant No. 2 at 79 Chapel St. CHICAGO 47, ILL. Hartford, Conn.



Designed for

YOUR APPLICATION PANADAPTOR

Whether your application of spectrum analysis requires high resolution of signals closely adjacent in frequency or extra broad

spectrum scanning, there is a standard model Panadaptor to simplify and speed up your job.

Standardized input frequencies enable operation with most receivers.

	MODEL SA-3 TYPES					MODEL SA-6 TYPES			
Maximum Scanning Width Input Center Frequency	T-50 50KC 455KC	T-100 100KC 455KC	T-200 200KC 455KC	T-1000 1MC 5.25MC	T-1000 1MC 10.2MC	T-6000 6MC 30MC	T-1000 1MC 5.25MC	T-10000 10MC 30MC	T-20000 20MC 30MC
Resolution at Maximum Scanning Width	2.5KC	3.4KC	4.4KC	13KC	11KC	25KC	11KC	75KC	91KC
Resolution at 20% of Maximum Scanning Width	1,980	2.7KC	4KC	.9KC	7.5KC	22K C	7.5KC	65KC	75KC

Investigate these

APPLICATIONS OF PANADAPTOR

- *Frequency Monitoring
- *Oscillator performance analysis
- *FM and AM studies

WRITE NOW for recommendations, detailed specifications, prices and delivery time.



TWIN Power Supply

Electronically Regulated for **Precise** Measurements

Two independent sources of continuously variable D.C. are combined in this one convenient unit. Its double utility makes it a most use-

ful instrument for laboratory and test station work. Three power ranges are instantly selected with a rotary switch:

> 175-350 V. at 0-60 Ma., terminated and controlled independently, may be used to supply 2 separate requirements. 0-175 V. at 0-60 Ma. for single supply. 175-350 V. at 0-120 Ma. for single supply.

In addition, a convenient 6.3 V.A.C. filament source is provided. The normally floating system is properly terminated for external grounding when desired. Adequately protected against overloads.



WIN POWER SUPPLY

- change from 0 to full
- Output voltage variation less than 1 V. with change from 105 to 125 A.C. Line Voltage.
- Output ripple and noise less than .010.

Twin Power Supply Model 210 Complete \$130.00
Dimensions: 16" x 8" x 8" Shipping Wt. 35 lbs.
(Other types for your special requirement)
Visit Our Booth No. 17 at the National Electronics Conference

ELECTRONICS

806 W. North Ave., Chicago 22, Illinois

Automatic trequency Control

on DC to AC CONVERTERS

AVAILABLE IN 22 TYPES AND 3 FRAME SIZES BY

Gothard



DYNAMOTORS CONVERTERS GENERATORS

DC to AC Rotary Converters having Automatic Frequency Control are now being offered in all models. Input voltages from 6 to 230 V DC; output: 110 to 1000 VA at 60 cycles, 90 to 800 VA at 50 cycles.

SPECIALLY DESIGNED for Television Sets, AC Radios, Radio-Phonographs and Recorders. For use where the power source is direct current: such as ships, vehicles, trains, office buildings, and urban DC areas.

GOTHARD Manufacturing Co.

Write today for illustrated cata-

log #48 on:

Springfield, Illinois

Export Division: 25 Warren St., New York 7, N. Y.

NEWS OF THE INDUSTRY

(continued)

9:00 a.m.—Session 9: INDUSTRIAL AP-PLICATIONS

Precision Photoelectric Control of High-Temperature Furnaces, by F. C. Todd of Battelle Memorial Institute, Columbus,

The Application of Radar Techniques to a System for High Speed X-Ray Movies, by D. Dickson, C. Zavales and L. F. Ehrke of Westinghouse.

CRT Applications in Photography and Optics, by Carl Berkley and Rudolf Feldt of DuMont.

of DuMont.

A 500-50,000 Volt Regulated Power Supply, by Roy E. Anderson of GE.

12:15 p.m.—Luncheon Meeting; The Decline and Fall of the Free Electron, by Donald G. Fink, Editor-in-chief, ELECTRONICS. TRONICS.

TRONICS.

2:00 p.m.—Session 10: TELEVISION
The Locked Oscillator in Television Reception, by Kurt Schlesinger of Motorola.
Master Television Antenna and Signal Distribution Systems for Large Buildings, by R. D. Duncan, Jr., of RCA.
Development of a Large Metal Kinescope for Television, by J. Kelar, H. P. Steier, C. T. Lattimer, and R. D. Faulkner of RCA.

Large Screen Television by R. V. Little.

of RCA.

Large Screen Television, by R. V. Little,
Jr. of RCA, with demonstration.
2:00 p.m.—Session 11: MANAGEMENT
OF RESEARCH
Organization of Research, by C. C.
Furnas of Cornell Aeronautical Laboratory.

Furnas of Corner Actions
tory.

Development of Physical Facilities for Research, by R. B. Dittmar of Los Alamos Scientific Laboratory.

Personnel Administration in Research and Development Organizations, by C. E. Barthel, Jr., of Armour Research Foundation

Information Exchange as a Management Tool in a Large Research Organization, by Allen H. Schooley of Naval Research

hy Allen H. Schooley of Naval Research Laboratory.

Research Ideas Go to Market, by Waldo H. Kliever of Minneapolis-Honeywell Regulator Co.

2:00 p.m.—Session 12: ELECTRONIC CIRCUITS

Response of an Amplifier to A Signat Varying Linearly in Frequency, by W. H. Hamilton of Westinghouse.

An Extremely Wide Range Electronically Deviable Oscillator, by Millard E. Ames of Philco.

Ames of Philco.

An Improved Regenerative Frequency Standard Application, by F. E. Wyman of Naval Research Laboratory.

Design of a Wide-Band Frequency Discriminator Circuit, by Vincent C. Rideout of Univ. of Wisconsin.

Circuit Design for Reduction of Hum, by Arthur F. Dickerson of GE.

8:00 p.m.—Demonstration — Baltroom; Large Screen Television, by R. V. Little, Jr. of RCA; repeat performance for those unable to attend earlier demonstration.

Saturday, November 6

9:00 a.m.-PLIFIERS -Session 13: MAGNETIC AM-

An Analysis of Magnetic Amplifiers with Feedback, by D. W. VerPlanck and M. Fishman of Carnegie Institute of Tech-

nology.

Influence of Core Material on Magnetic Amplifier Design, by A. O. Black, Jr. of U. S. Naval Ordnance Laboratory.

An Analysis of Interlinked Electric and Magnetic Networks with Application to Magnetic Amplifiers, by D. W. VerPlanck and M. Fishman of Carnegie Institute of Technology.

Magnetic Amplifiers, by D. W. VerPlanck and M. Fishman of Carnegie Institute of Technology.

9:00 a.m.—Session 14: ELECTRONIC INSTRUMENTATION—II

An Electronic Power Factor Meter, by E. B. Kurtz and Paul O. Erickson of State-Univ. of Iowa.

Cathode-ray Oscillograph with 100-Megacycle Bandwidth, by M. M. Newman of Lightning and Transients Research Institute and P. S. Christaldi and R. P. Featherstone of DuMont.

Absolute Accuracy—Primary Frequency

Absolute Accuracy—Primary Frequency Standard, by Harry R. Meahl of GE.

Low-Distortion A-M Signal Generator, by E. S. Sampson of GE.

An Electron Tube for Viewing Magnetic Fields, by S. G. Lutz and S. J. Tetenbaum of New York Univ.

9:00 a.m.—Session 15: ANTENNAS
Radio Direction Finding System Analyzer, by E. C. Jordan and J. J. Myers of
Univ. of Illinois.

Open-ended Waveguide Radiators, by



The Edison Model 501 Thermal Relay solves many circuit problems, such as timing, over- and under-voltage or current protection, cathode protection, motor starting, integration and "holdovers."

DELAY INTERVAL: 5 seconds to 8 minutes, factory preset.

CONTACT RATING: 6 amp. at 250 volts AC or DC, normally.

HEATER INPUT: 5 watts nominal, con-tinuous excitation, up to 115 volts AC or DC.

CONTACTS:

SPST, normally open or normally closed.

AMBIENT RANGE COMPENSATION: -60° C (-76° F) +60° C (+140° F).

DIMENSIONS: 11/4" diameter x 31/2" height, seated.

WEIGHT: 0.08 lb. to 0.14 lb.

MOUNTING: Standard octal or 4-prong tube base.

Write for Publication No. 3007 204 Lakeside Avenue . West Orange, New Jersey



INSTRUMENT DIVISION THOMAS A. EDISON, Incorporated

Flexible Shafts



PRECISION POTENTIOMETERS

Toroidal and Sinuspidal

For use in computing and analyzing devices; generation of low frequency saw tooth and sine waves; controls for radio and radar equipment; position indicators; servomechanisms; electro medical instruments, measuring devices—telemetering; gun fire control where 360° rotation, high precision and low noise levels are essential.

The type RL14MS sinusoidal potentiometer is illustrated. It is wound to a total resistance of 35,400 ohms and provides two voltages proportional to the sine and cosine of the shaft angle. It will generate a sine wave true within $\pm .6\%$. Overall dimensions are $4\frac{3}{5}$ diameter x 4 11/32 long plus shaft extension $\frac{1}{4}$ diameter x



Write for Bulletin F-68

THE GAMEWELL COMPANY

Newton Upper Falls 64, Massachusetts



PYRO-**FERRIC** IRON CORES

Since 1933 PYROFERRIC has been the standard source for IRON CORES manufactured to desired permeability, frequency, "Q", resistance and physical strength to fit any circuit.

PYROFERRIC, with its background of research and experience, will glady consult with you on your IRON CORE requirements.

YROFERRIC C

621 EAST 216 ST.

NEW YORK 67, N.

431 VENICE BLVD.

LOS ANGELES 15, CAL

A NEW V-O-M "MODEL 500"



SENSITIVITY 20000 ohms/volt AC-DC

RANGES

AC-DC Volts: 0-3/15/150/300/750/ 1500/7500

DC Current: 0-150 UA/1.5 MA/30 MA/1.5 A/15 A

OHMS: 0-5000/50,000/50,000,000 DB: -10/0/ + 73 in 7 ranges

FEATURES:

Highest sensitivity—Damped movement-Accurate-Rugged-Portable—Long mirrored scale—with added center zero range. Complete with High Voltage test leads. Housed in handsome hardwood case.

Measure from a low of 10 microamperes to a high of 15 amperesfrom .2 volts to 7500 volts—from 1 ohm to 50 million—from minus 10 to plus 73 DB.

So accurate it is used in the Laboratory. So rugged it withstands portable field use. Write for Catalog 4423 or see your jobber.

ROLLER-SMITH

BETHLEHEM, PA.



NEWS OF THE INDUSTRY

(continued)

R. E. Beam, M. M. Astrahan and H. F. Mathis of Northwestern Univ.
Measurement of Phase of Radiation Around Antennas, by John N. Hines and Charles H. Boehnker of Ohio State Univ. Research Foundation.
The Measurement of Antenna Impedance Using a Receiving Antenna, by Donald G. Wilson of Univ. of Kansas.
A. High-Gain Cloverleaf Antenna, by P. H. Smith of Bell Labs.

BUSINESS NEWS

SYLVANIA ELECTRIC PRODUCTS, INC., Emporium, Pa., doubles its television tube output rate with the establishment of a new plant at Ottawa, Ohio.

ARTHUR ANSLEY MFG. Co., Doylestown, Pa., was recently organized for the production of high-fidelity sound reproducing equipment.

A. C. Monteith has been elected vice-president in charge of engineering and research at Westinghouse Electric Corp. after 25 years with the organization. He holds the company's Order of Merit, highest employee award for distinguished service and accomplishment.

MOTOROLA INC., Chicago, Ill., manufacturers of radio and television sets, recently purchased the Car Radio division of the International Detrola Corp., Detroit, Mich., and can now supply auto radios directly to automobile manufacturers.

SUBMARINE SIGNAL Co., subsidiary of Raytheon Mfg. Co., has purchased the building at 148 California St., Newton, Mass., to integrate operations with the parent company.

NATIONAL ELECTRONICS, INC., industrial tube manufacturer, recently added a 5,000-sq-ft factory building to its plant in Geneva, Illinois.

BROWN INSTRUMENT Co., a division of Minneapolis-Honeywell Regulator Co., hired 40 newly graduated engineers as one part of its \$2,500,-000 physical expansion program.

AIRBORNE INSTRUMENTS LABORA-TORY, INC., Mineola, N. Y., has es-

A WORKSHOP HIGH-GAIN **ANTENNA**

will ...

More than triple the effective power of the transmitter.

Increase the effective power of the mobile transmitter.

Increase the operating area.

Permit the use of low power, low cost equipment.

Workshop High-Gain Beacon Antennas are designed specifically for the 152-162 megacycle band -taxicab, fire, police, and private fleet communications.

Design Features

- Low angle of radiation concentrates energy on the horizon.
- Symmetrical design makes azimuth pattern circular.
- Can be fed with various types of transmission lines. Special fittings are available for special applications.
- Enclosed in non-metallic housing for maximum weather protection.

Available for immediate delivery through authorized distributors or your equipment manufacturer.

—THE— **WORKSHOP** ASSOCIATES

INCORPORATED

Specialists in High-Frequency Antennas 64 NEEDHAM STREET

Newton Highlands 61, Mass.

NEW Subscription Order

Please enter my new subscription for THREE YEARS of ELECTRONICS for \$12.

(If you prefer I year of ELECTRONICS for \$6 check here [])

Name:	Position
Home Address:	val 1
City:	Zone State
Company Name:	
Foreign Rates (1 yea	r) Canada \$7, Latin America \$10, Other \$15

Subscription Order

Please enter my new subscription for THREE YEARS of ELECTRONICS for \$12.

(If you prefer I year of ELECTRONICS for \$6 check here [])

Name:		Position	
Home Address:		•••••	
City:	Zone	State	
Company Name:			

Foreign Rates (1 year) Canada \$7, Latin America \$10, Other \$15

11-48





BUSINESS REPLY CARD

First Class Permit No. 64 (Sec. 510, P. L. & R.) New York, N. Y.

4¢ POSTAGE WILL BE PAID BY --

McGRAW-HILL PUBLISHING CO., Inc.

ELECTRONICS

330 WEST 42nd STREET
NEW YORK 18, N. Y.





BUSINESS REPLY CARD

First Class Permit No. 64 (Sec. 510, P. L. & R.) New York, N. Y.

4¢ POSTAGE WILL BE PAID BY -

McGRAW-HILL PUBLISHING CO., Inc.

ELECTRONICS

330 WEST 42nd STREET

NEW YORK 13, N. Y.

ELECTRICAL & ELECTRONIC EQUIPMENT

ELECTRONIC TUBE EQUIPMENT



36 HEAD RADIO TUBE EXHAUSTING MACHINE

We Make Complete Equipment For The Manufacture Of Incandescent Lamps addio and Electronic Tubes.

TRANSFORMERS OF ALL TYPES







SIZES 1/4 to 250 KVA SPOT WELDERS

OF ALL TYPES
FOR ALL PURPOSES
SIZES ½ to 250 KVA
Butt Welders - Gun Welders
Arc Welders
Neon Sign Units
Fluorescent Tube
Manufacturing Equipment

CHAS. EISLER

EISLER ENGINEERING CO., INC.

751 So. 13th St. (Near Avon Ave.), Newark 3, N. J.

Lavite STEATITE GERAMIC



Design engineers and manufacturers in the radio, electrical and electronic fields are finding in LAVITE the precise qualities called for in their specifications . . high compressive and delectric strength, low moisture absorption and resistance to rot, fumes, acids, and high heat. The exceedingly low loss-factor of LAVITE plus its excellent workability makes it ideal for all high frequency applications.

Complete details on request

D. M. STEWARD MFG. COMPANY

Main Office & Warks: Chattanooga, Tenn. Needham, Mass. • Chicago • Los Angeles New York • Philadelphia

special nails • rivets • screws • made to your order

HASSALL cold-heading may solve your immediate special part problem ... Special nails, rivets and threaded parts made in diameters from 1/32" to 3/8"—lengths up to 7"... Rivets 3/32" diameter and smaller a specialty ... Variety of metals, finishes and secondary operations ... Economy, quality and quick delivery in large or small quantities ... Tell us what you need

.. We will answer promptly. ASK FOR FREE CATALOG. 3-color Decimal Equivalents Wall Chart free on request.



Manufacturers of Cold-Headed Specialties-Established 1850







Fairchild **Precision Potentiometers**

long life sustained accuracy low noise level absolute resolution resetability multiple ganging

For further information address: Dept. 'K', 88-06 Van Wyck Boulevard, Jamaica I, New York





Built to laboratory standards of electrical, mechanical, and musical excellence, this 20-watt amplifier includes these features . . . proved essential to satisfactory custom performance in both FM and AM radio reproduction as well as in record playing.

Extended listening range . . . 30 to 20,000 cycles, with negligible intermodulation or transient distortion,

*Dynamic noise suppressor . . . designed particularly for this unit . . . allows widest use of high- and low-frequency gain,

Twenty-watt output . . . with less than 2% harmonic distortion; range and power-handling capability exceed RMA broadcast station requirements,

Minimum controls for maximum flexibility . . . easy selection of exact tonal balance to please every ear.

GUARANTEED FOR A FULL YEAR FOR RADIO RECEPTION

IN RECORD REPRODUCTION

... the H. H. Scott 210-A enhances enjoyment of both FM and AM minimizing clicks, broadcasting, whistles, and noise.

. . the H. H. Scott 210-A laboratory amplifier provides unsur-passed realism, with freedom from scratch, hiss and rumble.

For full details, request Bulletin 4811-E. *Licensed under U.S. and foreign patents pending and issued.



tablished fellowships at Stanford University and MIT to help young men obtain advanced degrees in the field of communications and electronics

RADIO CORP. OF AMERICA, Camden, N. J., recently held a four-day television seminar for 40 consulting engineers.

FEDERAL TELEPHONE AND RADIO CORP., Clifton, N. J., has installed a modernized f-m two-way radio system in place of the former a-m equipment in 215 mobile units on



One of five fireboats operated by the Baltimore Fire Department. It is equipped with Federal's 2-way f-m mobile radiotelephone

land and water, for police and fire department operations in Baltimore, Md. The units will operate in the 152 to 162-mc band. Changeover took place without interrupting the city's 24-hour service.

PERSONNEL

GEORGE C. KUCZYNSKI, attached to the staff of Sylvania Electric Metallurgical Laboratory, Bayside, N. Y., for basic research on the electron theory of metals, delivered a series of lectures on the physics of metals at the National University, Bogota, Columbia.

H. MYRL STEARNS, formerly in charge of the Tube Research and Development Laboratory and of tube production at Sperry Gyroscope Co., has been appointed vicepresident and general manager of



Now Junior can listen to serials and mysteries without disturbing anyone. Sister can listen to her favorite programs while Mother listens to another radio. It's really a child's very own. The telephone "dial" is a carefully pre-set, highly selective radio dial. Brings in any station within a 100 mile radius. Tuned for every radio frequency from 540 to 1600 kilocycles. Includes all the features of expensive portables.

RADIO PHONE HAS THESE!

RADIO PHOME HAS INESE:

• Private earphone for hours of non-disturbed listening.
• Special long life battery—Only the flashlight bottery need be

replaced.
Beautiful plastic telephone case.
Factory guarantee against defects of material or workman-

ship.




This sensational new radio is complete in every detail. Includes its own tube and a special, easily attached aerial that brings in programs with plenty of volume. Your Radiophone comes to vou complete. Any child will reaptich benefits from having his own radio. For education, anusement, rainy-day entertainment, there's nothing like a Radiophone for keeping every youngster occupied. These perfectly engineered radios are available in limited supply—so mail for your order today. Satisfaction guaranteed. SEND NO MONEY—pay postman only \$4.98 plus \$1.00 for long life Lattery and few cents postage—OR remit by check or money order and we pay postage.

Prudential Sales Co., Dept. 1511 141 Broadway, New York 6, N.Y.



NFY Precious Metals in Industry

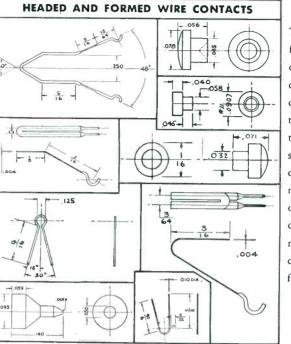YOUR DESIGN PROBLEM SIMPLIFIED WITH THE USE OF ONE OF OUR STANDARD CONTACTS



This simplified chart shows the form and overall dimensions of a few of the many types of contacts made from Ney Precious Metal Alloys with electrical and physical properties that have proved exceptionally satisfactory for brush or wiping contact applications. Full technical and test data are available on request. Other Ney Precious Metal Alloys have solved many special industrial application problems. Consult us freely without obligation.

> NEY GOLD

Write or phone (Hartford 2-4271) our Research Department.

THE J. M. NEY COMPANY 179 ELM STREET . HARTFORD I, CONN. SPECIALISTS IN PRECIOUS METAL METALLURGY SINCE 1812



MAKERS OF STEATITE, TITANATES, ZIRCON PORCELAIN, ALUMINA, LIGHT-DUTY REFRACTORIES, CHEMICAL STONEWARE

OFFICES and PLANT: CROW'S MILL ROAD, KEASBEY, N.J.

A practical and concise treatment of the

FUNDAMENTALS

OF

ELECTRIC WAVES

Second Edition

By HUGH H. SKILLING

Professor of Electrical Engineering and Executive Head of the Department, Stanford University

This book clearly presents the principles of electro-magnetic theory and their practical applications to engineering practice. The author has placed particular emphasis on the basic ideas of Maxwell's equations, and has included many examples to demonstrate them. The rationalized mks system of units has been introduced throughout the book, and explanatory notes in the early chapters clarify this system for those used to the cgs system.


Completely up to date

Much new material has been included in this second edition. The latest information on cylindrical and rectangular wave guides has been incorporated, and there has been an increase and reorganization of the data on the reflection of waves and on antennas. The discussion of wave transmission through semi-conducting media and in ionized regions has been expanded.

Contents include:

 Experiments on the Electrostatic Field;
Vector Analysis; Certain Theorems Relating to Fields; The Electrostatic
Field; Electric Current; The Magnetic
Field; Examples and Interpretation;
Maxwell's Hypothesis; Plane Waves;
Reflection; Radiarion: Antennas:





JOHN WILEY & SONS, INC.
440 Fourth Ave., New York 16, N. Y.
Please send me, on 10 days' approval,
a copy of Skilling's FUNDAMENTALS
OF ELECTRIC WAVES. If I decide
to keep the book, I will remit price
plus postage; otherwise I will return
the book postpaid.

the book postpaid.	
Name	•
Address	•
City State	
Employed by	•
(Offer not valid outside U.S.)	

NEWS OF THE INDUSTRY

(continued)

Varian Associates, new microwave and electronic research and development laboratory at San Carlos, Calif.

GEORGE F. MURPHY, with General Electric Co. in Schenectady since 1913, was appointed manager of the equipment development works of GE's Electronics Department.





G. F. Murphy

J. T. Lucas

JOHN T. LUCAS, formerly in charge of product engineering for all Sylvania proximity fuze plants in Pennsylvania, has been appointed supervisor of quality control and customer service for the Huntington Radio Tube Plant of Sylvania Electric Products Inc.

A. C. GABLE, formerly assistant engineer, was recently appointed division engineer of GE's Tube Divisions, Schenectady, N. Y.





A. C. Gable

E. W. Stone

ELLERY W. STONE, executive vicepresident of Federal Telephone and Radio Corp., has been elected president of that organization and its subsidiary, the International Standard Electric Corp.

EDWIN H. COLPITTS, holder of 24 U. S. patents on telephone inventions and director of the Engineering Foundation in New York since 1941, was presented with the 1948 Cresson Medal by the Franklin In-



You can buy General Electric sockets now... when you buy G-E tubes. These quality sockets were designed specifically for G-E power tubes, rectifiers, thyratrons, etc. They fit, they last. They aid in obtaining optimum performance from G-E tubes in service.


It's convenient to purchase G-E sockets along with G-E tubes, because you get them from the same source, making it easier to order, and simplifying paperwork.

One manufacturer as a source of supply, means one-manufacturer responsibility for both products. Use G-E tubes and G-E sockets as a team; play safe by demanding the G-E brand throughout! Prices and full details are available from your nearby G-E electronics office, or write to Electronics Department, General Electric Company, Schenectady 5, New York.

183-65-8850



BAACH-INTERNATIONAL

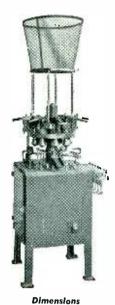

24"x24"x72" high

Can be synchronized with automatic Stem machine. Cuts off and flares in

EIGHT HEAD HOT-CUT

FLARE MACHINE

Automatic throughout.

one operation.

Production 1250 flares per hour. For minia-ture flares, fluores-cent starters, stand-ard size lamps, fluo-rescent and radio

RANGE OF MACHINE Glass tubing 27 to 45 gauge

Length of flares 5 mm. to 80 mm.

Forms flares up to 47 mm. diam.

Net weight, 960 lbs. Gross weight 1450 lbs.

INTERNATIONAL MACHINE WORKS

Manufacturers of High Vacuum Pumps, Automatic Machinery for Incandescent Lamps, Electronic Tubes since 1916.

> 2027 - 46TH STREET NORTH BERGEN, N. J., U. S. A.

Tel. UNion 3-7412, Cable Address "Intermach" North Bergen, N. J.

WANTED

Middlewestern manufacturer has excellent openings for two engineers:

CIRCUIT ENGINEER

Must be experienced in measurement work, FM and television frequencies, and have thorough knowledge of the performance characteristics and correct application of ceramic capacitors.

CERAMIC


Must be experienced in all phases of the development and manufacture of high dielectric ceramic body capacitors.

Kindly give full information covering your educational background, practical experience, age, dependents, and compensation expected. Address

P-6702, Electronics, 520 North Michigan Ave., Chicago 11, Ill.

New Tools You Should Have FOE PRESSURE RESEARCH

The Syncro-Marker **PRESSUREGRAPH**

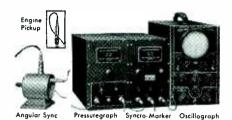

Here is your complete answer in instrumentation for checking pressure variations, both regular and instantaneous. Provides oscillograph pictures showing relation of pressures to engine shaft rotation (top dead center) or indications in degrees of rotation and also relates pressures to time (milliseconds).

Accurately measures pressure rise with time. Can be applied to hydraulic, gas, steam or pressure line measurement of static, dynamic or instantaneous pressures. New detachable diaphragm permits measurement in any pressure range from vacuum to 14,000 p.s.i.

Now used in oil fields by many leading producers.

ITS LITERATURE



Write for your copy of "Pressure Patterns" illustrating typical Pressuregraph applications: and "Pressure Indications in Engine Fuel Research," giving data on dynamic studies of pressure waves.


ELECTRO PRODUCTS LABORATORIES

549 W. Randolph St.

Chicago 6, III.

Phone STate 2-7443

PLANO-CONCAVE QUARTZ CRYSTALS

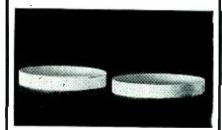

Use Clark plano-concave crystals for maximum prefocused ultrasonic output.

- * 250 kc to 2000 kc
- * 1 cm to 10 cm diameter
- * 100 mm to 500 mm radius of curvature
- * gold or silver plating optional

Complete ultrasonic transducers with impedance matching network available for use under insulating or non-insulating

CLARK CRYSTAL CO.

MARLBORO, MASS., U.S.A.

Export Department Rocke International Corp. New York, N. Y.

FREE ALLIED'S **NEW 1949** RADIO CATALOG **Everything in Radio** and Electronic Supplies Complete, Expert Service for Radio Engineers

You'll find everything you need in radio and development work, in the new 180-page ALLIED Catalog. Rely on one dependable source for the world's largest stocks—thousands of parts, tubes, tools, books, test instruments, sound operating the source for the source for the world's largest stocks—thousands of parts, tubes, tools, books, test instruments, sound operating and for instruments. struments, sound apparatus-ready for instant expert shipment at lowest market prices. Write today for your FREE copy of ALLIED's newest Buying Guide.

ALLIED RADIO CORP., Dept. 11-L-8 833 W. Jackson Blvd., Chicago 7, III.

☐ Send FREE New ALLIED Catalog.
Name
Address

POLARAD LABORATORY Equipment

for studio • laboratory • manufacturer

- Flat frequency response from 100 cps to 20 mc, \pm 1.5db.
- Uniform time delay of .02 microseconds,
- · Gain of 50 db.
- Frequency compensated high impedance attenuator calibrated in 10 db steps from 0-50.
- Fine attenuator covers a 10 db range.
- Phase Linear with frequency over entire band.

This unit is designed for use as an oscilloscope deflection amplifier for the measurement and viewing of pulses of extremely short duration and rise time, and contains the Video Amplifier Unit, Power Unit and a a Low Capacity Probe.


Specifications:

Input Impedance: Probe—12mmf + 470,000 ohms: Jack—30mmf + 470,000 ohms: Output Impedance 18mmf + 470,000 ohms each side push pull: Max. input Volts 500 peak to peak with probe: Max. Output Volts 120 volts peak to peak to peak to peak to peak input Volts peak to peak (push pull); Power: 115 volts 50,60 cps AC Line: Size 19¼"x22"x143¼".

20 MC VIDEO AMPLIFIER

Model V



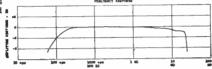



9 FERRY STREET

NEW YORK 7, N. Y.

TELEVISION ENGINEERS and CONSULTANTS TO THE NATION'S LEADING TELEVISION STATIONS ${\mathscr J}$



Barker and Williamson's Bristol, Pa. plan

From the simplest to the most complex electronic device, B & W is equipped and prepared to meet your most exacting needs. Three B & W plants, comprising 150,000 square feet, completely equipped with a competent engineering staff; machine shop; tool

room including all machines for drilling, milling, turning, stamping and forming metals and plastics, and a complete woodworking shop, are ready to go to work on your design and production problems. Your inquiries are invited. Write Dept. EL-118 for prompt reply.

BARKER & WILLIAMSON, Inc.
237 FAIRFIELD AVENUE UPPER DARBY, PA.

NEWS OF THE INDUSTRY

(continued)

stitute, Philadelphia, for achievements leading to the development of practical systems of long-distance communication.

C. Russell Cox, formerly sales manager and chief engineer of Andrew Corp., Chicago, Ill., has taken over the newly-created office of director of sales and engineering.





C. R. Cox

J. S. Brown

JOHN S. BROWN, associated with Andrew Corp. since 1943, has been promoted from assistant chief engineer to chief engineer.

WALTER F. KEAN, in charge of the company's broadcast consulting division since 1944, is now sales manager at Andrew Corp., Chicago, Ill.





W. F. Kean

O. S. Duffendack

O. S. DUFFENDACK, until 1944 professor of physics at the University of Michigan where he directed research for 16 years, and now president, vice-chairman of the board and director of research for Philips Laboratories, Inc. at Irvington-on-Hudson, N. Y., was recently decorated with the ribbon of the King's Medal for Service in the Cause of Freedom, by the British Consul General, for services to the Allied war effort as division member and chief of a section of NDRC.

Lewis W. Chubb, director emeritus of the Westinghouse Research Laboratories and recipient of the 1947 John Fritz Medal, has retired after 43 years of scientific research.

BUSINESS OPPORTUNITY

- The Technical Director and owner of well known British firm manufacturing electrical measuring and testing equipment, seeks to contact active U. S. business man with a view to opening works in U. S. A.
- It is intended to produce equipment which is not already on the U. S. market. In the first instance please reply stating experience in this field and amount of capital available.

BO-6543, Electronics

330 West 42nd St., New York 18, N. Y.





COMPOUNDS

Scientifically compounded for specific applications from waxes, resins, asphalts, pitches, oils, and minerals. Available in wide range of meiting points and hardnesses. Special potting compounds are heat conducting and crack resistant at extremely low temperatures. Recommendations, specific data, and samples will be furnished on request.

for

IMPREGNATING

radio coils transformer coils ignition coils wire coverings paper tubes and forms porous ceramics

DIPPING Coils Transformers Condensers SEALING condensors batteries switch base terminals socket terminals light fixtures

POTTING Radio Transformers Light Units Loading Coils

BIWAX CORPORATION



3445 HOWARD STREET SKOKIE, ILLINOIS



MODEL 28 0.45 Actual size illustrated RECHARGEABLE • NON-SPILL

VITAMITE

1 OZ. BATTERIES

(Smaller Than 2 Pen-Lights) IDEAL FOR USE WITH

Miniature And Sub-Miniature Filament Type Tubes for HEARING AIDS, PORTABLE EQUIPMENT, ETC.

LARGER MODELS ALSO AVAILABLE
Write for Data and Literature

THE VITAMITE COMPANY

227 West 64th Street

New York 23, N. Y.

2460 W. GEORGE ST





NEW BOOKS

Vacuum Tube Circuits

By Lawrence Baker Arguimbau, Assistant Professor, Electrical Communication, Massachusetts Institute of Technology; John Wiley & Sons, Inc. 1948, 668 pages, price \$6.00.

IN A REALISTIC appraisal of the field, the author of a rather unusual book admits the temporary value of texts on electronics, so rapidly does the art change. His aim, therefore, is to equip students and engineers with the intellectual ability to solve problems rather than to describe equipment or circuits. He dissects circuits to their basic status, shows how to determine what these circuits do, and illustrates his methods with many useful examples. Problems are provided to test the reader's ability to learn from the text.

The book is unusual in that it does not follow the cut-and-dried pattern so customary in books on electronics. One is likely to find in an early portion of the book material usually discovered in the final chapter of the conventional book. The idea is not to present a slowly-developed and consistent treatment but to bring to the student the techniques of solving problems—in brief to aid the student to think.

In twelve chapters Professor Arguimbau treats many aspects of radio communication, diodes and rectifiers, triodes, pentodes and linear amplifiers, transient response in video amplifiers, amplitude modulation and tuned amplifiers, power amplifiers, oscillators, inverse feedback, amplitude and frequency modulation, pulses and television and microwaves.

From unofficial reports, the author is a popular professor—and his book should be well received.

K. H.

Principles and Methods of Telemetering

By Perry A. Borden and Gustave M. Thynell. Reinhold Publishing Corporation, New York, 1948, 230 pages, \$4.50.

The material contained in this book fully justifies its title. Skillfully blending basic principles and current practice, the authors have produced a thoroughly practical text, of value to the potential user



KIT COMES COMPLETE.
HAS STANDARD G.E.,
R.C.A. (etc.) PARTS CAN
BE ASSEMBLED READY
TO USE IN A FEW
HOURS. FOLLOW SIMPLE
INSTRUCTIONS. ALL
YOU NEED IS SOLDERING IRON, PLIERS AND
SCREW DRIVER.

The Economy Flash Unit
Kit has been sold in
stores throughout the
country, already assembled for \$98.00. You
save, by assembling the
kit yourself, more than
\$55.00.

Comes complete including: chassis, 60 watt second condenser, relay transformer, vibrator, flash indicator, switch, 3 outlet plugs, flash adapter assembled with bulb and cord.

Operates from 2 dry cell batteries.



Set of 2 batteries, \$1.00 extra

Send no money. Pay postman \$39.95 plus few cents postage upon delivery, or remit by check or money order and save C.O.D.

ntial Sales Co., Dept. [3F-11] roadway, New York 6, N.Y.

TELEVISION HIGH VOLTAGE METER 0 to 30 KV



Include 25% Deposit with Order, Balance C.O.D.

Pioneers in Projection Television SPELLMAN TELEVISION CO., INC. 130 WEST 24th STREET . NEW YORK 11, N. Y











PIPE COUPLINGS

ELECTRICALLY HEATED PRESSURE HEADS

CONTINUOUS FILM RECORDING CAMERAS


AND EQUIPMENT FOR CATHODE RAY

OSCILLOGRAPHY, ETC.



We undertake the Design, Development and Manufacture of any type of Optical-Mechanical -Electrical Instrument. Including Cameras for special purposes.

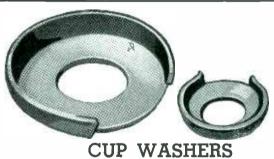Avimo Limited, Taunton, England · Telephone Taunton 3634



for Binding Screws

WHITEHEAD STAMPING CO.

N EVERUEERINE DE

1691 W. Lafayette Blvd.

Detroit 16, Michigan

referred

as a source of precision - made

WASHERS and STAMPINGS

manufactured to your specifications



Our Engineering Department is at your service. Samples cheerfully analyzed without obligation.

TRANSFORMERS Made To Order


Not just any coil but the exact coil winding you need, skillfully made to your exact requirements. The dependability and service behind our name are your assurance of perfect coil performance.

ELECTRIC CO. 93 MAIN ST

★ TOROIDAL FILTER INDUCTORS

★ LOADING COILS

* TOROIDAL TRANSFORMERS

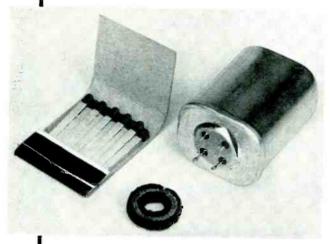

Miniature band
pass filter with
60 decibels attenuation in rejection bands
and using pictured "wedding
ring" coils.

We wind high Q toroid coils to $4^{\prime\prime}$ outside diameter and down to $1/4^{\prime\prime}$ residual inside diameter, wire sizes 22 to 38.

We offer a complete filter design and production service, plus a bank of toroid winders available to produce coils to your specifications. All popular core sizes are stocked and cover frequencies to 200 KC.

Your inquiries on special requirements are invited. Our immediate attention is assured.

COMMUNICATION ACCESSORIES COMPANY

110th St. and Hillcrest Road • Box 345 • Hickman Mills, Missouri



NEW BOOKS

(continued)

as well as the designer of telemetering equipment.

The various telemetering systems in common use are classified on the basis of the electrical variable in the transmitting channel, and the discussion proceeds accordingly. Approximately half of the book is devoted to current, voltage, frequency, position and impulse systems. The remainder of the book is given over to an explanation of interconnecting circuits, carrier-current systems, the remote reading of dials and registers, and data on coordinating, totalizing, computing and integrating equipment. Fluid telemetering is treated briefly in an appendix.

At the close of the book the authors present a bibliography, which they freely admit is incomplete, and a classified list of outstanding patents in telemetering technology as recommended reading. The potential user or design engineer who cannot take time for extended reading or research in basic principles or current practices will find this book a valuable addition to his reference library. R. H. Schaaf, National Radio Institute.

Microwave Receivers

Volume 23 in MIT Radiation Laboratory Series, EDITED BY S. N. VAN VOORHIS. McGraw-Hill Book Co., New York, 1948, 618 pages, \$8.00.

A COMPREHENSIVE treatment of microwave receivers is found in this volume. The book contains 21 chapters written by nineteen contributing authors. The first nine chapters deal with electrical elements of microwave receivers, such as microwave mixers and oscillators, i-f amplifiers, second detectors, gaincontrol circuits and video amplifiers. The mechanical construction of microwave receivers is reviewed in Chapter 10, and Chapters 11 and 12 discuss test equipment. The last nine chapters are devoted to an analysis of microwave receivers for several specific applications. Some of the receivers considered in these chapters are: An Airborne Receiver Incorporating Anticlutter Circuits, A Receiver for an Automatic-Tracking Radar, Wide-band F-M Receiver, Beacon Superheterodyne Receivers, Crystal-video Receivers and Superregenerative Receivers. These several types of receivers are



Now . . . the TV high voltage test problem solved with safety and operational confidence.

A super high voltage, custom-molded test probe, "Application Engineered" for the job . . . tested on the job . . . approved for the job.

Designed for SAFETY FIRST.

Rapid removal and interchange of the cartridge multiplier permits the TV probe to be used with more than one multi-range test set, via purchase of appropriate cartridge.*

Series TV High Voltage Test Probes are now on display at leading radio parts distributors and are available as follows: TVP—High Voltage Test Probe LESS multiplier cartridge. \$12.35 Net

TV-1—Model TVP WITH Cartridge for Precision Series EV-10 VTVM. \$15.45 Net

TV-2—Model TVP WITH Cartridge for Precision (or any) 20,000 ohms per volt test set with built-in 6000 V. D.C. range. \$15.45 Net

*Stock and special value multiplier cartridges available to match popular high sensitivity test sets.

Series TV High Voltage Test Probes provide direct kilovoltmeter facilities with existing high sensitivity test sets, and VTVM's such as the "Precision" models described below: Write for illustrated 1948 catalog describing complete line of electronic test instruments.

Lab. Type 20,000 ohms per volt AC-DC test set. 34 rotary selective ranges to 6000 V., 60 Megs., 12 Amps., 70 DB, 4½" meter. \$38.75

- MODEL 858-L-

20,000 ohms per volt Multi-Master, AC-DC V-O-M. 54 push-button operated ranges to 6000 V., 600 Megs., 12 Amps., 70 DB. $4\frac{1}{2}$ " meter. \$54.10

- MODEL EV-10-MCP -

Multi-range, zero-center VTVM plus AC-DC V-O-M facilities to 6000 V., 2000 Megs., 12 Amps., 70 DB. With large 7" meter. \$89.95

- MODEL 10-54-P-

Electronamic Tube Tester, and 20,000 ohms per volt AC-DC V-O-M. Ranges to 6000 V., 12 Amps., 60 Megs., 70 DB. 41/2" meter. \$134.40

PRECISION

APPARATUS CO., Inc. 92-27 Horace Harding Blvd. Elmhurst 10, N. Y.

Export Division, 458 Broadway, New York City, U. S. A. Cables, MORHANEX **NEW BOOKS**

(continued)

used to illustrate combinations of the circuits treated in the preceding chapters.

In view of the large number of authors who contributed to this volume, the coherence attained in the treatment of the several phases of the subject is to be commended. It should be admitted that one reading the book from cover to cover will encounter some repetition. On the other hand, the completeness with which each chapter presents its subject makes it ideal as a reference volume. While the discussion of receiver elements such as microwave mixers is of necessity not as exhaustive as found in the Microwave Mixer volume (No. 16), nevertheless a thorough treatment of each subject is provided. The book is written in a clear, easily understood manner. It contains an excellent balance between theoretical and practical information. The text is illustrated with numerous photographs, circuit diagrams and curves.

This volume should prove of great value to anyone interested in the design, test or maintenance of microwave receivers. It will enable the student to obtain a greater understanding of microwave receiver problems.—G. L. BEERS, RCA Victor Division, Camden, N. J.

Elementary Manual of Radio Propagation

Edited by Donald H. Menzel. Published by Prentice-Hall, Inc., New York, N. Y., 1948, 222 pages, looseleaf binding, \$7.65.

PROFESSOR MENZEL states the objective of this book in the preface when he says, "The range of frequencies useful for communication purposes depends upon a large number of factors, the most important of which are the location of the points of transmission and reception, the distance between the stations....By following the rules outlined in this elementary manual, we shall be able to analyze and predict the behavior of radio signals over any type of circuit and have further understanding of the whys and wherefores of our complicated but interesting communication system."

The present text is an outgrowth of a wartime Navy training pamph-

TECHNICAL Manuals

CUSTOM DESIGNED TO YOUR SPECIFICATIONS

Planned, written and illustrated by a select staff . . . experts in creating radio and electronic manuals for civilian & military use.

When you call upon Boland & Boyce to create your manuals you are relieved of every detail in their preparation. The entire operation is taken over and completed by a specialized staff with years of experience in publishing books & manuals.

First the requirements for your manual are completely surveyed. The working conditions to which they will be put are studied and the operations or equipment described in the manual are thoroughly analyzed. A complete outline is then prepared and submitted for your approval, along with a dummy of the manual as it will appear when finished. Upon your approval the job is completed and delivered with your satisfaction guaranteed.

Boland & Boyce manuals incorporate only the most modern editorial and illustrative style. Each project is treated with individual attention in technique of presentation and editorial approach. The Boland & Boyce military and civilian manuals now in use throughout the world are our best recommendations.

U. S. Navy
U. S. Signal Corps.
Sylvania Electric Products, Inc.
The National Company
Western Electric Co.
Bell Telephone Laboratories
Maguire Industries, Inc.
Allen B. Dumont Laboratories, Inc.
General Electric Co.
Mine Safety Appliances Co.

Write or wire Boland & Boyce today for more information.

BOLAND & BOYCE INC., PUBLISHERS

Radio Maintenance
Technical Manuals
Manual Division M-3
CHICAGO: 228 No. LaSalle St.

Radio Data Book Video Handbook Montclair, N. J.



GENERAL ELECTRIC THERMOCELLS for ACCURACY

G-E thermocells are as small as it is practical to make them and still retain all of the advantages which broaden their field of application and simplify the problems of design engineers.

Design engineers will appreciate especially the octal base feature. Add in these other major advantages in G-E thermocells—then specify them for every job you have under consideration.

- G-E thermocells ore filled with an inert gas and sealed to inhibit atmospheric contamination of both crystal and thermostat contacts.
- Warm-up time is extremely short because of the low thermal capacity of the unit as a whole.
- The heat loss is low, which permits low operating power and consequently less load and longer life for the thermostot contacts. Radiant heat loss is minimized by the pollshed chromium-plated shell.
- 4. Durable platinum-iridium thermostat contacts are used in G-E thermocells.

A typical example of the G-E line of thermocells is the Type G31:

Frequency Range 2500-10,000 K.C.
Size and ShapeSame as 616
Freq. Adj. at Normal
Ambient Temperature0015%
Ambient Temp. Operating Range0 to 55°C.
Long Time Frequency Stability
better than
Heater Power
Crystal Cuts Normally Used AT & BT
Electrodes and MountingPressure Airgap
Warm-up Time

For further information on this and other G-E thermocells, quartz crystals and germanium diodes write today to: General Electric Company, Electronics Park, Syracuse, New York.

185-G2



NEW BOOKS

(continued)

let that resulted from the need for rapid instruction of large numbers of personnel having a limited technical background.

Approximately half the book is devoted to the properties of the ionosphere and procedures for calculating quantities such as interstation distance, great-circle mans. maximum usable frequency, and lowest useful high frequency. Intermingled with the computation rules is a large amount of descriptive material concerning the general characteristics of the ionosphere and their relation to the sun, solar phenomena such as sunspots and prominences, and terrestrial and cosmic noise. This material makes highly readable text and is useful in giving a qualitative understanding of ionospheric propagation, but the manner in which it is distributed throughout the manual does not contribute to efficient use of the computational material.

The second half of the book is divided principally among ground-wave transmission, methods for calculating field strengths at frequencies above 30 mc, and discussion of the effect of the atmosphere on coverage and its operational implications. Calculation methods are necessarily limited to the case of a well-behaved atmosphere, but anomalies are discussed in an interesting manner.

An excellent feature of the manual is the predominance of welldesigned alignment charts and nomograms. The arithmetical work involved in computation is reduced to a minimum number of simple operations with quantities obtained from the charts. The few accompanying equations are written with coefficients collapsed to numerical values, and are not always well labeled with regard to units. Such a procedure is suitable for rapid calculation after the system has been learned but is likely to annoy the informed person who is attempting to follow the material or compare it with other techniques. There are no derivations in the text, but some of the important relations are derived in two highly condensed and not particularly readable appendices.

In keeping with the elementary nature of the text, many compli-



USE

TERMALINE DIRECT-READING RF WATTMETERS



MODEL 61

POWER RATING 80 Watts
Standard Ranges 0-15 & 0-60 W
(Dual) 0-20 & 0-80 W
Special Ranges 0-1 & 0-2½ W
0-2½ & 0-10 W
0-1 & 0-5 W
0-2 & 0-20 W

MODEL 67

> MODEL 67C (woter-cooled)

POWER RATING 22 2500 Watts Single, Dual or Triple ranges to order.





Visit Our Display Booth, I.R.E. Show, March 7-10, 1949

The theory and application of electronics in industry

INDUSTRIAL ELECTRONICS REFERENCE BOOK


By Electronics Engineers of the Westinghouse Electric Corp.

> This book was compiled to answer the need for complete and clear information on the application and design of industrial electronic equipment. Written by a group of engineers, each an expert in his particular branch of electronics, the Industrial Electronics Reference Book contains the most recent in-

formation on the subject. The material is directed at the practicing engineer. Its aim is to give him a better understanding of the scope and limitations of electronic apparatus as it is applied to industrial processes.

1948 680 Double-column Pages \$7.50

				AL C	OUP	ON	
10HN 440 Fo					D.T.	37	
Please INDUS BOOK	send : TRIAL If I plus p	me, on L EI decide ostage;	ECT to ke	days' RONIC	appro	REF	ERENC vill remi
Name							
Addres	5						

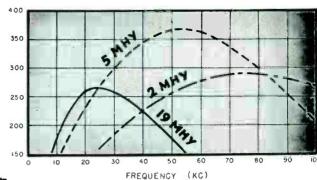

For OUTSTANDING CORE **Performance**

MOLDED TRANCORS Lenkurt Trancors are now being made to the remarkable Q characteristics above. Infinite care is required to make such parts. Available in a broad variety of low-cost standard cores and assemblies, or special items.

Write for catalog

LENKURT ELECTRIC CO. SAN CARLOS, CALIFORNIA

LENKURT KNOWS HO

"Where Professional Radiomen Study"

CAPITOL RADIO Engineering Institute

An Accredited Technical Institute 16th and Park Rd., N.W. Dept. E-11 Washington 10, D.C.

Advanced Home Study and Residence Courses in Practi-Radio-Electronics and Television.

Approved for Veteran Training.



WASHERS • SMALL STAMPINGS • WIRE PARTS

TO YOUR SPECIFICATIONS

- any quantity
- any material

any finish

LONG OR SHORT RUNS

For prices and delivery send blue-print or sample.

Sheffco Manufacturina Co.

116 W. RUBY AVE. . PALISADES PARK, N. J.

SELF-LOCKING SOCKET SET SCREW



The KNURLED cup point of this popular "Unbrako" Socket Set Screw makes it a Self-Locker . . . because the keen edges of the counter-clock-wise KNURLS won't creep, regardless of the most chattering vibration. A real fastener, if ever there was one . . . positively won't shake loose!

Knurling of Socket Screws originated with "Unbrako" in 1934.

Write us for the name and address of your nearest "Unbrako" Industrial Distributor and your copy of the "Unbrako" Catalog.

Over 45 Years in Business

JENKINTOWN, PENNA. CHICAGO

BOX 596

DETROIT . INDIANAPOLIS . ST. LOUIS . SAN FRANCISCO



IN COMMUNICATIONS TERMINAL EQUIPMENT

ROANWELL . . . the successor to Aviometer who for years has provided the communications industry with the finest terminal equipment. Aviometer has been completely reorganized . . . new plant, expanded production facilities and quality control. New engineering talent has been added to the former staff long recognized as tops in its field. These changes and additions now make it possible to provide engineeringly correct, economical and speedy solutions to any terminal equipment problem.

SPECIALISTS IN SPECIAL REQUIREMENTS

In addition to their standard line, designed to meet normal needs, ROANWELL is well equipped to engineer and produce special units to meet the most exacting requirements. Their catalog, now available upon request on company stationery, tells the ROANWELL story and their successful solutions for some of the industry's top manufacturers.

The AVIOMETER Div.

ROANWELL CORPORATION

662 PACIFIC STREET, BROOKLYN 17, N. Y.

NEW BOOKS

(continued)

cated phenomena have been reduced to rules of thumb or much-simplified descriptions; in general, these are interesting and readable but should not be taken too literally. There are numerous errors and half-truths, particularly in connection with the effects of atmospheric refraction, but as no coverage calculations are based upon them little harm is likely to result. There are several well-worded warnings to operators concerning such matters as the interim nature of much of the basic data and the use of "standard" radar targets to check set performance.

This manual will undoubtedly be very useful for its announced purpose, that of training operating personnel in some of the practical aspects of the effects of the propagation path on radio and radar set performance. It is not suitable as a scientific reference or text, but contains some practical material that could be useful to a student after the basic physics of the subject has been mastered.—Donald E. KERR, Research Laboratory of Electronics, MIT.

Fluorescent and Other Gaseous Discharge Lamps

By WILLIAM E. FORSYTHE AND ELLIOT Q. Adams, Nela Park, Cleveland. Murray Hill Books, Inc., New York, 1948, 292 pages, \$5.00.

DEPENDING on where you may open this book, it looks like a text on chemistry, physics, photography, illumination, television, or electronics. This is as it should be, because today the discharge of electricity through gases and vapors encompasses all these fields.

Approximately two-thirds of the book is devoted to the fluorescent lamp that was introduced in 1938 and has today become a major source of industrial illumination. The first three chapters trace the physical basis by reviewing light and radiation, characteristics of electrical discharges, and the phenomena of fluorescence, phosphorescence, luminescence and photoluminescence. Engineering details of problems encountered in making straight and circular lamps in various lengths an sizes are covered.

An entire chapter is devoted to fluorescence as applied to television and radar cathode-ray tubes. Valu-

light, Folding Hand set Style 197 shown

open position.

Style 197 shown in folded position. Small and light enough to be

able tables list color, brightness and decay time of various phosphors used as single screens and as cascade screens.

It is significant that much of this book was written during working hours, with drafting and stenographic help being made available to the authors by their employer. The writing of a technical book is for most people the hardest type of work, with relatively small financial recompense, and continued encouragement of this nature can in many cases stimulate competent authors to action. Commendation for the high quality and overall technical value of this book must therefore go to General Electric Co. as well as to the authors.—J.M.

Books Received for Review

ATOMIC ENERGY. By Karl K. Darrow. John Wiley & Sons, Inc., New York, 1948, 80 pages, \$2. The 1947 series of four Norman Wait Harris lectures delivered at Northwestern University describes to the nonphysicist "the basic facts most pertinent to the transformation of energy of rest mass into energy of motion and energy of heat".

IONOSPHERIC RADIO PROPAGATION. National Bureau of Standards Circular 462, 209 pages, available from Superintendent of Documents, U. S. Government Printing Office, Washington 25, D. C. Remit \$1 in U. S. currency only; foreign orders add one-third to cover postage. Physical and mathematical theories underlying radio-wave propagation by reflection from the ionosphere are brought into understandable relation with practical problems of radio communication. Several problems are worked out in detail to assist the reader in specific applications.

DESIGN OF CRYSTAL VIBRATING SYSTEMS. By William J. Fry, John M. Taylor, and Bertha W. Henvis. Dover Publications, Inc., New York, 182 pages, \$3.50. Eliminates lengthy design computations for systems incorporating piezoelectric materials by presenting design procedures involving graphs based on fundamental piezoelectric relations. Originally published as a confidential war-time report of the NRL.

AMERICAN ELECTRICIANS' HAND-BOOK. By Terrell Croft. McGraw-Hill Book Co., New York, 1948, Sixth Edition, 1773 pages, \$6.00. Revision of 1942 edition to agree with 1947 edition of National Electrical Code, with approximately 250 pages of new material on latest developments. An entire new 80-page division deals with electron tubes and circuits as used in industry.

SURVEY OF EXISTING INFORMATION AND DATA ON RADIO NOISE OVER THE FREQUENCY RANGE 1—30 MC. By H. A. Thomas and R. E. Burgess. Radio Division, National Physical Laboratory, His Majesty's Stationary Office, London, 1947, 126 pages, paper cover, 3 shillings. Types of noise that can limit the sensitivity of receivers are considered theoretically and comparison is made with measurements, from which the noise level at various locations can be assessed.

TELEVISION PRODUCTION PROB-LEMS, By John F. Royal and ten contributors. McGraw-Hill Book Co., Inc., New York, 1948, 179 pages, \$2.50. Symposium based on lectures given jointly by Columbia University and National Broadcasting Co. One Chapter, The Science of Television, is by NBC engineer F. A. Wankel and presents simplified technical data: the remaining ten chapters cover programming.

be exact...



with this industry-accepted

TIME DELAY TIMER

Synchronous motor driven, automatic reset, designed to delay closing or opening of a timed electrical circuit for electronic equipment, heat application, conveyors, X-ray equipment, plastic extrusion and molding, and for recycling operations. Available in maximum intervals of 15, 30 and 60 seconds, 3 or 5 minutes. Bakelite cased, 3 in. diameter.


A few of the timers we build for industry:

- Automatic Reset
 Signaling
- Push-button Automatic Reset
 Panel-mount Time Delay
- Behind-the-panel-mount Time Delay
 Others for special purposes.

We have more than 400 types of timers for you to choose from. Write us your requirements.

INDUSTRIAL TIMER CORPORATION

111 Edison Place, Newark, New Jersey

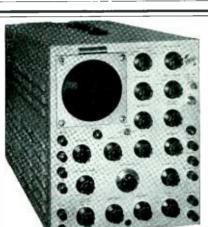

Tektronix Type 511-A Oscilloscope

- Wide band vertical amplifiers (10 mc. 1 stage; 8 mc. 2 stages).
- Vertical amplifiers individually adjusted for optimum transient response at high and low frequencies.
- Vertical deflection sensitivity 0.27 V to 200
 V per cm. (peak to peak).
- 0.25 microsecond video delay line may be incorporated at nominal charge.

AUGMENTED ACCURACY...

IDUSTRIX

The Tektronix Type 511-A Oscilloscope retains all of the features that have made its predecessor, the Type 511, the universally accepted instrument in its category, **PLUS** a completely new power supply providing full regulation in all DC circuits, including the accelerating voltage. Line voltage fluctuation between 105 and 125 volts produces no noticeable effect on image intensity, sweep speed or deflection sensitivity.

The Type 511-A is a truly portable precision instrument—total weight 50 pounds and self-contained.

TYPE 511-A FEATURES

- Continuously variable sweep speed 0.1 sec. to 1 microsec. (10 cm. deflection).
- Calibrated direct reading sweep speed dial, permitting quantitative measurement to 5% accuracy.
- Choice of triggered, recurrent or single sweeps at all speeds.
- Any 20% of normal sweep may be expanded 5 times.

Price \$795.00 f.o.b. Portland Your inquiry will bring more detailed information and name of the nearest Field Engineering Representative.

Phone, EAst 6197
Cables, TEKTRONIX



712 S. E. Hawthorne Blvd.
Portland 14, Oregon



Backtalk

This department is operated as an open forum where our readers may discuss problems of the electronics industry or comment upon articles which ELECTRONICS has published.

Frequency Allocations


DEAR SIRS:

THE faulty assumption in Courtney's article (ELECTRONICS, August 1948, p 73) is that monitoring is a sufficient index upon which to base allocations. Such is obviously not the case.

If a given service, e.g., police, is recognized by the FCC, frequencies must, of course, be reserved for an indeterminate period to allow every municipality, county and state to obtain equipment and put it into use. Inevitably there will be a period, varying according to the nature of the service, up to several years when frequencies so reserved have not been put into use in particular areas. Only chaos could result if other services were licensed on the frequencies so reserved for a given recognized service.

The licensing of any service presumes it has been recognized as being in the public interest and its establishment on any frequency can only be done as the result of the purchasing of communication equipment. The displacement of such a service at a later date without having replacement frequencies available simply would mean shutting down the service for lack of frequencies. The purpose of the allocation table, in other words, is to reserve bands of frequencies for the several services. The locations and widths of these bands are intended to represent a balance based upon the relative public interest, convenience, and necessity of each of

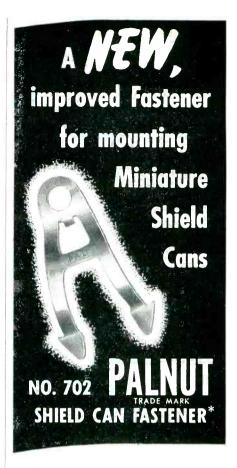It is inevitable that some services will exploit their frequencies sooner than others. If adjustments in the allocations were made solely on the basis of the rate of growth of the different services, then the situation that Courtney envisages might,



- · Strong, positive grip
- No tolerance problem
- Low assembly cost

Installs in popular shaped holes shown below



Live spring arch bolds can tightly against chassis

Will not pull out until deliberately released



A quick snap of the PALNUT Shield Can Fastener into the chassis provides a secure job, speedily assembled at low cost. Good ground contact is maintained. May be used on any chassis thickness,

SAMPLES and data on PALNUT Shield Can Fasteners sent upon request on your Company letterhead.

*Par. Pending



The Latest News of Science **Now Yours in One Big Magazine!**

Now at last you can keep up with the new inventions and discoveries of science that affect you and your industry. Every month Science Illustrated is filled with new advances in vital fields...Electricity, Construction, Aviation, Atomic Energy, Radio, Synthetics, Mining, Chemistry, Electronics, Home Appliances, etc. Home Appliances, etc.

Science Illustrated shows you new products and designs and explains why, when and how they were made. Every monthly issue is packed with 30 complete, authentic articles and 140 photographs, diagrams.

ORDER NOW AND SAVE \$4!

You can order 36 big issues of Science Illustrated (3 full years) for ONLY \$5! This special rate saves you \$4 over the one-year price. We'll start your subscription with the big new issue now on the press-if you order within 10 days!

MAIL THIS ORDER FORM TODAY!

Science Illustrated 330 West 42nd Street, N. Y. 18, N. Y. YES! I accept your special offer. Start my subscription to Science Illustrated with the new issue now on press. I prefer 2 yrs. at \$4 (Saves me \$2 compared with the 1-yr. rate) I prefer 3 yrs. at \$5 (Saves me \$4) I prefer 1 yr. at \$3 Bill me later Payment enclosed
Name
Address
, colyster .
CityZoneState
ALSO ON SALE AT ALL NEWSSTANDS 25c
E-11-48

BETA HIGH VOLTAGE POWER SUPPLIES



Input: 115 volts, 50/60 cycles; 75 volt-amperes, Output: 0-45 KV, negative grounded, 100 ua available at 40 KV. Short-circuit current limited to 500 ua. Safety Features: Internal interlock on cabinet door, Provision for external interlock on test

door, Frogston for the state of the same apparatus.

Size: 21" x 40" x 15".

Insulation: Air insulation throughout.

Power Supplies up to 200,000 volts DC. regulated or unregulated, built to specifications. Compactness, low cost and rapid delivery featured. Submit your high voltage power supply requirements to us for a prompt bid on price and delivery.

Other BETA products include:

KILOVOLTMETERS up to 50 KV. PORTABLE 0-30 KV DC POWER SUPPLIES. ELECTRONIC MICROAMMETERS — 0.01 μ a full-scale. Send for descriptive literature

Field Engineers throughout the country are at your service to discuss our products more thoroughly with you.

BETA ELECTRONICS CO 1762 Third Ave., New York 29

A B RESISTORS

Prompt Delivery From Stocks

ALL LEADING MAKES RESISTORS AND POTENTIOMETERS **ERIE CAPACITORS** SILVER MICA CAPACITORS

We are nationally recognized as a dependable source of supply—by the "blue chips" of the electronic industry (names on request).

We supply many Manufacturers, Universities, Research Laboratories and fill Government orders per JAN specifications.

Wire, write or telephone at once for price list. State your requirements. Courteous reply and service is guaranteed.

LEGRI S COMPANY, INC.

130 WEST 102ND STREET

Telephone: ACademy 2-0019



SMALL PARTS

Filaments, anodes, supports, springs, etc. for electronic tubes. Small wire and flat metal formed parts to your prints for your assemblies. Double pointed pins. Wire straightened and cut diameter up to 1/8-inch. Any length up to 12 feet.

LUXON fishing tackle accessories. Inquiries will receive prompt attention.

> ART WIRE AND STAMPING CO.

227 High St.

PERFECT COILS!

Newark 2, N. J.




PAMARCO tensions are the perfect answer to lower coil winding costs!

- ★ FINGER-TIP TENSION CONTROL
- **★ OPERATOR MAKES OWN ADJUSTMENTS**
- * NO TOOLS OR ACCESSORIES NEEDED
- * FITS ALL COIL WINDERS

The free-running action of the PAMARCO tension practically eliminates defective coils. Their compact size permits more simultaneous coil winds on any machine. Operator makes all adjustments for any gauge wire with simple thumbscrew.

Write Dept. E-1 for Literature Today

 PAPER MACHINERY & RESEARCH, INC. 014 OAK STREET . ROSELLE, NEW JERSEY



TO MEET YOUR SPECIFICATIONS

BASIC DECADE COUNTER

To meet your specifications, basic decade counters are combined with electronic switching circuits by us to provide counters and timers for factory and laboratory.

FEATURES

Over 150,000 counts per second.
Elapsed time measured to less
than 7 Micro Seconds.
Decimal indication of count.
Number of decades specified.
Ouput signals switchable to any

Presetting switchable to any count. Simultaneous inputs to two or decades.

+ or — difference counts directly indicated.

Automatic sequencing of two or more counters.

These and many other features are available at a price comparing favorably with stock counters. Send us your counting or timing problem for quotation.

Production Control Equipment Engineered and Constructed to the Customer's Satisfaction.

Technitrol Engineering Co., Inc. 3212 MARKET ST.



SEND FOR ARBOR LIST
OF OVER 1000 SIZES
OF OVER 1000 stock arof over 1000 stock arobligation.

With a wide range of stock arbors... plus the specialized ability to engineer special tubes... PARAMOUNT can produce the exact shape and size you need for coil forms or other uses. *Hi-Dielectric, Hi-Strength.* Kraft, Fish Paper, Red Rope, or any combination, wound on automatic machines. Tolerances plus or minus .002". Made to your specifications or engineered for YOU.

Inside Perimeters from .592" to 19.0"

PARAMOUNT PAPER TUBE CORP.

616 LAFAYETTE ST., FORT WAYNE 2, IND.

Manufacturers of Paper Tubing for the Electrical Industry


indeed, come to pass. That is, a commercial service whose benefit from the use of the spectrum is the saving of money or making of a profit, due to the use of radio, logically would invest in communication equipment more rapidly than a safety service, such as city fire departments, where the obtaining of equipment is dependent upon the approval of tax-supported budgets by the local citizens. Further, the comparative frequency loading. from a traffic-handling standpoint, by two such services can represent a wide range of extremes. Aside from routine testing of radio equipment, a fire department might have very few messages to pass for protracted periods of time, depending upon the number of fires which

Would it be feasible to allow taxicabs to employ fire station frequencies during periods when there is no fire? Obviously not, since when a fire occurs the fire frequency must be instantly available on a noninterference basis and no time could be allowed for clearing taxicabs from such frequencies. Even if it were possible to do so, the service to taxicabs on the basis of such uncertainty of frequency time would be impracticable from the point of view of the taxicabs.

The railroad example Courtney mentions was the subject of an FCC action prior to publication of his article, but his article apparently was written prior to the FCC action. I will not discuss it here because it involves a pending Commission hearing as do some of the other detailed examples. The extent to which these problems would be solved by the FCC proposals may be judged by each person concerned after inspection of the public announcements in Dockets 8965, 8972, 8973, and 8974.

Monitoring is a tool but it is not sufficient. Nor is the so called "need" a sufficient tool. Presumably any one who requests the use of radio can demonstrate a "need" and even "frequency requirements." As to whether these requirements can be satisfied by an allocation depends just as much upon the relative importance of other services as upon the needs of the service requesting the allocation.

The main theme of Courtney's

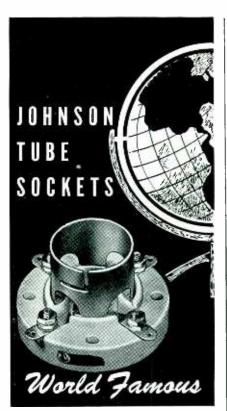

Thoughtful design, superb workmanship and top quality materials are combined in the manufacture of JOHNSON sockets to earn for them the reputation as the world's finest.

Illustrated above is the JOHNSON 123-209, a 4 pin bayonet type socket for medium power tubes having a medium 4 pin bayonet base, such as the 866.

Also available is the 123-210, a similar JOHNSON socket that fits the same tubes as the 123-209 but which is slightly smaller in size.

The 123-211 is a larger 4 pin socket for tubes such as the 872.

The 123-216 is for tubes having a GIANT 5 pin bayonet base such as the 803 and KK28.

These high quality JOHNSON tube sockets, which represent only a part of the extensive JOHNSON tube socket line, are available in porcelain or steatite.

See them at your dealers or write for latest catalog.




BACKTALK

article deals with the dual jurisdiction in the United States over the radio spectrum. Let us examine this question from the standpoint of our philosophy of government, and more particularly from the standpoint of what can be done about the situation. The present jurisdiction is contained in the Communications Act of 1934, but the plan now in force also was contained in the preceding law, the Radio Act of 1927, which was superseded by the Act of 1934. The system has, in fact, been followed since 1922. The existing legislation provides that the FCC may assign frequencies to non-federal stations throughout the radio spectrum. There is no restriction on the Commission's authority in this respect. The very same legislation provides, however, that the President assigns frequencies to federal government stations. Here again, there is no limit or restriction of any kind on the President's authority. Moreover, and this is the interesting point, there is no procedure established in the legislation which provides for a reconciliation of conflicts between assignments made by the FCC and those made by the President. The legislation is silent on this point, except for a "time sharing" section which is not applicable in all cases. It is doubtful the courts would be in a position to resolve conflicts of this kind since it would be necessary to such a court's decision to evaluate the determinations made by the President and by the Commission. Fear of a court reversal might cast a shadow upon the investment of substantial sums

(continued)

Next, we recall that the President has no authority over the FCC in matters of substance. The President appoints the Commissioners subject to ratification by the Senate but he does not have authority to direct, control, or veto actions of the Commission, nor can the Commission direct the President. In practice, the President has delegated his authority, under Section 305 of the Communications Act of 1934, in the matter of assignment of frequencies to government radio stations, to the Interdepartment Radio Advisory Committee. This is a voluntary committee composed

in given bands of frequencies.

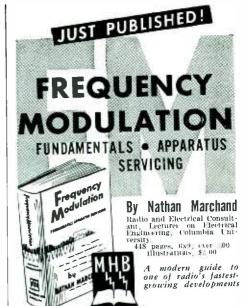

SIMPLIFIES SERVICE -**ENGINEERING PROBLEMS!**

It takes more than ordinary radio servicing knowledge to handle the complicated special problems and methods of modern FM work! This new book by a well known radio and electrical consultant has been specifically written, first to help you understand FM clearly and, second, to explain fully just how to go about handling FM work.

handling FM work.

With a minimum of mathematics, but with a copious use of easily understood illustrations, schematic diagrams and practical on-the-job examples, it covers the complete field of frequency modulation. Basic theory, circuit, transmitters, receivers and mobile equipment are fully explained — and special emphasis is placed on up-to-the-minute methods of installing, adjusting and repairing FM receivers.

ing, adjusting and repairing FM receivers. Here at your fingertips you have everything necessary for a complete understanding of the subject — from circuit peculiarities, tuning indicators, to antennas, mobile equipment, FM test units, receiver alignment, general servicing procedure, and a host of other essential subjects. Particular attention is paid to outlining the important points of difference between FM and ordinary AM work.

Here's What It Includes

- I. Fundamentals of Modu-lation. 9. FM Detectors 10. Amplitude Limiters
- 2. Fidelity of Band Width Requirements 10. Amplitude Linuxus 10. Amplifiers, Oscillators, and Converters
- 3. Noise and Interference 4. Direct Frequency Modu-lation
- 6. Direct FM Transmitters
- 7. Phase to Frequency Modulation
- 8. FM Transmitters Using Phase Modulation 18. Phasor Calcul
- 12. Intermediate Frequency and Audio Circuits
- 13. FM Receivers
- 5. Frequency Control Circuits 13. FM necessors
 14. FM Transmitting Antennas 15. FM Receiving Antennas
 - 16. Mobile FM Equipment

 - 18. Phasor Calculations, etc.

READ IT AT OUR RISK!

We're so sure you'll want to keep this new FREQUENCY MODULATION book for day to day study and reference, that we'll gladly send it to you for 10 days' examination. Read it carefully. See how quickly it brings you up-to-date on developments in this fast-growing field. Then decide whether or not you want to buy it or return it. We'll take the risk! Send no money, just mail the coupon now.


10	DAY	TRIAL	COUPO	ì
			,	

232 N	ladiso	n .	A٧	e.,	- 1	Ne	w	•	Y	ıΓ	k	1	6,		N		Υ							
TION 10 da returi	d me for ys I w i book return only.	10 111 100	da se stj	ne ne pa	id id	\$5 	Y.	n pl o	iii iii sta te	18 8 2 8 2	t t te	in fe	n 'W	id n	e e l	n to	aj ts	p p a a	re oo sl	ov st a	a a o	l. ge rd i a	i, le	I rs i
Name																								
Addre	ess													٠.										
City.	Zone,	81	at	۴.																				
Occur	ation																							

NOW FOR TELEVISION RECEIVERS

SUPER CONVERTERS WITH PICTURE CONTROL



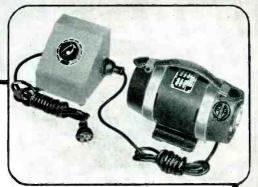

The Ideal DC to AC Portable Power Supply for Popular 7" Television Receivers

Now you can operate TELEVISION in DIRECT CURRENT districts, with perfect picture reception. Simply plug in Carter Super Converter, connect your receiver, and tune in! Exclusive Carter "Picture Control" assures clear reception, without drift, wave, or flutter. Converter AC output requires NO FILTER. Operates on 110 to 135 v. DC. Model D1010CT operates 7" receivers up to 125 watts load. Compact, lightweight.

GET NEW BULLETIN, INFORMATION, PRICES

Special TELEVISION CONVERTER BULLETIN #948 just off the press. Gives complete information, pictures, prices. Sent FREE by return mail. WRITE TODAY



2646 N. MAPLEWOOD AVENUE

CABLE: GENEMOTOR

HEAT RESISTANT WIRES FOR EVERY APPLICATION . .

DESIGN ENGINEERS.

Do those new circuit designs present new wire problems?

Then check with Lewis Engineering for an economic solution and fast delivery. For twenty years we've successfully been solving the heat and age resistance wire problems of industry. We don't stock wire-we make it to your specs-for an experimental run or for the production line. If you're designing in the electronic, electrical or appliance field . . .

HEATING UNITS

HEATING ELEMENTS

RESISTANCE LINE CORD

THERMOCOUPLE WIRE

ASBESTOS LEAD & FIXTURE WIRE

INSULATED RESISTANCE WIRE

FIBERGLAS INSULATED WIRE

WIRE TO ANY **SPECIFICATIONS**

Let Lewis Build The Wire For You

Send your electronic control, communications or appliance wiring specifications for a recommended solution by our engineers. FOR A TRIAL ORDER OR A CARLOAD consult



LEWIS ENGINEERING

Dinnision NAUGATUCK

CONNECTICUT

BACKTALK (continued) of those agencies operating government radio stations. The Commission obviously cannot deal di-

rectly with the President on each frequency assignment since there are thousands of such assignments every year. Even on basic matters of frequency allocations it would be safe to assume that the President would seek the advice of his cabinet officers in those Departments which operate government radio stations. The views of such cabinet officers would be the same as those ex-

pressed by the same departments in the IRAC. Since there are differences of opinion on many problems solely as between the government agencies using radio, the President presumably would seek a compromise in each such problem.

To the extent IRAC can (and has for over 25 years) arrived at such equitable compromises on a voluntary basis it would be unlikely that the President would arrive at decisions drastically different from those arrived at voluntarily by the IRAC. In any case, his own independent decision most probably would represent a point of view different from that arrived at by 4 or more of the 7 Commissioners of the FCC. This is a thoroughly reasonable assumption since the 7 Commissioners seldom are unanimous on such matters as frequency allocations. Considering the President as an eighth individual, and recognizing that he would be motivated by reasons different from those that motivate the Commission (because the President would base his decision upon the views of the government agencies whereas the Commission would base its thinking upon the cases presented by the public to the Commission), there might still be an area of disagreement or difference of opinion as between the Commission and the President. A deadlock would mean that no frequency could be assigned anyone until a decision was made. The possibilities exist of requesting Congress to resolve any dispute which might arise, or of direct negotiations between the President and the Commission, or, as is presently done, by arrangements between the IRAC, and the representative of the President, and the Commission.

This explanation is a little clearer



Manufacturers of Quality Capacitors—Oil and Wax

Fabricated Plate ELECTROLYTICS

- **★ RADIO**
- * AUTOMOTIVE
- **★** TELEVISION
- **★ ELECTRONICS**
- **★ MOTOR STARTERS**
- * POWER FACTOR CORRECTION

Your Specifications for Quotation will be given Prompt Attention

CHICAGO CONDENSER CORPORATION

3255 WEST ARMITAGE AVENUE

CHICAGO 47, ILLINOIS

Send For This Valuable Mailing List Data!

To aid you in planning your direct mail, check any of these mailing lists you may be interested in . . .

business i			
Electrical	Appl	iance	Dealers
Manufaetu	ring	Indust	ries

- ☐ Metal-Working Industries Aviation Industries
- ☐ Bus Industry
 ☐ Chemical Processing Industries Bus Industry ☐ Civil Engineering and Construc-
- tion Industries Coal Mining Industries Electrical Industries
- Electronic Engineers
- Food Industries
- Metal Mining Industries Power Plant Engineers
- Product Design Engineers
- ☐ Textile Industries ☐ Welding Industry Textile Industries

. . attach this 'ad' to your business letterhead . . . and mail. We'll send you complete information, selections, list counts, and prices. No obligation, of course.

Direct Mail Division

McGRAW-HILL Publishing Company

330 W. 42nd St., New York 18

DEVELOPMENT **ENGINEER**

Communications Engineer or Physicist with a minimum of ten years' electronic development experience wanted for circuit development work on commercial test equipment.

Excellent opportunity for permanent employment in congenial surroundings with good working conditions.

All replies held in confidence. Please submit complete resume directly to

Dr. G. A. Downsbrough

BOONTON RADIO CORPORATION

BOONTON, NEW JERSEY

COIL WINDING **MACHINES**

We manufacture machines to wind all types of coils on a laboratory or production basis.

also

Assembly Fixtures Miniature Tube Pin Straighteners **Dummy Tubes** Tube Pullers

Production Equipment Co.

37 West Main St.

Oyster Bay, Long Island, New York

Phone Oyster Bay 6-0009

FREE! send for our

- a complete and diversified line-up of:
 - electronic equipment
 - o sound systems
 - o recording equipment
 - amateur gear
 - television components and kits
 - o replacement parts
 - · laboratory and service test equipment

Save time and money—buy direct from distributor! Consult the NEWARK radio buying guide, featuring all standard makes ... a value-packed listing of 20,000 essentials for expert servicemen, engineers, soundmen, experimenters, teachers, hobbyists, amateurs!

24 HOUR SERVICE ON ALL ORDERS Free technical advisory service!


> JUST MAIL THIS COUPON TO GET YOUR CATALOGUE Newark Electric Co., Inc., Dept. 8 242 West 55th St., New York 19 Please send me the FREE Newark Buying Guide of fine radio equipment.

Name Address City_ State

RADIO & TELEVISION

115 W. 45th St. & 212 Fulton St., NEW YORK and 323 West Madison Street in CHICAGO

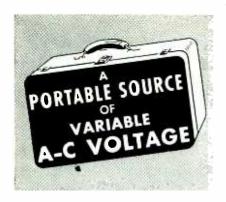MAIL DRDER DIVISIONS 242 West 55th Street, NEW YORK 19, N. Y. 323 West Medison Street, CHICAGO 6, N.L.



VOLTBOX A-C POWER SUPPLY

- COMPACT
- PORTABLE
- HANDY

Operation of the Superior Electric VOLTBOX is simple. Plug into 50/60 cycle single phase source, snap "ON-OFF" switch to "ON". Snap "LINE-LOAD" switch to "LOAD", rotate knob to produce continuously adjustable output voltage, from 0 to 17 per cent above line voltage. Read line voltage by snapping "LINE-LOAD" switch to "LINE".



INPUT:

115 volts, 50/60 cycle,

single phase

OUTPUT-

0-135 volts, 7.5 amperes,

1000 VA

Type UC2M available for 230 volt operation.

ALL THIS IN ONE PORTABLE PACKAGE

Cast aluminum case • POWER-STAT variable transformer • Easyto-read voltmeter • Superior 5-Way Binding Posts • Output receptacles • "ON-OFF" switch • "LINE-LOAD" switch • Renewable fuse for overload protection • Six foot cord-plug.

FOR FULL DETAILS WRITE

THE SUPERIOR ELECTRIC COMPANY 411 MEADOW STREET BRISTOL, CONN.

BACKTALK

than the actual situation which Courtney describes. Up to this point neither Courtney's article nor this letter has examined the reasons behind this most peculiar situation. An understanding of these reasons is fundamental to the drafting of a plan for improvement. The reasons are briefly these. The military, that is the Army, Navy, and the Air Force, probably would not wish to apply to an independent civilian board or commission for frequencies to be used for the national defense. Presumably, the President, as Commander-in-Chief, could direct the military to do just that but it is an unlikely situation and one which will certainly not come to pass at a time when the country is arming for defense. As long as there is a requirement to maintain the Armed Forces in peacetime, it is unlikely that the President and the Congress would allow a nonmilitary agency to parcel out frequencies to be used for military purposes. This is the situation that appears to exist. Only to the extent it is fallacious can this factor be ignored.

(continued)


Next, it certainly can be stated that the public, in peacetime, would not wish its frequencies to be parceled out by the Armed Forces. Here again is an assumption based upon our way of life, and only to the extent that this assumption is invalid could this factor be ignored. The source of the federal authority to regulate the use of the radio spectrum is recognized by all to be the Congress, and the so-called dual jurisdiction over the radio spectrum could be eliminated only by new legislation. The 1927 Act and the 1934 Act obviously intended a dual jurisdiction and the final report of the Select Committee of the House of Representatives (H.Res. 21-78th Congress) which reviewed this point in detail in 1943-4 stated in part: "The broad division of jurisdiction seems to be a logical one."

One might suggest that appropriate military authorities be made Commissioners ex officio, at least to the extent of having veto power over actions of the Commission which might affect military frequencies. A little thought will reveal weakness in such a plan. The position taken by such military

CORONA-FREE RF FILAMENT TRANSFORMERS FOR TELEVISION AND NUCLEAR RESEARCH



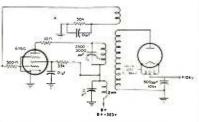TYPICAL 10KV CIRCUIT SHOWING USE of CORONA-FREE RF FILAMENT TRANSFORMER



This unit is designed to operate in conjunction with RF step-up coils of approximately 200 KC frequency, solving the problem of research workers and experimenters in the construction of CORONA-FREE HIGH VOLTAGE RF POWER SUP-PLIES. Ideal for use with our 10KV coil_ To obtain 20, 30, 40 KV—or higher voltages—merely use doubler, tripler or quadrupler circuits. To obtain still higher voltage, additional cascade units can be added

These Corona-Free RF Filament Transformer Units are provided with diagrams and instructions.

A PRECISION-MADE PRODUCT ACTUALLY PRE-TESTED IN CIRCUITS Net Price—No. V055..\$5.50 Also Available With A Tested 1B3 Type Tube Complete With Plate Cap.

Net Price-No. V056. . \$7.65 AVAILABLE FOR IMMEDIATE DELIVERY!

LIMITED QUANTITIES AVAILABLE! HIGH-VOLTAGE COILS! 15KV-25KV-30KV Prices sent on request, Write-phone today for yours!

Include 25% Deposit With Order, Balance C.O.D.

Pioneers in Projection Television SPELLMAN TELEVISION CO., INC. 130 WEST 24th STREET . NEW YORK 11, N. Y.





Graham Model 200-A

POWER OUTPUT: 20 watts
FREQUENCY RESPONSE: Within ± 1 db, 30 to 15,-

000 cycles
MAXIMUM GAIN: 62 db
NOISE: 79 db below full output unweighted
INPUT IMPEDANCES: 150,600 ohms. Also bridging
OUTPUT IMPEDANCES: 125,500, 4 ohms
DISTORTION:

DISTORTION:
At +43 VU. Less than 2%, 50 to 10,000 cycles
Less than 3%, 50 to 15,000 cycles
POWER: 105-125 volts, 50/60 cycles, 140 VA.



Graham Model 180-A

Specifications same as 200-A with these exceptions: POWER OUTPUT: 8 watts NOISE: 74 db below full output unweighted DISTORTION: At +39 VU. Same as Model 200-A. POWER: 105-125 volts, 50/60 cycles, 110 VA.

Other input and output impedances optional on either model. Preamplifiers available for low and high impedance microphones or pickups.

- Precision-engineered to the exacting standards required for wired-music services, broadcast station monitors and top-quality public address systems.
- Input transformers may be operated directly from telephone lines (local telephone practice permitting), eliminating the necessity of using repeat coils.
- Generous interleaving of the output transformers results in reduced leakage reactance, permitting excellent wave form up to highest frequencies at full power.
- Thorough testing at each stage of manufacture, from raw material to finished product, assures rigid adherence to specified characteristics, and lona life.

Write for further details

GRAHAM DIVISION

of the

ACRO TRANSFORMER MFG. CO.
21-20 33rd AYE., L. I. CITY 2, N. Y.


BACKTALK

Commissioners necessarily would be based upon advice received from the Armed Forces. By the time such military Commissioners stated their positions, matters would have progressed to the point where the possibility of negotiation, adjustment and equitable compromises would be minimized or eliminated. This would be true whether such a system was tried under the existing legislation or a new agency was given exclusive authority over the spectrum. The net result would lead in the direction of deadlock.


(continued)

The present system has, in fact, worked for more than a quarter of a century. In the end, the fundamental consideration of utilizing the radio spectrum for the greatest good of the greatest number will govern the allocations to the several services. If the military chooses to use too large a percentage of the spectrum in peacetime, to the actual detriment of public uses of radio, then certainly the President or Congress will make the necessary curtailment in such military uses of radio consistent with the national interest. If, on the other hand, the civilian agency allocating the frequencies to the non-government services fails to take sufficiently into account the requirements of the military for frequencies for the National Defense, then that agency can expect a Congressional overhauling.

We do not have adequate publicity as to the importance of frequencies used by government agencies as compared to the importance publicly acclaimed for non-government uses. Nor is there any mechanism for any single agency other than the Congress to evaluate the relative public importance of Federal government uses and non-government uses. But we do know that the Congress has a direct control over the funds available for all government radio stations, and that the cost of each such station and its maintenance is "justified" in the government agency concerned, to the Bureau of the Budget, to the President, to the House, and to the Senate. Also, in recent months, the Congress has provided large sums for particular programs leading to the installation of large numbers of new government radio stations. Surely, these

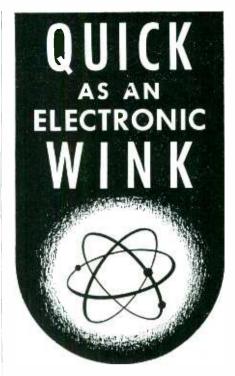

That's how fast a STABILINE Automatic Voltage Regulator corrects line voltage fluctuations. Type IE (Instantaneous Electronic) has no moving parts — is completely electronic in operation. Designed to act instantaneously—with a waveform distortion not exceeding 3 percent — and to keep output voltages stable within ±0.1 of 1 percent of the preset value, regardless of line variations. For any load current change or load power factor change from lagging .5 to leading .9, the STABILINE Type IE will hold the output to within ±0.15 volts of nominal. Various models available in numerous ratings.

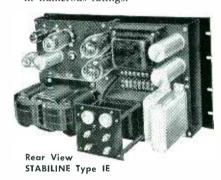

Bulletin 547 gives you information on this and other Superior Electric voltage control equipment. Write for your copy today.



S.S. White RESISTO

ARE USED IN HIGH VOLTAGE "HIPOT" COUPLERS

S.S. White resistors are connected in series to permit a current flow to ground, when the "Hipot" Coupler is used to measure or to synchronize voltage of high voltage lines.

Canadian Line Materials, Ltd.—maker of "Hipot" Couplers and other transmission and lighting equipment—says, have always found S.S.White resistors of the highest quality". This checks with the experience of the many other pro-ducers of electrical and electronic equipment who use S.S.White resistors.

WRITE FOR BULLETIN 4505

It gives details of S.S.White Resistors including construction, characteristics, dimensions, etc. Copy with price list on request.


tion for actuation. Another ver-sion the Model 311, uses an

electromagnetic pick-up coil for counting shaft rotation

tation on high speed counting, timing and control problems call or write Dept. 6R.

complete literature or consul-

without contact.

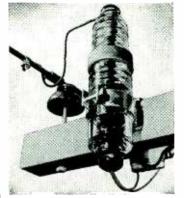

S.S.WHITE RESISTORS

are of particular interest to all who need resistors with low noise level and good stability in all climates.

HIGH VALUE RANGE

STANDARD RANGE 1000 Ohms to 10 Megohms

DEPT. R TO BAST 40th ST., NEW YORK 14, N. Y.



PLEXIBLE SHAFTS . FLEXIBLE SHAFT TOOLS . AIRCRAFT ACCESSORIES SHALL CUTTING AND GRINDING TOOLS . SPECIAL FORMULA BUBBER MOLDED RESISTORS . PLASTIC SPECIALTIES . CONTRACT PLASTICS MOLDING

... and accurately! MODEL 310 ILLUSTRATED PRICE \$18500 new Photo-electronic Counter was designed for in-dustrial applications in which Counter was designed for industrial applications in which mechanical counters do not count accurately or wear rapidly because of counting speed. One of the well-known Potter electronic counter decades is used to scale down the operating speed of a reliable electromechanical register. In the Model 310, the photo-electric reye" is located inside the cabinet and the light enters through a small window at the rear. In the Model 312, the photo-electric "eye" is housed separately for remote counting. Small objects as well as closely spaced parts can be accurately counted since the width of the photo-electric beam is only ¼ inch, and does not require complete interruption for actuation. Another version, the Model 311, uses an **NEW POTTER** PHOTO-ELECTRONIC

★ High speed—counts at rates up to 6000 per minute ★ Long life—mechanical register operates at only 1/10 normal rate

COUNTER

- ★ Direct reading—units digit is read from electronic counter, other digits from mechanical counter
- * Accurate-mechanical register not affected by detector "on-off" time
- * Compact completely self-contained, no wiring required, easy to install
- ★ Flexible—self-contained "eye", separate "eye" or electromagnetic pick-up coil may be used for actuation

POTTER INSTRUMENT COMPANY N C O R P O R A T E

136-56 ROOSEVELT AVENUE . FLUSHING . NEW YORK



must be in the public interest.

The government agencies other than the military which use frequencies would seem to be in a sort of neutral position in that they could receive their frequencies from the same source as the military or from the same source as the public. Treatment of this feature of the problem would not, in itself, eliminate the dual jurisdiction.

We might look briefly at the situation in the United Kingdom. The procedure followed there is remarkably similar to that used in the United States. The British Post Office functions in much the same way as the FCC, but, in addition, acts as an operating agency for some of the public radio services. The British military sit on the Wireless Telegraph Board, which is a rough counterpart of the IRAC in the United States, and the military therefore look to the British Cabinet, which contains representatives of its Army, Navy, and Air Forces as well as the Postmaster General. for the resolution of conflicts. Neither the system in the U.S. nor in the U. K. seems to have been patterned after the other. The net difference in the two systems is rather slight.

The attention of those interested in this important subject is invited to the testimony of former FCC Chairman Fly before a Select Committee of the House of Representatives (78th Congress-H. Res. 21, Part 3, page 2860) where Mr. Fly testified at length and stated in part, in regard to the IRAC: "I think it would be unwise to tamper with that successful and cooperative (IRAC) operation. I have no particular objection to spelling out the same sort of thing by legislation, but as a practical matter, I don't see how it could be improved upon."

Former Commissioner Craven, testifying before the same House Committee, expressed a somewhat different view. He said, in part:

"It seems to me that Congress could settle this matter by specifying in the law more clearly the various jurisdictions and what procedures shall be adopted in reconciling conflicts with respect to the use of the radio frequency spectrum, as between the Government departments, on the one hand, and private enterprise on the other.

I would suggest that first the President be empowered in the act to appoint an Interdepartment Radio Advisory Committee having much the same functions, powers, and department representation as

PROFESSIONAL SERVICES

Consulting — Patents — Design — Development — Measurements

Radio, Audio, Industrial Electronic Appliances

THE BARRY CORPORATION

Specialists in the Control of VIBRATION IMPACT

Engineering Development Manufacturing

179 Sidney Street Cambridge, Mass. Telephones: ELIot 0861-0140

H. RUSSELL BROWNELL

Consultant

Specializing in Measurements & Testing Instruments & Techniques - Electrical - Elec-tronic - Magnetic

188 West 4th St. New York 14, N. Y. Chelsea 2-4208

CANOGA CORPORATION

Electronic Engineers

Radar, Pulse Techniques, MTI Systems, Pulse and Television Receivers, Video Amplifiers, Test Equipment, Microwave Antenna Applications, Electronic Controls, and Microwave Equipment.

SHOP AND LABORATORY FACILITIES 14315 Bessemer St. Van Nuys, Calif.

STate 5-9722

EDGERTON, GERMESHAUSEN & GRIER, Inc.

Consulting Engineers

Research, Development and Manufacture of Electronic and Stroboscopic Equipment Specialists in High-Speed Photography 155 Massachusetts Avenue. Cambridge 39. Mass.

ELECTRO IMPULSE LABORATORY

Consulting Physicists
Radio Interference and Noise Meters; Interference
Suppression Methods for Ignition Systems and
Electrical Devices.
P. O. Box 250
Red Bank, New Jersey Red Bank, New Jersey Red Bank 6-4247

ELECTRO-MECHANICAL RESEARCH INC. Specialized Research and Manufacture

High and Low Frequency Circuit Development Electronic Measuring and Test Equipment Optical and Infra-Red Studies Special Geophysical Equipment Magnetic Susceptibility Meters

Ridgefield, Conn.

ELECTRONIC ENGINEERING CO. of CALIFORNIA

Radio and Electronic Consulting and Designing.

2008 W. Seventh St. DRexel 8323

Los Angeles

ERCO RADIO LABORATORIES, INC.

Radio Communications Equipment Engineering - Design - Development - Production Pioneers in Frequency Shift Telegraph

Garden City . Long Island . New York

FRANKEL & NELSON

Consultants in Mathematical Physics

7716 Firenze Ave.

Los Angeles 46, Calif.

Granite 6970

GENERAL INSTRUMENT & ENGINEERING

CONSULTATION RESEARCH DEVELOPMENT

ELECTRONICS, E. E., PHYSICS

100 Barr Building

Washington 6, D. C.

GLOBE PRODUCTS CORPORATION

Blectronic Division

Specializing in Test Methods and Techniques—
Development and Design of Electronic Test and
Measurement Equipment—Automatic and Manual
—Production and Laboratory types.

P.O. Box #7

870 Maplewood Ave.
Bridgeport, Conn

PAUL GODLEY CO.

Consulting Radio Engineers

GREAT NOTCH, N. J.

Est. 1926

Little Falls 4-1000

HANSON-GORRILL-BRIAN INC.

Product & Mfg. Development ELECTRICAL - ELECTRONIC

HYDRAULIC - MECHANICAL

One Continental Hill Glen Cove, N. Y. Glen Cove 1922

LERU LABORATORIES, INC. Design and Development of Electronic Equipment for industrial and scientific purposes

Special experience in microwaves, spectrum analyzers, photo-electric circuits, test equipment, etc. 360 Bleecker Street

New York 14

WAtkins 9-4194

MEASUREMENT ENGINEERING LIMITED

Consultants on Special Equipment for measur-ments and production tests, communications and audio systems.

61 Duke St. Toronto, Ont.

Arnprior, Ont.
2235 Addington Ave.
Montreal, Que.

Eugene Mittelmann, E.E., Ph.D.

Consulting Engineer & Physicist

High Frequency Heating - Industrial Electronics Applied Physics and Mathematics

549 W. Washington Blvd. State 2-8021

Chicago 6, Ill.

ALBERT PREISMAN

Consulting Engineer

Television, Pulse Techniques, Video Amplifiers, Phasing Networks. Industrial Appliances

Affiliated with

MANAGEMENT-TRAINING ASSOCIATES
3308-14th St., N.W. Washington 10, D.C.

RADIO ENGINEERING COMPANY

Design and Development

R.F. IF, Osc. Coils
Test Equipment
Measurements
F.M.-A.M. Receivers—High Fidelity Audio Systems
1.4 RORATORY FACILITIES

COMPLETE LABORATORY FACILITIES
8 State Street, New York 4, N. Y. Whitehall 4-5266

A. F. SMUCKLER & CO.

Electronic Engineers Electronic Product Manufacturing Contractors to United States Government 238-346 East 23rd St. New York 10, N. Y. GRamercy 5-8151

SPECTRUM ENGINEERS

Electronic & Mechanical Designers

540 North 63rd St., Philadelphia 31, Pennsylvania GRanite 2-2333; 2-3135

TELEREGISTER LABORATORIES

Development - Design Studies and Investigation Automatic Data Handling Storage Digital Computers Coded Pulse Techniques 157 Chambers Street New York City Digby 9-4440

THE

REAL

VALUE

of placing your unusual problem in the hands of a competent consultant is that it eliminates the elements of chance and uncertainty from the problem and provides real facts upon which to base decisions.



The WAVEFLEX waveguide incorporates all of the advantages of rigid waveguides while offering the additional feature of flexibility. Designers of radar, FM, and television transmission equipment have discovered that this combination of properties simplifies many of their design problems.

WAVEFLEX waveguides offer lower attentuation loss, excellent impedance match, and extreme flexibility without loss of efficiency. They are made in ac-

cordance with joint Army-Navy specifications. Let us work with you in developing special waveguides for your special applications.

Literature on request TITEFLEX, INC. 410 Frelinghuysen Ave., Newark 5, N. J.





BACKTALK

that body has today. This would legalize in every respect such a radio frequency coordinating agency for the Government departments.

coordinating agency for the Government departments.


I likewise suggest that in all matters having to do with broad policies of radio frequency allocation, the President be authorized to consider independent recommendations from both the Interdepartment Radio Advisory Committee and the Federal Communications Commission. In the event of differences between these two agencies, the President should be authorized to appoint a special Radio Advisory Board, such as I mentioned this morning, comprised of the Secretary of State, other Cabinet members, selected members of the Interstate and Foreign Commerce Committee of the House, and the Interstate Commerce Committee of the Senate, and perhaps private citizens. The latter I would choose on the basis of their well-known leadership in matters having to do with the social, economic, and scientific aspects of radio, and their broadness of vision, men who would have the confidence of the public. I think it will become increasingly important that these matters be determined on a broader scale than they are now."

The significance in Mr. Craven's statement seems to be that the President apparently would be the final authority, but that the FCC and IRAC both would be continued. Whether such a system would prove too cumbersome in practice would be subject to test; but it would not seem to lend itself to prompt, decisive actions.

> A. L. McIntosh, Chief Frequency Allocation & Treaty Div. Federal Communications Commission Washington, D. C.

MANUFACTURE ofpiezoelectric quartz crystals identical to natural quartz seems possible in the near Early in this century Giorgio Spazia in Italy grew quartz crystals at rates of an inch a year. During the recent war Richard Nacken, a German geologist, obtained somewhat higher rates. This August, Ernest Buehler and A. C. Walker of the Bell Telephone Labs described a method before the International Union of Crystallography at Harvard University whereby rates of growth in excess of an inch a month are obtained under conditions suitable for quantity production; faster rates can be obtained under laboratory conditions. The method consists of placing finely powdered silica and an aqueous alkaline solution in a steel bomb at the top of which is suspended a seed plate of quartz. The bomb is sealed and placed in a furnace. Under pressures exceeding 15,000 pounds per square inch and at temperatures of about 750 F, silica dissolves, rises to the cooler portion of the bomb and deposits atom by atom on the seed plate producing a large clear quartz crystal from which filter and oscillator plates can later be cut.

FOR THE FIELD OF ELECTRONICS

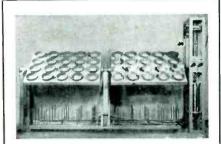

TILTING TABLES for C. R. Tubes

For settling, decanting and drying C. R. Tubes. Manual or automatic timing. Standard or Special Design for any tube size.

ALSO Special equipment of any type-mechanical; electrical; electronic.

BUCK ENGINEERING CO., INC. 37-41 Marcy St. Freehold, N. J.

MICROMETER

FREQUENCY METER

Checking Transmitter from 100 Kc to 175 Mo within 0.01 per cent


LAMPKIN LABORATORIES, INC. Bradenton, Fla., U. S. A.



This **CONTACTS** Section

supplements other advertising in this issue with these additional announcements of products essential to efficient and economical production maintenance. Make a habit of checking this page, each issue.

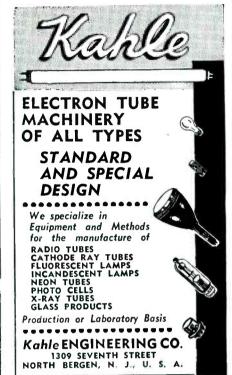Classified Advertising Division **ELECTRONICS**





Quality and accuracy in our fabrica-tion of Tungsten & Molybdenum Rib-bons have characterized our service to the Electronic industry.

A development of



STRIP WIRE FASTER with Speedex Wire Strip

STRIPS 300 OHM TWIN TELEVISION LINE OR ANY SINGLE OR DOUBLE WIRES — MODELS FOR ALL SIZES. The Ideal Wire Stripping Tool for Craftsmen: Radio, Maintenance, Auto (gnition Men; Electricians; Manufacturers,

Men; Electricians; Manufacturers. Fast, easy to use. SPEEDEX strips all types of solid and stranded wires. Models for every purpose. Use on job, or in production wiring—FAST—strips 750-1,000 wires per hour, makes anyone an expert wire stripper. Hardened Steel cutting blade, interchangeable, Regular Model No. 733 strips No. 12 to No. 20 wires. ORDER TODAY or write for literature.



GENERAL CEMENT MFG. CO., ROCKFORD, ILL., U.S.A



WE manufacture a complete line of equipment

SPOT WELDERS, electric from ¼ to 50 KVÅ
TRANSFORMERS, special and standard types
INCANDESCENT LAMP manufacturing equipment
FLUGRESCENT TUBE MAKING EQUIPMENT
LUGRESCENT TUBE MAKING EQUIPMENT
ELECTRONIC EQUIPMENT, racuum pumps, etc.
WET GILASS SLICING and cutting machines for laboratory use
GENERAL GLASS working machines and burners
COLLEGE GLASS WORKING units for students and laboratory

AC ABC WELDERS from 100 to 400 Amps

EISLER ENGINEERING CO.
731 So. 13th St. (near Avon Ave.)
Newark, New Jersey



BEARINGS



Antenna Coils, Grid Clips, Dial Cord Springs and Precision Springs of all types pertaining to RADIO and TELEVISION.

Your inquiries invited

WEBSTER SPRING CORPORATION

ALL

97 South 5th Street Brooklyn 11, New York



LOCKING TYPE Stainless Steel TUBE CLAMPS

Send for Illustrated catalog and engineering date THE GEORGE S. THOMPSON CORPORATION



INVESTIGATE THIS OPPORTUNITY

To join the staff of one of the largest research organizations in the country devoted exclusively to

VACUUM TUBE RESEARCH

Working conditions are ideal in these laboratories which are located in the New York Suburh of Orange, New Jersey. Your associates will include men of many

years experience in vacuum tube research and development.

This rapidly expanding organization is devoted to both commercial and military research. It is a division of one of the oldest vacuum tube manufacturers in America. Security and stability for the years to come are assured. You will have an opportunity to gain experience with the different kinds of vacuum tubes, receiving, power, cathode ray, sub-miniature, micro-wave, radial beam and various special types.

If you can qualify as a

PHYSICIST • MATHEMATICIAN • ELECTRICAL ENGINEER CIRCUIT TECHNICIAN • VACUUM TUBE TECHNICIAN

write at once to

RESEARCH DIVISION

NATIONAL UNION RADIO CORPORATION

350 SCOTLAND RD.

ORANGE, NEW JERSEY

WANTED

Mathematicians, Engineers, **Physicists**

Men to train in oil exploration for operation of seismograph instruments, computing seismic data, and seismic surveying. Beginning salary \$230.00 to \$300.00 per month depending background. Excellent opportunity for advance on determined on ingenuity and ability. Nature of work requires several changes of address each year; work indoors and out; general location in ell producing locations.

To apply write giving scholastic and employment background, age, nationality, marital status, and include recent snapshot to

NATIONAL GEOPHYSICAL CO., INC. 8800 Lemmon Ave. Dallas 9, Texas

Positions open for

PHYSICISTS SR. ELECTRONIC **ENGINEERS**

Familiar with Ultra High frequency and micro wave technique.
Experience with Electronic Digital and/or Analog Computer Research and Development Program. Salaries commensurate with experience and ability. Excellent opportunities for qualified personnel. Contact:

C. G. Jones, Personnel Department, GOODYEAR AIRCRAFT CORPORATION

Akron 15, Ohio

RESEARCH & DEVELOPMENT ENGINEERS

Wanted for advanced research and development. Should have extensive experience on analysis of electronic systems in the fields of microwaves, missiles, radar, servomechanisms, communications, navigational devices. Outstanding ability in E. E. or Physics reauired.

quirea.
Please furnish complete resume, salary requirements and availability to: Personnel

W. L. MAXSON CORPORATION 460 WEST 34TH STREET NEW YORK, NEW YORK

ELECTRONIC ENGINEER

An opportunity for a man with considerable experience to head a small developing and engineering group in a growing company in Chicago. Pulse experience a necessity and a background of work with nuclear radiation instrument and nuclear detectors very desirable. Please give full details.

P-6593, Electronics 520 North Michigan Ave., Chicago 11, Ill.

WANTED

ELECTRICAL ENGINEER

A nationally known Chicago company is in need of a high grade, experienced electrical engineer. He must be a college graduate with a B.S. in E.E. degree, with high scholastic record. Should have from two to five years experience in electronics, preferably with a minimum of two years in the design of audio amplifiers. In reply give all particulars and state expected salary.

P-6750, Electronics

520 North Michigan Ave., Chicago 11, Ill.

ELECTRICAL ENGINEER

Good opening for electrical engineer with suit-Good opening for electrical engineer with suitable training and three to five years of experience in industrial electronics or allied work, including design and development of relay and tube circuits. Project method used in development work on timers, sensitive photo-electric relays, amplifiers, counters, measuring and recording devices.

Employment of long-range, permanent nature for properly qualified individual. Superior industrial relations and employee benefit programs. Replies will be treated in confidence and should give full details concerning personal qualifications, education, and experience.

P-6794. Electronics

330 West 42nd Street, New York 18, N. Y.

TELEVISION ENGINEERS

The Crosley division, Avco Manufactur-

The Crosley division, Avco Manufacturing Corporation is expanding its television receiver activities on a long term basis, creating a few positions for qualified supervisory and senior engineers.

Requirements: College degrees. Three or more years' experience in television and radar design and development of which at least two years have been spent in advanced or product development of television receivers. Specialists in circuit elements will be considered.

Ideal working conditions in well equipped modern laboratories with unlimited opportunities for advancement. Forty hour week, insurance, hospitalization and pension plans. Responsibilities and excellent salaries based on experience and ability.

Replies (which will be kept confidential)

abinity.

Replies (which will be kept confidential) stating age, experience, education and salary requirements should be addressed to:

Director of Research and Engineering CROSLEY DIVISION

AVCO MANUFACTURING CORPORATION

1329 Arlington St. Cincinnati 25, Ohio

SCIENTISTS AND ENGINEERS

Wanted for research and advanced development in the fields of microwaves, radar, gyroscopes, servo-mechanisms, instrumentation, computers, and general electronics. Scientific or engineering degrees required. Salary commensurate with experience and ability. Direct inquiry to Manager, Engineering Personnel.

BELL AIRCRAFT CORPORATION
P. O. Box 1, Buffalo 5, New York

REPLIES (Box No.): Address to office nearest you NEW YORK: 330 W. 42nd St. (18) CHICAGO: 520 N. Michigan Ave. (11) SAN FRANCISCO: 68 Post St. (4)

POSITION VACANT

TELEVISION-ENGINEERS with various de-TELEVISION—ENGINEERS WITH VARIOUS de-grees of training and experience required by a leading Chicago manufacturer of tuners and other television components. Reply fully in con-fidence giving all details, including age and salaries. Our staff is aware of these openings. P-5592 Electronics P-6528, Electronics.

SELLING OPPORTUNITY OFFERED

MANUFACTURER HIGH class varnished fab-ric tubings wants representatives in the elec-tronic, radio line. RW-6674, Electronics.

EMPLOYMENT SERVICES

SALARIED POSITIONS \$3,500-\$35,000. If you SALARIED POSITIONS \$3,500-\$35,000. If you are considering a new connection communicate with the undersigned. We offer the original personal employment service (38 years recognized standing and reputation). The procedure, of highest ethical standards, is individualized to your personal requirements and develops overtures without initiative on your part. Your identity covered and present position protected. Send only name and address for details. R. W. Bixby Inc., 266 Dun Bidg., Buffalo 2, N. Y.

EXECUTIVES \$3,000-\$25,000. This reliable service, established 1927, is geared to needs of high grade men who seek a change of connection under conditions assuring, if employed, full protection to present position. Send name and address only for details. Personal consultation invited. Jira Thayer Jennings, Dept. E, 241 Orange St., New Haven, Conn.

POSITIONS WANTED

ASSISTANT PLANT Manager, 7 yrs. experience on incentives, simplification, layout, job evaluation. Degrees in management. PW-6481, Electronics.

RESEARCH ELECTRONICS: M.S. Physics 1947; electronics design, testing, 3 years; asst. Prof. Physics 1 year; Sigma Xi; Knowledge of nuclear processes and audio sound field; with concentrated study could qualify to do top research in other fields such as optics. PW-6621, Electronics.

PROFESSOR OF electronics and communica-tion desires position in research or teaching, industrial experience, many papers published, advanced degree. PW-6655, Electronics.

SPECIAL SERVICE

Service Organization

New Orleans area, available to manufacturers of any Electronic apparatus on Service Agency setup. Industrial, medical and commercial radio. Write "Delta Electronics", Box 476, Naw Orleans 1 La New Orleans 1, La

ENGINEERS

Attractive positions immediately available for:

PROJECT ENGINEERS

Experienced in design of automobile radio receivers.

SENIOR DRAFTSMEN

Experienced in the handling of mechanical layout work and design of automobile radio receivers.

RADIO ENGINEERS

To handle liaison work with radio and television production department.

In reply give only brief outline of work experience. Standard application blanks will be forwarded if detailed information or personal interview is desired.

Personnel Manager,

BENDIX RADIO DIVISION

Towson 4, Maryland

WESTINGHOUSE RESEARCH

Openings in Pittsburgh

ENGINEER having three or more years experience in radar or television for work on television systems and television receiver research.

ENGINEER or PHYSICIST with experience in underwater acoustics.

PH.D. PHYSICIST with background for working on solid state problems.

ENGINEER or PHYSICIST for work on magnetic circuits and materials.

ELECTRONIC ENGINEER to work on advanced circuit design problems.

ENGINEER OR PHYSICIST with three centimeter wave guide experience.

For application address
Manager, Technical Employment

WESTINGHOUSE ELECTRIC CORP. 306-4th Ave., Pittsburgh, Pennsylvania

ENGINEERS

PROGRESSIVE ELECTRONIC RESEARCH AND DEVELOPMENT COMPANY

has several openings for Senior Electronic Engineers of superior ability, with experience in design and development. Excellent opportunities for top flight men. Send complete resumes and salary requirements to:

Personnel Department

MELPAR, INC.

452 SWANN AVENUE, ALEXANDRIA, VIRGINIA

ELECTRONIC ENGINEERS PHYSICISTS SERVO & COMPUTER ENGINEERS PROJECT ENGINEERS SENIOR ELECTRONIC ENGINEERS

This is your opportunity to go places in Electronic Research and Development

MEN ARE ESPECIALLY NEEDED TO DO ORIGINAL WORK IN THE FOLLOWING FIELDS:

- Pulse circuits including ranging, scope, video, trigger and square wave generator circuits.
- Radar type transmitters, including high voltage power supplies, receivers and modulators.
- Micro-wave antennae, radomes, wave guides and other radio frequency components of radar systems.
- 4. Servo-mechanism and controls.
- 5. Electronic Instrumentation.

For Personal Interview in Chicago on November 4, 5 and 6, Contact The Glenn L. Martin representative attending the National Electronics Conference

or send resume to

PERSONNEL DEPARTMENT

THE GLENN L. MARTIN COMPANY

Baltimore 3, Maryland

NO HOUSING PROBLEM IN BALTIMORE, MARYLAND

ELECTRONIC ENGINEERS WANTED

TELEVISION

experienced in circuit designs, either video amplifier design or scanning circuit design.

TRANSMITTER

SENIORS . .

Technical graduates with a minimum of 6 years engineering and supervisory experience, capable of assuming responsibilities for directing engineers and designers on specific projects connected with pulse type transmitters and timer equipment.

INTERMEDIATE ENGINEERS . . .

Technical graduates or equivalent with at least a minimum 4 years practical experience in design of transmitter and associated equipment.

JUNIOR ENGINEERS . . .

Technical degree, minimum 1 year experience in development for production of electronic equipment.

RESEARCH CHEMIST . . .

Technical degree and experience for development work on selenium rectifier.

ENGINEERS . . .

Also needed having experience with telephone systems in general, particularly in voice frequency equipment engineering, toll transmission systems and carrier telephone equipment.

SALARY COMMENSURATE WITH ABILITY APPLY IN PERSON OR WRITE PERSONNEL MANAGER

FEDERAL TELEPHONE & RADIO CORP.

100 Kingsland Road, Clifton, N. J.

Bachelors, Masters, PhD's in PHYSICS or E.E.; Experienced Electronic Engineers; Recent Graduates; and Technicians:

OPPORTUNITY ON LONG ISLAND

offers attractive working conditions, salary commensurate with ability, access to graduate schools, first-rate research and plant facilities, other advantages.

Projects underway in fields of microwave receivers, transmitters, antennas; radar, air traffic control; servos, motor-control systems; general electronics.

In reply, write Personnel Manager

Hirborne Unstruments INCORPORATED 160 OLD COUNTRY ROAD . MINEOLA, N.Y.

EXPERT DIAGNOSIS and TREATMENT

for Ailing Communication and Television Receivers and Transmitters by TRAINED SKILLED TECHNICIANS
When trouble comes and your receiver acts up, don't blame sun spots

NATIONAL

HALLICRAFTERS HAMMARLUND PIERSON

COLLINS

Complete realignment—Bandspread Calibration—Sensitivity Measurements—Image Rejection Ratios-S Meter Calibration. Rebuilding to rigid factory standards.

Authorized Collins, Hallicrafter, National and RME Service Center

WINTERS RADIO LABORATORY 11 WARREN STREET

Cortland 7-1361

New York 7, N. Y.

PROJECT ENGINEERS

Real opportunities exist for Graduuate Engineers with design and development experience in any of the following: Airplane Stability and control, Servomechanisms, radar, microwave techniques, microwave antenna design, communications equipment, electron optics, pulse transformers, fractional h.p. motors.

Send complete resume to employment office.

SPERRY GYROSCOPE CO.

Division of the Sperry Corp. GREAT NECK, LONG ISLAND

ELECTRONIC ENGINEERS PHYSICISTS

"A leading Electronics Company in Los Angeles, California offers permanent employment to persons experienced in advanced research and development. State qualifications fully."

P 6606 Electronics 68 Post St., San Francisco 4, Calif.

CHIEF ELECTRICAL ENGR PROJECT ENGRS SENIOR ENGRS

Must have extensive experience in home radio receivers and/or television, lesign & development.

Address Replies To

Vice President in Charge Engineering

AIR KING PRODUCTS CO., INC. 170-53rd St. Brooklyn, N. Y.

X-RAY TUBE ENGINEER

EXPERIENCED MAN familiar with X-ray production and design methods. Excellent opportunity. Salary is open. Call or write. Amperex Electronic Corporation, 25 Washington St., Brooklyn 1, N. Y.

RADIO CABINETS

ond wood cabinets of all types built to your specifications. "Engineered Wood Production" THOMAS MANUFACTURING CO. NEENAH, WISCONSI WISCONSIN

SAVE RESEARCH TIME BY CONSULTING The Indispensable Bibliographical Reference

ELECTRONIC ENGINEERING MASTER INDEX

Descriptive Literature on Request ELECTRONICS RESEARCH PUBL. CO., 2 W. 46th St., N. Y. 19

UIPMENT SURPLUS



PORTABLE (CHRONOMETRIC) **TACHOMETER**

TACHOMETER

Jaeger Watch Co. Model #43A-6

Can be used for speeds up to 20.000 R.P.M.
Can be used for ineal speed measurements to 10.000 F.P.M.
Ideally suited for testing the speeds of motors, particularly of fractional horse power, generators turbines, centrifugals, fans, etc.
Very small Torque—requires practically no power to drive.
Unequalled Readability 2" Open face dial—each division on large dial equals 10 R.P.M.; each division on small dial equals 1.000 R.P.M.
Greatest Accuracy—meets Navy specifications—guaranteed to be within ½ of 1%.
Results of test reading remain on dial until next test taken.
Push button for automatic resetting.
Complete with the following accessories 1—Large hoilder rubber tip 1—Large pointed rubber tip 1—Greicrumference Wheel tip 1—Operating Instructions 1—Temperature Correction chart
The combination of the above features will give accurately, within a few seconds, by direct reading, the R.P.M. of shafts or the lineal speeds of surfaces without any accessories or timing of any kind. Each unit comes complete in a red velvet lined carrying case 5*x3½/z*x1½. Net List Price \$70.00—Surplus —New—Guaranteed.

A.C. VOLTMETERS

0-15, WH NA-35, 3½" rd fl bake case, (100 MA) \$3.95
0-75. Weston 517, 2" rd fl metal case, ring mtd. \$2.95
0-150, GE AO-22, 3½" rd fl hake case \$5.50 0-150, Triplett 331-JP, 3½" rd fl bake case \$4.50
0-150, W Resist to increase range to 300 V, Triplett 331-JP, 31/2" rd fl bake case\$5.50
0-300, Burlington 32A, 3½" rd fl bake case\$8.00 0-500, GE AO-22, 3½" rd fl bake case\$12.00

A. C. AMMETERS

0-30, Triplett 331-JP, 3½" rd fl bake case\$4.00 0-50, GE AO-22, 3½" rd ft bake case\$4.50
0-60 & 0-120, Burlington 32XC, with current
transformer\$7.50
0-75, Triplett 331-JPC, 31/2" rd fl bake case\$3.50

R. F. AMMETERS

0-250 MA, WH NT-33, 2½" rd fl bake case, black sc cal 0-5
0-1, GE DW-44, 2½" rd fl bake case, black scale\$2.95
0-1.5 Weston 507, 21/2" rd fl metal case, black
scale
0-2, Simpson 35, 3\\\ " rd fl bake case\$4.95
0-3, Simpson 135, 2½" rd fl bake case\$3.50
0.4, GE DW-44, 2½" rd fl bake case, black scale
0-6, GE DW-44, 2½" rd fl bake case, black
scale
0-30, Triplett, 0347-A, 3" sq fl hake case, W. ext. leads & couple

D. C. MICROAMMETERS

0-200 microampere myt., GE 100-41, 31/2" rd fl
hake case, Knife edge pointer, sc mkd "Set Carrier" supp with paper V.O.M.A. sc\$6.00
0-200, Superior, 4"x41/2" flush case, Knife edge
pointer se cal 0-200 Meg & 20,000 ohms In-
salation Tester, 500 ohms resistance\$7.50
0-400, Triumph, 4" Rect fl bake case, 500
ohms resist, se cal 3/15/60 V MA\$5.50
0-500, Greun 221-T, 21/2" rd fl bake case\$3.95
0-500. GE DO-41, 3\%" rd ft bake case, sc cal
0-20 KV, supp with paper V.O.M.A sc\$4.95

D. C. MILLIAMMETERS

0-1. Sun 3AP259, 31/2" rd fl bake case\$3.0	10
1-0-1, GE DO-53, 3" sq fl bake case\$4.5	
0-15, Simpson 26, 31/2" rd fi bake case \$4.5	
0-20, GE DO-53, 3" sq fl bake case\$3.2	
0-25, Weston 301, 3 1/2" rd fl bake case\$4.9	15
0-80, GE DO-41, 31/2" rd fl bake case\$3.2	
0-100, Weston 506, 21/2" rd fl bake case\$3.5	
0-150, Gruen 508, 21/2" rd fl bake rase\$3.0)0
0-200, Marion, 31/2" rd fl bake case\$4.0)0
0-500, WH NX-33, 2½" rd fl bake case\$3.9)5

D. C. AMMETERS

0-5. Gruen, 2 1/2" rd fi bake case	\$3.50
0-15, Triplett 0321-T, 31/2" rd ft bak	e case\$4.00
30-0-30, GE DW-51, 21/2" rd fl meta	l case\$3.50
0-200, GE DO-41, 31/2" rd fl bake of	ease, with
ext 50 MV (Aircraft style) shunt.	\$9.50

D. C. VOLTMETERS

	WH NX-33, 21/2" rd fl bake case, 200 r/v.\$3	
0-10,	Sun 2AP458, 2½" rd # bake case, 100 \$2	50
0-15,	Gruen GW 505, 2½" rd fl bake case\$3	.50
0-30.	GE DW-41, 2½" rd it bake case, approx) r/v	95
0-50,	WH NX-35, 31/2" rd fl bake case, 200 r/v \$3	.95



PORTABLE TACHOMETER

PORTABLE TACHOMETER

Multiple Range Continuous Indicating
This unit is of the centritugal mechanical tyne and
is designed to show INSTANTANEOUSLY and
CONTINUOUSLY the speed or change in speed of
any revolving shaft or surface. No stop watch or
other mechanism renuired.

• Three ranges in R.P.M. and three in F.P.M.
Low Range 300-1.200 (Each division equals
10 R.P.M.)

Medium Range 1,000-4,000 (Each division equals
10 R.P.M.)

Large open dial 4" diameter.

Ruggedly constructed for heavy duty service.

Ball bearing and oilless bearings—require no
librication whatsee-fits neally into hand.

Geap shift for selecting low, med., high ranges,
Made by Jones Motrola, Stanford, Connecticut,
Comes complete in hile velvet lined carrying case;
71/6"L x 4"H x 5"W. List Price \$95,00—Surplus—
New—Guaranteed. Your cost \$24.50 F.O.B. N.Y.

Gasoline Heater Motorola Model GN-3-24



An internal combustion type heater which will give 15,000 B.T.U. of heat per hour. Ideally suited for use with equipment, farms, boats, bungalows, cabins, trailers, work sheds, darkrooms, mobile entipment, transmitter stations etc. and any place where a quick heat is required in volume. Very economical in operation—tank holds one gallon of gasoline which is sufficient for 6 hours operation. Uses any grade gasoline.

operation. Uses any grade gasoline.

This unit is designed primarily for aircraft installation, 24-28 volts d.c., but it can be readily adapted for a 115 or 230 volt 60 cycle power supply by use of a transformer and rectifier. Simple circuit diagram for adaption to 115 or 230 volt 60 cycle use supplied with each unit. Can be used on 32 volt farm or hoat systems as is without the installation of additional transformers etc. Power consumption approximately 75 to 100 watts.

Takes very little space—can be readily stored when not in use—measures approximately 12 long x 9½" high x 9½" wide—weighs only 30 lbs complete with all accessories.

These units are complete with exhaust pipe, 3" air duct elbow, control switch and cord, as illustrated, and are supplied with Technical Manual and Parts Catalog.

SIMPLE TO INSTALL—SAFE TO USE— NO ODORS BRAND NEW-IN ORIGINAL CARTONS-

Made by Galvin (Motorola) Mfg. Company.

\$22.50 NET PRICE.....

SPECIAL METERS

FREQUENCY METER—Range 350 to 450 cycles, 115 volt A.C. Iron core dynamometre type movement, 5 cycles per scale division. Black scale luminous markings. Weston Model 637, 33, Aircraft style. . . \$4.95

ton Model 637, 372 Alleratt skyle.

FREQUENCY METER—J.B.T. 30-F dual range covers Frequency ranges from 48-52 cycles and 58-62 cycles; Dual element, Vibrating Reed type 115 volt, 3½" rd flush metal case \$5.95

DECIBEL METER—Weston 506 minus 10 to plus 6, 6 MW in 600 ohms, 2½" rd ft base

Case

**Nour METER—Totals to 99,999.9 hours and repeats. Wif Nii-35, 3½" rd fi bake case. Operates on 230 volt 60 cycle. \$8.50

D.C. MILLIAMMETER—Weston 271 fan type. 1-0-1 MA (60-0-60 MV) movement Sc cal 600-0-600 R.P.M. \$12.50

SWITCHBOARD METERS

FREQUENCY METER—58 to 62 cycles, Westinghouse IIV 54" square proj. intd case; accuracy within 1%, Electric Dynamometor type movement: Comp. with ext. reactor...\$39.50

FREQUENCY METER—50 to 70 cycles, Westinghouse IIY 5½" square proj. mtd case; Accuracy within 1%. Electric Dynamometer type movement; Comp. with ext. reactor...\$45.00

All items are Surplus—New—Guaranteed. C.O.D.'s not sent unless accompanied by 25% Deposit.
Orders accepted from rated concerns, public institutions, etc., on open account.
The above is only a partial listing of the many items we have in stock. Send free circular.
MANUFACTURERS, EXPORTERS, DEALERS—we invite your inquiries.

336 Canal Street

Worth 4-8217

New York 13, N. Y.

We carry a complete line of surplus new meters suitable for every requirement, such as portable, panel, switchboard, laboratory standards, etc.

OVER 50,000 METERS IN STOCK

We also have in stock various surplus components, tubes, code keying and recording units, cole training sets, tachometers, analyzers; tube testers, convertes, precision resistors, current transformers, transmitters, receivers, condensers, and other electronic units, parts and accessories.

SEARCHLIGHT SECTION



MICROWAVE TS-12AP TEST SETS



ANTENNA MATCHING
NETWORK 1001A 1
KW RF NEW 1.5 to 7
mc's convertible to Hifreqs. PiNetwork adjustable IN & Output
CASED 15 x 15 x 23"
RACK MTG Ribboncoil
& 250mmf/7000V Vconder PEmbr Lighter condsr RFmtr, Instrs
Techmanual will match
most ANTS. NEW requires recementing coil
turn SPECIAL \$9.95



Same Unit NEW.\$12.95 SAME UNIT, NEW, NEW, . .8.95 SAME UN broken coil



CONSTANT V'REGULATOR NEW RAYTHEON in 95-130V/60 cy; Output 115V/60 cy Csd...\$10.95 RAYTHEON in 198 to 242 Vinpt/50-60 cys; Output 200V/500 Watts/0.5% Rulth Rack mtg.\$36.00 SOLA CONSTANT V'REGUTR USN Cased in 95 to 190V/50-60 cys; Output 115 or 220V 2KW/17.4 Amps/Constant Duty 1% Regulation LN*.\$130.00 Same Unit NEW USN Cost \$369. Only...\$162.00

BATTERIES STORAGE AND DRY **TYPES**



(A)	BR18/BB52/5oz/36V minSBaty ea. \$1.49
,,	8 for
(B)	BURGESS 3V F2BP/dated 6/47 5 for\$1.00
(C)	GOULD 6V/15AH S'Baty USN NEW\$3.98
(D)	BB54/2V 27 amp WILLARD S'Baty\$1.98
(Ē)	WILLARD 4V/40AH/TBY S'Baty\$5.95
)=(PROCEED AND MILLARD C'Raty \$1.80



operates 110VACDC SPECIAL



PRECISION RESISTORS SPECIAL. ISTS IN PRECISION Write Qty \$

	"NO	MFGRS (CHOICE, W	e ship type	s in stock
1	116	179	680	2600	13500
	425	182	684	2635	14000
	607	199 200	689 697	2700 2850	14400 14440
	007	209.4	700	2860	14460
	7	916	733	2900	14500
1		220	750	3000	15000
3	3.75	220 220 . 4 225 230	800 806	3100	15000 15500 16500
3	.83	220	854	3290 3384 3500	17000
4	1.00	235	900	3500	17000 17500
-4		240	910	3509 3509 3700 3730 3760	18000 18380 18500
5		245.4 250	917	3700	18380
6	3.025	260 260	946 978	3730	18500
7	.25	271	1000	4000	19000 19500
7		271 275 280	1030 1056	4200 4280	20000
7	. 5	280	1056	4280	20520
7		286 289	1060 1100	4300 4314	21000
8	3.9	299	1110	4440	21500 22000
1	0	300	1110 1150	4444	22500
- 1		310	1155	4500	22990
1	0.48	311.5	1162	4720	22990 23000 23150 23325
i	1.25 2 3.52 4.2 4.5	320 325	1175 1200	4750 4850	23150
î	3 52	340	1200 1225 1250 1260 1322 1350 1355	4885	23325
1	3.52 4.2 4.5	350	1250	4885 4900	24000
1	4.5	366.6	1260	5000	24600
1	5	370	1322	5100	25000
i	6.37	375 380	1350	5210	25200 25400
ī	7	390	1400	5210 5235 5200 5500	26600
2	0	400	1495	5500	27500
2	1	410	1500	5600	29000
2	0 1 5 6	414.3	1510 1518	5600 5730 5910	29500
2	ñ	425	1600	6000	29900 39000 31000 33006 35000
- 3	7	426 9	1640	6140	31000
4	8	427 440	1646 1650 1670	6200 6300	33006
	0	440	1650	6300	35000
- 5	1.78 5	452	1680	6495 6500	37000 38140
6	3	470	1680 1710 1740 1770	6840	38500
-6	3	475	1740	6990	39500
- 6	8	478	1770	7000	40000
7	1.4	480 487	1800 1818	7500 7700	43000 47000
- 7	5	500	1830	7930	48000
- 8	0	520	1865	8000	48660
- 8	1.4	525	1900	8250	49000
ŏ	9.8	540 550	1910 1960	8500 8700	50000
9	5	575	2000	8992	52000 54000
1	00	580	2045	9000	56000
	01	600	2080	9445	60000
1	05 7	$\begin{array}{c} 607 \\ 612 \end{array}$	2095 2145	9500	61430
î	07.1	625		9710 10000	62000 64000
î	13.1	625 633	2195	10430	65000
1	20	640	2200	10500	68000
1	05 05.7 07 13.1 20 21.2 25 47.5	641	2195 2200 2250 2300	10600	70000
1	25 47.5	649 650	2300 2400	11000 11400	72000 75000
1	50	650 657	2450	11400 11500	80000
		665	2463	11600	84000
1	65	669	2485 2490	12000	90000
1	70	670 675 E SIZES	$\frac{2490}{2500}$	12000 12600 13220 @TEN	91000
1	75 BOVI	E SIZES	EACH 30¢	@TEN	95000 FOR \$2.50
	00000	155000		353500	575000
1	10000	166750	240000 245000	353500	600000

| 3000 | 1550 | 25000 | 166750 | 25000 | 166750 | 25000 | 169380 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 25000 | 235500 | 33000 | 235500 | 235500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 23500 | 353500 75000 380000 600000 100000 621000 102000 621000 422000 654000 478000 761300 520000 80000 521000 900000 521000 950000 TEN FOR \$3.50 1.23 Meg 10 Meg 4.23 Meg 10 Meg 4.5 11.5 5 12.83 5 12.85 9.05 20 ...TEN FOR \$6.50 1.8 3.673 4 ABOVE SIZES EACH 75¢

ABOVE SIZES EACH 75: TEN FOR \$6.50


Vacuum Precision Hivolt Resistors (C)
.12, .25, .6, .75, .83, .99 megohms
.1, 1.5, 2, 3, 3.75 megohms 0.5% accuracy

SPECIAL \$1.00@ TEN FOR \$7.50

SEALED.10or12Men/10KV/9W \$1.35@10for \$10.00 MVZ8/20Watt/30Megolims/25KV\$1.98@6for \$10.00

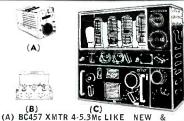mrbioJ/imey/.J*/oacty/Jan,n-29
198@6for \$10.00
Type 2/20megJANR29/20KV/0.5%accy\$29.95
200B/675Watt/0-135V GR
200C/860Watt/0·135V GR 16.50
100R/0-230or270/2KW/115or220Vin 39.95
AN/APR4 RECEIVER & COILS Write for details
OIL5MFD/600WV/220VAC&brckts 2 for98
FIECTDI VTIC SDECIAL





& TUBES S7
(A) BC457 XMTR 4-5.3Mc Good used & tubes 5
(A) BC457 XMTR 4-5.3 Mc As IS less tubes . 3
(A) BC458 XMTR 5.3-7Mc LIKE NEW & Tubes 7
(A) BC458 XMTR 5.3-7Mc Good used & tubes 5
(A) BC458 XMTR 5.3-7Mc As IS less tubes . 3
(B) BC456 Modulator & Tubes & Dyn used . 1
(V) BC375 XMTR Good used w/tubes & Dyn used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1
(V) BC375 XMTR Good used w/tubes & Den used . 1 TUBES tubes 5.95 49 1.69 BC375 or BC191 as is, less tubes & TU...

PHOTOFLASH & AIRCORPS 1503 SET CONTAINS PWR 2 KRYPTON

1000

SUPPLY LAMPS

Reflectors, HV rectifier, Condensers 2x25 mfd, HV transformer Relay, light output 12,000,000 lumens, 15to30000flashes for Color&BWfilm KIT includes INSTRUCTIONS & PARTS to CONVERT 12 to 24VDC unit 115VAC OPERATION "TAB" SPECIAL \$59.95 PHOTOFLASH 1503 & RECTIFIED POWER SUPPLY for 115VAC operation READY TO WORK...99.50 PHOTOFLASH KRYTON LAMPS&Reflector 2 for \$21 PHOTOFLASH CONDENSERS 8mfdGE/660VAC/3000VDCintermittent 4 for 11.95 16mfd/330VAC/2000VDCintermittent ...7.95 15mfd/330VAC/2000VDCintermittent ...7.95 15mfd/330VAC/2000VDCintermittent ...7.95 16mm/PAN/50Film GSAP Camera...54 for 8.98 16mm/PAN/50Film GUN Camera GSAP...10 for 1.98 SUPPLY LAMPS



METER GE/200MICROAMPdc/4"SQUARE 5 scales A K.E.Pointer ACDCV&Ohms in Red & Black, NEW 6.95 K.E. Pointer NEW
METER 50MICROAMP.dc/4"SQUARE/VOM 5
scales, 9 ranges ACDCV & DC ma & DB
in Red & Black, K.E. pointer, used in GE Onimeter
METER DB WESTON 506 minus 10 plus 6/
6MW 600 0hm Bakelite Cased JAN MR25W123 spec 9.49 123 spec
METER TUNING 5ma WESTON 21/2"B'CSD...
METER One Ma DeJUR 21/2"B'CSD...
METER Two Hidamping 4"/10&40 Ma/.5% METER VOITSUL 30 VOITS AN 2½° D LS0
WSTGHSE ... 2.49
METER VDC/200Vor500V/Mohmsp/v3½° B°C/W.E. 4.95
METER VDC 200V/Mohms p/v/2½° B°Csd GE 5.95
METER VDC 10000V/Mohms p/v/3½° B°Csd .12.95
METER AC 150V/25to125/cy/2½° WSTGHSE 8.6F 3.95 1.20 TEST PRODS 4' insltd plugs&tips Red&Blk49¢

Blowers-Cool That Tube!

B"MONEY BACK GUARANTEE MIN. ORDER F.O.B. N.Y. C. DO SHIPPING CHARGES AND V₄ DEPOSIT. PHONE WO. 2-7230

40 CFM/28VACDC 2.98 100 CFM/12VADC 5.95 100 CFM/28VACDC 4.95 XFORMER 12 or 28V to 115VAC for above 1.69 250 CFM/28VACDC 8.95 250 CFM above plus 28/115VAC XFORMER .10.95 CHAT'S BUX BUY 11E SIX CHURCH ST. NEW YORK 6, N.Y., U.S.A. - COR NEB CHURCH & LIBERTY STS. DEPT.

"TAB" MONEY BACK GUARANTEE \$3 MIN. ORDER F.O.B. N.Y.C. ADD SHIPPING CHARGES AND 25% DEPOSIT. PHONE WO.2-7230

SEARCHLIGHT SECTION



COMPLETE TELEVISION POWER SUP-PLY Kit Hi Voltage 5000VDC/5ma LO Voltage 300VDC/175ma output, fil 6.4V/ 10.3A, fil 5.4V 8A, 5.1V/3A&5V/3:5A inpt 105, 115, 125V/50 to 425cys & soc-kets & Rect tube 5U4G&3B24& filter condensers & choke & diagram oil filled USN Transf W.E.D303184 "TAB" SPECIAL \$27.95 TRANSFORMER only, \$22.95

SAME TELEVISION POWER SUPPLY KIT & added

parts for providing Hi VOLTAGE DOUBLER ci	rcuit
I With IBOOD Volts de outquit "TAR" CRECIAL	@24 OF
TRANSFORMERS 115 V/60 Cv. Inc	ut
/500V or 5000V'D011RFFR/35ma	\$15 OF
10800VCT or 21000V'DOUBLER/95ma	10 05
1100VCT/212ma \$5.95; 10V/8A/12KV	6.95
1100VCT/212ma \$5.95; 10V/8A/12KV 5V/115Amp \$10.95; 2.5V/10A/10KV 220 to 440V-or-110 to 220V 250Watt	3 95
220 to 440V-or-110 to 220V 250Watt	4 95
880VCT/125ma, 6.3V/2A, 6.3V 3A&5V/3A	7.55
880VCT/125ma, 6.3V/2A, 6.3V 3A&5V/3A delivers 250ma on hiv	4.45
DV/6UAMO KENYON HV instal	6.95
840VCT/110ma, 540VCT 21ma, 5V/3A	0.22
840VCT/110ma, 540VCT 21ma. 5V/3A, 5V/3A&6.3V/1A, 6.3V/.6A USN Csd 2X	
safety factor 2.5V 40Amp GE instin 25KV 6800V or VCT/IA1/TKVinsttn, 208 to 251V 3400V or VCT/IA1/TKVinsttn, 107 to 126V.	4 95
2.5V 40Amp GE insltn 25KV	7 95
6800V or VCT/1A/17KVinsltn 208 to 251V	81.00
3400V or VCT/1A17KVinsltn, 107 to 126V	81.00
	19.95
115 or 230V SAmn/1 SKW AUTOTRANCE	16.95
DV/6.DAMO/36KV instrn & carket IIX	6 05
7.5VCT 6.5A, 6.3VCT/3A	3.75
7.5VCT 6.5A, 6.3VCT/3A 700VCT/150ma, 10V/3.25A, 2.5V/10A &	2.12
.3VCT/2A, 5V/3A, H V insttd. Cased 1100VCT/150ma, 6.3V/3A, 5V/3A HV ins	5.95
1100VCT/150ma, 6.3V/3A, 5V/3A HV ins	4.50
10V 8A/12KV or 2x5V/8A/12KV inc	6.95
1000VC1/150ma,300Vbias, 6.3V/5A, 5V/3A	0.55
&2x6.3V/6.5A, 6.3V/1.25A CSD50-800cvs&	
Dri tans 0-80 115VAC Hmt coaled	4.50
7.5V/12A/HV \$4.95: 4x6.3V 4A&3x5V/4A	4.50
	4.95
5VCT/20A/220Vin or 2.5VCT/20A/110Vin.	5.95
5VCT/20A/220Vin or 2.5VCT/20A/110Vin. 10VCT/10A, 12VCT/.7A, 3x6V/1A, 2x6V/2A	7.95
3x5V/3A, 2.5V 1.75A, 6.4V/12A, 6.4V/10A	4.95
1200VCT/300ma \$4.50 @Two for	9.98
3200VCT/200ma & 780VCT, 12VCT/.5A	12.95
3x5V/3A, 2.5V 1.75A, 6.4V/12A, 6.4V/10A 1200VCT/300ma \$4.50 @ Two for 3200VCT/200ma \$780VCT 12VCT/5A 700VCT/120ma, 115V/100ma, 6.3V/2A& 6.3V/2A	
0.24 EA. 24/EA CASED HVINSIII	3.25
Universal Vibrator Transf 6.12.24,115DC&	
115&230VAC50-60cy,420VCT/85ma.6.3V/3A	2.49
500V/3A\$10; 2/\$19; 75V/24A/220Vin	3.95
2240VCT/500ma, Pri105to250V/50-60cy2.5 V/10A,12V/4.5A,19V2.5A\$24.95 2	
V/10A,12V/4.5A,19V2.5A\$24.95 2	47.00
250VCI/60ma, 6.3VI.5A Small	1.49
CHOKES	
13.5Hy/1Amp/42ohm/17KVinsl	54.00
13.5Hy/1Amp/42ohm/17KVinsl 15-29Hy/150ma Swinging Cased	2.95
12Hy/300ma \$3.95; 3Hy/40ma 3 for 15Hy 400ma or 20Hy/300ma/12KV ins	1.00
15Hy 400ma or 20Hy/300ma/12KV ins	7.95
8Hy/150manewUTCcrckdBkIteT'Bd2/2.25	

CERAMICONS.	otol.
8Hy/100ma/\$1.10; 12Hy 275ma	3.29
50 Hy/125ma Csd	1.95
8Hy/150manewUTCcrckdBklteT'Bd2/2.25	1
15Hy 400ma or 20Hy/300ma/12KV ins	7.95
12ny/200111a \$2.92, 2ny/40ma 2 for	1.00

HIQ, CAPACI-TORS NEW! (A) ERIEDUAL TD2A/4-30mmfe45@10/2.49
(B) ERIE TS2A/4-5-5-25mmf e27@ 10/2.49
(B) ERIE TS2A/4-30mmf e27@ TEN for . 2.49
(C) ERIE TS5D/5-30mmf e54@ TEN for . 4.98
(C) ERIE TS5D/5-10.110mmf e54@ TEN for . 4.98
(D) MEISSNER 11012mmfHFradder e12; 10/\$1
(E) TRIMMER 21030mmf e9@ 12 for 98
F H J 2,3.4.7, 5, 7.5, 10, 11, 22, 25, 33, 43, 47, 50, 60, 75, 100, 120, 200, 1000, 6200mmf, "TAB" SPECIAL e9; 10/75e; 100/6.95

6.95 (G) ERIE K/CC21 5. 39mmf &20@ 6 for . 1.00 (G) ERIE L/CC26/27, 30mmf &20@ 6 for . 1.00 (G) ERIE M/CC36 33mmf &25@ 5 for . 1.00 (G) ERIE M/40.45,50,100,1000mmf.e09@12for 1.00 ERIE Feedthru 50 or 100 mmf &18@ 7 for . 1.00 ERIE 370 EF Button 400mmf &18@ 7 for . 1.00 ERIE 370 EF Button 400mmf &18@ 7 for . 1.00 ERIE 741A/N750/50mmf; HIKap 10KV Peak . 25 ERIE 741A lug type185,200,280,400mmf . 1.25

VARIABLE CONDENSERS



(A) CardwellorMillen150mm/3000VgapHF (B) DUAL 15 mmf per Sect/3000V gap	1.00
(B) BUD DUAL 75mmf/sec/1000V gap/HF. (C) JOHNSON 70H30/74mmf/3000V gap/.	1.49
(U) CARDWELL NEUT 7T/12mmf/5000	1.29
PHASING CONDSR W.E. 900 Quadrants/A	.98
taps, 360° SINEWAVE GENERATOR Variable	2.39



GE GL434A similar to 7C29 TRIODE GE GL434A similar to 7C29 TRIODE useable maxinpt 110mc's Upto1200 Watts input, UP to 600W output. 3 Terminal Grid & C. T. filament, forced air Cooling 75-200CFM, Ef 10-11V Dsgn for RADAR/BC-677 operated 215mc's/12KV/310ma inpt "TAB" SPECIAL \$7.95 SPECIAL \$7.9
REL36ACORN similar 6J4 1.9
9LP7 Magnetic DEFL&FOCUS Suit able for TELEVISION 3.98



TUBES

OA4G	\$1.04 85	6N7	85	5 872A	2.4
UZ4	85	657	87	7 884	8
1B3G1,	. 2.00	6SA7GT.	. ,59	1 918/GE1G	. 1.4
1824	2.95 2.95 3.95 1.25	6SC7 6SF5 6SG7	60	922	1.4
1B24 1B27 1D5GP	3.95	6SF5 6SG7 6SH7 6SJ7 6SJ7GT 6SK7 6SK7 6SN7GT	71	931A	3 9
1D5GP	1.25	6SH7	63	8 954	.4
1G6GT.	. 85	6SJ7	72	955	. 6.
1L4	1.05	6SJ7GT	58	956	. 6.
1LC6	. 1.05	6SK7	58	957	.4.
1LH4	1.05	6SL7.	85	958A	. 6.
1PSCT	81	6507		1612/6763	.2
1P24	2.95	6SQ7	54	1614/616V	1.5
1LH4 1LN5 1P5GT 1P24 1R4/1294 2A71 2C21/1642 2C26 2C34/RK3 2C40/446A	1.00		71	1613/6F6X 1614/6L6X 1616 1619 1622	1 30
2AP1A	2.85	6V6GT. 6U7G. 6X4. 6X5. 6Y6G. 6Z4/84. 6Z7GT. 7BP7-1812 7C29/434. 7C4/1203. 9JP1. 9JP12. 9LP7.	58	1619	30
2A3	1.04	6X4	53	1622	1.69
2C21/1642	81	6X5	81		.98
2C26	59	6Y6G	87	1625	.45
2C26 2C34/RK3 2C40/446A 2C43 2D21 2E22 2E25/HY6 2J21/725 2J26 2J30 2J31 2J32	4 .55	6Z4/84	1.23 3.95	1626	.45
2C40/446A	18.	7DD2 1913	1.23	1629	58
2D21	1 49	7C29/434	7.95	1641	1.90
2E22	1.49	7C4/1203	0.73	2050	.75
2E25/HY6	5 2.95	91P1	3.95	2051	96
2J21/725	12,95	9JP12	4.50	7193	38
2J26	12.95 18.50	9LP7	4.35	8005	4.70
2J30	18.50	10Y	60	8012	4.70
2J31	16.95	12A6	.49	8013A	3.95
2332	10.95	12AH7GT	87	8020	3.49
2134	18.05	12AK7	14.75	9001	.49
2142/700	18.50 16.95 16.95 14.50 18.95 29.95	9JP1 9JP12 9LP7 10Y 12A6 12AR7 12DP7 12GP7 12SA7GT, 12SK7 12SK7 12SK7 12SK7	14.75 14.75 .58	9002	.59
2149	29.95	IZSAZGT.	.58	9004	49
2J55	35.00 39.95 9.95	12SG7	.65	9006 C6J CE206	45
2J61A	39.95	12SH7	.71	C6.J	4.95
2K25	9.95 7.00 6.95 1.05	12SK7 12SQ7 12X3. 15E. 24G/3C24 25L6GT. 25Z5 35L6GT. 35Z5GT. 37 41 80	. 58	CE206 CE215 CK1005 F127A FG104 FG106 HY65/2E25 REL36/6J4	3.95
2K28	7.00	12SQ7	.58	CE215	5.95
2K29	0.95	12X3	.90	CK1005	.35
2 7 3 6	1.05	24C /2C24	1.39	F127A	18.00
344		25I 6CT	.68	FC104	14.95
3B7/1291	.95	257.5	.53	FG166	49 00
3B24	1.27	35L6GT	.58	HY65/2F.25	2 95
3BP1	1.49	35Z5GT	.58	REL36/6J4	1.98
3BP1A	2.95	37	.78	RX215	7.95
3C23,	4.95	41	.58	T200	12.00
3D0/1299	2.05	50L6GT	.58	VR90/OB3	.74
3E27/027D	3.00	9237	1.05	VR92	.39
31P12	2 95	11776	1 10	VRIUS	.74
3S4	.69	205B/VT2	1.98	WESTER	1 90
3B24. 3BP1A. 3C23. 3C23. 3D6/1299. 3E29/829B. 3FP7. 3JP12. 3S4. 4J47. 5AP1. 5BP1/5GP	1.05 .54 .95 1.27 1.49 2.95 3.85 3.85 3.95 3.95 3.95 3.95 3.86	50L6GT 80 83V 117Z6 205B/VT2 211 250TH 250TL 304TH	.58 .52 1.05 1.10 1.98 .89 19.49	FG105 FG166 HY65/2E25 REL36/6J4 RX215 T200 VR90/OB3 VR92 VR105 VR150 WE215A	9 95
5AP1	2.75	250TH 250TH 304TH 304TH 304TL 307A/RX9 388 393 450TH/ 6C2L 150TL 527/1000S, 631P1/SN4 632A 701A 702A	19,49	WL530.	49.50
5BP1/5GP	1 1.95	250TL	19.49 5.95 1.98 5.4.25	WL531	9.95
5BP4	3.95	304TH	5.95	WL619	9.95 20.00 12.95 2.95
DOI:	19,00	304TL	1.98	WL632A	12.95
5D21	19,00 2,95 4,95 1,25 1,25 ,53 ,87	397A/KX9	4.25	UX6653	2.95
5HP1	4 95	202	5.95	I UNGAR*	
5R4G	1.25	450TH/	0.75	20 X 672*. 199698* 289881*. MAZDA PI 49**Box 10 64** S6/T4**.	2.75
5T4	1.25	6C21	24.90 29.95 11.95 3.95 8.95 3.95 3.49 4.90	289881*	2 50
5U4G	.53	150TL	29.95	MAZDA PI	**
5V4	.87	527/1000S.	11.95	49**Box 10	.60
5W4	.87	631P1/SN4	3.95	64**	.07
572	80	034A	3.95	S6/T4**	.14
57.4	.88	702A	3.49	212/287**	.25
6AB7	.98	703A	4.90	373/3V**	10
6AC7	.81	704A	1.75	Aviation L	ots.
6AG5	.93 1.05	703A 704A 705A 707B/2K28 710A/8011 717A 722, 287A 723AB 726A	1.75 2.25 6.95 2.75 1.49	C1249/12V	
6AG7	1.05	707B/2K28 710A/8011. 717A	6.95	GR-25 for.	1,00
6AVE	.78	710A/8011.	2.75 1.49	Sealed Bea	m ~
6AL5	1.71	722 287A	9 95	4522 250 W	2.50
6B4G	1.11	722 287A. 723AB 726A 802 803 804 805 807	5.50	NEON BIII	3.70 BS
6B8G	1.05	726A	6.95	NF2-100	103
6C4	.27	802	2.95	Oty	.4.50
6C5	1.05 .27 .54 .71 1.05 1.85 .59	803	2.95 7.95 9.75 4.50 1.24 2.25	NE16/991.	.4.50 .25 .08
C6	1.71	804	9.75	NE51/NE20	.08
6D4	1 85	805	1.34	Qry100-	/ 00
6D6	59	808	2 25	FOCKETE.	0.00
6E5	.71	810	6.95	2 Y 2HIV	30
6F6/1613	.69	811	2.20	705/715	.69
SIF S	1.04	813	6.95	803/304T	.90
G5/6U5.	.85	814	2.98 2.49 1.15 .72 10.00	64** 100W/20V* 100W/20V* 133/28V** 323/3V** Aviation L. C1249/12V GR-25 for. Sealed Rea 4566/600W NFON BUI NF2-100 Oty NE16/991 NE20 OTRED SOCKETS 2 Y 2 HV 705/715 803/304T 807 813 829/832 866 872/211	.27
BLCT	.86	815	2.49	813	.69
H6	54	816	1.15	29/832	.25
14	5.95	828	10 00	872/211	.24
J5	.53	829B/3E29	3.95	ACORN	
J6	.90	832	3.95 3.75 1.12	5 for	1.00
J7	.70	836	1.12	Diheptal	.69
K5GT	.86	837	2.25	Maginal .	.59
	.54	845	4.75	829/832 866 872/211 ACORN 5 for Dihental Maginal Loktal 49SSL	
K6GT	70				. 24
K6GT	.70	860	2.49	4933L	2.
K6GT K7	.86	864	.67	Octal 7858	.06
K6GT K7 K8 L6 L6	1.27	865	.67 1.00 1.00	Octal 7858 Octal 49558 Min 50500	3 .15
K6GT K7 K8 L6 L6G	1.27		.67 1.00 1.00 1.85	Octal 7888 Octal 49888 Min 59500, Min & SH	.06 3 .15 .12
K6GT K7 K8 JL6 JL6G JL7	.86 1.27 1.04 .85	865 866A 868	.67 1.00 1.00 1.85	Octal 7888 Octal 49888 Min 59500, Min & SH. CHANGE	.06 3 .15 .12 .25



RECTIFIERS BRIDGE OUT AMPS PRICE IN OUT 14 1.35 2.49 36 28 14 3.5 3.49 36 28 14 5. 4.85 36 28 IN OUT AMPS PRICE 36 28 1.5 3.95 36 28 3.5 4.75 1.5 3.95 3.5 6.75 5. 7.50 0.15 1.49 28 75 .320 190 .04 Write for LIST



1.98



RELAYS
G'DIAN 500AC/op18-24VAC/4PSTN0/8A...\$
S'DUNN 32AXX10Reset&0'land 10ma&115VAC G'DIAN 500AC/op18:24VAC/4PSTN0/8A...\$1.25
S'DUNN 32AXXIDReset&C'Iand 10ma&i15VAC 4.95
GE Sealed plugin 2000ohm/SPDT/5A cts... 1.98
ALLIED STK/f6to12VDC DPDT&SPN0&NC... 98
ALLIED CONTROL STK/7.5to24VDC/SPDT... 75
GE CR2791B100J3 3PDT/24V/5A contacts. 1.39
S'DUNN 17AXXIO9/115VAC/SPN0/6C cts... 1.98
KURMAN 4maSens 650ohm/DP1N0&1NC/5amp.2.25
GE CR2791-B100F3/24V DPDT/5Amp Cts... 98
G'DIAN 125DV/4to 12VDC/SPDT/8A Cts... 98
G'DIAN 125DV/4to 12VDC/SPDT/8A Cts... 98
G'DIAN 4500 ohmCoil/SPST/5A Cts... ... 98
G'DIAN 4500 ohmCoil/SPST/5A Cts... ... 98
EACH 115VAC/DPDT/10Amp Contacts... 1.69
U) ABradley 702/110VAC/3PSTD break 25A 4.49
V) ALLIED BJ 6V/DPDT/5Amp Contacts 1.98
V) ALLIED BJ 6V/DPDT/5Amp Contacts 1.98
V) ALLIED BJ 6V/DPDT/5Amp Contacts 1.98
V) ALLIED BJ 4V/5A/SPDT/5A Cts... ... 98
W) ADVANCE 4001B Ant DPDT&SPN0 15A
CeramicHFins/75to110V\$2.75@& Recl15VAC 3.25
X) ABradley 0'load adjl8.1 15.2/12/9&6.3A 3.98
Y) Potter & B 115VAC/DPN0/8A CTS... 1.79
2) CLARE VAC.NITROGEN sealed SK5010/DPDT/
18-28V 3AmpCts octalbased\$1.49@ with Rect115
VAC 1.98

VAC 1.98
A1) GE Inst V'Relay Calib70, 85, 110, 160V
for115VAC 9.95
B1) GM 24V/SPN0/20A Cts Dbl make 1.49
C1) G'DIAN 17-29V/SPDT/12A/.05sec delay 1.69
D1 A'Chimrs,194PrecCompaT'0'ld ... 7.95
E1) G'DIAN G26483 750ohm/50DC1/20sec delay/3PST 2ND1NC 1.79
F1) GE CR2792B117A3/28V/50Amp/SPN0
Dbl break 1.98

THAT'S

A BUY Corner Church & Lib-erty Sts. Room 200 "TAB" Money Back Guarantee \$3 Min. Order F.O.B. N. Y. C. Add Shipping Charges and 25% Deposit. Tel. WO. 2-7230

"TAB" Money Back Guarantee \$3 Min. Order F.O.B: N. Y. C. Add Shipping Charges and 25% Deposit. Tel. WO. 2-7230

THAT'S A BUY

DEPT. 11E SIX CHURCH ST., NEW YORK 6, N. Y., U.S.A.

ELECTRONICS — November, 1948

AN/CPN-6, 3 CM RADAR BEACON INSTALLATIONS

*WIRE WOUND RESISTORS

Stock No.	Description
46-189-2	Ferrule Resistor RW 14F
	9000 cy. @ 40 watts
46-189-12	9000 cy. (# 40 watts RW 13F 400 ohms (# 40 watts RW 14F 70 ohms (# 90 watts RW 12D 20 ohms (# 90 watts RW 12D 30 ohms (# 90 watts RW 12D 0,000 ohms (# 40 watts RW 14F 10,000 ohms (# 40 watts RW 14F
	5.000 ohms @ 40 watts RW 14F
46-189-22	70 ohms @ 90 watts RW 12D
46-189-17	20 ohms @ 90 watts RW 12D
46-189-18	30 ohms @ 90 watts RW 12D
46-189-4	0,000 ohms @ 40 watts RW 14F
46-189-20	40 onms @ 90 watts Rw 12D
46-1985T-1	5000 ohms 10 watts 5%
46-2065	7500 ohms 10 watts 10%
46-128-7	7500 ohms 10 watts 10%
46-58 T -8	7500 ohms 50 watts
1 W-996-2	8300 ohms @ 20 watts, 70F
1W-996-3	1750 ohms @ 10 watts, 10F
1 W-996-4	200 ohms 5% @ 10 watts, 10F
1W-996-5	20 ohms 5% @ 15 watts, 15F
1 W-996-6	800 ohms 5% @ 20 watts, 20F
1W46-1766-1	5000 ohms 5% @ 20 watts
2	1000 ohms 5% @ 20 watts
-3	2000 ohms 5% @ 20 watts
3W-46-1076-1	0.33 ohrs 10% @ 5 watts
3W-46-188-6	160 ohms @ 25 watts 10%
-11	250 ohms @ 90 watts
	2500 ohms @ 50 watts
-29	1.0 ohms @ 90 watts
	2500 ohms @ 120 watts
-5	50 ohms @ 120 watts
-9	1250 ohms @ 120 watts
46-189-23	75 ohms @ 90 watts
46-189-26	100 ohms @ 90 watts RW 12D
46-189-27	775 ohms @ 50 watts RW 12D
46-189-28	800 ohms @ 50 watts RW 13D
46-189-29	4000 ohms @ 50 watts RW 13D
40-100-20	
13786-T-2 13786-T-3	
13/80-1-3 1	
13786-T-12 2	
46-1022T-1 1	4,000 @ 6 watts
6-1023T-4	100
6-1023T-4 46-597-T-15	100
6-1023T-4 46-597-T-15 46-597-T-19	100
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33	100
6-1023T-4 46-597-T-15 46-597-T-19	100 CSF 1 30 ohms, 100 W, Ferrule, #CAO 63179 70 ohms, 120 W, Ferrule #CAO 63366 450 ohms, 120 W, 9 taps, Ferrule #CAO 500 ohms, 120 W, 9 taps, Ferrule #CAO
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-35	100 W. Ferrule, & CAO 63179 70 ohms, 120 W. Ferrule, & CAO 63179 70 ohms, 120 W. Ferrule & CAO 63366 450 ohms, 120 W. Ferrule & CAO 63196 500 ohms, 120 W. 9 taps, Ferrule & CAO 63231
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33	100 W, Ferrule, /CAO 63179 70 ohms, 120 W, Ferrule, /CAO 63366 450 ohms, 120 W, Ferrule /CAO 63366 500 ohms, 120 W, 9 taps, Ferrule /CAO 63231 198 ohms, 120 W, 10 taps, Ferrule
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-35 46-597-T-28	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & CAO 63179 70 ohms, 120 W, Ferrule & CAO 63366 450 ohms, 120 W, 9 taps, Ferrule & CAO 63231 198 ohms, 120 W, 10 taps, Ferrule & CAO 631134D
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-28 46-597-T-28	100 W, Ferrule, #CAO 63179 70 ohms, 120 W, Ferrule, #CAO 63366 450 ohms, 120 W, Ferrule #CAO 63366 500 ohms, 120 W, 9 taps, Ferrule #CAO 63231 198 ohms, 120 W, 10 taps, Ferrule #CAO 631134D 225 ohms, 120 W, Ferrule #CAO 63191
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-35 46-597-T-28 46-597-T-25 46-3818-T-13	100 W, Ferrule, /CAO 63179 70 ohms, 120 W, Ferrule, /CAO 63177 70 ohms, 120 W, Ferrule /CAO 63366 450 ohms, 120 W, Ferrule /CAO 63366 63231 198 ohms, 120 W, 10 taps, Ferrule /CAO 631134D 225 ohms, 120 W, Ferrule /CAO 63191 4500 ohms, CSF 63211
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-28 46-597-T-28	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & CAO 63179 70 ohms, 120 W, Ferrule & CAO 63366 450 ohms, 120 W, Ferrule & CAO 63196 500 ohms, 120 W, 9 taps, Ferrule & CAO 63231 198 ohms, 120 W, 10 taps, Ferrule & CAO 631134D 225 ohms, 120 W, Ferrule & CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-35 46-597-T-28 46-597-T-25 46-3818-T-13 46-3818-T-13	100 W, Ferrule, \$\tilde{\ell}\$CAO 63179 70 ohms, 120 W, Ferrule, \$\tilde{\ell}\$CAO 63366 450 ohms, 120 W, Ferrule \$\tilde{\ell}\$CAO 63366 500 ohms, 120 W, 9 taps, Ferrule \$\tilde{\ell}\$CAO 63191 198 ohms, 120 W, 10 taps, Ferrule \$\tilde{\ell}\$CAO 631134D 225 ohms, 120 W, Ferrule \$\tilde{\ell}\$CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule \$\tilde{\ell}\$CIR 63236-D
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-35 46-597-T-28 46-597-T-25 46-3818-T-13	100 W, Ferrule, fCAO 63179 70 ohms, 120 W, Ferrule, fCAO 63179 70 ohms, 120 W, Ferrule fCAO 63366 450 ohms, 120 W, Ferrule fCAO 63196 500 ohms, 120 W, 9 taps, Ferrule fCAO 63231 198 ohms, 120 W, 10 taps, Ferrule fCAO 631134D 225 ohms, 120 W, Ferrule fCAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule fCIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps,
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-35 46-597-T-28 46-597-T-25 46-3818-T-13 46-3818-T-12	100 W, Ferrule, \$\tilde{\chi}\chi\$ AO 63179 70 ohms, 120 W, Ferrule, \$\tilde{\chi}\chi\$ AO 63366 450 ohms, 120 W, Ferrule \$\tilde{\chi}\chi\$ CAO 63366 500 ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\chi\$ CAO 63191 198 ohms, 120 W, 10 taps, Ferrule \$\tilde{\chi}\chi\$ CAO 631134D 225 ohms, 120 W, Ferrule \$\tilde{\chi}\chi\$ CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\chi\$ CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\tilde{\chi}\chi\$ CHO 631135D
6-1023T-4 46-597-T-15 46-597-T-35 46-597-T-35 46-597-T-25 46-597-T-25 46-3818-T-13 46-3818-T-11 46-3818-T-11	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63186 450 ohms, 120 W, Ferrule & AO 63366 450 ohms, 120 W, Ferrule & AO 63196 500 ohms, 120 W, 9 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & AO 63134D 630 ohms, 120 W, Ferrule, 10 taps, & AO 63135D Meg-o-max, 8000 ohms & AOSF 63152-F
6-1023T-4 46-597-T-15 46-597-T-19 46-597-T-33 46-597-T-35 46-597-T-28 46-597-T-25 46-3818-T-13 46-3818-T-12	100 W, Ferrule, & AOA 63179 70 ohms, 120 W, Ferrule, & AOA 63179 70 ohms, 120 W, Ferrule & AOA 63186 450 ohms, 120 W, 9 taps, Ferrule & AOA 63196 500 ohms, 120 W, 9 taps, Ferrule & AOA 63231 198 ohms, 120 W, 10 taps, Ferrule & AOA 631134D 225 ohms, 120 W, Ferrule & AOA 63191 4500 ohms, 120 W, 9 taps, Ferrule & CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, & AOA 631135D Meg-o-max, 9000 ohms & ACSF 63152-F Meg-o-max, 12,500 ohms, & ACSF
6-1023T-4 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-397-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-11 46-3818-T-1 46-3818-T-1	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63187 70 ohms, 120 W, Ferrule & AO 63366 450 ohms, 120 W, 9 taps, Ferrule & AO 63196 500 ohms, 120 W, 9 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & ACIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, & ACHD 631135D Meg-o-max, 8000 ohms & ACSF 63152-F Meg-o-max, 12,500 ohms, & ACSF 63831-F
6-1023T-4 46-597-T-15 46-597-T-33 46-597-T-33 46-597-T-28 46-597-T-25 46-3818-T-13 46-3818-T-11 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-3818-T-1	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule & AO 63366 450 ohms, 120 W, Ferrule & AO 63196 500 ohms, 120 W, 9 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & ACHD 631135D Meg-o-max, 000 ohms & ACSF 63152-F Meg-o-max, 12,500 ohms, & ACSF 63831-F Meg-o-max, 100 ohms, & RW11F101
6-1023T-4 46-597-T-15 46-597-T-13 46-597-T-33 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-14 46-3818-T-14 46-597-T-21 46-597-T-21	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63366 450 ohms, 120 W, 9 taps, Ferrule & AO 63196 500 ohms, 120 W, 9 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, & ACHD 631135D Meg-o-max, 8000 ohms & ACSF 63152-F Meg-o-max, 12,500 ohms, & ACSF 63831-F Meg-o-max, 100 ohms, & RW11F101 125 olms (100 W) Ferrule & AOA 63187
6-1023T-4 46-597-T-15 46-597-T-35 46-597-T-35 46-597-T-25 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-597-T-21	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule & AO 63366 450 ohms, 120 W, Ferrule & AO 63366 450 ohms, 120 W, Ferrule & AO 63196 198 ohms, 120 W, 10 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & AO 63135D Meg-o-max, 120 W, Ferrule, 10 taps, & AO 6310 & AO 63105 Meg-o-max, 100 ohms, & AO 6315-F Meg-o-max, 100 ohms, & AO 63187 Meg-o-max, 100 ohms, & AO 63187 250 ohms (120 W) Ferrule, & AO 63187
6-1023T-4 46-597-T-15 46-597-T-13 46-597-T-33 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-14 46-3818-T-14 46-597-T-21 46-597-T-21	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule & AO 63366 450 ohms, 120 W, Ferrule & AO 63366 450 ohms, 120 W, Ferrule & AO 63196 198 ohms, 120 W, 10 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & AO 63135D Meg-o-max, 120 W, Ferrule, 10 taps, & AO 6310 & AO 63105 Meg-o-max, 100 ohms, & AO 6315-F Meg-o-max, 100 ohms, & AO 63187 Meg-o-max, 100 ohms, & AO 63187 250 ohms (120 W) Ferrule, & AO 63187
6-1023T-4 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 M-37471	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63366 450 ohms, 120 W, 9 taps, Ferrule & AO 63196 500 ohms, 120 W, 9 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & AO 63103D 630 ohms, 120 W, Ferrule, 10 taps, & ACHD 631135D Meg-o-max, 8000 ohms & ACSF 63152-F Meg-o-max, 12,500 ohms, & ACSF 63831-F Meg-o-max, 100 ohms, & MW11F101 125 ohms (120 W) Ferrule, & AO 63187 250 ohms (120 W) Ferrule, & AO 63192 Meg-o-max, 80 ohms, 15W, 5%, Non- 1nd, CSF 63262-F
6-1023T-4 46-597-T-15 46-597-T-35 46-597-T-35 46-597-T-25 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-597-T-21	100 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63366 450 ohms, 120 W, Ferrule \$\(\) CAO 63366 500 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63196 500 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63131 198 ohms, 120 W, 10 taps, Ferrule \$\(\) CAO 631134D 225 ohms, 120 W, Ferrule \$\(\) CAO 63191 4500 ohms, 120 W, 9 taps, Ferrule \$\(\) CIR 63236-D 630 ohms, 120 W, 9 taps, Ferrule \$\(\) CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\(\) CIR 031135D Meg-0-max, 9000 ohms, \$\(\) CSF 63315-F Meg-0-max, 12,500 ohms, \$\(\) CSF 6331-F Meg-0-max, 100 ohms, \$\(\) RW11F101 125 ohms (100 W) Ferrule \$\(\) CAO 63187 250 ohms (120 W) Ferrule, \$\(\) CAO 63192 Meg-0-max, 80 ohms, 15W, 5%, Non- Ind, CSF 632262-F 125 ohms, 120 W, 9 taps, Ferrule,
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-31 M-37471 46-597-T-23	100 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63186 450 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63366 450 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63191 198 ohms, 120 W, 10 taps, Ferrule \$\(\) CAO 631134D 225 ohms, 120 W, Ferrule \$\(\) CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule \$\(\) CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\(\) CIR D 631135D Meg-0-max, 8000 ohms \$\(\) CSF 63152-F Meg-0-max, 100 ohms, \$\(\) CSF 63831-F Meg-0-max, 100 ohms, \$\(\) RW11F101 125 olms (100 W) Ferrule, \$\(\) CAO 63187 250 ohms (120 W) Ferrule, \$\(\) CAO 63187 250 ohms (120 W) Ferrule, \$\(\) CAO 63187 250 ohms, 120 W, 9 taps, Ferrule, \$\(\) CAO 63230
6-1023T-4 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 M-37471	100 W, Ferrule, *CAO 63179 70 ohms, 120 W, Ferrule, *CAO 63179 70 ohms, 120 W, Ferrule, *CAO 63366 450 ohms, 120 W, 9 taps, Ferrule *CAO 63196 500 ohms, 120 W, 9 taps, Ferrule *CAO 63231 198 ohms, 120 W, 10 taps, Ferrule *CAO 631134D 225 ohms, 120 W, Ferrule *CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule *CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, *CHD 631135D Meg-o-max, 12,500 ohms, *CSF 63152-F Meg-o-max, 12,500 ohms, *CSF 63831-F Meg-o-max, 100 ohms, *RW11F101 125 ohms (120 W) Ferrule, *CAO 63187 250 ohms (120 W) Ferrule, *CAO 63192 Meg-o-max, 80 ohms, 15W, 5%, Non- 1nd, CSF 632262-F 125 ohms, 120 W, 9 taps, Ferrule, *CAO 63230 Meg-o-max, 16,000 ohms, *CSF Meg-o-max, 16,000 ohms, *CSF
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-35 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-31 M-37471 46-597-T-23 46-597-T-23	100 W, Ferrule, \$\tilde{\chi}\$CAO 63179 70 ohms, 120 W, Ferrule, \$\tilde{\chi}\$CAO 63366 450 ohms, 120 W, Ferrule \$\tilde{\chi}\$CAO 63366 500 ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\$CAO 63196 500 ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\$CAO 6313134D 225 ohms, 120 W, Ferrule \$\tilde{\chi}\$CAO 63191 4500 ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\$CIO ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\$CIO 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\tilde{\chi}\$CID 631355D Meg-0-max, 8000 ohms, \$\tilde{\chi}\$CFF 63831-F Meg-0-max, 10,00 ohms, \$\tilde{\chi}\$RW11F101 125 olms (100 W) Ferrule, \$\tilde{\chi}\$CAO 63192 Meg-0-max, 80 ohms, 15W, 5\tilde{\chi}\$, Non- hd, CSF 632262-F 125 ohms, 120 W, 9 taps, Ferrule, \$\tilde{\chi}\$CAO 63230 Meg-0-max, 16,000 ohms, \$\tilde{\chi}\$CSF 63157-F
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 M-37471 46-597-T-23 46-3818-T-5 46-3818-T-5	100 W, Ferrule, \$\tilde{\chi}\$CAO 63179 70 ohms, 120 W, Ferrule, \$\tilde{\chi}\$CAO 63366 450 ohms, 120 W, Ferrule \$\tilde{\chi}\$CAO 63366 450 ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\$CAO 63165 198 ohms, 120 W, 10 taps, Ferrule \$\tilde{\chi}\$CAO 631134D 225 ohms, 120 W, Ferrule \$\tilde{\chi}\$CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule \$\tilde{\chi}\$CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\tilde{\chi}\$CIR 63135D Meg-0-max, 8000 ohms \$\tilde{\chi}\$CSF 63152-F Meg-0-max, 12,500 ohms, \$\tilde{\chi}\$CSF 63831-F Meg-0-max, 100 ohms, \$\tilde{\chi}\$RW11F101 125 ohms (120 W) Ferrule \$\tilde{\chi}\$CAO 63187 250 ohms (120 W) Ferrule, \$\tilde{\chi}\$CAO 63187 250 ohms, 120 W, 9 taps, Ferrule, \$\tilde{\chi}\$CAO 63230 Meg-0-max, 16,000 ohms, \$\tilde{\chi}\$CSF 63157-F Meg-0-max, \$\tilde{\chi}\$CSF 63830-F
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-35 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-31 M-37471 46-597-T-23 46-597-T-23	100 W, Ferrule, #CAO 63179 70 ohms, 120 W, Ferrule, #CAO 63179 70 ohms, 120 W, Ferrule, #CAO 63186 450 ohms, 120 W, 9 taps, Ferrule #CAO 63186 500 ohms, 120 W, 9 taps, Ferrule #CAO 63231 198 ohms, 120 W, 10 taps, Ferrule #CAO 631134D 225 ohms, 120 W, Ferrule #CAO 63191 4500 ohms, 120 W, 9 taps, Ferrule #CIR 63236-D 630 ohms, 120 W, 9 taps, Ferrule #CIR 63236-D 030 ohms, 120 W, Ferrule, 10 taps, #CHD 631135D Meg-0-max, 9000 ohms #CSF 63152-F Meg-0-max, 120 W, 9 taps, Ferrule 125 ohms (120 W) Ferrule #CAO 63187 250 ohms (120 W) Ferrule #CAO 63192 Meg-0-max, 80 ohms, 15W, 5%, Non- Ind. CSF 632262-F 125 ohms, 120 W, 9 taps, Ferrule, #CAO 63230 Meg-0-max, 16.000 ohms, #CSF Meg-0-max, 16.000 ohms, #CSF Meg-0-max, #CSF 63830-F Meg-0-max, #CSF 63830-F Meg-0-max, #CSF 63830-F Meg-0-max, #CSF 63830-F Meg-0-max, #CSF 6380-F Meg-0-max, #CSF 6380-F Meg-0-max, #CSF 6380-F Meg-0-max, #CSF 6380-F
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-397-T-25 46-3818-T-13 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-23 46-597-T-23 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21	100 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63164 50 ohms, 120 W, Ferrule \$\(\) CAO 63366 450 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63196 500 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63131 198 ohms, 120 W, 10 taps, Ferrule \$\(\) CAO 631134D 225 ohms, 120 W, Ferrule \$\(\) CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule \$\(\) CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\(\) CIR D 631135D Meg-0-max, 8000 ohms \$\(\) CSF 63152-F Meg-0-max, 12,500 ohms, \$\(\) CSF 63831-F Meg-0-max, 100 ohms, \$\(\) RW11F101 125 olms (100 W) Ferrule, \$\(\) CAO 63192 Meg-0-max, 80 ohms, 15W, 5\(\), Non- Ind, CSF 632262-F 125 ohms, 120 W, 9 taps, Ferrule, \$\(\) CAO 63230 Meg-0-max, \$\(\) CSF 63830-F Meg-0-max, \$\(\) CSF 63830-F Meg-0-max, \$\(\) CSF 638318-10P, \$\(\) K-7106845-8
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 M-37471 46-597-T-23 46-3818-T-5 46-3818-T-5	100 W, Ferrule, #CAO 63179 70 ohms, 120 W, Ferrule, #CAO 63179 70 ohms, 120 W, Ferrule, #CAO 63186 450 ohms, 120 W, Ferrule #CAO 63186 500 ohms, 120 W, 9 taps, Ferrule #CAO 63231 198 ohms, 120 W, 10 taps, Ferrule #CAO 631134D 225 ohms, 120 W, Ferrule #CAO 63191 4500 ohms, 120 W, 9 taps, Ferrule #CIR 63236-D 630 ohms, 120 W, 9 taps, Ferrule #CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, #CIHD 631135D Meg-o-max, 9000 ohms #CSF 63152-F Meg-o-max, 12,500 ohms, #CSF 63831-F Meg-o-max, 12,500 ohms, #CSF 63831-F Meg-o-max, 12,500 ohms, #CSF 63157-F Meg-o-max, 16,000 ohms, #CSF 63157-F Meg-o-max, #CSF 63830-F Meg-o-max, #CSF 63830-F Meg-o-max, #CSF 63830-F Meg-o-max, #CSF 63831-F Meg-o-max, #CSF 63830-F Meg-o-max, #CSF 63830-F Meg-o-max, #CSF 63831-F Meg-o-max, #CSF 63830-F Meg-o-max, #CSF 63831-F Meg-o-max, #CSF 63830-F Meg-o-max, #CSF 63831-F Meg-o-max, #CSF 63831-F Meg-o-max, \$550 ohms, \$W, #CSF633318-10P, K-7106845-8 Meg-o-max, 32.5 ohms, \$120.
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-35 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-23 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-31 M-37471 46-597-T-23 46-3818-T-5 46-3818-T-1 13084T-4 46-325T-1	100 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63186 450 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63366 500 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63196 198 ohms, 120 W, 10 taps, Ferrule \$\(\) CAO 631134D 225 ohms, 120 W, Ferrule \$\(\) CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule \$\(\) CIT 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\(\) CIT 63236-D 10 (apple of taps) 10 (apple ohms) 11 (apple ohms) 12 (apple ohms) 13 (apple ohms) 14 (apple ohms) 15 (apple ohms) 16 (apple ohms) 16 (apple ohms) 17 (apple ohms) 18 (apple ohms) 19 (apple ohms) 19 (apple ohms) 10 (apple ohms) 11 (apple ohms) 12 (apple ohms) 12 (apple ohms) 13 (apple ohms) 14 (apple ohms) 15 (apple ohms) 16 (apple ohms) 16 (apple ohms) 16 (apple ohms) 17 (apple ohms) 18
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-33 46-597-T-35 46-597-T-25 46-397-T-25 46-3818-T-13 46-3818-T-14 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-23 46-597-T-23 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-21	100 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63179 70 ohms, 120 W, Ferrule, & AO 63366 450 ohms, 120 W, Ferrule & AO 63186 500 ohms, 120 W, 9 taps, Ferrule & AO 63231 198 ohms, 120 W, 10 taps, Ferrule & AO 631134D 225 ohms, 120 W, Ferrule & AO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule & CIR 63236-D 630 ohms, 120 W, Ferrule, 10 taps, & CHD 631135D Meg-o-max, 8000 ohms & ACSF 63152-F Meg-o-max, 12,500 ohms, & FCSF 63831-F Meg-o-max, 100 ohms, & MW11F101 125 ohms (120 W) Ferrule & AO 63187 250 ohms (120 W) Ferrule, & AO 63187 250 ohms (120 W) Ferrule, & AO 63187 250 ohms, 120 W, 9 taps, Ferrule, & AO 63230 Meg-o-max, & Ohms, 15W, 5%, Non- tald, CSF 632262-F 125 ohms, 120 W, 9 taps, Ferrule, & AO 63230 Meg-o-max, & CSF 63830-F Meg-o-max, & CSF 63830-F Meg-o-max, & ACSF 63830-F Meg-o-max, & SSF 63830-F Meg-o
6-1023T-4 46-597-T-15 46-597-T-15 46-597-T-35 46-597-T-35 46-597-T-25 46-3818-T-13 46-3818-T-12 46-3818-T-14 46-3818-T-1 46-597-T-21 46-597-T-21 46-597-T-21 46-597-T-23 46-3818-T-1 46-3818-T-1 46-597-T-21 46-597-T-31 M-37471 46-597-T-23 46-3818-T-5 46-3818-T-1 13084T-4 46-325T-1	100 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63179 70 ohms, 120 W, Ferrule, \$\(\) CAO 63186 450 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63366 500 ohms, 120 W, 9 taps, Ferrule \$\(\) CAO 63196 198 ohms, 120 W, 10 taps, Ferrule \$\(\) CAO 631134D 225 ohms, 120 W, Ferrule \$\(\) CAO 63191 4500 ohms, CSF 63211 3,000 ohms, 120 W, 9 taps, Ferrule \$\(\) CIT 63236-D 630 ohms, 120 W, Ferrule, 10 taps, \$\(\) CIT 63236-D 10 (apple of taps) 10 (apple ohms) 11 (apple ohms) 12 (apple ohms) 13 (apple ohms) 14 (apple ohms) 15 (apple ohms) 16 (apple ohms) 16 (apple ohms) 17 (apple ohms) 18 (apple ohms) 19 (apple ohms) 19 (apple ohms) 10 (apple ohms) 11 (apple ohms) 12 (apple ohms) 12 (apple ohms) 13 (apple ohms) 14 (apple ohms) 15 (apple ohms) 16 (apple ohms) 16 (apple ohms) 16 (apple ohms) 17 (apple ohms) 18

TBK-17 500 WATT NAVY TRANS-MITTERS, 2-18 mc. AVAILABLE: 10 NEW TRANSMITTERS, 5 MOTOR GENERATOR SETS, 220/440 VAC.; 3 MODULATOR UNITS FOR PHONE OPERATION; 50 SPARE OSCILLA-TOR UNITS. SEND FOR INFORMATION.

*MICROPHONE ELEMENTS

APN-1 SPARE PARTS

Switch, #P-255299-502 2 for \$3.25 RELAY, #M25377-1 \$1.75

*INSULATORS

IN-84

SCR 578 Transmitters, alone, and com-plete sets very large quantities available







*MAGNETRONS PK.PWR FREQ.

TUBE	RANGE	OUT.	PRICE
2J31	2820-2860 mr.	265 KW.	\$15.00
2J21-A	9345-9405 mc.	50 KW.	\$25.00
2J22	3267-3333 n.c.	265 KW.	\$15.00
2J26	2992-3019 mc.	275 KW.	\$15.00
2J27	2965-2992 mc.	275 KW.	\$15.00
2J32	2780-2820 mc.	285 KW.	\$15.00
2J38 Pkg.	3249-3263 mc.	5 KW.	\$25.00
2J39 Pkg.	3267-3333 mr.	8.7 KW.	\$25.00
2J55 Pkg.	9345-9405 mc.	50 KW.	\$25,00
3J31	24,000 mc.	50 KW.	\$35.00
714AY			\$15.00
720BY	2800 mc.	1000 KW.	\$50.00
720CY			
725-A			\$25.00
730-A			
KLYSTRON	S: 723A/B		\$12.50
707B W/CAV	/ITY \$20.00	726-A	\$15.00
	MAACHETS	•	

MAGNETS
For 2J21, 725-A, 2J22, 2J26, 2J27, 2J31, 2J32 and 3J31 ... Each \$8.00 4850 Gauss, %" bet. pole faces, %" pole diam....\$8.00 1500 Gauss, 1½" bet. pole faces, 15%" pole diam. \$8.00 TUNABLE PKG'D "CW"

MAGNETRONS

QK59 2675-2900 Mcs. Q QK60 2800-3025 Mcs. Q New-\$55 each QK61 2975-3200 Mcs. QK62 3150-3375 Mcs.

	CENTIMETER PLUMBI	NG
65 deg.	twist, 6" long	\$10
12" sect.	ion, 45 deg. twist, 90 deg. bend.	\$6.
11" stra	ight waveguide section choke to c	over. Sp
	eavy construction, silver plated	
	ctions choke to cover	

5 ft. sections, choke to cover \$14.50 I8* flexible sections \$17.50 'E'' and 'H'' plane bends \$12.50 Bulkhead feed thru's \$15.50 DIRECTIONAL COUPLERS, 'N'' coupling 20 db. nominal COUPLERS, waveguide coup-D-164699 (3 cm) for mounting in "X" band guide D-164699 (3 cm) for mounting in A guide ... \$2.50
TS 108-AP dummy load ... \$65.00
"X" BAND calibrated attenuator ... \$85.00
SHIELDED KLYSTRON tube mount with rough attenuator ... \$90.00

TEST SET 159 TPX

Heasures frequency between 150 & 200 mc. by heterodyne method. Power of Xmtr can be directly measured, Measures DC voltages up to 500 Volts. Original operation on 110 V. 400 cy. but conversion kit makes it operable on 110 V. 60 cy. new, complete with tubes, crystal, cal. chart, antenna, meter & conversion kit and data for 110 V. 60 cy operation \$29.95

*PRECISION RESISTORS

Type Range Tol. Wat	ts Type Range Tol. Watts
WM-3 5 ohns 1%	0.1 meg. 1%
920 1%	0.12 meg. 1% 1
1.450 1%	0.15 meg 1% 1
2,230 1% 1	0.2 meg. 1%
5,000 2% 1	0.22 meg. 2% 1
2,230 1% 1 5,000 2% 1 7,000 1% 1	0.22 meg. 2% 1
7 500 1%	0.25 meg. 1%
7.500 1% 8.500 1%	0.5 meg. 1%
10,000 2%	1. meg. 1%
10,000 1%	WM-3L 20,000 ohms
920 1% 4 1450 1% 5 2,230 1% 1 5,000 2% 1 7,000 1% 1 7,500 1% 8 500 1% 10,000 2% 10,000 2% 10,000 15% 17,000 2% 17,000 2% 17,000 2% 13,000 1% 33,000 2% 33,000 1% 10,000 1% 10,000	
17,000 2% 1	WM-4L 50 ohms 1%
30,000 1%	75 1% 1
33,000 2%	82 1%
35,000 1% 1	120 1%
1%	120 1% 125 1%
75,000 1%	128 1% 1
0.1 meg. 1%	128 1% 1 150 1%
0.17 meg. 2%	75 1% 1 82 1% 120 1% 125 1% 128 1% 1 150 1% 200 1% 1
WM-4	250 i%
1.01 1%	1 WM-4L 50 ohms 1 % 1 % 1 % 1 % 1 % 1 % 1 % 1 % 1 % 1
3 1 1%	800 1% 1
3 5.05 1% .(CO 2%	800 1% 1 1,100 1% 25.000 1%
,((0 2%	25.000 1%
10 000 10	35,000 1%
12,000 1%	WM-4L 0.25 meg. 1%
$\begin{array}{cccc} 12,000 & 1\% \\ 40,000 & 1\% \\ 50,000 & 1\% \\ 55,000 & 1\% \\ 75,000 & 1\% \end{array}$	WL 18 ohms 1%
50,000 1%	XL 300 1%
55,000 1%	XL 300 1% TM 10 1% TM-1 1,000 1%
75,000 1%	TM 1 000 100
WM-5 10,000 5%	TM-1 1.000 1% X 10.1 1%
(C 2 %) 12,000 1% 40,000 1% 50,000 1% 55,000 1% 75,000 1% WM-5 10,000 5% 17,300 5% 17,300 5%	10.1 1%
WM-5 10,000 5% 17,300 5% 20,000 1% 30,000 1% 50,000 1%	WL 18 ohms 1 % XL 300 1 % TM 10 1 1% TM-1 1,000 1 % X 10.1 1 1% X 43.5 1 % 6 X 430 1 % X 1,906 5 %
30,000 1%	1 000 500
50,000 1%	X 1,906 5%
84,000 2%	1 X 4,300 2% 1
Note: Type with suffix	"L" have 3" wire leads.

Note: Type with suffix "L" have 3" wire lead otherwise they have solder lug terminals.

*M'F'G'S QUANTITIES AVAILABLE

*PLUGS AND CONNECTORS

PART NO. DESCRIPTION 148A—2Z7226—148A, Female Plug, ARC type, 3 Hlack, Some unpainted 277111 51—Jones #P-101/4, Male Connector Single Contact R & Severlock—Male Plug, 5 Pin, W/Cable Clamp Pl. 182—10H/258-B, 227226-182, NAF 68925-2, Male Plug, 7 Pin, Bakalite, Tube Base type W/Key Pl. 174—10/H258-B, NAF-68925-2, Same As Above, but w/Metal Cover Cannon W/G21C-½—223067-13, Female Plug, 8 holes W/Cable Clamp, ¾ FD Amphenol AN3064-12—Cable Ferrule 1½ FD Amphenol AN3064-12—Cable Ferrule 1½ FD Amphenol—AN3061-13 Cable Ferrule 1½ FD Amphenol—O7-3100-22-8, Female Plug 2 hole The Company of the Com

18 Pins ARC type
COA.—ES-677956-2, Transmission Line Connector
2Z-7227-10—Female Plug Ass. Chassis Mtg., ARC type
3 hole
AN-3057-16—222636-2, 42K103589, M289, Cable Clamp
Ambhenol 1½" FD
AN3102-148-2P—Male Chassis Plug 4 Pin 13/16" FD
GK.1-2-16-½—Female Cable Connector 12 hole, Cannon 1" FD
PL 123—Female Plug 2 hole Threaded Both Ends
15/16" FD
AN3102-148-2R—Male Chassis Plug 5 Pin ½" FD
AN3102-145-5A—Male Chassis Plug 5 Pin ½" FD
AN-3102-165-1P—PD20143-1, Male Chassis Plug 7 Pin
Amphenol 1" FD
UG21U, 227390-21—(Type N) Male Cable Connector
Original "Amphenol"
AN3108-28-128—Female Cable Plug 26 hole, Right Angle Harwood 1½" FD Matches BA10251-3 Below
BA10251-3—Male Chassis Receptical Hubbell, 26 Pin
1¾" FD Matches AN3108-28-128 Above
227116.3. WK.6-328—Male Chassis Receptical Hubbell, 26 Pin
1¾" FD Matches 227724-285 Below
227242-85, WK.6-325—Male Chassis Receptical Fin
Cannon 13/16" FD, Matches 227724-285 Below
227242-85, WK.6-325—Male Chassis Receptical Plug
22742-85, WK.6-23 ½" B—Female 6 Pin Cable Plug,
Right Angle ¾" FD, Matches 227716-3 Above, Cannon
227771, PL 71—Female Cable Plug 3 hole Cannon Semi
Heavy W.Right Angle Cable Feed
227242-88—WK.6-21½ B, A30088, Female Cable Plug
3 Hole Cannon, ¾" FD
223067-13—WK.6-21C%, Similar to above, but less
threaded End, with Cable clamp, Cannon
AN3102-20-17—Male Chassis Receptacle, 14 Pin Amphenol 1½" FD (Cable Plugs for Above PLP256,
AN3106-20-275)
PLP256, AN31062027S—227226-256.2, Female Cable
Plug, 14 hole, 1" FD "Amphenol"
UG25/U—Female type N chassis receptacle

101-A TWO-WIRE APPLIQUE



Provides necessary balancing facilities for four wire repeater when used on two wire lines which may be voice-frequency telephone lines of open wire, or non-loaded or loaded cable. Std. 19" channel iron rack mtg. Price, new, complete with tech manual, \$54.00

EE-89A REPEATER

BC 686 LINE AMPLIFIER

With magneto ringer, 3-tube 25L6 amplifier. For local point-to-point telephone operation, remote operation of Phone Emtr. remove reception of receiver output, monitoring facility. Requires only 24 vdc for tube "B" plus supply for full operation.

U. S. Army red and white star cluster flares, with cartridges. Types M52-A1 and M-18-A1. New, export packed in wooden carrying cases. 60,000 available.

131-E

ALL MERCHANDISE GUARANTEED. MAIL ORDERS PROMPTLY FILLED. ALL PRICES, F.O.B. NEW YORK CITY. SEND MONEY ORDER OR CHECK. SHIPPING CHARGES SENT C.O.D. RATED CONCERNS SEND P. O.

Liberty St. New York, N.Y. COMMUNICATIONS EQUIPMENT CO.

Cable "Comsupo" Ph. Digby 9-4124 MR. CHAS. ROSEN

SEARCHLIGHT SECTION

RELAYS MANUFACTURERS QUANTITIES

11 12 11 11 11 11 11 14 44 44 44 44 44 44	Stock No. 38TBD4 173-1 180-1 382T-1 382T-1 382T-1 3320T-2 68-800-1 352T-1 352T-1 352T-1 3166T-1 38T-2A 243-T-1 619T-2 1115T-1 61711T1 17T-2 116T-7 640T-1	Contacts DPDT (8 amp) SPDT 3PDT 1PDT, SPST (NO) DPDT, SPST (NO) DPST (NO) DPST (NO) 3PDT 3PDT (NO) 3PDT 3PDT (10 amps) DPDT 3PDT (NO) 2PST (NO) 3PDT (NO) 3PDT (NO) 3PDT (NO) 3PDT (NO) 3PDT (10 amps) DPDT DPDT DPDT DPDT DPDT DPDT DPDT DPD	Coil Rating 24-28 vde 28 vde 24-28 vde 24 vde 12-28 vde 22-28 vde 24 vde 24-28 vde 24-28 vde 24-28 vde 24-28 vde 24-28 vde 12-28 vde 21-28 vde 21-28 vde 21-28 vde 21-28 vde 22-28 vde 21-28 vde 21-28 vde 22 vde 10-14 vde 12 vde 10-12 v, 60 cy. 27.5 vde 9-14 vde	Coil Res. (Ohms) 170 ohms 1775 1870 1440 160 ohms 250 250 250 250 250 260 260 125	Mfr. & No. G.E.: CR2791B100F3 G.E.: CR2791B100F3 G.E.: CR2791B100C8 G.E.: CR2791B100C8 G.E.: CR2791B100X3 G.E.: CR2791G100K Leach: 1067-900 (antenna relay) Leach: 1067-90 (antenna re
8	38T-1-6 W46831	DPDT SPDT	24 v, 60 cy. 24 vdc	50 ohms	Allied G.E.: CR2791C104B28 (high speed
•			MINIATURE	RELAYS	The state of the s
2 4 4 1 2 4 6	608T-1 469T-1 117T-1 112TT-2 452T-1 95T-1 116T-A 90T-1 116T-6 121T-1	4PST (NO) 8PDT 8PDT DPDT DPDT DPDT DPST (NO) 8PDT 8PDT 8PDT 8PDT 8PDT	24-28 vdc 22-28 vdc 24-28 vdc 24-28 vdc 24-28 vdc 24-28 vdc 24-28 vdc 24-28 vdc 24-28 vdc 24-28 vdc 24-28 vdc	300 ohms 300 300 300 300 300 300 300 300 300	Clare: A16280 Clare: BA10059-3 Phileo: 452-1086 Phileo: 452-1148 Am. Tot.: A-8045 Allied: CA-5 Allied: C-C4 Phileo: 452-12 98 Phileo: 452-1086
		*ARC-3 E	QUIPMENT M	MINIATURE	RELAYS
	142R 83R 126-R 167R 149R 927T-4	SPDT, DPST 6PST (NO) SPST DPDT, DPST (NO) SPDT, SPST (NO) SPDT	28 vde 22-28 vde 22-28 vde 22-28 vde 22-28 vde 24-28 vde	300 ohms 300 300 300 300 300 300	RBM 55342 RBM 55251 RBM 55251 RBM 5531 RBM 55316 RBM 55826 RBM 55836

CADACITORS

BAT	HTUB CA	PACITORS
Stock No. 3DA100-2311	Mfr. & No. #16-NBN	Description 3 X .1 MFD @ 400
3DKA-100-169	¥10-1(D1)	VDC-Top Lugs
18B-95		VDC-Top Lugs
3DA-100-126-8		VDC-Top Lugs 3 X .1 MFD @ 600
18B83		V-Side Lugs 2 X .1 MFD @ 600
3DA-100-110		VDC Side Lugs 2 X .1 MFD @ 600
		VDC. Dot Ince
3DA-500-373		Side Lugs
3DA 500-87		VDC*-Side Lugs 2 X 1 MFD @ 600 VDC-Side Lugs 2 X 1 MFD @ 600 VDC-3 Side Lugs
18B-84		VDC-Side Lugs
46-1951T-9		2 X .1 MFD @ 600 VDC-3 Side Lugs CP50B4EF104V
2C4229-2	1574	2 X .1 MFD-2 Bot. Lugs
46-1311-107	P9728	2 X .1 MFD-2 Bot. Lugs 3 X .1 MFD @ 600 VDC-3 Bot. Lugs-CSF-
3DA-250-172		VDC-SIde Lugs 2 X .25 MFD @ 400 VDC-Side Lugs 3 X .1 MFD @ 600 VDC-Top Lugs 2 MFD @ 400 WVDC-2
3DA-100-423		3 X .1 MFD @ 600
1951 T- 5	£ 9453	2 MFD @ 400 WVDC-2
46-1951T-18		Side Lugs 3 X .1 MFD @ 400 VDC-3 Side Lugs CP50B5EE104B
4180T-2	430TR11	.1 MF @ 400 VDC-2
46-1951Т-6		11V 2 X .1 MF @ 600 VDC-3 Top Lugs
45B-4		.1 MFD @ 600 VDC-
3DA250-29		Side Lugs .25 MFD @ 600 VDC-
3DA100-97-27	RLO-650	Top Lugs .5 MFD @ 600 VDC-2
3DA-500-292		Side Luga .5 MFD @ 120 VDC-2
18B-97		Top Lugs 1 MFD @ 600 VDC-1
3D275		Side Lug 4 MFD @ 50 VDC-2 Side Lugs
3DA-1-230-1	230 M	1 MFD @ 400 VDC-1
18B-44		Side Lug 3 X 1 MFD @ 600
		VDC-3 Bot. Lugs CP52B5EF104M
0-0000	8A31231-C2	.5 MFD @ 200 VDC-2 Side Lugs
1W10540-2	CSF481391- 10	Side Lugs .05 MFD @ 600 VDC- 2 Top Lugs .5 MFD @ 600 VDC-2
3DA500-30		Side Luks
	630 R08-C	2 X .25 @ 600 VDC-3 Side Lugs
18B-60		Side Lugs 3 X .1 MFD @ 600 VDC Side Lugs
3DA100-42	DYRT-6111	CGF4B713B10 3 X .1 MFD @ 600 VDC-3 Top Lugs
3DB1A25-2 46-1081-1		VDC Side Lugs CGF4B713B10 3 X 1 MFD @ 600 VDC-3 Top Lugs 1.25 MFD-100 VDC 2 X 0.1 MFD-600 WVDC-3 Bot. Lugs CP52B4EF104

HEADSET PLUGS and JACKS PL-54 JK-26 **PLUGS**

*M'F'G'S QUANTITIES AVAILABLE

*OIL CAPACITORS

23F230G3 .55, 300 vdc, CG48328, P7765502-2 bot. lugs
5204555 .55, 300 vdc, Navy type CG48775, K787028 bot. lugs
231F218 0.25 mfd-1000 vdc-bot, lugs
23F298 .05 mfd-1000 vdc, P7767499-10, bot. lugs
23F114 0.5 mfd-500 vdc, CG481334, P7763475-4, bot. lugs
23F296 0.5 mfd-500 vdc, P7767499-4, bot, lugs
23F241 0.05mfd-600 vdc-top lugs
23F215 1.0 mfd-500 vdc, CG481854-10, top lugs
25F688 .55 mfd-490 vdc, CG481161, P720555-3
25F86 .05 mfd-1000 vdc, Navy type CG481333,
P7763475P10, bot. lugs
25F690 .5 mfd-600 vdc, CG481160, P720555-8
23F287EBK .25 mfd-600 vdc, K56J1888-11
25F689 .1mfd-400 vdc. P720555-7
9CEAGA4 1 mfd-500 vdc, Navy type, CG48553, P7763475-P5-top lugs
25F691 0075, bfd-500 vdc, CG48796, P720555-15
25F687 1 mfd-400 vdc, CG48595A, P720555-2
23F115 1 mfd-500 vdc, CG481190, 127763475-6, P721478-6
23F154 1 mfd-500 vdc-top lugs
23F210 1 mfd-500 vdc-CG48129-10, K44J334-2-top lugs
23F207G-3 1 mfd-500 vdc, P7767437-2-bot. lugs
25F790EBK .1 mfd-500 vdc, NP105168BU-top lugs
26F52 1 mfd-500 vdc, top lugs
231F211 1 mfd-500 vdc, G481852-10, NP94506E, K44J34-1-bot, lugs

CERAMICON CONDENSERS \$7.50 per 100

$\begin{array}{cccccccccccccccccccccccccccccccccccc$	5%
1 mmf +5 mmf 115 mmf +	20%
8.5 mmf±5 mmf 120 mmf±	5%
11 mmf±5% 240 mmf±	
15 mmf±2.5 mmf 250 mmf	
48 mmf±2% 500 mmf+15 —3	
50 mmf±20% 1000 mmf±	5%
60 mmf +3%	

*Silver-Mico Button Capacitors (Erie, Centralab) \$9.50 per 100

185 mmf	<u>±2.5 mmf</u>
	±2.5 mmf
500 mmf	±10%

*ELECTROLYTICS CAPACITORS

1986T-2 46-1814T-2		25-25 mfd-50 wvde 20 mfd-25 vdc, K-7104527
46-1909	D1223	30 mfd-50 vdc, f2C6494A/C6
W-173-A		2500 mfd-3 vdc 2 x 40 mfd-150 vdc, 20 mfd-25 wvoctal plug-in



LEAR AVIATION POWER UNITS

4 vdc drive, 90:1 gear ratio, High power. Origi-nally designed for landing gear retraction. Bleycle type sprocket for multi-purpose drive Large quan-tity available....\$16.50

*OIL CAPACITORS (STANDARD BRANDS)

	317110710	DRAITD3)
Stock No. 46-1384T-1	#25F649	Description 0.5 mfd-2,000 vac, 180 cy, 2 standoffs (M 7471333-1) 5" x 4\frac{1}{2}" x 3\frac{1}{2}" 0.2 mfd-10 kvdc-(CG-12)
13036 T-2	26F433	5" x 4 1" y 3 1" 0.2 mfd-10 kvdc-(CG
W-46988-1	CA255	0.2 mfd-10 kvdc-(CG-481703) 3 x 0.1 mfd-600 vdc-1 bot. lugs, 1 * x 2 * L 1
W-2381-"17"		
2864TA-1	AX-1089	2.0 mfd-@ 600 vdc-bot lugs, rd. cam 2" dlam 3 3½" H./w/mtg. bracke 3 x 0.5 mfd-500 vdc B34584 rect. can, w/mt bracket-3 top lugs, 2½"H x 1½" sq. 0.5 mfd-600 vdc
C5E66	XEM	bracket-3 top lugs, 21°H x 11° 8q. 0.5 mfd-600 vdc XEMRBW6, CSL. 481921-10, KS8545/M-2- bot. lugs w/mtg. brack 11° x 1° x 1° 1 mf @ 10.000 vdc CP70D1FS104K
		481921-10, KS8545/M-2, bot. lugs w/mtg, brack lif x lif x if 10.000 vdc CP70D1FS104K .005 x .005 x .01 mf @
	14F191	.1 mf @ 10,000 vde
	26F344	.005 x .005 x .01 mf @
	25F585-G2 25F774 23F299	.06 mf @ 15 kv
2265-12	23F299	1 mf @ 10.000 vde CP70D1FS104K .005 x .005 x .01 mf @ 10 kvde .06 mf @ 15 kv .1 x .1 @ 7000 vde 1 mtd-500 vde-upside down-2 lugs, 2" H x 14"
C-5D-46	616MB	0.1 mfd-600 vdc-2-bot-
C-5K-8	618CT	2 x 0.5 mfd-KS-8545-up. down mtg3 top lugs
C5D-4-6	616M	0.1 mfd-600 vdc-2 bot.
46-815 "E"		.06 mf @ 15 kv .1 x 1. @ 7000 vdc 1 mfd-500 vdc-upsid down-2 lugs, 2" H x 14" W x 1" W 0.1 mfd-600 vdc-2-bot tom lugs, 11" x 1" x 1" 2 x 0.5 mfd-K8-8545-up down mtg3 top lugs 31" x 11" x 1" 0.25 mfd-400 vdc-2 cRV481176, P720555, 1" x 11" x 1" 0.25 mfd-400 vdc, CRV481176, P720555, 1" x 11" x 1" 1.0 mfd-1500 vdc, 224365 SO1, 4" x 11" x 1" 1.75 mfd-400 vdc, 31" x 11" x 1" 0.5 mfd-1000 vdc, 27" x 0.75 mfd-1000 vdc, CP70E1FG504K, 21" x
3DA50-32 46-167T-30	∮5414 ∮2009M	3 x .05-300 vdc 0.5 mfd-1500 vdc, 224365
2281T-1	7030-19A	1.0 mfd-1500 vde, 4 x
14B-282		1.75 mfd-400 vdc, 31" x
13772T-1	€2ZF41	0.5 mfd-1000 vdc, CP70E1FG504K, 21" x
W-775		1.75 mfd-400 vdc, 3!" x (5.5 mfd-1000 vdc, CP70E1FG504K, 2!" x 1!" x 1" z x 2 x 2 mfd-500 vdc, 4 top lugs, 3!" x 2!" x 1 y" x 2 mfd-100 vdc, 1 20%, K7106152-P2, 3!" x 1!" x 1!" x 1"
		lugs, 31" x 21" x 11" 2 mfd-1000 vdc, I 20%, K7106152-P2, 31" x 11" 2 x 2 mfd-600 vdc, 3 4"
	(Vit. "Q")	2 x 2 mfd-600 vdc, 3 A" x 2 1 " x 1 1 "
46-167T-44	RYS	
829 "C" 13759T-5	PO2 25F805	2.0 mfd CA-59 1.0 mfd, 400 cy., @ 250 vac, 21" x 2" x 1"
	8A106494	2 x 0.5 mfd-1000 vdc.
8032-''D''	8A106495	2 mtd-600 vde, \$105095- x1? x1? x1? x1? x1? x1? x1? 2.0 mtd CA-59 1.0 mtd, 400 cy., @ 250 vac, 2; x2 x1? 2 x 0.5 mtd-1000 vdc, 2; x1; x1; 2 mtd-600 vdc, 1; dam. x2; x2; x2; dam.
47-167-43	2509M	2 mfd-600 vde, 1}" dlam. x 3" mfd-2500 vde, CP70E1EK104K, 2!" x 2!" x 1!" 2.0 mfd-600 vde, 1!"
46-582T-2	Co.6GA200	2 % x 1 % 2.0 mfd-600 vdc, 1 %
W-444 "F"	AX-	3 x .67 mfd-90 vac-3 lugs.
3DA250-207	1D69MSB 55908	2% X1" 2.0 mfd-600 vdc, 1;" diam. x 3" L 3 x. 67 mfd-90 vac-3 lugs, 3" x 2;" x 1;" 0.25 mfd @ 400 vdc, up- right, tubuler ;" dia. x 2" L
46-1308-T6	RO3	2.0 mfd-600 vde,
47-167 T -11	25F813	CA W 48777, 27" Y 17" x 1" 2 x .1 mfd-4800 vdc, type EB-K, Sperry PT 4701248, 5" x 31" x 11"
		27 L 27 L 20 mfd-600 vde, CAW48777. 2½* x 1½* x 1½* x 1° 2 x .1 mfd-4800 vde, type EB-K, Sperry pr 7701248. 5" x 3½* x 1½* 2 x .125 mfd-400 vde, CRV1167. P72055-P5 1 mfd-400 vde, CRV487896-10, 720555-P6 1 mfd-400 vde, CRV487896-10, 720555-55-56 1 mfd-400vde, CRV485v5- A, 720555-2² x .5 mfd-400 vde, 86072501
W		2 x .5 mfd-400 vdc, 86072501
Wash 13713"A' Wash 2342 P	}	4 mfd-25 vdc, 4 mfd @ 200 vdc, Navy type-CD 48773, 31" x 21" x 11" 0.1 mfd-6000 vdc,
13752T-13	# 25F509G2	CG481941-10. 34" x 34"
46-167- T-7 6	2009	x 11" 0.5 mfd-1500 vde

*MICA CAPACITORS

46-2010T-1	1860-500 Fil.
D-6343	Fil.
46-1951 T-1 2	type 1
46-3215T-1 46-1951-T-7	F2L
46-1534T-1	type 16

25 mmf @ 10 kvdc .0016 mfd-3000 v.-up-right lugs-2 mfg. holes 90 mmf-3000 v. upri gh lugs-2 mfg. holes 0.000047 mfd-2500 v. wkg. CM55A4 70 M. thread. connections .0004 mfd-6 kv. wkg. 0.01 mfd-500 w.v. Post stamps type-w lugs 90 mmf-3000 w.v.-2 amps @ 3000 KC-upright

Digby 9-4124

151 Liberty St., New York, N.Y.

COMMUNICATIONS EQUIPMENT CO.

Build YOUR OWN TEST EQUIPMENT

Heathkit ELECTRONIC SWITCH KIT DOUBLES THE UTILITY OF ANY SCOPE

\$3450

Gives two separately controllable fraces with Individual inputs on any scope. See both the input and output traces, locate

distortion, phase shift, etc., immediately. Individual gain controls and positioning control. Coarse and fine sweeping rate cantrols. Complete Heathkit matches others, with 5 tubes, All metal parts are punched, formed and cadmium plated. Complete with tubes, all parts, detailed blueprints and instructions. Shipping Wt. 13 lbs.

Nothing ELSE TO BUY

HEATHKIT CONDENSER CHECKER KIT

5 0 50

Nothing ELSE TO BUY



A condenser checker anyone can afford to own. Measures capacity and leakage from .00001 to 1000 MFD on calibrated scales with test voltage up to 500 volts. No need for tables or multipliers. Reads resistance 500 ohms to 2 megahms. 110V 60 cycle transformer operated complete with rectifier and magic eye indicator tubes.

Eosy, quick assembly with clear detailed blueprints and instructions. Small convenient size 9" x 6" x 43/4". Wt. 4 lbs.

HEATHKIT SIGNAL GENERATOR KIT



NOTHING ELSE TO BUY

Every shop needs a good signal generator. The Heathkit fulfills every servicing need, fundamentals from 150 Kc, to 30 megacycles with strong harmonics over 100 megacycles covering the new television and FM bands, 110V 60 cycle transformer operated power supply

400 cycle audio available for 30% modulation or audio testing. Uses 6SN7 as RF oscillator and audio amplifier. Complete kit has every part necessary and detailed blueprints and instructions enable the builder to assemble it in a few hours. Large easy to read calibration. Convenient size 9" x 6" x 4¾". Wt, 4½ lbs.

HEATHKIT SIGNAL TRACER KIT



Nothing ELSE TO BUY

RACER KIT

Reduces service time and greatly increases profits of any service shop. Uses crystal diode to follow signal from antenna to speaker. Locates faults immediately. Internal amplifier available for speaker testing and internal speaker available for amplifier testing. Connection for VTVM on panel allows visual tracing and gain measurements. Also tests phonograph pickups, microphones, PA systems, etc. Frequency range to 200 Mc. Complete ready to assemble. 110V 60 cycle transformer operated. Supplied with 3 tubes, diode probe, 2 color panel, all other parts. Easy to assemble, detailed blueprints and instructions.

Small portable 9" x 6" x 4¾4". Wt. 6 pounds. Ideal for taking on service calls. Complete your service shop with this instrument.

HEATHKIT SINE AND SQUARE WAVE AUDIO GENERATOR KIT

The ideal instrument for checking audio amplifiers, television response, distortion, etc. Supplies excellent sine wave 20 cycles to 20,000 cycles and in addition supplies square wave over same range. Extremely low distortion, less than 1%, large calibrated dial, beautiful 2 color panel, 1% precision calibrating resistors, 110 V 60 cycle power transformer, 5 tubes, detailed blueprints and instructions. R.C. type circuit with excellent stability. Shipping weight 15 pounds.



Nothing ELSE TO BUY

THE NEW HEATHKIT VACUUM TUBE VOLTMETER KIT

The most essential tool a radio man can have, naw within the reach of his pocketbook. The Heath-The most essential tool a radio man can have, now within the reach of his pocketbook. The Heathkit VTVM is equal in quality to instruments selling for \$75.00 or more. Features 500 microamp meter, transformer power supply, 1% glass enclosed divider resistors, ceramic selector switches, 11 megohms input resistance, linear AC and DC scale, electronic AC reading RMS. Circuit uses 65N7 in balanced bridge circuit, a 6H6 as AC rectifier and 6 x 5 os transformer power supply rectifier. Included is means of calibrating without standards. Average assembly time less than four pleasant hours and you have the most useful test instrument you will ever own. Ranges 0-3, 30, 100, 300, 1000 volts AC and DC. Ohmmeter hos ranges of scale times 1, 100, 1000, 10M and 1 megohm, giving range .1 ohm to 1000 megohms. Complete with detailed instructions. Add postage for 8 lbs.



2450 Nothing ELSE TO BUY

HEATHKIT FM AND TELEVISION SWEEP GENERATOR KIT



NOTHING ELSE TO BUY

THE BASIC FM AND TELEVISION SERVICE INSTRUMENT

At the lowest cost possible, anyone can now Ar the lowest cost possible, anyone can have service FM and television receivers. The Heathkit sweep generator kit operates with oscilloscope and covers all necessary frequencies. A few pleasant hours assembling this kit puts any organization in position to share the profits of the FM and TV boom

Every part supplied — grey crackle cabinet, two color calibrated panel, all metal parts punched, formed and plated. 5 tubes, complete detailed instructions for assembly and use. Shipping weight 6 lbs.

The NEW 1948 HEATHKIT 5 INCH OSCILLOSCOPE KIT



NOTHING ELSE TO BUY

New improved model of the famous Heathkit Oscilloscope, Building an oscilloscope is the finest training for television and newer servicing technique and you save two-thirds the cost. All the features and quality of instruments selling for \$100.00 or more. Supplied complete with cabinet, two color panel. 5BP1 tube, 2 5Y3 tubes, 2 6SJ7

tubes and 884 sweep generator tube. Power transformer supplies 1000V negative and 350 volt positive. Sweep generator 15 cycles to 30 M. cycles. Has vertical and horizontal amplifiers. Oil filled filter condensers for long life. Complete blueprints and instructions included,



QUANTLTIES LIMITED SUBJECT TO PRIOR SAL

APN/1 RADIO ALTIMETERS




NO. 200. The last chance to get a complete new 14 toget a complete new 14 toget and receiver, power supply, range switches, two antennas, meter indicator, and interesting and interesting and interesting the second secon antennas, meter indicator, all plugs and instruction manual. This unit makes excellent amateur station as it is right in the band. Shipped in original export crate. Weight 87 lbs.

G.E. BC 375 TUNING UNIT

NO. 203. Model TU10B covers
10 Mc. to 12.5 Mc. New complete with aluminum cabinet.
The best buy of surplus. Over
\$30.00 worth of new variable
condensers, coil, dials, switches, etc. Add postage for 20 lbs.



\$2.49

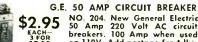

\$2.95
NO. 204. New General Electric
50 Amp 220 Volt AC circuit
breakers. 100 Amp when used
on 110V. Add postage for 4 lbs.

BC 347 AIRCRAFT INTERPHONE

AMPLIFIER

NO. 205. Interphone amplifier contains 6F8 tube, Ouncer transformers, diagrams, etc. in aluminum cabinet. Add postage for 4 lbs. \$2.95





274N COMMAND SET ACCESSORIES



NO. 238. 5" PM Speaker with output transformer matching head-NO. 240. Single transmitter rack NO. 259. Single transmitter rack NO. 240. Single transmitter rack S1.00

NO. 241. Spline shaft for use of regular tuning knob on BC 453-4-5 receivers \$.39



BC 451 CONTROL BOX
NO. 236. Control box for 274N
transmitters. Contains proper cwvoice switch, 4 channel switch,
power switch, mike jack and tele-

graph key. Add postage for 2 lbs......\$1.95

METER SPECIAL
NO. 237. Brand new DeJur Model
312 0-800 M.A. D.C. Square 3" 0-10
M.A. basic meter with built in
shunt. Probably the best buy ever
offered in a surplus meter. \$2.95



A-62 ARMY PHANTOM ANTENNA



NO. 206. Contains tuning condenser, coil, resistors, tuning dial, tuning indicator, binding posts, steel case, useful for building amateur tronsmitter. Add postage \$1.95

BENDIX MR9C COMPASS CONTROL UNIT

NO. 207. Tuning and control unit for Bendix MN 26 radio compasses contains tuning dial, band switch, crystal switch, AVC switch, volume control, fuses, phone jacks, \$9.50 etc. Shipping Weight 5 lbs.



BC731 CONTROL BOX

with Weston Model 476 AC Voltmeter NO. 208. Excellent buy in motor control box. Size 8"x10"x5½". Contains Weston 0-150V. AC 3½" voltmeter, motor starting switch, 28 fuses all 30 Amp 110V. and 8 fuse holders. Fuses and holders alone worth the price. \$7.95

BC 645 GENERAL ELECTRIC **TRANSCEIVER**



NO. 201. Complete 15 tube transmitter-receiver. Ideal for new citizens band 460 Mc. for commu-nication between of-

fice and car, home, boat, etc. Conver-sion article in August ELECTRONICS Magazine, Brand new in original G.E. with tubes. Add postage for 25 lbs. cartons

.50 . . . 2 for \$35.00 ACCESSORIES FOR BC 645 \$19.50

PE101C Dynamator for car use \$\ 3.95 110V 60 Cycle Power Supply for home or office use \$\ \$14.50

T32 TABLE MICROPHONE

NO. 210. One of the Army's best.
Built by Kellogg, ideal for factory
call system, public address, amateur
use. Brand new in original cartons.
Add postage for 5 lbs.
\$2.95

MINIATURE ELECTRIC MOTOR

NO. 211. Tiny Delco motor only 1" x 11/4"x2" 10,000 RPM. Operates from 6 to 24 V. Excellent for models. Add postage for 1 lb. \$2.95

P. E. 103 DYNAMOTOR

NO. 212. Dynamotor only from PE 103 power supply. Input 6 or 12 Volts, output 500 Volts at 160 MA. Brand new original cartons. Ship-ping Weight 29 lbs.



G. E. 1,000

G. E. 1,000
VOLT 330 MA DYNAMOTOR
NO. 213. An ideal dynamotor for mobile operation in taxicabs, police cars, sound systems and amateur stations. Supplies above voltage from 12 Volts or 500V. at 350 MA from 6 Volts. Complete with starting relay, and fuses. New. Our Dynamotor A. Shipping Weight 72 lbs.

DM-36 DYNAMOTOR

NO. 215. Western Electric 24 Volt input, 220V. at 60 MA out. With filter assembly. \$2.95 Shipping Weight 6 lbs.



G.E. BC 306 ANTENNA TUNING UNIT

NO. 231. Matches any aerial to 150 Watt transmitter, used on BC 375. Brand new. Add postage for 20 lbs. \$2.95

W.E. BC456 MODULATOR

NO. 217. Modulator from 274N command transmitters contains 3 husky relays, 3 tubes, VR150, 1215 and 1625.
Brand new. Add postage for 11 lbs. \$3.95



BE 77 TELETYPE TEST SET

NO. 218. Contains zero center volt-milliammeter, switches, relays, voltage divider resistors, neon indicator, etc.

\$7.95

Excellent foundation for radio tester.
Shipping Weight 10 lbs.

BENDIX MN 20E DIRECTION FINDER LOOP

NO. 219. Ring type loop excellent for use on boat or aircraft. Extreme-ly rugged construction. Low im-pedance manual type. \$9.95 EACH Add postage for 8 lbs. \$9.95 EACH

LP 18C DIRECTION FINDER LOOP



NO. 220. Motor driven streamline pod type loop used on automatic direction finders. Has Selsyn transmitter and motor, fits most military direction finders. Add postage for 20 lbs. \$14.50 EACH

KIT SPECIALS

POTENTIOMETERS NO. 232. Kit of 10 ex-cellent shaft type potentiometers \$1.95

SOCKETS NO. 233. Kit of 20 high quality sockets several different \$1.00 \$1.00 types.

RCA NAVY COMMUNICATION RECEIVER

NO. 202. The last of these beautiful RCA sets. Covers 195 Kc. to 9.1 Mc. continuously. Supplied complete with tubes, control box, tuning unit, 24 Volt dynamotor, band circuit diagram. Superheterodyne circuit covers aircraft, broadcast, short wave, marine, foreign broadcasts. Has sharp or braad 1.F.'s B.F.O., etc. Shpg. Wt. 30 lbs.



\$12.95

NO. 223. Operates from 12 to 24 Volts and supplies 500 Volts at 160 MA. Extremely rugged construction used in Army tanks. Complete with fuses — relays — filters, etc. Ideal for boots. Shipping Weight 73 lbs.

PE 125 TRANSMITTER

POWER SUPPLY

FM PUSH BUTTON TUNER

NO. 224. Brand new ten push button tuning assembly from Army FM receiver. Contains 4 gang 100 MMF silver plated tuning conden-\$2.50 EACH



RG 8/U FLEXIBLE

COAXIAL CABLE
NO. 225. Standard television lead
in 52 ohm. Any length up to 1,000 44 ft. Add for postage. PER FOOT

POWER TRANSFORMER Specials



NO. 226. Primary 117V. 60 cycle. Secondaries supply 746 V.CT at 220 MA. 6.3V. at 4.5 A., and 5V. at 4A. Will handle 13 tube radio receivers. Supply is limited, order early. Shipping Weight 11 lbs. each.
\$3.95...3 for \$9.95

OUTPUT TRANSFORMER

NO. 227. Push pull 6V6's to 6 - 8 ohm voice coil excellent 3 for \$1.95 characteristics.



TRANSMITTER TRANSFORMER

MILITARY POWER TRANSFORMERS

NO. 229. Convert your military receivers without rewiring the filament. "A" type supplies 500 VCT at 50 MA, 5V. at 2A. and 2V. at 1/2 A. "B" type supplies 500 VCT at 50 MA, 5V. at 2A. and 12V. at 1 Amp. State whether A ar B type desired. \$ 2.95 Shipping Weight 4 lbs.



HOME-WORKSHOP GRINDER KIT

NO. 230. Easily assembled 110V AC or DC ball bearing fully enclosed motor from Army surplus dynamotor. Purchaser to make simple changes and shaft extensions, detailed instructions and all parts supplied. Motor approximately 5,000 R.P.M. Ideal for tool-post grinder, flexible shaft tool, model drill press, saw. Shipping Weight 6 lbs.



\$3.95

HEARING AID HEADPHONES NO. 216. The Army's best — eliminate flat ears and outside noise. Complete with transformer for conversion from low to high impedance. With cord and plug complete. \$1.00 Add postage for 1 lb....

TELEVISION CONDENSERS

NO. 221. Tobe triple .2 MFD 4000 V.D.C. Filter used on Army radar. Ideal filter for H.V. television set. Add postage for 3 lbs. \$3,95


No. 222. Capacitor .25 MFD 6000 V.D.C. Porcelain insulated, an outstanding buy for high voltage filters. Add postage for \$3.95

HOW TO ORDER . . . GIVE PART NUMBER AND DESCRIPTION ... ADD POSTAGE FOR



MDAI 0

DEPT. E . . . BENTON HARBOR, MICHIGAN

 

SEARCHLIGHT SECTION IP

RADIOMEN'S HEADQUARTERS 💥 WORLD WIDE MAIL ORDER SERVICE []



GENERAL ELECTRIC RT-1248 15-TUBE TRANSMITTER-RECEIVER

GENERAL ELECTRIC RT-1248 15-TUBE TRANSMITTER-RECEIVER

TERRIFIC POWER—(20 watts) on any two instantly selected, easily pre-adjusted frequencies from 435 to 500 Mc. Transmitter uses 5 tubes including Western Electric 316 A as final. Receiver uses 10 tubes including 955's, as first detector and oscillator, and 3—717's as 1F's with a 4 slug-tuned 40 Mc. IF transformers, plus a 7117, TB6's and 7F7's. In addition unit contains 8 relays designed to operate any sort of external equipment when actuated by a received signal from a similar set elsewhere. Originally designed for 12 volt operation, power supply is not included, as it is a cinch for any experimenter to connect this unit for 110 AC, using any supply capable of 400 DC at 135 FA. The ideal unit for use in mobile or stationary service in the Citizen's Radio Telephone Band where no license is necessary. Instructions and diagrams supplied for running the RT-1248 transmitter on either code or voice in AM or FM transmission or reception, for use as a mobile public address system, on 80 to 110 Mc, as an FM broadcast receiver, as a Facsimile transmitter or receiver, as an Amateur Television transmitter or receiver for remote control relay hookups, for Geiger-Mueller counter applications. It sells for only \$29.95 or two for \$53.90. If desired for marine or mobile use the dynamotor which will work on either 12 or 24V DC and supply all power for the set is only \$15.00 additional.

BRAND NEW


BC-221 FREQUENCY METERS with calibrating Crystal and calibration charts. A precision frequency standard that is useful for innumerable applications for laboratory technician. service man, amateur, and experimenter at the give away price of only \$75.00.




BUFFALO RADIO SUPPLY, ONE OF AMERICA'S LARGEST ELECTRONIC DISTRIBUTORS, IS IN A POSITION TO SUPPLY MOST OF THE REQUIREMENTS OF FOREIGN PURCHASERS, DIRECTLY FROM ITS GIGANTIC STOCKS OR THOSE OF ITS AFFILIATES. EXPORT INQUIRIES ARE SOLICITED BOTH FROM EXPORT HOUSES AND FROM FOREIGN GOVT. PURCHASING COMMISSIONS HERE AND ABROAD. EXPENSE

CAN BE REDUCED AND REQUIRE-MENTS FILLED WITH A MINIMUM OF DELAY BY CONTACTING BUF-FALO RADIO SUPPLY INITIALLY.

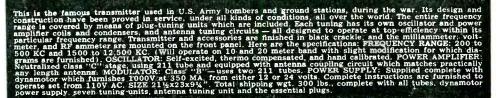GENERAL ELECTRIC 150 WATT TRANSMITTER Cost the Government \$1800.00 • Cost to You — BRAND NEW — \$100.00



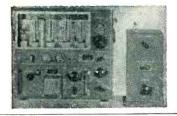

SCR-274N COMMAND SET

The greatest radio equipment value in history A mountain of valuable equipment that includes 3 receivers that use plug-in coils, and consequently can be changed to any frequencies desired without conversion. Also included are two Tuning Control Boxes; 1 Antenna Coupling Box; four 28V Dynamotors (easily converted to 110V. operation); two 40-Watt Transmitters including crystals, and Preamplifier and Modulator. 29 tubes supplied in all. Only a limited quantity available, so get your order in fast. Removed from unused aircraft and in guaranteed electrical condition. A super value at \$34.95, including crank type tuning knobs for receivers.

RT-1655—11 tube crystal controlled superheter-odyne receiver that covers the FM band. The ultra modern circuit uses the latest types of tubes including 7 miniature 6AJ5's. Beautiful chassis and aluminum cabinet. Tubes and schematic supplied.—\$14.95

World renowned 700 page tenth edition of the Radio Handbook in cloth binding and hard cover at the sensational reduced price, for a limited time only, \$1.49

(1) अ स्तु अर 1000 B 6 7.5

RADAGER* *Combination Autoradio-Battery charger Nationally advertised brand 1949 car radio, fits practically any car. Have plenty of eye appeal plus other features that no other radio regardless of cost can offer. Built in battery charger that will charge a car battery. Unique circuit of radio steps up the 6v input to 110v, that is available in a convenient outlet, for operation of an electric shaver or similar electrical appliance. Radio is a powerful of tube superheterodyne with a 3 gang condenser and stage of radio frequency amplification for increased sensitivity. Radio, complete with built in battery charger and power outlet, is a single compact unit easily installed. Sample—\$39.95; Dealer price, \$37.47—each in lots of 2 or more.

RADAGER* *Combination Auto radio-Battery charger

RADIO SET SCOOP. Product of a famous of the control of the control of the control of the control of the fload of recent govt orders. All in 5 ply genuine managany cabinets both regular and bleached 6 tube models have tone control. Original list price given first—then your cost. Sensational discounts.

Model 612X, Walnut. Model 613X, Mah...

\$595 Takes Both **BIG BARGAINS**

ALUMINUM GEAR BOX 18x8x7 that contions. Per matched pair\$4.95

RT 1463 7 tube amplifiers containing 3—7F7, 1—7Y4, 3—7N7, 4 potentiometers, numerous resistors, filter and bypass condensers, filter chokes, power and audio transformers, and six sensitive plate relays. A military development that provided amazing stepless control proportional to correction required for allerons, rudder and elevator, in the original application. A control amplifier of the ordinary type would deflect the rudder by some arbitrary amount when the ship was blown off the course to port or starboard. The result would either be that the correction was insufficient and the plane continued off course, or the correction would be too great, starting a series of tackings and would greatly increase fuel consumption and elapsed time in reaching the objective. This phenomenal unit, with its 3 amplifiers and six 5000 ohm, relays in bridge circuits, will accurately control any 3 operations, related or unrelated, in minutely adjustable uniquely quantitative variations in either forward or reverse directions, 9"x7"x8" black crackle aluminum case. Brand new in original carton, \$12.95, or used \$9.95. in either forward or or used \$9.95.



VACUUM TUBE VOLT-OHM-CAPACITY METER

There are more features engineered into this all purpose instrument than in any other instrument on the market regardless of price. It was designed not only to meet present ociditions but to be readily adaptable to future needs. At the sensationally low price of this precision instrument no school, plant, lab or service shop need deprive itself of the "now look" in measuring equipment. Here are a few of the many features of this outstanding meter:

• 5 inch easy to read meter.

• 5 DC voltage ranges from 0 to 1000 V (Input resistance as high as I megohm pr volt.)

• 5 AC voltage ranges from 0 to 1000 V (No dry disc rectifier to age and destroy the accuracy of this VACUUM TUBE VOLTMETER).

• 6 Resistance ranges from 2/10 ohm to 1000 megohms.

• 4 Capacity ranges from 2/10 ohm to 1000 megohms.

• 1 capacity ranges from 2/10 ohm to 1000 megohms.

• 1 solating resistor built into probe.

• Sturdy natural finish hard wood case.

This outstanding development of one of the leading manufacturers of test equipment costs only \$39.95 complete with all leads, as illustrated.

RT-1579 consists of a three stage, cascade 6817's and 6FG output stage high gain, high fidelity amplifier with 60 cycle, 110V power supply on the same 13\%\text{14\%} chassis, which is protected by a substantial steel cover over tubes and parts. Made by Western Electric with typical quality components such as a husky power transformer and oil condensers, this unit is obviously intended to give years of trouble-free service with no more need for repairs than a telephone. Disconnecting one wire each, from the special input and output filters, will result in as high a fidelity amplifier as can be obtained. Your cost with tubes, diagram and parts list included—314.95.

RT1711 Brand New 12 ube 150 Volt Receiver-Indicator-Oscilloscope complete with all tubes and power supply. Has hood over scope tubes, which is equipped with a detachable calibrated screen. Has centering and amplitude controls and two video imputs. A natural for television \$39.95

Cable Address: BUFRAD FOB BUFFALO UNLESS NOTED

Minimum order \$3.00—All prices subject to change—25% deposit with COD orders.

RADIO SUPPLY, 219-221 Genesee St., Dept. 9-E BUFFALO

SEARCHLIGHT SECTION

IN THE COUNTRY LARGEST STOCK OF TUBES

MINIMUM ORDER \$5.00 QUANTITY PRICES ON REQUEST

Туре	Price	Type	Price	Туре	Price	Type	Price	Туре	Price	Type	Price	Type	Price
	\$49.50	215A	3.00			KC4	105.00	2A4G	1.28	6S7	1.28	12SL7GT 12SN7GT	.88
1B24	4.95	217G	7.50 4.95	860	49.95	KU676 ML100	105.00	2A5	1.06	6S7G	1.28	12507	,60
1B27 1B56	4.95 8.00	218 221A		804	- 007	ML101	150.00	2A7	1.06	6SA7	.66	12SQ7GT	.60
1N21	59	222A	120.00	865 866A	2.98	ML502	300.00	2E5	.88	6SA7GT	.66	12SR7GT	.39
1N23	59	227A	3.95	868	1.95	MR4 QK59	39 50	2V3G 2X2A	1.98 1.25	6SD7GT	.72	12X3	
1P22 1P24		242C	5.95	86913	75,00	OK60 OK61	39.50	3.44	.39	6SF5	.66	1223	1.06
1S21	. 1.95	249G	3.49	872A	2.49	QK61	39.50	3A5 3A8GT	1 39	6SF5GT	.72	14A7/12B7 14AF7/XXD.	.88
2AP1 2B22	3.95 5.35	250R 250TH	$\frac{7.95}{19.50}$	876	.98	REL21	4.25	3137	. 36	68G7	.80	14B6	.88
2C22	39	250TL	19.50	878	2.49	RK12 RK21	1.95	3D6	.36	6SH7	.66	14B8	.88
2C26A	75	252A	4.95	879 884	1.49	RK22	4.95	304. 305GT	.88	6SJ7GT	.66	14C7	.88
2C34		274A	1.25	885	.70	KK25	2.75	354	.80	6SK7	. 66	14C7 14E6	.72 .88
2C43	7.50	274B	1.25	902P1 905	11 95	RK33 RK34	98	3V4	.80	6SK7GT 6SL7GT	.66	14E714F7	
2C44 2C46	7.50	282A	4.95	920	2.95	RK59	3.95	5R4GY	1.15	6SN7GT	. 88	14F8	1.06
2D21	. 1.09	304TH	6.95	923 931A		RK65	24.95	5'T4	1.28	6SQ7GT	.60	14H7 14J7	.88 1.06
2E22 2E24	1.50	304TL	1.49	931A	1.06	RK60	49.50	5V4G	.96	6SR7	.72	14N7	1.06
2E25	4.25	307A	4.95	95515	4.90	RK72	1.95	5W4. 5W4GT	1.06	6SR7GT	.72	1407 14R7	.88
2E26	. 3.95 2.49	310	4.95 1.98	954 955	4.95 .75 .75	RK73 RK75	3.95 6.25	5X4G	.66	6SS7	.66	1457	1.06
2E30		316A	.69	956	.75	RX120	10.00	5Y3GT	.42	6U5/6G5	.72	14W7	1.06
2J26	. 14.95	316A	120.00	957 958A	.75	TZ40 UX6653	2,45	5Y4G 5Z3	.60	6U7G	1.28	14X7 14X4	1.66
2J31		327 A	4.95	050	.75	V70D	6.95	574	1.06	6V6GT	.80	14Y4	.88
2J 33	. 24.95	338A	4 95	991. 1000 SPEC	.69 24.95	VR75 VR78	.98	6A3	1.28	6W7G	.88	19. 19 T 8	1.28 1.06
2.134	. 24.95	350/A/B 353A	2.95	10001	75.00	V K 90	.73	0A7	1.06	6X4 6X5GT	.60	22	1.28
2J37 2J38	. 37.50	368AS	4.95	1608	4.95	V KYI	1.47	0A8	.80	6Y6G	.96	24A 25A7GT	.88 1.16
2JB51	4.95	371A 371B	2.95 2.95	1611	.75	VR92 VR105	.75	6A8GT 6AB7 1853	1.06	6ZY5G 7A4/XXL	.88	25AC5GT	1.16
2J54 2K25	25.00 24.95	588A	1.90	1614	1.75	VR150	.98	6AC5GT	1.16	7A5	.72	25L6GT	.66
3AP1	4.95	393A	7.95	1616	.75	VR150 VT127A	3.00	6AC7 1852 6AD7G	1.16	7A6	.72 .72	25Y5 25Z5	1.16
3B22 3B23	4.95	394A	4.50	1621	1.98	WL460	14.95	6AG5	1.06	7A7	.72	25Z6GT	.60
31324	1.95	434A	3.95	1622 1624	1.75	WL468	14.95	0AG7	1.20	7AD7	1.06	26	.72
3B25	1.25	446A 450TH 503	1.95	1625	.49	W1.532A WL562	150.00	6AH6 6AJ5	.99	7AG7	.72 .88	27 28D7	.39
3BP1	3.95	503	195.00	1626 1627	7.95	WL616	105.00	6AK5	1.56	/An/	88	30	.39
3C21	. 5.95	527	12.95	1628	4.95	WL619	49.50 1.95	0AA0	.96	7B4	72	31	1.28
3C22 3C23		531 575A	24.50 14.95	1629	.69	0A2	1.69	6AL7GT	1.06	7B6	.72 .72 .72 .72	32L7GT	1.28
3C24	69	632A	9.95	1636	5.95	0A2 0A3/VR75	.98	6AQ5	.80	787	.72	33	
3C30 3CP1	1.50 3.00	701A	4.95	1658	. 70	0A4G 0B2	1.06 2.05	6AQ6 6AQ7GT	.88	7B8 7C4/1203A	.39	35/51	. 80
3BP1	3.95	703A	4.95	1641	.79	0B3 VR90	.75	6AR5	.66	7C5	.72	35A5	.72 .80
3EP1	3.95 4.95	704A	1.98	1644	1.49	0C3/VR105 0D3/VR150	.75	6AS5	.80	7C6	.72	35L6GT	. 66
3E29	3.95	705A	24 95	1654	1.98	OY4	88	6AT6	.80	7E5/1201	1.06	35W4	.46
4-65A	14.50	706CY 707A/B	24,95	1851	1.25	074	88	6AV6	1.60	7E6	.72	35Y4	.72 .72 .60
4-125A 4-250A	27.50 37.50	707A/B	7.95	1852	1.00	0Z4G		6B4G	1.28	7E7	.88	35Z4GT	.60
4A1	1.98	709A	. 9.95	1853	.95	1 1 3	.72	6B6G	. 88	71.8	1.06 1.06	35Z5GT	.50
4AP10	6.95 4.95	710A	2.95	2050	1.19	1A4 1A4P 1A5GT	1.28 1.56	6B7	1.28	7G7 /1232 7H7	.80	37	.39
4C35	19.95	714AY	14.95	2051 2140		1A5GT	.72	6B8G	1.28	7.17	1.06	38. 39/44	.39
4J26 4J33	110.00 49.50	715A/B 715C	9.95	5514	4.95	1A6 1A7GT	. 1.28	6BA6	.72	7K7	1.06	41	.00
5AP1	4.95	717A	99	5516 5562	40 00	1B3GT	1,49	6BG6G	1.92	7N7	.88	42	.66
5AP4	5,95	720CY	34.95	7193	.39	1B4 1B5/25S	1.56 1.28	0BH0	.80	707	.72	43	.66
5BP1	2.95 4.95	721A/B		8003	5.95 4.95	1C5GT	88	6BJ6	.39	757	1.06	45Z5GT	.72
5CP1	. 3.95	724A/B	4.95	8005 8008 8011	3.75	1C6	1.28	6C5 6C5GT	.66	7V7	1.06 1.06	47	1.06
5CP7 5D21	. 13.95 . 29.95	725A	23.50	8011	2.95 4.95	1C7G 1D5G	1.56	6C6	80	7W7. 7X7/XXFM.	1.06	50	1.50
5FP7	3.95	750TL	49.50	8012 8013 8016	2.95	1 1D5GP	1.56	6C8G	1.28	7Y4	.72 .72	50A5 50B5	.88
5GP1	9.95	800	. 2.25	8016	1.49 3.95	1D7G 1D8GT	1.20	6D8G	1.28	774	.69	50L6GT	.66
6AF6G	88			8027	7.95	1E7G	1.56	6E5	. 85	12A	.60	50Y6GT	.72
6G21	24.95 3.95	803	12 95	G5B	12.90	1F4 1F5G	1.06	6F5 6F5GT	.66	12A6 12A6GT	.39	56	. 72
6O5G	1.25	803 804 805	5.95	C6J	12.95	1F6	1.56	6F6	.80	12A7	1.28	57	.80
7BP7	17.95	806	17.50	CEO72	1.95	1F7G 1G4GT	1.56	6F6GT 6F7	.66 1.06	12A8GT 12AH7GT	.88	70L7GT	1.56
7GP4	19.40			CK1005	.69	1G6GT	. 1.06	6F8G	1.28	12AL5	.80	71A	
9GP7 9LP7	. 15.00 4.95	809 810 811	2.95	CK 1090	4.95	1H4G	88	6G6G	1.06	12AT6	1,06	75 76	.66
9MP7	14.95	811	2.45	EF50 EL3C	4.95	1H6G	. 1.28	6H6GT	.60	12AU6	.80	76	.66
10BP4	34.95	812 812H	2.95 6.90	EL225	1.95	1H6GT	1.28	6J5 6J5GT	. 34	12AU7 12BA6		79	. 88
10HP4	49.50	812H	8.95	F123A	12.95 22.50	1.16GT 1L4	. 80	6J6	1.16	12BE6	.72	00	
10 SPEC	69	XIA	3.95	F660	150.00	1UA4	1.06	0.17	.80	12C8	.39	81 82	1.30
12DP7 12GP7	14.95	815 816		FG17	3.25 9.95	1LR4	1.00	6.17GT 6.18G	1.28	12F5GT	. 39	83	. 88
12JP4	60.00	822	. 11.95	FG27A FG81A	6.95	1LC5	1.06	6K5GT	. 96	12.15GT	.39	83V 84/6Z4	. 1.28
15AP4 15E	1.50	826	99 50	FG105	19.95	1LC6	. 1.4747	6K6GT		12J7G		85	. 88
15R	1.50	828 829/A/B 829B/3E29	6.95	FG172A FG238B	160.00	11.53	1.06	6K7GT	.00	12K7GT	. 66	89	/ 2
20AP4	. 270.80	829/A/B 829B/3E29	7.95	GL146	. 11.00	11.(10	. 1.474	6K8		12K8	88	89Y 117L7GT	
45 SPEC	. 49	0.317	4.93	GL207 GL559	5.35	1LH4	1.06	6K8GT (L5G	1.06	12K8GT	.96	117M7GT	1.56
75TL	3.95 12.95	822/A	4 95	GL559 GL605	250.00	1I.N5 1N5GT	80	6L6	1.42	12SA7	. 66	117N7GT	. 1.56
100TS	3,00	833A	34.50	GL697	2 05	1P5GT	1.00	6L6G	1.16	12SA7GT	. 66	117P7GT	
IUZF	4.00	836	1.15	HF200	. 17,95	105GT		6L6GA	1.16	12SC7		117Z4GT	
114A 114B	. 1.25	837	2.50	H 1 24	. 1.50	1R4		6L7G	. 1.16	12SF5 12SF5GT	.80	117Z6GT	96
120		838		HY69		154	96	6N6G	. 1.56	12SF7	80	FM-1000	. 1.28
121A	. 2.65	843		HY75	1.25	1S5	72	6N7	96	12SF7GT	80	1273 9001	88
203B	19.95	845	4.95		1.25	1T4 1T5GT	80	6P5GT 6O6G/6T7G		12SG7 12SH7	72	9002	39
203R	49.95	849A	60.00	HY115 HY615		1U4	.80	6Q7	80	12SJ7	66	9003	. 69
2020					40			CORCT	72	1041100000		9004	49
205B	4.50	845W	5,95	HYE1148	48	1U5			./2	12SJ7GT		9005	
210HF	. 4.50 . 17.95	845W 851 852	. 75.00	HY1231Z	5.50	1V	88	6R7	1.06	12SK7	66	9005	98

(ALL TUBE TYPES IN STOCK NOW-SUBJECT TO PRIOR SALE-PRICES SUBJECT TO CHANGE WITHOUT NOTICE)

20% DEPOSIT WITH ORDERS

NIAGARA RADIO SUPPLY CORP.

160 GREENWICH STREET

NEW YORK 6, N. Y.

Phone Dlgby 9-1132-3-4 All Prices F.O.B. N. Y. C.

SURPLUS MATERIAL — Shipped Immediately

Thousands of Relays Available—Send for Complete Listings

TUBES! GUARANTEED!

TYPE		TYPE P	
1LA6		851	
		860	
1L4			2.75
1V	.65	864	.65
2X2/879		866A	.75
3A4		872A	1.65
5R4GY	.95	954	.45
6AC7	.95	957	.45
6AG7	.95	968	.25
6C4	.29	1613	.85
6F8	.95	1616	.95
6G6G	85	1625	.45
6H6GT	.55	1626	.45
6L6	1.10	1629	.18
6SA7	.65	1632	.18
6SD7	.45	1641/RK60	
6SQ7	.65	,	
6S J7		1644	
6Y6		1294/1R4	.65
6X5		3D6/1299	.65
7B7	.65	394A	3,95
7C7	.95	9002	.35
7F8		9003	.25
7N7		9006	.35
7Y4	.75	8013	2.95
12K8		RK60/1641	
12SL7	.55 .65	RK72	.75
12SN7		RK73	.45
30 SPECIAL		1B24	1.95
(VT67)		2C46	3.95
32	.65	3B27/836A	
25Y5	.85	3C23	2.95
25Z6		4B27	2.95
35L6		4C33	2.95
38	.65	4D32	9.50
45 SPECIAL		14E6	.55
(V152) 56	.35	23D4	.45
89	.55 15	HY114B	.45
210	.65	5CP1	3.95
250	.65	2J1005	.35
350B	4.95	Amperite Voltage	
801	.95	Regulator 13-4	.25
814	4.95	Hytron Ballast	
826/2J	.95	100-79	.25
841.	.65	E1148	,95
843	.65	VR78	.45

WIRE!

At Giveaway Prices

Thousands and thousands of feet available of various types, sizes, and colors.

VINELITE,	AEROGLAS	ROCKB	ESTOS
	BRAIDED	Size 7/.020TC	Price \$6,75/M
Size 22 20	Price \$3.75/M 4.25/M	Spec #NSH3S 10/.0105 TC Spec #NSH1S	4.75/M
18 16	4.75/M 5.75/M	PLAS	TIC
12	6.75/M 7.75/M	Size 27 28	Price \$2.25/M 2.25/M
SHIE	LDED	BARE SOLI	D TINNED
Size	Price	12	\$.50 16.
18 20	\$20.00/M 15.00/M	14 22	.65 lb. .85 lb.
22	12.00/M	22	.85 lb.

4000-6000 VOLT LOW CURRENT DC SUPPLY

Brand new completely wired and tested. Ready to operate from 115 volt power ine. D.C. output is filtered.

Price Complete \$12.50
2000-3000 Volt D.C. Supply similar to above, but with lower output voltage. Ready to operate from 115 Volt power line.

Price Complete \$7.95

HIGH FIDELITY INPUT TRANSFORMERS

Ferranti #4794 Balanced winding, shielded type. Description—Turns ratio step-up 2/1 primary inductance 133 Henrys ± 1 DB 60-9000 cycles. Can be used to match any single or push-pull plates to any single or push-pull grids—overall dimensions 2½"x3"x2½" ... Price \$1.75

STANDARD BRAND PRECISION RESISTORS

Following sizes are in 1% and 2% tolerance Price \$.35 1 meg .8 '' .75 '' .6 '' 268 '' 1500 1400 1200 66,000 54,500 46,000 33,000 12,000 12,000 10,000 7,500 4,500 4,500 2,230 2,230 1,700 1000 .268 ''
.22 ''
125,000
120,000
109,000
100,000
95,000
92,000 110 20 14 12 10 84,000 80,000 Following sizes are

5% or better	tolerance,	Price \$.15
110,000	70	40
22,000	50	35
15,000		30
2,500		
	wing sizes o etter Price	
1 % OF E	errer Price	\$.10

1 70 Or	better Frice	φ.10
4,285	53.32	4.35
1,123	33.22	4.3
988	23.29	3.94
366.6	13.52	3.5
220.4	13.333	1,563
147.5	10.2	.29
105.8	5.1	.268
53.96	4.4	.25

COAXIAL CABLE

TYPE	IMPEDANCE	PRICE
RG 6/U	76 Ohms	.041/2 ft.
RG 38/U	55 Ohms	.041/2 ft.
RG 62/U	93 Ohms	.071/2 ft.
RG 77/U	48 Ohms	.04½ ft.

MALLORY RADIO NOISE **FILTERS** Model NFRD

MODE! NFKU

Ellminates extremely noisy radio reception
due to power line disturbances caused
by lights, refrigerators, washing machines, vacuum cleaners, elevators, oil
burners, diathermy machines, etc.
Filters out man-made noises in the broadcast short-wave and ultra-high frequency bands.

Designed for radios, appliances, and electrical equipment consuming up to 1300
watts (12 amperes) at 120 voits AC or
DC.
Housed in a metal case 1% "x3"x7%" com-

Housed in a metal case 1%"x3"x7\%" complete with male and female line connectors.

PRICE ONLY \$1.95

Mallory NF 12-6EG—Housed in a bathtub type container and rated at 7 amps, 50 volts D.C. Solder lug terminals. Price \$.35

Bendix—model 3937—Generator Filter—50 amps, 120 Volts D.C.—Housed in shielded containers 4"x3 \%"x8" Price \\$1.25

Line Noise Filter—Unshielded and mount-ed on a bracket. Suitable for use on regular power lines—Consists of two .01 molded condensers and 140 turn solenoid choke coil Price only \$.10

TRANSTAT VOLTAGE **REGULATORS**

Model #29144
Fixed Winding 115 Volts—60 cycles
Commutator range 75-120 Volts
Maximum output .25 KVA
Housed in shielded case 5"x6"x6"
Price \$6.95

Type RH

Fixed Winding 115 Volts—400 cycles
Commutator ranges 75-120 Volts
Load—.72 KVA
Housed in Shielded case 5 ½ "x6"x6½"

Price \$1.95

Write for Latest Catalog

EDLIE ELECTRONICS, INC.

154 GREENWICH STREET

TELEPHONE Digby 9-3143

NEW YORK 6, N. Y.



DYNAMOTORS

D-101, 27 v. DC in @ 1.5 amps. DC output 285 v. @ .060 amps. Stock #SA-187. Price \$1.50 each. DM-40A. 14 v. DC in @ 3.4 amps. DC output 172 v. @ .138 amps. Stock #SA-188. Price \$3.25 each.

MICROWAVE ANTENNA-

AS-217A/APG 15B. 12 Cm dipole and 13 inch Parabola housed in weatherproof Ra-dome 16" diam, 24 V. DC spinner motor for conic scan. Stock #SA-95. Shipping wt. 70 lbs.





Remote Position Indicating System





6-12 V. 60 cycles 5 inch indicator with 0 to 360° dial. Heavy duty transmitter. Stock #SA-115.

Price \$9.95 per system

SPERRY PHASE ADAPTOR - 661102 115 volts 400 cy. Used for operating 3 phase equipment from single phase source. Stock #SA-194. Price \$6.75 each.



RATE **GENERATORS**

Elinco PM-2
Approx. 2.0 v. DC per 100
ipm. Use to 2000 rpm.
Stock #SA-53. Price
\$7.50 ea.

ELINCO F-16. 2 Phase AC. 1.3 v AC per
100 rpm. 60 cy. output at 1800 rpm. Stock
#SA-193. Price \$12.50 each.



400 CYCLE WESTINGHOUSE FL BLOWER

400 су. 17 V. c.f.m. Includes capacitor. Stock #SA-144. Price \$6.75 each.

SWEEP GENERATOR CAPACITOR



ELECTRONICS — November, 1948


Hi-speed bearings. Split stator. Silver plated coaxial type. 5-10 mmf.

Stock #SA-167. Price \$2.75 each.

TWX Pat-199.

Write for complete listing. or call ARmory 4-3366

INVERTERS

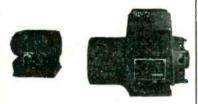

400 Cycle Three Phase

Holtzer-Cabot MG-153F — Input 28 volts DC at 52 amps. Output three phase 115 volts 400 cycles at 750 V.A. 0.90 P.F. Also second output of 26 volts 400 cycles at 250 V.A. voltage and frequency regulated. Stock #SA-135.

Pioneer 12123-1A — Input 28 v. DC at 12 amps. Output three phase 115 volts 400 cycles at 100 V.A. Voltage and frequency regulated. Stock #SA-5.

Leland SD-93 — Input 28 volts DC at 60 amps. Output 115 volts 3 phase 400 cycles at 750 V.A. 0.90 P.F. Second output of 26 volts 400 cycles at 50 V.A. 0.40 P.F. Voltage and frequency regulated. Designed for use with various autopilots. Stock #SA-209.

400 Cycle Single Phase

Wincharger PU7/AP — Input 28 v. DC at 160 amperes. Output 115 volts 400 cycles at 2500 V.A. Voltage and frequency regulated. Cont. duty. Wt. 75 lbs. Stock #SA-164.

Pioneer 12117-2 — Input 28 v. DC at 1 amp. Output 26 volts 400 cycles at 6 V.A. Cont. duty. Stock #SA-49.

Pioneer 12117-5—Input 14 v. DC at 2 amps. Output 26 volts 400 cycles at 6 V.A. Cont. duty. Stock #SA-96.

Holtzer Cabot MG-149F—Input 28 v. DC at 36 amps. Output 115 volts 400 cycles at 500 V.A. P.F. 0.40. Second output of 26 volts 400 cycles at 250 V.A. Stock #SA-86.

Holtzer Cabot MG-149H — Similar to MG-149F but draws 44 amps DC at 28 v. Out-put ratings are at 0.90 P.F. Equipped with high altitude brushes. Stock #SA-4.

General Electric 5D21NJ3A — Input 28 volts DC at 35 amps. Output 110 volts 400 cycles. 485 V.A. at 0.90 P.F. Weight 15 lbs. Stock #SA-41.

General Electric 5AS131JJ11A—(PE-218)
—Input 28 volts DC. 92 amps. Output 115
volts 400 cycles at 1500 V.A. 0.90 P.F.
Stock #SA-112.

800 Cycle Single Phase

Navy Type CRV-21AAR. G.E. 5AS121LJ2
—Input 27 v. DC at 45 amps. 120 volts 800
cycle out at 750 V.A. 0.90 P.F. Wt. 23 lbs.
Stock #SA-192.

NOTE

All merchandise is new and guaranteed to meet original manufacturer's specifications. Delivery from stock.

Servo Motor

Pioneer Type CK-2. phase 400 cycle. Fixed phase 26 V., var. phase. 49 V max. 1.05 oz/in. stall



torque. Stock #SA-97. Price \$4.75 ea. net



Blower Assembly MX-215/APG

John Oster C-2P-1L 28 V. DC. 7000 RPM 1/100 H.P. #2 L-R 1/100 Blower.

Stock #SA-202. Price \$3.75 each



G.E. 10 rpm DC Motor 5BA 10FJ12

Output 40 lb. in at 10 rpm. 24 V. @ 1.1 amps. Series-wound #2 wire reversible.

(Housing is Common Lead)
Ideal for relay servo-systems, Stock #SA17. Price \$8.75 each.

Phase Shift Capacitor — 4 stator single rotor 0-360° phase shift. (Use in complex wave synthesis.) Stock #SA-114.

Price \$4.75 ea.

Delco PM Motor-5068571



Alnico field. 27 v. DC. 10,000 rpm. 1" x 1" x 2" shaft 21/32 Lg. x 0.125 diam. Stock #SA-151. diam. Stock # Price \$3.75 each.

12V DC MOTOR John Oster B-9-2

1.4 amps. 5600 rpm.

1¾" Diam. x 3¾" Lg. Spline shaft CW rotation. Stock #SA-46. Price \$3.75 each

Delco PM Motor 5069600. 27 V. DC-250 RPM. Spline Shaft. Prices on Request.

LP-21-LM Compass Loops



Original Cartons Stock #SA-99.

Price \$9.50 each.

110 RPM MOTOR

G.E. 5BA10J18D, 27 V. @ 0.7 amps. 1 oz/ft. torque. 1%" diam. x 3½" lg. Operates on AC or DC. Stock #SA-98.



Include 15¢
for P.P.
and
handling Price \$2.95 ea. net

to rated concerns.

All prices F.O.B. Paterson, N. J

Paterson, N. J.

4 Godwin Ave.

SEARCHLIGHT SECTION

MYCALEX SOCKET for 813, 4E27/257B TYPE TUBES

Send for our new, fully illustrated catalog just off the press!

1 K.W. POWER SUPPLY KIT 2500-0-2500 Volts @ 500 MA

2300-0-2300 VOITS @ 300 MA
70
2000-0-200 Volts @ 500 MA
(oil-filled Xformer from BC610)\$39.95
1—Swinging choke14.95
1—Smoothing choke 7.95
1-Filament Xformer 9.95
2-2 Mfd., 3000 v. Condensers, ea 3.45
2-872A Tubeseach 1.95
2—Plate Caps for 872Aeach .20
2—Sockets for 872Aeach 1.19
2—Hash Filter Chokes.
2—Hash Filter Chokes. pr79 All parts New! Reduced to
All parts New! Reduced to

SELENIUM RECTIFIERS Full Wave Bridge Type

	ruii	MAGAG	briage	Type								
11	NPUT		OUTPUT									
up to	18v AC	up to	12v DC	1/2 Amp.	\$0.98							
up to	18v AC	up to	12v DC	1 Amp.	1.95							
up to	18v AC	up to	12v DC	3 Amp.	3.45							
up to	18v AC	up to	12v DC	5 Amp.	4.45							
up to	18v AC	up to	12 v DC	10 Amp.	7.45							
up to	18v AC	up to	12v DC	15 Amp.	9.95							
up to	18v AC	up to	12v DC	30 Amp.	14.95							
up to	36v AC	up to	28v DC	1 Amp.	3.45							
up to	36v AC	up to	28v DC	5 Amp.	7.45							
up to	36v AC	up to	28v DC	10 Amp.	12.45							
up to	36v AC	up to	28v DC	15 Amp.	18.95							
	115v AC		100v DC	.25 Amp.	2.95							
	115v AC		100v DC	.6 Amp.	6.95							
	115v AC		100v DC	5 Amp.	19.95							
up to	115v AC	up to	100v DC	3 Amp.	12.95							

OIL CONDENSERS NATIONALLY ADVERTISED BRANDS All Ratings D. C.

	Al	1 Rat	ings D. C.		
2x.1mfd.	600v	\$0.35	1mfd.	2000v	\$0.95
.25mfd.	600v	.35	2mfd.	2000v	1.75
.5mfd.	600v	.35	4mfd.	2000v	3.75
1mfd.	600v	.35	15mfd.	2000v	4.95
2mfd.	600v	.35	4mfd.	2500v	3.98
4mfd.	600v	.60	2mfd.	2500v	2.49
8mfd.	600v	1.10	.1mfd.	2500v	1.25
10mfd.	600v	1.15	.25mfd.	2500v	1.45
3x.1mfd.	1000v	.45	.5mfd.	2500v	1.75
.25mfd.	1000v	.45	.05mfd.	3000v	1.95
1mfd.	1000v	.60	.1mfd.	3000v	2,25
2mfd.	1000v	.70	.25mfd.	3000v	2.65
4mfd.	1000v	.90	1mfd.	3000v	3.50
8mfd.	1000v	1.95	12mfd.	3000v	6.95
10mfd.	1000v	2.10	2mfd.	4000v	5,95
15mfd.	1000v	2.25	1mfd.	5000v	4.95
20mfd.	1000v	2.95	.1mfd.	7000v	2.95
24mfd.	1500v	6.95	3mfd.	4000v	6.95
.1mfd.	1750v	.89	2mfd.	3000v	3,45
.1mfd.	2000v	.95	2x.1mfd.	7000v	3.25
.25mfd.	2000v	1.05	.02mfd.	12000v	9.95
.5mfd.	2000v	1.15	.02mfd.	20000v	11.95

HIGH CAPACITY CONDENSERS

10,000 mfd.—25 WVDC
2x3500 mfd.—25 WVDC
2500 mfd.—3 VDC
3000 mfd.—25 WV DC 2.49
2x1250 mfd.—10 VDC
1000 mfd.—15 WVDC
200 mfd.—35 VDC
100 mfd.—50 WVDC
4x10 mfd.—400 VDC
4000 mfd.—18 WVDC
4000 mfd.—25 WVDC
4000 mfd.—30 WVDC 3.25
-11 01101/-0

FILTER CHOKES

HI-VOLTAGE	INSULATION	
8 hy @ 550 ma \$7.95	325 hy @ 3 ma	\$3.45
8 hy @ 300 ma 3.95	1 hy @ 800 ma	14.99
25 hy @ 160 ma 3.49	10 hy @ 250 ma	2.45
12 hy @ 150 ma 2.25	10 hy @ 200 ma	1.98
30 hy @ 70 ma 1.39	10/20 @ 85 ma	1.59
	15 hy @ 125 ma	1.49
	15 hy @ 100 ma	1.39
	3 hy @ 50 ma	. 29
200 hy @ 10 ma 3.49		1.49
600 hy @ 3 ma 3.49		3.50
	10 hy @ 100 ma	1.29

RADIO TUBES

NEW.	ST	ANDA	RD	BRAN	DS!
1B24 1B26	\$1.95 4.95	726A 800	\$4.50 1.75	1Q5GT	\$.95 .79
1B29 1N21 1N23	.89	801 A 802	1.75 .75 2.95	184	.69 .65
IN34	1.60 .89	803 805 807	5.95 4.49	1T4 3Q4	.69
1P24 2AP1		808	1.25	3Q5 3S4	.69
2AP1 2C22 2C26 2C40 2C44 2C46 2D21	.19	809 810 811	1.50 5.95 1.49	5Y4GT 6A7	.59 .55
2C40 2C44	1.29	812		6ASGT 6AG5	.59
2D21	1.29 3.75 1.59	813 814 815	5.25 2.75 1.45 1.10	6AG7 6B4G	1.19
2J21 2J22	12.95 12.95 9.95	816	1.45	6BG6G 6C6	.98 1.98 .49
2J26 2J31 2J32 2J36 2J37	24.95	826 829B	4.85 2.95	6D6 6F5GT 6F6GT	.49
2J36	24.95	829B 832A 833A 836 837	2,95		.81
2138	24.95 14.75 18.95	837 838	29.50 .79 1.49 3.25 .50 .59 3.29 39.50 1.98 11.95	6H6GT 6J5GT	.49 .45 .59
2J40 2J46	24.95	841 843	.50	6J5 6J7GT 6K6GT 6K7GT 6L6G	.55
2.149	26.95 49.50	845 851	3.29	6K7GT	.55
2J51 2J54B 2J55	18.95 18.95	860 861	1.98		1.23
2J54B 2J55 2K25 2K28 2V3G 2X2 3AP1 3BP1 3B22	24.95 8.95	865 866A	.85	697GT	.99
2V3O 2X2	98	866.IR	.85 1.10 28.75	6SC7 6SE5GT	.55 .59
3AP1 3BP1	2.79 1.39	869B 874 876		6SH7 6SJ7GT	.49
3B22 3B24	.09	878 884	1.89	6SK7GT	. 40
3B22 3B24 3B26 3CP1 3C22 3C23 3C24 3C30 3C31	3.95 2.95 12.95 2.95	885 902121	.69 .98 7.95	617 627 6876T 68876T 68875GT 68877 6817GT 6817GT 6817GT 6807GT 6807GT 646GT 748GT 748GT 706 7777 774	.74 .59 .49
3C22 3C23	2.95 12.95 2.95	905	7.95 8.95 .69	6V6GT 6X5GT	.69
3C24 3C30	.59	954 955	.35	7A8GT 7B7GT	.79
3C31 3DP1	1.49 2.25	956 9 57	. 35	7C5 7C6	.79 .79 .49
3D21A 3E29	1.49 2.25 1.50 3.39 3.95	958 1611	.35	7F7 7Y4	.35
4E27	11.95	1611 1613 1616	.58	12ASGT 12AT6	.69
3C31 3DP1 3D21A 3E29 4B24 4E27 5AP4 5BP1 5BP4 5CP1 5D21	3.95 11.95 4.75 1.10 4.95 2.95	1619 1622	.75 .21 1.75	12AU6 12BA6	.75
5CP1 5D21	2.95 18.95	1622 1624 1625	.85 .19	12J5GT	.49 .49
5D21 5FP7 5JP1	.85	1626 1629	3.95	7Y4 12A8GT 12AT6 12AU6 12BE6 12BE6 12J5GT 12J7GT 12K7GT 12SC7GT 12SF5GT 12SF5GT 12SF7GT 12SF7GT 12SF7GT 12SR7GT 12SR7GT 12SR7GT 12SR7GT 12SR7GT	.49
5J29 5J30	11.95 18.95 18.95 11.95	1630 1638 1654	1.98	128A7GT	.49
5T.P1		1851 2050	.98	12SF7CT	.59
5R4GY 5T4 5U4G	.69	2051 8005	.75 .45 3.65 .65 2.75 .89	12SK7GT	.49
5V4 5X4 5Y3	.72 .59	8011	2.75	12SR7GT 14A7	.69
5 Y3 5 Z3 5 Z4		8012 8013 8014	16 95	1486	.69
	.79	8016 8020	.89	24 A	.49
6AC7 6AK5 6AL5 6C4 6D4	.59	8025 9001	4.95	257607	.49
6AL5 6C4	.59 .25 1.29	9002 9003	.35	20	.45 .45 .49
6J4 6J6	3.95	9004 9005	.29	30 Spec 32L7GT 35/51 35A5 35L6GT 35W4	1.19
605G 7EP4	1.25 17.95	9006 CK1005		35A5	.59 .72 .49
10Y	.89	CK1090	1.49	35W4	.39
10Y 12A6 12DP7 12GP7	.89 .25 13.95 12.95	9006 CK1005 CK1006 CK1090 EF50 F123A F127A F128A F660	12.95 17.50 69.50	35Y4 35Z3 35Z5GT	.79
15R		F128A F660	69.50 59.50	36	.79 .55
75TL 100TH	3.75 9.95	FG105	59.50 4.75 4.95	41 42 43	54
211 227A 231D		FG238B	98.50	45 45 Spec 47	.55 .35 .74
	3.75 2.49 1.75 19.49	Cilb97	149.50	DUAD	.74
250TH 304TL 304TH		HY75 HY615 ML100	1.25 .75 49.50 99.50 99.50	50B5 50L6GT	.89 .59 .52 .75
318A	3.95	ML100 ML101 ML502	99.50	50Y6GT 56 59	.75
327A 350B	3.95 4.95 2.95 6.95	ML502 VR75 VR90	.98	TOT TOT	
368AS 371B 450TH	.99		.65 .65 .65 3.49 1.29	71A 75 76 77 78	1.29 .74 .59
371B 450TH 527 531		VR150 VT127A VU111	3.49	77	.49
559 703 A	2.50 .75 4.95 1.85 18.95		.59	78 79 80	.85
705A	1.85	1A7GT	59	81	1.55 1.15 1.29
714AY 715B	9,95	1A5GT 1A7GT 1H5GT 1N5GT 1LA4	.59 .54 .59 .59	82 83 83V	1.29
715C 717A	18.95		.95	84 89	.69
721 A 723 A/B	.59 5.95	1LB4 1LC6 1LD5 1LE3	.95	117L7GT 117P7GT	1.15
724A/B	1.75	ILH4	.95	117Z3	.89
725A	7.45	1LN5	,95	117Z6GT	.75

500 WATT POWER SUPPLY KIT

(Ideal for BC-191 & BC-375E)
1—Transformer—Pri: 105/250v
60 cyc in 5v Steps
Sec: 1120-0-1120y @ 500 MA
21/2 + CT (a 10 AMP)
12v @ 14 AMPS
17v @ 21/2 AMPS
32v @ .025 AMPS\$32.50
2-Filter Chokes @ \$7.95 ea. 15.90
2-Condensers 3 Mfd @ 2000v
DC @ \$4.45 ea 8.90
2-866 Tubes @ \$.89 ea 1.78
2—Plate Caps Ceramic @ \$.20
ea
2Sockets @ \$.20 ea
1 Pair Hash Filter Chokes
\$40.50
Extra Special Buy JAM JU

TRANSFORMER-115 V. 60 Cy.

S access	HI-VOLTAGE INSULATION	,
1	3710v @ 10 ma.; 2x2½v @ 3A	\$9.95
۱	3710	6.50
	2500v @ 4 ma.; 2½v @ 2A. 6.3v @ 1 amp.	7.95
ı	2150v @ 15 ma	5.50
ı		6.50
ı	1600v @ 4 ma.; 700v CT @ 150 ma.; 6.3v	- 0-
ı	@ 9A	7.95
ı	020-0-525V @ 60 ma.; 925V @ 10 ma.; 2x5V	7.95
1	@ 3A; 6.3v @ 3.6A; 6.3v @ 2A; 6.3v @ 1A 515-0-515v @ 175 ma.; 5v @ 3A; 2.5v @ 5A	5.95
ı	500-0-500y @ 25 mg · 262-0-262y @ 55	0.75
I	500-0-500v @ 25 ma.; 262-0-262v @ 55 ma.; 6.3v @ 1A; 2x5v @ 2A	4.49
	500-0-500v @ 100 ma.: 5v CT @ 3A	4.95
H	450-0-450 @ 200 ma.: 315v @ 10 ma.: 6.3v	7
d	@ 7A; 5v @ 3A; 5v @ 2A; 110/220v Pri. 425-0-425 @ 200 ma.; 150-0-150 @ 100	10.95
ò	425-0-425 @ 200 ma.; 150-0-150 @ 100	
ì	ma.; 40v @ 1A; 6.3v @ 5A; 5v @ 3A; 110/	
ş	Dual Pri, tapped	7.50
à	400-315-0-100-315v @ 200 ma.; 2.5v @ 2A;	6.50
蒙	5v @ 3A; 6.3v @ 9A; 6.3v; 9A	4.95
Š.	400-0-400v @ 200 ma.; 5v @ 3A 350-0-350v @ 150 ma.; 5v @ 3A; 6.3v @	4.90
	№ 64 · 78v @ 14	4.95
S	▶ 6A; 78v @ 1A 385-0-385-550v @ 200 ma; 2½v @ 2A; 5v	1.70
H	@ 3A: 3x6.3v @ 6A—PRI, 110/220	7.95
Н	@ 3A; 3x6.3v @ 6A—PRI. 110/220 350-0-350v @ 150 ma.; 5v @ 3A; 6.3v @	11.
ı	7.5A; 6.3v @ 3A	4.99
Š	350-0-350v @ 35 ma	1.45
	7.5A; 6.3v @ 3A 350-0-350v @ 35 ma 340-0-340v @ 300 ma.; 1540v @ 5 ma.	5.95
3	335-U-335V (Ø 60 ma.; 5V (Ø 3A; 6.3V (Ø 2A;	4.05
ą	0-13-17-21-23v @ 70 ma.—PRI. 110/220	4.95
I	325-0-325v @ 120 ma.; 10v @ 5A; 5v @ 7A 300-0-300v @ 65 ma.; 2x5v @ 2A; 6.3v @	3.49
H	21/A · 6 2v @ 1 A	3.49
ā	250-0-250v @ 100 ma · 2v6 3v @ 4A · 6 3v	3,17
é	@ 5A: 63v @ 1A	4.95
H	2½A; 6.3v @ 1A 250-0-250v @ 100 ma.; 2x6.3v @ 4A; 6.3v @ 5A; 6.3v @ 1A 150-0-150 @ 80 ma.; 150 @ 40 ma.; 6.3v @	
ģ	3.5A; 6.3v @ 1A	1.98
d	3.5A; 6.3v @ 1A 150v @ 55A; 150v @ 2.13A; 5v @ 5A	5.95
ı	120-0-120v @ 50 ma 80-0-80v @ 225 ma.; 5v @ 2A; 5v @ 4A	.98
į	80-0-80v @ 225 ma.; 5v @ 2A; 5v @ 4A	3.95
ė	24v @ 6A	3.50
ľ	3x18v @ 2A 13.5v CT @ 3.25A	3.95 2.95
	3-10.3v @ 7A · CT	9.95
g	3x10.3v @ 7A; CT. 12.6v CT @ 10A; 11v CT @ 6.5A. 3x6.3v @ 1A; 2x6.3v @ 2A; 10v CT @ 10A;	7.95
18.50	3x6.3y @ 1A: 2x6.3y @ 2A: 10y CT @ 10A:	,0
i	12.6v CT @ 1A	4.95
į	12.6v CT @ 1A	3.95
۱	6.3v @ 10A; 6.3v @ 1A	3.50
S	6.3v @ 1A; 2½v @ 2A	3.45
١	5v @ 20A; Duai 110v PRI	3.49
۱	6.3v @ 10A; 0.3v @ 1A 6.3v @ 11A; 2½ @ 2A 5v @ 20A; Dual 110v PRI. 6.3v @ 21½A; 6.3v @ 2A; 2½v @ 2A. 5v—190A\$17.50 6.3v @ 1A. 5v—115A14.95 8v CT 1A 2.5v @ 20A3.49 .6v @ 15ARMS 6.3v CT @ 3A; 5v CT @ 4A.	5.95
	5v-150A \$17.50 0.5v @ IA	.98
Ē	2 5v @ 20A 3.49 6v @ 15APMS	2.98
ě	6 3v CT @ 3A: 5v CT @ 4A	4.25
ŝ.	0.01 02 9 0.21 0. 02 9 1111111111111111111111111111111111	2.40

All Prices Subject to Change Without Notice

All merchandise guaranteed, Mail orders promptly filled. All prices F.O.B. New York City. Send money order or check. Shipping charges sent C.O.D. Minimum order \$5.00. 20% Deposit required with all orders.

SEARCHLIGHT SECTION



Maria da de la companya del la companya de la compa

PARABOLOIDS

Ideal for microwave experimental work. Spun Magnesium dishes Reinforced Perimeter 171/2" Diameter x 4" Deep Two sets mounting brackets on rear Open center hole 11/2" x 15/8"

Per Pair, Brand New . . . \$8.75

MERCURY CONTACT RELAY Western Electric D-168479

For applications in all types of high speed switching devices. Long service life, high operating speeds. Large current and voltage handling capacity, uniform and constant operating characteristics inner adverse atmospheric conditions. Hermetically-sealed negacy-wetted contacts in gas-filled glass envelope. Free from moisture, dirt. corrosion and atmospheric pressure. Single pole double 'brow contacts.

1000 hours life at 60 operations per second. Two coils of 700 onms, and 3300 ohms. Operating current, coils series aiding—5.2 mils. Four page Technical Data on request.

Brand New in Original Cartons, \$4.75



STEPDOWN TRANSFORMERS

.

Input: 115V. 60 cycles.
Output: 20 V., at 10 amps.
Also tapped at 6V., for pilot light, 1deal for Selenium Rectifier Applications, etc.
Brand New \$2.45






SELENIUM RECTIFIER

Bridge Type Input: 36 V. AC. Output: 28 V DC., 1.1 Amps.

Brand New \$2.75

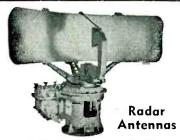


Following	types	available

SO-1 (10 cm.)	ı									į.		•11	\$149.50
SO-3 (3 cm.)													
SO-8 (10 cm.).						٠	,		,				.\$139.50
SO-13 (10 cm.)													
TDY (10 cm.).				٠	*		- 10	1					. \$95.00

TRANSTAT VOLTAGE REGULATOR

All Brand New

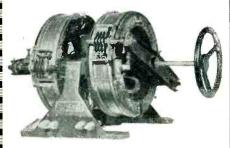

Max KVA Output11.5
Single Phase
Fixed Winding
Commutator Range 0-115 Volts
Max. Amperage100
With reconnection for 220 V. Opera-
tion: Max Amperage

This Transtat has wide application to control temperature, motor speed, illumination, tectifier output, filament supply, voltage compensation, instrument calibration, and general testing and laboratory use.

PAN-OSCILLO-RECEIVER

Ideal for laboratory, television and general service work.



Model AN/APA 10

Performs work of four units

- PANORAMIC ADAPTOR: For use with any receiver with I.F. frequency of 405-505 kcs., 4.75 to 5.75 mcs., and 29-31 mcs.
- OSCILLOSCOPE: Visually checks received signals, monitors transmitter output, percentage modulation, carrier put, percentage wave-shape, etc.
- SYNCHROSCOPE: External inputs provide synchroscope action. synchroscope action.
- RECEIVER: Three inputs provide facilities for use with convertors to cover wide range of frequencies to 10,000 mcs.
 FEATURES:
- 3" scope tube
- 21 tubes
- Variable sweep 35-40,000 cy
- Transformer built in for 110 V. 60 cycle
- 2 l.F. stages-double conversion
- 2 Video stages in push pull to vertical plates
- Pentode output audio monitor
- Multi-Vibrator horizontal sweep (radar
- Horizontal sweep amplifiers P.P. to horizontal plates

Surplus equipment tested and guaranteed in perfect operating condition. We have sold hundreds of these units to leading schools, laboratories, amateur operators all over the world

\$149.50

(Mail S3.50 for 80 page Technical manual and instruction book)

SHOCK MOUNTS



LINEAR SAWTOOTH POTENTIOMETER

W.E. No. KS 15138



W.E. No. KS 15138

The d-ce potentiometer consists of a closed type die-cast aluminum alloy frame consisting of a continuous resistance winding to which electric power is supplied through two flaced taps 180 degrees apart. Two rotatings brushes (180 degrees apart and bearing on the resistance winding) and two take-off brushes are provided for the output voltage. Varying the potentiometer is excited with 24-volt direct current, is arranged for panel or bracket mounting, is approximately 3-11/16 inches in diameter. 3 inches deep. 14% inches long, and has an approximate weight of one pound. External connections are made through a standard AN type counector.

Brand New \$5.75

Brand New \$5.75

DYNAMOTORS—500 Watts Navy Type CAJO-211444

Input: 105-130 Volts D.C., 6 amps. Output 13 or 26 Volts D.C. (26 V. at 20 amps. in series or 13 V. at 40 amps. in parallel). Designed for radio use, fully R.F. filtered, complete with separate Square D line

BRAND NEW \$59.50



SOUND **POWERED CHEST SETS**

No Batteries Required Ideal for television installers, or any antenna measurement work. Leaves hands free to make adjust-ments. Set consists of microphone and head-set as illustrated.

Brand New

Per Set \$19.50

SYNCHROS

(Selsyns, Autosyns, etc.)

Navy types: 1F, 5B, 5CT, 5DG, 5G, 5F, 5SDG, 5SG, 5SF, 6DG, 7G, etc.

Army types: 2J5FB1, 2J5S1, 2J1F3, C 18300, C 78414, C 78863, C 78411, etc.

Pioneer Precision Autosyns type AY 101D,

400 CYCLE **SERVO** AMPLIFIERS

All merchandise guaran-

teed. Immediate delivery, subject to prior sale.

G. E. Type 2CV1C1

Brand New \$29.50

Prices FOB, Tuckahoe, N. Y. Subject to Change Without Notice. 20% With Order on C.O.D. Shipments.

ELECTRONICRAFT

PHONE-TUCKAHOE 3-0044

TUCKAHOE 7, NEW YORK

5 WAVERLY PLACE

Brand New and Fully Guaranteed

SYNCHROS

- If Special Repeater, 115 volts, 400 cycle. Will operate on 60 cycle at reduced voltage.—Price \$15.00 each
- ICT Control Transformer, 90/55 volts, 60 cycle.—Price \$22.50 each net. 2J1G1 Control Transformer, 57.5/57.5 volts, 400 cycle.—Price \$2.00 each
- 2J1H1 Selsyn Differential Generator, 57.5/57.5 volts, 400 cycle.—Price
- \$3.25 each net. 5G Generator, 115 volts, 60 cycle.-Price \$25.00 each net.
- E. KS-5950-L2, Size 5 Generator, 115 volts, 400 cycle.—Price \$4.50 each net.
- ze 5 Generator, Army Ordnance Drawing No. C-78414, 115 volts, 60 cycle.—Price \$14.00 each net.

PIONEER AUTOSYNS

- AY1, 26 volts, 400 cycle.—Price \$4.00
- each net. Y20, 26 volts, 400 cycle.—Price \$5.50 each net.
- 26 volts, 400 cycle.—Price \$10.00 each net.
- AY31, 26 volts, 400 cycle. Shaft extends from both ends .- Price \$10.00 each net.
- AY38, 26 volts, 400 cycle. Shaft extends from both ends.—Price \$10.00

PIONEER PRECISION AUTOSYNS

- AY131D, new with calibration curve. PRICE-WRITE OR CALL FOR SPECIAL QUANTITY PRICES
- AY131D, new with calibration curve.
 —Price \$35.00 each net.

GENERAL ELECTRIC D. C. SELSYNS

- 8TJ9-PDN Transmitter, 24 volts.-Price \$3.00 each net.
- 8DJ11-PCY Indicator, 24 volts. Dial marked -10° to +65°.—Price \$4.00 each net.
- 8DJ11-PCY Indicator, 24 volts. Dial marked 0 to 360°.—Price \$6.50 each net.

PIONEER TORQUE UNITS

- Type 12602-1-A.—Price \$30.00 each net.
- Type 12606-1-A.--Price \$35.00 each net.
- Type 12627-1-A.—Price \$70.00 each

PIONEER TORQUE UNIT AMPLIFIER Type 12073-1-A.—Price \$17.50 each

RATE GENERATORS

- PM2. Electric Indicator Company, .0175 V. per R. P. M.—Price \$7.25 each net.
- F16, Electric Indicator Company, two-phase, 22 V. per phase at 1800 R. P. M.—Price \$12.00 each net.
- B-68, Electric Indicator Company, Drag Cup, 110 volts, 60 cycle, one phase.
 —Price \$14.00 each net.

INVERTERS

- 12117-4, Pioneer. Input 24 volts D. C. Output 26 volts, 400 cycle.—Price \$12.00 each net.
- 12117, Pioneer. Input 12 volts D. C. Output 26 volts, 400 cycle.—Price \$15.00 each net.
- 12123-1-A, Pioneer. Input 24 volts D. C. Output 115 volts, 400 cycle, 3 phase. Voltage and frequency 3 phase. Voltage and frequency regulated. 100 V. A.—Price \$75.00 each net.
- 153F, Holtzer Cabot. Input 24 volts D. C. Output 26 volts, 400 cycle, 250 V. A., and 115 volts, 400 cycle, 3 phase, 750 V. A. Voltage and frequency regulated.—Price \$150.00 each net.
- WG750, Wincharger, PU16. Input 24 volts D. C. Output 115 volts, 400 cycle, 1 phase, 6.5 amps. Voltage and frequency regulated.—Price \$35.00 each net.
- 149H, Holtzer Cabot. Input 28 volts at 44 amps. Output 26 volts at 250 V. A. 400 cycle and 115 volts at 500 V. A. 400 cycle.—**Price** \$39.00 each net.
- 149F, Holtzer Cabot. Input 28 volts at 36 amps. Output 26 volts at 250 V. A. 400 cycle and 115 volts at 500 V. A. 400 cycle.—**Price \$29.00** each net.

SPERRY PHASE ADAPTER

Type 661102, 115 volts, 400 cycle. Used for operating 3 phase equipment from a single phase source.— Price \$6.50 each nes.

SINE-COSINE GENERATORS (Resolvers)

FJE 43-9, Diehl, 115 volts, 400 cycle. -Price \$20.00 each net.

D. C. ALNICO FIELD MOTORS

- 5067127, Delco, 27 V., 250 R. P. M.-Price \$2.90 each net.
- 5069600, Delco, 27 V., 250 R. P. M.-Price \$4.00 each net.
- 5069466, Delco, 27 V., 10,000 R. P. M. -Price \$3.00 each net.
- WRITE FOR COMPLETE LISTINGS

D. C. MOTORS

- 069625, Delco Constant Speed, 27 volts, 120 R. P. M. Built-in reduction 5069625, gears and governor.—Price \$4.25 each net.
- A-7155, Delco Constant Speed Shunt Motor, 27 volts, 2.4 amps., 3600 R. P. M., 1/30 H. P. Built-in governor.—Price \$6.25 each net.
- 5BA10J18D, General Electric, 27 volts, 0.7 amps., 110 R. P. M.—Price
- \$2.90 each net. 5066665, Delco Shunt Motor 27 volts, 4000 R. P. M. Reversible, flonge mounted.—Price \$4.50 each net.
- C-28P-1A, John Oster Shunt Motor, 27 volts, 0.7 amps., 7000 R. P. M., 1/100 H. P.—Prics \$3.75 each net.

- A. C. MOTORS 5071930 Delco, 115 volts, 60 cycle, 7000 R. P. M.—Price \$4.50 each
- 36228, Hayden Timing Motor, 115 volts, 60 cycle, 1 R. P. M.—Price \$2.85 each net.

SERVO MOTORS

- CK1, Pioneer, 2 phase, 400 cycle.-Price \$10.00 each net.
- CK2, Pioneer, 2 phase, 400 cycle.— Price \$4.50 each net.
- FPE-25-11, Diehl, Low-Inertia, 75 to 115 V., 60 cycle, 2 phase.—**Price** \$16.00 each net.
- FP-25-2, Diehl, Low-Inertia 20 volts, 60 cycle, 2 phase.—Price \$9.00 each
- FP-25-3, Diehl, Low-Inertia 20 volts, 60 cycle, 2 phase.—**Price \$9.00** each net.

GYROS

- Schwein Free & Rate Gyro type 45600.
 Consists of two 28 volt D. C. constant speed gyros. Size 8" x 4.25"
 x 4.25".—Price \$10.00 each net.
- Schwein Free & Rate Gyro, type 46800. Same as above except later design,— Price \$11.00 each net.
- Sperry A5 Directional Gyro Part No. 656029, 115 volts 400 cycle, 3 phase.—Price \$17.50 each net.
- erry A5 Vertical Gyro. Part No. 644841, 115 volts 400 cycle 3 phase.—Price \$20.00 each net.
- Sperry A5 Amplifier Rack Part No. 644890. Contains Weston Frequency Meter. 350 to 450 cycle and 400 cy-0 to 130 voltmeter.-Price \$10.00 each net.
- perry A5 Control Unit Part No. 644836.—Price \$7.50 each net.
- Sperry A5 Azimuth Follow-Up Amplifier Part No. 656030. With tube. -Price \$5.50 each net.
- Pioneer Type 12800-1-D Gyro Servo Unit. 115 volts 400 cycle, 3 phose.
- —Price \$15.00 each net. Norden Type M7 Vertical Gyro. volts D. C.—Price \$20.00 each net.
 Norden Type M7 Servo Motor. 26 volts
 D. C. Price \$20.00 each net.

INSTRUMENT ASSOCIATES

147-57 41st AVENUE Telephone INdependence 3-1919 FLUSHING, N.Y.

AND-EYEFULS OF

ELECTRONIC SPECIALS TOO!



BC 1072 A IFF X'MITTER 150 to 200 Mcs. 115 V. 60 Cyc. in MAPLE CHEST

POWER SUPPLY gives: 0-5000 v.d.c. (variac control) 312 v.d.c., 700 v.d.c., 6.3 vac. Also control) 312 v.d.c., 700 v.d.c., 6.3 vac. Also contains: 11 tubes 645, 826, 6857, 51446, etc.), 5 kV meter, Blover, Condensers and many other useful parts too numerous to list. Shipping Wt. 245 lbs.

Only.....(slightly used) \$22.50

PULSE TRANSFORMERS

PULSE TRANSFORMERS

Phileo 352-7250-2A, 15/16 dia x 15%"
High D.C. Resistance, 10 ohm 3½ ohm. sine wave response 3db. 140 cy to 175 kc for long pulses (30 microseconds) (Can be used for vertical blocking in TV). \$1.26
800 KVA GE. No. 7710417, 50 ohms pulse cable connection, 450 ohm output, 9500 voit input. 28000 V. pk. output. Bifilar . 19.50
300 KVA GE. 757296, 50 ohm pulse cable connection; 3.850 V. in 17,300 V. out (250 KVA @ Mmicro second) . 15.00
Western Electric Permalloy Core, 150 turns, No. 33 AWG. Primary and 150 turns secondary Toridal windings, D166638, 13% x 13% x 13% x 24% . 1.25 2 ½ ... 1.25
UTA11 X 124 T-2 (9280, 9262). (Can be used for horizontal blocking oscillator in TV) X 143 T-1) ... 1.50

TRANSFORMER

W.E. \pm D 166173 high voltage input transformer, impedance 50 to 900 ohms. Frequency 10 Nc. to 2 Mc. 5%" dia. x 7 7/32" high for APQ-13 \$12.00



UNIVERSAL JOINT ALUMINUM

11/8" long x 1/2" O.D. 1/4" ID

35¢

POSTAGE STAMP MICAS

5MMF	60MMF	220MMF	560MMF	.0027*MFD	
8.2	68	300	630*	.003*	
10	82*	360	650*	.0033	
20*	90	390*	680*	.0039*	
22	110*	400	750	.0068*	
	120*	470	800		
39	150*	488*	.001MFD	.01	
47	180*	500*	.0016*		
50	185*	510	.002		
56	200	525*	.0022		
* Silver	Mica				

* Silver Mica

Price schedule

5MMF to .001MFD — 5¢
.0012MFD to .0027MFD — 7¢
.0029MFD to .0068MFD — 12¢
.0082MFD — 16¢ Silver Mica Silver Mica Silver Mica .01MFD

DELAY NETWORKS. 1400 ohm, in small caus (look like 1.F.) made up with ceranicans and R.F. chokes. Ideal for making pulse generators, etc.

T113—approx. 1.2 micro second delay. 856

T114—approx. 2.2 micro second delay. 856

T115—similar to T114 with ten brought out. 856

OIL FILLED CAPACITORS

MFD	N D C	Price 1	MFD	V.D.C.	Price
MFD	V.D.C.				
. 1	25,000	\$14.95	.2	750 V.A	
. 375	16,000 a	nd .75	(2	,200 V.D.	
	8,000	14.95	10	2,000	4.25
. 1	12.000	4.95	10	1,000	1.75
. 1.	7,500	12.50	8	1.000	1.50
. 1	7,500	1.95	4	1.000	1.00
.11	7,000	2.45	3	1,000	.80
. 1	7,000	1.85	2	1,000	.65
. 02 02	7,000	1.55	.05	1,000	. 29
. 1	6.000	1.75	1	800	.40
.0303	6,000	1.65	4	600	.69
. 1	6.000	9.50	2	600	.39
.01	5,000	1.35	1	500	. 29
.25	3,000	1.75	. 5	500	.24

FILAMENT TRANSFORMER

WESTINGHOUSE #6D4298

Tested at 34,000 volts Pri. 115 V. A.C., Sec. 5V@6.5 Amp. ONLY \$8.50



CHOKES

400 MA. 12 H	enry 90 Ohms,	6,000 V.I	O.C. Test.
Hermeticall	y Sealed. 4½"	x 5%" x	4 1/4 ", 12
110MA. 9 Henr	rv 3" diameter		

ALLEN SET SCREWS

	6-32x1/8	10-32x1/4
4-40y1/8	8-32x1/8	1/4-20x1/2 1/2-16x3/8
4-40x3/16	8-32x3/16	1/2-16x3/8
Ali sizes		\$1.50 per C
Wrenches (2-56	out of stock)	
Allen Socket F	lead Screws, stainl	ess steel, 10-32 size
3/8'', $1/2''$, $1/1$	/8"	\$3 per C

Wrapped-BALL BEARINGS-New

Mfg.	ID	OD	Width	Price
Fafnir 33K5E ND 38 Timken	3/16" 5/16" 1/2"	1/2" 1 3/64" 1 3/8"	5/32" 9/32" 7/16"	25; 45; 85; 1,25
ND5202C13M ND 88503 MRC 206SF Fafnir 545	1/2" 43/64" 1 5 324 2 1/6"	1 3/8" 1 37/64" 2 7/16" 2 5/8"	1 3/8" (dual) 21 32" 5/8" 15/32"	1.25 1.00 1.25 1.00

NEEDLE BEARINGS

	1D	OD	
B88 1/2" wide	1/2"	11/16"	25€
B108 1/2" wide	5/8"	13/16"	30€
GB34 X 1/4" wide	3/16"	11/32"	25 €

HARDWARE ASSORTMENT — (mostly brass) —screws, nuts, washers, solder lugs, etc.
3 lbs. \$1.00

ALLEN BRADLEY TYPE J POTENTIOMETERS

THE IS 6/								2000
DUY			Linear	Taper				and the t
Resis. 500 OHMS 1.5K OHMS 2K OHMS 2.5K OHMS 2.5K OHMS 10K OHMS 25K OHMS	1/4" SD 5/16" SD 1/4" 1/8" SD 1/8" SD 1/8" SD 1/8" SD	hing Lengs 1/4" 1/4" 1/4" 1/4" 3/8" 1/4" 5/8"	M440424-12 430116-9 440424-11 M254161-2 252729-36 CBZ631623-10 2275-CRA	100K 100K 100K 100K 500K 250K	OHMS MEG. MEG.	7/16" 1/4" SD 1/4" SD 3/8" SD 1/8" SD 1/8" SD 1/8" SD 1/8" SD 3/8"	3/8" 3/8" 1/4" 3/8" 1/2" 1/4" 1/2"	433196-4 440424-29 430116-26 253729-15 CBZ631497-10 253729-21 427471-1 9032105
50K OHMS	1/4" SD	1/4"	440424-13	SD., 1	indicates	slotted shaft	t for screw	ariver

MINIMUM ORDER \$3

All Orders f.o.b. PHILA., Pa.

ELIANCE MERCHANDIZING CO.

Arch St. Cor. Croskey, Philadelphia 3, Pa. Telephone Rittenhouse 6-4927

RG 8/U NEW-UNUSED 52 OHM COAXIAL CABLE 4¢ A FOOT 500-2,500 feet \$40.00 per M 3,000-5,000 feet 35.00 per M 3,500-10,000 feet 30.00 per M 10,500-20,000 feet 27,50 per M over 20,000 feet 25,00 per M COAXIAL FITTINGS ocket 40¢ Plug 40¢ Angle Adaptor SO-239 PL-259 20¢ 83-IR 83-ISP M-359 83-IAP PL259A, 83-1SPN, 83-1J, UG21U, UG22U, G, UG85U Baby 'N' plugs ... 40¢ each fittings, UG85U Baby 'N'' plugs ... 40¢ each UG87U Baby 'N'' Socket, Gold Plated with Hood Attached ... 50¢ each

A CONTROL OF LANGUAGE TO THE



831T, Tee

PRECISION RESISTORS

1% OR BETTER

Any Order For
100 pieces 10% Off
1000 pieces 20% Off

	/4	WATT-	—25¢	
6.68 10.48 10.84 11.25 11.74	12.32 13.02 13.52 13.89 14.98	16.37 20. 62.54 79.81 105.8	123.8 147.5 220.4 301.8 366.6	414.3 705 2193 10,000 59,148
	1/2	WATT-	-25¢	
.250 .334 .502 .557 .627 .76 1.01 1.53 2.04 2.25	11.1 13.15 46 52 55.1 75 97.8 125 180 210	235 260 270 298.3 400 723.1 2,500 2,850 3,427 4,000	4,451 5,000 5,900 6,500 7,000 7,500 8,000 8,500 10,000 14,825	15,000 15,750 17,000 20,000 25,000 30,000 100,000 150,000
	7	WATT-	-30¢	
1.01 2.58 3.39 5	5.21 10.1 10.9 100 270	1,250 3,300 5,000 7,000 9,000	18,000 20,000 50,000 55,000	65,000 70,000 75,000
	1	WATT-	-40¢	
100,000	128,000	180,000	470,000	600.000

1 Megohm, 1W, 1%, 65¢, 5%, 40¢

Mounting Brackets—(Bakelite) for selsyns and differentials shown below, 25c pair

SELSYNS



ONLY **7.**25 pair #C78248

115 V., 60 Cyc., 3¼" dia. x 4½" hody. Used in Pairs for Remote Control. Also 50 V., 50 Cyc. \$4.75 pair.

SELSYN DIFFERENTIAL ONLY \$9.25 ea. #C78249



115V., 60 Cyc.
Used between two #Cf8248's as dampener. Can
be converted to a 3600 RPM Motor in 10 Minutes.
Conversion sheet supplied.
Also 50 V., 50 Cyc., \$1.50 ea.

PARTS FOR EVERY LABORATORY AND FOR THE SMALL MFGR.



FREE RECTIFIER **OFFER**

#2-THERMOSTAT G. E. 10 AMP.



Adjustable to within 1°F, in range 135°F, to 185°F, with scale and knob. Contacts 110 volt. Good for heating wax, compound, in tanks also oven control, etc.—Quantity in stock: 1433.


#1-TERMINAL STRIP, 6 TERMINAL



5 x 1" by 1" high overall, hard black bakelie moulded, with \$x 32\$ brass studs, 6 lockwashers Good heavy or light wiring. Mours of the avy or light wiring Mours of the avy or light wiring Mours of the avy or light wiring Mours of the average of t


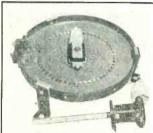
#99A-1600 Mrd. 12 volt: Quantity: 1288: Very Special at 49c.



BRAND NEW NAVY SURPLUS 14 INCH RHEOSTATS

Any voltage up to 600 volts—9.2 amperes continuous duty — 10 OHMS — EXTRA LONG SHAFT. Can be banked in socies or parallel.

#92A—Extra cost feature is linear ampere rating. Every section down to one ohm is wound for same current as the whole Rheostat—9.2 ampere to 9.2 ampere, no drop. Price—\$5.45 ca.

#79A-HEATER VULCAN D5

Ring 2" O.D. 1" I.D. \(\lambda'\) thick, fully armored, with upstanding porcelain bushing insulators \(\lambda'\) a" high for two terminal leads, \(35\mathbb{V}\), \(55\mathbb{V}\), \(65\mathbb{V}\) designed for two in series on 110V. Excellent for small compound heaters, wax heaters, small enough to hold and pour from. Liquid-proof design, easily installed in any pot or ladle, small tank, stamping die. Quantity in stock: 2.914. Priced at 19c, each.

STOCK UP ON AIRCRAFT LAMPS AT THESE EXCEPTIONAL BARGAIN PRICES

l	Ouan-					List	Оиг
	tity	Mfg	r. Number	Base		Price	Price
	3.840	West'	hse. 1747	Single Contact 50CP	12-16 V.	\$1.05	\$.21
		Silv	ered Bowl				967
	4.800	West'	hse. 1745	Single Contact 32CP	12-16 V.	.90	.18
		Silv	ered Bowl				
	2,000	West'	hse. 308	Red Double Contact 21C	P 28 V.	.55	.11
	2,400	West'	hse. 311	Single Contact 50CP	28 V.	.55	.11
	1,700	West'	hse. 986	Double Contact 2.5 Amp	. 28 V.	1.05	.21
	5.000	G. E.	77	Single Contact 3CP	12-16 V.	.30	.06
	28,000	G. E.	78	Double Contact 3CP			.06
	5,000	G. E.	M306	Double Contact 15CP	28 V.		.09
	11,000	G E.		Red Single Contact 21CP		.55	.11
	8,000	G. E.		Double Contact 32CP	28 V.	.55	.11
	6,500	G. E.	RP11	Flasher 5 Filament GE #	1039		
				Single Contact 6.6 Am		.50	.10
	34,000	Tung-		Double Contact 3CP	28 V.	.30	.06
		Tung-		Double Contact 6CP		.35	.07
				Single Contact 50CP		.55	.11
	All pack	ced in o	original pack	rage of ten; fifty packages	to a cart	on.	
	Minimu	m orde	er: 10 of any	one number (one packag	e).		
		Ex	tra 10% dis	count on any assortment	of 1,000		
		Ex	tra 15% dis	count on any assortment	of 5,000		
		Ex	tra 20% dis	count on any assortment	of 10,000		

#89-CANNON SOLENOID



This item just must be seen and tested to be appreciated. At 6 volts, draws 1-1/3 amperes, has ½ pound pull at ¾ in. stroke; 2 pound pull at ¾ in. stroke. At 12 volts, draws 2-2/3 amperes, has 1 pound pull at ¾ in. stroke. At 24 volts (rated voltage), draws 5 amperes, has 2 pound pull at ¾ in. stroke; 3 pound pull at ¾ in. stroke; 3 pound pull at ¼ in. stroke; 3 pound pull at ½ in. stroke; Very compact, easily mounted. Tapered shaft that goes clear through back of the case. Quantity; 2200—Priced at 69e each—Probably our greatest bargain.

NON-INDUCTIVE RESISTORS GLASS FERRULE

	GLA	SS FERRULE		
Quan.	Value	Wattage	Length	Price
196	2 Ohm	8 15	216"	\$.15
213	10 Ohm	8 15	216"	.15
65	10 Ohm	s 120	215° 215° 958°	.45
43	15 Ohm	s 120	95%	.45
450	25 Ohm	8 15	212	.15
780	40 Ohm	s 20	212	.20
72	150 Ohm	s 120	95%"	.45
20	500 Ohm	s 15	212"	.15
140	500 Ohm	s 90	716"	
255	800 Ohm	8 120	95%	.40
165	1000 Ohm	8 15	9/8	.45
75	2000 Ohm	s 15	212"	.15
140	4000 Ohm	8 20 -	3,2	.15
320	9000 Ohm	s 35		.20
	OUGO OHILL	8 30	41/2"	.25
	PORCELAIN	ENAMEL FE	DDIVE	
174	10 Ohm	s 100	RRULE	
144	15 Ohm		95/8"	.45
206	150 Ohm:		95/8	.45
-00	250 Onin	s 100	95/8	.45
	19	ERRULE		
1,100	1.3 Oh		0.7	4-
820	18 Oh		8"	.45
22		ms Type A	21/2"	.15
54	250000 Oh		8"	.40
13			12"	.50
39		ms Type B	10"	.45
39			10"	.45
	Ind Ore	ms Type B	12"	.50
Daige 8	ook regular v	V.W on hand.		

#85-G. E. THYRITE K-522332 (M)

Diameter 3 in. Thickness 1/8 in. Hole 1/2 Good voltage regulator, 3rd harmonic

Good voltage regulator, 3rd narm generator. Current: 5 ma. at 18 volts; 10 ma. at 23 volts. 20 ma. at 29 volts; 40 ma. at 36 volts. Rating; 3 watts maximum in air. Quantity: 2,808—Priced at 25c, each. We have sold these at 81, right along.

#82-G. E. THYRITE K-8396832-I.

Diameter 1%". Thickness \(\frac{\pi}{n} \). Hole \(\frac{\pi}{n} \) Thickness \(\frac{\pi}{n} \). Hole \(\frac{\pi}{n} \) Hole \(\frac{\pi}{n} \) armonic generator.

Current: 5 ma. at 21 volts

10 ma. at 24 volts

20 ma. at 28 volts

40 ma. at 33 volts

Rating 1\(\frac{\pi}{n} \) watt maximum in air.

#80-EDISON FIXED **THERMOSTAT**

THERMOSIAI
Hermetically sealed. Explosion proof. 135
degrees Fahrenheit, normally closed. Opens
above 135 degrees. Sealed in glass. One
ampere contacts. Fine for fire alarm system. Another 29c. bargain. Lists for over
\$3.00. Quantity in stock; 460.



#12—CARBON PILE VOLTAGE REGULATOR

VOLTAGE REGULATOR supplied with 30 watt, 50 hm slide wire adjustable resistor; the voltage regulator has an even 18½ volt output with a variable input of from 21 to 30 volts D.C. The coil and upper bed make a very ET-FICTENT magnetizer if supplied 80 to 100 volt D.C. and an efficient DEMAGNETIZER on 110 A.C. The regulator can be disassembled for the above purpose in less than 1 minute. Can also be used as a small magnetic chuck—Quantity in stock: 10,500. Special price for both regulator and resistor: 89c.

#4-300 OHM WIRE WOUND POTENTIOMETER

watts, 1%" diameter x %" ep. ½" shaft above threads. Quantity in stock: 1,690— Price 22c. We also have 437 of the 200 ohms—same price.

SELENIUM RECTIFIER, FULL-WAVE BRIDGE

Up to 90 volt A.C. input, 20 plate, output, 150 m.a. continuous duty.

Special \$1.35 each. Only 350 available

#76—60 DEGREE FAHRENHEIT THERMOSTAT

Fixed thermostat. Closes at 60 degrees and opens at 65 degrees. 10 ampers contacts. Snap action. Made by Klixon. Excellent for auto heater control. Quantity in stock: 2,500.

—We are closing these out at 22c. each, less quantity discounts.

DONGAN Navy Type Ignition TRANSFORMER

Catalogue No. 2705T
This is a 115 wait enclosed job with a 460 volt primary nd a secondary of 5000 volt at 20 ma.
Can you adapt it?

Special \$2.45 each

FAMOUS ROBSON-BURGESS CONDENSER TESTER AND CIRCUIT CHECKER

Attractively cased item for use on 110 A.C. or D.C., consisting of 125 voit full-wave bridged rectifier, resistor switch and neon light with six foot line-cord and plug and test leads. This is one of the best inexpensive condenser testers, because it actually puts D.C. current into the condenser, our price, while 300 last, \$2.95 each. Original cartons.

TERMS

Net 30 days to rated mfgrs and to schools. All shipments F.O.B. New York. 20% deposit on C.O.D. orders.

EXCESS INVENTORY CORP.

56 LISPENARD ST.

Tel. Walker 5-9135-9136

NEW YORK 13, N. Y.

Finest of surplus at a fraction of cost

PEAK ELECTRONICS CO.

Industrials Schools - Labs

50 MICROAMP METER



This is the exact meter utilized in the General Electric model YMW-1A Lab-Type Unimeter.

- 50 Microamp Movement ± 2%
 2500 Ohms Resistance ± 2%
 Knife-Edge pointer
 Uncrowded Multi-Range Scale
 4 x 4½" Black Bakelite Case
 50 Microamp scale available
- Microamp scale available at 25c additional

BRAND NEW only \$9.75 ea.

METER SPECIALS

2" GF	0-30 amps, D.C	2.95
2" GF	0-1 amp RF (enternal thermo)	2.95
	0-5 ma (amp scale)	1.95
	0-1.2 ma (0-100 scale)	2.49
	O-1.2 mu (C-103 scule)	
2" GE	0-1 ma (vc.) scile)	2.95
	en 0-3V DC (1000 ohms-volt)	2.45
2" Wes	ton 150-0-150 Microamps	3.49
3" Wes	stighouse 0-50 amps. AC	4.95
3" Trip	lett 0-75 amps. AC	3.95
3" WE	0-80 ma DC	2.95
	200-0-200 volts DC	2.95
	lintock 0-1 ma	3.95
	stinghouse 0-2 ma DC	3.95
3" Wes	stinghouse 0-20 ma DC	3.95
3" GE	0-15 ma DC (square)	3.95
	stinghouse 0-150V AC	3.95
	ning time meter 110 v. 60 cy	7.95

DAVEN AUDIO FREQUENCY METER MODEL 837E



Direct readings from 0-30 KC in 4 separate ranges on 6" Weston Model 27! Fan Meter. Built-in voltage regulated power supply operates from 115 volts 60 cycles, has high input impedance. With pick-up can be used to determine frequency in vibration tester. With suitable mixer can check deviation of R.F. carrier from standard. Mounts of 83%/x19" rack panel. Complete with tubes. Slightly used but perfect. Only....\$59.50

"A POWERFUL BABY"

This plate transformer built to rigid Signal Corps spec. Input 118 volts, 25 to 60 cycles. Has 2 separate 118 volt primaries and can be used on 110 or 220 volts. Secondary 800 volts center tapped at 775 mills. Exceptional regulation even when loaded to 900 mills! Fully cased—4 mtg holes, 37 lbs. net wt. 6½ x 6½ x 7½. Peak value at 7.95. 10 for \$70.00

CHOKE BARGAINS

6 Henry 45 MA 300 ohms	39
8 Henry 75 MA 230 ohms	59
8 Henry 160 MA 140 ohms	39
10 Henry 200 MA 150 ohms	
1.5 Henry 250 MA 72 ohms	
10 Henry 350 MA 60 ohms	
6 Henry 550 MA 30 ohms 4.	95
4.3 Henry 620 MA 42 ohms 4.	95
10 Henry 750 MA 95 ohms	50

FILAMENT TRANSFORMER

Two separate 118 volt, 25 to 60 cycle primartes. Can be used on 110 or 220 volts. Secondary 5 volts at 15 amps. Built to Signal Corps specs. Fully encased, 5 x 41/4 x 5%. Net wt. 10 lbs. \$3.75 each, 10 for \$30.00.

VERSATILE POWER

These transformers have many uses—filament, isolation, stepdown, bias, etc.
All have 2 separate primaries for 110/220 volt 25-60 cycle operation. Primaries. Can be used in series or parallel.
3 Choices of Secondaries:
Type 501—115 volts 500 mills and 6.3 volts 5 amps.
Type 505—115 volts 500 mills and 6.3 volts 2 amps.
Type 505—0.70-75 volts at 2.5 amps. (35-37 v. in. series)

series)
Fully encased—4 mtg. holes, $5\frac{1}{8} \times 4\frac{1}{4} \times 5\frac{1}{8}$.
Your cost any type.
10 for \$17.00

AN/APT-2 AIRCRAFT RADAR JAMMER



425-750 mos. Contains 10 425-750 mos. Contains IU tubes:
(1)—807 (2)—703A (2)—
6AC7 (2)—6AG7— (2)—
5R4GY (1)—2x2 (1) 931Unit has blower motor and 400 cycle pwr supply complete with all tubes etc.
BRAND NEW. \$19.95 each

HIGH VOLTAGE—HIGH CURRENT PLATE



PLATE

1500-0-1500 volts at 1.5 amps. Tapped at 1350 and 1250. Pri. 110/220 volts 50/60 cycles in 2 Separate windings. Built to rigid Navy specs by American. Suitable for broadcast transmitters, induction heating, etc. Size 10" x 10" x 7" x.w. 125 lbs. \$67.50 each.

WARLARIE CERAMICONE

		V	AKIABI	LE C	LEKAM	IIC	ONS	
1.5	to	7	MMF	.24	1 .4 to	30	MMF	.24
3	to	13	M M F	.24			MMF	
5	to	20	MMF	.24	10 to	110	MMF	.39

AMERTRAN FILAMENT TRANS. 5.25 volts at 21 amps. plus 2 x 7.75 v at 6 amps. Pri. 110 v 60 cy. H.V. Ins. 6" x 5½ x 4½". . 7.75

SOLA CONSTANT VOLTAGE
Transformer, input 95 to 130 output 115v. 350 VA.
2.9 amps. 29.95

AMERTRAN 500 VOLT PLATE 1800 volt et at 300 ma. Pri. 110 v. 60 cy. 6" x 5½". 6.3 v 21 amps. Hermetically sealed. 110 v 60 cy. Pri. 4.75



4 Stator Single Rotor. 0-360 Degrees Rotation Only 2.95 each

I-196-B SIGNAL GENERATOR 175-220 Mcs. With Tube and Carrying Case, \$5.95.

STEPDOWN TRANSFORMER

220-110 volts. 110 watts. Fully encased. 51/8 x 41/4 x 51/8. 110V. 60 cycle......\$2.49 each

WIRE WOUND RESISTORS

5 Watt type AA, 20-25-50-200-470-2500-		
4000 ohms	.09	ea.
10 watt type AB, 25-40-84-400-470-1325-		
1900-2000-4000 ohms	. 15	ea.
20 watt type DG, 50-70-100-150-300-750-		
1000-1500-2500-2700-5000-7500		
10000-16000-20000-30000 ohms	.20	ea.
30 watt type D1, 100-150-2500-3000-4500-		
5300-7500-18000-40000 ohms	.24	ea.

1% PRECISION RESISTORS 200-2500-5000-8500-10000 ohms \$.39 ea. 100000-95000 ohms .49 ea. 100000-750000-1 mee .89 ea.

H. V. VARIABLES

250 per section .1	is,
	95
250 per section .051	95
75 MMF .3 Spacing 9.	50
250 MMF .5 Spacing 19.	50
150 MMF .5 Spacing\$17.	50

W. W. POWER RHEOSTATS

Dual 20																		
150 Ohm																		
50 Ohm																		
300 Ohm																		
25 Ohm	25	W	att	 		4			 			 		٠			.39	

Veltage Regulated Power Supply—input 110 v. 60 cy. Delivers 150 v. DC—Well filtered (3 chokes) uses VR 150 and 6X5. Has extra 6.3 v. winding. Swell for eco's. freq. meters, etc., 16x3%x5 with tubes. Only ... 6.95

HIGH VOLTAGE - HIGH CURRENT LOW PRICE MICA CAPACITORS**

XR .0001 MMF 5 KV	75
F2L .0005 MMF 5 KV	85
F2L .001 MMF 5 KV	
F2L .0015 MMF 5 KV	1.69
F2L .003 MMF 5 KV	1.00
XS .005 MMF 5 KV	2.50
F3L .007 MMF 5 KV	2.75
	. 2.73
	4.50
	4.75
	3.50
F3L .0025 MMF 6 KV	. 3.60
F3L .003 MMF 6 KV	3.75
*MX .004 MMF 6 KV	4.95
F3L .0005 MMF 8 KV	. 2.90
F3L .006 MMF 8 KV	. 3.00
*PL.001 MMF 8 KV	4.95
F3L .0015 MMF 8 KV	3.50
F3L .002 MMF 8 KV	4.00
F3L .0025 MMF 8 KV	4.50
F3L .003 MMF 8 KV	5.00
F3L .004 MMF 8 KV	5.50
F3L .005 MMF 8 KV	6.00
F3L .01 MMF 8 KV	6.50
*G2 .0005 MMF 10 KV	5.95
*G2 .002 MMF 10 KV	6.95
XA .0005 MMF 12 KV	4.90
*G4 .008 MMF 12 KV	20 50
*G4 .0033 MMF 20 KV	22.50
*C4 .0035 NIMIT 20 IVV	.22.30
*G4 .004 MMF 20 KV	. 24.50
	.32.50
*G4 .0015 MMF 25 KV	. 32.50
**All ratings_"working-voltage."	
Tolerance ±5%	
*Ceramic case.	

MEGOHM METER

MEGOHM ME
Industrial Instruments Model
L2AU 110/220 volts 60 cycle
input. Direct reading from
0-100000 megohms on 4"
meter. Can be extended
to 500000 megohms
with external supply.
Sloping hardwood
Cabinet 15"x8"x10".
Brand new with tubes
plus running spare
parts including extra
tubes. Great value
only \$69.95.



SPERTI RF VACUUM SWITCH

9200 volts peak, 8 amps. Used as antenna switch in Collins ART 13. BRAND new\$1.75



U. H. F. COAX. CONNECTORS UG12U-831R-831J-UG21U-831AP 831SP .39 ea.

Precision 15 Meg. 1% Accuracy Resistor. Non-inductive, 1 watt, hermetically sealed in glass .39c each; 10 for \$3.50.

OIL CONDENSERS

OIL CONTENTS											
1.1	mfd	250 vac85	1.1/.1 mfd 7000								
5	mfd	150 vac49	vdc-2.25								
- 1	mfd	600 vdc29	.1 mfd 7500 vdc-1.95								
2	mfd	600 vdc39	1 mfd 7500 vdc-9.25								
4	mfd	600 vdc59	4 mfd 8 kv dc-19.95								
3/3	mfd	600 vdc79	.01./.01 mfd 12 kv								
10	mfd	600 vdc— .95	dc-5.75								
14		600 vdc-1.35	.005/.01 mfd 12 kv								
2	mfd	1000 vdc— .79	dc-5.50								
4	mfd	1000 vdc95	.03 mfd 16 kv dc-5.75								
15		1000 vdc2.95									
2			.65 mfd 12,500 vdc—12.95								
- 1		2000 vdc1.45									
2	m fd	4000 vdc5.50	.75/.35 mfd 8/16 kv—12.95								
3		3000 vdc-3.95									
1	mfd	5000 vdc-4.50	.02 mfd 20 kv dc-7.95								

1 KW TRANSTAT or Stepdown Transformer

IIO/220 volts 60 cycle input. Output variable plus or minus 10% of 115 volts at 8.5 amps. Also can be connected to give different voltage combinations. Brand new....Special 9.95



MIDCET WADIABLE BARCAING

MIDGEL VAKIABLE BAKGAL	143
Hammerlund MC 250S 250 mmf	\$.60
Hammerlund MC 320S 320 mmf	79
Hammerlund APC 100 100 mmf	39
Bud MC 913 35 mmf., D.S	1.25
Hammerland HF 15 15 mmf	39
National TMS 150 mmf	79

Tremendous stocks on hand. Please send requests for quotas. Special quantity discounts. Price f.o.b. N. Y. 20% with order less rated, balance C. O. D. Minimum order \$3.00.

PEAK ELECTRONICS CO. 188 Washington St., New York 7, N. Y.

PHONE CO-7-6443 DEPARTMENT EA SEND FOR BULLETIN

SURPLUS-CLEARANCE SALE-CHOICE ELECTRONICS



5-Meter Walkie-Talkie


Malkie-Talkie

Model BC-322 Transceirer; simple, popular communications unit. Freu. range 52-65 mc. Uses only two tubes, types 33 and 30. Includes a 5 mc. crystal in a crystal calibrator circuit. Range 5 to 50 miles, depending upon location and a diritude. Operates from single battery block (not supplied) available from mfr., or other sources. Supplied with handset, less antenna, battery. Excellent condition.

PRICE, EACH \$20.95

Telescoping Antenna for Above \$2.00

12 V.D.C. P.A. SYSTEM

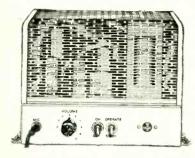

- 25 watts peak power output amplifier. Powered from 12 volt storage battery, drain 6 amps."operate"and only 2 amps. in "standby."
- Mfd. by RCA, supplied with RCA close-talking Dynamic microphone, miscellane-ous accessories and instruction booklet. Output Impedance—15 ohms (2—8 ohm

Ideal for sound trucks, portable amplifier requirements, boat or ship installations, etc. Beautifully constructed, shock mounted, and compact. Dim: 114"x8"x6%". Uses a 647 driving a 68NY-GT, driving 2-616 beam power tubes. Self-rectifying 12 volt Vibrapack within amplifier. Equipment is New, surplus, and guaranteed. With tubes.

PRICE, with misc. accessories and DYNAMIC MICROPHONE \$54.75



32 VDC 110 AC CONVERTER

Mfd. by Kato Engineering, for marine or farm installation. Rotary type, compact and ruggedly built for continuous duty. Rubber shock mounting on filter case, with complete input and output filtering. Output 110 volts, 60 cycles AC, .225 KVA, but will operate efficiently on loads up to 300 watts. New units only.

PRICE, EACH Quantities, 10 or more, Each \$32.00

RADIO TRANSMITTERS Immediate Delivery from Stock

BC-325 Transmitter, 400W.-AI, 100 W.-A2 & A3. 1.5 to 18.0 me. M.O. or X'tal control on 6 frequen-cies. Operates from 110/220/1/60c. AC. With tubes in excellent condition.

PRICE, EACH\$400.00

BC-447, 300 W. AI, 2-Channel Transmitter. Complete and self-contained in one cabinet, 35x29x72" H., includes RIF sections, power supplies, and control equipment. Freq. range 4.0 to 13.4 mc. Operates from 110/220/V/1/50-60. AC. With tubes.

PRICE, EACH\$425.00

TCR-Radiomarine Transmitter, 125

watts (conservative) A1, A2, & A3. For ship or shore station radio telephony, 6 channels in 2 to 3 mc band controlled by remote control box supplied. Complete RF, modulator and power supply Gor 110 or 220 V. 50/60 cycles AC) in one cabinet. Excellent condition, with tubes and remote control box. mote control box.

BC-319-A Transmitter, CW only 300 watts output.
Preq. range 4.0 to 13.4 mc. Operates from 110/220 volts, 60 cvoles AC. Excellent condition.
Satubes, PRICE EACH
Wildox, 96-200A 2-40W Rif section. Large cabinet with complete RF end containing the VFO, intermediate sections and PA stage. Almost new, but lacks PA inductance only. Power supply separate unit not available, but can be built. Less tibes, FRICE
RMCA 8023 HF Ship Transmitter. 200 watts output. Al and A2. Freq. range 4.0 to 20 mot. Operates from mg set (not supplied) in F main transmitter (RMCA type 8024). With tubes, but not acceiver. Excellent cond. PRICE, E350.00

mitter (RMCA type 8024). With tubes, but no radio receiver. Excellent cond. PRICE, EACH \$350,00 MACKAY SHIP TRANSMITTERS. The following Mackay ship-radio types are available: 150-AY, 151-A1, 149-A, 136-A, 104-M, 147-M. Some new, most in excellent condition. Write for prices. LINK F M Transmitter-Receiver, 70-100 MC. Model 1498 DC, Wall style cabinet containing transmitter, receiver and 14 V.D. C. power supply, bandset. Din: 34"x21"x11". NEW CONDITION. Complete with tubes, crystals, special telescopic antenna, instruction book. 50 W. output. PRICE EACH...\$600.00 NOTICE: Price quoted cbove do not include crating or packing. Price for packing will be quoted upon specification as to whether export or domestic packing is desired. BC-620 FM Transmitter-Receiver. Mobile or portable unit main part of SCR-510. KEW, with tubes and complete crystals but less accessories or power supply). Export packed. PRICE EACH...\$50.00 BC-603, 604, 683, 684, Transmitters, Receivers, Main components of SCR-508, 528, and 608, 628 FM mobile installations. Dynamotor and tubes supplied.

FM module instantances supplied Receiver, w/dynamotor. PRICE, New 18:-603 Receiver, w/dynamotor. \$40.00 tubes \$40.00 \$30.00 PRICE. New 10:-603 Receiver, w/dynamotor, tubes . \$40.00 PRICE. Used but excellent condition . \$30.00 PRICE. New BC-604 Transmitter, w/dynamotor, tubes, crystals . \$50.00 BC-683 Receiver, New w/dynamotor and tubes, EACH . \$10.00 BC-684 Transmitter, New w/dynamotor, tubes and crystals. EACH . \$50.00 BD-72 Switchboards. 12-position field switchboards. New and complete, packed two to case. EACH . \$50.00 BL-1/GT Large Airport Switchboard. With separate power supply, operates from 110 V. AC. 50-60 Cyoles. 10 charge telephone batteries and operate supply. Supprobact. Both in handsome metal cabinets, approbact. Both in handsome metal cabinets, each country and the supprobact. Both in handsome metal cabinets, approbact. Both in handsome metal cabinets, each country and the supprobact. Both in handsome metal cabinets, each capital cabinets, approbact. Both in handsome metal cabinets, each capital cabinets, and capital cabinets, approbact and processes and capital cabinets.

eapt. PRICE, per Switchboard and Fower Supply.\$300.00

MISCELLANEOUS SPECIALS

APQ2 Transmitter, only, with tubes. Almost New. \$37.50 APQ2 Transmitter, only, with tubes. Almost New Each \$37.50
SN-1/APQ5 Synchronizer, with tubes. Almost New Each \$37.50
Collins Autotune Remote Control Unit, Type 4°0L
23377. Has 10-position dial selector for remote control of transmitters, plus two meters for channel indication and volume level, and speech amplified stages with limiter stage. Good cond. Excellent and accessories, but with tubes. Excellent and accessories, but with tubes. Excellent condition. EACH SCR-551-T2 D.F. Equipment, consists of large metal calinet with rado receiver Nat'l Nc-100-A, Input Amplifier and Electronic Switch, Oscilloscope and P.C. Amplifier (for sisual DP indication), plus self-contained 140, 460 cycle AC power supply. With tubes of the accessories or loop. Excellent condition. Price. EACH and "G" bands. Battery operated. With rubes, but less batteries or phones. Excellent condition of the self-contained 140, and "G" bands. Battery operated With rubes, but less batteries or phones. Excellent condition. Grant G

EXTRA SPECIALS!!

VT-127A. platinum grid tubes. New. Each \$2.50 Antenna Relays, GM 4P-DT, 250 ohms. Each . 95¢ Adlake Time Delay Relays, type 902-72-1, 220V, 50/60 cycles, normally open. EACH....\$4.95 Same as above, but type 1040-65-4, 110 Volts.

Amerran Reactor, type W, .04 H., 10Kv. RMS test, 120 cycles, DU resist. 0.24 ohms, 2.4 amps. Each Side Priple Potentiometers, 80 ohms per section; 2 Watts each section; for attenuators, etc. Each .90c. Allen-Bradley dual pois, type J, 25M/2M, 1-watt. Each .55c. Same as above, but 5M/2M. Each .55c. Same as above, but 5M/2M. Each .25m/4/4.000 Brandey tutal pols. (356 as above, but 5M/2M. Each ... 556 ard Brand Capacitor, type 23F47, 2 mrd/4,000 \$3.95 Same as attor.
Standard Brand Capacitor, type 23F41, 2 33.95
Standard Brand Capacitor, M-7466764-2, 2 mid/15,0060V. Each
Standard Brand Capacitor, M-7466764-2, 2 mid/15,0060V. Each

\$10.00

SCR-536 HANDY-TALKIES



We have just a few of these popular Handy-Talkies, and they won't last long. All are in very excellent condition, and complete with crystals (receiving and transmitting) and batteries. All are in top op-erating condition, and preset at various operating frequencies ranging from 3.5 to 6.0 mc Some available for operation in 80 meter ham band. We will supply units with matched frequencies as long as quantity permits. First come, first served!

PRICE, EACH \$49.50 Extra Set Batteries (A&B) ... \$2.50




FREQUENCY METER TS-69/AP

Frequency range 400 mc to 1.000 mc, continuous. Ideal for labs, schools, or for hams experimenting with eqpt, for civilian phone band. Black-crackle finished metal case, dim: 6x6"x22", contains variable length coax resonating cavity with crystal rectifiers and 0-200 micro-ammeter. Veeder - Root counter and callbration-charts insure extreme precision. Telescopic antenna, and coax line probe, with metal carrying case for entire equipment. New equipment.

COMPLETE, EACH \$42.50

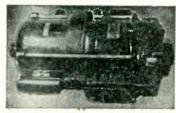AMPLIDYNE MG SET Motor 110/220, 60 C. A. C.



For Automatic or Remote Control of heavy equipment, Mfd. by General Electric. Generator is Type V-5875677, motor 73AB38; Navy type CG-21ABU. Generator delivers 250 volts. DC, 375 watts. Motor, 115 or 220 volts 1-phase, 60 cycles AC, rated at ¾ HP H/M-1725. Includes capacitor for starting, and instructions for 115 or 230 volt connections. Generator section can be removed, and entire assembly shortened to make valuable ¾ H. P. AC motor. Quantity sufficient to warrant this conversion.

PRICE, EACH. \$50.00

DECK ENTRANCE INSULATORS
Bowl and Flange Type
Manufactured by OHIO BRASS CO. for Army and
Navy use. Has heavy galvanized metal flange 8%"
diameter, powelain bowl set in rubber gaskets, top
bell is 6% in diameter. Brass feed-thru rod 11%"
long. Insulation distance between top bell and
flange is 41%". Individually packed in cartons.
Quantities available.

NEW, price each \$2.75 Spare porcelain bowl, only, each. \$.75

All Prices F.O.B. N.Y.C.


All Material Offered Subject to Prior Sale

280 Ninth Ave., N. Y. 1, N. Y.

TELEMARINE COMMUNICATIONS COMPANY

TRANSTATS"

Voltage Regulator

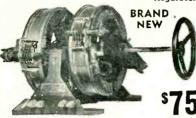

11.5 KVA: 50/60 cy. Commutator Range 0-115 V.
 Max. Amp. 100. Can be reconnected for 230 volts
 50 Amperes.

WESTINGHOUSE MOTOR

#1171198-1.4 Horse Power 21 Volt, 70 Amps. 1800 RPM Pump mounting on each end Ball bearing, compound wound 18" L x 8" H x 7" W. \$8.50 BRAND NEW

OIL FILLED CAPACITORS

UNI; 2 A . IMIQ (000 W V DC
CN35: 2Mfd 600WVDC Bathtub716
CN38: 1Mrd 600WVDC Bathtub49¢
CN42: 2 X .64Mfd 600V Bathtub30c
CN61: 3 X .1Mfd 600V Bathtub
CN72: 1Mfd 500V55c
CN65: .01Mfd 600V Bathtub
CN95: IMrd 200V Bathtub
CN103: 100Mfd 25WVDC Plug-In35c
CN104: .02Mfd 200WVDC Tubular10c
CN113: 3 X .22Mrd 600V
CN120: .046/.055Mfd 600V Bathtub15c
CNX01: .2/.035Mrd 500V
CNX02: 2 V 05Mtd Cylindrical

MICA CAPACITORS

.25 Mfd 500																			
.000051Mfd	3000 W	VDC																.3	50
.15Mfd 500	WVDC .																	. 2	5¢
.01 Mfd 120	0 WADC														٠	,		. 3	9¢
.115Mfd 20	0014ADC	TYDE	e.	I	ıL	1	1#	19	- !	31	н	Ι		٠.			S	3.	50

A.C. CAPACITORS

CN78: 2.5Mfd 450 VAC 41/2" x 2"D	\$1.75
CN112: 400Mfd 450VAC 5" x 2"D	\$1.75
CN204W: .366/.127/.055Mrd 330VAC	

RELAYS

R521: 24VDC SPST, 2A G.E. #55837ea. 25c R568: 6VDC 3PDT, 15A G.E. #B100.11ea. 50c R565: 24VDC DPST, 15A, Allied B04D32.ea. 30¢ R572: 24VDC SPST, 200A, Guardian #B7B.ea. 75c R561: 24VDC SPST, 15A, Allied B013D55. ca. 25c R563: 24VDC SPST, 200 A, A.B. #X89309.ea. 75c R533: 24VDC DPDT, 15A, G.E. #CR 2791.ea. 25c R552: 24VDC DPDT, 15A, Leach #1054ARW
R566: 24VDC DPDT, 15A, GM =13013ea. 30¢
R567: 24 VDC 3PDT, 15A, Allied
R559: 24VDC 4PDT, 15A, GM #13016ea. 35c
Best Part C 41 D1, 13A, GM #15010 ba. 309
R564: 32VDC, SPST, 75A, Leach #7220-32
ea. 70c
R526: 75VDC DPST. Struthers Dunn Norm.
Open 30Aea. \$1.35
Open 601
R571: 115VDC DPDT, Price #311, 1900 Ohms
ea. 70c
R522: 115VAC 3PST, 6A, S.D. #1CXX100
ea. \$1.75
R534: 115VAC DPDT, Thermal Time 40
ASST. III AC DIDI, Incimal Ilmo to
Sec. 2A
Roll: 20 VAC Annunciator Drop Type SPST
6 Ampea. 20c
6 Ampea. 20¢ R:00: 115VAC 10A 3PDT Allied #D0X1
Midd. Hover Lond of Dr. Milita Whom

HEAVY DUTY RESISTORS

WEST. WATTMETERS (NEW)

Type CS. 240V/60cy/lph 15 Amp., 3W....\$12.50 Type CS, 120V/60cy/lph 15 Amp., 2W....\$9.50 Type CA, 120V/60cy/lph 15 Amp., 2W....\$9.50 LORAN RECEIVER/INDICATOR Model DAS-1.

110V/60 cy. input. Complete with 32 tubes.
Uses 5CPI CRT as Indicator tube. Like

WESTINGHOUSE FLEXARC WELDERS

WESTINGHOUSE FLEXARC WELDERS
Transformer type, for single operator. These
welders have been used but are in the same condition as new. Fully guaranteed to operate satisfactorily, Operates at primary input of 440 or 550
voits, AC, single phase. Has output of 300 amperes.
Unit has current adjustment to fit wide range of
work. Machines have low input KVA and high
power factor giving more welding amperes output
for a given input KV-a or line capacity. Welders
are of sturdy construction enclosed in heavy sheet
steel, providing mechanical protection to the windings and internal connections. Unit is self cooling
and has built in circuit breaker to de-energize the
welder and also to give overload and short circuit
protection.

Special Price\$125

WESTON PORT. VOLTAMMETER



Model 280 Two Ranges 3 / 15 / 150 Volts and 3 / 15 / 30 Amperes. Ac-1% curacy Com plete with black leather carry ing case. Brand New. Special

\$21

60 CYCLE TRANS. AND CHOKES

POTENTIOMETERS and RHEOSTATS

#5673 15K 4W 11/2" Shaft W.W	00
#5[49: 5K 4W Screw Shart W.W 4/\$1.	00
#5039: 5K 4W 1" Shaft W.W	00
#1001: 5K 2W 1" Shaft Carbon4/\$1.	00
#1002; 2Meg 2W 34" Shaft Carbon 3/\$1.	
#1003; 75 Ohms 3W 1/2" Shaft W.W4/\$1.	.00
#1004: 6K/6K 3W 1/2" Shaft Carbon 4/\$1.	
50 Watts-25 Ohms, 40 Ohms, 50/50 Ohn	
300/300 Ohms, 400/400 Ohms, 10K Ohm	
1" Sharts. Your choiceea. 7	
25 Watts-2 Ohms, 25 Ohms, 50 Ohms, 225 Ohm	18,
350 Ohms, 500 Ohms, 3000 Ohms, 5000 Ohm	
20K Ohms; W.W. Your choiceea. 5	
The above are only a few representative samples	
the many THOUSANDS we have in stock. Let	u:
quote you on your requirements.	

AIR COOLED TRANS. (NEW)

Pennsylvania 10 KVA: Two insulated windings. 220/110 Volts. A remarkable value at. \$65.00 Westinnhouse. 460/230-230/115 Volts, 1½ KVA. Type JR. \$21.90 General Electric. 1 KVA: 00 cycle, 460/230-230/115 Volts. 1 KVA. User the second value of the s

Outdoor Distribu

General Electric 3 KVA; Type IIS; 3000/5200Y - 115/ 230. Style 3266596

In original Factory Cases \$36

Westinghouse CSP 2400/4160Y Volts to 120/240

71/2 KVA.. \$100 3 KVA..... \$50

11/2 KVA \$37.50

400 CYCLE TRANSFORMERS

TR1024; Pri: 115V 400 Cv. Sec: 700V 120MA; 2.5V 3.0A; 2.5V 3.0A; 6.3V 2.25A; 6.3V 2.25A; TR1016; G.E. Pri: 115V 400 Cy. Sec: 800VCT 159
MA: 5V 3.0A. Sl.00
TR1031; Pri: 115V 400 Cy. Sec: 700V 315MA: 200V 100MA; 6.3V 15A; 18V 600 MA; 5V 800 1.75A ... 127 400 Cy. Sec. 5.3V 500MA; 2.3V 1.75A ... 127 400 Cy. Sec. 787V 399A : 374V 46MA; 7.30V 170MA; 6.3V 600MA; 6.3V 900MA; 6.3V 150MA: 6.7V 5.5A ... \$1.00 TR1021; G.E. Pri: 115V 400 Cy. Sec. 6.3V 7.0A; 6.7V 900MA; 6.3V 300MA ... \$1.00

RESISTORS

.3 Ohms Dual 150 Watts Bracket. 60 .45 Ohms Dual 150 Watts Bracket. 60
4 Ohms 150 Watts "Ribflex" Ferrule600
20 Ohms 30 Watts Bracket
100 Ohms 50 Watts Bracket
250 Ohms 90 Watts Bracket
1000 Ohms 40 Watts Flat Type
5000 Ohnis 40 Watts Bracket
300 Ohms 50 Watts Bracket
250 Ohms 50 Watts Bracket "Non Inductive" 17
1200 Ohms Lamp Adapter (S846358A)500
Multi Tap 1600 Ohms/2000/100/100 Flat Type 14
Multi Tan 1600/2000/3600/2700 Flat Type 14
2000 Ohms 34 Watts Bracket
5000 Ohms 10 Watts Bracket 7
5000 Ohms 5 Warts Ferrule
12.000 Ohms 16 Watts Bracket Type EN!
14,000 Ohms 120 Watts Ferrule
50.000 Ohms 50 Watts Bracket
40 Megs 10.000 Volts Max Ferrule
45 Ohms 25 Watts Bracket
5 Ohms 5 Watts Bracket
10 Ohms 25 Watts Bracket
MINE DETECTOR CON 40° On which with the

MINE DETECTOR SCR 625 Complete with tubes. Ideal for locating buried metal, pipes, treasure, metallic fragments in lumber. Approx. depth of detection 6' depending on soil conditions. New \$65. Like New. \$45.

CRYSTAL CONTROLLED MV SIGNAL GENERATOR, MM-144. Hickok. 15KC—30 MC. Crystal control at 100 KC and 1000 KC. Output Voltage Ranges RF ½ MV to 100,000 MV. Complete with instruction book. Like New...\$45.

DELUXE STREAMLINED CABINET RACKS.
Chrome decorated, hinged door on top weatch
and hinged door on back. Anateur or W.E.
notched panels fit. Black crackled 28-½" high,
18" deep. Panel space 26-½" St. de. 2/527.

All prices F.O.B. Boston. Orders accepted from rated concerns on open accounts. Net 30 days.

Write for 112 Page Catalog оп company letterhead



Dept. E. 11. 110 Pearl Street, Boston 10, Mass.

ECK HESE

OIL CAPACITORS

ndard brand oil-filled capacitors at ces far below present manufacturers' st.

8		Volts			
Price	Mfd.	D.C.	Price		
\$1.89	2	1500	1.90		
3.95	2	2000	2.95		
.49	2	2500	3.40		
.89	2		3.90		
1.90	2		4.95		
.39	2		9.90		
.89	2.5-2.5-5		.49		
1.10	4		.89		
.89	4		1.49		
3.25	6		.89		
.39	8		1.79		
.89	8		2.25		
.89	8		3.25		
1.90	10		1.10		
2.65			1.90		
.69			2.80		
.79	50	400	9.00		
	Price \$1.89 3.95 .49 1.90 .89 1.10 .89 3.25 .39 .89 1.90 2.65	Price Mfd. \$1.89 2 3.95 2 .89 2 .89 2 1.90 2 1.39 2 .5-2.5-5 1.10 4 .89 4 3.25 6 .39 8 .89 8 .89 8 .89 10 2.65 10 2.65 10	Price Mfd. D.C. \$1.89 2 1500 3.95 2 2000 4.99 2 3500 1.90 2 4000 3.99 2 5500 1.90 2 4000 1.10 4 600 3.25 6 600		

STANDARD BRAND **POWER RESISTORS**

Durably manufactured to comply with the

most ri	gid cod	es.			
Ohms	Гуре	Tol.	Class	Coat	Price
55 55 55 55 56 50 100 300 400 500 500 1000 1256 1500 1500 2500 2500 2500 2700 2700 2700 2700 2	AAAAAJ DJ BABAABBAABBAABBAABBAABBAABBAABBAABBAAB	\$55555%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%	ABAABBBBABCBACACBBAAAAABBAAAAABAAAACABAAA	CAAAAAA BA . AA AAAAA . AAAAAA . AAAACC . AAAACAA . CCCC	\$0.07 .07 .07 .18 .18 .10 .15 .10 .10 .10 .18 .18 .18 .18 .18 .18 .18 .18 .18 .18

Caldwell fixed plug-in air condenser Type JD100-OS; 0.125 air gap; 100 pfd. capac-ity. Only \$1.19

SPAGHETTI

Fibre Glass Sleeving

in 36-inch lengths; #20; red, black. green, and tracer.
Per 36-inch length46

Plastic Sleeving

%" clear;					
Per foot					20
¼" black;	in	400-foot	rolls.	Per	foot3¢
1/2" black;	in	150-foot	coils.	Per	foot 4¢

Varnished Fabric Sleeving

In 36-inch lengths

Size																		ľ	•	I	16	91	1	gtlı
#18	,				,																			. 46
#10							÷				è		ż	á	á	,			,					. 90
#5 .			٠																				٠	.90
#2 .																								190
5/16	w																							110
7/16	w																							190
1/2"				٠,	,												'n							19

TUBES! TUBES! TUBES!

From ignitions thru photocells—from simple germanium crystal diodes to multi-element photocells—the RADIO SHACK carries all types at competitive prices. *Manufacturers: write or wire for our low prices on large quantities.

Туре	Price	Type	Price
6AC7*	\$ 0.99	1B32	\$ 3.95
6AG5*	.99	2J49	
6AG7*	1.06	2.J55	35.00
6AK5*	1.39	2J61	
6C4*	.29	3B24	1.50
6AK6*	.89	3B26/RK	R73
C5B	1.90	•	4.95
C6A	9.00	3C23	6.50
FG27A	12.50	3C24	39
QK59	45.00	4J36	45.00
QK60	45.00	4J37	45.00
QK61	45.00	5JP1	19.00
QK72	45.00	5JP2	19.00
VR90*	.75	5JP4	
VR105*		6C21	
VR150*	.75	274B	
VT127A	3.95	304TH .	
WL417	22.50	304TL	
WL653	22.50	350A	
ZP653	22.50	371B	
ZP679	22.50	723/AB	
1B22	3.95	724B	
1P23	3.95	725A	
		813	
4 D.0 m	3.95	866A	
1B27	3.95	872A	1.75

Silver Mica Capacitors. This bag of 100 silver micas in at least ten values between 15 pfd. and 1000 pfd. is easily worth \$25.00. Our low price only........\$2.49

Jensen 15-inch PM Speaker A15PM. Used,

but in good condition, these speakers provide a terrific sock at frequencies up to 10,000 cycles. A punch value.....\$19.00

Struthers-Dunn Type ADBT8 Relay; ten-ampere DPST contacts; 110-volt 60-cycle coil \$2.95

Super-sensitive SPDT Relay; one-ampere contacts; 11,300-ohm coil; contacts of at 700 microamperes and open at 600 croamperes ...

Shielded Push-pull Audio Output Transformer originally designed for Super-Pro; matches two 6V6's to 500 ohms.....89¢

The IRAINI

CABLE ADDRESS & RADIOSHACK 167 WASHINGTON ST., BOSTON, MASS., U.S.A.

GRAIN OF WHEAT LAMPS



Used for Huminat ing meters, compass dials, airplane struments, etc. Sol-dering iron removes lamp from base to use in models, doll houses, miniature trains, Xmas trees, etc.



Mazda G.E. 323 3V.,19 A


Mazda G.E. 328 6V..2 A

Photographs 3 times actual size. Glass Bulb

Either type

\$1.50 doz.

\$75.00 per M.

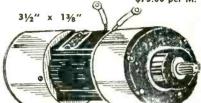

Operates on Flashlight batteries, speed depending on the voltage. Fairly strong on 6 volts, full power and speed on 27 volts. Designed to be used in bombsights, automatic pilots, etc., 250 RPM. FEW MORE AT.... \$5.00



HAYDON OF TELECHRON SYNCHRONOUS MOTOR

to operate switches, etc., I Rev. per minute at this

SPECIAL

\$3.85

other speeds available at \$5.25 up

BLAN

Experimenters and Inventors Supplies

64 Dey St., New York 7, N. Y.

BARGAIN BUYS

RADAR SETS:

RADAR SETS:

APR/1 with tuning unit, \$150.00—also available—3 cm types.

APS/3 and APS/4 complete.

TUNING UNITS:

TN/54 for APR/4-\$125.00 (New)

TN/54 10.
TUBES:
3BP-1 ...\$3.00
3EP-1 ...3.50 08ES: 3BP-1 \$3.00 723A/B \$5.00 3EP-1 3.50 725 15.00 531 2.50 726A 12.50 827R \$60.00

3"--0-150v DC (10 ma movement) \$2.50 Minimum order \$5.00; F.O.B. New York Write for listings of other surplus bargains

LERU LABORATORIES, INC. 360 Bleecker St. New York 14, N. Y.

CORRECTION

 In the October Issue of ELEC-TRONICS the advertisement of the

POWERTRON Electrical Equipment Co.

117 Lafayette St., N. Y. 13, N. Y.

(On page 290)

should have included the line: "Rebuilt . . . Thoroughly Re-Conditioned ... Mechanically, Electrically Checked and Adjusted ... Instruments Shipped Ready to Put into Actual Operation"

The foregoing was omitted through our error.

Classified Advertising Division ELECTRONICS

STANDARD POTENTIOMETER TYPE - MICROMAX

& N INDICATORS — CONTROLLERS — RECORDERS

Rebuilt . . . Thoroughly re-conditioned . . . Mechanically, electrically checked and adjusted ... Instruments shipped ready to put into actual use.

Model S-RECORDER-CONTROLLER



H.C.L. CONTACTS-115 V, AC Motor.

> Ranges 0-1000°F C/A 0-1500°FC/A 0-1800°F C/A 200-2000°F C/A 1000-2000°F C/A

> > \$210.00

Madel S-RECORDER-CONTROLLER

H.C.L. Contacts-115 V. AC motor Extra set H.C.L. Contacts—115 v. 120 on-off contacts. Range 0-1500°F C/A \$195.00



MODEL R RECORDER-CONTROLLER

H.C.L. Contacts -115 V. AC motor,

RANGES

0- 800°F C/A 700-1400°F I/C 200-2000° C/A \$175.00

Model S-RECORDER-CONTROLLER

Single Pen—2 Thermocouples—2 sets H.C.L. Contacts—115 V. AC motor. Ranges: 0-1200° F C/A, 0-1800° F C/A. \$195.00

Model S-RECORDER-CONTROLLER Single Point—Chart tear-off feature —H.C.L. Contacts—115 V. AC Motor. Range 0-1500°F C/A.



MODEL C INDICATOR-CONTROLLER

H.C.L. Contacts—115V. AC Motor Ranges: 0-1500°F I/C, 0-1800°F C/A, 0-2000° C/A, 200-2000°F C/A.

Model C \$135.00

MODEL S-RECORDER

MODEL 5—KEUNDER
with alarm feature using relay & cam operated contacts. Can be used as on-off controller without temperature setting device.
115 V. AC motor. Range 0-1800°F C/A.
\$180.00

MODEL S-2 PT. RECORDER

110 V. AC Motor Range 0-1800°F C/A (No Controlling Action)

\$235.00

SURPLUS BARGAINS

SELENIUM RECTIFIERS

New—Fresh Stock—Not over 6 mos. old.
Full wave bridge . . . single phase . . resistive inductive load . . . continuously rated
. . . conservative design.

	Max.	A15 TO 1	A pr
	R.M.S.	Max. D.C. Output	
Type	Input	at 35° C	Price
5B-1	24	18 V @ 3.1 A	\$5.03
₹5B-1	24	18 V @ 5.2 A	6.73
10B-1	24	18 V @ 10 A	8.71
1B-1	24	19 V @ 1.6 A	4.04
16B-1	24	19 V @ 16 A	16,40
24B-1	24	19 V @ 24 A	23.76
		.37 V @ 1.2 A	7.21
3B-2	48	37 V @ 3.1 A	9,60
5B-2	48	37 V @ 5.2 A	13.37
10B-2	48	37 V @ 10 A	17.18
16B-2	48	37 V @ 16 A	30.89
24B-2	48	37 V @ 24 A	44.67
5B-6	144	.110 V @ 5.2 A	35.70
	144		21.86
	144		17.34
	168		25.51
	168		19.68
	168		41.10
	CTIFIED	TRANICEORALERC	

RECTIFIER TRANSFORMERS PRI-105/110/115/120 V.-50/60

C,	/cl	es-	—O p	en	Fre	am	e C	con	stru	ıct	ioi	n	
SEC-18	v	(a)	2.5	Am	ps.			4	lbs.				\$3.35
18	\mathbf{v}	(a)	5	Am	ps.			5.5	Ibs				5.25
18	v	(a)	10	Am	ps.		1	0	lbs.		٠.		6.75
18	V	(a)	25	Am	ps.		2	5	lbs.				14.95
18	\mathbf{v}	(a)	50	Am	рв.		3	0	lbs.				24.75
36	\mathbf{v}	<u>@</u>	2.5	Am	ps.			7.5	lbs.				5.25
36	\mathbf{v}	<u>@</u>	5	Am	рв.		1	0	lbs.				6.50
36	\mathbf{v}	@	10	Am	ps.		2	0	lbs.				10.95
36	\mathbf{v}	0	25	Am	ps.		3	0	ıbs				22.50

PRI—115 Volts—50/60 Cycles

	Open rrume	•	JIISTIUCI	1011	
SEC-	135/145/155/165 V	@	.5 Amps	5 lbs.	\$5.25
	135/145/155/165 V	@	1.5 Amps	15 lbs.	7.95
	135/145/155/165 V			25 lbs.	13.50
- :	135/145/155/165 V	@	5 Amos	35 lbs.	24.50

HIGH VOLTAGE CAPACITORS 1 MFD 20 KV DC 18"x13 ½"x5"......

		V DC-13"x7			9.85
.001 M	IFD 50	KV DC-51/8" high	'x7¾"x4"	insulators	12.50
Cap.	Volts				
Mfd.	D.C.	Height			Price
10	1000	5-7/8 x	1-3/4 x	3-7/8	\$1.85
4	1000	5-7/8 x	2-3/4 x	1-1/4"	.85
1	1000	3-5/7 x	2 x	1-1/16"	.50
1	500	2" x	1-1/4" >	1-1/16"	.25
.25	1000	1-1/2 x	1" x	3/4"	.25

HEINEMAN CIRCUIT BREAKER

For use with low voltage, D.C., 100 Amps. Dimensions: 3¼"H x 4"D x 1" W \$1.75 15 Amp, 115 V AC, Curve 3, CAT.AM 2511-15 \$1.75 35 Amp, 120 V AC, Curve 2, CAT.AM 1510R-35 1.5 Amp, 117.5 V AC, Instant Trip.....\$1.75

WESTON Model 622—New!

D.C. Portables . . . 1/2 of 1% accuracy ... High sensitivity ... Moulded bakelite case... A famous instrument at a real low price.

		Your
0-20 Range	List	Price
U-3C Mlcroamps— 280 ohms	\$232,50	\$139.50
U-30 Microamps-1800 ohms	202.50	121.50
U-au Microamps— 150 ohms	217.50	130.50
0-10 Microamps— 90 ohms	210.00	126,00
0-2 0 Microamps— 45 ohms	210.00	126.00
U-100 Microamps- 10 ohms	210.00	126.00
U-1/5/20/50/100 Millivolts	274.50	165,00
U5 Mills Thermal	300.00	180.00
0−2 Mills Thermal	300.00	180.00
1.5/3/7.5/15/30/75		
150/300/750 Volts	294.75	237,00

QUANTITIES LIMITED! ACT NOW!

WHSE PORTABLE GALVANOMETER



Type PX-12-7 M.A. movement, special scale, solid connecting terminals, contains a 1 volt internal cell which can be easily removed for conversion to DC AMMETERS & VOLTMETERS, with leather case & canvas carrying strap.

A buy at \$4.95

GE TYPE DO 50 DC AMMETER

50 MV FULL SCALE, RECTAGULAR 34" x 3", Barrel 24" DIAM, x 14" DEEP, MOUNT-ING HOLES 25" x 25" c. to c. SPECIAL SCALE, CAN BE USED WITH EXT. SHUNT FOR ANY RANGE, BAKELITE CASE

Price 10 for \$27.50

GE TYPE DO 50 DC VOLTMETER

3 VOLTS FULL SCALE, 100 OHMS 1V, SPE-CIAL SCALE, SAME DIMENSIONS AS ABOVE, BAKELITE CASE Price 10 for \$27.50

MICROVOLTER—FERRIS Model 20B

2 to 100,000 microvolts output, continuously variable . . operates on 115 V. 60 cycle AC . . . push button selector for 18 frequencies from 455 K.C. to 22 M.C. . . with or without 400 cycle 30% modulation . . frequency may be varied ±2% by screwdriver adjustment. 400 cycle 30 70 mounts be varied ±2% by screwdriver adjustment.

Your Price.....\$100.00

GE STEPDOWN TRANSFORMER

PRI 115/230 V 60 cycles. SEC 32 V. Rating .5 KVA Isolation type cat 61G60 enclosed, bell end, cont. duty.

Your Price\$7.50

STEPDOWN TRANSFORMER—SPECIAL

Made by GE heavy duty considerable	
over-design open frame ideal for	
rectifier application size 3 1/2" x 3 1/2" x 4".	
Primary—115 V 60 cycles.	
SEC-15 V. @ 12 amps a buy at \$3.75 SEC-10 V. @ 18 amps a buy at 3.76	

POWER TRANSFORMER

Pri.—440/220 V 60 Cy Sec—125/115/105 V. Rating .8 KVA RCA Open construction. Bracket mounted, pri & sec terminal board, Overall dimensions: 5% "H. x 7½" W. x 8" D. Mounting Dimensions 6%" x 5%".

Price\$12.50

TRANSTAT—3 K.V.A.



Type RH Input: 115 V. 10%. Output: 115 V. Max. Amps: 26 A. Made as a line voltage corrector 10% of input voltage, or can be connected to give plus 20% or minus 20% of input. Can also be reconnected to be type stendown with variance.

used as an isolated type stepdown with variable secondary. Input: 115 V. Output: 0-30 Volts at 30 Amps. No Knob.

A Real Buy at \$18.00

(Same type but .25 KVA. Input: 103-126 V. Output: 115 V.-2.17 A.)

Price \$6.50

RHEOSTAT

Ohms .87	Amps 13	Size-Diam.	Price \$2.50
.01		9 22	
b	2	1 32"	1.75
10	9.2	14"	5.95
10 22	4.5-3.1	6*	6.50
30	1.79	2 1/4"	1.50
32	2,4	3 1/4"	4.95
32 40	1.12	2*	2.50
50	1.11	2"	2.50
75	3.5	6*	7.50
100	1	3″	2.95
200	. 25	1 1/2"	.75
250	2.551	6# -	7.50

STRUTHERS-DUNN RELAYS

D.P.S.T., Normally open, 115 V, 60 Cycle, AC coil, 30 Amp. contacts, fibre base with 4 holes for mounting. Dimensions, 4½" L x 3" W x 2%" H 3¾ ″ H. A Real Buy At.....\$2.50

ALL PRICES INDICATED ARE FOB OUR WAREHOUSE NYC. SHIPMENTS WILL BE MADE VIA RAILWAY EXPRESS UNLESS SUFFICIENT POSTAGE IS INCLUDED OR OTHER INSTRUCTIONS ISSUED. WE WILL REFUND EXCESS POSTAGE IN STAMPS.

Electrical Equipment Co.


117 LAFAYETTE STREET

Phone: WOrth 4-8610

NEW YORK 13, N. Y.

A LEEDS LEADER

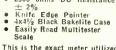- 50 microamp movement ±
- 2500 ohms DC Resistance



This is the exact meter utilized in the G.E. YMW-IA Lab Type Unimeter ... Each \$9.75

A Great Special.....

50 Microamp Scale 25c extra

RECTIFIER TRANSFORMER

DUAL PRIMARY Secondary 0-35, 371/2 volt 0-70, 75 volt This transformer is completely shielded.

Extra Special \$1.95



BIAS TRANSFORMER

Primary 115 V @ 0.5 Amg. Secondary 6.3 V @ 1.2 Amps.

180 V @ .02 Amps.

5.1 V @ 7.0 Amps. C.T. 300 V @ .02 Amps.

This transformer is completely shielded and hermetically sealed Brand New

\$1.95 Special

AMERTRAN TRANSTAT

Input: 230/115 V AC. Output: 103 to 126 volts at 8.5 amps. Rated at .88 KVA. Will make a perfect 230 to 115 volt step down transformer at about 880

\$9.95 A real buy at



Variable Transformer for precise Voltage Control. Excellent mechanical construction, design, and durability.

VARIABLE TRANSFORMERS

TYPE 20: 115V. input, 0-135 V. output @ 3.0 amps. 0.4 KVA \$12.50 TYPE 116: Mounted; 115V input, 0-135 V. output @ 7.5 amps. 1.0 KVA TYPE 116U: Unmounted; 115V. input, 0-135 V. output @ 7.5 amps. 1.0 KVA 19.00 TYPE 1126: 115V. Input, 0-135_V. output @ 15.0 amps. 2.0 KVA TYPE 1226: 230V. input, tapped at 115 V., 0-270 V. output @ 9.0 amps. 2.4 KVA TYPE 1156: 115V. input, 0-135 V. output @ 45.0 46.00 46.00 amps. 6.1 KVA 118.00

If not rated 25% with order, balance C.O.D. All prices F.O.B. our warehouse New York. We ship to any part of the globe. Write Dept. EL



75 VESEY STREET COrtlandt 7-2612 N. Y. C. 7

SURPLUS

LABORATORY EQUIF

We have in stock, for immediate delivery, the following surplus Laboratory Instruments, fully tested and guaranteed.

General Radio: 107M Variable Inductors: 224A, 724A. Wavemeters; 821A Twin-T Bridge; 775A Frequency Limit Monitor. 620A Het. Freq. Meter; 805A Std. Signal Generator.

Ferris: 18B Signal Generator; 33A, 34A Crystal Calibrators; 16C Std. Signal Gen-

Boonton: 120A V.H.F. Circuit Checker; 140A Wide Range BFO; 155A FM Signal Generator.

Hewlett-Packard: P-6255B Interpolation Oscillator 510-1000 & 1280-2520 CPS.

L&N: 4223 Precision Resistor; 7655 Portable indicators and Standard Cell.

Millen: P4E Synchroscopes.

Western Electric: RA 90A High Voltage
Power Supplies, +4900 V, -1000V DC, Input 110V, 400; TS/5AP Range Calibrator
(Sweep Marker Generator); 15154, D
152213 Modulator Oil Units; TS9/APQ-5
Range Calibrator Modulator; 157A Output

Transformers; Breakdown Testers, 500

Weston: Model 1; 0-300 M.A.; 0-500 Volt D.C. Model 45; 0-75 Volt; 0-300 Volt; 0-1500 Volt; 0-150 M.A.: 0-300 M.A. D.C.; 785 Industrial Analyzer.

Dumont: 213 Modulation Monitor. G.E.: LU Radar Test Equipment. Distillation Products: Pirani Gauge. Industrial Instruments: RN-1 Wheatstone Bridges; MBS Megohm Bridge. Shallcross: 621 Resistance Limit Bridge.

WRITE FOR COMPLETE PRICE LIST All Equipment-F.O.B., New York City. Subject: To prior sale

THE NATIONAL INSTRUMENT CO.

FAR ROCKAWAY, N. Y. Cable Address: NATINSTRU, New York

11

The

An all purpose self-reactivating dehydrating unit. To be used for removing moisture from gases. Numerous applications in the fields of Physics, Electronics and Chemistry. Dual insulated tanks with thermoand Chemistry. Dual Institute.

statically controlled heating elements. Scale Complete with 20 lbs. of Silica gel..

Complete with 20 lbs. of salety heating elements, shut-off and safety valves. F.O.B., N. Y.

INTERSTATE Appliance Co., Inc.

Dept. KD, 600 Broadway, NEW YORK 12, N. Y.

SOLID SAVING SALE

CLARE 200 OHMS 24v SPST Normally open. No. R13, 15 amp contacts. Ship wt. 1 lb. 49c ea. Clare 3500 ohms. SPST 6MA Plate circuit relay No. R30.

89c ea.

1ST RF TRANS.

Ass'y MN26 & ARN 7 Sik#2C-3035-5/T7. Ship, wt. 3½ lbs.
ANT Trans Ass'y MN26 & ARN 7 Sik#3CK-1084C-24. Ship, wt. 3½ lbs.

\$2.50 ea.



G. E. ANTENNA

Changeover relay, DPDT & SPST-N.C. 50 ohms, 12v DC, 10 amp contacts. No. 37843 R57. Ship. contacts.

89c ea.

POWER TRANSFORMER

1500v C.T. at 150 ma, 6.3v 2.5a, 6.3v 1.6a, 5v 3a, 115v 50-60c pri G.E.

\$5.25 ea.



FILTER CHOKE

4% x 3½ x 4½ h. 9 lbs. W.E. 1000ma lby 4 ohms. No. T46. Ship. wt. 21 lbs.

\$2.89 ea.

Hi-Voltage Oil Filled Capacitor 0.2 mf 500 wydc. Std. makes with Mtg.
Brackets, \$1.89 ea.
Sigma Sensitive Relay-Type 4AH, SPDT,
2,000 ohms, 4 ma in, 1.5 ma hold. Sealed
unit. 5 prong plug in base. 99c ea.

MIN. ORDER \$2.50. PRICES NET F. O. B. OUR PLANT



BEST SURPLUS BUYS

RECTANGULAR OIL CONDENSERS

1 mfd 600vdc25 2 mfd 600vdc30 3.5 mfd 600vdc49	2 mfd 5000vdc4.95 4 mfd 5000vdc6.50 1 mfd 7500vdc9.95
4 mfd 600vdc 45	.1 mfd 15,000vdc
5 mfd 600 vdc49	8.95
10 mfd 600vdc85	2 X.005 mfd 4000
2 mfd 1000vdc65	vdc1.95
4 mfd 1000vdc	2.1 mfd 7000vdc 1.95
4 mfd 1500vdc1.95	.15 mfd X 8000-
1 mfd 2000vdc 85	vdc; .15v X
2 mfd 2000vdc 1.50	5000vdc 1.95
6 mfd 2000vdc . 4.50	.25 mfd 20,000-
2 mfd 3000vdc . 2.65	vdc 19.95
4 mfd 3000vdc 4.50	

1	.0001 X 20,000VDC MICA SANGAMO
	G3
ı	0.02 mfd

LOWEST TUBE PRICES

2C26A .49 7C4 .75 10Y .49 12A6 .29	RKR73 \$2.9 VR-150 .7 801A .7 814 3.9	864 .59 1625 .39 5 24G .39
15R .98	826 .5	9 957 .43

TUBE SOCKETS

Acorn, Ceramic Octal, Mica Filled, Ring Mounting, An	1-	
phenol		.06
Octal, Ceramic, Ring Mounting		.12
Johnson #247 for 826,829 etc		.25
Johnson 210 4 Pin Med, Bavonet		.29
4 Prong Ceramic for 705, 715B etc		
Millen Plate Cap 3600L F/866 etc		

FUSES - HOLDERS - LAMPS

4AG, 3A 250V Little Fuse \$2.50 C, \$22.00M
Renewable 2" X 19/16" GE 30A 250V 20ea.
Fuse Holder Little Fuse (341001)
Mazda #323-3V Grain of Wheat

TRANSFORMER - CHOKES

Amertran Filament Transformer 2.5V Ct	
@ 20A;—115V., 50/60 CPS PRI; HV.	
INS	95
Filter Choke 15H @ 150MA Sealed 1.3	.5
Filter Choke 15H @ 100MA Sealed	19
UTC 41866 Standard AC-DC Choke 65MA	
Strap Mounting	9

IF TRANSFORMER

ALLÁDIN GA101 & GA102, Polyiron core; Air Tuned: Excellent Quality receiver, Re-placements—Input & Output IF; 465 KCS. PAIR.....\$1.00

COAX. CABLE

RG 7	7 U	\$35M	RG :	29U	\$35M
RG 8	ВŲ	\$37.50M	RG !	58U	\$59M
RG 1	110	\$100M			

DYNAMOTOR SUPPLY, for Mark II, Input, 12V @ 9.4A, Output, 275 @ .110 and 500V 28V Used Perfect

ALTIMETER RECEIVER

RT7/APN1, Complete with 14 tubes, and dynamotor, Specially Priced......\$7.95

All Material Fully Guaranteed, Minimum order \$2.00 Unrated Accounts 25% with order. All equipment new Surplus, unless otherwise indi-cated. All prices FOB, N. Y. C.

STANDARD RADIO-**ELECTRICAL PRODUCTS**

2260 Washington Avenue New York 57, New York

SELENIUM RECTIFIERS

AND SPECIALIZED ELECTRONIC COMPONENTS

THIS MONTH'S SPECIALS!!

VACUUM CAPAGITOR



50 MMFD.

20 KV.

125 MFD. 27 KV.DC.

With mounting brackets


OIL CAPACITOR

\$1750

TRANSFORMER

HIGH CURRENT

AMERTRAN

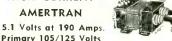

Primary 105/125 Volts Can easily deliver 250 Amps. Insulation 35 Kv. Test. Approx. Shipping weight 75 lbs.

\$1750

Full Wave Bridge Types Input 0-18V AC Typef B1-250 500 MA 5.98 B1-500 500 MA 1.95 B1-1 1 AMP. 2.49 B1-13 3 AMP. 3.49 B1-3 3 AMP. 3.49 B1-15 1 5 AMP. 5.95 B1-1 5 AMP. 5.95 B1-10 10 AMP. 9.95 B1-16 15 AMr. 13.95 B1-20 10 AMP. 15.95 B1-25 10 AMP. 15.95 B1-25 10 AMP. 15.95 B1-30 10 AMP. 24.95 B1-30 10 AMP. 36.95 B1-30 10 AMP. 36.95 B1-30 10 AMP. 36.95

Input 0-126VA		Types utput 30*VDC
Type#	Current	Price
3B7-4	4 AMP.	\$32.95
3B7-6	6 AMP.	
3B7-11	11 AMP.	65.00
Input		utput
0-234VA		50*VDC
Type /		Price
3B13-4		
3B13-6	6 AMP.	
3B13-11	11 AMP.	110.00

Full W	ave Bridge	Types
Input		tput_
9-54VAC		10*VDC
Type#	Current	
B3-150.	150 MA.	\$1.25
B3-250	250 MA.	1.95
B3-600		3.25
Input		itput
0-72VAC		54*VDC
Type /	Current	
B4-1X2	1.2 AMP.	\$7.95
B4-3X5	3.5 AMP.	15.95
B4-5	5 AMP.	17.95
Input		tput
0-115VA	C 0~11	0*VDC
0-115VA Type#	C 0~11 Current	0*VDC Price
0-115VA Type∦ B6-150	C 0~11 Current 150 MA,	0*VDC Price \$1.95
0-115VA Type # B6-150 B6-250	C 0~11 Current 150 MA, 250 MA	Price \$1.95
0-115VA Type# B6-150 B6-250 B6-400	Current 150 MA, 250 MA, 400 MA,	0*VDC Price \$1.95 2.95 4.95
0-115VA Type # B6-150 B6-250 B6-400 B6-600	Current 150 MA, 250 MA, 400 MA, 600 MA.	10*VDC Price \$1.95 2.95 4.95 5.95
0-115VA Type # B6-150 B6-250 B6-400 B6-600 B6-800	C 0-11 Current 150 MA. 250 MA. 400 MA. 600 MA. 800 MA.	0*VDC Price \$1.95 2.95 4.95 5.95 7.95
0-115VA Type # B6-150 B6-250 B6-400 B6-600 B6-800 B6-1X2	Current 150 MA. 250 MA. 400 MA. 600 MA. 800 MA. 1.2 AMP.	Price \$1.95 2.95 4.95 5.95 7.95 9.95
0-115VA Type # B6-150 B6-250 B6-400 B6-600 B6-800 B6-1X2 B6-2	Current 150 MA. 250 MA. 400 MA. 600 MA. 800 MA. 1.2 AMP. 2 AMP.	Price \$1.95 2.95 4.95 5.95 7.95 9.95 12.95
0-115VA Type # B6-150 B6-250 B6-400 B6-600 B6-800 B6-1X2	Current 150 MA. 250 MA. 400 MA. 600 MA. 800 MA. 1.2 AMP.	Price \$1.95 2.95 4.95 5.95 7.95 9.95

B6-7X5 B6-10	7.5 AMP. 10 AMP.	32.95 36.95
Input 0-234VA		itput 80*VDC
Type /	Current	Price
B13-4	4 AMP.	\$54.95
B13-7X5	7.5 AMP.	63.95
B13-10	10 AM.	69.95

Inpa		Types
0-36VA		
Type# B2-150		Price
B2-150 B2-220		3.98
B2-220		1.25
B2-450		
B2-600		2.25
B2-2	1 AMP. 2 AMP.	4.95
B2-3		
B2-5		
B2-6	6 AMP.	
B2-7X		13.95
B2-10	10 AMP.	15.95
B2-15		
B2-20	20 AMP.	27.95
B2-30	30 AMP.	36.95

CENTER	TAPPED 1	TYPES
Input 12-0-12V	AC O	tput -8*VDC
Type#		Price
C1-10	10 AMP.	
C1-20 C1-30	20 AMP. 30 AMP.	12.95
C1-40	40 AMr.	17.95
C1-50	50 AMP.	25.95
C1-80	80 AMP.	34.95
C1-120	120 AMP.	46.95

* Select Proper Capacitor From List Shown Below, to Obtain Higher D.C. Voltages Than Indicated

RECTIFIER	MOUNTING	BRACKETS	
or Types B1 through	B6, and Type (31\$.35 pe

			C1\$.35 per set
				.80 per set
For Types	313	 		1.20 per set

Rectifier	Transformers
	es 1 15VAC 50/6

	Cycles	8	
Type / Vol XF15-12 TXF36-2 TXF36-5 TXF36-10 TXF36-15 TXF36-20	15 36 36 36 36	12 2 5 10 15 20	Price \$3.95 3.95 4.95 7.95 11.95
AHTYE			

	All	TX	FT	ypes	are	Tap	pe
to	De	live	r 32	, 34,	36	Volte	

RECTIFIER	СНОК	ES
`****	A mino	D1.

HY2	.03 Hy	2	\$2.25
HY3	.03 Hy	3	2.95
HY5	.02 Hy	5	3.25
HY8X	5 .02 Hy	8.5	7.95
HY10	.02 Hy	10	9.95
HY12	.125Hy	12	12.95
HY 15	.01 5H y	15	13.95

1	CF-13	6000 MFD	10VDC	\$2.49
1	CF-14	3000 MFD	12VDC	1.69
=	CF-15	6000 MFD	12VDC	2.95
и	CF-1	1000 M FD	15VDC	.98
	CF-2	2000 MFD	15VDC	1.69
	CF-3	1000 MFD	25VDC	1.69
ž.	CF-4	2X3500 MFD	25VDC	3.45
н	CF-18	10000 MFD	25VDC	4.95
1	CF-5	1500 MFD	30VDC	2.49
П	CF-6	$4000 \mathrm{\ MFD}$	30VDC	3.25
П	CF-7	3000 MFD	35VDC	3.25
H	CF-8	$100 \mathrm{\ MFD}$	50VDC	.98
e	CF-16	2000 MFD	50VDC	3.25
2	CF-17	50 MFD	150VDC	.59
н	CF-9	200 MFD	150VDC	1.69
ı	CF-10	500 MFD	150VDC	3.25
d	CF-11	100 M FD	350VDC	2.25
a	CF-12	125 MFD	350VDC	2 40

RECTIFIER CAPACITORS

ELECTROLYTIC CAPACITORS

	Lots	Lots
	of 10	of 100
100 MFD 50 VDC	\$2.20	\$19.00
50 MFD 150 VDC	2.00	18,50
8-8-20 MFD 350,150 VDC	4.70	43.00
*20-20 MFD 400,250 VDC	4.50	38.00
10 MFD 450 VDC	2.50	20.00
15 MFD 450 VDC	2.50	20.00
15-15 MFD 450 VDC	3.00	22.00
40 MFD 450 V C	4.20	36.00
* 4 prong plug- in type.		
a prome prome and pro-		

11121213	
O-15 MA.D.C. Weston #506 2" Rd. O-30 A.D.C. Weston W/shunt 2 ½" Rd., aircraft	\$2.95
type. Q-50 A. D.C. Weston #301 3 ½" Rd., Enclosed shunt	2.95
O-60 A.D.C. West., w. shunt, 21/2" Rd., aircraft	
0-120 A.D.C. West. w. shunt, 21/2" Rd., aircraft	3.25
O-8 V.A.C. G.E. 3½" Round	4.95 2.95
O-30 V.D.C. West, 21/2" Rd., aircraft type	2.95

METERS

To avoid shipping errors, kindly order by type #. All prices subject to change without notice.

ATTENTION !!!

INDUSTRIALS, EXPORTERS, SCHOOLS GOV'T AGENCIES, LABORATORIES
Our engineering staff is at your service to facilitate the application of rectifiers for your specific requirements.

Write for quantity discount on company letterhead.

Minimum order \$3.00. No C.O.D.'s under

\$25.00. 25% deposit on C.O.D. Add 10% for Parcel Post and handling. Terms: Net 10 days to rated concerns only. Orders Promptly Filled From Our Stocks

OPAD_GRE Warren St. Phone: BEekman 3-7385 New York 7, N.

AIRCRAFT RADIOS STOCK DELIVERY

Static Discharge Wicks AN/ASA-3

Brand new approved type wick at unprecedented low price89c εa.

BOX OF 200 \$150.00

GLIDE PATH SET

AN/ARN-5A companion to localizer equipment. 100% complete including all plugs, shockmount. Brand New \$25.00

Localizer—Extra Special!!

LOCGIIZEF — EXTRO SPECIAL:
Instrument landing localizer set RC-103, 100% complete, including antenna (not shown). This equipment is sold with the type-pertificable receiver BC-733-D and all cables, including RG-22/U, are completely fabricated. Save over \$50.00 on installation. (24V).

112V additional \$7.00 ...\$49.50

R89B/ARN-5 Glide Path ...\$60.00

Flexible Shafting MC-215

For 274-N, ARC-5, RL-42, 53" lengths...\$1.25 ea. 154" lengths...\$1.85 ea.

FL-8 Range Voice Filters \$1.95 ea

PLUGS

ANY "AN" Type Connector - 50% off list. 20 or more 60%. Order by "AN" number or general description.
274-N or ARC-5 Plugs: PL-147, 148, 151, 152, 153, 154, 156
PLUGS for Radio Compass: PL-108 75¢ each, PL-112, \$1.00 each, PL-118, \$1.00, PL-122, \$1.50

RADIOS

MN-26-C or Y 100% complete, brand new 24-V \$125.00 set (12 volt MN-26 available at \$15.00 additional) ADF SCR-269-G 100% complete brand new \$295.00 set ADF SCR-253-G 100% complete brand new \$295.00 set SCR-183 Transmitter-Receiver, complete with \$37.00 set \$37.0 Bendix Receiver RA-10-DB, 100% complete, brand new \$39.00 set AN/ARC-3 VHF Transceiver 100% complete, less crystals, including mounts, plugs, dynamotors, etc. Brand New \$450.00 Marker Beacon Rec. 100% complete incl. mount, plugs, prefab, antenna and indicator 24 v \$24.50 12V \$17.50 set

Bendix VHF Field Strength Meter

1-95 Brand New A must for every radio repair shop & VHF operator. Range 100-156 MC. Checks frequency, field strength & radiation pattern\$24.50 ea.

RL-42 Antenna Reels \$4.50

DYNAMOTORS

PE-86 w/filter 24 V. in 250 @ .80 ma out \$ 3.75 ea.
DM-53-A (BC-733) 24 V. in
DM-28 w/filter (BC-348) 24 V in 5 75 69
BD-83 W/filter (SCR-183) 12 V in 10 00 ea
PE-73 w/filter (BC-375) 24 V. in 20.00 ea.
BD-77 w/filter (BC-191) 12 V. in 20.00 ea.
DM-53-AZ 12 V. in 7.00 ca.
PE-100 12 V. inverter 50.00 ea.
MG-149-F 24 V. inverter 25.00 ea.
MG-149-II inverter\$35.00
DY-21/ARC-3 \$10.00
DY-22/ARC-3\$4.00

BRUSH SETS

DM-24 (BC-224) 2 ea. LV & HVS	.75	set
DM-28 (BC-348) 2 ea. LV & HV	75	cat
UM-52 (274-N Rec.) 2 ea LV & HV	25	cot
DM-33 (274-N Mod.) 2 ea. LV & HV	.45	
BD-77 or PE-73 2 LV 2 HV	.60	
Compass Band-change Motor	.95	
Compace Automore Motor	.45	
Compass Autosyns PE-94 or PE-98 (SCR-522) set of 8 ea	.35	set
1 19 01 Ut 1 U-85 (5U:R-522) set of 6 og	n S	

CONTROL BOXES GALORE

MN-28-C Y or LB or B	G-4	34-	Α.	 	 	\$10.00	ea.
Loop Control Box MN-	52. .					3 50	ea.
BC-602 for SCR-522						2.50	
BC-732 for BC-733						2.50	ea.
BC-450 for SCR-274-N	Rec			 		2.50	ea.
BC-451 for SCR-274-N	Xn	itte	er.	 	 	2.00	
BC-1366 Jack Box						.95	ea.
Ant. Reel Control Box I	3C-4	61.		 	 	.95	ea.
Bendix Jack Box M1-22						2.50	88.
Change-Over Relay BK	-22	-K.		 	 	4.50	
Compass Relay SW-182	(12)	٧).		 	 	3.95	ea.
Antenna Relay BC-442.				 	 	2.50	

ALL MATERIAL BRAND NEW GUARANTEED

"Our Reputation Is Your Protection"
ASK ANY CERTIFICATED AIRLINE TERMS: If not rated, 25% with order, balance C.O.D.



INDUSTRIES INC. NEW HAVEN, CONNECTICUT



PHONE 6-6893

101-E DIXWELL AVE.

Height: (over insulators), 16". Width: 12". Depth: 4". Net weight: 36 pounds. Shipping

weight: 50 pounds.

15,000 V. Working 1 mfd. Capacitor

Nationally Known Brand, Oil-Filled

Priced at a fraction of original cost, these husky capacitors have hundreds of applications-in communications, in industry, as capacitordischarge spot welders and power-factor correctors,-in the research laboratory.

Only 1200 available,—Act Now!

500 EACH

NEW--SURPLUS Individually packed for overseas shipment.

WIRE-WRITE or PHONE (Market 1-4568)

SAN FRANCISCO RADIO & SUPPLY CO.

1284 Market St. San Francisco 2, Calif.

BOONTON

140-A BEAT FREQUENCY GENERATOR Range 20 CPS to 5 MC. Output Voltage I MV to 32 Volts. We have one unit for immediate delivery. RECONDITIONED GUARANTEED

THE NATIONAL INSTRUMENT CO. FAR ROCKAWAY

ELECTRONIC TUBE-MAKING MACHINERY

For manufacturing radio tubes, electronic tubes, cathode-ray tubes, lamps. New and used. Reasonably priced, satisfaction

used. Heasonably priced, satisfaction guaranteed.

AMERICAN ELECTRICAL SALES CO.

67 E. 8th St. New York, N. Y.

300 New Surplus **Relays or Contactors**

All in original manufacturers cartons

- 110 volt, 60 cycle
- Cutler Hammer Type 619 unmounted contactors
- 4 pole, 25 amp., 600 volt normally open contactors
- Some have pilot contacts.

L. R. RUOFF

94-18 51 Ave.

Elmhurst, N. Y.

We have one of the largest stocks in the country of

AN-UG and UHF and BRITISH TYPE CONNECTORS

Write us your requirements

Attention:

INDUSTRIALS . LABS SCHOOLS & AMATEURS

Let us quote on components and equipment that you require. We have too many items to be listed here. Place your name on our mailing list now for news of exceptional buys!

Write for FREE CATALOG

ACORN ELECTRONICS CORPORATION

80 Vesey St. Dept. E-11 New York 7, N. Y.

An Investment

Productive advertising is an INVESTMENT rather than an EX-PENDITURE.

"Searchlight" advertisers almost invariably report prompt and satisfactory results.

BE CONVINCED send us your advertisement TODAY.

Address Classified Advertising Division

ELECTRONICS 330 W. 42nd St., N. Y. 18 N. Y.



OUTSTANDING VALUES!

PIONEER #2K20

LS-3 SPEAKERS Navy type. In waterproof metal case. Jensen six inch PM Speaker. \$7.95 \$7.95

Army type. Enclosed in metal case. Six inch Jensen PM Speaker. Used. \$4.95

A NATURAL!!!

The Ideal Companion for Outdoor Activities A Year Around Must Precision Built — Beautl-fully Designed Excellent Tone Quality Portable Batt. Operated Radio

Portable Batt. Operated Radio Reflex Type Camera 16 Pictures on Standard #127 Film Dealer Price

TUBES

1B24.... 2x2/8 79... 3C24... 3E29... 4E27... 15E... 33... 45 Spec... 304TH... 371B.

371B.
393A.
531.
702A.
702B.
713A.
805.
811.
813.
815.
826.
830B.
832.
84.
84.
852.
852.

2051 8012 9006 C5B HY69 HY615 RK73 10T1 amperite 3BP1 5BP1

3BP1 5BP1 5EP4 5CP1 5FP7 6AC7W 68H7 6V6GT 25L6GT 25Z5

0

TOM

THUMB

CAMERA

RADIO

Dealer Price

\$2.50 .750 .4.95 8.60 1.10 98 .4.95 2.80 7.95 3.75 3.75 3.75 3.75 2.00 6.95 2.10 3.75 2.10 6.95 2.10

ROTARY CONVERTER

Input: 230VDC. 1.5 amperes. Output: 110VAC, 60 cycle—200 volt amperes. 1.82 amperes Power factor 0.9 Sleeve bearing type. 3600

RPM.
Dimension: 11%" x 6"x 8%".
Includes—filter unit to suppress high frequency currents
—5 foot cord with male and female plugs—Manual—spare brushes. New \$49.95

SENSATIONAL! RECHARGE YOUR AUTO BATTERY with the NEW AUTOMATIC AUTO RADIO



Dealer \$34.97 Price State Price With BUILT-IN BATTERY CHARGER Patent pending Sensational Features Powerful 6 Tube Radio RADIO State Price Price

- rowerful 6 Tube Radio
 RADIO
 3 Gang Condenser
 Extra R.F. Stage
 For Increased Sensivity
 Large P.M. Speaker
 Single Compact Unit
 Easily Installed
 BATTERY CHARGER
 Charges Through Radio
 Simply plug Radio Cord
 into 110 v. A.C. Electric
 Makes Winter Starting
 Sure

CAPACITORS (Standard Brand)

	В	ATH TUB	Each	Ten
	.05mfd	600vdc	\$0.10	\$0.08
2	x.05mfd	600vdc	.15	.12
	1mfd	600vde	.20	.15
	1mfd	600vdc	.40	.35
	2mfd	600vdc	.50	.45
	.05mfd	1000vdc	.55	.50
		CERAMIC	3	
	135mmf	5000vde	3 fo	.29
	ELECTE	OLYTIC	Each	Ten
	ELECTE 2500mfd	OLYTIC 3vdo	\$0.30	\$0.28
2				\$0.28 4.65
2	2500mfd	3vde	\$0.30 4.95 .90	\$0.28 4.65 .75
2	2500mfd 24000mfd	3vde	\$0.30 4.95	\$0.28 4.65
2	2500mfd 24000mfd 1000mfd	3vde 3vde 25vde	\$0.30 4.95 .90 .39	\$0.28 4.65 .75 .35
2	2500mfd 24000mfd 1000mfd	3vde 3vde 25vde 350vde 0il-Filled 400vde	\$0.30 4.95 .90 .39 \$0.50	\$0.28 4.65 .75 .35 \$0.45
2	2500mfd 24000mfd 1000mfd 24mfd	3vde 3vde 25vde 350vde Oil-Filled	\$0.30 4.95 .90 .39	\$0.28 4.65 .75 .35

4mfd	400vdc	\$0.50	\$0.45
.25mfd	600vde	.20	.17
1mfd	600vdc	.35	.30
1mfd	600vdc	.35	30
2mfd	600vdc	.35	.30
4mfd	600vdc	.55	.50
5mfd	600vdc	.60	.55
8mfd	600vdc	.80	.75
10mfd	600vdc	1.00	.90
10mfd	1000vdc	1.75	1.60
2mfd	5000vdc	6.50	6.25
.0008mfd	15000vdc	6.95	6.50
.045mfd	16000vdc	2.95	2.75
	Paper		
.5mfd	200vdc	\$0.20	\$0.17
.006mfd	400vdc		
	Tubular	.19	.15
16mfd	400vdc	1.50	1.30
8-8mfd	600vdc		
	Filtermite	.85	
3x8mfd	600vde	1.49	1.25
8-8-4mfd	650vdc	1.49	1.25

POTENTIOMETERS (STANDARD BRANDS)

							Pri	ce
Cat. No.	Type	Ohms	Watt	Taper	Bush	Shaft	Each	Ten
.092B2	WW	3,000	2	Ĺ	1/2"	1"	\$0.25	\$0.20
.136B1	WW	5,000	2 3	L	1/2"	5/8"\$1	25	20
.063	ww	20,000	3	L	3/8"	1 1/16"81	25	20
.187B1	ww	3,000	4	L	3/8"	1 3/32"sl	27	22
.N2107	ww	100	25	L	3/8"	1/2"	55	50
.155B1	WW	15,000	25	L	1/2"	1"	69	55
. 105	ww	20,000	25	L	1/2"	1"	69	55
.100B1	Carbon	200/200) 2	L	1/2"	1"	28	25
		dual		_				4 %
.123B1	C	5,000	2	L	1/4"	3/4"	22	19
.108B2	Č	5,000	2	L	1/2"	7/8"	22	17
.N52	C	25,000	2 2 2 2 2 2 2	L	3/8"	1 3/4"	25	.20
.120B1	C	25,000	2	L	1/2"	5/8"	.25	.20
.122B3	C	50,000	2		3/8"	7/8"	.25	.20
.125B1	C	50,000	2		1/4"	3/4"	.25	.20
.N139	C	IMEG	2	L	3/8"	5/16"	.40	.35

JUST ARRIVED! RS/ARN-7

ADIO COMPASS RECEIVER

Alrborne 15 tube Superhet re-ceiver. Capable of C W tone, and voice reception over fre-quency range of 100—175 Kc, operates from 115V, 400 cycle AC. Can be easily converted to home use. New. \$44.50

Used. Excellent \$32.95

SPECIAL!!



Portable RADIO ATTP own Dry

FAMOUS

TOM

THUMB

Recharges I Batteries Operates on D.C. Four Tube Superhet-erodyne Battery—A.C.-Less Batteries \$25.95

Dealer Price

SPECIALS

Sound Powered Chest SetHeadset
and Mike\$18.95
6 Henry Swinging Choke 7-5 HY
90MA 2000 HM\$2.25
DC Voltammeter I-23 0-10 Volt 0-35
Amps, 21/4 Dia. Pocket Type in
Leather Case. Battery Testing. \$1.20
HS-33 Headset 600 Ohm Cord and
P1 354\$2.39
2 J33 Magnatron\$15.00
700B Magnatron\$35.00

	RELAYS
ŀ	6VDC. DPDT, Antenna, Coll 15-196
ı	HMs\$0.4
ı	6VDC, DPDT, contacts, 6 S. coil, 33
	ohm, nur, open\$0.4
	24VDC, 5A, DPDT, Allied
	#BJ6D36\$0.4
	24 VDC, 50A, SPST, current,
	Leach \$14
	Leach
	Dunn CXA1970, 230 VDC,
	Dulli CARISIO, 250 VDC.
	Amp\$1.9
	110VAC, DPDT, RF antenna,
	change-over\$3.5
	110VAC, Mercury time delay, 30-4
	sec., release .3 sec\$12.9
	115VAC. DPST. contacts Struther
	Dunn 84BXX103, 115VAC, 3
	Amp\$2.4
	115VAC, Time delay, 1 minute enclose
	in waterproof metal box \$3.9
	120VAC contacts:
	4037 204 ACI 204 TOC
	48V 30A, AC 20A, DC
	115V 30A, AC 20A, DC 230V 15A, AC 3A, DC
	230 V 15A, AC 3A, DC

enclosed in metal case, hinged front \$4.50

CIRCUIT BREAKERS 24VDC. 220 AMP, Heinemann. 115V, 30 AMP, Heinemann. 125V, 20 AMP, Westinghouse. \$0.49 \$2.25 \$1.95

FILAMENT TRANSFORMERS 115V—0.12A. 60 cycle output 6.60 @ .6A 2000V Ins. 2.6V @ 1.75A 2700V Ins. 52.95 115V—0.7A 60 cycle output 6.4V @ 10A. 6.3V @ 6A Step-Down Transformer \$3.25 KVA \$2.25

POWER EQUIPMENT
Inverter PE 151 12VDC output 110
VAC 150 W new. \$10.95
Vlhrapack VI'G 369 12VDC 250V @
70 M A synchronous, output Mallory, new 3.45
Voltage Regulator Raytheon 95/130V
1.25 AMPS 60 cycle output 115V
60 Watt, new \$9.50

CAPACITORS

COLVIAL		^	. 1	n				
.0012MFD, 20,000V	D	C					,	23.95
.000375, 5000 VDC .	, .			,	. ,			1.10
.005MFD, 3000VDC		į.						.60
.002MFD, 2500VDC			,					.45
.003MFD, 2000VDC	٠.							. 35
70MMFD, 1140VDC								
.1MFD, 1000VDC .								
Amitto				*				

COAXIAL CABLE
Minimum Order 1000 Feet
RG5U ...\$43.50/M RG11 ...\$58.00/M
RG8U ...\$40.00/M RG22 ...\$85.00/M

Mail orders promptly filled—all prices F.O.B. Boston, Mass. Send M.O. or check. Ship-ping charges sent C.O.D. Minimum order \$5.00. 25% deposit required with all orders. TERMS:

SEND FOR OUR CATALOGUE NOW!

Inquiries from Dealers, Schools and Industrial Firms Invited

ELECTRONIC SALES CO.

24 Tremont St. Tel. CApitol 7-1594 Boston 8, Mass.

COAXIAL CABLES AND CONNECTORS



	83	SERIES
No.	An. No.	Description Price
83-1SP	(PL259)	Plugea. 22¢
83-1SPN	(PL259A.	Plug ea. 22¢
83-168	(UG176U)	Reducing adapter for
	RG 29, 55	
	83-1SP or 83	-1SPN ea 12¢
83-1R	(S0239)	Receptacle ea. 284
83-1AP	(M359)	Angle Plug adapter ea. 226
83-1T	(M358)	Connector ea. \$1.12
83-22R	(UG103U)	Receptacle ea. 35¢
83-22SP	(UG102U)	Plug ea. 35¢
N	Inimum Quai	ntity - 100 of a type
	-	

COAXIAL CABLES



UG TYPE CONNECTORS Deduct 10% from prices shown on quantities of 100 or more of any type

AN Price AN	Price
UG- 9/U 1.14 UG- 97/U	ea 3.50
UG-10/U 1.56 UG- 98/U	1.55
UG-11/U 1.45 UG-100/U	2.34
UG-12/U f.14 UG-101/U UG-13/U 1.56 UG-106/U	2.95
UG-13/U 1.56 UG-106/U	.45
UG-14/U 1.45 UG-107/U	2.25
UG-15/U 1.14 UG-108/U UG-16/U 1.56 UG-109/U	1.75 1.75 1.50
IIG-17/II 1 45 IIG-114/II	1.50
UG-18/U 1 25 UG-115/U	1.35
UG-18A/U 1 05 CW-123/U	.45
UG-18B/U .99 UG-155/U	3.75 3.75
UG-19/U 1.28 UG-154/U	3.75
UG-19A/U 1.38 UG-155/U UG-19B/U 1.45 UG-156/U	3.75
UG-19B/U 1.45 UG-156/U UG-20/U 1.17 UG-160/U	4.25 1.90
UG-20A/U 1 26 UG-160A/I	1 1 55
UG-20B/U 1.41 UG-167/U UG-21/U .99 UG-173/U	2 25
UG-21/U 99 UG-173/U	.30 ≡
UG-21A/U 1 05 UG-175/U	.15
UG-21/U .99 UG-176, U	.15
UG-22/U 1.08 UG-188/U UG-22A/U 1.38 UG-201/U UG-22B/U 1.34 UG-202/U	1.30
UG-22A/U 1.38 UG-201/U UG-22B/U 1.34 UG-202/U	1.22 2.75
DG-205/11	1.02
UG-23A/U 1.26 UG-208/U	28.50
UG-23B/U 1.29 UG-27A/U 2.25 UG-213/U	4.50 4.50
UG-27A/U 2.25 UG-213/U	4.50
UG-28/U 2.34 UG-215/U	3.35
UG-29/U 1.22 UG-216/U UG-30/U 1.75 UG-213/U	8.70 3.10
UG-30/U 1.75 UG-213/U UG-313/U UG-218/U UG-218/U	6.50
UG-33/U 30.00 UG-218/U UG-34/U 35.00 UG-222/U UG-35A/U 28.00 UG-231/U UG-36/U 35.00 UG-231/U	35.00
UG-35A/U 28.00 UG-231/U	2 00 =
UG-36/U 35.00 UG-236/U UG-37/U 28.00 UG-241/U	11.75
	2.20 2.50
UG-37A/U 30.00 UG-242/U UG-57/U 99 UG-243/U	2.50
UG-57/U .99 UG-243/U UG-58/U .63 UG-244/U	2.75
UG-59/U 2.75 UG-245/U	1 25
UG-59A, U 1 70 UG-246/II	1.45
UG-60/U 1.90 UG-252/U	4.50 ■
UG-60A/U 1.30 UG-254/U	1.82
UG-61/U 2.05 UG-255/U UG-61A/U 1.80 UG-260/U	1.85
UG-61A/U 1.80 UG-260/U UG-62/U 28.00 UG-261/U	1.12
UG-62/U 28.60 UG-261/U UG-83/U 1.50 UG-262/U	1.12 .95 1.05
	2.60
UG-86/U 1.69 UG-273/U	1.50 ≡
UG-87/U 1.40 UG-274/U	1.98
UG-88/U 1.17 PL-274 UG-89/U .95 UG-290/U	1.12
UG-90/U 1.05 UG-291/U	.85 1.05
UG-91/U 1.25 UG-306/U	2.03 =
TIC-91 A / II 1 05 TIC-333 / II	4.70
HG-92/H 1 10 HG-334/H	4.70 5.75 6.00
UG-92A/U 1.35 UG-352/U UG-93/U 1.25 UG-287/U	6.00
UG-93/U 1.25 UG-287/U UG-93A/U 1.45 UG-270/U	5.25 6.50
HG-94/H 1 25 F HG-959/TI	4.10
UG-94A/U 1.05 UG-279/U	2.40
UG-95/U 1.10 UG-157/U	4 25
UG-94A/U 1.05 UG-279/U UG-95/U 1.10 UG-157/U UG-96A/U 1.35 MX-195/U UG-96/U 1.25 UG-197/U	.55 5.25
UG-96/U 1.25 UG-96A/U 1.45 UG-197/U UG-23/U	28.50
UG-80A/U 1.45 UG-23/U	20.30 =

LIFE ELECTRONIC SALES

91 Gold St., N. Y. 7, N. Y. Tel: DI gby 9-4154

ELECTRONIC SPECIALS

RA-34 power supplies—0-1000V-350MA- 12V-2A-DC-12V-14A-AC
RA-38 power supplies—0-15000V-500MA \$275.00
RA-58 power supplies-0-15000V-35MA \$140.00
Switches for above—15000V-1.5Amp. Oil filled—110VAC\$42.50
Relays—6VDC-5PST & 5PDT-120 ohms- 2200 turns
Relays—Sensitive-8000 ohms-SPDT-Silver contacts
Relays—Aircraft Radio Antennae—24VDC SPDT—Silver contacts
Relays — Allied Control — DPDT-24VDC- .079-Type BJ\$.95
Condensers—Standard Brand-D168574-16 MFD-120VAC 400 Cy-400VDC\$2.75

SCR-296 — Basic Components, Complete Parts, Stock Plumbing, etc.

Transformers-3000 items of transformers

Test equipment—Over a thousand items in stock of practically every type. Let us know of your needs. We specialize in hard to get electronics.

MONEY BACK GUARANTEE ON DEFECTIVE MATERIAL

SUBJECT TO PRIOR SALE

VETERANS SALVAGE CO., INC.

9 Kulik St.

Passaic-3-6370

Clifton, N. J.

PRECISION CAPACITORS

Standard Brand

D-166602 Oil	18	mfd	800	WVDC\$2.95
289A Oil	7	mfd	500	WVDC\$1.95
D-162003 Oil	4	mfd	500	WVDC\$1.35
231A Paper	3	mfd	250	WVDC\$.95
D-162031 Paper	2	mfd	550	WVDC\$.95
D-170908 Paper	.152	mfd	300	WVAC\$.95

TELEGRAPH V.F. BAND PASS FILTERS W.F.

D-162235	Mid band f	req 935	cps
D-162240	Mid band f	req1955	cps
D-164911	Mid band f	req2125	cps
D-164912	Mid band f	req2295	cps
	Ahove filte	rs \$35.00 each	

SPECIALS

W.E. 2' P2AA cord with 2 No. 241A	
W.E. twin plugs	\$4.95
McElroy SR900 Signal Recorder (used).	10.00
Jones 4-141 Terminal Strips, per C	\$9.50
Lord Shock Mounting #200P45, per C	\$9.50

Write for Quantity Prices No Orders Less Than \$5.00 Accepted

RAILWAY COMMUNICATIONS, Inc.

P. O. Box 1783

Phone 2-6487

Lincoln, Nebraska

A/N Connectors


We have a large selection of war surplus A/N Connectors of Standard line manufacture. Our catalog will be furnished to Industrials, Manufacturers and Laboratories upon request.

MARCO ELECTRONICS, INC.

513A W. Franklin Street

Balto, 1-Md.

Lex. 0198

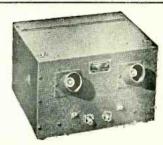

BOONTON 120A VHF CIRCUIT CHECKER

This instrument was developed by the Boonton Radio Corp. to permit checking at VHF: Capacitance, Inductance and complete Resonant Circuits, Ideal for Television and FM Tuners, Quality control, etc. Three Frequency Ranges. Available for immediate delivery.

Catalog price is \$320.00—Our price is \$150.00 f.o.b. N.Y.C. Reconditioned, in good operating condition, subject to prior sale.

THE NATIONAL INSTRUMENT CO. FAR ROCKAWAY, N. Y.

SEARCHLIGHT SECTION OP

	1N23 Crystal Dioc	les
	10c Ea.	
	Limit 3 To a Customer	
	ELECTROLYTIC CONDENSER	es.
	2 X 4500 Mfd. 2 V 2 X 3000 Mfd. 3 V 2 X 1250 Mfd. 10 V 600 Mfd. 25 V 2 X 500 Mfd. 25 V 2 X 3500 Mfd. 25 V 2 X 3500 Mfd. 50 V 100 Mfd. 50 V 50 Mfd. 100 V 2 X 40 Mfd. 150 V 500 Mfd. 200 V 30 Mfd. 450 V 2 X 8 Mfd. 475 V 2 X 19 Mfd. 575 V	,60 ,90
The state of the s	OIL FILLED CONDENSERS 2 X 5 Mid. 400 VDC 1 Mid. 400 VDC 2 Mid. 600 VDC 5 Mid. 600 VDC 3 X 4 Mid. 600 VDC 4 X 3 Mid. 600 VDC 7 Mid. 600 VDC 2 X 8 Mid. 600 VDC 2 X 8 Mid. 600 VDC 2 X 4 Mid. 1000 VDC 4 Mid. 1000 VDC 4 Mid. 4000 VDC 4 Mid. 2000 VDC 4 Mid. 4000 VDC 5 Mid. 4000 VDC 1 Mid. 7500 VDC 25 Mid. 100 VDC 1 Mid. 7500 VDC 25 Mid. 2 0 KVDC 08 Mid. 12.5 KVDC	.30 .20 .35 .35 .35 .70 1.45 1.45 1.75 1.75 1.70 .95 7.95 1.25 19.95 9.95
	VARIABLE CONDENSERS (Maximum Ratings Per Section)	
	Single Sec. 18 Mmfd. 5000	V. — V. — V. — V. — V. — 1.75 1.45 1.75 9.95 3.75 4.95
	MICA CONDENSERS	.25
	.0001 Mfd. 600 VDCW .005 Mfd. 600 VDCW .4 Mfd. 600 VDCW .0001 Mfd. 5000 VDCW .0004 Mfd. 5000 VDCW .005 Mfd. 5000 VDCW	.25 1.45 .75 .75 .75
	MISCELLANEOUS 300 Ohm Twin Leadper ft. \$.025
	Swinging Choke 9-36 H. @ .75/.075	.055
	Relay 115 VAC DPDT-30 Amp. Con-	4.95
	100 Insulated Resistors—1/2 & 1 W. Asst'd. 110 V. Line Filter 2 Amp. Blocking Oscillator Transformer (Wemco)	1.45
	Blocking Oscillator Transformer (Wemco) Hookup Wire—Asst'd, Lengths & Col-	.45
	ors W/Tinned Ends. Approx. 500	1,45
	4AG Fuse Extractor Post (Ideal Crystal Diode Holder). Pulse Transformer (300 K.V.). 1. Power Transformer (800/2400 Cps. For Scope)	.15 4.95
	Power Transformer (800/2400 Cps. For Scope)	2.75
10000	Reactor (2000 Henries @ 10 Ma.) Reactor (2000 Henries @ 0 Amp.) Reactor (19000 Henries @ 0 Amp.) Transformer (7670 V. @ 483 Ma.) 22	1.25 2.50 2.50 2.50 2.50
	Discounts to Quantity Buyers Min. Mail Order \$2.00—	
	25% Dep. With Order Bal. COD Write Your Needs	
	wine rour reeds	

MARCO ELECTRONICS, INC.

513-515 W. Franklin St., Baltimore 1, Md.

Phone—Lexington 0198

10 Cm OSCILLATOR BC-1096-B with 30 mc pre IF amplifier 1078 B, klystron	125/APR ANTENNA
power supply and 417-A klystron, 110 v, 60 cps, new in transit-case, p/o SCR	TS 10/AP for APN-1\$40.00
584\$125.00	TS 102/AP CALIBRATOR\$75.00
10 Cm TEST LOAD TPS-55 PB/T. \$5.00	TS 203/AP CALIBRATED SELSYN \$13.00
10 Cm TUNABLE REFERENCE CAVITY, with IN27 crystal and holder, type N Fitting	TEST SET I-178 CALIBRATOR\$75.00
CALIBRATED S BAND FIXED ATTENU-	TEST SET IE-21-A, for SCR-518A\$75.00
ATOR, type N fittings\$10.00 S BAND RECEIVER TRANSMITTER RT-	TEST SET IE-19-A, for SCR-522 \$175.00
72/UPN-1, less tubes, for battery operation	TELEFONE TEST SET EE-65-F\$30.00
X BAND VSWR TEST SET TS-12/AP, complete with linear amplifier, direct	SYNCHRONIZER W.E. BC1043B\$75.00
reading VSWR meter, slotted wave guide with gear driven traveling probe, matched	SYNCHRONIZER W.E. BC1155-A\$50.00
termination and various adapters, with carrying case, new.	MODULATOR W.E. BC748-A, 10 kw, 1.3 microseconds, 750-850 PPS, new, less tubes
X BAND PICK-UP HORN AT-48/UP, with coaxial fitting	TRANSMITTER RECEIVER BC800M,
X BAND POWER METER TS-36/AP,	new\$30.00
new	MODULATOR BC 1007-A\$75.00
X BAND WAVE METER [S-33/AP, new	RECTIFIER-POWER UNIT, 110 v, 400 cps, PP-4/APQ-2
X BAND POWER LOAD TS-108/AP,	HI VOLTAGE SUPPLY, RA-90-A, 110 v, 400 cps\$10,00
microwave Test Cable, 15' RG-9U cable with UG-24U connectors. 15 feet long \$4.00 8 feet long \$3.50	GO-9 TRANSMITTER, less tubes\$100.00
LOSSY CABLE, 10 db at 3300 megacycles, type N connectors\$3.00	TRANSMITTER BC-AR-230, new, less coils\$5.00
TYPE N CONNECTORS AND ADAPTERS, UG-10, 12, 21, 22, 24, 25, 27, 29, 30, 58, 59, 83, 86, 167, 190, 201, 245 and	W.E. NETWORKS, D-162630, D-162629, D-161637, D-162634\$1.00 each.
UHF Connectors SO-239, PL-259, 83, IAP, UG-266, complete with center contacts, immediate delivery.	G.E. DELAY LINE, 4 microseconds 1000 ohms, O-2 mc
RADAR JAMMER, T-26/APT-2, 435-715	TRANSFORMERS, 115 volts, 60 cps primaries:
megacycles. 110 volts, 400 cps, new, complete with antenna\$40.00	1. 6250, 3250 and 2000 volts, tapped primary
SD-3 SHIPBOARD RADAR EQUIPMENT, complete with all accessories, operates on 115 volts, 60 cps, new.	2. 6250 volts 80 ma, ungrounded, G.E
SA-1 RADAR TRANSMITTER, Receiver and Indicator, 115 volts, 60 cps, new.	PULSE INPUT TRANSFORMER, permalloy
RADAR RECEIVER BC 1068-A, 150-200 megacycles, individual tuning for the r.f. stages, band widths 4 megacycles, 115	core, 50 to 4000 kc impedance ratio 120 to 2350 ohms
volts, 60 cps, 14 tubes\$45.00	VARISTORS WE D171528, D171628,
GENERAL RADIO PRECISION WAVE- METER, type 724A, range 16 kc to 50 megacycles, 0.25 % accuracy, V.T.V.M. resonance indicator, complete with acces-	D161871-A
sories and carrying case, new. \$175.00	Westinghouse NX-35\$4.50

ELECTRO IMPULSE LABORATORY

66 Mechanic St., Red Bank, N. J.

Red Bank 6-4247

MARINE EQUIPMENT—NAVAL & COMMERCIAL

Partial Listing

ET-8023D1—200 watts ship transmitter, 2.0-24.0 mcs. Mfd by Radiomarine Corp. of America. NEW in original cases w/ installation material and set of spare

136A—Mackay ship transmitter, 40 watts cw, 5.5-22 mcs. Supplied complete w/110 V dc motor generator and spares for both m/g and XMTR. NEW, export packed, \$115 per set.

phone, 350 watts cw, 2.0-20.0 mcs. Operates from 110 AC. Condition: EXCELLENT, One only at \$825.00.

INSULATORS—Standoffs, Feedthru's and Strains. We have tens of thousands in stock. Please advise size and quantity desired.

stock. desired.

TBK-500 watts cw Navy transmitter, 2.0-20.0 mcs

TAJ — 500 watts cw Navy transmitter,
150-550 kcs
TBL—350 watts cw, 50 watts phone, 175600 kcs and 2.0-18.1 mcs.
Each of the above supplied with 115 or 230
vdc motor generator and magnetic controller. TBL has speech input eqpt. Condition: EXCELLENT.
Underwater Sound Beacons—Model NAA.
Consists of a buoy-shaped water-tight,
welded container fitted with omnidirectional electrosonic transducer. Inside are
batteries, oscillator-amplifier, vibrator
power supply, timer and self-destroying
device, which can be removed if desired.
Beacon emits 5 watts audio at 10 to 20
kcs at chosen code for 48 hours. NEW,
original packing.

original packing.
SPECIAL INTRODUCTORY OFFER-12 in. standoffs w/brass or bronze base and cap at \$1.00 each.

AIRCRAFT EQUIPMENT

Partial Listing

ASB-5-515 Mes. Airborne Radar. Complete Brand New early search and homing sets, including transmitter, indicator switching unit, rectifier power unit, control unit, etc. Mfr. Bendix.

Z A — Blind Landing Eqpt. 90-100 Mcs., complete, new with test oscillators and spares for same.

GP-7 transmitter complete w/8 plug-in tuning units covering range of 350-9050 kcs, emission A₁, A₂, A₃, 85-125 watts. Mfr. Westinghouse. Condition: Brand

MN-26-Bendix Radio Compasses-Com-

plete, new. APS-4—Junction boxes, J-84. Brand new in original packing.

TEST SETS

TS-263A/TPS-10—Complete, portable f.m. field test set used to check radar in band 8990-9170 Mcs.
Power Requirements: 60 watts at 115 V, 50 to 1200 cps.
Power Output to Waveguide: 5 decibels above 1 milliwatt, max.
Power Output to Coaxial Cable: 4 decibles above 1 milliwatt, max.
Price: \$545.00.

This set is new, complete in one portable unit and ready for use. No permanent or special installation procedures are necessary. Quantity: Very limited.

METER MULTIPLIERS — PRECISION RESISTORS. 20,000 volts, 20 megohms. Accurary ± 0.5%. New, in original packing. Standard Brands. Manufacturer's current list is more than \$240.00! Our price: \$12.00

TDY Radar jammer — Power Oscillator only; 110 V AC, 60 c. Brand new, less tubes at \$95.00 ea.

TYPE O—Reversible magnetic starters, 1 to 2 hp., 110, 220, 440 V. AC. Mfr. Westinghouse.

We carry an extensive stock of marine and aircraft electronic accessories Your requests for quotations are invited

All material is offered subject to prior sale, f.o.b. our warehouse. Terms: Cash

COMPASS COMMUNICATIONS CO.

37 Montgomery Street

Phone: Delaware 2-4656

Jersey City 2, N. J.

ALLIS-CHALMERS

MOTOR GENERATORS U. S. Navy specifications



1.88 KVA—1.5 KW—.8 PF
Input—115 VDC—20 Amps
Output—120 VAC—15.65 Amps
Single phase—60 cycle
Allis Chalmers Motor—2.2 HP—3600 RPM
Centrifugal Starter
Ward Leonard Speed Regulator

Price \$175.00—Gov't Cost \$1028.94

SPEED REGULATOR

1.25 KVA—1 KW—8 PF Input—115 VDC—14 Amps Output—120 VAC—14.4 Amps Single phase—60 cycle Allis Chalmers Motor—1.93 HP 3600 RPM Centrifugal Starter

Price \$90.00-Gov't Cost \$439.52 COMPLETE WITH SPARES • EXPORT PACKED IN ORIGINAL CASES

SHIPS & POWER EQUIPMENT CORPORATION

829 Newark Avenue

Elizabeth 2-6925

Elizabeth, New Jersey

SHEET METAL MACHINERY

NEW and Used — Brokes — Shears Forming Rolls — Folders — Punches — Di-Acro, Pexto, Niagara & Whitney Equip-

R. D. BROOKS CO., INC. 361 Atlantic Ave., Boston, Mass.

ART-13 POWER SUPPLIES AND LOW FREQUENCY OSCILLATORS

High Power R.F. Ampliflers, Special Equipment. Quotations on request.

SPECTRA PRODUCTS
rs St. New York 7, N. Y. 155 Chambers St.

SIGNAL GENERATORS

GENERAL RADIO	805-A
FERRIS	16-C
FERRIS	18-B
MEASUREMENTS	65-E
BOONTON	155-A
BOONTON	140-A

IMMEDIATE DELIVERY - RECONDITIONED GUARANTEED

Subject to Prior Sale, F.O.B., N. Y. C.

THE NATIONAL INSTRUMENT COMPANY FAR ROCKAWAY

TUBES

(No Government Surplus)
Made by one of the nationally known, first-line tube
manufacturers, each and every tube is new, individually tested, boxed, and carries the standard
RMA guarantee. Your money back if not completely
satisfied

1S5 1T4 3S4 6AT6 6BA6 6BE6 6K5GT	6SA7GT 6SJ7GT 6SK7GT 6SQ7GT 6V6GT 6X5GT 12AT6 12BA6 12BE6	12SA7GT 12SJ7GT 12SJ7GT 12SQ7GT 35L6GT 35W4 35Z5GT 50B5 50L6GT	Any Type 36⊄ each
--	---	--	----------------------------

Minimum order \$3. 20% with order, bal. C.O.D. Write Dept. 4011 for FREE CATALOG. Store open daily 9 to 6, Sat. 9 to 5.

RADIONIC EQUIPMENT CO. 170T Nassau Street, New York 7, N. Opp. City Hall: Near B'klyn Bridge

Special Values

D. C. MICROAMMETERS

0-100	ua.	4" sq.	G.E.	DO 58		. \$12.00
same	with	ı "Vo	t-Ohn	1-M.A."	scale.	. 12.00
0-100	ua.	21/2"	Gruen			. 4.00
0-100	ua.	41/2"	round	Westor	643.	. 12.00
0 - 200	ua.	41/2"	round	Westor	643.	. 10.00

R. F. MILLIAMMETERS

0-100	Ma.	31/2"	Weston	425 .					è		. 2	9.00
0 - 120	Ma.	21/2"	Weston	507		41				٠		7.00
0-10	ма.	4 1/9 "	Weston	(vac	u	u	n)	٠	٠		22.00

SHUNTS

150 or 240 Amps-50 Mv-aircraft type \$1.00

PRECISION ELECTRICAL INSTRUMENT CO. 146 Grand Street New York 13, N. Y.

VILLAGE RADIO EQUIPMENT CO. Announces a New Service THE TEST EQUIPMENT EXCHANGE

PURCHASING AGENTS: Do you require an item of TEST EQUIPMENT presently unavailable? Do you have equipment surplus to your present operations? LIST YOUR REQUIREMENTS and SURPLUS with us to effect an advantageous exchange or purchase.

Write for Full Details

VILLAGE RADIO EQUIPMENT CO. 201 West 16 St., New York 11, N. Y.

TELEVISION CAMERAS

Available for immediate delivery.

DUMONT Type 5027-A IMAGE ORTHICON PICKUP HEADS, with type 5047-A ELECTRONIC VIEW FINDERS, complete with all tubes,—including 2P23 Image Orthicons. EKTAR 90 MM. f 3.5 Lens

Factory Reconditioned—Perfect Condition f.o.b. N.Y.C. Subject to prior sale

WRITE FOR COMPLETE INFORMATION

THE NATIONAL INSTRUMENT COMPANY

FAR ROCKAWAY

COMMUNICATION DEVICES CO. offers **CLEAN ELECTRONIC SURPLUS!**

The Versatile U. S. Navy TDE Transmitter

An all-band (300-18,100 kcs) two section transmitter in one steel cabinet complete with tubes and M.G. with outputs of 125 watts A-1, A-2; 35 watts 'phone. In 115 or 230 Volt DC models. Tested, clean, and complete.

RADIOTELEPHONES-

SCR-281 (BC-441-Hallicrafter) for 110 V. AC, xtal controlled, 25 watt unit with all tubes, speaker, hand telephone and mtg. Less crystals, excellent condition, each\$169.50

MQ (Mfged by R.C.A.) for small craft. Five watts output, uses 6/12 Volt DC source, range 2-3.5 Mc, w/speaker, remote hand telephone, tubes, less xtals, NEW, each\$100.00

F.M. Point-To-Point RADIO LINK

Our large stocks of SCR-528 (20.0-27.9 Mc) transmitters and receivers are complete with all components and accessories export packed for immediate delivery, weight 163 lbs. Write for our bulletin describing its minute completeness!

RECEIVERS—

Wilcox 602-A, xtal, fixed freq, 110 V. AC, receiver for VHF (30-160 Mc) airline monitoring. NEW w/tubes, less xtals, each\$39.50

Wilcox CW-3, xtal, fixed freq, 110 V. AC, for medium freqs. with tubes, manual, 1 set of coils, less xtals. NEW each\$29.50

THIP ANTENNAS — AN-131-A, as threaded base, 10'6" long, folds into 8 WHIP interconnected sections for stowing. NEW, each\$1.49

OTHER ITEMS-Bludworth, R.C.A. direction finders complete; 220/110 stepdown transformers all ratings; vibrapacks.

Complete walkie-talkies, Model MAB


Offerings subject to prior sale. Catalog sent on request.

COMMUNICATION DEVICES CO.

2331 Twelfth Avenue at 133rd St. New York 27, N. Y.

Cable: Communidev Tel: WA-6-6606, 7

Industrial Power Supply Equipment

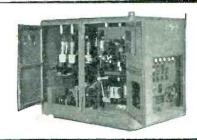

NEW RA38 POWER SUPPLIES

115V., 60 cyc. input adjustable output 0.15,-000V. A.C. or D.C. @ 500 Mils. Complete with extra set of new tubes and remote control. Shipping weight 2100 lbs. \$250.00

RECTIFIERS - Dry Disc Type-**Continuous Duty Ratings**

٠	3.5V. A.C. 1.8V. D.C. 1.0 Amps Full Wave Bridge	.90
٠	6.5V. A.C.—2.2 V. D.C. @ 3.0 Amps Full Wave Center Tap	1.20
	36V. A.C. 200 Mil D.C. H.W	.75
٠	36V. A.C. 2.2 Amps. D.C. Full Wave Bridge	3.75
٠	54V. A.C.—1.6 Amps. D.C. G.E. Full Wave Bridge	4.40
٠	154V. A.C.—600 Mil D.C. Full Wave Bridge	6.85
٠	180V. A.C.—400 M.A. D.C. G.E. Full Wave Bridge	6.90

CONDENSERS

500 Mfd 200V dry Electrolytic	95
2 Mfd 600V Tubular Oil	39
10 Mfd 600V Oil	95
2 Mfd 2500V Oil	40
2 Mfd 3000 Oil 2.	75
.25/.25 6000V D.C. or .125 Mfd-	
12000V D.C. Oil	75
1.0 Mfd 25 KV	00
.001/25 KV Mica	00
50 MMF 32 KV Tubular vacuum 4.	95

RELAY

TRANSFORMERS -



T-103—Voltage regulator Transtat, American Transformer Co. Spec. 29145 Max KVA output 11.5 50/60 cyc. 0.115V. 100 amps. or 230 V. 50 amps. \$75.00

Net Wt. 134 lbs. Dim. 25" W x 16" D x 17½" H (Encl. 8" shaft ext.)

T-102—Filament Transformer, American Transformer Co. Spec. 29106, Type WS. 050 KVA, 50/60 cyc. Single phase, 35 KVA test, 12 KV D.C. operating. Primary 115 V., secondary 5 V., 10 amps with integral standoff insulator and socket for 250T, 371, 872 5563, etc rectifier tubes.

tubes\$12.50 Net Wt. 15% lbs. Dim. 6½" W x 6" D x 12" H.O.A.



\$1.60 \$1.25

METERS

Weston Model 476-3" A.C. Ammeter, 3 Amps full scale, Calibrated 0.120 Amps., with 40/ Net wt. 3 pounds \$8.50 current trans

M-143 A.B. Weston Kilovoltmeter-3". Model 301, 20 KV. @ 1000 ohms per volt, flush type calibrated for steel panel mountings with 20 meg. 20 KV Weston resistor complete with clips and standoff insulators. \$18.00

Net wt. 4 pounds.

Multimeter, Supreme model 543-S \$12.95

R. F. ammeter Weston 425-0-3 amps \$5.95

TRANSTATS

 115 V. 50/60 cycle input 103-126 V. output @ 2.17 amps\$9.50
 115/230 V. 50/60 cycle input 0.260 V. output @ 2½ amps\$21.50
 GR Variac, 115 volts 50/60 cycle in- put 0.135 V output @ 5 amps cased.\$14.50
 115 V. 50/60 cycle input, 0.135 V. output @ 10 amps\$24.50
THERMOSTAT SWITCH

TUBES

TRANSMITTING	THYRATRONS	RECTIFIERS
RK75/307A 4.50 450TH/6C21 22.50 750TL 47.50 WL533 750W U.H.F. Triode 17.50 714AY Magnetron 9.50 730A Magnetron 10.75	2D21 Min. 1.25 3c23 4.75 FG81A 4.75 C6A 8.50 C6J 9.50 931A Photo-Multiplicr 2.75 All Tubes New, Boxed and of Standard Mfg.	FG32 4.00 371B 5.95 531 18.00 872 1.75 3B22 2.95 4B28/289414 6 Amp. Rectigon 3.95

MOTOR GENERATORS

G.E. Type CC-21991 Input 115 volts D.C., @
5.7 amps. Output 115 V. A.C. 60 cycle, single
phase 350 V.A. @ 85%\$58.00
G.E. Type CC-21990 Input 32 V. D.C. @ 22
amps. Output 115 V. A.C. 60 cycle, single
phase, 350 V.A. @ 85% P.F\$63.00
Leland Type CLL-21985 Input 115 V. D.C. @

4.2 amps. Output 115 V. A.C. 60 cycle, single phase, 240 V.A. @ 86% P.F. \$47.00

WESTINGHOUSE-Type "AB"

De-ion circuit breakers

Thermal trip-without enclosure 3 pole-50 amp frame size Style 545-389 D 15 amp rating ... 9.50 ea.
Style 545-391 D 25 amp rating ... 9.50 ea.
Style 545-393 D 50 amp rating ... 9.50 ea.

HEATERS

All merchandise in "as new" condition. Add approximately 20% to net weights for estimated shipping weights. Terms are 30% with order, balance C.O.D. All prices f.o.b. Los Angeles Warehouse, Write for additional detailed information on any of the above items and for special quality discounts.

1527 E. Seventh Street



Los Angeles 21, California

SEARCHLIGHT SECTION ID

MAGNETRONS

	1-1-1-1
In Q	uantities
2j31	12
714AY	6
725 A	12
730 A	6
ask us if y	ou need others
	STRONS
723a/b	6.95
2K25	18
707B	6.95
2K28	15
P	ULSE
MOD	ULATORS
715B	9
5D21	18
701A	6
STAR FLECT	RONICS CORP.
	iberty St.
New York 6	Phone Worth 7-8262
ILEM LOLK O	Filone Worth /-0202

WANTED

WANTED

W. E. Carrier Telephone and Carrier Telegraph Equipment and Filters, repeating components. Coils, Transformers, Equalizers. Type CF1, CF2, H, C, and other carrier equipment, telephone and telegraph repeaters.

W-6660, Electronics 330 West 42nd St., New York 18, N. Y.

WANTED 12 Sets of ARC5 Equipment

as follows: R25 Receiver (1.5-2 mc.) MT7A Receiver Rack MT5 Receiver Base T18 Transmitter (2.1-3 mc.) MT69 Transmitter Rack MT68 Transmitter Rack MT68 Transmitter Base MD7 Modulator DY8 Dynamotor MT76 Modulator Base, MT77 Relay Base T17 Microphone HS33 Headset E39 Receiver Local tuning knob PL152 Plug PL147 Plug PL151 Plug PL148 Plug 9377 Plug 9377 Plug. W-6640, Electronics, 330 W. 42 St., N. Y. 18, N.Y.

WANTED

Teletypewriters complete, components or parts. Any quantity and condition.

W-6654. Electronics 330 West 42nd St., New York 18, N. Y.

WANTED

WESTERN ELECTRIC VACUUM TUBES
Types 101F, 102F, 272A, 274A or B, 310A
or B, 311A, 313C, 323A, 328A, 329A, 348A, 349A, 352A, 373A, 374A, 393A, 394A, 121A Ballast Lamps.

W-6641, Electronics

330 West 42nd St., New York 18, N. Y.

WANTED

TEST EQUIPMENT

All types of Laboratory Test Equipment, new, used or surplus. Send description to

W-4861, Electronics 330 West 42nd Street, New York 18, N. Y.

WANTED, AIRCRAFT RADIOS

AN/ART-13, BC-348, RTA-1B, AN/ARN-9, R5A/ARN-7, AN/ARC-1, AN/ARC-3, SCR-718, BC-788-C, I-152, MN-26-C, Test Sets with TS- or I- prefix. State quantity, condition and best price first letter.

HI-MU ELECTRONICS

BOX 105, NEW HAVEN, CONN.

8-DRAWER EQUIPTO STEEL SHOP CABINET



NOW IN STOCK!

Despite current steel shortages, we have a limited quantity of these remarkably useful cabinets in stock NOW. Contains 8 drawers, each with 4 compartments. Overall: 251/2" ide, 10" high, 12" deep. Olive green baked enamel finish. Can be stacked up to six high. Your Cost, each

Please include 25% Deposit with order. Balance C.O.D. Dept E-11

FEDERATED PURCHASER Inc. NEW YORK CITY ALLENTOWN, P. 80 Park Place JIS Hamilton St Digby 9-3050 Allentown 3.744

SURPLUS BARGAINS

WESTINGHOUSE HYPERSIL CORE TRANSFORMERS

Pri 115V 60cy, ¼ KVA, Sec #1-240V # 1.56A, Sec. #2-240V @ 1.56A, Wt. 30 lbs.—\$11.50 ea., 10 @ \$10.00 ea.

Pri 115V 60cy tapped, Sec 5V @ 30A\$3.32
ELINCO PM-2 Rate Generator\$6.00
EAD J-36 Rate Generator \$7.00
FILTER CHOKE-Hermetically sealed 10H at 400
MA DC, 90 ohm res. wt. 11 lbs\$3.85
W. E. Sound Powered Hand Set
W. E. Sound Powered Chest Set\$14.88
TUBES AT SENSATIONALLY LOW PRICES
WRITE FOR LATEST BARGAIN BULLETIN

LECTRONIC RESEARCH LABORATORIES 5832 N. Hegerman St., Philadelphia 24, Pa. Phone—Cumberland 8-4737

EMPLOYMENT . . . EQUIPMENT BUSINESS

OPPORTUNITIES Whatever your need—

think "SEARCHLIGHT" FIRST

LEGAL NOTICE

LEGAL NOTICE

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACT OF CONGRESS OF AUGUST 24, 1912, AS AMEXDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946

Of Electronics, published monthly at Albany, N. Y., for October 1, 1948. State of New York}

State of New York}

Before me, a Notary Public in and for the State and county aforesaid, personally appeared J. A. Gerardi, who, having been duly sworn according to law, deposes and says that he is the Secretary of the McGraw-Hill Publishing Company, Inc., publisher of Electronics, and that the following is, to the best of his knowledge and the publisher of the ownership, management, etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, as amended by the Acts of March 3, 1933, and July 2, 1946 (section 537, Postal Laws and Regulations). printed on the reverse of Form 3526, to wit:

1. That the name and address of the publisher, editor, managing editor and business manager is: Publisher, McGraw-Hill Publishing Company, Inc.; Editor, Donald G. Fink, Managing Editor, W. W. MacDonald; Business Manager, Wallace B. Blood, all of 330 West 42nd Street, New York 18, N. Y.

2. That the owner is: McGraw-Hill Publishing Company, Inc., 330 West 42nd Street, New York 18, N. Y.; James H. McGraw, Jr., 330 West 42nd Street, New York 18, N. Y.; James H. McGraw, Jr., 330 West 42nd Street, New York 18, N. Y.; James H. McGraw, Jr., Stockholders holding 1% or more of stock: Curtis W. McGraw, Jr., 2012 and 11 of 330 West 42nd Street, New York 18, N. Y.; James H. McGraw, Jr., 1912 and 11 McGraw, Jr., 2012 and 201

total amount of bonds, mortgages, or other securities are:

None.

4. That the two paragraphs next above, giving the names of the owners, stockholders, and security holders are:

if any, contain not only the list of stockholders and security holders as they appear upon the books of the company but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given: also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.

J. A. GERARDI, Secretary.

McGRAW-HILL PUBLISHING COMPANY, INC.

Sworn to and subscribed before me this 29th day of September, 1948.

ELVA G. MASLIN.

(My commission expires March 30, 1950.)

Use National

CLASSIFIED ADVERTISING

for bringing business needs or opportunities to the attention of men associated in administrative, executive, management, sales and responsible technical, engineering and operating capacities with the industries served by McGraw-Hill publications.

For advertising rates or other information address: Classified Advertising Division

McGRAW-HILL PUBLISHING CO., Inc. 330 W. 42nd St., New York 18, N. Y.

