




**RF**  
PHOTOFACT

# REPORTER


for the Electronic Service Industry



### This Month's Highlights

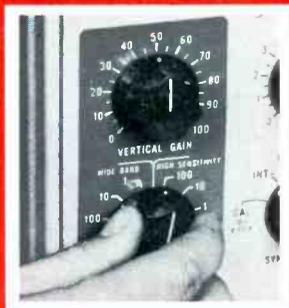

**CHOOSING A SCOPE**  
(see page 25)

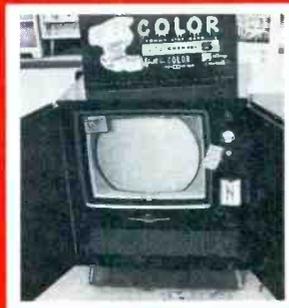


**WHAT'S COOKING  
IN COLOR TV**  
(see page 21)



**WORKING WITH  
SOLDER GUNS**  
(see page 16)


# New IRC Dual Diodes

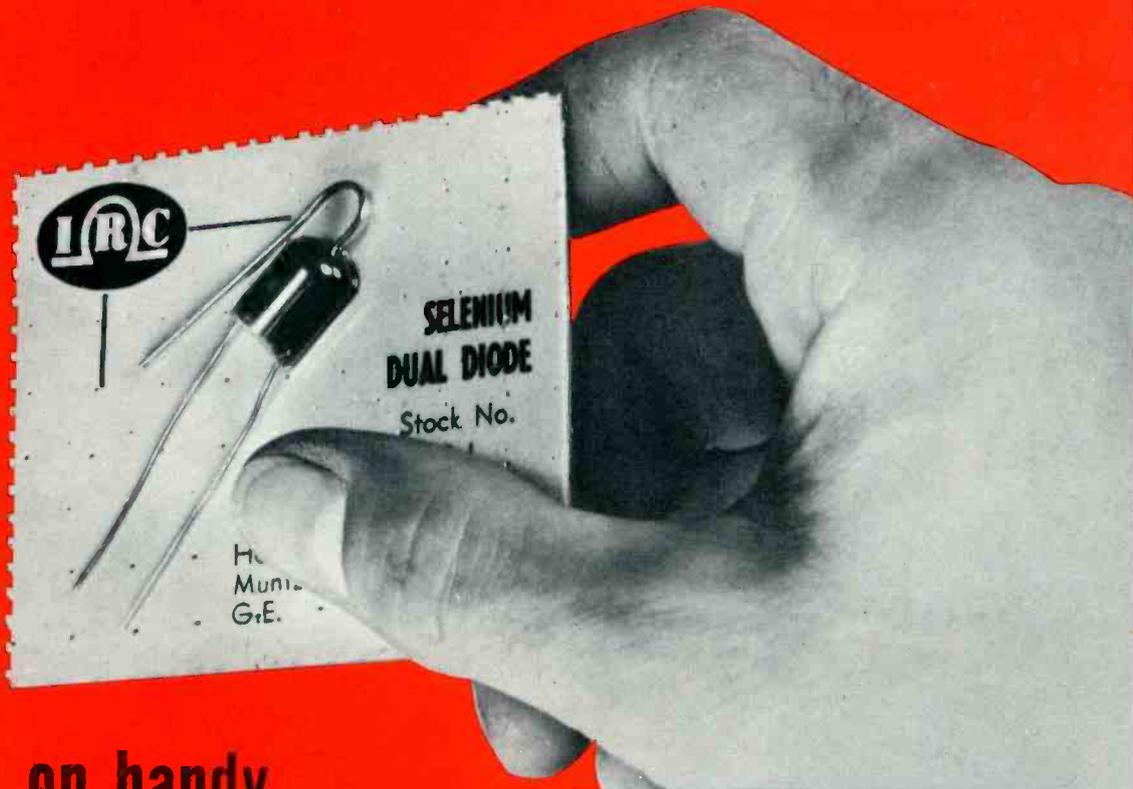

## on handy "skin-packed" cards

Now that many TV set manufacturers are using selenium dual diodes instead of vacuum tube diodes, there's a new replacement market for you. And here are the three best ways to meet replacement needs . . . IRC's new exact duplicate dual diodes! These units are especially designed to provide exact duplicate replacements. What's more, each and every one is completely identified on an individual card and fully protected from dirt, dust, and handling by revolutionary IRC "skin-packing".

**ORDER FROM YOUR IRC DISTRIBUTOR**

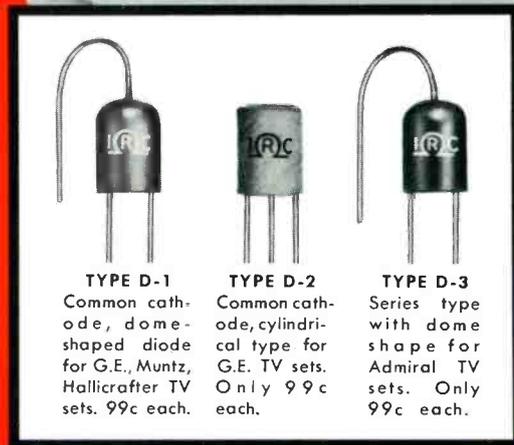

<b>TYPE D-1</b>	<b>TYPE D-2</b>	<b>TYPE D-3</b>
Common cathode, dome-shaped diode for G.E., Muntz, Hallicrafter TV sets. 99c each.	Common cathode, cylindrical type for G.E. TV sets. Only 99c each.	Series type with dome shape for Admiral TV sets. Only 99c each.

*Wherever  
the Circuit Says*



## INTERNATIONAL RESISTANCE CO.

Dept. 367, 401 N. Broad St., Phila. 8, Pa.

In Canada: International Resistance Co., Ltd.,  
Toronto, Licensee


Send complete details about the new IRC Selenium Dual Diodes.

NAME \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

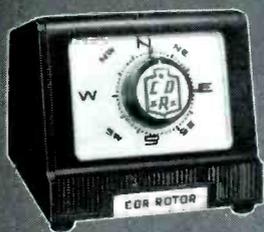

AR 1 and 2




AR-22



TR-2



TR-4

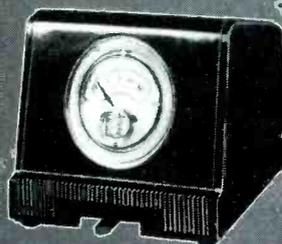

TR 11 and 12



CORNELL-DUBILIER  
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.  
CLEVELAND 13, OHIO

Everything You Need for Profitable Rotor Sales

# CDR ROTORS

## have EVERYTHING



### THE COMPLETE LINE

... a model for every need ... whatever the application there is a CDR Rotor that meets the situation best!

### PRE-SOLD FOR YOU!

The greatest coverage and concentration of full minute spot announcements on leading TV stations in every major rotor market is working for YOU...pre-selling your customers!

MF C	50+30 MF 150 WVDC	10+10 MF 300 WVDC	40/25 MF 250/25 WVDC	40+40 MF 150 WVDC	60/15 350/15
	<b>SPRAGUE</b>	<b>SPRAGUE</b>	<b>SPRAGUE</b>	<b>SPRAGUE</b>	<b>SPRAGUE</b>
	TWIST-LOK* LYTIC <b>TVL-2510</b> 10+10 MF 150 WVDC	TWIST-LOK* LYTIC <b>TVL-2575</b> 40+40 MF 300 WVDC	TWIST-LOK* LYTIC <b>TVL-2515</b> 20+20 MF 250 WVDC	TWIST-LOK* LYTIC <b>TVL-2570</b> 60+60 MF 300 WVDC	
	<b>SPRAGUE</b>	<b>SPRAGUE</b>	<b>SPRAGUE</b>	<b>SPRAGUE</b>	<b>SPRAGUE</b>
	TWIST-LOK* LYTIC <b>TVL-2438</b> 60+60 MF 150 WVDC	TWIST-LOK* LYTIC <b>TVL-2435</b> 50+50 MF 150 WVDC			
	<b>SPRAGUE</b>	<b>SPRAGUE</b>			
	TWIST-LOK* LYTIC <b>TVL-2430</b>	TWIST-LOK* LYTIC <b>TVL-2435</b>			

for the **RIGHT**  
'LYTIC replacement

...Use an exact  
**SPRAGUE** replacement



When you buy a Sprague Twist-Lok® electrolytic capacitor, you get the design preferred by the leading TV-Radio set makers, for Sprague makes far more twist-mount capacitors than any other source. Every Sprague TVL replacement electrolytic is made to original equipment specifications with the same know-how and production facilities that serve the discriminating set-makers. There is no guesswork in the design of Sprague Twist-Loks. Sprague has the original circuit requirements which must be designed for.

Every TVL for every voltage rating is made with the more expensive high-purity etched-foil anode construction using ultra-stable film formation techniques. Cathodes are etched to meet high ripple requirements. Sprague TVL's give maximum trouble-free service as well as long shelf life. They perform as well in auto sets in cold climates as they do in TV receivers in the sub-Tropics, and yet this premium quality costs you no more.

don't be vague...insist on

**SPRAGUE**®

*world's largest capacitor manufacturer*

**SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU**

Sprague Products Company • Distributors' Division of the Sprague Electric Company • North Adams, Massachusetts.



for the Electronic Service Industry

**PUBLISHER**  
Howard W. Sams

**GENERAL MANAGER**  
Mal Parks, Jr.

**EDITOR**  
Glen E. Slutz

**TECHNICAL EDITOR**  
Verne M. Ray

**ASSOCIATE EDITORS**  
Leslie D. Deane      Thomas A. Lesh  
Calvin C. Young, Jr.

**CONSULTING EDITORS**  
William E. Burke      C. P. Oliphant  
Robert B. Dunham      George B. Mann  
Paul C. Smith

**ART DIRECTOR**      **EDITORIAL ASSISTANT**  
Glenn R. Smith      Gwen Bigham

**PHOTOGRAPHY**      **PRODUCTION**  
Robert W. Reed      Douglas G. Bolt



**BUSINESS DEPARTMENT**

Joe H. Morin, Sales & Circulation Mgr.  
Billie Paul, Business Manager  
Pat Tidd, Circulation Dept.

**ADVERTISING SALES OFFICES**

Midwestern: PF REPORTER,  
2201 East 46th Street, Indianapolis 5, Ind.  
Clifford 1-4531

Eastern: Paul S. Weil and Donald C. Weil,  
39-01 Main Street, Flushing 54, New York.  
Independence 3-9098.

Western: The Maurice A. Kimball Co., Inc.,  
2550 Beverly Blvd., Los Angeles 57, Calif.  
Dunkirk 8-6178; and 681 Market Street,  
San Francisco 5, Calif. EXbrook 2-3365.

**PUBLICATION INFORMATION**

Published monthly by Howard W. Sams & Co., Inc., at Indianapolis 5, Indiana.

Entered as second class matter October 11, 1954, at the Post Office at Indianapolis, Indiana, under the Act of March 3, 1879.

Copyright 1956 by Howard W. Sams & Co., Inc. No part of the PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to the use of information contained herein.

A limited quantity of back issues are available at 35c per copy.

**CONTENTS**

**Letters to the Editor** ..... 6

**Shop Talk** ..... Milton S. Kiver 9  
Considerations and special test equipment for installing master antenna systems

**Dollar and Sense Servicing** ..... John Markus 11

**Quicker Servicing** ..... Calvin C. Young, Jr. 13  
Intermittent troubles in sync circuits; Connecting 300-ohm lead-in wire

**Servicing New Designs** ..... Thomas A. Lesh 14  
Admiral 14YP3B portable chassis— special features; disassembling and servicing

**Working with Soldering Guns** ..... 16  
A useful tool becomes even more useful

**TV Sound from the 6DT6** ..... Thomas A. Lesh 19  
Operating theory and alignment instructions on a new FM detector

**What's Cooking in Color TV** ..... Thomas A. Lesh and Verne M. Ray 21  
A field report on the sales and service picture in Chicago

**Printed Wiring Boards—Part V** ..... Calvin C. Young, Jr. 23  
Connecting test leads; Special test probes; Circuit tracing; Special applications

**Choosing a Scope** ..... Leslie D. Deane 25  
A thorough discussion of specifications to consider when buying a new scope

**Trouble Shooting with George** ..... Leslie D. Deane 38  
The case of mistaken identity

**Product Report** ..... 48

**Stock Guide for TV Tubes** ..... 50

**1956 Subject Reference Index** ..... 62  
Complete listings of this year's articles indexed by subject

**Supplement to SAMS Master Index** ..... 73

Please enter my subscription to PF REPORTER for:

1 Year \$3.00       2 Years \$5.00       3 Years \$7.00

In Canada: One Year \$3.60      Two Years \$6.20      Three Years \$8.80

Remittance Enclosed\*       Bill Me

USE CARD AT BACK OF ISSUE FOR SPECIAL CHRISTMAS GIFT SUBSCRIPTION OFFER

Name \_\_\_\_\_

Firm \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

\*Two extra issues free if remittance accompanies order.


01  Independent Serviceman      14  Part Time Serviceman

02  Dealer with Service Shop      37  Student

38  Other \_\_\_\_\_

Give to your Electronic Parts Distributor or mail, with remittance, to PF REPORTER, 2201 East 46th Street, Indianapolis 5, Indiana.
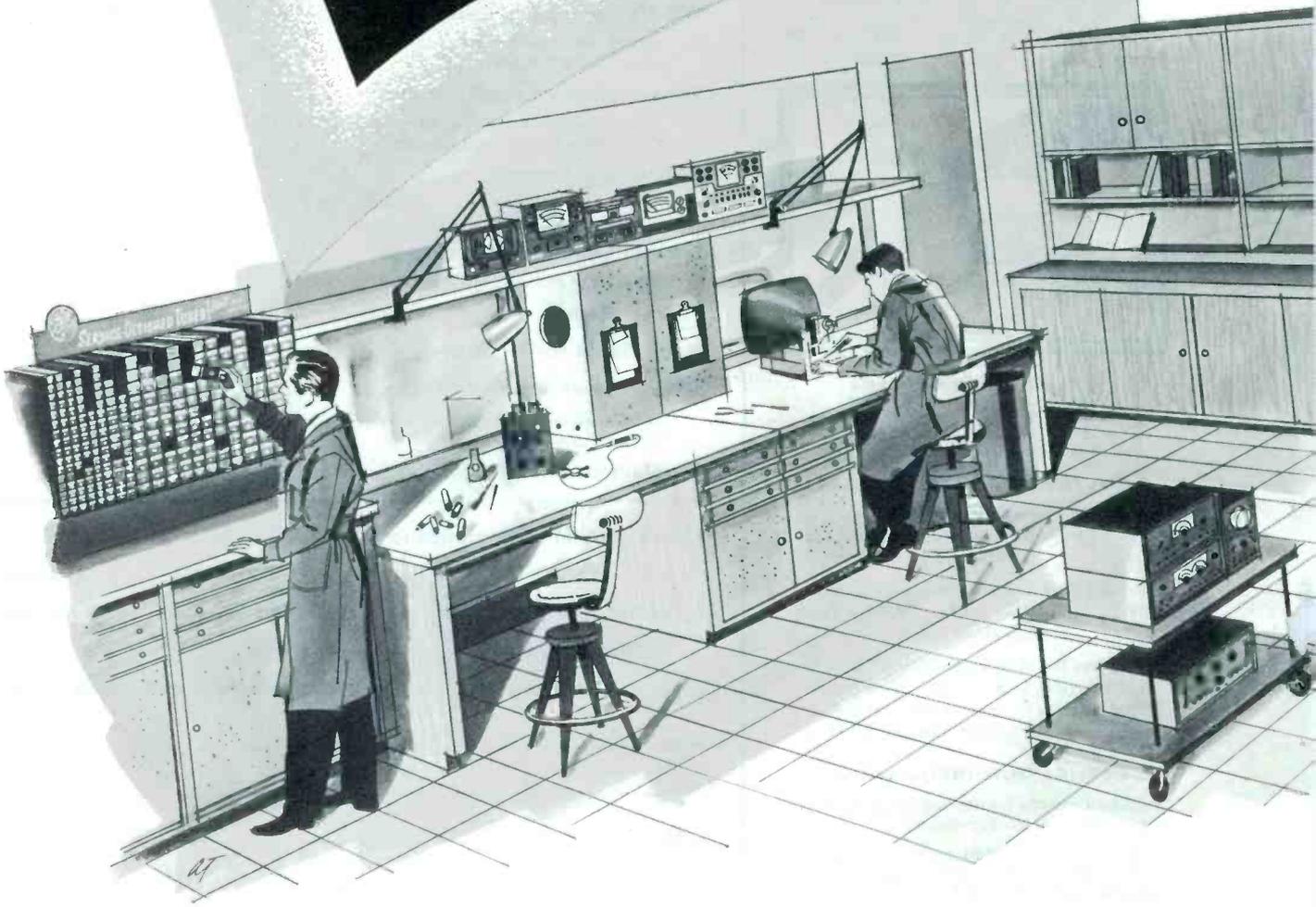
# *Now* .... FROM G.E. .... HELP YOU MODERNIZE



# NEW SHOP PLANS THAT FOR BUSINESS GROWTH!

**T**ODAY the servicing of TV receivers, plus tubes and parts needed, adds up to more dollars than TV-set sales. In order for you to obtain your share of this fast-growing volume, General Electric has prepared new shop plans that help you handle more service business...more efficiently, more economically.

Giles van der Bogert, American Institute of Architects, drew on the experience of TV-service experts for General Electric's shop layout. It is planned for an average-size service dealer, yet can

easily be expanded or reduced to meet varying requirements. The plan can be used as a whole, or individual parts adapted to your needs.

Efficient work-flow...well-planned bench and counter areas...adequate space for set storage...these and other advantages will improve your servicing facilities, add to your profit opportunities. Study the features below! Then phone your G-E distributor for the complete plans! *Electronic Components Division, General Electric Co., Schenectady 5, N.Y.*

\* Layout provides complete facilities for two bench technicians, but can be expanded to accommodate up to ten.

\* Modular, or unit-by-unit design, permits wide flexibility in adapting plan to your individual needs. Also, you can start with any part of the layout, and complete the plan by easy stages.

\* Complete dimension drawings and material lists are supplied. Any carpenter or builder can start the job for you immediately upon your request.


\* Service-bench area includes many new time-and-work-saving features. A TV-test and storage rack with ample dimensions has compartments for portables up to large-size color receivers. There are custom-designed cabinets for technical manuals and service records.

\* Plan calls for standard-dimension lumber and other easily obtained construction materials, so that cost to you will be as low as possible.

\* Layout includes separate display and sales area for over-the-counter transactions. Floor and window displays can be accommodated effectively.

\* There is an enclosed manager's office, which also can be used for TV, radio, and hi-fi demonstration. Coat closet and lavatory room are provided.

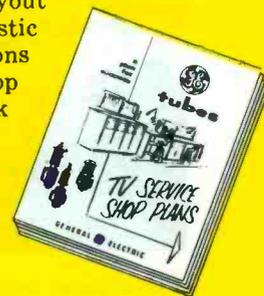\* The complete shop-layout book you receive has realistic three-dimension illustrations to show how your new shop and store will look. Ask your G-E tube distributor for your copy!



*Progress Is Our Most Important Product*

**GENERAL  ELECTRIC**

161-1A5

# "SURE, I use **CLEAR BEAM** **Antenna Kits**...they've doubled my installation business!"

Using Clear Beam Antenna Kits makes sense right from the start! Attractive packaging and do-it-yourself label creates customer interest in a new or replacement antenna—makes it a cinch to sell complete installations.

Servicemen installing Clear Beam Antenna Kits have eliminated "loose stock" inventory problems and are now able to price installation jobs accurately and profitably due to fixed material costs!

Start doubling your installation business with Clear Beam Antenna Kits now. Display them in your shop—show them from your service truck—let Clear Beam's self-selling antenna kits clinch extra installation sales for you!




Kits for Conicals, Arrows, Yagis, Dipoles, UHF, VHF  
complete with mast, lead-in and all necessary hardware ready to install!



**CLEAR ANTENNA CORP.,**  
**BEAM** CANOGA PARK, CALIF.

Warehouses in Seattle, Portland, San Francisco, Honolulu, Dallas, Kansas City, Detroit, Baltimore

Letters  
to the  
Editor

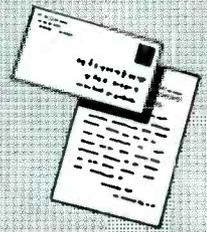

Dear Editor:

I would appreciate your help in figuring out the solution to an unusual trouble I have encountered in servicing a Truetone television receiver of the 2D2301A series.

The trouble is that the lower half of the picture has a flutter or jitter. When the set is first turned on, it doesn't act up, but after five or ten minutes of operation, the trouble appears. The upper half of the picture may have a very slight jitter but not enough to amount to anything. I have tried changing the cathode capacitor in the vertical output circuit, but no luck. The thing that stumps me is that only the lower half seems to be acting up—if the whole picture were affected, I would have something to go on.

RALPH BAUGHMAN

Akron, Ohio

We recommend that the grid waveform W8 (Photofact Set 229—Folder 17) in the vertical output stage be checked for size, shape and stability. If this waveform is satisfactory, the trouble is very probably in the vertical output stage, and a check of waveform W9 at the secondary of the vertical output transformer should be made for any unusual condition. The presence of a spurious oscillation or ringing in W9 would indicate poor filtering of the boost B+ to the vertical output stage or trouble in the yoke or output transformer. Capacitors C49 and C50 could also be defective. Incidentally, the values of R89 and R90 in this schematic should be 560 ohms, not 560K ohms.

If waveform W8 is not satisfactory, then a check of the components associated with the oscillator stage including T2, C48, C47 and R68 should reveal the trouble. It would also be a good idea to check the vertical sync signal for the presence of video information or an unwanted horizontal pulse.

Questions on special problems, such as this one sent in by Mr. Baughman, are worthy contributions to this column.—Editor

Dear Editor:

PF REPORTER is a wonderful buy for anyone learning servicing or anyone in the trade. It's strictly a serviceman's magazine.

How about a few ideas on how to circuit trace these printed-board TV sets? I had an Admiral in the shop . . . and, boy, I had some problems. Some parts on one side, some on the other—at times I was almost on my head trying to follow one point to another.

I have been taking the RCA color TV correspondence course and have found that I can answer quite a few questions at a glance. I know it's the information I already had from PF REPORTER coming back to mind.

I read in our local newspaper that one manufacturer is starting production soon on the flat wall-mounted picture tube. I haven't heard a word about it in any of the service magazines I've read. That's information we could use.

Thanks for a swell informative magazine.

ANDREW J. OLSEN

Cut Off, La.

*Printed wiring boards and the servicing of them have been covered in a series of articles. Part 5 of which appears in this issue. Reader Olsen's other fine suggestions have been added to our editorial planning chart.—Editor*

Dear Editor:

I have studied your magazine for 18 months and have learned much from each issue. One of the best articles by far, in my humble opinion, is Mr. Dines' article "Operation of Damper Circuits" in your August, 1956 issue. After reading this article, even I fathomed the operation of the damper and its associated circuits better than ever before.

I have talked to many TV techs and find they too have the greatest difficulty pinpointing a definite faulty component in the high-voltage, flyback, yoke and damper circuits. It is therefore requested that you do an article in the very near future on the over-all trouble shooting of the above-named circuits, with a point-by-point procedure to follow to locate and pinpoint faulty components in these circuits.

O. E. TAYLOR

Dallas, Texas

*Excellent suggestions like this one from reader Taylor are certainly welcomed by us. We're adding this idea to our future editorial planning chart.—Editor*

December, 1956 • PF REPORTER

Save servicing time with

# Authoritative Technical Publications on RCA VICTOR RADIO, PHONO and TV sets

Directories, Guides, and Service Data Books published by RCA—these are the basic RCA reference works for a technical library you'll depend upon now and in years to come. In these publications you'll find exact replacement parts lists for all RCA Victor home instruments, servicing and alignment instructions, and circuit diagrams—all detailed, *factory-originated data*—much of which cannot be obtained elsewhere.

## BOUND VOLUMES OF RCA VICTOR SERVICE DATA

You'll save time and dollars by maintaining a complete file of these handsome, sturdily bound volumes. Here's authoritative data for rapid, profitable servicing of RCA Victor home instruments. Included are schematic diagrams, wiring diagrams, alignment procedures, waveforms, troubleshooting suggestions, production changes, complete parts lists, top and bottom chassis views, voltage charts, and shop tips. Vol. I (1923-1937) \$3.50; Vol. IV (1947-1948) \$6.00; Vol. V (1949) \$5.00; Vol. VI (1950) \$5.50; Vol. VII (1951) \$5.00; Vol. VIII (1952) \$5.00.



## SERVICE PARTS DIRECTORIES FOR RCA VICTOR TV RECEIVERS



These publications contain schematic diagrams, top and bottom chassis views (except as noted), replacement parts lists, a cross reference index between model name and model number, and an index to previous publications.

**SP-1007**—1946 through June 1950 TV receivers (56 models). Does not include chassis views. 75 cents a copy.

**SP-1014**—1950 through 1951 TV receivers (71 models). \$1.50 a copy.

**SP-1021**—1952 TV receivers (27 models). 50 cents a copy.

**SP-1028**—1953 TV receivers (108 models). Includes Radio-TV combinations. \$1.35 a copy.

**SP-1035**—1954 TV receivers (106 models). Includes information on the CT-100 and 21-CT55 color TV receivers and the RP-197 and RP-198 3-speed record-changers. \$1.25 per copy.

## RCA VICTOR TV SERVICE PARTS & TUNER PARTS GUIDE

**SP-2001B**—Available in December, lists stock numbers of major replacement parts for RCA Victor TV sets by receiver-model number and corresponding receiver-chassis number. Also listed are stock numbers of tuner-replacement parts for individual tuner-chassis. Covers the years 1946 through 1956. 25 cents per copy.

## RCA PHONOGRAPH CARTRIDGE GUIDE

**SP-2003B**—Lists stock numbers of RCA cartridges and styli. Also lists stock numbers of RCA cartridges and RCA Victor model numbers of record-changers in which they are used. Single copy free on request.



RCA TECHNICAL PUBLICATIONS ON RCA SERVICE PARTS ARE AVAILABLE THROUGH YOUR RCA TUBE DISTRIBUTOR—OR FROM RCA, COMMERCIAL ENGINEERING, 415 S. 5TH ST., HARRISON, N. J.



# SERVICE PARTS

RADIO CORPORATION OF AMERICA, HARRISON, N. J.

# another Raytheon

# FIRST



**100% INTERCHANGEABLE TV TUBES  
THAT ELIMINATE SNIVETS\***



## 6DQ6 12DQ6 17DQ6



Thanks to an exclusive new Raytheon fin design, the Raytheon 6DQ6 is the first TV tube which eliminates SNIVETS that is 100% interchangeable — will work without special selection. It eliminates borderline performance, too, because its new design gives it additional and improved sweep characteristics not available in ordinary types.

Raytheon 6DQ6 tubes provide SNIVET free performance because they are individually tested for deflection operation and are given special tests under sweep amplifier conditions. Raytheon 12DQ6 and 17DQ6 Tubes incorporate this same fin construction and will provide the same superior, trouble-free performance.

An added bonus from the Raytheon 6DQ6 is that its interchangeability simplifies stocking. (It's an improved replacement for 6CU6 and 6BQ6GA series.)

Finally, the Raytheon 6DQ6 is another outstanding example of how Raytheon's superior engineering skill and production know-how have brought you still another tube that is first and finest in the field.

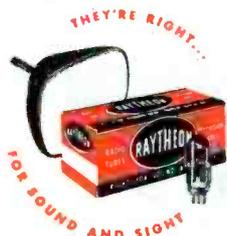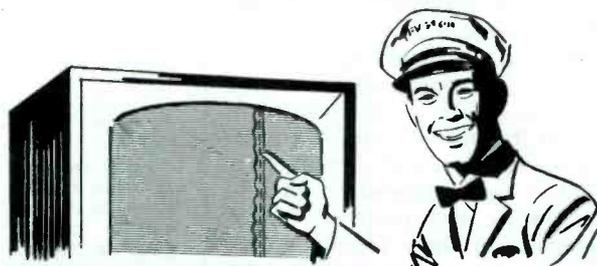\* SNIVET — a vertical disturbance on the right hand area of the screen.



### RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



Excellence in Electronics

# ShopTalk

**MILTON S. KIVER**

Author of . . .  
*How to Understand and Use TV Test Instruments  
 and Analyzing and Tracing TV Circuits*



Photo courtesy of Jerrold Electronics Corp.

Installer connecting a receiver to signal outlet in apartment wall.

## Installing Master Antenna Systems

In last month's column, we outlined the various components that form a master antenna system. We started at the antenna, where the signal is initially captured, and followed the signal down through the system to the tenant's receiver. Basically, a master antenna system is an uncomplicated signal amplification and distribution network. But practically, there are a number of considerations that must be carefully evaluated; otherwise the entire system can bog down and either fail to operate at all, or else function so inefficiently that the initial investment or the subsequent upkeep and modifications will make the operation economically unsound.

From an economic standpoint, the way a system can be installed with the least investment on your part is to install it for someone who is purchasing it outright and paying you for the cost of the component sections plus your time spent in installing it. In addition, you may subsequently be called upon to service it, should trouble develop. However, while you run the least economic risk with this mode of operation, you also stand to make less money. For when you own the system, you have the right to charge each tenant an installation fee (for bringing the line into his apartment), plus a yearly service fee for its maintenance. This is a continuing arrangement that applies for as long as the system remains in that building. Average fees for bringing the signal line into an apartment run \$20-\$25 while the

yearly service fee ranges between \$15 and \$18. (These are figures common in such cities as Chicago and New York.)

It is important to weigh the pros and cons of both methods, so that whichever approach you choose, you know exactly what you're doing. Since master antenna systems—even simple ones—can soon represent a considerable outlay of money, you have to make very certain that you are not only capable of installing them, but also of servicing them over a long period of time.

## Provisions for Future Changes

Another consideration in installing master antenna systems is to make certain that each is flexible enough to handle any future demands that may be made upon it. It is not unusual, when a system is first installed, to find that not all the tenants in the building make use of its facilities. However, it is entirely possible that at some future date, all sets in the building will have to be tied into the distribution lines. Consequently, the system should be flexible enough to handle these additional loads.

Also to be considered is the possibility of future additional transmitting stations in the area. When these come, either on VHF or UHF, will the system be able to cope with them? Or will a complete overhauling be necessary? Remember that if you own the system, you may be called upon to make the change without any further charge to the tenants. If an extensive alteration is required, the cost to you may be so great

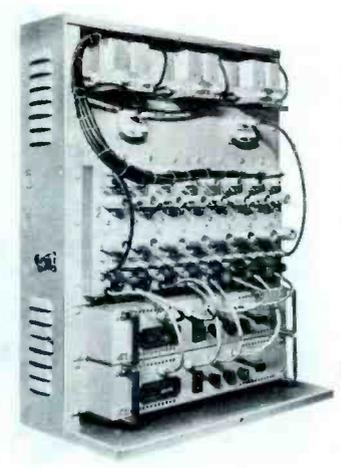


Photo courtesy of Jerrold Electronics Corp.

A typical signal amplifier set-up. 8 channel strips are mounted in the center of the unit with suitable power supplies positioned just below.

that it will wipe out your profit from that source for one or more years. Can you stand such a loss?

Incidentally, whether or not a new station in your area is a possibility can readily be determined from the Federal Communications Commission. They have published a list which shows the maximum number of stations allowed in your area and the assigned channels. If all of these frequencies are not now occupied, it is safe to assume that at some future date they will be. Hence, the system should be so set up that additional signals can be fed to it when the occasion arises.

In the case of UHF stations, the most common procedure is to convert the signal down to an unused VHF channel. This is done as soon as possible after the sig-

• Please turn to page 70


# PROTECT YOUR REPUTATION!

Cut price TV tuners are surplus from a *special* run of a *special design* for one particular model of one particular manufacturer. Chances are overwhelmingly against your ever being able to use a surplus tuner properly—in the set for which it was designed. PROTECT YOUR REPUTATION—don't force match a "bargain" tuner to your customer's set—use only STANDARD APPROVED REPLACEMENT TUNERS (which are furnished you complete with schematic). These will cover over 90% of your service replacement needs. Designed exclusively for service by the manufacturer of more than 19,000,000 TV tuners in use today.
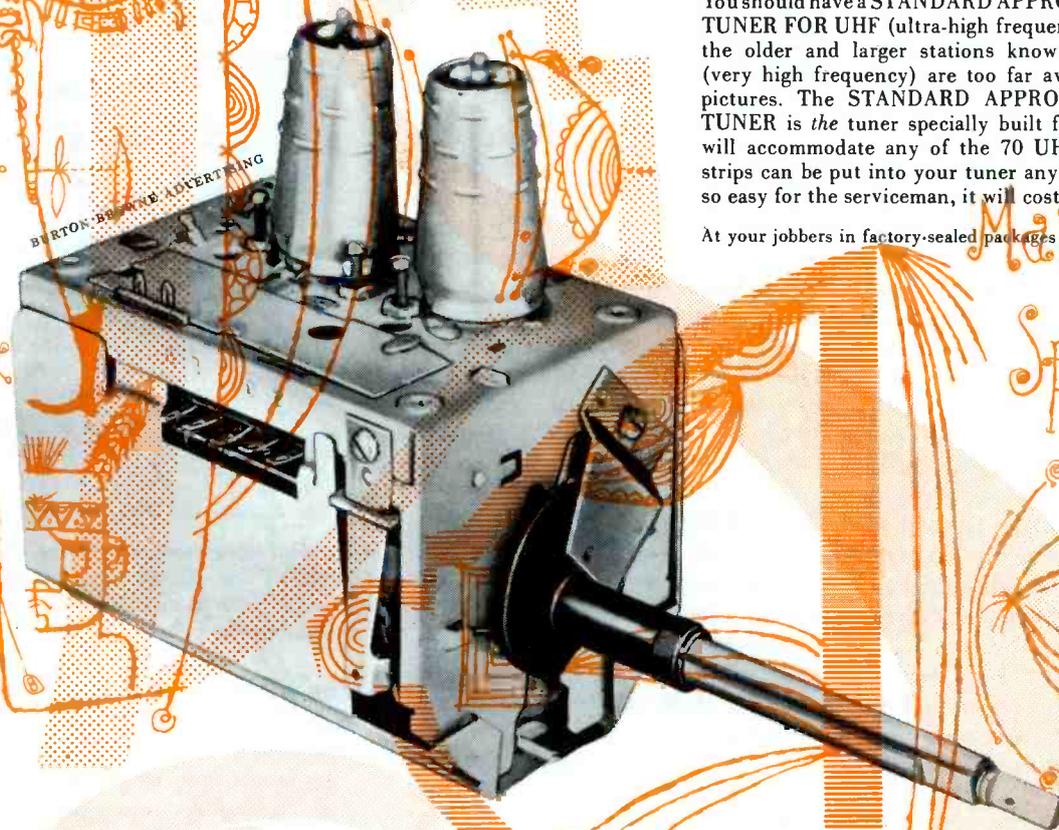
## Tell The Customer . . . .

“ You should have a STANDARD APPROVED REPLACEMENT TUNER FOR UHF (ultra-high frequency) STATIONS. Often the older and larger stations known as VHF STATIONS (very high frequency) are too far away to give top quality pictures. The STANDARD APPROVED REPLACEMENT TUNER is the tuner specially built for UHF conversion. It will accommodate any of the 70 UHF TV Channels! UHF strips can be put into your tuner any time, and because it is so easy for the serviceman, it will cost less in service charges.”

At your jobbers in factory-sealed packages only.



Master  
Specialists  
in  
Tuned Circuits

*Standard* COIL PRODUCTS CO., INC.

CHICAGO—LOS ANGELES—BANGOR, MICH.—NO. DIGHTON, MASS.

Export Agent: Scheel International, Inc., Chicago

ORIGINATORS of the Turret Style Tuner

ORIGINATORS of the Standard Cascode Tuner

ORIGINATORS of the Standard Pentode Tuner

ORIGINATORS of the New Neutrode Tuner

Master Specialists in Tuned Circuits

World's Largest Manufacturer of Electronic Components

**TEMPTATION.** Even factories are having trouble with pilferage of small transistor radios. In one plant six of these sets were stolen right from the production line within half an hour—making it necessary to station a plant policeman along the line just to keep an eye on the merchandise.

Still smaller are Philco's new Audipage units for silent paging and a host of other uses. The output of the audio amplifier is fed to a wire encircling a room or entire building. Anyone within this loop can pick up the messages or music with the playing-card-size transistor unit which has its own batteries and ferrite-rod antenna. The only exterior connection is a tiny wire running up to the ear plug. Although intended primarily for industrial use, there are interesting potentialities here for radio listening in homes where ordinary radios running full blast annoy neighbors. Just run a wire around the house under the eaves and hook it up to the output transformer of a radio for silent listening with the transistor unit in any room of the house, even over the noise of a vacuum cleaner.

### \$ and ¢

**TAXES.** If your hobby can be considered a business because it increases your income, you can deduct from hobby income whatever expenses you have had in earning that income. If hobby expenses exceed hobby income, hobby losses can be used as deductions against income from your regular servicing business.

From an income tax standpoint, much hairsplitting is involved in determining legally when a hobby becomes a business. If you think you have a good case, tax accountants generally urge that you try taking these hobby expense deductions; the most you have to lose is the interest on the deductions that are not allowed, and this is insignificant in comparison to what you save if the deduction is allowed. The services and advice of a tax accountant may pay off many times over.

Here are some rough tests to determine if your hobby is a business. Do you spend a substantial amount of time on it to try to make a profit? Do you publicize the fact that you are in such a business? Can you prove that your intent is to make money on your hobby? If your answer is yes to all three, take the deductions, and worry about battling it out with Treasury only if they question the return.



**BY JOHN MARKUS**

*Editor-in-Chief, McGraw-Hill Radio Servicing Library*

Even hunting dogs can be a tax deduction if you go about it right. First investigate thoroughly the profit-making possibilities in the field of breeding hunting dogs. Keep bills of sale and cancelled checks for all books you buy on the subject, for breeding stock, for kennel construction materials and labor, for "HOUNDS FOR SALE" signs and ads and all other expenses. Don't forget travel expense for training the dogs in the field while you are hunting. On Schedule C of your Federal Income Tax Return, take all of these deductions. Since a portion of your home will be devoted to your hobby for profit, deduct this portion of the rent, heat, electric, water, repair and maintenance bills, and depreciate furniture and equipment used. It is wise to allocate one or two rooms in the house for your hobby business and install in these rooms the files, shelves, desk and other equipment you might need for your hobby-business planning, reading and writing.

If you come up with a profit after making all these deductions, you will owe the government additional taxes on your hobby. If your sideline ends up in the red, you can use this loss to offset regular income and perhaps even get a tax refund. There is one limitation on hobbies for business, however—the maximum loss that you can deduct over a five-year period cannot average more than \$50,000 per year.

### \$ and ¢

**COLOR NOTES.** Chief worry of color receiver prospects is failure of the color picture tube. On a per-call servicing basis, this will run well over a hundred dollars unless subsidized somehow, because manufacturers themselves are still paying upwards of \$75.00 for these tubes in quantities of thousands at a time.

One solution that would help servicemen as well as set owners would be for manufacturers to offer

a five-year insurance policy, guarantee or similar contract on the color picture tube alone. With this worry eliminated beforehand, more people would be willing to pay for their color servicing on a per-call basis just as they do today for black-and-white TV. Which manufacturer will be the first to come up with a working solution to this problem?


### \$ and ¢

**CONTROL.** "In some homes the only switch used to control the children is the one on the TV set." Thus does the *Saturday Evening Post* express in one perfect sentence the exact situation existing in our own home and probably in many others.
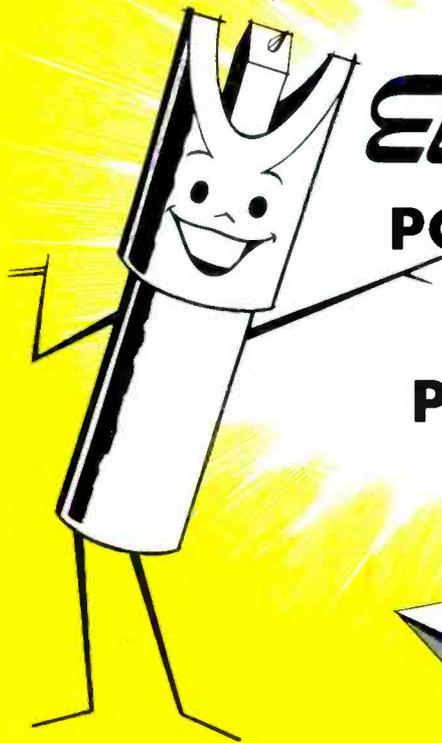
### \$ and ¢


**ELECTRONIC RANGES.** With Raytheon, Kelvinator, Hotpoint, etc. already offering electronic ranges, the problem of servicing this type of equipment may soon become of personal interest and profit to you. With alignment and test procedures very much like those required for television sets, these ranges are definitely unwelcome to the average appliance serviceman.

A typical Kelvinator range uses a QK390 magnetron, four 866A rectifiers and a full-wave selenium rectifier, along with an assortment of relays, transformers, resistors, timers, fuses and other components. With the simple magnetron circuit clearly in mind and with the manufacturer's service instructions, you should have no trouble in handling these jobs. Be sure to work in collaboration with the manufacturer, however. Because of the danger involved in working near terminals rated for 4,800 volts DC at 1/3 amp (pretty close to electric chair ratings), seals are placed on the back panel. In service instructions, Kelvinator gives this warning: "Death is final. Unauthorized service will void all guarantees."



# Electro-Voice

## POWER-POINTS THE WAY TO PLUS-PROFITS!

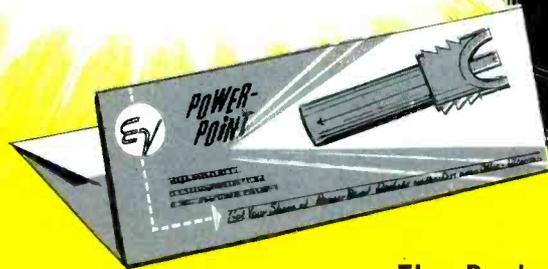

### Here's Power-Point Pete's CASH BOX

### —A NEW and Profitable Promotion

**The Package Deal With Extra Profit Built Right in!** Power-Point Pete's CASH BOX is a self-contained point-of-purchase package containing two each of three Power-Point models and two each of three Power-Point mounts. You get the whole package, plus direct-mail merchandisers in color, at a merchandising price. **THERE'S NO CHARGE AT ALL** for some items! You get extra profits and you pass on an extra profit margin to your dealers, too!



#### Electro-Voice Ads Hit Your Major Markets!

Electro-Voice ads this month in **RECORD & SOUND RETAILING** and **THE BILLBOARD** pre-sell your prime customers—record dealers! Eight thousand record dealers account for 85% of total phono and record sales. These are the people who can sell Power-Points in volume. They're the big-order customers you want. Go get 'em with—Electro-Voice direct mail pieces and these hard-sell ads! See them! Sell them! Profit along with them!



**POWER-POINT**—the Electro-Voice phonograph needle-and-cartridge combination—is taking the market by storm! The fact that over a million Power-Points are in use now as original equipment means *guaranteed* replacement sales for you! *Production has tripled!* Power-Point is a natural for customers, a profit builder for dealers, and very profitable for **YOU!**



**Electro-Voice Follow-Through Merchandising** helps you move merchandise! You'll remember the first Power-Point promotion—the phonograph records, slide film, wall racks, wall and window banners, the colorful envelope stuffers, the 4-page, color folder that tells the Power-Point story. Have you used these sales tools? They will help you sell more merchandise to more merchants!


# Electro-Voice

ELECTRO-VOICE, INC.

BUCHANAN, MICHIGAN

Canada: E-V of Canada Ltd., 1908 Avenue Road,  
Toronto, Ontario  
Export: 13 East 40th Street, New York 16, U. S. A.  
Cables: ARLAB

# Quicker Servicing




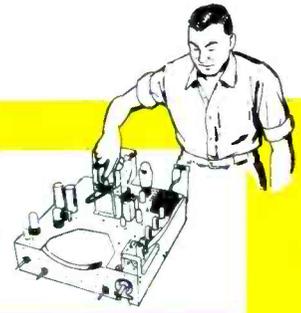


by Calvin C. Young, Jr.
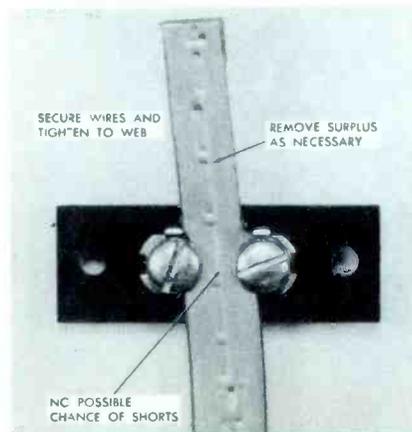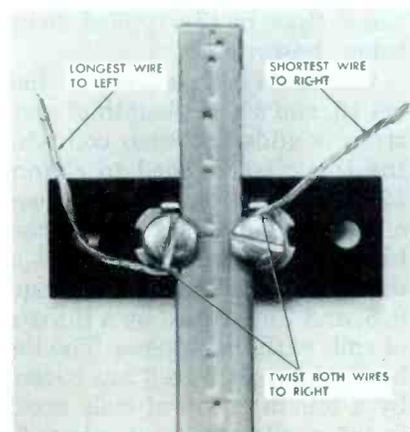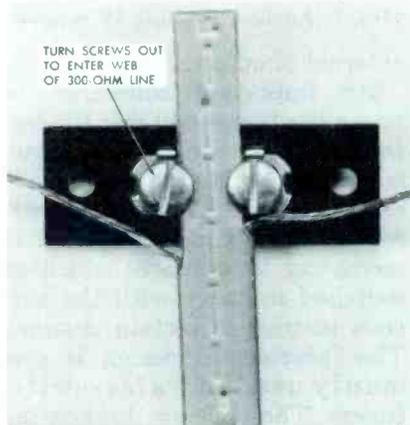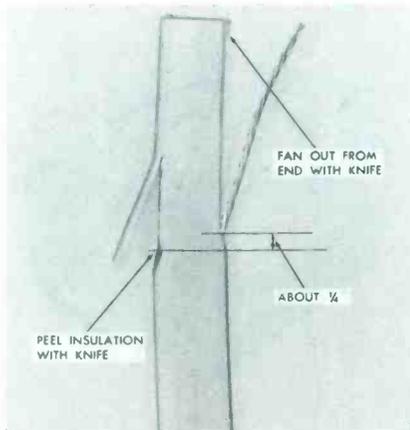
## Method for Attaching 300-Ohm Lines to Terminals

Securing the antenna lead-in wires to a terminal block is a job that is encountered by every technician in his daily work. It is desirable to secure the antenna lead-in wire in such a manner that shorts between the wires cannot occur. If the wires are merely wrapped around the screws, there is a danger that the housewife, in cleaning around the set from time to time, will flex and move the lead-in and thus cause fine strands of wire to break. A poor connection or a short across the antenna terminals can thus result.

The sequence of pictures shown here illustrates a method of connecting lead-in wires so that good mechanical support is provided and shorts between the wires are unlikely. This helpful suggestion was submitted by Mr. J. R. Stanton of Scranton, Pa.



## Intermittents—the Curse of TV Technicians

Just when everything seems to really be going along fine, a bad case of intermittent operation will pop up to cast the proverbial monkey wrench into the works. To say the least, an intermittent trouble of any description is difficult to deal with and is a most unwelcome visitor at any time.

Three types of intermittent conditions consistently arise in television servicing. These are intermittent picture, intermittent sync and intermittent sweep. Of these, intermittent sync is probably the most troublesome because it can originate in more stages of the receiver.

To help the television technician combat intermittents in the sync section, the following discussion will present several recent cases of intermittent sync encountered by the author.

### "S"-Pattern Distortion

In the first case, a severe case of "S" distortion developed in the picture after about an hour of operation in the cabinet. This distortion was so severe that it had many of the characteristics of "Christmas-tree" effect. The horizontal oscillator coil even emitted an audible whistle. When the receiver chassis was removed from the cabinet and placed on the bench, the trouble disappeared. Heat directed from a 60-watt bulb in the trouble lamp onto the horizontal oscillator and AFC circuit components did not cause the trouble to appear.

To save time, the operation of the receiver was carefully checked and several troubles were located, two of which were in the hori-

• Please turn to page 67

### Admiral Portable TV

A new entry in the "personal" portable television field is the Admiral set shown in Fig. 1. Admiral's choice among the several sizes of small 90° picture tubes that have recently been made available is the 10ABP4 tube, having a 10 $\frac{3}{8}$ " diagonal measurement. This tube is teamed with the 14YP3B chassis which contains 13 receiving tubes, 3 semiconductor diodes and a pair of selenium rectifiers. An almost identical chassis is employed in a larger 14"

portable TV set being made by the same manufacturer.

#### Disc Tuner

One of the most interesting features of the Admiral portable TV chassis is a unique disc tuner (Fig. 2) which combines certain construction principles of both turret and switch type tuners, and is mounted so that the control shaft protrudes from the top of the receiver cabinet. Attached to the shaft inside the tuner are two large discs upon which the tuning

inductors are arranged—antenna coils on the lower disc and RF and oscillator coils on the upper one. A detent mechanism resembling that of a turret tuner is mounted on the lower disc.

To get a rough idea of the layout of each disc, imagine that the strips of a turret tuner are arranged in a radial pattern like spokes of a wheel and then joined together. Contact buttons and fingers, much like those of a turret tuner, are used to make connections between the discs and the

# servicing new designs

by Thomas A. Lesh

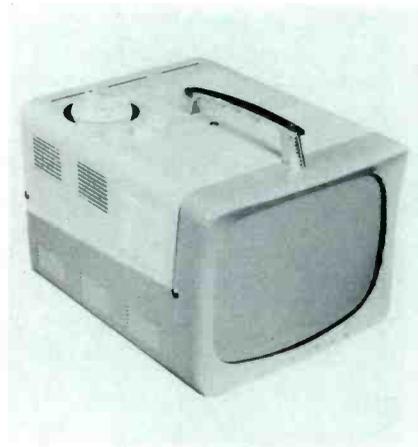


Fig. 1. Admiral portable TV receiver.

external circuitry.

An important difference between the turret and disc tuners is that the latter does not have a completely separate set of coils for each channel. There are several sets of basic coils plus small incremental inductances which are switched in series with the basic coils to tune in certain channels. The incremental design is commonly used in wafer-switch tuners. The coils are broken into more separate groups in the disc tuner than in the typical switch tuner, however.

One set of coils is used on channel 13, and a short length of metal strap is added to each coil when the tuner is switched to channel 12. A second group of coils is used alone on channel 11 and in combination with an incremental inductance on channel 10. Channels 9, 8, and 7 are tuned by a third set of coils with increments. The low-band channels 2 to 6 are covered by a fourth group of coils except in the oscillator circuit, where the coils for channels 2 to 4 are sep-

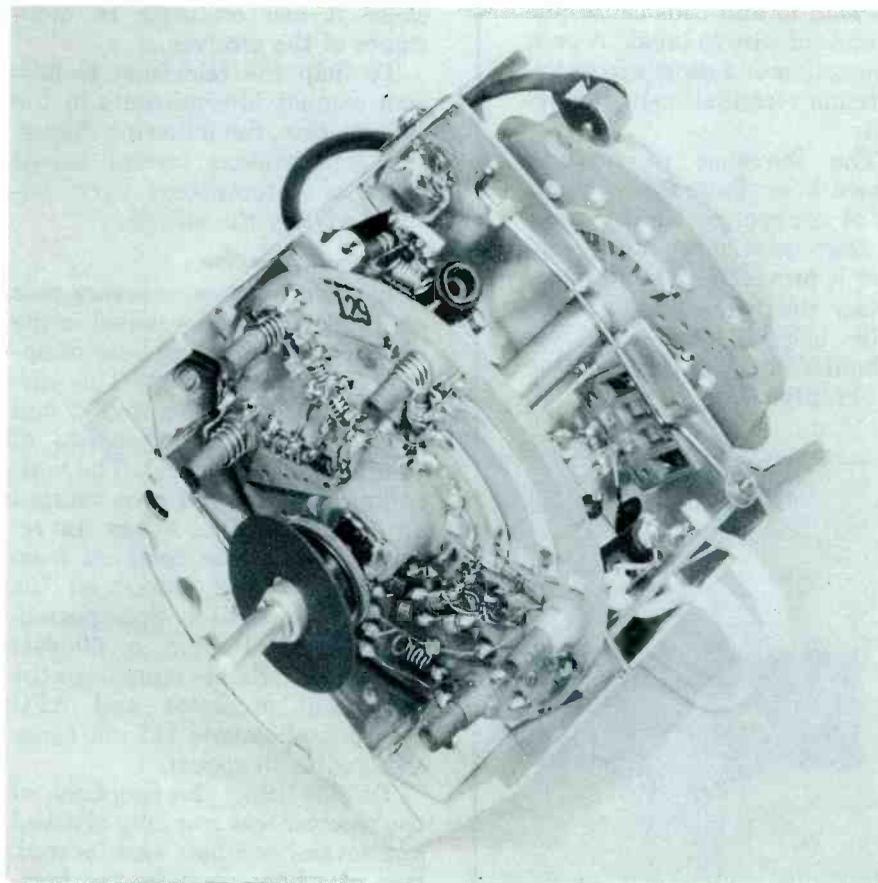


Fig. 2. Disc tuner used in the Admiral portable.

arate from those for channels 5 and 6.

Five oscillator-adjustment slugs correspond to the five groups of oscillator coils, and these slugs can be adjusted while the chassis is in its cabinet. There are three holes in the control panel so that the appropriate slug will always be accessible regardless of the channel setting. On high channels, two slugs may be visible; in this case, the slug nearer the rear of the receiver should be adjusted. The technician should first adjust the

slug on the lowest active channel and should then make the other adjustments in ascending order to the highest channel.

The contact buttons on the upper disc form six concentric circles. The innermost two of these are connected to the plate coils for the 3BC5 RF amplifier, the middle two are for the 5J6 mixer input circuit and the outer two are connected to the oscillator coils. A 1.5-mmfd capacitor connects the low-band RF coils to the corresponding mixer coils.

The fine-tuning capacitor is located just outside the cover of the tuner at the top end (foreground in Fig. 2). The movable plate is a strip of metal attached to the tuning shaft, and the fixed plate is printed on a small wiring board.

#### Other Features


The Admiral portable set has a local-distant switch that acts upon the signal before it ever enters the receiver. In the DISTANT position, used normally, the switch has no effect, but if signal strength is excessive, the switch may be changed to LOCAL, placing an attenuator pad in series with the antenna lead to the tuner. This pad consists of two 330-ohm series resistors and a 470-ohm shunt resistor.

Two 3CB6 pentodes are used as IF amplifiers, and the video detector is a 1N295 crystal diode. The sound IF signal is taken from the detector and fed to a 3-stage audio section including the new 6DT6 locked-oscillator detector. A 12CU5 output tube drives a 3" speaker, and the pentode section of a 6U8 is used as a sound IF stage. The video amplifier is the pentode section of a 6BA8A. The triode sections of the latter two tubes are utilized as sync stages.


The sweep tubes include a 6CM7 vertical multivibrator and output stage, a 6CG7 horizontal multivibrator, a 12DQ6 horizontal-output tube, a 1X2B high-voltage rectifier, and a 12AX4GTA damper. Twin selenium diodes are used in the horizontal AFC stage—a practice, by the way, which is becoming widespread. Selenium rectifiers are used in a voltage-doubler circuit which provides a B+ supply of 260 volts. Anode potential of the picture tube is 9kv.
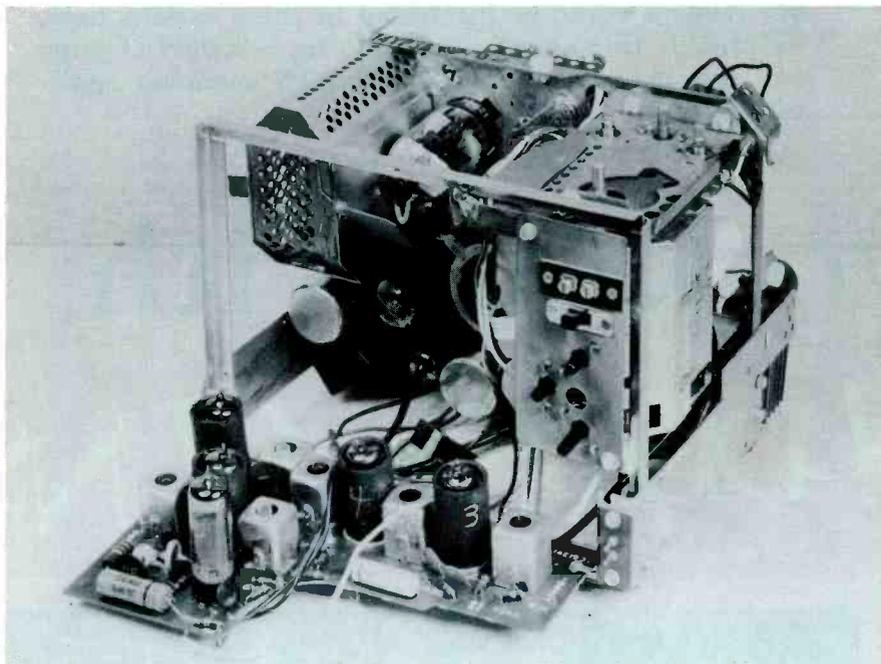
#### Disassembly

In an effort to make components reasonably accessible while producing extremely compact receivers to satisfy public demand, manufacturers have come up with some highly unorthodox chassis layouts in portable TV sets. Disassembling one of these receivers can be time-consuming if the



(A) From rear.

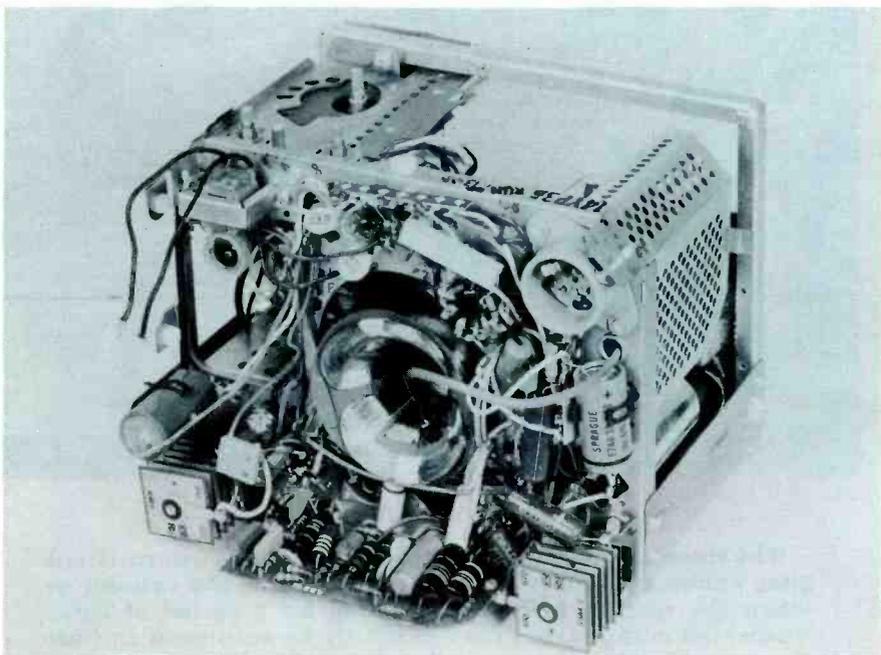

(B) From front.

Fig. 3. Views of Admiral portable TV chassis.


• Please turn to page 65



The soldering gun is a tool designed to take the place of an iron in applications where instant heat is desirable. While servicing in the home for example, the TV technician may find that a soldering job will sometimes complete a repair. Much time could be wasted as he waits for an iron to heat—even more as he waits for the iron to cool so it can be put away. For this reason, many technicians consider a soldering gun a necessary part of their everyday servicing equipment.



Although the prime use of a soldering gun is for soldering operations, many other ways of utilizing this product have been developed by technicians and by gun manufacturers. Today there are several makes and models available, each designed to use a variety of tips which modify the gun for specific duties. Feeling that our readers would be interested in these various uses, we present this photo story showing a variety of guns and tips being used in radio and TV servicing applications.

# working with SOLDERING GUNS

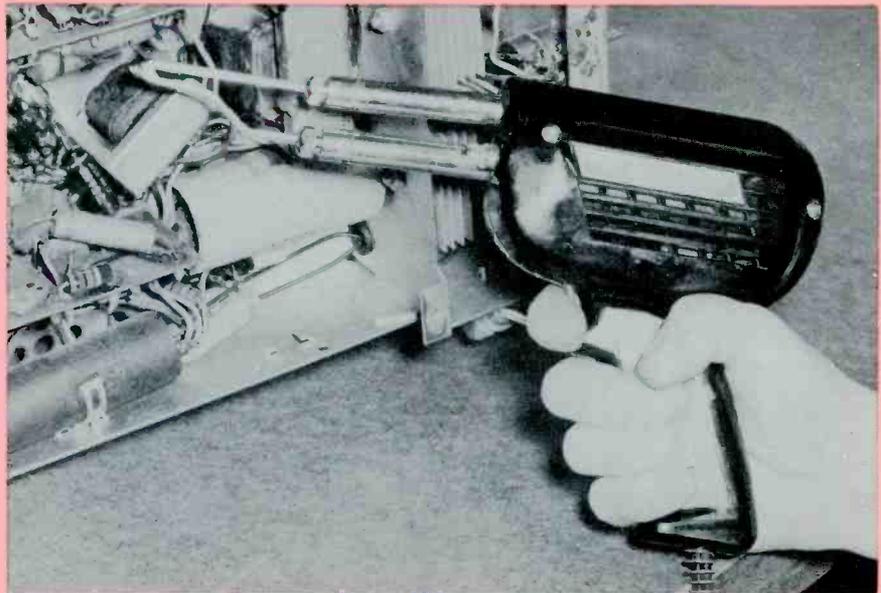
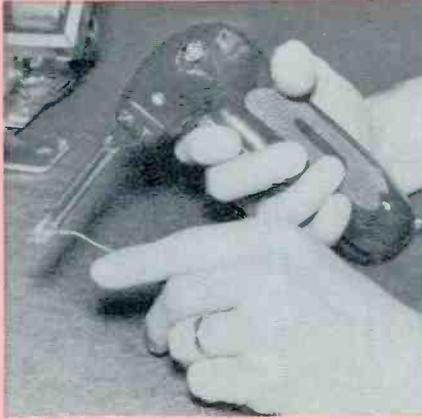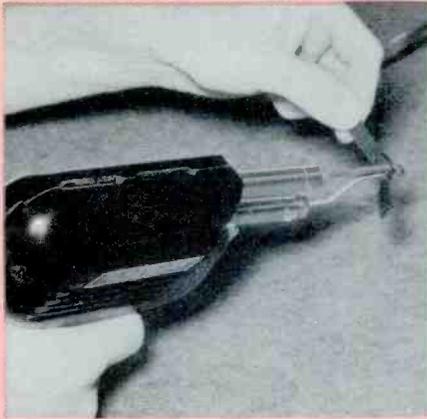
## THERMAL INTERMITTENTS

The most exasperating type of trouble is the intermittent that shows up only when the chassis is in the cabinet or when the receiver has been operated for a period of time. Suspected components may carefully be subjected to heat from a soldering gun to simulate normal ambient temperature conditions and thus to expedite the trouble-shooting procedure.



### WIRE STRIPPING

When making circuit repairs, the technician usually is involved in soldering operations. With the gun at his finger tips, hook-up wire can be rapidly stripped and readied for connection into a circuit. A soldering gun is also useful in stripping the ends of 300-ohm lead-in wire.



### SIGNAL SOURCE

A soldering gun may also serve as a signal source. The gun is placed near the circuit being checked, and the 60-cycle signal radiated by the gun's transformer can be used in a signal-tracing process.



### PRINTED-BOARD REPAIRS

A soldering gun fitted with a small tip is adaptable to printed-board work, particularly in the removal of small components having a minimum of soldered connections. **CAUTION**—never allow the heated tip to remain in contact for more than a few seconds at a time. Excessive heat may result in an unbonded section of foil.


### RECESSED AREAS


Long, slender, special-ended tips lend themselves to soldering work in hard-to-get-at areas. In this photograph, a connection is being soldered on a printed board mounted below the chassis level.



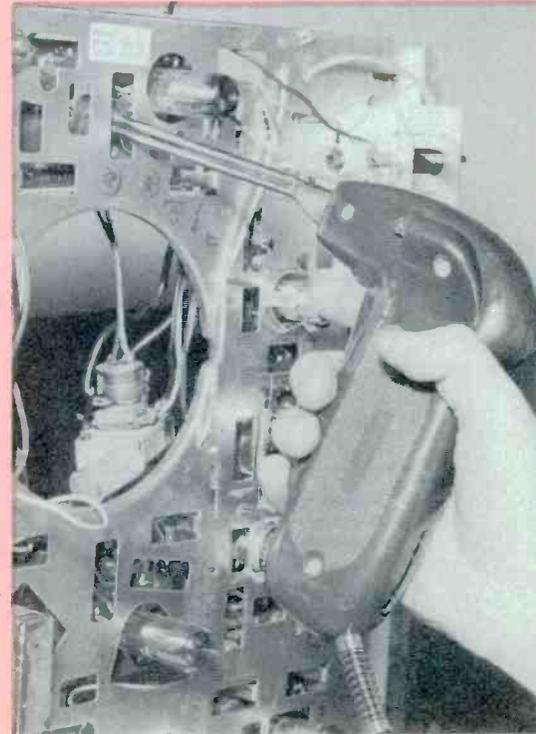
### CABINET REPAIRS

Modified by the use of special tips, a soldering gun is an aid in simple cabinet-patching work. Dents can be effectively eliminated by covering them with a damp cloth and applying heat with a special tip. This causes the wood in the heated area to swell until the dent is no longer noticeable. Dents or marred areas which cannot be repaired in this way can be filled in with stick shellac. A special soldering-gun tip can be used to melt the shellac and smooth it into the damaged area.



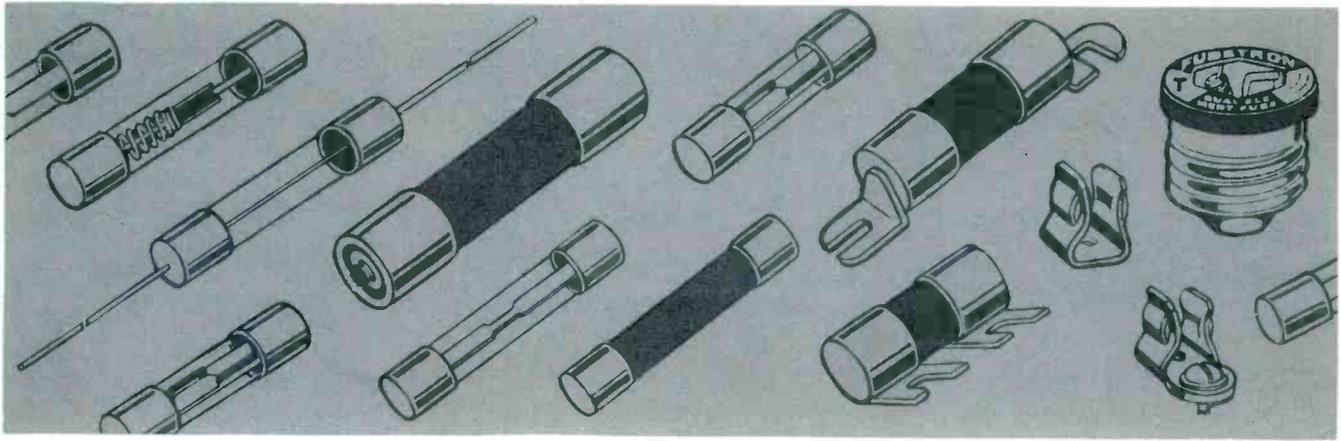

**Whenever you need fuses...**

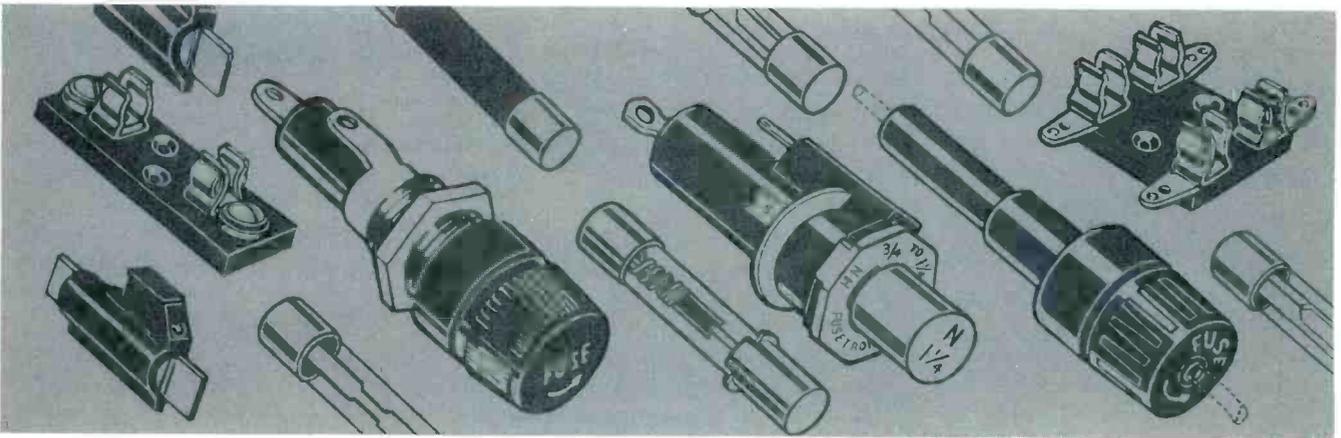

**you'll save time and trouble  
by turning FIRST to BUSS!**



Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.

By relying on BUSS as your source for fuses, you can quickly and easily find the type and size fuse you need. The complete BUSS line of fuses includes: Standard types, dual-element (slow blowing), renewable and one-time types . . . in sizes from 1/500 amp. up—plus a companion line of fuse clips, blocks and holders.

**BUSS fuses are made to protect—  
not to blow needlessly**

When you sell or install BUSS fuses—you can be sure that users receive maximum protection against damage due to electrical faults. And just as important, users are safeguarded against irritating, useless shut-downs caused by faulty fuses blowing needlessly.

**BUSSMANN MFG. CO.** (Division of McGraw Electric Co.)  
UNIVERSITY AT JEFFERSON ST. LOUIS 7, MO.

There are no kicks or complaints from your customers about the operation of BUSS fuses. Servicemen avoid costly, unnecessary call-backs. That's why it pays to rely on dependable BUSS fuses.

**Capitalize on the  
BUSS trademark**



The universal trade and consumer acceptance of BUSS fuses is based on the millions upon millions of BUSS fuses used in homes, on farms and in industry over the past 42 years. Sales are easier to make when you handle BUSS . . . the *Known* brand of fuses.

*For more information on BUSS and Fusetron small dimension fuses and fuseholders... Write for bulletin SFB.*



# TV SOUND FROM THE 6DT6

## All about the New FM Detector in Some 1957 TV SETS

by Thomas A. Lesh

A new circuit with the jaw-breaking name of "locked-oscillator quadrature-grid detector," utilizing the brand-new 6DT6 pentode, is making its first appearance in the sound section of several 1957 models of television receivers. While not very catchy, this name is nevertheless highly descriptive. Let's break it down into its separate parts. First, think of the 6DT6 circuit as merely "a special kind of quadrature-grid detector." This puts it in the same general class with the 6BN6 sound detector often found in TV sets. Although the 6BN6 is popularly known as a gated-beam detector, it actually does its demodulating with what is known as a quadrature-grid circuit.

"Locked-oscillator" refers to a unique feature which sets the 6DT6 circuit apart from other quadrature-grid detectors. This feature tends to improve the sensitivity of the detector to very weak signals. Except for the locked-oscillator arrangement and for differences in tube construction, the 6DT6 and 6BN6 circuits are very similar. Both of them accomplish limiting and audio amplification besides their main function of demodulation. Both are therefore used in efficient, economical, three-stage sound sections composed of one IF amplifier, a detector, and an audio output amplifier.

The 6DT6 circuit has such good self-limiting properties that the audio output voltage remains nearly linear over an extremely wide range of input signal strengths. The graph in Fig. 1 shows the effect on the detector output voltage as the amplitude

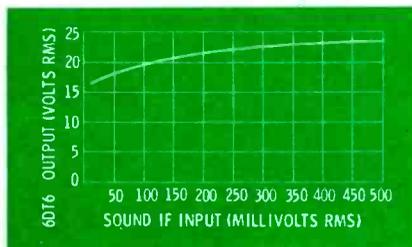


Fig. 1. Input vs. output voltages for a typical 6DT6 detector circuit.

of the input signal to the sound IF stage is varied. An extreme change from 15 to 500 millivolts rms in the input signal amplitude causes only a relatively slight change from 17 to 23 volts rms in the output.

### Review of 6BN6 Circuit

The 6DT6 circuit can best be described by reviewing the operation of the more familiar 6BN6 circuit and then by discussing the similarities and differences between them. At the same time, the theory of the 6BN6 can also be made more understandable during this discussion.

An example of a commercial 6BN6 circuit is shown in Fig. 2A. This circuit is found in a current Zenith chassis having series-string tubes, and the tube is actually a 3BN6; but, since circuit performance is the same with a 3-volt tube as with the 6-volt type and since we have already begun to talk about 6BN6 circuits in general, we shall continue to refer to the 6BN6 instead of specifying the 3BN6 during the following discussion.

The performance of the 6BN6 type of circuit depends mainly on the special construction of the tube. Although the external connections are the same as for a pentode, the internal structure is such that plate current is formed into a concentrated beam. The passage of this beam through the tube is controlled by a limiter grid and a quadrature grid which correspond roughly to the control and suppressor grids of an ordinary pentode.

Limiting of the signal peaks is readily accomplished in the 6BN6 because the range between cutoff and saturation voltages is very small for both grids. When an input signal with an amplitude as low as  $1\frac{1}{2}$  or 2 volts is applied to the limiter grid, plate current will be alternately cut off and brought to maximum value if the tube is properly biased. Further increases in signal amplitude have very little effect on the amount of plate current which is allowed to pass through the grid; for this reason, amplitude modulation of the FM signal by noise pulses is effectively removed from the signal.

The response of the detector to FM can be explained in a simplified way if we think of the limiter and quadrature grids as being gates which swing wide open on positive signal peaks and slam shut on negative peaks. Both gates have to be open for current to reach the plate of the tube; if either one closes, plate current is cut off. The amount of current which reaches the plate is determined by the length of time that both gates remain open.

This length of time continually

• Please turn to page 42



**need a TV  
TRANSFORMER?**



**need an exact  
replacement?**



**wonder where  
to get it?**



**STANCOR  
TRANSFORMERS**  
are AVAILABLE from better  
distributors EVERYWHERE!

**FREE**

The latest Stancor TV  
Replacement Guide and  
Catalog listing replace-  
ments for over 9000 TV  
models and chassis.




**CHICAGO STANDARD  
TRANSFORMER  
CORPORATION**

3503 ADDISON STREET, CHICAGO 18, ILLINOIS

Export Sales: Roburn Agencies, Inc.  
431 Greenwich St., New York 13, N. Y.



## What's Cooking in Color TV

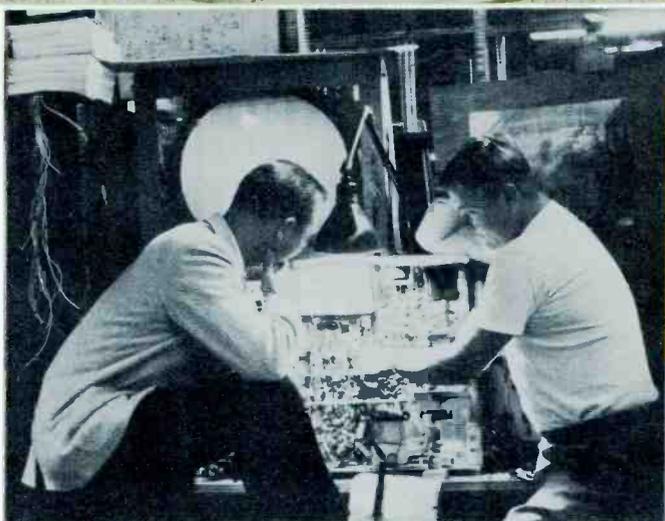

### FIRST-HAND REPORT ON SERVICE AND SALES IN THE CHICAGO AREA

by *Thomas A. Lesh and Verne M. Ray*

We went to Chicago in September and visited consumers, service shops, retail stores, distributors, and television stations to find out what they were doing with color. Our impressions can be summed up in one statement: the kettle is beginning to simmer.

#### Servicing

At the time of our survey, the amount of color servicing which had been done in Chicago was unimpressive in terms of cold statis-

• Please turn to page 54

The color TV situation at the present time might well be compared to a huge kettle in which vast new profits—and problems—are being cooked up for the TV industry. Color TV is provoking an air of expectancy throughout the country—both among the public and among dealers and servicemen, with the latter wondering

how soon they will be facing large-scale color servicing. To help in answering their questions, we decided to lift the lid on the color TV kettle and look inside. We chose the Chicago area for our field investigation because that city has been the site of perhaps the most active promotional campaign for color TV.

# Here They Are!



## CLAROSTAT A47 composition-element controls

meet your servicing needs for radios of practically every make and model, regular or portable, communications or automotive. And in television, black-and-white or color, portable or industrial, you're set with Clarostat A47s. Even test equipment, audio systems, PA equipment and theatre sound systems use Clarostat A47 controls.

For A47 controls are available in linear, tapered, plain or tapped elements; 500 ohms to 10 megohms; 1/2 watt rating, single or dual.

There are five types of "Ad-A-Switches" available that attach to the A47 control in seconds. It's also your selection on shafts — a selection of 13 different lengths and shapes to choose from.

Your Clarostat distributor has A47 controls, switches, shafts, for your immediate convenience.




for **P**erformance... **D**ependability... **Q**uality



**CONTROLS and RESISTORS**  
**CLAROSTAT MFG. CO., INC.** Dover, New Hampshire  
In Canada: Canadian Marconi Co., Ltd. Toronto 17, Ont.

# PRINTED WIRING BOARDS

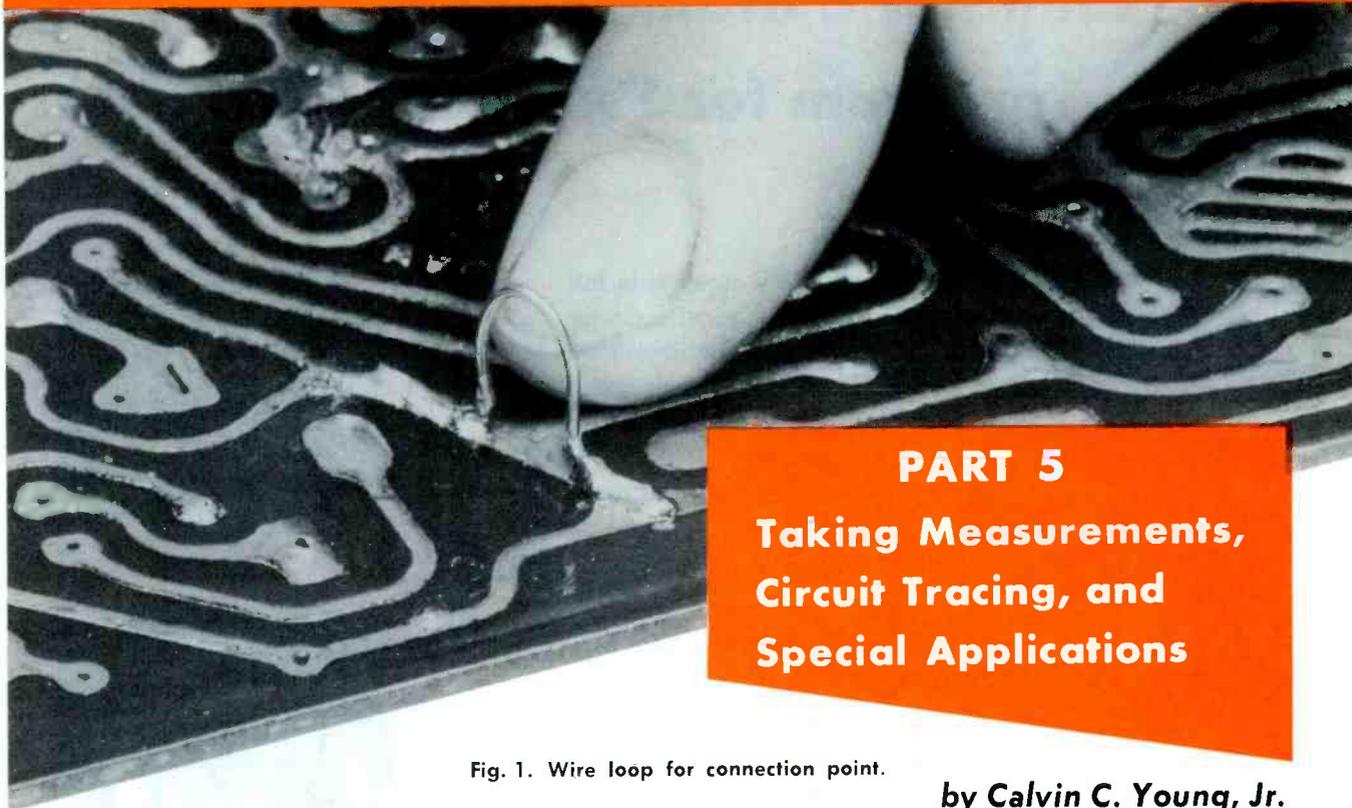

## PART 5 Taking Measurements, Circuit Tracing, and Special Applications

Fig. 1. Wire loop for connection point.

In this, the fifth and final article of the "Printed Wiring Board" series, we will discuss the more routine problems encountered when working with circuits that employ printed wiring boards. These include application of signals, taking voltage and resistance readings, circuit tracing and some special applications.

### Application of Signals

The application of a signal from a piece of test equipment to the circuits of a receiver that employs conventional wiring poses no problem since there are component leads, terminal strips, and lugs on tube sockets which are convenient points to which the test equipment leads may be fastened. When printed wiring boards are employed, most of these points are no longer available and therefore some must be fabricated to make it possible to connect test leads at the required places without having to hold them in place by hand.

The first connection point which must be provided is the ground or B— reference point. This is generally the common-reference point for both signal and DC voltages and is used quite often in trouble-shooting procedures. A short loop of wire soldered to the B— or ground conductor strip as shown in Fig. 1 makes an excellent connecting point for ground leads. Since this connection is needed each time the receiver is serviced, the wire loop can be permanently soldered and left for future use. The loop need be only  $\frac{1}{4}$ " in length to permit one connection such as the ground lead of a signal generator or oscilloscope. Other ground leads could then be connected to

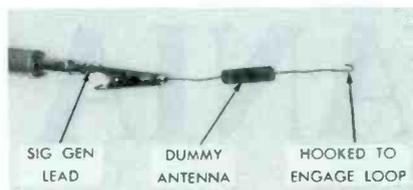


Fig. 2. Hooked lead on dummy antenna.

by Calvin C. Young, Jr.

the ground terminal of the generator or scope. This would provide the necessary common-reference point for all equipment.


Trouble-shooting procedures usually require that an appropriate signal be applied at some point ahead of a suspected stage and that an oscilloscope or VTVM be used to check voltages and signal amplitudes at various points in the suspected stage or stages. A wire loop may be fastened to a conductor in the proper circuit to provide a signal-injection point such as that used for the connection of a dummy antenna. As shown in Fig. 2, the end of the appropriate dummy-antenna component should be formed into a hook so that it may be conveniently fastened to the loop.

It takes but a few minutes to figure out the necessary locations for the wire loops and to make them. The time spent will be more than made up by the time

• Please turn to page 51
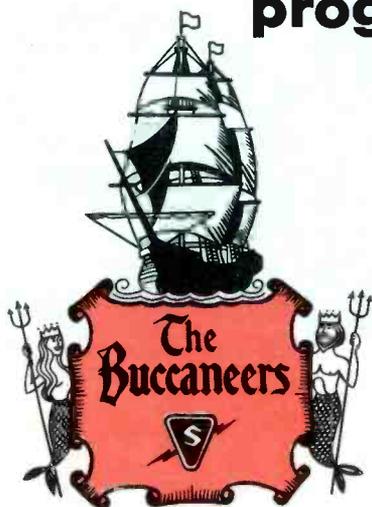
# new Sylvania TV SHOW

launches a dramatic new advertising program for TV Service Dealers



Biggest TV news this fall for you as a service dealer is Sylvania's new adventure thriller "The Buccaneers." Packed with exciting pirate lore, Sylvania's new TV show offers entertainment for the entire family.

And it offers you a brand-new opportunity to build your service business through a dramatic new consumer advertising campaign, "TV SMOG."

Millions of TV set owners will be reminded that TV Smog comes from old worn out picture tubes and receiving tubes. And they'll be reminded to see the service dealer who displays the Sylvania Radio & TV service sign for a TV Smog check-up.

To supplement this powerful TV advertising, a complete campaign in *TV Guide* magazine will also steer the TV set owner to you for a TV Smog check-up.

Get behind this TV Smog promotion: identify yourself as the dealer in your neighborhood who features "Silver Screen 85" picture tubes and Sylvania's quality brand receiving tubes.

And keep in touch with your Sylvania distributor for new Buccaneer promotion pieces and premiums.

SYLVANIA ELECTRIC PRODUCTS INC.  
1740 Broadway, New York 19, N. Y.  
In Canada: Sylvania Electric (Canada) Ltd.  
Shell Tower Building, Montreal

LIGHTING • RADIO • ELECTRONICS  
TELEVISION • ATOMIC ENERGY



# SYLVANIA


"Buccaneers" seen Saturday,  
CBS Network carries  
"TV SMOG" commercials, sells service



... get a "TV SMOG" rating on  
your set



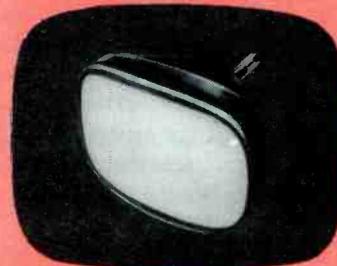... the serviceman who displays  
this sign



... will install a genuine  
"Silver Screen 85"



... and replace worn-out  
receiving tubes with Sylvania's  
quality brand

# CHOOSING A SCOPE

How to Interpret the Manufacturer's Terms and Select the Instrument Best Suited for You

by Leslie D. Deane

Before they have been in the service business very long, most TV technicians realize that an oscilloscope is one of the most valuable and versatile instruments they can possess. In trouble shooting or aligning a television receiver, a great deal of time and effort can be saved through the proper use of a good scope. Thus the question, "What is a good scope?" is highly important to technicians.

At one time or another, the technician will be confronted with the problem of choosing an oscilloscope to fit his particular needs. On this occasion, he may consider questions such as:

"Should I let price govern my selection entirely?"

"Will a general-purpose scope fill all of my servicing needs, or should I look for a special type of instrument?"

He naturally wants a unit that will do an adequate job; but if he is like most of us, he hopes to find one that will not make too big a dent in his pocketbook.

This discussion is intended to acquaint the reader with some of the things to look for when choosing an oscilloscope, and it will also clarify the meanings of various terms used in manufacturers' specifications.

Test equipment manufacturers have refrained from completely standardizing the electrical char-

acteristics of oscilloscopes because these instruments have many different applications. Industrial plants, research laboratories, and other users of oscilloscopes have placed demands upon the manufacturer to produce instruments that differ widely in both physical and electrical features. For this reason, you should first determine the exact type of scope your work requires. The scope used solely for alignment work need not have some of the features which a scope used for signal tracing might need, and vice versa. Keep in mind the other pieces of test equipment you have and how the scope will fit in with them. You might also consider the future—for example, servicing color TV sets places certain special requirements upon the scope used for that purpose.

A human element is involved in the choice of a scope because technicians follow different servicing procedures for a given trouble. One technician may use a scope to solve a particular problem while another may feel it advantageous to use a different piece of equipment. Regardless of where you stand on the subject or how ac-

curately and precisely you do your work, there are certain features you should investigate when purchasing an oscilloscope.

You should consider such points as the vertical sensitivity, frequency response, horizontal sweep-frequency range, screen size, input impedance and whether or not the scope produces a

SENSITIVITY

RISE TIME

ASTIGMATISM

INPUT IMPEDANCE

TIME BASE

Z-AXIS



Fig. 1. Wide-Band—High-Sensitivity switch on an oscilloscope.

# CERAMIC CARTRIDGES



*American*  
"Clearamic"

## LOADED with PROFIT

- Lightweight, miniature size, greater compliance
- New mechanical construction gives higher output
- New "throw-away" element
- Simple replacement, snap-in action
- Assorted stock orders totaled for maximum discount
- "Clearamic"—The "new look in good listening"

### New Turnover Type



Response . . . 40-12,000 cycles  
Output . . . 1-1.2 volts

### New Single Needle Type



Response . . . 40-12,000 cycles  
Output . . . 1-1.2 volts

Turnover type features "throw-away" element offering snap-in replacement of both element and needle assembly for essentially the price of a good replacement needle. Single needle type features simplified self-locating needle replacement.

Ask for the handy new "dispenser" assortment — meets almost all replacement needs.



## ELECTRONICS DIVISION

ELGIN NATIONAL WATCH COMPANY

For Cartridges:

2435 N. NAOMI STREET,  
BURBANK, CALIFORNIA


Sales representatives in principal cities.

sufficiently bright trace when the screen is filled with a large or expanded pattern. In addition, the frequency-response characteristics of accessories (such as probes) should be investigated.


Judging the capabilities of a scope from specifications put forth in advertising literature is sometimes difficult, especially if one is not too familiar with the manufacturer's method of expressing the various electrical characteristics. We will examine a few of these characteristics individually and expand upon some of the terms commonly used to denote special features found in commercial oscilloscopes.

### Sensitivity

The sensitivity factor is of in-

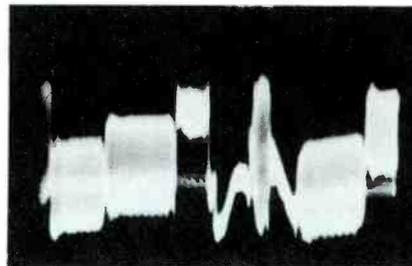

(A) On a wide-band scope.

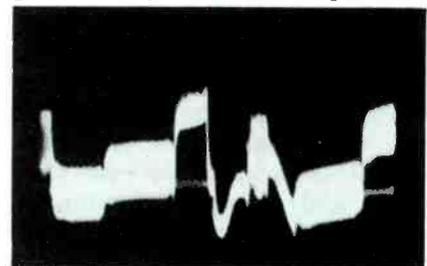

(B) On a narrow-band scope.

Fig. 2. Composite color signal.

terest to the technician because it determines the weakest signal that can be successfully viewed on the oscilloscope screen.

The amount of beam deflection varies directly with the magnitude of the voltage applied to the deflection plates, and this of course depends upon the input signal and the gain of the amplifiers within the instrument. Usually, the sensitivity is expressed in volts or millivolts per inch. For example, a certain general-purpose scope may be said to have a vertical-deflection sensitivity of 20 mv rms per inch. This specification indicates that the scope requires 20 mv rms at the vertical input terminals to produce a 1" peak-to-peak deflection on the screen. Such a specification may be written as "20 mv (RMS)/inch" or ".02 RMS volts/inch."

Unfortunately, gain and frequency response of amplifiers do not go hand-in-hand. In order to obtain an increase in one, a decrease in the other must usually be tolerated. For this reason, many manufacturers are more

specific and may give two or more sensitivity ratings for various frequency-response ranges.


Some instruments have provisions which permit the user to select either a high sensitivity or a wide frequency response. The instrument pictured in Fig. 1, for example, incorporates a selector switch on the front panel, providing for either wide-band or high-sensitivity operation.

The sensitivity of a scope should be relatively high for alignment purposes. This is especially true when aligning the higher channels of a television tuner because the output of most conventional sweep generators will fall off slightly at the higher frequencies. A vertical sensitivity of approximately 10 millivolts per inch


is usually ample for TV alignment work. One should pay particular attention to this point because nothing is more aggravating in service work than attempting to compare a small insufficient response pattern to a recommended standard.
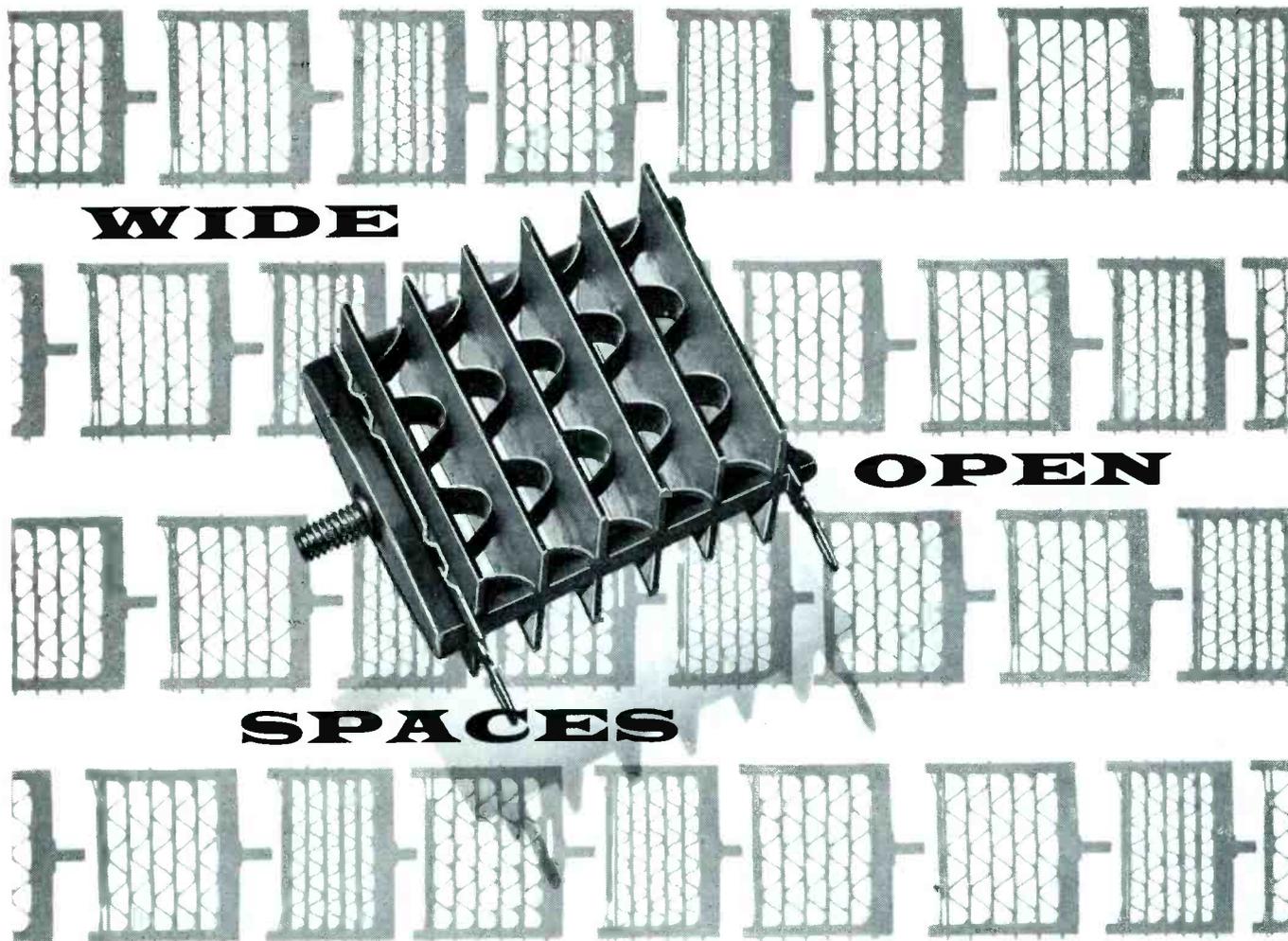
### Frequency Response

Another important specification of an oscilloscope is its band-pass characteristics or the ability of the vertical and horizontal amplifier systems to pass certain ranges of frequencies with relatively equal amplification. The vertical amplifier system is usually designed to have as wide a frequency response and as great a sensitivity as economically practical. The horizontal amplifier system, however, is often designed with a narrower frequency response and with less sensitivity, although in some instruments both the vertical and horizontal systems may be identical in these characteristics. Requirements for the horizontal system are usually less because this section is more



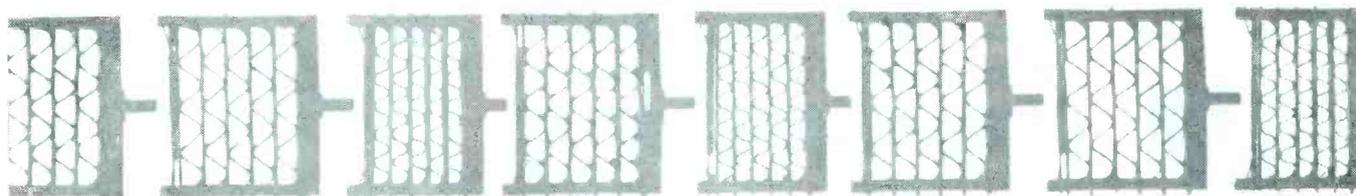**keep operating temperatures down—dependability up!**



RCA SELENIUM RECTIFIERS utilize modern design—*full surface ventilation* with no chance of center-core hot-spots. Note the corrugated spring-steel separators which provide positive multiple-area contacts with each plate. This open construction facilitates free-flow of air and efficient cooling of the plates, and minimizes the possibilities of overheated components in compact TV, radio, and phonograph designs.


The one-piece assembly-yoke with the molded mounting stud prevents *twisting* or *squeezing* the stack during installation. Rigid construction minimizes the possibility of “barrier” breakdowns—*gives greater assurance of dependability in operation.*

So, when you need a replacement selenium rectifier, ask your distributor for a dependable, long life RCA SELENIUM RECTIFIER. Available now in 12 types, ratings from 65 Ma to 500 Ma.


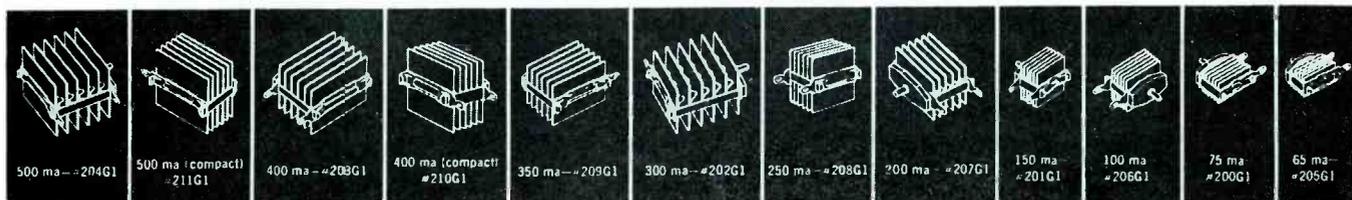
## SELENIUM RECTIFIERS

Radio Corporation of America • Harrison, N. J.



often used to amplify the sawtooth sweep signal generated within the unit itself. These signals are usually large in amplitude and relatively low in frequency.

The vertical deflection system of a typical general-purpose scope may have a frequency response from 20 cycles to 2 megacycles within  $\pm 3$  db. This indicates that the over-all vertical system of the scope is capable of providing uniform power amplification within 3 decibels for frequencies between 20 cycles and 2 megacycles.

Many technicians are under the

impression that a scope used for conventional TV alignment should have a vertical-amplifier response up to 4 megacycles. This is not the case. The signal from the sweep generator goes through a complete frequency swing at a specific rate (usually 60 cps). The repetition rate of the rectified signal at the output of the detector is therefore the same as that of the sweep frequency, and the response curve which appears on the screen results from the application of a signal which falls into the category of a 60-cycle square wave.

This type of pattern can be reproduced on any scope having a flat vertical-amplifier response from 20 to 1000 cycles.

Various signals containing a number of frequencies are actually present in the circuits of a television receiver, and in order to examine all of their waveforms accurately, a frequency response up to 4 megacycles or more would be necessary. For general servicing such as observing only the presence of signals in various circuits, however, uniform frequency response up to only 100,000 cycles will suffice.

The technician will, on occasion, want to examine the shape of various signals and the amplitude relationships between signals of different frequencies. For this function, a scope should have a uniform vertical frequency response down to at least 30 cycles and up to not less than 300,000 cycles. If the technician intends to service color television receivers, he should look for a scope having

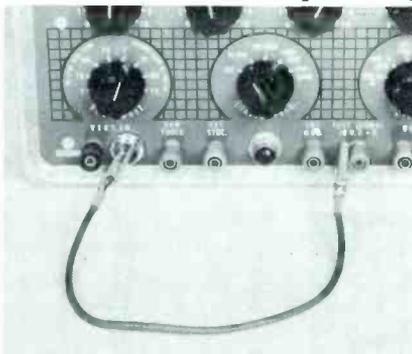


Fig. 3. Calibrating voltage applied to vertical input from test-signal jack.


a usable frequency range of at least 4 megacycles. It will be necessary to have an instrument of this type to observe accurately the color burst and chrominance portions of a composite video signal. This does not suggest, however, that a scope with a narrower response cannot be used in the servicing of color receivers. Any scope is of value in servicing as long as the user realizes its limitations.

The waveforms in Fig. 2 illustrate a composite color signal as it appears in the video circuit of a typical color TV receiver. The waveform in Fig. 2A was observed with a scope having a relatively wide frequency response. Fig. 2B shows the same signal reproduced

# SHOW ANY PICTURE or PATTERN

at any time — ON ANY TV SET



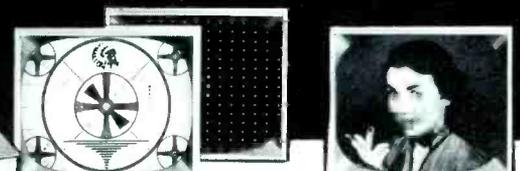

- For Servicing Black & White and Color TV
- For Merchandising and Advertising Promotions
- For Paging, Educational and Industrial Use

## New MODEL 1000 **B&K DYNA-SCAN**

### PICTURE AND PATTERN VIDEO-GENERATOR

**3 SLIDE TRANSPARENCIES ARE SUPPLIED**

1. Indian Head Pattern
2. White Dot Pattern
3. White Line Crosshatch

Plus One Clear Acetate

These are broadcast quality and assure high-definition TV images. You can also transmit slides of any subject you wish.

Simplify and speed servicing with this unique, new, COMPLETE FLYING SPOT SCANNER. Produces composite video and sync signal that operates any standard VHF black and white or color TV receiver. Easily reproduces standard Indian Head test pattern or any other pattern—in home, shop or store—for proper TV set alignment; enables you to make all color TV static and dynamic convergence adjustments with stable White Dot and White Line patterns. Can be used with one or more standard TV receivers or fed into master antenna system. Reproduces from any film transparency. Transmits messages typed or written on clear acetate.

Size: 16½ in. long, 10⅝ in. high, 9½ in. wide. Net wt. 28 lbs. . . . . **\$199<sup>95</sup>**<sub>NET</sub>



**MODEL 950**

**Model 950 Dyna-Scan Pickup and RF Generator Only**

Make your own picture and pattern generator. Just connect Model 950 to any properly modified 10-inch TV set which acts as your external flying spot scanner. Size: 3½ in. high, 10½ in. wide, 5 in. deep. Complete with 3 slide transparencies and 1 clear acetate. Net wt. 5 lbs. . . . . **\$69<sup>95</sup>**<sub>NET</sub>

See Your Distributor or Send For Bulletin 1000-R

**B & K MANUFACTURING CO.**  
3726 N. Southport Ave. • Chicago 13, Illinois  
Makers of DYNA-QUIK, CRT, CALIBRATOR and DYNA-SCAN



on a narrow-band instrument. Notice the reduction in the relative amplitudes of the high frequency components in Fig. 2B as compared to Fig. 2A.

The technician should remember that a wide frequency response is achieved by sacrificing gain; thus, to obtain a reasonable amount of both, additional stages must be utilized in the oscilloscope. This, of course, increases the cost of the instrument.

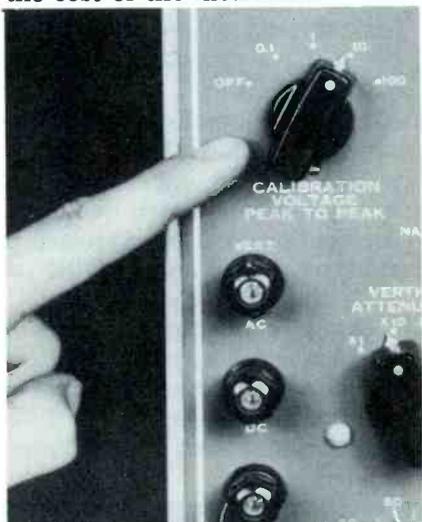


Fig. 4. Oscilloscope with an internal, switch-controlled calibrating voltage.

#### Voltage Calibration

Another feature often desired in an oscilloscope is a means of calibrating the instrument to indicate the values of peak-to-peak voltages—this provision is especially important in checking those circuits where signal amplitude is critical. Some scopes have a special jack from which a source of constant voltage of known amplitude is available. The photograph of Fig. 3 illustrates this method of calibration. The instrument shown features a separate front-panel jack which provides an 18-volt peak-to-peak test signal.

In other designs, a line-frequency signal of known value can be applied to the vertical amplifier system by placing either the vertical attenuator or calibration switch in the calibrate position. An example of this method is pointed out in Fig. 4. This particular instrument incorporates a separate calibration switch. The switch provides four different peak-to-peak values and works in conjunction with the vertical attenuator.




# 5 IMPORTANT REASONS WHY


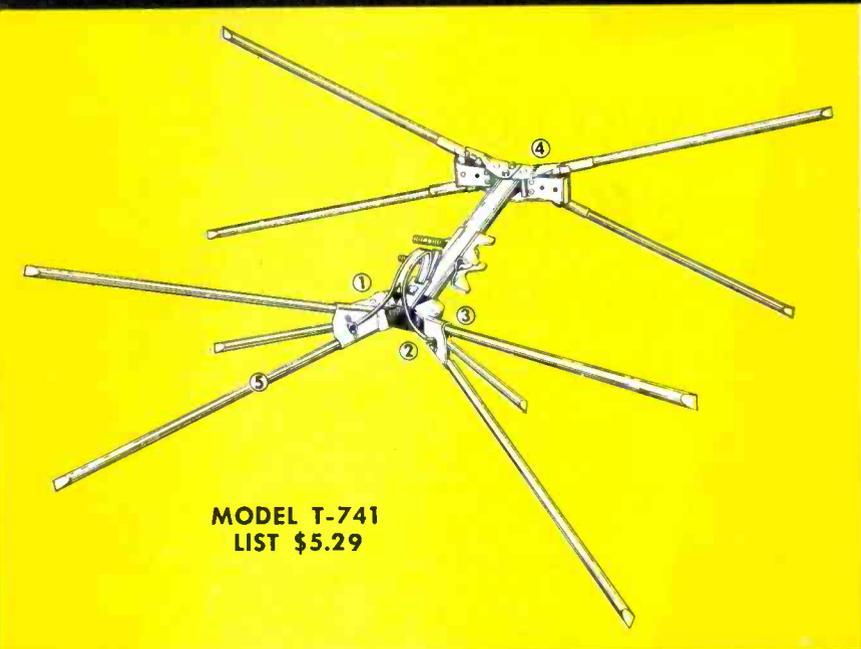
# IS YOUR BEST BUY IN CONICALS!

Full line to select from; 8 single array antennas, 8 stacked antennas and 8 "Do-It-Yourself" antenna kits.




## The Facts Prove It!

- FACT No. 1** Completely pre-assembled. "Presto" Instant Mount Assembly opens antenna as easily and quickly as an umbrella.
- FACT No. 2** New Polyethylene Cable Anchor takes all tension off of terminals, prevents cable from breaking at terminal points.
- FACT No. 3** Front Bracket made of heavy spring temper aluminum alloy with High Q molded plastic insulator.
- FACT No. 4** Rear Bracket is made of heavy gauge aluminum to assure long life and resist heavy ice and strongest gales.
- FACT No. 5** Arrays are full size and of all aluminum construction. Elements are doweled to increase strength and prevent whistling.

The **TENNA** Manufacturing Co.  
CLEVELAND 25, OHIO

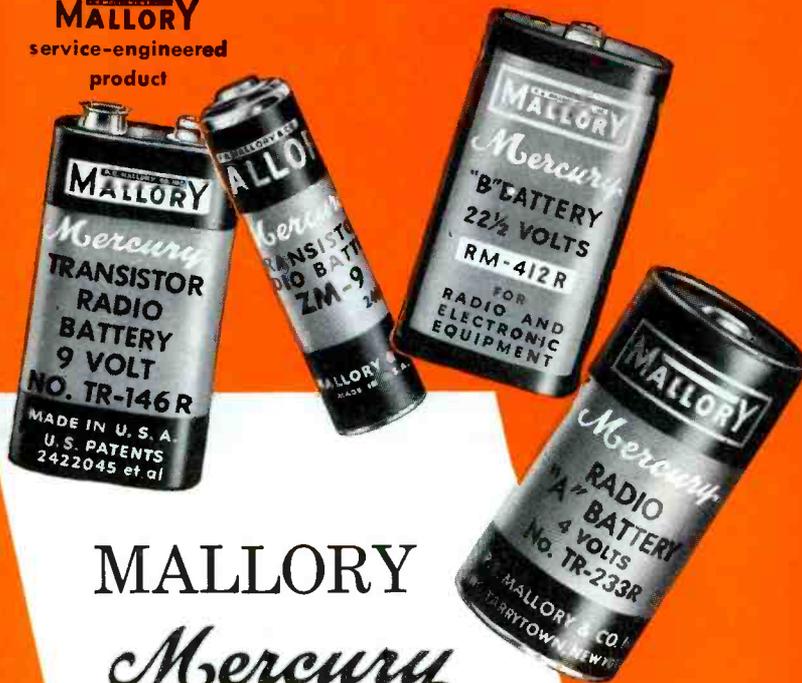... another  
**MALLORY**  
service-engineered  
product




# MALLORY *Mercury* BATTERIES ...

leading line for transistor portables

Cash in on the growing battery replacement market for transistorized portables—with the line that offers you an unequalled combination of prestige and profit.

Mallory pioneering of mercury batteries helped make these new miniature radios possible. Leading set makers supply Mallory Mercury batteries in original equipment ... recommend them to set owners, too!

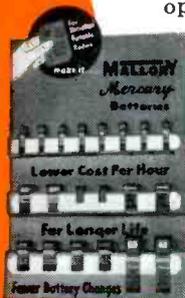Mallory performance builds business, assures repeat sales and profit to you. They're the value leader, because they cost less per hour of operation.



### SPECIAL INTRODUCTORY BATTERY MERCHANDISER

Because of the remarkable shelf life of Mallory Mercury Batteries, now for the first time you can stock batteries without fear of inventory loss. This introductory assortment covers all popular transistor portables. No extra charge for the display unit! Order yours today!

P. R. MALLORY & CO. Inc.  
**MALLORY**

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Controls
- Vibrators
- Switches
- Resistors
- Rectifiers
- Power Supplies
- Filters
- Mercury Batteries

### Input Impedance

Oscilloscopes have a relatively high input impedance, a characteristic which is desirable in any piece of test equipment because it minimizes the loading effect on high-impedance circuits.

The ideal input circuit for an oscilloscope would exhibit infinite resistance and no capacitance across the input terminals. In actual practice, of course, this condition can only be approached. The majority of general-purpose scopes have impedance ratings which range from 1 to 5 megohms with 25 to 50 mmf of capacitance across the input. From this we can see that the impedance term usually found in a manufacturer's specifications will be expressed in series resistance and parallel capacitance. A rather large DC-blocking capacitor is usually placed in series with the input circuit; however, this component can be ignored because of its relatively low reactance even at the lowest frequencies.

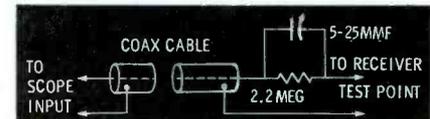


Fig. 5. Low-capacity probe circuit.

When observing waveforms made up of relatively high frequencies, the input shunt capacitance of the scope and its connecting leads becomes very important. To minimize the effect of this capacitance upon the circuit under test, a special low-capacity probe can be used. The probe places a relatively low capacitance in series with the existing capacitance, thus decreasing the over-all value. A typical low-capacity probe circuit is shown in Fig. 5. The value of the variable capacitor will usually range from 10 to 15 mmf, while the parallel resistor may be in the neighborhood of 2 megohms.

Without a suitable low-capacity probe in series with the input capacitance of the scope, the shape of the waveform under examination may be seriously distorted. The lower the effective series capacitance within the probe the less shunting action the instrument will have upon a high-impedance circuit.

The only disadvantage in using a low-capacity probe is the fact that the voltage actually reaching the scope will be reduced in the same proportion as the input capacitance, i. e., if the input shunt capacitance is reduced 25% by using a probe, the applied signal voltage will also be reduced 25%. As far as television servicing is concerned, the low-capacity probe is used most often in the video, sync, and sweep circuits where the voltages are of sufficient amplitude to overcome the loss within the probe.


#### Rise Time

Oscilloscope manufacturers often make mention of the term "rise time." This term denotes the time it takes the amplifiers within the scope to respond to an input signal. The definition of rise time in itself has little meaning to the technician; but since it is directly related to the high-frequency response of the unit, it becomes of some interest. The shorter the rise time the more accurate the scope is in reproducing the waveforms of applied signals. If a scope has a relatively short rise time, it has good high-frequency response and the technician can expect pulses having steep leading edges to be accurately reproduced. This feature can be used to great advantage when servicing color receivers.

#### Push-Pull Amplifiers

Often found in the specifications for oscilloscopes is the statement that push-pull amplification is employed. This indicates that the instrument makes use of a push-pull output stage in the deflection system. In this arrangement, a positive-going signal is applied to one deflection plate of the CRT while a negative-going signal of the same amplitude is applied to the other plate. Perhaps the most important advantage of this circuit is that it provides balanced voltages for each set of deflection plates. This results in greater signal drive for the same supply voltage, better hum cancellation, and the reduction of second-harmonic distortion.

In connection with amplifier

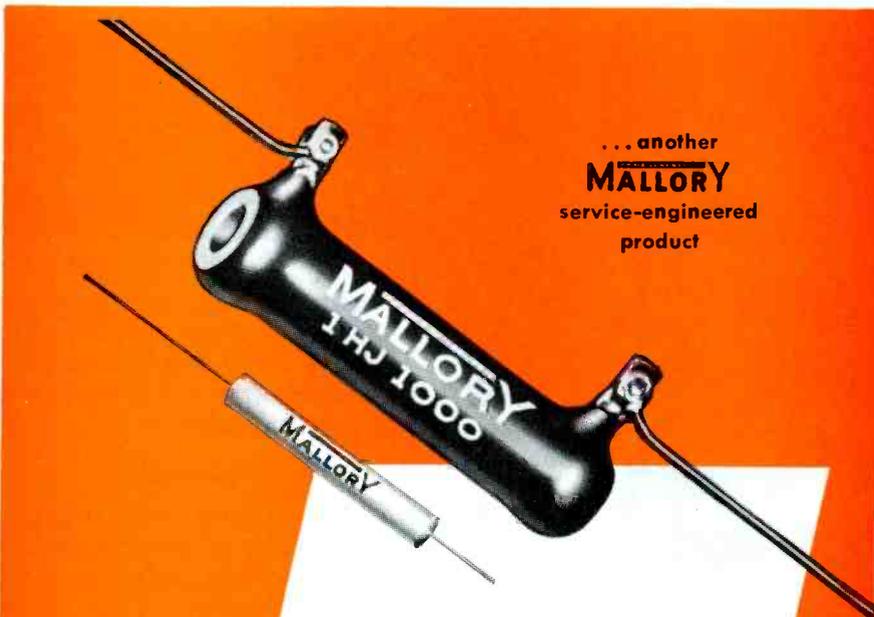

... another  
**MALLORY**  
service-engineered  
product

## for value in "wire-wounds" make it **MALLORY**

Take your choice of these Mallory wire-wound resistors, and you're sure of long service and stability on any replacement job.

**Mallory vitreous enamel resistors** are protected against moisture and corrosion by a special non-porous, non-alkaline vitrified coating . . . are wound on a high-stability steatite core. In both fixed and adjustable types, 5 to 200 watts.

**Mallory axial lead resistors**, famous for cool operating and easy mounting, are coated with a dense, non-corrosive cement that keeps moisture out, and assures good heat dissipation. Leads can't pull away from the winding. 4-watt and 7-watt ratings, in a full range of resistance values.

Order now—from your nearby Mallory distributor!



- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Controls
- Switches
- Rectifiers
- Filters
- Mercury Batteries

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

do you  
know  
what to  
charge  
your  
customers?

for this



or this




or this



or this



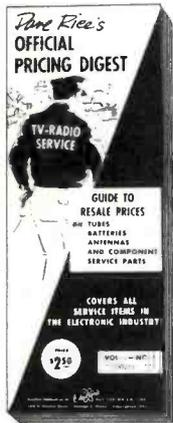you can find out  
in seconds  
when you use  
*Dave Rice's*  
**OFFICIAL PRICING DIGEST**



When your customer questions the cost of replacement parts, you can quickly prove your prices are correct when you use the Official Pricing Digest . . . with list or resale prices on over 60,000 components. Arranged alphabetically by manufacturer and product, numerically by part number. Always up-to-date, issued every three months. Compact, convenient size fits in tube caddy, tool box or pocket. \$2.50 per copy.

### FOR EVERY TV-RADIO SERVICE SITUATION

use Dave Rice's  
**OFFICIAL SERVICE ORDER BOOK**  
(FORM TVR-100)

Has separate listings for six tubes, receiving tubes, parts serial numbers, labor and tax charges, signatures. 50 sets of triplicate orders in each book—carbons bound in. 75c per copy, \$6.50 for box of ten.



At your distributor or direct from  
**ELECTRONIC PUBLISHING COMPANY, INC.**  
180 NORTH WACKER DRIVE  
CHICAGO 6, ILLINOIS


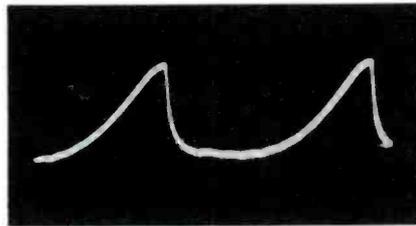


Fig. 6. Horizontal-sweep waveforms at different time-base frequencies.

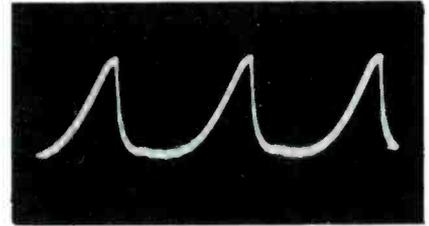

design, some manufacturers use a system of direct-coupled amplifiers whereby it is possible to extend the frequency response down to zero frequency or DC.

#### Time Base

The internal sweep systems of an oscilloscope are often referred to as time-base generators. A time base is provided as the electron beam travels across the screen at a rate determined by the frequency of the sweep signal. When an input signal is applied to the scope, the beam is deflected at right angles to the time base and amplitude is plotted graphically against time by the beam trace.

Vernier-controlled frequency ranges of the internal sweep oscillator can be adjusted to provide a variety of time bases. In Fig. 6, two different time bases have been selected to view a signal having a frequency of 15,750 cps. A time-base frequency of 7,875 cycles was used in Fig. 6A. This frequency is exactly one half of the observed-signal frequency, thus producing two full cycles on the screen. In Fig. 6B, a time-base frequency of 5,250 cycles was used. This is one third of the signal frequency, so three full cycles appear on the screen.

Time-base expansion may be obtained through the use of an expanded sweep. Many scopes are designed to expand the horizontal sweep from 5 to 40 times the normal full-screen deflection. The use of an expanded-sweep trace permits a microscopic examination of the detail in a portion of the pattern.

#### Maximum Input Potential

Most manufacturers specify the maximum voltage which may be applied across the vertical input terminals of a scope. This usually refers to the DC voltage which the input circuit can handle safely. If the maximum voltage

rating is exceeded in an instrument having a DC-blocking capacitor, this component may break down, and damage to the instrument will result. When a scope employs DC-coupled amplifiers, the maximum input DC voltage is governed by the ability of the input attenuator circuit to dissipate power. Except for second-anode voltages, most general-purpose scopes have an adequate rating for the DC voltages encountered in TV service work.

Should the technician desire to observe the waveform of an AC voltage which approaches the maximum rating of the instrument, it is advisable to use a voltage-divider network in series with the scope input.

#### Astigmatism

Another term often appearing in manufacturers' specifications for oscilloscopes is "astigmatic focus." The technician should not let this term throw him. Astigmatism may be generally defined as the condition of good focus along one axis while poor focus exists along an axis at right-angles to the first. In the case of an oscilloscope, this condition will reveal itself as a poorly focused spot on the CRT screen. The spot of light produced by the beam of electrons will not focus into a small circular area but will appear as an oval. The spot may focus properly near the center of the screen, but when it is deflected toward the outer screen circumference, it becomes oval and will appear out-of-focus in these areas. Fig. 7 illustrates how

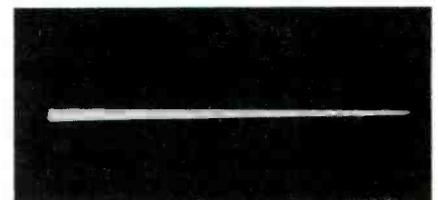


Fig. 7. Oscilloscope trace which exhibits the effect of astigmatism.



*One gift you can give yourself . . .*

## PROFITS FROM YEAR-END RCA BATTERY SALES

More portable radios will be found under the Christmas trees this year than ever before. And just as sure as there's a Santa, there's a clause that says portables need batteries—RCA Radio Batteries. So, give yourself a gift of year-end battery profits. Ask your RCA distributor to fill in your stock with consumer-accepted RCA Radio Battery types. Then, play up your RCA Battery line. Promote yourself into a big share of both the new-set business and the replacement business that's coming as sure as '57. And, with RCA's national advertising and colorful promotional material supporting your efforts, you're sure to wrap up a cheerful package of profits for yourself this year.



### RADIO BATTERIES

RADIO CORPORATION OF AMERICA • CAMDEN, N. J.

AMERICAN TELEVISION &  
RADIO CO. ST. PAUL, MINN.

For those who  
want the finest!

**ATR TV**

*Full Door Console  
Receiving Sets*

UNSURPASSED  
IN BEAUTY

UNEQUALLED  
IN PERFORMANCE

UNMATCHED IN  
QUALITY  
CONSTRUCTION

exclusive  
profitable  
dealer  
franchises  
now available



*designed  
with the  
Serviceman  
in mind  
... easy to  
get at*



WRITE TODAY FOR COLORFUL  
BROCHURE SHOWING THE  
NEW LINE OF ATR TV SETS

ALSO MANUFACTURERS OF DC-AC INVERTERS,  
"A" BATTERY ELIMINATORS, AUTO RADIO VIBRATORS

**ATR** AMERICAN TELEVISION & RADIO CO.  
Quality Products Since 1931  
SAINT PAUL 1, MINNESOTA - U. S. A.

the spot can exhibit astigmatism by focusing on the left side of the screen and not on the right.

Astigmatism as related to oscilloscopes is usually a result of misalignment of the deflection plates within the CRT, or it may be due to incorrect deflection plate potentials. In order to compensate for astigmatism, it is necessary to control the potential of each pair of deflection plates separately. Some scopes therefore incorporate an anti-astigmatic circuit to overcome this undesirable effect. This circuit provides a variable control over the mean potential for each pair of deflection plates, thus neutralizing the conditions causing the oval spot on the screen at any particular point.

#### Z-axis

The Z-axis of an oscilloscope may be referred to in connection with retrace blanking and intensity modulation. Actually, the Z-axis is represented by an increase or decrease in the CRT beam current. Oscilloscopes having provisions for Z-axis modulation are usually capable of controlling the intensity of the beam by voltages from either internal or external sources. The return trace of the electron beam can be blanked out by reducing the beam intensity during retrace time. This feature is incorporated in many general-purpose scopes. Some designs have fixed blanking, while others provide control over this blanking action. With the retrace blanked out, the technician may find it easier to study the waveform reproduced during trace time.


Intensity or Z-axis modulation differs from ordinary sweep blanking in that it conveys some form of intelligence by varying the brilliance of trace on the screen. Blanking merely removes retrace lines from the screen, while intensity modulation in its true sense either intensifies or removes certain portions of the trace. By using the Z-axis modulation characteristics of a scope, time markers can be introduced into the observed pattern. This makes it possible to determine the time duration of a wave or to denote various time intervals on a given pattern.



**Converts Battery Radio  
to Electric Operation!**



**At All Distributors**

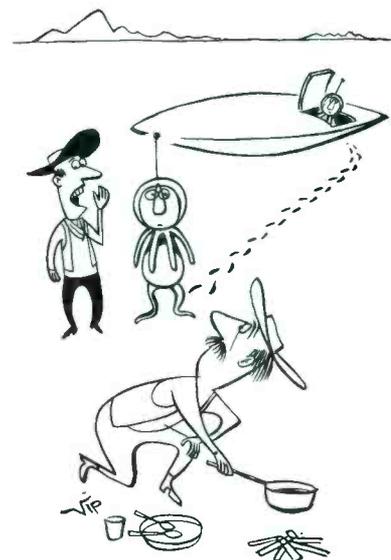

*"Hey, Sam. This guy wants  
to know where's the nearest  
place he can find  
JENSEN NEEDLES."*

# Bull's-eye every time!

We hit the target again . . .  
with this new, modern version of the  
most wanted service-test instrument.

Pyramid introduces the CRA-2  
Capacitor-Resistor Analyzer, a versa-  
tile, up-to-date, moderately priced test  
instrument. The CRA-2 is the perfect  
multi-purpose analyzer for the techni-  
cian, serviceman and engineer, in  
industrial and military electronics,  
black and white, and color television,  
and all related fields.

The guesswork has been removed  
from circuit trouble shooting. When  
making leakage-current measurements,  
the values are read directly from the  
meter while the rated operating volt-  
age is applied to the capacitor. A  
vacuum-tube ohmmeter circuit dis-  
plays accurate insulation-resistance  
values on the meter for many types of  
capacitors. The extended range cali-  
brated power factor control permits  
power factor measurements of electro-  
lytic capacitors rated as low as 6 volts  
DC working and as high as 600 volts  
DC working. This special "QUICK  
CHECK" circuit performs rapid "IN  
CIRCUIT" test for short, open, inter-  
mittent high RF impedance and high  
power factor without removing or dis-  
connecting the component from its  
operating circuit.

MODERN DESIGN

VERSATILE

DEPENDABLE

TIME SAVING



### FEATURES

- "Quick Check" in circuit test for Open Circuits. Short Circuits. Intermittents. High RF Impedance. High Power Factor.
- Speedily and accurately checks: Capacitance. Power Factor. Resistance. Insulation-Resistance. Leakage Current.
- Precision meter for accurate readings of leakage current, applied voltage and insulation resistance.
- Combination Wien and Wheatstone bridge.
- Accurate vacuum-tube meter circuit.
- Parts of the highest quality are used. Wire and wiring meet military specifications.

Examine it today  
Being introduced by leading Electronic Parts Distributors

## PYRAMID ELECTRIC COMPANY

1445 Hudson Blvd., North Bergen, New Jersey

Burton Browne / New York



**THE UNGAR... ESPECIALLY  
DESIGNED FOR PRINTED CIRCUIT  
REPAIR AND PRODUCTION  
LINE SOLDERING**

The famed Ungar Pencil soldering iron with its series of 16 interchangeable tips has been especially designed for printed circuit production and repair.

Tip temperature can be controlled simply by changing tips.

For printed circuit service heating Unit No. 535 with tiplet is recommended. This unit provides a 650° tip temperature at 23½ watts.

For operators well skilled in printed circuit soldering, heating


Unit No. 1235 with tiplet drawing only 37½ watts delivering 750° tip temperature is recommended.

For heavy duty chassis service, an Ungar Super Hi Heat tip at 47½ watts delivering 1000° tip temperature is used.

Ask your parts distributor about the Ungar PRINTED CIRCUIT MANUAL.



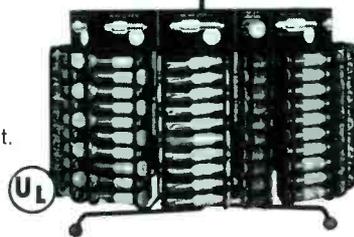
Better jobbers everywhere handle this Ungar iron and display it with 16 interchangeable tips and tiplets in this counter dispenser. Look for it.



The patterns pictured in Fig. 8 represent a 15,750-cycle saw-tooth signal viewed at a time-base frequency of 2,625 cps. This normally produces six cycles on the screen as shown in Fig. 8A. In Fig. 8B, however, every other cycle has been blanked out by applying a sine-wave signal of 7,875 cps to the Z-axis input. The frequency of any signal can be determined by blanking or intensifying every other cycle of the unknown frequency with a calibrated signal applied to the Z-axis of the oscilloscope.

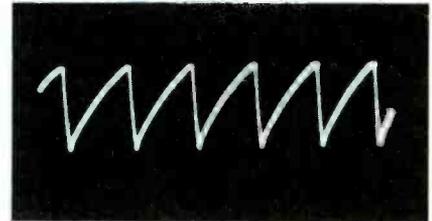**Conclusion**

The scope characteristics and design features covered in this article all lend themselves to the over-all usefulness of a general-



(A) Unmodulated waveform.



(B) Z-axis modulation at 7,875 cps.

**Fig. 8. Comparative waveforms which show the effects of intensity modulation.**

purpose oscilloscope. Sensitivity and frequency response are two of the foremost factors, although accessory items available for use with a particular scope are also important. When servicing TV receivers, the technician will often find it advantageous to have a detector probe, low-capacity probe, and a voltage-dividing probe.

Each individual has his own ideas as to the particular problems he intends to solve with the use of an oscilloscope. We feel this discussion will aid you in understanding the many features listed in manufacturers' sales literature and thus help you to evaluate the utility of various commercial scopes. Good shopping! ▲

**Ungar** ELECTRIC TOOLS, INC. 4101 Redwood Avenue, Los Angeles 66, Calif.

# JERROLD Introduces TRAP-EASE\*

**Revolutionary New TV  
Filter Knocks Out  
Adjacent Channel  
Interference . . . Opens  
New Sales Market For  
The Television Trade!**



**Only \$19.95 List**

This tunable "deep notch" antenna trap (greater than 50 db) permits TV viewers to remove "beat" or "herringbone" patterns caused by strong adjacent channel sound or video carriers. Permits clear reception of even weak distant stations.





Works with any TV receiver and any 300 ohm antenna that would normally bring in pictures from the distant stations if the interfering adjacent channel was not on the air. Does not affect reception of regularly viewed channels.

**BRINGS IN PICTURES FROM OUT OF NOWHERE! TRAP-EASE**


**Before TRAP-EASE is Installed**

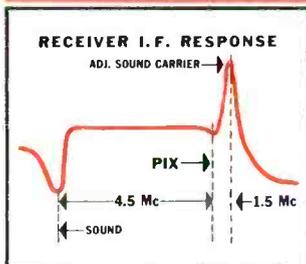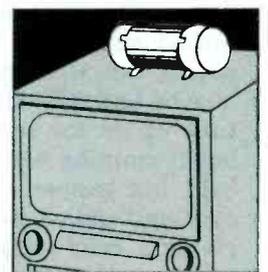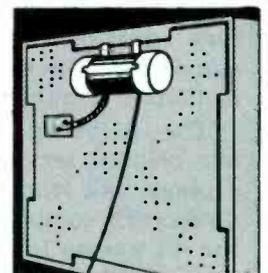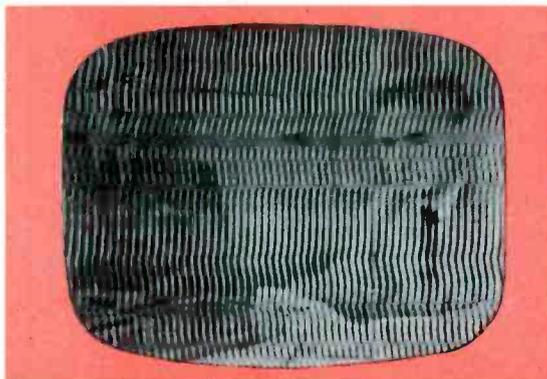**After TRAP-EASE is Installed**

**EASILY  
INSTALLED  
ON ANY  
TV SET!**



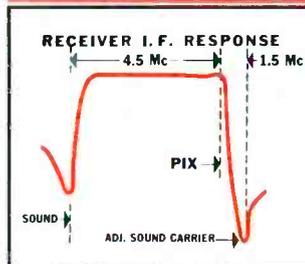In case shown Receiver AGC is held down by a strong adjacent channel sound carrier. This lowers receiver gain and prevents proper reception of the desired channel. "Beat" or "Herringbone" pattern is predominant on the screen.



The adjacent sound carrier has been suppressed by some 50 db, which: (1) Enables the signal level of the desired channel to control the AGC action of the receiver. (2) Completely removes the "beat", leaving a clear, strong picture.

**TRAP-EASE  
SELLS ITSELF**

Let the amazing performance of the Jerrold Trap-Ease do its own selling. One demonstration and the Trap-Ease sells itself with the greatest of ease. Simple to demonstrate either in your store—or in the customer's home.

**MONEY BACK GUARANTEE**

Never before a TV accessory that achieves such startling results. Contact your Jerrold distributor today for details on the complete sales promotion package available to you.

**TWO MODELS AVAILABLE**

Low Trap-Ease (Model HQ-91) covers Channels 2 to 6.  
High Trap-Ease (Model HQ-92) covers Channels 7 to 13.

**JERROLD ELECTRONICS CORPORATION**

**23rd and Chestnut Streets • Philadelphia 3, Penna.**

\*©Jerrold Electronics Deep Notch Adjacent Channel Trap

Let us once again look in on George Fleiback, who at the moment seems to have but one objective in mind—namely, the repair of a certain TV set which has already caused him one costly call back.

It may be well to briefly review the facts of the case before we proceed. Just the other day, George made a house call on this particular receiver and found the trouble to be loss of horizontal sync. The receiver, a 17" model about three or four years old, had no horizontal-hold control on the front panel, but there was a horizontal frequency adjustment on the rear of the chassis. George adjusted the horizontal frequency coil and the picture snapped into sync. He then changed the horizontal-oscillator tube and the picture went out of sync again. Since a glance at the code date on the old tube revealed it to be an original one, he left the new tube in the circuit and readjusted the frequency coil for proper synchronization of the picture. As an added check, he moved the channel selector switch off-station and back again, but the picture remained in sync. He also turned the set off for a few minutes and then back on—again the picture stayed in sync. Before leaving, he told the customer that he had replaced one tube and had made all necessary adjustments. The customer agreed that the set seemed to be in perfect working order.

The following day, however, our beloved serviceman received a phone call from the same customer. She complained that after the set was on for awhile the picture would go into lines just as before. The woman was very disturbed and rather rude over the phone, but George, remembering how he had felt when a \$20 motor tune up on the service truck had left it running worse than before, held his temper. He went right over and pulled the chassis after giving a brief explanation to the customer that the heat generated within the receiver was undoubtedly affecting some circuit component.

George hadn't as yet encountered many of these "dog" troubles in his somewhat limited serv-

**trouble shooting with GEORGE**

The Case of Mistaken Identity

by Leslie D. Deane

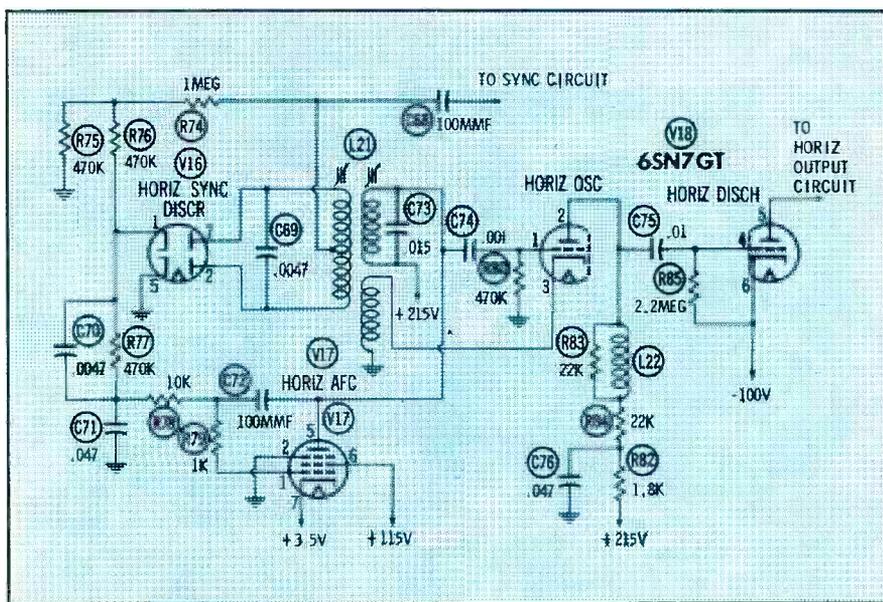


Fig. 1. Circuit diagram of the horizontal-sync stages in George's "tough dog" set.

icing career, and he wasn't too sure just where to begin. The customer had mentioned, however, that it took about 20 or 25 minutes before the trouble began. George naturally wanted to check the set while it was acting up, but there were other chassis on the bench that needed work. So instead of applying external heat to the chassis, he turned it on and let it cook. With George keeping an eye on the set, we are now up-to-date on the history of the case.

After the receiver had been in operation for about 30 minutes, George noticed that the picture was starting to drift out of horizontal sync. With his scope he checked the horizontal sync pulses at the input to the horizontal AFC circuit. The pulses appeared normal, so he figured the trouble must be the result of an unstable component in the horizontal AFC or oscillator stage. A circuit diagram for this section of the receiver is shown in Fig. 1.

# NEW MASTER VOLT<sub>OH</sub>MYST®

*Accuracy of  
±3% full scale  
on both AC and DC*



**RCA-WV-87B—offers many time-saving work-simplifying features for laboratory, production, servicing—can help improve the quality of your work!**

The WV-87B is housed in a durable metal case for general use around the service shop or the lab or for shelf- or rack-mounting on the production line. The unusually large meter face, clearly calibrated scales, and VoltOhmyst circuit permit extraordinary ease and speed in taking highly accurate readings. Helps you work better, faster, more efficiently. You can be positive of the measurements you take when you use the RCA Master VoltOhmyst.

RCA WV-87B Master VoltOhmyst—newest addition to the world-famous line of RCA superior-quality Test Instruments—is available through your RCA DISTRIBUTOR. Price \$137.50†. See him now for details and literature or write RCA, Commercial Engineering, Section L33W, Harrison, N. J.



**Radio Corporation of America**  
Components Division  
Camden, N. J.


#### Check these outstanding features:

- wide-vision open-face extra-large (7½") meter scale
- mirror-strip on scale to eliminate needle-to-scale parallax
- two-color, separate scales for speedy peak-to-peak and rms voltage readings
- work-simplifying single probe with built-in switch for all Ohms and DC/AC Voltage measurements
- high stability circuit free from effects of line voltage variations
- meter tracking error only ±1% or less
- accuracy of ±3% full scale on all AC and DC ranges
- DC current readings as low as 10 µa.

ELECTRICAL SPECIFICATIONS			
Operation	Ranges	Input R, C	Freq. Response
DC Volts	0 to 1500 (7 ranges) Low Scale, 0 to 1.5	*11 meg., 2 µmf	
AC Volts (RMS, sine waves)	0 to 1500 (7 ranges) Low Scale, 0 to 1.5	0.83 to 1.5 meg. 75 µmf to 85 µmf	30 cps to 3 Mc** (for source im- pedance of 100 ohms)
AC Volts (Peak-to-Peak values, sine or complex wave forms)	0 to 4200 (7 ranges) Low Scale, 0 to 4		
Direct- Current	0 to 15 a. (9 ranges) Low Scale, 0 to 500 µa		
Ohms	0 to 1000 megohms (7 ranges)		
MECHANICAL SPECIFICATIONS			
Height: 10"; Width: 13½"; Depth: 7"; Weight: 8 lbs.			

\*1100 meg. with WG-289 Probe and WG-206 Multiplier Resistor.  
\*\*Crystal-Diode Probe WG-301A available to extend range to 50 Kc to 250 Mc within ±10%.  
†User price (optional) Complete with WG-299C DC/AC-Ohms Probe, Low-Capacitance Flexible Cable, Current Leads, Ground Lead, Instructions.

have fun . . . save money

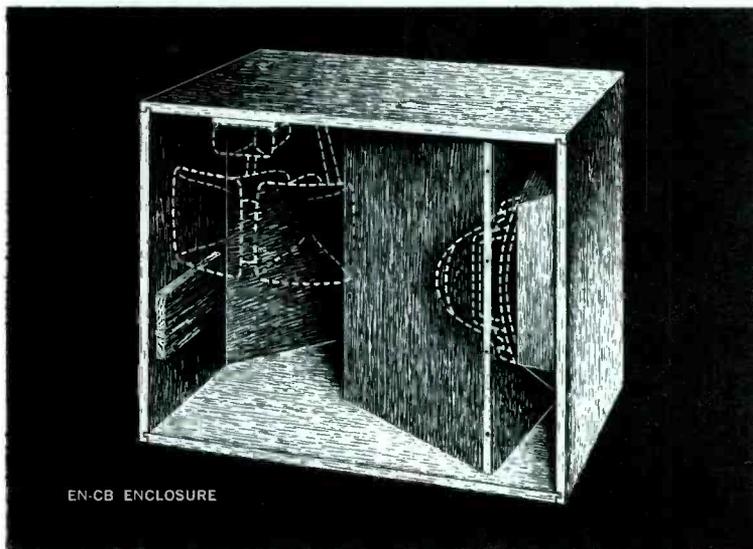

EN-CB ENCLOSURE

The famous University CLASSIC speaker system (shown at right), represents the highest achievement in audio engineering, the ultimate in sound! The CLASSIC is a true, folded, self-contained exponential horn which operates the woofer as a compression driver for maximum efficiency. Each detail has been so carefully worked out that the complete system functions as a beautifully coordinated team. A truly self-sufficient cabinet, it functions independently of walls and floor, achieving an amazing realism . . . almost like having a concert orchestra in your own home. The superb craftsmanship of the cabinet and high University standards to which the CLASSIC components have been built make the price really attractive. Mahogany \$450.00, Blond \$460.00.



## BUILD ONE OF THE FINEST SPEAKER SYSTEMS IN THE WORLD

University has taken the heart of the magnificent CLASSIC system and made it available as the EN-CB UNFINISHED-UTILITY enclosure. It came about as a result of an overwhelming demand on the part of "do-it-yourself" enthusiasts who wanted to build their own CLASSIC system. The price of the EN-CB is only \$120.00

The EN-CB is a superb piece of craftsmanship—constructed of Grade 1 Birch plywood using locked and mitred joints and braced with heavy glue blocks for maximum efficiency. Supplied with full instructions to mount speakers and network components. Designed acoustically to permit versatile use as "lowboy" or "highboy."

Naturally, all speakers sound better in an EN-CB. Recommended are CLASSIC components: C15W woofer, Cobreflex-2 mid-range horn with T-30 driver, HF-206 "Reciprocating-Flare" super-tweeter and N-3 ACOUSTIC BATON crossover network.

**The EN-CB is a boon to the home decorator** who plans to custom build part of his furniture. Decorating ideas are limitless: **BUILT-INS**—Easily installed into closet or wall, or into large wall-to-wall installations.

**ROOM-DIVIDERS**—Can be used vertically or horizontally.

**PICK A PERIOD**—Any furniture period can be achieved by treatment of front frame moulding, base, grille fabric, etc.

**CUSTOM FINISHING**—Can be stained and finished Blond, Mahogany, etc. Surface treatments: enamel, leather, formica, etc.

THE COMPONENTS THAT MAKE THE CLASSIC THE ULTIMATE IN SOUND



C15W



HF-206



COBREFLEX-2



T-30




N-3



BUILT-INS



ROOM-DIVIDERS

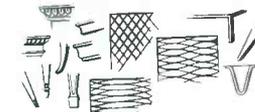

PICK A PERIOD



CUSTOM FINISHING

George checked the waveform on the grid of the oscillator stage, but with the oscillator out of synchronization with the incoming signal, he wasn't sure that this would give him anything to go on—and it didn't. He then decided to check all of the voltages in the circuits under suspicion. The readings he obtained offered no clue, for they were all within tolerance of those given in the service literature.

George noticed that when the frequency drifted he could correct it by adjusting the secondary slug of L21. He suspected the fault might be either in the AFC transformer or in one of the capacitors forming its tuned circuit. In this particular set, a .0047-mfd capacitor was connected across the primary of the AFC transformer and a .015-mfd capacitor across the secondary. Although it was against George's principles to change components without first determining the actual cause of a trouble, this set had him stumped, and he decided that a more direct method of approach was necessary.

He strongly suspected that the capacitor across the secondary of L21 was the cause of the trouble. This capacitor is identified as C73 in the circuit diagram of Fig. 1. George quickly scraped off some of the dirty wax from this component and found its rating to be .015 mfd at 600 volts. He had a .015 mfd, 600v capacitor in stock, so he replaced the part, turned the set on, and waited for results. Since the set was still warm, he assumed that the trouble would show up within a short time if this capacitor were not at fault.

It seemed to George that he had found the trouble because after 30 minutes of operation the horizontal sync remained stable. Ten minutes later, however, George was very disheartened. Yes—you've guessed it—the horizontal oscillator frequency had again started to drift.

Before calling in the FBI, George sat down and once again carefully examined all of the clues. He discovered his mistake—did you? Turn to page 61 for the simple solution of the baffling case. ▲

LISTEN


University sounds better



UNIVERSITY LOUDSPEAKERS, INC., 80 SOUTH KENSICO AVENUE, WHITE PLAINS, N. Y.
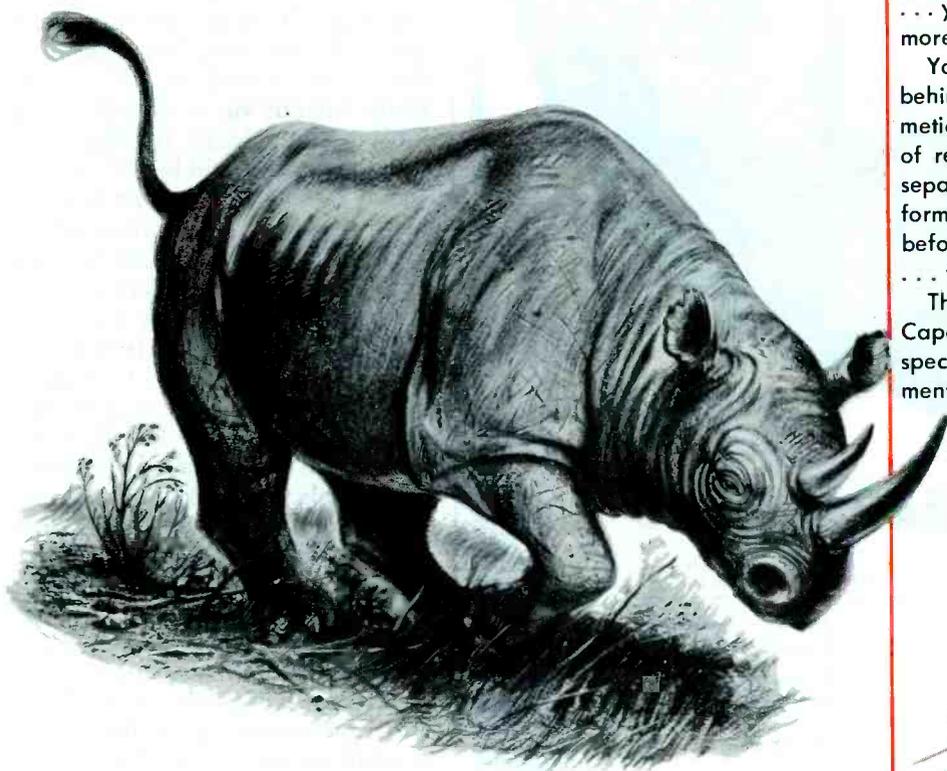
# ASTRON *"Staminized"* CAPACITORS ARE **rugged**

ASTRON CAPACITORS HAVE THAT BUILT-IN "NO-CALL-BACK" CONSTRUCTION!



Only the very finest of raw materials pass Astron's "Selected Purchasing System". Astron's special production techniques build extra rugged capacitors that create complete customer satisfaction . . . your key to repeat business and more profit.

You can put your trust in Astron, for behind each Astron capacitor is the meticulous quality control that insures you of real staying power . . . over 10 separate production line tests are performed, plus a 100% final inspection before any capacitor is sent out by Astron . . . your guarantee of top performance.

There is an Astron "Staminized" Capacitor built especially to fill the specific, exacting replacement requirements of any job you tackle.

### FREE Servicing Aid



Save time, use handy Astron pocket-sized Replacement Catalogue and Pricing Guide (AC-4D) — Write Today!



Safety Margin  
"SM" Minimate\*



Safety Margin  
"SM" Twist Prong



Safety Margin  
"SM" Cardboard Tubular



Blue-Point (R) Molded  
Plastic Paper Tubular

\*Trademark

# ASTRON

C O R P O R A T I O N

255 GRANT AVENUE

EAST NEWARK, N. J.



WEST COAST WAREHOUSE: 9041 WEST PICO BLVD., LOS ANGELES—EXPORT DIVISION: ROCKE INTERNATIONAL CORP., 13 EAST 40TH ST., N. Y., N. Y.—IN CANADA: CHARLES W. POINTON, 6 ALCINA AVE., TORONTO, ONTARIO

Pre-packaged,

with Lugs!



## AMPHENOL TWIN-LEAD HANKS

Part No.	Description	Available in Hanks of			
		25 ft.	50 ft.	75 ft.	100 ft.
214-318	Indoor—60 mil, 7/28 pure copper cond.	✓	✓	✓	✓
214-056	Standard—60 mil, 7/28 pure copper cond.	✓	✓	✓	✓
214-559	Steelcore—72 mil, 7/28 copperweld cond.		✓	✓	✓
214-298	Rotator—4 conductor—7/28 pure copper cond.		✓	✓	✓
214-100	Century—100 mil, 7/28 pure copper cond.		✓	✓	✓
Now Available in Coils					
214-271	Air-Core—U.S. Pat. 2543696 7/28 pure copper cond.		✓	✓	✓

takes the work out of selling!

Your selling job is easier with AMPHENOL Twin Lead hanks! AMPHENOL has done the cutting, lug-assembly (for greater customer satisfaction) and packaging, saving your time, eliminating waste and odd lengths at the end of spools. Now available in convenient 25, 50, 75 and 100 ft. lengths, AMPHENOL hanks are easy to handle—and even easier to sell.

Increase your sales and increase your profits by displaying America's largest selling hanks!

*make your selling job easier—*

STOCK & DISPLAY AMPHENOL HANKS!



## TV Sound From 6DT6

(Continued from page 19)

varies during reception of an FM signal. When a 4.5-mc sound IF signal is applied to the limiter grid of the 6BN6, a similar signal reaches the quadrature grid through space-charge coupling which exists between the plate-current beam and the grid. As a result of the continual frequency changes of the 4.5-mc FM signal, the signal developed across the quadrature grid circuit undergoes a variable phase shift with respect to the input signal.

In summary, the action is as follows. When the incoming signal is at the center or resonant frequency—that is, unmodulated—the voltage induced on the quadrature grid through the capacitive space-charge coupling will lag the beam current by 90°. Since beam current varies directly with limiter-grid voltage, the signal on the quadrature grid lags the input signal by 90°. As long as there is no modulation, the phase angle between these two signals does not change and the average plate current remains at a constant value. At the resonant frequency, the reactances of the two components in the tank circuit are equal and will have no effect on the phase relationship between the signals. Refer to Fig. 3A and note that plate current will flow only during the time that the voltages on both grids are above cutoff level. (An arbitrary value of cutoff level is shown in Fig. 3 for the purpose of illustration.)

On positive swings of modulation, the input signal frequency rises above resonance. This causes the quadrature-grid voltage to lag the input voltage by some angle greater than 90° because the capacitive current in the tank circuit increases while the inductive current decreases. The angle of lag is proportional to the amount by which the frequency deviates from resonance. Since the lag is abnormally great, the positive half cycles of the signals on the two grids coincide for a shorter-than-normal interval. Fig. 3B shows that the "gates" are opened for a briefer interval than they are under the condition depicted in Fig. 3A. As a result, the average

## PRODUCTION TECHNIQUES:

# for the manufacturing of High Reliability Capacitors

To produce capacitors free from any possibility of latent defects, for use in the most critical applications, the Sangamo Electric Company has recently intensified its high reliability program of fabrication and inspection methods.


Incoming materials are rigidly inspected to meet stringent high reliability standards and are stored in areas where temperature, humidity and dust are controlled at all times.

Complete production histories are kept on the basis of small capacitor lots. X-raying of individual units, heat tests, vibration tests, altitude tests, and total destruction tests of a given percentage of all finished units assure components with an extremely low AQL. Testing facilities and resultant performance characteristics are far in excess of military specifications. Specify these high reliability capacitors for your critical applications.

**SANGAMO ELECTRIC COMPANY**  
MARION, ILLINOIS



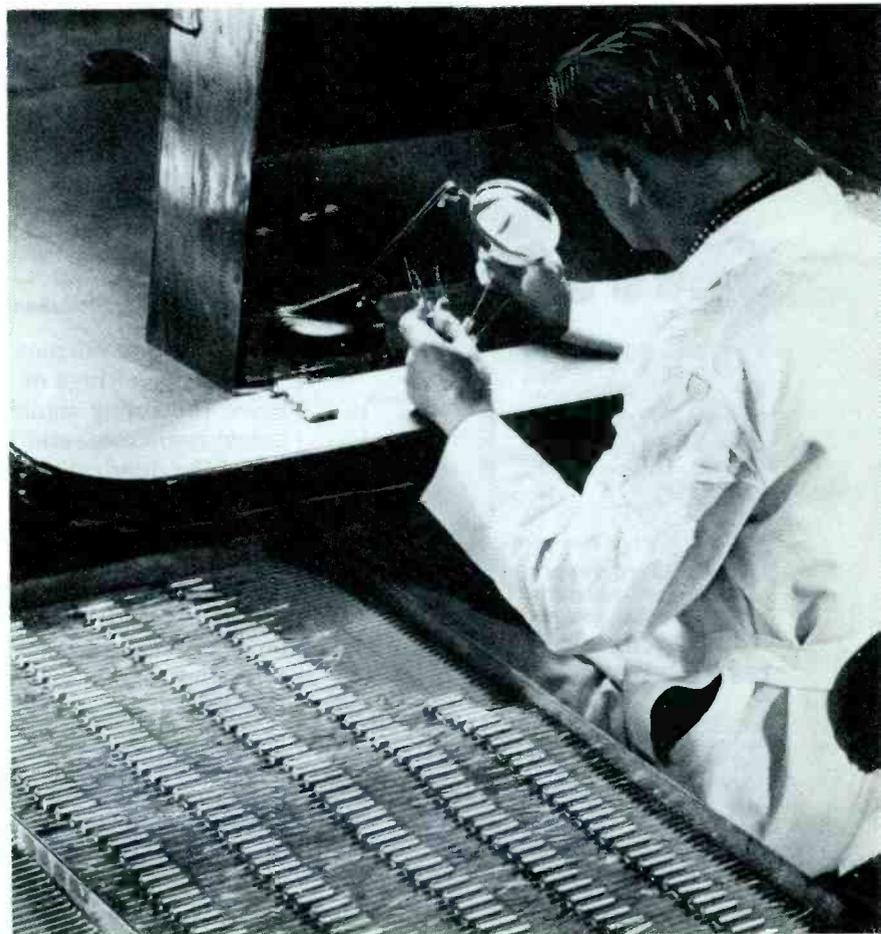Separate facilities are maintained for the exclusive processing and manufacture of high reliability capacitors. Only specially trained, highly skilled operators, who wear special clothing to prevent any possible source contamination, work here.



Oil-filled capacitors are subject to vacuum under elevated temperatures, then are individually examined to insure complete hermetic seal.



High temperature test ovens are used to check insulation resistance of Sangamo high reliability capacitors under sustained temperatures of 125° C.

This vibration testing machine brutally punishes Sangamo high reliability capacitors at accelerations up to 10 G's to determine their ability to resist vibration without damage to leads or elements.

SC56-2




# YOU BUILD EICO KITS IN ONE EVENING BUT THEY ... LAST A LIFETIME AND YOU SAVE 50%



New #480 Color & Black-&-White Wide Band 5" Scope Kit \$79.95 Wired \$129.50



425K 5" Scope Kit \$44.95 Wired \$79.95

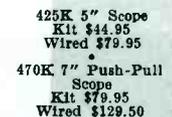

470K 7" Push-Pull Scope Kit \$79.95 Wired \$129.50



291K VTVM Kit \$25.95 Wired \$39.95

New 324K RF Signal Gen. Kit \$26.95 Wired \$39.95



150 kc - 435 mc; 6 fund. bands.

50 MODELS TO CHOOSE FROM! - THE INDUSTRY'S MOST COMPLETE LINE OF

## MATCHED TEST INSTRUMENTS

1/2-million EICO Instruments are now in use the world over! That's the proof of EICO's leadership in Value.

For latest precision engineering, finest components, smart professional appearance, lifetime performance and rock-bottom economy—see and compare the EICO line at your Jobber before you buy any higher-priced equipment! You'll agree with over 100,000 others that only EICO Kits and Instruments give you the industry's greatest values at lowest cost.

Write NOW for FREE latest Catalog PF-12

Prices 5% higher on West Coast

377K Sine & Square Wave Audio Gen. Kit \$31.95 Wired \$49.95



1050K Battery Elim. Kit \$29.95 Wired \$38.95



625K Tube Tester Kit \$34.95 Wired \$49.95

• Tests new 600 ma series string type tubes



©56

84 Withers Street, Brooklyn 11, N. Y.

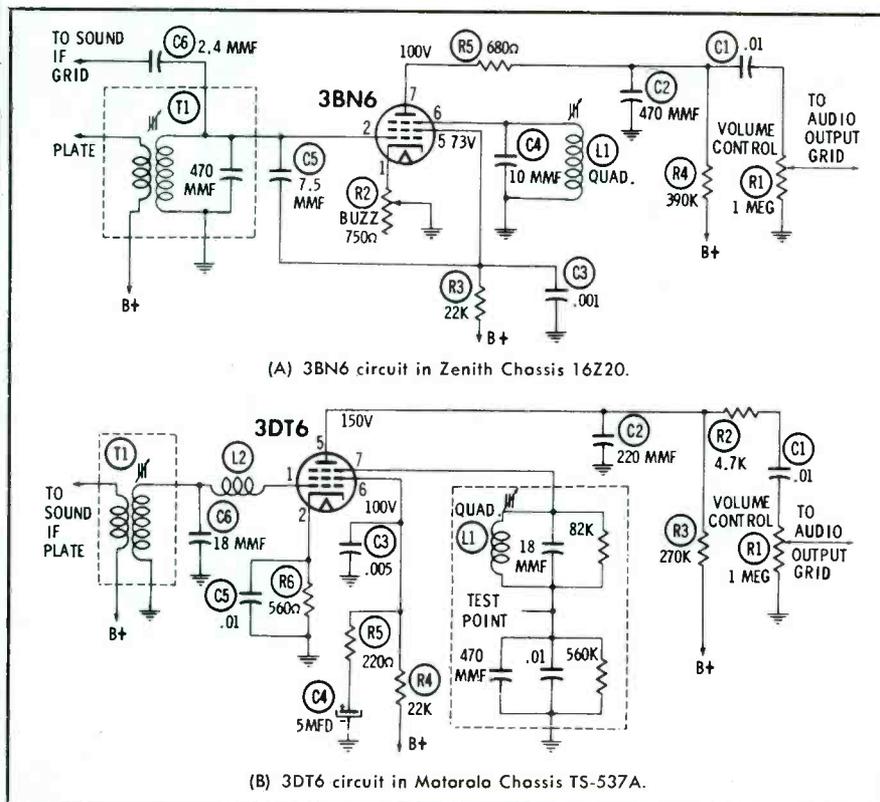


Fig. 2. Schematic diagrams of quadrature-grid detectors.

value of plate current is reduced.

Negative swings of modulation drive the input signal frequency below resonance, and the angle of lag of the quadrature-grid voltage is reduced to less than 90°. Since the signals on the two grids are more nearly in phase than they were under conditions of no modulation, the gates stay open for a longer period and more plate current flows. This is illustrated in Fig. 3C.

The signal in the plate circuit of the 6BN6 consists of pulses having a repetition rate of 4.5 mc, but modulation is present in the form of varying widths of the pulses. The 4.5-mc component of the signal is bypassed from the plate to ground, and the pulse-width changes are translated into an audio-frequency voltage which has an amplitude of approximately 15 volts rms. This output is sufficient to drive directly a power amplifier tube such as a 6AQ5.

The 6BN6 detector includes a buzz control located in the cathode circuit of the tube. This control is used to adjust the tube bias so that the incoming signal will drive the limiter grid into both saturation and cutoff, thus resulting in effective limiting of amplitude modulation.

### Operation of 6DT6 Circuit

The first locked-oscillator detector which we have examined is used in the Motorola Chassis TS-537A, shown schematically in Fig. 2B. Notice that a 3-volt, series-string counterpart of the 6DT6 is used. In the following discussion, as in the description of the 6BN6, the difference in filament voltage will be ignored because it does not affect detector operation.

The similarity between the 6BN6 and 6DT6 circuits can be clearly seen in a comparison between the two parts of Fig. 2. The most obvious difference is that the locked-oscillator detector lacks a buzz control.

Although it is not apparent in the diagram, the 6DT6 is not as complex in construction as the 6BN6. It is very much like an ordinary pentode except that the control and suppressor grids are both able to effect sharp-cutoff of plate current. During reception of moderate or strong signals, quadrature-grid detection takes place much the same as it does in the 6BN6 circuit except that there are a few differences in limiting action.

The locked-oscillator mode of operation of the 6DT6 circuit does not come into play until the input

# Free!

## to Service Technicians Only

### THE NEW SAMS INDEX TO PHOTOFACT FOLDERS

it keeps you up-to-the-minute on receiver coverage

PHOTOFACT Folders give you the world's finest Service data on TV and radio models just as soon as they hit the market. Now—with the new INDEX SYSTEM to PHOTOFACT, you locate the *latest* PHOTOFACT coverage *immediately*.

If you're a Service Technician, you can get the new Sams Index FREE. Here's how it keeps you up-to-date on receiver coverage: The Master Index (36 pages—issued twice yearly) is the complete reference to *all* PHOTOFACT Folders produced up to the date of its issue. In addition, you get an Index Supplement each month covering that month's releases of PHOTOFACT Folders. Thus, the Master Index *plus* the supplements keep you right up with *current* PHOTOFACT coverage. (The Index Supplements also appear each month in "PF Reporter" Magazine.)

It's easy to get your complete Index service to PHOTOFACT at NO COST TO YOU. If you're a Service Technician, just fill in the coupon and mail to us today. It will bring the Master Index direct to your shop, and monthly supplements will be mailed to you regularly thereafter. YOU'LL KEEP RIGHT UP-TO-THE-MINUTE ON PHOTOFACT COVERAGE—you'll be able to locate the data you need on over 30,000 models, as well as on CURRENT MODEL RELEASES.

Mail coupon today for your free subscription to the Sams Photofact Index

**HOWARD W. SAMS & CO., INC.**

**free!**  
TO SERVICE  
TECHNICIANS

Howard W. Sams & Co., Inc.  
2201 E. 46th St., Indianapolis 5, Indiana

Send me your FREE Master Index to PHOTOFACT Folders (twice yearly), and put me on your mailing list to receive all Index Supplements. My letter-head and/or business card is attached.

I am a Service Technician:  full time;  part time.

My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_


Attn: \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

TAKE THE RIGHT STEP TO TIME-SAVING PROFIT-BUILDING BUSINESS: Sign up with your Parts Distributor to get PHOTOFACT Folder Sets automatically each month.


**DO IT NOW!**

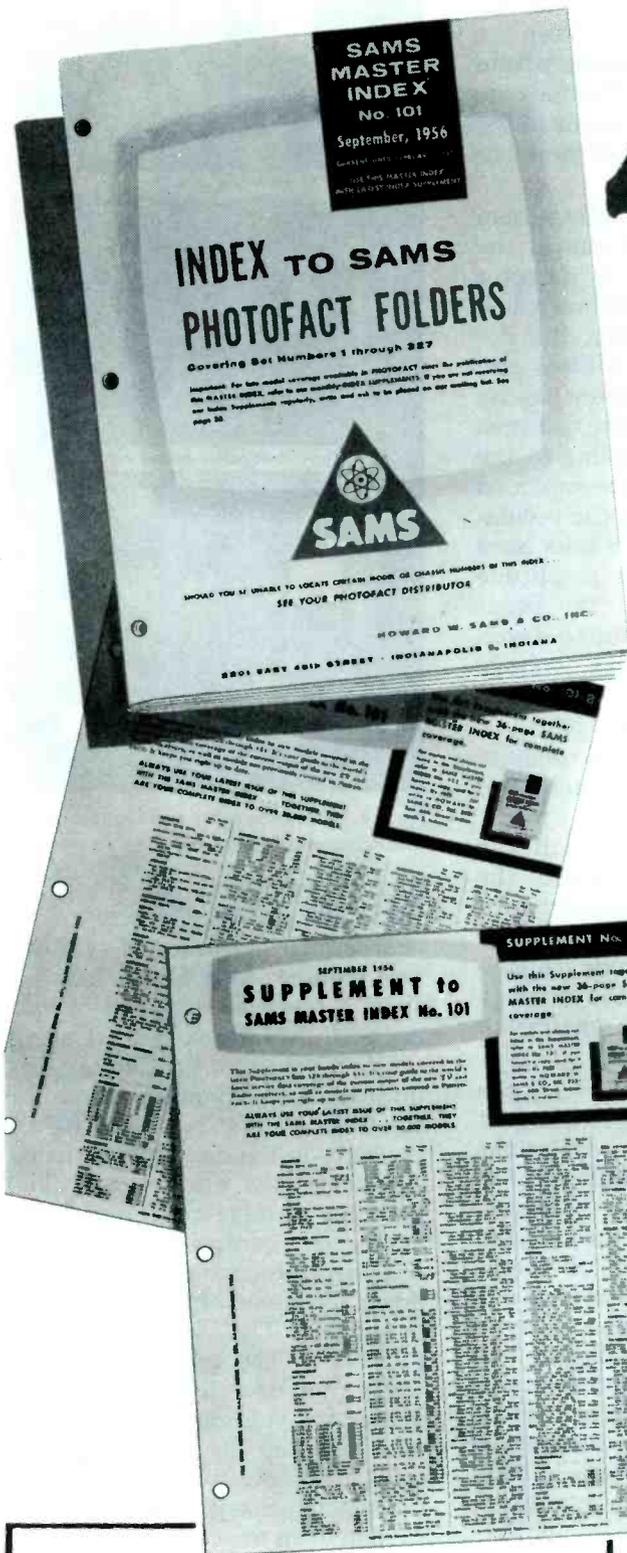

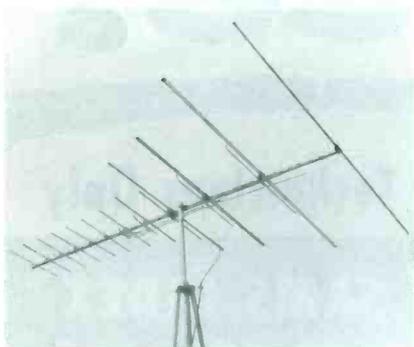
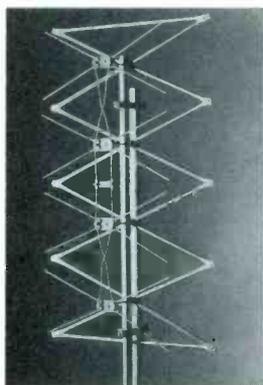
### POWERFUL FRINGE AREA VHF ANTENNA


- \* Completely factory assembled on boom, with quick-rigging that strengthens rather than weakens.
- \* Re-inforced at all stress points, double-wall thickness boom.
- \* New one-piece dipoles pre-attached to the boom.
- \* Superb quality all-aluminum construction.
- \* One of our vhf antenna line is just right for your area.



ARE YOU LOOKING FOR QUALITY ALL-ALUMINUM UHF ANTENNAS?

Pictured are two new antennas that give really "hot" UHF reception

- ◀ Model U-Z1
- ▼ Model U-Z2

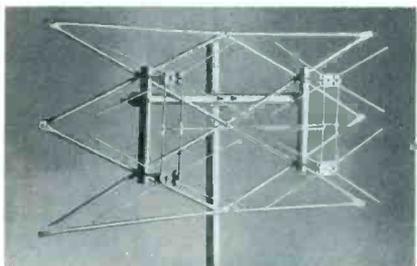

### THE SIX L-S UHF MODELS FEATURE

- Quality construction found in no other uhf line.
- Low wind resistance.
- ALL-aluminum riveted construction.
- Moderately priced.

DISTRIBUTORS: Your inquiries will receive our prompt attention.



signal becomes fairly weak. Below a certain signal amplitude, the detector will break into a 4.5-mc oscillation. This tends to keep the signal amplitude constant within the detector in spite of amplitude variations which may occur in the input signal because of noise or fading.

The input signal voltage can drop as low as 1/3 volt rms at the secondary winding of the detector input transformer without a loss of oscillation. Normally, the signal generated in the control grid circuit by the oscillation has an approximate value of one volt rms. The space-charge coupling to the quadrature grid is accompanied by a voltage gain, and the oscillations in the quadrature tank have about three times the amplitude of the oscillations in the input circuit. This is sufficient to develop the required bias voltage across the 560K-ohm resistor in the quadrature circuit.

The circuit is able to oscillate because of positive feedback from the quadrature-grid circuit to the control-grid circuit through the interelectrode capacitance of the tube. A similar arrangement cannot be set up using a 6BN6 because the interelectrode capacitance of that tube is too small to provide the required amount of feedback.

The "locked" feature of the 6DT6 oscillator refers to the fact that the phase of the oscillations in the control-grid circuit will follow the phase of the incoming sound-IF signal. During the locked-oscillator mode of operation, the input signal serves as not much more than a type of sync signal having little amplitude but yielding frequency information. Normal quadrature-grid detection takes place in the oscillating detector, and the process is kept under the control of the input signal at all times. The oscillation boosts the weak-signal sensitivity of the quadrature-grid circuit so that its performance becomes comparable to that of a ratio detector. Clear sound can be received even when the station signal is so weak that the picture is not fit to watch.

We have mentioned that limiting of strong signals is accom-

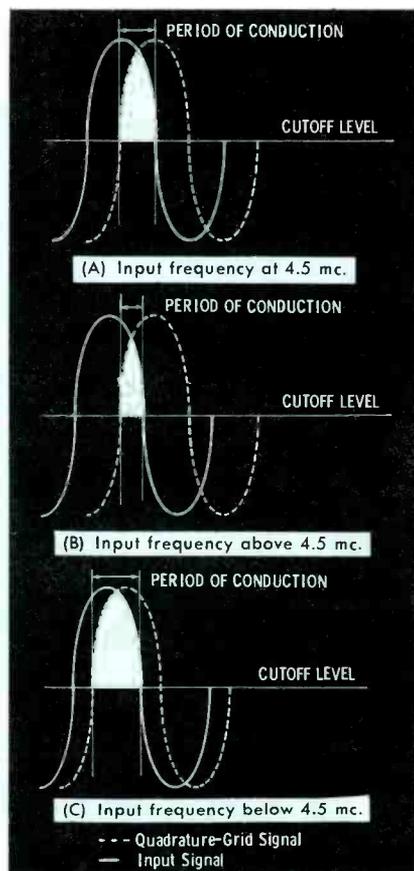


Fig. 3. Plate-current conduction in a quadrature-grid detector.

plished somewhat differently in the 6DT6 and 6BN6 circuits. The characteristic curve of control grid voltage of the 6DT6 does not show a rapid leveling out or saturation of plate current at small positive values of grid voltage, as does the corresponding curve for the 6BN6. Limiting in the 6DT6 depends on the damping of strong signals in the grid circuit. The presence of a strong input signal causes the control grid to draw considerable current which loads down the tuned circuit connected to the grid. The oscillation is suppressed by the grid loading, the tuning of the input circuit is broadened out, and the peak voltage swing at the grid is held to only a few volts.

Degeneration of audio-frequency signals in the cathode circuit of the 6DT6 also contributes to limiting. The value of cathode resistance required in the 6DT6 circuit for best AM rejection is not critical, and no control is needed in the cathode circuit.

#### Alignment of 6DT6 Detector

The alignment procedure for the 6DT6 detector is simple and

can be carried out with a sound signal from a station. The first step in alignment is the tuning of the quadrature coil. This should be done while a strong signal is being applied to the detector so that the locked oscillation will be suppressed. Since the tuning of the input circuit is broadened under strong-signal conditions, the setting of the quadrature coil will not be affected by a slight misalignment of the input transformer.

The quadrature coil is adjusted for a maximum VTVM reading—about 5 volts—at the test point in the quadrature circuit. If more than one peak of voltage is obtained, the coil should be tuned to the higher peak to get the correct bias for the quadrature grid.

During the remainder of the alignment procedure, the input signal should be reduced to such a small amplitude that noise can be heard in the sound. While it may take some ingenuity to obtain a weak enough signal to perform proper alignment in metropolitan areas, if a stronger signal were used, the adjustments would become far too broad to be made with any degree of accuracy. To obtain a weak signal, a step attenuator might be used between the antenna and the receiver, or the antenna might be disconnected or the RF amplifier tube removed.

The weak-signal part of alignment consists of tuning the detector input transformer and the sound-IF takeoff coil for maximum signal output with minimum noise. On one side of the correct setting, the volume does not fall off but the noise increases; and on the other side, volume and noise both gradually fade away.

It should now be evident that the alignment of the 6DT6 circuit is generally similar to that of the 6BN6 circuit, except for the use of a strong signal during part of the 6DT6 alignment.

The locked-oscillator detector is expected to appear in several makes of 1957 television receivers. There will be some variations in component values to allow for such factors as different B+ voltages, but the various 6DT6 circuits will have a fairly close resemblance to the one which has been described here. ▲

**NEW**

# PHAOSTRON PROBE-LITE

**ILLUMINATED TEST PROBE  
SELF-CONTAINED  
SEE WHAT YOU ARE TESTING!**

**\$250**  
LIST



It is just like having an extra hand. Simply insert the probe from your tester into the jack of the Probe-lite and the Probe-lite becomes alive to instantly give you a brilliant, pre-focus spot-light on the area that you are testing plus a long, extra slender, probe tip for making electrical contact in difficult places which previously were inaccessible. It could pay for itself the first time you use it. Hurry, call your distributor today!


**PHAOSTRON**

PHAOSTRON INSTRUMENT & ELECTRONIC CO., 151 Pasadena Avenue, South Pasadena, Calif.

# Product Report



## KNOBS FOR CLOCK RADIOS

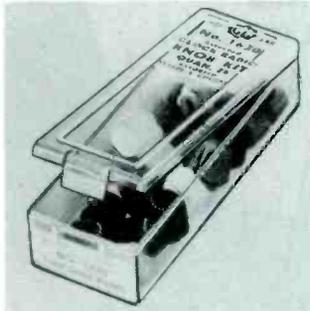

An assortment of 25 knobs for clock radios is included in kit No. 1630, sold by Gee-Lar Mfg. Co. (Division of General Cement-Textron, Inc.), 400 S. Wyman St., Rockford, Ill. Gold-finished metal knobs of the double-barrier type and three styles of plastic knobs (single-barrier, double-

barrier, and spring) in six colors are supplied in the kit. The knobs are packed in a transparent plastic box. List price is \$3.75.

## VARIABLE VOLTAGE TRANSFORMER




A compact, low-priced auto-transformer, designed to supply a variable AC voltage to electronic and electrical equipment, has been introduced by Standard Electrical Products Co., Dayton, Ohio. The auto-transformer is toroidally

wound and is enclosed in a case measuring only 3 7/8" x 3 1/2".

The Model PA-1 variable transformer converts a 120-volt line voltage into any desired output voltage from 0 to 132 volts AC. The companion Model PA-1L has a range of 0-120 volts output for 120 volts input. Maximum output current for both transformers is 1.25 amperes.

## TV-FM SET COUPLER

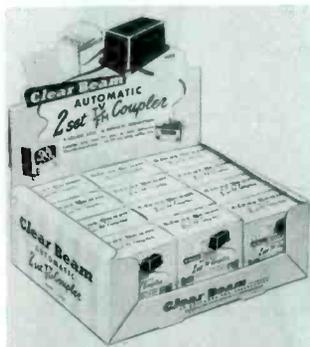

Clear Beam Antenna Corp., 21341 Roscoe Blvd., Canoga Park, Calif. is marketing a two-set coupler especially designed to supply signals to both a TV set and an FM receiver from the same all-channel VHF antenna with minimum interaction between the two tuners. Incoming FM radio signals are filtered out of the TV set input

and are fed to the FM tuner.

The Model FM-TV 2SC coupler is suitable for either indoor or outdoor mounting. Retail price is \$3.95.


## PRINTED CIRCUIT REPAIR KIT



Now being displayed by parts jobbers is the Master Printed Circuit Repair Kit packaged by Walsco Electronics Corp., 3225 Exposition Place, Los Angeles, Calif. Included are copper foil with a thermoplastic backing, solder, tweezers,

a fiber glass brush, silicone resin spray lacquer and solvent, a "Solder-Ease" tool, a pencil-type soldering iron, and a wiring board to practice on. Dealer net price is \$7.95. A smaller kit without the soldering iron, lacquer, and practice board is \$4.95.

## QUICKLY INSTALLED CONICAL ANTENNA

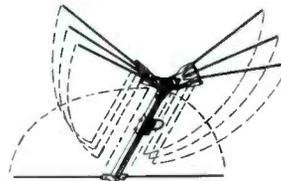


Telrex Labs., Asbury Park, N.J., has introduced the "Quickie," a conical V-beam antenna designed to be low-priced, durable, and easy to install. The antenna is of all-aluminum construction

with doweled tubular elements that can be swung out and locked into the correct position.

List prices for "Quickies" are \$9.05 for the Q-2X single-bay model; \$19.30 for the Q-4X having two stacked units; and \$42.25 for the Q-8X four-bay model.

## COMMUNITY TV CABLES

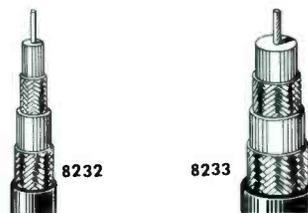

Two new types of coaxial cables for community TV antenna systems have been added to the line of electronic wire and cable made by Belden Mfg. Co., Chicago, Ill. These new double-jacketed and double-

shielded cables are designed for low losses, flat frequency response over the television band, and a minimum of line radiation.

Cable No. 8232 is recommended for tap-off lead-ins, and the larger cable, No. 8233, is for use in secondary leads.


## SOLDERLESS CABLE CONNECTORS



Two new solderless connectors for coaxial cables are now being supplied by Blonder-Tongue Labs., 526-536 North Ave., Westfield, N. J. Model P-11S connector fits RG-11/U cables,

while the Model P-59S is for RG-59/U cables.

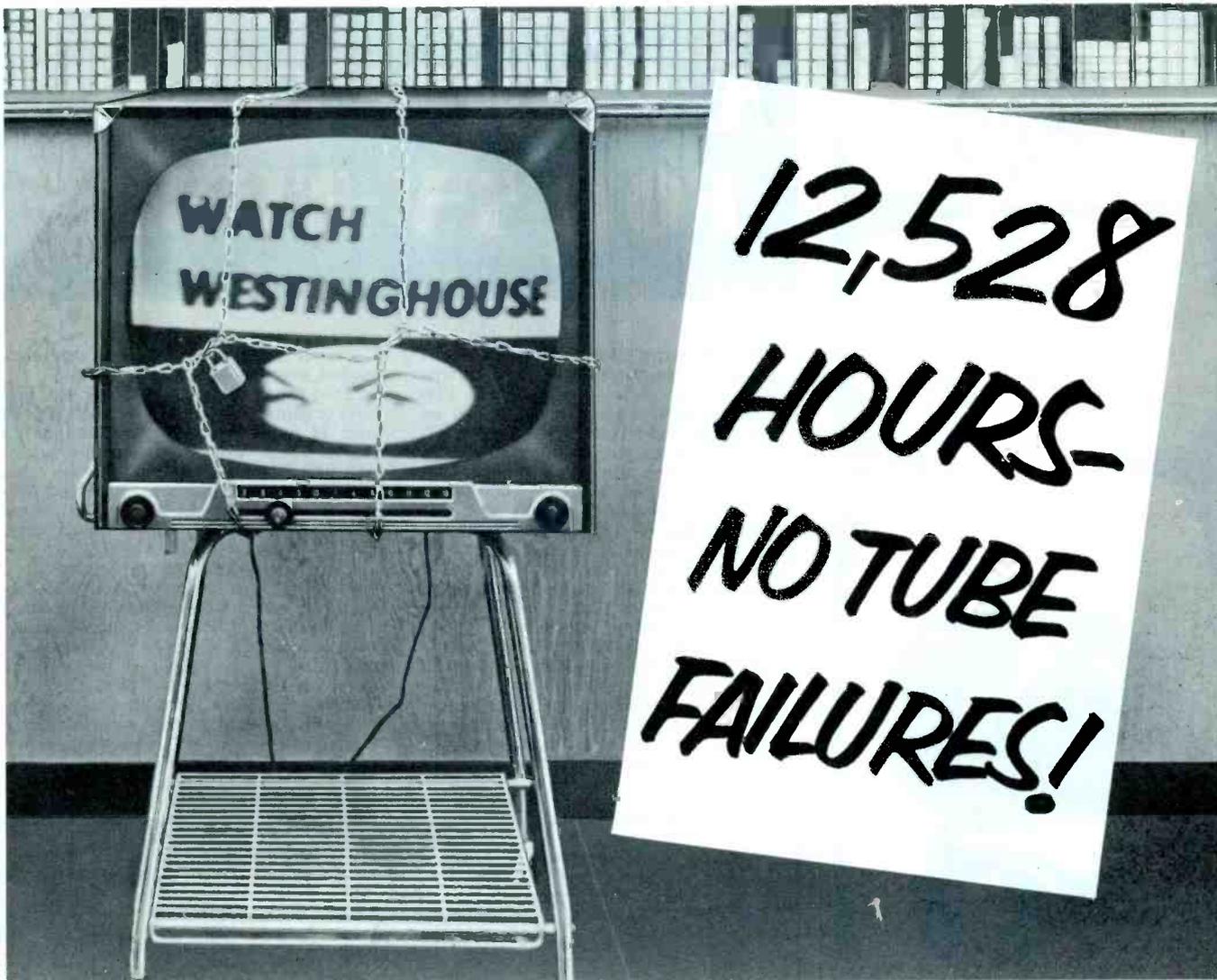No special tools are required for installation. A two-step thread clamps the outer jacket of the cable and grounds the shield, and an easily inserted tubular spring locks the center conductor to insure positive electrical contact.



At the Lew Bonn Company, lock and chain are still on this now-famous TV set. And the total useful life of its Westinghouse RELIATRON Tubes is still to be discovered.

## Westinghouse 12,000-hour Locked-TV Marathon Shows how "Pre-Ship" tube test cuts call-backs

On April 25, 1955, the Lew Bonn Company set out to demonstrate the superior performance of Westinghouse RELIATRON® Picture and Receiving Tubes . . . and to prove the benefits of the Westinghouse policy of testing every tube in the warehouse *before final shipment!* They started one of the most amazing marathons in years!

A TV set, chained and locked, was put on display in the showroom of the Lew Bonn Company, Minneapolis. The set was equipped completely with Westinghouse Reliatron tubes—all taken right from stock!

Here's what happened: at first check, 5,472 hours later, all tubes were reported perfect. At second check, 8,784 hours (or over *six years'* viewing time) later, still no failure! After 9,144 hours, still perfect! Now the tubes have chalked

up 12,528 hours—and *they're still going strong!*

*What made possible this superior tube performance?* Westinghouse manufacturing quality, for one thing! For another, PRE-SHIP TESTING . . . rigorous, six-step testing of tubes for shorts, open circuits, excessive gas, loose mounts, defective glass, and bad seals—all the common causes of call-backs—all done at the local warehouse, *just before the tubes are shipped to your distributor!*

This unique testing policy is insisted upon by Westinghouse as the only way of assuring quality-perfect tubes every time . . . the best way to eliminate costly call-backs, win customer confidence. Stock up on Westinghouse tubes—"pre-ship tested" to guarantee dependability and top performance. Call your Westinghouse distributor today!



**WATCH WESTINGHOUSE**  
WHERE **BIG THINGS** ARE HAPPENING FOR YOU!

6ET-4115



another  
EXACT  
REPLACEMENT  
first



MDF-79 for exact replacement in over 50 Motorola models and chassis; equipped with plug. Another in the complete line of exact transformers, yokes and coils. Merit is the only manufacturer of transformers, yokes and coils who has complete production facilities for all parts sold under their brand name.

**MERIT**

MERIT COIL AND TRANSFORMER CORP.  
4427 N. CLARK ST., CHICAGO 40, ILLINOIS

# A STOCK GUIDE FOR TV TUBES

The following chart is presented as a guide for the maintenance of an up-to-date stock of television tubes. The figures in this chart are expressed as proportions based on a total of 1,000 tubes. For example, if the figure 6 is given for a particular type of tube, this means that six out of every 1,000 tubes in television receivers which are now in service are of that type. The minimum entry in the chart is 1 per 1,000. Tubes which are used less frequently than this are listed only if they have special applications in UHF or color receivers or if they have recently been placed on the market. A cumulative record of the tubes which appear in new models of receivers is kept for the compilation of this chart. The figures which are obtained are adjusted to take into account the quantities of production of different models and the re-

tirement of old receivers at an estimated average age of six years.

Two separate listings are given. The first column of figures is labeled '46-'56 and is for the use of technicians in areas where television stations began operation before allocations were frozen. The second column is labeled '52-'56 and is meant to be used in areas which had no TV service until after the freeze was lifted in 1952.

The listing of a large figure for a particular type of tube is not necessarily a recommendation for stocking that number of tubes. (Some consideration should be given to the frequency of failure of the tube.) A large figure does indicate, however, that the tube is used in many circuits and emphasizes the necessity for maintaining a sufficient stock to fill requirements between regular tube orders.

TUBE TYPES	46-56 Models	52-56 Models	TUBE TYPES	46-56 M9dels	52-56 Models	TUBE TYPES	46-56 Models	52-56 Models
c1B3GT	42	43	6AT8	1	1	c6DC6	-	-
1X2	3	1	c6AU4GT	3	3	6DE6	2	2
1X2A	3	4	6AU5GT	3	3	6J5	3	2
c1X2B	3	3	c6AU6	109	102	c6J6	27	25
#2AF4	-	-	6AUB	1	2	6K6GT	12	8
#2AF4A	-	-	6AV5GT	2	3	6S4	8	9
c3A2	-	-	c6AV6	15	17	c6S4A	-	-
c3A3GT	1	1	6AW8	3	3	6SH7GT	1	-
3AL5	2	1	c6AX4GT	13	13	6SL7GT	2	2
3AU6	1	1	c6AZ8	-	-	c6SN7GT	68	62
3BC5	1	1	c6BA6	11	8	c6SN7GTA	8	8
3BN6	2	2	6BC5	8	6	6SN7GT8	4	4
3BZ6	1	1	c6BC7	-	-	6SQ7	2	2
3CB6	6	6	c6BD4A	-	-	6SQ7GT	2	2
4BQ7A	1	1	6BE6	6	7	#c6T4	1	1
5AQ5	1	1	c6BG6G	9	4	c6T8	13	13
c5U4G	40	42	6BH6	5	-	c6U8	15	17
5U4GA	2	2	c6BJ7	-	-	6V3	2	2
5U4GB	2	2	c6BK4	-	-	c6V6GT	17	16
5U8	3	3	c6BK5	3	3	6W4GT	21	21
5V4G	5	-	6BK7	2	4	6W6GT	7	11
c5Y3GT	3	2	c6BK7A	3	3	c6X8	7	8
6AB4	2	2	c6BL4	-	-	6Y6G	2	-
6AC7	5	5	c6BL7GT	4	6	7AU7	1	1
c#6AF4	4	4	c6BN6	8	6	7N7	1	-
#6AF4A	-	-	6BQ6GA	2	2	c12AT7	11	10
6AG5	22	6	6BQ6GT	15	21	c12AU7	41	32
c6AG7	2	2	6BQ7	4	9	12AU7A	2	2
c6AH4GT	3	4	c6BQ7A	8	8	c12AV7	2	2
c6AH6	7	7	c6BY6	2	2	12AX4GT	2	4
6AK5	3	2	6BZ6	2	2	12AX4GTA	2	2
c6AL5	68	69	c6BZ7	8	4	12AX7	4	5
6AL7GT	4	-	c6C4	9	8	12AZ7	-	1
c6AMB	3	3	c6CB5	-	-	12B4A	1	1
#6AN4	-	-	c6CB6	106	135	c12BH7	10	13
c6AN8	7	7	c6CD6G	9	2	12BH7A	1	1
c6AQ5	14	14	6CF6	1	1	c12BY7	8	9
6AQ7GT	2	2	6CG7	2	2	12BY7A	1	1
6AS5	2	3	c6CL6	3	3	12BZ7	2	-
c6AS6	-	-	c6CS6	3	3	12CU6	1	1
6AT6	3	3	c6CU6	3	3	12L6GT	2	2
						12SN7GT	4	4
						25BQ6GT	-	4
						25L6GT	4	5
						25W4GT	-	1
						5642	1	-
						c6505	-	-

#A stock of these tubes should be maintained in UHF areas.

\*New tubes recently introduced.

cThese tubes have been used in color television receivers.

**You're Ready  
for any Service Job**

with

**JACKSON**

*"Service Engineered"  
Test Equipment*



**TVG-2  
Sweep  
Marker  
Generator**

Dealer Net \$259.95

A complete TV generator plus crystal calibrator. Sweep 30KC through 216MC. Width adjustable from 0 through 18MC. Accurate Marker 4MC through 216MC. Crystal oscillator for frequencies to 20MC. Provision for Video Modulation.

**CRO-2  
Wide Band  
High Sensitivity  
5-inch Scope**



Dealer Net \$225.00


Flat within 1 db from 20 cycles through 4.5MC. Sensitivity from .018RMS volts per inch. Positive or Negative internal horizontal sync. Saw tooth sweep 20 cycles through 50KC. Many accessories including low capacity probes.



**Model 655  
Wide Range  
Audio Oscillator**

Dealer Net \$135.00

Highly stable RC sine wave generator. Range 20 cycles to 200 kc in 4 steps. Up to 500 milliwatt output at impedances of 10, 250, 500, 5000 ohms or HiZ. Frequency characteristic 1db., 30 to 15k cycles. Accuracy 3% or 1 cycle.

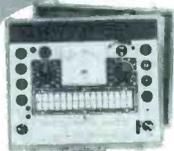

**Model 648A  
Dynamic®  
Tube Tester**

Dealer  
Net \$129.95

Fastest tester on the market—and featuring famous Jackson Dynamic Circuit. Meter calibrated in Good-Bad, as well as percent Transconductance. Correct test voltage for all tubes including latest 600-mil types. Line Voltage Indicator.

**JACKSON**  
ELECTRICAL INSTRUMENT CO.

World's largest exclusive makers of  
factory-built service test equipment.

16-18 S. Patterson Boulevard • Dayton 2, Ohio  
In Canada: The Canadian Marconi Co.

## Printed Wiring

(Continued from page 23)

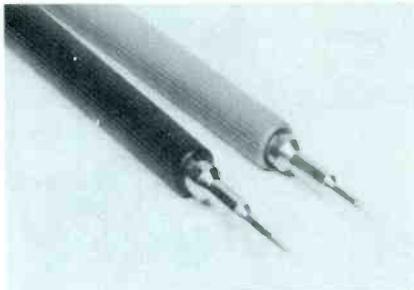


Fig. 3. Needle-pointed test leads.

saved in not having to look for ready-made points.

### Voltage and Resistance Measurements

The lugs on terminal strips and tube sockets in a conventionally-wired receiver provide relatively large contact surfaces for test leads. The probe tips of instruments can be placed against these lugs and little trouble will be experienced with the tips slipping off.

Printed wiring boards have terminal points which are usually small, slightly-rounded areas of solder. Tube-socket lugs are either passed through a conductor or bent over a conductor and soldered. This results in no large contact areas, and probes with ordinary tips can slip off the test points. To help overcome this slight difficulty, sharp points may be filed on existing test probes or new needle-pointed probes may be obtained. A set of test leads with needle points is shown in Fig. 3. Since the ground or common leads

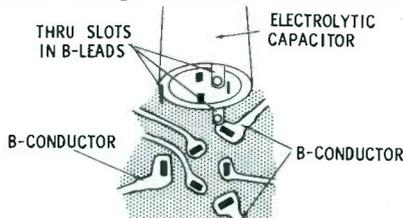


Fig. 4. Metal body of electrolytic filter capacitor used in B— circuit.

of many meters are equipped with alligator clips, it may be desirable to fasten a small loop of wire to the common bus as mentioned previously.

In servicing conventional chassis which use wires and terminal strips, it is often the practice to clip off or unsolder component leads at tube sockets in order that resistance checks may be made. Also, components are sometimes

**"Anyway you look at it  
... this is DYNAMIC!"**

SATIN BRASS, SATIN COPPER and SATIN CHROME FINISHES.

**\$18.95** List

**Beautiful!**

T. M. REG. Patents Pending.

**FILTER**

The first truly Electronic indoor TV Antenna to give you clear filtered reception ... with the **EXCLUSIVE** built-in **HI-PASS FILTER**

Manufactured by ... **DYNAMIC ELECTRONICS**—NEW YORK, FOREST HILLS, LONG ISLAND, NEW YORK

TV FM AM

# HANDBOOK OF BASIC CIRCUITS

By  
**Matthew Mandl**

At last—a quick, convenient reference to all types of communications circuits

**including**

- SWEEP SYSTEMS • SYNC SYSTEMS
- AUDIO & RF AMPLIFIERS • POWER SUPPLY DETECTORS
- OSCILLATORS • DISCRIMINATORS
- TRANSISTORS

**136 important circuits**

each illustrated by schematic drawing and explained as to characteristics and purpose. Math and formulas at a minimum.

**An absolute necessity for**

Graduate Engineers    Students  
Technicians            Amateurs

Price \$7.50

**MANDL'S TELEVISION  
SERVICING**    Rev. Ed.

By Matthew Mandl—\$6.50

**NOW YOU CAN USE THE  
METHODS OF THE EXPERTS**

Simple, clear explanations of the fundamentals of monochrome and color TV. Complete servicing instructions for UHF and VHF. Servicing details for the latest types of equipment: transistor, gated beam detector, color TV circuits and 100 more.

You'll learn the time-saving methods used by the experts without unnecessary theory or involved math. Illustrated every step of the way.

**guarantee your future  
SEND NOW!**

**STUDY ONE OR BOTH FREE  
FOR 10 DAYS WITHOUT  
OBLIGATION**

**CLIP AND MAIL TODAY**

The Macmillan Company, Dept. PF1  
60 Fifth Avenue, New York 11, N. Y.

Please send me:

- HANDBOOK OF BASIC CIRCUITS \$7.50
- MANDL'S TELEVISION SERVICING \$6.50


I will either remit the full price or return the book(s) in 10 days.  
 Check or money order enclosed saving me delivery charge.

Name.....


Address.....

City..... Zone..... State.....

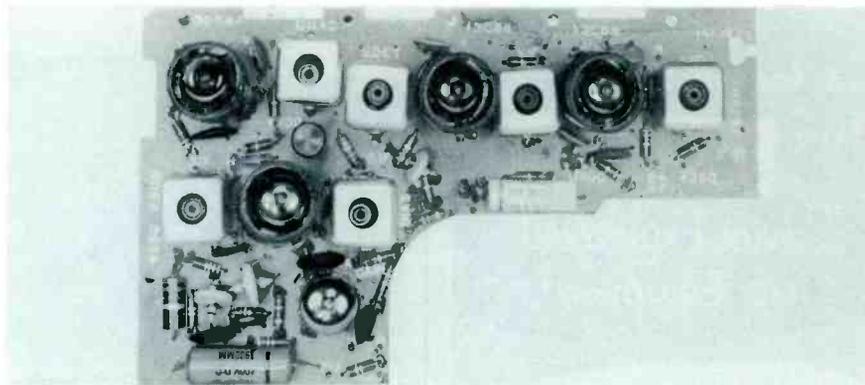Distributors in Canada: Brett-Macmillan Ltd.  
25 Hollinger Road, Toronto 16.



(A) Component side of board.

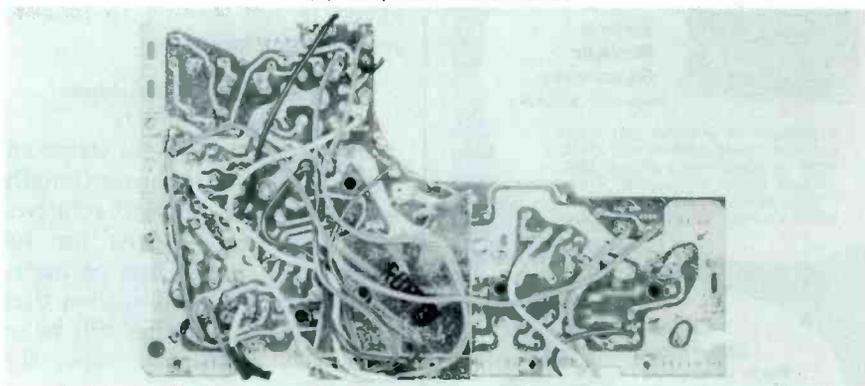

(B) Foil side of board.

**Fig. 5. Printed board with points labeled.**

substituted in wholesale quantities. When a receiver employing a printed wiring board is serviced, these practices can lead to much difficulty for the technician. It is much more desirable to isolate the trouble to the defective circuit components with orthodox trouble-shooting procedures before disconnecting any leads. A thorough check of the service literature with regard for the electrical operation of the circuit at fault and the physical layout of the associated conductor strips will make it possible to take any necessary voltage and resistance readings in the least possible time.

If the printed wiring board was not originally coated on the foil side with a protective coating of plastic, no trouble will be experienced in taking the necessary readings, but under conditions of high humidity and considerable dust, some trouble with high resistance leakage between conductors may be encountered. If it is not known whether or not the board was coated with a protective plastic spray, it may save a lot of time if you brush all dust away, clean the board with a suitable solvent, and make a resistance check for leakage. If no leak-

age is apparent, spray the board with a coating of silicone resin or acrylic plastic. During the cleaning process, you should also make a close visual inspection for such faults as minute cracks in the boards or conductor strips, evidence of arcing between conductors, etc.

**Circuit Tracing**

Circuit tracing in a receiver that employs printed wiring boards is somewhat different from checking continuity through a maze of wires, components, terminal strips and tube sockets. It is not more difficult! If you will stop and think, you will realize that with all components neatly in place on one side of the board and all wires (conductors) neatly in place on the other side it should be easier to trace from point to point. Most service literature covering printed board circuits have a layout of components and a diagram of the conductor patterns, which if used should make all circuit tracing a routine matter. It is often helpful to position a lamp on the component side of the board so that the position of the components can be seen from the wiring-foil side.

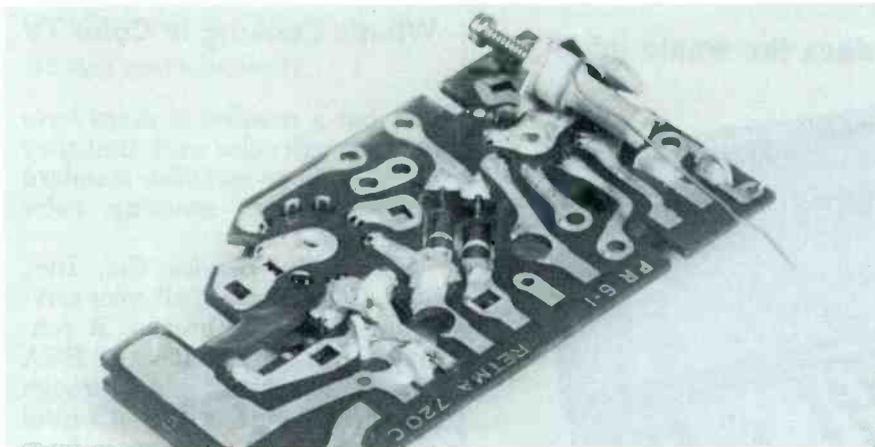


Fig. 6. Printed wiring board from Standard Coil tuner.

Generally, it has been the practice to avoid using the metal of a component body such as a filter capacitor or transformer to complete ground paths; however, on occasion you may find that such a component has been used for this purpose. An example of this type of connection is shown in Fig. 4. When this condition is encountered, always make sure all connections to the body of the unit are securely soldered to avoid later trouble.

In Figs. 5A and 5B, various sections and points have been labeled by the manufacturer. The points labeled on the component side will be especially helpful in circuit tracing. On the foil side, the key points which are very often used in trouble shooting are labeled during the etching process, thus providing permanent reference points.

#### Special Applications

Although it is commonplace to see printed boards used in radios, video IF strips, sync sections, audio sections and other parts of a receiver, it may be a surprise to some that a tuner has been constructed using a printed board for all wiring with the exception of that on the turret strips. A printed board from one of these tuners is shown in Fig. 6. You will notice that most of the capacitors are somewhat unusual in appearance since they consist of only a small ceramic disc. The ceramic is the dielectric and the two plates are covered by the solder that secures them to the conductor strips. As an aid to service technicians, the following information is given on

the inside shield of each printed circuit tuner.

"Do not remove wiring panel. There are no hidden components. Use a low wattage soldering iron with a small tip. Use 3% silver-bearing solder.

"To remove feed-thru capacitors, use two irons—one on the chassis, one on the wiring panel.

"To remove disc condensers, use a forked soldering tip, straddling condenser.

"Defective socket lugs may be replaced by removal through top of socket."

If replacement of one of the disc capacitors is required, a conventional insulated disc ceramic capacitor with its leads cut short may be used. The correct temperature coefficient and tolerance rating must be observed to avoid trouble.

Printed wiring boards have been employed in radio and television receivers for only a relatively short time, but their use is becoming so widespread that you may expect to see TV receivers entirely comprised of printed wiring boards. The newest RCA color chassis incorporates printed wiring boards for almost every circuit—exceptions being the tuner, high-voltage and low-voltage circuits.

This series of five articles should help the service technician to achieve a better insight into the reasons printed wiring boards are being used, as well as a basic idea of how to approach the problem of servicing these units. Good servicing practice, however, is something which will be acquired only with knowledge, practice, and patience. ▲

# BEST BUY IN SCOPES



new!  
**Simpson**  
**COLORSCOPE**  
MODEL 458

Compare the new Simpson Colorscope Model 458 with any oscilloscope on the market. It is an advanced, seven-inch, high-gain, wide-band scope especially designed for color-TV service. Ideal for black and white, too.

**100% RESPONSE** at 3.58 mc color-burst!

**DUAL bandwidth**—narrow or wide!  
**FLAT FREQUENCY RESPONSE**, within 1 db to 4.5 mc!

**RISE TIME** less than 0.05 microsecond (wide band)!

**FULL RANGE** compensated vertical attenuator!

Price with shielded input cable, manual... **\$229.95**

Four accessory probes available for extra utility!

See your distributor for details or write—



**SIMPSON Electric Company**

WORLD'S LARGEST MANUFACTURER  
OF ELECTRONIC TEST EQUIPMENT

5200 W. Kinzie St., Chicago 44, Illinois  
Phone: ESTebrook 9-1121  
In Canada: Bach-Simpson Ltd., London, Ont.

**AT LAST . . . one tester that does the whole job!**

**Faster—Easier—Better**

**NO OTHER  
QUICK-TEST  
TUBE CHECKER  
IS SO  
COMPLETE**



*The Advanced, Improved,*

# **ANKO TELETEST**

**TV and RADIO TUBE CHECKER**

with the Exclusive Anko "Grid-Snooper"

that spotlights troubles

**CHECKS MULTI-SECTION TUBES—  
UP TO 4 SECTIONS—  
ONE SECTION AT A TIME—  
WITHOUT ADDITIONAL  
SWITCHING!**

## **A Necessity for Profitable Operation**

The Anko-Teletest is so advanced in design that it not only accurately tests over 300 tubes in use today, but also has 10 spare sockets for new tubes that cannot be tested on presently wired sockets, so that it will fill your needs for years to come.

Tells the "inside story" of every set quickly and reliably—speeds bench work, pleases customers on service calls.

### **Simple to Use**

No special skill or experience required—anyone can operate with speed and efficiency. A model of simplicity in spite of its advanced design.

### **Costs Little More But Worth It**

You can own the all-inclusive Anko-Teletest for just a few dollars more than partial, inadequate testers, and have the benefit of top quality, serviceable equipment for years to come.

**Ask Your Jobber for  
a Free Bench  
Demonstration on  
Your Toughest  
Problem!**

1. Checks for shorts from any element to any adjacent element—requires no additional set-up. Special tests for gas, grid emission and grid shorts on all one and two section tubes.

2. Quick-test feature eliminates roll chart and multiple switching. Tests an entire set of tubes in minutes.

3. Dynamic loaded test puts tubes under fully loaded conditions.

4. Long life case—so light it can be carried anywhere, easily. Heavy duty wood case is covered with imported fabric that resists scratches and scuffing. Trimmed with genuine leather. Detachable hinged cover with firm holding catch.

**Fully Guaranteed.  
90 day warranty on  
all defective material  
and workmanship.**

**ANKO MANUFACTURING  
COMPANY, INC.**

5042 W. State St., Milwaukee 8, Wis.

## **What's Cooking in Color TV**

*(Continued from page 21)*

tics, but a number of shops have done enough color work that they could begin to establish standard procedures for servicing color sets.

The RCA Service Co., Inc., does a large share of all color servicing in Chicago because it contracts for maintenance of RCA Victor receivers sold through many retail outlets. Out of a total of around 7,000 contracts in force at the west side branch of this company at the start of the 1956 fall season, 277 were for color sets. Activity at this same branch during a period of three weeks in late summer of 1956 included an average of 15 requests per week for color installations and 50 requests per week for color service calls. Not included in the above figures are receivers which were installed and set up for home demonstrations. An average of 12 of these home-demo installations were made each week during the above-named period.

In addition to the actual service calls which have been mentioned, periodic courtesy calls are made a part of color service contracts. On these calls, the technician checks for customer satisfaction as well as proper receiver operation.

We visited several independent service shops which advertised that they did color servicing. Each of these had a small number of color contracts—as few as three. In addition, they did some service work on a single-call basis. The number of calls made by these shops ranged from several per week to "few and far between."

### **Service Charges**

It is probably safe to say that most color servicing is done on a contract basis. An example of a price schedule for color contracts is that of the RCA Service Co., Inc.:

\$39.95 Unlimited service and parts for 90 days.

\$69.95 Above plus service for remainder of one year at a flat rate of \$7.50 per call, parts included.

\$99.50 Unlimited service and parts for one year.

Color service calls not on a contract basis were priced at \$12.50 by one independent dealer and at \$10 by another. These prices include one hour's labor. Complete purity, convergence, screen, and background adjustments on a color receiver are not included in this charge because, taken together, they are regarded as too complex to be within the scope of an ordinary service call. All dealers queried said that a flat rate of \$25 is charged for a set-up job.

#### Technical Training

The training situation varies considerably among different shops. Here are some of the answers we got to questions about training:

SHOP NO. 1. Out of 25 bench and field men, 14 are qualified to do color work. They learn by experience and by home study of factory training courses.

SHOP NO. 2. Out of 10 men, 3 have been to color training schools run by manufacturers. They continue to study on their own. At one time, they participated in a group who hired an engineer to give color lectures. They received one manufacturer's home study course as a premium by buying a certain quantity of tubes from a distributor.

SHOP NO. 3. The head technician services all color sets at present. Other men are studying color in their spare time.

SHOP NO. 4. Technicians here have been taking home study courses, but interest is lagging. If a qualified color man is not available when a color service call is requested, another man is sent. He fixes the set if he can; if he gets stumped, he calls the shop for instructions or else takes the set into the shop.



The factory color schools which offer courses lasting 1 or 2 weeks have a big backlog of prospective students. Dealers say that good men trained in color work are in extremely short supply and will continue to be scarce.
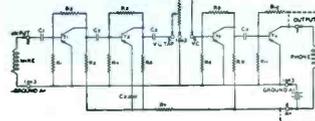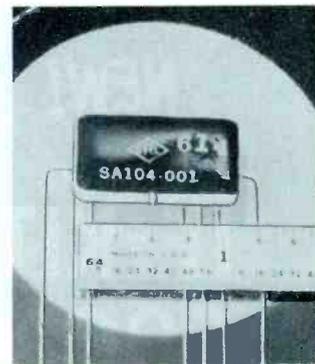
#### Test Equipment

A dot generator, considered the most essential piece of color test equipment, is used in set-up procedures on home calls. Most shops soliciting color work also have a



Model TA-11  
Measures only  
1/2" x 1" x 1/4"



# TALK ABOUT FUN!

*It starts here, with this*

## New Centralab Four-Stage Transistor Amplifier

-  You can use it in building all sorts of pocket-size radios and recorders, test equipment, computers, other projects where an ultraminiature, low-power, high-gain, dependable audio amplifier is desired.
-  The most advanced form of Packaged Electronic Circuit. Includes four special transistors, in addition to five capacitors, 12 resistors, and wiring.
-  Gain, 75 db. Supply voltage, 1.3v. Signal to noise ratio, 38 db. nominal.
-  Ask your Centralab distributor for Model TA-11. Send coupon for Bulletin EP-75 containing complete information, schematics, and curves.

# Centralab

A DIVISION OF GLOBE-UNION INC.  
9421 East Keefe Avenue, Milwaukee 1, Wisconsin Y-5624

Send me free Bulletin EP-75.

Name.....  
Company.....  
Address.....  
City..... Zone..... State.....



**NEW!**

VO-TRON  
**IF-KIT  
5000**



*subminiature*

IF Transformers  
Impedance Matched  
to Popular Transistors

*KEY components for  
BUILD-IT-YOURSELF  
6-TRANSISTOR RADIO*

Each kit contains: 3 Vo-Tron 455KC IFs (1/2" sq. x 5/8" high), matching Oscillator Coil, and 6-Transistor Radio Circuit diagram with complete parts list.

Over a million and a quarter of these high-quality components have been produced by Vokar for the leading manufacturers of Transistor Radios.

Order Colorful 6-Kit Display Card Today!

VOKAR VIBRATORS AND SUBMINIATURE COMPONENTS—PREFERRED BY LEADING ELECTRONICS MANUFACTURERS!



**VOKAR**

VOKAR CORPORATION  
DEXTER 1, MICHIGAN

color-bar generator and a wide-band oscilloscope. Independent shops generally have only one set of color-test instruments but plan to buy more as the demand develops.

We saw only one test bench especially equipped for color work. It included substitute 21" and 15" picture tubes. In most shops, it has not been thought practical to build a special color bench because most of the color sets encountered have been repaired in the home.

One shop prefers to remove a color set from the home, cabinet and all, if it requires bench work. The shop manager claims that time and money are saved in the long run, since unnecessary disassembly is avoided and an accurate set-up can be accomplished in the shop with only slight additional work needed when the set is returned to the home.

**Customer Attitudes**

Surprisingly enough, technicians who had serviced color TV agreed that the average customer is not highly critical of the quality of the picture on his color set. When a new receiver is delivered, the technician usually goes through a complete set-up procedure only if the customer indicates dissatisfaction with the performance. Sets are normally received from the factory in such good alignment that there are only minor imperfections in convergence and purity, and many customers overlook the slight color fringing or shading that results.

The general opinion was that most customers were also satisfied with the black-and-white pictures on color receivers. Although they frequently keep their old black-and-white sets, many use them in other rooms in their homes as second sets.

In some color sets after several months of use, color fringing in black-and-white pictures makes its appearance. This happens because the electron beams in the color picture tube sometimes tend to drift gradually out of alignment. Viewers usually fail to notice this effect because it is so gradual. We were told of one receiver which had assumed a sepia tone during monochrome pro-



**Little Devil** COMPOSITION RESISTORS

Meet all MIL-R-11A requirements. Rated at 70C rather than 40C. Available in 1/2, 1, and 2-watt sizes in all standard RETMA values.



**BROWN DEVIL** RESISTORS

Vitreous-enameled. In 5, 10, and 20-watt sizes.

**TYPE AB POTENTIOMETERS**

Resistance material is solid-molded, noise-free. Rated at 2 watts.



**FR-7.5 FUSE RESISTOR**

For easy replacement in all television receivers. 1/2" Tinned wire leads.

WRITE FOR STOCK CATALOG

*Be Right with*

**OHMITE**

**DEPENDABLE  
RESISTANCE UNITS**

Eliminate call-backs due to faulty replacements. Use Ohmite components.

**AXIAL-LEAD RESISTORS**

Vitreous-enameled, power-type units designed to withstand high temperatures.

**OHMITE**  
3 WATT SIZE  
9/16" x 1/4"

**OHMITE**  
5 WATT SIZE  
1" x 11/32"

**OHMITE**  
1500 OHMS  
10 WATT SIZE  
1-3/4" x 13/32"

**OHMITE**

OHMITE MANUFACTURING CO.  
3644 Howard Street, Skokie, Illinois

grams. When the technician restored the original gray appearance, the customer objected, saying that he liked the tint!

In problem locations (districts of skyscraper apartment buildings, for example), we heard of several customers who showed amazing patience even though they were able to obtain color pictures only occasionally. One set owner was "delighted as a kid" when a technician managed to obtain some weak color on his receiver after a great deal of effort.

We received several reports of shorted or burned focus and screen potentiometers on certain models of color sets but there were no repeated failures in the chrominance circuits. In the main, color receivers have the same types of failures as black-and-white sets and present many of the same servicing problems.



#### Programming

Station WNBQ, channel 5 in Chicago, has been widely publicized as the world's first all-color TV station. Since last spring, all local live programs (more than five hours daily) have been telecast in color. Except for a few hours weekly, the NBC network shows have been in black and white, but the network has laid plans to transmit at least one color show every evening during the 1956-57 winter season.

We toured the WBNQ studios and saw an impressive array of color transmitting equipment. Even more impressive, however, was a public lounge designed especially for the display of color TV. This is advertised over the station and attracts large crowds daily. About 10 closed-circuit color receivers are distributed throughout the lounge. The general atmosphere of the room, with its soft seats and low illumination, invites the public to relax and see color TV in living-room surroundings.

The effectiveness of this display was revealed when we interviewed some of the people in the lounge. Our impression was that the display causes many people to think seriously for the first time about buying a color set.

The following comments were

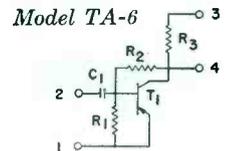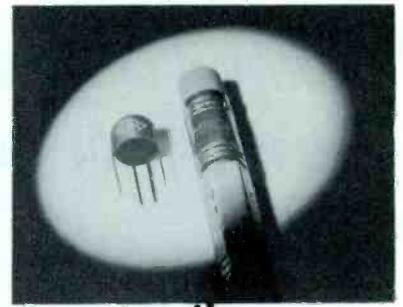

## A PRIZE TROPHY

*for miniaturized audio amplification*

*No closed season... no limit... to its applications*

### New Centralab Single-Stage Transistor Amplifier

- ◊ High-gain, low-power transistor amplifier can be used by itself in microphones and other miniature circuit designs. Or, you can combine several units, to get a multiple-stage unit for other audio applications.
- ◊ This is a complete amplifier housing capacitance, resistance, transistor, and wiring. Gain, 24 db. Noise level, less than 1/2 millivolts. Supply voltage, 1.35 v.
- ◊ As small as an eraser on an ordinary lead pencil.
- ◊ Ask your Centralab distributor for Model TA-6—or TA-7. Send coupon for Bulletin EP-75 containing complete information, schematics, and curves.

## Centralab

A DIVISION OF GLOBE-UNION INC.

9421 East Keefe Avenue, Milwaukee 1, Wisconsin

Y-5625

Send me free Bulletin EP-75.

Name.....


Company.....

Address.....

City..... Zone..... State.....



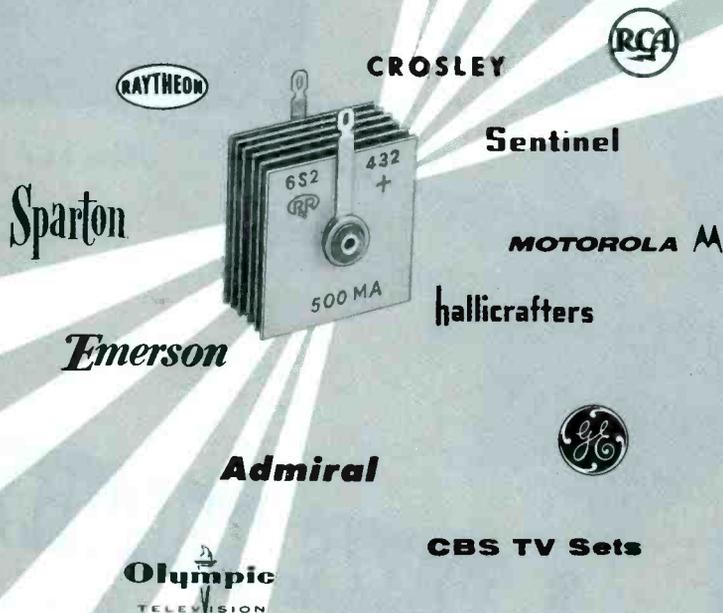*Original components in these and other leading Radio and TV sets since 1948*



## RADIO RECEPTOR

### Selenium Rectifiers

*That's why they're the best replacements in any Radio and TV circuit!*

These famous trademarks represent a few of the many long-time users of RRco. Selenium Rectifiers. The complete list reads like a "Who's Who" in electronics.

Manufacturers' choice in so many models, RRco. "Safe Center" rectifiers are ideal replacements in *any* set. Your parts distributor can supply you with standard Radio Receptor replacements for sets of all radio and TV manufacturers. Demand "Safe Center" rectifiers and insure the quality of your repair work.

Semiconductor Division

**RADIO RECEPTOR COMPANY, INC.**

*In Radio and Electronics Since 1922*

240 WYTHE AVENUE, BROOKLYN 11, N. Y. • EVERGREEN 8-6000



gleaned from some of the interviews. An elderly woman said that she liked color and found it easier on the eyes than black and white, but she could not yet afford a color set. Two couples would definitely have been interested in color if they had not recently bought elaborate black-and-white consoles. Each said their next set would probably be color. Another couple, recently married, were just furnishing a house and had no TV set. They intended to check over their budget to see if they could afford a color receiver as their first set.

We heard a minority of negative comments, including dissatisfaction with the quality of the color. One woman complained that the faces of people on the screen had a bluish cast and that the background colors were faint. Several people seemed bothered by the fact that the colors were reproduced somewhat differently by the various sets on display, even though all the sets were adjusted for a pleasing picture. Many of their doubts were cleared up with an explanation of the use of the hue and saturation controls—something which could profitably be done in a store as part of a demonstration.

Color activity is not confined to WBNQ, although that station carries the most color programming by far. We visited WBBM-TV, the CBS station in Chicago, and learned that it could transmit network shows which originate in color. This station has not yet installed equipment for local color-casting because of the feeling that color does not particularly improve the effectiveness of local

### YOU SHOULD KNOW...

... the following about your PF REPORTER subscription:

- ✓ To determine expiration date of your subscription, refer to number at right on bottom line of your address inscription. Example: 357 means that your subscription expires with the March, 1957 issue.
- ✓ To assure uninterrupted delivery when moving, please notify us at least a month in advance and include your present address or send along an address label from one of your back issues.
- ✓ Copies of the PF REPORTER are mailed by the first of the month at latest. If your copy arrives late it is due to conditions beyond our control.

Circulation Department, PF REPORTER  
2201 East 46th St., Indianapolis 5, Ind.

programs (such as news) nearly as much as it enhances the appeal of big network shows. A third Chicago station is also working with color—independent WGN-TV has installed color equipment and is experimenting with it.

### Sales

It is no secret that RCA is feeding the fire under the color kettle. A spokesman for the RCA Victor Distributing Co. in Chicago told us that about 90% of his firm's newspaper advertising in the fall of 1956 would emphasize color. A 480% increase in color receiver sales was achieved in the third quarter of 1956, compared to the last quarter of 1955. The goal for the final quarter of 1956 was said to be a sales increase of greater than 1000% over the corresponding period of 1955. It was estimated that over 6,000 color sets had been installed in homes in the Chicago area by the end of September, 1956.


Some of the biggest retail promotions of color TV are being staged by a major department store and its 16 neighborhood branches, a well-known music store, and one of the largest appliance stores. Several smaller appliance outlets have also been aggressively selling color. The RCA Victor distributor told us that color accounted for 30% of the TV sales of one local service dealer.

Color receivers are being exposed to groups of people as widely as possible by such methods as loaning sets to neighborhood organizations and donating other sets for raffles. Home demonstrations are hard work, but they have been effective. Several dealers are getting good results by arranging special demonstration rooms where color programs can be shown under ideal conditions. Color TV is sometimes grouped with hi-fi equipment in such a room.

On one occasion, we watched a color set demonstrated in an ordinary salesroom side by side with black-and-white receivers. The light level in the room was so high that the colors were partly washed out, and the picture was full of color contamination because the
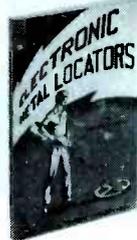
## SAMS BOOKS keep you ahead in ELECTRONICS

SAMS books cover every phase of Electronics for the service technician, engineer, student or experimenter. Listed below are a few of the many valuable SAMS books available at electronic parts distributors and leading book stores.



### 2 NEW SAMS BOOKS

#### "ELECTRONIC METAL LOCATORS"


by

Harold S. Renne

Explains how Metal Locators operate, describes commercial types available, shows how to construct home-built units, describes applications. Fully analyzes the three basic types of Metal Locators: transmitter-receiver, beat-frequency and induction bridge. Includes chapter showing construction details for several different units, including transistorized types. Reveals the interesting applications of Metal Locators in industry. Special chapters are devoted to prospecting and mine detection applications. Includes valuable bibliography. 124 pages; 5½ x 8½"; illustrated. Order today, postpaid only. . . . \$2.50

#### "SCATTER PROPAGATION Theory & Practice"

by Kamen & Doundoulakis

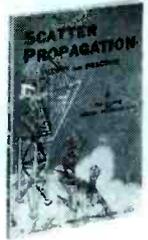

An invaluable book not only for engineers but for technicians who will play an important part in the installation, operation and maintenance of scatter propagation systems. Covers theory and characteristics of Scatter Propagation; equipment used in ionospheric communications systems; tropospheric propagation and equipment utilized; design and construction of parabolic antennas; the importance of Scatter Propagation for the electronic technician; discusses DEW Line and other northern radar and scatter lines. Written so you can understand it. 204 pages; 5½ x 8½"; illustrated. Order today, postpaid only. . . . \$3.00

### USE THIS ORDER FORM

**ELECTRONIC METAL LOCATORS** . . . . . \$2.50

**SCATTER PROPAGATION** . . . . . \$3.00

**Color TV Training Manual.** Prepares the Technician for Color TV service work. Covers principles of the Color TV system; Color receiver circuits; installation and servicing sets. Includes color blocks outlining the use of color test equipment. 260 pages; 8½ x 11"; 300 illustrations. . . . \$6.95

**Tape Recorders—How They Work.** Explains recording theory, tape characteristics, motorboard mechanisms, drive motors, amplifiers, magnetic heads, volume indicators, equalization circuits—covers everything you want to know about recorders. 176 pages; 5½ x 8½". . . . \$2.75

**TV Test Instruments.** Revised and enlarged to include latest data on instruments used in Color TV servicing. Tells clearly how to operate each type of test instrument used in TV service work. 180 pages; 8½ x 11"; illustrated. . . . \$3.50

**Servicing AGC Systems.** Describes the operation and circuit variations of the various types of AGC systems and explains the servicing techniques that can be applied. Illustrated by actual case histories and photographs of symptoms. 132 pages; 5½ x 8½"; illustrated. . . . \$1.75

**Key Checkpoints in TV Receivers.** Prepared by the Howard W. Sams engineering staff. Provides many applications for general TV service work, including time-saving information on how to make quick tests at key points to determine where trouble lies, and how to check overall performance of the receiver after repair, to insure against callbacks. 182 pages; 5½ x 8½"; illustrated. . . . \$2.00

**Servicing & Calibrating Test Equipment.** Shows you how to keep your test instruments in reliable working order, how to determine proper operation and avoid erroneous indications. Explains calibration procedures; gives method for performance record-keeping; shows simple ways to check instrument accuracy; describes proper maintenance and servicing of instruments. 192 pages, 5½ x 8½". . . . \$2.75

**Servicing TV Sweep Systems.** Describes the operation, circuit function and circuit variations of vertical and horizontal sweep systems common to most TV receivers. Tells how to analyze circuits; trouble-shoots for you. 212 pages; 5½ x 8½"; illustrated. . . . \$2.75

**So You Want to Be a Ham.** Tells you what you need to know about getting your license and acquiring equipment. Covers such subjects as: Conquering the Code; Getting Your Ticket; Going on the Air; Electronics as a Career; etc. 196 pages; 5½ x 8½"; illustrated. . . . \$2.50

**Radio Receiver Servicing.** Covers the basic receiver types—gives time-saving hints for solving basic troubles, such as dead set, weak set, noisy set, etc. 192 pages; 5½ x 8½". . . . \$2.50

**TV Servicing Guide.** Explains how to apply proper trouble-shooting procedures based on analysis of symptoms (most of which are illustrated by picture-tube screen photos). Shows how to locate and eliminate trouble in every section of the receiver. 132 pages, 8½ x 11". . . . \$2.00

There is an authoritative Sams book on virtually any Electronic subject in which you're interested. Check below for FREE Book List describing all Sams books.

Send Book List



### ...HOWARD W. SAMS & CO., INC. ....

Order from your Parts Jobber today, or mail to Howard W. Sams & Co., Inc., Dept. 3-M6 2201 East 46th St., Indianapolis 5, Indiana.

Send books checked above. My (check) (money order) for \$..... is enclosed.

Name.....

Address.....

City..... Zone..... State.....

(outside U.S.A. priced slightly higher)

Look for SAMS BOOKS on the "Book Tree" at your Parts Distributor



## TYPICAL COLOR TV SALES DISPLAYS



# QUAM

*Adjust-a-Cone®*

## SPEAKERS



are the  
**SAME PRICE**  
but they  
**COST LESS**

They cost less because they fit right . . . the first time . . . and they work right . . . the first time.

With Quam Adjust-a-Cone Speakers there are no callbacks—caused by defective or non-fitting speakers—to eat up your profits.

Remember: a guarantee does not pay for your time or protect your reputation and customer goodwill . . . so use Quam, the “no-callback” speaker.

*ask for QUAM,  
the quality line,  
for all your speaker needs*

**QUAM-NICHOLS COMPANY**

234 EAST MARQUETTE ROAD •

CHICAGO 37, ILLINOIS

receiver was improperly set up. Several customers who had expressed interest in color were scared away by this careless demonstration. If this were their first impression of color TV, they were very possibly ruined as color prospects for years to come. To effectively sell color, we have become convinced that a color set should not even be turned on in the showroom unless it will look as good there as it would in the customer's home.

Who buys color? Dealers say that wealthy people are not buying as many sets as one might think, although a good percentage of buyers are in a position to pay cash for their sets. People in the middle income brackets can afford color at present prices, and the majority of color owners are said to be in the \$4,500-\$7,500 income group. Some of the earlier color receivers were sold to taverns, but the big effort today is the home market.

### Summary

We found three general attitudes toward color in the Chicago area:

1. RCA, NBC, and several stores are enthusiastic about color and are going all out to create a big demand for it. They are convinced that prices and programming have been brought to such levels that substantial amounts of color receivers can now be sold.

2. Many organizations are making definite preparations for color, but they are being somewhat cautious in their efforts. As one spokesman put it, "Why should we go out on a limb with color when black-and-white sales have never been better?" Two Chicago manufacturers, Motorola, Inc. and Admiral Corp., who are both producing new color sets for sale at competitive prices, intend to advertise these receivers but to proceed cautiously with production. The CBS network has a similar attitude toward color programming. In the "middle-of-the-road" category are many TV dealers who have a few color sets on their floors. They let their customers know that color is available but do not push it to any great extent.

3. A large number of service dealers are not yet interested in selling or servicing color TV receivers—not until color becomes more popular with the public.

Color, even in Chicago, still appears to be in a formative stage of commercial development. Nevertheless, the color situation is gradually improving, and it is our personal opinion, judging from the comments received from both the general public and members of the TV industry, that color TV will not create the tremendous boom that black-and-white TV did but will instead enjoy a steady, substantial growth. ▲

**TROUBLE SHOOTING WITH GEORGE**  
The Solution

George had actually detected the faulty component, but a slight case of mistaken identity arose because of his hasty attempt to solve the mystery. When he examined the original capacitor more closely (*see below*), he found it to be of a special type used in many horizontal AFC circuits. You will notice that the markings indicate a tolerance of  $\pm 5\%$  from 0 to 85°. Had George either taken heed to all the markings on the capacitor or consulted the parts list in the service literature before selecting a replacement, he would have arrived at an earlier solution.



# THE *Miraculous* M-500

## SARKES TARZIAN SILICON RECTIFIER

Replaces  
All Types Selenium Rectifiers  
In Radio and Television Sets

### ALL THESE FEATURES AT NO EXTRA COST

- Rejuvenates old T.V. sets with clearer, brighter pictures
- Operates in high humidity (even under water)
- Higher efficiency—20 Volts more output in doubler
- Small enough to fit any set
- Only one size needed to replace all existing rectifiers
- Conversion Kit or single units available from your distributor



Sarkes  
Tarzian, INC.

RECTIFIER DIVISION

415 N. College Ave., Bloomington, Indiana

IN CANADA: 700 WESTON RD., TORONTO 9, TEL. ROGERS 2-7535  
EXPORT: AD AURIEMA, INC., NEW YORK CITY





SUBJECT	ISSUE
Selenium-rectifier tester, Jackson Model 49R <i>Notes on Test Equipment</i> .....	May
Signal generator, Eico Model 324 <i>Notes on Test Equipment</i> .....	May
Sweep-circuit analyzer, Wintronix Model 820 <i>Notes on Test Equipment</i> .....	Feb.
Tube checkers, operation of <i>Notes on Test Equipment</i> .....	Nov.
Tube tester, Jackson Model 49 <i>Notes on Test Equipment</i> .....	May
Tube-transistor tester, RCP Model 325 <i>Notes on Test Equipment</i> .....	Sept.
VTVM, checking <i>Shop Talk</i> .....	May
Video multimeters, RCA WG-295A and 295B <i>New Alignment Techniques</i> .....	Sept.
Vitamer, Electronic Test Instrument Corp. <i>Notes on Test Equipment</i> .....	July

**THEORY**

AGC circuit in Zenith 17Y20 chassis <i>Examining Design Features</i> .....	June
Alignment <i>New Alignment Techniques</i> .....	Sept.
Antenna phasing <i>Within the Antenna</i> .....	Aug.
B+ circuits <i>Voltage Dividers in B+ Circuits</i> .....	May
Capacitive reactance <i>Shop Talk</i> .....	Oct.
Cathode followers in audio circuits <i>Audio Facts</i> .....	Aug.
Color TV <i>Looking Over the New Color Receivers</i> .....	Nov.
Courses, upgrading <i>Shop Talk</i> .....	Oct.
DC restoration <i>Video Amplifiers</i> .....	Aug.
Damper circuits <i>Operation of Damper Circuits</i> .....	Aug.
Decibels <i>Notes on Test Equipment</i> .....	July
Frequency and phase comparison <i>Analyzing Lissajous Patterns</i> .....	Oct.
FM sound detector <i>TV Sound from the 6DT6</i> .....	Dec.
Horizontal sweep <i>The Horizontal Flyback System</i> .....	Apr.
Keyed AGC <i>Operation of Keyed AGC Systems</i> .....	July
Modules, described and illustrated <i>A New Development Toward Automation</i> .....	Apr.
Quadrature-grid FM detector <i>TV Sound from the 6DT6</i> .....	Dec.
RC circuits <i>Time Constants</i> .....	Mar.

SUBJECT	ISSUE
Rectifiers, selenium <i>Selenium Rectifiers</i> .....	Oct.
Schools, how to choose <i>Shop Talk</i> .....	Sept.
Shop Talk.....	Oct.
Vertical sweep <i>Troubles in Vertical Sweep Systems</i> .....	June
Video circuits <i>Video Amplifiers</i> .....	Aug.

**TRANSFORMERS**

Foreign-made <i>Let's Take a Look at Foreign-Made Radios</i> .....	July
Phase relationships <i>Voltage Phases in Transformers</i> .....	Jan.
Quadrature-FM detector in Crosley V-series <i>In the Interest of Quicker Servicing</i> .....	Apr.
Replacement <i>Replacing Rivet-Mounted Components</i> .....	June

**TRANSISTORS**

Checking with ohmmeter <i>Shop Talk</i> .....	July
Collector-saturation current <i>Shop Talk</i> .....	Mar.
Diffused-junction types <i>Shop Talk</i> .....	Feb.
Frequency response of junction types <i>Shop Talk</i> .....	Jan.
Heat dissipation <i>Shop Talk</i> .....	Mar.
Junction types <i>Shop Talk</i> .....	Feb.
n-p-i-n type <i>Shop Talk</i> .....	Feb.
p-n-i-p type <i>Shop Talk</i> .....	Feb.
Power transistors <i>Shop Talk</i> .....	Mar.
Shop Talk.....	July
Silicon transistors <i>Shop Talk</i> .....	Mar.
Specifications <i>Shop Talk</i> .....	Apr.
Surface-barrier type <i>Shop Talk</i> .....	Feb.
Tester, RCP Model 325 <i>Notes on Test Equipment</i> .....	Sept.
Tester, CG Electronics Corp. <i>Shop Talk</i> .....	June
Tester, GE <i>Shop Talk</i> .....	June
Testing <i>Shop Talk</i> .....	June
Tetrode-junction type <i>Shop Talk</i> .....	Feb.

SUBJECT	ISSUE
<b>TRANSISTOR RECEIVERS</b> Mitchell Model 1103 portable radio <i>Examining Design Features</i> .....	Jan.
Motorola Model 6TAS8 auto radio <i>Shop Talk</i> .....	July
<b>TRANSMISSION LINES</b> Connecting to terminals <i>Quicker Servicing</i> .....	Dec.
Terminals, insulating and moisture-proofing <i>Chemical Aids to Servicing</i> .....	Mar.
Tubular type, water drainage from <i>In the Interest of Quicker Servicing</i> .....	Jan.
UHF <i>Life on a UHF Island</i> .....	Sept.
<b>TUBES, RECEIVING</b> 6BU8 "Siamese-twin" pentode <i>Examining Design Features</i> .....	June
6DT6 gated-beam discriminator <i>TV Sound from the 6DT6</i> .....	Dec.
Horizontal-output <i>Changes in Tube Design</i> .....	Apr.
Modifications <i>Changes in Tube Design</i> .....	Apr.
Radio tubes <i>In the Interest of Quicker Servicing</i> .....	July
Replacement hints <i>In the Interest of Quicker Servicing</i> .....	Mar.
Series-string operation <i>Changes in Tube Design</i> .....	Apr.
Shields <i>Examining Design Features</i> .....	June
Stock guide <i>A Stock Guide for TV Tubes</i> .....	Dec.
Substitution guide <i>Quicker Servicing</i> .....	Aug.
<b>TUNERS</b> Neutrode, Standard Coil <i>Examining Design Features</i> .....	Oct.
Philco automatic tuning <i>Examining Design Features</i> .....	May
Printed-board tuner <i>Printed Wiring Boards—Part V</i> .....	Dec.
Remote-control, Sentinel <i>Examining Design Features</i> .....	Jan.
Servicing tuner in Zenith chassis 20J21 <i>In the Interest of Quicker Servicing</i> .....	Apr.
Standard Coil T-series <i>Examining Design Features</i> .....	Apr.
UHF <i>Life on a UHF Island</i> .....	Sept.
<b>VOLTAGE REGULATION</b> CBC Regomatic automatic regulator <i>In the Interest of Quicker Servicing</i> .....	Mar.



**The Capacitor Package that means Quality**

1 year service guarantee

When you see this package in the familiar red and black box, you know it contains "trouble-free" Planet capacitors—mechanically and electrically tested throughout manufacture.

This rigid system of quality control makes our unconditional one-year guarantee possible. But making Planet capacitors correctly from the start means reasonable prices too!

**PLANET MANUFACTURING CORPORATION**

225 BELLEVILLE AVENUE  
BLOOMFIELD, N. J.



Write for Catalog listing specifications on stock items.

**XCELITE Hand Tools**  
PREFERRED BY THE EXPERTS

**NEW**

**TRANSPARENT POCKET KITS!**

**CK-20 ZIPPER CASE!**

That big, husky Xcelite handle and tough, precision-pointed blades for quick change to Nos. 1 & 2 Phillips, 3/8" & 1/4" regular blades—instantly visible in durable plastic pouch with zipper! Fits hip pocket, tool box, glove compartment, any 4" x 8" space! What a kit to own, and what a gift idea! Ask your supplier.

**Only \$4.40 LESS DISCOUNT**

**STUBBY AND REGULAR HANDLES ARE ALSO 3/8" HEX NUT DRIVER!**

**SK-20 STUBBY KIT!**

1 1/4" x 2" combination handle, 2 quick-change stubby blades, Nos. 1 and 2 Phillips, 3/8" and 1/4" regular.

**Only \$3.70 LESS DISCOUNT**

**XCELITE, INCORPORATED**  
Dept. Q, Orchard Park, N. Y.  
In Canada—Charles W. Pointon Ltd., 6 Alcina Ave., Toronto, Ont.

**For Originality**  
**LOOK TO XCELITE**

## Servicing New Designs

(Continued from page 15)

proper service information is not at hand. This article includes a detailed explanation of the disassembly of the Admiral portable set because this information will be particularly helpful to the reader.

In this receiver, components are fastened to two vertical chassis which are braced and bolted together into a rigid unit. Three braces extend from the front of this assembly, and their outer ends support a strap which holds the bell of the picture tube firmly in place. The yoke is supported by the picture-tube neck and is fastened in place by a pinch clamp and a rubber wedge. Rear and front views of the chassis assembly (with the picture tube, its mounting braces, and the speaker removed) are shown in Fig. 3.

The control panel on top of the receiver contains the on-off and channel-selector switches and the volume, fine-tuning, vertical-hold and contrast controls. The height, vertical-linearity, horizontal-hold and brightness controls and the local-distant switch are accessible through the back cover of the receiver.

Considerable service work can be done on the Admiral receiver with the chassis in the cabinet and the back cover removed. The metal cover can be pried off when two screws at the sides are taken

out, and power can be supplied to the receiver through a cheater cord. The printed wiring board visible in the foreground in Fig. 3A is normally mounted in a vertical position so that the tubes point forward. When six screws are removed, the board can be swung outward, remaining attached to the chassis through numerous leads. All tubes except those in the tuner are then accessible, the components on the printed board can be serviced, the receiver can be aligned, and the ion trap and centering device can be adjusted. The horizontal output tube is shielded by a small metal plate, but this can be pivoted out of the way to permit removal of the tube.

To service some components, it is necessary to remove the chassis from the cabinet. Items which must be removed so that this can be done are the control knobs, 4 rubber feet, 2 screws holding the carrying handle, 4 screws on the bottom and sides of the front cover and 3 additional screws securing the chassis to the cabinet—one on top and 2 underneath. The front cover with its tinted-plastic protective mask may then be pulled off and the chassis can be taken out through the front of the cabinet.

The tubes and adjustments in the tuner then become accessible from the side. The picture tube and the speaker (normally attached to the front chassis by two screws) may be removed as they were for the photographs in Fig. 3. The mounting braces for the picture tube are fastened to the upper corners and the bottom center of the front chassis.

The Admiral portable set is much like the larger sizes of vertical-chassis receivers in the degree of accessibility which it offers. Most of the components on the front chassis can be reached with test probes while the picture tube is in place and some (e. g., rectifiers) can be unsoldered. The hardest components to reach are the ones on the small printed-wiring board that extends from the bottom edge of the chassis. Parts of the horizontal AFC and horizontal and vertical oscillator stages are on this board.

(Advertisement)

MODEL 648		MODEL 715/115/561	
TUBE TYPE	FIL. D.	FIL.	X. PLATE YZ
4BC5	4-2 A234	4-2	5 28 2LMS
4BN6	4-2 C123	4-2	- 29 5JKMQ
4CB6	4-2 AC1234	4-2	- 26 3KMQ
4CE5	4-2 AC123	4-2	5 35 2JMS

MODEL 49		MODEL 48	
TUBE TYPE	SEC. A. B. C.	CATH. SHORTS	E.
4BC5	4-2 3 2X	156	7 30
4BN6	4-2 3 -	2587	1 90
4CB6	4-2 3 X	1567	2 30
4CE5	4-2 3 7X	156	2 30

Latest Chart Form 648-17, 715/115/561-9, 48-3

# IMPROVE your AMPLIFIER in 5 ways



with the

## Amperex® GZ34 RECTIFIER

A LOW-IMPEDANCE, INDIRECTLY HEATED, FULL-WAVE RECTIFIER WITH 250 MA OUTPUT CAPACITY

The unique AMPEREX GZ34 replaces without circuit changes, in the majority of amplifier circuits, an entire line of popular, heavy-duty 5-volt rectifiers—5U4G, 5V4G, 5T4, etc. — with the following benefits:

- Better voltage regulation due to lowered power supply impedance;
- Higher power supply output voltage for more power;
- Added filter condenser protection due to reduced ripple;
- Cooler operation due to lower voltage drop;
- Protection of costly power output tubes through delayed warm-up.

---

OTHER **Amperex TUBES** FOR HIGH-FIDELITY AUDIO APPLICATIONS:

EL84/6BQ5 9-pin power pentode; 17 W PP  
 6CA7/EL34 High-power pentode; 100 W PP  
 EF86/6Z67 Low-noise high- $\mu$  pentode  
 ECC81/12AT7 Low-noise medium- $\mu$  dual triode  
 ECC82/12AU7 Low-noise low- $\mu$  dual triode  
 ECC83/12AX7 Low-noise high- $\mu$  dual triode  
 EZ80/6V4 9-pin rectifier; cathode; 90 ma.  
 EZ81/6CA4 9-pin rectifier; cathode; 150 ma.

At All Leading Electronic Parts Distributors



**Amperex  
ELECTRONIC CORP.**  
 230 Duffy Ave., Hicksville, Long Island, N.Y.

Quickly locates  
"TOUGH DOGS"



# Senco Tube and Capacitor

## Leakage Checker Model LC-2

Dealer Net  
**\$19.95** Kit  
Complete with  
test leads.  
Simple to  
operate.  
\$24.95  
wired

**"Two Testers In One"**  
Now—checks 70 critical tube types

- Quickly locates tubes with gas, grid to cathode or heater to cathode leakage, and grid emission in RF, IF and AGC Circuits.
- Only type tester that finds all tubes causing picture overload, low sensitivity, poor sync, etc.
- Checks all capacitors for leakage with voltage applied.

At Leading Distributors

Mfg by  
**SERVICE INSTRUMENTS COMPANY**  
171 OFFICIAL ROAD • ADDISON, ILL.



*Cancer can't strike me,  
I'm hiding.*



*Cancer?*

*The American Cancer Society says that too many people die of it, NEEDLESSLY: That's why I have an annual medical checkup however well I feel. I know the seven danger signals. And when I want sound information, I get it from my Unit of the*

**AMERICAN CANCER SOCIETY**

The fusible resistor in the rectifier circuit is mounted on one of the braces which hold the two chassis together, and it can be reached from the underside of the receiver.

The tuner is suspended from the front chassis by two brackets, and three screws must be removed to loosen it. When extracting the tuner from the chassis, it is simplest in the long run to spread the two chassis apart in order to provide room for maneuvering. Removal of 8 screws from the rear chassis frame makes it possible to move the chassis back far enough so that the tuner can be eased out with little trouble.

The chassis is electrically "hot", but the screws holding the control panels and cabinet to the chassis are driven into nylon fasteners that insulate the external metal portions of the receiver from the power line.

The cabinet contains many ventilating louvers and the flow of air through these must not be blocked off for any length of time if damage to components from overheating is to be avoided. Customers should be cautioned not to pile objects beside the receiver or on top of it.

The technician should not be misled into assuming that all portable TV sets are difficult to service just because they are constructed differently from large-screen sets. Although portables have some disadvantages arising from the cramped quarters inside the cabinet, many larger sets also have their drawbacks. With portables, there are no problems such as the precarious balancing of heavy cabinets to get at the bolts on the bottom, or the care and handling of large bulky picture tubes.

#### High-Voltage Section of Color TV Set

The high-voltage sections in recently produced color TV receivers are simpler in design than in earlier models but are still characterized by large, rugged components and heavy-duty insulators built to keep under control an anode voltage of approximately 25 kv.

The components in the high-voltage cage of the Sentinel Model 1U816C color receiver are shown in Fig. 4. Note the heavy

plastic shield which surrounds the base of the high-voltage rectifier (left foreground), the large polyethylene cap on the regulator tube (right foreground) and also the massive polyethylene high-voltage anode lead hanging down in front of the chassis. The circular ridges that give the anode connector a "Buck Rogers" look are for the purpose of increasing the length of the leakage path across the surface of the insulator.

An additional component built to withstand high potentials is the interlock being held in the technician's hands in Fig. 4. The re-

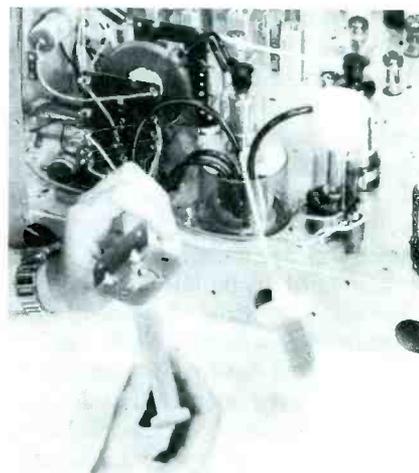


Fig. 4. High-voltage section of Sentinel Model 1U816C color set.

ceptacle in the left hand is normally screwed to the back wall of the cage, and the polyethylene plug in the right hand is normally mounted to the rear and is inserted into the receptacle when the cover has been fastened in place. Removing the cover pulls out this plug and causes the second-anode supply to be shorted to ground.

The manufacturer states that to measure the second-anode voltage, a small hole may be drilled in the end of a spare interlock plug and a meter probe inserted while this plug is in the receptacle. It has been found that the high voltage sometimes arcs to the chassis from the probe. If this occurs, the plug may be pulled out about  $\frac{1}{2}$ " to  $\frac{3}{4}$ " or the metal receptacle may be detached from the chassis while measurement is being made. (The spare plug should not be used in normal receiver operation because of the shock hazard from the high-voltage terminal exposed by the small hole.) ▲

## Quicker Servicing

(Continued from page 13)

zontal section. The horizontal ringing coil was defective, and one sync-coupling capacitor had a small amount of leakage. Since the "S" pattern did not appear, it was assumed that the trouble had been eliminated, and the receiver chassis was reinstalled in the cabinet. A test operation with the chassis in the cabinet resulted, however, in the appearance of the "S" pattern after about one hour.

Because the trouble had disappeared while the chassis was being removed the first time, the receiver was kept in operation while the chassis was readied for a second removal. When all of the chassis bolts, the rear cover, the speaker cable, and other necessary parts had been disconnected, the receiver was quickly placed on the bench and a check of the signals present in the horizontal AFC section was made. A schematic of the horizontal AFC and oscillator section is shown in Fig. 1. All of the signals were so distorted that no concrete conclusion could be drawn.

Since this signal check revealed no clue as to the cause of the trouble, a check of the capacitors in the output or filter circuit from

the phase detector was made. When the .15-mfd capacitor was bridged with a new unit, the trouble disappeared. Because of the previous reoccurrence, the new .15-mfd unit was disconnected to see if this was really the cause of the trouble. Sure enough—the trouble came back.

The logical conclusion was that the presence of an unwanted 60-cycle signal at the output of the phase detector had varied the conduction of the oscillator-control stage and thereby caused the "S" distortion.

After further thought about this trouble, the author recalled that the audible sound from the oscillator had been steady and the pattern produced by the trouble had not been the erratic condition known as Christmas-tree effect. Had this been realized earlier, much trouble could have been avoided. It should have been more obvious that the cause might be due to poor filtering of the AFC voltage from the phase detector.

### Double Image

A Motorola receiver that produced two pictures side by side during the first few minutes of operation was a recent visitor to the shop. The picture size was reduced



## CHICAGO STANDARD TRANSFORMER CORPORATION

3503 Addison Street • Chicago 18, Illinois

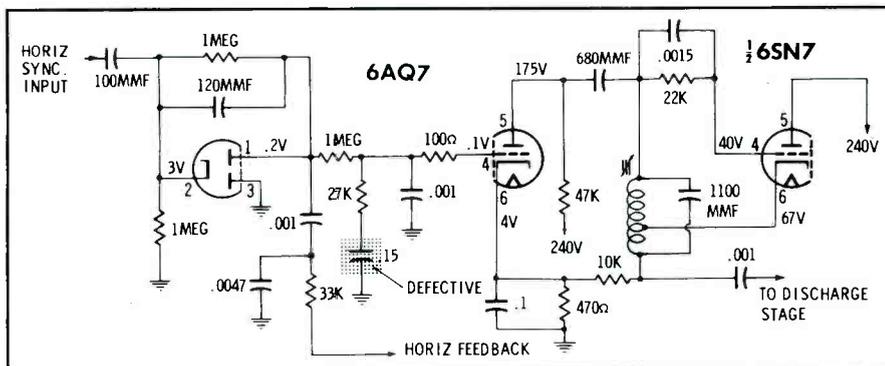


Fig. 1. Gruen horizontal AFC circuit.

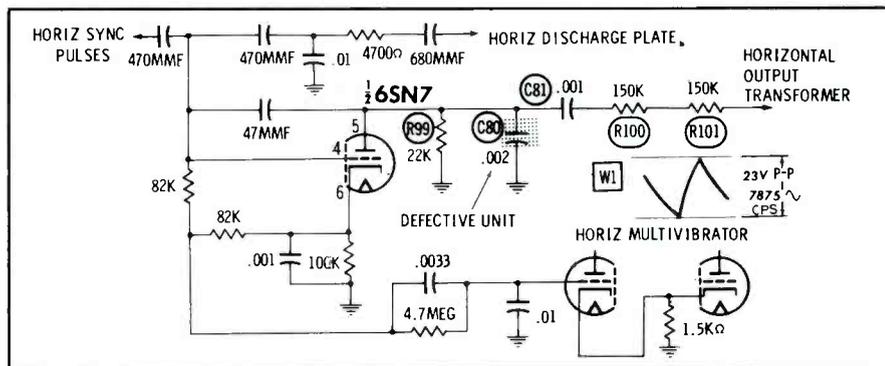


Fig. 2. Triode phase detector for horizontal AFC.

## LOOK FOR US IN THE JANUARY PF REPORTER

### TRANSISTOR APPLICATION CHART

An inventory of the transistor types used in the first 25 transistor radios to reach the market.

### AN INTRODUCTION TO COMMERCIAL SOUND SYSTEMS

Description of a typical sound installation used in a business establishment.

### SILICON RECTIFIERS

Practical information about the applications of these newly-developed units in TV power supplies.

### DRESSING UP TRADE-IN'S

A photographic history of a traded-in TV set from its first to its second owner.

### THE COLOR-KILLER CIRCUIT

How it works and how to trouble shoot it.

AND MANY OTHER INTERESTING SUBJECTS

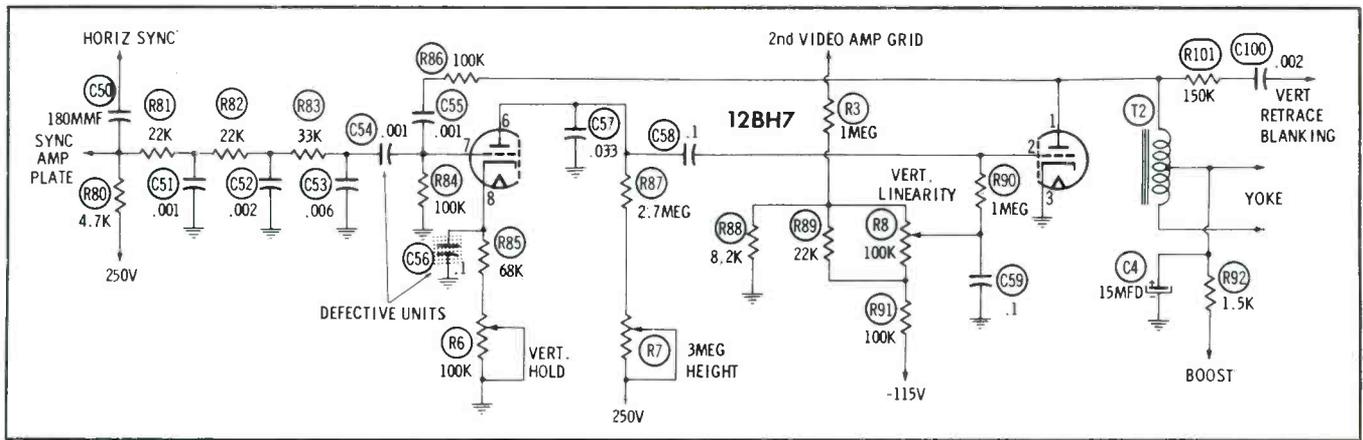


Fig. 3. RC-coupled vertical multivibrator.

# NOW FIDELITONE DIAMONDS

world's  
finest  
phonograph  
needles

ONLY **\$16.95**  
and up

PERMO, INCORPORATED

CHICAGO 26, ILL.

both vertically and horizontally during this period but become normal after the picture finally synchronized.

As stated previously, this condition existed only during the first few minutes of operation. In just about the time it took to make a few voltage readings or check and calibrate a waveform, the receiver would return to normal operation. The reader will sympathize, since this is characteristic of an intermittent trouble.

After repeated efforts by the technician, a clue to the trouble finally appeared. The feedback waveform W1 at the phase detector was a sharp pulse rather than the correct sawtooth shape. (Consult the diagram in Fig. 2.) Once this indication had been obtained, it was a simple matter to analyze the circuit and determine the source of the trouble. The network made up of R99, R100, R101, C80, and C81 is designed to shape this feedback pulse and couple it to the phase detector. Capacitor C80 was open until heat caused the poor connection to be corrected, after which the feedback pulse became normal. The initial sharp feedback pulse was causing erratic operation of the AFC phase-detector stage, which in turn caused the sweep circuits to produce a double picture.

#### Unstable Vertical Sync

In the third case of intermittent operation, the picture rolled vertically after a few minutes of operation. The picture could be locked in by adjustment of the vertical-hold control, but in a short time it began to roll again. After this cycle of events had oc-

curred three or four times, the hold control was at the limit of its range and could no longer be used to lock the picture in place.

It appeared that something, probably heat, was causing the RC time constant in the oscillator-grid circuit to change at a slow but steady rate. The schematic diagram of the vertical-oscillator section of this receiver is shown in Fig. 3. A check made of the values of R84, R85, R86 and R6 (both hot and cold) proved these resistors to be good. On the assumption that a related capacitor was defective, a check was made of C54 and C55.

After substitution of each capacitor, the receiver was given a test run. In each trial, the picture began to roll after a few minutes of operation. The old units were then returned to the circuit.

At this point, another look at the schematic and a close analysis of how the circuit performed seemed to be in order. The 0.1-mfd cathode bypass capacitor C56 could cause the trouble if it were leaky. To test this theory, heat was applied to one of the leads to the capacitor while the picture was locked in place. Immediately, the picture began to roll. Replacement of this unit cured the trouble.

As an added precaution against a call-back, however, capacitors C54 and C55 were rechecked for leakage. This proved to be wise since C54 developed leakage when it got hot. If it were not replaced, it could cause future trouble.

The leakage in C56 and possibly in C54 had allowed the bias on the stage to vary. This had the same effect as changing the RC grid time constant and thus the oscillator frequency.

These three intermittent troubles, all involving capacitors in the sync section, represent three different types of failures that can occur in a capacitor. In the first case, the capacitor was opening up as the heat in the chassis rose. In the second, an open capacitor was making contact as the heat rose, and in the third case, capacitors were developing leakage. The fact that a capacitor may fail in any of these three ways is what often makes it difficult to locate a defective capacitor that is causing an intermittent sync condition. ▲

## THE NEW WRENCH WITH THE "INNER GRIP"

WALDEN

# in-a-grip<sup>®</sup> WRENCHES

TRADE MARK PATENTS PENDING

... GRIP and DRIVE ALL HEX HOLLOW-HEAD SET SCREWS AND CAP SCREWS!

NO FUMBLING  
NO DROPPING



OVER 200 TYPES AND SIZES IN STOCK

WRITE FOR CATALOGUE

MANUFACTURED EXCLUSIVELY BY


MAKERS OF SPINTITES, GRIP SPINTITES, — FORCE-FORMED SOCKET WRENCHES — AND ALL TYPES OF MECHANICS' HAND TOOLS FOR OVER 50 YEARS

**STEVENS WALDEN Inc.**  
500 SHREWSBURY STREET  
WORCESTER, MASSACHUSETTS
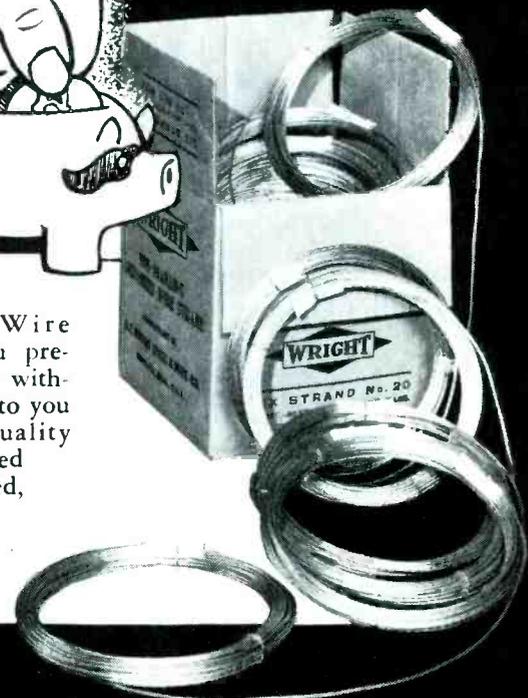
## SAVE with SECURITY



Because Wright Wire Strand comes to you pre-measured and uncoils without snarling, it gives to you unique economy. Quality wire, perfectly stranded and heavily galvanized, the bright Wright way. SAVE with Wright.



Prompt deliveries from stocks in Worcester, Chicago, Atlanta, New Orleans, Houston, Dallas and Los Angeles.

**G. F. WRIGHT STEEL & WIRE CO.**  
249 Stafford St. • Worcester, Mass.

## Shop Talk

(Continued from page 9)

nal has been received. Thereafter, the signal is treated like any normally received VHF signal. This is done for two reasons. First, VHF signals suffer less line attenuation than UHF signals and, second, VHF amplifiers provide greater amplification than similar UHF units.

Part of the expense that must be anticipated when considering master antenna system mainte-

nance is the cost of additional replacement strips or even full amplifiers. When an amplifier becomes defective, and the trouble cannot be cleared up by tube replacement, then the entire unit must be removed to the shop and a working substitute inserted in its place. Any other course of action will leave the entire system inoperative and lead to irate tenants. Television is today classed as a necessity; if only one or two tenants are affected, the situation can usually be handled without


fuss. But where there are many sets, the pressure on you may become intolerable. By having substitute replacement units available, the system can be kept in operation while the defective section is repaired at your leisure in the shop.

One of the advantages that accrues from an antenna system that you install is the extra business when one of the tenant's receivers becomes defective. When a system is installed, each of the occupants of a building is notified of this fact, generally through a direct mailing. At this time or in a subsequent mailing, mention can be made of the fact that your firm is also engaged in servicing and that their business is solicited. If this is handled properly and the system functions satisfactorily, you are certain to garner most of the service business of the building.

One of the difficulties that frequently arises after a system has been installed and is operating satisfactorily is a sizable increase in power in one or more of the stations being received. This can upset the equilibrium of your system by overdriving the amplifiers, causing picture distortion because of signal compression, sync clipping, or cross-modulation. Fortunately, any appreciable increase in radiated power is usually well publicized in advance, so that when the day arrives you can be prepared for it. The most widely used means of coping with increased signal is the insertion of pads between the antenna receiving the signal and the master amplifier. If you are using a single wideband antenna to receive several signals and a single all-channel master amplifier to amplify them, it may be necessary to set up a separate antenna for this station alone, so that the received signal can be properly attenuated. A situation such as this is one of the reasons why many prefer to use separate antennas for each received signal. It makes for a more flexible arrangement.

Of equal interest in these days of extensive construction is the effect that a tall steel building can have if it is erected between your system and the transmitting

# C-D's CUB BEST-BAR NONE

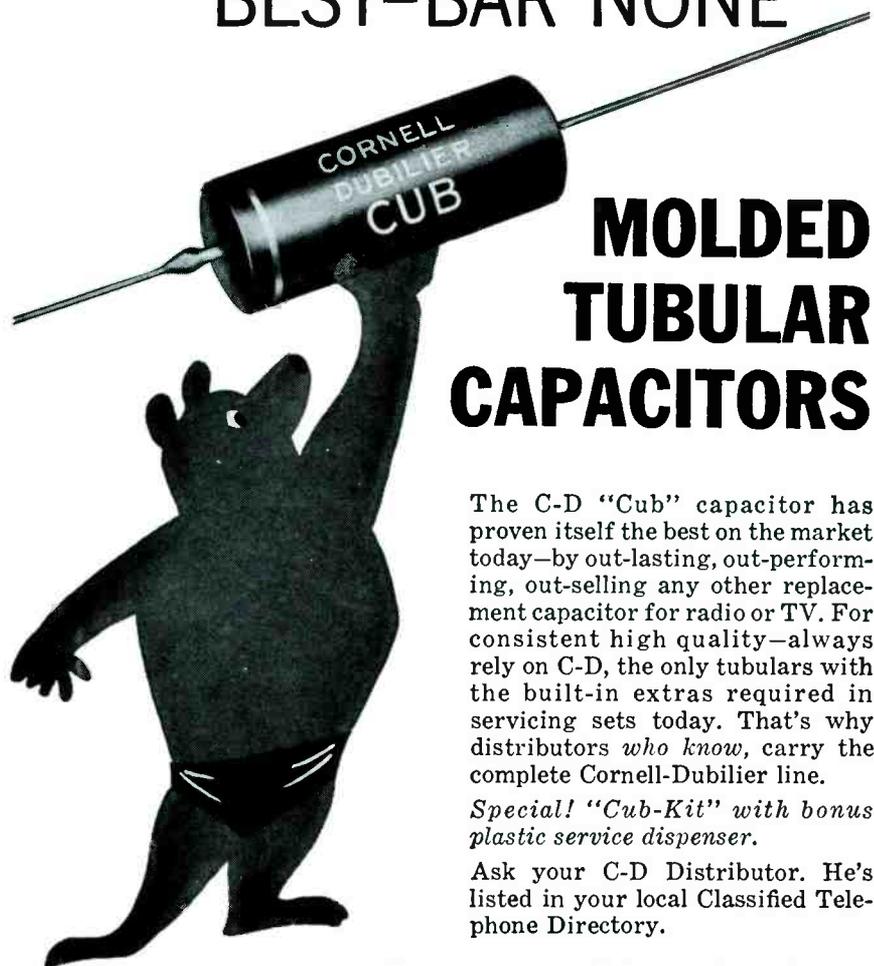

## MOLDED TUBULAR CAPACITORS

The C-D "Cub" capacitor has proven itself the best on the market today—by out-lasting, out-performing, out-selling any other replacement capacitor for radio or TV. For consistent high quality—always rely on C-D, the only tubulars with the built-in extras required in servicing sets today. That's why distributors *who know*, carry the complete Cornell-Dubilier line.

*Special! "Cub-Kit" with bonus plastic service dispenser.*

Ask your C-D Distributor. He's listed in your local Classified Telephone Directory.

*There are more C-D capacitors in use today than any other make*



CONSISTENTLY DEPENDABLE  
**CORNELL-DUBILIER CAPACITORS**

PLANTS IN SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD AND FUGUAY SPRINGS, N. C.; SUBSIDIARY: THE RADIART CORPORATION, CLEVELAND, O.

antenna. The most marked result is a significant signal decrease. This may be solved by more amplification or by antenna reorientation, or both. There are also occasions when a tall building, erected near your building but off to one side or behind you, reflects signals to your antenna system and thereby creates ghosts. Here, the answer is not more signal amplification but rather a more directive antenna. All this, of course, only underscores the fact that you cannot install a signal distribution system and forget all about it. External as well as internal conditions change and each change must be dealt with.

#### Special Test Equipment

Incidentally, signal strength is one of the prime factors in any master antenna system, and because of this, one of your most valuable (actually indispensable) servicing and installation tools is a field strength meter. With it you can measure the intensity of the signal at the antenna, before and after the master amplifier, and at various points along the distribution system. Because of the importance of the field strength meter, it is desirable that an accurate meter be employed—one whose readings are reliable and are given in actual microvolts rather than in relative indications. Several suitable instruments are available, both AC and battery-powered.

In an organization where a fair amount of master antenna work is done, it is also desirable to have a reliable standard against which field strength meters can be calibrated periodically. At Central Television Service in Chicago, a Measurement Corp. Model 80 signal generator is used for this purpose. Checks include frequency calibrations and measurements of the accuracy with which the field strength meter indicates signal intensity. The latter characteristic is, by far, the more important of the two. In a firm that does only an occasional amount of master antenna installation and servicing, it is perhaps more economical to have an outside testing company check the field strength meter. But whatever the


circumstances, it is imperative to know that your instruments are accurate.

A portable test set is also required to reveal the visual quality of the signal and to point up any ghosts that may be present. The new, small 8½" or 10" receivers serve admirably for this purpose. The same set is an excellent tenant pacifier. One of your headaches will be complaints of line failure when, in fact, it is the tenant's receiver which is at fault. By proving your point with the test set, you leave no room for doubt.
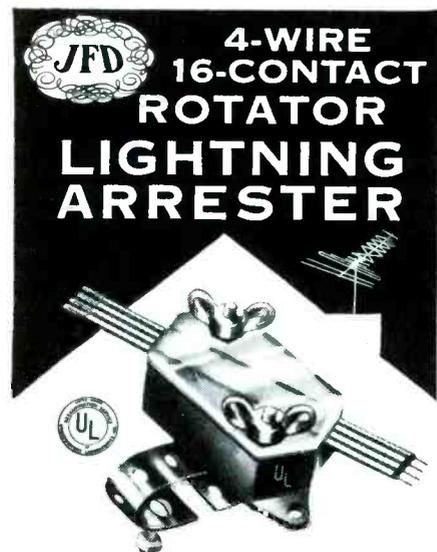
#### Color Reception

A final consideration in master antenna system installation is the reception of color television signals. These require a more uniform response over the frequency band and closer impedance matching throughout the distribution system than monochrome signals. The matching factor can be particularly important because of the visual effect that reflected signals have on color reproduction. Also, the signals developed at the antenna should be checked at both the video and color carrier frequencies to make certain their amplitudes are within 1 or 2 db of each other. If the deviation exceeds this figure, and it is not being caused by an uneven response of the antenna, then some compensation should be attempted in the master amplifier. When a single amplifier strip per channel is being used, this compensation is readily achieved. In an all-channel or wideband amplifier, similar adjustment may be difficult or even impossible. Signals should be checked at all outlets to make certain nothing in the distribution system has upset the balance.

This balance, it should be noted, refers only to the receivers along a single line or riser. It is entirely possible that the voltage levels between different risers may vary considerably. This is permissible and will lead to no difficulties unless the line shielding is inadequate to the point that appreciable radiation takes place. More information on achieving proper signal distribution will appear in next month's column. ▲



Today's only UL approved rotator lightning arrester.

16-positive contacts for sure and easy installation.

NO. **AT104** LIST **\$1.50**

(wall mounting)

**AT104S** **1.75**

(stainless steel strap)

"World's largest manufacturer of TV Lightning Arresters"



MANUFACTURING CO., Inc.  
BROOKLYN 4, NEW YORK

Sandy Says!  
For Every Need—  
**Anchor**  
Truly  
**Universal**  
UB-160 Picture Tube  
**Britener**

Use

- Parallel Boost
- Parallel Isolation Normal
- Parallel Isolation Boost
- Series Boost
- Series Isolation Normal
- Series Isolation Boost
- Electromagnetic
- Electrostatic

Ways  
AT YOUR  
DISTRIBUTOR

**anchor** products co.  
ELECTRONIC COMPONENTS  
2712 W. Montrose • Chicago 18, Ill.

**INDEX TO ADVERTISERS**

December, 1956

Advertisers	Page No.
American Microphone Co.	26
American Television & Radio Co.	34
Amperex Electronic Products, Inc.	65
Amphenol Electronics Corp.	42
Anchor Products Company	71
Anko Mfg. Co., Inc.	54
Astron Corp.	41
B & K Mfg. Co.	28
Bussmann Mfg. Co.	18
Centralab, A Div. of Globe-Union, Inc.	55, 57
Chicago Standard Transformer Corp.	20, 67
Clarostat Mfg. Co., Inc.	22
Clearbeam Antenna Corp.	6
Cornell-Dubilier Electric Corp.	70
Dynamic Electronics-New York, Inc.	51
Electro-Voice, Inc.	12
Electronic Instrument Co., Inc. (EICO)	44
Electronic Pub. Co.	32
General Electric Co.	4-5
International Resistance Co.	2nd Cover
Jackson Electrical Instr. Co.	51, 65
Jensen Industries, Inc.	34
Jerrold Electronics Corp.	37
JFD Manufacturing Co.	71
Littelfuse, Inc.	4th Cover
Luper & Sundberg	46
MacMillan Company, The	52
Mallory & Co., Inc., P. R.	30, 31
Merit Coil & Trans. Corp.	50
Ohmite Mfg. Co.	56
Perma-Power Co.	34
Permo, Inc.	68
Phaotron Co.	47
Planet Sales Corp.	64
Pyramid Electric Co.	35
Quam-Nichols Co.	60
Radiart Corp.—Cornell-Dubilier Electric Corp.	1
Radio Corp. of America	7, 27, 33, 39, 3rd Cover
Radio Receptor Co., Inc.	58
Raytheon Mfg. Co.	8
Sams & Co., Inc., Howard W.	45, 59
Sangamo Electric Co.	43
Sarkes Tarzian, Inc.	61
Service Instruments Co.	66
Simpson Electric Co.	53
Sprague Products Co.	2
Standard Coil Products Co., Inc.	10
Stevens Walden, Inc.	69
Sylvania Electric Products, Inc.	24
Tenna Mfg. Co.	29
Ungar Electric Tools, Inc.	36
University Loudspeakers, Inc.	40
Vokar Corp.	56
Westinghouse Electric Co.	49
Wright Steel & Wire Co., G. F.	69
Xcelite, Inc.	64

**PF  
REPORTER**

**CATALOG and LITERATURE SERVICE**  
valuable manufacturers' data available  
to our readers

- 1Z. B & K (B & K Mfg. Co.)**  
Bulletin 1000 describes new DYNA-SCAN picture and pattern video-generator. Explains its use in servicing black and white and color TV and how it acts as a closed-circuit TV. Bulletin 750 describes new, low-cost, lab-type Test Equipment Calibrator Model 750 that checks instrument accuracy. Also Bulletin 500 on Dyna-Quick Dynamic Mutual Conductance Tube Tester and Bulletin 400 on CRT Cathode Rejuvenator Tester. *See advertisement on page 28.*
- 2Z. BUSSMANN (Bussmann Mfg. Co.)**  
New and very comprehensive book on fuses and fuse mountings used by the electronics industries. *See advertisement page 18.*
- 3Z. CHICAGO STANDARD (Chicago Standard Transformer Corp.)**  
New 1957 STANCOR TV Transformer Replacement Library. *See advertisements pages 20, 67.*
- 4Z. CLAROSTAT (Clarostat Mfg. Co., Inc.)**  
Form No. 751774 RTV-IZE. Program of radio and TV replacement controls. *See advertisement page 22.*
- 5Z. CLEAR BEAM (Clear Beam Antenna Corp.)**  
Literature on antenna kits. *See advertisement page 6.*
- 6Z. CORNELL-DUBILIER (Cornell-Dubilier Electric Corp.)**  
Guide to electrolytic replacement capacitors, XTR200D-3E. *See advertisement page 70.*
- 7Z. DYNAMIC (Dynamic Electronics-New York, Inc.)**  
Booklet on accessories for TV, Hi-Fi, and recorders with service aids and hints. *See advertisement page 51.*
- 8Z. EICO (Electronic Instrument Co., Inc.)**  
Free 1956 Catalog shows how to save 50% on electronic test equipment in both kit and wired form: describes VTVM's, scopes, generators, tube testers, etc. *See advertisement page 44.*
- 9Z. ERIE (Erie Resistor Corp.)**  
D-56 Catalog.
- 10Z. HICKOK (Hickok Electrical Instrument Co.)**  
Brochure covering new Hickok Model 225K electronic voltmeter kit.
- 11Z. IRC (International Resistance Co.)**  
Form S-023—New dealer parts stock data. *See advertisement 2nd Cover.*
- 12Z. JENSEN (Jensen Industries, Inc.)**  
Brand New 1957 Wall Chart; completely illustrated; shows all needles (foreign and domestic) by cartridge number; also, shows number of needles in cartridge; point size and point material of each needle; list price. *See advertisement page 34.*
- 13Z. LUPER & SUNDBERG**  
Brochure describing complete line of UHF-VHF antennas, with technical information on operation. Includes charts, etc. *See advertisement page 46.*
- 14Z. MACMILLAN (The MacMillan Company)**  
Circular H-83 "Books on Electronics" describes 12 recent books, basic and advanced, on radio, TV, circuits and electronic equipment. *See advertisement page 52.*
- 15Z. MALLORY (P. R. Mallory & Co., Inc.)**  
Replacement guide for radio batteries plus price list. *See advertisements pages 30, 31.*
- 16Z. SAMS (Howard W. Sams & Co., Inc.)**  
Complete details on how to keep your Service Data library up to date with the Sams automatic monthly purchasing plan. Also complete details on the Sams popular Time Payment Plan. *See advertisements pages 45, 59.*
- 17Z. SIMPSON (Simpson Electric Co.)**  
No. 2056 Test Equipment Catalog Bulletin and No. 2052 Panel Meter Catalog Bulletin, both 6-page illustrated bulletins on enameled stock. *See advertisement page 53.*
- 18Z. VOKAR (Vokar Corp.)**  
Circuit diagram for 6-transistor superheterodyne radio. Bulletin on Vokar IF-Kit 5000. *See advertisement page 56.*
- 19Z. WARD PRODUCTS (Ward Products Corporation)**  
Picture story booklet, "The Story Behind Ward Top Quality Auto Aerials," Form 54-313. Also Form 54-309 folder on complete line of Ward auto aerials.
- 20Z. WELLER (Weller Electric Corp.)**  
Weller General Catalog.
- 21Z. WRIGHT (G. F. Wright Steel & Wire Co.)**  
Wright TV Guy Wire Circular. *See advertisement page 69.*
- 22Z. XCELITE (Xcelite, Inc.)**  
Folder on new plastic transparent screwdriver kit with zipper; catalog on screwdrivers, nut drivers, pliers. *See advertisement page 64.*

DECEMBER 1956

# SUPPLEMENT to SAMS MASTER INDEX No. 101

File this Supplement with your 36-page SAMS MASTER INDEX. Together, they give you complete PHOTOFACT coverage.

This Supplement is your handy index to new models covered in the latest PHOTOFACT Sets 328 through 341. It's your guide to the world's finest service data coverage of the current output of the new TV and Radio receivers, as well as models not previously covered in PHOTOFACT. It keeps you right up to date.

ALWAYS USE YOUR LATEST ISSUE OF THIS SUPPLEMENT WITH THE SAMS MASTER INDEX . . . TOGETHER, THEY ARE YOUR COMPLETE INDEX TO OVER 30,000 MODELS.

For models and chassis not listed in this Supplement, refer to SAMS MASTER INDEX No. 101. If you haven't a copy, send for it today. It's FREE . . . just write to HOWARD W. SAMS & CO., INC. 2201 East 46th Street, Indianapolis 5, Indiana.



FILE WITH YOUR SAMS MASTER INDEX No. 101, DATED SEPTEMBER, 1956  
**IMPORTANT: THIS SUPPLEMENT REPLACES NOVEMBER SUPPLEMENT No. 101-C**  
 Discard prior supplement, since this issue includes all previous listings plus latest models

	*Set Folder No. No.	Set Folder No. No.			
<b>ADMIRAL</b>					
Chassis 3D1B, 3D1C	321-1, 329-2				
Chassis 5W3	341-2				
Chassis 14U3B, 14U3C					
	330-13-5				
Chassis 14Y3B	333-12-5				
Chassis 20Y4H, HF	329-2				
Chassis 21A3BZ (See PCB 174—Set 341-1 and Ch. 21A3AZ—Set 275-2)					
Chassis 21B3Z (See PCB 174—Set 341-1 and Ch. 21A3AZ—Set 275-2)					
Chassis 21D3Z (See PCB 174—Set 341-1 and Ch. 21A3AZ—Set 275-2)					
Chassis 21E3Z (See PCB 174—Set 341-1 and Ch. 21A3AZ—Set 275-2)					
Chassis 21H3Z (See PCB 174—Set 341-1 and Ch. 21A3AZ—Set 275-2)					
Models CA2316Z, CA2317Z (See Ch. 21B3Z)					
Model CA2326Z (See Ch. 21B3Z)					
Model CA2326ZN (See Ch. 21B3Z)					
Model CA2327Z (See Ch. 21B3Z)					
Models CA2826Z, CA2827Z (See Ch. 21H3Z)					
Models FA2326Z, FA2327Z, FA-2328Z (See Ch. 21B3Z)					
Models L2386, L2387 (See Ch. 20Y4H)					
Models LA2326Z, LA2327Z (See Ch. 21D3Z)					
Models T101, T102, T103, T104, T105AL, T106AL, T107AL (See Ch. 14Y3B)					
Model TA2311Z (See Ch. 21B3Z)					
Model TA2311ZN (See Ch. 21B3Z)					
Model TA2312Z (See Ch. 21B3Z)					
Model TA2316Z, TA2317Z (See Ch. 21B3Z)					
Models TS2526Z, TS2527Z (See Ch. 20Y4H)					
Models TS101, TS102, TS103, TS104, TS105AL, TS106AL, TS107AL (See Ch. 14Y3B)					
Models 5B42, 5B43, 5B48 (See Ch. 5W3)					
Models 5W32, 5W33, 5W34, 5W38, 5W39 (See Ch. 5W3)					
<b>AIRLINE</b>					
GAA-954A	332-2				
GAA-978B, GAA-978C	341-3				
GAA-990B (See Model GAA-990A—Set 320-3)					
GAA-1000A	333-2				
GAA-2501B, C, GAA-2502A, B (See Model GAA-2501A—Set 308-3)					
GRX-1619A (See Model GSL-1614A—Set 289-2)					
WG-2618A, WG-2619A (See Model WG-2602A—Set 307-3)					
WG-5017A (See Model WG-4011A—Set 313-2)					
WG-5117A (See Model WG-4011A—Set 313-2)					
25GAA-997A, B, C (See Model 25GAA-996A—Set 182-2)					
45XGAA-927A	332-3				
45XGAA-947A, 45XGAA-948A, 45XGAA-949A	332-3				
45XGAA-978B, C	341-3				
2509	328-2				
<b>AMERICAN MOTORS</b>					
89Y0378 (6MA)	329-3				
<b>ARVIN</b>					
950T1, 951T1	340-2				
954P1 (Ch. RE-389) (See Model 954P—Set 300-2)					
856S (Ch. RE-412) (See Model 954P—Set 300-2)					
Ch. RE-412 (See Model 856S)					
<b>BAGPIPER</b>					
SKR101	335-2				
<b>BENDIX</b>					
K2250, U, K2251, U (Ch. T20, T20-1)	328-3				
T2150, U, T2151, U (Ch. T20, T20-1) (See Model K2250)					
<b>BIGG OF CALIF.</b>					
"George Gott" GP 30P	341-4				
7266505, 7266535	338-3				
<b>CADILLAC</b>					
7266505, 7266535	338-3				
<b>CAPEHART</b>					
2P56 (Ch. CR-218)	330-2				
3T216BD-4, -5, 3T216MD-4, -5 (Ch. CX-385)	331-7				
6T216BD-4, -5, 6T216MD-4, -5 (Ch. CX-385)	331-2				
11C216BD-4, -5, 11C216MD-4, -5 (Ch. CX-385)	331-2				
16C216BD-4, -5, 16C216FD-4, -5, 16C216MD-4, -5 (Ch. CX-385)	331-2				
46TP56B, M (Ch. CA-239)	330-3				
75C3 (Ch. CR-242)	340-3				
8BP68BN1	331-3				
Ch. CA-239 (See Model 46TP56B) Ch. CR-218 (See Model 2P56)					
Ch. CR-242 (See Model 75C3)					
Ch. CX-385 Series (See Model 3T216BD-4)					
<b>CBS-COLUMBIA</b>					
C220 (Ch. 656)	337-1				
C230, C231, C232 (Ch. 636)	337-1				
C240 (Ch. 616)	337-1				
T200, T201, T202, T203, T204 (Ch. 216)	338-1				
6K321, U, 6K322, U, 6K327U, 6K328U (Ch. 2001, 2002)	334-2				
6KR323, 6KR324, 6KR327, 6KR328 (Ch. 2001)	334-2				
6T101, 6T103, 6T104 (Ch. 2017)	333-4				
6T301, U, 6T303, U, 6T304, U (Ch. 2001, 2002)	334-2				
6TR305, 6TR306 (Ch. 2003)	338-2				
7K325, U, 7K326, U (Ch. 3001, 3002)	338-2				
7K329U, 7K330U, 7K332U (Ch. 3002)	338-2				
7K333U, 7K334U (Ch. 3012)	338-2				
7KR329, 7KR330, 7KR332 (Ch. 3003)	338-2				
7KR333, 7KR334, 7KR335, 7KR336 (Ch. 3013, 3015)	338-2				
7T307, U, 7T309, U, 7T310, U (Ch. 3001, 3002)	338-2				
7TR311, 7TR312 (Ch. 3003)	338-2				
5440 (See Model T200)	340-4				
Ch. 616 (See Model C240)					
Ch. 636 (See Model C230)					
Ch. 656 (See Model C220)					
Ch. 2001, 2002 (See Model 6K321)					
Ch. 2003 (See Model 6K323)					
Ch. 2017 (See Model 6T101)					
Ch. 3001, 3002 (See Model 7K325)					
Ch. 3003 (See Model 7K329)					
Ch. 3012 (See Model 7K332U)					
Ch. 3013, 3015 (See Model 7KR333)					
<b>CHEVOLET</b>					
987368	331-4				
<b>COLUMBIA RECORDS</b>					
412	336-1				
416	338-1				
424	331-5				
<b>CONTINENTAL (Auto Radio)</b>					
68C (4047424)	335-4				
<b>CONTINENTAL</b>					
738.44	341-5				
<b>CORONADO</b>					
RA1-9243A, RA1-9244A, RA1-9245A, B, RA1-9246A, B	337-2				
TV1-9305A (Code 17724)	335-5				
TV2-9338A, TV2-9339A, TV2-9340A, TV2-9341A	334-3				
TV1-9356A, TV1-9357A (Code 2479)	339-2				
<b>CORONADO—Cont.</b>					
TV1-9404A, TV1-9406A, TV1-9407A, TV1-9408A, TV1-9409A, TV1-9410A, TV1-9411A	340-22-5				
TV2-9324A, B, TV2-9325A, TV2-9326A, B, TV2-9327A, TV2-9334A, B, TV2-9335A, TV2-9336A, B, TV2-9337A, TV2-9350A, B, TV2-9351A, TV2-9352A, B, TV2-9353A	336-2				
<b>CROSLY</b>					
AC-10B, AC-10M, AH-10B, AT-10B, AT-10M (Ch. 487)	334-14-5				
AC-11B, AC-11M (Ch. 488)	336-16-5				
AH-11B (Ch. 488)	336-16-5				
AT-11B, AT-11M (Ch. 488)	336-16-5				
AT-70B, M, W (Ch. 481) (See Model J-17ABH—Set 332-3)					
BC-12B, BC-12M, BC-12MZ, BC-13B, BC-13M, BC-14M, BC-15M (Ch. 489, 490)	341-18-5				
BT-13M (Ch. 489, 490)	341-18-5				
J-17TABH, TAMM, TAWH (Ch. 481)	332-3				
J-21CABH, CABU, CAMH, CAMU (Ch. 483, 484)	336-3				
J-21RABH, RABU, RAMH, RAMU (Ch. 483, 484)	336-3				
J-21TABH, TABU, TAMH, TAMU, TAWH, TAWU (Ch. 483, 484)	336-3				
JC-8BK, BN, TN, WE (Ch. R-104)	340-5				
JM-8BC, BK, BN, GN, MN, WE (Ch. R-102)	334-4				
JM-8BG, BK, GNo, MNo, WNo (Ch. R-102-1) (See Model JM-8BG—Set 334-4)					
T-41BK, GN, GY, IY, RD (Ch. 41T)	341-5				
Ch. R-102 (See Model JM-8BG)					
Ch. R-104 (See Model JC-8BK)					
Ch. 41T (See Model T-41BK)					
Ch. 483, 484 (See Model J-21CABH)					
Ch. 483, 484 (See Model J-21RABH)					
Ch. 488 (See Model AC-11B)					
Ch. 489, 490 (See Model BC-12B)					
<b>DAVID BOGEN</b>					
D8130	332-4				
DO110	337-4				
FM50	337-4				
R660	336-4				
R710	330-4				
RR501B	339-3				
RR550	331-6				
<b>DEWALD</b>					
K-701-A	329-5				
<b>DUMONT</b>					
RA-346, RA-346-A4, RA-346-A5	340-6				
A50	339-4				
RA-356, RA-357	334-5				
Cambridge (See RA-356)					
Colefax (See RA-356)					
Trainer (See RA-356)					
Travis (See RA-356)					
<b>ELECTRO-VOICE</b>					
A15	341-7				
A20	340-7				
A50	339-4				
A100	337-5				
PC1	338-4				
<b>EMERSON</b>					
832B (Ch. 120266-B)	340-8				
842	332-5				
846B (Ch. 120243-D) (See Model 825B—Set 287-7)					
1146 (Ch. 120333-Z) (See PCB 159—Set 322-1 and Model 1102D—Set 299-4)					
1176 (Ch. 120292-P, V)	331-7				
1177 (Ch. 120293-T, X)	331-7				
1178 (Ch. 120292-P, V)	331-7				
1179 (Ch. 120292-T, X)	331-7				
1180 (Ch. 120292-P, V)	331-7				
1181 (Ch. 120293-T, X)	331-7				
1186 (Ch. 120299-V)	331-7				
1187 (Ch. 120300-W)	331-7				
1188 (Ch. 120299-V)	331-7				
1189 (Ch. 120300-W)	331-7				
<b>EMERSON—Cont.</b>					
1232 (Ch. 120331-H)	337-15-5				
1233 (Ch. 120332-R)	337-15-5				
1234 (Ch. 120333-Z) (See PCB 159—Set 322-1 and Model 1102D—Set 299-4)					
1246 (Ch. 120245-Z) (See PCB 159—Set 322-1 and Model 1102D—Set 299-4)					
2026A, 2028A, 2030A (Ch. 120292-P, V) (See Model 1177)					
2032A (Ch. 120299-V) (See Model 1186—Set 331-7)					
Ch. 120266-B (See Model 832B)					
Ch. 120292-P, V (See Model 1176)					
Ch. 120299-T, X (See Model 1177)					</



**SILVERTONE—Cont.**

PC-6184 (Ch. 456.38500, 456.38503, 456.42900) [See Model 6122—Set 329-13]

PC-6185 (Ch. 456.38100, 456.42700) [See Model 6122—Set 329-13]

PC-6186 (Ch. 456.38500, 456.38503, 456.42400) [See Model 6122—Set 329-13]

PC-6187 (Ch. 456.38100) [See Model 6122—Set 329-13]

PC-6190 (Ch. 456.38400, 456.38404) [See Model 5160—Set 325-12]

PC-6190A (Ch. 456.45900) [See Model 5160—Set 325-12]

PC-6191 (Ch. 456.35606, 456.42400) [See Model 5161—Set 330-10]

PC-6192 (Ch. 456.38400, 456.38404) [See Model 5160—Set 325-12]

PC-6192A (Ch. 456.45900) [See Model 5160—Set 325-12]

PC-6193 (Ch. 456.35606) [See Model 5161—Set 330-10]

PC-7106 (Ch. 456.47400) [See Model 6190A—Set 330-10]

5161 (Ch. 528.39300) ... 330-10

5171 (Ch. 528.39300) ... 330-10

6025, 6026 (Ch. 528.40400) ... 328-10

6100 (Ch. 528.43502) [See Model 5161—Set 330-10]

6100 (Ch. 528.42900, 528.43500, 528.43501) [See Model 5161—Set 330-10]

6101 (Ch. 528.38900, 528.38901, 528.38902, 528.42000, 528.42001, 528.42002) ... 330-10

6104, 6105 (Ch. 549.20030, 549.20031, 549.20032, 549.20033, 549.20034) ... 333-12

6106 (Ch. 528.43000, 528.43600, 528.43601) ... 330-10

6106 (Ch. 528.43602) [See Model 5161—Set 330-10]

6107 (Ch. 528.35001, 528.35002, 528.35003, 528.42300, 528.42301, 528.42302) ... 330-10

6108 (Ch. 528.43000, 528.43600, 528.43601) ... 330-10

6108 (Ch. 528.43602) [See Model 5161—Set 330-10]

6109 (Ch. 528.35003, 528.42300, 528.42301, 528.42302) ... 330-10

6110 (Ch. 528.43700, 528.43701) ... 330-10

6111 (Ch. 528.35303, 528.35304, 528.42100, 528.42101, 528.42102) ... 330-10

6111 (Ch. 528.42103) [See Model 5161—Set 330-10]

6112 (Ch. 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6112 (Ch. 528.43802) [See Model 5161—Set 330-10]

6113 (Ch. 528.42400) ... 330-10

6114 (Ch. 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6114 (Ch. 528.43802) [See Model 6106—Set 330-10]

6115 (Ch. 528.35603, 528.35604, 528.35606, 528.42400, 528.42401, 528.42402, 528.42403, 528.42404) ... 330-10

6115 (Ch. 528.42405) [See Model 5161—Set 330-10]

6115Y (Ch. 528.35605) ... 330-10

6116 (Ch. 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6116 (Ch. 528.43802) [See Model 6106—Set 330-10]

6117 (Ch. 528.35603, 528.35604, 528.35606, 528.42400, 528.42401, 528.42402, 528.42403, 528.42404) ... 330-10

6117 (Ch. 528.42405) [See Model 5161—Set 330-10]

6120 (Ch. 528.43900, 528.43901) ... 330-10

6121 (Ch. 528.37900, 528.37901, 528.42103, 528.42200, 528.42201, 528.42202) ... 330-10

6122 (Ch. 528.39400, 528.39401, 528.39402, 528.44300, 528.44301) ... 329-13

6123 (Ch. 528.39500, 528.39501, 528.39502, 528.42800, 528.42801, 528.42802) ... 329-13

6124 (Ch. 528.39400, 528.39401, 528.39402, 528.44300, 528.44301) ... 329-13

6126 (Ch. 528.43700, 528.43701) ... 330-10

6127 (Ch. 528.35301, 528.35302, 528.35304, 528.42100, 528.42101, 528.42102) ... 330-10

6128 (Ch. 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6128 (Ch. 528.43802) [See Model 6106—Set 330-10]

6129 (Ch. 528.35014, 528.35604, 528.35606, 528.42400, 528.42402, 528.42403, 528.42404) ... 330-10

6129 (Ch. 528.42405) [See Model 5161—Set 330-10]

6129A (Ch. 528.42400) ... 330-10

6130 (Ch. 528.35602, 528.35604, 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6130 (Ch. 528.43802) [See Model 6106—Set 330-10]

6131 (Ch. 528.35303, 528.35601, 528.35602, 528.35604, 528.42402, 528.42403, 528.42404) ... 330-10

6131 (Ch. 528.42405) [See Model 5161—Set 330-10]

6131A (Ch. 528.42400) ... 330-10

6132 (Ch. 528.38700, 528.38701, 528.38702, 528.44100, 528.44101, 528.44200) ... 329-13

6133 (Ch. 528.38600, 528.38601, 528.38602, 528.42600, 528.42601, 528.42602) ... 329-13

**SILVERTONE—Cont.**

6133 (Ch. 528.42603) [See Model 6122—Set 329-13]

6160 (Ch. 528.45500, 528.45501, 528.45600, 528.45601) ... 330-10

6161 (Ch. 528.45601) [See Model 5161—Set 330-10]

6164 (Ch. 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6164 (Ch. 528.43802) [See Model 6106—Set 330-10]

6165 (Ch. 528.42400, 528.42402, 528.42403, 528.42404) ... 330-10

6165 (Ch. 528.42405) [See Model 5161—Set 330-10]

6166 (Ch. 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6166 (Ch. 528.43802) [See Model 6106—Set 330-10]

6167 (Ch. 528.42403, 528.42404) ... 330-10

6167 (Ch. 528.42405) [See Model 5161—Set 330-10]

6170 (Ch. 528.44000, 528.44001) ... 330-10

6171 (Ch. 528.37300, 528.37301, 528.42500, 528.42501, 42502, 528.42503) ... 330-10

6172 (Ch. 528.44000, 528.44001) ... 330-10

6174 (Ch. 528.44200, 528.44201, 528.44900, 528.44901, 528.45000, 528.45001, 528.45200, 528.45201) ... 330-10

6175 (Ch. 528.38100, 528.38101, 528.38102, 528.42700, 528.42701, 528.42702) ... 329-13

6176 (Ch. 528.38500, 528.38501, 528.38502, 528.38503) ... 329-13

6176 (Ch. 528.44200, 528.44201, 528.44900, 528.44901, 528.45000, 528.45001, 528.45200, 528.45201) ... 330-10

6177 (Ch. 528.38100, 528.38101, 528.38102, 528.42700, 528.42701, 528.42702) ... 329-13

6184 (Ch. 528.38500, 528.38501, 528.38502, 528.38503) ... 329-13

6184 (Ch. 528.44200, 528.44201, 528.44900, 528.44901, 528.45000, 528.45001, 528.45200, 528.45201) ... 330-10

6185 (Ch. 528.38100, 528.38101, 528.38102, 528.42700, 528.42701, 528.42702) ... 329-13

6186 (Ch. 528.38500, 528.38501, 528.38502, 528.38503) ... 329-13

6186 (Ch. 528.44200, 528.44201, 528.44900, 528.44901, 528.45000, 528.45001, 528.45200, 528.45201) ... 330-10

6187 (Ch. 528.38100, 528.38101, 528.38102, 528.42700, 528.42701, 528.42702) ... 329-13

6190A (Ch. 528.45900, 528.45901, 528.47600, 528.47700) ... 330-10

6191 (Ch. 528.35305, 528.35601, 528.35602, 528.35604, 528.35606, 528.42400) ... 330-10

6191A (Ch. 528.45201) [See Model 5161—Set 330-10]

6192 (Ch. 528.35602, 528.35604, 528.43800, 528.43801 and Radio Ch. 528.40300) ... 330-10

6192A (Ch. 528.45900, 528.45901, 528.47600, 528.47700) ... 330-10

7003, 7004 (Ch. 132.41000) ... 341-14

7100 (Ch. 528.50000, 528.50002) ... 339-13

7100A, AY, AZ (Ch. 528.50000, 528.50002) ... 339-13

7100Y (Ch. 528.50000, 528.50002) ... 339-13

7100Z (Ch. 528.50000, 528.50002) ... 339-13

7101 (Ch. 528.50010, 528.50012, 528.50014) ... 339-13

7101A, AY, AZ (Ch. 528.50030) ... 339-13

7101Y (Ch. 528.50010, 528.50012, 528.50014) ... 339-13

7101Z (Ch. 528.50010, 528.50012, 528.50014) ... 339-13

7102 (Ch. 528.50020, 528.50021, 528.50022) ... 339-13

7103, R, S, T (Ch. 528.50030) ... 339-13

7106 (Ch. 528.47600) [See Model 6190A—Set 330-10]

7107 (Ch. 528.47700, 528.47701) [See Model 6190A—Set 330-10]

7108 (Ch. 528.47600) [See Model 6190A—Set 330-10]

7110 (Ch. 528.50000, 528.50002) ... 339-13

7110A (Ch. 528.50020, 528.50021, 528.50022) ... 339-13

7111 (Ch. 528.50010, 528.50012, 528.50014) ... 339-13

7111 (Ch. 528.50030) ... 339-13

7112 (Ch. 528.50000, 528.50002) ... 339-13

7112A (Ch. 528.50020, 528.50021, 528.50022) ... 339-13

7113 (Ch. 528.50010, 528.50012, 528.50014) ... 339-13

7113A (Ch. 528.50030) ... 339-13

7126 (Ch. 528.50000, 528.50002) ... 339-13

7126A (Ch. 528.50020, 528.50021, 528.50022) ... 339-13

7127 (Ch. 528.50010, 528.50012, 528.50014) ... 339-13

7127A (Ch. 528.50030) ... 339-13

7212, 7213 (Ch. 528.33000) [See Model 4217—Set 303-13]

Ch. 132.40500 [See Model 2014]

Ch. 132.41000 [See Model 7003]

Ch. 456.35606 [See Model PC-6115]

Ch. 456.37300 [See Model PC-6171]

Ch. 456.37700 [See Model PC-6170]

Ch. 456.37900 [See Model PC-6121]

Ch. 456.37901 [See Model PC-6121]

**SILVERTONE—Cont.**

Ch. 456.38100 [See Model PC-6175]

Ch. 456.38200 [See Model PC-6110]

Ch. 456.38204 [See Model PC-6110]

Ch. 456.38400 [See Model PC-6114]

Ch. 456.38404 [See Model PC-6114]

Ch. 456.38500 [See Model PC-6174]

Ch. 456.38503 [See Model PC-6174]

Ch. 456.38600 [See Model PC-6133]

Ch. 456.38700 [See Model PC-6132]

Ch. 456.38702 [See Model PC-6132]

Ch. 456.38800 [See Model PC-6132]

Ch. 456.38801 [See Model PC-6100]

Ch. 456.38900 [See Model PC-6101]

Ch. 456.39000 [See Model PC-6106]

Ch. 456.39002 [See Model PC-6106]

Ch. 456.39100 [See Model PC-6120]

Ch. 456.39101 [See Model PC-6122]

Ch. 456.39500 [See Model PC-6123]

Ch. 456.42000 [See Model PC-6120]

Ch. 456.42001 [See Model PC-6107]

Ch. 456.42002 [See Model PC-6115]

Ch. 456.42403 [See Model PC-6115]

Ch. 456.42405 [See Model PC-6115]

Ch. 456.42406 [See Model PC-6171]

Ch. 456.42407 [See Model PC-6133]

Ch. 456.42601 [See Model PC-6175]

Ch. 456.42701 [See Model PC-6175]

Ch. 456.43500 [See Model PC-6160]

Ch. 456.43700 [See Model PC-6106]

Ch. 456.43800 [See Model PC-6114]

Ch. 456.44000 [See Model PC-6170]

Ch. 456.44400 [See Model PC-6120]

Ch. 456.44500 [See Model PC-6174]

Ch. 456.45900 [See Model PC-6190A]

Ch. 456.45600 [See Model PC-6161]

Ch. 456.45500 [See Model PC-6160]

Ch. 456.45502, 528.35002, 528.35003 [See Model 6107]

Ch. 528.35301, 528.35302 [See Model 6127]

Ch. 528.35303, 528.35304 [See Model 6129]

Ch. 528.35305 [See Model 6129]

Ch. 528.35601, 528.35602 [See Model 6129]

Ch. 528.35603, 528.35604, 528.35605 [See Model 6115]

Ch. 528.37300, 528.37301 [See Model 6171]

Ch. 528.37900, 528.37901 [See Model 6171]

Ch. 528.38100, 528.38101, 528.38102 [See Model 6175]

Ch. 528.38500, 528.38501, 528.38502, 528.38503 [See Model 6175]

Ch. 528.38600, 528.38601, 528.38602 [See Model 6133]

Ch. 528.38700, 528.38701, 528.38702 [See Model 6132]

Ch. 528.38900, 528.38901, 528.38902 [See Model 6101]

Ch. 528.39300 [See Model 5161]

Ch. 528.39400, 528.39401, 528.39402 [See Model 6123]

Ch. 528.39500, 528.39501, 528.39502 [See Model 6123]

Ch. 528.40400 [See Model 6025]

Ch. 528.42000, 528.42001, 528.42002 [See Model 6101]

Ch. 528.42100, 528.42101, 528.42102 [See Model 6111]

Ch. 528.42103 [See Model 6121]

Ch. 528.42200, 528.42201, 528.42202 [See Model 6121]

Ch. 528.42300, 528.42301, 528.42302 [See Model 6107]

Ch. 528.42400 [See Model 6131]

Ch. 528.42401, 528.42402, 528.42403, 528.42404 [See Model 6115]

Ch. 528.42405 [See Model 6115]

Ch. 528.42500, 528.42501, 528.42502, 528.42503 [See Model 6171]

Ch. 528.42600, 528.42601, 528.42602 [See Model 6133]

Ch. 528.42700, 528.42701, 528.42702 [See Model 6175]

Ch. 528.42800, 528.42801, 528.42802 [See Model 6123]

Ch. 528.42900 [See Model 6106]

Ch. 528.43000 [See Model 6106]

Ch. 528.43500, 528.43501 [See Model 6106]

Ch. 528.43502 [See Model 6100]

Ch. 528.43600, 528.43601 [See Model 6106]

Ch. 528.43700, 528.43701 [See Model 6106]

Ch. 528.43800, 528.43801 [See Model 6130]

Ch. 528.43802 [See Model 6112]

Ch. 528.43900, 528.43901 [See Model 6120]

Ch. 528.44000, 528.44001 [See Model 6170]

Ch. 528.44100, 528.44101 [See Model 6170]

Ch. 528.44200 [See Model 6132]

Ch. 528.44201, 528.44202 [See Model 6174]

Ch. 528.44300, 528.44301 [See Model 6174]

Ch. 528.44900, 528.44901 [See Model 6174]

Ch. 528.45000, 528.45001 [See Model 6174]

Ch. 528.45200, 528.45201 [See Model 6174]

Ch. 528.45500, 528.45501 [See Model 6106]

Ch. 528.45600, 528.45601 [See Model 6106]

Ch. 528.45900, 528.45901 [See Model 6190A]

Ch. 528.47700 [See Model 6190A]

Ch. 528.50000 [See Model 7100]

Ch. 528.50002 [See Model 7100]

Ch. 528.50010 [See Model 7101]

Ch. 528.50012 [See Model 7101]

**SILVERTONE—Cont.**

Ch. 528.50014 [See Model 7101]

Ch. 528.50020 [See Model 7100A]

Ch. 528.50021 [See Model 7100A]

Ch. 528.50022 [See Model 7100A]

Ch. 528.50023 [See Model 7100A]

Ch. 528.50024 [See Model 7100A]

Ch. 528.50025 [See Model 7100A]

Ch. 528.50026 [See Model 7100A]

Ch. 528.50027 [See Model 7100A]

Ch. 528.50028 [See Model 7100A]

Ch. 528.50029 [See Model 7100A]

Ch. 528.50030 [See Model 7100A]

Ch. 549.20030, 549.20031, 549.20032, 549.20033, 549.20034 [See Model 6104]

**SPARTAN**

1115 Series ... 339-14

1116 Series ... 340-17

Chassis CMUA4658B, CMUA4668B, CMUA4698B, CMUA4738B (1115 Series) ... 339-14

Chassis CMUA4758B, CMUA4768B, CMUA4798B, CMUA4808B, CMUA4818B (1116 Series) ... 340-17

Chassis CTA4658B, CTA4668B, CTA4698B, CTA4738B (1115 Series) ... 339-14

Chassis CTA4758B, CTA4768B, CTA4798B, CTA4808B, CTA4818B (1116 Series) ... 340-17

**SPARTAN**

5290, 5296, 5297 (Ch. 255D202 and Power Ch. 25D202) [See Photofact Servicer Set 336]

20312, 20313 (Ch. 24U213) [See Photofact Servicer Set 334]

21322, 21324 (Ch. 24U213) [See Photofact Servicer Set 334]

Ch. 25D202 [See Model 5290]

Ch. 24U213 [See Model 20312]

Ch. 25D202 [See Model 5290]

**STEELMAN**

3AR4 ... 340-18

3R4 ... 333-13

**STUDEBAKER**

AC-2745, AC-2747 ... 333-14

**SYLVANIA**

14P101, 14P102 Series (Ch. 1-525-1, -2) ... 339-18-5

21C401, 21C403 Series (Ch. 1-532-1, -2) ... 328-11

21C401, 21C404, 21C405 (Ch. 1-532-3, -4) ... 341-15

21C508, 21C509 (Ch. 1-532-5, -6, -7) ... 341-15

21T101, 21T102, 21T104 Series (Ch. 1-532-1, -2) ... 328-11

21T101, 21T102, 21T104, 21T105, 21T106, 21T110 (Ch. 1-532-3, -4) ... 341-15

21T207, 21T208 (Ch. 1-532-5, -6, -7) ... 341-15

24T101 Series (Ch. 1-532-1, -2) ... 328-11

24T101 (Ch. 1-532-3, -4, -4, -7) ... 341-15

24T201 (Ch. 1-532-5, -6, -7) ... 341-15

919 (Ch. 1-609) ... 329-14

949 (Ch. 1-609) ... 329-14

Ch. 1-525-1, -2 [See Model 14P101 Series]

Ch. 1-532-3, -4 [See Model 21C401]

Ch. 1-532-5, -6, -7 [See Model 21C508]

Ch. 1-609 [See Model 919]

**TELEFUNKEN**

"Jubilee" ... 339-15

Opus No. 6 (Ch. A, B) ... 341-16

**TRAVLER**

517-106, 517-107, 521-111, 521-112 (Ch. 520B5, 520B05) ... 333-15

517-106, 517-107 (Ch. 520A5) ... 330-11

517-106, 517-107 (Ch. 520A5) ... 338-10

521-111, 521-112 (Ch. 520C5) ... 330-11

521-111, 521-112 (Ch. 520A5) ... 338-10

617-33, 617-34 (Ch. 627A6) ... 337-14

617-73 (Ch. 627-16) ... 335-14

621-20, 621-21, 621-22, 621-25, 621-26 (Ch. 612M6) ... 334-10

621-20, 621-21U, 621-22U, 621-25U, 621-26U (Ch. 421E5, 421G5, 421M6) ... 331-14

621-30, 621-31, 621-32 (Ch. 627A6) ... 337-14

621-R40 (Ch. 627A6) ... 337-14

621-74, 621-75, 621-76 (Ch. 627-16) ... 335-14

Ch. 412M6 [See Model 621-20]

Ch. 421E5, 421G5, 421M6 [See Model 621-20U]

Ch. 520A5 [See Model 517-106]

Ch. 520B5, 520B05 [See Model 51

Set No.	Folder No.
ZENITH—Cont.	
22222C, E, R, Y [Ch. 17221]	331-16-5
22229R, RU, Z2230E, EU, R, RU [Ch. 19222, U]	341-17
22229RD, Z2230ED, RD [Ch. 19Y22] [See Model Y2229R—Set 334-13]	
22232E, R [Ch. 17Y22] [See Model Y2232E—Set 335-19]	
22247E, H, R [Ch. 17222]	331-16-5
22248E, H, R, Z2250, E, R [Ch. 17Y22] [See Model Y2232E—Set 335-19]	
22255E, EU, R, RU, Z2257E, EU, M, MU, R, RU [Ch. 19222, U]	341-17
22258E, H, R [Ch. 17222]	331-16-5

Set No.	Folder No.
ZENITH—Cont.	
22282E, R [Ch. 17222]	331-16-5
22359, U, Z2360R, RU [Ch. 22220, U]	340-21
22636Y [Ch. 17X23] [See Model X2636E—Set 338-12]	
23000E, R, Z3004E, R, Z3006E, R, Z3008E, R [Ch. 17222G]	331-16-5
Z3010E, EU, H, HU, R, RU, Y, YU [Ch. 19222G, GU]	341-17
Z3012H, HU, R, RU, Z3014H, HU, R, RU [Ch. 22220G, GU]	340-21
3Y02 [See Model HFY17E]	
5Y01 [See Model Y513F]	
5Z03 [See Model Z522]	
7Y02 [See Model Y724G]	
7Y03 [See Model Y733G]	
7Y04 [See Model Y723G]	

Set No.	Folder No.
ZENITH—Cont.	
12X21 [See Model HFY17E]	
16Y20, U [See Model Y1814Y]	
16Z20 [See Model Z1814R]	
16Z21 [See Model Z1816C]	
17X23 [See Model X2636E]	
17Y20, U [See Model Y2220R]	
17Y22, U [See Model Y2232E]	
17Z21 [See Model Z2222C]	
17Z22 [See Model Z2247E]	
17Z22G [See Model Z3000E]	
19Y22, U [See Model Y2229R]	
19Z22 [See Model Z2255E]	
19Z22G, GU [See Model Z3010E]	
19Z22, U [See Model Z2229R]	
22Y21, U [See Model Y2671R]	
22Z20G, GU [See Model Z3012H]	
22Z20, U [See Model Z2359]	

Set No.	Folder No.
RECORD CHANGERS	
CHRYSLER	
Highway Hi-Fi	335-3
GARRARD	
RC88, RC98	338-5
MIRACORD	
XA-100	337-12
MIRAPHON	
XM110, XM110A	335-11
MOTOROLA	
VM8C, VM9RC, VM10RC [See PFF290-11]	

Set No.	Folder No.
RECORDERS	
AMPRO	
745 "Career"	333-3
BELL	
RT-75	329-4
PENTRON	
T-90	331-10
RC	
SRT-401, SRT-402	332-11
7-TR-2, 7-TR-3	340-16
SILVERTONE	
6072A [Ch. 567.34003 ond Amp. Ch. 567.35009] [See Model 4072—Set 297-8]	
WEBCOR	
2611, 2612	328-13

NOTE: PCB Denotes Production Change Bulletin. • Denotes Television Receiver. S Denotes Schematic Coverage Only.

# Free!

to Service Technicians Only

## THE NEW SAMS INDEX TO PHOTOFACT FOLDERS


it keeps you up-to-the-minute on receiver coverage

PHOTOFACT Folders give you the world's finest Service data on TV and radio models just as soon as they hit the market. Now—with the new INDEX SYSTEM to PHOTOFACT, you locate the *latest* PHOTOFACT coverage *immediately*.

If you're a Service Technician, you can get the new Sams Index FREE. Here's how it keeps you up-to-date on receiver coverage: The Master Index (36 pages—issued twice yearly) is the complete reference to *all* PHOTOFACT Folders produced up to the date of its issue. In addition, you get an Index Supplement each month covering that month's releases of PHOTOFACT Folders. Thus, the Master Index *plus* the supplements keep you right up with current PHOTOFACT coverage. (The Index Supplements also appear each month in "PF Reporter" Magazine.)

It's easy to get your complete Index service to PHOTOFACT at NO COST TO YOU. If you're a Service Technician, just fill in the coupon and mail to us today. It will bring the Master Index direct to your shop, and monthly supplements will be mailed to you regularly thereafter. You'll KEEP RIGHT UP-TO-THE-MINUTE ON PHOTOFACT COVERAGE—you'll be able to locate the data you need on over 30,000 models, as well as on CURRENT MODEL RELEASES.

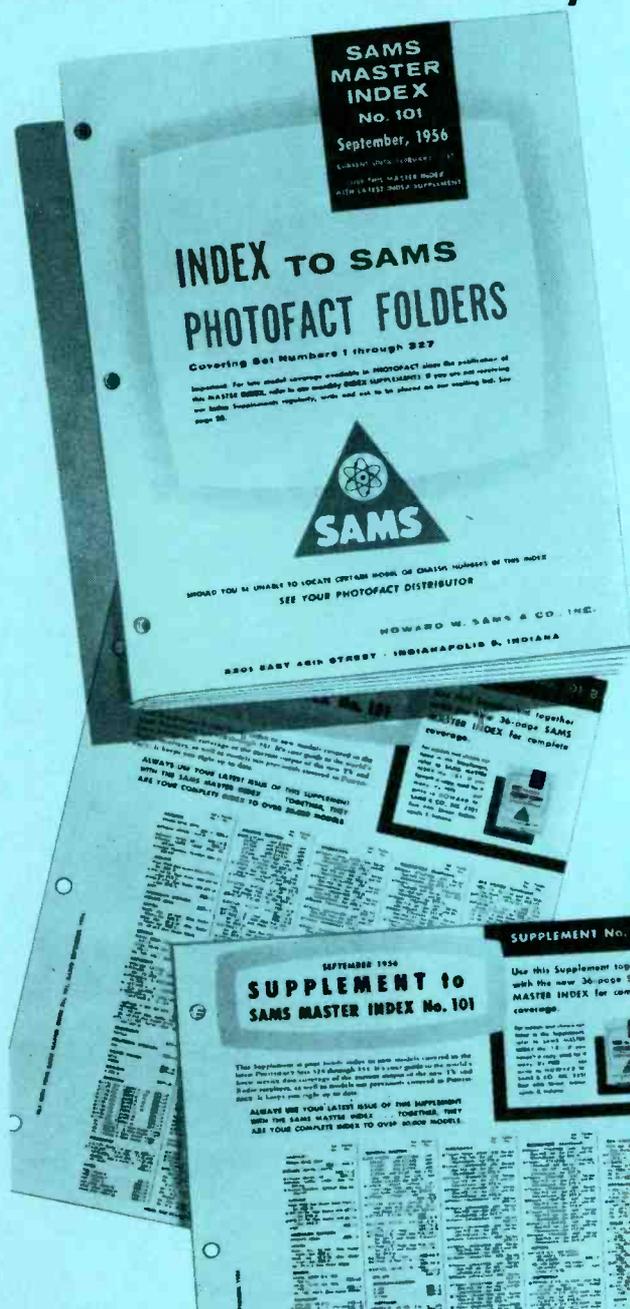Mail coupon today for your free subscription to the Sams Photofact Index



### HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc.  
2203 E. 46th St., Indianapolis 5, Indiana

Send me your FREE Master Index to PHOTOFACT Folders (twice yearly), and put me on your mailing list to receive all Index Supplements. My letter-head and/or business card is attached.

I am a Service Technician:  full time;  part time.

My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn: \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**free!**  
TO SERVICE  
TECHNICIANS



*Important features of RCA RECEIVING TUBES  
for dependable replacement in radio, phono, and TV sets!*

“Low Background Noise...Long Life...Electrical Uniformity” are technical terms your service customers may not appreciate when talking to you about set troubles. But they do know when you have restored their sets to “like new” performance.

When the trouble is tube failure, you certainly want to minimize “tube juggling” and circuit realigning... to complete the service job quickly, confidently, profitably—with full customer satisfaction.


RCA enables you to give full customer satisfaction by controlling the quality of your replacement tubes. RCA’s “don’t spare the quality” selection of raw materials, stringent control of all manufacturing processes and techniques, second-to-none final inspection and testing methods are your assurance of tubes with low background noise, long life, electrical uniformity—your assurance that RCA RECEIVING TUBES are your most dependable replacement tubes!



**RECEIVING TUBES**

RADIO CORPORATION OF AMERICA  
TUBE DIVISION • HARRISON, N. J.

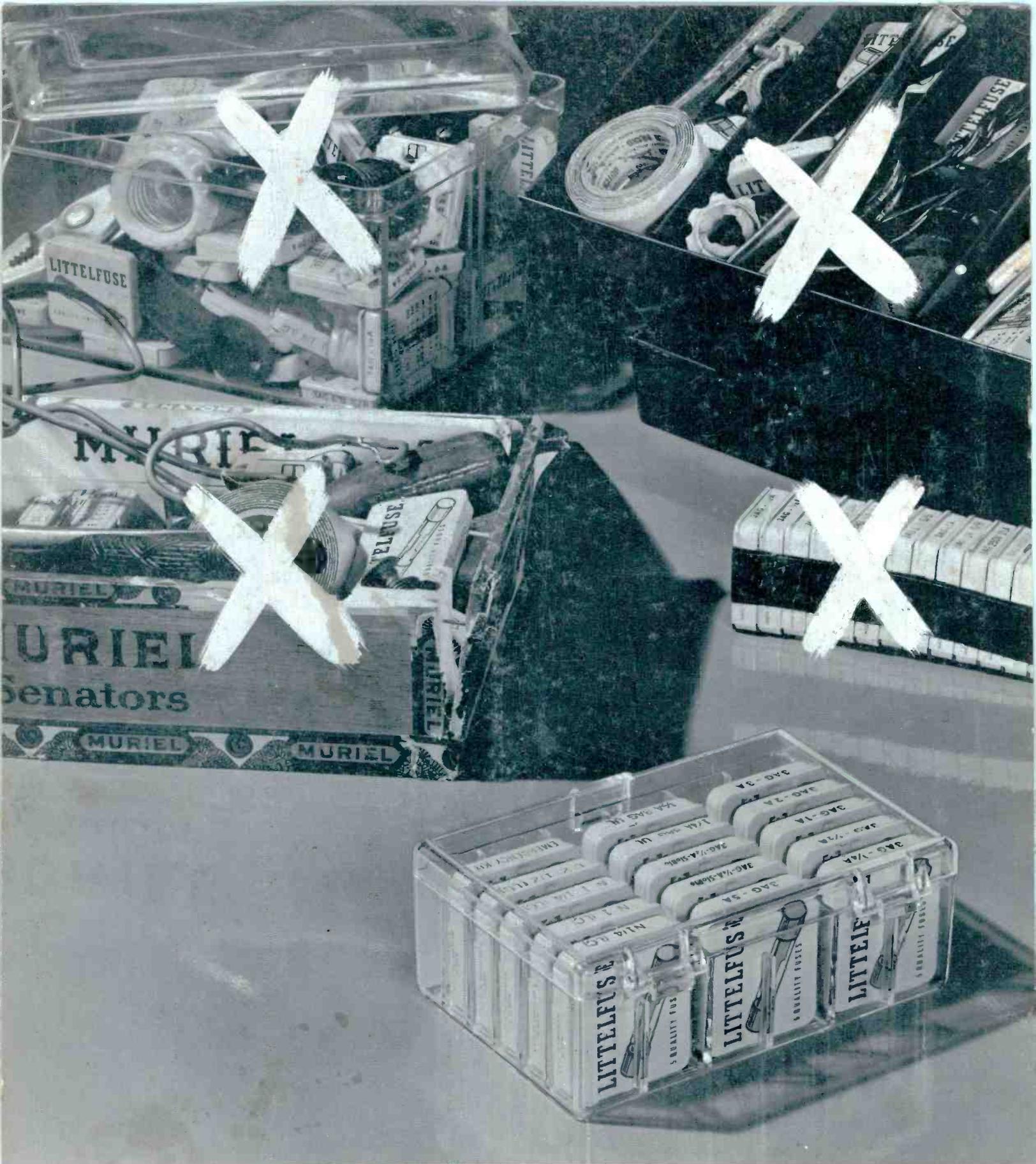**ALWAYS USE DEPENDABLE-QUALITY TUBES... RCA TUBES**



Burton browne advertising

## THERE'S ONLY ONE RIGHT WAY

A fuse caddy for your tube caddy: 18 individual compartments for fingertip selection. The fuse caddy is complete with the 15 boxes of fuses required to service 93% of all TV sets. Three spare compartments are provided for additional fuses of your own selection.

**LITTELFUSE** Des Plaines, Ill.