

INFRARED SYSTEMS FOR WIRELESS STEREO

Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

OCTOBER 1977/\$1.25




**TELETYPEWRITER
FUNDAMENTALS
FOR COMPUTER
HOBBYISTS, HAMS
& SWL'ers**

**How To Design TTL
Digital Systems**
**Build a Low-cost,
High-sensitivity
SWR Meter**

**TESTED
THIS ISSUE:**

**Sony EL-5 Elcaset, Scott R376
AM/Stereo FM Receiver, Hy-Gain
2716 AM Mobile CB Transceiver**

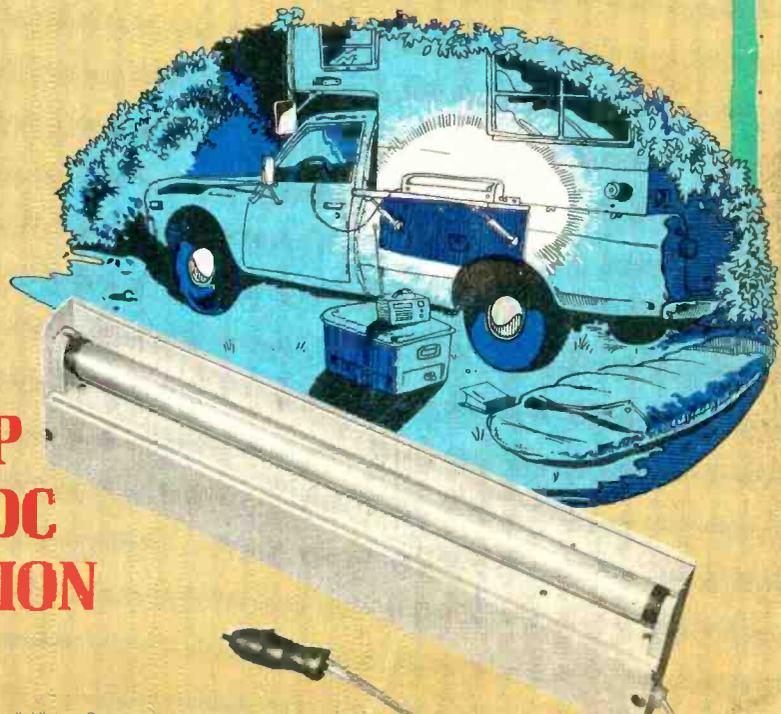**BUILD A
FLUORESCENT LAMP
FOR 12 VDC
OPERATION**



The Cobra 50XLR CB has it all. AM/FM Stereo. Cassette. And CB. All in one compact unit. All engineered to bring you the same loud and clear sound Cobra is famous for.

The remote mike houses the channel selector, squelch control, and channel indicator. So all you need for talking CB is right there in your hand. The cassette player features through the dial loading and four-way fader control.

Because they're only five inches deep, there's a Cobra in-dash radio to fit almost any car with little or no modification to the dash. This feature, plus the step-by-step Installation Manual and Universal

Installation Kit makes them the easiest in-dash radios to install. And our Nationwide network of Authorized Service Centers makes them the easiest to service.

There are four Cobra in-dash models to choose from including AM/FM/Stereo/8-track/CB. But no matter which you choose you can be sure of getting the best sounding radio going. The ultimate car radio.

The Cobra.


Cobra[®]

Punches through loud and clear.

Cobra Communications Products
DYNASCAN CORPORATION
6460 W. Cortland St., Chicago, Illinois 60635

Write for color brochure
EXPORTERS: Empire • Plainview, N.Y. • CANADA: Atlas Electronics • Toronto
Subject to FCC type acceptance.

CIRCLE NO. 11 ON FREE INFORMATION CARD

THE ULTIMATE CAR RADIO.



Security is Mallory.

With Mallory Security Products on the job, intruders get the message loud and clear, anyplace, anytime. For the few dollars they cost,

here are mighty effective ways to signal forced entry of a building, home, apartment, office, automobile.

Put the Mallory CA3 Intrusion Alarm in your living room, for instance. It'll easily pass for a radio or stereo tuner while transmitting a 20-foot ultrasonic wavelength field. One that will detect the slightest intruder movement and activate an alarm. This compact area-and-perimeter device comes with solid-state



circuitry and big reliability. And a wide variety of indoor and outdoor warning accessories to choose from—

bells, horns, sirens, rotating red lights, tape switches, many more.

For automobile security, install the Mallory ABA1 Car Alarm with entry sensing and instant siren alert for doors, hood and trunk. It comes as an easy-to-install kit, complete with switches, wire, keys, warning decals.

From any angle, Mallory Security Products mean protection. See your Mallory distributor. Or send for our Security Products Bulletin No. 9-654.

Mallory Distributor Products Company. A division of P. R. Mallory & Co. Inc., Box 1284, Indianapolis, Indiana 46206. (317) 856-3731.



**Mallory CA3 Intrusion Alarm
and ABA1 Car Alarm.**

MALLORY

Capacitors • Controls • Fastening Devices • Resistors • Security Products • Semiconductors • Solderless Terminals • Switches

CIRCLE NO. 30 ON FREE INFORMATION CARD

SWTPC announces first dual minifloppy kit under \$1,000



Now SWTPC offers complete best-buy computer system with \$995 dual minifloppy, \$500 video terminal/monitor, \$395 4K computer.



\$995 MF-68 Dual Minifloppy

You need dual drives to get full benefits from a minifloppy. So we waited to offer a floppy until we could give you a dependable dual system at the right price.

The MF-68 is a complete top-quality minifloppy for your SWTPC Computer. The kit has controller, chassis, cover, power supply, cables, assembly instructions, two highly reliable Shugart drives, and a diskette with the Floppy Disk Operating System (FDOS) and disk BASIC. (A floppy is no better than its operating system, and the MF-68 has one of the best available.) An optional \$850 MF-6X kit expands the system to four drives.



\$500 Terminal/Monitor

The CT-64 terminal kit offers these premium features: 64-character lines, upper/lower case letters, switchable control character printing, word highlighting, full cursor control, 110-1200 Baud serial interface, and many others. Separately the CT-64 is \$325, the 12 MHz CT-VM monitor \$175.



\$395 4K 6800 Computer

The SWTPC 6800 comes complete with 4K memory, serial interface, power supply, chassis, famous Motorola MIKBUG® mini-operating system in read-only memory (ROM), and the most complete documentation with any computer kit. Our growing software library includes 4K and 8K BASIC (cassettes \$4.95 and \$9.95; paper tape \$10.00 and \$20.00). Extra memory, \$100/4K or \$250/8K.

Other SWTPC peripherals include \$250 PR-40 Alphanumeric Line Printer (40 characters/line, 5 x 7 dot matrix, 75 line/minute speed, compatible with our 6800 computer and MITS/IMSAI); \$79.50 AC-30 Cassette Interface System (writes/reads Kansas City standard tapes, controls two recorders, usable with other computers); and other peripherals now and to come.

Enclosed is:

- _____ \$1,990 for the full system shown above (MF-68 Minifloppy, CT-64 Terminal with CT-VM Monitor).
- _____ \$995 for the Dual Minifloppy
- _____ \$325 for the CT-64 Terminal
- _____ \$175 for the CT-VM Monitor
- _____ \$395 for the 4K 6800 Computer

- _____ \$250 for the PR-40 Line Printer
- _____ \$79.50 for AC-30 Cassette Interface
- _____ Additional 4K memory boards at \$100
- _____ Additional 8K memory boards at \$250
- _____ Or BAC # _____ Exp. Date _____
- _____ Or MC # _____ Exp. Date _____

Name _____ Address _____
City _____ State _____ Zip _____

CIRCLE NO. 54 ON FREE INFORMATION CARD



Southwest Technical Products Corp.

219 W. Rhapsody, San Antonio, Texas 78216
London: Southwest Technical Products Co., Ltd.
Tokyo: Southwest Technical Products Corp./Japan

Coming Next Month

BUILD AN AUDIO COMPANDER

ADD SYNTHESIZED SOUNDS TO ANY MODEL RAILROAD

HOW TO DRESS UP YOUR PROJECTS

PIRACY ON THE AIRWAVES

TEST REPORTS:

- Dual 1245
- Automatic Turntable
- Burwen DNF 1201A
- Noise Reduction System
- Radio Shack TRC-449
- CB Mobile Transceiver

POPULAR ELECTRONICS, October 1977, Volume 12, Number 4. Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S. \$12.00. Possessions and Canada: \$15.00; all other countries, \$18.00 (cash orders only, payable in U.S. currency). Second Class postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada, and for payment of postage in cash.

POPULAR ELECTRONICS including ELECTRONICS WORLD, Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature.

COPYRIGHT © 1977 BY ZIFF-DAVIS PUBLISHING COMPANY. ALL RIGHTS RESERVED.


Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review.

Material in this publication may not be reproduced in any form without permission. Requests for permission should be directed to Jerry Schneider, Rights and Permissions, Ziff-Davis Publishing Co., One Park Ave., New York, NY 10016.

Editorial correspondence: POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models.

Forms 3579 and all subscription correspondence: POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address. Include your old address, enclosing, if possible, an address label from a recent issue.

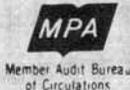The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



Feature Articles

- 32 THE ELCASET HAS ARRIVED / *Julian Hirsch*
- 43 TELETYPEWRITER FUNDAMENTALS
FOR HAMS, SWL'ERS & COMPUTER HOBBYISTS / *Larry Kahaner*
- 52 RECHARGEABLE BATTERIES FOR CONSUMER PRODUCTS
- 56 HOW TO DESIGN TTL DIGITAL SYSTEMS / *Jim Huffman*
- 69 A POWER NOMOGRAPH / *Mark L. McWilliams*
- 70 INFRARED SYSTEMS FOR WIRELESS STEREO / *Arthur Makosinski*

Construction Articles

- 49 HEX-TO-ASCII CONVERTER FOR YOUR TVT-6 / *Don Lancaster*
- 53 BUILD A FLUORESCENT UTILITY LAMP / *Joe Duncan*
Operates from a 12-volt dc source.
- 59 HIGH SENSITIVITY SWR METER
FOR LOW-POWER COMMUNICATIONS EQUIPMENT / *William Vancura*
- 66 1/2-OCTAVE REAL TIME AUDIO ANALYZER, PART 2 / *Bob Jones & Richard Marsh*
Test and calibration procedures and how to add optional Logarithmic Converter.

Columns

- 22 STEREO SCENE / *Ralph Hodges*
The Big June Trial Balloon.
- 80 SOLID STATE / *Lou Garner*
Hooray for Arrays.
- 88 EXPERIMENTER'S CORNER / *Forrest M. Mims*
IC Voltage Regulators
- 90 HOBBY SCENE Q&A / *John McVeigh*
- 94 CB SCENE / *Ivan Berger*
Trends in CB.
- 97 COMPUTER BITS / *Leslie Solomon*
More Good News for the Computer Group.

Julian Hirsch Audio Reports

- 34 SONY MODEL EL-5 ELCASET TAPE DECK
- 35 H. H. SCOTT MODEL R376 STEREO RECEIVER
- 39 SHURE MODEL 516EQ MICROPHONE

Electronic Product Test Reports

- 91 HY-GAIN MODEL 2716 MOBILE AM CB TRANSCEIVER
- 93 CONTINENTAL SPECIALTIES MODEL MAX-100 FREQUENCY COUNTER

Departments

- 4 EDITORIAL / *Art Salsberg*
The Future of Home Computers.
- 12 LETTERS
- 14 OUT OF TUNE
"How to Convert a 'Four Banger' for Stopwatch Functions" (August 1977)
- 16 NEW PRODUCTS
- 17 NEW LITERATURE
- 102 ELECTRONICS LIBRARY
- 103 OPERATION ASSIST

JOSEPH E. MESICS
Publisher

ARTHUR P. SALSBERG
Editorial Director

LESLIE SOLOMON
Technical Editor

JOHN R. RIGGS
Managing Editor

IVAN BERGER
Senior Editor

ALEXANDER W. BURAWA
Features Editor

EDWARD I. BUXBAUM
Art Director

JOHN McVEIGH
Associate Editor

ANDRE DUZANT
Technical Illustrator

PATRICIA GIRRIER-BROWN
Production Editor

DORIS A. MATTHEWS
Editorial Assistant

Contributing Editors
Hal Chamberlin, Lou Garner, Glenn Hauser
Julian Hirsch, Ralph Hodges, Forrest Mims
Ray Newhall, Wilfred Scherer

JOSEPH E. HALLORAN
Advertising Director

JOHN J. CORTON
Advertising Sales

LINDA BLUM
Advertising Service Manager

PEGI McENEANEY
Executive Assistant

EDGAR W. HOPPER
Publishing Director

ZIFF-DAVIS PUBLISHING COMPANY
Editorial and Executive Offices
One Park Avenue New York, New York 10016
212-725-3500

Hershel B. Sarbin, President
Philip Korsant, Executive Vice President
Furman Hebb, Executive Vice President
John R. Emery, Sr. Vice President, Finance and Treasurer
Phillip T. Heffernan, Sr. Vice President
Edward D. Muhlfeld, Sr. Vice President, Sports Division
Philip Sine, Sr. Vice President
Frank Pomerantz, Vice President, Creative Services
Arthur W. Butzow, Vice President, Production
Lawrence Sporn, Vice President, Circulation
George Morrissey, Vice President
Sydney H. Rogers, Vice President
Sidney Holtz, Vice President
Albert S. Traina, Vice President
Paul H. Chook, Vice President
Edgar W. Hopper, Vice President
Robert N. Bavier, Jr., Vice President
Charles B. Seton, Secretary

William Ziff, Chairman
W. Bradford Briggs, Vice Chairman

Midwestern Office
The Pattis Group, 4761 West Touhy Ave.,
Lincolnwood, Illinois 60466, 312 679-1100
Thomas Hockney, Michael Neri, Gerald E. Wolfe
Western Office
9025 Wilshire Boulevard, Beverly Hills, CA 90211
213-273-8050; BRadshaw 2-1161
Western Advertising Manager: Bud Dean
Japan James Yagi
Oji Palace Aoyama: 6-25, Minami Aoyama
6 Chome, Minato-Ku, Tokyo 407-1930/6821,
582-2851

Editorial

THE FUTURE OF HOME COMPUTERS

It has been almost three years since POPULAR ELECTRONICS introduced the first powerful, low-cost microcomputer mainframe. In this short time, many changes have taken place in the field. For example, then you could only buy a home computer by ordering it through the mail, sight unseen. Now there are many hundreds of retail computer stores where prospective buyers can observe computers in action and ask questions about their operation before making a purchase. Soon there will be even more such stores (in the thousands) with Radio Shack's and Heath's recent announcements of computer models joining the fold.

Other changes are evident, too. Whereas virtually every home computer purchased a few years ago was in kit form, sales of factory-assembled versions are growing. Moreover, we used to have just mainframes with separate peripherals; now we can buy single-board computers and mainframes incorporating terminals. For storing programs, the use of paper tape programs is giving way to audio cassette systems, with many a computer buff hoping for a floppy disc under his Christmas tree . . . BASIC in ROM is "in," if only because more and more electrical blackouts are anticipated . . . computer clubs are springing up all over the country as if they were fast-food operations.

Naturally, the question arises: "Where are non-commercial computers headed?" Undoubtedly, computers will one day reach the mass market; but when and where will they be merchandised? Here, views are divided.

Many people think computers will be sold by mass-market merchandisers, such as the large department stores. Supporting this view, a spokesman for Commodore Business Machines indicated that its personal computer (not yet available for sale) will indeed be sold by department stores, starting with the California division of R.H. Macy & Co. "In about five years or so, it'll be just like the calculator market is today," one computer hobbyist opined.

I don't agree.

Right now, we have virtually no true personal computer systems. Rather, we have a hobbyist and small-business market, as opposed to the appliance-type of computer. The field for the latter is bound to grow, of course. However, I don't believe that the *general public* is ready to plunk down \$600 or more for a computer system that is largely based on playing games, doubling as a hand-held calculator, and maintaining the family checking account. It's a nice thought, but, in my view, an over-optimistic one. This is an area which will appeal to the hobbyist, who will take the time to learn what the machine can do, explore different ways in which to expand the computer's utility, join computer clubs, etc. This person is not the button pusher.

Furthermore, I cannot visualize computers being sold in great numbers in a general type of retail outlet where one cannot even get the attention of a clerk to pay a bill, let alone obtain counsel. It's the *specialist* store that will be best equipped to move computer merchandise in the foreseeable future. I draw a parallel here with stores that merchandise hi-fi components and photography equipment. Sure there are department stores that sell such equipment, but most of it is sold in specialty stores whose sales personnel can hold a customer's hand while he makes a buying decision and support him after the sale is made. And that's the computer or electronic retail store.

The mass appeal of computers to the public will likely take place when a terminal can be used in the home for a variety of pushbutton applications: shopping for and buying merchandise in various stores while sitting at home, selecting video presentations of material from newspapers and reference books in libraries, and so on. When this comes to pass (in the 1990's?), I'm confident that the terminals will be supplied initially by the "phone company" or IBM, rather than the comparatively small computer manufacturer. The latter is more likely to enter the competition after the former has established a major market by installing fibre optic cable lines to carry digital data, contracting with sellers, and offering the public a line of terminals for home use (with a monthly rental fee, of course).

Meanwhile, I anticipate the continued, burgeoning growth of the hobbyist and small business computer field for the next decade.

Art Salsberg

The \$99.95 mystery...



B&K-PRECISION's new 3½ digit DMM

For over two years, our competition has been trying to figure out how B&K-PRECISION could sell a full-feature 3-digit DMM for only \$99.95. They've dissected it, analyzed it, and some even asked us how we did it. Well, they can start all over because we did it again!

B&K-PRECISION's new Model 2800 portable DMM features 3-1/2 digit display, auto-zeroing and 100% overrange reading for only \$99.95. Basic DC accuracy is 1%. Twenty-two ranges read up to 1000 volts DC or AC, 1000mA and 10 megohms.

All ranges are well protected against overloads. Even if you should accidentally apply +1000VDC to the 2800 while switched to an ohms range, no instrument damage will result. All DC and AC voltage ranges are protected up to ±1000 volts DC or AC. The current ranges receive the double protection of diodes and a series fuse.

For accurate in-circuit resistance measurements, the 2800 measures with high- or low-power ohms ranges. At low-power ohms, less than 0.2 volt is developed across the measured resistance. To forward bias semiconductor junctions, the high-power ohms ranges develop about 2 volts.

B&K-PRECISION also has a full complement of optional accessories for the 2800. Accessories include a carrying case, wire tilt stand, AC adapter/charger, high-voltage probe, direct/isolation probe NiCad Batteries and 10-amp current shunt.

The B&K-PRECISION 2800 may be a mystery to our competitors, but for you—it takes all the mystery out of which DMM to buy.

See your local distributor for immediate delivery.

B&K PRECISION DYNASCAN CORPORATION

6460 West Corland Avenue, Chicago, Illinois 60635 • 312/889-9087

In Canada: Atlas Electronics, Ontario • International Sales: Empire Exporters, Inc., 270 Newtown Road, Plainview, LI, NY 11803

TEACHING DEVICE · ARCADE GAME · MUSICAL INSTRUMENT · HOME COMPUTER

Home Library Computer



The handsome and highly styled Bally Library Computer is made of high impact clear plastic and imitation walnut with gold trim. It measures 5" x 11" x 15" and weighs five pounds.

The new Bally Library Computer provides more entertainment and services than man has ever dreamed possible from a single consumer product.

This is the story of an incredible product. So incredible that we know of no future consumer product that will have such a far-reaching technological impact on society.

The Bally Library Computer is a small console unit that resembles a programmable TV game but whose computing capabilities resemble that of the IBM 5100 currently selling for \$10,000. This calculating power and its present and future programs will provide more convenience and benefits than any other recent electronic product.

ELECTRONIC PRINTING CALCULATOR

Imagine the computer as a printing calculator with ten separate memories. You enter the data on the unit's keyboard, but instead of a paper tape, you use your TV screen to scroll out the answers similar to the credits on a movie screen. You can balance your check-book and then double check your calculations by scrolling back to your first entry. By comparison, an electronic calculator with ten memories alone would cost what this entire computer costs—but there's much more.


A CHALLENGING TEACHING TOOL

Your child inserts a cartridge in the Bally console. Three random math table problems are then flashed on your TV screen. Depending on the speed and accuracy with which those problems are answered, the Bally automatically programs the computer with your child's math level. Problems in addition, subtraction, multiplication and division are then flashed on the screen for the next three minutes, and the computer continually adjusts to a level slightly better than the math level indicated by the previous three answers. The math tables, therefore, remain a challenge no matter how good your child becomes. Psychologists, who were consulted by Bally, helped design the cassette. They stated that the cassette should stimulate math learning and improve grades.

On the same math cartridge is a two player game called Math Bingo. It adjusts to each player's ability so a parent can play against a child or two children can compete against each other at their own math levels—both with an equal opportunity to win. You first answer a math table problem similar to the first exercise; and with a pistol-grip pointer you move a square on your TV screen to the correct answer position on your TV bingo card. The game involves both math skill and dexterity. Each game is totally different since the bingo cards have a million different possibilities. Scoring is constantly displayed, and a typical game lasts approximately three minutes. You can play as many consecutive games as you wish. However, to start the score over, you press the reset button.

FUN AND ACTION ARCADE GAMES

Picture nine baseball players running out on your TV screen to the sounds of "Take Me Out to the Ball Game" as you step up to bat. That's the scene with Baseball, the arcade cartridge that plays two teams against each other with play so real that you hear all the music, sound effects and see all the action. There are walks, balls, and such realism that the pitcher covers first base when a ball is hit to right field—just like the real game. There are double plays, walks and errors—all part of nine innings of Baseball. On the same cartridge are several paddle ball games but with a new twist. Players can move the paddle, not only up or down like most TV games, but sideways and diagonally.

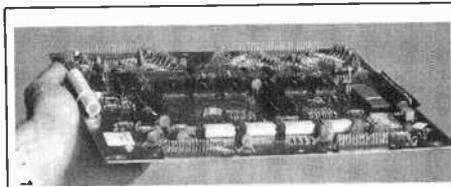

The Bally circuit board contains 34 integrated circuits including a Z80 microprocessor. This package represents more computing power in the hands of the consumer than was thought possible this early in the history of micro electronics. The mass production of these components and circuit board has made possible a quantum leap in lowering the cost of what normally would be a very expensive system.

Other popular arcade games include, Sea Wolf, Red Barron, Panzer Attack (similar to Tank) and dozens of games only previously available at arcades. These same games cost arcade owners up to \$2,000 each.

MORE VALUE PER FEATURE

Let's quickly review the features—an electronic printing calculator with ten memories, a teaching machine that adjusts to your child's math level and an arcade center that replaces about \$10,000 worth of electronic arcade games with just a few cartridges. Use any one of these features and you could justify buying this unit—but there's plenty more.

With all its sophistication, the Bally Library Computer was designed to keep current with advancing computer technology no matter how sophisticated the development. Bally has provisions in its present system for expansion modules. These devices will permit you to: 1) draw directly on your TV screen with an electronic wand in 32 different colors and eight shades of each color, 2) compose, record and playback music on an electronic synthe-

sizer, 3) record your personal belongings and their value for security purposes and add or delete items while keeping the list in tact, 4) record all your phone numbers and then use the system to dial those numbers on your telephone, 5) play chess on the phone with another player and be able to see all the moves on your TV screen.

EXCELLENT BUSINESS TOOL

With these expansion modules, businessmen will be able to do all their bookkeeping functions, payroll, inventory control and billing. There will be printers, telephone modems and a variety of peripheral computer equipment that will turn your Bally Library Computer into a significant business tool. And, when used in your business, your Bally unit is depreciable like all your other capital equipment. Even large corporations can use the Bally for specific applications to avoid tying up their larger computer systems.

The Bally Library Computer will turn these incredible add-on features into reality in a planned program starting now. Each month, a new cartridge or accessory expanding the unit's capability will be announced. If you purchase your system from JS&A, you will be alerted to these new accessories by mail on a regular basis in advance of their availability and before any national announcement. You may then order the accessories directly.

Each new cartridge or accessory will offer you a new way to use your system—a way that would justify, by itself, the purchase of the entire system.

NOT JUST A TV GAME

Don't confuse the Bally Library Computer with the many inexpensive programmable TV games. The Bally computer is a powerful system using the Z80 microprocessor whose cost per byte (the measure of computer memory power) is even lower than a home computer. Yet it has 12,000 bytes of computer power in its most basic system and you are not just limited to teaching, music, entertainment or business applications. The Bally computer can be programmed to do anything any mini-computer can do. A programmable TV game at any price is (and will always be) just a programmable TV game. It cannot be expanded. The Bally Library Computer is actually a computer with a variety of expansion capabilities.

A COMPUTER IN EVERY HOME

This is the first time a full-scale computer has been offered to the consumer. The home hobbyist with his home computer started the revolution a few years ago. With the specific programs, software and accessories available

POPULAR ELECTRONICS

from Bally, the age of affordable consumer computer ownership is here now.

INTERNAL TASK LIBRARY

The computer you buy now has within its 34 integrated circuits an internal library of over forty tasks that it performs. With such an extensive internal library, your computing power is already in the unit you buy. This also means that the Bally unit is a smart computer. (There are such things as dumb computers.) A smart computer can complete a function faster and more efficiently because it depends less on the data it gets and more on what it can already do.

SAFE FOR YOUR TV

The task library includes a built-in electronic timer which determines the end of a game or program by either score or elapsed time. It also times the arcade games and automatically turns off your unit and blanks out your screen if it is left on too long. Most TV set manufacturers have excluded sets that use TV games from warranty coverage because of the possible lines that appear on the screen from sets left on too long with the same picture. This is impossible with the Bally.

If you get a phone call in the middle of a game, you press the pause control which lets you freeze the action right in the middle of a play and blanks out the screen so you won't damage your picture tube.

The library has sound effects so that each arcade game is complete—from the sound of a baseball bat to that of a torpedo hitting a submarine. It has a math program capable of turning your unit into a scientific, statistical or engineering calculator with the addition of the appropriate cartridge. The library contains the capability of creating patterns on your TV screen, playing music, and accepting typewriter entries. It even has an index that displays everything in your library.



The cassette cartridges add between eight to thirty-two thousand additional bytes of computer power to the basic 12,000 byte system. The pistol grip arcade accessory can be used to play all the arcade games.


THE MAJOR BREAKTHROUGH IN BALLY'S COMPUTER

Its extensive internal library and the tremendous power in the computer are the big breakthroughs in the Bally unit. The internal computer has over 12,000 bytes with a minimum of 8,000 bytes in its cartridges. This puts more computer power in the hands of the consumer than six typical programable TV games or an average hobbyist home computer. It has the computational capabilities of one \$10,000 IBM 5100 computer, and each time you add a cassette cartridge you increase that capability.

Good resolution on your TV screen is one of the end effects of so much computer power. By comparison, the best programable TV game image is projected on a screen composed of 64 dots wide by 64 dots deep or 4,096 total dots. The Bally unit is 160 by 100 or 16,000 dots—four times more—so the Bally image is sharper and has finer detail, better resolution, smoother motion, and clearer letters for math or text applications.

SIGNIFICANT EXPANSION MODULES

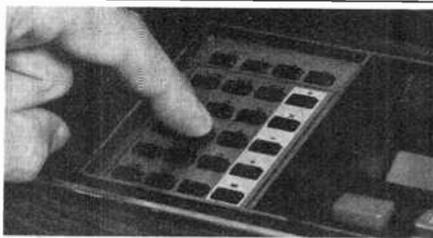The most significant expansion accessory will be the dual magnetic tape decks with an alpha numeric (typewriter) keyboard. With this accessory package, which will cost under \$500 and be introduced by JS&A next year, you can record data and software programs and do everything you can do on any main-frame computer system within the data storage capacity of the Bally unit.



The Bally console keyboard is used to select specific programs from each cassette.

The implications of this add-on module are mind-boggling. First, it adds an additional 16,000 bytes of memory to the powerful 12,000 already in the basic system. Secondly, it provides not only more power and features than are presently available in any home computer, but it contains peripherals that would normally cost thousands of dollars extra and are considered accessories on all other mini-computer systems. Thirdly, it uses the computer basic language which is easy to understand. And finally, each cassette tape in the system will contain an additional one quarter million bytes of storage capability. With the tape decks and keyboard, the consumer will now own the equivalent of an entire computer system complete with peripherals, storage and memory.

HIGH SPEED PRINTER

A quality high-speed printer will also be available next year. This will give you written records from your storage tapes. Store your most frequently called phone numbers, your income tax figures, your savings account deposits, the value of your stocks and bonds or a net worth statement. Then, when you need the information, press a button for a printed record.

DIAL-A-BARGAIN® ORDERING SYSTEM

Our technicians have programmed JS&A's main computer so you can use the Bally to access our computer directly when Bally's dual tape decks become available. With a special module and cassette, you will be able to 1) call our computer on our toll-free number, 2) place an order, and 3) find out when it will be shipped. Since you communicate directly with our computer, your order is processed immediately and can be shipped within a few hours after receipt. To do this, JS&A engineers developed a \$100 hardware ordering package that will be sent free to those customers who order the basic unit this year.

THE BIG DIFFERENCE

When you order the Bally computer today, you are making an investment in the future. The basic unit you receive, without a single accessory, will provide more benefits than any other product of its kind in history.

When you buy an expensive product, you must be absolutely satisfied that you get the service and a solid company standing behind your purchase for many years to come. The Bally Library Computer is backed by a substantial company, Bally—in business since 1931 and now the world's largest manufacturer of coin-operated amusement games. JS&A is America's largest single source of space-age consumer products and also a

substantial company—further assurance that your investment is well protected.

A FRANK DISCUSSION OF SERVICE

The Bally unit is a solid-state computer with its electronics condensed on 34 integrated circuits—all hermetically sealed and all pre-tested for a lifetime of service. The Bally Computer is also self-diagnostic. We have developed a cartridge that lets the unit itself check every integrated circuit and every solid-state component and which displays any malfunction on your TV screen. Then all you do is send the circuit board or your entire unit to JS&A's service-by-mail center for prompt replacement. The cartridge will be sent free-of-charge only to JS&A customers after you receive your unit.

Please don't think service requirements are common. They're not. But we wanted to assure you that service was such an important consideration in the Bally design that the unit practically repairs itself.

COMPLETE AS IT ARRIVES

Each unit comes complete with four pistol grips for use with the arcade and teaching games, an AC adapter (batteries are not required), three free arcade games, the calculator program, its internal library of tasks, complete easy-to-understand instructions and a one year parts and 90 day labor limited warranty—all for only \$299.95.

The arcade games include 1) Gun Fight, in which two cowboys shoot at each other around cactus, covered wagons and other obstacles, 2) Checkmate, a one to four player game in which you build walls around your opponent to win and, 3) Scribbling, a one to four player game that utilizes the pistol grip to doodle different designs on your TV screen (in color with a color set).

A keyboard lets you use your printing memory calculator and a special scroll button lets you scan your entries up or down to review or check your calculations. You may also order with your unit the Baseball and Paddle Games cartridge for \$24.95 or the Math Table/Math Bingo cartridge for \$19.95. A bulletin will accompany your unit listing all the other cartridges and accessories that are available or will be available in the near future.

We feel so positive about this product that we will 1) not charge you anything for postage and handling and 2) give you a 30 day extended trial period to prove that the Bally is everything you expected after reading this article. When you receive your unit, reconcile your checkbook with the calculator, let your child practice with the math programs or have your entire family play the arcade games. After you have used the system under your own conditions and have personally experienced its fun and benefits, then decide if you want to keep it. If not, return it within our 30 day extended trial period for a prompt and courteous refund. You can't lose.

JS&A is marketing a product that will not only greatly influence the future of the computer industry, but will dramatically add consumer conveniences never before dreamed possible. Order your Bally Library Computer, at no obligation, today.

Unit pending FCC approval—allow 4 weeks delivery.
Dial-A-Bargain is a registered trade mark of the JS&A National Sales Group.

JS&A NATIONAL SALES GROUP

Dept. PE One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-9000
CALL TOLL-FREE... 800 323-6400
In Illinois call... (312) 498-6900

©JS&A Group, Inc., 1977

Learn to service Communications /CB equipment at home...with NRI'S COMPLETE COMMUNICATIONS COURSE

Learn design, installation and maintenance of commercial, amateur, or CB communications equipment.


The field of communications is bursting out all over. In Citizens Band alone, class D licenses grew from 1 to over 2.6 million in 1975, and the FCC projects about 15 million CB'ers in the U.S. by 1979. That means a lot of service and maintenance jobs . . . and NRI can train you at home to fill one of those openings. NRI's Complete Communications Course covers all types of two-way radio equipment (including CB), AM and FM



Transmission and Reception, Television Broadcasting, Microwave Systems, Radar Principles, Marine Electronics, Mobile Communications, and Aircraft Electronics. The course will also qualify you for a First Class Radio Telephone Commercial FCC License or you get your tuition back.

Learn on your own 400-channel digitally-synthesized VHF transceiver.

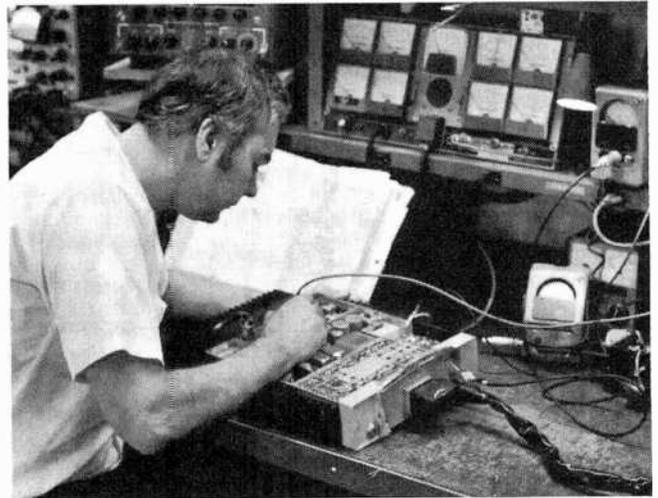You will learn to service all types of communication equipment, with the one unit that is designed mechanically and electronically to train you for CB, Commercial and Amateur communications: a digitally-synthesized 400-channel VHF transceiver and AC power supply. This 2-meter unit gives you "Power-On" training. Then we help you get your FCC Amateur License with



special instruction so you can go on the air.

The complete course includes 48 lessons, 9 special reference texts, and 10 training kits. Included are: your own electronics Discovery Lab, Antenna Applications Lab, CMOS Frequency Counter, and an Optical Transmission System. You'll learn at home, progressing at your own speed, to your FCC license and into the communications field of your choice.

NEW CB SPECIALIST COURSE NOW OFFERED



NRI now offers a special course in CB Servicing. You get 37 lessons, 8 reference texts, your own CB Transceiver, AC power supply and multi-meter . . . for hands-on training. Also included are 14 coaching units to make it easy to get your commercial radio telephone FCC license—enabling you to test, install, and service communications equipment.

NRI offers you five TV/Audio Servicing Courses

NRI can train you at home to service TV equipment and audio systems. You can choose from 5 courses, starting with a 48-lesson basic course, up to a Master Color TV/Audio Course, complete with designed-for-learning 25" diagonal

solid state color TV and a 4-speaker SQ™ Quadraphonic Audio System. NRI gives you both TV and Audio servicing for hundreds of dollars less than the two courses as offered by another home study school.

All courses are available with low down payment and convenient monthly payments. All courses provide professional tools and "Power-On" equipment along with NRI kits engineered for training. With the Master Course, for instance, you build your own 5" wide-band triggered sweep solid state oscilloscope, digital color TV pattern generator, CMOS digital frequency counter, and NRI electronics Discovery Lab.



™ Trademark of CBS Inc.

NRI's complete computer electronics course gives you real digital training.


Digital electronics is the career area of the future . . . and the best way to learn is with NRI's Complete Computer Electronics Course. NRI's programmable digital computer goes far beyond any "logic trainer" in preparing you to become a computer or digital technician. With the IC's in its new Memory Kit, you get the only home training in machine language programming . . . experience essential to trouble shooting digital computers. And the NRI programmable computer is just one of ten kits you receive, including a TVOM and NRI's exclusive electronics lab. It's the quickest and best way to learn digital logic and computer operation.

You pay less for NRI training and you get more for your money.

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuitions and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

More than one million students have enrolled with NRI in 62 years.

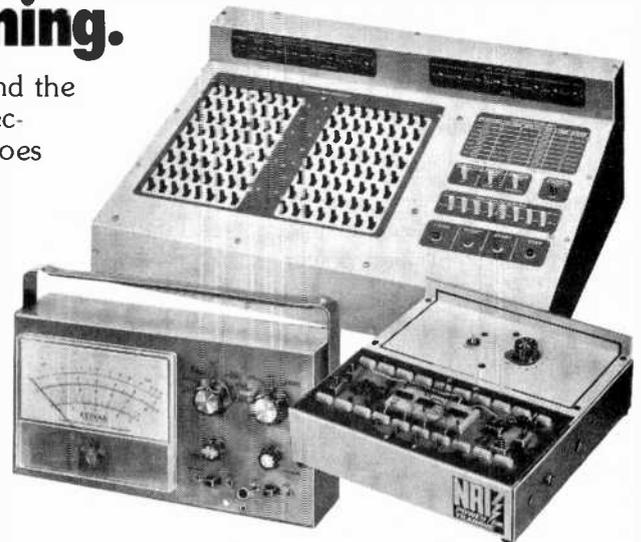Mail the insert card and discover for yourself why NRI is the recognized leader in home training. No



salesman will call. Do it today and get started on that new career.

APPROVED UNDER GI BILL
if taken for career purposes Check box on card for details.



NRI SCHOOLS
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington, D.C. 20016



Letters

EMERGENCY CALL SIGN "STANDARD"


In the May 1977 "CB Scene" it was stated that the PURAC was considering the 0911 number for an Emergency Call Sign. Within

the past year, most single-sideband clubs in Ohio have adopted the Emergency Call Sign of 999, which is quickly being adopted throughout the U.S. On SSB, we use the "Q" signals, which many SSB clubs have adopted, to cut down on air time. (Q signals do not have an emergency call as is the case with the 10 Code.) I suggest that if an emergency call is made, it should coincide with one that has already been voluntarily adopted by CB'ers. —Denton C. Rastall, President, USB, Willowick, OH

COMPREHENSIVE, GENERAL, AND SPECIFIC

"FM Tuner Ratings and Measurement" by Julian Hirsch in the April 1977 issue was very informative. The article was comprehensive

"PERFECT BALANCE"™ sound - clean, clear and brilliant

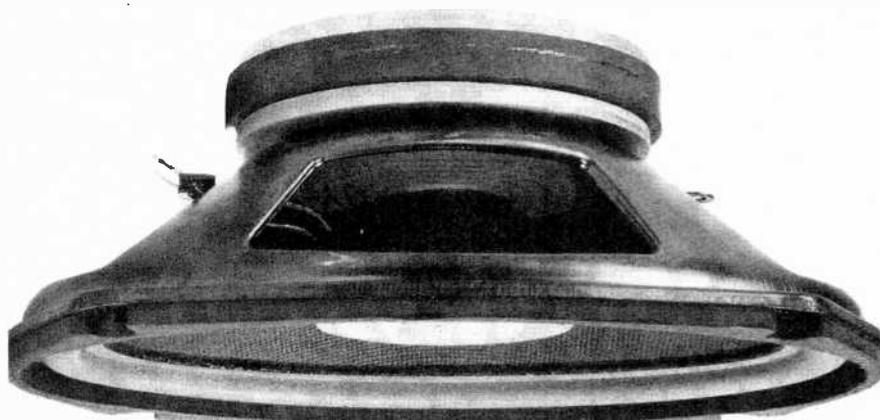

MODEL 8971

You can drive 30 watts RMS through our 6" x 9" coaxial speakers all day, and they'll just keep cookin'.

Frequency response, power handling and efficiency are balanced to provide superb sound definition from the smallest stereo radios to 60 watt power amplifiers.

Let your ears be the judge. If you listen to a **KLASSIC™** speaker, you'll buy it.



afs/Kriket Acoustic Fiber Sound Systems, Inc.
Indianapolis, Indiana

All afs®/KRIKET® products are manufactured in the U.S.A.
Copyright 1977, Acoustic Fiber Sound Systems, Inc.

enough to be specific and general enough to be applied to just about any FM tuner available. After reading this article, I took a check, as suggested, of my tuner and compared the results I obtained to the results obtained from a test of a friend's FM tuner. I noted a substantial difference between the two sets of results. Finally, when playing the two tuners side by side, we could hear the difference. Cary R. Patten, Northville, MI

WORD SPACING IS VERY COMMON

I question the statement in "Morse Code Automatic Readout On a TV Screen" (May 1977) that "word spacing is rarely sent in Morse Code." After the original "Morse-A-Letter" project appeared in the January 1977 issue of POPULAR ELECTRONICS, I made my own interface that produces perfect word spaces. I send the parallel data out to my video terminal in RS-232 via a UART. I would have submitted a photo of a full "page" of a news broadcast that shows perfect word spacing were it not illegal. Except in the case of crude or unusual keying, I find word spacing is very common, even if it does occur naturally rather than intentionally. After all, any pause longer than a character will register as a word space. —Joseph A. Maddox, Cincinnati, OH

HOW ABOUT A TRANSLATION?

I enjoyed "How To Program Calculators for Fun and Games." However, the programs given are in Reverse Polish Notation (RPN) and not suitable directly for use with my algebraic-entry calculator. Needless to say, I had difficulty in trying to decipher and rewrite the programs. I hope that next time POPULAR ELECTRONICS publishes programs they are listed in a form that will make it easier to program any calculator. —Marc Wester, Burlingame, CA

We'll try.

ANOTHER COUNTING APPROACH

With reference to the June 1977 "Out Of Tune" for the "Westminster Clock" that appeared in the November 1976 issue, I had the same problem in getting IC18 to count from 1 to 12 properly. It took me several weeks of learning about MOS to find the fault. In my studies, I learned about a different approach to use to get my clock working. To obtain a positive pulse to reset IC18 at 1 o'clock, I connected IC2, pin 12, to the spare inverter in IC5 (pins 12 and 13) and IC5, pin 11, to IC18, pin 15, and eliminated C3 and R9. Pins 23 and 37 of IC19 (output common source and unblanking, respectively) require a positive supply.

This was the best project yet. It made me learn something about CMOS.—K.G. Burnett, Errington, B.C., Canada.

MORSE CODE DETERRENT

I read the November 1976 Editorial with interest and would like to state that amateur radio operators should remember that they are

POPULAR ELECTRONICS

FREQ. OUT.

CSC's done it again.

Broken the price and performance barriers with new MAX-100. The multimode, professional portable frequency counter that gives you more range, visibility, accuracy, and versatility than any comparable unit at anywhere near its low, low price.

MAXimum performance.

MAX-100 is a cinch to use. It gives you *continuous readings* from 20-Hz to a *guaranteed 100MHz*, with 8-digit accuracy. Fast readings with 1/6-sec. update and 1-sec. sampling rate. Precise readings, derived from a crystal-controlled time base with 3ppm accuracy. High-sensitivity readings from signals as low as 30 mV, with diode overload protection up to 200V peaks.

Input signals over 100MHz automatically flash the most significant digit. And to indicate low-battery condition and extend remaining battery life, the *entire display flashes* at 1-Hz.

MAXimum versatility. Wherever and whenever you need accurate frequency readings, MAX can do the job. Use it with clip-lead cable supplied. Mini-whip antenna. Or low-loss in-line tap with UHF connectors. For AM or FM; CB, ham, business radio and R/C transmitter or receiver alignment. Monitoring audio and RF gener-

ators. Checking computer clocks and other digital circuits. Repair of depth sounders and fish finders. Troubleshooting ultrasonic remote controls. For these, and hundreds of other applications, you'll find it indispensable.

MAXimum visibility. MAX-100 features a big, bright 10.6" multiple-ec 8-digit LED display, with leading-zero blanking. So you don't have to squint or work up close. And, MAX's flip-up stand is *built-in*.

MAXimum flexibility. MAX-100 operates from *four* power sources, for use in lab or field. Internal alkaline or NiCad batteries. 11C or 220V wall charger/eliminator. 12V with automobile cigarette-lighter adapter/charger and external 7.2-10V supply.

MAXimum value. With all its impressive specs, you'd expect MAX to cost a lot more than a low \$134.95, complete with clip-lead cable and applications/instruction manual. But that's another nice thing about MAX: though it's accurate enough for lab use, it's well within the reach of hobbyists' and CB-ers' budgets.

Try MAX for yourself at your CSC dealer—or contact us for full specs and your local dealer's name. Once you see how handy MAX is, you'll want to "freq out" too. With CSC.


Specifications.

Range: 20Hz to 100 MHz, guaranteed. **Gate time:** 1 sec. **Resolution:** 1 Hz. **Accuracy:** ± 1 count + time base error. **Input Impedance:** 1 M Ω /56 pF. **Coupling:** AC. **Sine Wave Sensitivity:** 30 mVRMS @ 50 MHz. **Internal Time Base Frequency:** 3.579545 MHz crystal osc. **Stability:** ± 3 ppm @ 25°C. **Temp. Stability:** Better than 0.2 ppm/°C. **0-50°C. Max. Aging:** 10 ppm/year. **Display:** Eight 6" LED digits; anti-glare window. **Lead-zero blanking:** decimal point appears between 5th and 7th digit when input exceeds 1 MHz. **Overflow:** with signals over 99,999,999 Hz, most significant (left hand) digit flashes, allowing readings in excess of 100 MHz. **Display update:** 1/5-second plus 1 sec. gate time. **Low Battery Indicator:** When power supply falls below 6VDC, all digits flash @ 1 Hz rate. Flashing display extends battery life. **Power:** 6 AA Alkaline or NiCad cells (internal); **External:** 110 or 220VAC Eliminator/charger; Auto cigarette lighter adapter; 7.2-10VDC ext. supply; **Bat. Charging:** 12-14hr. **Size (HWD):** 1.75" x 5.63" x 7.75" (4.45 x 14.30 x 19.69cm) **Weight:** Less than 1.5 lb. (0.38 kg; w/batteries). **Accessories Included:** Clip-lead input cable; manual.

CONTINENTAL SPECIALTIES CORPORATION




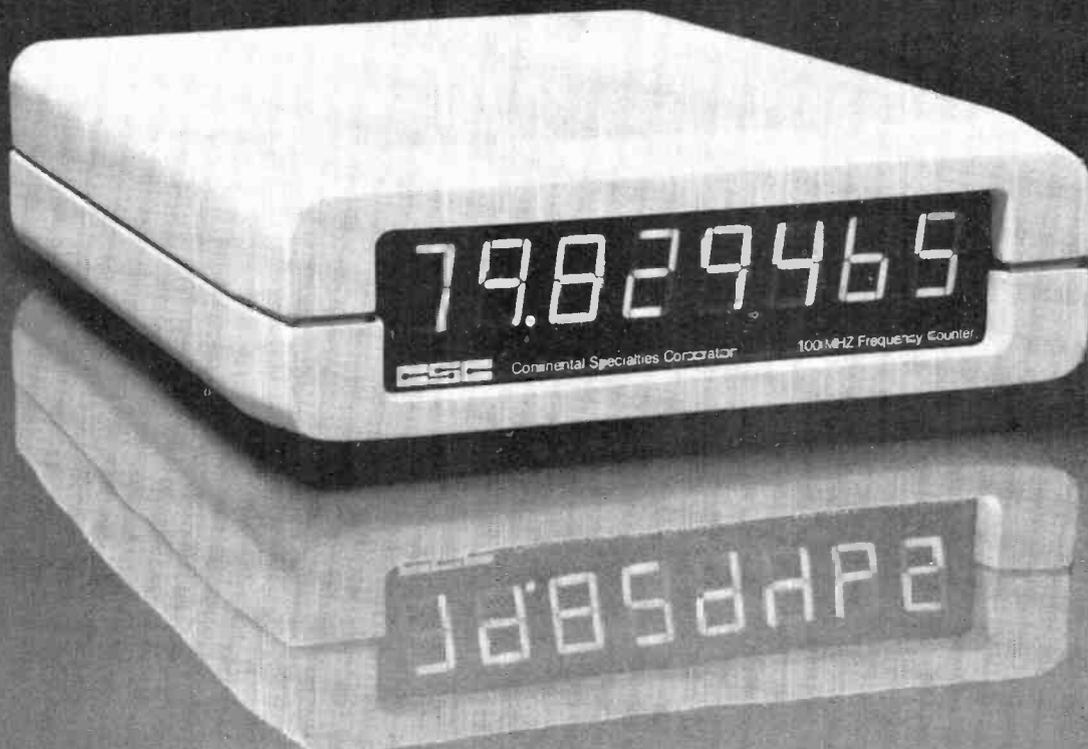34 Kencall Street, Box 1942,
New Haven, CT 06509
203-624-3903 TWX 710-465-1227
West Coast: 351 California St.,
San Francisco, CA 94104
415-421-3872 TWX 910-372-7392
MEXICO: ELPRO, S.A. Mexico City 5-23-30-04
CANADA: Len Finkler Ltd.; Onario



CIRCLE NO. 13 ON FREE INFORMATION CARD

Two-way improvement

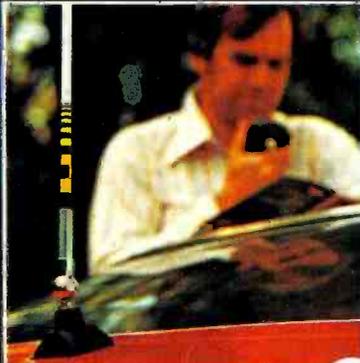

Adjustable Signal Kicker trunk lip mount and fiberglass antenna with exclusive Micro-tuneable Tip.



Turner offers two ways to improve your CB performance. First, there is talk power. The new Expander 400 mobile mike has all you need. A fine-tuning volume control sets full modulation level. The compression pre-amp keeps it there, regardless of mouth-to-mike distance. It's a clear improvement over your standard mike. A built-in monitor light automatically checks 9-volt battery condition.

Second, Turner gives you more ways to get your signal out. Take your choice of stainless steel or fiberglass Signal Kicker antennas. Both have a full choice of mounts and Turner durability.

The talk of the road

TURNER | MICROPHONES
ANTENNAS

CONRAC CORPORATION

716 Oakland Road N.E., Cedar Rapids, Iowa 52402

an elite group by our choice, not theirs. I have worked in industrial electronics with hams and found them to be a good group of guys who know their electronics and their equipment very well. I, too, have been interested in ham radio, but I decided to pass on it because of the Morse Code requirement, which I do not understand and do not like. I feel the code requirement is a deterrent to highly qualified electronics technicians who simply can do without. Letting technicians into ham radio would be an enhancement, not a dilution.—*Gil Duddles, Princeton, IL.*

VALUABLE TEST INSTRUMENT

I recently built the "Automatic Diode Checker" featured in the June 1976 issue of POPULAR ELECTRONICS. It proved to be the most valuable test instrument I have ever seen. It is so simple and effective that I cannot help but wonder if the same principle could not be applied to the testing of transistors, inasmuch as they are basically a couple of diodes connected back-to-back. I service quite a few electronic photoflash units and since diodes and transistors are trouble spots in them, I know the diode tester will become an indispensable troubleshooting tool.—*Edward A. Bollinger, Satellite Beach, FL.*

SOLAR CONTROLLER KIT

I read with interest "Build a Solar Controller" (July 1977), and while this device is suitable for actuating attic ventilators, it does have some deficiencies when used to control solar collection systems. Because the circuit provides no hysteresis, the system will cycle on and off at the same temperature difference between the sensors. Most solar controllers (or differential thermostats) are designed to turn on only when collector temperature exceeds the storage temperature by 20° F and then cycle off when this temperature difference falls to 3° F. This prevents rapid cycling of the system in early morning and late afternoon when only marginal solar energy is available, resulting in greater overall efficiency.

Our company offers a complete solar controller kit for less than \$30. It includes the turn-on hysteresis, as well as freeze protection circuitry. This enables the controller to turn on the circulation system when the outside temperature falls to 36° F, thereby warming the collectors and preventing freezing when water is the circulating fluid.—*Charles Morton, Wind Sun Systems, 5209 Ave. H, Austin, TX 78751*

Out of Tune

In "How To Convert a 'Four Banger' For Stopwatch Functions" (August 1977), the identifications of IC2 and IC3 should be interchanged in the component installation diagram on page 57.

The Touch by Regency is the first fully synthesized, 16 channel scanner to put over 15,000 action radio frequencies at the command of a fingertip.

There's no complicated programming to do. No crystals to buy.

Simply tap out the frequency number you want on the pressure sensitive touch pads, and you're there.

Touch SC, and scan your 16 possible stored frequencies.

Or search for the unknown by pressing SS. The Touch seeks out frequencies you may never

know existed. When you find new action, The Touch tells you what you've found with the exact frequency number in LED display.

If you think that's the ultimate in scanning, wait. There's more.

One. You're never more than 1.2 seconds away from your favorite channel. The Touch lets you set up Channel 1 as a priority receiver; and it samples that frequency every 1.2 seconds. So you never miss a call.

Two. You'll also never miss a severe weather warning. Just set Channel 16 to the National

Weather Service emergency frequency, if available in your area. The Touch automatically alerts you to any severe weather broadcast.


Three. Our mobile filter screens out code noises from car telephones. Completely. Automatically. So all you hear is full, clear action.

See your Regency dealer for a demonstration. It's an experience you'll want to take home with you.

**The Touch by Regency.
The Ultimate Scanner.**



Introducing the Ultimate Scanner.

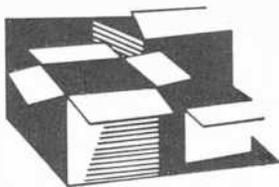

New Products

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Reader Service Card inside the back cover or write to the manufacturer at the address given.

DYNACO STEREO OCTAVE EQUALIZER

Dynaco's stereo octave equalizer, SE-10, has 10 slide controls for each channel, one control for each octave of frequency. Equalizer range is ± 12 dB from 30 Hz to 15 kHz. THD is said to be typically less than 0.01%, while hum and noise is rated 85 dB below two volts. The SE-10 has eight integrated circuits, two FET's, five transistors, and an IC-regulat-



ed power supply. A three-transistor circuit electronically prevents switch pops. Other features include independent channel gain control from -12 to +6 dB; low impedance (600 ohm) output; and 16 amplifiers in the four low-frequency sliders of both channels. An independent source/tape switch enables equalization of a second program. Factory assembled \$349, kit \$249.

CIRCLE NO 88 ON FREE INFORMATION CARD


TAU EXPONENTIAL VCO AND VCF KITS

The Tau Systems Model 1050 vco kit features 1-volt/octave response over a full 10-octave range. Accuracy is claimed to be better than 1% over the range of 10 to 20,000 Hz. The vco generates up- and down-ramp and width-modulated pulse outputs of 10 volts peak-to-peak. The Model 1010 vcf kit offers a 24-dB octave response over the entire audio range, in addition to providing 10-octave exponential, 1-volt/octave control characteristics. The vcf has adjustable Q (resonance control) and can be made to generate what is claimed to be a very pure sine wave over the entire audio range. Both kits should be of particular interest to those involved in electronic music, artificial voicing, instrumentation, spectrum analysis, and sweep generation. Model 1050, \$32.50; Model 1010, \$47.00.

CIRCLE NO 89 ON FREE INFORMATION CARD

REALISTIC MOBILE CB AM TRANSCEIVER

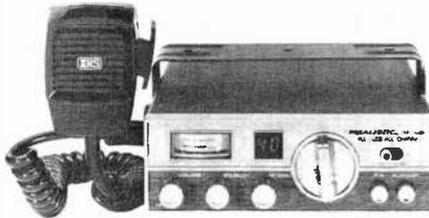Radio Shack has introduced the Realistic TRC-424 as its top-of-the-line 40-channel mobile. It features PLL circuitry, an automatic modulation gain control circuit for 100% modulation, and r-f power output of 4 W. Other



features include an r-f gain control, delta tuning switch, switchable noise blanker, LED digital readout, r-f/S meter, and PA capability. It operates on 12 V dc, positive or negative ground, and comes with mounting bracket and detachable mike. Measures $8\frac{1}{2}$ " \times $6\frac{5}{8}$ " \times $2\frac{3}{16}$ " (21 \times 17 \times 6 cm). \$169.95.

CIRCLE NO. 91 ON FREE INFORMATION CARD


POLY 88 SYSTEM SIXTEEN COMPUTER

The POLY 88 System Sixteen from Polymorphic Systems is a ready-to-run computer system that can be used to solve home finance problems, perform statistical analysis, and provide a host of challenging games. The 16k system features a high-speed video display and alphanumeric keyboard. Cassette tapes are used for permanent program storage. Programming is made simple by a BASIC software package. PLOT and TIME are unique features that rely on the video graphics and real-time clock. Other features include VERIFY that tells when a tape is good before another is loaded. Scientific functions, formatting options, and string capabilities are also included. \$2250; kits start at \$735.

CIRCLE NO. 92 ON FREE INFORMATION CARD

YAMAHA STEREO RECEIVER

The Model CR-2020 is Yamaha's top-of-the-line stereo receiver, rated at 100 watts/channel into 8 ohms at less than 0.1% THD, 20 to 20,000 Hz. Specifications include: 10 to 100,000 Hz ± 2.5 dB audio frequency response; 35-45 dB stereo separation; 1.8 μ V FM sensitivity; 1.0 dB capture ratio; 80 dB usable selectivity; 73 dB S/N; 30 to 15,000 Hz ± 0.5 dB FM frequency response. Features include dual output power meters; signal and FM tuning meters; selectable turnover frequencies; bass, presence and treble tone

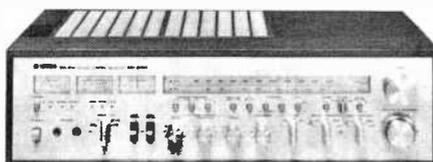

controls; selection of three pairs of speaker systems; Dolby FM selection; audio muting; FM blend switch; choice of phono input levels; and low and high filter switches. Dimensions: $21\frac{1}{4}$ "W \times $16\frac{5}{16}$ "D \times $6\frac{9}{16}$ "H (540 \times 415 \times 167 mm). \$700.

CIRCLE NO 93 ON FREE INFORMATION CARD


EV•GAME CB/AM/FM ANTENNA

"Breaker Beam" From EV•Game Inc. is a fully automatic, motor-driven CB/AM/FM antenna that is claimed to provide an exclusive "fail-safe" mast nesting function with ignition switch off. It also provides a transmit-actuated neon lamp that glows when the transmitter to which it is connected is keyed. The automatic fail-safe nesting action is said to ensure automatic retraction of the antenna mast into its housing mount as soon as the vehicle ignition or the transmitter/transceiver is turned off. The glowing neon lamp atop the antenna is easy to see by other CB'ers at night. The antenna extends to 40" (1 m) and has a loading coil on the fourth section of its five-section whip. The SWR is claimed to be extremely low, made possible with a fine-tuning, signal-splitting coupler that uses a CB tuning/trimmer capacitor. \$79.00.

CIRCLE NO. 94 ON FREE INFORMATION CARD

HANDIC CB TRANSCEIVER/STEREO RADIO

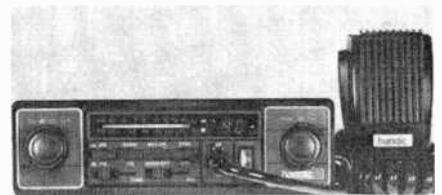Handic-USA's Model 240, is a 40-channel CB transceiver and AM/stereo FM receiver combination. The transceiver features PLL synthesizer, digital LED channel readout, r-f/S



meter, TX and RX indicator light, radio/CB select switch, standby/on/off switch for monitoring CB while listening to the radio, and anl. The radio has a tone control system, stereo balance control, AM/FM band select switch, and MPX/Mono switch. The entire unit is designed for in-dash installation. \$259.95.

CIRCLE NO. 95 ON FREE INFORMATION CARD

WAWASEE CB FREQUENCY DISPLAY

The latest in Wawasee Electronics' line of CB accessories is a compact frequency counter, Model JB 1004 FC, that displays the operating frequency of CB and ham transceivers. It has a specified frequency range of from 100 Hz to 50 MHz, with a display accuracy of 100 Hz and a 50-mV sensitivity. Designed to be operated from 12-volt dc sources, the system's power requirements are said to be minimal because the leading zeroes of the 0.5" (12.7-mm) displays come on only when the

POPULAR ELECTRONICS



transceiver's microphone is keyed. Mounting is via Velcro-type "spots." The size of the counter is 4½"W x 3¾"D x 1¾"H (11.4 x 9.8 x 4.4 cm). \$99.95.

CIRCLE NO 96 ON FREE INFORMATION CARD

MULTICORE EMERGENCY SOLDER

Multicore Solders has introduced a new tape-like solder strip, called Emergency Solder, that requires only an ordinary match or candle flame to melt and form a solder joint. The Emergency Solder strip contains multiple cores of rosin flux, which is noncorrosive and can safely be used in electronic circuits. In use, the strips are loosely wrapped around the joint to be soldered and an open flame is moved back and forth until the solder flows into the joint. To solder sheet metal, the solder is placed either between or on the metal parts to be connected and heat from a candle or soldering gun is applied as the parts are held together. Available from Multicore Solders, Westbury, NY 11590.

AUDIOANALYST SPEAKER SYSTEM

Model M6 is one of a new group of speaker systems called PhaseMatrix™ introduced by Audioanalyst, Inc. It is an 8-ohm system that has a specified frequency response of 30 to 20,000 Hz ±3 dB and a maximum power handling capability of 150 watts. Minimum driving power is rated at 15 watts. The three-way speaker system has crossovers at 700 and 2000 Hz. It uses a 10" (25.4-cm) woofer,



4½" (11.4-cm) midrange driver, and 1" (2.54-cm) tweeter. The system is housed in a lacquer-finished walnut-veneer cabinet that measures 24¾" x 13¾" x 11¾" (61.9 x 34.9 x 30 cm) and weighs 47 lb (21.3 kg). Behind the removable black fabric grille are three-position midrange and high-frequency controls that provide nine different contour setting combinations.

CIRCLE NO 97 ON FREE INFORMATION CARD

OCTOBER 1977

HF TRANSMITTER MONITOR

The Model WM-1000 by Communications Power, Inc. monitors transmitter performance in the 1.8-to-30-MHz frequency range. It contains three separate meters—an r-f wattmeter, an SWR meter, and a modulation level meter. The wattmeter reads either average or peak power output on 20-, 200-, and 1000-watt scales. Wattmeter operating mode (average or peak) and scale are selected by front-panel switches. The SWR and modulation meters have front-panel calibration controls and function with power levels of 1 to 1000 watts. The SWR meter employs a 30-dB directional coupler for improved accuracy at low SWR levels. Modulation level is measured by a full-wave circuit which functions over the full modulation wave form. The unit also features a built-in battery check circuit and automatic shut-off.

CIRCLE NO 98 ON FREE INFORMATION CARD

HEGEMEN PRE-PREAMP

Hegemen Input Probe (HIP) is a low-noise, wide-band preamplifier designed to mount next to a phonograph or tape deck. HIP is said to provide an audible increase in high-frequency detail, dynamic range, dimen-



sional perspective and a reduction in record surface noise. It works directly from either a tapehead or phonograph cartridge and is battery-powered to avoid hum pickup. Technical specifications include frequency response of 2 Hz to 350 kHz ±1dB, 0.1% harmonic distortion, 60 dB channel separation. Dimensions: 6" x 2¾" x 1½" (15.5 x 6.5 x 3.7 cm), (battery pack) 5½" x 5" x 1½" (14 x 12.5 x 3.8 cm). \$135.

CIRCLE NO 99 ON FREE INFORMATION CARD


AVANTI CB BASE ANTENNA

The new Saturn antenna by Avanti Research and Development, Inc. is an omnidirectional base station antenna with switchable horizontal or vertical polarization. Overall height is 22' (6.7 m), radials measure 9' (2.7-m), and the antenna weighs 25 lb (11.3 kg). The Model AV-501 switchbox for remote polarization selection is included.

CIRCLE NO. 100 ON FREE INFORMATION CARD

CORRECTION

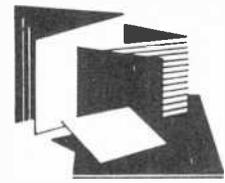In the September issue, the price of the McKay Dymek DR-22 Receiver was incorrectly given as \$2900. It should have been \$995.



New Literature

CB ACCESSORIES CATALOG

The Magitran Co. offers an 8-page catalog of its line of citizens band radio accessories. Included in the listing are anti-theft alarm systems, an antenna matcher, power supply, power regulator-booster, receive signal booster/attenuator, remote/PA speakers, and a radio check monitor. Each piece of equipment is illustrated and technical specifications are provided. Address: The Magitran Co., 311 E. Park St., Moonachie, NJ 07074.

NBS SMOKE DETECTOR PAMPHLET

The Commerce Department's National Bureau of Standards is offering a guide to homeowners who are interested in purchasing a smoke detector. Titled "Smoke Detectors . . . What They Are and How They Work," the pamphlet describes the two types of smoke detectors; ionization chamber and photoelectric; and answers questions most commonly asked about selection and placement of the detectors in the home. Address: "Detectors," Consumer Information Center, Pueblo, CO 20234.

REPLACEMENT ANTENNAS CATALOG

Russell Industries has a six-page brochure illustrating its line of "Rubber Duckie" antenna replacements for 2-way communications and scanner applications. Categories include citizens band, uhf, vhf, ham and business band radios, and walkie talkies. Address: Russell Industries, 3069 Lawson Blvd., Oceanside, NY 11572.


CHROME TAPE PAPER

A report on chromium dioxide cassette tape, "The Advent Chrome Paper," is available from Advent Corp. It discusses chromium dioxide tape, which was introduced in 1970, and compares it to other iron-oxide cassettes on the market. Address: Advent Corp., 195 Albany St., Cambridge, MA 02139.

SMALL-COMPUTER CATALOG

A 22-page Small Computer Catalog by Processor Technology describes the company's line of computers, computer systems, personality modules, software, memories, disk storage, interfaces and peripherals. Performance and application information is provided, with charts and illustrations. Address: Processor Technology Corp., 6200 Hollis St., Emeryville, CA 94608.

Go after the best of everything.

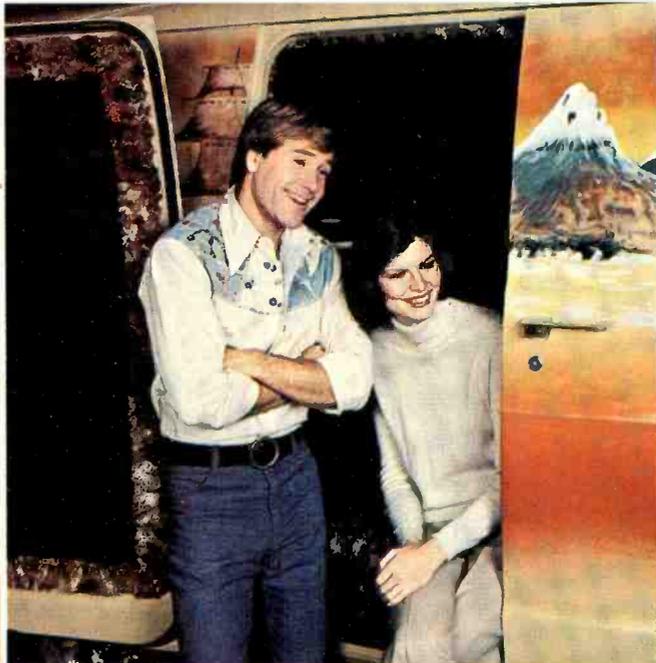

Don't settle for less. Especially when it comes to electronics training... because everything else in your life may depend on it. That's why you ought to pick CIE!

You've probably seen advertisements from other electronics schools. Maybe you think they're all the same. They're not!

CIE is the largest independent home study school in the world that specializes exclusively in electronics.

Meet the Electronics Specialists.

When you pick an electronics school, you're getting ready to invest some time and money. And your whole future depends on the education you get in return.

That's why it makes so much sense to go with number one... with the specialists... with CIE!

There's no such thing as bargain education.

If you talked with some of our graduates, chances are you'd find a lot of them shopped around for their training. Not for the lowest priced but for the best. They pretty much knew what was available when they picked CIE as number one.

We don't promise you the moon. We do promise you a proven way to build valuable career skills. The CIE faculty and staff are dedicated to that. When you graduate, your diploma shows employers you know what you're about. Today, it's pretty hard to put a price on that.

Because we're specialists, we have to stay ahead.

At CIE, we've got a position of leadership to maintain. Here are some of the ways we hang onto it...

Our step-by-step learning includes "hands-on" training.

At CIE, we believe theory is important. And our famous Auto-Programmed® Lessons teach you the principles in logical steps.

But professionals need more than theory. That's why some of our courses train you to use tools of the trade like a 5 MHz triggered-sweep, solid-state oscilloscope you build yourself—and use to practice troubleshooting. Or a beauty of a 19-inch diagonal Zenith solid-state color TV you use to perform actual service operations.

Our specialists offer you personal attention.

Sometimes, you may even have a question about a specific lesson. Fine. Write it down and mail it in. Our experts will answer you promptly in writing. You may even get the specialized knowledge of all the CIE specialists. And the answer you get becomes a part of your permanent reference file. You may find this even better than having a classroom teacher.

OCTOBER 1977

Pick the pace that's right for you.

CIE understands people need to learn at their own pace. There's no pressure to keep up... no slow learners hold you back. If you're a beginner, you start with the basics. If you already know some electronics, you move ahead to your own level.

Enjoy the promptness of CIE's "same day" grading cycle.

When we receive your lesson before noon Monday through Saturday, we grade it and mail it back—the same day. You find out quickly how well you're doing!

CIE can prepare you for your FCC License.

For some electronics jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of your specific knowledge and skills!

More than half of CIE's courses prepare you to pass the government-administered exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

For professionals only.

CIE training is not for the hobbyist. It's for people who are willing to roll up their sleeves and go to work... to build a career. The work can be hard, sure. But the benefits are worth it.

Send for more details and a FREE school catalog.

Mail the card today. If it's gone, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail the card or the coupon or write CIE (mentioning name and date of this magazine) at: 1776 East 17th Street, Cleveland, Ohio 44114.



Patterns shown on TV and oscilloscope screens are simulated.

CIE Cleveland Institute of Electronics, Inc.
1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES... I want the best of everything! Send me my FREE CIE school catalog—including details about troubleshooting courses—plus my FREE package of home study information. PE-44

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill information: Veteran Active Duty

MAIL TODAY!



Stereo Scene

By Ralph Hodges

THE BIG JUNE TRIAL BALLOON

Well, it's come and gone—another June Consumer Electronics Show in Chicago. This year's JCES was marked by two developments of note. The first was a concession on the part of show management to the demands of audio exhibitors for listening facilities. Several floors of meeting rooms in the McCormick Inn (across the street from the McCormick Place convention center that formerly hosted the entire show) were made available, thus greatly expanding the scope and sprawl of the affair. Second, in what almost seemed a counter-concession, a number of prominent very-high-end audio manufacturers left their aeries in the renegade Bismarck Hotel (one of the few large hotels not affiliated with the show) and moved their exhibits closer to or actually into CES territory. (Not that this "sank" the Bismarck; the vacancies were promptly usurped by a whole new generation of little companies looking to make their marks.)

Both developments dramatize the new importance of audio—and, recently, high-end audio—to the show's well-being. More than ever, high-end was the big game at JCES, and almost every-body played.

The Heavy Hitters. If pure power grabs you, you will not be immune to the Marantz Model 2500, the show's most powerful receiver, with a continuous (FTC) rating of 250 watts per channel. This receiver also re-introduces Marantz's small front-panel scope, a popular feature on previous deluxe models from the company. The continuous-power rating of Hitachi's SR-2004 receiver is a "mere" 200 watts per channel. However, since the amplifier section operates in Hitachi's novel Class G, it is said to be entitled to a short-term ("music power," if you will) rating of 400 watts per channel. Several other receiver manufacturers are now crowding the 200-watt mark, such as Technics by Pa-

nasonic (with 165 watts) and Nikko (175 watts).

Where does this power escalation put separate basic amplifiers? Well, you can get up to 500 watts per channel with the Rotel RB-5000. This product, incorporating enough transformer iron to pose a serious threat to any sidewalk on which it may be dropped, has a glorious brutality to its appearance that devotees of high power will appreciate on sight.

Many of the other major manufacturers now seem inclined to eschew brute force for its own sake and adopt the "purist" attitude that characterizes the audiophile-oriented smaller companies. Pioneer, for example, which retains its credentials in the high-power club (its new SPEC 4 power amplifier is rated at 150 watts per channel), has chosen to lead this year with the M-22 Class-A power amplifier (\$650) at 30 watts per channel. Onkyo's outlook on high-end equipment is similarly conservative, as exemplified by the P-303 preamplifier and M-505 power amplifier introduced earlier this year. Nikko established itself as a leader in Class-A power amplifiers some time ago. This year the company presents the Alpha V stereo power amplifier, featuring a healthy 100 watts per channel and a healthier price of \$3,000.

Meantime, integrated amplifiers evolve in their own fascinating ways. Kenwood believes in isolated power supplies, and the new 90-watt-per-channel KA-9100 has three: one for each output section and a third for the preamplifier. Sansui believes in wide bandwidth—not necessarily for the preamplifier section, where it may cause trouble, but certainly for the power-output stages. The AU-717 (\$450) and AU-517 (\$370) pursue this philosophy.

The Innovators. Soundcraftsmen's major contribution to the show was a claim for a new mode of amplifier operation, "Class H." Like Class G, Class H employs two power-supply voltages for

the output stage, the lower voltage being active most of the time and the higher voltage coming into use only on large waveform peaks. But Class H dispenses with Class G's two sets of output transistors and simply switches the supply voltages fed to one set. As in Class G, the object is to keep the output stage in the most efficient mode of operation possible, no matter what power level is being delivered to the load. Soundcraftsmen's initial Class-H offerings are the MA5002 power amplifier at 250 watts per channel, and a smaller Class-H power amplifier, the EA5003, with a built-in octave-band equalizer.

In the DL-2, Crown introduces the preamplifier it says it has always wanted to build. It is in three pieces: a power supply, a phono-preamplifier module designed to be located close to the record player, and a "switching module" (the DL-2 itself). This sports a complex-looking panel, with digital readouts of gain settings and a forest of controls. But inside, all is said to be simplicity itself, with none of the special control functions allowed to intrude on the signal path unless "enabled" by means of digital switching circuitry that operates high-quality relays.


A digital-readout frequency-synthesizing tuner is built in to the Setton RCS-X-1000 preamplifier/control center. The unit has throttle-like controls for gain and LED indicators for virtually everything. For remote control use, much of its circuitry is contained in a separate "black-box" module with generously long cable connection.

A little outboard air compressor is the key feature in the Infinity Black Widow "Air-Table." The Compressor floats the belt-driven platter on a compressed-air "bearing."

The Elaborators. While we're on the subject of turntables, you may recall ADC's digitally controlled Accutrac 4000. This year brings a changer version, the Accutrac +6, with the likable ability to return any records that have been "dropped" to the platter ("gently escorted" is a more accurate expression in this case) back up to the spindle-supported stack for another go-round. This is accomplished by punching appropriate buttons on the control panel (or on an ultrasonic remote controller), and the Accutrac +6 retains all the other automatic programmable features of the 4000.

In its MT-6225, Fisher has developed a new configuration for a direct-drive turntable motor. Its drive signal is de-

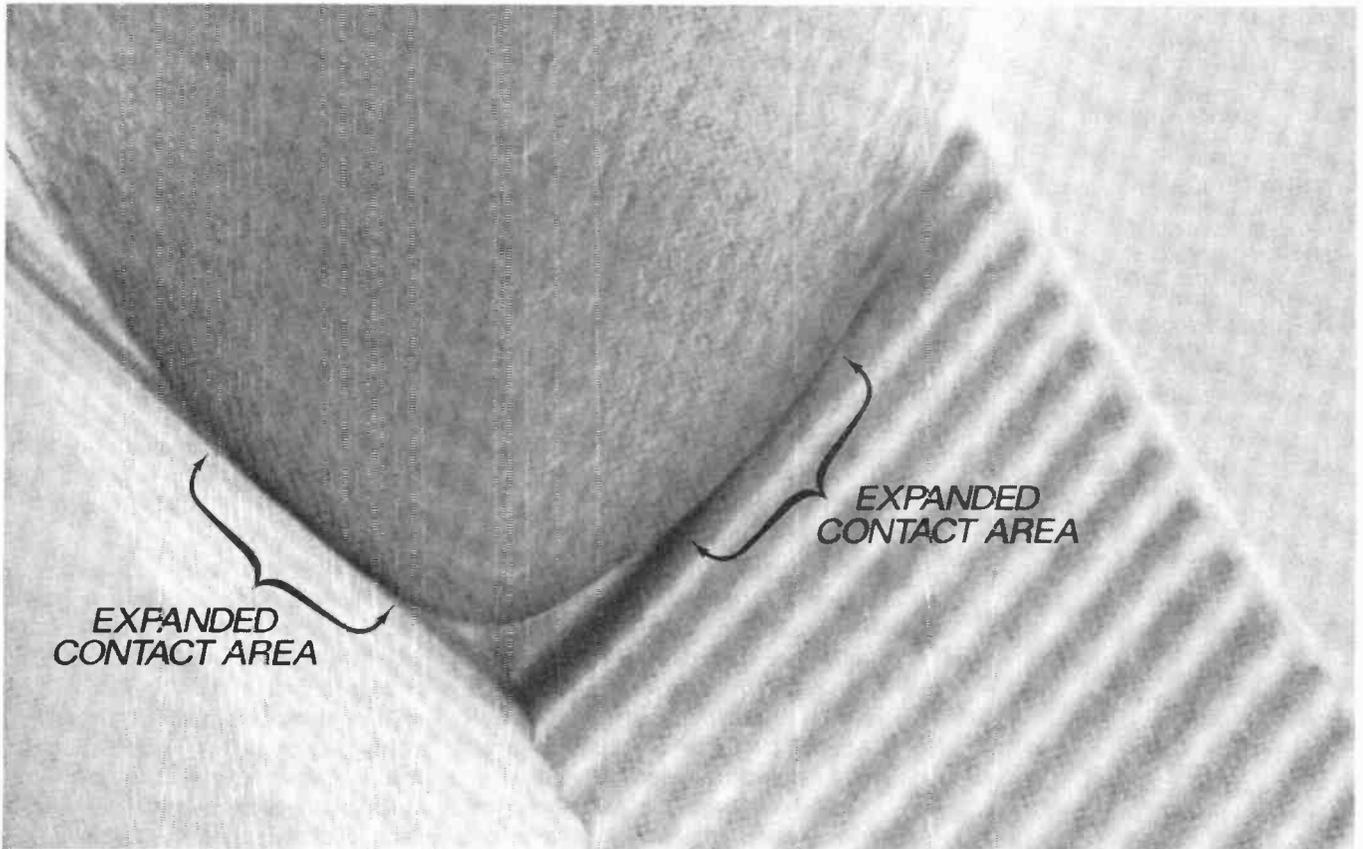Better records are the result of better playback pick-ups



© Stanton Magnetics, Inc., 1977

Scanning Electron Beam Microscope photo of Stereohedron Stylus; 2000 times magnification. Brackets point out wider contact area.

Enter the New Professional Calibration Standard, Stanton's 881S



Mike Reese of the famous Mastering Lab in Los Angeles says: "While maintaining the Calibration Standard, the 881S sets new levels for tracking and high frequency response. It's an audible improvement. We use the 881S exclusively for calibration and evaluation in our operation."

The recording engineer can only produce a product as good as his ability to analyze it. Such analysis is best accomplished through the use of a playback pick-up. Hence, better records are the result of better playback pick-up. Naturally, a calibrated pick-up is essential.

There is an additional dimension to Stanton's new Professional Calibration Standard cartridges. They are designed for maximum record protection. This requires a brand new tip shape, the Stereohedron®, which was developed not only for better sound characteristics but also the gentlest possible treatment of the record groove. This cartridge possesses a revolutionary new magnet made of an exotic rare earth compound which, because of its enormous power, is far smaller than ordinary magnets.

Stanton guarantees each 881S to meet the specifications within exacting limits. The most meaningful warranty possible, individual calibration test results, come packed with each unit.

Whether your usage involves recording, broadcasting or home entertainment, your choice should be the choice of the professionals... the STANTON 881S.



For further information write to Stanton Magnetics, Terminal Drive, Plainview, New York 11803

This new Stanton advertisement will appear in major consumer publications.

ALTAIR™ COMPUTER CENTERS

TUCSON, AZ 85711
4941 East 29th St.
(602)-748-7363

BERKELEY, CA 94710
1044 University Ave.
(415)-845-5300

SANTA MONICA, CA 90401
820 Broadway
(213)-451-0713

DENVER, CO 80211
2839 W. 44th Ave.
(303)-458-5444

ATLANTA, GA 30305
3330 Piedmont Road
(404)-231-1691

PARK RIDGE, IL 60068
517 Talcott Road
(312)-823-2388

ANN ARBOR, MI 48104
310 East Washington Street
(313)-995-7616

MADISON HEIGHTS, MI 48071
505-507 West 11 Mile St.
(313)-545-2225

EAGAN, MN 55122
3928 Beau D'Rue Drive
(612)-452-2567

ST. LOUIS, MO 63130
8123-25 Page Blvd.
(314)-427-6116

DAYTON, OH 45414
5252 North Dixie Drive
(513)-274-1149

TULSA, OK 74135
110 The Annex
5345 East Forty First St.
(918)-664-4564

BEAVERTON, OR 97005
8105 SW Nimbus Ave.
(503)-644-2314

LINCOLN, NB 68503
611 N. 27th St. Suite 9
(402)-474-2800

CHARLOTTE, N.C. 28205
1808 E. Independence Blvd.
(704)-334-0242

ALBUQUERQUE, NM 87110
3120 San Mateo N.E.
(505)-883-8282, 883-8283

ALBANY, NY 12211
269 Osborne Road
(518)-459-6140

NEW YORK, NY 10018
55 West 39th Street
(212)-221-1404

DALLAS, TX 75234
3208 Beltline Road, Suite 206
(214)-241-4088 Metro - 263-7638

HOUSTON, TX 77036
7302 Harwin Drive, Suite 206
(713)-780-8981


RICHMOND, VA 23230
4503 West Broad St.
(804)-355-5773

SPRINGFIELD, VA 22150
6605 A Backlick Road
(703)-569-1110

CHARLESTON, W.VA. 25301
Municipal Parking Building
Suite 5
(304)-345-1360



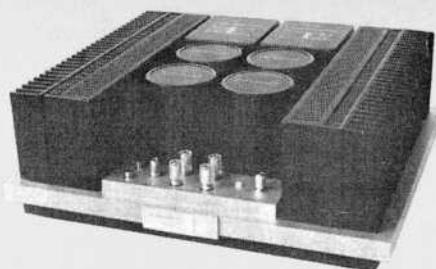
Marantz 2500 AM/Stereo FM Receiver is rated at 250 watts per channel.



Pioneer M-22 Power Amplifier is rated at 30 watts per channel.



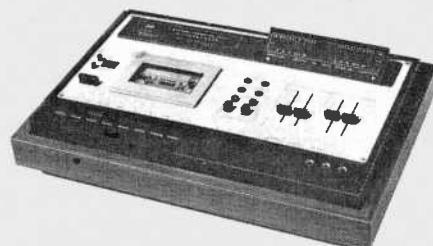Kenwood's KA-9100 Integrated DC Stereo Amplifier has three separate power supplies.



Model C-939 Cassette Deck from Dual has automatic reversing in both recording and playback.

rived from a 120-pole rotor (part of the platter) which amplitude-modulates a 60-kHz oscillator signal that passes through sensing coils in close proximity to the rotor. The back-EMF from the motor itself is routed through the motional-feedback circuit, where it is compared with a stable dc reference voltage.

I'm personally glad to note some new developments in tonearms, prominent among which is the Technics EPA-100, offered on the new SL-1000 Mark II direct-drive turntable. The EPA-100 is a damped arm designed to accommodate itself to almost any cartridge. The arm has "dynamic damping" which not only dulls arm/cartridge resonance, but adjusts to match cartridge compliance. Very-low-mass arms continue to appear, the latest being the LMF from ADC, offered with and without detachable headshells. The LMF has a tapered carbon-fiber shaft and an appearance of high precision.

Dual's Model C-939 cassette deck offers automatic reversing in both recording and playback, and it introduces the erase head as a tape-editing feature. A unique control admits continuously variable erase current to the head, where it can be used to create fade-outs, fade-ins, or total obliteration of a previously recorded signal.

The Upstarts. With so many pursuing the serious-audiophile segment of the market, where does that leave the devotedly audiophile-oriented companies? More rarefied than ever. Threshold, which in its short history has established

itself as one of the country's most prominent manufacturers of Class-A power amplifiers, introduced this year a preamplifier, the NS 10, with a response that extends to 5 MHz. The Van Alstine Model One preamplifier handily matched this feat by playing a color TV set through its circuits. While you recover from the shock of these revelations, you might want to contemplate the limited-bandwidth school of preamplifier design. The Apt Corporation's Holman Preamplifier will have nothing to do with ultrasonic or infrasonic signals. Tom Holman's arguments for eliminating out-of-band information are sophisticated and persuasive. Some would call his preamplifier radical for its inclusion of tone controls and other amenities that have been rapidly disappearing from such products.

Vacuum tubes, until recently so beloved by the audiophile "fringe" for their alleged sonic superiority, are gradually passing away as more and more designers work out transistorized circuits that can suit their purposes. But the end of tubes is not here yet, as witness the remarkable Audionics BA-150 power amplifier with a transistorized front end and tube output stages. The chunky unit is rated at 200 watts per channel, which is very substantial. As for heat and its pernicious effect on tube life, this has been thwarted by "floating" bias and operating voltages that are under the benign governance of high-speed digital control circuitry. I expect this amplifier was a lot of fun to design.

The Indefatigables. The untiring

Powerful in computing muscle, yet small in physical size, the Altair™ 680b offers many special features at an affordable price. Based on the 6800 microprocessor, the 680b comes with 1K of static RAM, Serial I/O port, PROM monitor and provisions for 1K of PROM as standard components. It's good thinking, when you're interested in making a modest investment on a highly reliable computer, to consider the Altair 680b.

Our PROM monitor eliminates the necessity for toggling front panel switches to load bootstraps or manipulate memory contents. Only a terminal and programming language are required for complete system operation. With Altair System software—Altair 680 BASIC, assembler and text editor—you may begin problem solving immediately with ease.

By adding the 680b-MB Expander card, many options are currently available:

*16K Static Memory Board—Increase your system memory with 16K bytes of fast access (215 ns), low power (5 watts per board) static RAM. 680 BASIC and assembler/text


editor are included free with purchase.

*Process Control Interface—A PC card that uses optically isolated inputs and relay outputs that transmit sensory information to and control signals from the computer. A diverse world of control applications is opened up with the Altair 680b-PCI.

*Universal Input/Output Board—If your I/O needs exceed the serial port already on the main board, augment your I/O channels with the 680b-UI/O. By implementing the optional serial port and two parallel ports, you can simultaneously interface to four terminals.

*New Addition—Kansas City Audio Cassette Interface—Use the 680b-KCACR to interface your Altair 680b with an audio cassette recorder for inexpensive mass storage of programming languages, programs and data.

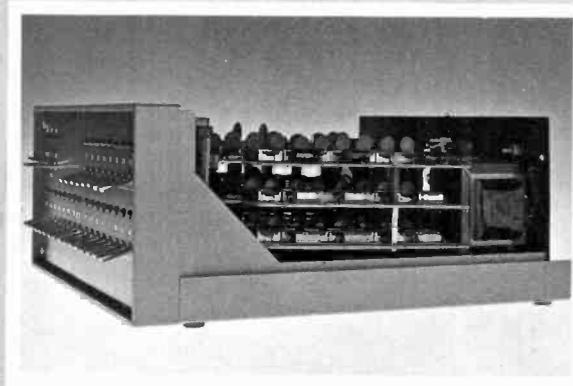Available in either full front panel or turnkey models, the Altair 680b presents many computing capabilities at a low cost—without skimping on performance. See it today at your local Altair Computer Center or contact the factory for further details.




Good Thinking.



2450 Alamo S.E. Albuquerque, New Mexico 87106
dealer inquiries invited.

CIRCLE NO. 29 ON FREE INFORMATION CARD

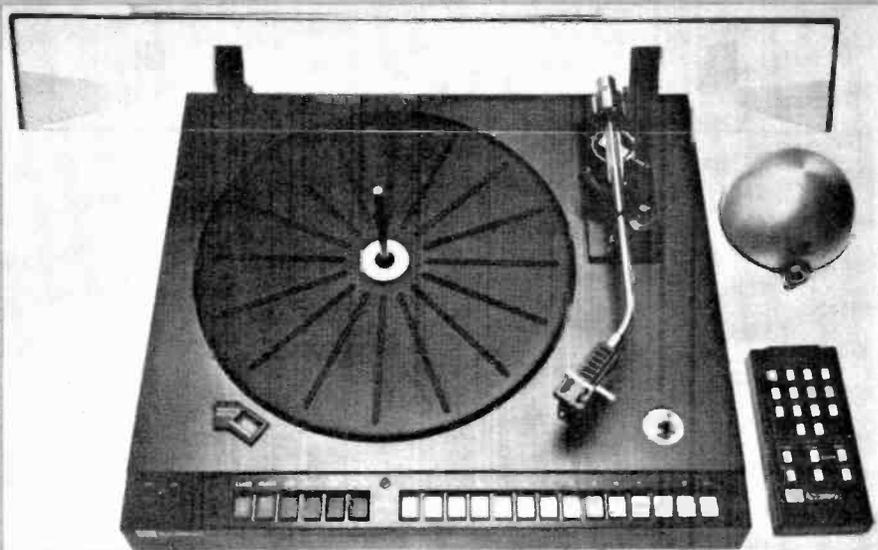


The Accutrac +6 Turntable has the automatic programmable features of its predecessor, the 4000, and also can be set to return a record to the stack on top of the spindle.

A digital-readout frequency-synthesizing tuner is built in to the Setton RCS-X-1000 preamplifier/control center.



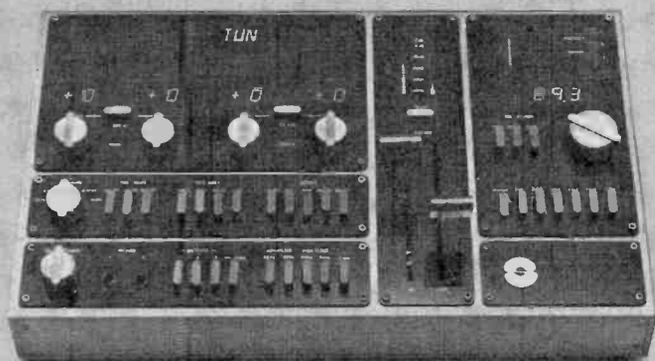Crown's DL-2 preamplifier has a "switching module" with all of the controls and a phono-preamp module (right) to be located close to the record player.



search for perfection in phono cartridges continues, and you can now pay \$325 for a Satin moving-coil cartridge with Shibata stylus and beryllium cantilever. The Satin cartridges remain the only moving-coil designs with user-replaceable styli, and among the few such designs with output sufficient to drive most phono preamplifiers without assistance from a transformer or intermediate gain stage. So far as I know, Satin commands the top price point in phono cartridges today, but others are not too far behind. The Model 9210SG from RAM Audio Systems, a strain-gauge pickup is \$300 with the necessary external power supply. The Micro-Acoustic 530-mp is \$200. And the Stanton 881S is \$150.

Nor is there a lack of associated equipment for these new cartridges. The precision phono preamplifier for moving-coil and other pickups is now an established product. The Accuphase C-220 Stereo Disc Equalizer is designed to load and equalize any cartridge properly, supply gain that is immaculate in terms of noise and distortion, and bal-

ance the outputs of the two channels. A&E Technical Research offers a similar product, with elaborations that include a front-panel meter to read levels.

A year ago the manufacturers of the new sub-woofers were speaking out loudly for attention. Since then, several prophets have asked the question: "With a good sub-woofer, who needs a woofer?" And it's proved to be a good question. Audio enthusiasts around the country have been combining the phenomenally good (but bass-lacking) mini-speakers from ADS, Braun, and Visonik, among others, with sub-woofers from Janis, Dahlquist, etc., to produce full-range bi-amplified speaker systems for the home. They often sound as good as the best while costing little more than the mediocre. Janis has even devised an accessory to facilitate this—a stereo electronic crossover combined with a single-channel, 70-watt amplifier for the woofer. The phase relationship between the low- and high-frequency signals is continuously variable.

This year's new wave in four-channel

sound will come from the Tate SQ decoder, now finally completed and encapsulated in three integrated circuits. The decoder boasts remarkable specifications, and the demonstration I heard left little doubt in my mind that many of the claims made for it are justified. The Tate people intend to offer the decoder to amplifier and receiver manufacturers, among which licensees are now being gathered. (Audionics has already announced its Tate decoder.)

The End. The end, obviously, is not yet in sight. More than anything else, this year's JCES was erected on shaky foundations laid down some years ago that have become much firmer in the intervening period. The serious audiophile is once more at the top of the heap, and his requirements are being elaborately—even extravagantly—catered to. In coming months this should lead to a vast proliferation of products that are claimed to "sound good." Ultimately, with luck, it will result in a whole community of products that "sound better." ♦

Para - Power

(Parametric Equalizers by SAE)

SAE has long been involved in the field of tone equalization. From our pioneering efforts in variable turn over tone controls to our more recent advancements in graphic equalizers, we have continually searched for and developed more flexible and responsive tone networks. From these efforts comes a new powerful tool in tone equalization — the Parametric Equalizer. Now you have the power of precise control.

Our 2800 Dual Four-Band and 1800 Dual Two-Band Parametrics offer you controls that not only cut and boost, but also vary the bandwidth and tune the center frequency of any segment of the audio range.

With this unique flexibility, any problem can be overcome precisely, and any effect created precisely.

With either of these equalizers, you have the power to correct any listening environment or overcome any listening problems that you are faced with. Whether you need a third octave notch filter, tailored bandwidth to resurrect a vocalist, or a tailored cut to bury an overbearing bass, the control flexibility of Parametric Equalizers can fill these needs and many more. And of course, as with all SAE products, they offer the highest in sonic performance and quality of construction.



only by

SAE

Scientific Audio Electronics, Inc.

P. O. Box 60271 Terminal Annex, Los Angeles, CA 90060

Learn electronics easier... with HEATHKIT®


MONEY-BACK GUARANTEE

We're so confident you will enjoy and benefit from these five courses, that if for any reason you are dissatisfied, we will refund the full purchase price of the course text material.

Unique Heathkit Electronics Courses are designed to provide you with a complete overview of basic and advanced electronics.

You learn at your own pace, without pressure or deadlines, and all material is presented in a clear, logical, step-by-step fashion. It's the ideal, effective way to learn about electronics if you're a beginner, or to "brush up" on the latest techniques and theory.

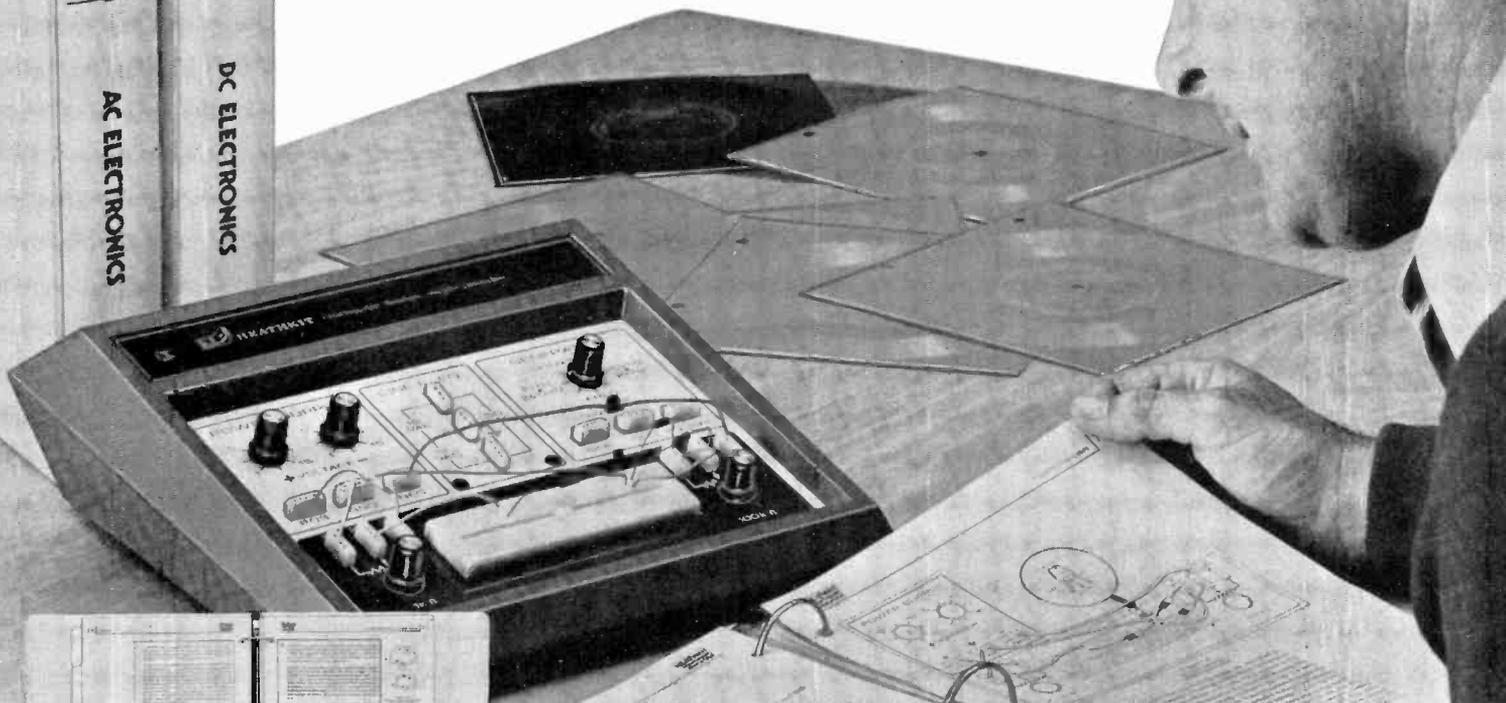Courses start as low as **\$39⁹⁵** (less trainer)



Thousands of people just like you have already learned electronics the easy Heathkit way — and you can, too. The secret is our efficient approach to self-learning with easy, step-by-step "programmed" instructions; audio records to introduce and reinforce key concepts; self-evaluation quizzes to test your understanding; and interesting experiments that let you learn the easy "hands-on" way. All you need is a record player, small tools and a VOM. The optional Heathkit experimenter/trainer is specifically designed to help you do the experiments in each course, and when you finish the course, you can use it to design and breadboard your own circuits. After completing each course, you can take the optional final exam (passing grade 70%) and receive both a Certificate of Achievement and Continuing Education Units, a nationally recognized way of acknowledging participation in non-credit adult education.

ORDER NOW — GET THESE BONUS SAVINGS!

GET THIS
WELLER
SOLDERING
IRON
worth

FREE!
WITH YOUR ORDER
A 40-watt
iron for easy
kitbuilding

Buy Any Single Course
with Trainer and —

SAVE \$9⁹⁵

Buy Courses 1 thru 4
with Trainer and —

SAVE \$24⁹⁵

Heath Company, Dept. 010-341 Benton Harbor, Michigan 49022

faster...at lower cost... Learn-at-home Courses!

COURSE 1: DC Electronics

An ideal introduction to electronics. Covers current, voltage, resistance, magnetism, Ohm's law, electrical measurements, DC circuits, inductance and capacitance. Discusses matter, atoms, current, flow, voltage rises and drops, series and parallel connections, magnetic fields, voltage dividers, network theorems, more. Includes text, records and 56 parts for 20 different experiments. Average completion time, 20 hours. 2.0 Continuing Education Units and certificate for passing optional final exam.

Course EE-3101 39.95

COURSE 3: Semiconductor Devices

Essential for understanding latest solid-state equipment. Covers fundamentals, diodes, zener diodes, special diodes, bipolar transistor operation and characteristics, FET's, thyristors, integrated circuits and optoelectronics. Discusses holes, current flow, N and P types, biasing, tunnels and varactors, PIN, IMPATT, gain, cutoff and leakage current, SCR's, bi-directional triodes, light sensitive and light emitting devices, more. Includes text, records and 27 parts for 11 different experiments. Average completion time, 30 hours. 3.0 Continuing Education Units and certificate for passing optional final exam.

Course EE-3103 39.95

COURSE 2: AC Electronics

Provides an understanding of most commonly used circuits. Covers alternating current, AC measurements, capacitive and inductive circuits, transformers and tuned circuits. Discusses waveforms, period and frequency, meters, scopes, series and parallel circuits, RC filters, dividers, phase shifts, reactance, vectors, transformer theory and characteristics, series and parallel resonance, more. Includes text, records and 16 parts for 8 different experiments. Average completion time, 15 hours. 1.5 Continuing Education Units and certificate for passing optional final exam.


Course EE-3102 39.95

COURSE 4: Electronic Circuits

Outstanding explanations of basic circuits. Covers basic amplifiers, special purpose amplifiers, operational amplifiers, power supplies, oscillators, pulse circuits, modulation and demodulation. Discusses amplifier functions and configurations, class of operation, audio characteristics, video amplifiers, buffers, IF's, rectifiers, voltage multipliers, voltage regulation, basic oscillators, RC waveshaping, clipping, AM, FM and SSB, modulation fundamentals and more. Assumes knowledge of courses 1 through 3 or equivalent and requires an oscilloscope for some experiments. Includes text, records and over 110 parts for 18 different experiments. Average completion time, 30 hours. 3.0 Continuing Education Units and certificate for passing optional final exam.

Course EE-3104 49.95

LEARN DIGITAL TECHNIQUES

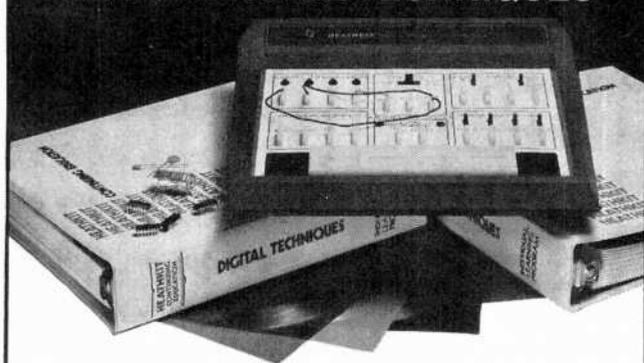

Our most advanced self-learning course prepares you for the world of computers and microprocessors, with particular emphasis on circuit design. Covers digital fundamentals, semiconductor devices for digital circuits, digital integrated circuits, Boolean algebra, flip-flops and registers, sequential logic circuits, combinational logic circuits, digital design and digital applications. Discusses TTL, ECL, CMOS, PMOS, NMOS; integrated circuits; SSI, MSI and LSI; ROM's, PLA's, microprocessors,

computers and more. Assumes completion of Heathkit courses 1 through 4 above, or equivalent knowledge. The special digital techniques experimenter/trainer helps you perform all the experiments in the course, and when you complete the course, build and design your own circuits. Course includes text, records and 44 parts for 24 different experiments. Average completion time, 40 hours. 4.0 Continuing Education Units and a certificate for passing final exam.

ORDER DIGITAL TECHNIQUES PROGRAM AND TRAINER... **\$109⁹⁵**

HEATH IM-17 VOLT-OHM METER

All Electronic Learning Programs require a VOM to make electrical measurements. We suggest the Heath IM-17 as the ideal "all-purpose" unit. All solid state with FET input for better accuracy. Portable battery operation, zero and ohms adjust, accessory probe jack. Comes with DC polarity switch, three test leads; batteries not included. Easy 3 hour assembly.



ORDER KIT IM-17 **\$32⁹⁵**

HEATHKIT EXPERIMENTER/TRAINER

For use with Heathkit Electronics Courses 1 through 4 — helps you perform all the experiments quickly and easily. Has solderless breadboarding sockets, dual variable power supply for positive and negative voltages, sine and square wave signal source, center-tapped line transformer. After you complete the course, the trainer is ideal for experimenting and breadboarding with your own circuit designs.

Kit ET-3100 **\$59⁹⁵**

HEATH

Schlumberger

Order Form/Agreement

Heath Company, Dept. 010-341
Benton Harbor, Michigan 49022

Please send me items checked below and include FREE \$7.95-value Weller Soldering Iron (GDP-1105).

Send one course (checked below) with the Experimenter/Trainer (ET-3100) at the special price of only \$89.95 plus \$3.00 shipping and handling.

DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103)
 Send me the Electronic Circuits Course (EE-3104) with the Experimenter/Trainer (ET-3100) at the special price of only \$99.95 plus \$3.00 shipping and handling.

Send all four of the courses above (EE-3101, 3102, 3103, 3104) with the Experimenter/Trainer at the special price of just \$199.95 plus \$4.50 shipping and handling.

In addition, please send the following courses (less trainer):

DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103) for just \$39.95 plus \$1.50 shipping and handling each.

Electronics Circuits (EE-3104) for just \$49.95 plus \$1.50 shipping and handling.

Send me the Digital Techniques Course (EE-3201) with its Experimenter/Trainer (ET-3200) for only \$109.95 plus \$3.00 shipping and handling.

Also send me that IM-17 VOM kit for just \$32.95 plus \$1.50 shipping and handling.

Michigan residents add 4% sales tax.

I enclose check money order for \$ _____; or, Charge to my:

BankAmericard Acct. No. _____ Exp. Date _____

Master Charge Acct. No. _____ Exp. Date _____

If Master Charge, include Code No. _____

Signature: X _____

Name (please print) _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____



Audio Reports

THE ELCASET HAS ARRIVED

MORE than a year ago, the Elcaset was announced to the high-fidelity audio world. Its name is derived from "large cassette," which is a fairly accurate description of this new tape format as far as its physical shape is concerned. Developed by a consortium of Japanese manufacturers—including Matsushita (Technics), Sony, and Teac—it is intended to bridge the gap between the standard cassette and the open-reel formats, with the convenience of the former and the performance of the latter. In addition, the Elcaset has a few advantages peculiar to itself. At present, all Elcaset tapes are made by Sony, but each of the participating manufacturers and some of their subsidiaries and affiliates produce their own competitive lines of tape decks based on their tapes.

The Elcaset itself is considerably larger than the conventional compact cassette. Resembling the cassette in general configuration, the Elcaset measures 6" × 4"D × ¾"H (15.2 × 10.1 × 1.9 cm), making it slightly larger than an 8-track tape cartridge pack. The Elcaset is loaded with standard ¼" (6.4-mm) tape, which can be recorded in four parallel tracks, two in each direction just as with the standard cassette. In addition, the Elcaset has provisions for recording two narrow control tracks between the pairs of signal tracks. These two extra tracks can be used for controlling slide projectors or for operating sophisticated signal processors when an Elcaset deck is used with devices designed to use the control feature.

At present, Elcasets are available in LC-60 and LC-90 versions. The two versions hold 30 and 45 minutes of program material on each side.

Unlike the standard cassette, with its 1⅞-inch/second (4.8-cm/s) tape speed, the Elcaset is designed to operate at 3¾ ips (9.5 cm/s). The combination of nearly double the tape width and double the tape speed gives the Elcaset a powerful advantage over the standard compact cassette in its freedom from high-frequency tape saturation (which is perhaps the most serious fundamental limitation of cassettes). Another unique feature of the Elcaset is that the tape is withdrawn from the cassette housing and passed over fixed heads in the tape deck, just as in an open-

reel tape deck. This makes possible almost any type of head configuration. This contrasts sharply with the standard cassette, which requires the heads to be moved to make contact with the tape within the cassette housing and where a third head can be used only by exercising considerable design ingenuity.

The Elcaset housing contains a number of notches and holes that give it a potential capability for almost totally automatic selection of operating parameters. For example, three types of Elcaset have been announced or are contemplated, each with a different formulation that requires its own particular bias and equalization adjustments. Type I tape is a low-noise ferric-oxide type that is currently used in Sony's SLH. Type II is Sony Ferrichrome (FeCr), while Type III is a chromium-dioxide formulation. Holes near one corner of the Elcaset's housing can identify the type of tape contained in the Elcaset so that, in a tape deck equipped to make use of this feature, the bias and equalization could automatically be selected as the tape is inserted. Other breakout tabs similar to those used for standard cassettes for recording lock-outs are used for switching in Dolby noise reduction system decoders when a tape has been Dolbyized.

Like the cassette, the Elcaset can be made to prevent accidental recording over a piece of tape whose contents are to be preserved. Instead of breaking out a tab, however, one moves a slide near one corner of the Elcaset housing to its safety position. If it is desired to rerecord over a protected portion of tape, the slide can easily be returned to its original, or "unprotected," position. (The Elcaset's design makes accidental movement of the slide impossible.)

The internal tape reels are locked in place when the Elcaset is removed from the recorder to prevent the creation of tape slack in shipping and handling. Hinged protectors minimize the likelihood of the tape being pulled from the housing accidentally. When the Elcaset is inserted into the tape deck, the hinged protectors move aside to allow the tape to be withdrawn and brought into contact with the tape heads. From then on, tape handling is completely automatic as the deck's controls are operated.



(Audio Test Reports start on page 34.)





**The first complete
low-cost microcomputer
system for home,
business or education!**

Radio Shack TRS-80

The TRS-80 is for people who want to use a computer now — without the delay, work and problems of building one. The system is fully wired, tested and U.L. listed — ready for you to plug in and use! Program it to handle your personal finances, small business accounting, teaching functions, kitchen computations, innumerable games — and use Radio Shack's expanding line of prepared programs on cassettes. The Z80-based system comes with 4K read/write memory and Radio Shack Level-I BASIC stored in read-only memory. Memory expandable to 62K bytes. Includes CPU, memory, keyboard, display, power supply, cassette data recorder, 300-page manual, 2-game cassette program. Designed and built in USA by Radio Shack. Only 599.95.



Includes everything
you need to start
using it immediately!



Clip and Mail Coupon Today!

Mail to: Radio Shack, Dept. TRS-80
205 N.W. 7th St., Ft. Worth, TX 76101

C003

Send me more data on the TRS-80 microcomputer

- Description of applications, software and peripherals available through Radio Shack • Owners' newsletter
- Price list • List of stocking stores and dealers

NAME _____ APT. NO. _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____


Radio Shack®

A TANDY COMPANY • FORT WORTH, TEXAS 76102
OVER 6000 LOCATIONS IN NINE COUNTRIES

Price may vary at Individual stores and dealers

SONY MODEL EL-5 ELCASET TAPE DECK

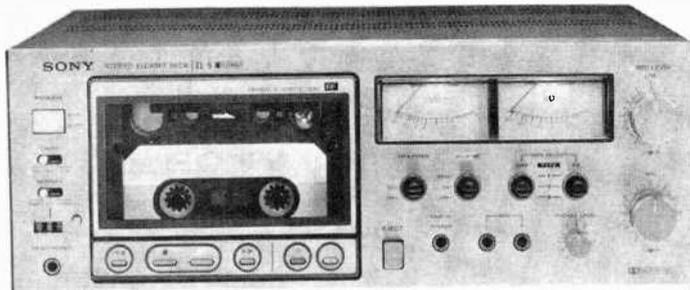Offers the convenience of a tape cartridge with performance of open reel.



In physical appearance, the Sony Model EL-5 Elcaset deck resembles a front-

loading cassette deck. The Model EL-5 is a relatively simple, basic deck, with no automatic parameter selection features. It uses a two-head configuration with a combined recording and playback head. (Although the Elcaset design makes three-head transports a practicality, the EL-5 uses only two heads, but Sony does make another model that offers the three-head feature.)

The Model EL-5 measures 17"W x 12 5/8"D x 6 3/4"H (43 x 32 x 17 cm) and weighs 23 lb (10.5 kg). Its nationally advertised value is \$599.50.

General Description. The Elcaset loads into the Model EL-5 vertically in a transparent hinged door that is opened by pressing an EJECT button. Below the door are light-touch pushbuttons that control the transport functions through solenoids and include rewind, fast forward, play, record, and pause functions. Colored symbols above the buttons glow to indicate the operating mode of the deck. A logic system allows the buttons to be operated in any sequence without damaging the tape.

To the left of the Elcaset door is a pushbutton POWER switch, and two three-position levers that control the TIMER and MEMORY functions. The TIMER switch can be used to start the deck with an external clock timer in the power line, in either the recording or the playback mode. The MEMORY circuit can be set to stop the tape in rewind when the counter returns to 000, or to go into PLAY automatically at that point if desired. Below the MEMORY switch are the index counter and its reset button and a headphone jack for low-impedance phones.

Across the upper right of the panel are two large illuminated VU meters and a red REC light. Below these are four lever

switches, two of which separately control the recording bias and equalization for the three types of Elcaset tape. A third switch controls the Dolby system, with an extra position for recording Dolby FM broadcasts. In the DOLBY FM mode, the tuner's deemphasis time constant is changed to the required 25 μ s, and the recording level is set by a pair of controls in the rear of the machine so that the Dolby level tone transmitted by some FM stations gives a 0-dB meter reading on the EL-5. The signal is recorded in its Dolbyized form, and the recorder's Dolby circuits are placed in the playback path, where it is monitored with the correct frequency response and noise level, and heard in that form when subsequently played through the recorder with its Dolby system on. The fourth switch turns on the MPX filter that removes the 19-kHz pilot carrier from signals being recorded with Dolby.

At the right of the panel are concentric recording level controls for the LINE and MIC inputs, which can be mixed. Across the bottom of the panel are the two microphone jacks, a stereo LINE input jack that replaces the normal LINE jacks on the rear apron when a plug is inserted, and a small knob that controls the playback level through the headphone jack.


The rear panel contains the LINE input

and output jacks, a LEVEL adjustment for the LINE outputs, two FM CAL level controls, a socket for an optional REMOTE CONTROL accessory, and one switched and one unswitched accessory outlet.

Laboratory Measurements. The Model EL-5 Elcaset deck we tested came with a prerecorded demonstration tape and samples of Type I and Type II blank Elcaset. (Type III is not yet available.) Since there are no standard test tapes as yet for the Elcaset, we made all our measurements by recording and playing back the same tape.

With the Type I (Sony SLH) tape, the record/playback frequency response at a -20-dB level was within ± 0.5 dB from 60 to 20,500 Hz. It was down 4 dB at 20 and 22,400 Hz. At a 0-dB recording level, the playback output dropped rapidly above 10,000 Hz, due to tape saturation. The superior high-frequency qualities of Type II (FeCr) tape were dramatically demonstrated by its frequency response, which was within ± 0.5 dB from 60 to 24,000 Hz at -20 dB, down 4 dB at 20 and 26,200 Hz. Even at 0 dB, the Type II tape revealed little evidence of tape saturation, with a response within ± 2 dB from 20 to 21,500 Hz. The MPX filter, which operates only during recording and had no effect up to 15,000 Hz, cut the 19,000-Hz response by at least 25 dB.

To reach a 0-dB recording level, a LINE input of 56 mV or a MIC input of 0.145 mV was needed. The resulting playback level was about 650 mV. The microphone preamplifier overloaded at a 70-mV input. The superior tape headroom of the Elcaset format was further demonstrated by very low distortion at a 0-dB recording level of only 0.08% with Type I and 0.28% with Type II tape. To reach a 3% playback distortion level, we had to record the tapes at +10 and +12 dB, respectively. The unweighted S/N

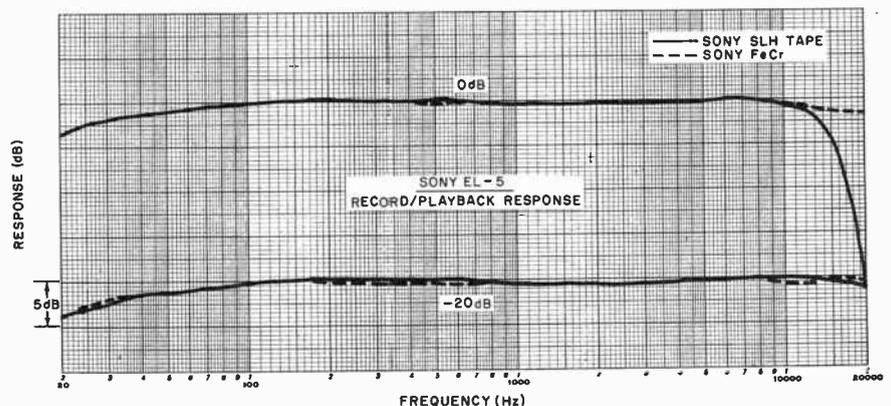

Record/playback response for two kinds of tape at 0 and -20 dB.

ratio, without Dolby, was 47.5 dB with Type I and 50 dB with Type II. With the Dolby system switched in, and using the CCIR weighting recommended by Dolby Laboratories, the S/N figures were improved to 67.7 and 70.5 dB. Through the microphone inputs, at maximum gain, the noise increased by 8.5 dB. The Dolby circuits tracked closely between recording and playback modes. The Dolby system changed the overall record/playback frequency response by no more than 1 dB at levels from -20 to -40 dB.

The unweighted rms wow and flutter was only 0.07%. An LC-60 Elcaset was moved from end to end in the fast speeds in about 76 seconds. The VU meters were slower in their response than a true VU meter. They reached 65% to 70% of their steady-state readings on 0.3-second tone bursts. The headphone volume was good with 8-ohm phones but was rather low with 200-ohm phones.

User Comment. There can be no doubt that the Elcaset, especially with the Type II (FeCr) tape, is a vastly superior medium to the compact cassette, especially with respect to high-frequency recording headroom. It is not inferior to cassettes in any of its performance characteristics. This is not surprising, given the Elcaset's 3 3/4 ips and 1/4-inch tape. A more dramatic contrast is that it matches the performance of the

many open-reel decks that operate at 7 1/2 ips. Of course, much of the credit for this must go to the FeCr tape, which is not generally available for open-reel machines (nor are such decks, with the exception of one or two Sony models, equipped to use FeCr tape).

Judged solely on its own merits, the Elcaset, even in the modestly priced Model EL-5 deck appears to be a no-compromise high-fidelity recording medium for the home recordist. Used with extreme care, only the best cassette recorders can approach the overall performance of the Elcaset, and this is possible only by careful control of recording levels. (Such machines, incidentally, are considerably more expensive than the model EL-5.)

We found the Model EL-5 to be a very easy deck to use, too. The absence of a third head for monitoring caused us some concern at first, but we soon found that the entire recording process was so noncritical that there was little need to monitor while recording.

The Elcaset is as easy to handle as a regular cassette (perhaps easier, due to its larger size). Presumably, it could be spliced and edited like open-reel tape, although we would have misgivings about withdrawing any substantial amount of the tape from an Elcaset housing.

Like most people closely involved with high-fidelity matters, we have given considerable thought to the place of the El-

caset in the hi-fi picture. Our first reaction to its announcement was one of skepticism. After all, who needs a "better" cassette? Having lived with the Model EL-5 for some time, we appreciate how much of a "better cassette" it really is. The Type II Elcaset (and probably the Type III, when it becomes available), is really a full equivalent of 7 1/2-ips open-reel tape in sheer quality. In contrast to the clumsiness of handling open-reel tape, the Elcaset offers all the convenience of use that has helped make the compact cassette so popular. Further, the Elcaset recorder is closer in size and weight to a cassette deck than to the open-reel machine. We understand, too, that the Elcaset tapes will be priced comparably to open-reel tapes.

One should be aware that, for dubbing most phonograph records and FM broadcasts, the Elcaset does not offer any quality advantage over the compact cassette. Only when the dynamic range of cassettes is inadequate or marginal, as in the case of almost all "live" recording, does the Elcaset clearly demonstrate its superiority. There are no commercially recorded Elcasets on the market, and we would not expect any significant number to be produced. The Elcaset is strictly for the "do it yourself" tape enthusiast who does not intend to do much editing but wants the convenience of a tape cartridge with the performance quality of an open-reel tape deck.

CIRCLE NO. 101 ON FREE INFORMATION CARD

H.H. SCOTT MODEL R376 STEREO RECEIVER

More receiver than modest specifications imply.



The Model R376 AM/stereo FM receiver, which heads the current line from H.H.

Scott, is rated to deliver 75 watts/channel into 8-ohm loads at less than 0.2%


THD. Manufactured in Japan to Scott's specifications, this receiver features contemporary styling with a distinct European touch in its panel markings.

The satin-finished silver-colored front panel has a large, clear glass window, behind which is a similarly finished dial

scale, tilted slightly back for better visibility. Above the dial scales are five colored lights that indicate which input has been selected and separate tuning meters for relative signal strength on AM and FM and center-channel tuning on the latter.

The receiver is supplied with a walnut finished wooden cabinet. It measures 19 3/8"W x 15 7/8"D x 5 3/4"H (49 x 40 x 14.4 cm) and weighs 30.8 lb (14 kg). Price is \$549.95.

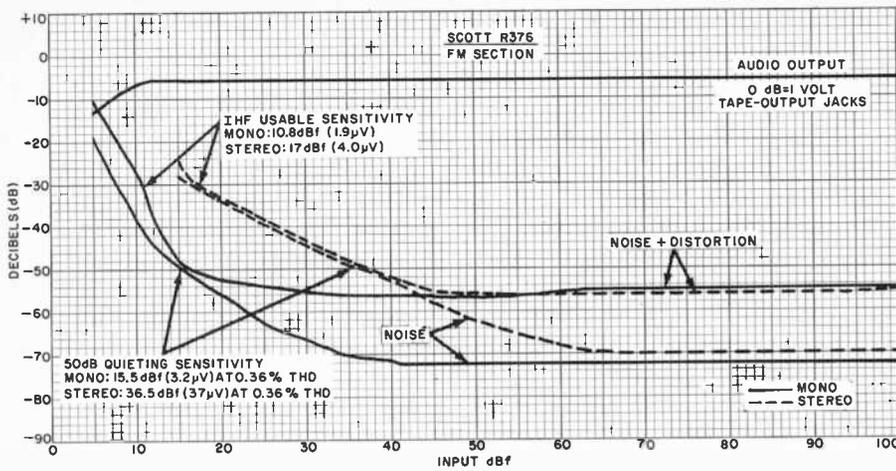General Description. The input SELECTOR switch has positions for AM and FM tuners, magnetic PHONO cartridge, dynamic MIC (through a jack on the front panel), and high-level AUX program source. The BASS, MIDRANGE and TREBLE controls each have 11 detented positions. The POWER/SPEAKERS switch can be set to connect to the amplifier, ei-



Noise and sensitivity curves for FM section of receiver.

ther, both, or neither of two pairs of speaker systems.

The VOLUME and BALANCE controls are concentric. The VOLUME control has 41 detented positions, while the BALANCE control is a standard potentiometer with a detented center position. A push-button switch activates the LOUDNESS compensation that works with the VOLUME CONTROL. Two other pushbuttons are used to switch in and out the LOW and HIGH audio FILTERS. Pushbuttons also switch in and out the FM MUTING and select STEREO/MONO modes.

The only remaining controls are the large TUNING knob and two three-position lever switches for the tape recording functions. One of the switches for the tape recording functions is a COPY switch that cross-connects two tape decks for dubbing from either machine to the other. The other switch is labelled MONITOR and is used for connecting either the selected source or the playback output from either tape deck to the receiver's audio amplifiers.

On the rear apron are phono jacks for the various signal inputs and outputs, a

DIN socket that duplicates the TAPE 1 functions, and insulated spring clips for the speaker connections. Binding posts are used for the antenna connections, and there is a hinged AM ferrite-rod antenna. Slide switches are provided for selecting 25-, 50-, or 75-μs FM deemphasis time constants and high and low sensitivities to accommodate high- and low-output phono cartridges. One of the two accessory ac outlets on the rear apron is switchable.


Laboratory Measurements. Although the rear apron of the receiver became quite hot during the one-hour preconditioning period at one-third rated power and subsequent tests, the rest of the receiver's exterior remained cool. Driving 8-ohm loads with both channels at 1000 Hz, the output clipped at 109 watts/channel. Into 4 and 16 ohms the clipping power was 96 and 75 watts, respectively.

The 1000-Hz THD was very low at all usable power levels. It increased smoothly from 0.006% at 0.1 watt to 0.11% at the rated 75 watts and to

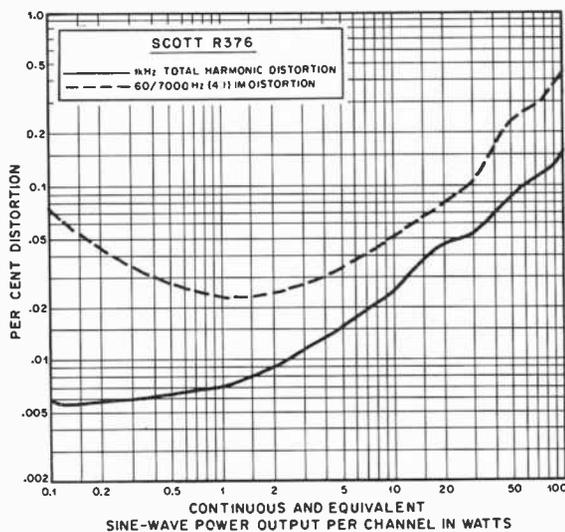
0.16% at 100 watts. The IM distortion was less than 0.075% from 0.1 to 20 watts output and increased to about 0.3% at 75 watts and to 0.42% at 100 watts. At the rated 75-watt output into 8 ohms, the THD was typically between 0.06% and 0.1% from 20 to 1000 Hz. It rose to 0.27% at 5000 Hz, after which it remained at about 0.27% all the way up to 20,000 Hz. At lower power levels, the shape of the distortion curve was similar, but the values were considerably lower. (At 7.5 watts output, distortion was under 0.07% from 20 to 20,000 Hz.)

To develop a reference output of 10 watts, a high-level input of 50 mV or a phono input of 0.82 mV (1.9 mV with the lower input sensitivity switch setting) was required. The S/N was roughly the same for all inputs at about 72 dB, referred to 10 watts. The phono overload input was a very safe 130 mV (290 mV with the lower sensitivity setting).

The bass tone control had the usual sliding turnover frequency characteristics. It varied from about 100 to 700 Hz as the control was moved from its center position. The treble response curves were "hinged" at about 1000 Hz. The midrange control affected most of the audible range, its maximum effect being between 1000 and 2000 Hz. The maximum range of this control was about ± 6 dB, making it unlikely to produce bizarre effects if used incautiously. The filters had the highly desirable (and rare) 12-dB/octave slopes, although Scott does not mention this in the specifications. The -3-dB response frequencies of the filters were 120 and 3700 Hz. The loudness compensation boosted both low and high frequencies at reduced volume control settings. The RIAA phono equalization was very accurate, within ± 0.5 dB of the extended ideal characteristic from 20 to 20,000 Hz. The interaction



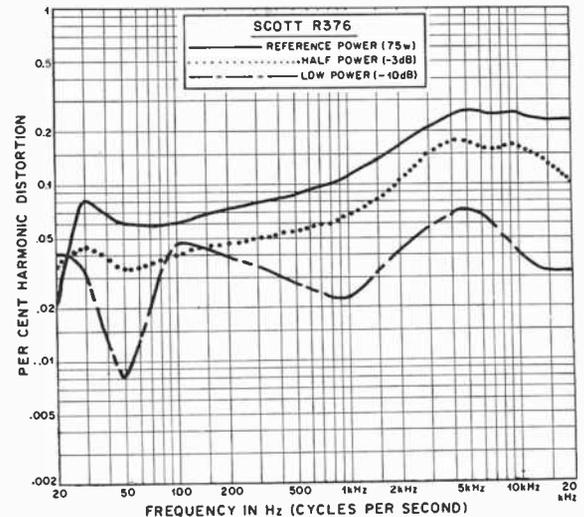Total harmonic distortion and 60/7000-Hz distortion.



Harmonic distortion at three power levels.

You're looking at the world's best-designed tonearm.

This is a Dual tonearm. It can make a big difference in the way your records sound. And how long they last.

The four-point gyroscopic gimbal is widely acknowledged to be the finest suspension system for a tonearm. It pivots the tonearm precisely where the vertical and horizontal axes intersect. The arm remains perfectly balanced in all planes of movement.

Further, the straight-line tubular design achieves the shortest distance between pivot and stylus. That's basic geometry. Curving the tonearm adds mass, decreases rigidity and makes the arm prone to lateral imbalance.

The vernier counterbalance permits you to balance the tonearm with micrometer-like precision. Tracking force is applied so that the stylus remains perpendicular to the record, even if the chassis is not level.

All this serves to establish and maintain the correct cartridge-to-groove relationship. So the stylus can trace the rapidly changing undulations of the groove walls freely, precisely and with the lowest practical force. In short, flawless tracking.

Despite the advantages of the gimbal-mounted tonearm, you won't find many around. But now, you will find one on every Dual turntable. Even our lowest-priced model, the new, fully automatic 1237.*

It's one more example of Dual's total commitment to engineering excellence.



Dual

For the life of your records

United Audio, 120 So. Columbus Ave., Mt. Vernon, NY 10553

*Less than \$135. Other Duals to \$400. Actual resale prices are determined individually by and at the sole discretion of authorized Dual dealers.

CIRCLE NO. 4 ON FREE INFORMATION CARD

AmericanRadioHistory.com

unique ballpoint

BY Xcelite®



DRIVES HEX SOCKET SCREWS FROM ANY ANGLE

Ever try to drive hex socket screws from an odd angle? Want an easier, faster way to drive 'em under any conditions? HERE'S YOUR ANSWER: With unique "ballpoint," you can slip these Xcelite screwdrivers into hex sockets . . . slick as a whistle and secure as a vise . . . straight-on or from any angle . . . to drive 'em home in a flash! 9 sizes: .050"-3/16." With fixed handles, singly or complete set in roll up kit, and as interchangeable Series 99 blades, singly or with handle and extension in compact case. Metrics, too.



Ask your local distributor or write . . .


**Weller-Xcelite
Electronics Division**



The Cooper Group

P. O. BOX 728,
APEX, NORTH CAROLINA 27502

CIRCLE NO. 62 ON FREE INFORMATION CARD

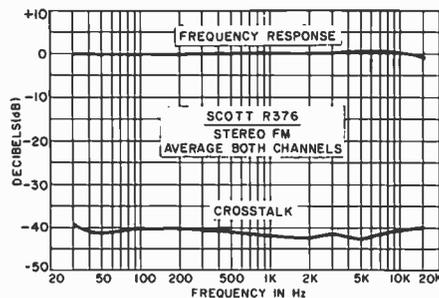

Frequency and crosstalk averaged for both channels.

with phono cartridge inductance was slight, producing a drop of about 1 dB in response between 10 and 20 kHz.

The FM tuner section generally met or surpassed its specifications, within normal measurement tolerances. The IHF usable sensitivity was 10.8 dBf (1.9 μ V) in mono and 17 dBf (4 μ V) in stereo. The 50-dB quieting sensitivity was 15.5 dBf (3.2 μ V) in mono and 36 dBf (37 μ V) in stereo, both with only 0.36% THD. The distortion at 65 dBf (1000 μ V) input was 0.19% in mono and 0.16% in stereo, and the respective S/N figures were 72 and 69.5 dB. In stereo, the THD at 65 dBf with a L - R modulating signal was 0.45% at 100 Hz. It was a very low 0.075% at 1000 Hz, 0.08% at 6000 Hz.

The FM frequency response was flat within ± 0.5 dB from 30 to 15,000 Hz, yet the 19-kHz pilot carrier was suppressed to a barely measurable -85 dB. This implies either an unusually effective low-pass filter or some form of pilot cancellation circuitry in the multiplex section. There was no mention of such special features in the instruction manual, and no schematic was included, so we can only conjecture as to how this remarkable performance was achieved. The stereo channel separation was equally impressive, almost perfectly uniform at 39 to 42.5 dB from 30 to 15,000 Hz, and practically the same in both channels. This type of performance suggests the use of a phase-locked-loop (PLL) stereo demodulator, but there is no specific information on that subject.

Other FM performance specifications were generally of the same caliber. The capture ratio was 0.8 dB at 45 dBf and 1 dB at 65 dBf. AM rejection was an acceptable 56 dB at 45 dBf, improving to a very good 70 dB at 65 dBf input. The image rejection was 78.5 dB, and alternate channel selectivity was identical above and below the receiver's center frequency, measuring 72.3 dB. Adjacent-channel selectivity was 4.9 dB. The factory settings of the muting and stereo thresholds were identical, at 12 dBf (2.2 μ V).

In view of Scott's former reputation for

exceptional AM tuner quality, we were somewhat disappointed to find that the AM section of the Model R376 was very ordinary in its frequency response. The response was down 6 dB at 3000 Hz, although it was maintained at full level down to 20 Hz.

User Comment. The performance specifications of the Model R376, whether published by Scott or the results of our measurements, leave no doubt that this is a fine receiver. As often occurs, the bare measurements do not adequately define the true quality of a product. For example, instead of the distortion remaining low until the amplifier clips abruptly and the distortion rises rapidly, in this receiver, the distortion increases so gradually that the clipping point is not at all obvious from the distortion measurements. This soft clipping characteristic is recognized as being the best way for an amplifier to overload, since it does not tend to produce very-high-order harmonics that are unpleasant to the ear. In spite of its rather modest (by today's standards) 75-watt power rating, the Model R376 could fairly be described as a 100- or 110-watt receiver. It will deliver that much power without sounding unpleasant. (Its distortion is almost all second- and third-harmonic.)

The real quality of the FM tuner section may not be apparent to anyone who has not made measurements on a number of tuners. In almost every case, one must make allowances for departures from ideal performance, so that the tuning is adjusted for minimum distortion rather than for a center indication on the tuning meter. One also expects the tuning setting for minimum distortion or maximum separation to be quite critical (and not necessarily the same). Also, virtually all i-f response characteristics are asymmetrical so that selectivity measured above and below the set frequency will be different, requiring the two values to be averaged to obtain a final figure. These conditions are so "normal" that the IHF measurement standard defines the methods necessary to derive numerical results from sometimes ambiguous measurements.

All of this leads us to the fact that the FM tuner in the Model R376 had both minimum distortion and maximum separation at the same tuning point, which happened to coincide with a center meter indication. Tuning was not critical, which means the average user should have no difficulty realizing the same kind of performance we measured. The FM muting was both positive and noise-free.

Although it probably has little to do with actual performance (except as an indicator of how well the receiver is put together), we noted that the flywheel tuning mechanism would cover the entire band with one spin of the knob.

The receiver's top-notch electrical performance was unfortunately not completely matched by its human engineering aspects. If we seem to be nit-picking here, it is only because of the contrast

between the two. For example, the antenna terminals are too close together and are smooth (non-*knurled*) binding posts, creating difficulty in connecting the antenna. This was in sharp contrast to the excellent speaker connectors. In another area, the unusually long (9 1/4 inch) dial scale should have made accurate tuning a simple matter, but the dial markings at 1-MHz intervals would require a degree of care in interpolation to

set the tuning to a known frequency within the required 200-kHz accuracy.

Aside from these minor criticisms, we found the Model R376 to be a thoroughly enjoyable receiver to use. Its sound is faultless and its appearance and "feel" are what one would expect from a company's top receiver. And as we discovered, the R376 is more receiver than its modest specifications imply.

CIRCLE NO. 102 ON FREE INFORMATION CARD

SHURE MODEL 516EQ MICROPHONE

Has four built-in equalizer filters centered on 190, 560, 1650, and 4950 Hz.



A "flat" microphone frequency response is not always ideal for making a live tape

recording. The placement of the microphone relative to the performers, the acoustic properties of the room, and one's personal taste, among other factors, may make it desirable to modify the overall frequency response. ("Graphic equalizers," so popular among amateur recordists, are often used for this purpose.) There are many situations that call for equalization in which one does not have access to a graphic equalizer or its equivalent. Shure's Model 516EQ "E-Qualidyne" microphone is a novel and effective answer to that problem for the amateur tape recording enthusiast.

This unidirectional (cardioid) dynamic microphone has a nominal rated impedance of 150 ohms. It is compatible with microphone inputs having rated impedances between 25 and 3000 ohms, which encompasses the majority of


home-type open-reel or cassette recorders. The 1000-Hz output level, for one microbar of pressure, is rated at -81 dBV, or 0.09 millivolts. A three-pin male connector in the tapered end of the microphone's body mates with the furnished cable or any other cable fitted with a Cannon XL, Switchcraft A3, or equivalent plug. The cable supplied with the microphone is 4.6 meters (15 feet) long, and has a metal-bodied 6.3 mm (1/4 inch) phone plug at its free end. A 36" (0.91-m) adapter cable is supplied so that the microphone can be used with recorders equipped with miniature phone jacks for their microphone inputs.

The novelty of the Model 516EQ lies in its integral four-band equalizer that is controlled by four tiny switches recessed into the body of the microphone. Each switch introduces a broad response notch, nominally 6 dB deep, with center frequencies of 190, 560, 1650, and 4950 Hz. The 16 possible combinations of switch settings permits the response of the microphone to be tailored for a wide variety of circumstances. The instruction leaflet shows typical response curves for each of the switch combinations and describes the sonic effect of each.

The Shure 516EQ is supplied in a

rugged plastic storage case, with signal cable, mini-plug adapter, wind screen, and swivel adapter for stand mounting. For stereo recording, one can buy the Model 516EQ-PR that contains two complete Model 516EQ systems in a single carrying case. The price of the Shure Model 516EQ is \$75.

Laboratory Measurements. A rigorous measurement of microphone frequency response requires elaborate and specialized test facilities. Fortunately, it is also possible to make less exact measurements that show the microphone's effective response and how it compares to other microphones measured in the same manner. We use the same basic setup employed for speaker system testing. A speaker system, driven from the swept frequency output of a General Radio response plotter, is used as a sound source. First, the output of the speaker is plotted through our calibrated laboratory microphone at a distance of about 15" (38.1 cm) from the grille and on the central axis of the drivers. Then the test microphone is substituted for the reference microphone, making sure that both are positioned identically relative to the speaker. The swept measurement is

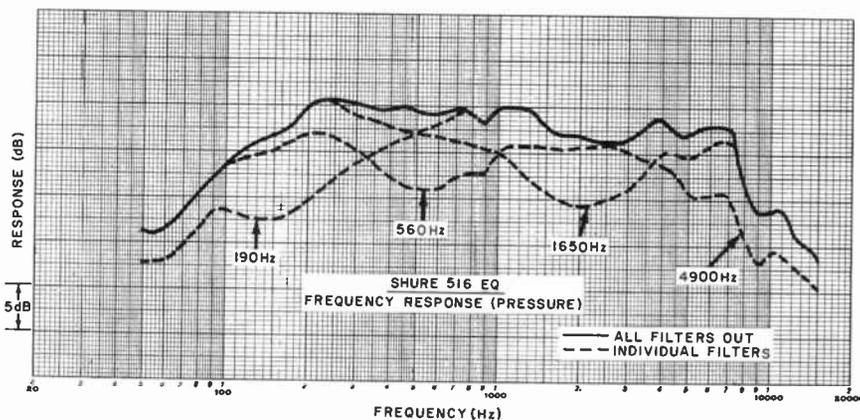

Frequency response (pressure) with all filters out and with individual filters in.

The Affordable Programmable

Never Before A Fully Programmable Calculator Available To The Scientific Community At Such A Low Cost!



by Mail Order
\$59⁹⁵

CALL TOLL FREE
800-323-2272
24 HOURS - 7 DAYS

SUMMARY OF SPECIFICATIONS

- 12 DIGIT RED L.E.D. DISPLAY entries or results in 3 modes, scientific, fixed point or engineering
- PROGRAMMABLE - 72 Keystroke program storage
- TRIG FUNCTIONS - Calculates in radians or degrees or grads
- HYPERBOLIC FUNCTIONS Ln, log, e^x, 10^x
- POWERS Y^x, Roots^x, Y^Y
- FUNCTIONS OF X - 1/x, X
- LINEAR REGRESSION: TREND ANALYSIS: SLOPE AND INTERCEPT
- STATISTICAL: Σ +, Σ -, averages, standard deviation, variance, permutations, combinations
- PERCENTAGE CALCULATION - add on/discount/yield Δ percentage
- π AND CHANGE SIGN KEY
- 10 MEMORIES - 7 functions - M+, M-, MR, Mx, M÷, STORE, 9M
- DEGREES/DEGREE, MINUTE, SECONDS CONVERSION
- RADIAN/DEGREE CONVERSION
- POLAR/RECTANGULAR CONVERSION
- 8 METRIC CONVERSIONS
- SPHERICAL/CARTESIAN CONVERSIONS

The Commodore PR (Personal Resource) 100 - Allows You To Personally Program According To Your Own Problem-Solving Needs!

WHY A PROGRAMMABLE?

The Commodore PR-100 Programmable Calculator introduces a new, innovative dimension in highly sophisticated mathematical and scientific problem-solving. It decentralizes and personalizes the decision-making power of the computer, bringing to you what was never before available in a programmable calculator with such features, yet at an amazingly affordable price.

Method of Entry: The Commodore PR-100 is designed for "Think and Touch" operation utilizing an algebraic mode of entry. You can enter equations which have up to 4 levels of parenthesis. Add to these features the 10 memory registers, and you can work the most complicated mathematical, scientific, engineering, business, statistical and combinational functions. Furthermore, you can also perform unit conversions: metric to English and English to metric.

Keyboard: The keyboard consists of 40 keys and 2 switches. 35 keys are for number and function entry. 10 of these keys are dual function (shifted keys).

SPECIALIZED FUNCTIONS:

Most of the important functions found on large scale computer systems are finally now available to you on the ultimate hand-held programmable calculator: iterative and recursive problem solving techniques; looping; conditional and unconditional branching.

ADVANTAGES OF THIS PROGRAMMABLE:

Consider for a moment the advantages of the Commodore PR-100. In terms of increased productivity you can now achieve the capability of: optimizing mathematical and scientific models; making trend and risk analyses; projecting and forecasting more accurately; performing statistical reductions; automating time-consuming "number-crunching."

The PR-100 is also a pre-programmed calculator that can achieve a multitude of functions: Basic + - × ÷ and = functions; clear entry or the entire calculation; Hyperbolic functions include: sinh, cosh, arc cosh and arc tan; Trigonometric functions include: sin x, cos x, tan x, arc sin x, arc cos x, and arc tan x. Calculates in radians, degrees or gradians. Enter x 0° to 360° (0 to 2π) or multiples of 360° (2 π). Natural Log (Ln x), Common Log (log x), Exponential (e^x), Antilog (10^x); Algebraic Functions include: x, x², 1/x, Powers: (Y^x); π (pi). Change Sign (+/-); x ↔ y exchange function; Parenthesis () enter equations that contain up to 4 levels of parenthesis without using temporary or intermediate storage.

Memory Functions: The PR-100 has 10 separate memory registers. For each memory there are 7 operations that can be performed: memory storage and clear, recall, addition, subtraction, multiplication, division and performs the desired functions on each memory.

NO LANGUAGE TO LEARN

Truly this programmable calculator is a powerful personal scientific and mathematical computing resource. And you don't need to know programming to make it work for you. There is no special language to learn. The entry system is so easy and flexible to use that you can apply it quickly to your own personal problem-solving techniques and style.

Special Functions of the PR-100: To allow you greater flexibility in programming, there are 3 special functions: 1. HALT - The program will halt and allow the user to read or enter data. 2. GOTO - Allows branching from one section of a program to another. 3. SKIP - Allows conditional flow of a program on an intermediate result; that is - the program goes one way if an answer is negative and another way is positive.

Loading, Editing and Modifying Programs: You can single step through a program to check it out, backstep through a program, easily read entered steps and modify a single step of a program.

Now personal programming is here. A step-function increase in capability over sophisticated slide-rule calculators. Capability you won't fully discover until you own a PR-100 yourself. Fill out the coupon below or call our toll free number for your two week trial. The Commodore PR-100 is powered by rechargeable NiCad batteries and is furnished with an AC adapter/charger, leatherette carrying case and full instruction booklet. One year manufacturer's warranty. Dimensions: 3 1/4" x 6 1/2" x 1 1/8" Weight: 4 oz.

Compute With It For Two Weeks - No Obligation

Please send _____ Commodore PR-100 Calculator(s) at the introductory price of only \$59.95 (plus \$3.95 shipping and insurance) each. If not completely satisfied, I can return it within two weeks for a prompt refund.

Instead, I/we would like to take advantage of your quantity price offering of \$54.95 (plus \$3.95 shipping and insurance) each. OFFER GOOD ONLY ON QUANTITY ORDERS OF 6 UNITS OR MORE! You can save \$30.00!

Check or M.O. Enclosed (Ill. residents add 5% sales tax)
 Please charge my credit card checked below:
 American Express BankAmericard Carte Blanche
 Others Club Master Charge

Credit Card # _____
 Master Charge Bank # _____ Exp. Date _____
 Name _____
 Address _____
 City _____ State _____ Zip _____
 Signature _____ PE 10/77

Send Coupon To:
Contemporary Marketing, Inc.
790 Maple Lane, Bensenville, Ill. 60106
Call Toll Free: 800-323-2272, Ill. call: 312-595-0461

repeated on the same chart paper. The frequency response of the reference microphone is known (and is flat within better than 1 dB to beyond 10,000 Hz), so the difference between the two curves is taken as the response of the test mike.

The curve we obtained in this manner from the Shure Model 516EQ microphone (with all four filters OUT) has less high-frequency emphasis than was shown on Shure's "typical response" curves, but it was otherwise fairly similar. It was flat within ± 3 dB from 110 to 7500 Hz, dropped about 9 dB in the 9000-to-11,000-Hz range, and fell more rapidly at higher frequencies. The low-frequency response followed Shure's curve closely, rolling off below 200 Hz to -13 dB in the 50-to-60-Hz range.


We repeated the response measurements using the filters, one at a time, and plotted the effect of each filter on the same coordinates used for the equalized response curve. Each filter had the specified effect, although the attenuation was usually closer to 8 or 10 dB than the nominal 6 dB, which will vary with load impedance. (We used a high-impedance load in our tests).

User Comment. The effect of the filters on the sound of the microphone can best be judged by making a recording (of one's own voice, for example), using all possible combinations of switch settings. We would suggest that one keep a small screwdriver or a pencil handy for operating the equalizer switches.

It was soon apparent that the microphone can be adjusted to sound like almost anything from a nasal constricted "telephone" sound to an excellent wide-range response very close to that of our calibrated capacitor microphone. We did not use the microphone in the field for live recordings, but our experience with it suggests that the built-in equalizers should be able to cope with many of the acoustic problems one might encounter.

This is one of the least expensive microphones we have seen whose sound quality is reasonably well matched to that of a modern cassette deck. Other microphones may come closer to utilizing the full capability of such a recorder, but they will probably cost more than the Model 516EQ and will not have its equalizing ability. Although we could not make meaningful measurements of the sensitivity of the Model 516EQ, its output was compatible with the requirements of several good cassette decks with which it was used.

CIRCLE NO. 103 ON FREE INFORMATION CARD

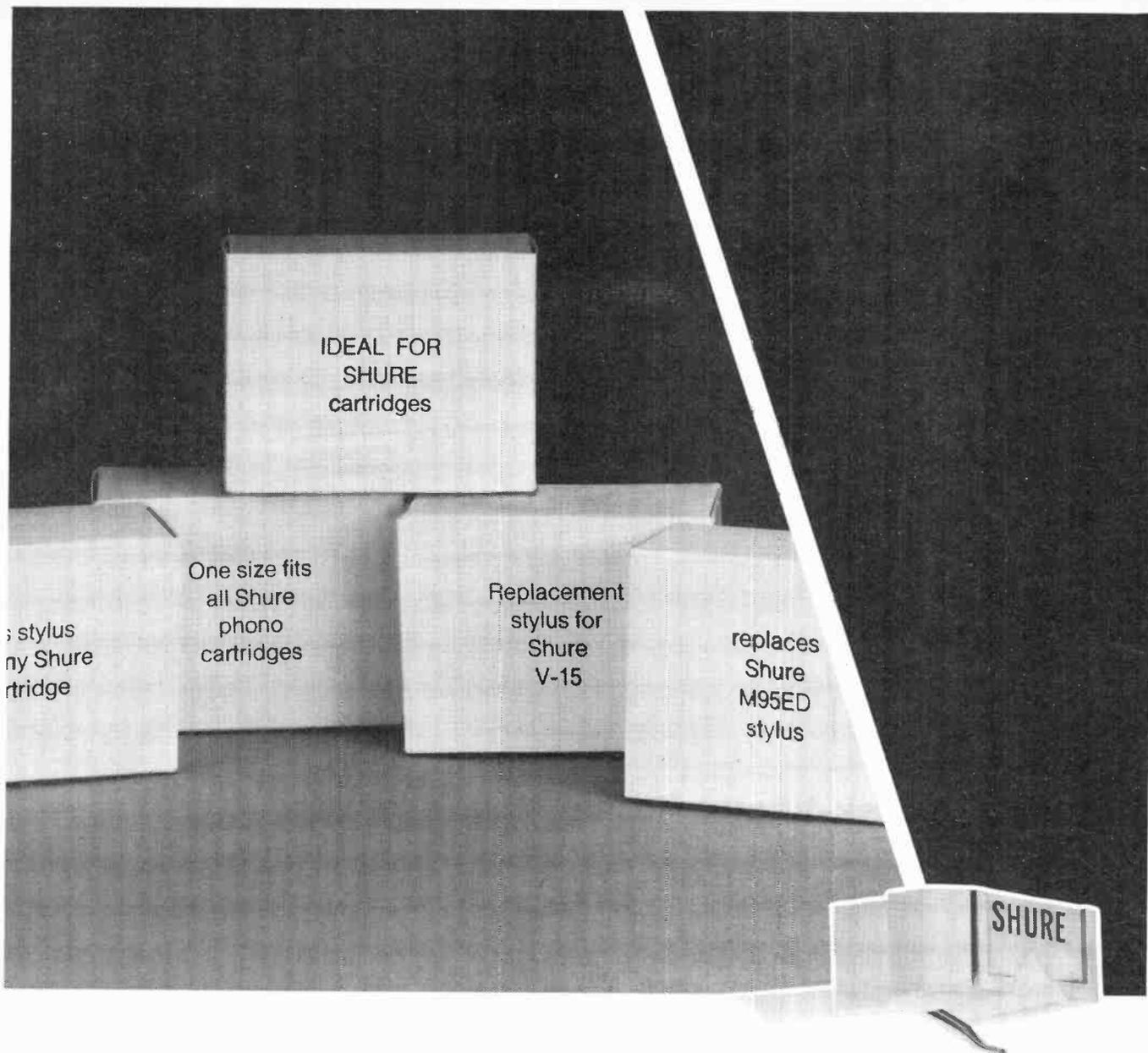

Needle in the hi-fi haystack.

Even we were astounded at how difficult it is to find an adequate other-brand replacement stylus for a Shure cartridge. We recently purchased 241 random styli that were not manufactured by Shure, but were being sold as replacements for our cartridges. Only ONE of these 241 styli could pass the same basic production line performance tests that ALL genuine Shure styli must pass. But don't

simply accept what we say here. Send for the documented test results we've compiled for you in data booklet #AL548. Insist on a genuine Shure stylus so that your cartridge will retain its original performance capability—and at the same time protect your records.

Shure Brothers Inc.
222 Hartrey Ave.,
Evanston, IL 60204
In Canada:
A. C. Simmonds & Sons Limited

TECHNICORNER

The criteria for these tests involved the eight standard production line inspections used for all Shure styli: Visual and mechanical inspection, tip configuration, trackability, vertical drift, 1,000 Hz output level measurement, channel separation at 1,000 Hz, channel separation at 10,000 Hz, and frequency response.

Only genuine Shure styli have the name SHURE on the stylus grip and the words "This Stereo Dynetic[®] stylus is precision manufactured by Shure Brothers Inc." on the box.




Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

OCTOBER 1977

CIRCLE NO 52 ON FREE INFORMATION CARD

41

NOW, DISKS TOO!

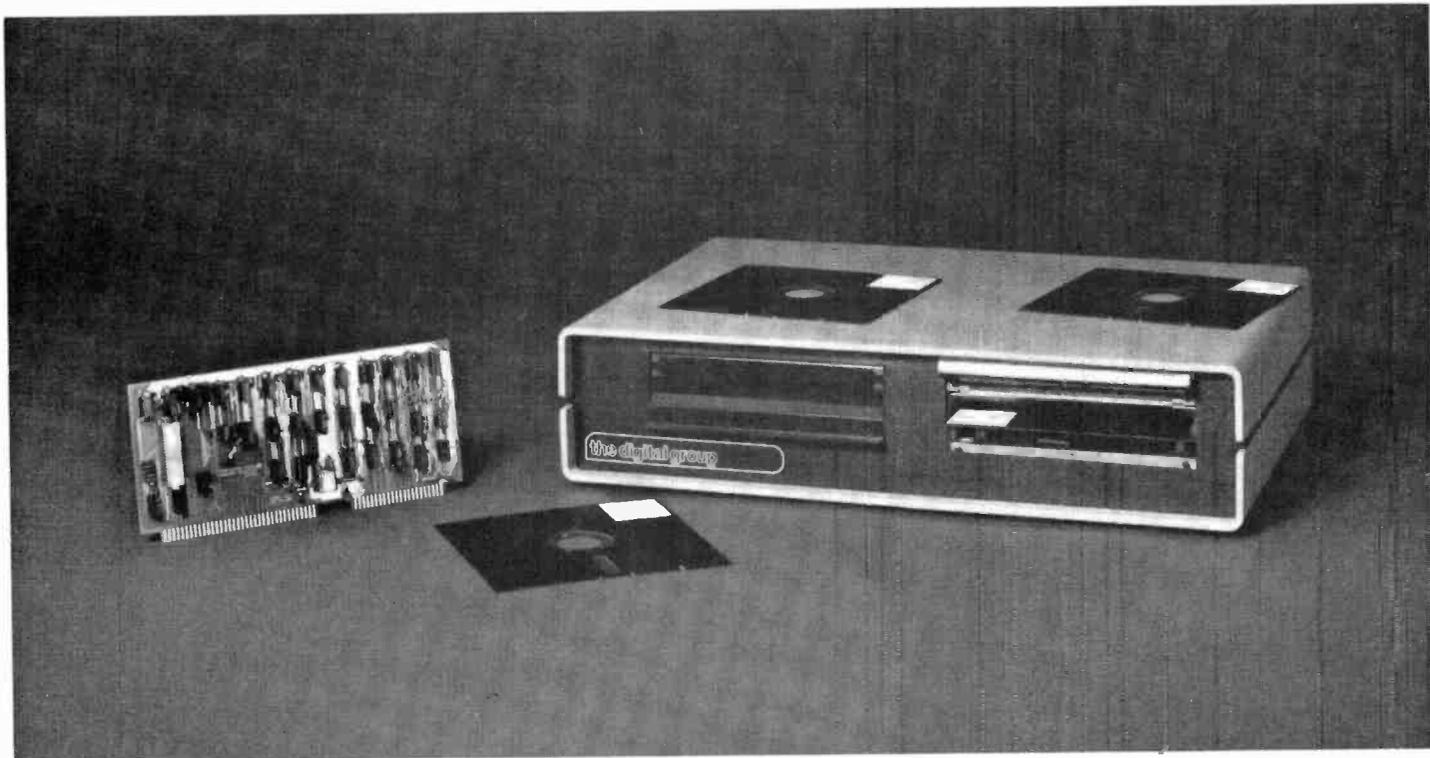

(And they're **Disk-tinctly** Digital Group.)

With the addition of our all-new Disk Subsystem, the Digital Group becomes the only manufacturer of microprocessors to offer you a real choice. Tape or disk. Or both. Whatever you want.

We spent a lot of time designing and testing our new Disk Subsystem, and it shows in the result. The Subsystem is highly flexible. . . gives you direct access to data. . . and completes your Digital Group System.

Here's what the Disk Subsystem consists of:

Disk Interface Card--provides the electrical interface between the disk drives and the computer.

Disk Power Supply--provides all power required for up to 2 drives.

Disk Cabinet and Cables--cabinets provide housing for 1 to 2 drives plus the power supply; assembled cabling is provided for connection between all system components.

Disk Drives--the Digital Group Disk Subsystem supports standard 8" floppy disk drives from a number of manufacturers. Drives can be mixed, and in addition, mini-floppy drives are available for the function of a disk at minimum cost.

Documentation and Software--the Digital Group's standard documentation includes construction guides, maintenance manual, theory of operation and other useful information to help you get the fullest value from your new Disk Subsystem. And there's also software to provide initial support.

The price? Low. It's become a tradition with the Digital Group to offer you high-quality, state-of-the-art equipment at the lowest possible prices. Our new Disk Subsystem is no exception.

For only \$745, you can get a standard 8" floppy drive and an interface card. A complete single-drive Disk Subsystem with interface, power supply, cabinet, and cables is as low as \$995.




Now the Digital Group system is really complete. If you don't own it all yet, take another longing look. In addition to our CPU, keyboard and video monitor, you can add an impact printer and the cassette storage system. All in our beautifully coordinated custom cabinets. All unmistakably Digital Group.

The Digital Group now has disks. And a lot more. Why not find out about all of our exciting products? Simply call or write today for direct information. From the Digital Group.

the digital group_{Jr.}

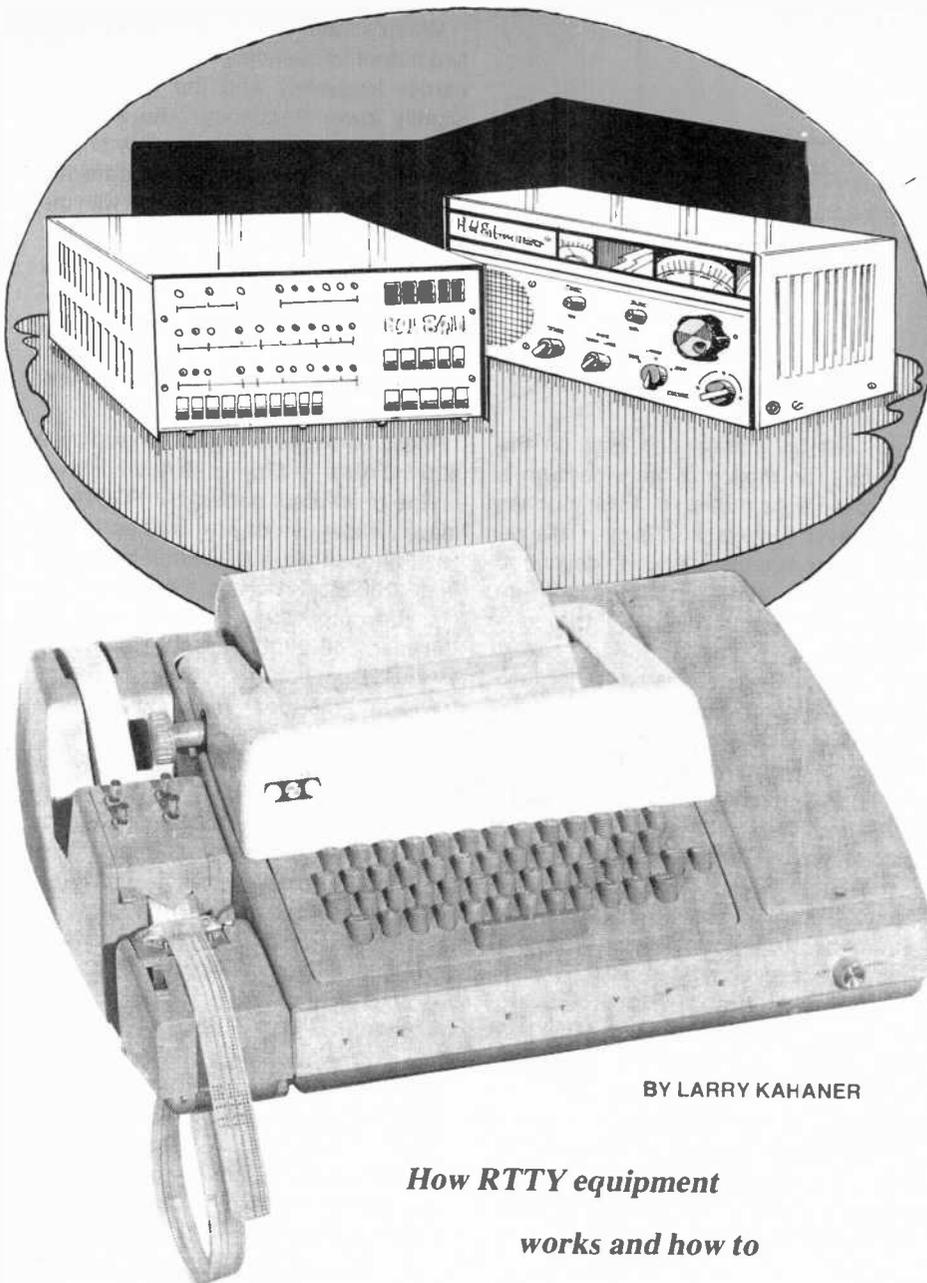box 6528 denver, colorado 80206 (303) 777-7133



BY LARRY KAHANER

How RTTY equipment works and how to get started using it.

TELETYPEWRITER FUNDAMENTALS FOR HAMS, SWL'ers & COMPUTER HOBBYISTS

HAVE you ever wondered about those strange "deedle-deedle" signals on the shortwave bands? They are actually radioteletype (RTTY) transmissions. You can receive them using your communication receiver and readily available teletypewriter equipment. In this article, we will cover the basics of radioteletype and detail how to set up an RTTY listening post at home.

The Teletype Code. All teletypewriters, whether they communicate by radio or land-line links, "talk" to each other in a language called Baudot, or five-level code. Each character (letter, numeral, punctuation mark) in the Baudot code is uniquely defined by a sequence of five time slots, or *elements*, each of which contains a *mark* or a *space*. For example, the letter A is "mark-mark-space-space-space." When the teletypewriter is operating at 60 wpm (words per minute), each mark or space is exactly 22 milliseconds (ms) long.

A sixth slot is added to the basic five-level code to act as a "flag" that indicates the end of a character. To make this stop flag stand out from the others, its interval is 31 ms instead of 22 ms. Still another time slot is placed at the beginning of each character to give the teletypewriter time to prepare itself for a new character. This is the "start" slot. The 31-ms stop slot contains a mark, while the 22-ms start slot contains a space. A complete character, therefore, consists of seven slots, six 22-ms intervals and one 31-ms interval for a total of 163 ms (see Fig. 1).

The Equipment. A complete station for transmitting and receiving radioteletype signals is shown in Fig. 2. The transmitter and receiver are of conventional "communication" design. The teletypewriter is a combination keyboard/printer. On transmit, the keyboard drives a keyer that, in turn, modulates the transmitter. On receive, signals are coupled from the communication receiver

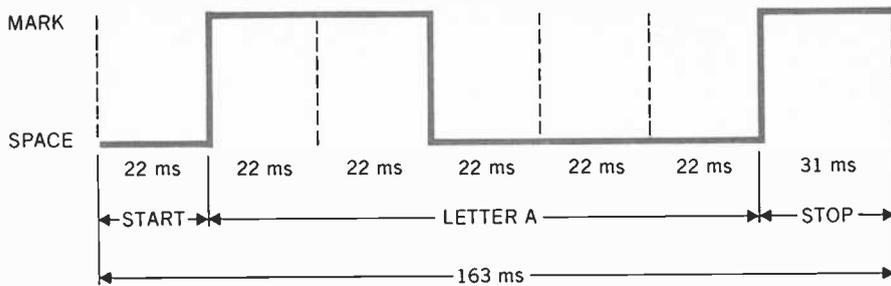


Fig. 1. Waveform showing the pulse sequences that make up the letter "A".

er to the demodulator or terminal unit (TU), which drives the printer.

Now let us examine each component in the system in detail:

Keyboard. A mechanical teletypewriter keyboard resembles the keyboard on a conventional typewriter, but its operation is quite different. When a key is operated, it selects mechanical levers that produce mark and space pulses that correspond to the key's character. Also, there are no lower-case letters—all are capitals. To type punctuation marks, the SHIFT key is pressed first, followed by operation of a key that corresponds to the character you wish to type.

The diagram in Fig. 3 illustrates how one keyboard might work. Each key has a notched lever, which when pressed down can touch five "fingers" that will be either depressed or not, depending upon the notch positions of the lever.

After the key is pressed and the mark and space levers have moved accordingly, a wiper arm sweeps across the mark levers but cannot touch the space levers. An electrical connection is made between the wiper arm and mark fin-

gers, but no current can flow on the spaces. The motion of the wiper arm is controlled by a motor so that it touches each lever for exactly 22 ms. This results in the five-element code described above. Start and stop commands are generated automatically by the keyboard.

The above process is typical of keyboard operation, but it is not absolute. There are variations in keyboard design from one teletypewriter to another. The latest generation of teletypewriters, however, uses electronic instead of electromechanical means for generating the Baudot code. Digital matrix keyboards with clock-controlled digital IC's that generate precisely timed code elements have recently become common.

Transmitter Keying. Dc pulses produced by the keyboard drive a keyer that, in turn, modulates the transmitter. Most often used is frequency shift keying (FSK), a form of frequency modulation so that there is some discrimination against noise.

When a transmitter is FSK modulated, two output frequencies result, one at the carrier frequency and the other at a slightly lower frequency. The simplest way to accomplish the frequency shift is to add more capacitance to the transmitter's vfo tank circuit or in parallel with the oscillating crystal. In practice, the dc pulses from the keyboard control a relay or solid-state switch that rapidly connects and disconnects the additional capacitor. Hence, the transmitted frequency varies in step with a character's mark and space code.

Most commercial systems employ a 425-Hz shift. A 170-Hz shift is common on the hf amateur bands, but FCC regulations allow use of any shift up to 900 Hz. For example, if the carrier frequency is 15.000000 MHz and the shift is 425 Hz, the output frequency will alternate between 15.000000 and 14.999575 MHz. By convention, the space is the lower and the mark the higher frequency. In this example, marks appear at 15.000000 MHz and spaces appear at 14.999575 MHz.

Receiving FSK. A bfo (beat frequency oscillator) is commonly used for CW reception. The bfo generates a signal that beats against the incoming CW signal to produce an audible tone. If the frequency of the bfo's output is variable, the frequency of the audible tone can be changed. In RTTY communication, signals are received as in ordinary CW, but the bfo is tuned to provide 1275- and 1700-Hz tones, which are 425 Hz apart.

The reason for using 1275- and 1700-Hz tones is that a terminal can demodulate only one pair of frequencies at a time. This pair was chosen by TU

The new breed of teleprinter equipment: Morse and RTTY keyboard (left), demodulator (right bottom), video display unit (right top) and video monitor (top center). Courtesy HAL Corporation.



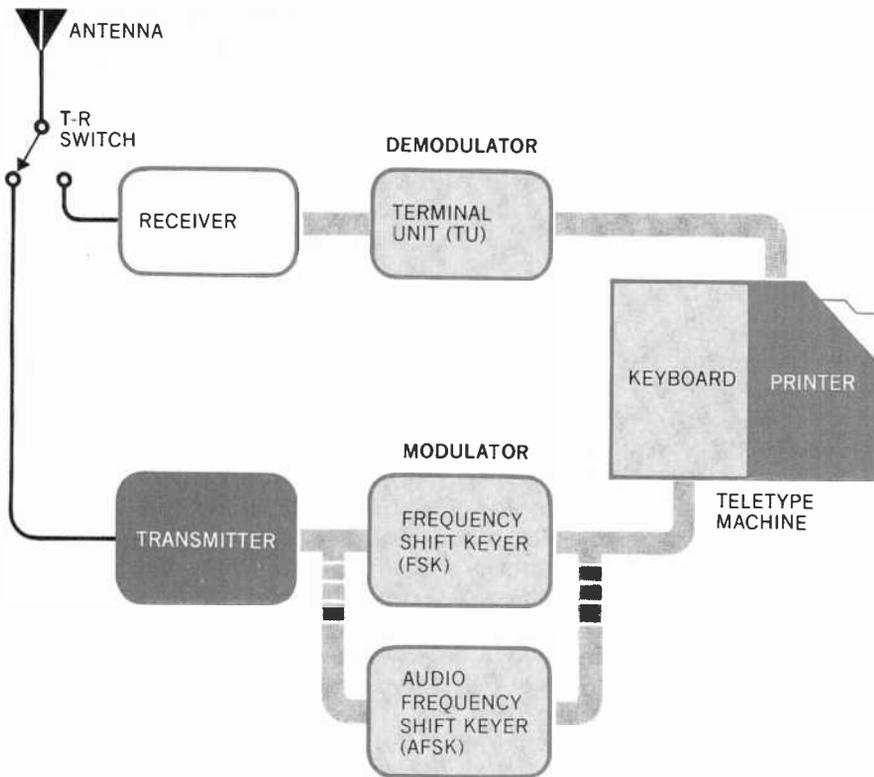


Fig. 2. Block diagram of the equipment in a complete RTTY station.

manufacturers for demodulation of a 425-Hz shift. (However, you can adjust the bfo or the main tuning knob if the bfo is fixed to produce any pair of tones your TU can demodulate.) Other shifts and tone pairs used in RTTY communication are listed in Table I.

An RTTY terminal unit looks and acts like an FM receiver, but it accepts audio signals. Called an *audio TU*, its block diagram is shown in Fig. 4. The limiter accepts the audio outputs of the receiver and amplifies and clips them to keep the signal level fairly constant. Mark and space filters remove any extraneous signal content. The two filtered tones are converted into dc pulses by the audio discriminator. Any ripple on the dc pulses is smoothed by the low-pass filter. The dc pulses are then applied to the keyer, which uses them to generate commands for the printer's magnets.

AFSK. Another method of keying is audio-frequency shift keying, or AFSK. It produces a result similar to FSK but is derived in a different manner. Two audio tones, separated by the frequency shift, modulate an AM or an SBB transmitter. The low-distortion sine-wave tones are applied to the transmitter's microphone input.

If the output from the transmitter is conventional AM, no bfo is required in the receiver. The detected envelope is coupled to the TU from the receiver's

audio output. If, on the other hand, SSB equipment is used, the receiver must be carefully tuned for the correct output frequencies and allowances must be made in the transmitter for a 100% duty cycle. As in FSK, the two tones commonly used are 1275 and 1700 Hz.

The Printer. Although printer design varies from one machine to another, the following description is representative of printer operation. A simplified printer is shown in Fig. 5. The selector magnet is energized by each mark pulse. This closes the relay that corresponds to a moving cam connected to each mark and space lever. At the proper time, the cam either pulls down or does not affect the lever. Each lever is connected to a bar with many notches, which are placed at different intervals along the bar.

In the illustration shown in Fig. 5, the first, third, and fifth levers are pulled by the cam. The other levers remain in their original positions. After a character is completed (all five pulses received), one set of notches lines up directly under the appropriate character's striker. (Strikers are in a row, as in a regular typewriter.) When the stop pulse is received, a hammer hits all strikers, but only the one with the lined-up notches moves and imprints the paper. After the strike occurs, the bars and their notches return to their original positions.

The new teletypewriter printers literally do not print at all. They are actually special types of TV receivers that process the dc pulses and apply control signals to form letters on-screen. The advantages of screen printers are that they are quiet, clean, and have no moving

TABLE I—STANDARD SHIFTS AND TONE PAIRS (Hz)

| | | | |
|---------------------------|------|------|------|
| Shift | 170 | 425 | 850 |
| Space | 1275 | 1275 | 1275 |
| Mark | 1445 | 1700 | 2125 |
| OTHER PAIRS IN USE | | | |
| Space | 2125 | 2125 | 2125 |
| Mark | 2295 | 2550 | 2975 |

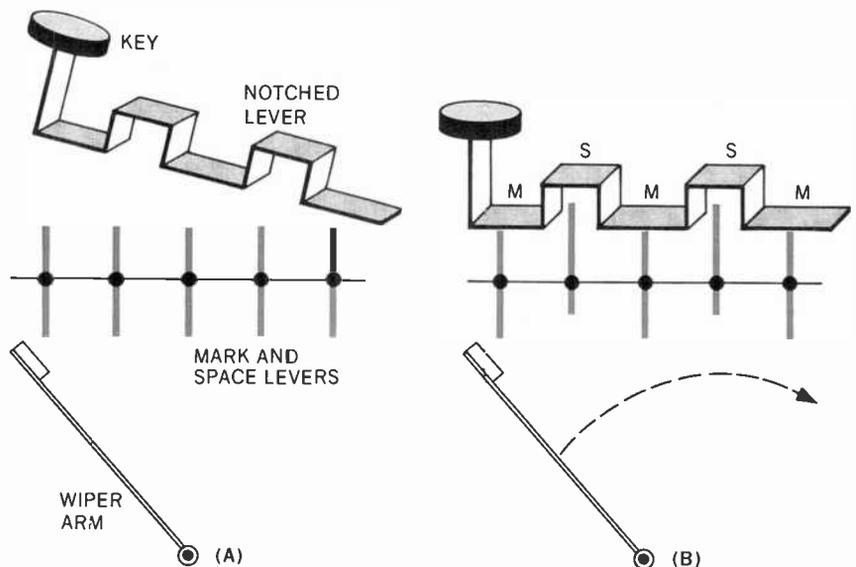


Fig. 3. Simplified diagram shows how key depresses levers at (B).

parts to wear out. Some screen printers have memories that allow storage and playback of messages. These "glass teletypewriters" cannot produce "hard" copy on paper; for this, you must use a regular teletypewriter printer.

Some teletypewriters have perforators that punch holes in 1" (25.4-mm) wide paper tape. The holes in the tape correspond to character codes. Tapes can be made from either an incoming signal or from a message typed on the machine's keyboard. To play back the message, you feed the tape through a tape reader called a transmitter-distributor (TD). The teletypewriter then prints the message. You can also transmit taped messages over the air.

The most commonly used speed is 60 wpm, but stations also transmit at 66, 75, and 100 wpm. To receive different speeds, no changes need be made in the terminal unit, but the printer must be altered. Printers rely on gears to set the speed. Changing gears allows the machine to print at different speeds. TV teletypewriters usually accommodate many speeds with just the turn of a switch.

The number of words per minute tells you only part of the printer's story because each speed requires different slot lengths. A slot for 60-wpm copy is not the same length as one at 100 wpm. So, another word—"baud"—was invented to take slot length into account. The baud is a measure of the rate at which data is sent and is defined as a rate of one pulse (of the shortest duration used in the system) per second. The baud rate is calculated by finding the reciprocal of the shortest slot length. For 60 wpm, the shortest length is 22 ms or 0.022 s; the baud rate is $1/0.022 = 45.5$ baud. Other baud rates are detailed in Table II.

When printer gears are changed, the baud rate is altered. The printer's magnets sweep the levers in step with the length of each pulse and, hence, the baud rate.

Equipment Considerations. Any good communication receiver can be used for receiving RTTY. Due to the small, critical frequency shift, however, stability is essential. If your receiver's CW filter bandwidth is 400 Hz, it will probably be suitable for shifts up to 425 Hz. It might not work well with wider shifts, such as 850 Hz, especially if signals are weak. Of course, the SSB filter can be used if the received shift is too great for the CW filter.

Your choice of TU's hinges on your

TABLE II—RATES AND SLOTS

| Bauds | Words/Min. | Millisec./Pulse |
|-------|------------|-----------------|
| 45 | 60 | 22.0 |
| 50 | 66 | 20.0 |
| 57 | 75 | 17.57 |
| 74 | 100 | 13.47 |
| 100 | 132 | 10.0 |

needs and your budget. (Sources of teletypewriter gear are listed in Table III.) One inexpensive approach is to build your own TU. A simple two-chip TU can be built for less than \$20. Alternatively, you might decide that a more sophisticated demodulator with built-in oscilloscope tuning indicator and sharp filtering and a choice of shifts fills your needs. Plans for many different TU's can be found in published literature.

If you prefer not to build your own TU, you can buy factory assembled units. Some features to look for here are a choice of shifts, reverse/normal switching, filtering, tuning indicator, baud-rate selection, adequate loop current for the printer magnets, and selectivity.

Most RTTY enthusiasts buy "surplus" printer/keyboard combinations. After these machines are used commercially, surplus dealers buy, recondition, and resell them. Old teletypewriters are rugged and, if properly reconditioned, should last a long time. Prices range from \$50 to \$250, depending on model, age, and

condition. New machines are quite expensive and can cost as much as \$2000.

You might wish to buy a video monitor instead of a mechanical printer. (Of course, you can modify an old TV receiver for use as a monitor.) A video monitor requires the use of a visual display unit (VDU), which converts the dc pulses from a TU into a form suitable for onscreen display. VDU's cost \$350 to \$600. You can however, build your own VDU from plans that have been published in the literature.

If you are a computer hobbyist, consider using your existing monitor and VDU. Be aware, of course, that computers use ASCII, an eight-level computer code, rather than the five-level Baudot code used in RTTY. Baudot signals must be converted to ASCII before reaching the VDU. Baudot-to-ASCII converters are commercially available, or you can make one yourself.

Making Connections. If you buy a teletypewriter, be sure you get the manual, because it contains the machine's wiring diagram and color code. Each machine is wired differently. Bear in mind that, in spite of the jungle of wires inside the teletypewriter, only six wires are necessary for RTTY operation. Two are for the motor, two for the printer magnets, and two for the keyboard. Once you locate the appropriate wires, the hookup necessary to put the tele-

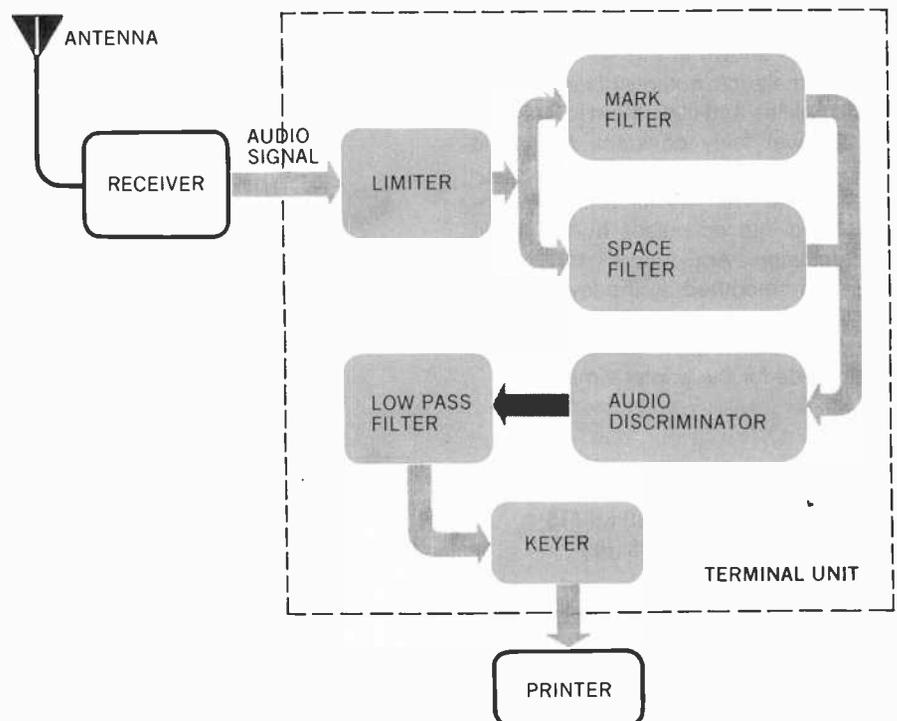


Fig. 4. Block diagram of typical audio terminal unit.

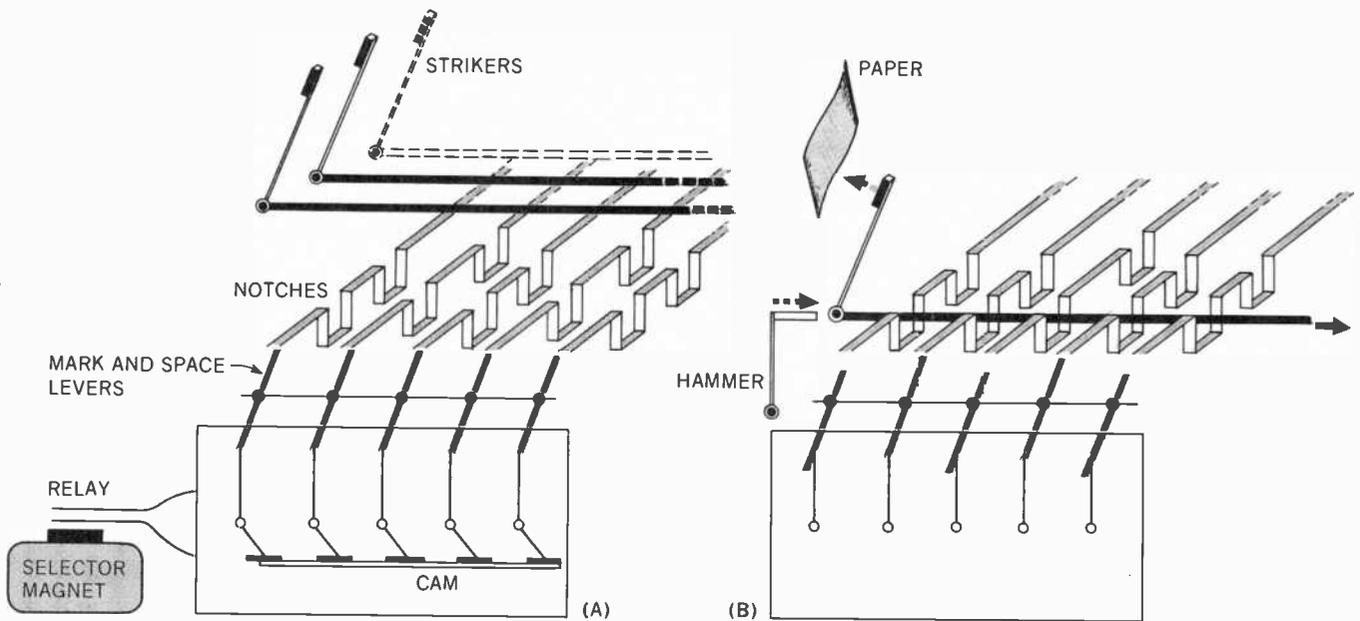


Fig. 5. Typical printer action. At (A), before letter is sent, notches are in random order. At (B), after letter is sent, one set of notches lines up under the correct striker.

typewriter in service is easily accomplished.

Local copy (typing on the keyboard and obtaining a print-out but no transmission) can be accomplished with the circuit shown in Fig. 6. Many teletypewriters employ two selector magnets (check your manual on this) that are connected either in series or in parallel with each other. Use an ohmmeter to check the resistance of the magnet circuit. Each magnet has approximately 100 ohms of dc resistance; so, an ohmmeter reading of 200 ohms indicates a series connection, while a 50-

ohm reading indicates a parallel hookup. Because each magnet requires about 30 mA of current, parallel wiring calls for 60 mA in the loop circuit, while series wiring requires 30 mA in the loop. Adjust the series resistor for the proper magnet current.

Turn on the motor by applying 117 volts ac to its winding. With proper magnet current flowing and the motor running, you should be able to type on the keyboard and obtain a printed hardcopy message. If you have trouble obtaining local copy, check your wiring. Garbled or no printing at all could also be caused by poor adjustment of the "range selector."

Sometimes, distortion occurs in RTTY transmissions. Pulses often become longer or shorter because of propagation conditions. To counteract this, machines are designed to respond to only a small section in the middle of the pulse width. The exact location of this "window" is controlled by the range selector,

a movable arm that has graduations from 0 to 120.

To test the range selector, type the letters RY. These letters, when alternately typed, produce a mark pulse in each of the five slots. Move the range selector toward 0. As you approach 0, the teletypewriter will begin to lose intelligibility and print random characters. Note the setting at which this occurs. Then increase the setting until the machine's printer "locks up," again noting the setting. Set the range selector midway between these two points.

The terminal unit should be connected as shown in Fig. 7. TU's vary in design, but some share basic characteristics. For example, they all have a method for adjusting the shift frequency, which is usually a variable inductance. And they all have controls for adjusting printer current, usually via a potentiometer. Both controls must be properly adjusted for correct TU operation.

TABLE III—SOURCES OF RTTY EQUIPMENT

Alltronics-Howard

Box 19
Boston, MA 02101

Atlantic Surplus Sales

3730 Nautilus Ave.
Brooklyn, NY 11224

Dovetron

627 Fremont Ave.
S. Pasadena, CA 91030

Fair Radio Sales

Box 1105
Lima, OH 45802

Teletype Corp.

5555 Touby Ave.
Skokie, IL 60076

Typetronics

Box 8873
Fort Lauderdale, FL 33310

Nat Stinette Electronics

890 Virginia Ave.
Tavares, FL 32778

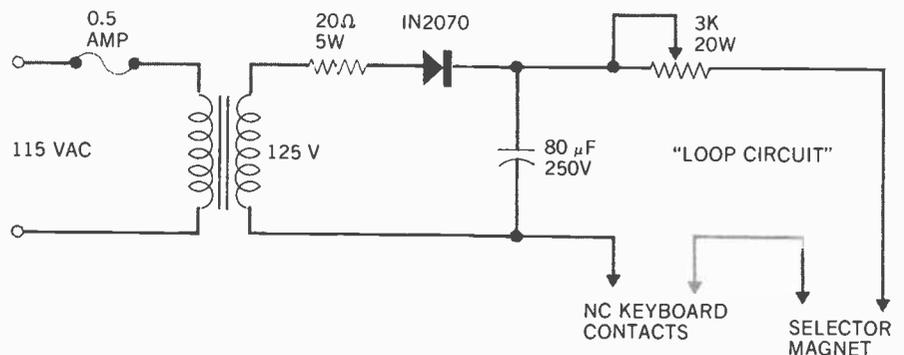


Fig. 6. Local copy can be obtained using the loop circuit shown here.

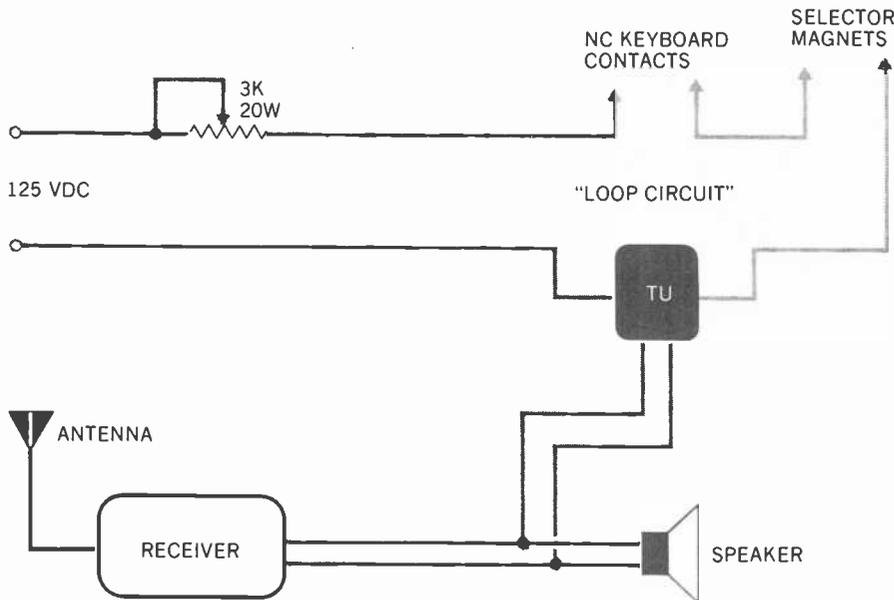


Fig. 7. How to set up an RTTY receiving station with a terminal unit.

Connect the TU to the receiver's audio output, keeping the speaker online so that you can hear the incoming signals. Find an RTTY station and tune it in carefully, using the TU's tuning indicator for accuracy. Because tuning in RTTY stations is tricky, you may get garbled copy until you become accustomed to tuning. Some operators tune until legible copy appears, while others can tune in the proper tones by ear. Either method is fine, but do not expect to be able to emulate this right away. It takes lots of practice.

If you get garbled copy, it may be due to one of several causes. The most common is that the station is transmitting at a different shift or speed from your settings. Again, experienced operators can "hear" different speeds and shifts. You will, too, after a while.

A station might be transmitting in reverse shift, with the space high and the mark low. Switching sidebands on your

receiver or shifting the bfo output to the other side of zero beat will compensate for this. Many TU's have a reverse/normal switch that accomplishes the same thing. Military stations often transmit secret cipher messages that look like gibberish. If you are not aware of this practice, you can go crazy trying to copy them.

Listening. At least 200 stations, excluding radio amateurs and the military, transmit RTTY (see Table IV). Most use shifts of 425 to 850 Hz and speeds of 60 to 100 wpm. By tuning to them, you can receive news reports, weather forecasts, and commercial radiograms, as well as conversations between radio amateurs and military traffic. However, you should read Section 605 of the Communications Act of 1934 that concerns secrecy of communications.

In brief, the Act prohibits a listener from divulging to a third party or using

TABLE IV—RTTY STATIONS

| Call | Frequency (MHz) | Location | Service |
|-------|-----------------|----------|----------------------------------|
| 9PX29 | 6.910 | Barbados | Reuters |
| WFK80 | 10.7535 | New York | Reuters |
| RVW57 | 12.315 | Moscow | Tass (some English news) |
| WER73 | 13.480 | New York | UPI |
| WER24 | 14.770 | New York | UPI |
| WEY45 | 15.914 | New York | AP (some English news) |
| SOP29 | 15.989 | Poland | Polish Press (some English news) |

Note: Most ham operators use a 170-Hz shift at 60 wpm near 3.620, 7.040, and 14.090 MHz.

TABLE V—REFERENCE LIST

Confidential Frequency List
By Robert B. Grove
Pub. by Gilfer Assoc.
Box 239
Park Ridge, NJ 07656
(Extensive lists of stations transmitting RTTY. Updated periodically.)

The New RTTY Handbook
73 Publishers
Peterborough, NH 03458
(Good for beginners, slanted for hams.)

RTTY News
Canadian Amateur Radio Teletype Group
Gwen Burnett
85 Fifeshire Rd.
Willowdale, Ont., Can. M2L 2G9
(Technical information and amateur operating news.)

Teleprinter Handbook
By D. L. Goacher & J. G. Denney
Radio Society of Great Britain
35 Doughty St.
London, WC1N 2AE, England
(Thorough treatment of RTTY. Large section on machine repair and maintenance.)

RTTY Journal
P. O. Box 837
Royal Oak, MI 48068
(Published 10 times per year. Slanted for the ham, but has classified ads, technical pieces, and a DX-RTTY column. Publishers of *The Beginner's RTTY Handbook*.)

The Radio Amateur's Handbook
and
Specialized Communications Techniques for the Radio Amateur
American Radio Relay League
225 Main St.
Newington, CT 06111

for his own or a third party's benefit the contents of any interstate or foreign communication by radio or wire. Note, however, that this section does not apply to the contents of any radio communication broadcast or transmission by radio amateurs or others for use of the public or relating to ships in distress.

Getting Help. Besides the books listed in Table V, there are other sources of information and help to which you can turn. Although relatively few shortwave listeners use RTTY, many hams transmit and receive radioteletype messages. Most of them will be glad to show you the "tricks of the trade" they use to obtain perfect copy. Also, many computer hobbyists use teletypewriters to get hard copy or punch tape. ◇

Hex-to-ASCII Converter for your TVT-6

Simple module produces op-code display for entire computer.

BY DON LANCASTER

THE LOW-COST "Hex-to-ASCII Converter" described here allows you to simultaneously display the contents of every register, stack location,


and memory slot in your microcomputer. The converter fits easily between the TVT-6 (July 1977) or most any other TVT and the μ C with which it is working.

In operation, the video monitor used in the system automatically converts and displays the hex op codes for the ASCII character set. This allows your TVT to act as a super "front panel" that permits you to check as many memory locations as there are in your system. This includes all registers, accumulator, stacks, RAM and ROM programs, I/O, or anything else connected to the system. Properly used, the converter is also an excellent debugging tool.

The complete hex-to-ASCII converter is built on a single compact printed circuit board. The circuit itself consists of three low-cost IC's and only five other parts.

About the Circuit. As shown in Fig. 1, the eight input lines from the display memory that normally drive the TVT character generator are intercepted and split into upper- and lower-case charac-

(Continued on page 51)

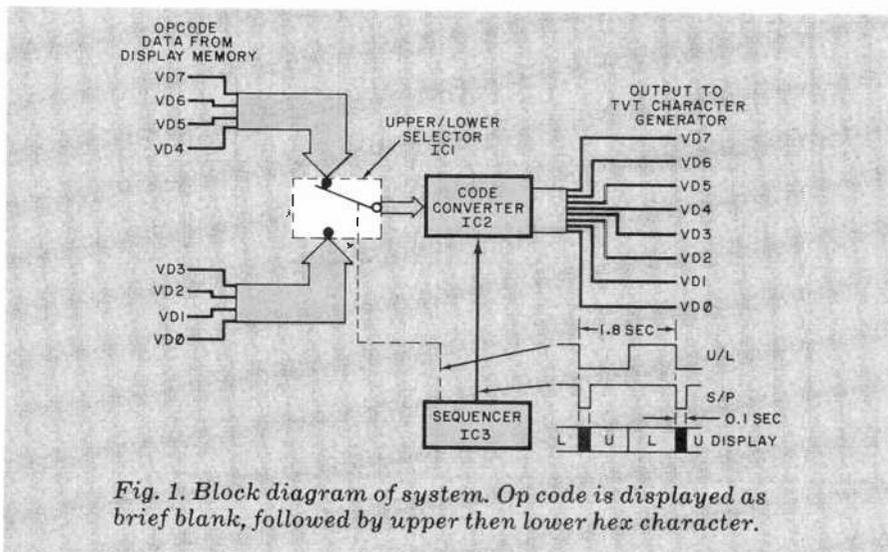

| WORD | NOTES | 8/7 | 7/6 | 6/5 | 5/4 | 4/3 | 3/2 | 2/1 | 1/0 |
|------|-------|-----|-----|-----|-----|-----|-----|-----|-----|
| 0 | Blank | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 2 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 3 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 4 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 5 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 6 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 7 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 8 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 9 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 10 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 11 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 12 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 13 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 14 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 15 | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 16 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 17 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 18 | 2 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 19 | 3 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 20 | 4 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 21 | 5 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 22 | 6 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 23 | 7 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 24 | 8 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 25 | 9 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 26 | A | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 27 | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 28 | C | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 29 | D | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 30 | E | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 31 | F | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

0-WHITE; 1-BLACK

Fig. 3. Truth table for PROM IC2.

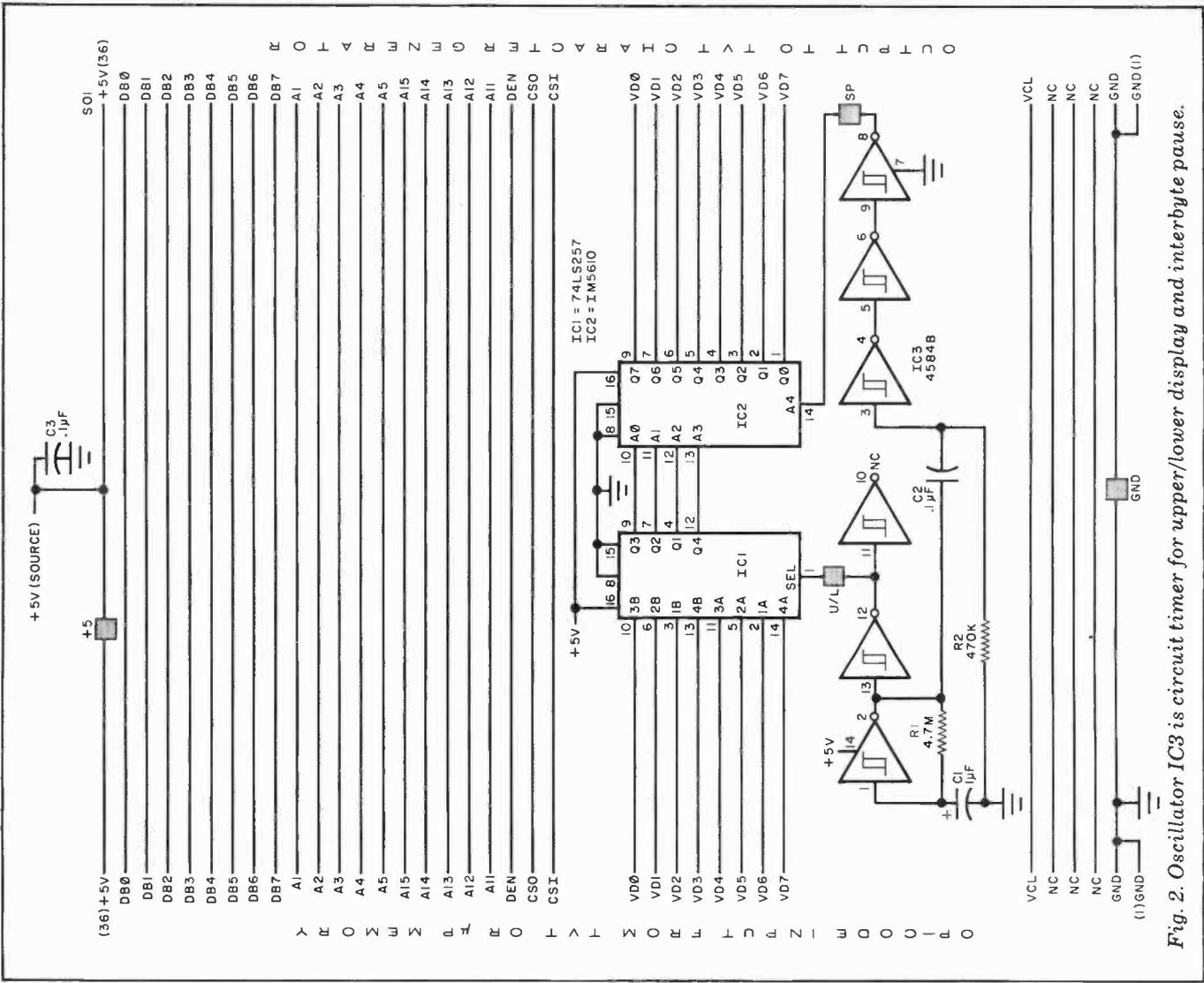


Fig. 2. Oscillator IC3 is circuit timer for upper/lower display and interbyte pause.

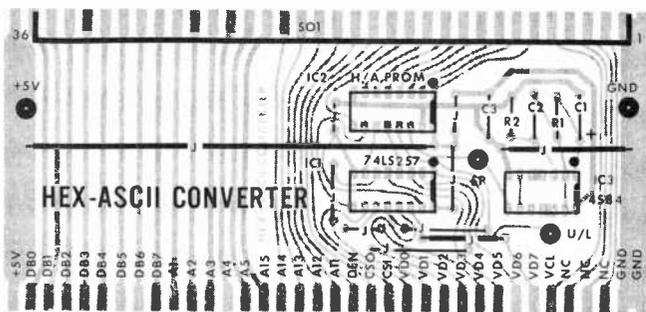


Fig. 4. Actual-size etching and drilling guide (right) and component layout (above) for the pc board. The board is connected between the TVT-6 and the KIM-1 microcomputer.

PARTS LIST

- C1—1- μ F, low-leakage tantalum electrolytic capacitor
- C2, C3—0.1- μ F Mylar capacitor
- IC1—74LS257 quad 1-of-2 data selector
- IC2—IM5610 or similar 32X8 bipolar tristate PROM (programmed in accordance with Fig. 3)
- IC3—4584B CMOS hex Schmitt trigger
- R1—4.7-megohm, 1/4-watt resistor
- R2—470,000-ohm, 1/4-watt resistor
- SO1—36-contact, single-entry edge connector with contacts located on 3.96-mm centers
- Misc.—Sockets for IC's (one 14-pin, two 16-pin); press-fit test point terminals; printed circuit board; jumper wire; insulated sleeving; solder; etc.

Note: The following items are available from PAIA Electronics, Box 14359, Oklahoma City, OK 37114: No. HAC-1B etched and drilled pc board for \$4; No. HAC-1P programmed IC2 for \$5; No. HAC-1K complete kit of all parts for \$14.95. All prices postpaid.

(Continued from page 49)

ters of four bits each. These two hex characters are alternately routed to a PROM that converts the hexadecimal input code to the equivalent ASCII output. The resultant display alternately flashes the upper hex character and then the lower hex character, with both appearing on-screen at the same location. Each character is displayed for slightly less than a second. A brief space command is sent to the PROM during the transition from the lower character of one set to the upper character of the following set.

To identify the memory locations, an overlay can be used on the CRT screen of the video monitor, or a china marker can be used to label the operating registers and other important slots with which you are working. If the TVT-6 is being used with the "Cruncher the Bear" mode in the August 1977 issue, it is possible to

simultaneously display the 4096 hex characters that result from the 2048 opcode words simultaneously.

The complete schematic diagram of the converter is shown in Fig. 2 and the coding for the 32 \times 8 code-converter PROM is shown in Fig. 3.

Integrated circuit IC1 (Fig. 2) is used as a four-pole, double-throw data selector that drives IC2, the code converter. The hex CMOS Schmitt trigger (IC3) serves as a symmetrical oscillator that is used for automatically selecting the upper and lower character and to generate the brief blanking pulse that indicates a new character display.

Construction. The converter circuit is best assembled on a printed circuit board. The etching and drilling and components placement guides for the pc board are shown in Fig. 4.

Note on the components placement guide that 10 jumpers are used to interconnect various pads on the board. Only two of these jumpers, indicated by heavy lines, require insulated sleeving to be slipped over them before installation to preclude the possibility of accidental short circuits.

Install and solder into place press-fit terminals at the four test points labelled +5, GND, SP, and U/L. Then install and solder into place the three capacitors, two resistors, and the 36-contact connector. Sockets are recommended for the three IC's. Once the sockets are installed and soldered into place, install the IC's in their respective locations, taking care to properly orient them.

Checkout. To initially check out the converter, connect the TVT-6 to the KIM-1 microcomputer and use the

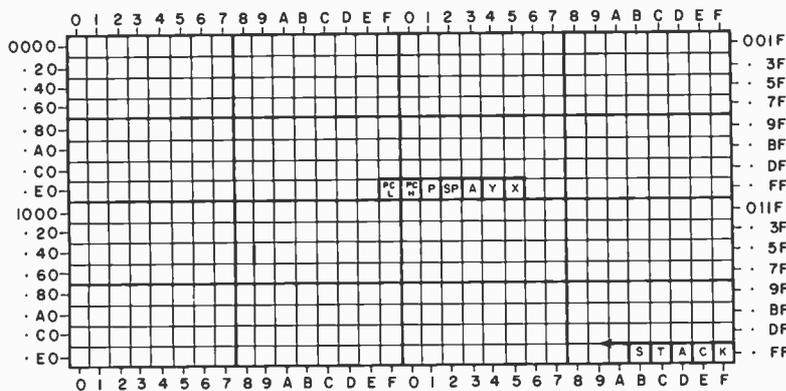


Fig. 5. Overlay mask for the KIM-1. All internal registers are displayed simultaneously with the entire stack.

512-character, page 2 and page 3 display of Table II in the August 1977 TVT-6 article. Make sure that the system is operating properly. Then remove the power and connect the hex-to-ASCII converter between the TVT-6 and μ C. Power up again, reload the program, and run the computer. The original ASCII display should now appear in hexadecimal op code.

Test point U/L should have a 1.8-second square wave, while test point SP should be high for 1.7 seconds and low for 0.1 second. It is possible to "force

feed" control signals into these test points. Connecting test point SP to +5 volts displays the characters; grounding SP blanks the screen. Connecting test point U/L to +5 volts displays the lower four bits, while grounding it displays the upper four bits.

Operation. If you are planning to run Table II from the August 1977 TVT-6 article, the usual display is of pages 02 and 03. This can be converted to a page 00 and 01 display by changing instruction 17AA to 82 and 17d2 to 80.

An overlay that identifies the stack and all important machine registers is shown in Fig. 5. The physical size of the overlay, of course, depends on the size of the CRT used in the monitor. A sharp china marker can alternatively be used as a low-cost, workable substitute for the overlay.

To debug a program, simply use the hex-to-ASCII converter with the KIM-1 operating system in the single-step mode. Each time the operating system returns to the keyboard display mode, all registers have their values reloaded into the proper slots shown in Fig. 5.

Hit AD 17 80, switch to SST OFF, and press GO to view the accumulator, stack pointer, program counter, status register, and the X and Y index registers simultaneously. To return to the keyboard display mode, simply press ST.

The Hex-to-ASCII converter can be used between memory and the character generator of many other TVT systems as long as an 8-bit word is used in the TVT's page memory. You can ignore the "Pass-through" lines on the converter, or you can redefine them in any way you need. The converter's processing delay is about 100 ns, which is fast enough usually to be ignored. \diamond

Rechargeable Batteries for Consumer Products



THE USE of batteries to power electrical and electronic devices is on the rise. As more and more such products are introduced, the consumer is faced with the problem and cost of constant replacement of batteries.

General Electric has introduced an alternative with two new lines of rechargeable batteries and cells. A nickel-cadmium line consists of the most common-size cells and batteries used in such low- and medium-power items as handheld calculators, photoflash camera

units, and portable receivers. A sealed lead-acid (SLA) cell line is designed for devices that require medium-to-high-power, such as alarms, emergency lighting, and computer memory systems.

The new sealed lead-acid cells are designed to be completely maintenance-free. They can be used in any position without posing a problem with electrolyte spillage. The outer metal case of the cell is electrically isolated from the power-carrying plates. Both the positive and the negative terminals are at the top of the cell. A special glass fiber separator used in construction permits the cell to withstand high temperatures without suffering damage.

The discharge characteristics and cycle life of the SLA cells duplicate or exceed those of other lead-acid cells. The SLA cells are said to have a charge/discharge life of about 300 cycles, which favorably compares with the life of nickel-cadmium cells whose life is typically about 1000 cycles.

The internal resistance of the SLA cell is 10 milliohms (0.01 ohm). This low val-

ue makes possible high charge/discharge rates with minimum danger of overheating the cell. A resealable safety vent in the cell prevents cell bursting under extreme abuse.

The first of the new SLA cells to come on the market is a cylindrical D cell. It is designed to deliver 2.5 ampere-hours at a 250-mA discharge rate. The cell is capable of delivering up to 40 amperes of continuous current and 75 amperes of momentary (1-second) current. The line of SLA cells will eventually include batteries rated at 6 and 12 volts and 2.5 AH.

The rechargeable nickel-cadmium battery system consists of AA, C, and D cells and a 9-volt transistor size battery, each of which is available separately or packaged with its appropriate snap-on module that connects it to the Model BC3 miniature charger. The rechargeable NiCd cells and batteries are designed for any application where ordinary carbon-zinc batteries are used. They are directly interchangeable with other AA, C, and D cells and 9-volt transistor batteries. \diamond

Build
a


FLUORESCENT

Utility Lamp

Operates from 12-volt dc source.

BY JOE DUNCAN

A PORTABLE, battery-powered emergency lamp can be a life-saver on the highway and a great convenience at camp sites. To be truly useful, it should provide reasonable illumination without quickly depleting the battery or confining its light output within too narrow a beam. The utility fluorescent lamp described here satisfies these requirements. It uses a conventional 15-watt fluorescent tube and drive circuitry compact enough to fit in the fixture that houses the tube. Operating power can be drawn from any 12-volt source capa-

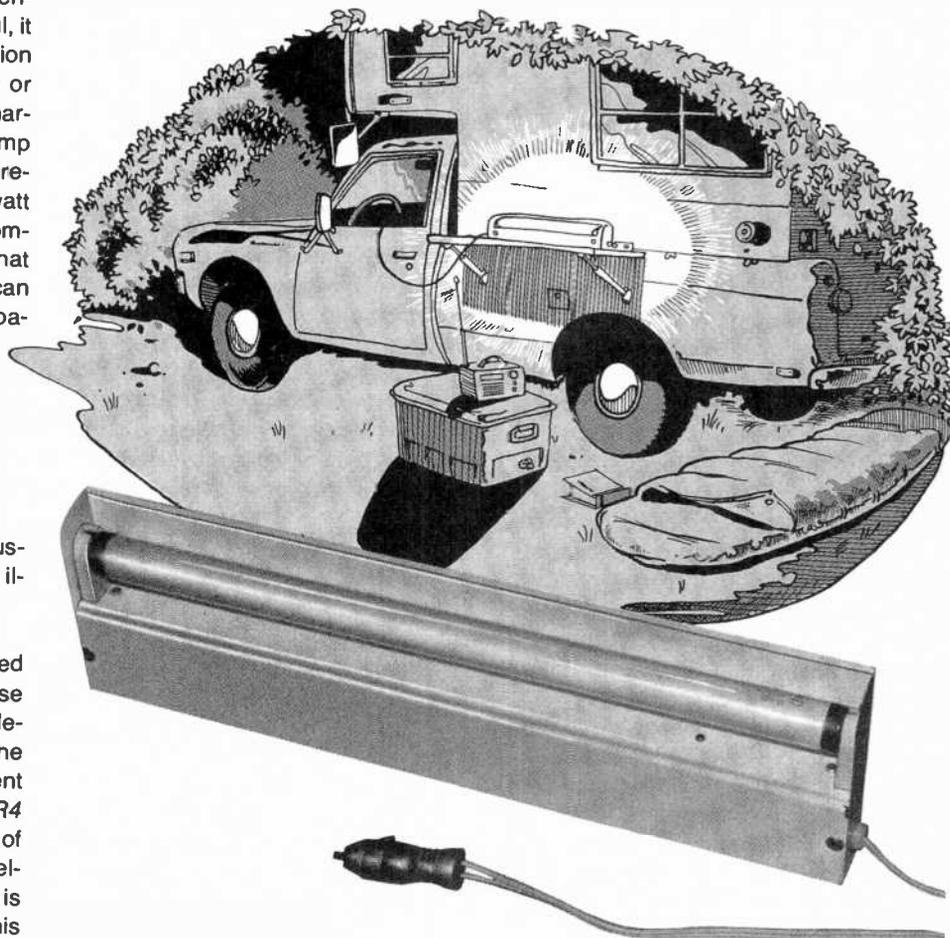

ble of delivering 2 amperes continuously. Thus, the lamp can also be used to illuminate the inside of a camper.

Circuit Operation. Timer integrated circuit *IC1* in Fig. 1 serves as a pulse generator whose output frequency is determined by *R1*, *R2*, and *C3*. When the output of *IC1*, at pin 3, goes low, current flows from the base of *Q2* through *R4* and *R5* and then to ground via pin 1 of the 555 timer. The voltage drop developed by the load current across *R3* is applied to the base of *Q1*, turning on this transistor, while part of the load current from *R4* and *R5* flows through transistor *Q1* to ground.

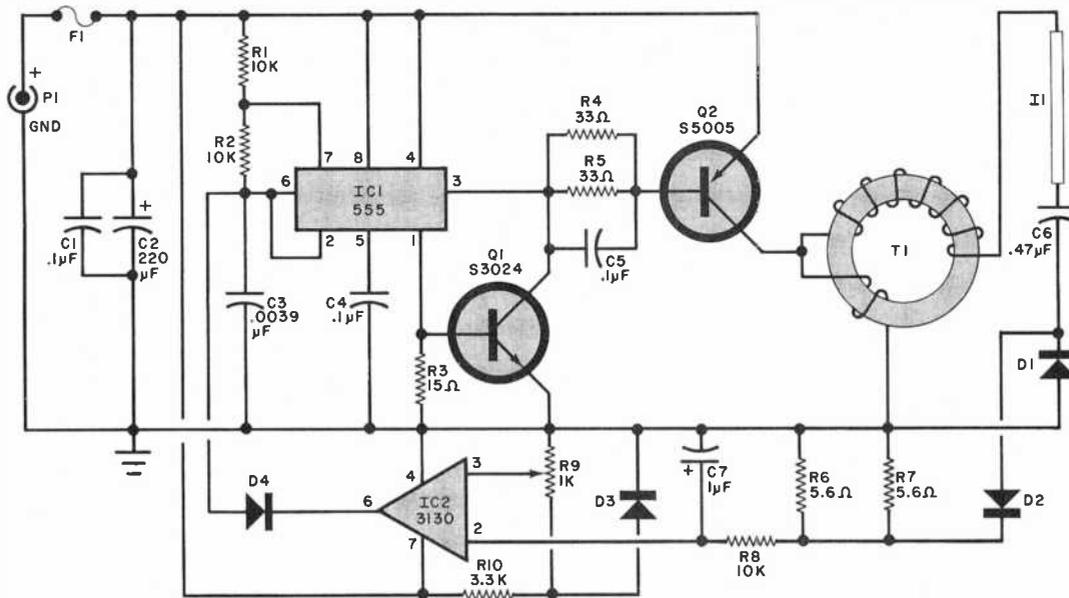


Fig. 1. The 555 oscillator drives Q2 which causes a high voltage across the lamp through T1. The IC2 circuit is a form of voltage regulator.

PARTS LIST

- | | | |
|---|--|---|
| <p>C1, C4, C5—0.1-μF, 50-V disc capacitor C2—220-μF, 50-V electrolytic capacitor C3—0.0039-μF silver-mica or polystyrene capacitor C6—0.47-μF, 200-V capacitor C7—1-μF, 35-V electrolytic capacitor D1, D2—1N4001 (1-ampere, 50-PIV) rectifier diode D3, D4—1N914 or similar switching diode F1—3-ampere fuse</p> | <p>I1—F15T8 15-watt fluorescent lamp (with fixture, Sears Model 8934 or similar) IC1—555 timer IC2—CA3130 op amp (RCA) P1—Auto lighter accessory plug (Radio Shack No. 274-331 or similar) Q1—HEP S3024 transistor (Motorola) Q2—HEP S5005 transistor (Motorola) R1, R2, R8—10,000-ohm, 1/4-watt resistor R3—15-ohm, 1/2-watt resistor R4, R5—33-ohm, 2-watt resistor R6, R7—5.6-ohm, 1/2-watt resistor</p> | <p>R9—1000-ohm trimmer potentiometer (Radio Shack No. 271-227 or similar) R10—3300-ohm, 1/2-watt resistor T1—See text (No. T-184-2 ferrite core available for \$3.50, including postage and handling, plus 6% tax for California residents, from Amidon Associates, 12033 Ostego St., N. Hollywood, CA 91607) Misc.—In-line fuse holder for F1; 18' No. 20 enamelled wire; 126' No. 26 enamelled wire; 18' conventional twin-lead lamp cord; machine hardware; hookup wire; solder; etc.</p> |
|---|--|---|

When the output of IC1 goes high, the voltage drop across R3 is very low. This turns off Q1 and the transistor increases the current-drive capability of IC1 without altering the output wave-shape.

The current-booster output of IC1 is applied to switching transistor Q2, which drives step-up transformer T1. The transistor for Q2 has an 80-volt breakdown rating and can handle 8 amperes. In operation, fluorescent lamp I1 requires 1.75 amperes, and the peak current flowing through Q2 is slightly greater than 6 amperes.


During the first few moments of operation and before the fluorescent lamp strikes, the rapidly changing magnetic field of T1 produces voltage pulses in excess of 600 volts. It is these pulses that are applied to the lamp to cause it to conduct. After the lamp starts, it serves as the load for T1 and limits the output potential of T1 to about 90 volts. The time between power-on and lamp lighting is about a second.

A vehicle's electrical system voltage might vary by 15% or more, depending on whether or not the engine is running

and also on the condition of the battery. In the utility light circuit, a 15% input voltage variation could mean low lamp brightness and might cause Q2 to burn out. The IC2 circuit is used to obviate these possibilities. Operational amplifier IC2 functions as a current regulator that maintains a constant light level over the range of battery voltages usually encountered in mobile electrical systems.

The voltage drop across R6 and R7 is proportional to the current through the fluorescent lamp. This voltage is filtered and smoothed by C7 and R8 before being applied to IC2. The op amp then compares the filtered voltage from C7 with a reference voltage that is preset by R9. The output of IC2 then develops a correction signal that is fed to IC1 to vary the oscillator's frequency and pulse

Fig. 2. Wiring diagram for T1. Conductor "a" is No. 20 wire. Others are No. 26.

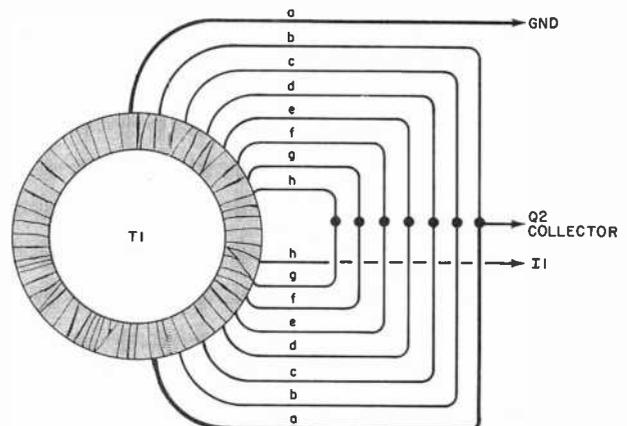

width as required to maintain a constant current and lamp brightness.

During operation, the potential at pins 2 and 3 of *IC2* is only on the order of 0.5 to 0.6 volt above ground, which is sufficient to drive the FET input stage of the CA3130 used for *IC2*. This potential, however, is too low to drive other op amps, such as the 741, that do not have FET input stages.

Construction. With the exception of *F1*, *Q2*, and *T1*, all components should be mounted on a small piece of perforated board or a printed circuit board of your own design. The circuit board assembly and other components then mount inside the selected fluorescent lamp fixture. Hence, select the fixture before making the board assembly so that you are sure the latter has space to fit inside the fixture. Also, select a metal fixture so that it can serve as a heat sink for *Q2*. The fixture should have at least a 2½" (6.4-cm) wide by 1" (2.54-cm) deep channel to accommodate the board as-

sembly and *T1* (see Fig. 3). If the selected fluorescent fixture has a ballast and starter, remove them.

enough cement to make all wires adhere to each other. Remove the contact cement from your hand with acetone or nail polish remover. Allow the cement on the bundle to dry before removing it from the support.


The wire bundle forms about 75 turns around the ferrite toroid core specified in the Parts List. Before proceeding, carefully scrape away about ½" (12.7 mm) of the enamel coating from all wire ends. Then, referring to Fig. 2, locate one end of the No. 20 wire and attach a tag labelled GND to it. Now, using an ohmmeter, identify and label all remaining wire ends for quick identification.

Once the No. 26 wires have been identified, connect them in series exactly as shown in Fig. 2. As you twist together and solder each wire connection, be sure to insulate the connection. Note that the unconnected end of the wire labelled *h* goes to the fluorescent lamp and that the junction where the heavy *a* and lighter *b* wires meet connects to the collector of *Q2*. This method of winding

the power input before final mounting of all elements. Fuse *F1* goes in an in-line fuse holder located in the power cable. The free end of the cable can be terminated with an automobile cigarette lighter plug or some other type of connector that mates with its counterpart in an electrical system. Make certain that the correct polarity is observed when connecting the power line leads.

There is only one adjustment that need be made to get the lamp operating properly. This is to set the current drawn by the lamp by adjusting *R9*. To do this, it is necessary to measure the current to the lamp. Set your multimeter to the 2- or 5-ampere range and connect it in series with the fuse holder. (If your meter does not have a 2- or 5-ampere measuring capability, temporarily connect a 0.1-ohm resistor in series with the fuse holder and measure the voltage across it. The current is then this voltage divided by 0.1.)

Set *R9* to midscale when you initially power up the utility lamp. As you adjust

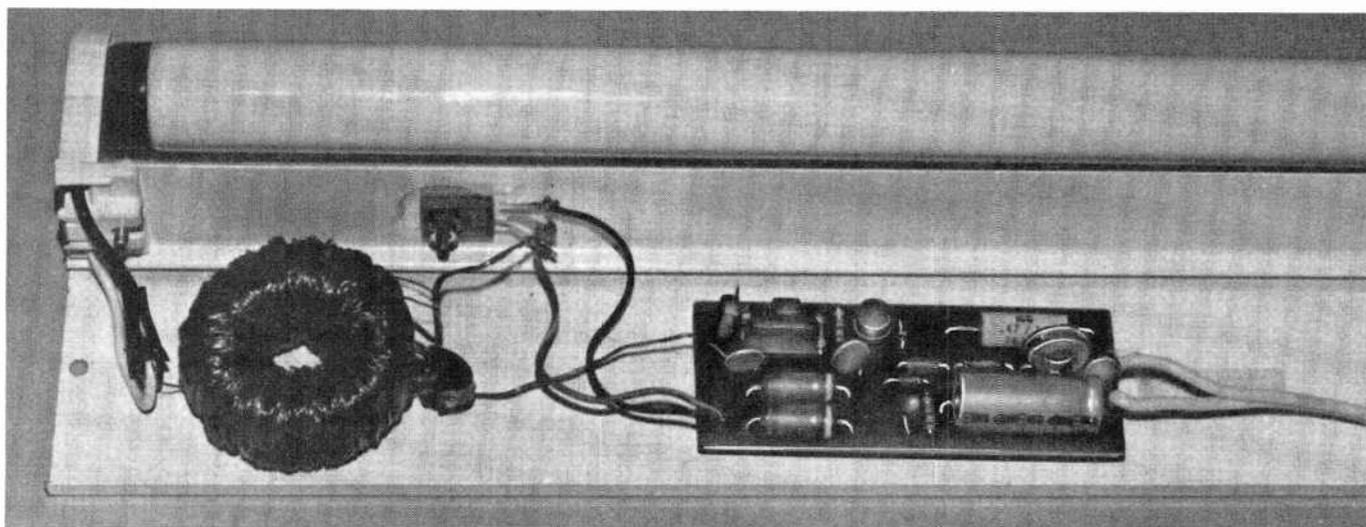

*Fig. 3. Photo shows author's prototype. Note how fixture is used (with insulation) as heat sink for *Q2*.*

sembly and *T1* (see Fig. 3). If the selected fluorescent fixture has a ballast and starter, remove them.

Transformer *T1* must be home fabricated by winding enamelled wire on a ferrite core. Cut an 18' (5.5-m) length of No. 20 enamelled wire and seven 18' lengths of No. 26 enamelled wire. Form the eight wires into a single bundle and temporarily tie one end to a door knob or other support. Liberally coat the bundle with contact cement. The easiest way to do this is to pour a small amount of the cement into the palm of your hand and pull your hand along the length of the bundle. Leave one end of the bundle attached to the support as you coat it with

produces the tight coupling required to prevent high-voltage switching transients from appearing at the collector of *Q2*. The finished transformer can be mounted in the trough of the fixture with silicone rubber or urethane adhesive.

Transistor *Q2* mounts on the metal fixture so that it makes thermal but not electrical contact. Use a mica insulator and silicone heat-transfer compound to assure good heat-sinking action. A typical installation of the components in the central channel of the light fixture is shown in Fig. 3.

Test and Adjustment. You can test the utility lamp by applying 12 volts dc to

the setting of *R9* to both sides of its center position, you will note that the meter indication will vary from a low of about 0.5 ampere to a high in excess of 2 amperes. Adjust *R9* for a 1.75 ampere indication (0.175 volt across the 0.1-ohm resistor). Once *R9* is properly set, daub some nail polish on its rotor to fix the setting. If you used a 0.1-ohm resistor in series with the fuse holder, remove it. The lamp is now ready to use.

One word of caution is necessary at this point: DO NOT plug the utility light into a power source unless a fluorescent lamp is in the circuit. Without the lamp serving as a load, high voltage switching transients are likely to destroy *Q2*. ◇

HOW TO DESIGN TTL DIGITAL SYSTEMS

BY JIM HUFFMAN

tips
for the
circuit designer
on using
the popular
Transistor-
Transistor
Logic family

DIGITAL circuits and techniques are finding their way into all areas of electronics, including many of the "all-linear" circuits of just a few years ago. Because of this ever-increasing popularity, it behooves the electronics experimenter to sharpen his knowledge of digital circuits and devices. The focus here is on the popular and low-cost transistor-transistor logic, or TTL, family of digital integrated circuits.

The TTL Family. The transistor-transistor logic family uses built-in transistors both as electronic switches and gates, is highly immune to noise, and has very fast operating speeds. The most common forms of the TTL family are the industrial-grade 7400 and military-grade 5400 series. Some manufacturers have 8000 and 9000 series of TTL devices. There is no relationship between the type of IC function and the last two digits in the IC's identifying number. A 7400 is a quad NAND gate, while a 7490 is a decade counter.

Within the 7400 series, letter designations are often added to further identify the type of IC. For example, the 7400 is a standard four-input NAND gate, but the L in 74L00 identifies the IC as a low-power four-input NAND gate. To get this characteristic, one sacrifices speed. The H in 74H00, on the other hand, tells us that this is a high-power version of the same IC. Its output stage can drive higher current loads and is capable of driving normal loads faster because of its ability to charge the inherent output capacitance at a faster rate.

The 74S00 is a fairly high-power de-

vice that is extremely fast because its inputs are clamped by Schottky diodes. These diodes have very fast switching characteristics and thus make the 74S00 series the fastest of the TTL devices. The Schottky diode approach has been combined with the low-power approach to produce the 74LS00 series. The typical 74LS00, for example, consumes very little power, yet it operates at speeds as high as the conventional 7400 device.

Each of the types of TTL devices described above has its place in your circuit designs. Your choice of devices will be dictated by the power and speed requirements of your specific project.

Application. TTL IC's have very good noise immunity characteristics and operate with a good tradeoff in speed. Even so, they must be used with some care in circuit design to minimize interaction between elements. For example, in Fig. 1, gates A and B can suffer from unwanted coupling through the invisible but very real inductance of the common ground lead that ties the two gates to the negative side of the power supply line and the input to buffer C that is not supposed to operate at this time.

When gate A discharges the stray capacitance at its output, an erroneous signal appears because of the ground inductance at gate B. These undesirable outputs are commonly called "glitches." They can be eliminated mostly through proper circuit layout. The way to do this is illustrated in Fig. 2. Here the ground interconnection between the two gates is a "bus" lead.

Assume that gate A in Fig. 2 is a low-power 74L00 series IC and that buffer B is a high-power 74H00 device. As soon as the high-power stage switches on, a high-speed, high-current switching transient is generated and causes a voltage drop through the resistance of the ground or V+ bus. This voltage is applied to the input of the low-power gate, which "sees" it as a real signal. The usual remedy for this situation is to use bypass capacitors directly at the V+ and ground pins of the IC's. Proper circuit layout, however, can minimize glitches in the wiring without the need for bypass capacitors.

An example of bypassing is shown in Fig. 3. Note that there still exists a slight variation in the power supply along the bus and that although the transients (compared to Fig. 2) are almost eliminated by the bypass capacitors, the high current drain will still affect the voltage at one end of the bus. The point to remember in designing TTL circuits, and any other logic system, is that it is best to know what will be the effect of an action taken rather than attempt to make up for inadequacies after the fact.

The best way to lay out a TTL logic system is to use the V+ bus and ground-plane approach. Ideally, it would be best to have all V+ points in the circuit on one side of the board and all ground points on the other side. Unfortunately, circuit considerations dictate otherwise, since interconnections between elements must be made somewhere. However, it is possible to simulate the V+/ground bus approach by using the layout illustrated in Fig. 4. IC's can be

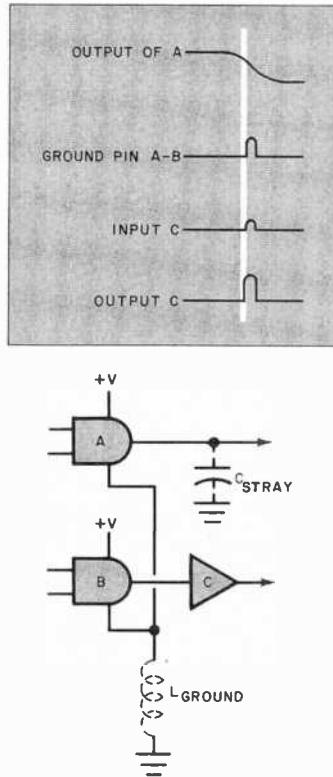


Fig. 1. Common ground inductance and stray capacitance cause "glitch" at output gate of C.

distributed along this bus system. Each of the two buses appears on both sides of the board. It matters little that each bus begins on one side of the board and ends on the other; electrically, each is a continuous bus.

The Fig. 4 approach lessens the effect of distributed capacitance, while the capacitors at the points where the buses cross over through the printed circuit

board are adequate for bypassing. If this type of layout is not possible, it is best to locate the ground bus entirely on one side of the board and the V+ bus entirely on the other side of the board.

High-current devices should be located as close as possible to the V+ and ground bus connections. This will assure a minimal effect by these devices on the more sensitive, lower-current devices in the circuit. Bypassing at the input stages will then have greater effect.

Once you have fabricated a pc board for a certain digital function, you may find it necessary to include more than one pc board assembly in your finished system. In this case, each pc assembly must be designed to minimize the inherent stray inductance and capacitance and heavy bus structures should be used to connect the V+ and ground lines to all boards. In some cases, it may even be necessary to use separate ground leads to high-power circuits.

Design Hints. The first step in designing a logic system is to lay it out on paper. The next is to breadboard your layout. While you are breadboarding the circuit, try to use the same physical layout you plan to use in the finished project. This will reduce the chances of any surprises after you etch a pc board and are committed to a given layout.

In the breadboarding stage, there are a few things to keep in mind. The popular "solderless" breadboard has a distinct problem—there is very high capacitance between the interconnecting strips within the socket. At high frequencies and at very fast switching speeds, capa-

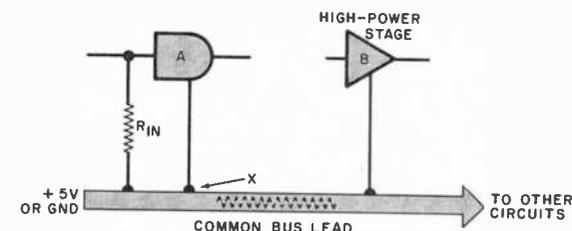
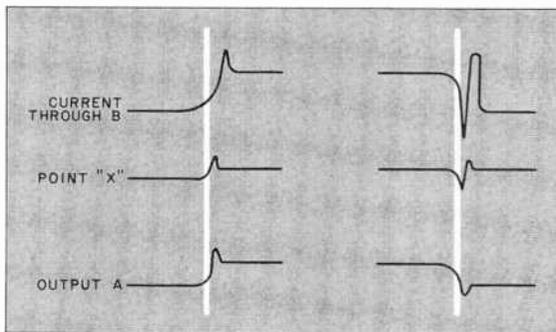


Fig. 2. Both glitch and voltage drop can occur along a common bus lead as shown here.

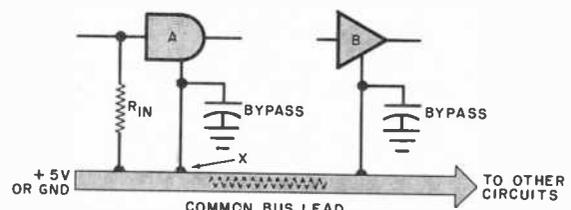
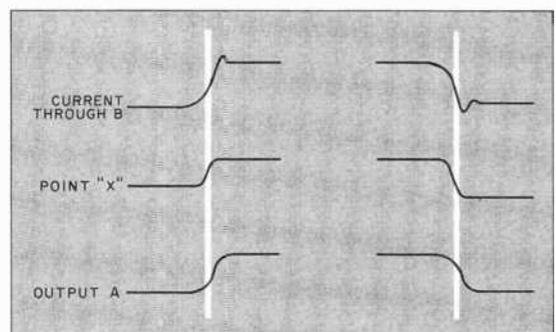


Fig. 3. Bypassing can eliminate glitch but not voltage change which produces erroneous signal.

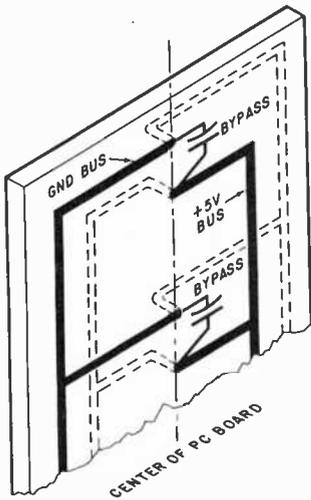


Fig. 4. Ground plane simulation where buses start on one side of board and cross to other side, with bypassing at crossovers.

citive coupling may occur between the closely spaced internal "tracks" or between the holes on the board. Do not use these breadboards for high-frequency circuits. They are, however, adequate for breadboarding low-frequency circuits in which the switching speeds are low.

The last and perhaps most important design stage is to debug the circuit you set up on the breadboard. To do this, you will need certain test equipment, such as an oscilloscope or logic probe. The logic probe is handy to have in cases where your scope has a limited bandwidth that prevents it from registering on-screen fast pulses. Almost any type of multimeter can be used to check for the presence of the proper dc voltages on the various IC pins.

Typical Design. To illustrate the general procedure to use in designing a TTL system, let us work up a six-decade decoder/driver/display system for a 30-MHz frequency counter. Since operation is to 30 MHz, we can use standard 7490 decade counters and 7447 decoder/drivers for the seven-segment LED displays. We will also use separate 5-volt supplies for the display system and IC portion of the circuit.

First, we would start by laying out on paper the basic circuit configuration. Then, we circle the portions of the system that draw high current, as shown in Fig. 5. The areas of highest current demand are the outputs of the 7447 LED drivers and the LED displays, neither of which are required to do high-speed switching. The highest speed device in this circuit is IC1, which must operate at frequencies up to 30 MHz. Consequently, this IC must be located at the point of

least possible noise and bus glitches. By using independent V+ and ground leads at the input of IC1, there is no need for bypass capacitors.

The next step is to breadboard the circuit and debug it. Once this is done, a

separate wire jumpers to interconnect all points in the circuit.

Closing Remark. As you can see from the foregoing, designing with TTL is relatively easy—if you give careful at-


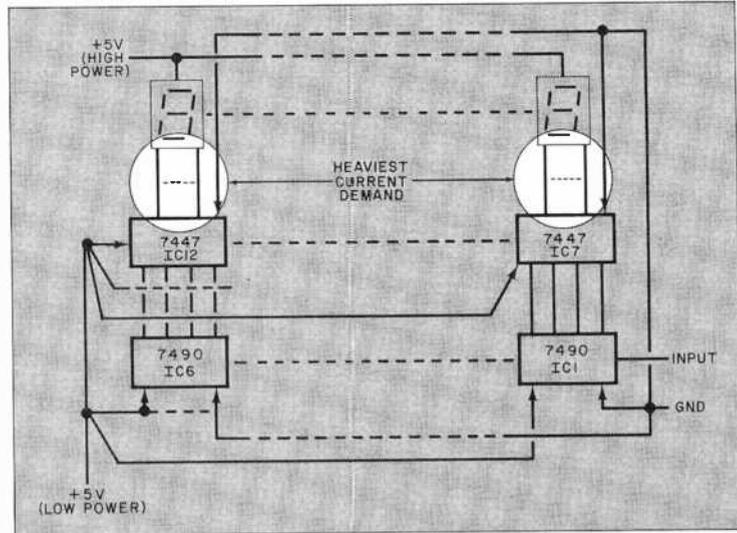


Fig. 5. Sample circuit has independent grounds and supplies to reduce glitches. Circled areas have own supply leads.

printed circuit board can be made. An actual pc assembly for this circuit is shown in Fig. 6. Note that the pc board has copper traces on both sides of the board, which eliminates the need for

attention to circuit layout. One way you can get a "feel" for proper design is to experiment with the various types of TTL IC's available at low cost from the advertisers in the back of this magazine. ◇

Fig. 6. The final layout of the decade counter follows the general outline suggested in Fig. 5.

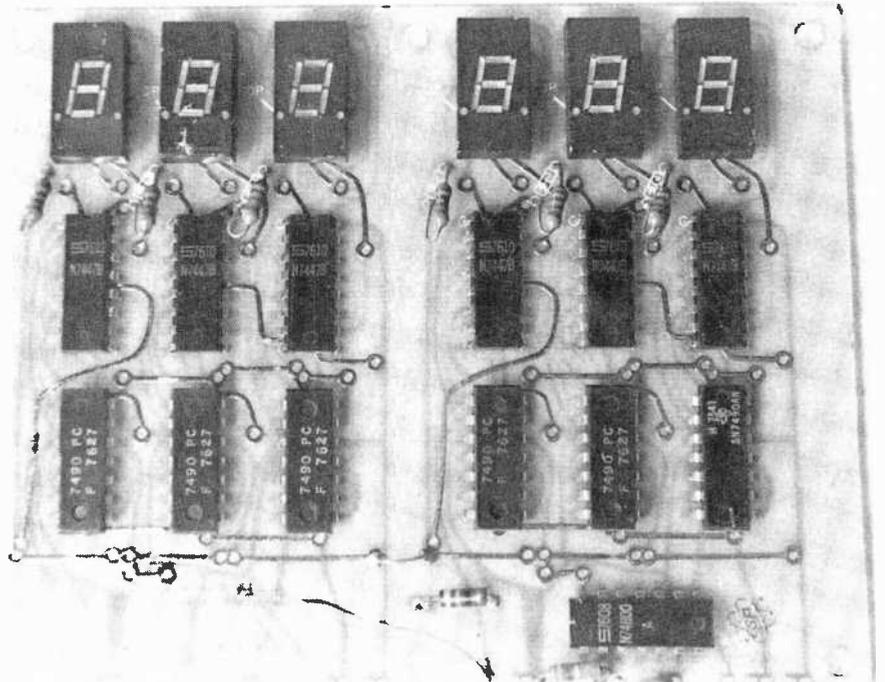

HIGH SENSITIVITY SWR Meter for Low-Power Communications Equipment

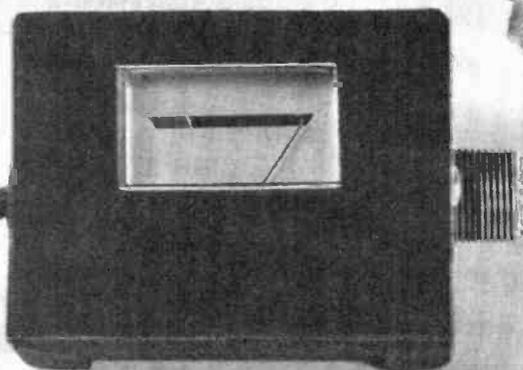
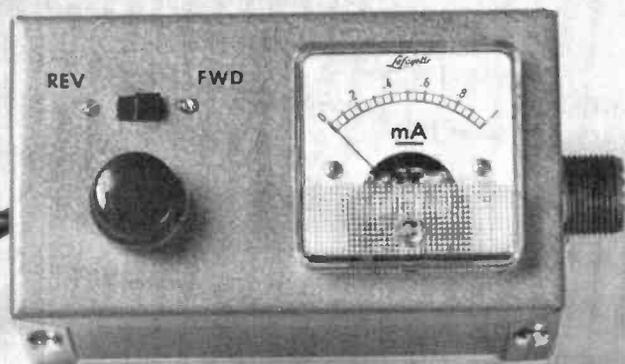


Photo of full SWR meter (top) and reflected-power-only meter (bottom).

Easy-to-build instrument uses a ferrite toroid coil for accurate readings at low power levels.

BY WILLIAM VANCURA

LOW-POWER communications gear such as CB transceivers and amateur QRP rigs have no r-f output to spare. So it's especially important to make maximum use of available power (as well as receive capability) by properly tuning the antenna system. These adjustments are most often made with an SWR meter, such as the instrument described here.

This SWR meter is easy to build and inexpensive. Moreover, it features a ferrite toroid pickup coil to achieve high sensitivity. This makes it possible to get an accurate SWR reading even at low r-f power levels.

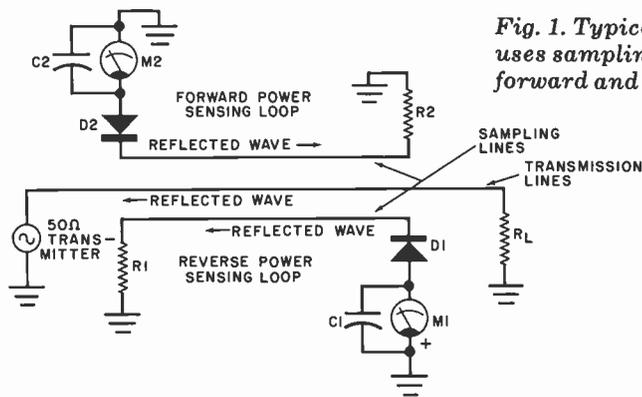


Fig. 1. Typical SWR meter uses sampling lines to detect forward and reflected waves.

How It Works. The SWR meter indicates the relative amplitudes of the forward and reflected waves travelling on the transmission line. (These two combine to create a standing wave.) When the line is connected to a perfectly matched load, no standing wave exists. The forward-going wave will travel down the line and will be completely transferred to the load. A mismatched load, however, will not accept all of the energy from the line. It will reflect a portion back toward the source, causing a standing wave to appear on the line.

The forward and reflected waves must be isolated to effect their measurement. This is done by sampling lines (Fig. 1) that are properly terminated at one end and mismatched at the other. When energy is coupled to a sampling line, the mismatched termination will reflect some portion toward the proper termination, just as the transmission line will. However, the reflection produces a travelling wave on a sampling line, as opposed to the standing wave on the transmission line. This travelling wave corresponds to either the forward or reflected component of the energy on the transmission line.

Figure 1 shows that the two sampling lines are identical except for the physical locations of the matched (resistors) and mismatched (diodes, capacitors, and meters) terminations with respect to the transmission line. The reflected waves on these lines travel from the mismatch to the matched terminations, and are therefore moving in opposite directions. But only one is travelling in the opposite direction of the reflected wave on the transmission line. Thus, reflected waves on the sampling lines are out of phase.

When the reflected waves on a sampling line and the transmission line are moving in the same direction, the reflected component on the sampling line is reinforced and the forward component is cancelled. This occurs in the reverse power sensing loop, and *M1* will display the relative magnitude of the reflected

wave on the transmission line. When the reflected waves are travelling in the same direction, the reflected component is cancelled, leaving the forward wave for display by *M2*.

In this project, a toroid coil is used in place of the sampling lines, greatly simplifying construction and increasing sensitivity as compared to standard "trough line" designs. Two SWR meter configurations are presented. The first, shown schematically in Fig. 2, is the simpler of the two. It is intended for CB applications where the only requirement is to measure SWR on a line with a fixed input power of four watts. The meter reads only reflected power. A zero indication suggests a perfect match, and any reading above half scale points to a bad mismatch that should be corrected.

The second configuration (Fig. 3) is more flexible, containing a switch and a sensitivity control to allow measurements of both forward and reflected power. It is more at home in amateur operations where power levels are com-


monly varied. To obtain a meaningful reading, the sensitivity control must be adjusted each time the meter is used.

Construction. Decide which circuit you will build, and select a suitable meter for *M1*. The one used in the author's reflected-power-only prototype is a 300- μ A meter, while the meter in his full-SWR prototype has a 1-mA movement. Any meter from 50 μ A to 1 mA can be used with good results. The project should be housed in a metal enclosure just large enough to accommodate the meter, switch, potentiometer (if used) and SO-239 coaxial connector. A 4" x 2 $\frac{1}{8}$ " x 2 $\frac{1}{8}$ " (10.2 x 5.4 x 5.4 cm) aluminum utility box can be used for the full-SWR meter.

Attach a PL-259 connector to one end of an 18-to-36-inch (45.7-to-91.4-cm) length of RG-58-U cable. Remove 1" (2.54 cm) of the cable's black vinyl outer jacket, and comb out the exposed braid. Twist the combed braid to form one large stranded conductor. Then remove $\frac{1}{4}$ " (6.4mm) of the insulation around the inner conductor. Drill a hole on one side of the enclosure to accommodate the coaxial cable. Mount a rubber grommet in the hole and push the coax through it. Drill holes for an SO-239 coaxial connector on the opposite side of the enclosure and mount the connector and a solder lug as shown in Fig. 4.

Pass the inner conductor through a ferrite toroid (see parts list) before soldering the coaxial conductors to the con-

Fig. 2. Schematic diagram of reflected-power-only meter.

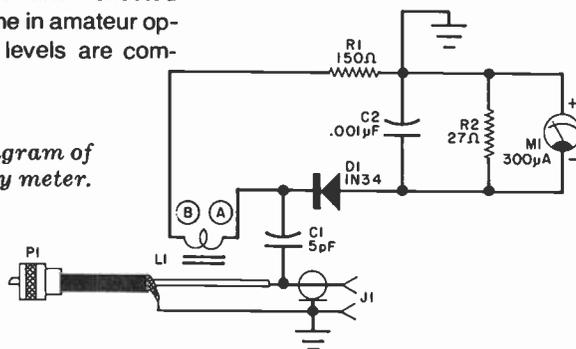

PARTS LIST

- C1—5-pF, 500-volt disc ceramic or silver mica capacitor
- C2—0.001- μ F, 500-volt disc ceramic or silver mica capacitor
- D1—1N34 or 1N914 diode
- J1—SO-239 coaxial connector
- L1—Two turns of No. 26 enamelled copper wire on a Fair-Rite Products Corp. 638MT-L (No. 5963000301) ferrite toroid. See note.
- M1—300- μ A or 1-mA meter (see text)
- P1—PL-259 coaxial connector

- R1—150-ohm, 10%, $\frac{1}{2}$ - or $\frac{1}{4}$ -watt carbon composition resistor
- R2—27-ohm, 10%, $\frac{1}{2}$ - or $\frac{1}{4}$ -watt carbon composition resistor OR 100-ohm trimmer or panel-mount potentiometer (see text)
- S1—DPDT switch
- Misc.—RG-58-U coaxial cable, No. 26 enamelled copper wire, insulated sleeving, solder lug, terminal strip, suitable enclosure, rubber grommet, machine hardware, solder, etc.
- Note: Ferrite toroids for *L1* are available for \$1.00 each from William Vancura, 4115 35th Ave., Moline, IL 61265. Include a stamped, self-addressed envelope.

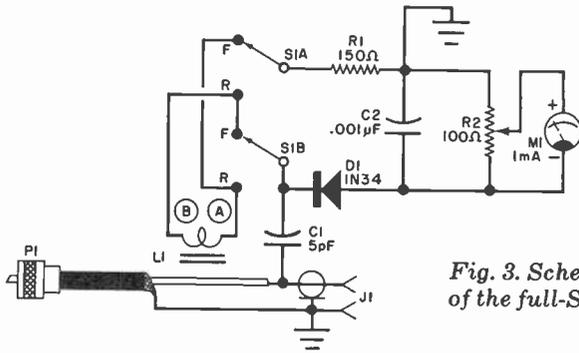


Fig. 3. Schematic diagram of the full-SWR meter.

necter and solder lug. Prepare a 6" (15.2-cm) length of No. 26 enamelled copper wire and wrap two turns around the toroid *exactly* as shown in Fig. 4. Mount the meter (and switch and potentiometer, if used) on the front of the enclosure. Follow the appropriate schematic (Fig. 2 or Fig. 3) and wire the circuit, using the switch lugs and meter terminals as tie points. You can also use a terminal strip to provide circuit tie points and mechanical support for components. Use insulated sleeving, if necessary, to prevent accidental shorting between leads, and keep all leads as short as possible. Be sure to scrape 1/4" (6.4 mm) of enamel from the end of each lead of the pickup coil before soldering. Observe the lead designation in Fig. 4 when soldering these leads to the rest of the circuit.

Testing the Meter. Fashion a dummy load by soldering a 50-ohm, 2-watt carbon resistor between the inner and outer conductors of a PL-259 coaxial connector. Insert the dummy load into the SO-239 connector on the meter enclosure, and attach the PL-259 on the length of cable from the meter to the antenna output jack of the transmitter or transceiver. Then close the PTT microphone switch or telegraph key.

If you built the full-SWR meter, switch S1 to the FORWARD position, adjusting R2 for a full-scale reading. Then switch S1 to the REVERSE position. The meter needle should barely move, if at all. If you built the reflected-power-only meter, key the transmitter briefly. Similarly, the meter needle should barely move, if at all. Do not apply r-f to the dummy load for more than a few seconds, however, to avoid overheating.

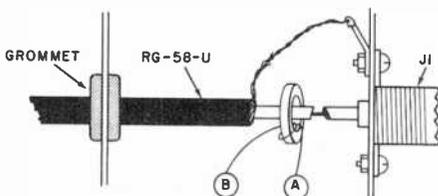


Fig. 4. Detail of toroid coil.

Replace the dummy load resistor with an 18-ohm, 2-watt carbon component. Key the transmitter briefly. The meter should read about half-scale. If the full-SWR meter was built, recalibrate by adjusting R2 for full-scale FORWARD deflection before taking a REVERSE reading. If the reflected-power-only meter was built—and a meter movement other than 300 μA used—consult Fig. 5. A small trimmer potentiometer is included in this alternate meter wiring to compensate for different movement sensitivities. Reverse toroid leads A and B, and adjust R2 for full-scale deflection as the transmitter is keyed. Then reverse leads A and B once more, taking care not to disturb the setting of R2.

Using the Meter. The SWR meter will not read SWR directly, but will indicate the reflection coefficient ρ . The SWR is related to ρ by the equation $SWR = (1 + \rho)/(1 - \rho)$. The following is a list of various values of ρ and SWR.

| Reflected Meter Reading (% of full scale) | SWR |
|--|--------|
| 0 | 1:1 |
| 10 | 1.22:1 |
| 20 | 1.5:1 |
| 30 | 1.85:1 |
| 33 1/3 | 2:1 |
| 40 | 2.33:1 |
| 50 | 3:1 |
| 60 | 4:1 |
| 66 2/3 | 5:1 |
| 70 | 5.66:1 |
| 80 | 9:1 |
| 90 | 19:1 |
| 100 | ∞ |

If desired, a new scale for the meter can be drawn and glued onto the faceplate to read SWR directly. At any rate, a reading of 25% of full scale (SWR 1.7:1) or less means the antenna is closely matched to the transmission line. Readings greater than 33 1/3% of fullscale (SWR 2:1) indicate a mismatch that should be investigated.

In practice, the short length of coax from the SWR meter is connected to the

antenna output jack on the transceiver, and the feedline from the antenna is connected to the coaxial jack on the meter enclosure.

Antenna Tuning. The SWR meter can be used to adjust a CB antenna for resonance. Antenna tuning should be done in a clear, open area, away from any substantial metallic objects. Keep your hands and tools away from the antenna when checking the SWR. Connect the meter to the transceiver and the antenna, and momentarily key the transmitter at both edges of the band (channels 1 and 23 or 1 and 40, depending on your transceiver's capabilities). Note the meter readings.

If the needle stays below 25% of full scale at both band edges, the antenna is

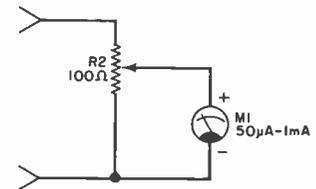


Fig. 5. Alternate meter wiring.

already properly tuned. A reading at the band center (channel 13) should show an even smaller meter deflection. When the meter reads above 25% at either end, the antenna is either too short or too long. If the deflection is greater at channel 1, the antenna is too short. A larger meter reading at channel 23 or 40 implies that the antenna is too long.

Most mobile CB antennas have provisions (usually a set screw) for length adjustment. Loosen the set screw and shorten or lengthen (whichever is required) the antenna by about 1/4" (6.4 mm). Take new readings at the band center and edges. Continue this procedure until an acceptable match exists across the band. Most loaded antennas are very sensitive to length adjustments, especially when they are near resonance. Accordingly, determining the "right" setting requires patience.

Some full-size antennas don't have a length adjustment and will have to be cut to resonance. *Never* cut off more than 1/4" at a time—you can't lengthen a short antenna! Remember that it's not absolutely necessary to have a 1:1 SWR. You will rarely achieve this ideal in practice. In fact, you won't measure much under 2:1 with mobile miniwhips. Thus, your antenna adjustments goal should be for a tolerable *minimum* SWR. The high sensitivity of this SWR meter project will pinpoint this reading with high accuracy. ◇

If you can't go to college for your career in electronics —read this!

**CREI brings college-level training
to you with eight educational
advantages, including special
arrangements for engineering degrees**

The best way to qualify for top positions and top pay in electronics is obviously with college-level training. The person with such training usually steps more quickly into an engineering level position and is paid considerably more than the average technician who has been on the job several years.

A regular college engineering program, however, means several years of full-time resident training—and it often means waiting several years before *you can even start your career*. This, of course, is difficult if you must work full time to support yourself and your family.

If your career in electronics is limited without college-level training, take a look at the advantages a CREI home study program can offer you.

1. Convenient Training

CREI brings the college to you. Through the convenience of home study, you receive exactly the same level of training you will find in any college or university offering programs in electronic engineering technology. With CREI, however, you can “go to college” whenever you have spare time at home or on the job.

2. Specialized Programs

With CREI, you enjoy the advantage of *specialized* training. That is, your program will include only those courses directly applicable to your career in electronics. We omit such courses as English, social studies and other subjects, which are usually required in resident schools. Therefore, with CREI, you move ahead faster to the more interesting and useful part of your training.

3. Practical Engineering

CREI programs give you a *practical engineering* knowledge of electronics. That is, each part of your training is planned for your “use on the job.” By using your training, you reinforce the learning process. And by demonstrating your increased knowledge to your employer, you may qualify for faster career advancement.

4. Engineering Degrees

CREI offers you a number of special arrangements for earning engineering degrees at recognized colleges and universities. You can earn college credit while you are taking your CREI program or apply later, whatever is best for your career plans.

Career Training at Home

5. Unique Laboratory

Only CREI offers you the unique Electronic Design Laboratory Program. This complete college laboratory makes learning advanced electronics easier and it gives you extensive practical experience in many areas of engineering, including design of electronic circuits. No other school offers this unique program. It is a better "Lab" than we have found in many colleges. And the professional equipment included in the program becomes yours to keep and use throughout your professional career.

6. Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

7. Prepared by Experts

Experts in industry and technical organizations of government develop CREI programs. Each part of your training is developed by a recognized expert in that area of electronics. That means you get the most up-to-date and practical instruction for your career.

8. Industry Recognition

That CREI training is recognized by industry and government is evident from the fact CREI provides training to advanced technical personnel in over 1,700 technical organizations. Many subsidize the training of their employees with CREI. If there is any question about the advantages of CREI training for you, ask your employer or any engineer to evaluate the outline of a CREI program for you.

Other Advantages

Of course, there are many other advantages to CREI training. For example, throughout your training, CREI's staff gives you personal instruction for each step of your program. And in many industrial areas, both in the U. S. and abroad, CREI Field Service Representatives provide a number of important personal services for your training and your career.

FREE Book

There isn't room here to give you all of the facts about career opportunities in advanced electronics and how CREI prepares you for them. So we invite you to send for our free catalog (if you are qualified). This fully illustrated, 80 page catalog describes in detail the programs, equipment and services of CREI.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Send for this **FREE Book** describing your opportunities and CREI college-level programs in electronics



Mail card or write describing qualifications to

CREI **CAPITOL
RADIO
ENGINEERING
INSTITUTE**


McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

CREI programs are approved for training of veterans and servicemen under the G.I. Bill.

1/2-Octave Real Time Audio Analyzer

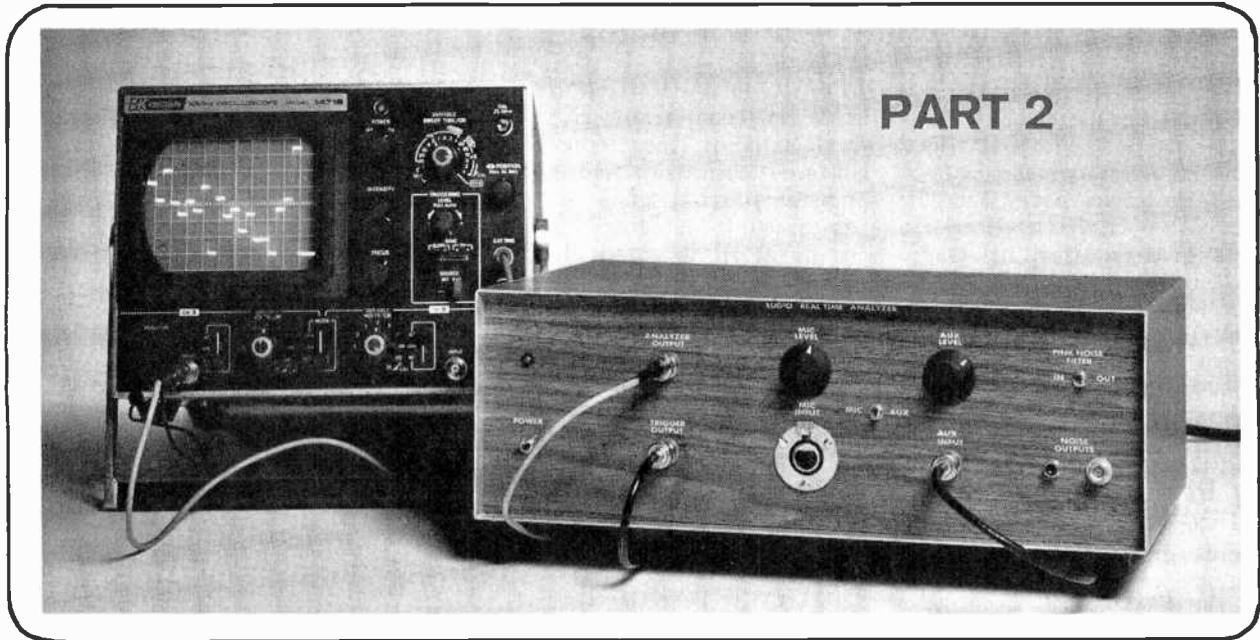

Test and calibration procedures, typical applications and how to add an optional logarithmic converter.

BY BOB JONES AND RICHARD MARSH

LAST month, we discussed the circuitry of the Real Time Analyzer, examined overall system operation, and presented construction details. Now we'll describe the optional Logarithmic Converter and outline test and calibration procedures. Also, typical applications for the Analyzer will be suggested.

The Log Converter, shown schematically in Fig. 11, is a useful accessory which allows display of amplitude variations on the scope directly in dB. The heart of this linear-to-logarithmic converter is IC36, a 76502 integrated circuit. One half of IC35A is used as a buffer for log converter IC36. This buffer is powered by a bipolar 5-volt supply, so its output (and thus the input to IC36) is limited to +5 volts maximum. The ORIGIN ADJUST control (R144) and op amp IC35B determine the amount of dB per division of scope display. Stages IC37A and IC37B provide gain and rectification, respectively. The rectifying action of IC37B prevents any negative voltages from reaching the scope's vertical input. However, "negative" outputs are generated by IC36 whenever its input signal drops below the ORIGIN level.

Power for the log converter is derived from the RTA, with zener diodes D26 and D27 providing the required ± 5 volts

dc. Etching and drilling and parts placement guides for the log converter pc board are shown in Fig. 12. Use IC sockets or Molex Soldercons to facilitate installation of the integrated circuits. Pay attention to pin basing and polarities.

Tests and Calibration. With all IC's removed from their sockets (except the voltage regulators), plug the line cord into a wall socket and close S2. Measure the following regulated dc voltages: +5 volts across C112; -15 volts across C111; +15 volts across C110. Then see if LED1 lights. If not, check the polarity of the LED. If all is well, turn off the ac power and insert all IC's.

If you are installing the optional log converter, perform the following steps (1) through (7). Otherwise, they can be bypassed.

(1) Decide how many dB/division you want displayed on the scope, and determine how many dB will be shown in a full-scale deflection. For example, if the vertical scale of the scope is 6 cm and 4 dB/cm is desired, 24 dB will be displayed full-scale.

(2) Calculate the origin voltage. (See Table II.) The maximum permissible input to the log converter chip (IC36) is one volt. In our example, -24 dB referenced to one volt is 0.063 volt.

(3) Apply 0.5 volt dc across the converter input and adjust R140, the INPUT LEVEL control, so that the voltage at TP1 equals the calculated origin voltage.

(4) Adjust R144, the ORIGIN ADJUST potentiometer, for zero volt (± 0.1 volt) at TP2. This is a sensitive adjustment.

(5) Increase the dc voltage applied across the input to 1.5 volts. Then adjust R140 so that 1.0 volt appears at TP1. Monitor the converter output on your oscilloscope and adjust R148, the SLOPE ADJUST control until full-scale deflection of the scope trace occurs. Set the scope's vertical sensitivity to whatever value is most suitable for adjustment.

(6) Repeat steps (3), (4), and (5) until all adjustments are correct.

(7) Adjust the INPUT LEVEL control, R140, so that the signal voltage at TP1 never exceeds one volt. The RTA's maximum level reference (which appears at the Analyzer output at clock pulses 23 and 24) is 10 volts. You can use this as the signal applied to the converter input for this adjustment. But be sure to back down on R140 before you apply 10 volts at the converter input. When R140 is properly adjusted, the 10-volt reference from the RTA will cause full-scale deflection.

Next, adjust all LEVEL ADJUST controls (R75 through R94) on the filter boards to

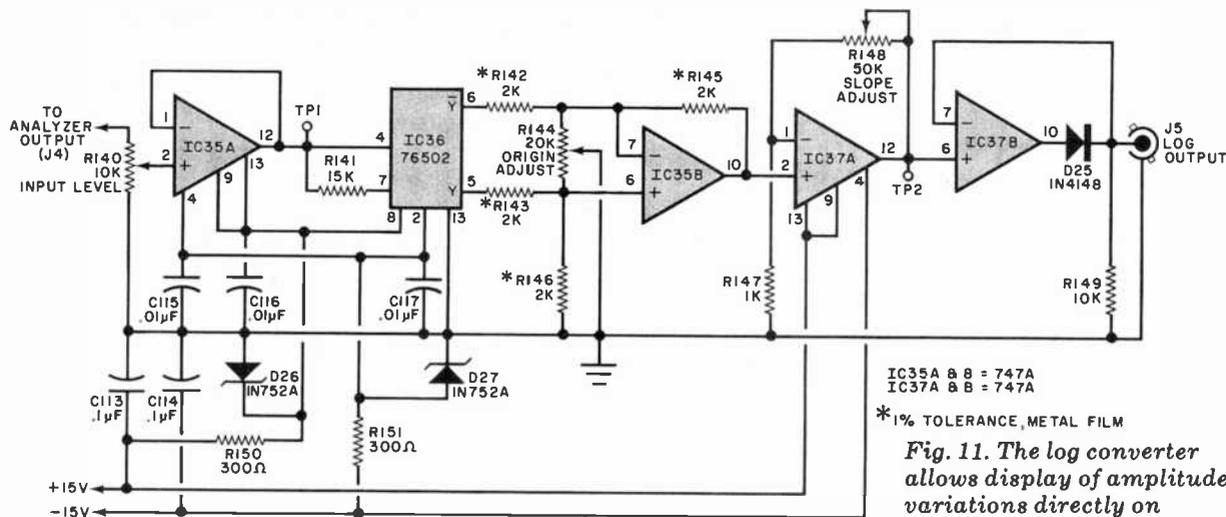


Fig. 11. The log converter allows display of amplitude variations directly on the scope in decibels.

LOG CONVERTER PARTS LIST

- C113, C114—0.1- μ F, 50-volt disc ceramic capacitor
- C115 through C117—0.01- μ F, 50-volt disc ceramic capacitor
- D25—1N4148 silicon diode
- D26, D27—5.6-volt, 4-watt zener diode (1N752A, HEP Z0212 or equivalent)
- IC35, IC37—LM747A dual operational amplifier IC
- IC36—SN76502 linear-to-logarithmic converter IC (Texas Instruments)**
- J5—BNC connector

The following fixed resistors are 5% tolerance, carbon composition components.

- R141—15,000 ohms, 2 W
- R147—1,000 ohms, 2 W
- R149—10,000 ohms, 2 W
- R150, R151—300 ohms, 4 W

The following fixed resistors are 1% tolerance, 1-watt metal film components

- R142, R143, R145, R146—2000 ohms

The following resistors are multi-turn, 6-watt Cermet trimmer potentiometers (Spectrol type 43Y or equivalent).*

- R140—10,000 ohms
- R144—20,000 ohms
- R148—50,000 ohms

Misc.—Printed circuit board, IC sockets or Molex Soldercons, hookup wire, pc board spacers, coaxial cable, machine hardware, solder, etc.

Note: The following is available from Southwest Technical Products Corp., 219 W. Rhapsody, San Antonio, TX 78216: etched and drilled pc board LC-2b for \$3.25 ppd.

*Available through distributors such as Allied Radio or Newark Electronics.

**Consult a Texas Instruments local distributor or sales representative.

their maximum or full clockwise positions, and all Q ADJUST potentiometers to their minimum or full counterclockwise positions. Apply ac to the RTA by closing S2. Connect your dc-coupled oscilloscope to the RTA output. Set the front panel AUX LEVEL potentiometer to its full clockwise position. Adjust the scope's vertical sensitivity for approxi-

mately $\frac{2}{3}$ -scale display of the 10-volt reference signal from the RTA. Place S1 in the AUX position, and apply a 0.1-volt rms, 22.4-Hz sine wave to the AUX input.

Adjust R15 (the Q ADJUST potentiometer for filter one) until an increase in dc level occurs. (There may have already been a dc level at the RTA output if there was an offset at IC31.) As the control is


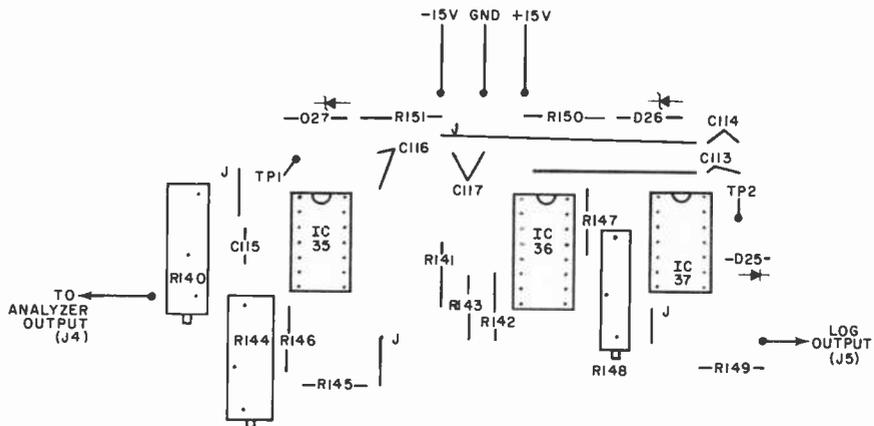


Fig. 12. Etching and drilling guide for the pc board is at right. Component layout shown above.

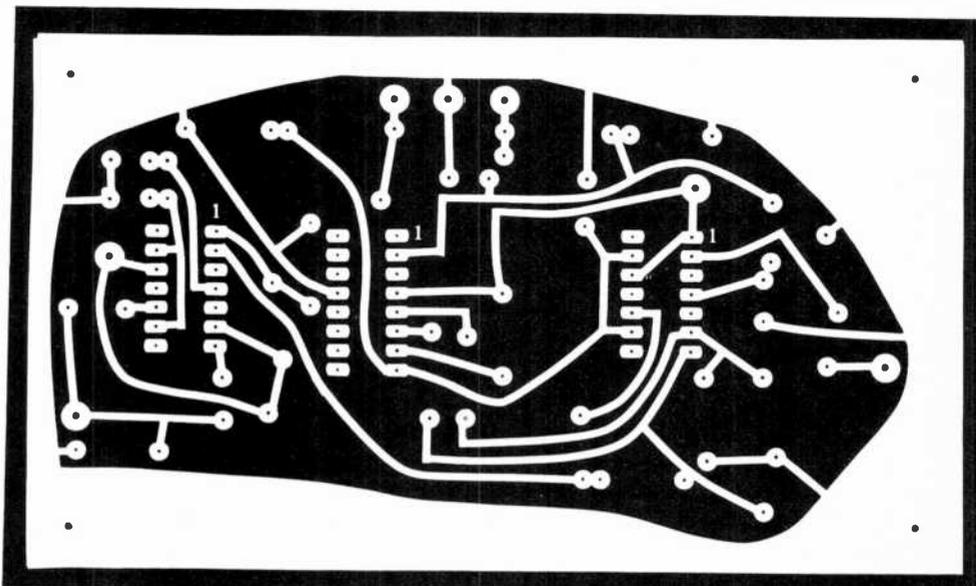

further adjusted and filter Q increased, the dc level will rapidly increase. Eventually, if the Q is set to high, the filter will break into oscillation. When you notice the increase, retune the sine-wave oscillator for a peak dc reading. Read the frequency off the oscillator control dial or with a frequency counter. This is the true center frequency of the filter. It may be somewhat different from the calculated f_c due to component tolerances.

As the Q increases, it will be more difficult to locate the center frequency. The band-pass slope will become very steep, so vary the oscillator frequency very slowly to be sure you are on the very top of the filter peak. Note the voltage level on the scope and adjust the vertical position control so the trace is at some convenient reference position. Retune the oscillator so that it is one-quarter octave above the center frequency you have just measured. The output voltage should decrease.

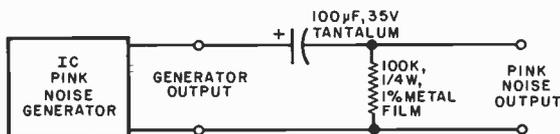


Fig. 13. Modifying the IC pink noise generator for use with the RTA.

Now, adjustments will be made so that the output will be more than 12 dB below that at the center frequency. The ideal value is -18 dB, but it is more critical to adjust the filter for the necessary response. Also, it will then be close to oscillating or ringing when excited by a steep input signal.

Alternately set the oscillator output frequency to the center frequency of the filter and at a frequency one-quarter octave away. Each time you retune the oscillator, trim the Q ADJUST potentiometer to obtain the desired response. You will find that varying this control will change the center frequency gain. Therefore, be sure to reset the center frequency output level to your reference position and/or note the new level. Keep in mind that -12 dB is 0.251 times the center frequency output level, -14 dB is 0.199, -16 dB is 0.159, and -18 dB is 0.128. When the first filter is properly adjusted, move on to the next and repeat the procedure for each remaining filter.

If the log converter has been installed and calibrated, you can use the calibrated dB (vertical) scale on your oscilloscope. Adjust the center frequency output level to equal the maximum reference level at bands 23 and 24 on the right side of the scope trace. Then tune half-way toward the next filter's center frequency and trim the Q for -12 to -18

TABLE II—SELECTING LOG CONVERTER ORIGIN POINT

| Total cm on Scope Face | dB/cm Desired | Total dB | Origin Voltage (volts) |
|------------------------|---------------|----------|------------------------|
| 10 | 2 | 20 | 0.100 |
| 10 | 3 | 30 | 0.031 |
| 8 | 3 | 24 | 0.063 |
| 8 | 4 | 32 | 0.025 |
| 6 | 4 | 24 | 0.063 |
| 6 | 3 | 18 | 0.126 |

Origin volts = $1/\text{antilog}(\text{total dB}/20)$

Example: Scope has 6-cm vertical scale.

4 dB/cm desired yields 24 dB total.

Origin volts = $1/\text{antilog}(24/20)$

= $1/\text{antilog} 1.2 = 1/15.8$

= 0.063 V or 63 mV

dB as read directly on the scope. Try to adjust all filters to the same Q or bandwidth, preferably at -18 dB.

Next, the filter output LEVEL ADJUST potentiometers will be trimmed. The

noise is defined as having equal energy at all frequencies, and is thus represented on a frequency vs. amplitude plot as a straight horizontal line. Pink noise, on the other hand, is wideband noise with an amplitude characteristic that decreases 3 dB per octave.

This Analyzer is a "constant percentage bandwidth" type. That is, the bandwidth of each filter is an unchanging percentage of its center frequency. This implies that, as the center frequency increases, so does the bandwidth. If a white noise input is applied to the RTA, the "flat" signal will show a rising amplitude characteristic (see Fig. 14) as the multiplexer samples the output of higher-frequency filters. However, pink noise has a complementary decreasing characteristic (-3 dB/octave) that produces a flat display on the scope. Pink noise also more closely approximates the energy distribution of natural sounds, and thus is a more accurate source for measurements.

You will also need a microphone to pick up the sounds you want to analyze. (A microphone stand or camera tripod is very useful.) One microphone characteristic that must be known is its random-incidence response. This describes the output signal voltage generated by the

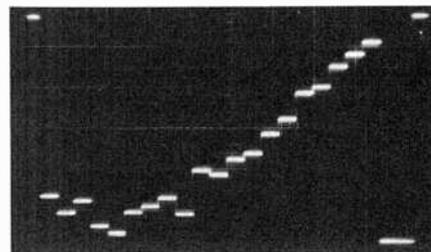


Fig. 14. Typical RTA output on a dc-coupled oscilloscope when "semi-white" noise from an FM tuner is applied to the Analyzer.

best way to do this is to apply pink noise to the AUX input and set the LEVEL ADJUST controls (R75 through R94) to obtain a flat, horizontal scope trace. You can use the pink noise generator which appeared in the July 1977 issue of POPULAR ELECTRONICS, or one of the test records available which have a pink noise cut. If you use the pink noise generator, you must add a high-pass filter (a $100\text{-}\mu\text{F}$ tantalum capacitor and a $47,000\text{-ohm}$ resistor) as shown in Fig. 13. This filter will block the 8.5-volt dc level at the noise generator output, but its cutoff frequency is so low that the spectral content of the pink noise will not be disturbed.

If you don't have a pink noise generator or a suitable test record, here's a "ballpark" adjustment procedure. Find the one-half octave filter center frequency with the lowest output level and adjust the other filter output levels so they equal this minimum. (The variation in filter gain is partly due to the roll-off at high frequencies of the operational amplifiers' open-loop gains.)

Using the RTA. Now that you've built the RTA, how is it used? First of all, you will need a signal or sound source. This can be a frequency-swept oscillator or a wideband noise generator. There are two types of wideband noise. White

microphone when it is placed in a diffuse sound field—the most common type due to the effects of nearby reflecting surfaces. In such a field, the flow of sound energy in any direction is (almost) equally probable.

Several companies, such as General Radio and Bruel & Kjaer, supply microphones with flat random-incidence response, as well as flat 0° (perpendicular) or flat grazing (90°) incidence responses. These measurement microphones are omnidirectional. Unfortunately, most other manufacturers only supply the on-axis (0° incidence) responses of their omnidirectional microphones. This is fine if you want to perform, say, loudspeaker measurements when most of the sound comes from one direction—in the outdoors or in an anechoic chamber. Otherwise, the random-incidence response should be known.

For a high quality, wide bandwidth, omnidirectional microphone, the 70°-incidence response closely approximates the random-incidence response. Suitable dynamic measurement microphones include the AKG Model D160E (calibration curve \$10 extra), the Beyer Model 101 (calibration curve included), the Electro-Voice Models RE55 and 654A (calibration curves \$15 extra), the Shure Model SM76 (no charge for calibration curve) and the Sennheiser Model MD 21N (calibration curve \$1 extra).

Experience has shown that rooms are best equalized first by employing acoustic methods, followed by graphic equalizer adjustments. For example, you should first try repositioning the loudspeakers, modifying the absorption coefficients in the room, and adjusting the loudspeakers' crossover level controls. Only after these steps are taken should you begin to compensate with the equalizer.

Most often, a lack of deep bass and extreme highs will show up on the scope trace. This is usually due to the limitations of dynamic drivers, and is less severe when sub-woofers and electrostatic or piezoelectric tweeters are employed. Don't use your equalizer to try to force flat response at these audio extremes. The results of such attempts frequently include overloaded amplifiers, excessive distortion, and blown voice coils. Remember—equalization should be used only as a last resort, and must not be used with a heavy hand.


There are many other uses for the RTA, as mentioned earlier. Avenues of RTA-aided research include noise pollution analysis, psychoacoustics, and circuit design. ◇

A POWER NOMOGRAPH

BY MARK L. McWILLIAMS

THE NOMOGRAPH shown here can be quite a time saver when designing and/or breadboarding a circuit. It shows at a glance the maximum resistance required to safely pass a given

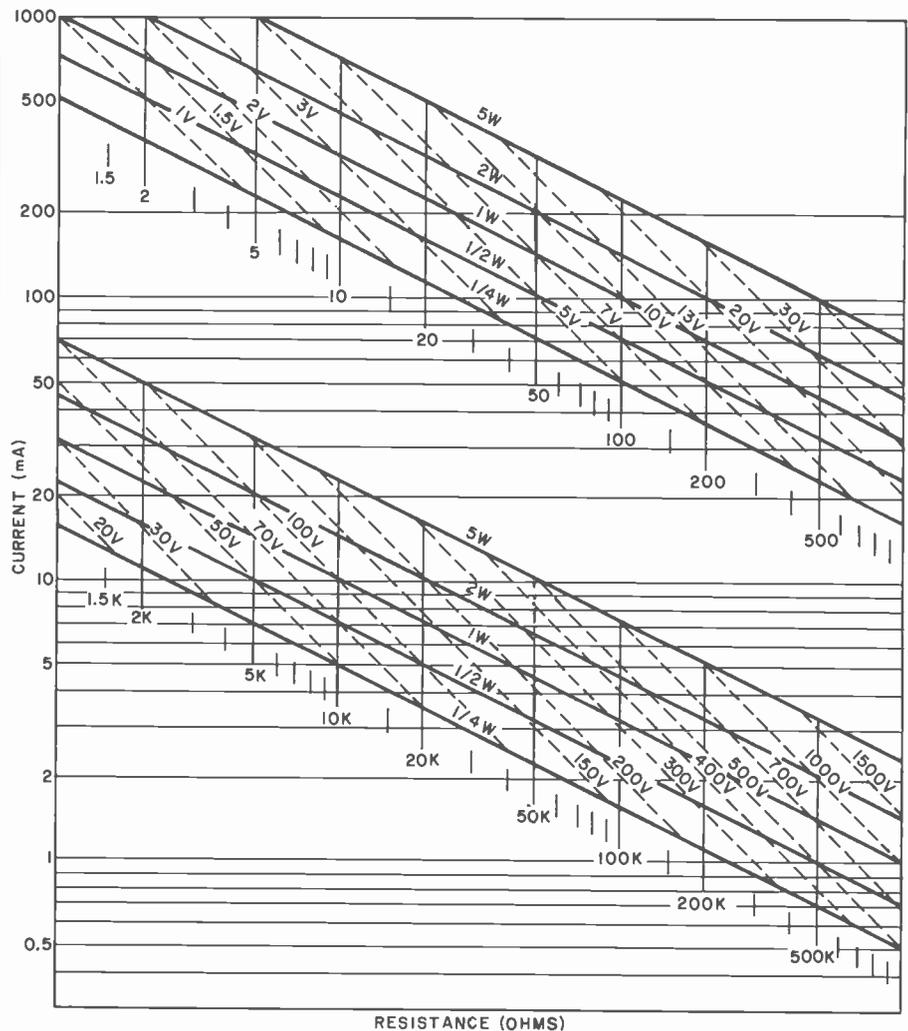current across the ½-watt resistor, we can see that the minimum allowable resistance must be 20,000 ohms. This means that 5 mA of current would flow through the 20,000-ohm resistor at 100 volts.




current as well as the minimum resistance required for a given voltage drop to be applied safely across it. In addition, the nomograph tells what the wattage rating for a given resistor should be, given the voltage and current.

The nomograph is used as follows. Assume a 10-mA current is to be passed through a ½-watt resistor. Referring to the nomograph, we can see that the maximum allowable resistance is 5000 ohms. This would be a 50-volt drop across the resistor. Using another example, if 100 volts were to be applied

Other combinations of voltage, current, resistance, and power rating, keeping two figures constant and determining the third figure, are possible.

The seemingly linear plot of the nomograph can be explained by the fact that the plot is made on log-log paper. From Ohm's Law, $P = I^2R$ (P is power in watts, I is current in amperes, and R is resistance in ohms). Hence, I versus R on log-log paper is a straight line with a slope of $-1/2$. This greatly simplifies plotting and makes it easy to use the nomograph in calculations. ◇

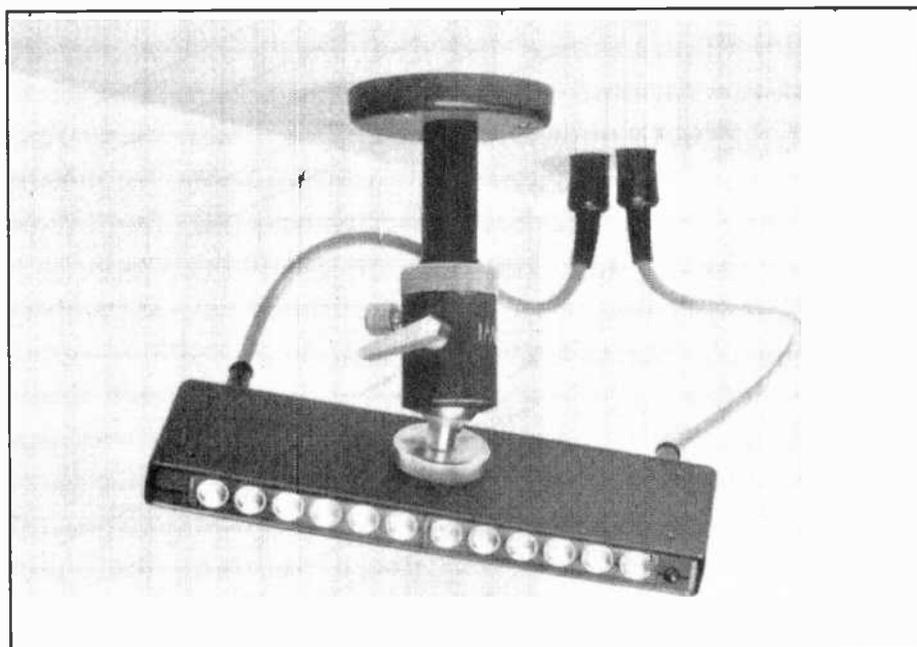Infrared Systems **for** *Wireless Stereo*



Siemens
infrared
radiator
for ceiling
mounting.

IR technology and how receivers and transmitters are used in audio.

BY ARTHUR MAKOSINSKI

UNTIL a couple of years ago, infrared communication devices were almost unheard of in high-fidelity electronics. Then, the availability of relatively inexpensive IR light-emitting diodes that could be conveniently and easily amplitude, frequency, or pulse modulated started manufacturers on a whole new line of audio products for hi-fi. With the introduction of the first IR products, a heretofore untapped area of electronics

technology began to create a revolution in hi-fi listening.

In this article, we will briefly discuss the history of IR communication and the devices that made it possible. Then we will detail some of the audio IR products that have been developed and marketed during the past two years.

A Brief History. Experiments in data transmission and communication using

light beams can be traced back to 1880 and Alexander Graham Bell. But modern work in this area has been concentrated mostly on the use of infrared radiators in line-of-sight communication systems. Early experimental infrared data transmission and voice communication suffered from complexity and high cost insensitive IR detectors and inefficient radiators that often had to be liquid-helium cooled.

Why you should buy a digital multimeter from the leader in digital multimeters.


If you're shopping for your first multimeter, or moving up to digital from analog, there are a few things you should know.

First, look at more than price. You'll find, for instance, that the new Fluke 8020A DMM offers features you won't find on other DMMs at *any* price. And it's only \$169.*

Second, quality pays. Fluke is recognized as the leading maker of multimeters (among other things) with a 30-year heritage of quality, excellence and value that pays off for you in the 8020A.

Third, don't under-buy. You may think that a precision 3½-digit digital multimeter is too much instrument for you right now. But considering our rapidly changing technology, you're going to need digital *yesterday*.

If you're just beginning, go digital.

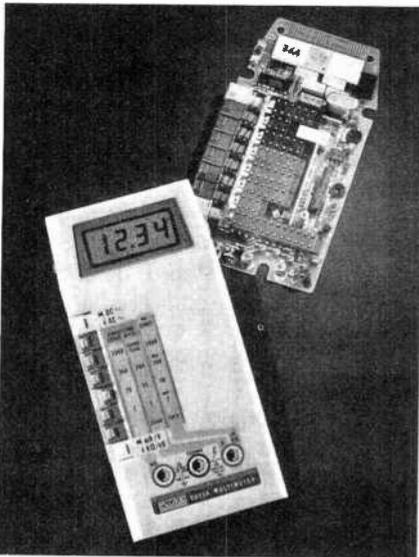

Why not analog? Because the 8020A has 0.25% dc accuracy, and that's *ten*

times better than most analog meters.


Also, the 8020A's digital performance means things like 26 ranges and seven functions. And the tougher your home projects get, the more you need the 8020A's full-range versatility and accuracy. The 8020A has it; analog meters don't.

If you're a pro.

You already know Fluke. And you probably own a benchtop-model multimeter.

Now consider the 8020A: smaller in size, but just as big in capability. Like 2000-count resolution and high-low power ohms. Autozero and autopolarity. And the 8020A is MOV-protected to 6000V against hidden transients, and has overload protection to 300V ac.

Nanosiemens?

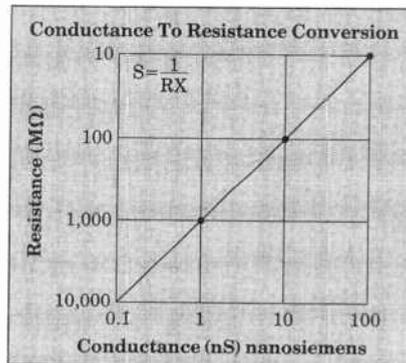

Beginner or pro, you'll find the meter you now have can't measure nanosiemens. So what? With the 8020A *conductance* function, you can measure the equivalent of 10,000 megohms in nanosiemens. Like capacitor, circuit board and insulation leakage. And, you can check transistor gain with a simple, homemade adapter. Only with the 8020A, a 13-oz. heavyweight that goes where you go, with confidence.

What price to pay.



\$169.*

Of course, you can pay more. Or less. In fact, you could pay almost as much for equally compact but more simplistic meters, and get far less versatility. And, the 8020A gives you the 'plus' of custom CMOS LSI chip design, and a minimum number of parts (47 in all). All parts and service available at more than 100 Fluke service centers, worldwide. Guaranteed, for a full year.

Rugged. Reliable. Inexpensive to own and to operate; a simple 9V battery assures continuous use for up to 200 hours.

Where to buy.

Call (800) 426-0361 toll free. Give us your chargecard number and we'll ship one to you the same day. Or, we'll tell you the location of the closest Fluke office or distributor for a personal hands-on feel for the best DMM value going.

*U.S. price only

Fluke 8020A DMM for Home Electronics Experts: \$169



they're here!

the new HEATHKIT® Computers... plus exciting new kits for fall!



GD-1186
Digital
Scale Kit
\$99⁹⁵




AD-1304 Active
Audio Processor Kit \$199⁹⁵



IO-4555 Single-Trace
Experimenter
Oscilloscope Kit
\$299⁹⁵

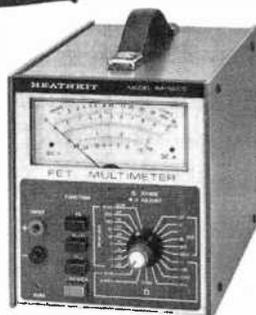IM-5225 Deluxe
FET Multimeter Kit
\$119⁹⁵



The new Heathkit Fall catalog has a lineup of new products for just about every interest. Along with our complete line of personal computer systems and accessories, you'll find interesting and useful products for your home, your hi-fi system, your test or hobby bench. Learn more about these exciting new kits YOU can build — send for your FREE Heathkit catalog today!

NEW H8 8-Bit Computer. The 8080A based machine with the "intelligent" front panel. 9-digit readout and keypad entry make it one of the easiest-to-use personal computers available today!

NEW H11 16-bit Computer. Heath, world leader in kit form products, and Digital Equipment Corporation, world leader in minicomputers, combine to bring you the ONLY 16-bit personal computer priced within reach of the general public. Based on the powerful LSI-11.

NEW H9 CRT Terminal. General-purpose peripheral for use with the H8 or H11 or others. Has long and short-form display, 80-character lines, full ASCII keyboard, auto-scrolling, plot mode and more. An excellent terminal value.

NEW H10 Paper Tape Reader/Punch. Paper tape mass storage peripheral for use with the H8 or H11. Features totally independent punch and reader; a copy mode for fast, easy tape duplication; precision machined punch block for accurate, consistent punching.

NEW GD-1186 Digital Electronic Scale. Tells you your weight (up to 300 lbs.) in big, bright, easy-to-read digits. Reads out to 2/10ths of a pound with far more precision than conventional dial scales. Extra cable lets you mount the readout at eye level.

NEW AD-1304 Active Audio Processor. Minimizes background noise from records or broadcast sources. Also adds 7 dB dynamic range to your hi-fi system. Provides greatly enhanced sound reproduction.


NEW IO-4555 Single-Trace Oscilloscope. A bright, easy-to-read scope ideal for radio-TV servicing, design experiments, general-purpose troubleshooting. Has super-bright trace, easy to operate controls, TV trigger switch, lots more.

NEW IM-5225 deluxe FET Multimeter. Quality general-purpose tester measures AC and DC volts, AC and DC current and resistance. Checks semiconductors in or out-of-circuit too! Has pushbutton function switches, full overload protection, easy-to-read meter with color-coded scales.

H8
8-Bit
Computer Kit
\$375⁰⁰



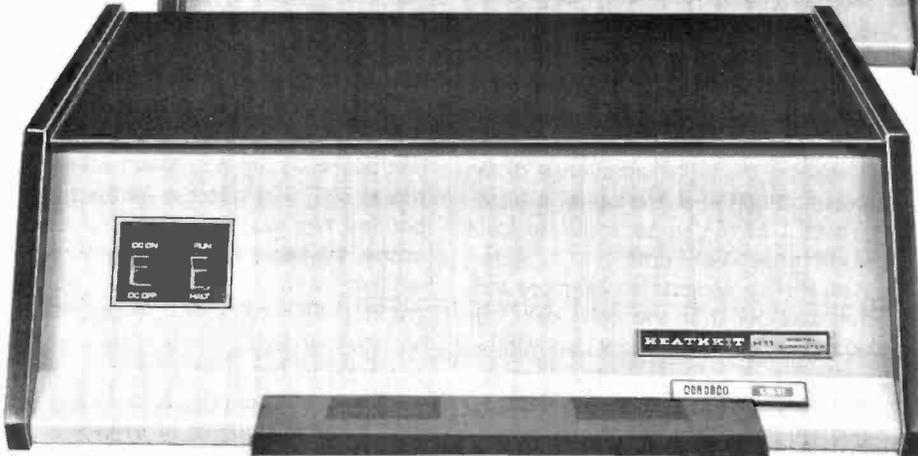ALSO AVAILABLE:
The famous LA36 DEC
Writer II Keyboard Print-
er Terminal at a sensa-
tional low price. **\$1495**



H10
16-Bit
Computer Kit
\$1295⁰⁰



H9
CRT
Terminal Kit
\$530⁰⁰



H10
Paper Tape
Reader/Punch Kit
\$350⁰⁰

FREE

New Heathkit catalog describing nearly 400 fun-to-build, money-saving electronic kits, plus a variety of Heath-recommended top-value assembled products. Send for your FREE copy. Use card or coupon today!

Heath Company, Dept. 010-340
Benton Harbor, Michigan 49022



HEATH
Schlumberger

Heath Company, Dept. 010-340
Benton Harbor, Michigan 49022

Please send me my FREE Heathkit Catalog.
I am not on your mailing list.

Name _____

Address _____

City _____ State _____ Zip _____

CP-130

All prices net FOB, Benton Harbor, Michigan.
Prices and specifications subject to change without notice.

What a Brain!


New Realistic® belt-drive changer with electronic speed control

These days a multi-play turntable can't make it on brawn alone. Not if it's going to cope with the challenges of power "brown-outs," surges, extremely light-tracking cartridges, and the increasingly stiff demands of hi-fi listeners for both performance *and* convenience.

That's why we put an electronic "brain" in the LAB-200. The sophisticated IC chip uses a phase-locked loop oscillator for steady speed despite wide fluctuations in voltage. And it instantly handles your commands for speed change (33⅓ or 45 RPM) and pitch adjustment (±3%) — all with the precision of a far more expensive turntable.

A high-torque, 24-pole synchronous motor provides the muscle for the LAB-200. Its slow-speed design keeps rumble well below audible limits. Wow and flutter: <0.06% WRMS. Rumble: -65 dB (DIN B).

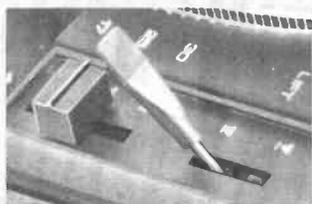
A brain like this belongs on a pedestal, and it is — just look at the ultra-modern base! Check out the amazing Realistic LAB-200 — it's a smart buy at just 119.95.*



Two-way viscous damped cueing raises and lowers arm gently to protect cartridge and records



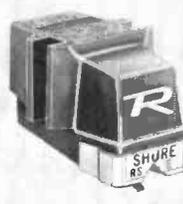Lightweight, dynamically balanced tonearm with counterweight and built-in stylus force gauge



30-20,000 Hz magnetic elliptical cartridge by Realistic/Shure — a \$29.95-value in itself!



Strobe ring with neon lamp helps you make precise settings at 33⅓ or 45 RPM



FREE! New '78 Catalog

Come in for your copy and see what's *really* new in electronics. 164 pages, 100 in full color.


Over 2000 exclusive items.

SOLD ONLY WHERE YOU SEE THIS SIGN:

Radio Shack®

A TANDY COMPANY • FT. WORTH, TX 76102 • 6000 LOCATIONS IN 9 COUNTRIES

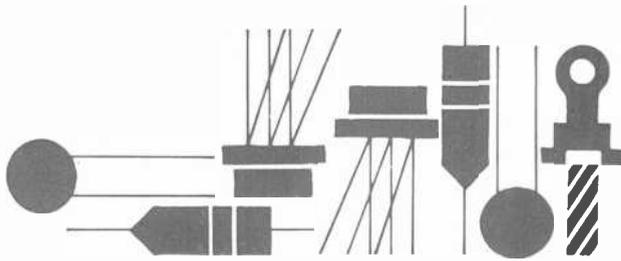*Price may vary at individual stores and dealers. Does not include optional dust cover.



Solid State

By Lou Garner

HOORAY FOR ARRAYS!

COMBINING the flexibility and versatility of discrete devices with the economy and minimum space requirements of integrated circuits, semiconductor arrays offer the best features of both classes. Suitable for a wide range of experimenter and hobbyist projects, arrays consist of two or more devices or circuits in a single package. Each unit in the package may be as simple as a diode or as complex as an operational amplifier. The individual devices may be completely independent, even though assembled on the same substrate, or share an element or connection, such as a common anode, cathode, emitter, collector, power source, or ground terminal.

By strict definition multiple logic circuits, such as dual or quad NAND or NOR gates, flip-flops, latches and multiplexers, may be considered arrays. However, the term generally is reserved for packages containing discrete devices such as diodes and transistors, amplifiers, special function circuits such as timers and comparators, and combinations of these. Semiconductor arrays are available from virtually every major sem-

iconductor manufacturer, including Fairchild, Motorola, National, RCA, Signetics, Siliconix, Intersil, Texas Instruments, Plessey, Sprague, Raytheon, Teledyne and Harris.

Depending on specific type and manufacturer preferences, semiconductor arrays are offered in 8-pin miniDIP's, 8-to-12-pin cylindrical cases, or 14- and 16-pin DIP's, with the latter the most popular. The maximum number of individual devices which can be contained in a single packaged array depends on the number of electrodes per device and on the total number of terminals available. For example, a maximum of seven independent diodes can be provided in a 14-pin DIP, but as many as thirteen may be included if there is a common cathode (or anode) connection. Similarly, only five transistors can be supplied in a 16-pin DIP, but up to seven can fit in the same package if there is a common emitter (or collector) terminal.

Typical diode array package diagrams are shown in Fig. 1. RCA's CA-3039, Fig. 1A, offers six diodes in a 12-pin TO-5 style package, while the firm's CA3019, Fig. 1B, includes a four-diode, full-wave bridge and two independent diodes in a 10-pin case. Ten diodes are grouped as five pairs, three with common cathodes, two with common anodes, in a 16-pin DIP as RCA's CA3141, Fig. 1C. Fairchild's FSA2619M, Fig. 1D, is a typical monolithic diode arrangement in a 16-pin DIP, offering 8 independent diodes similar to the 1N914 and 1N4148. Thirteen diodes are supplied in the FSA2565M, a 14-pin DIP (Fig. 1E), by using a common-cathode connection. Common-anode diode arrays are also available, not only from Fairchild, but from most other manufacturers. Diode arrays can be used in test and musical instruments, communications equipment, control systems, and computers. They are especially useful as part of the drive circuitry for core and matrix memories.

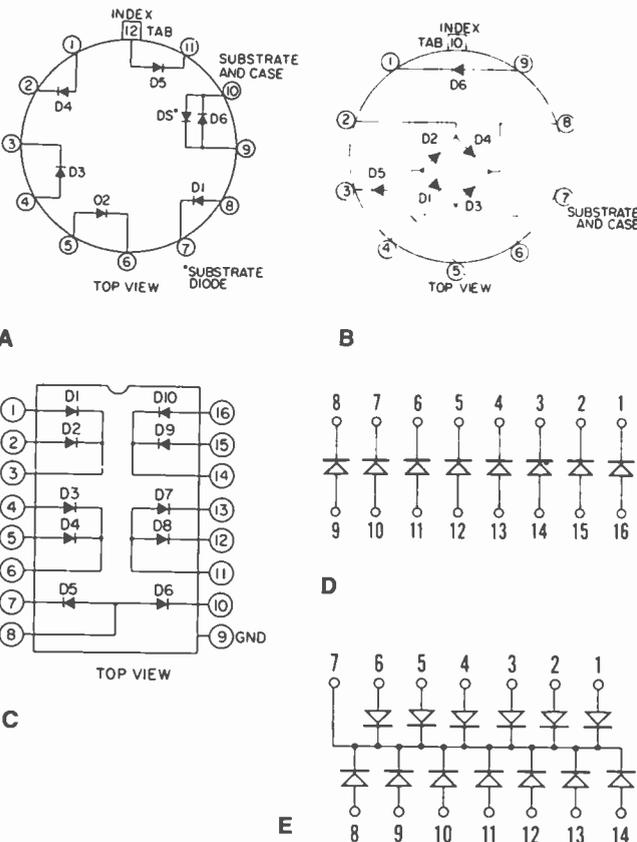


Fig. 1. Typical diode arrays: (A) CA3039; (B) CA3019; (C) CA3141; (D) FSA2619M; (E) FSA2565M.



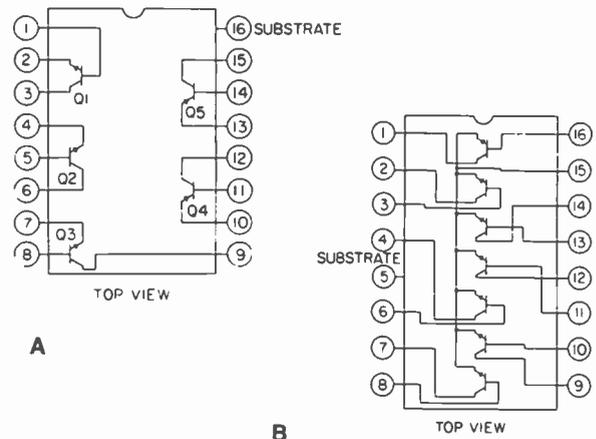


Fig. 2. Transistor arrays: (A) CA3096; (B) CA3081.

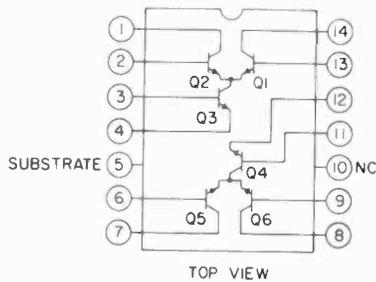

A

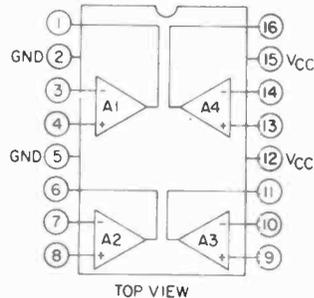

B

Fig. 3. Amplifier arrays: (A) CA3054; (B) CA3048/CA3052.

Representative transistor arrays in 16-pin DIP's are shown in Fig. 2. Three npn (Q_1 , Q_2 , and Q_3) and pnp (Q_4 and Q_5) types are offered in RCA's 5-transistor CA3096, Fig. 2A, while seven npn types are included in the CA3081 by using common-emitter connections, as shown in Fig. 2B. Where independent units are furnished, they can be used in practical applications as if they were discrete devices, provided maximum ratings are observed. In addition, one or more transistors can

be connected as a diode if needed to meet circuit requirements. Where there is a common connection between devices, on the other hand, this must be considered when designing circuits using the array. Common-emitter and common-collector arrays are used extensively as 7-segment LED display drivers, but also can be used in multiple filter, distribution, and output applications.

Semiconductor arrays can feature multiple amplifiers as well as simple discrete devices. Dual differential amplifiers, each consisting of three npn transistors, are offered in RCA's types CA3054 (Fig. 3A), CA3026, CA3049, and CA3102. Of these, types CA3026 and CA3049 are supplied in 12-pin round cans, while types CA3054 and CA3102 are furnished in 14-pin DIP's. Supplied in 16-pin DIP's, similar arrays CA3048 and CA3052 each contain four independent ac amplifiers, as shown in Fig. 3B. Versatile quad op amp arrays, generally in 14-pin DIP's, are available from many sources. Popular types include the LM124/LM224/LM324, LM148/LM248/LM348, and LM2900/LM3900 families, the TL084 series, and the HA4741.

Except where common power and ground connections may cause cross-coupling or feedback problems, the separate units of an amplifier array can be used in the same applications as their individual counterparts. Amplifier arrays are particularly valuable for multi-channel equipment designs, such as stereo and quadraphonic audio systems, color organs, and instrument recorders.

The special semiconductor arrays illustrated in Figs. 4 and 5 are samples of the scores of types offered by various manufacturers. RCA's CA3095, supplied in a 16-pin DIP (Fig. 4A), includes three independent npn transistors (Q_6 , Q_7 and Q_8)

ok® wire wrapping center ok®

**NEW HOBBY WRAP
MODEL BW 630**



Battery
wire
wrapping
tool


\$34.95
ONLY \$29.95
COMPLETE WITH BIT
AND SLEEVE

**STRIP/WRAP/UNWRAP
MODEL WSU-30**




\$5.95*

**RIBBON CABLE
ASSEMBLY**

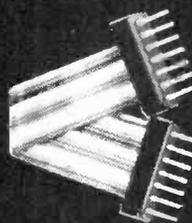

DIP SOCKETS

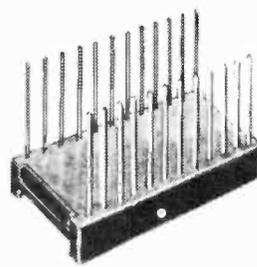

**DIP IC INSERTION
TOOL WITH PIN
STRAIGHTENER**

**MODEL
INS-1416**



\$3.49*

**WIRE DISPENSER
MODEL
WD-30-B**




\$3.45*

**PRE-CUT
PRE-STRIPPED WIRE**



WIRE WRAPPING KIT

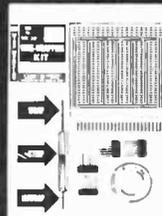

\$15.45*

*MINIMUM ORDER \$25.00, SHIPPING CHARGE \$1.00, N.Y. CITY AND STATE RESIDENTS ADD TAX




OK MACHINE AND TOOL CORPORATION

3455 CONNER STREET, BRONX, NEW YORK, N.Y. 10475 U.S.A.

PHONE (212) 994-6600 TELEX NO. 125091

The better the training the better you'll

Send for
FREE
illustrated
career
guide

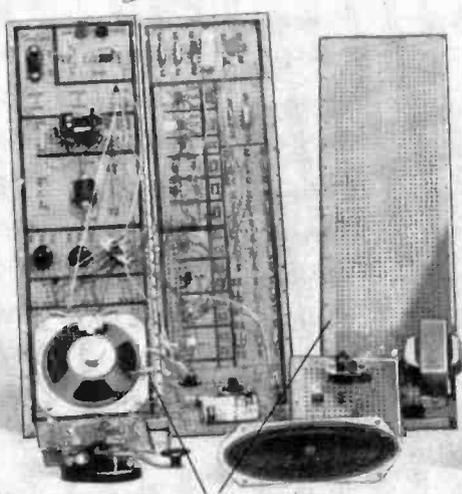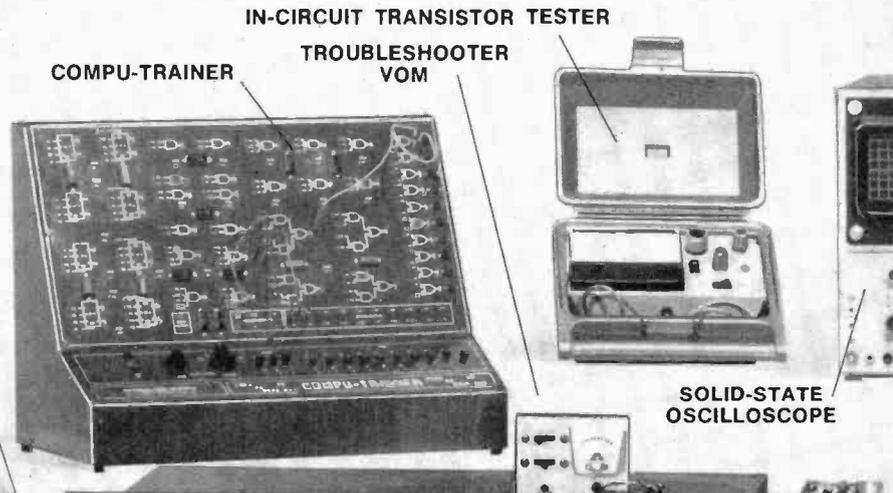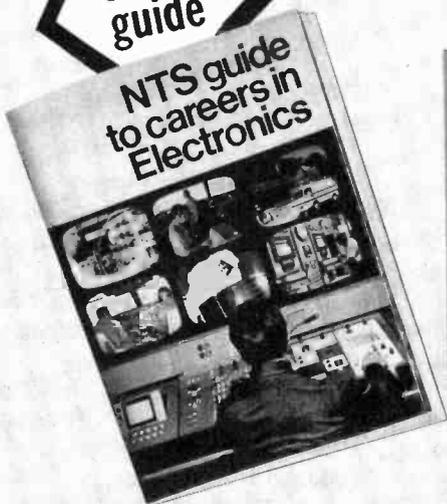

(Simulated TV Reception)

ELECTRO-LAB

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath GR-2001 computerized color TV (25" diagonal)** with varactor diode tuning and digital read-out channel selection; (optional programming capability and digital clock avail.).

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multi-meter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

and the equipment be equipped.

COMPARE OUR
KITS AND LESSONS.
COMPARE OUR
TUITION.



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL

APPROVED FOR VETERAN TRAINING

Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 205-107
4000 South Figueroa St., Los Angeles, Calif. 90037

Please send FREE Color Catalog and Sample Lesson.
NO OBLIGATION. NO SALESMAN WILL CALL.

- | | |
|---|--|
| <input type="checkbox"/> Color TV Servicing | <input type="checkbox"/> Electronics Technology |
| <input type="checkbox"/> B & W TV and Radio Servicing | <input type="checkbox"/> Computer Electronics |
| <input type="checkbox"/> Electronic Communications | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> FCC License Course | <input type="checkbox"/> Audio Electronics Servicing |

NAME _____ AGE _____

ADDRESS _____ APT # _____

CITY _____ STATE _____

Please fill in Zip Code for fast service

- Check if interested in G.I. Bill information.
 Check if interested ONLY in classroom training in Los Angeles.

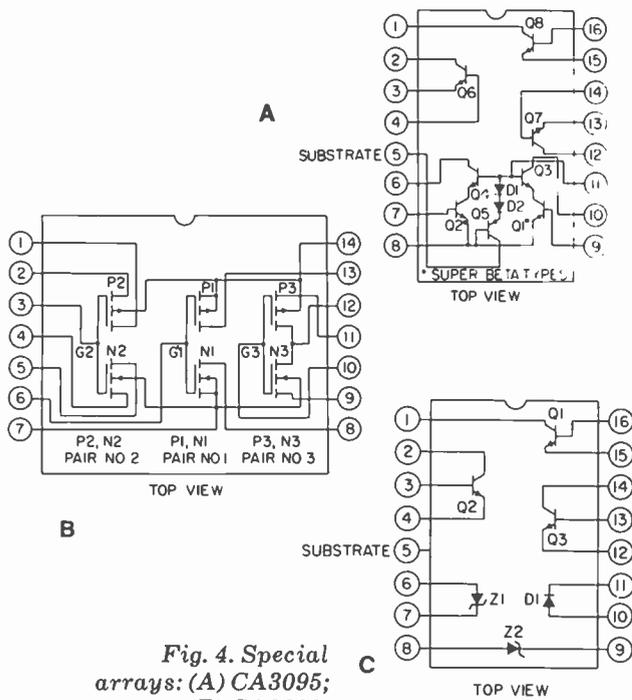


Fig. 4. Special arrays: (A) CA3095; (B) CA3600; (C) CA3093.

and a differential cascode amplifier using super-beta devices. It is especially useful as a high impedance transducer amplifier or in long-interval timer applications.

Three COS/MOS transistor pairs are featured in the CA3600, Fig. 4B, with each stage offering a typical gain of 32 dB and an input impedance of 100 Gohms. The CA3093, Fig. 4C, contains three npn transistors, Q1, Q2, and Q3, two 7-volt zeners, Z1 and Z2, and a general-purpose diode, D1.

Each member of Motorola's MC1411 array family (MC1411/12/13/16) comprises seven npn high-gain Darlington transistors with integral suppression diodes in a 16-pin DIP, as shown in Fig. 5. With relatively high voltage and peak current ratings, these arrays can be used as drivers for incandescent lamps, relays or printer hammers. Finally, Hewlett-Packard's HCPL-2770 array offers four independent optocouplers in a single 16-pin package. Each section has a 1500-V dc insulation voltage rating and requires an input current of only 0.5 mA. The input elements are GaAsP LED's and the outputs are photodiodes coupled to modified high-gain npn split Darlington pairs.

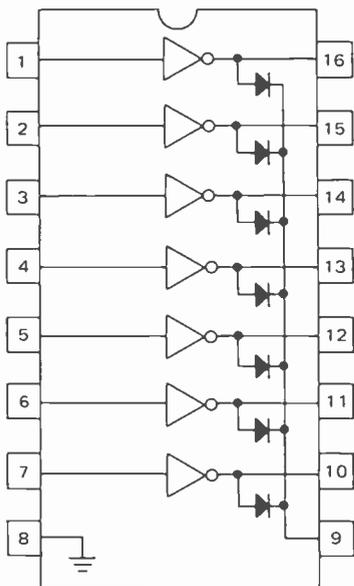


Fig. 5. Another special array: the MC1411 family.

Array Applications. The potential applications for semiconductor arrays are virtually unlimited. Generally, the separate elements of such arrays can be used in the same applications as their corresponding discrete or individual IC counterparts as long as maximum ratings are observed. However, arrays usually require less space and volume than their discrete counterparts and are frequently less expensive. In addition, the special combinations found in some arrays offer unique project possibilities. Representative of the hundreds of designs possible with semiconductor arrays are the circuits shown in Fig. 6.

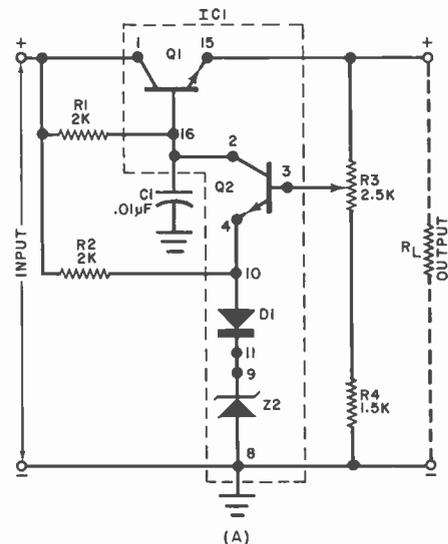


Fig. 6. Array applications: (A) Temperature compensated series regulator; (B) Frequency comparator.

Featuring a CA3093 (IC1), the temperature-compensated series voltage regulator in Fig. 6A requires only five additional components—three half-watt resistors, a low voltage ceramic capacitor, and a potentiometer. Designed to accept an unregulated dc input of 18 volts, the regulator can supply a regulated output of 8.5 to 15 volts, depending on the setting of R3. If adjusted for 12 volts output, the temperature regulation is 0.009%/°C, while the load regulation is ±0.4% from 0 to 40 mA and the typical line regulation is ±0.45%/V. The circuit can be used as part of an overall power supply design or assembled as an "add-on" accessory for an existing supply.

An audio frequency comparator circuit (Fig. 6B) using the CA3096 5-transistor array is designed for operation on a 10-V dc supply. Accepting input signals up to 10 kHz (f1 and f2), the circuit develops an output voltage which varies from a median level of 5 volts proportionally to the relative difference in frequencies. In operation, the output remains at 5 volts if the two input signals have the same frequency, rising if f1 is greater

than f2 and dropping below this level if f2 is greater than f1. Four of the transistors in the array (Q1, through Q4) serve as conventional amplifiers with the fifth (Q5) used as a diode by connecting its collector (pin 15) and base (pin 14) terminals together. One external diode, D1 (type 44003), is required to complete the circuit. Among its possible applications, the frequency comparator can be used in test instruments, as a second demodulator in FM/FM telemetry systems, and in communications equipment.

Reader's Circuit. Intended for checking TTL circuits, the logic test probe shown in Fig. 8 was contributed by reader David K. Merriman (Lockheed Electronics Co., Las Cruces, NM 88001). The probe will provide a visual readout of a low logic state as a "0" and of a high logic state as a "1," while identifying a pulse train as "P."

Easily assembled in a single evening, the project requires one section of a 7402 quad NOR gate, IC1, a 7-segment numeric LED display, two half-watt resistors, R1 and R2, plus mounting hardware, wire, etc. The unit derives its dc operating power from the equipment under test, as do most logic probes. Terminal 1 is connected to display segments a, b, f and g, while terminal 2 is connected to segment e, or vice versa, depending on whether a common-cathode or common-anode type display is used.

The series current limiting resistor values (R1 and R2) are calculated by dividing the difference between the dc supply

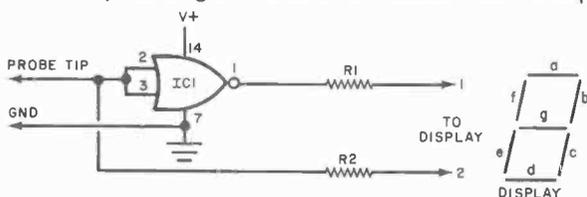


Fig. 8. Reader's logic probe circuit.

voltage (generally 5 V) and the rated display voltage by the total drive current required by the LED segment(s). These currents range, typically, from less than 5 to as much as 20 mA per segment, depending on the display used. The lower current types are preferred to avoid overloading the NOR gate or test circuit.

In operation, the display is connected so that segments a, b, f and g are activated when a logic zero level is applied to the probe tip, forming a 0, with segment e activated when a high logic level is applied, forming a 1. When a pulse train is applied, the 0 and 1 segments are activated alternately, with persistence of vision blending the two together to form a P.

Device/Product News. If you're working with high-frequency circuits, you should be interested in the new products recently announced by the Amperex Electronic Corporation (Hicksville, NY 11802). First, the firm has introduced a new line of uhf power transistors. Types BLW79, BLW80 and BLW81 offer r-f power gains of 10, 9 and 7 dB with power outputs of 2, 4 and 10 watts, respectively. Each transistor can withstand VSWR's of 50:1 with high line voltage and 20% overdrive at a heatsink temperature of 70°C. All three are for operation in the mobile frequency band of 380 to 512 MHz at collector voltages of 12.5 volts. Available in either flange or stud packages, unit prices range from \$5.25 to \$7.90.

Amperex is also offering a new line of vhf amplifier modules containing internal matching networks for broadband applications. Identified as types BGY32 and BGY36, the units are de-

(Continued on page 118)

MAKE GREAT CONNECTIONS!



IC INTERCONNECT ASSEMBLIES

26 Ga. Ribbon Cable



IC SOCKETS

3 Level Wire Wrap Gold

| | | |
|------------|-------|--------|
| 1-9 | 10-24 | 25-100 |
| 14pin .38 | .37 | .36 |
| 16pin .42 | .41 | .40 |
| 18pin .73 | .65 | .59 |
| 24pin 1.00 | .91 | .83 |
| 40pin 1.69 | 1.51 | 1.37 |

Low Profile D.I.P. Solder tail. (TIN)

| | | |
|-----------|-------|--------|
| 1-9 | 10-24 | 25-100 |
| 8 pin .15 | .15 | .14 |
| 14pin .18 | .17 | .16 |
| 16pin .20 | .19 | .18 |
| 18pin .27 | .26 | .25 |
| 20pin .29 | .28 | .27 |
| 22pin .35 | .34 | .33 |
| 24pin .36 | .35 | .34 |
| 28pin .42 | .41 | .40 |
| 40pin .60 | .57 | .53 |

SINGLE END

| | | | | | | |
|--------|------|------|------|------|------|------|
| 14 pin | 6" | 12" | 18" | 24" | 36" | 48" |
| 14 pin | 1.51 | 1.62 | 1.77 | 1.83 | 2.05 | 2.26 |
| 16 pin | 1.64 | 1.74 | 1.87 | 1.99 | 2.21 | 2.44 |
| 24 pin | 2.49 | 2.69 | 2.88 | 3.08 | 3.48 | 3.87 |

DOUBLE END

| | | | | | | |
|--------|------|------|------|------|------|------|
| 14 pin | 2.76 | 2.87 | 2.97 | 3.08 | 3.30 | 3.51 |
| 16 pin | 3.01 | 3.13 | 3.24 | 3.36 | 3.58 | 3.81 |
| 24 pin | 4.55 | 4.75 | 4.94 | 5.14 | 5.54 | 5.93 |

DUAL-IN-LINE PLUGS



Use for mounting diodes, resistors, jumpers, etc.

| | | | | |
|--------|--------|--------|------|-------|
| PLUGS | | COVERS | | |
| 8 pin | 1-24 | 25-49 | 1-24 | 25-99 |
| 14 pin | .46 | .39 | .10 | .09 |
| 16 pin | .48 | .40 | .10 | .09 |
| 18 pin | .56 | .47 | .10 | .09 |
| 24 pin | .79 | .72 | .15 | .13 |
| 40 pin | \$1.23 | \$1.08 | .25 | .22 |

S-100 BUS (2 X 50) CONNECTORS



Highest quality connectors for the popular S-100 bus card edge systems. 2 x 50, .125" pin spacing with .25" row spacing for IMSAI and most other machines. Will not fit ALTAIR. Available in gold or NASGLO finish. NASGLO is a new tin-nickel process which has contact properties similar to precious metal. Bodies are rugged polyester, not Bakelite as in some connectors.

Our solder-tail sockets have heavy square pins. No fold-over problem on insertion.

| | | |
|----------------|-----------------------|-----------------------|
| PCC-100WW-G... | (Gold, wire wrap) | \$4.50, 4 for \$17.00 |
| PCC-100ST-G... | (Gold, solder tail) | \$4.50, 4 for \$17.00 |
| PCC-100WW-N... | (NASGLO, wire wrap) | \$3.75, 4 for \$14.00 |
| PCC-100ST-N... | (NASGLO, solder tail) | \$3.75, 4 for \$14.00 |

| | | |
|------|------|---------------------|
| 7805 | 7905 | VOLTAGE REGULATORS. |
| 7806 | 7906 | 1A |
| 7808 | 7908 | In TO-220 |
| 7812 | 7912 | 95¢ - 5/\$4.50! |
| 7815 | 7915 | |

TRI-tek, inc.

6522 R NORTH 43RD AVENUE,
GLENDALE, ARIZONA 85301

MASTER CHARGE/BAC (602) 931-6949

50V, 3Amp Epoxy Bridge

Repeat of popular sell-out. Heavy silver leads.

BR-503...79c

Minimum Order. USA, \$10
Foreign, \$15 in US Funds.
Surface Shipping Prepaid.
Add 50c insurance

SEND FOR FREE CATALOG

CIRCLE NO. 59 ON FREE INFORMATION CARD

**1977
CITIZENS
BAND
HANDBOOK**



CITIZENS BAND HANDBOOK, by the editors of **POPULAR ELECTRONICS**, has it all... all the authoritative information you need on CB two-way radios to make an intelligent buying decision for transceivers, antennas and accessories. Here's a partial look at what the experts have packed into one volume.

- You'll have over 500 CB models at your fingertips, fully described with technical specifications, features, latest prices and photographs.
- The latest 40 channel CB transceivers, antennas and accessories are covered in detail.
- An expert evaluates new 40-channel CB radio power and performance.
- Manufacturers' specifications are "decoded" so anyone can read a "spec" sheet.
- What to look for when buying a transceiver.
- Mobile antenna types and performance judgments.
- How to sound like a CB pro when you're transmitting.
- Tips on eliminating ignition interference.
- How to prevent CB theft.

This packed-with-information Handbook is the CB publication you've been waiting for. Only \$1.95!


CITIZEN'S BAND HANDBOOK
Consumer Service Division
595 Broadway, N.Y., N.Y. 10012

PE-107

Please send the 1977 CITIZENS BAND HANDBOOK. I'm enclosing \$2.50.* (\$1.95 plus 55c for postage and handling.) Outside U.S.A. \$3, postpaid.

Print Name _____
Address _____
City _____ State _____ Zip _____

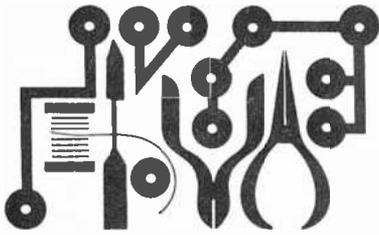*Residents of CA, CO, FL, IL, MI, MO, NY STATE, DC and TX add applicable sales tax. (Postage and handling charges non-taxable.)



Experimenter's Corner

By Forrest M. Mims

IC VOLTAGE REGULATORS

Batteries are ideal for powering portable electronic equipment, but you should think twice before using them to power anything within reach of an ac power outlet. Why? To save money! Electricity from batteries is much more expensive than electricity from a wall socket.

Batteries are rated in ampere-hours (AH). A 1-AH battery, for example, can deliver a current (I) of 1 ampere for 1 hour before its voltage (E) falls below a specified level. If the battery puts out 1 ampere at 1 volt, it delivers 1 watt of power ($P=EI$).

Now let's convert this analysis into dollars and cents by applying it to a typical 1.5-volt alkaline "C" cell rated at 5 AH. You can buy such a cell at a dis-

signed for radios, tape recorders, shavers, and calculators. These adapters are compact—usually housed in a molded enclosure with the ac power plug—and are ideal for applications requiring unregulated voltage at moderate current

even be used to improve the operation of the first two. It's the integrated circuit voltage regulator. Many computer hobbyists and manufacturers place several IC voltage regulators "on-card" to provide regulated power for each of several circuit boards in a computer system. IC voltage regulators are also useful as power supplies for solderless prototyping breadboards.

IC voltage regulators are ideal for use even with comparatively simple circuits and projects. Many have only three connection terminals or pins: input, output, and common. This makes them easy to use—even though the IC chip may contain dozens of transistors, resistors, and diodes. For example, Fig. 1 shows the amazing simplicity of a typical IC voltage regulator circuit. Anyone who has tried to design and build a precision regulator with an automatic shutdown capability

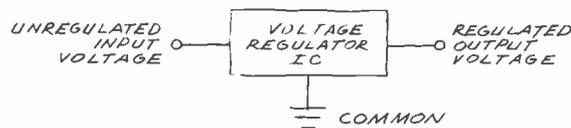


Fig. 1. Basic 3-terminal IC voltage-regulator power supply circuit.

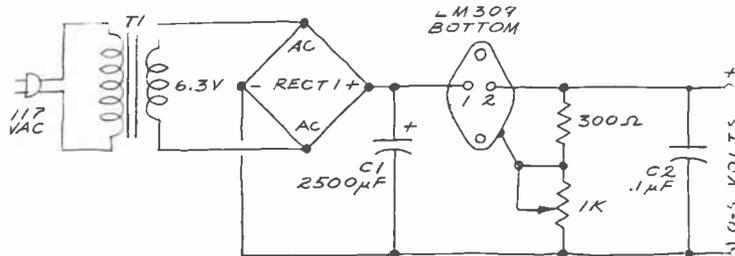


Fig. 2. Five-volt TTL power supply.

count house for about 65¢. Neglecting any internal voltage drop, the cell has a potential power output of 7.5 watts over its useful life. This means an equivalent cost of \$86.67 per kilowatt-hour for electricity from the battery! That's over a thousand times more costly than electricity supplied by power companies.

There are at least two ways to avoid the high cost of battery power. One is to use rechargeable nickel-cadmium or lead-acid storage cells instead of the expendable variety. You can charge the cells with a commercial charger or with solar energy. (See "Experimenter's Corner," November 1976.) Another alternative is to use one of the inexpensive, unregulated power supply adapters de-

signed for radios, tape recorders, shavers, and calculators. These adapters are compact—usually housed in a molded enclosure with the ac power plug—and are ideal for applications requiring unregulated voltage at moderate current

levels. Most adapters have output leads terminated with some type of small plug. If you attach appropriate jacks to each of your projects, you can use the same adapter to power each project. What's more you can quickly disconnect the adapter from one circuit and apply it to another by unplugging the output leads from one and plugging it into the other.

There's a third alternative which can

can appreciate the engineering sophistication provided by these chips.

5-Volt TTL Supply. Some TTL devices (the 7441 decoder for example) are designed to tolerate as much as 70 volts on their output lines, but all TTL chips require a single power supply voltage of 5 volts, plus or minus a quarter of a volt.

Several IC voltage regulators are designed to deliver a regulated 5-volt output. One is the LM309, a readily available regulator which can accept up to 35 volts at its input. The LM309 is available in both TO-39 and TO-3 cases. The latter package will dissipate more than 3 watts at room temperature without a heatsink and more than 10 watts with the addition of a Wakefield 680-75 heatsink. If these power levels are exceeded, an automatic sensor circuit will detect the resultant increase in chip tem-

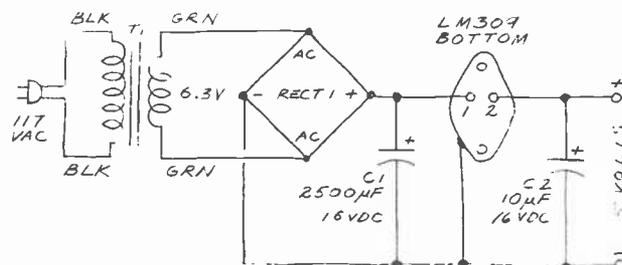


Fig. 3. Variable 0-5-volt power supply.

perature and shut down the regulator to protect it from damage.


Figure 2 shows how to use the LM309 in a simple TTL 5-volt power supply. Transformer *T1* is a 6.3-volt filament transformer which reduces the line voltage to a practical level and provides line isolation. Modular bridge rectifier *RECT1* converts alternating current into pulsating direct current. Any 60-to-200-PIV bridge, such as Radio Shack 276-1147 can be used. Capacitor *C1* filters the rectifier output into a reasonably ripple-free voltage which is applied to the input of the regulator IC. The regulated voltage appearing at the IC's output pin is 5.05 volts plus or minus 0.2 volt.

You can assemble this circuit on a small perforated board in under an hour using readily available components. Since the circuit is line powered, use care in connecting the power supply cord to the primary (black) leads of *T1*. You'll have a safer circuit if you mount *T1* on the board with 6-32 hardware. Insert the free end of the power cord through a hole drilled in the board near *T1*, and tie a knot a few inches from the end of the cord. Then solder the free end of the cord to the two black leads of *T1* and carefully insulate the connections with heat-shrink tubing or several layers of black electrical tape.

Variable-Voltage Supply. You can convert the fixed 5-volt supply in Fig. 2 to a variable 0-to-5-volt supply by adding a voltage divider as shown in Fig. 3. The result is handy for experimenting with LED's and other low-voltage components and circuits.

Other IC Voltage Regulators. IC voltage regulators with outputs of from 5 to 24 volts are readily available from many of the parts suppliers who advertise in POPULAR ELECTRONICS. Chances are one of these regulators can be used to power almost any IC circuit or project you have in mind. For example, the 78L12 will deliver 12 volts plus or minus half a volt at a current up to 100 milliamperes. The 78L12 is part of a series of three-terminal regulators with a wide range of regulated voltage outputs.

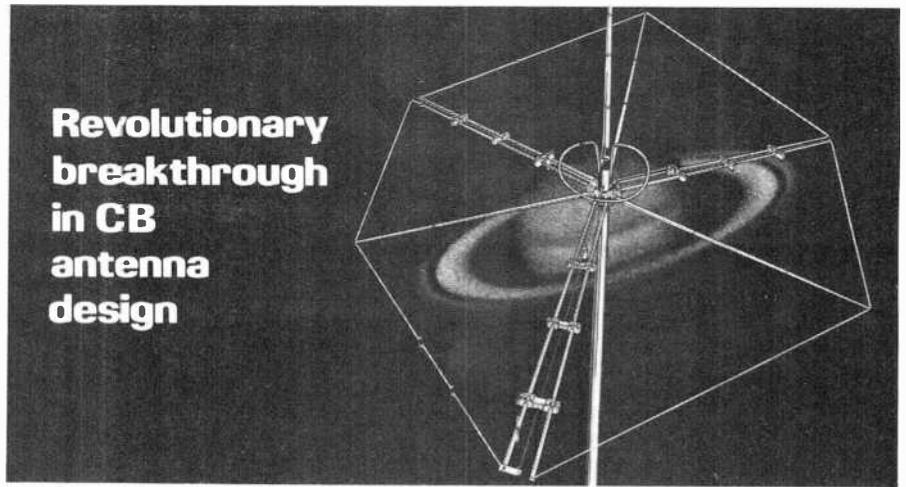You can get lots of design tips and application ideas about using voltage regulator IC's from manufacturer's data sheets and the excellent data books which are available. One such book is National's "Voltage Regulator Handbook." You'll soon find that IC voltage regulators can increase the reliability of your circuits while saving you a bundle of battery money. ◇




Revolutionary breakthrough in CB antenna design

AVANTI Invents the Saturn™ Base

The reason the "Saturn" is so revolutionary is that it is absolutely the only combination vertical and horizontal omni-directional antenna. That's right, it needs no rotor! You can pick up mobiles (which are vertical) or horizontal and vertical beams.

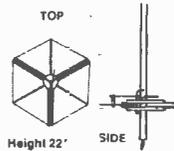The "Saturn", invented after years of research by Avanti engineers, is the latest development using



Height 22'
Radials 9'
Weight 25 lbs.
Omni-directional — No rotor
AV-501 Switchbox included
PATENT PENDING

AVANTI's unique CO-INDUCTIVE principle to give you the performance of two antennas combined into one.

The P.D.L. and Moonraker made dual polarity famous as the only antennas to have during the last sun spot cycle, and this time around any serious C.B.'er will want to have the "Saturn".

Avanti makes a complete line of high performance base and mobile CB antennas from \$11.95 to \$404.00. Write today for free catalog.

avanti

AVANTI RESEARCH AND DEVELOPMENT, INC.
340 Stewart Avenue, Addison, IL 60101

© Copyright 1977, all rights reserved

Creators of the famous



CIRCLE NO 8 ON FREE INFORMATION CARD

BUILD YOUR OWN

BIG SCREEN COLOR TV!

- Sporting Events Are An Experience As Exciting as Being There!
- Movies Are Seen The Way They Were Meant To Be Seen!
- Ping And Other Video Games Are More Exciting Than Ever!
- Can Be Used With Video Tape Playback Equipment!

YOU ASKED FOR IT!

THE NEW LIFESCREEN II

WE HAVE RECEIVED THOUSANDS OF INQUIRIES!

YOU REQUESTED PLANS FOR A BIG SCREEN TV THAT WOULD: utilize any portable TV as an image source — require a minimum of floor space — be a beautiful piece of furniture.

NOW — EXTRON IS HAPPY TO ANNOUNCE

THE ORIGINAL LIFESCREEN I



The SELF-CONTAINED internal projection TV that will utilize any transistor portable TV (12" to 19") . . . requires only 2 x 4 feet of floor space — fits neatly against any wall . . . and lends its beauty to the decor of any room.

COMPONENT LIST

- 1 set of LIFESCREEN II Plans
- 1 Portable transistor Color TV (12" to 19")
- 1 LIFESCREEN Lens
- 2 LIFESCREEN Front Surface Mirrors: one 8" x 10" and one 14" x 20"
- 1 EXTRON LS 50 Screen, 32" x 40" / 50" Diag.

The LIFESCREEN was designed for the Do-It-Yourself enthusiast who wishes to have the enjoyment and excitement of a professional Big Screen TV — but refuses to pay the \$1500 to \$4000 that most manufacturers charge for this luxury.

FACTS

The special LIFESCREEN Lens and Front Surface mirror supplied by Extron are the same type used by major Big Screen TV manufacturers (Sony, Muntz, etc.). THESE PROFESSIONAL COMPONENTS SHOULD NOT BE CONFUSED WITH THE CHEAP PLASTIC MAGNIFYING IMITATIONS NOW FLOODING THE MARKET BECAUSE OF THE POPULARITY OF BIG SCREEN TV.

The EXTRON TV Screen — the same used by the major Big Screen TV manufacturers — is 16 TIMES BRIGHTER than a flat matte surface and 6 TIMES BRIGHTER than most flat beaded movie screens. Its parabolic shape rejects extraneous light, concentrating a highly efficient and directionally selective television image that is exceptionally sharp and colorful.

COMPLETE LIFESCREEN II

\$299

COMPLETE LIFESCREEN I

\$269

The INDEPENDENT projection system that can be used with ANY SIZE screen up to 80" Diagonal — one of the many reasons for its tremendous success.

COMPONENT LIST

- 1 set of LIFESCREEN I Plans
- 1 Sharp 13" Model 13A21 Color TV or Sony 15" Model KV-1541R Color TV
- LIFESCREEN Lens
- LIFESCREEN Front Surface Mirror, 8" x 10"
- EXTRON LS 50 Screen 32" x 40" / 50" Diagonal

LARGER SCREENS can be ordered through EXTRON (67" or 80" Diag.)

THE EVERYTHING GUARANTEE

EXTRON GUARANTEES EVERYTHING: THE PROFESSIONAL QUALITY, ACCURACY OF DESCRIPTION, AVAILABILITY AND PROMPT DELIVERY OF COMPONENTS DESCRIBED IN THIS AD. If, after building your LIFESCREEN PROJECTION SYSTEM, you are not satisfied for any reason, return all components to EXTRON, 8831 Sunset Boulevard, West Hollywood, California for instant refund of the purchase price.

- PLEASE RUSH ME ONE COMPLETE SET OF LIFESCREEN I PLANS . . . @ \$9.00
- PLEASE RUSH ME ONE COMPLETE SET OF LIFESCREEN II PLANS . . . @ \$9.00

PLEASE ALSO SEND ME THE ITEMS CHECKED BELOW:

- LIFESCREEN LENS . . . @ \$150.00
- LIFESCREEN FRONT SURFACE MIRROR, 8" x 10" . . . @ \$20.00
- LIFESCREEN FRONT SURFACE MIRROR, 14" x 20" . . . @ \$30.00
- EXTRON LS 50 SCREEN 32" x 40" / 50" Diagonal . . . @ \$90.00

- COMPLETE LIFESCREEN I PACKAGE . . . @ \$269.00
- COMPLETE LIFESCREEN II PACKAGE . . . @ \$299.00



EXTRON LIFESCREEN® PROJECTION SYSTEM
8831 Sunset Boulevard,
West Hollywood, California 90069

Name _____ Address _____
City _____ State _____ Zip _____
CARD NAME _____ CARD NUMBER _____ EXPR. DATE _____

All Prices F.O.B. factory — Cal. residents add 6% sales tax.

TOTAL: \$ _____

INFO PAK — 50c



CIRCLE NO 20 ON FREE INFORMATION CARD



By John McVeigh

Have a problem or question on circuitry, components, parts availability, etc? Send it to the Hobby Scene Editor, POPULAR ELECTRONICS, One Park Ave., New York, N.Y. 10016. Though all letters can't be answered individually, those with wide interest will be published.

TIMER IC INFO

Q. Can you provide any information on using the LM322 precision timer?—Rene Buteau, Quebec, Canada.

A. The LM322 can operate with unregulated supplies from 4.5 to 40 V, maintaining constant timing over a wide range of periods. The output of the timer is a floating transistor with current limiting. It can drive either ground- or supply-referenced loads up to 40 V and 50 mA. This floating output offers the user great flexibility in circuit design. Also included is an on-chip "logic reverse" circuit that can be programmed by the user to have the output transistor either on or off during the timing period. The trigger input has a 1.6-volt threshold (independent of supply voltage), but is protected against inputs as large as ± 40 volts, even when a 5-volt supply is used. The IC reacts only to the rising edge of the trigger signal, and is immune to any trigger pulse during the timing period.

An internal 3.15-volt regulator keeps the timing period independent of supply fluctuations and provides the user with a

convenient reference. External loads drawing up to 5 mA can be driven by the regulator. An internal 2-volt divider between the reference and ground provides a timing period of $T = RC$. This timing period can be voltage controlled by driving the divider from an external source through the V_{ADJ} pin. Timing ratios of 50:1 can be achieved. The LM322's internal comparator has a 300-pA typical input bias current over a common-mode range of 0 to 3 volts. A boost terminal allows the user to increase comparator operating current for timing periods less than 1 millisecond. This allows the timer to function over a 3- μ s to multi-hour timing range.

Some circuits using the LM322, from the National Semiconductor catalog, are shown. At A, is a basic timer with the output taken at the emitter of the floating transistor. A basic timer with collector output is shown at B. A timer with collector output and manual reset and cycle end is illustrated at C, and a timer triggered by the negative edge of the trigger pulse is shown at D.

FINDING VARIABLE CAPACITORS


Q. I have searched high and low, but have not been able to find anyone who stocks or manufactures three-section, 10-to-365-pF "variable condensers." I'm very surprised by this. A few years ago I could find these condensers anywhere. Do you know of any parts distributors who carry them?—Jerry John Raimondo, Astoria, NY.

A. Variable capacitors are getting very scarce. Many of the companies that used to make them (e.g. Hammarlund) are no longer in business. Accordingly, you'll have the greatest chance of finding the parts you're looking for at a surplus outlet. (Since you are near Manhattan, try the electronics dealers on Canal Street or Barry Electronics at 512 Broadway.) Also, procure a copy of the catalog published by Fair Radio Sales Co., 1016 E. Eureka Street, Box 1105, Lima, OH 45802. Fair Radio carries a large line of surplus equipment and components.

ADJUSTABLE REVERB

Q. I am building an electronic organ and need adjustable reverberation in the audio output. I would appreciate your help with a circuit diagram using the new "bucket brigade" IC for this application.—Colin Nusum, Willowdale, Ontario, Can.

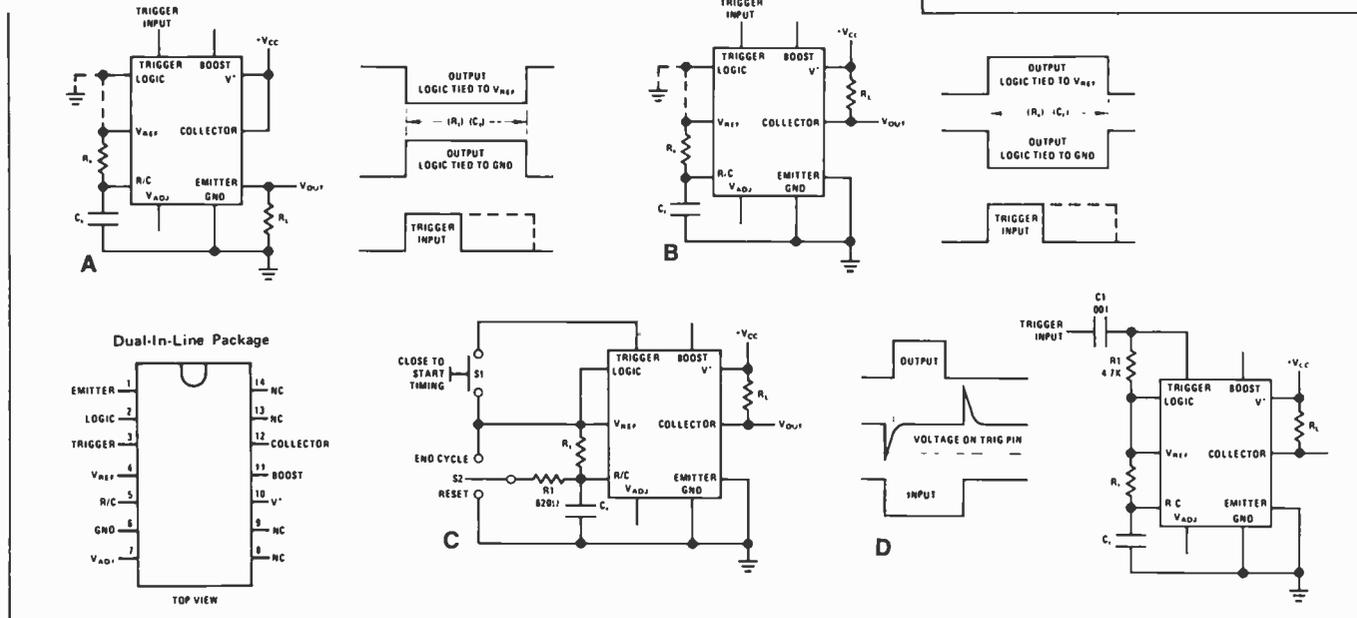A. The "Bucket Brigade" Audio Delay Line in the June 1976 issue is well suited for this application. It employs the Matsushita MN3001 dual 512-stage analog shift registers. Total delay time depends on various resistor values. A table is included for component selection.





Product Test Reports

HY-GAIN MODEL 2716 MOBILE AM CB TRANSCEIVER

Calculator-type keyboard controls remote transceiver.



DURING the past year or so, a number of mobile CB transceivers have been designed to be operated by remote control, with the transceiver itself located somewhere other than under the dashboard. The operating controls for such rigs are on the case of the microphone, which generally serves as the speaker, and is connected to the transceiver via a detachable cable. This type of setup permits the transceiver to be installed in a hidden location to minimize the possibility of theft.

The Hy-Gain Model 2716 40-channel rig is this type of remotely controlled AM mobile transceiver, but with a new twist. It differs from the usual control scheme in that instead of rotary controls and switches, the microphone housing has a calculator-like keyboard to control all (14) functions except power on/off. Moreover, a number of unusual functions are provided. Among these are a LED clock display; two independent channel memories; and S/r-f numerical LED indicators. Other facilities include digital frequency synthesis; VOLUME, SQUELCH, and CHANNEL up/down con-

trol buttons; channel 9 override key; switchable noise blanker; and PA operation. All functions are operated by depressing pushbutton keys.

The main transceiver unit includes an automatic noise limiter, external-speaker jacks; 13.8-volt dc, negative- or positive-ground operation; reverse-polarity protection; and line filter.

The main transceiver unit measures $7\frac{1}{2}'' \times 6\frac{1}{2}'' \times 2\frac{1}{4}''$ (19.1 x 16.5 x 5.7 cm). The entire system carries a price tag of \$249.95, with mounting hardware, microphone, and cables for "up-forward" installations. An extension-cable pack for trunk installation is available at additional cost.

General Description. The main transceiver unit has only the necessary connectors and speaker jacks mounted on its simple plastic housing. It also has flanges for convenient installation. A 5' (1.5-m) control cable can be installed on an L-shaped bracket (supplied) and mounted on a dashboard or transmission hump. The mike cable is then plugged into it.

The case of the microphone is somewhat similar to a telephone handset. The numeric display "window" is located at the top of the housing, the 12 calculator-type pushbutton "keys" are in the middle, and the microphone/speaker is at the bottom. The push-to-talk lever is on the left side of the mike's housing, and the power on/off switch and mike hanger clasp are on the rear of the housing.

Neither the volume nor the squelch operate continuously. They function at a fixed step each time the appropriate button is pressed. The VOLUME steps are about 3 dB each. CHANNEL selection, in either direction, can be stepped sequentially one at a time or continuously when the up or down button is tapped or held down, respectively.

A MEMORY button permits a channel in use to be stored so that the operator can quickly return to the original channel (by pressing MEMORY again) after

checking out other channels. Another button, labelled EMERG CH-9, instantly goes to Channel 9 when pressed.

Separate buttons switch in and out the noise blanker. Setting the hours and minutes for the clock is accomplished with the same buttons used for the noise blanker after first pressing a special F button. This same button switches between CB and PA operation after the F button is first tapped.

The S/r-f readings appear in place of the channel numerals in the display each time a button labelled # is pressed. A green indicator lights during receive. A red indicator comes on on transmit.

Technical Details. The double-conversion receiver, which includes the usual r-f and mixer stages and a noise blanker, provides i-f's of 10,695 and 455 kHz. Selectivity is obtained with a 455 kHz ceramic filter. The remainder of the receiver section includes a diode detector, agc, series-gate anl, and squelch. A single IC contains the entire audio section, including the power-output stage, which doubles as the modulator for the transmitter.


The digital frequency synthesis system utilizes the usual phase-locked-loop (PLL) principle in which a voltage-controlled oscillator (vco) provides the heterodyning frequencies required to produce the 10,695-kHz i-f at the first mixer. A 10,240-kHz crystal oscillator converts the first i-f to 455 kHz at the second mixer. The standard-reference signal is also derived from this oscillator.

In the transmitter section, the carrier is obtained at a mixer by combining the vco frequency with that from a 10,695-kHz crystal-controlled oscillator. Following a spurious-noise-rejection filter are predriver, driver, and the r-f power-amplifier stages. A multi-section network matches the output of the r-f power amplifier to 50-ohm loads and minimizes harmonics. Collector modulation includes automatic modulation control

The quick charge iron with 16 different quick change tips.



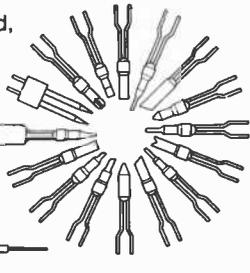ISOATIP®
QUICK CHARGE
 Cordless Soldering Iron completely recharges in 3½-4 hours. Low voltage, battery powered, ground free isolated tip design.




16 snap-in tips to fit any job plus a PC Drill.

WAHL CLIPPER CORPORATION
 ORIGINATORS OF PRACTICAL CORDLESS SOLDERING
 • Sterling, Illinois 61081 • (815) 625-6525
 "Manufacturing Excellence Since 1919"
 CIRCLE NO. 61 ON FREE INFORMATION CARD

Now! Write and run machine language programs at home plus design circuits using a microprocessor!

microprocessor/minicomputer

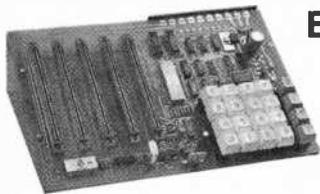

ELF II

\$99⁹⁵

SEND TODAY

NETRONICS R&D LTD., Dept. PE107
 Phone (203) 354-9375
 333 Litchfield Road, New Milford, CT 06776

Yes! I want to run programs at home and have enclosed: \$99.95 plus \$3 p&h for ELF II kit. Featured in POPULAR ELECTRONICS. Including all components plus everything needed to write and run machine language programs plus the new Pixie chip that lets you display video graphics on your TV screen. Designed for engineers, students and hobbyists who need training in computer programming and microprocessor circuit design. Features RCA 1802 COSMAC COS/MOS 8-bit microprocessor addressable to 64k bytes, 256 byte RAM, full hex keyboard, two hex-digit output display, crystal clock for timing applications and double-sided plated-through pc circuit board. Requires 6.3 VAC transformer. Optional 5 card expansion bus (less connectors) for memory expansion, cassette I/O, A to D and D to A converters, PROM and a host of other I/O's. Manual includes instructions for assembly, testing, programming, video graphics and games plus how to receive ELF Users' Club bulletins.

\$149.95 plus \$3 for ELF II wired & tested. (Includes 6.3 VAC power supply and RCA 1802 User's Manual.)

\$5.00 for RCA 1802 User's Manual. Connecticut residents please add sales tax.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Send me information on your other kits!

(amc). Transmit/receive switching is accomplished electronically.

Laboratory Measurements The sensitivity of the receiver section of the transceiver is rated at 0.7 μV for 10 dB (S + N)/N. We measured a 0.5- μV sensitivity on our test transceiver, using a 1000-Hz test tone and 30% modulation. The range of the squelch threshold was 0.5 to 200 μV . The agc system held the change in audio output to 10 dB with a 26-dB r-f input signal change at 0.5 to 10 μV . The change was held to 5 dB with an 80-dB input-signal change at 1 to 10,000 μV . A nominal 50- μV signal registered S9 on the S meter numeric display.

Adjacent-channel rejection and desensitization were 50 dB. Image and i-f rejection measured 70 dB, while other unwanted or spurious signals were down 50 to 60 dB.

The audio output of the transceiver measured 2.5 watts at less than 1.5% THD, using a 1000-Hz test tone and an 8-ohm load. The overall 6-dB response was 275 to 1850 Hz (+1 dB at 700 Hz). Using a 1000-Hz test tone and an 8-ohm load, the output power on PA measured 5 watts at 1.1% THD. At 400 Hz on PA, the power was down to 4.5 watts and the THD was up to 2.2%.

Powering the transceiver from a nominal 13.8-volt dc source, the transmitter's carrier output measured 4.5 to 4.75 watts, depending on the channel in use. The modulation held to up to 100% with only an occasional spill-over, even with mike input levels 16 to 25 dB greater than required for 50% modulation. The THD under these conditions was less than 3% and 5% at 1000 and 500 Hz, respectively. Adjacent-channel splatter with a test tone and with voice was 50 to 55 dB down at ± 5000 to 10,000 Hz from the carrier frequency. The overall 6-dB audio response was 440 to 3600 Hz (375 to 5300 Hz at -10 dB).

User Comment. The Model 2716 represents the exciting new breed of CB transceivers coming to the fore that takes fuller advantage of modern solid-state technology. For example, the MEMORY function enables a CB'er to recall at the push of a button a channel that's been stored instead of going through the cycle of up to 40 channels to locate it. This proved to be a boon to us during our road test, when we quickly switched directly to channel 10 from channel 19 as we turned from one highway to another. The same convenience factor (and safety consideration) held

true when switching to channel 9, where there is a separate emergency channel override key.

The "hide-away" aspect of the 2716 is most welcome as a theft preventive measure, of course. Besides this, the transceiver section does not usurp leg room in an auto. Owing to its shallowness, it can be mounted on the auto's firewall, where it will not be in the way of a passenger and is virtually invisible.

The use of a keyboard-type control system is most interesting. Whereas other types of microphone control systems offer severely limited controls, this one has almost a plethora of functions. As a result, one has to have some practice with the control head in order to use it effectively. Since the keys are not illuminated, handling them at night requires greater familiarity with the keypad layout than one would ordinarily expect. Since CHANNEL selector, VOLUME and SQUELCH buttons are located at the right side of the handset's control panel and arranged in logical order, the positions are rather easy to memorize for one-hand operation.

There are a few other minor discomforting factors with this new control facility, most of them due to basic unfamiliarity with the system—which should be simple to overcome. For instance, one cannot see where the VOLUME and SQUELCH controls are set since they are electronically stepped controls. The S/r-f display, too, operates in a different manner. It's in whole numbers, which precludes being able to read in-between values. In addition, the signal-strength reading comes up for the level only at the particular instant it is called up and remains the same for any given signal level as long as the display is on. The numbers do not change in step with the changes in signal level as they do with a conventional meter. Even so, the disadvantages in the display are not really important. After all, the object is to adequately hear a signal, not look at it.

The built-in digital clock functions continuously as long as the microphone is plugged in, even when the vehicle is not in use. However, disconnecting the mike interrupts the clock's operation. Therefore, it is necessary to reset the clock when the mike is disconnected and again plugged into its connector. (The current drain with just the clock in operation is about 200 mA, which makes it desirable to disable the mike when the vehicle is not to be used over an extended period of time.)

The main transceiver unit features a phono jack that can be used with certain

Hy-Gain AM/FM radios to permit reception of the broadcast bands when the CB rig is squelched. The CB signal has priority in this case so that when a signal is detected, the AM/FM radio is automatically squelched to allow the CB to come through. This is a nice touch, though we did not have an opportunity to test it out.

In addition to providing certain conveniences as well as minimizing the possibility of theft, this transceiver provides good overall performance. Particularly impressive is its ability to suppress noise via its full-time anl system. In our noisy test vehicle, we seldom had to add the noise blanker. In any case, weak sig-

nals could be easily copied without adverse deterioration of the S/N ratio.

The small calculator-size LED numeric displays used for indicating the channel are bright and readable even in sunlight. This contrasts sharply with the large-size displays normally used, which readily wash out in bright light.

Our overall personal reaction to this transceiver is very good, except for the lack of illumination for the control buttons at night. For anyone with especially small hands, though, one-hand operation was sometimes cumbersome, inasmuch as the width of the handset's case is about 3" (7.6 mm).

Of special import is the high quality of reception and reported transmission signals. The mike-contained speaker is driven very well by the transceiver's audio amplifier, producing a loud, clear signal. Furthermore, we had no difficulty contacting CB'ers a few miles away on the lower 23 channels, whereas a pre-40-channel unit could barely reach out one mile in the testing area. On a channel-32 contact, we reached out an extra mile, which says a lot for the advantage of communicating on the 17 new channels.

CIRCLE NO. 104 ON FREE INFORMATION CARD

CONTINENTAL SPECIALTIES MODEL MAX-100 FREQUENCY COUNTER

No-controls counter indicates frequency to 100 MHz with 8 digits.



FEW TEST instruments are as simple to operate as the Model MAX-100 frequency counter from Continental Specialties Corp. It is devoid of all controls except a power on/off switch. You simply turn on the power and connect the instrument's input cable to the circuit under test. Unlike most other low-cost counters that have a frequency range of 30 MHz and a four- or six-digit numeric display, the MAX-100 goes out to 100 MHz and indicates the frequency directly on its eight-digit display.

The frequency counter can be operated from any of three possible power sources. In its basic configuration, the MAX-100 is powered by alkaline cells (or optional rechargeable nickel-cadmium cells). For on-the-bench use, an optional battery charger/eliminator allows operation from 117/220-volt ac line power sources. And for extended field use, another optional charger/eliminator allows operation from mobile electrical systems.

The MAX-100 comes in a modernistic package. It measures 7.75"D x 5.63"W x 1.75"H (19.7 x 14.3 x 4.5 cm) and weighs 1.5 lb (0.68 kg), less batteries. The price of the basic MAX-100 frequency counter, which includes the input cable, is \$134.95. Optional accessories in-

clude: the ac and mobile battery charger/eliminators mentioned above; a mini-whip antenna for inductively coupling in r-f signals; and a low-loss tap-off for physically coupling to an r-f line under test.

General Description. The MAX-100 has a guaranteed specified frequency range of 20 Hz to beyond 100 MHz (110 MHz typical). Its rated sine-wave input sensitivity is 30 mV between 50 MHz and 80 MHz, and 300 mV beyond 80 MHz. The crystal-controlled time base accuracy is specified as ± 1 count. Overload protection is provided for potentials up to 200 volts between 10 and 500 Hz; 100 volts between 500 and 1000 Hz; 75 volts between 1000 Hz and 10 MHz; and 50 volts between 10 and 100 MHz.

The eight-digit display consists of 0.6" (15.2-mm) high red seven-segment numerals. There is no leading-zero blanking for all but the least-significant digit. When the display indicates greater than 1 MHz, a decimal point automatically appears between the sixth and seventh digits. When the instrument is operated on battery power, if the potential drops to less than 6.6 volts, all eight numerals in the display flash once per sec.

Alkaline cells (six AA size) can power


the MAX-100 for about three hours under continuous use or up to eight hours of intermittent use conditions. When operation is from NiCd cells, up to three hours of continuous use or six hours of intermittent use can be expected. Using the optional recharger, the NiCd cells can be fully charged in 12 to 14 hours.

User Comment. The only practical way of evaluating the performance of a frequency counter is to measure a number of signal frequencies of known accuracy across the instrument's entire response range. Bench tests verified that the MAX-100 very accurately indicated the full range of frequencies down to the single hertz. Our test counter was able to measure frequencies well beyond 100 MHz and maintain its basic accuracy. When we did measure frequencies beyond 100 MHz, the display (which has a maximum count range of 99.999999) indicated the proper frequencies and flashed the most-significant digit at the far left to indicate an overflow condition.

We also made a series of sensitivity tests, again covering the entire frequency range of the instrument. In direct physical connections, the MAX-100 was considerably more sensitive than its published ratings. The same held true for our inductively coupled signal tests. We used a relatively low-powered signal generator (a grid-dip meter) at a distance of a couple of inches away from the r-f connector for the inductive-coupling test and obtained excellent results.

We particularly like the no-controls approach to the operation of the MAX-100. This plus its large, bright displays and relatively low price should make it a popular counter.

CIRCLE NO. 105 ON FREE INFORMATION CARD

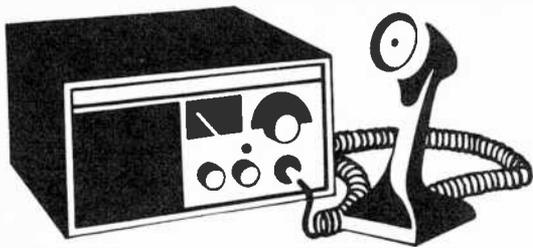

CB Scene

By Ivan Berger

TRENDS IN CB

WITH ALL of the publicity that CB radio has garnered in the past few years, you'd think it would have dominated the Consumer Electronics Show last June. It didn't. (Audio did!) But, then, CB radio has its own show going for it—the Personal Communications Show, held a few months earlier. Nonetheless, there were still plenty of CB rigs displayed at the gigantic CES show, and it was most interesting to observe new trends in equipment.

For example, the outstanding developments last year were in the use of phase-locked-loop circuitry (PLL) and theft-proofing accessories. This year, everyone utilized PLL circuits, a not-surprising fact in view of the new 17 channels added to the CB band. Anti-theft movement was in two areas: new antennas and remotely located CB transceivers.

Manually retractable AM/FM/CB antennas were shown by Tenna, Shur-Lok and SparkOmatic, pointing to those people who can't afford the power types that proliferated last year. Shur-Lok's (also available in a CB-only version) can also be roof-mounted, which permits the user to retract or remove it from the inside of the car. Antenna Systems' "Automatch" antenna is a nonretracting "disguise" type with a matching box beneath it. When the user transmits on a new chan-

nel, a motor in the box adjusts a matching network to retune the antenna to that channel to maximize radio power output. A few companies also exhibited networks which use the car's whole body as an antenna.

New designs, which included remotely located CB transceivers with microphone control systems, were given heavy emphasis this year. Hy-Gain led the pattern for this type of transceiver design last year with its 23-channel Hy-Gain 9. At this year's CES, I observed new versions from Hy-Gain, as well as remotes from Audiovox, Boman, Clarion, Johnson American, Medallion, Pace, Panasonic, SBE, Sharp, SparkOmatic, Surveyor and Texas Instruments (not yet FCC type accepted at show time), among others. As you'd expect, each company has added a few ideas to the basic theme.

One interesting new feature is the linking of a CB transceiver to a car's stereo system with a "stand-by" switch so that one can monitor a channel and listen to stereo at the same time. When a CB signal overrides the squelch level, the stereo source is automatically cut off and the CB communication comes through. The stereo sound also cuts off when transmitting, of course. It appears that Audiovox and SBE units work this way with any car-stereo unit, while Cla-



rion, Hy-Gain and SparkOmatic interface with specific car stereo models of their own. Kraco has one built into a car radio. There are also combination AM/FM/CB in-dash units with controls in the mike head and the channel display on the radio itself from Clarion, Cobra, JIL, Kraco, Medallion, and Superscope, among others. (Note that using a car's stereo speakers does not necessarily mean clearer CB sound since stereo speakers cover a wider frequency range than CB produces and might, therefore, reproduce noise of higher frequency than CB speakers will.)

Most remote control CB transceivers use the microphones as speakers, too, though most also have jacks for external speakers. But those from Johnson American, Sharp, and Texas Instruments employ speakers that are not contained in the mike. These speakers are located in the small junction boxes that the microphone/control units plug into, generally at a location under the dashboard and near the driver. Though this does not necessarily make for better sound quality, the mike unit can be made smaller for easier handling.

In one of Sharp's models, the box also has a big signal/r-f meter on its face. Johnson's box, which also contains the digital channel readout can be mounted above or below the dash.

Some microphones used as speakers lack top-quality sound performance. Even the full-size speakers of underdash rigs may not produce audio as well as they might because the sound waves go way down to the floor carpeting and bounce back up to you. There were a lot of external speakers at CES to solve these problems. I also noted external speaker models with built-in tone controls from SparkOmatic and Kraco, as well as AFS's flush-mounted CB radio speaker. The latter saves space, and helps to conceal the fact that you have a

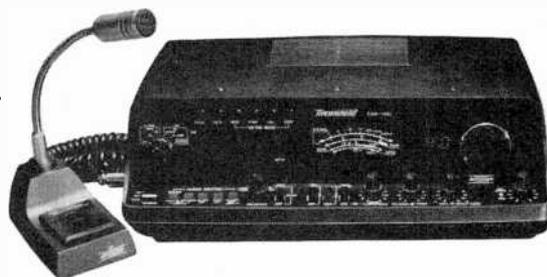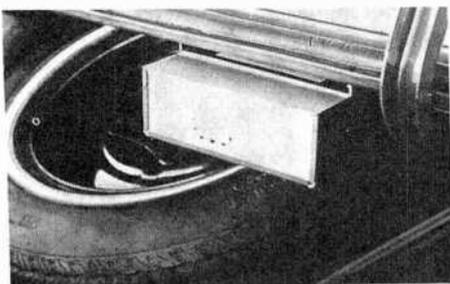Panasonic's "Big Mike Model RJ-3450 with microphone control system (left) and remotely located transceiver (below).



Superscope Aircommand Model CBB-1050 base station with channel 9 scan.

CB unit in the car (assuming you've hidden the transceiver and the antenna). Still another method to enhance sound was offered by Prime Electronics with its PR-1000 Variable Audio Filter. The filter's center frequency and bandwidth can be varied to exclude as much or as little sound as one likes. It's for 115-V ac operation.

Digital Designs. Digital channel display is a great advance, especially for mobile CB use. It's far easier to read one big number than a cluster of little ones around a dial.

The early digital-display units had little else digital about them. Now digital circuitry is showing up in a number of new ways. For example, the displays themselves are giving more than just the channel number. Hy-Gain's new 2716 remote unit and Pace's 8092 mobile have digital clocks built-in, and both the 2716 and the new Texas Instruments SSB base and remote display signal strength and r-f output digitally. (Many Johnson American models and SBE's Stowaway" remote unit take a different approach to this: a line of LED's above the digital channel display serves as an S/r-f "meter.")

Texas Instruments' SM-172 mobile unit and matching SM-173 base also display SWR when a keypad button is depressed. But more important is TI's automatic SWR monitor that automatically shuts down the transmitter when it senses that the SWR is approaching the point where transmitter damage might occur. In this event, the user is alerted by the display, "AAAAA."

Monitoring SWR is just one of several functions handled by a microprocessor built into TI's main circuit module. The processor also controls a variable-bandwidth filter that narrows when adjacent channels are busy. And when talking to another TI set on SSB, the same filter shifts frequency as well, acting as an automatic clarifier.


Microprocessors are also built into the Hy-Gain 2716 and the SBE Key-Com. Others are sure to follow suit.

Smarter Tuning. Microprocessors and other digital techniques are changing the way we tune our transceivers—and for the better. Most of the new digital sets have two-button tuning—one button to scan up the scale, and the other to scan down. (An improvement I'd like to see here is the inclusion of a soft beep

each time the channel changes, so a driver could count how many channels he's shifted without taking his eyes off the road. With a nondigital set, one can count clicks.)

Several SBE and Sparkomatic transceivers have two-speed tuning, so you can zip quickly to the other end of the "dial" (more time on 40 than on 23 channels), then slow down so as not to overshoot your mark. Panasonic's RJ-3450 "Big Mike" model, SBE's colorful Key-Com and TI's units scan the band to find clear channels (if you want to move your conversation to a less crowded one) or to find active ones (if you're looking for someone to talk to). SBE's version of this feature scans the whole band for an open channel and scans the 10 stations you use most (and have stored in its memory) for activity, on the assumption that you're looking for someone specific to talk to. TI's clear-channel scan returns you to the channel you were originally talking on so you can tell the other party to your conversation what channel you should both switch to.

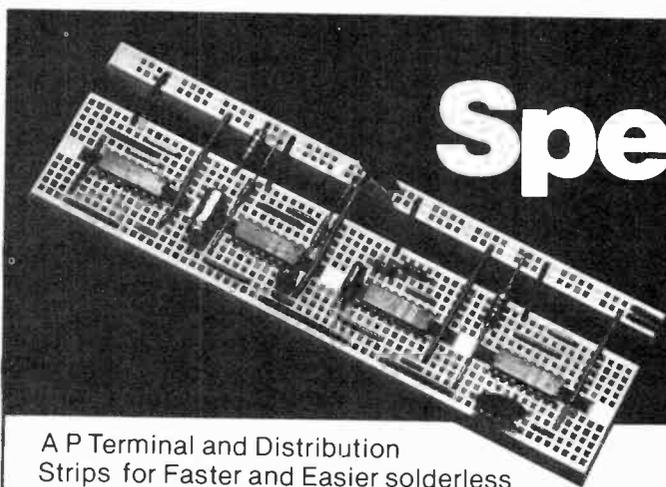In emergencies, you can jump directly to channel 9 by hitting just one switch or button on CB transceivers from a growing number of manufacturers, including



Special Bonus Offer!

A P Terminal and Distribution Strips for Faster and Easier solderless circuit building and testing. No special patch cords are required, and any solid wire up to No. 20 AWG can be used for connection. Strips accept all components with leads up to .032" diameter, and hardware and mounting templates are provided with every strip. Terminals are non-corrosive nickel/silver.

For the name of the distributor nearest you call Toll-Free 800-321-9668.


Send for our complete A P catalog The Faster and Easier Book.

Faster and Easier is what we're all about.



A P PRODUCTS INCORPORATED

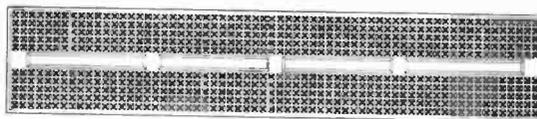Box 110 • 72 Corwin Drive, Painesville, Ohio 44077 • 216/354-2101 TWX: 810-425-2250



Buy this Model 264L **TERMINAL STRIP**, with 128 five-tie-point terminals, #923261 for only **\$12.50**.

And get this Model 212R **DISTRIBUTION STRIP**, with 24 four-tie-point terminals, #923277 **FREE** of added cost.

Free offer also applies to other sizes.

Look for the Special Bonus Offer Display at your A P distributor.

*Special bonus offer expires 12/31/77

PROFESSIONAL DISCOUNTS

Texas Instruments electronic calculator

| | | | |
|-------------|---------|-------------------------|---------|
| TI-150 LCD | \$19.95 | SR-40 | \$24.95 |
| TI-2550 III | 24.95 | SR-51 II | 49.95 |
| Little Prof | 12.95 | TI-57 NEW | 64.95 |
| Dataman NEW | 22.50 | TI-58 NEW | 39.95 |
| TI-5100 | 44.95 | TI-59 NEW | 249.95 |
| TI-5015 NEW | 65.00 | PC-100A | 147.00 |
| TI-5050 M | 84.95 | Money Mgr. | 17.95 |
| TI-5040 PD | 95.00 | Bus. Anytst. | 29.95 |
| TI-30 SP | 17.95 | All Libraries Available | |



HEWLETT  PACKARD

We are franchised H-P dealer All accessories at discount

| | | | |
|------------|----------|------------|----------|
| HP-10 NEW | \$139.00 | HP-27 | \$140.00 |
| HP-19C NEW | 299.00 | HP-29C NEW | 159.00 |
| HP-21 | 64.00 | HP-80 | 235.00 |
| HP-22 | 100.00 | HP-67 | 360.00 |
| HP-25 | 100.00 | HP-91 | 275.00 |
| HP-25C | 128.00 | HP-92 | 515.00 |
| | | HP-97 | 599.00 |

Also SCM, Olivetti, National Semiconductor, Casio, Canon, Corvus, APF, Sharp, Craig, Sanyo, Record-A-Call, and more. All at great prices!

FAIRCHILD

Programmable Video Game \$135.00
(2000 games possible)
Cartridges 17.95
Also Fairchild Watches!

WE WILL BEAT OR MEET ANY COMPETITORS' PRICE IF HE HAS MERCHANDISE ON HAND. All units shipped in original factory cartons with accessories according to manufacturers' specifications. In Calif. call (213) 370-5795 or CALL (800) 421-0367 (other than CA). Above prices are for cash only. Credit card prices differ. BankAmericard/Visa & Master Charge accepted. Send money order. Pers. ck (2 wks to clear). In CA add 6% sales tax. Add \$3.50 min. shipping charges. WE SHIP AIR on request. Subject to availability. Send mail orders to DEPT. PE-J.

2 locations in So. California
enterprises
RETAIL BUSINESS PRODUCTS

16611 Hawthorne Blvd., Lawndale, Ca. 90260
(213) 370-5795 (800) 421-0367

CIRCLE NO. 56 ON FREE INFORMATION CARD

CB

where the ACTION'S at

Millions of 2-way CB radios are in use—millions of new ones are being sold annually to new CBers and for replacing old units—what a market for repair service. It's the biggest thing in electronics since color TV. There's only one thing wrong with CB growth—the lack of technicians capable of servicing CB radios. That's why many TV shops are expanding into CB and why new CB shops are opening up all over the country. Going CB servicing rates run from \$12 to \$24 per hour.

To get into CB radio servicing, full-time or part-time, you need test equipment, an FCC operator license and to learn how. To learn how, you can buy the **CB RADIO REPAIR COURSE** for cash, on a monthly payment plan, or charge the cost to your BankAmericard or Master Charge account.

To make it easy to study, this 70-lesson course employs the **PROGRAMMED** teaching technique and sticks to the target—CB radio. Study at your own pace as you receive the self-examining lessons. We can't guarantee that you will become a CB expert since that depends on you.

To get the facts about this course, write a letter or card or mail the coupon below today. No salesman will call.

CB RADIO REPAIR COURSE, INC.

Dept. PE-107

531 N. Ann Arbor
Oklahoma City, OK 73127

Please send information about your Course to:

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE NO. 10 ON FREE INFORMATION CARD



Johnson 4330 has remote control mike with speaker and channel indicator in separate box.



Cobra 45XLR combines 40-channel CB with AM/FM/stereo FM.

Texas Instruments' Model SM-172 has remote computer control.

Hy-Gain, Pace, Panasonic, SBE, Sharp, and Superscope "Aircommand." To jump directly to any other station, calculator-type keyboards are used to punch in the number on many rigs: SBE's Key-Com (again), Pace's 8117 base station and the TI units, for example. The latter also have a unique, keyboard-operated selective-call system. Select a 5-digit number and a channel, tell you friends with TI units what your number is, and your receiver section will be silent until they "dial" you. Unlike most selective-call systems that use tones, the TI sets can access up to 100,000 CB "phone numbers" for each AM or SSB channel and store the five most frequently called numbers in a memory, to be recalled at the touch of a key.

Interestingly, there's a move afoot at the Electronic Industries Association to standardize selective calling signals for CB radio use. The purpose is to head off incompatibility among products of different manufacturers.

Rigs That Remember. Memory—another digital feature—is found on many of the latest transceivers. Sharp's IMC and Hy-Gain's 2716 remote models are examples of CB transceivers that remember which channel you last used so you don't have to re-tune to it when you turn the unit on again. The 2716 also remembers other settings when it's in



SBE Key-Com 1000 has built-in microprocessor and a calculator type keyboard channel selector.




"stand-by" mode. Sparkomatic has a model with a 5-channel memory. You can use its scanning feature or manual tuning to search through all 40 channels or just through the 5 channels you use most in search of activity. Pace's 8047 can scan channel 9, 19 and any other channel you choose and its 8117 base station has a 10-channel memory that can be scanned as does SBE's Key-Com mobile. Both Sharp and Superscope Aircommand have models that monitor channel 9 as well as the channel you're using.

These weren't the only CB products at CES of course; just some of the ones with the most exotic features. Furthermore, not all CB manufacturers exhibited at CES. And at least one who did—Motorola—held off introducing new CB models so that it could show them for the first time a few weeks later at a distributor's convention. Here it introduced a 40-channel base station with an automatic "on-setting" digital clock function (Model 4025) and an under-dash "public safety" monitor mobile (Model 4009) with dual receivers that features a channel 9 crystal that can be replaced by another channel's crystal.

About the only other possible trend observed was the growing number of CB in-dash "entertainment centers" available. That is, CB transceivers combined with AM, stereo FM and a choice of cassette or 8-track tape units. ◇

POPULAR ELECTRONICS

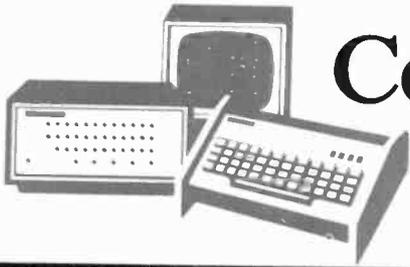

Computer Bits

By Leslie Solomon

MORE GOOD NEWS FOR THE COMPUTER GROUP

THE NUMBER and variety of hardware and software items available to computer hobbyists continue to increase—with no end in sight at present. Let's take a look, then, at a few of the "goodies" that have come across our desk in the last several weeks. First, the hardware items.

Radio Shack Too! The latest entry into the hobby computer scene is from Radio Shack. Packaged in an attractive and functional plastic case only 16½" by 8" by 3½" are a 53-key ASCII keyboard, a Z80 microprocessor and support logic, a video display unit, 4k of ROM and 4k of RAM (internally expandable to 12k ROM and 16k RAM), and a cassette interface. Soon to be available at most Radio Shack outlets, the wired and tested TRS-80 Microcomputer can be purchased for \$399.95. An associated 12" video monitor and cassette recorder package is also available to create a complete personal computing system for \$599.95.

The video display is memory mapped with graphics and alphanumeric (upper case) controlled by BASIC commands. Cursor control and automatic scrolling are also featured. Connections to the cassette recorder and the video monitor are made via rear-apron connectors. Also on the rear apron is a small door that, when opened, exposes a bus connector that is used for system expansion. Although the computer can physically hold only 16k of RAM, it has a total memory capacity of 62k by using its bus connector.

The video display is 16 lines of 64 characters but can be software controlled for 32 characters per line. The video graphics are formed on a 128 (horizontal) by 48 (vertical) matrix and both graphics and text can be interspersed in any manner by software.

The BASIC software comes in ROM and features floating point arithmetic; numeric, array, and string variables; video graphic commands; and cassette save and load commands. The software




Radio Shack's TRS-80 microcomputer system.

OCTOBER 1977

FREE!

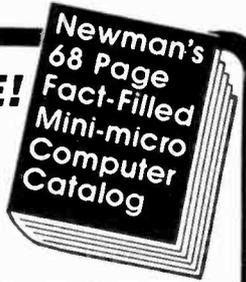with your business card or send \$1.00 (refundable on 1st order)



LARGEST CATALOG IN ITS FIELD

Catalog Includes:

- Manufacturer's catalogs
- News about amazing breakthroughs in the Mini-micro computer field.
- \$2.00 Discount Certificate
- Discounts up to 90% on Used Equipment

• A Complete Computer System Just \$289



COMPUTER DEALERS ASSOCIATION

- Everything:
- Fully Assembled
- Fully tested
- Fully Warranted
- KIM-1 — MOS Technology Computer Module 1K-RAM, audio cassette interface, 15 bidirectional I/O lines, 24-key keyboard and six-digit LED display
- System Power Supply (5V at 1.2A, 12V at 0.1A), with power line and switch
- Software — System Executive, Sample application programs.
- Documentation.
- User hardware & programming manuals, wall size System Schematic
- Programmer's Reference Card

Money-Back Guarantee

Return items undamaged for any reason within 10 days of receipt and get a complete refund.

• Computer Books

- An Introduction to Microcomputers, Vol 1 - Basic Concepts (Osborne). A complete book. \$7.50
- Vol 2 - Some Real Products. Details today's real products. \$12.50
- Basic BASIC: An Introduction to Computer Programming in BASIC Language (Coan) An excellent introduction to BASIC. \$7.95
- Advanced BASIC: Applications and Problems (Coan) Advanced techniques and applications. \$8.95
- Hobby Computers are HERE Green Simplified introductions to various aspects of hobby computing. \$4.95
- Telephone Accessories You Can Build (Gullder). Remote telephone ringing, speech scrambler for privacy, automatic dialing, etc. \$3.95

Bankard/Visa & Master Charge accepted

Order From:

NEWMAN COMPUTER EXCHANGE
1250 N. Main St. Ann Arbor, Mi. 48104
(313) 994-3200 Dept. PE

CIRCLE NO. 36 ON FREE INFORMATION CARD

SAVE!

MONEY • TIME • FREIGHT

QUALITY STEREO EQUIPMENT AT LOWEST PRICES.

YOUR REQUEST FOR QUOTATION RETURNED SAME DAY.

FACTORY SEALED CARTONS—GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:

| | |
|---------|--------|
| PIONEER | SANSUI |
| KENWOOD | DYNACO |
| SHURE | SONY |
| MARANTZ | KOSS |

AND MORE THAN 50 OTHERS
BUY THE MODERN WAY
BY MAIL—FROM


illinois audio

12 East Delaware
Chicago, Illinois 60611
312-664-0020

CIRCLE NO. 23 ON FREE INFORMATION CARD

NOW! "3rd Hand"

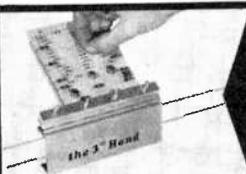Makes Circuit Assembly a Breeze!
Lets you work with Both Hands



STEP 1
Clamp "3rd Hand" on bench, insert circuit board, position components — note convenient working angle.



STEP 2
Flip circuit board to flat position for soldering and clipping. Reverse procedure for double sided boards.

Dealer/Distributor inquiries invited

Send Check or Money Order

ORDER NOW!

Fully Guaranteed

(Not sold in stores)

No C.O.D.'s + .75 Postage

\$695

THE 3RD HAND
P.O. BOX 60579
SACRAMENTO, CA 95860

Amount Enclosed \$
California residents add 6% tax

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

98

CIRCLE NO. 40 ON FREE INFORMATION CARD

level is between "tiny" BASIC and "regular" BASIC and includes the special commands used for graphics.

Along with the computer, the customer will be supplied with a free cassette that "plays" blackjack (with graphics) and backgammon. Other available cassettes provide a 15-person payroll program (\$19.95), a Math-1 package that teaches multiplication, addition, and subtraction, and includes a teacher's guide (\$19.95 for a three cassette portfolio); a kitchen program that covers menus, conversion tables, a computer directory, and a message center (\$4.95); and a personal finance program for \$14.95 which includes a seven-cassette portfolio.

Radio Shack intends to support its new baby and plans to introduce Extended BASIC (more memory is required), a disc and DOS system, a hard-copy printer, an expansion unit for additional circuit boards (connecting the expander bus), and a modem.

A number of interesting software packages have also been promised for the near future with the hope of making the TRS-80 a useful hobby and personal computer.

For Fans of the Z80. If you are interested in the Z80 processor, you should be aware of the Martin Research (3336 Commercial Ave., Northbrook, IL 60062; tel: 312-498-5060) MIKE-8 Model 882. It sells assembled for \$895. The 882 has 4k of RAM, a 1k monitor program in PROM, and a "console" board with a calculator-type keypad and six 7-segment LED displays. Besides the usual functions, the monitor offers advanced debug features, RAM test, signal-step, and trap setting. The system also includes a 2708 PROM programmer and a UV erase lamp. The Model 882 is mounted on a base and has its own switching regulator power supply. The firm's Microcomputer Design book fills out the package.

PROM Programming. Oliver Audio Engineering (7330 Laurel Canyon Blvd., North Hollywood, CA 91605; tel: 213-765-8080), which introduced the low-cost optical tape reader some time ago, has now introduced a new PROM programmer, the OAE PP-2708/16. (As a kit, it is \$249; wired and tested, it's \$299.) Containing address counters, timing and control logic, switching voltage regulator, and a zero-insertion-force socket, this new programmer can handle either the 1k 2708 or the new 2k 2716 PROM's. A simple parallel inter-

face connects the programmer to almost any microcomputer and very little software is required to support the system. You just dump the data via the output port into the PROM. The system comes with one 8-bit I/O port and three switch-programmable status lines, with all lines TTL compatible. A 5-foot, flat ribbon cable is provided.

Cassette Interface. Compatible with the Altair/S-100 bus, the Universal Cassette Recorder Interface (UCRI) is now available from Dajen Electronics (7214 Springleaf Ct., Citrus Heights, CA 95610; tel: 916-723-1050) for \$135 in kit form, \$175 assembled and tested. Using bi-phase recording and having no adjustments, the UCRI can operate from 520 to 41,000 baud—switch selectable. There is also a switch-selectable board address, and independent selection of transmit and receive data inversion for use with different recorders. A level-indicator light comes on at correct levels, and a sync indicator light shows reception of the sync byte. User selectable sync character, under software control allows Tarbell, KC or other sync character format. Relay options for control of two recorders are available. An independent latched input port can be used for a keyboard. Output connectors for recorder and parallel port, recorder cable, IC sockets, pre-recorded cassette with sync, and a full manual are included.

Super Hobby Terminal. If your dreams include a super hard-copy terminal, take a look at the new Texas Instruments Silent-700 Model 765 Portable Memory Terminal or the Model 763 Memory Send-Receive Terminal. About the size of an office typewriter, the 765 is designed for portable use and includes a



TI's Silent 700 Terminal.


POPULAR ELECTRONICS

built-in carrying case and a phone coupler. The 763 is for use where portability is not required.

Each of these new terminals comes with 20k characters of nonvolatile bubble memory expandable to 80k. A 9900 processor controls the system. Both units include a keyboard with upper and lower case, a built-in calculator-type numeric keypad cluster, and a quiet 30-character/second nonimpact printer. Both models have file management systems, and an operator command mode to allow the user to select the communications mode, configure memory, and enter or edit text. The Model 765 is \$2995 and the 763 is \$2695.

Economical Terminal. If you have a computer, the next thing you need is a CRT-type terminal so you can "talk" to your machine. Southwest Technical Products (219 W. Rhapsody, San Antonio, TX 78216), the producer of the CT-1024 terminal, has announced its CT-64 CRT Terminal (\$325 in kit form, with assembled CT-VM Video Monitor \$175). This new terminal features 16 lines of 32 or 64 characters per line, scrolling or page operation, upper and lower case, reversed character printing, full cursor control, and complete character decoding. The kit includes power supply, keyboard, serial I/O, beeper, chassis, and cover.

6800 Software. Impro Micro Systems (Box 7776, Van Nuys, CA 91409) recently announced its MIKADOS+D (mini instant keyboard assembler, debug, operating system + disassembler) package. The \$17.95 software package occupies only 3k of RAM and with 4k bytes, 1k is still left for user programs and the label table. The assembler generates object code for the 72 basic variable-length 6800 instructions with all addressing mode variations—a total of 197 different instructions. The assembler generates object code for user-entered mnemonics, enters them into memory, and outputs formatted object code and address on the same line as user input. Relative addressing for branch instructions with symbolic labels are resolved,

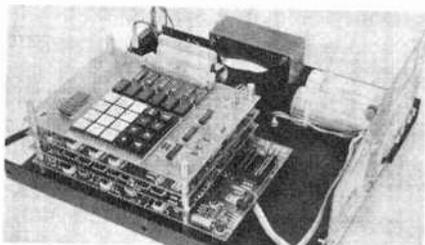

Martin MIKE-8 882 processor.

OCTOBER 1977

"Our whole family helped assemble this wonderful Schober Organ... now we all play it!"



Talk about real family fun! We all worked together, for a few hours almost every day. Almost too soon, our Schober Organ was finished. Our keen-eyed daughter sorted resistors. Mom soldered transistor sockets, although she'd never soldered anything before. And it did our hearts good to see the care with which our son—he's only 12—installed the transistors. Me? I was the quality control inspector—they let me do the final wiring. And when it came time to finish the beautiful walnut cabinet the easy Schober way, we all worked at it!

Now, we gather around our Schober Organ every evening to play and sing together. Some of us play better than the others, but we're all learning—with the help of the easy Schober Organ playing courses. I might add that I'm especially pleased with all the money we saved. Our completed Schober Organ compares favorably with a "ready-made" one costing twice as much! (The five models range from \$650 to \$2850.) And we didn't even need to pay the whole amount all at once, because we were able

to buy Schober Kits a component at a time, to spread costs out. Or we could have had two-year time payments!

Families like ours have been building Schober Organs for 20 years. How about your family? You can have all the details, without cost or obligation. Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a 12-inch LP record that lets you hear as well as see Schober quality). Clip the coupon right now—and mail it TODAY!

The Schober Organ Corp., Dept. PE-73
43 West 61st Street, New York, N.Y. 10023

Please send me Schober Organ Catalog.

Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

CIRCLE NO. 51 ON FREE INFORMATION CARD

FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER

SEND TODAY!

McIntosh Laboratory, Inc.
East Side Station P.O. Box 96
Binghamton, N.Y. 13904
Dept. PE

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

If you are in a hurry for your catalog please send the coupon to McIntosh. For non rush service send the Reader Service Card to the magazine.

CIRCLE NO. 31 ON FREE INFORMATION CARD

and a label table is maintained. There are 18 useful directives on line at all times including ASCII character I/O, hex character input formatted hex character output, disassembly of object code into source code with complete instruction mnemonics and absolute branch addresses, label table formatted output, data transfer from one memory area to another, clearing all or part of memory, controlling execution of user programs, setting and clearing breakpoints, and setting and clearing monitor points.

Another 6800 software producer, TSC (Technical Systems Consultants, Box

2574, W. Lafayette, IN 47906) has announced its Text Editing System (stock number SL68-24 at \$23.50) which supports many of the standard commands such as PRINT, INSERT, DELETE, FIND, REPLACE, and VERIFY. It also provides file TOP and BOTTOM, an APPEND command allowing any string to be added to any or all lines starting in a specified column, text block COPY and MOVE, and an extensive CHANGE command that allows changing any or all specified occurrence of one string into a second string. Other features include TAB, SET, NUMBERS, EXPAND, NEXT, RENUMBER, STOP, LOG,

and OVERLAY that allows line changing by typing over an existing line. There is a HEADER command, a ZONE feature and, for tape users, READ, WRITE, and SAVE.

6502 Software. If you are more concerned with the 6502, you should know that Microcomputer Associates Inc. (2368-C Walsh Ave., Santa Clara, CA 95050; tel: 408-247-8940) has a new 6502 RAP (resident assembler program) and Tiny BASIC on ROM. The two 2k ROM's house the 1.75k resident assembler and the 2.2k Tiny BASIC. RAP is a single-pass resident assembler. Statements are entered either from paper tape or from a terminal keyboard, and RAP generates a listing and places object code into RAM for immediate execution. A minimum of 4k RAM is needed in the user's computer. Tiny BASIC statements include LET, IF, THEN, INPUT, GOTO, GOSUB, RETURN, END, REM, CLEAR, LIST, RUN, RND, andUSR (user subroutine). The ROM software has been designed so that most I/O devices can be used. The RAP/Tiny BASIC package (SW101) is \$200 with full documentation. Tiny BASIC is available in paper tape format (SW300) for \$25, or in nine 1702A PROM's (SW202) for \$275.

Altair 680 Doings. If you have an Altair 680b, you should be aware that MITS has introduced the 680b-KCACR Audio Cassette Interface for this machine. Using the KC Standard, the device features a digital demodulator, CMOS logic, motor control for starting and stopping tape motion, test points at all key circuits, and sockets for all IC's. BASIC Version 1.2 is available on cassette and includes all standard functions, plus the capability of storing and loading software through the KCACR.

Three-Dimensional Graphics. Sublogic Co. (Box 3442, Culver City, CA 90230) has a new software package that will provide 3-dimensional graphics for microcomputers. With it, you can view two-dimensional perspective projections of three-dimensional scenes from any location in space. A minimal subset BASIC version of the package, for \$22 is for general-purpose, slow-speed graphics on any system. Another version, the 6800, at a slightly higher price, has optimized assembly language with dynamic graphic capabilities for advanced simulation and complex graphics. Driving and flying simulations, artistic projections, design projections, engineering analysis, and advanced games are possible uses. ♦

NEW LSI TECHNOLOGY FREQUENCY COUNTER

TAKE ADVANTAGE OF THIS NEW STATE-OF-THE-ART COUNTER FEATURING THE MANY BENEFITS OF CUSTOM LSI CIRCUITRY. THIS NEW TECHNOLOGY APPROACH TO INSTRUMENTATION YIELDS ENHANCED PERFORMANCE, SMALLER PHYSICAL SIZE, DRASTICALLY REDUCED POWER CONSUMPTION [PORTABLE BATTERY OPERATION IS NOW PRACTICAL], DEPENDABILITY, EASY ASSEMBLY AND REVOLUTIONARY LOWER PRICING!



1 3/4 LBS.
COLOR:
BLACK

SIZE:
3" High
6" Wide
5 1/2" Deep

ORDER BY PHONE OR MAIL
COD ORDERS WELCOME

FEATURES AND SPECIFICATIONS:

DISPLAY: 8 RED LED DIGITS .4" CHARACTER HEIGHT
GATE TIMES: 1 SECOND AND 1/10 SECOND
[AUTO DEC. PT. PLACEMENT]
RESOLUTION: 1 HZ AT 1 SECOND, 10 HZ AT 1/10 SECOND.
FREQUENCY RANGE: 10 HZ TO 60 MHZ. [65 MHZ TYPICAL].
SENSITIVITY: 10 MV RMS TO 50 MHZ, 20 MV RMS TO 60 MHZ TYP.
INPUT IMPEDANCE: 1 MEGOHM AND 20 PF.
[DIODE PROTECTED INPUT FOR OVER VOLTAGE PROTECTION.]
ACCURACY: ± 1 PPM [± .0001%] AFTER CALIBRATION TYPICAL.
STABILITY: WITHIN 1 PPM PER HOUR AFTER WARM UP [0.001% XTAL]
IC PACKAGE COUNT: 8 [ALL SOCKETED]
INTERNAL POWER SUPPLY: 5.2 V DC AT 800 MA. REGULATED.
INPUT POWER REQUIRED: 8-12 VDC OR 115 VAC AT 50/60 HZ.
POWER CONSUMPTION: 4 WATTS
INPUT CONNECTOR: BNC TYPE

| | | |
|----------------------|--------------------------------------|----------|
| KIT #FC-50C | 60 MHZ COUNTER WITH CABINET & P.S. | \$119.95 |
| KIT #PSL-650 | 650 MHZ PRESCALER [NOT SHOWN] | 29.95 |
| MODEL #FC-50WT | 60 MHZ COUNTER WIRED, TESTED & CAL. | 165.95 |
| MODEL #FC-50/600 WT. | 600 MHZ COUNTER WIRED, TESTED & CAL. | 199.95 |

KIT #FC-50C IS COMPLETE WITH PREDRILLED CHASSIS ALL HARDWARE AND STEP-BY-STEP INSTRUCTIONS. WIRED & TESTED UNITS ARE CALIBRATED AND GUARANTEED. PRESCALERS WILL FIT INSIDE COUNTER CABINET.

TERMS: FOR SHIPPING, HANDLING & INSURANCE
TO US & CANADA ADD 5% ALL OTHERS 10%.
FLORIDA RES. ADD 4% SALES TAX. COD
CHARGE \$1.00.



OPTOELECTRONICS, INC.

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056

CIRCLE NO. 39 ON FREE INFORMATION CARD

POPULAR ELECTRONICS

Bearcat® 210

\$289.



Bearcat® 210 Features

- **Crystal-less**—Without ever buying a crystal you can select from all local frequencies by simply pushing a few buttons.
- **Decimal Display**—See frequency and channel number—no guessing who's on the air.
- **5-Band Coverage**—Includes Low, High, UHF and UHF "T" public service bands, the 2-meter amateur (Ham) band, plus other UHF frequencies.
- **Deluxe Keyboard**—Makes frequency selection as easy as using a push-button phone. Lets you enter and change frequencies easily... try everything there is to hear.
- **Patented Track Tuning**—Receive frequencies across the full band without adjustment. Circuitry is automatically aligned to each frequency monitored.
- **Automatic Search**—Seek and find new, exciting frequencies.
- **Selective Scan Delay**—Adds a two second delay to prevent missing transmissions when "calls" and "answers" are on the same frequency.
- **Automatic Lock-Out**—Locks out channels and "skips" frequencies not of current interest.
- **Simple Programming**—Simply punch in on the keyboard the frequency you wish to monitor.
- **Space Age Circuitry**—Custom integrated circuits... a Bearcat tradition.
- **UL Listed/FCC Certified**—Assures quality design and manufacture.
- **Rolling Zeros**—This Bearcat exclusive tells you which channels your scanner is monitoring.
- **Tone By-Pass**—Scanning is not interrupted by mobile telephone tone signal.
- **Manual Scan Control**—Scan all 10 channels at your own pace.
- **3-Inch Speaker**—Front mounted speaker for more sound with less distortion.
- **Squelch**—Allows user to effectively block out unwanted noise.
- **AC/DC**—Operates at home or in the car.

Bearcat® 210 Specifications

| | |
|----------------------------------|-------------|
| Frequency Reception Range | |
| Low Band | 32—50 MHz |
| "Ham" Band | 146—148 MHz |
| High Band | 148—174 MHz |
| UHF Band | 450—470 MHz |
| "T" Band | 470—512 MHz |

*Also receives UHF from 416—450 MHz

Size
10 1/2" W x 3" H x 7 1/8" D

Weight
4 lbs. 8 oz.

Power Requirements
117V ac, 11W; 13.8 Vdc, 6W

Audio Output
2W rms

Antenna
Telescoping (supplied)

Sensitivity
0.6µv for 12 dB SINAD on L & H bands
U bands slightly less

Selectivity
Better than -60 dB @ ± 25 KHz

Scan Rate
20 channels per second

Connectors
External antenna and speaker; AC & DC power

Accessories
Mounting bracket and hardware
DC cord

The Bearcat® 210 is a sophisticated scanning instrument with the ease of operation and frequency versatility you've dreamed of. Imagine, selecting from any of the public service bands and from all local frequencies by simply pushing a few buttons. No longer are you limited by crystals to a given band and set of frequencies. It's all made possible by Bearcat space-age solid state circuitry. You can forget crystals forever.

Pick the 10 frequencies you want to scan and punch them in on the keyboard. It's incredibly easy. The large decimal display reads out each frequency you've selected. When you want to change frequencies, just enter the new ones.

Automatic search lets you scan any given range of frequencies of your choice within a band. Push-button lockout permits you to selectively skip frequencies not of current interest. The decimal display with its exclusive "rolling zeros" tells you which channels you're monitoring. When the Bearcat 210 locks in on an active frequency the decimal display shows the channel and frequency being monitored.

With the patented track-tuning system, the Bearcat 210 automatically aligns itself so that circuits are always "peaked" for any broadcast. Most competitive models peak only at the center of each band, missing the frequencies at the extreme ends of the band.

The Bearcat 210's electronically switched antenna eliminates the need for the long low band antenna. And a quartz crystal filter rejects adjacent stations as well as noise interference.

Call toll-free 800-521-4414 now to place a BankAmericard or Mastercharge order. This is our 24 hour phone to our order department and only orders may be processed on this line. To order in Michigan or outside of the U.S. dial 313-994-4441.

Add \$5.00 for U.S. shipping or \$9.00 for air UPS to west coast. Charge cards or money orders only please. International orders invited. Michigan residents add tax. Please write for quantity pricing.

COMMUNICATIONS ELECTRONICS

Box 1002 Dept. 733
Ann Arbor, Michigan 48106 USA



Try this exciting new hobby!

Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send \$2.00 (refundable) with coupon for colorful 104 page catalog.

W WERSI



Wersi Electronics, Inc.
Dept. 42, Box 5318
1720 Hempstead Road
Lancaster, PA 17601


Enclosed is \$2.00 for my copy of your 104 page catalog.

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE NO. 71 ON FREE INFORMATION CARD

FREE... Fascinating NEW XENON FLASH TUBE Catalog...

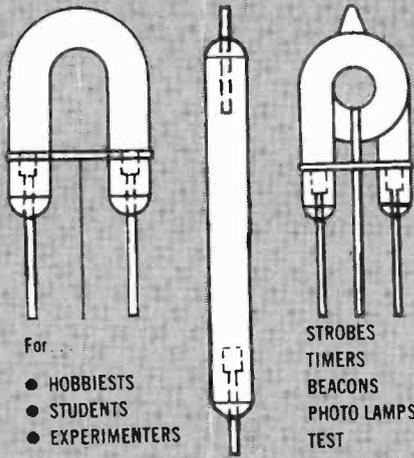OVER 100 ELEVAM XENON FLASH TUBES ILLUSTRATED



For...
● HOBBISTS
● STUDENTS
● EXPERIMENTERS

UNSURPASSED QUALITY AND PRICES

STROBES
TIMERS
BEACONS
PHOTO LAMPS
TEST
PHOTOLYSIS
SYSTEMS


...and more.

CALL OR WRITE FOR YOUR FREE ELEVAM CATALOG

TEC/WEST (U.S.A.) INC.

Kirkeby Center-Suite 1220 10889 Wilshire Blvd.
Los Angeles, CA 90024 (213) 477-9529

CIRCLE NO. 57 ON FREE INFORMATION CARD

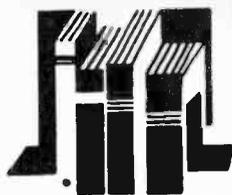

Electronics Library

BASIC SOFTWARE LIBRARY

by R. W. Brown

Here, in two volumes, are dozens of computer programs in 8½" x 11" page size, all written in BASIC, with a wide variety of applications. Volume I covers business and recreational programs, such as those for true interest rate, mortgage term comparisons, checkers, lunar landing, roulette, tank, horse racing, and computer pictures. Volume II, on engineering and statistics, has programs for solving polynomials, integration by spline fits, and one-way analysis of variances. Memory required to store and execute programs is indicated.

Published by Scientific Research Institute, Box 2096, Ashland, VA 23005. Vol. I, 292 pages. Vol. II, 243 pages. Both soft cover, \$24.95 each.

HOBBY/EXPERIMENTER GUIDES

In *Electronic Components* (\$5.25, 104 pages), author M.A. Colwell details the different types of electronic components, what they are and what they do, and how to choose the right component for the job. The lineup includes all the commonly used components, including electromechanical and electromagnetic types. The text tells how to recognize faults and how to prevent breakdowns. Photos and drawings help to identify the various components. *Electronic Diagrams* (\$4.95, 104 pages), also by Mr. Colwell, takes the reader through the logical steps of building up circuit diagrams from elementary circuit symbols. Illustrations and descriptions explain how to read circuit diagrams, block diagrams, flow charts, graphs, and oscillograms. *Printed Circuit Assembly*

(\$4.50, 88 pages), by M.J. Hughes and M.A. Colwell, describes the characteristics of the various bases used in printed-circuit systems and guides the reader through the stages of translating diagrams into pc layouts. Image transfer, etching, milling, and trimming methods are described.

Distributed by Hayden Book Co., Inc., 50 Essex St., Rochelle Park, NJ 07662. Soft cover.

ARRL CODE KIT

The new ARRL Code Kit is a follow-up to the League's popular "Tune in the World with Ham Radio" beginner's package. The Code Kit consists of two one-hour tape cassettes and an illustrated manual. The cassettes contain one-half hour sessions of random text at 5, 7½, 10 and 13 wpm. The use of random characters extends the useful life of the cassettes by making the text impossible to anticipate or memorize. Learning tips, receiving and transmitting techniques, a table of commonly used abbreviations and a schematic and pc layouts for a simple practice oscillator are included in the manual.

Published by the American Radio Relay League, 225 Main St., Newington, CT 06111. Two C-60 cassettes and 30-page soft cover manual. \$8.00.

DIGITAL PRINCIPLES AND APPLICATIONS (SECOND EDITION)

by A. Malvino and D. Leach

This book introduces the reader to digital electronics through a historical discussion, and examination of logic families, number systems, binary codes, Boolean algebra, arithmetic circuits, and sequential logic. Logic simplification, registers, counters, D/A and A/D converters, I/O devices, and memories are explored. Revisions of the book include new chapters on Karnaugh mapping and computer organization, discussions of TTL, ECL, and CMOS logic, material on discrete, dot- and bar-matrix displays, and standard SSI, MSI and LSI circuits. An understanding of semiconductors and electronics is advised. Summaries, glossaries, review questions and problems appear at the end of each chapter. Published by McGraw-Hill Book Co., 1221 Ave. of the Americas, New York, NY 10020. 436 pages. \$13.95 hard cover.

New From Davis Electronics

7200 SERIES MINI COUNTER

60 MHz
600 MHz
(with optional prescaler)



General Purpose Low Cost Counter
Without The Sacrifice Of Basic Performance

"Check the features we have that some other low cost counters don't have."

- All Metal Cabinet
- 8 Digit 4" LED Display
- Input Cable Included
- 12V Operation Possible
- Push Button Controls
- Completely Auto Decimal Point
- Selectable Gate Times (1 sec & .1 sec)
- State of the Art LSI Circuitry
- Sensitivity <10 MV
- Crystal Time Base

ORDER NOW
Call Toll Free
1-800-828-7422

DAVIS

Model 7208 60 MHz Kit \$119.95
Model 7208A 600 MHz Kit \$149.95

DAVIS ELECTRONICS 636 Sheridan Dr., Tona., N.Y. 14150 716/874-5848

CIRCLE NO. 65 ON FREE INFORMATION CARD

projection television

Convert color to Giant Screen with the

f1.85 Projection TV Lens

FASTEST LENS SPEED FOR BRILLIANCE & BRIGHTNESS
3 ELEMENTS; 6 OPTIC SURFACES
FOCAL LENGTH: 12-INCH (305mm)
MEASURES: 6.5" DIA. x 6.5" LENGTH

SPECIAL PRICE \$150

Write For Quantity Prices.
Send \$1 For Building Projection TV.

THE FINEST PROJECTION LENS THAT IS AVAILABLE TODAY

PROJECTAPIX, LTD.

300 WEST 53 STREET
NEW YORK, N.Y. 10019

TELEPHONES: (212) 765-7869

CIRCLE NO. 64 ON FREE INFORMATION CARD

Cramped for Antenna space?



The answer to your problem is here!!!

The McKay DYMEK DA 100.

The DA 100 is a compact, wide dynamic range, broadband, untuned, omni-directional receiving antenna covering the frequency range of 50 kHz to 30 MHz.

The exterior module, a small weather-proof box with a 56 inch (142 cm) whip delivers the signal to the power supply unit through a supplied 50' coaxial cable.

The power supply locates near your general coverage receiver and attaches with a supplied patch cord.

The DA 100 antenna is small, but will equal or outperform a 100' long wire antenna, and is priced within reach of everyone!

Order factory direct. Call toll free today! Money-back guarantee. Rent/own plan available. Complete specs and details on request.

Nationwide 800/854-7769
California 800/472-1783

MasterCard



MK McKay Dymek Company
675 N. Park Ave., P.O. Box 2100
Pomona, Calif. 91766

CIRCLE NO. 32 ON FREE INFORMATION CARD

Operation Assist

If you need information on outdated or rare equipment—a schematic, parts list, etc.—another reader might be able to assist. Simply send a postcard to Operation Assist, POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. For those who can help readers, please respond directly to them. They'll appreciate it. (Only those items regarding equipment not available from normal sources are published.)

Paco Model S-50 push-pull oscilloscope. Schematic and/or service calibration data. David N. Tenney, Apt. C, 1528 Lee St., Charleston, WV 25311

RCA Model 1-MBT-6, S/N RVU-006521 "Strato World" radio. Chrysler Model S/N MB 174 auto radio. Schematics needed. Jose Varas, 515 4th St., Union City, NJ 07087

Heathkit Model OM-3 oscilloscope. Operating and assembly manuals needed. M. Chadwick, 1465 Stuckert Rd., Warrington, PA 18976

Heathkit Model FMO-1 FM oscillator. Manual needed. C.E. Garrison, Meadowdale Rt 3, Warrenton, VA 22186

Heathkit DX100 instruction manual and wiring harness hookup information. A.B. Coleman, 3396 Via Arnez, Lompoc, CA 93436

Knight-Kit wireless broadcaster amplifier. Schematic and/or parts list. John S. Williams, Rt. 1 Box 312 E., Zanesville, OH 43701

Sylvania Model CTR-175W stereo cassette recorder with AM-FM radio. Schematics and operation manual. Stan Pittman, 110 Michigan #115, Lawrence, KS 66044

Precise Model 30 oscilloscope. Need operating instructions. Anthony Vitale, 5222 9th Ave., Brooklyn, NY 11220.

Stephens "Truphonic" midrange horn system. Need hookup data and parts source. Frank J. Burris, 35640 Avenue F, Yucaipa, CA 92399

SCM Marchant Model "Cogito" 240 SR calculator. Logic, schematic and wiring diagrams and operating manual. Dan Entingh, 5111 Colorado Ave., La Junta, CO 81050.

Signal Corp. U.S. Army BC-348-P receiver. Operator's manual needed. Owen Scotland, Box 356, Cayman Islands, B.W.I.

Sierra Model 121A wave analyzer. Schematic and/or service manual. Charles H. Scholten, 1313 Marshall St., Manitowoc, WI 54220

Precision Apparatus Series 10-54 tube and set tester. Operating instructions, schematic and servicing instructions. Martin A. Weiner, 16 Judith Lane, Monsey, NY 10952.

Superior Model 85 tube tester. Tube chart needed. C.A. Harris, Box 20 C, Glasgow AFB, MT 59231

Radio Apparatus Model M-51A 30-50-MHz receiver. Schematic and/or service manual. David Roe, 631 N.W. 22, Oklahoma City, OK 73103.

Dumont Type 304A oscilloscope. Technical information or instruction manual. Glen A. Kilts, 8214 McClelland Pl., Alexandria, VA 22309

Kinsman Duchess Model E electronic organ. Need diagram of generator. W.H. Weiss, 1208 Greenhill Dr., Wausau, WI 54401

Jackson Electronic Model 641-A FM-AM signal generator. Schematic and alignment information. Bob DeVance, Box 13038, Omaha, NB 68113.

Panoramic Model PCA-2 T200 panadaptor. Operator or service manual. Servo Model R5200 receiver. Operator or service manual. John W. Schwerdtfeger, 5361 Westminster, Austin, TX 78723.

Hallcrafters Model SX-71 shortwave receiver. Operating manual or any available information. Jeff Cherry, 603 S. Cedar, Brea, CA 92621.

Pilot Model R-700 stereo receiver. Tape monitor switch and balance control or schematic. Richard K. Shaddock, 209 Camelford Rd., McMurray, PA 15317.

Hallcrafters Model S-40A receiver. Schematic and manual. John Myers, 138 W. Harrison St., Alliance, OH 44601.

Grundig Model 2220-U AM/FM/SW radio (circa 1955). Schematic needed. Al Cowan, 3101 Lorna Rd., #1824, Birmingham, AL 35216.

(continued on page 120)

Includes Functional Tilt Stand!

NEW EICO 270 3 1/2 DIGIT DMM KIT ONLY \$79.95

Introductory Offer—FREE AC ADAPTOR

The first and only lab accuracy portable DMM Kit featuring MOS/LSI IC economy and reliability. Measures DC/AC Volts, Kilohms, DC/AC milliamps in 21 ranges. Polarity indicators and overload protection are provided, and 0.5 inch LED displays give easiest-to-read digital readout to 1999. The 270 features a basic 0.5% DC accuracy, 10 Megohm input impedance, low voltage drop in all current ranges and automatically-flashing overrange indicator. **Assembled \$109.95**

FREE '78 EICO CATALOG

Check reader service card or send 75¢ for first class mail. See your local EICO Dealer or call (212) 272-1134, 9:00 a.m.-5:00 p.m. EST. Major credit cards accepted.

EICO—283 Malta St., Brooklyn, N.Y. 11207



CIRCLE NO. 18 ON FREE INFORMATION CARD

TVT-6
Low cost
Direct Video
Display



only \$35

Don Lancaster's ingenious design provides software controllable options including:

- Scrolling • Full performance cursor
- Over 2K on-screen characters with only 3MHz bandwidth
- Variety of line/character formats including 16/32, 16/64
-even 32/64
- User selectable line lengths

TELL ME MORE!

() Send instruction manual for the TVT-6 Kit with full operational details. \$1 enclosed.

Name: _____

Address: _____

City: _____ State: _____ Zip: _____

RAIA
ELECTRONICS, INC.

() SEND FREE CATALOG

DEPT. 10-P 1020 W. WILSHIRE BLVD., OKLAHOMA CITY, OK 73116

CIRCLE NO. 41 ON FREE INFORMATION CARD

DIGI-KEY CORPORATION

Quality Electronic Components

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES MICROPROCESSORS

Best Values Yet!

| | | |
|--------|---|---------|
| 8080A | 8-BIT CPU, 2 USEC CYCLE | \$12.95 |
| 8212 | 8-BIT I/O PORT | \$ 3.95 |
| 8216 | BI-DIRECTIONAL BUS DRIVER | \$ 4.25 |
| 8224 | CLOCK GENERATOR | \$ 3.95 |
| 8228 | SYSTEM CONTROLLER | \$ 6.95 |
| 8251 | COMMUNICATIONS INTERFACE | \$12.95 |
| 8255 | PERIPHERAL INTERFACE | \$11.95 |
| 1702A | 2K EPROM (256x8) | \$ 6.95 |
| 2708 | 8K EPROM (1Kx8) | \$29.50 |
| 2102-1 | 1K RAM 500 NS | \$ 1.79 |
| SC/MP | 5 VOLT SC/MP CPU | \$ 9.95 |
| 2650 | MICROPROCESSOR 1.25 MHZ-2 CLOCK 40 DIL. | \$24.95 |

8080A CHIP SET

ONE EACH 8080A, 8212, 8224 and 8228 PLUS SIXTEEN 2102-1's — ALL FOR

\$49.95

PRICE BREAKTHROUGH ON 74LS'

| | | | | | | | | | |
|--------|-----|--------|----|---------|-----|---------|-----|---------|-----|
| 74LS00 | 28 | 74LS30 | 28 | 74LS90 | 57 | 74LS157 | 75 | 74LS248 | 79 |
| 74LS01 | 28 | 74LS32 | 33 | 74LS92 | 57 | 74LS158 | 75 | 74LS249 | 79 |
| 74LS02 | 28 | 74LS33 | 33 | 74LS93 | 57 | 74LS160 | 102 | 74LS253 | 84 |
| 74LS03 | 28 | 74LS34 | 33 | 74LS94 | 57 | 74LS161 | 102 | 74LS254 | 84 |
| 74LS04 | 28 | 74LS35 | 33 | 74LS95 | 57 | 74LS162 | 102 | 74LS255 | 84 |
| 74LS05 | 29 | 74LS42 | 67 | 74LS112 | 39 | 74LS163 | 102 | 74LS266 | 39 |
| 74LS08 | 29 | 74LS47 | 79 | 74LS113 | 39 | 74LS164 | 102 | 74LS269 | 79 |
| 74LS09 | 29 | 74LS48 | 77 | 74LS114 | 39 | 74LS168 | 117 | 74LS290 | 65 |
| 74LS10 | 28 | 74LS51 | 28 | 74LS125 | 49 | 74LS169 | 114 | 74LS293 | 49 |
| 74LS11 | 28 | 74LS54 | 28 | 74LS126 | 49 | 74LS170 | 173 | 74LS365 | 67 |
| 74LS12 | 28 | 74LS55 | 28 | 74LS132 | 81 | 74LS173 | 134 | 74LS366 | 67 |
| 74LS13 | 47 | 74LS57 | 39 | 74LS136 | 81 | 74LS174 | 106 | 74LS367 | 67 |
| 74LS14 | 102 | 74LS74 | 39 | 74LS139 | 73 | 74LS175 | 84 | 74LS368 | 67 |
| 74LS15 | 28 | 74LS75 | 53 | 74LS139 | 73 | 74LS190 | 118 | 74LS386 | 39 |
| 74LS20 | 28 | 74LS76 | 39 | 74LS151 | 75 | 74LS191 | 118 | 74LS670 | 234 |
| 74LS21 | 28 | 74LS83 | 39 | 74LS152 | 86 | 74LS196 | 86 | 81102-1 | 179 |
| 74LS22 | 28 | 74LS83 | 39 | 74LS155 | 110 | 74LS197 | 86 | 81159 | 77 |
| 74LS26 | 33 | 74LS86 | 39 | 74LS156 | 75 | 74LS247 | 79 | 811597 | 77 |
| 74LS27 | 33 | | | | | | | 811598 | 77 |

INTEGRATED CIRCUITS TTL, CMOS, LINEAR

| | | | | | | | | | |
|------|----|-------|-----|-------|-----|------|-----|-----------|--------|
| 7400 | 21 | 7476 | 32 | 74181 | 215 | 4012 | 23 | 4520 | 114 |
| 7401 | 21 | 7480 | 70 | 74182 | 219 | 4013 | 40 | 4527 | 168 |
| 7402 | 21 | 7482 | 70 | 74184 | 219 | 4014 | 96 | 4528 | 88 |
| 7403 | 21 | 7483 | 70 | 74185 | 219 | 4015 | 96 | 4585 | 123 |
| 7404 | 21 | 7485 | 89 | 74189 | 310 | 4016 | 114 | 4586 | 123 |
| 7405 | 21 | 7486 | 78 | 74189 | 350 | 4017 | 105 | 8080A | 129.95 |
| 7406 | 25 | 7489 | 219 | 74190 | 123 | 4018 | 105 | CA3046 | 125 |
| 7407 | 25 | 7491 | 70 | 74191 | 123 | 4019 | 23 | LM211N | 75 |
| 7408 | 21 | 7491 | 70 | 74192 | 88 | 4020 | 114 | LM309K | 180 |
| 7409 | 21 | 7492 | 44 | 74193 | 88 | 4021 | 114 | LM324A | 128 |
| 7410 | 21 | 7493 | 44 | 74194 | 88 | 4022 | 96 | LM340T-5 | 125 |
| 7411 | 21 | 7494 | 70 | 74195 | 88 | 4023 | 23 | LM340T-6 | 125 |
| 7412 | 21 | 7495 | 70 | 74196 | 88 | 4024 | 23 | LM340T-7 | 125 |
| 7413 | 25 | 7496 | 70 | 74197 | 88 | 4025 | 23 | LM340T-12 | 125 |
| 7414 | 89 | 74100 | 128 | 74198 | 149 | 4026 | 168 | LM340T-15 | 125 |
| 7415 | 25 | 74101 | 128 | 74199 | 149 | 4027 | 40 | LM340T-18 | 125 |
| 7416 | 25 | 74102 | 61 | 74200 | 149 | 4028 | 168 | LM340T-24 | 125 |
| 7417 | 25 | 74109 | 33 | 74201 | 109 | 4029 | 114 | LM3900N | 88 |
| 7418 | 21 | 74121 | 35 | 74202 | 114 | 4030 | 114 | LM3909N | 69 |
| 7419 | 21 | 74122 | 44 | 74203 | 67 | 4031 | 23 | MC1455V | 100 |
| 7420 | 21 | 74123 | 61 | 74204 | 44 | 4032 | 114 | MC1468V | 100 |
| 7421 | 25 | 74125 | 40 | 74205 | 67 | 4033 | 114 | MC3302P | 115 |
| 7422 | 25 | 74126 | 40 | 74206 | 67 | 4034 | 30 | NE536T | 324 |
| 7423 | 25 | 74127 | 40 | 74207 | 67 | 4035 | 114 | NE540L | 204 |
| 7424 | 25 | 74128 | 40 | 74208 | 67 | 4036 | 70 | NE555A | 88 |
| 7425 | 25 | 74129 | 40 | 74209 | 67 | 4037 | 70 | NE560B | 383 |
| 7426 | 25 | 74130 | 40 | 74210 | 67 | 4038 | 70 | NE567V | 136 |
| 7427 | 33 | 74132 | 70 | 74211 | 67 | 4039 | 70 | NE562B | 383 |
| 7428 | 28 | 74134 | 163 | 74212 | 67 | 4040 | 70 | NE565A | 88 |
| 7429 | 25 | 74135 | 65 | 74213 | 67 | 4041 | 70 | NE565A | 88 |
| 7430 | 21 | 74136 | 65 | 74214 | 67 | 4042 | 70 | NE566V | 128 |
| 7431 | 25 | 74137 | 65 | 74215 | 67 | 4043 | 70 | NE567V | 136 |
| 7432 | 25 | 74138 | 65 | 74216 | 67 | 4044 | 70 | uA709CV | 44 |
| 7433 | 30 | 74139 | 65 | 74217 | 67 | 4045 | 70 | uA710CA | 44 |
| 7434 | 25 | 74140 | 65 | 74218 | 67 | 4046 | 70 | uA711CA | 44 |
| 7435 | 25 | 74141 | 65 | 74219 | 67 | 4047 | 70 | uA712CA | 44 |
| 7436 | 25 | 74142 | 65 | 74220 | 67 | 4048 | 70 | uA713CA | 44 |
| 7437 | 25 | 74143 | 65 | 74221 | 67 | 4049 | 70 | uA714CA | 44 |
| 7438 | 25 | 74144 | 65 | 74222 | 67 | 4050 | 70 | uA715CA | 44 |
| 7439 | 25 | 74145 | 65 | 74223 | 67 | 4051 | 126 | uA716CA | 44 |
| 7440 | 21 | 74146 | 65 | 74224 | 67 | 4052 | 126 | uA717CA | 44 |
| 7441 | 21 | 74147 | 65 | 74225 | 67 | 4053 | 126 | uA718CA | 44 |
| 7442 | 53 | 74148 | 103 | 74226 | 67 | 4054 | 126 | uA719CA | 44 |
| 7443 | 53 | 74149 | 103 | 74227 | 67 | 4055 | 126 | uA720CA | 44 |
| 7444 | 53 | 74150 | 61 | 74228 | 67 | 4056 | 126 | uA721CA | 44 |
| 7445 | 70 | 74151 | 60 | 74229 | 67 | 4057 | 126 | uA722CA | 44 |
| 7446 | 70 | 74152 | 60 | 74230 | 67 | 4058 | 126 | uA723CA | 44 |
| 7447 | 70 | 74153 | 60 | 74231 | 67 | 4059 | 126 | uA724CA | 44 |
| 7448 | 70 | 74154 | 60 | 74232 | 67 | 4060 | 126 | uA725CA | 44 |
| 7449 | 70 | 74155 | 60 | 74233 | 67 | 4061 | 126 | uA726CA | 44 |
| 7450 | 70 | 74156 | 60 | 74234 | 67 | 4062 | 126 | uA727CA | 44 |
| 7451 | 21 | 74157 | 60 | 74235 | 67 | 4063 | 126 | uA728CA | 44 |
| 7452 | 21 | 74158 | 60 | 74236 | 67 | 4064 | 126 | uA729CA | 44 |
| 7453 | 21 | 74159 | 60 | 74237 | 67 | 4065 | 126 | uA730CA | 44 |
| 7454 | 21 | 74160 | 60 | 74238 | 67 | 4066 | 126 | uA731CA | 44 |
| 7455 | 21 | 74161 | 60 | 74239 | 67 | 4067 | 126 | uA732CA | 44 |
| 7456 | 21 | 74162 | 60 | 74240 | 67 | 4068 | 126 | uA733CA | 44 |
| 7457 | 21 | 74163 | 60 | 74241 | 67 | 4069 | 126 | uA734CA | 44 |
| 7458 | 21 | 74164 | 60 | 74242 | 67 | 4070 | 126 | uA735CA | 44 |
| 7459 | 21 | 74165 | 60 | 74243 | 67 | 4071 | 126 | uA736CA | 44 |
| 7460 | 21 | 74166 | 60 | 74244 | 67 | 4072 | 126 | uA737CA | 44 |
| 7461 | 21 | 74167 | 60 | 74245 | 67 | 4073 | 126 | uA738CA | 44 |
| 7462 | 21 | 74168 | 60 | 74246 | 67 | 4074 | 126 | uA739CA | 44 |
| 7463 | 21 | 74169 | 60 | 74247 | 67 | 4075 | 126 | uA740CA | 44 |
| 7464 | 21 | 74170 | 60 | 74248 | 67 | 4076 | 126 | uA741CA | 44 |
| 7465 | 21 | 74171 | 60 | 74249 | 67 | 4077 | 126 | uA742CA | 44 |
| 7466 | 21 | 74172 | 60 | 74250 | 67 | 4078 | 126 | uA743CA | 44 |
| 7467 | 21 | 74173 | 60 | 74251 | 67 | 4079 | 126 | uA744CA | 44 |
| 7468 | 21 | 74174 | 60 | 74252 | 67 | 4080 | 126 | uA745CA | 44 |
| 7469 | 21 | 74175 | 60 | 74253 | 67 | 4081 | 126 | uA746CA | 44 |
| 7470 | 21 | 74176 | 60 | 74254 | 67 | 4082 | 126 | uA747CA | 44 |
| 7471 | 21 | 74177 | 60 | 74255 | 67 | 4083 | 126 | uA748CA | 44 |
| 7472 | 21 | 74178 | 60 | 74256 | 67 | 4084 | 126 | uA749CA | 44 |
| 7473 | 21 | 74179 | 60 | 74257 | 67 | 4085 | 126 | uA750CA | 44 |
| 7474 | 21 | 74180 | 60 | 74258 | 67 | 4086 | 126 | uA751CA | 44 |
| 7475 | 21 | 74181 | 60 | 74259 | 67 | 4087 | 126 | uA752CA | 44 |

DIAMOND
MS54
4 1/2" Length
\$6.58

See Our Catalog For More Diamond Tool

A-C-E 200-K
Part No. 923333
18 96

Two 5-way binding posts
Size: 4.9" x 1.6" by 5-1/16"
Kit form — lowest cost

Digi-Key Stocks the Entire AP Line

ok
WSU-30 Regular Wrap ... \$5.95
WSU-30M Modified Wrap ... \$6.95

STRIPS — WRAPS — UNWRAPS

TOTALLY ASSEMBLED CRT AT LOWER THAN KIT PRICE

CRT TERMINAL
\$895.00
MANUAL ONLY \$200

Bishop Graphics 5"x6"
1X Scale PCB Design Template
No. 3365 \$12.50

The Digi-Key Catalog features many more quality Bishop Graphics products.

LED DIGITS and LAMPS

| | | |
|--------|-----------------------|-----------------------|
| FN357 | 375' Single Digit, CC | \$1.35 |
| FN500 | 5' Single Digit, CC | \$1.35 |
| FN507 | 5' Single Digit, CC | \$1.35 |
| FN600 | 8' Single Digit, CC | \$2.50 |
| FN607 | 8' Single Digit, CC | \$2.50 |
| NS312 | 3' Dual Digits, CC | \$2.20 |
| NS374 | 3' Dual Digits, CC | \$2.20 |
| NSN82 | 5' Dual Digits, CC | \$2.60 |
| NSN84 | 5' Dual Digits, CC | \$2.60 |
| NSN85 | 5' Dual Digits, CC | \$2.60 |
| NSN86 | 5' Dual Digits, CC | \$2.60 |
| NSN87 | 5' Dual Digits, CC | \$2.60 |
| NSN88 | 5' Dual Digits, CC | \$2.60 |
| NSN89 | 5' Dual Digits, CC | \$2.60 |
| NSN90 | 5' Dual Digits, CC | \$2.60 |
| NS2053 | 1 1/4" Lamp | \$1.80/10 \$16.00/100 |
| NS2056 | 1 1/4" Lamp | \$1.80/10 \$16.00/100 |

SILICON TRANSISTORS

| | | | | | | | | |
|----------|----|---------|---------|----|---------|--------|----|---------|
| MPS918 | 16 | 1.55/10 | MPS3640 | 16 | 1.55/10 | PNS133 | 16 | 1.55/10 |
| MPS930 | 16 | 1.55/10 | MPS3641 | 16 | 1.55/10 | PNS134 | 16 | 1.55/10 |
| MPS930A | 16 | 1.55/10 | MPS3642 | 16 | 1.55/10 | PNS137 | 16 | 1.55/10 |
| MPS2222A | 16 | 1.55/10 | MPS3643 | 16 | 1.55/10 | PNS138 | 16 | 1.55/10 |
| MPS2369A | 16 | 1.55/10 | MPS3644 | 16 | 1.55/10 | PNS139 | 16 | 1.55/10 |
| MPS2712 | 16 | 1.55/10 | 2N3906 | 16 | 1.55/10 | 2N5210 | 16 | 1.55/10 |
| MPS2907A | 16 | 1.55/10 | 2N4124 | 16 | 1.55/10 | DK3055 | 68 | 6.59/10 |
| MPS3392 | 16 | 1.55/10 | 2N4126 | 16 | 1.55/10 | 2N3055 | 99 | 9.20/10 |
| MPS3393 | 16 | 1.55/10 | 2N4401 | 16 | 1.55/10 | MJ2955 | 99 | 9.20/10 |
| MPS3394 | 16 | 1.55/10 | 2N4403 | 16 | 1.55/10 | MPF102 | 36 | 3.35/10 |
| MPS3395 | 16 | 1.55/10 | 2N4410 | 16 | 1.55/10 | 2N5457 | 48 | 4.50/10 |
| MPS3563 | 16 | 1.55/10 | 2N5087 | 16 | 1.55/10 | MJ5A13 | 28 | 2.60/10 |
| MPS3565 | 16 | 1.55/10 | 2N5089 | 16 | 1.55/10 | MJ2955 | 99 | 9.20/10 |
| MPS3638 | 16 | 1.55/10 | PNS129 | 16 | 1.55/10 | TIP120 | 99 | 9.20/10 |

SEND FOR OUR FREE CATALOG
WE STOCK A WIDE VARIETY OF PARTS NOT IN THIS AD PLUS MANY SPECIALLY PRICED BARGAINS!

5% CARBON FILM RESISTORS

MORE THAN 20,000 DIFFERENT COMPONENTS

7400 TTL

| | | | | | |
|------|------|-------|------|-------|------|
| 7400 | .18 | 7442 | 1.08 | 74107 | .49 |
| 7401 | .21 | 7448 | 1.15 | 74121 | .55 |
| 7402 | .21 | 7450 | .26 | 74122 | .49 |
| 7404 | .21 | 7451 | .27 | 74123 | 1.06 |
| 7405 | .24 | 7453 | .27 | 74125 | .60 |
| 7407 | .45 | 7454 | .41 | 74126 | .81 |
| 7408 | .25 | 7460 | .22 | 74132 | 3.00 |
| 7409 | .25 | 7472 | .39 | 74141 | 1.15 |
| 7410 | .20 | 7473 | .45 | 74150 | 1.10 |
| 7411 | .30 | 7474 | .45 | 74151 | 1.25 |
| 7413 | .85 | 7475 | .80 | 74153 | 1.35 |
| 7416 | .43 | 7482 | 1.75 | 74154 | 1.54 |
| 7417 | .43 | 7483 | 1.15 | 74157 | 1.30 |
| 7420 | .21 | 7485 | 1.12 | 74161 | 1.45 |
| 7422 | 1.50 | 7486 | .45 | 74164 | 1.65 |
| 7425 | .43 | 7489 | 2.48 | 74185 | 1.65 |
| 7427 | .37 | 7490 | .69 | 74186 | 1.10 |
| 7428 | .35 | 7491 | 1.20 | 74174 | 1.95 |
| 7430 | .26 | 7492 | .82 | 74175 | 1.95 |
| 7432 | .31 | 7493 | .82 | 74180 | 1.05 |
| 7437 | .47 | 7494 | .91 | 74181 | 3.55 |
| 7438 | .40 | 7495 | .91 | 74191 | 1.50 |
| 7440 | .21 | 7496 | .91 | 74195 | 1.00 |
| 7441 | 1.10 | 74100 | 1.25 | 74197 | 1.00 |

74L SERIES TTL

| | | | | | |
|--------|------|---------|-----|---------|------|
| 74L00 | .33 | 74LS04 | .45 | 74LS113 | .98 |
| 74L10 | .33 | 74LS10 | .39 | 74LS138 | 1.89 |
| 74L30 | .33 | 74LS20 | .39 | 74LS174 | 2.50 |
| 74L42 | 1.50 | 74LS51 | .39 | 74LS386 | 5.50 |
| 74L86 | .69 | 74LS74 | .85 | 74LS153 | 2.25 |
| 74LS00 | .39 | 74LS112 | .65 | 74S387 | 1.95 |

74H00 TTL

| | | | | | |
|-------|-----|-------|-----|-------|-----|
| 74H00 | .33 | 74H11 | .33 | 74H53 | .39 |
| 74H01 | .33 | 74H20 | .33 | 74H55 | .39 |
| 74H04 | .33 | 74H21 | .33 | 74H73 | .59 |
| 74H06 | .35 | 74H30 | .33 | 74H74 | .59 |
| 74H10 | .33 | 74H40 | .33 | 74H76 | .65 |

MOTOROLA

| | | | |
|---------|------|-----------|------|
| MC663P | 2.50 | MC1460 | 3.95 |
| MC666P | 1.60 | MC1469R | 2.50 |
| MC670P | 1.60 | MC1489 | 4.60 |
| MC679P | 2.50 | MC1496 | 1.65 |
| MC725P | 1.50 | MC1510G | 8.00 |
| MC789P | 1.50 | MC1514L | 4.50 |
| MC790P | 1.50 | MC1595L | 6.25 |
| MC817P | 1.30 | MC1723CL | 3.60 |
| MC836P | 1.35 | MC1741CG | 1.20 |
| MC844 | 1.25 | MC1810P | 1.25 |
| MC853P | 2.25 | MC3004L | 2.25 |
| MC876P | 2.25 | MC3007P | 2.25 |
| MC1004L | 1.25 | MC3021L | 2.15 |
| MC1010L | 1.25 | MC3060L | 2.65 |
| MC1305 | 1.95 | MC3062L | 3.00 |
| MC1352P | 1.55 | MC4024P | 2.20 |
| MC1357 | 1.70 | MC4044P | 4.80 |
| MC1371 | 1.85 | MC14507CP | 1.25 |
| MC1439 | 2.65 | MC14511CP | 2.76 |
| MC1458P | .50 | MC14512CP | 1.70 |

CMOS

| | | | |
|--------|------|--------|------|
| 4001AE | .29 | 4023AE | .29 |
| 4002AE | .29 | 4024AE | 1.50 |
| 4007AE | .29 | 4025AE | .35 |
| 4010AE | .58 | 4028AE | 1.60 |
| 4011AE | .29 | 4029AE | 2.90 |
| 4012AE | .29 | 4030AE | .65 |
| 4015AE | 1.25 | 4037AE | 4.50 |
| 4016AE | .65 | 4040AE | 2.40 |
| 4018AE | 1.10 | 4044AE | 1.50 |
| 4019AE | .65 | 4049AE | .75 |
| 4020AE | 1.75 | 4050AE | .75 |
| 4021AE | 1.50 | | |

RECTIFIERS

| | | |
|--------|------|-------|
| 1N4001 | .60 | 5.00 |
| 1N4002 | .70 | 6.00 |
| 1N4003 | .80 | 7.00 |
| 1N4004 | .90 | 8.00 |
| 1N4005 | 1.00 | 9.00 |
| 1N4006 | 1.10 | 10.00 |
| 1N4007 | 1.20 | 11.00 |

UNIUNCTIONS

| | | |
|-----------|-----|------------|
| 2N2160 | .65 | MU4892.50 |
| 2N2646 | .45 | MU4893.50 |
| 2N2647 | .55 | MU4894.50 |
| 2N4851 | .75 | 2N6027 .55 |
| 2N4852 | .75 | 2N6028 .70 |
| 2N4870 | .50 | D5E37 .35 |
| 2N4871 | .50 | MU10 .35 |
| 2N4871.50 | | MU20 .40 |

HARDWARE - SOCKETS

| | |
|---|------------------------|
| Nylon Screws, Nuts and Rivets - 50 piece assortment | \$1.99 |
| MK 20 TO-3 Mounting Kit | 5 for \$9.99 |
| IC-505 Mica and Bushing | |
| TO-3, TO-66 or TO-22 | |
| NT Socket | 14-Pin DIL \$1.25 each |
| IC Socket | 16-Pin DIL \$2.27 each |
| Wire Wrap | 16-Pin DIL \$3.32 each |

POPULAR JEDEC TYPES

| | | | | | | | | | | | |
|--------|------|---------|------|---------|------|--------|------|---------|------|--------|------|
| 1N34 | .25 | 2N1540 | .90 | 2N2712 | .18 | 2N3394 | .17 | 2N3856 | .20 | 2N4402 | .16 |
| 1N60 | .25 | 2N1544 | .80 | 2N2894 | .40 | 2N3414 | .17 | 2N3866 | 1.25 | 2N4403 | .20 |
| 1N270 | .25 | 2N1554 | 1.25 | 2N2903 | 3.30 | 2N3415 | .18 | 2N3903 | 1.10 | 2N4409 | .20 |
| 1N914 | .10 | 2N1560 | 2.80 | 2N2904 | .25 | 2N3416 | .19 | 2N3904 | .16 | 2N4410 | .16 |
| 1N4148 | .25 | 2N1565 | 1.75 | 2N2904A | .30 | 2N3417 | .20 | 2N3905 | .16 | 2N4416 | .75 |
| 1S1555 | .35 | 2N1613 | .50 | 2N2905 | .25 | 2N3442 | 1.85 | 2N3906 | .16 | 2N4441 | 1.00 |
| | | 2N1711 | .50 | 2N2905A | .30 | 2N3553 | 1.50 | 2N3954A | 3.75 | 2N4442 | 1.15 |
| 2N1713 | 1.75 | 2N1907 | 4.10 | 2N2906 | .25 | 2N3563 | .20 | 2N3955 | 2.45 | 2N4443 | 1.35 |
| 2N338A | 1.05 | 2N2102 | .70 | 2N2906A | .30 | 2N3565 | .20 | 2N3957 | 1.25 | 2N4452 | .55 |
| 2N404 | .75 | 2N2160 | .70 | 2N2907 | .25 | 2N3638 | .20 | 2N3958 | 1.20 | 2N5061 | .30 |
| 2N443 | 2.50 | 2N2188 | .25 | 2N2907A | .30 | 2N3642 | .20 | 2N4037 | .60 | 2N5064 | .50 |
| 2N508A | .45 | 2N218A | .30 | 2N2913 | .75 | 2N3643 | .20 | 2N4093 | .85 | 2N5130 | .20 |
| 2N706 | .25 | 2N2219 | .25 | 2N2914 | 1.40 | 2N3645 | .20 | 2N4124 | .16 | 2N5138 | .15 |
| 2N718 | .25 | 2N2219A | .30 | 2N3019 | 1.00 | 2N3646 | .14 | 2N4126 | .20 | 2N5139 | .50 |
| 2N718A | .30 | 2N2221 | .25 | 2N3053 | .30 | 2N3731 | 3.75 | 2N4141 | .20 | 2N5296 | .50 |
| 2N918 | .60 | 2N2221A | .30 | 2N3054 | .70 | 2N3740 | 1.00 | 2N4142 | .20 | 2N5296 | .50 |
| 2N930 | .25 | 2N2222 | .25 | 2N3055 | .75 | 2N3771 | 1.75 | 2N4143 | .20 | 2N5306 | .20 |
| 2N956 | .30 | 2N2222A | .30 | 2N3227 | 1.00 | 2N3772 | 1.90 | 2N4220A | .45 | 2N5400 | .40 |
| 2N1302 | 1.25 | 2N2270 | .40 | 2N3247 | 3.40 | 2N3773 | 3.00 | 2N4234 | .95 | 2N5401 | .50 |
| 2N1305 | .75 | 2N2369 | .25 | 2N3250 | .50 | 2N3819 | 4.00 | 2N4400 | 1.16 | 2N5457 | .35 |
| 2N1420 | .20 | 2N2484 | .32 | 2N3393 | .20 | 2N3823 | .70 | 2N4401 | .16 | 2N5458 | .30 |

ALL PARTS GUARANTEED WRITE FOR FREE CATALOG

CIRCLE NO 35 ON FREE INFORMATION CARD

LINEAR

| | | | | | |
|---------|------|---------|------|---------|------|
| 75450BP | .49 | LM301H | .35 | LM741CH | .45 |
| 75451BP | .39 | LM307H | .35 | LM747 | .90 |
| 75452BP | .39 | LM309K | 1.25 | LM1748H | .45 |
| 75453BP | .39 | LM311H | .90 | LM1458N | .80 |
| 75454BP | .39 | LM318N | 1.50 | N5566V | 1.50 |
| 75491BP | .79 | LM339N | 1.85 | N5558 | 1.50 |
| 75492BP | .85 | LM351AN | .65 | N5565V | .60 |
| CA3006 | 1.60 | LM370N | 1.25 | N5566 | 1.50 |
| CA3006 | 3.50 | LM380N | 1.45 | UA702 | .80 |
| CA3018 | 1.10 | LM566 | 2.25 | UA703CH | .45 |
| CA3018A | 1.80 | LM711CH | .80 | UA709CH | .30 |
| CA3026 | 1.50 | LM723H | .75 | UA749CH | .45 |
| CA3046 | .35 | LM741CN | .45 | | |

NEW FROM NEW-TONE

Dry Transfer Patterns for PC Boards, Includes IC pads, donuts, angles, and 3-and 4-conductor pads. Over 225 patterns on a 2" x 7 1/4" sheet \$1.49

PC BOARDS - MIL GRADE

Glass-epoxy. 2 oz. copper.

6" x 3" \$.50 • 6" x 6" \$.90 • 6" x 8" \$1.20

5400 SERIES

| | | | | | |
|------|------|--------|------|-----------|------|
| 5400 | 1.00 | 5475 | 1.50 | LM340K-5 | 1.95 |
| 5404 | 1.25 | 5486 | 1.90 | LM340K-6 | 1.95 |
| 5410 | 1.00 | 5493 | 2.00 | LM340K-8 | 1.95 |
| 5426 | 1.25 | 54100 | 1.80 | LM340K-15 | 1.95 |
| 5473 | 1.50 | 54LS04 | 1.00 | LM340K-18 | 1.95 |
| | | | | LM340K-24 | 1.95 |
| | | | | LM340T-5 | 1.75 |
| | | | | LM340T-6 | 1.75 |
| | | | | LM340T-8 | 1.75 |
| | | | | LM340T-12 | 1.75 |
| | | | | LM340T-15 | 1.75 |
| | | | | LM340T-18 | 1.75 |
| | | | | LM340T-24 | 1.75 |

RESISTORS

1/4 Watt ± 5% Packed 5 of any one value \$25
 1/2 Watt ± 5% Packed 5 of any one value \$30
 STANDARD RESISTANCE VALUES

MINIMUM ORDER \$5.00

All orders add \$1.00 Postage and Handling.
 Canada \$1.50.
 N.J. Residents add 5% sales tax

ELECTROLYTIC CAPACITORS

| | | | | | |
|---------|-------------|-----|----------|--------------|-----|
| 2.2MF50 | Axial Leads | .15 | 30MF25 | Radial Leads | .18 |
| 3.3MF10 | Axial Leads | .15 | 47MF25 | Radial Leads | .19 |
| 3.3MF10 | No Polarity | .15 | 47MF50 | Radial Leads | .24 |
| 10MF25 | Axial Leads | .15 | 100MF16 | Radial Leads | .19 |
| 10MF50 | Axial Leads | .16 | 100MF25 | Radial Leads | .24 |
| 10MF150 | Axial Leads | .20 | 500MF50 | Axial Leads | .60 |
| 25MF35 | Axial Leads | .18 | 1000MF35 | Axial Leads | .65 |

MICROPROCESSOR

| | | | | | |
|--------|------|---------|-------|-------|-------|
| C1702A | 9.95 | 2708 | 34.95 | 8008 | 19.95 |
| 2101 | 5.75 | C5101-3 | 4.50 | 8080A | 19.95 |
| 2102 | 1.75 | MM5013 | 3.25 | 8224 | 10.45 |

Contact us for all your microprocessor needs.

JAPANESE TRANSISTORS

| | | | | | | | | | |
|--------|------|--------|------|--------|------|---------|------|--------|------|
| 2SA473 | .75 | 2SC373 | .70 | 2SC778 | 3.00 | 2SC1306 | 4.75 | 2SD180 | 2.75 |
| 2SA484 | 3.00 | 2SC374 | .70 | 2SC777 | 4.00 | 2SC1307 | 5.75 | 2SD187 | .80 |
| 2SA489 | .80 | 2SC375 | .65 | 2SC778 | 4.00 | 2SC1308 | 4.75 | 2SD188 | .95 |
| 2SA495 | 1.65 | 2SC380 | .70 | 2SC781 | 3.00 | 2SC1317 | .60 | 2SD201 | 1.95 |
| 2SA496 | 1.15 | 2SC381 | .70 | 2SC784 | .70 | 2SC1318 | .70 | 2SD213 | 3.75 |
| 2SA497 | 1.00 | 2SC382 | .70 | 2SC785 | 1.00 | 2SC1327 | .70 | 2SD218 | 4.75 |
| 2SA562 | 1.70 | 2SC387 | .70 | 2SC788 | 2.15 | 2SC1342 | .50 | 2SD223 | 4.50 |
| 2SA564 | 1.50 | 2SC394 | .70 | 2SC789 | 1.00 | 2SC1347 | .60 | 2SD234 | 1.00 |
| 2SA806 | 4.25 | 2SC403 | .65 | 2SC790 | 1.75 | 2SC1359 | .65 | 2SD235 | 1.00 |
| 2SA828 | .65 | 2SC454 | .65 | 2SC793 | 2.50 | 2SC1377 | 5.50 | 2SD257 | 2.00 |
| 2SA834 | 1.25 | 2SC458 | .70 | 2SC798 | 3.10 | 2SC1382 | 1.00 | 2SD281 | .80 |
| 2SA836 | 1.25 | 2SC460 | .70 | 2SC799 | 3.50 | 2SC1383 | .75 | 2SD287 | 4.00 |
| 2SA843 | .85 | 2SC478 | .80 | 2SC815 | .75 | 2SC1384 | .85 | 2SD288 | 1.00 |
| 2SA873 | .85 | 2SC481 | 1.85 | 2SC821 | 4.00 | 2SC1447 | 1.25 | 2SD291 | .85 |
| 2SA878 | .75 | 2SC482 | 1.75 | 2SC828 | .75 | 2SC1448 | 1.25 | 2SD300 | 2.50 |
| 2SA879 | 3.75 | 2SC484 | 1.75 | 2SC829 | .75 | 2SC1449 | 1.30 | 2SD313 | 1.10 |
| 2SA880 | 3.75 | 2SC485 | 3.25 | 2SC830 | 1.80 | 2SC1475 | 1.50 | 2SD314 | 1.10 |
| 2SA882 | .85 | 2SC493 | 2.75 | 2SC838 | .70 | 2SC1507 | 1.25 | 2SD315 | .75 |
| 2SA883 | .90 | 2SC494 | 3.50 | 2SC839 | .85 | 2SC1589 | 1.25 | 2SD318 | .95 |
| 2SA884 | .95 | 2SC495 | 1.10 | 2SC863 | 1.00 | 2SC167 | | | |

CRYSTALS

THESE FREQUENCIES ONLY

| Part # | Frequency | Case/Style | Price |
|--------|--------------|------------|--------|
| CY1A | 1.000 MHz | HC33/U | \$5.95 |
| CY2A | 2.000 MHz | HC33/U | \$5.95 |
| CY2.01 | 2.010 MHz | HC33/U | \$1.95 |
| CY3A | 4.000 MHz | HC18/U | \$4.95 |
| CY7A | 5.000 MHz | HC18/U | \$4.95 |
| CY12A | 10.000 MHz | HC18/U | \$4.95 |
| CY14A | 14.31818 MHz | HC18/U | \$4.95 |
| CY19A | 18.000 MHz | HC18/U | \$4.95 |
| CY22A | 20.000 MHz | HC18/U | \$4.95 |
| CY30B | 32.000 MHz | HC18/U | \$4.95 |

XR-2206KB Kit \$29.95 Special XR-2206KA Kit \$19.95

| WAVEFORM GENERATORS | EXAR | XR-555CP | \$ 39 |
|---------------------|------|----------|----------|
| XR-205 | | | \$ 58.40 |
| XR-2206CP | | | 3.85 |
| XR-2207CP | | | 3.85 |

STEREO DECODERS

| | | | | | |
|-----------|--------|---------|------|----------|------|
| XR-1310CP | \$3.20 | XR-1468 | 3.85 | XR-210 | 5.20 |
| XR-1310EP | 3.20 | XR-1468 | 5.80 | XR-215 | 6.60 |
| XR-1800P | 3.20 | XR-1489 | 4.80 | XR-567CP | 1.95 |
| XR-2567 | 2.99 | XR-2208 | 5.20 | XR-567CT | 1.70 |

CONNECTORS

PRINTED CIRCUIT EDGE-CARD

156 Spacing-Tin-Double Read-Out

| Bifurcated Contacts | Fits .054 to .070 P.C. Cards | Price |
|------------------------|------------------------------|--------|
| 15/30 | PINS (Solder Eyelet) | \$1.95 |
| 18/36 | PINS (Solder Eyelet) | \$2.49 |
| 22/44 | PINS (Solder Eyelet) | \$2.95 |
| 50/100 | PINS (Wire Wrap) | \$6.95 |
| 50/100A (1.00 Spacing) | PINS (Wire Wrap) | \$6.95 |

25 PIN-D SUBMINIATURE

| | | |
|-------|--------|--------|
| DB25P | PLUG | \$3.25 |
| DB25S | SOCKET | \$4.95 |

HEAT SINKS

| | | |
|----------|---|--------|
| 205-CB | Beryllium Copper w-black finish for TO-5 | \$.25 |
| 291-.36H | Aluminum for TO-220 Transistors & Regulators | \$.25 |
| 680-.75A | Black Anodized Aluminum for TO-3 | \$1.60 |
| 401-A | Black Anodized Aluminum — predrilled mounting holes for TO-3 — 4 1/4 x 1 1/4 x 2" | \$1.75 |

DIP SWITCHES

| | | |
|-----------------------|---------------|------------|
| #206-4 (8 pin dip) | 4 switch unit | \$1.75 ea. |
| #206-7 (14 pin dip) | 7 switch unit | \$1.95 ea. |
| #206-8 (16 pin dip) | 8 switch unit | \$2.25 ea. |

Etching Kits (cannot be shipped via air)

| | | |
|----------|---|-------------|
| 32 X A-1 | P.C. Etch Materials Kit enough for 5 circuit boards | \$29.95 ea. |
| 27 X A-1 | Etched Circuit Kit Complete kit — only add water | \$ 9.95 ea. |

Plugboards

| | | |
|-------|---|-------------|
| 3662 | 6.5 x 4.5 x 1/16 Epoxy Glass P-Pattern-44 P.C. Taps-spaced 156" | \$ 6.95 ea. |
| 22/44 | Mating connector for plugboard — 22 pin double row | \$ 2.95 ea. |

8800V Universal Microcomputer/Processor plugboard — Epoxy Glass — complete with heatsink and mounting hardware \$5.313 X 10 X 1/16 copper clad \$19.95 ea.

1/16 VECTOR BOARD

| Material | Part No. | Hole Spacing | P.Pattern | W | L | Price |
|-------------------------|----------------|--------------|-----------|------|------|-------|
| PHENOLIC | 68P44 062X4XP | 4.50 | 6.50 | 1.72 | 1.54 | |
| | 169P44 029X3XP | 4.50 | 17.00 | 3.69 | 3.32 | |
| EPOXY GLASS | 68P44 062 | 4.50 | 6.50 | 7.07 | 1.86 | |
| | 68P44 062 | 4.50 | 8.50 | 2.36 | 2.31 | |
| EPOXY GLASS COPPER CLAD | 169P44 062 | 4.50 | 17.00 | 5.04 | 4.53 | |
| | 169P44 062 | 8.50 | 17.00 | 9.23 | 8.26 | |
| | 169P44 062C1 | 4.50 | 17.00 | 6.80 | 6.12 | |

SLIT-N-WRAP WIRE WRAP TOOL

- Slits and opens insulation exposing bare wire
- No pre-cutting or pre-stripping.
- Comes complete with two - 100 ft spools #28 AWG wire

Model P180 \$24.50

HEXADECIMAL ENCODER 19-KEY PAD

- 1-0
- ABCDEF
- Return Key
- Optional Key (Period)
- Key

\$10.95 each

63 KEY KEYBOARD \$24.95

This keyboard features 63 unenclosed SPST keys, unattached to any kind of P.C.B. A very solid molded plastic 13 x 4 1/2 case suits most applications.

HD0165 16 LINE TO FOUR BIT PARALLEL KEYBOARD ENCODER CHIP \$7.95

TOOLS

| | | |
|--------|-------------------------------------|------------|
| A97MS | Diagonal Cutter - 4" semi-flush cut | \$8.50 ea. |
| A110MS | Chain Nose Pliers - 4 1/2" long | 7.50 ea. |
| T-6 | Wire Stripper - #16 to #26 gauge | 3.75 ea. |
| 55B | Wire Stripper - #10 to #20 gauge | 2.50 ea. |
| CS-8 | Cutter-Crimper Tool - 8 1/4" long | 8.50 ea. |

Nibbling Tool — Cuts, Trims or Notches Metal up to #18 gauge 6.95 ea.
Nibbling Tool Replacement Punch 3.75 ea.

PERMACEL® P-29 PLUS Electrical Tape - All Weather 3/4" wide x 66 ft. Black vinyl \$6.95/10 roll package

MICROPROCESSOR COMPONENTS

| | | | |
|---------------------------------|---------|-------------------------------------|---------|
| 8080A CPU | \$19.95 | 8228 System Controller - Bus Driver | \$10.95 |
| 8212 8 Bit Input/Output | 4.95 | MC6800 8 Bit MPU | 22.50 |
| 8214 Priority Interrupt Control | 15.95 | MC6820 Periph. Interface Adapter | 15.00 |
| 8216 Bi-Directional Bus Driver | 6.95 | MC6810AP1 128 x 8 Static RAM | 6.00 |
| 8224 Clock Generator/Driver | 10.95 | MC6830L8 1024 x 8 Bit RDM | 18.00 |
| CDP1802 - with user manual | 39.95 | Z80 CPU | 49.95 |

| CPU'S | RAM'S | PROMS |
|---------------------|----------------------------|------------|
| 3080 Super 8008 | 1101 256 x 1 Static | 4N83 3.95 |
| 8080A Super 8008 | 2101 256 x 4 Static | 8T20 2.00 |
| 2650 8 BIT MPU | 2102 1024 x 1 Static | 8T87 2.00 |
| | 2107/5280 4096 x 1 Dynamic | 93421 7.95 |
| 2504 1024 Dynamic | 2111 256 x 4 Static | 93422 7.95 |
| 2518 Hex 32 BIT | 2189 16 x 4 Static | 93423 7.95 |
| 2519 Hex 40 BIT | 8101 256 x 4 Static | 93424 7.95 |
| 2524 512 Dynamic | 8111 256 x 4 Static | 93425 7.95 |
| 2525 1024 Dynamic | 8999 16 x 4 Static | 93426 7.95 |
| 2527 Dual 256 BIT | 9102 1024 x 1 Static | 93427 7.95 |
| 2529 Dual 512 BIT | 74220 256 x 1 Static | 93428 7.95 |
| 2532 Quad 80 BIT | 93421 768 x 1 Static | 93429 7.95 |
| 2533 1024 Static | 93422 2K x 1 Dynamic | 93430 7.95 |
| 3341 File | | |
| 7415670 16 x 4 Reg. | | |

PARATRONICS

Featured on February's Front Cover of Popular Electronics

Logic Analyzer Kit MODEL 100A \$229.00/Kit

- Analyzes any type of digital system.
- Checks data rates in excess of 8 million words per second
- Trouble shoot TTL, CMOS, DTL, RTL, Schottky and MOS families
- Displays 16 logic states up to 8 digits wide
- See ones and zeros displayed on your CRT, octal or hexadecimal format
- Tests circuits under actual operating conditions
- Easy to assemble — comes with step-by-step construction manual which includes 80 pages on logic analyzer operation.

Some applications are:

- Troubleshooting microprocessor address, instruction, and data flow
- Examine contents of ROMS
- Tracing operation of control logic
- Checking counter and shift register operation
- Monitoring I/O sequences
- Verifying proper system operations during testing

PARATRONICS TRIGGER EXPANDER - Model 10

Adds 16 additional bits. Provides digital delay and qualification of input clock and 24-bit trigger word. — Connects direct to Model 100A for Integrated unit.

Model 10 — \$229.00
Baseplate — \$6.95

BUGBOOK Continuing Education Series

BUGBOOK I & II - Basic concepts of TTL Logic — over 90 experiments \$17.00/set

BUGBOOK Ila - Introduces UART — recommended for RTTY enthusiast \$5.00/book

BUGBOOK III - Explores 8080 chip — introduces Mark 80 Microcomputer \$15.00/book

555 TIMER APPLICATIONS SOURCEBOOK WITH EXPERIMENTS — over 100 design techniques \$6.95/book

CMOS-M-DESIGNERS PRIMER AND HANDBOOK a complete CMOS instruction manual \$6.00

INSTRUCTORS MANUAL Necessary for instruction on Bugbook I and II. \$3.00

Introductory Offer — all 6 books (worth \$49.95) (does not include Instructors Manual) SPECIAL - \$42.95

CONTINENTAL SPECIALTIES

PROTO BOARD 6 \$15.95 (6" long X 4" wide)

Other CS Proto Boards

| | |
|-------------------------------|----------|
| PB100 - 4.5" x 6" | \$ 17.99 |
| PB101 - 5.8" x 4.5" | 29.95 |
| PB102 - 7" x 4.5" | 39.95 |
| PB103 - 9" x 6" | 59.95 |
| PB104 - 9.5" x 8" | 79.95 |
| PB203 - 9.75 x 6 1/2 x 2 1/4 | 75.00 |
| PB203A - 9.75 x 6 1/2 x 2 1/4 | 120.00 |

PROTO CLIPS

| | |
|--------|--------|
| 14 PIN | \$4.50 |
| 16 PIN | 4.75 |
| 24 PIN | 8.50 |

DESIGN MATES

| | |
|--------------------------|-------|
| DM1 - Circuit Designer | 54.95 |
| DM2 - Function Generator | 69.95 |
| DM3 - RC Bridge | 59.95 |

Logic Monitor \$84.95 for DTL, TTL, TTL or CMOS Devices

MAX-100 Frequency Counter 20 MHz-100MHz — 8 digit — 6' LED Available September 15, 1977 \$134.95

QT PROTO STRIPS

| | |
|--------|--------|
| OT-595 | OT-185 |
| OT-596 | OT-186 |
| OT-475 | OT-125 |
| OT-476 | OT-85 |
| OT-355 | OT-75 |
| OT-356 | |

OT type #notes price
OT-595 200 12.50
OT-596 200 12.50
OT-475 470 10.00
OT-476 bus strip 2.25
OT-355 350 8.50
OT-356 bus strip 2.00
OT-185 180 4.75
OT-125 120 3.75
OT-85 80 3.25
OT-75 70 3.00

Experimenter 300 \$ 9.95
Experimenter 500 \$10.95

\$5.00 Minimum Order — U.S. Funds Only
California Residents — Add 6% Sales Tax

Spec Sheets - 25¢ — Send 35¢ Stamp for 1977A Catalog
Dealer Information Available

James ELECTRONICS

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
PHONE ORDERS WELCOME — (415) 592-8097
All Advertisements Prices Good Thru October

Timeband Digital Alarm Clocks

A trademark of Fairchild Camera and Instrument Corporation

● 24-hour alarm
● Onze Button
● 100% Solid State
● Large Red LED Display (8 high)
● AM-PM indicator
● Seconds display at touch of button
● Power failure indicator
● One year factory warranty

C-500 - Ivory Case \$16.95
C-8211 Woodgrain Case \$19.95

Timeband LAMP CLOCK

● 24 hour alarm
● Doze button
● Alarm-on indicator
● 8" high Red LED Display
● AM/PM indicator
● High intensity lamp
● Lamp shuts off when collapsed

Model C-590 (Ivory) \$29.95

ERC AM/FM 8-Track Stereo Receiver

With BSR Changer

- PLL System
- BSR Record Changer
- Slide Controls
- Automatic AFC Control
- 4 Speaker Output
- Walnut finish vinyl covered wood veneer with smoke dust cover

Size: 20"W x 9 1/2"H x 15 1/4"D
Model 8365 \$149.95

DIGITAL STOPWATCH

- Bright 8 Digit LED Display
- Times to 99 minutes 59.99 seconds
- Crystal Controlled Time Base
- Three Stopwatches on One Times Single Event — Split & Taylor
- Size 4.5" x 2.15" x .90" (4 1/2 ounces)
- Uses 3 Penrite Cells

Kit — \$39.95
Assembled — \$49.95
Heavy Duty Carry Case \$5.95

Stop Watch Chip Only (7205) \$19.95

IMC 3 1/2 DIGIT DVM KIT

This 0-2V DC .05 per cent digital voltmeter features the Motorola 3 1/2 digit DVM chip set. It has a 4" LED display and operates from a single +5V power supply. The unit is provided complete with an injection molded black plastic case complete with bezel. An optional power supply is available which fits into the same case as the 0-2V DVM allowing 117 VAC operation.

A. 0-2V DVM with Case \$49.95
B. 5V Power Supply \$14.95

JE700 CLOCK

The JE700 is a low cost digital clock but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6" x 2 1/2" x 1". It utilizes a MAN72 high brightness readout, and the MM5314 clock chip.

12 or 24 Hour
KIT ONLY \$17.95

Rejected ATARI GAME BOARDS

Over 60 Reusable IC's, misc. transistors, resistors, diodes, caps, crystals, switch, etc. (8 1/2" x 16"). Limited Quantity.

\$4.95 ea.

INSTRUMENT/CLOCK CASE

Injection molded unlt. Complete with red bezel. 4 1/2" x 4" x 1-9/16"

\$3.95 ea.

JE803 PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test; drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (MS - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can be used at MOS levels or circuit damage will result.

\$9.95 Per Kit
printed circuit board

T²L 5V 1A Supply

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only

\$9.95 Per Kit

7400N TTL

| | | | | | |
|---------|-----|----------|------|----------|-------|
| SN7400N | 16 | SN7459A | 25 | SN74154N | 1.00 |
| SN7401N | 16 | SN7460N | 22 | SN74155N | 99 |
| SN7402N | 21 | SN7470N | 45 | SN74156N | 99 |
| SN7403N | 16 | SN7472N | 39 | SN74157N | 99 |
| SN7404N | 18 | SN7473N | 37 | SN74160N | 1.25 |
| SN7405N | 24 | SN7474N | 32 | SN74161N | 1.25 |
| SN7406N | 20 | SN7475N | 30 | SN74163N | 99 |
| SN7407N | 29 | SN7476N | 32 | SN74164N | 1.10 |
| SN7408N | 25 | SN7479N | 5.00 | SN74165N | 1.10 |
| SN7409N | 25 | SN7480N | 5.00 | SN74166N | 1.25 |
| SN7410N | 18 | SN7482N | 99 | SN74167N | 5.50 |
| SN7411N | 30 | SN7483N | 7.75 | SN74170N | 2.10 |
| SN7412N | 33 | SN7485N | 89 | SN74172N | 8.95 |
| SN7413N | 45 | SN7486N | 3.50 | SN74173N | 1.50 |
| SN7414N | 70 | SN7489N | 2.49 | SN74174N | 1.25 |
| SN7415N | 35 | SN7490N | 45 | SN74175N | 99 |
| SN7420N | 21 | SN7491N | .75 | SN74176N | .90 |
| SN7421N | 33 | SN7492N | .49 | SN74177N | .90 |
| SN7422N | 49 | SN7493N | .49 | SN74180N | .99 |
| SN7423N | 37 | SN7496N | .79 | SN74181N | .95 |
| SN7424N | 29 | SN7495N | .75 | SN74182N | 1.95 |
| SN7426N | 29 | SN7496N | .89 | SN74185N | 2.20 |
| SN7427N | 37 | SN7497N | 4.00 | SN74186N | 15.00 |
| SN7429N | 42 | SN74100N | 1.00 | SN74187N | 2.20 |
| SN7430N | 16 | SN74107N | .39 | SN74188N | 3.95 |
| SN7432N | 31 | SN74121N | .39 | SN74190N | 1.19 |
| SN7437N | 27 | SN74122N | .39 | SN74191N | 1.25 |
| SN7438N | 27 | SN74123N | .50 | SN74192N | 8.99 |
| SN7439N | 25 | SN74125N | .60 | SN74194N | 1.25 |
| SN7440N | 15 | SN74126N | .50 | SN74195N | 1.25 |
| SN7441N | 89 | SN74132N | 1.09 | SN74196N | 1.25 |
| SN7442N | 59 | SN74136N | .95 | SN74197N | 7.5 |
| SN7443N | .75 | SN74141N | 1.15 | SN74198N | 1.25 |
| SN7444N | .75 | SN74142N | 4.00 | SN74199N | 1.25 |
| SN7445N | .75 | SN74143N | 4.50 | SN74199N | 1.75 |
| SN7446N | 81 | SN74144N | 4.50 | SN74200N | 5.59 |
| SN7447N | 59 | SN74145N | 1.15 | SN74201N | 9.00 |
| SN7448N | 79 | SN74147N | 2.35 | SN74202N | 9.00 |
| SN7449N | 25 | SN74148N | 2.00 | SN74203N | 6.00 |
| SN7451N | 26 | SN74150N | 1.00 | SN74204N | 6.00 |
| SN7452N | 27 | SN74151N | .89 | SN74205N | 6.00 |
| SN7454N | .20 | SN74153N | .89 | SN74206N | 7.5 |

Timeband® by FAIRCHILD

— Watches —
Men's & Ladies

- Solid State
- Displays hour, minute, second, month & day
- Free set of replacement batteries
- Choose LED or LCD styles
- One year factory warranty

T249 White w/bracelet \$19.95
T248 Yellow w/bracelet \$22.95
LED

T237 White w/bracelet \$22.95
T236 Yellow w/bracelet \$25.95
LED

T2437 White w/bracelet \$29.95
T2436 Yellow w/bracelet \$34.95
LED

T235 White w/strap \$24.95
T234 Yellow w/strap \$27.95
LED

WIRE WRAP CENTER

HOBBY-WRAP TOOL-BW-630

- Battery Operated (Size C)
- Weights ONLY 11 Ounces
- Wraps 30 AWG Wire onto Standard DIP sockets (.025 inch)
- Complete with built-in bit and sleeve

\$34.95 (batteries not included)

WIRE-WRAP KIT — WK-2-W

WRAP • STRIP • UNWRAP

- Tool for 30 AWG Wire
- Roll of 50 Ft. White or Blue 30 AWG Wire
- 50 pcs. each 1", 2", 3" & 4" lengths — pre-stripped wire.

\$11.95

WIRE WRAP TOOL WSU-30

WRAP • STRIP • UNWRAP \$5.95

WIRE WRAP WIRE — 30 AWG

25 ft. min. \$1.25 50 ft. \$1.95 100 ft. \$2.95 1000 ft. \$15.00
SPECIFY COLOR — White - Yellow - Red - Green - Blue - Black

WIRE DISPENSER — WD-30

- 50 ft. roll 30 AWG KYNAR wire wrap wire \$3.45 ea.
- Cuts wire to desired length
- Strips 1" of insulation Specify — Blue-Yellow-White-Red

BK PRECISION New

3 1/2-Digit Portable DMM

- Overload Protected — 3" High LED Display
- Battery or AC operation / Auto Zeroing
- 1mv, 1Va, 0.1 ohm resolution / Overrange reading
- 10 meg input impedance
- DC Accuracy 1% typical

Ranges: DC Voltage — 0-1000VAC Voltage: 0-1000V
Freq. Response: 50-400 Hz/DC AC Current: 0-1000mA
Resistance: 0-10 meg ohm
Size: 6" x 4" x 4" z 2"

Model 2800 **\$99.95**
AC Adapter BC-28 **8.00**
Rechargeable Batteries BP-28 **20.00**
Carrying Case LC-28 **6.00**

CHANNEL F™ FAIRCHILD VIDEO ENTERTAINMENT SYSTEM

\$159.95

- Freeze Action • Speed Option
- Automatic time and scorekeeping
- Battery-Free AC operation
- Dual controls with 8-way action
- Built-in Pro Hockey and Tennis games
- Easy hook-up on any B/W or Color TV
- Factory warranty

Channel F — additional cartridges — \$17.95 ea.

0813 — Blackjack (1 or 2 players)
0814 — Spirtire (1 or 2 players)
0815 — Tic-Tac-Toe/Shooting Gallery
0816 — Quadra-doodle/Doodle/0817 — Spacewar (2 players)
0818 — Desert Fox/Shooting Gallery
0819 — Drag Strip (1 or 2 players)
0820 — Maze (2 players)
0821 — Magic Numbers (computer logic)
0822 — Baseball (2 players)

DISCREET LEADS

| 125" dia. | 185" dia. | 200" dia. | 180" dia. | 985" dia. |
|-------------------|-------------------|-------------------|-------------------|-------------------|
| XC209 Red 10/51 | XC256 Red 4/51 | XC556 Red 5/51 | XC556 Red 5/51 | XC556 Red 5/51 |
| XC209 Green 4/51 | XC256 Green 4/51 | XC556 Green 4/51 | XC556 Green 4/51 | XC556 Green 4/51 |
| XC209 Orange 4/51 | XC256 Yellow 4/51 | XC556 Yellow 4/51 | XC556 Yellow 4/51 | XC556 Yellow 4/51 |
| XC209 Yellow 4/51 | XC256 Orange 4/51 | XC556 Orange 4/51 | XC556 Orange 4/51 | XC556 Orange 4/51 |
| | XC256 Clear 4/51 | XC556 Clear 4/51 | XC556 Clear 4/51 | XC556 Clear 4/51 |

DISPLAY LEADS

| TYPE | POLARITY | HT | TYPE | POLARITY | HT |
|----------|-----------------------|-----------|----------|-----------------------|----------|
| MAN 1 | Common Anode | 270 2.95 | MAN 3540 | Common Cathode-orange | 300 1.75 |
| MAN 2 | 5 x 7 Dot Matrix | 300 4.95 | MAN 4710 | Common Anode-Red | 400 1.95 |
| MAN 3 | Common Cathode | 125 31.99 | DL 701 | Common Anode-red | 300 99 |
| MAN 4 | Common Cathode | 187 1.95 | DL 750 | Common Cathode | 300 99 |
| MAN 7 | Common Anode-green | 300 1.25 | DL 707 | Common Anode | 300 99 |
| MAN 7Y | Common Anode-yellow | 300 1.55 | MAN 4740 | Common Anode-Red | 400 99 |
| MAN 7Y | Common Anode-yellow | 300 1.99 | DL 741 | Common Anode | 600 1.50 |
| MAN 52 | Common Anode-red | 300 99 | DL 747 | Common Anode | 600 2.25 |
| MAN 64 | Common Anode-red | 400 99 | DL 750 | Common Cathode | 600 2.49 |
| MAN 74 | Common Cathode | 300 1.50 | DL 338 | Common Cathode | 110 5.00 |
| MAN 82 | Common Anode-yellow | 300 99 | FND70 | Common Cathode | 250 75 |
| MAN 84 | Common Cathode-yellow | 300 99 | FND503 | Common Cathode | 500 1.00 |
| MAN 3620 | Common Anode-orange | 300 1.75 | FND507 | Common Anode | 500 1.30 |

CMOS

20% Discount for 100 Combined 7400's

| | | | |
|--------|-------|---------|------|
| CD4000 | .25 | 74C00N | .39 |
| CD4001 | .35 | 74C02N | .55 |
| CD4002 | .25 | 74C04N | .75 |
| CD4006 | 2.50 | 74C10N | .85 |
| CD4007 | 2.50 | 74C20N | .85 |
| CD4009 | .25 | 74C04N | 5.55 |
| CD4010 | .59 | 74C04N | 2.15 |
| CD4011 | .25 | 74C04N | 1.50 |
| CD4012 | .25 | 74C74 | 1.15 |
| CD4013 | .47 | 74C03N | 1.00 |
| CD4016 | .56 | 74C05N | 1.25 |
| CD4017 | 1.35 | 74C107N | 1.25 |
| CD4019 | .55 | 74C151 | 2.90 |
| CD4020 | 1.49 | 74C154 | 4.00 |
| CD4022 | 1.25 | 74C154 | 1.15 |
| CD4023 | .25 | 74C160 | 3.25 |
| CD4024 | 1.50 | 74C161 | 3.25 |
| CD4025 | .25 | 74C163 | 3.00 |
| CD4026 | 53.95 | 74C164 | 3.75 |
| CD4027 | .69 | 74C173 | 2.60 |
| CD4028 | 1.55 | 74C193 | 2.75 |
| CD4029 | .90 | 74C415 | 2.75 |
| CD4030 | 2.50 | MC1404A | 4.50 |
| CD4035 | 1.85 | MC1456B | .56 |

LINEAR

| | | | |
|------------|------|---------|------|
| LM309H | .80 | LM1458C | .65 |
| LM3010 | .35 | LM1496B | .65 |
| LM3010C | .35 | LM1556V | 1.85 |
| LM302H | .75 | LM1812N | 6.95 |
| LM304H | 1.00 | LM1812N | 1.95 |
| LM305H | .95 | LM1812N | 2.95 |
| LM3070C | 1.00 | LM3055C | 1.50 |
| LM308H | 1.35 | LM3055N | .69 |
| LM308CN | 1.00 | LM3900N | .55 |
| LM309H | 1.10 | LM3900N | 1.75 |
| LM309CN | .99 | LM3900N | 1.00 |
| LM3100N | 2.95 | LM5558N | 1.85 |
| LM311H | .90 | MC5558V | 1.00 |
| LM311CN | .90 | LM7325N | .90 |
| LM313H | 6.50 | LM7325N | 1.25 |
| LM313CN | 1.50 | BO888 | 4.95 |
| LM319N | 1.30 | LM75450 | .49 |
| LM320K-5 | 1.35 | 75451CN | .39 |
| LM320K-5.2 | 1.35 | 75452CN | .39 |
| LM320K-1.2 | 1.35 | 75453CN | .39 |
| LM320K-1.5 | 1.35 | 75454CN | .39 |
| LM320K-1.5 | 1.35 | 75455CN | .39 |
| LM320T-5 | 1.75 | 75456CN | .79 |
| LM320T-5.2 | 1.75 | 75457CN | .89 |
| LM320T-8 | 1.75 | 75458CN | .89 |
| LM320T-12 | 1.75 | LM7093N | .45 |
| LM320T-15 | 1.75 | LM7093N | .29 |
| LM320T-18 | 1.75 | LM7093N | .29 |
| LM320T-24 | 1.75 | LM7093N | .29 |
| LM323K-5 | 9.95 | LM7111N | .39 |
| LM324N | 1.80 | LM723H | .55 |
| LM339N | 1.70 | LM723H | .55 |
| LM340K-5 | 1.95 | LM733N | 1.00 |
| LM340K-6 | 1.95 | LM733N | 1.00 |
| LM340K-8 | 1.95 | LM733N | 1.00 |
| LM340K-9 | 1.95 | LM741CN | .35 |
| LM340K-15 | 1.95 | LM741CN | .35 |
| LM340K-15 | 1.95 | LM741CN | .39 |
| LM340K-18 | 1.95 | LM747N | .79 |
| LM340K-24 | 1.95 | LM747N | .79 |
| LM340T-5 | 1.75 | LM748A | .39 |
| LM340T-6 | 1.75 | LM748A | .39 |
| LM340T-8 | 1.75 | LM1303N | .90 |
| LM340T-12 | 1.75 | LM1304N | 1.19 |
| LM340T-15 | 1.75 | LM1305N | 1.40 |
| LM340T-18 | 1.75 | LM1307N | .85 |
| LM340T-24 | 1.75 | LM1310N | 2.95 |
| LM350N | 1.00 | LM1351N | 1.55 |
| LM351CN | .65 | LM1414N | 1.75 |
| | | RC4195 | 3.25 |

74LS00 TTL

| | | | |
|--------|------|---------|------|
| 74LS00 | 29 | 74LS159 | 1.95 |
| 74LS02 | 29 | 74LS151 | 1.55 |
| 74LS03 | 29 | 74LS153 | 1.89 |
| 74LS04 | 35 | 74LS157 | 1.59 |
| 74LS05 | 35 | 74LS162 | 2.25 |
| 74LS06 | 29 | 74LS163 | 2.25 |
| 74LS10 | 29 | 74LS164 | 1.95 |
| 74LS13 | 29 | 74LS165 | 1.95 |
| 74LS14 | 7.75 | 74LS169 | 1.95 |
| 74LS20 | 29 | 74LS192 | 2.65 |
| 74LS26 | 29 | 74LS193 | 2.85 |
| 74LS27 | 37 | 74LS195 | 2.85 |
| 74LS28 | 29 | 74LS197 | 1.89 |
| 74LS30 | 29 | 74LS197 | 1.89 |
| 74LS32 | 39 | 74LS199 | 1.89 |
| 74LS40 | 39 | 74LS199 | 1.89 |
| 74LS51 | 29 | 74LS252 | 7.5 |
| 74LS52 | 29 | 74LS252 | 7.5 |
| 74LS55 | 29 | 74LS136 | 59 |
| 74LS73 | 49 | 74LS138 | 1.89 |

CLOCK CHIPS

| | | |
|--------|---|--------|
| MM5309 | 6 Digit, BCD Outputs, Reset Pin. | \$9.95 |
| MM5311 | 6 Digit, BCD Outputs, 12 or 24 Hour | 4.95 |
| MM5312 | 4 Digit, BCD Outputs, 1 PPS Output | 6.95 |
| MM5314 | 6 Digit, 12 or 24 Hour, 60 or 90 Hz | 9.95 |
| MM5316 | 4 Digit, Alarm, 1 PPS Output | 4.95 |
| MM5318 | Video Clock Chip, For Use With MM5841 | \$9.95 |
| CT1001 | 6 Digit, Calendar, Alarm, 12 or 24 Hour | 9.95 |

FCS 8000A — 3 1/2 Digit — .8" Display

NEW! 25 Pin Version with color & amp/m indicator

- Connects almost one for one with 3817, 3817A or D. (3817 available at \$5.00 each)
- Typical segment current: 8mA except color, 10 hrs. b & c and 10 mA, a & d which are 16 mA
- Forward voltage drop: 1.5 volts

\$4.95 EA.

* MAXIMUM FORWARD CURRENT — 25 mA

HP 5082-7300 Series — Multi-Digit

- 1/2" chip • Common Cathode Red
- 3-5 volts @ 5 mA/segment
- 7 segment Monolithic
- Dip Package

2 Digit \$.79 69
3 Digit \$.89 79
4 Digit \$.99 89
5 Digit \$ 1.19 99

TV GAME CHIP SET — \$14.95

Includes AY-3-8500-1 Chip and 2.010 mhz crystal (2.010 crystal — \$1.95 ea; AY-3-8500-1 chip — \$13.95 ea.)

50 PCS. RESISTOR ASSORTMENTS \$1.75 PER ASS'T.

| ASST. 1 | 5 ea. | 27 OHM | 33 OHM | 39 OHM | 47 OHM | 56 OHM | 1/4 WATT 5% — 50 PCS. |
|----------|--|--------------------|---------|---------|---------|---------|-----------------------|
| ASST. 2 | 5 ea. | 180 OHM | 220 OHM | 270 OHM | 330 OHM | 390 OHM | 1/4 WATT 5% — 50 PCS. |
| ASST. 3 | 5 ea. | 1.2K | 1.5K | 1.8K | 2.2K | 2.7K | 1/4 WATT 5% — 50 PCS. |
| ASST. 4 | 5 ea. | 2.2K | 2.7K | 3.3K | 3.9K | 4.7K | 1/4 WATT 5% — 50 PCS. |
| ASST. 5 | 5 ea. | 56K | 68K | 82K | 100K | 120K | 1/4 WATT 5% — 50 PCS. |
| ASST. 6 | 5 ea. | 390K | 470K | 560K | 680K | 820K | 1/4 WATT 5% — 50 PCS. |
| ASST. 7 | 5 ea. | 1.2M | 1.5M | 1.8M | 2.2M | 2.7M | 1/4 WATT 5% — 50 PCS. |
| ASST. 8R | Includes Resistor Assortments 1-7 (350 PCS.) | \$10.95 ea. | | | | | |

\$5.00 Minimum Order — U.S. Funds Only
California Residents — Add 6% Sales Tax

Spec Sheets — 25c — Send 35c Stamp for 1977A Catalog
Dealer Information Available

James ELECTRONICS

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
PHONE ORDERS WELCOME — (415) 592-8097
All Advertised Prices Good Thru October

DATA HANDBOOKS

7400 Pin-out & Description of 5474-7400 ICS **\$2.95**
CMOS Pin-out & Description of 4000 Series ICS **\$2.95**
Linear Pin-out & Functional Description **\$2.95**
ALL THREE HANDBOOKS **\$6.95**

ZENERS — DIODES — RECTIFIERS

| TYPE | VOLTS V | PRICE | TYPE | VOLTS V | PRICE | |
|--------|---------|-------|--------|---------|----------------|---------|
| 1N4746 | 3.3 | 400mm | 411.00 | 1N4005 | 500 PIV 1 AMP | 10/1.00 |
| 1N751A | 5.1 | 400mm | 411.00 | 1N1184 | 800 PIV 1 AMP | 10/1.00 |
| 1N752 | 5.6 | 400mm | 411.00 | 1N4001 | 1000 PIV 1 AMP | 10/1.00 |
| 1N753 | 6.2 | 400mm | 411.00 | 1N3600 | 50 200m | 6/1.00 |
| 1N754 | | | | | | |

Watch for our supermarket bargains each month!

HOT NEWS!

POLY PAKS® IS THE WORLD'S LARGEST ELECTRONIC SUPERMARKET

FEATURING THE BARGAINS OF THE MONTH!!!!

DISCOUNT OCT. 77 - POP. ELECTRONICS SPECIALS

RCA High quality "POCKET" VOM

- 1000 ohms per volt
- Model WV-539A. Features 1 1/2 precision movements diode protected against burnout. Measures DC volts 0-15-150-1000; AC volts 0-15-150-1000; DC current 0-150ma; resistance X1000. Sensitivity 1000 ohms/volt AC-DC. Uses penlite cell, not included. Size 2 3/4 x 3 1/2 x 1 3/4". Wt. 5 ozs. Cat. No. 10E3921

\$8.88

QUAD AM-FM-MPV TUNER AMP Save \$10 Now

BUILT-IN QUAD STEREO TAPE PLAYER

For 2 and 4 spkrs.

\$3.95

MOTHERBOARD EDGE CONNECTOR

106 pins (1/2 inch each side). Use with IMSAI & ALTAIR. 0.125" pin cts, goldplated. 1/2" wire wrap leads. Open ends. fit wide PC boards. 8 ozs. Cat. No. 10E3987

TRW 900 MHz UHF POWER TRANSISTOR

For NPN: CB's, Hams take note! Replaces many trans. mitter diodes and output transistors. TO-181 case, 3/8" dia. with 1/2" leads. 2W. min. Bypass 26V. Ise (beta) 30-60. Ic max 1.25 amps. **\$4.95**

Order by Cat. No. 10E1981

\$5.50 TV GAME & HI-JOY STICK

Includes four 100K pots

For TV & computer games, and quadrophonic balancing. 1 1/2 x 1 1/2 x 1 1/2". With 1/2" handle. Wt. 6 ozs. Cat. No. 10E3808

Cat. No. 10E3971

69.95

Reg. \$79.95 at Poly Paks!

- 5 watts per channel x 4 RMS, 20W total.
- Psychedelic panel lighting effect.
- Brushed aluminum Streamlined styling.

The finest unit we've ever offered. The "SYMPHONY" plays quad 8-track tapes in full dimension quad. Also features Matrix-Quad, drives quad sound from stereo records, tapes and FM-150" phono input cables and has outputs for 4 speakers, jacks for "Quad tape-output" and terminals for external FM antenna. Fits easily into wall, console, or cabinet of your own design. FM stereo indicator. Pushbutton switches select stereo, matrix, 1D discrete, power ON/OFF. Bass and treble slide control. Additional multifunction switch selects AM, FM, FM-MPV, phono, tape; blue panel lights indicate these functions. Master slide volume control with individual balance controls for each channel. Output jacks for quad headphones. Tape deck panel light indicates when a quad tape is inserted. Other lamps indicate the track being played. 115 VAC. Size: 22 x 5 x 6" deep. Wt. 9 lbs.

15% OFF

25% OFF

Order by Cat. No. 10E1981

NOISE-CANCELLING CB-HAM MIKE

Cuts noise of machinery, highway for clear transmission! Fits virtually all rigs.

Low-impedance, freq. resp. 300-5000 Hz. With 6' coiled cord. Includes instructions for 100's of Chis. Wt. 20 ozs. No. 10E3902

\$6.66

J.C. PENNEY'S 8-Track TAPE TRANSPORT

Shielded preamp

\$12.95

Excellent replacement or design your own quality tape system! Automatic or manual track selection with program indicator lights. Player shuts off automatically when tape is removed. Built-in low-distortion preamp and auto-reverse motor. With input & output cables. Requires external power supply. With instructions. Size 8 x 5 x 3 1/2". Wt. 4 lbs. Cat. No. 10E3010

| Type | Sale | Type | Sale |
|--------|--------|---------|------|
| SN7400 | \$0.14 | SN7460 | .26 |
| SN7401 | .14 | SN7462 | .14 |
| SN7403 | .14 | SN7464 | .14 |
| SN7404 | .17 | SN7465 | .14 |
| SN7405 | .18 | SN7470 | .14 |
| SN7406 | .19 | SN7471 | .26 |
| SN7407 | .24 | SN7472 | .69 |
| SN7410 | .14 | SN7473 | .31 |
| SN7411 | .19 | SN7475 | .48 |
| SN7413 | .39 | SN7476 | .33 |
| SN7414 | .61 | SN7477 | .79 |
| SN7416 | .24 | SN7480 | .33 |
| SN7417 | .24 | SN7482 | .59 |
| SN7420 | .14 | SN7485 | .88 |
| SN7422 | .24 | SN7486 | .26 |
| SN7427 | .26 | SN7487 | .69 |
| SN7430 | .14 | SN7492 | .63 |
| SN7432 | .24 | SN7493 | .69 |
| SN7437 | .24 | SN7494 | .69 |
| SN7438 | .24 | SN7495 | .69 |
| SN7440 | .14 | SN7496 | .69 |
| SN7444 | .17 | SN7497 | .69 |
| SN7445 | .61 | SN7499 | .29 |
| SN7447 | .69 | SN74102 | .31 |
| SN7450 | .14 | SN74123 | .49 |
| SN7451 | .14 | SN74125 | .39 |
| SN7453 | .14 | SN74126 | .39 |
| SN7454 | .14 | SN74132 | .83 |
| SN7455 | .14 | SN74140 | 1.00 |
| SN7456 | .14 | SN74285 | 4.25 |

ECCO 10-POSITION BCD THUMBWHEEL SWITCH

1-2-4-8 BCD recalling. Positions labelled 0-9. 1 for 1, 2 for 2, 3 for 3, 4 for 4. White numerals on a black background. Ecco 900 series. 1 1/4 x 1 1/4 x 1 1/4". Wt. 1.49

DUAL 6-WATT STEREO AMP

LM-3170 - for AM-FM's, phono, tape recorders, & more! 6 watts x 2 RMS into 8 ohms. 5" TID, AVO 100 db typ. 75 db channel separation. Supply 10-35V. With spers. 2 for \$9. Cat. No. 10E3447

GE NI-CAD POWER PAKS

AA penlite cells, grouped in series! 1.25V each cell. Rechargeable! Wt. 2 oz. per cell. No. Cells Volts Sale

| | | | |
|---------|---|------|--------|
| 10E368B | 2 | 2.5 | \$2.50 |
| 10E368C | 3 | 3.75 | 3.50 |
| 10E369A | 4 | 5 | 4.50 |

1-AMP REGULATED POWER SUPPLY

In 5-12-15 volts!

| | | | |
|----------------|---------|----------------|---------|
| 2 for \$8.88 | 10E3854 | 2 for \$8.88 | 10E3857 |
| 15 for \$15.95 | 10E3858 | 15 for \$15.95 | 10E3858 |

BARREL KITS

BARREL KIT #203 CALCULATOR KEYBOARDS

10 for \$1.98

It's true! 20-key, 4 function keyboards at ridiculous give-away. Wt. 12 ozs. Cat. No. 10E3524

BARREL KIT #253 LINE CORDS

8 for \$1.98

100's of AC power uses! Heavy-duty, 6-ft. long, 18 gauge. White vinyl insulation & molded plug. Wt. 6 ozs. Cat. No. 10E3843

BARREL KIT #200 DIGIT READOUT MODULES

5 for \$1.98

Barrels and barrels and no time to test. Calculator and driver chips beneath epoxies on back. Wt. 6 ozs. 10E3729

BARREL KIT #244 1702A ROMS

3 for \$1.98

Hobby fallout of the famous erasable programmable ROM. 2048 bit. Cat. No. 10E3729

BARREL KIT #188 400 PARTS

\$1.98

Includes resistors, capacitors, diodes, IC's, for PC work, some on PC boards. Dumped into barrels by factory. 100% material. Wt. 12 ozs. Cat. No. 10E3401

BARREL KIT #224 PRE-CUT NIPPED HOOKUP WIRE

200 lengths* \$1.98

Breadboarders note: 22 gauge, precut into 4" to 8" lengths. Assort. color plastic jackets. Wt. 12 ozs. *200 ft. approx. No. 10E3959

BARREL KIT #205 MINI BLOCK CAPACITORS

50 for \$1.98

Unbelievable! Worth \$50. High precision submini caps for all applications. Wt. 3 ozs. No. 10E3528

BARREL KIT #201 6V INDICATORS w/leads

15 for \$1.98

Test lamp manufacturer dumps inventory! Worth 69¢ ea. Like grain-o-wheat. Cat. No. 10E3526 hobby

BARREL KIT #194 6V IN-LINE BRIDGES

20 for \$1.98

Factory dumped in barrels. We can't test 'em, but for the price you can't go wrong. Hobby. Wt. 8 ozs. Cat. No. 10E3475

BARREL KIT #188 400 PARTS

\$1.98

Includes resistors, capacitors, diodes, IC's, for PC work, some on PC boards. Dumped into barrels by factory. 100% material. Wt. 12 ozs. Cat. No. 10E3401

BARREL KIT #184 1/2-WATT METAL FILM

150 for \$1.98

100% metal film resistors. Long leads. 10E3413

BARREL KIT #182 JUMBO RED LEADS

15 for \$1.98

100% material, user cancellation from factory dumps, 3V, 10 mils. For 100's of projects, red lens. Cat. No. 10E3369

BARREL KIT #163 MINI TRIM POTS

30 for 1 oz. \$1.98

Asst. values 100 to 1 meg. What a buy. Single turn. 1/4 W. Wt. 6 oz. 10E3345

BARREL KIT #181 POP PLASTIC TRANSISTORS

25 for \$1.98

Calculator maker dumps 2N3904's with some 2N3906's of 100% material. TO-92. Preformed. Cat. No. 10E3343

BARREL KIT #160 HOBBY VOLTAGE REGULATORS

10 for \$1.98

LM-109K TO-3 barreled, but by the pound, but who wants to check 'em? Your gain. Wt. 20 ozs. 10E3330

BARREL KIT #138 PANEL SWITCHES

30 for \$1.98

Did you hear of OAK? Another great barrel! All types of rotary, electric, slides, etc. 10E3268

BARREL KIT #128 MINI-DIP IC'S

100 for \$1.98

741's, LM380, 703, 567, 555, who knows? Factory mixed, you test. Untested and hobby. Wt. 1 lb. Cat. No. 10E3245

BARREL KIT #127 AXIAL ELECTROS

40 for \$1.98

Asst. capacities and voltages. Cat. No. 10E3227

BARREL KIT #126 UPRIGHT ELECTROS

40 for \$1.98

Time to 300mf in mixture of voltages. 100% material in good. 10E3226

BARREL KIT #115 MOLEX SOCKETS

100 for \$1.98

Calculator maker dump! We got a million of 'em.

BARREL KIT #109 TERMINAL STRIPS

100 for \$1.98

Wide asst. of terminal strip connectors, from 1 contact up. Strip manufacturers barrel dump your gain. Wt. 1 lb. Cat. No. 10E3136

BARREL KIT #104 SLIDE VOLUME CONTROLS

10 for \$1.98

Factory rejects, hobby, cosmetic rejects. Your gain. 5, 6, 12, 15, 18 or 24 volts. TO-220 power tab. Wt. 4 ozs. Cat. No. 10E2635

BARREL KIT #101 RESISTOR SPECIAL

200 for \$1.98

Includes: 1/2, 1/4, 1/2, 1, 2-watt, carbon, 8 oz. 100% kond. 10E3054

BARREL KIT #99 PHOTO ELECTRIC CELLS

10 for \$1.98

Asst. GE types, CDS types. Mixed by factory. Big job for us to separate. 100% good. Cat. No. 10E1052

BARREL KIT #93 HALF WATTERS

200 for \$1.98

Resistor factory tried to fool us by mixing 100% color-coded resistors in barrel. But value is there. 4 oz. 10E3046 Untested

BARREL KIT #87 NAT. IC BONANZA

100 for \$1.98

Hobby and untested, factory mixed in barrels. Linears, 7400's, ROMS, DTL'S, resistors, clock and calculator chips and more. Wt. 12 ozs. Cat. No. 10E2860

BARREL KIT #86 HOBBY LEADS

40 for \$1.98

WOW! Not U.S.A. maker dumps factories in barrels. Hobby and untested. Useable yield 50% or better! Wt. 4 ozs. Cat. No. 10E2859

BARREL KIT #83 LM-340T VOLTAGE REGULATORS

15 for \$1.98

Factory rejects, hobby, cosmetic rejects. Your gain. 5, 6, 12, 15, 18 or 24 volts. TO-220 power tab. Wt. 4 ozs. Cat. No. 10E2635

BARREL KIT #71 CAPACITOR SPECIAL

100 pcs. \$1.98

We got barrels of a and 100 1/4, 100 1/2 watt, 100% good. Cat. No. 10E2738

BARREL KIT #68 2 WATTERS

100 for \$1.98

Suppliers throw 'em in the barrel. It's a lil' gold mine. All marked. Cat. No. 10E2735

BARREL KIT #61 POLYSTYRENE CAPS

100 for \$1.98

Finest caps made. As a gamble we bought 10 barrels from factory, mixed values; all good. Cat. No. 10E2729

BARREL KIT #58 SLIDE SWITCHES

30 for \$1.98

All shapes, sizes, spst, spdt, momentary, etc. Troncoon color-coded resistors in barrel. But value is there. 4 oz. 10E2726 100% good

BARREL KIT #40 15P WATT PNP POWER TRANSISTORS

15 for \$1.98

Popular germanium and silicon TO-3's, factory "off-spec" and fallout. 100% hobby, no opens, no shorts. Wt. 16 ozs. Cat. No. 10E2618

BARREL KIT #39 HOBBY NPN POWER TRANSISTORS

15 for \$1.98

Factory fallout and "off spec" 7400's, 100% hobby, no opens, no shorts. Wt. 1 lb. Cat. No. 10E2617

BARREL KIT #31 METALLIC RESISTORS

100 for \$1.98

Made mostly by Corning, the finest resistor made. Mostly 1/2 watt, 1% to 5% tol., & a barrel of values. Cat. No. 10E2609

BARREL KIT #30 REFORMED RESISTORS

200 for \$1.98

We got barrels of a and 100 1/4, 100 1/2 watt, 100% good. Cat. No. 10E2608 100% good

BARREL KIT #27 REFORMED DISCS

150 for \$1.98

Hi-Fi mp's shelf inventory but he dumped 'em in barrels. Preformed, for PC use. Mixed values. 100% good. Cat. No. 10E2605

BARREL KIT #26 PLASTIC TRANSISTORS

100 for \$1.98

Untested and hobby transistors. TO-92 (TO-18) ass't. 2N numbers, asst. manufacturers. Wt. 8 ozs. 10E2604

BARREL KIT #24 HIGH VOLTAGE RECTIFIERS

200 for \$1.98

Up to 12,000 volts, 1 mils. epoxy, axial leads. Cat. No. 10E2602

BARREL KIT #22 LONG LEAD DISCS

100 for \$1.98

"function sale" Prump marked only. Long leads. Cat. No. 10E2598 100% good

BARREL KIT #20 DIPPED MYLARS

60 for \$1.98

Finest capacitors made, shiny finish. Imagine factories dumping 'em in barrels. Cat. No. 10E2597 100% good

BARREL KIT #14 PRECISION RESISTORS

200 for \$1.98

Marked and unmarked 1/2, 1/2, 2 watt. No. 10E2428

BARREL KIT #7 VOLUME CONTROL

30 for \$1.98

Singles, duals, variety of values, styles, big ones, small ones. Cat. No. 10E2421

BARREL KIT #3 SWITCHING DIODES

100 for \$1.98

Imagine famous switching diodes at these prices! Cat. No. 10E2418 Untested.

BARREL KIT #1 SN7400 DIP IC'S

75 for \$1.98

Marked 14 and 16 pin dips, may include gates, flip-flops, registers, counters, who knows? Untested, hobby. Wt. 14 ozs. 10E2415

POLY PAKS

P.O. BOX 942E LYNNFIELD, MA. 01940

Terms: Add postage. Rated: net 30
Phone: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield.

POLY PAKS

Send for FREE Fall-Winter CATALOG

C.O.D.'S MAY BE PHONED

Radio Hut

Money back guarantee. NO COD'S. Texas residents add 5% sales tax. Add 5% of order for postage and handling. Orders under \$15.00 add 75 cents. Foreign orders add 10% for postage.

For your convenience, call your BankAmericard or Master Charge orders in on our Toll Free Watts Line: 1-800-527-2304. Texas residents call collect: 1-214-271-8423.



P. O. Box 38323P
Dallas, Texas 75238



Memorex computer boards with IC's, diodes, transistor, etc. 5 Boards containing 100 - 200 IC's
ONLY \$ 4.25

BRIDGE RECTIFIERS

| | | |
|--------|-----|------|
| 6 Amp | 50V | 1.10 |
| 10 Amp | 50V | 1.25 |
| 25 Amp | 50V | 1.39 |

MK 5005

4 digit counter/latch decoder; 7 segment output only. 24 pin dip with specs.
\$ 8.00 EACH

UNSCRAMBLER KIT for all Scanners

- Tunes easily
 - Full instructions included
 - Easy to install
 - 3 1/2" x 3 1/2" x 1 1/2"
- Only \$19.95**

RESISTORS

Over 50,000,000 in stock

| | |
|----------|----------|
| *330 ohm | 22K ohm |
| 470 ohm | 27K ohm |
| *680 ohm | 33K ohm |
| 1K ohm | 39K ohm |
| 1.2K ohm | 43K ohm |
| 2.2K ohm | 47K ohm |
| 3.3K ohm | 82K ohm |
| 4.7K ohm | 100K ohm |
| 6.8K ohm | 150K ohm |
| 10K ohm | 220K ohm |
| 20K ohm | |

*1/8 W only
**1/2 W only

All resistors are P.C. Lead but are not pull offs.
100 min order for each value
NO MIX 100/99

PLASMA DISPLAY KIT

Kit Includes: 12 digit display .4" Character Power supply for display above Complete specs for hookup.

Line cord Not Included. **ONLY \$ 3.95**



SPECIAL DEVICES

| | |
|------------|-------|
| 82S23 | 2.19 |
| 2513 | 10.00 |
| 2102-1 | .99 |
| 1101A | .75 |
| 1103A | 1.10 |
| 8T13 | 1.50 |
| 8T97 | 1.25 |
| MM5233 | 1.50 |
| 300KC xtal | 1.50 |

REGULATORS

| | |
|------|------|
| 7805 | 7818 |
| 7806 | 7824 |
| 7808 | 7905 |
| 7812 | 7912 |
| 7815 | 7915 |

Your Choice \$.95


READOUTS

Best Value!

FND70 .4"C.C. .59
FND800 .8"C.C. 1.69
TI 6 digit array C.C. 3/1.00
MAN 8 .3"CA Yellow .89
LT767 .7"C.C. 4 digit stick **\$ 3.95**

WATERGATE SPECIAL

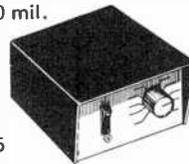Telephone Relay automatically starts and stops tape recorder. No batteries required. Kit complete with drilled P.C. Board.
Parts and Case **ONLY \$ 10.95**



VARIABLE POWER SUPPLY KIT NO. 1

- *Continuously variable from 5V to 20V
- *Excellent regulation up to 500 mil.
- *4400 Mfd of filtering
- *Drilled fiberglass PC Board
- *One hour assembly
- *Kit includes all components
- *Case Included **ONLY \$ 10.95**

VARIABLE POWER SUPPLY KIT NO. 2

Same as above but with 1 amp output, also with case. **ONLY \$ 13.95**

CLOCK KIT

- Kit includes
- LT701 clock module
 - Power Supply
 - Punched Case
 - 12 hour operation only



Complete except for line cord

| | |
|--------|---------------|
| LT701E | 12 hour clock |
| LT701G | 24 hour clock |

ONLY \$ 14.95

BATTERY CLIPS

Standard 9V battery clip with 4-1/2" tinned leads. 25/\$1.00

TRANSISTORS DIODES

| | |
|-------------------|---------|
| *MJE1103 | 3/1.00 |
| MJ3001 | 1.30 |
| 2N2222 | 6/1.00 |
| 2N2369 | 6/1.00 |
| *2N2905 | 4/1.00 |
| *2N2907 | 15/1.00 |
| *2N3906 | 6/1.00 |
| 2N4400 | 6/1.00 |
| 2N4443 SCR | 3/1.00 |
| 1N4004 | 15/1.00 |
| 1N4007 | 10/1.00 |
| 1N4148 (1N914) | 20/1.00 |
| 3N201 VHF Pre-amp | .80 |
| D40C1 Power Darl. | 8/1.00 |
| EN930 | .20 |
| IN746 | .25 |

*House numbered and P.C. Lead

T T L

| | | | |
|-------|------|--------|------|
| 7400 | .17 | 7473 | .21 |
| 7401 | .17 | 74H74 | .45 |
| 7402 | .17 | 7474 | .35 |
| 7403 | .17 | 7475 | .55 |
| 74H04 | .25 | 7476 | .35 |
| 74S04 | .30 | 7480 | .45 |
| 7404 | .17 | 7483 | .76 |
| 7406 | .25 | 7485 | .89 |
| 7408 | .17 | 7486 | .35 |
| 7409 | .17 | 7490 | .71 |
| 7410 | .17 | 7491 | .71 |
| 7411 | .25 | 7492 | .71 |
| 7413 | .45 | 7493 | .67 |
| 7420 | .17 | 7494 | .90 |
| 7421 | .17 | 7495 | .90 |
| 7423 | .35 | 7496 | .85 |
| 7425 | .27 | 74100 | .96 |
| 7426 | .25 | 74121 | .31 |
| 7427 | .17 | 74123 | .61 |
| 7430 | .25 | 74125 | .44 |
| 7432 | .30 | 74141 | .71 |
| 7437 | .35 | 74145 | .97 |
| 7438 | .35 | 74151 | .71 |
| 7440 | .17 | 74153 | .81 |
| 7442 | .60 | 74154 | .97 |
| 7443 | .60 | 74161 | .91 |
| 7444 | .65 | 74163 | 1.05 |
| 7446 | .85 | 74164 | 1.05 |
| 74L47 | 1.75 | 74174 | .91 |
| 7447 | .81 | 74175 | 1.40 |
| 7448 | .81 | 74180 | .76 |
| 7450 | .20 | 74181 | 2.25 |
| 7451 | .17 | 74191 | 1.20 |
| 7453 | .17 | 74192 | 1.20 |
| 7454 | .17 | 74193 | .95 |
| 7470 | .35 | 74S195 | 1.05 |
| 7472 | .21 | 74195 | .65 |

SOCKETS

| | |
|------------------|-----|
| 14 pin | .22 |
| 16 pin | .25 |
| 18 pin | .25 |
| 24 pin (ww only) | .95 |
| 28 pin | .35 |
| 40 pin | .50 |

CMOS SALE

| | |
|--------|------|
| CD4000 | .16 |
| CD4001 | .16 |
| CD4002 | .16 |
| CD4003 | .16 |
| CD4009 | .45 |
| CD4010 | .45 |
| CD4011 | .16 |
| CD4012 | .16 |
| CD4013 | .29 |
| CD4014 | .75 |
| CD4015 | .75 |
| CD4016 | .29 |
| CD4017 | .80 |
| CD4018 | .80 |
| CD4019 | .39 |
| CD4020 | .85 |
| CD4021 | .90 |
| CD4022 | .90 |
| CD4024 | .70 |
| CD4025 | .19 |
| CD4027 | .39 |
| CD4028 | .75 |
| CD4029 | .99 |
| CD4030 | .16 |
| CD4034 | 2.30 |
| CD4035 | .90 |
| CD4040 | 1.00 |
| CD4041 | .69 |
| CD4042 | .59 |
| CD4043 | .60 |
| CD4044 | .59 |
| CD4046 | .90 |
| CD4047 | .99 |
| CD4049 | .35 |
| CD4050 | .35 |
| CD4051 | .90 |
| CD4053 | .90 |
| CD4056 | 1.00 |
| CD4058 | .90 |
| CD4060 | 1.00 |
| CD4066 | .69 |
| CD4069 | .30 |
| CD4071 | .16 |
| CD4076 | .99 |
| 74C04 | .29 |
| 74C107 | .29 |
| CD4116 | .39 |
| CD4507 | .40 |
| CD4512 | .50 |
| CD4516 | .85 |
| CD4518 | .85 |
| CD4520 | .85 |

LS

| | | | |
|---------|------|---------|------|
| 74LS00 | .26 | 74LS145 | 1.00 |
| 74LS02 | .27 | 74LS151 | .70 |
| 74LS03 | .26 | 74LS153 | .70 |
| 74LS04 | .30 | 74LS155 | .69 |
| 74LS05 | .32 | 74LS156 | .76 |
| 74LS08 | .26 | 74LS157 | .95 |
| 74LS09 | .26 | 74LS158 | .85 |
| 74LS10 | .26 | 74LS160 | .85 |
| 74LS11 | .35 | 74LS161 | .85 |
| 74LS13 | .58 | 74LS162 | .85 |
| 74LS14 | 1.05 | 74LS163 | .85 |
| 74LS15 | .26 | 74LS168 | .85 |
| 74LS20 | .24 | 74LS169 | .85 |
| 74LS21 | .35 | 74LS170 | 2.00 |
| 74LS22 | .35 | 74LS173 | 1.10 |
| 74LS26 | .35 | 74LS174 | 1.00 |
| 74LS27 | .35 | 74LS175 | 1.00 |
| 74LS30 | .34 | 74LS190 | .95 |
| 74LS32 | .35 | 74LS191 | .95 |
| 74LS37 | .33 | 74LS192 | .95 |
| 74LS38 | .38 | 74LS193 | .95 |
| 74LS40 | .34 | 74LS194 | .95 |
| 74LS42 | .59 | 74LS195 | .95 |
| 74LS51 | .26 | 74LS196 | .85 |
| 74LS54 | .26 | 74LS197 | .85 |
| 74LS55 | .26 | 74LS251 | .85 |
| 74LS73 | .75 | 74LS253 | .85 |
| 74LS74 | .49 | 74LS257 | .85 |
| 74LS76 | .49 | 74LS258 | .85 |
| 74LS86 | .45 | 74LS260 | .26 |
| 74LS90 | .85 | 74LS266 | .26 |
| 74LS92 | 1.00 | 74LS279 | .55 |
| 74LS93 | 1.00 | 74LS290 | .75 |
| 74LS109 | .49 | 74LS293 | .75 |
| 74LS112 | .49 | 74LS295 | .95 |
| 74LS113 | .40 | 74LS298 | .95 |
| 74LS114 | .40 | 74LS365 | .55 |
| 74LS125 | .55 | 74LS366 | .55 |
| 74LS126 | .65 | 74LS367 | .55 |
| 74LS132 | 1.00 | 74LS368 | .55 |
| 74LS133 | .35 | 74LS390 | 1.75 |
| 74LS136 | .39 | 74LS393 | 1.45 |
| 74LS138 | .85 | 74LS670 | 3.25 |
| 74LS139 | .85 | | |

ORDER BY PHONE. Charge your order to BankAmericard or Master Charge.

USE OUR TOLL FREE WATTS

1-800-527-2304

60 Hz L(•)(•)K


Crystal Time Base Kit - Kit enables a MOS clock circuit to operate from a DC power source. Ideal for car, camper, van, boat, etc.

60Hz output with an accuracy of .005% (typ.) Low power consumption 2.5 ma (typ.). Small size will fit most any enclosure. Single MOS IC oscillator/divider chip 5-15 volts DC operation.

ONLY \$ 5.95
2 for \$10.00

NOW! For the Dallas Area Residents.
Come Visit Our Retail Store.
3717 Lincoln Court, Garland, Texas
Tues. - Fri. 10 AM to 6 PM
Sat. 10 AM to 3 PM
CLOSED MONDAY

NLS NON-LINEAR SYSTEMS, INC.

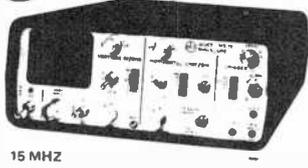

15 MHz OSCILLOSCOPE Case \$30.00 Probe 24.50 \$289.00

MICROPROCESSOR CRYSTALS

| FREQ (MHz) | CASE | P/N | PRICE | FREQ (MHz) | CASE | P/N | PRICE |
|------------|------|------|--------|------------|------|-------|--------|
| 1.00 | HC33 | CY1A | \$8.55 | 10.00 | HC18 | CY12A | \$4.35 |
| 2.00 | HC33 | CY2A | 6.75 | 14.31818 | HC18 | CY16A | 4.35 |
| 3.2768 | HC33 | CY3B | 4.80 | 15.00 | HC18 | CY15A | 4.35 |
| 4.00 | HC18 | CY3A | 4.80 | 18.00 | HC18 | CY19A | 4.35 |
| 4.434 | HC18 | CY4C | 4.80 | 20.00 | HC18 | CY22A | 4.35 |
| 5.00 | HC18 | CY7A | 4.80 | 23.684 | HC18 | CY23B | 4.35 |
| 5.068 | HC18 | CY5B | 4.80 | 27.00 | HC18 | CY27A | 4.35 |
| 5.7143 | HC18 | CY6C | 4.80 | 32.00 | HC18 | CY30A | 4.35 |
| 6.00 | HC18 | CY6B | 4.80 | | | | |

MICROPROCESSOR & SUPPORT CIRCUITS

| Part No. | QTY | Part No. | QTY | Part No. | QTY |
|----------|-------|----------|-------|----------|------|
| PR800A | 17.50 | AVB238PC | 8.20 | MH0026CN | 5.00 |
| CR800A | 19.50 | CR851 | 14.30 | MH0026CM | 5.00 |
| C1702A | 13.40 | CR855 | 13.50 | P2101 | 2.90 |
| C2108 | 33.50 | P2405 | 9.90 | P2101.1 | 4.20 |
| P8212 | 4.10 | 2512K | 4.30 | P2102 | 1.70 |
| P8214 | 8.95 | 2524V | 4.00 | P2102.1 | 3.45 |
| P8216 | 3.90 | 2526V | 2.40 | P2111 | 3.70 |
| AM8224PC | 6.20 | 2533V | 4.90 | P2111.1 | 3.45 |
| P8226 | 3.90 | N8128B | 3.10 | P2112 | 2.90 |
| AM8228PC | 8.20 | N8127 | 1.60 | P2112.2 | 2.90 |



MOTOROLA'S EDUCATOR II MICROCOMPUTER HEP KIT

Motorola M6800 Technology
 Test-as-you-build in easy steps - normally one evening assembly
 Completely self-contained with all parts, cabinet and instructional manual
 Get started in the fascinating world of Micro Computers for only **\$169.95**

EDUCATOR II POWER SUPPLY KIT

5 V @ 1.0 Amps
 Designed specifically for Educator II Microcomputer Kit
 Complete Kit - all parts, cabinet and construction manual **\$29.95**

RESISTOR KITS 5% CARBON FILM RESISTORS

Only in Multiples of 100 pcs per value (ohms)
 1/4W ... \$1.69 per 100
 1/2W ... \$1.79 per 100

| 10 100 1K 10K 100K 1M | 10 100 1K 10K 100K 1M |
|-----------------------|-----------------------|
| 11 | 11 |
| 12 | 12 |
| 13 | 13 |
| 15 | 15 |
| 16 | 16 |
| 18 | 18 |
| 20 | 20 |
| 22 | 22 |
| 24 | 24 |
| 27 | 27 |
| 30 | 30 |
| 33 | 33 |
| 36 | 36 |
| 39 | 39 |
| 43 | 43 |
| 47 | 47 |
| 51 | 51 |
| 56 | 56 |
| 62 | 62 |
| 68 | 68 |
| 75 | 75 |
| 82 | 82 |
| 91 | 91 |

COMPLETE WITH STORAGE BIN
 1/4 WATT KIT 42 Different Values (68Ω to 4.7 MΩ) 20 Each Value
 1/2 WATT KIT 42 Different Values (68Ω to 4.7 MΩ) 20 Each Value
 1/4W - \$24.90 PER KIT
 1/2W - \$29.90 PER KIT

RESISTOR ASSORTMENTS

Each assortment contains 5 pcs each of 10 different values
 Values included are shown in (Ohms)

1/4W.5% (50 pcs total) ... \$1.75 / 1/2W.5% (50 pcs total) ... \$1.85
 Ass1: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56 ohm
 Ass2: 68, 82, 100, 120, 150, 180, 220, 270, 330, 390 ohm
 Ass3: 470, 560, 680, 820 ohm, 1K, 1.2K, 1.5K, 1.8K, 2.2K, 2.7K
 Ass4: 3.3K, 3.9K, 4.7K, 5.6K, 6.8K, 8.2K, 10K, 12K, 15K, 18K
 Ass5: 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K
 Ass6: 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K
 Ass7: 1M 1.2M, 1.5M, 1.8M, 2.2M, 2.7M, 3.3M, 3.9M, 4.7M, 5.6M
 (1% Assortment No 7 doesn't include 5.6M)
 Ass8.R. (All seven assortments above)
 1/4W 5% 350 pcs total \$10.95 1/2W 5% 350 pcs total \$11.55

DIP SOCKETS

LOW PROFILE, SOLDER, TIN

| Pin | 1-24 | 25-49 | 50 UP |
|--------|------|-------|-------|
| 8 Pin | 16 | 15 | 14 |
| 14 Pin | 19 | 18 | 17 |
| 16 Pin | 21 | 20 | 19 |
| 18 Pin | 28 | 27 | 26 |
| 20 Pin | 34 | 33 | 32 |
| 22 Pin | 36 | 35 | 34 |
| 24 Pin | 37 | 36 | 35 |
| 28 Pin | 44 | 43 | 42 |
| 36 Pin | 59 | 58 | 57 |
| 40 Pin | 62 | 61 | 60 |

STANDARD, SOLDER, TIN

| Pin | 25 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 |
|-------|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| 8 Pin | 25 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 |

STANDARD, SOLDER, GOLD

| Pin | 45 | 41 | 37 | 33 | 29 | 25 | 21 | 17 | 13 | 9 | 5 | 1 |
|-------|----|----|----|----|----|----|----|----|----|---|---|---|
| 8 Pin | 45 | 41 | 37 | 33 | 29 | 25 | 21 | 17 | 13 | 9 | 5 | 1 |

JUMPER, XL-1 MINI HOOK TO STACKING BANANA PLUG

Order No. Length Price
 201W 32" \$1.35
 Specify color.

WIREWRAP GOLD (Level No. 3)

| Pin | 45 | 41 | 37 | 33 | 29 | 25 | 21 | 17 | 13 | 9 | 5 | 1 |
|--------|----|----|----|----|----|----|----|----|----|---|---|---|
| 10 Pin | 45 | 41 | 37 | 33 | 29 | 25 | 21 | 17 | 13 | 9 | 5 | 1 |

SANKEN Series SI-1000G amplifiers

are self-contained power hybrid amplifiers designed for Hi-Fi, stereo, musical instruments, public address systems and other audio applications. The amplifiers have quasi-complementary class B output. The circuit employs flip-chip transistors with high reliability and passivated chip power transistors with excellent secondary breakdown strength. Built-in current limiting is provided for SI-1050G and all devices can be operated from a single or split power supply.

SI-1010G (10W output) ... \$ 6.90
 SI-1020G (20W output) ... \$13.95
 SI-1030G (30W output) ... \$19.00
 SI-1050G (50W output) ... \$26.80

Data Sheet Application Notes - \$0.50

E-Z-HOOK

E-Z Hooks have been designed and field tested through the industry to save time and money in commercial electronic production and servicing. The spring-loaded hook attaches firmly, yet so gently it will not damage component - frees hands while testing. Durably constructed and fully insulated to a single contact point assuring true readings. Meets exacting laboratory and space age computer technology requirements. AVAILABLE IN 10 RETMA COLORS: Red, black, blue, green, orange, yellow, white, violet, brown or gray.

MICRO HOOK

XM Micro Hook 11.75" long <1 gram for difficult IC Testing. Permits hookups to delicate wires where weight and leverage may damage component ... \$ 8.80 ea.

Specify color. ORDER P/N XM

Jumper with XM Micro Hooks

| Order No. | Length | Price |
|-----------|--------|--------|
| 204XM-12" | 12" | \$1.70 |
| 204XM-24" | 24" | 1.70 |

Specify color.

XM-S MICRO HOOK SET

(includes 1 ea. red, black, blue, green, orange, yellow, white, brown, violet and gray Micro Hook). At this low price you can afford more than one set.

COMPLETE SET (10) MICRO HOOKS \$7.95

MINI HOOK

X100W Mini Hook (2.25" long) combines rugged construction, miniature size and Finger-size Hypo Action for all the best test connections. Hook is large enough for component leads, yet small enough to get into tight places ... \$ 7.95 ea.

Specify color. ORDER P/N X100W

Jumper with X-100W Mini Hooks

| Order No. | Length | Price |
|-----------|--------|--------|
| 204-12W | 12" | \$1.60 |
| 204-24W | 24" | 1.60 |

Specify color.

Jumper with X-100W Mini Hook to Stacking Banana Plug

| Order No. | Length | Price |
|-----------|--------|--------|
| 201W | 32" | \$1.35 |

Specify color.

EXTRA LONG MINI HOOK

XL 1 Mini Hook (5.0" long) combines all the proven features of the X100W with an extra long body. It will make safe, short-free test connections in card racks and through deep wiring nest up to 4" ... ORDER P/N XL-1

Specify color. \$1.25

JUMPER, XL-1 MINI HOOK TO STACKING BANANA PLUG

| Order No. | Length | Price |
|-----------|--------|--------|
| 201XL-1 | 32" | \$1.95 |

Specify color.

AUDIO POWER AMPLIFIERS 5.5 WATT AN315

Designed for mobile radios, tape players, etc. Easy to use, High Gain - 53 db (Closed Circuit). \$3.90 ea.

SPECIAL FAIRCHILD LM74-PC 3 for \$1.00

INTERFIL 8038 PRECISION WAVEFORM GENERATOR AND VCO

For simultaneous sine, square and triangular waveforms <.001 Hz to 1 MHz. PART NO. 8038CCPD \$3.90

74LS

| 74LS00N | 36 | 74LS08N | 36 | 74LS10N | 32 | 74LS11N | 32 | 74LS12N | 32 | 74LS13N | 32 | 74LS14N | 32 | 74LS15N | 32 | 74LS16N | 32 | 74LS17N | 32 | 74LS18N | 32 | 74LS19N | 32 | 74LS20N | 32 | 74LS21N | 32 | 74LS22N | 32 | 74LS23N | 32 | 74LS24N | 32 | 74LS25N | 32 | 74LS26N | 32 | 74LS27N | 32 | 74LS28N | 32 | 74LS29N | 32 | 74LS30N | 32 | 74LS31N | 32 | 74LS32N | 32 | 74LS33N | 32 | 74LS34N | 32 | 74LS35N | 32 | 74LS36N | 32 | 74LS37N | 32 | 74LS38N | 32 | 74LS39N | 32 | 74LS40N | 32 | 74LS41N | 32 | 74LS42N | 32 | 74LS43N | 32 | 74LS44N | 32 | 74LS45N | 32 | 74LS46N | 32 | 74LS47N | 32 | 74LS48N | 32 | 74LS49N | 32 | 74LS50N | 32 | 74LS51N | 32 | 74LS52N | 32 | 74LS53N | 32 | 74LS54N | 32 | 74LS55N | 32 | 74LS56N | 32 | 74LS57N | 32 | 74LS58N | 32 | 74LS59N | 32 | 74LS60N | 32 | 74LS61N | 32 | 74LS62N | 32 | 74LS63N | 32 | 74LS64N | 32 | 74LS65N | 32 | 74LS66N | 32 | 74LS67N | 32 | 74LS68N | 32 | 74LS69N | 32 | 74LS70N | 32 | 74LS71N | 32 | 74LS72N | 32 | 74LS73N | 32 | 74LS74N | 32 | 74LS75N | 32 | 74LS76N | 32 | 74LS77N | 32 | 74LS78N | 32 | 74LS79N | 32 | 74LS80N | 32 | 74LS81N | 32 | 74LS82N | 32 | 74LS83N | 32 | 74LS84N | 32 | 74LS85N | 32 | 74LS86N | 32 | 74LS87N | 32 | 74LS88N | 32 | 74LS89N | 32 | 74LS90N | 32 | 74LS91N | 32 | 74LS92N | 32 | 74LS93N | 32 | 74LS94N | 32 | 74LS95N | 32 | 74LS96N | 32 | 74LS97N | 32 | 74LS98N | 32 | 74LS99N | 32 |
|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|
|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|---------|----|

NEW ANCRONA DISCOUNT POLICY FOR ALL 7400 SERIES TTL IC'S

BUY 10 PER TYPE ... 5% DISCOUNT
 BUY 25 PER TYPE ... 10% DISCOUNT
 BUY 100 MIXED (100 PER TYPE) ... 15% DISCOUNT
 BUY 1000 MIXED (25 PER TYPE) ... 20% DISCOUNT

USE LAST MONTH'S AD FOR 7400 SERIES PRICES

NEW from FLUKE - MODEL 8020A THE DMM FOR THE PROFESSIONAL

- 200 Hr Battery Life
- 26 Ranges for 7 Functions
- 2000 Count Resolution
- High-Low Power Ohms
- Autozero and Auto-polarity
- MOV-protected to 6000V against hidden transients and overload protection to 300 V AC
- Diode Test Function
- Conductance Function checks leakage resistance to 10,000 meg ohms
- Size: HWL (7.1x3.4x1.8 IN) (18.0x8.6x4.5 cm)
- Weight: 13 oz.

ONLY \$169.00

BUILD A WORKING DPM IN 1/2 HOUR WITH THESE COMPLETE EVALUATION KITS.

Test these new parts for yourself with Intersil's low-cost prototyping kits, complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials, including PC board, for a functioning panel meter.

ICL7106EV (LCO) \$29.95
 ICL7107EV (LED) \$24.95

RCA COSMAC MICROPROCESSOR IC CDP1802CD 4-6 Volt \$29.50

CAPACITORS

50V CERAMIC DISC \$1.00 Per Package

| 5pf | 9/pkg | 300pf | 7/pkg | 0.047mf | 9/pkg |
|-------|-------|---------|-------|---------|-------|
| 15pf | 9/pkg | 330pf | 7/pkg | 0.05mf | 9/pkg |
| 25pf | 9/pkg | 390pf | 7/pkg | 0.1mf | 9/pkg |
| 27pf | 9/pkg | 470pf | 7/pkg | 0.15mf | 8/pkg |
| 47pf | 8/pkg | 560pf | 7/pkg | 0.22mf | 8/pkg |
| 68pf | 8/pkg | 680pf | 7/pkg | 0.22mf | 8/pkg |
| 100pf | 8/pkg | 0.01mf | 9/pkg | 0.3mf | 8/pkg |
| 150pf | 8/pkg | 0.015mf | 9/pkg | 0.39mf | 7/pkg |
| 220pf | 8/pkg | 0.022mf | 9/pkg | 0.47mf | 7/pkg |
| 270pf | 7/pkg | 0.03mf | 9/pkg | 0.1mf | 6/pkg |

PLESSEY POLYESTER MINI BOX

| MF | V | S | MF | V | S | MF | V | S |
|-----|------|----|-----|-----|----|-----|-----|----|
| 001 | 1000 | 14 | 015 | 400 | 15 | 100 | 20 | 0 |
| 002 | 1000 | 14 | 015 | 400 | 15 | 100 | 21 | 0 |
| 005 | 1000 | 14 | 018 | 400 | 15 | 22 | 100 | 23 |
| 008 | 1000 | 14 | 022 | 400 | 15 | 27 | 100 | 26 |
| 022 | 1000 | 14 | 027 | 400 | 15 | 33 | 100 | 30 |
| 027 | 1000 | 14 | 033 | 250 | 15 | 39 | 100 | 33 |
| 033 | 1000 | 14 | 039 | 250 | 15 | 47 | 100 | 36 |
| 039 | 630 | 14 | 047 | 250 | 15 | 56 | 100 | 44 |
| 047 | 630 | 14 | 056 | 250 | 15 | 68 | 100 | 47 |
| 056 | 630 | 14 | 068 | 250 | 15 | 82 | 100 | 54 |
| 068 | 630 | 14 | 082 | 250 | 17 | 100 | 100 | 60 |
| 082 | 630 | 14 | 1 | 100 | 17 | | | |
| 01 | 630 | 14 | 12 | 100 | 18 | | | |

MATSUO DIPPED TANTALUM

| MF | V | S | MF | V | S | MF | V | S |
|-----|----|----|----|----|----|----|----|------|
| 1 | 35 | 33 | 2 | 35 | 40 | 15 | 20 | 45 |
| 15 | 35 | 33 | 2 | 35 | 40 | 15 | 20 | 45 |
| 22 | 35 | 33 | 3 | 35 | 42 | 15 | 35 | 1.32 |
| 33 | 35 | 33 | 4 | 35 | 45 | 22 | 16 | 45 |
| 47 | 35 | 33 | 6 | 16 | 40 | 33 | 20 | 1.32 |
| 68 | 35 | 33 | 6 | 35 | 45 | 47 | 20 | 1.53 |
| 1.0 | 35 | 33 | 10 | 16 | 42 | 68 | 16 | 1.62 |
| 1.5 | 35 | 40 | 20 | 25 | 45 | | | |

1% MICA 500V

| 51 PF | 29 | 220 PF | 41 | 1500 PF | .60 |
|--------|----|---------|----|----------|------|
| 62 PF | 29 | 240 PF | 46 | 2000 PF | .90 |
| 75 PF | 29 | 300 PF | 50 | 2200 PF | .94 |
| 82 PF | 29 | 350 PF | 50 | 4700 PF | 1.80 |
| 100 PF | 30 | 470 PF | 50 | 5100 PF | 1.80 |
| 120 PF | 32 | 620 PF | 52 | 10000 PF | 3.60 |
| 150 PF | 35 | 820 PF | 53 | | |
| 180 PF | 41 | 1000 PF | 60 | | |

ALUMINUM ELECTROLYTIC (RADIAL LEAD)

| MF | V | S | MF | V | S | MF | V | S |
|----|----|----|----|----|----|----|----|----|
| 1 | 10 | 12 | 10 | 16 | 15 | 33 | 25 | 32 |
| 10 | 12 | 10 | 16 | 15 | 33 | 25 | 32 | 30 |
| 10 | 12 | 10 | 16 | 15 | 33 | 25 | | |

ANNOUNCING NEW LOW PRICES AT RADIO SHACK, THE "PARTS PLACE"

Top quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well known American manufacturers, and all have to pass

manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market! Count on Radio Shack for the finest quality parts.



TTL Digital ICs

First Quality Devices Made by National Semiconductor and Motorola

| Type | Cat No. | Last Year | Now Only |
|-------|----------|-----------|----------|
| 7400 | 276-1801 | \$ 49 | 35¢ |
| 7402 | 276-1811 | \$ 49 | 39¢ |
| 7404 | 276-1802 | \$ 59 | 35¢ |
| 7406 | 276-1821 | \$ 69 | 49¢ |
| 7410 | 276-1807 | \$ 49 | 39¢ |
| 7413 | 276-1815 | \$1 19 | 79¢ |
| 7420 | 276-1809 | \$ 49 | 39¢ |
| 7427 | 276-1823 | \$ 69 | 49¢ |
| 7432 | 276-1824 | \$ 69 | 49¢ |
| 7441 | 276-1804 | \$1 59 | 99¢ |
| 7447 | 276-1805 | \$1 99 | 99¢ |
| 7448 | 276-1816 | \$1 99 | 99¢ |
| 7451 | 276-1825 | \$ 49 | 39¢ |
| 7473 | 276-1803 | \$ 79 | 49¢ |
| 7474 | 276-1818 | \$ 79 | 49¢ |
| 7475 | 276-1806 | \$1 19 | 79¢ |
| 7476 | 276-1813 | \$ 79 | 59¢ |
| 7485 | 276-1826 | \$1 59 | 1.19 |
| 7486 | 276-1827 | \$ 69 | 49¢ |
| 7490 | 276-1808 | \$1 19 | 79¢ |
| 7492 | 276-1819 | \$1 19 | 69¢ |
| 74123 | 276-1817 | \$1 69 | 99¢ |
| 74145 | 276-1828 | \$1 49 | 1.19 |
| 74150 | 276-1829 | \$1 79 | 1.39 |
| 74154 | 276-1834 | \$1 79 | 1.29 |
| 74192 | 276-1831 | \$1 69 | 1.19 |
| 74193 | 276-1820 | \$1 69 | 1.19 |
| 74194 | 276-1832 | \$1 69 | 1.19 |
| 74196 | 276-1833 | \$1 69 | 1.29 |

74C and 4000 Series CMOS ICs

| | | | |
|--------|----------|--------|------|
| 74C00 | 276-2301 | \$ 69 | 49¢ |
| 74C02 | 276-2302 | \$ 69 | 49¢ |
| 74C04 | 276-2303 | \$ 69 | 49¢ |
| 74C08 | 276-2305 | \$ 69 | 49¢ |
| 74C71 | 276-2310 | \$1 29 | 89¢ |
| 74C76 | 276-2312 | \$1 59 | 89¢ |
| 74C90 | 276-2317 | \$2 29 | 1.49 |
| 74C192 | 276-2321 | \$2 49 | 1.69 |
| 74C193 | 276-2322 | \$2 49 | 1.69 |
| 4001 | 276-2401 | \$ 69 | 49¢ |
| 4011 | 276-2411 | \$1 29 | 89¢ |
| 4013 | 276-2413 | \$1 69 | 49¢ |
| 4017 | 276-2417 | \$2 49 | 1.49 |
| 4020 | 276-2420 | \$2 49 | 1.49 |
| 4027 | 276-2427 | \$1 29 | 89¢ |
| 4049 | 276-2449 | \$ 99 | 69¢ |
| 4050 | 276-2450 | \$ 99 | 69¢ |
| 4511 | 276-2447 | \$2 69 | 1.69 |
| 4518 | 276-2490 | \$2 49 | 1.49 |

Linear ICs


First Quality Devices by National Semiconductor and Motorola



| Type | Cat No. | Last Year | Now Only |
|--------|----------|-----------|----------|
| 301AH | 276-017 | \$ 69 | 49¢ |
| 324N | 276-1711 | \$1 99 | 1.49 |
| 339N | 276-1712 | \$1 99 | 1.49 |
| 386CN | 276-1731 | \$1 99 | 99¢ |
| 555CN | 276-1723 | \$1 49 | 79¢ |
| 556CN | 276-1728 | \$2 79 | 1.39 |
| 566CN | 276-1724 | \$2 99 | 1.69 |
| 567CN | 276-1721 | \$2 99 | 1.99 |
| 723CN | 276-1740 | \$ 99 | 69¢ |
| 741CN | 276-007 | \$ 69 | 49¢ |
| 741H | 276-010 | \$ 69 | 49¢ |
| 3900N | 276-1713 | \$1 39 | 99¢ |
| 3909N | 276-1705 | \$1 29 | 99¢ |
| 3911N | 276-1706 | \$2 19 | 1.59 |
| 4558CN | 276-038 | \$ 99 | 79¢ |
| 75491 | 276-1701 | \$1 49 | 99¢ |
| 75492 | 276-1702 | \$1 49 | 99¢ |
| 7805 | 276-1770 | \$1 59 | 1.29 |
| 7812 | 276-1771 | \$1 59 | 1.29 |
| 7815 | 276-1772 | \$1 59 | 1.29 |

Experimenter's PC Board

Simplifies IC Projects

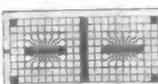


Ideal for two-circuit projects. Fire-retardant copper-clad board is only 2 1/2 x 5 x 1/16". Really simplifies integrated circuit projects by extending leads for easy soldering. 276-151 2.99

Microcomputer Chip


8080A Microprocessor. With a 16-bit address bus capable of addressing up to 65k bytes of memory and up to 256 I/O ports. "TRI-State" data bus gives it DMA and multiprocessing capability. All buses TTL compatible. Up to 244 variable length instructions, with 6 general purpose registers plus an accumulator. 40-pin DIP. 100% Prime. 276-2510 17.95

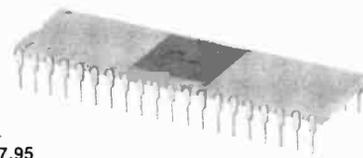RS2102 Static RAM. 1024-word by one bit random access read/write memory. Under 750 nS access. Single +5V power supply. 276-2501 2.49 each or 8/14.95



1795

LEDs/Optoelectronics

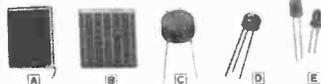

| Item | Cat. No. | Reg. | Now Only |
|----------------------|----------|-------|----------|
| Ⓐ Solar Cell | 276-115 | | 1.59 |
| Ⓑ Silicon Solar Cell | 276-128 | | 1.99 |
| Ⓒ Photocell | 276-116 | | 99¢ |
| Ⓓ FPI 100 | 276-130 | | 79¢ |
| Ⓔ Lg Red LED | 276-041 | 2/69c | 2/49c |
| Ⓕ Lg Cir LED | 276-047 | 2/69c | 2/49c |
| Ⓖ Med Red LED | 276-026 | 2/69c | 2/49c |
| Ⓗ Med Cir LED | 276-040 | 2/69c | 2/49c |
| Ⓙ Sm Red LED | 276-042 | 2/69c | 2/49c |


Digital Displays



| Digits | Size | Drive | Cat. No. | Last Year | Now Only |
|--------|------|-------|----------|-----------|----------|
| Ⓐ 4 | 0.5" | Anod. | 276-1201 | \$9.95 | 6.95 |
| Ⓑ 4 | 0.5" | Cath. | 276-1202 | \$9.95 | 6.95 |

| Digits | Size | Drive | Cat. No. | Last Year | Now Only |
|--------|------|-------|----------|-----------|----------|
| Ⓐ 1 | 0.6" | Anod. | 276-056 | \$3.99 | 2.99 |
| Ⓑ 1 | 0.6" | Cath. | 276-066 | \$3.99 | 2.99 |
| Ⓒ 1 | 0.3" | Anod. | 276-053 | \$2.99 | 1.99 |
| Ⓓ 1 | 0.3" | Cath. | 276-052 | \$2.99 | 1.99 |
| Ⓔ 1 | 0.3" | Anod. | 276-1210 | 4/88.97 | 4/6.99 |
| Ⓕ 1 | 0.3" | Cath. | 276-1211 | 4/88.97 | 4/6.99 |

Project Accessories

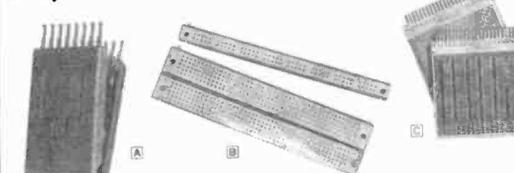

Ⓐ IC Troubleshooting Test Clip. Test up to 14 pins with probes or clips. Reg. 4.59. 276-1950 Sale 2.99

Ⓑ IC Troubleshooting Test Clip. Test up to 16 pins with probes or clips. Reg. 4.99. 276-1951 Sale 3.49

Ⓒ Experimenter Socket. 2x47 rows of 5 connected tie points. 276-172 9.95

Ⓓ Bus Strip. 2x40 connected tie points. Clips to socket above. 276-173 1.99

Ⓔ Standard Edge-Card Board. 1295 mounting holes. 276-152 2.99

Ⓕ 2-Voltage Source Edge-Card Board. 1368 mounting holes. 276-154 2.99

Ⓖ 3-Voltage Source Edge-Card Board. 1368 mounting holes. 276-153 2.99

Ⓗ 22-Pin Edge-Card Board Connector. 44-terminals. 276-1551 2.99

Ⓙ 100-Pin Edge-Card Board Connector. For standard S-100 hobby computer bus. 276-1554 4.99 each or 5/19.95

Ⓙ DIP Header. 16-pin spacing. 276-1980 1.29

Ⓙ Right Angle IC Socket. Mount LED's vertically. 16-pin spacing. 276-1985 1.45

Ⓙ Metal Cabinet. 3 1/2 x 2 1/2 x 4" 2.59

Ⓙ Metal Cabinet. 4x2x6" 3.49

Ⓙ Metal Cabinet. 6 1/2 x 2 1/2 x 7 1/2" 4.49

Transformers

| | | |
|--|----------|-----------|
| 6-3 Volts 1.2 Amps. 1 1/2 x 1 1/2 x 1 1/2" | 273-050 | 2.29 |
| 6-3 Volts, 3 Amps. 2 1/2 x 2 1/2 x 1 1/2" | 273-1510 | 3.99 |
| 12 Volts 5 Amps. 4x2x2 1/2" | 273-1513 | Sale 6.95 |
| 18 Volts (Center Terminal), 4 Amps. Ideal for 5V (using CT), or 12V solid-state regulators. 4x2x2 1/2" | 273-1514 | Sale 6.95 |

Selected Diodes

| Type | Cat. No. | Last Year | Now Only |
|---------------|----------|-----------|----------|
| 1N4001 | 276-1101 | | 2/39c |
| 1N4003 | 276-1102 | 2/59c | 2/49c |
| 1N4004 | 276-1103 | 2/69c | 2/59c |
| 1N4005 | 276-1104 | 2/79c | 2/69c |
| 1N4735 | 276-561 | | 2/89c |
| 1N4739 | 276-562 | | 2/89c |
| 1N4742 | 276-563 | | 2/89c |
| 1N4744 | 276-564 | | 2/89c |
| Trigger Diode | 276-1050 | \$ 49 | 39¢ |
| 1N5401 | 276-1141 | | 2/69c |
| 1N5402 | 276-1142 | 2/89c | 2/79c |
| 1N5403 | 276-1143 | 2/99c | 2/89c |
| 1N5404 | 276-1144 | 2/1.19 | 2/99c |

SCR's and Triacs

| Device | Rating | Cat No. | Last Year | Now Only |
|--------|--------------|----------|-----------|----------|
| LASCOR | 200V, 1.6A | 276-1095 | \$1.59 | 99¢ |
| SCR | 200V, 6A | 276-1067 | \$1.39 | 89¢ |
| SCR | 400V, 6A | 276-1020 | \$1.49 | 99¢ |
| Triac | 200V, 6A | 276-1001 | \$1.39 | 89¢ |
| BR | 400V, 6A | 276-1000 | \$1.49 | 99¢ |
| BR | 50PIV, 1.4A | 276-1151 | | 79¢ |
| BR | 100PIV, 1.4A | 276-1152 | | 99¢ |
| BR | 100V, 4A | 276-1171 | | 1.49 |
| BR | 200V, 4A | 276-1172 | | 1.69 |
| BR | 400V, 4A | 276-1173 | | 1.89 |
| BR | 50PIV, 6A | 276-1180 | | 1.99 |

Digital Car Clock Module



Just add switches and install! Type MA1003, with MOS/LSI clock circuit chip, green fluorescent display with four 0.3" digits. Has 2.09 MHz crystal, blinking colon activity indicator. Six-pin edge-connector. For any 12VDC source. 277-1003 24.95

Low-Profile DIP Sockets

| | | | |
|---------|-----------|-------------------|-------|
| 8-Pin. | 276-1995. | Reg. 2 for \$6.69 | 2/59c |
| 14-Pin. | 276-1999. | Reg. 2 for \$1.19 | 2/89c |
| 16-Pin. | 276-1998. | Reg. 2 for \$1.19 | 2/89c |
| 28-Pin. | 276-1997. | Reg. \$1.19 Each | 89c |
| 40-Pin. | 276-1996. | Reg. \$1.39 Each | 99c |



8-Rocker DIP Switch

Incorporates 8 on-off switches. For easy change of preset logic states. Fits any 16-DIP socket. 275-1301 1.99



WHY WAIT FOR MAIL DELIVERY?
IN STOCK NOW AT OUR STORE NEAR YOU!

Radio Shack®

Prices May Vary at Individual Stores and Dealers

A TANDY COMPANY • FORT WORTH, TEXAS 76102
OVER 6000 LOCATIONS IN NINE COUNTRIES

POPULAR ELECTRONICS

S.D. SALES CO. P.O. BOX 28810 - D DALLAS, TEXAS 75228

★ Imsai - Altair "A" Compatible Kits ★

Dealer inquiries welcome on these items:

Z-80 CPU BOARD

From the same people who brought you the \$89.95 4K RAM KIT. We were not the first to introduce an Imsai/Altair compatible Z-80 Card, but we do feel that ours has the best design and quality for the lowest price! The advance features of the Z-80 such as an expanded set of 158 instructions, 8080A software compatibility, and operation from a single 5VDC supply, are all well known. What makes our card different is the extra care we took in the hardware design. The CPU card will always stop on an M1 state. We also generate TRUE SYNC on card, to insure that the rest of our system functions properly. Dynamic memory refresh and NMI are bought out for your use. Believe it or not, not all of our competitors have gone to the extra trouble of doing this. As always this kit includes all parts, all sockets, and complete instructions for ease of assembly. Because of our past experience with our 4K kit we suggest that you order early. All orders will be shipped on a strict first come first served basis. Kit includes Zilog Manual and all parts. Kit shipped with 2 MHZ crystals.

Z-80 Chip & Manual - \$49.95; Add \$5.00 for Z-80A
Z-80 Manual - \$7.50 Separately.

Complete kit - \$149.

4K LOW POWER RAM

IMSAI AND ALTAIR 8080 PLUG IN COMPATIBLE. USES LOW POWER STATIC 21L02 - 1 500ns. RAM's. FULLY BUFFERED, DRASTICALLY REDUCED POWER CONSUMPTION, ON BOARD REGULATED, ALL SOCKETS AND PARTS INCLUDED. QUALITY PLATED THROUGH PC BOARD. For 250 ns RAM's add \$10.

THE WHOLE WORKS **\$89.95** kit

NEW! DESIGN CONSOLETTA KIT - \$89.95

S.D. Sales announces the inexpensive way to beat the wire wrap jungle. Our latest kit gives you 124 solderless quick connect terminals, enough for eight 16 pin IC's and provides 50 x 8 common buss matrix. Has regulated +5VDC and +/- 15VDC, all at 1 AMP. Voltage regulation at 100%. Also includes a pulse generator variable from 10hz to 50mhz and .01 sec. to 100 nano seconds. Generator output is +5V. In kit form only and includes all parts, sockets; front panel measures 7 1/4" x 8 1/4", and hardware. case not available.

CAR/BOAT KIT

\$34.95

Music to your Ears!

New Item!

MUSICAL HORN

Musical Horn kit for car, boat or home. Plays any tune from Mozart to Led Zeppelin. Change tunes in seconds; complete solid state electronics. Standard or custom tunes available at \$6.95 each. (You supply the sheet music - we supply electronics for your favorite tune.) One song supplied with original order. Standard tunes available: DIXIE - EYES OF TEXAS - ON WISCONSIN - YANKEE DOODLE DANDY - NOTRE DAME FIGHT SONG - PINK PANTHER - AGGIE WAR SONG - ANCHORS AWAY - NEVER ON SUNDAY - BRIDGE OVER RIVER OUI - CANDY MAN - Standard 2 inch 8 ohm speaker supplied. Power horn available for car/boat kit.

HOME KIT

\$26.90

Kit includes speaker which operates from your door bell. When door bell is pushed your favorite tune is played. Car/boat kit includes speaker which operates from car/boat horn ring. Allow 4 weeks delivery on both kits.

Limited Quantity!

\$9.95 kit

6 DIGIT ALARM CLOCK KIT

We made a fantastic kit even better. Redesigned to take advantage of the latest advances in IC technology. Features: Litronix Dual 1/2" displays, Mostek 50250 super clock chip, single I.C. segment driver, SCR digit drivers. Greatly simplified construction. More reliable and easier to build. Kit includes all necessary parts (except case). For P.C. board add \$3.00; AC XFMR add \$1.50. Do not confuse with Non-Alarm kits sold by our competition! Eliminate the hassle - avoid the 5314!

NEW! WITH JUMBO LED READOUTS!

1000 MFD Filter Caps Rated 35 WVDC Up right style with PC leads. Most popular value for hobbyists.

4/\$1.00

SLIDE SWITCH Assortment Our best seller. Includes miniature and standard sizes, single and multi-position units. All new.

12/\$1.00

POWER RESISTOR 15 OHM 25W BY CLAROSTAT

75¢ ea.

RESISTOR ASSORTMENT 1/4W 5% & 10% PC leads. A good mix of values! Special!

200/\$2.

P.C. LEAD DIODES 1N4148/1N914

100/\$2.

1N4002 1A 100 FIV

40/\$1.

THERMISTORS MEPCO - NEW! 1.5K OHM

5/\$1.00

DISC CAP ASSORTMENT P.C. Leads. At least 10 different values. Includes .001, .01, .05 plus other standard values.

60/\$1.00

AMD-1702A

Huge Factory Purchase

FACTORY PRIME UNITS! BRAND NEW!

1.5 Micro-Seconds Access Time.

10/\$40. \$4.95 ea.

★ *Special!* ★

3.579545 MHZ Time Base Crystal \$1.25

28 PIN SOCKETS 3 for \$1.00

11,000 MFD 50WVDC Computer Grade Cap \$3.00 each

39 MFD 16 V Mallory Electrolytic 15 for \$1.00

FACTORY PRIME!

21L02-1

Not only are our RAM'S faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02-1 Low Power and Super Fast RAM'S. Allows you to STRETCH your power supply farther and at the same time keep the wait light off!

500ns 8/\$12.95

250ns 8/\$15.95

IC'S REMOVED FROM PC BOARDS ALL TESTED; FULL SPEC.

IC's from XEROX

1402 A Shift Regulator - 50c MH0025CN - 55c

| | | |
|------------|------------|--------------------|
| 7400 - 9c | 7430 - 9c | 7493 - 26c |
| 7402 - 9c | 7440 - 9c | 74121 - 22c |
| 7404 - 9c | 7437 - 10c | 74123 - 32c |
| 7406 - 11c | 7438 - 10c | 74151 - 9c |
| 7407 - 11c | 7451 - 9c | 74155 - 22c |
| 7410 - 9c | 7474 - 16c | 74193 - 35c |
| 7416 - 13c | 7475 - 24c | 8233 - 35c |
| 7420 - 9c | 7486 - 16c | Intel - 1302 - 45c |

MK50397-\$8.95

S.D. Sales Exclusive! Elapsed time IC. Specially modified six digit counter circuit to measure 59 min., 59 sec., 99/100 sec. Perfect for dark room timers, chess timers or any timing applications. Supplied with data sheet and applications.

MOS 6 Digit Up/Down Counter

40 PIN DIP. Everything you ever wanted in a counter chip. Features: Direct LED segment drive, single power supply (12 VDC TYPE), six decades up/down, pre-loadable counter, separate pre-loadable compare register with compare out-put. BCD and seven segment outputs, internal scan oscillator, CMOS compatible, leading zero blanking, 1MHZ. count input frequency.

\$12.95

CALL IN YOUR BANK-AMERICARD OR MASTER CHARGE ORDER IN ON OUR CONTINENTAL UNITED STATES TOLL FREE WATTS LINE:

Texas Residents Call Collect:

214/271-0022

1-800-527-3460

TERMS:

Money Back Guarantee!

NO COD'S. TEXAS RESIDENTS ADD 5% SALES TAX. ADD 5% OF ORDER FOR POSTAGE & HANDLING. ORDERS UNDER \$10.00 ADD 75c. FOREIGN ORDERS - U.S. FUNDS ONLY!

Orders over \$15. - Choose \$1. FREE MERCHANDISE!

MINI-KITS

FM WIRELESS MIKE KIT

Transmit up to 300 to any FM radio. Sensitive mike input requires dynamic crystal or ceramic mike. Runs on 3 to 9 volts.

TONE DECODER KIT

A complete tone decoder on a single PC board. Features: 400 to 5000 Hz adjustable frequency range, voltage regulation, 56T IC useful for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touch-tone decoding. Runs on 5 to 12 volts.

Complete Kit, TD-1 \$4.95

LED BLINKY KIT

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, or warning type panel lights.

Complete Kit, BL-1 \$2.95

SUPER-SNOOP AMPLIFIER

A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as a general purpose test amplifier. Full 2 watt output, runs on 5 to 12 volts, uses any type of mike. Requires 8-ohm speaker.

Complete Kit, BN-9 \$4.95

MUSIC LIGHTS KIT

See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nice clubs and more.

Complete Kit, ML-1 \$7.95

SIREN KIT

Produces upward and downward wail characteristic of police siren. 2000 mhz audible tone, runs on 3-9 volts, uses 8-ohm speaker.

Complete Kit, SM-3 \$2.95

CODE OSCILLATOR KIT

Powerful 1 watt audio oscillator of approx. 1 mhz, good for many uses. Great for monitoring alarm, battery checker, voltage indicator and code oscillator.

Complete Kit, CPD-1 \$2.60

POWER SUPPLY KIT

Complete triple regulated power supply provides variable 1-5.5 volts at 200ma and 4-5 volts at 1 amp. 500m load regulation, good filtering and small size. Kit tests transistors. Requires 6-8V at 1 amp and 18 to 30VCT.

Complete Kit, PS-3LT \$6.95

DECADE COUNTER PARTS KIT

Includes: 7490A 33 mhz counter, 7475 latch, 7447 LED driver, LED readout, current limit resistors, hook up details and instructions on how to build an easy low cost freq. counter.

Kit of Parts, DCU-1 \$3.50

NEW

Frequency Counter \$79.95 KIT

You've requested it, and now it's here! The CT-50 Frequency Counter Kit has more features than counters selling for twice the price. Measuring frequency is now as easy as pushing a button, the CT-50 will automatically place the decimal point in all modes, giving you quick, reliable readings. Want to use the CT-50 mobile? No problem, it runs equally as well on 12 VDC as it does on 110 VAC. Want super accuracy? The CT-50 uses the popular TV color burst freq. of 3.579545 MHz for time base. Tap off a color TV with our adapter and get ultra accuracy — .001 ppm! The CT-50 offers professional quality at the unheard of price of \$79.95. Order yours today!

CT-50, 60MHz Counter Kit \$79.95
 CT-50WT, 60 MHz counter, wired and tested \$159.95
 CT-600, 600 MHz prescaler option for CT-50, add \$29.95



UTILIZES NEW MOS-LSI CIRCUITRY

SPECIFICATIONS

Sensitivity: less than 25mV
 Frequency range: 5Hz to 60MHz, typically 65MHz
 Gate time: 1 second, 1/10 second, with automatic decimal point positioning on both direct and prescale
 Display: 8 digit red LED .4" height
 Accuracy: 10 ppm, .001 ppm with TV time base!
 Input: BNC, 1 meg ohm direct, 50 ohm with prescale option
 Power: 110 VAC 5 watts or 12 VDC @ 1 Amp
 Size: Approx. 6" x 4" x 2", high quality aluminum case
 Color burst adapter for .001 ppm accuracy available in 6 weeks. CB-1, Kit \$14.95

VIDEO TERMINAL KIT \$149.95

A compact 5 x 10-inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are single 5-volt supply, crystal controlled sync and baud rates (up to 9600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard-operated cursor and page control, parity error display and control, power-on initialization, full 64-character ASCII display, block-type see-thru cursor, keyboard/computer control backspaces, forward spaces, line feeds, rev. line feeds, home, returns cursor. Also clears page. The card requires 5 volts at approx. 300 ma and outputs standard 75 ohm composite video.

TH3216 Kit \$149.95
 TH3216, Assembled and Tested \$239.95
 VD-1, Video to RF Modulator Kit \$ 6.95



600 mhz Prescaler

Fully assembled and tested. Extend the range of your counter to 10 times higher in frequency. Works with any counter. High sensitivity input with built-in on-chip pre-amp.
 PS-1B—10 \$59.95

SIX DIGIT 12/24 HR CLOCK KIT

Want a clock that looks good enough for your living room? Forget the competitor's kludges and try one of ours! Features: jumbo .4" digits, Polaroid lens filter, extruded aluminum case available in 5 colors, quality PC boards and super instructions. All parts are included, no extras to buy. Fully guaranteed. One to two hour assembly time. Colors: silver, gold, black, blue and bronze (specify).

Clock Kit, DC-5 \$22.95
 Alarm Clock, DC-8, 12 hr, only \$24.95
 DC-5 with 10 min. ID timer \$25.95
 Mobile Version, DC-7 \$25.95
 Assembled and tested clocks available, add \$10.00 to kit price.

741 MINI DIP, house marked 10/\$2.00



Satisfaction guaranteed or money refunded. Orders under \$10 add 75c. COD add \$1.00. NY add 7% sales tax.

CAR CLOCK KIT \$27.95



12/24-Hour 12-Volt AC or DC
 • High Accuracy (1 minute/month)
 • 6 jumbo .4" LED readouts
 • Easy, no-polarity hookup
 • Display blanks with ignition
 • Case, mounting bracket included
 • Super Instructions
 Complete Kit, DC-11 \$27.95

LINEAR REGS TRANSISTORS

| | | | | | |
|------|------|---------|------|-------------------|-----------|
| 555 | 50 | 309K | 99 | NPN 2N3904 type | 10/\$1.00 |
| 556 | 75 | 340K-12 | 99 | PNP 2N3906 type | 10/\$1.00 |
| 566 | 1.49 | 7805 | 99 | NPN Power Tab 40W | 3/\$1.00 |
| 567 | 1.49 | 7812 | 99 | PNP Power Tab 40W | 3/\$1.00 |
| 324 | 1.49 | 7815 | 99 | FET MPF-102 type | 3/\$2.00 |
| 1458 | 49 | 78MG | 1.50 | UJT 2N2646 type | 3/\$2.00 |
| 380 | 1.49 | 723 | 49 | 2N3055 NPN Power | .75 |

ramsey electronics

BOX 4072A ROCHESTER, NY 14610 (716) 271-6487

CIRCLE NO. 47 ON FREE INFORMATION CARD

TTL PLASTIC DUAL-IN-LINE I.C.

| | | | | | | | |
|----------|-----|----------|------|-----------|------|-----------|------|
| SN7400N | .12 | SN7453N | .14 | SN74132N | .69 | SN74186N | 7.50 |
| SN7401N | .14 | SN7454A | .14 | SN74136N | .59 | SN74188AN | 1.85 |
| SN7402N | .14 | SN7460N | .14 | SN74141N | .88 | SN74190AN | 1.04 |
| SN7403N | .14 | SN7470N | .26 | SN74142N | 3.70 | SN74191N | 1.04 |
| SN7404A | .17 | SN7472N | .25 | SN74143N | 3.98 | SN74192N | 8.4 |
| SN7405N | .17 | SN7473N | .29 | SN74144N | 3.98 | SN74193N | 8.4 |
| SN7406N | .25 | SN7474N | .28 | SN74145A | .69 | SN74194A | 89 |
| SN7407N | .25 | SN7475N | .46 | SN74147N | 1.58 | SN74195N | 54 |
| SN7408N | .17 | SN7476N | .30 | SN74148N | 1.19 | SN74196N | .87 |
| SN7409N | .17 | SN7480N | .35 | SN74150N | .94 | SN74197N | .73 |
| SN7410N | .14 | SN7481AN | .95 | SN74151N | 61 | SN74198N | 1.60 |
| SN7411N | .20 | SN7482N | .55 | SN74152N | 3.45 | SN74199N | 1.64 |
| SN7412N | .21 | SN7483AN | .65 | SN74153N | .61 | SN74221N | 1.14 |
| SN7413N | .39 | SN7484AN | 1.50 | SN74154N | .95 | SN74246N | 1.95 |
| SN7414N | .62 | SN7485N | .84 | SN74155N | .70 | SN74247N | 1.70 |
| SN7416N | .24 | SN7486N | .30 | SN74156N | .64 | SN74248N | 1.75 |
| SN7417N | .29 | SN7489N | 1.85 | SN74157N | 59 | SN74249N | 1.75 |
| SN7420N | .14 | SN7490AN | .43 | SN74159N | 2.50 | SN74251N | 1.05 |
| SN7421N | .20 | SN7491AN | .59 | SN74160N | .85 | SN74259N | 1.35 |
| SN7422N | .20 | SN7492AN | .44 | SN74161N | .85 | SN74265N | .85 |
| SN7423N | .25 | SN7493AN | .44 | SN74162N | .85 | SN74273N | 1.35 |
| SN7425N | .25 | SN7494N | .69 | SN74163N | .85 | SN74276N | .75 |
| SN7426N | .22 | SN7495AN | .67 | SN74164N | .98 | SN74278N | 1.99 |
| SN7427N | .25 | SN7496N | .65 | SN74165N | .97 | SN74279N | .57 |
| SN7428N | .28 | SN7497N | 2.50 | SN74166N | 1.09 | SN74283N | 1.39 |
| SN7430N | .14 | SN74100N | .97 | SN74167N | 2.75 | SN74284N | 4.50 |
| SN7432N | .23 | SN74104N | .42 | SN74170N | 1.69 | SN74285N | 4.50 |
| SN7433N | .30 | SN74105N | .42 | SN74172N | 8.75 | SN74290N | .85 |
| SN7437N | .21 | SN74107N | .28 | SN74173N | 1.24 | SN74298N | 83 |
| SN7438N | .21 | SN74109N | .47 | SN74174N | .94 | SN74298N | 1.64 |
| SN7440N | .14 | SN74110N | .52 | SN74175N | .84 | SN74351N | 1.92 |
| SN7442N | .37 | SN74111N | .69 | SN74176N | .77 | SN74365N | .65 |
| SN7443N | .68 | SN74116N | 1.50 | SN74177N | .76 | SN74366N | .65 |
| SN7444N | .85 | SN74120N | 1.40 | SN74178N | 1.19 | SN74367N | .65 |
| SN7445N | .65 | SN74121N | .34 | SN74179N | 1.49 | SN74368N | .65 |
| SN7446AN | .70 | SN74122N | .38 | SN74180N | .67 | SN74376N | .75 |
| SN7447AN | .59 | SN74123N | .48 | SN74181N | 1.94 | SN74390N | 1.40 |
| SN7448N | .69 | SN74125N | .40 | SN74182N | .59 | SN74393N | 1.40 |
| SN7450N | .14 | SN74126N | .40 | SN74184N | 1.75 | SN74426N | 4.45 |
| SN7451N | .14 | SN74128N | .59 | SN74185AN | 1.74 | SN74490N | 1.90 |

| | | | | | |
|----------|------|----------|------|----------------|----------------------------------|
| CD4000BE | .13 | CD4052BE | 1.15 | 74C14/40014PC | .75 |
| CD4001BE | .16 | CD4053BE | .89 | 74C85/40085PC | 1.20 |
| CD4002BE | .16 | CD4055BE | 1.29 | 80C97/40097PC | .65 |
| CD4006BE | .99 | CD4060BE | .99 | 80C98/40098PC | .65 |
| CD4007BE | .16 | CD4066BE | .59 | 74C160/40160PC | 1.50 |
| CD4008BE | .80 | CD4068BE | .24 | 74C161/40161PC | 1.50 |
| CD4009BE | .37 | CD4069BE | .24 | 74C162/40162PC | 1.50 |
| CD4010BE | .37 | CD4070BE | .24 | 74C163/40163PC | 1.50 |
| CD4011BE | .16 | CD4071BE | .24 | 74C174/40174PC | 1.40 |
| CD4012BE | .16 | CD4072BE | .29 | 74C175/40175PC | 1.40 |
| CD4013BE | .29 | CD4073BE | .29 | 74C192/40192PC | 1.50 |
| CD4014BE | .74 | CD4075BE | .29 | 74C193/40193PC | 1.50 |
| CD4015BE | .74 | CD4076BE | .98 | 74C194/40194PC | 1.40 |
| CD4016BE | .29 | CD4078BE | .24 | 74C195/40195PC | 1.40 |
| CD4017BE | .79 | CD4081BE | .24 | | |
| CD4018BE | .79 | CD4082BE | .29 | SG3501AT | 3.20 |
| CD4019BE | .38 | CD4085BE | .75 | SG3524J | 7.65 |
| CD4020BE | .84 | CD4086BE | .75 | SG4501T | 1.80 |
| CD4021BE | .89 | CD4502BE | 1.15 | RC4194TK | 3.95 |
| CD4022BE | .89 | CD4507BE | .39 | RC4195T | 2.35 |
| CD4023BE | .16 | CD4518BE | 1.05 | RC4195TK | 3.15 |
| CD4024BE | .67 | CD4511BE | 1.25 | 78H05KC | 6.35 |
| CD4025BE | .16 | CD4512BE | .69 | 7800 Series | .99 |
| CD4026BE | 1.39 | CD4514BE | 2.50 | 7800 Series | 5, 6, 8, 12, 15, 18, 24 Volts |
| CD4027BE | .38 | CD4515BE | 2.50 | 7800 Series | 1.39 |
| CD4028BE | .74 | CD4516BE | .84 | 7800 Series | 5, 6, 8, 12, 15, 18, 24 Volts |
| CD4029BE | .78 | CD4518BE | .84 | 7800 Series | 1.49 |
| CD4030BE | .37 | CD4519BE | .79 | 7800 Series | 5, 6, 8, 12, 15, 18, 24 Volts |
| CD4033BE | 1.60 | CD4520BE | .79 | 7800 Series | 2.29 |
| CD4034BE | 2.95 | CD4522BE | 1.98 | 7800 Series | 2.6, 5, 6, 2, 8, 2, 12, 15 Volts |
| CD4035BE | .98 | CD4526BE | 1.50 | 7800 Series | 1.25 |
| CD4040BE | .99 | CD4527BE | 1.50 | 7800 Series | 5, 6, 8, 12, 15, 18, 24 Volts |
| CD4041BE | .67 | CD4528BE | 1.20 | 7800 Series | 1.35 |
| CD4042BE | .58 | CD4531BE | 1.25 | 7800 Series | 5, 6, 8, 12, 15, 20, 24 Volts |
| CD4043BE | .45 | CD4539BE | 1.20 | 7800 Series | 1.75 |
| CD4044BE | .45 | CD4555BE | .75 | 7800 Series | 1.75 |
| CD4046BE | 2.45 | CD4556BE | .75 | 7800 Series | 1.20 |
| CD4047BE | 2.45 | CD4581BE | 2.25 | 7800 Series | 1.20 |
| CD4049BE | .34 | CD4582BE | .95 | 7800 Series | 1.45 |
| CD4050BE | .34 | CD4585BE | 1.80 | 7800 Series | 1.25 |
| CD4051BE | .89 | | | 7800 Series | 1.80 |
| | | | | 7800 Series | 2.10 |

| | | | | | |
|--|--|--|--|--|--|
| | | | | | TEXAS INSTRUMENTS I.C. SOCKETS (Low Profile Solder Tail) |
| | | | | | Description |
| | | | | | Unit Price |
| | | | | | 8 Pin DIL (C840802) |
| | | | | | 15 |
| | | | | | 14 Pin DIL (C841402) |
| | | | | | 18 |
| | | | | | 16 Pin DIL (C841602) |
| | | | | | 19 |
| | | | | | 18 Pin DIL (C841802) |
| | | | | | 21 |
| | | | | | 20 Pin DIL (C842002) |
| | | | | | 35 |
| | | | | | 22 Pin DIL (C842202) |
| | | | | | 34 |
| | | | | | 24 Pin DIL (C842402) |
| | | | | | 45 |
| | | | | | 28 Pin DIL (C842802) |
| | | | | | 34 |
| | | | | | 40 Pin DIL (C844002) |
| | | | | | 65 |
| | | | | | |
| | | | | | VOLTAGE REGULATORS |
| | | | | | |

Sonar

POLICE
FIRE

RA-422




3-Channel VHF RECEIVER 150-174 MHz

REG. 29.99 **22.99**

•Less Crystals

BSR SMOKE & FIRE DETECTOR

XM-646

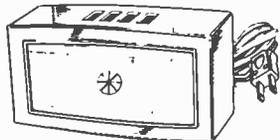


14.99 REG. 19.99

•Protect Your Family

Toshiba TRANSISTOR AMPLIFIER MODULE

XM-670

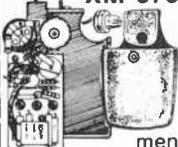

3.99 Reg. 6.99

•Experimenter's Delight



NI-CAD BATTERY "AA SIZE"

\$1 BA-341 EA. REG. 1.50

•1.2 Volts •Rechargeable

REG. NOW

| | |
|--|-------------|
| 2" PM Speaker, 8 Ohms, SS-295 | 2.99 |
| 8-Track Tape Deck with Play-back Pre-Amp., 4-Pole AC Motor, Less Cabinet, RA-604 | 9.99 |
| Ni-Cad Batt. Packs, 2-AA cells-2.4 Volts, BA-359 | 9.99 |
| Ni-Cad Batt. Packs, 3-AA cells-3.6 Volts, BA-327 | 3.50 1.49 |
| Ni-Cad Batt. Packs, 4-AA cells-4.8 Volts, BA-361 | 2.29 |
| Volume Control Kit, 12 Pcs. Assorted, VC-274 | 1.00 .59 |
| Stereophone with Cord & Plug, PH-331 | 7.00 2.99 |
| 100 Pcs. Resistor Kit, 1/4-1/2 Watt, RR-077 | 1.79 .79 |
| 50 Pcs. Elect. Cap. Kit, Low Voltage, Axial-Radial, CD-407 | 5.00 2.99 |
| 40 Pcs. Solder Terminal Strips, XM-501 | 1.30 1.00 |
| AM Pushbutton Auto Radio-New, AU-580 | 10.99 9.99 |
| Sonar 30-50 MHz. (3-Ch.) plus AM std. Broadcast Pocket Receiver, RA-577 | 39.00 29.99 |
| Electronic Camera Shutter Assembly, XM-637 | .99 |
| Singer 12 Digit MOS Calculator Chip with Data Sheet, XM-635 | 2.98 1.79 |
| VHF Varactor Tuner, Data Incl., XM-676 | 1.99 1.49 |
| Electronic "Choo-Choo" Module for Model Railroad, AM-549 | 1.99 .99 |
| Siphon Pump-6 Ft. Squeeze Type, XM-675 | .59 .39 |
| 6 VDC to 12 VDC Converter, AU-297 | 16.00 7.00 |
| 4 Channel Converter for Car Stereo, HF-213 | 7.98 2.00 |
| Tuning Motor 1 Rev. Every 4 Hours 120 VAC, MD-407 | 1.69 .59 |
| Teletron Digital Clock Movement, 1 1/2" Numerals, 117 VAC, 60 Hz. Removed from Equipment, SW-853 | 5.99 4.99 |
| 2 1/2" 60 Ohm Speaker, SP-435 | 1.19 .69 |
| AM-FM-MPX Receiver Chassis, Solid State 11-12 VAC Input, Tape Out Jacks, RA-574 | 9.99 7.99 |
| Universal AC Adapter, 117 VAC Input, 6, 7.5 and 9 VDC Output @ 300 Ma, BA-159 | 7.00 4.99 |

Olson[®] electronics

260 S. FORGE ST.
DEPT. I-4 AKRON, OHIO 44327

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____
ENCLOSE POSTAGE AND SALES TAX

| QTY. | STK # | DESCRIPTION | PRICE EA. | TOTAL |
|------|-------|-------------|-----------|-------|
| | | | | |
| | | | | |

SOLID STATE (Continued from page 87)

signed for operation at 68 to 88 MHz and 148 to 174 MHz, respectively. Each module will deliver better than 18 watts when driven with less than 150 mW at a supply voltage of 12.5 volts.

Motorola Semiconductor Products, Inc. (P.O. Box 20294, Phoenix, AZ 85036) has introduced its own line of wideband r-f amplifier modules. Designed for radio and cable communication systems as well as r-f instrumentation, the Motorola units have a source and load impedance range of 50 to 100 ohms and offer a typical power gain of 36 dB. Types MHW590 and MHW592 are designed for operation on 24-volt dc power sources and cover the ranges of 10 to 400 MHz and 1.0 to 250 MHz, respectively. Types MHW591 and MHW593 require 13.6-volt dc supplies and cover the ranges of 1.0 to 250 MHz and 10 to 400 MHz, respectively. All four modules are designed for operation with a bar-type heatsink for optimum thermal characteristics.

Motorola has entered the solar energy field with a line of semiconductor photovoltaic panels. Initial products are 48-cell and 36-cell arrays. Consisting of interconnected 3-inch silicon wafers, they are available in a variety of series-parallel arrangements to provide various voltage/current output combinations. The panels are suitable for powering remote, unattended equipment, such as microwave relays, navigational aids, cathode protection systems, forestry equipment, and other systems. Energy storage, if required, is provided by batteries. Featuring a unique textured surface consisting of a dense population of microscopic pyramids to provide maximum light absorption, each solar cell is capable of producing in excess of one half-watt of peak power at 25°C. ◇


KEY TO MAGNETIC TAPE RECORDER

Singer/Perlec 4301-7 & 4311-7 systems with display station, keyboard, 7 track magnetic data recorder, controller, etc. Units are used, and were in good running order when removed from service. Sold "AS IS", tapes not included, shipped via truck, freight collect - customer pays all shipping. Manuals available separately. Sh. Wt. 200 Lbs. Md. 4301-7 . . . \$218.88
Complete Manual . . . \$28.50
Md. 4311-7 (includes remote data communication channel) . . . \$248.88
Complete Manual . . . \$28.50



OTHER SINGER SYSTEMS . . . including Md. 52 Line Printer, Work Station, Employee Entrance Station, etc. . . are available from B&F. Send for catalog.

SPEAKER SYSTEMS KIT

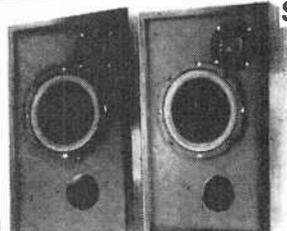

B&F does it again! New speakers and enclosures, includes 8" woofers, 4" dome tweeters, enclosures (21x12x8"), grill cloth, crossover networks, damping, hardware and instructions. A complete kit with quality components at low B&F prices . . . this system sells for \$198 if bought ready-to-go. Now you can afford quality sound! Qty. Ltd., Sh. Wt. 45 Lb. 7ZU70283 . . . \$69.95/pair
Save \$100! . . . 10 kits for \$599.00
CABINETS Only: Sh. Wt. 30 Lb. 70B70197 . . . \$25.00/pair



"THE NAME CALLER"
A fantastic automatic dialing system that will hold up to 38 phone numbers in "memory". You may never see a unit at this low price again! Two (2) types are available: Business (with 40 pin connector for multi-line phones); and Home type. New, ready-to-go. Sh. Wt. 12 Lb. Business type . . . 7ZU70266 . . . \$38.88
Home type . . . 7ZU70265 . . . \$28.88

TV REMOTE CONTROL UNIT

A universal control unit operates your TV at your command from up to 35 feet away. Turns set on or off, as well as changing channels. Fits all sets with turret tuners (dial type channel selector). New, ready-to-go. Sh. Wt. 15 Lbs. 7M170225 . . . \$39.95 ea. . . \$150 for 4

Send Orders To:
B&F ENTERPRISES
Dept. "P"
119 FOSTER STREET
PEABODY, MA. 01960
(617) 531-5774

PHONE ORDERS WELCOME! (617) 531-5774. BANKAMERICARD. MASTERCHARGE. AMERICAN EXPRESS ACCEPTED

T SEND FOR OUR FREE CATALOG - THOUSANDS OF SURPLUS BARGAINS AVAILABLE FOR HOBBYIST & ENGINEER

MIND-ABSORBING PROJECTS FOR EXPERIMENTERS AND HOBBYISTS



ELECTRONIC EXPERIMENTER'S HANDBOOK

Published each year by the editors of Popular Electronics, here's the one publication that helps you get it together . . . with a score of build-it-yourself projects.

The all-new 1978 edition goes on sale nationally October, 1977

It will again be packed with features and articles and complete lab-tested instructions that are sure to guarantee successful days and months of mind absorbing projects for fun and practicality.

**RESERVE
YOUR COPY NOW
AT THE
PRE-PUBLICATION
PRICE OF
ONLY \$1.50**

This offer is being made to readers of Popular Electronics only. Regular price is \$1.95; mail order \$2.50. Save money and enjoy the convenience of having the 1978 ELECTRONIC EXPERIMENTER'S HANDBOOK mailed to you from first-off-the-press copies when published. Complete the Reservation Form and return it promptly with your remittance.

PRE-PUBLICATION RESERVATION FORM

Electronics Experimenter's Handbook
Consumer Service Division
595 Broadway, N.Y., N.Y. 10012 PE-107

Enclosed is \$1.50* (outside U.S.A. \$2) for my copy of the 1978 ELECTRONIC EXPERIMENTER'S HANDBOOK to be mailed to me in October, 1977 when published.

Print Name _____
Address _____
City _____
State _____ Zip _____

*Residents of CA, CO, FL, IL, MI, MO, NY STATE, DC and TX add applicable sales tax.

ABOUT YOUR SUBSCRIPTION


Your subscription to POPULAR ELECTRONICS is maintained on one of the world's most modern, efficient computer systems, and if you're like 99% of our subscribers, you'll never have any reason to complain about your subscription service.

We have found that when complaints do arise, the majority of them occur because people have written their names or addresses differently at different times. For example, if your subscription were listed under "William Jones, Cedar Lane, Middletown, Arizona," and you were to renew it as "Bill Jones, Cedar Lane, Middletown, Arizona," our computer would think that two separate subscriptions were involved, and it would start sending you two copies of POPULAR ELECTRONICS each month. Other examples of combinations of names that would confuse the computer would include: John Henry Smith and Henry Smith; and Mrs. Joseph Jones and Mary Jones. Minor differences in addresses can also lead to difficulties. For example, to the computer, 100 Second St. is not the same as 100 2nd St.

So, please, when you write us about your subscription, be sure to enclose the mailing label from the cover of the magazine—or else copy your name and address exactly as they appear on the mailing label. This will greatly reduce any chance of error, and we will be able to service your request much more quickly.

The J.M.J. DIGITAL DISPLAY BEZEL FOR APPEARANCE AND PERFORMANCE!

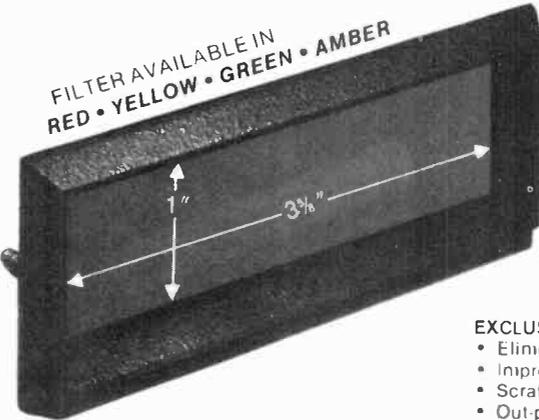Now you can add a truly professional appearance to your digital projects and improve their performance as well . . . With the JMJ BEZEL. It will vastly improve the readability of the display and put a finishing touch on any front panel. And that's important, for obviously, the display is the most looked-at feature on any piece of digital equipment.



\$4.95 EACH
(Please order by color)

**UNIVERSAL SIZE
HANDLES MOST REQUIREMENTS**

EXCLUSIVE CHROMAFILTER® SCREEN

- Eliminates glare and reflections
 - Improves contrast and readability
 - Scratch resistant—easily cleaned
 - Out-performs circular polarized types
 - Available in four colors
- #### DIE CAST METAL FRAME
- Nonreflective black finish
 - Durable—heat resistant
 - Integral 6-32 mounting studs
 - No exposed hardware
 - Mounts in panels up to 3/16" thick
 - Includes all hardware and a special template for easy installation.

© Panelgraphic Corp., W. Caldwell, N.J.

DEALERS INQUIRIES INVITED

ATTENTION CLOCK BUILDERS

Adapters for mounting clock modules and clock displays directly to the JMJ-BEZEL. Assures perfect alignment and simplifies mounting (Please Order by Number).

\$.69 ea.

ADAPTER #1 (Fits the following)

| | | | |
|----------|--------|-------------|------------|
| National | Liton | Texas Inst. | Bowmar |
| MA 1001 | LT 601 | TIL 364 | Opti-Stick |
| MA 1002 | LT 442 | thru | |
| NSB5917 | LT 446 | TIL 372 | |
| NSB5921 | LT 447 | | |
| NSB5922 | | | |

ADAPTER #2 (Fits the following)

| | |
|----------|--------|
| National | Liton |
| MA 1010 | LT 701 |
| MA 1012 | |
| MA 1013 | |

ADAPTER-3 (Universal Mount) For mounting any PC Board to the JMJ-BEZEL (Requires two mounting holes in PC Board).

TERMS: Minimum Order \$4.95
Add \$1.00 for Postage & Handling
N.J. Residents Add 5% Sales Tax
Send Check or M.O. — No COD's

| | | |
|---|-------|-----|
| NAME | | |
| ADDRESS | | |
| CITY | STATE | ZIP |
| ___ J.M.J. BEZELS at \$4.95 EA. (COLOR: _____) | | |
| ___ ADAPTERS at \$.69 EA. (NUMBER: _____) | | |
| POSTAGE & HANDLING | 1.00 | |
| 5% N.J. SALES TAX | | |
| AMOUNT ENCLOSED | | |
| J.M.J. TECHNICAL PRODUCTS, INC. BOX 26, KENDALL PARK, N.J. 08824 | | |

OPERATION ASSIST (continued from page 103)

Halicrafters Model SX-28 "Super Skydrider" receiver. All available information. Matthew Isaacs, 150 Santa Margarita, San Clemente, CA 92672.

Philco Model 39-35 radio. Need schematic, parts list and operating instructions. J.M. Dubiel, 1129 Marion St., Peckville, PA 18452.

Lincoln Model L 2000A, Class D CB transceiver. Schematic and any available information. E.O. Kirkwood, Sr., 137 Snow Hill Dr., Charleston, WV 25311.

Heathkit Model MW-33 CB transceiver. Schematics or manual. Fred J. Winkler, 315 Nashua Dr., Port Richey, FL 33568.

Knight Model T-60 transmitter. Schematic and operating manual. Richard L. Schaut, 1218 Marshall Ave., Green Bay, WI 54301.

Fluke Model 102 VAW meter and Tektronix Model 536 oscilloscope. Need service manuals. Bernard Budny, 434 E. Wilbur Ave., Milwaukee, WI 53207.

Scott "Philharmonic" receiver. Schematic, operating instructions and any available restoration information. Douglas Lake, Box 5101 Station F, Baseline Rd., Ottawa, Ontario, Canada K2C 3H4.

Halicrafters Model S-107. Manual and/or service information. Hart Model 75 shortwave receiver. Schematic and manual and/or service information. Daniel W. Kelly, Box P, Middleton, MA 01949.

Lafayette Model HE-10 or KT-200 receiver. Need alignment procedure information. P. Kaeding, 3917 Kipling Ave. So., St. Louis Park, MN 55416.

Wurlitzer Model 2910 phonograph juke box. Need technical manual. J. Chadek, 2609 River Hills Rd., Two Rivers, WI 54241.

Hammarlund Model HQ-110. Schematics and any available information. Steve Ruten, 3513 57th, Lubbock, TX 79413.

Commercial Trades Institute Model SC30 oscilloscope.

Built from a kit as part of electronics course. Schematics or other available information. Ronald M. Kardos, 2703 Parkland Dr., Brighton, MI 48116.

Precise Model 300B oscilloscope. Schematic and manual. Frank Doering, 6878 S.E. Division, Portland, OR 97206.

Lloyd Model 9M39W-94A solid-state FM multiplex stereo. Need schematic. Dan Viscigiosi, 32 Cresthill Rd., Brighton, MA 02135.

National Model NC-303 receiver. Need instructions and/or schematic. Dumont Model 208-B oscilloscope. Schematic or any available information. Brian Matheny, 7933 Russell Rd., Alexandria, VA 22309.

Dumont Type 274 oscilloscope. Need schematic, service manual and/or operating manual. Stacey Marsella, 27 Hudson Hill Rd., Cranston, RI 02905.

U.S. Navy Type CV-57 teletype demodulator. Operators manual or schematic. Mark A. Vargas, 260 Ft. Wash Ave., New York, NY 10032.

Grand Model FP 1211-G 5-band radio. Need dial stringing

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

| | | | | | | | | |
|--------|----------|----|---------|------|--------|-----|--------|------|
| 7400T1 | 74LS238N | 33 | LM437T | 4.50 | CD4011 | 22 | 74C14 | 2.10 |
| 7400N | 74LS238 | 31 | LM437 | 4.50 | CD4012 | 22 | 74C20 | 2.10 |
| 7402N | 74LS157N | 51 | LM3875 | 1.00 | CD4013 | 39 | 74C30 | 2.90 |
| 7404N | 74LS157 | 51 | LM3875 | 1.00 | CD4015 | 94 | 74C74 | 2.95 |
| 7409N | 74LS283N | 55 | LM3831 | 1.50 | CD4018 | 99 | 74C145 | 1.40 |
| 7410N | 74LS283 | 55 | LM3831 | 1.50 | CD4019 | 100 | 74C90 | 1.15 |
| 7414N | 74LS107N | 38 | LM7079N | 1.50 | CD4020 | 100 | 74C106 | 2.10 |
| 7420N | 74LS112N | 38 | LM7079 | 1.50 | CD4020 | 111 | 74C107 | 2.10 |
| 7422N | 74LS112 | 38 | LM7079 | 1.50 | CD4021 | 111 | 74C107 | 2.10 |
| 7423N | 74LS112N | 38 | LM7079 | 1.50 | CD4022 | 111 | 74C107 | 2.10 |
| 7424N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7425N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7426N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7500N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |

P.O. Box 44300 Santa Clara, CA 95054
(408) 988-1640

| | | | | | | | | |
|--------|----------|----|---------|------|--------|-----|--------|------|
| 7400T1 | 74LS238N | 33 | LM437T | 4.50 | CD4011 | 22 | 74C14 | 2.10 |
| 7400N | 74LS238 | 31 | LM437 | 4.50 | CD4012 | 22 | 74C20 | 2.10 |
| 7402N | 74LS157N | 51 | LM3875 | 1.00 | CD4013 | 39 | 74C30 | 2.90 |
| 7404N | 74LS157 | 51 | LM3875 | 1.00 | CD4015 | 94 | 74C74 | 2.95 |
| 7409N | 74LS283N | 55 | LM3831 | 1.50 | CD4018 | 99 | 74C145 | 1.40 |
| 7410N | 74LS283 | 55 | LM3831 | 1.50 | CD4019 | 100 | 74C90 | 1.15 |
| 7414N | 74LS107N | 38 | LM7079N | 1.50 | CD4020 | 100 | 74C106 | 2.10 |
| 7420N | 74LS112N | 38 | LM7079 | 1.50 | CD4020 | 111 | 74C107 | 2.10 |
| 7422N | 74LS112 | 38 | LM7079 | 1.50 | CD4021 | 111 | 74C107 | 2.10 |
| 7423N | 74LS112N | 38 | LM7079 | 1.50 | CD4022 | 111 | 74C107 | 2.10 |
| 7424N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7425N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7426N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7427N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7428N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7429N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7430N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7431N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7432N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7433N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7434N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7435N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7436N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7437N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7438N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | 22 | 74C160 | 1.44 |
| 7439N | 74LS112N | 38 | LM7079 | 1.50 | CD4023 | | | |

Instructions or diagram. Bernard Grupe, 3012 Highland Dr., Cary, IL 60013.

ET/D Tekfax. Diagrams wanted, prior to #1294 (May 1970). Donald R. Hicke, 11381 Bootes St., San Diego, CA 92126.

Knight-Kit Model 83 YZ 945 lab oscilloscope. Operation manual and/or schematic. P.J. Strimple, Rt. 1, Box 1091, Bay City, TX 77414.

Precision Model E200-C signal generator. Schematic needed. Harold McCann, 803 South Oak, 3D, Ottawa, KS 66067.

Hammarlund Model BC779 general coverage receiver. Schematic and owner's manual and/or alignment information. Daniel Ginsberg, Box 163, Albion, CA 95410.

Philco Model 37-630. Need schematic diagram. Danny To-var, 4700 Rockmoore Ln, Fort Worth, TX 76116.

Sears Model 562-41920101 portable color television. Need service manual. George Comber, 122 Maline Ave., Cherry Hill, NJ 08002.

Motorola Model DS9660-B Conelrad receiver. Operating manual, schematics and crystal. D. Smith, 1369 Tree Garden Place, Concord, CA 94518.

Zenith Model 7G605 5-band shortwave radio. Need any information. Bruce Kahn, 2034 Ramlow Place, St. Paul, MN 55116.

Motorola Model HI3-11AH SP2 "Handie-Talkie." Schematic and operations manual. Also plug-in modules for unit. David Moody, 4305 S. 8th St., Terre Haute, IN 47802.

U.S. Navy Surplus signal generator, military designation TS-413/U. Covers 10 kHz to 40 MHz. Schematic, tech manual, or any other available information. Jack Rutherford, Box 3124, Burlington, NC 27215.

Philco Models 16; 37-62; PT-38; 46-132; 40; 120 radios. Schematics or any available information. Martin Nevros, 850 Main St., Oxford, FL 32684.

Lago Model C86 (serial no. C860001110) desk calculator. Schematic, parts list and manual. Charles Dawson, 10503 Kibbee Ave., Whittier, CA 90603.

WOW!

THIS MONTH'S LINEAR SPECIALS!

340K-5
5volt 1amp
TO-3 REG. **59¢**

723 volt. reg. 14 pin dip **.29**
747 dual 741 14 pin dip **.39**
748 hi-perf 741 8 pin dip **.20**
1458 dual 741 8 pin dip **.39**

ALL 100% PRIME!



EDGE CONNECTORS

22 PIN, 0.156" centers, for 1/16" board. GOLD contacts, solder term. C-3104

YOUR CHOICE **99¢ ea**

22 DUAL (44) PIN, 0.156" centers, 1/16" board, GOLD contacts, WIREWRAP terminals. C-3103

STOCK UP NOW ON 'POP' SEMI'S!

1N4148 Si signal diode UHF... 20/51
1N4448 similar to 1N4148... 25/51
2N706 NPN hi speed switch... 10/51
2N930 NPN RF amp... 10/51
2N1132 PNP comp. to 2N2219... 8/51
2N2219 NPN 3W 250 Mhz amp... 8/51
2N2222 NPN gen. purpose... 10/51
2N2905 PNP hi speed sw... 10/51
2N2907 PNP gen. purpose... 10/51



See our prices are for real and so in our merchandise. This is 100% prime, marked, banded and guaranteed stuff! COMPARE OUR PRICE & QUALITY.

DATA BOOKS

RCA CMOS 845 PAGES Complete electrical, mechanical info for all 4000 series devices.


YOUR CHOICE **99¢**

MOTOROLA REFERENCE VOLUME Includes data for most 1N, 2N type nos., diodes, trans., transistors, varactors, etc., plus linear, digital IC selector guides.

MORE GOODIES

1N4001... 10/64
1N4002... 10/66
1N4003... 10/68
1N4004... 10/70
7001 clock/calendar IC... 6.50
8038 Function Gen. IC... 4.95
40901 ea 200V Triac lab... .49
MA1003 Car Clock... \$24
DL707 0.3" CA Display... .95
DL707 0.6" CA Display... 1.95
RED LED's Lumbo diff... 10/51
GREEN LED's Lumbo diff... 6/51
6.3 x 1A XFORMER... 1.50
1,000 Mid 35v anat.lytic... .50
2,000 Mid 35v anat.lytic... .50
8,000 Mid 35v anat.lytic... 1.29

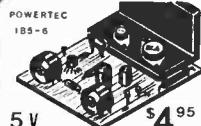AMPHENOL 15 PIN EDGE CONNECTORS GOLD - WITH KEY UNHEARD OF PRICE!




5V 6AMP REGULATOR CARD **\$4.95**

Build a 5V, 6A Supply

1N3209 15A 100V **29¢** RECTIFIER ea.

30,000 MFD 10V FILTER CAPACITOR Computer grade **\$1.49** Mfg by STM

MOLEX PINS

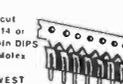

14 Pin **10¢**
16 Pin **12¢**



ROCKER SWITCHES **10¢/\$1**



PC SLIDE SWITCHES **20¢/\$1**



VOLUME CONTROLS **6¢/\$1**

DIAMONDBACK ELECTRONICS COMPANY
PO BOX 194
SPRING VALLEY, IL 61362

SEND STAMP FOR Free Catalog
TERMS: ALL MERCHANDISE 100% GUARANTEED
MINIMUM ORDER \$5
PLEASE INCLUDE SUFFICIENT POSTAGE
ILL RESIDENTS ADD 5% SALES TAX
PHONE ORDERS: 815/664-1511

UNIVERSAL 4K x 8 MEMORY BOARD KIT \$74.50
32-2102-1 fully buffered, 16 address lines, on board decoding for any 4 of 64 pages, standard 44 pin buss.

EXPANDABLE F8 CPU BOARD KIT \$99.00
featuring Fairbug PSU, 1K of static ram, RS 232 interface, documentation, 64 BYTE register

4K BASIC FOR FAIRBUG F8 on paper tape \$25.00

C/MOS (DIODE CLAMPED)
74C10 .22 4012-.22 4023-.22 4042-.78
74C193-1.50 4013-.40 4024-.75 4046-2.25
4001-.22 4015-.95 4025-.22 4049-.40
4002-.22 4016-.40 4027-.40 4050-.40
4006-1.20 4017-1.05 4028-.88 4055-1.50
4007-.22 4018-1.00 4029-1.10 4066-.80
4005-.42 4019-.25 4030-.22 4071-.27
4010-.42 4020-1.05 4033-1.50 4076-1.05
4011-.22 4022-.95 4035-1.10

WSU-30 Hand wire wrap tool used to wrap, unwrap & Strip #30 wire **\$5.50**

#24, EIGHT CONDUCTOR SPECTRA FLAT CABLE 10/51.50
#30 WIRE WRAP WIRE SINGLE STRAND 100/\$1.40

2/08 BK EPROM \$20.95
2522 STATIC SHIFT REG \$1.95
2513 CHARACTER GEN \$9.95
2518-HEX 32 BIT SR \$2.50
2102-1 1024 BIT RAM \$1.29
21078 \$4.25
MK4008P \$1.95
5280 4K DYNAMIC RAM \$4.75
1101A 256 BIT RAM \$3.85
MMS203 UV PROM \$6.95
1702A UV PROM \$4.95
504-4K PROM \$10.95
AY-5-1013 UART \$6.95

LIGHT ACTIVATED SCR TO 18, 200V 1A \$1.10
IN 4148 (IN914) 15 \$1.00
MCA 81 OPTICAL LIMIT SWITCH \$1.50

LED READOUTS
FND 359 C.C. 4" \$50 HP 7740, 3" C.C. \$1.25
FND 70 C.C. 4" \$55 MAN-7, 3" C.A. \$.95
FND 503 C.C. 5" \$85 NS 33-3 dig array \$.75
FND 510 C.C. 5" \$85 DL 747 C.A. 6" \$1.95

Terms: FOB Cambridge, Mass. Send 25¢ for our catalog featuring Send Check or Money Order. Include Postage, Minimum Order \$5.00, COD \$20.00. Transistors and Rectifiers 145 Hampshire St., Cambridge, Mass.

PRINTED CIRCUIT BOARD
4 1/2" x 6 1/2" SINGLE SIDED EPOXY BOARD 1/16" thick unetched \$5.60 ea. 5/52.60

7 WATT LED-65 LASER DIODE IR \$89.50
2N3820 P FET \$4.45
2N5457 N FET \$4.45
2N2646 \$4.45
ER 900 TRIGGER DIODES 4 \$1.00
2N 6028 PROG UJT \$6.00

MINIATURE MULTI-TURN TRIM POTS 100, 500, 1K, 2K, 5K, 10K, 25K, 50K, 100K, 200K, 500K 1 Meg. \$7.50 each. 3/52.00
MULTI-TURN TRIM POTS Similar to Bouras 3010 style 3/16" x 5/8" x 1 1/4" 50, 100, 1K, 10K, 50K ohms \$1.50 ea. 3/54.00

VERIPAX PC BOARD
This board is a 1/16" single sided paper epoxy board, 4 1/2" x 6 1/2" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with buses for power supply connector. \$4.00
MV 5691 YELLOW-GREEN \$4.00
BIPOLAR LED \$.90
FP 100 PHOTO TRANS \$.50
RED, YELLOW, GREEN or AMBER \$1.00
LARGE LED'S \$.75
1LS (MCT-2) \$.75
MOLEX PINS 1000/\$1.00 1000/\$8.00

10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 12, 15, 18, 22, 100, 150 or 200V. ea. \$.60
1 WATT ZENERS 4.7, 5.6, 10, 12, 15, 18 or 22V. ea. \$.25
MC6860 MODEM CHIP \$9.95

Silicon Power Rectifiers
PRV 1A 3A 12A 50A 125A
100 06 14 30 80 3 70
200 07 20 35 115 4 25
400 09 25 50 140 6 50
600 11 30 70 180 8 50
800 15 35 90 2 30 10 50
1000 20 45 110 2 75 12 50

SILICON SOLAR CELLS
2 1/2" diameter
4V at 500 ma. \$4.00 / 2V at 200 ma. \$2.00

REGULATORS
309K \$.95 340K \$ 12.15
723 \$.50 or 24V \$.85
LM 376 \$.60 340T-5, 6, 8, 12
320K-5 or 15V \$1.40 15, 18 or 24V \$1.10
320T-5, 12, 15 78 MG \$1.35
or 24V \$.85 79 MG \$1.35

RS232 DB 25P male \$2.95
CONNECTORS DB 25S female \$3.50

TRANSISTOR SPECIALS

2N3585 NPN Si TO-66 \$.95
2N3772 PNP Si TO-3 \$ 1.60
2N1546 NPN GE TO-3 \$.75
2N4908 PNP Si TO-3 \$ 1.00
2N5086 NPN Si TO-3 \$ 1.70
2N5086 PNP Si TO-3 \$ 1.00
2N4898 PNP TO-66 \$.60
2N404 PNP GE TO-5 \$ 5/100
2N3919 NPN Si, TO-3 RF \$ 1.50
3/52 100
MPSA 13 NPN Si TO-92 \$.70
2N3767 NPN Si TO-66 \$.70
2N2222 NPN Si TO-18 \$ 5/100
2N3055 NPN Si TO-3 \$.70
2N3904 NPN Si TO-92 \$ 5/100
2N3906 PNP Si TO-92 \$ 5/100
2N5296 NPN Si TO-220 \$.50
2N6109 PNP Si TO-220 \$.55
2N3638 PNP Si TO-5 \$ 5/100
2N651 7 NPN TO-92 Si 3/5 1.00

TTL IC SERIES
7400-.14 7445-.55 74151-.60
7401-.14 7446-.65 74153-.60
7402-.14 7447-.65 74154-.95
7403-.14 7448-.65 74155-.70
7404-.18 7450-.15 74157-.58
7405-.18 7472-.29 74161-.85
7406-.25 7473-.29 74163-.80
7407-.25 7474-.29 74164-.95
7408-.18 7475-.45 74165-.95
7409-.17 7476-.30 74173-1.20
7410-.14 7480-.35 74174-.95
7411-.20 7483-.62 74175-.82
7412-.20 7485-.87 74176-.75
7413-.39 7486-.30 74177-.75
7414-.63 7489-1.85 74180-.65
7416-.25 7490-.42 74181-1.90
7417-.25 7491-.58 74190-1.00
7420-.14 7492-.43 74191-1.00
7425-.25 7493-.45 74192-.83
7426-.22 7494-.70 74193-.83
7427-.25 7495-.65 74194-.85
7430-.14 7496-.65 74195-.52
7432-.25 74107-.28 74198-.86
7437-.21 74121-.33 74257-1.25
7438-.21 74123-.65 74279-.87
7440-.14 74125-.40 75324-1.75
7441-.70 74126-.40 75491-.65
7442-.40 74150-.90 75492-.65

MINIATURE DIP SWITCHES
CTS-206-4 Four SPST switches in one minidip package \$1.75
CTS-206-8 Eight SPST switches in a 16 pin dip package \$1.95

5.8V SPST Miniature reed. relay, normally open, 330 Ohm coil resistance \$.75, 3/52.00

ALCO MINIATURE TOGGLE SWITCHES
MTA 10V SPDT \$1.20
MTA 20V DPDT \$1.70

Full Wave Bridges

PRV 2A 6A 25A
200 75 1.25 2.00
400 90 1.50 3.00
600 1.20 1.75 4.00

SANKEN AUDIO POWER AMPS
Si 1010 G 10 WATTS \$ 7.95
Si 1020 G 20 WATTS \$15.95
Si 1050 G 50 WATTS \$27.95

TANTALUM CAPACITORS
.22UF 35V 5/51.00 10UF 20V \$.25
47UF 35V 5/51.00 15UF 35V 3/51.00
1UF 35V 5/51.00 30UF 6V 5/51.00
2.2 UF 20V5/51.00 33UF 35V \$.40
3.3UF 35V 4/51.00 47UF 20V \$.35
4.7UF 15V 5/51.00 68UF 15V \$.50
6.8UF 35V 4/51.00

M/001 ALARM CLOCK CHIP \$5.75

74LS SERIES
74LS00-.23 74LS126-.65
74LS02-.23 74LS136-.80
74LS03-.23 74LS138-.38
74LS04-.28 74LS139-.72
74LS05-.28 74LS139-.72
74LS08-.23 74LS139-.98
74LS09-.33 74LS153-.92
74LS10-.23 74LS155-1.40
74LS11-.23 74LS156-.92
74LS12-.23 74LS156-1.00
74LS13-.23 74LS156-1.00
74LS14-.23 74LS156-1.00
74LS100-.23 74LS156-1.00


TRIACS 2CR'S

PRV 1A 10A 25A 15A 6A 35A
100 40 1.0 1.30 40 50 1.20
200 70 1.10 75 60 70 1.60
400 1.10 1.60 2.60 1.00 1.20 2.00
600 1.70 2.30 3.60 1.50 3.00

SOLID STATE SALES
P.O. BOX 74A
SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

| READER SERVICE NO. | ADVERTISER | PAGE NO. |
|------------------------|--|----------------|
| 1 | A P Products Incorporated | 95 |
| 2 | Ace Electronics | 120 |
| | Acoustic Fiber Sound Systems, Inc. | 112 |
| 3 | Active Electronic Sales Corp. | 116 |
| 6 | Advanced Computer Products | 117 |
| 7 | Ancrona Corp. | 113 |
| 8 | Avanti Research & Development, Inc. | 89 |
| 68 | B & F Enterprises | 118 |
| 9 | B&K Precision, Dynascan Corporation | 5 |
| 10 | CB Radio Repair Course, The | 96 |
| | CREI Capitol Radio Engineering Institute | 62, 63, 64, 65 |
| | Cleveland Institute of Electronics, Inc. | 18, 19, 20, 21 |
| 11 | Cobra, Division of Dynascan | SECOND COVER |
| 67 | Communications Electronics | 101 |
| 12 | Contemporary Marketing, Inc. | 40 |
| 13 | Continental Specialties Corporation | 13 |
| 65 | Davis Electronics | 102 |
| 14 | Diamondback Electronics Co. | 121 |
| 15 | Digi-Key Corporation | 104 |
| 16 | Digital Group, The | 42 |
| 17 | E.D.I. | 117 |
| 18 | EICO | 103 |
| 66 | Eastman Kodak | 126 |
| 19 | Edmund Scientific Co. | 108 |
| 20 | Extron LIFESCREEN Projection System | 89 |
| | Fluke | 71 |
| 21 | Godbout Elecs., Bill | 122 |
| | Health Company | 28, 29, 30, 31 |
| 5 | Health Company | 72, 73, 74, 75 |
| 23 | Illinois Audio | 98 |
| 24 | International Electronics Unlimited | 122 |
| 25 | J.M.J. Technical Products Inc. | 119 |
| 26 | JS&A | 6, 7 |
| 27 | James Electronics | 106, 107 |
| 28 | James Electronics | THIRD COVER |
| 33 | Johnson Co., E.F. | FOURTH COVER |
| 29 | MTS | 24, 25 |
| 30 | Mallory & Co., Inc., P.R. | 1 |
| 31 | McIntosh Laboratory, Inc. | 99 |
| 32 | McKay Dymek Co. | 103 |
| | NRI Schools | 8, 9, 10, 11 |
| | National Technical Schools | 82, 83, 84, 85 |
| 34 | Netronics R & D Ltd | 92 |
| 35 | New-Tone Electronics | 105 |
| 36 | Newman Computer Exchange | 97 |
| 37 | OK Machine & Tool Corporation | 81 |
| 38 | Opton Electronics | 118 |
| 39 | Optoelectronics, Inc. | 100 |
| 40 | Orient-Pacific | 98 |
| 41 | PAIA Electronics, Inc. | 103 |
| 42 | Poly Paks | 111 |
| 64 | Projectapix, Ltd. | 103 |
| 43 | Quest Electronics | 120 |
| 44 | Radio Hut | 112 |
| | Radio Shack | 33, 79, 114 |
| 47 | Ramsey Electronics | 116 |
| 48 | Regency Electronics | 15 |
| 49 | S.D. Sales Co. | 115 |
| 51 | Schober Organ Corp., The | 99 |
| 50 | Scientific Audio Electronics, Inc. | 27 |
| 52 | Shure Brothers Inc. | 41 |
| 53 | Solid State Sales | 121 |
| 54 | Southwest Technical Products Corporation | 2 |
| 55 | Stanton Magnetics, Inc. | 23 |
| 56 | T K Enterprises | 96 |
| 57 | Tec-West U.S.A. Inc. | 102 |
| 59 | Tri-Tek, Inc. | 87 |
| 60 | Turner Division, Conrac | 14 |
| 4 | United Audio Products, Inc. | 37 |
| 61 | Wahl Clipper Corporation | 92 |
| 62 | Weller-Xcelite, Inc. | 38 |
| 71 | Wersi Electronics Inc. | 102 |
| CLASSIFIED ADVERTISING | | 123, 124, 125 |

COMPUTERS

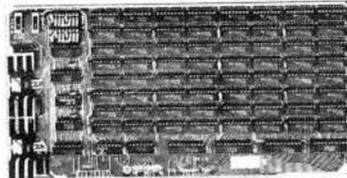

8K ECONORAM II™ \$16384

3/\$450 (24K OF MEMORY!)

S-100 compatible; configured as two separate, protected 4K blocks. Provides interrupt on write attempt into protected block. Buffered address and data in, buffered tri-state outputs. Static memories with low power Schottky support gives 450 ns speed, under 1.5A current as guaranteed specs. Writes on PWR or MWRITE (switch selectable); wait state option also available. Lots of bypass caps; sockets for all ICs. Solder masked board.

Prices above are kit form. Also available assembled, tested, and warranted for 1 year. 1 board....\$188.50 3 boards....\$525.00

10 Slot Motherboard \$90

18 Slot Motherboard \$124

Both have edge connectors, active terminations

CPU POWER SUPPLY \$50

5V @ 4A, +12V @ ½A, -12V @ ½A. With crowbar.

TERMS: Prices good thru 10/31. Add 50¢ to orders under \$10. Cal. res add tax. Add 5% shipping, more for power supplies; excess refunded. BankAmericard®/VISA®/Mastercharge® (\$15 minimum) call (415) 562-0636, 24 hours.

COMPONENTS

Selected from our large inventory of parts:


| | |
|---------------------------------------|---------|
| 75454 interface driver | \$ 0.31 |
| 75461 interface driver | \$ 0.31 |
| 78L12 +12V regulator, TO-92 package | \$ 0.30 |
| 78L15 +15V regulator, TO-92 package | \$ 0.30 |
| 2102L-1 fast, low power 1K static RAM | \$ 1.95 |
| 8080A 8 bit microprocessor | \$12.95 |
| 2708 full speed EROM | \$25.00 |
| VECTOR 8800V prototype board | \$19.95 |
| 8PST Dip switch, toggle action | \$ 2.25 |

We also stock a full line of CMOS, low power Schottky, and linear ICs at very competitive prices. See our flyer for full listings.

...AND KITS

12 Volt, 8 Amp Power Supply

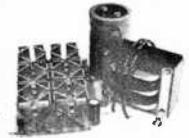\$44.50 + postage. Ideal for CB, ham, bench use. 0.05V regulation, short proof, crowbar overvoltage protection. Current limited. Less hardware and case.



Grandson of a Cheap Clock

\$14.50 6 digit clock features 4/10" digits, separate driver and segment transistors for extra brightness, and choice of 12/24 hour or 50/60 Hz operation. Includes transformer, but less case and hardware.

GODBOUT

send for our flyer

BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614
CIRCLE NO 21 ON FREE INFORMATION CARD

INTERNATIONAL ELECTRONICS UNLIMITED

10% OFF WITH \$25 ORDER
15% OFF WITH \$100 ORDER

THESE DISCOUNTS APPLY TO TOTAL OF ORDER — SPECIALS INCLUDED

| | | | | | |
|------|-----|-------|------|-------|------|
| TTL | .13 | 7451 | .17 | 74153 | .89 |
| 7400 | .16 | 7453 | .17 | 74154 | 1.20 |
| 7402 | .15 | 7454 | .17 | 74155 | .97 |
| 7403 | .15 | 7460 | .17 | 74156 | .97 |
| 7404 | .16 | 7464 | .35 | 74157 | .99 |
| 7405 | .19 | 7465 | .35 | 74158 | 1.79 |
| 7406 | .26 | 7470 | .30 | 74160 | 1.23 |
| 7407 | .28 | 7472 | .30 | 74161 | .97 |
| 7408 | .29 | 7471 | .35 | 74162 | 1.39 |
| 7409 | .19 | 7474 | .28 | 74163 | 1.09 |
| 7410 | .16 | 7475 | .49 | 74164 | .99 |
| 7411 | .25 | 7476 | .30 | 74165 | .99 |
| 7413 | .43 | 7483 | .48 | 74166 | 1.25 |
| 7414 | .65 | 7485 | .88 | 74170 | 2.10 |
| 7416 | .35 | 7486 | .40 | 74171 | 1.49 |
| 7417 | .35 | 7489 | 2.25 | 74174 | 1.23 |
| 7420 | .16 | 7490 | .43 | 74175 | .97 |
| 7422 | .30 | 7491 | .75 | 74176 | .89 |
| 7423 | .29 | 7492 | .48 | 74177 | .84 |
| 7425 | .27 | 7493 | .48 | 74180 | .90 |
| 7426 | .26 | 7494 | .78 | 74181 | 2.45 |
| 7427 | .29 | 7495 | .79 | 74182 | .79 |
| 7430 | .20 | 7496 | .79 | 74184 | 1.90 |
| 7432 | .27 | 74100 | .98 | 74185 | 2.20 |
| 7437 | .25 | 74105 | .44 | 74187 | 5.75 |
| 7438 | .25 | 74107 | .37 | 74190 | 1.15 |
| 7441 | .89 | 74121 | .38 | 74191 | 1.25 |
| 7440 | .15 | 74122 | .38 | 74192 | .95 |
| 7442 | .59 | 74123 | .65 | 74193 | .85 |
| 7443 | .73 | 74125 | .54 | 74194 | 1.25 |
| 7444 | .73 | 74126 | .58 | 74195 | .74 |
| 7445 | .73 | 74132 | .89 | 74196 | 1.25 |
| 7446 | .81 | 74141 | 1.04 | 74197 | .73 |
| 7447 | .79 | 74145 | 1.04 | 74198 | 1.73 |
| 7448 | .79 | 74150 | .97 | 74199 | 1.69 |
| 7450 | .17 | 74151 | .79 | 74200 | 5.45 |

SPECIALS

| | | | |
|--------|-------|--------|-------|
| 1101 | \$.69 | MAN 72 | \$.99 |
| 1103 | .69 | DL702 | .99 |
| 1702A | 5.95 | 556 | .99 |
| 5262 | .99 | 567 | 1.19 |
| 74S200 | 3.25 | 7493 | .35 |
| 82S23 | 2.75 | 7438 | .15 |
| 93410 | 1.39 | 9602 | .69 |

MV10B 6/\$1.00
MV50 16/\$1.00

2708 \$16.95
1 x 8K EROM

CENTRAL PROCESSING UNIT

8008 \$16.95

8080A \$16.95

2102 \$1.29
1024 bit static RAM 16 pin

KEYBOARD

20 KEYS
2 SLIDE SW
3" x 3"




99¢

SPECIAL DEVICES

| | | |
|---------|-----------------------------------|-------|
| 372 | AF-If Strip Detector DHP | 2.93 |
| 546 | AM Radio Receiver Subsystem DHP | .75 |
| 530 | FM Stereo Demodulator DHP | 2.98 |
| 1906 | Balanced Modulator-Demodulator | .99 |
| 1800 | Stereo Multiplexer DHP | 2.48 |
| ULN2208 | FM Gain Block 34db (typ) mDHP | 1.18 |
| ULN2209 | FM Gain Block 40db (typ) mDHP | 1.35 |
| 2513 | Character Generator 64x8x5 DHP-24 | 18.28 |
| 3846 | Translator Array DHP-14 | .73 |

MINIATURE SOLID STATE ELECTRONIC BUZZER

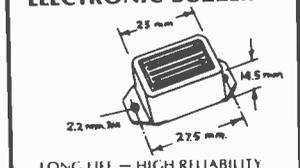

LONG LIFE — HIGH RELIABILITY
LOW CURRENT DRAIN
NO MOVING CONTACTS

78 dB min AT 1 FT. — 450 Hz 1A

EB-106 6V 15mA 4-9 VDC \$1.99
EB-112 12V 15mA 8-20 VDC 1.99

UART AY51013A \$6.95

CARBON FILM RESISTORS ±5%
ALL STANDARD VALUES

¼ OR ½ WATT

QTY. PRICE (each) PRICE (Minimum 10 per value)

0-10 \$1.0 ea
10-100 \$1.0 ea \$0.5 ea
100-1000 \$0.4 ea

METAL FILM RESISTORS ALL STANDARD VALUES ±1% ¼ WATT

QTY. PRICE PRICE PRICE (Minimum 10 per value) (Minimum 100 per value) (Minimum 1000 per value)

0 - 10 5.20
10 - 100 .20 5.15
100 - 1000 .10
1000 - .10 .09 .08

IC SOCKETS Solder Tail - low profile

| | | | | |
|--------|-----|--------|--------|----|
| 8 pin | 5 | 17 | 24 pin | 42 |
| 14 pin | .20 | 28 pin | .59 | |
| 16 pin | .22 | 40 pin | .69 | |
| 18 pin | .25 | | | |

MM 5330 \$6.95
4 ½ DIGIT DVM LOGIC

LH 0070 \$6.95
BCD BUFFERED REF.

MM 5616 \$1.25
QUAD BI-LATERAL SWITCH

MM5369 Divider mDIP 2.49
Crystal 3.58 MHz color TV 1.73
Crystal 2.010 MHz 3.95

Date sheets on request. Add 30¢ each if item is priced below \$1.00 each.

FREE CATALOG AVAILABLE ON REQUEST

Satisfaction guaranteed. Shipment will be made postage prepaid within 3 days from receipt of order. Payment may be made with personal check, charge card (include number and exp. date), or money order. Phone Orders — BofA and M/C card or C.O.D.

Add \$1.00 to cover shipping and handling if order is less than \$10.00. California residents add sales tax. Include shipping expense for orders shipped out of U.S. and Canada approx. 10% of order.

INTERNATIONAL ELECTRONICS UNLIMITED

VILLAGE SQUARE, P.O. BOX 449 DEPT P
CARMEL VALLEY, CA 93924 USA
PHONE (408) 659-3171

CIRCLE NO 24 ON FREE INFORMATION CARD

Electronics Classified

REGULAR CLASSIFIED: COMMERCIAL RATE: For firms or individuals offering commercial products or services, \$2.25 per word. Minimum order \$33.75.
EXPAND-AD CLASSIFIED RATE: \$3.35 per word. Minimum order \$50.25. Frequency discount; 5% for 6 months; *0% for 12 months paid in advance. **READER RATE:** For individuals with a personal item to buy or sell, \$1.35 per word. No minimum! **DISPLAY CLASSIFIED:** 1" by 1 column (2-1/4" wide), \$260.00. 2" by 1 column, \$520.00. 3" by 1 column, \$780.00. Advertiser to supply film positives. For frequency rates, please inquire.
GENERAL INFORMATION: Payment must accompany copy except when ads are placed by accredited advertising agencies. First word in all ads set in caps. All copy subject to publisher's approval. All advertisers using Post Office Boxes in their addresses **MUST** supply publisher with permanent address and telephone number before ad can be run. Advertisements will not be published which advertise or promote the use of devices for the surreptitious interception of communications. Ads are not acknowledged. They will appear in first issue to go to press after closing date. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st. Send order and remittance to **POPULAR ELECTRONICS**, One Park Avenue, New York, New York 10016. Attention: Hal Cymes

FOR SALE

FREE! Bargain Catalog—I.C.'s, LED's, readouts, fiber optics, calculators parts & kits, semiconductors, parts. Poly Paks, Box 942PE, Lynnfield, Mass. 01940.

GOVERNMENT and industrial surplus receivers, transmitters, snooper scopes, electronic parts. Picture Catalog 25 cents. Meshna, Nahant, Mass. 01908.

LOWEST Prices Electronic Parts. Confidential Catalog Free. KNAPP, 3174 8th Ave. S.W., Largo, Fla. 33540.

ELECTRONIC PARTS, semiconductors, kits. **FREE FLYER.** Large catalog \$1.00 deposit. **BIGELOW ELECTRONICS**, Bluffton, Ohio 45817.

RADIO—T.V. Tubes—36 cents each. Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

AMATEUR SCIENTISTS, Electronics Experimenters, Science Fair Students... Construction plans—Complete, including drawings, schematics, parts list with prices and sources... Robot Man — Psychedelic shows — Lasers — Emotion/Lie Detector — Touch Tone Dial — Quadraphonic Adapter — Transistorized Ignition — Burglar Alarm — Sound Meter... over 60 items. Send 50 cents coin (no stamps) for complete catalog. Technical Writers Group, Box 5994, University Station, Raleigh, N.C. 27607.

METERS—Surplus, new, used, panel or portable. Send for list. Hanchett, Box 5577, Riverside, CA 92507.

MECHANICAL, ELECTRONIC devices catalog 10 cents. Greatest Values — Lowest Prices. Fertik's, 5249 "D", Philadelphia, Pa. 19120.

SOUND SYNTHESIZER KITS—Surf \$12.95, Wind \$12.95, Wind Chimes \$17.95, Electronic Songbird \$6.95, Musical Accessories, many more. Catalog free. PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

BUGGED??? New locator finds them fast. Write, Clifton, 11500-L N.W. 7th Avenue, Miami, Florida 33168.

YOU WILL SAVE BIG MONEY! Surplus, Clearouts, Bankruptcy, Inventory, Deals. Catalog \$1 (redeemable). ETCOA Electronics, Box 741, Montreal, H3C 2V2. U.S. Inquiries.

HEAR POLICE / FIRE Dispatchers! Catalog shows exclusive directories of "confidential" channels, scanners. Send postage stamp. Communications, Box 56-PE, Comack, N.Y. 11725.

UNSCRAMBLERS: Fits any scanner or monitor, easily adjusts to all scrambled frequencies. Only 4" square \$29.95, fully guaranteed. Dealer inquiries welcomed. PDQ Electronics, Box 841, North Little Rock, Arkansas 72115.

RECONDITIONED Test Equipment. \$0.50 for catalog. Walter's Test Equipment, 2697 Nickel, San Pablo, CA 94806.

POLICE/Fire scanners, large stock scanner crystals, antennas. Also CBs. Harvey Park Radio, Box 19224, Denver, CO 80219.

TELETYPE EQUIPMENT for sale for beginners and experienced computer enthusiast. Teletype machines, parts, supplies. Catalogue \$1.00 to: ATLANTIC SALES, 3730 Nautilus Ave., Brooklyn, NY 11224. Tel: (212) 372-0349.

BREAKERLESS ELECTRONIC ignition: Auburn Spark-plugs, Synthetic Lubricants, Wheel Stabilizers. Information 26 cents. Anderson Engineering, Epsom, N.H. 03234.

WHOLESALE C.B., Scanners, Antennas, Catalog 25 cents. Crystals: Special cut, \$4.95, Monitor \$3.95. Send make, model, frequency. G. Enterprises, Box 461P, Clearfield, UT 84015.

COMPUTER HOBBYISTS—classified advertising newsletter. \$3.75/year. Free Sample. **ON-LINE**, 24695 Santa Cruz Hwy., Los Gatos, CA 95030.

NAME BRAND Digital/Analog Test Equipment. Discount prices. Free catalog. Salen Electronics, Box 82, Skokie, Illinois 60076.



YES, YOU CAN BUILD AN ELECTRONIC ORGAN

That has a PIPE ORGAN SOUND

With **DEVTRONIX** easy to build assemblies. Own the ultimate in organ design & sound at 1/3 the cost of commercial organs.

BROCHURE AND DEMO RECORD \$1.00



Dept. C
5872 Amapola Dr.
San Jose, CA 95129

BUILD AND SAVE. TELEPHONES, TELEVISION, DETECTIVE. BROADCAST Electronics. We sell construction plans with an Engineering Service. Speakerphones, Answering Machines, Carphones, Phonevision, Dialers, Color TV Converters, VTR, Games, \$25 TV Camera, Electron Microscope, Special Effects Generator, Time Base Corrector, Chroma Key, Engineering Courses in Telephone, Integrated Circuits, Detective Electronics. **PLUS MUCH MORE.** NEW Super Hobby Catalog PLUS year's subscription to Electronic News Letter, \$1.00. Don Britton Enterprises, 6200 Wilshire Blvd., Los Angeles, Calif. 90048.

SURPLUS COMPONENTS, Communication and test equipment. Illustrated catalog 25 cents. E. French, P.O. Box 249, Aurora, Illinois 60505.

TELEPHONES UNLIMITED, Equipment, Supplies, All types, Regular, Keyed, Modular. Catalog 50 cents. Box 1147E, San Diego, California 92112.

POWERFUL, ADJUSTABLE, REGULATED, THREE OUTPUT POWER SUPPLY and 900 easily removable parts in complete CARTRIVISION television recorder electronic assembly with documentation. Perfect for MICRO-PROCESSOR, IC, transistor, television, CB radio applications. \$24.95 total. Free brochure. BankAmericard, Master Charge. MADISON ELECTRONICS, INCORPORATED, 369, D55, Madison, Alabama 35758. SATISFACTION GUARANTEED.

CARBON FILM RESISTORS 1/4W, 1/2W - 1.7 cents each. FREE sample / specifications. Other components. COMPONENTS CENTER, Box 134P, New York, N.Y. 10038.

BUILD YOUR OWN SPEAKERS AND SAVE UP TO 50%

Send for our free fact-packed 44 page catalog manual and learn how to assemble your own multi element stereo speakers from scratch or from kits. Our catalog includes chapters on design construction x-overs enclosures midranges woofers tweeters and horns. Write us today!

SPEAKERLAB
Dept. PE-A, 5500 35th N E
Seattle, Washington 98105



PROFESSIONAL UNSCRAMBLERS — several models that fit any scanner. Free information. Capri Electronics, 8753T Windom, St. Louis, MO 63114.

UNSCRAMBLE CODED MESSAGES from Police, Fire and Medical Channels. Same day service. Satisfaction guaranteed. Don Nobles Electronics, Inc., Rt. 7, Box 265B, Hot Springs, Arkansas 71901. (501) 623-6027.

ANYTHING ELECTRONIC — we've got it. Catalog \$1.00. Razoo, Box 1224, Cupertino, Calif.

SEEKING ORIGINAL JAPANESE TRANSISTORS FOR CB REPAIR? Request: complete list. Compare 1 to 9 prices. 25C710, 59 cents; 25C517, \$3.95; 25C799, \$3.60; 25C1306, \$4.40; 25C1678, \$2.25; TA7205P, \$3.90; BA521, \$3.70, BA511, \$3.40. Fuji-Svea Enterprises, Dept. P, Box 40325, Cincinnati, OH 45240.

UNBELIEVABLE Goldmine of Electronic Schematics. Over 200, Useful, Novel, and Amazing Projects. Only \$9.99! Money Back Guarantee. Send for Free Project list. Space-tech, Box 182, Gillette, N.J. 07933.

USED TEST EQUIPMENT — Tektronix, HP, GR. Write: PTI, Box 8699, White Bear Lake, MN 55110. Phone: (612) 429-2975.

DIGITAL TACHOMETER 4-6-8 cylinder two digit display. Complete \$59.95. Cosmos Electronics, P.O. Box 33278, Seattle, WA 98133.

AMAZINGLY Low component prices! Ask for free flyer. Write: EEP, 11 Revere Place, Tappan, NY 10983.

WEATHER MAP RECORDERS: Copy Satellite Photographs, National-Local Weather Maps. Learn How! \$1.00. Atlantic Sales, 3730 Nautilus Ave., Brooklyn, N.Y. 11224. Tel: (212) 372-0349.

AUDIO EXPERIMENTERS, Serious Music Synthesizer Stuff: literature, kits, components, circuits and more. Send SASE for FREE INFO. CFR Associates, POB F, Newton, NH 03858.

UNSCRAMBLER SUPER SALE: Our famous Code-Breaker works with all scanners and tunes all scramble frequencies only \$29.95. COD's (501) 273-5340. Mail orders to: KRYSTAL KITS, BOX 445, BENTONVILLE, AR 72712.

PROMS PROGRAMMED — New low prices — 13 cents stamp brings information. Or send \$1 check for program cards, specs, PROM postage credit.

RBH Enterprises, Box 12344, Wichita, KS 67277.

PC BOARDS from your art. Send SASE for information. ASSEMBLY SYSTEMS, Box 221, Wadsworth, OH 44281.

CARTRIVISION OWNERS! Sony Color Tuner/Modulator plugs into Cartrivision. Record off channels not viewed. Record without TV on. Play into any TV without interlacing. \$250.00. (Specify channel 3/4). D.H.V., Inc., Box 12, Langhorne, Pennsylvania 19047.

WHY WORRY about leaving car lights on? **ALARM ALERTS**, with pulsing tone. \$11.75. **INFORMATION AVAILABLE.** CFL Enterprises, Box 415, Export, PA 15632.

PHONO preamplifier for headphones. Inexpensive, high performance. Plans \$3.00. Paul Meyer, 1-60 CalTech, Pasadena, CA 91126.

BUILD YOUR OWN TV CAMERA!
— Ideal for home & business —

THE ECONOMICAL ANSWER TO HOME MONITORING OF NURSERIES, ENTRANCES, DRIVEWAYS... BUSINESS and INDUSTRIAL SURVEILLANCE... TV... AMATEUR TV PLUS HUNDREDS OF OTHER APPLICATIONS.

MODEL: XT-1A, SERIES D - KIT FORM \$185; ASSEMBLED \$275. SOLID-STATE. WORKS ON ANY TV SET. OPTIONAL SOUND KIT \$28.95.

PHONE or WRITE for catalog. Dial 402-987-3771

1301 BROADWAY **ATV Research** DAKOTA CITY, NE. 68731

TURN THOSE Old (possibly broken?) transistor radios (AM or FM) into a variety of fascinating and useful devices. A potpourri of ideas. \$1.00 plus stamp. Retro, Box 143, Hatboro, PA 19040.

FREE CATALOG. Solar Cells, Nicads, Kits, Calculators, Digital Watch Modules, Ultrasonics, Strokes, LEDs, Transistors, IC's, Unique Components. Chaney's, Box 27038, Denver, Colorado 80227.

CIRCUIT BOARDS. Circuit Boards made to order from your designs and drawings. Ten-Tec equipment enclosures — Custom Digital Designing — Hickok Test Equipment — Consumer Wire and Cable products — Complete line of CB Products — Electronic Parts. All products sold below suggested retail prices. Write today for your free catalog. R-S Electronics, 1019 East Clay, Decatur, Illinois 62521.



CALCULATOR STAND

Are you using your hand calculator without a stand? Yes? Then you need a Cal Pal. Cal Pal allows you to operate your calculator with one hand and makes the calculator display easier to see. Order now. Just \$1.50 each postpaid. Utah residents please add sales tax.

Platform. Metric conversion table. Walnut woodgrain finish. Size: 3-1/4" X 5-1/2"

GEMAR SPECIALTIES
Dept. PE1, P.O. Box 706
Clearfield, Utah 84015


8K BYTE EPROM BOARD KIT (less 2708's), S-100: \$49.95; 2107A: \$4.50; 2513, 32wd, 981T F1FO: \$6.50; NE 526: 65 cents; NE553: \$2.10; Electroluminescent Panel, glows green, 115VAC: 95 cents; 20MHZ Crystal: \$4.50; 24PIN Socket: 40 cents; 8 position DIP Switch: \$2.25; coming soon (S-100 compatible): Phase Encoded Cassette Interface, Programmable Serial Port, Dual Recorder, Tarbell or K-C; 2708 Programmer. SASE for info. **ELECTRONIC DISCOUNT SALES**, 138 N 81st Street, Mesa, Arizona 85207.

TEN POUNDS fantastic variety capacitors, resistors, ICs, transistors, more: \$10. **FIFTEEN** Western Electric relays/two foot rack: \$9.75. Postpaid. Satisfaction guaranteed! **Computron**, Box 18160-E, Cleveland, OH 44118.

PC BOARD design-fabrication, also electronics, plexiglas and more, free list. **Chemlab**, Box 41472M, Chicago, Ill. 60641.

HARDCOPY. Attachments to convert Smith-Corona, IBM Selectric, and IBM Executive typewriters into micro-computer printers. Free Brochure. **Tim Stout Microcomputer Products**, Box 1573, Fremont, CA 94538.

HIGH VOLTAGE PROJECT MANUAL

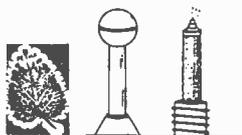

*Van de Graaff Gen.
*Kirlian Photography
*H.V. Piezoelectrics
*Tesla Coils, etc.

\$5.00 ppd.
THE ILSL COMPANY
2124 Kentucky
Lawrence, Ks. 66044

EXPERIMENTERS—Stop Buying Special Transformers—New Concept—Universal transformer alterable in minutes, any number of windings at any voltage (Max 50VA). Imagine winding SV at 5A plus two 12C at 1A and 15V at .4A today then changing tomorrow! Only \$16.50 — 30 day refund — other models available. ETS, 398 Sound Beach Ave., Old Greenwich, CT 06870.

X MARKS THE SPOT where you will find top quality parts. Free catalog. U.S., Canada. **Brand X**, Rt 3, Box 223, Ontario, OR 97914.

WEAK HEAD DEMAGNETIZERS—are generally ineffective. The Han-D-Mag readily demagnetizes ALL tape transport components. Write for "Demagnetizing Notes" & literature. **R. B. Annis Company**, 1105 N. Delaware, Indianapolis 46202.

MODULAR PHONE CORDS, Jacks, etc. Free catalog of telephones and supplies. **Flemco Sales**, 20272 37th Ave., N.E., Seattle, WA 98155.

PRINTED CIRCUIT BOARDS manufactured from artwork, prototypes and production quantities. **OMEGA ENTERPRISES**, Box 48239, Niles, Ill. 60648.

TV GAME LIQUIDATION—\$10. Some need adjustment. Sold as is with wiring diagram. No COD. California residents add 6% sales tax. Dept. TVCO, 1100 West Walnut, Compton, Calif. 90220.

SEE WHAT YOU WANT—(including home movies)—when you want—on your TV—with cartridge television! Free fascinating facts. Video, 5835 Herma, San Jose, California 95123.

MICROCOMPUTER SYSTEMS. Troubleshooting Techniques-Digital Gate Decode Chart, both \$5.00. Micro Info Assoc., Box 849, Castroville, Calif. 95012. Calif. residents add 6% tax.

QUALITY KITS, Test Equipment, Tools, Books, IC's, Components, Hobbyist Services, Newsletter, over 7000 schematics and plans. \$1 (refundable), brings big value packed catalog. Bargains! Tek-Devices, Box 19154A, Honolulu, HI 96817.

PROTECT YOUR CBI! Invisible antenna—installs minutes—no tools! Free information. Sensor, 87 Lambert, Central City, Pennsylvania 15926.

ALL TOP QUALITY BRANDS COMPONENTS. No down payment. 36 hour delivery anywhere in U.S. No-Lemon Guarantee. **Altec, Bose, Cerwin-Vega, DBX, Infinity, Lux, Micro-Acoustics, OHM, Phase-Linear, others.** International Hi-Fi Distributors, Moravia Center Industrial Park, Balto., Maryland 21206. Phone: (301) 488-9600.

HEAR WHISPERS 250 Yards Away! Amazing new project. Unique, Box 534-P, Nitro, W.V. 25143.

CB RADIOS, radar detectors, antennas, monitors, monitor crystals, crystalless monitors. Southland, Box 3591-B, Baytown, Texas 77520.

DIAGRAMS, Servicing Information, Radio-Television, \$3.50. Specify make, model. **Beitman**, 1760 Balsam, Highland Park, IL 60035.

500 MHZ COUNTER. 8 digit; two ppm TCXO time base kit, \$249.95. Immediate delivery. Call toll free: 1-800-828-7422. **Davis Electronics**, 636 Sheridan Dr., Tonawanda, N.Y. 14150.

SCIENCE SUPPLIES send 25 cents for catalog. **Schubel & Son**, Dept. C, Box 214848, Sacramento, CA 95821.

NRI OSCILLOSCOPE with probes, \$115.00; **ATR 20A Power Supply**, \$50.00; **NRI Tuned Signal Tracer**, \$40.00; **Heathkit 50W Audio Amplifier**, \$85.00; **GE 8-Track Recorder Deck**, \$95.00; **Player Deck**, \$29.00; **RC Tester**, \$22.95; **Transistor Tester**, \$25.00; **BSR Turntable with Cueing**, \$60.00; **Heathkit Stereo Cassette Recorder**, \$95.00 (plus \$1.80 postage). **Bill Sudderth, Rt. 1, Brassstown, North Carolina 28902.**

CBERS: Understand your antenna system. Optimize range, performance. \$1. **American Information**, Dept. 47, Box 740, Katy, TX 77450.

PLANS AND KITS

AMAZING ELECTRONIC PRODUCTS

LASERS SUPER POWERED, RIFLE, PISTOL, POCKET - SEE IN DARK - PYRO, TECHNICAL, DE-BUGGING - UNCRAMBLERS - GAWT TESLA - STUNWAND TV DISRUPTER - ENERGY PRODUCING, SCIENTIFIC DETECTION, ELECTRIFYING, CHEMICAL, ULTRASONIC, CB, AERO, AUTO AND MECH DEVICES. HUNDREDS MORE - ALL NEW PLUS INFO UNLTD PARTS SERVICE.

INFORMATION unlimited
CATALOG \$1 Box 626 Lord Jeffery PZ. • Amherst, N.H. 03031

FREE KIT Catalog contains Test and Experimenter's Equipment. **Dage Scientific Instruments**, Box 1054P, Livermore, CA 94550.

TIGER SST SIMPLI-KIT

FOR THE DO-IT-YOURSELFER NOW! a high quality CD Electronic Ignition System in kit form.

Contains all components and solder to build complete Solid-State Electronic CD Ignition System for your car. Assembly requires less than 3 hours.

- Increases MPG 15%
- Increases horsepower 15%
- Eliminates 4 of 5 tune-ups
- Instant starting, any weather
- Plugs and Points last 50,000 miles
- Dual system switch

Fits only 12 volt neg. ground... Only \$21.95 postpaid

7-7 Star Corporation
P.O. Box 1727 Grand Junction, Colorado 81501

POCKET COLOR/BAR GENERATOR kit, 16 patterns, \$49.95. Plans, \$4.95. **Workshop**, Box 393PF, Bethpage, New York 11714.

MIXERS — Preamps — Speakers, Top Quality Kits — Plans — Parts. Send 25 cents for catalog. **Audio Design & Engineering Co.**, P.O. Box 154, Lee, Mass. 01238. (413) 243-1333.

CONVERT TV TO NEW! 6 FT. WIDE SCREEN!

Easy Do-It-Yourself Kit

Project a giant 5'x6' picture onto wall or screen. B&W/Color. Kit contains detailed plans, Inst. and Precision Lens System. Only \$15.95 ppd., or write for Free illustrated details.

The Macrocoma Co., Dept. DB
Washington Crossing, PA 18977

THE "KING OF KITS". Artisan Organ Kits feature all new modular construction, with logic-controlled stops and RAM Preset Memory System. Write for brochure to: **AOK Manufacturing, Inc.**, P.O. Box 445, Kenmore, WA 98028.

LASER WELDING PLANS—\$9.00; Five Laser Plans—\$8.00; catalog—\$2.00. **Solaser**, PE1077, Box 1005, Claremont, Calif. 91711.

NEGATIVE ION Generator, (dual-stage). Detailed Construction Plans, \$10.00. **Golden Enterprises**, Box 1282-PE, Glendale, Arizona 85311.

BURGLAR ALARMS

Burglar . Smoke Fire Alarm Catalog

• Billions of dollars lost annually due to lack of protective warning alarms.

FREE CATALOG Shows you how to protect your home, business and person. Wholesale prices. Do-it-yourself. Free engineering service.

Burdex Security Co.

Box 82802 PE 107 Lincoln, Ne. 68501

C.B.'s BECOME BURGLAR ALARMS with Modex Alarm Circuit. Plans \$1.99. **Modex**, Box 887, Middletown, Conn. 06457.

DIALING UNIT automatically calls police. \$29.95. Free security equipment catalog. **S&S Systems**, 5619-C St. John, Kansas City, MO 64123. (816) 483-4612.

WANTED

GOLD, Silver, Platinum, Mercury wanted. Highest prices paid by refinery. Ores assayed. Free circular. **Mercury Terminal**, Norwood, MA 02062.

TUBES

RADIO & T.V. Tubes—36 cents each. Send for free Catalog. **Cornell**, 4213 University, San Diego, Calif. 92105.

TUBES receiving, factory boxed, low prices, free price list. **Transleteronic, Inc.**, 1365 39th Street, Brooklyn, N.Y. 11218A, Telephone: 212-633-2800.

TUBES: "Oldies", Latest, Supplies, components, schematics. Catalog Free (stamp appreciated). **Steinmetz**, 7519-PE Maplewood, Hammond, Ind. 46324.

TAPE AND RECORDERS

RENT 4-Track open reel tapes—free brochure. Stereo-Parli, P.O. Box 7, Fulton, CA 95401.

8-TRACK and CASSETTE BELTS — money back guarantee. Long wearing. Free Catalog — \$3 minimum order. **PRB Corp.**, Box 176, Whitewater, Wisconsin 53190.

VIDEO TAPE, Brand new. 1/2 inch, \$10.50/hour. Free information. **Oregon Magnetics**, P.O. Box 13374P, Portland, OR 97213.

OLDTIME RADIO PROGRAMS make special Christmas gifts. Free Catalogue. **Carl R. Froelich**, Route One, New Freedom, Pennsylvania 17348.

RECORDS—TAPES! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **Discount Music Club**, 650 Main St., Dept 5-1077, New Rochelle, New York, N.Y. 10801.

GOVERNMENT SURPLUS

MANUALS for Govt Surplus radios, test sets, scopes. List 50 cents (coin). **Books**, 7218 Roanne Drive, Washington, D.C. 20021.

GOVERNMENT SURPLUS. Buy in your Area. How, where. Send \$2.00. Surplus, 30177-PE Headquarters Building, Washington, D.C. 20014.

JEEPS, TRUCKS, Typically from \$52.40... Automobiles, Boats, Motorcycles, Airplanes, Oscilloscopes, Tools, Clothing, Sports, Camping, Photographic, Electronics Equipment... 200,000 Bid Bargains Nationwide Direct from Government... Low as 2 cents on Dollar! Surplus Catalog and Sales Directory \$1.00 (refundable). **National Surplus Center**, 240 Eastcass-PEL, Joliet, Illinois 60432.

POPULAR ELECTRONICS

PERSONALS

MAKE FRIENDS WORLDWIDE through international correspondence. Illustrated brochure free. Hermes-Verlag, Box 110660/Z, D-1000 Berlin 11, Germany.

INVENTIONS WANTED

INVENTORS: Manufacturers Need New Products. Free "Recommended Procedure," by a creative fee-based invention service company. Washington Inventors Service, 422-T Washington Building, Washington, D. C. 20005.

INVENTORS

RECOGNITION...FINANCIAL REWARD...OR CREDIT FOR "INVENTING IT FIRST" MAY BE YOURS!

If you have an idea for a new product, or a way to make an old product better, contact us, "the idea people" We'll develop your idea, introduce it to industry, negotiate for cash sale or royalty licensing. Write now without cost or obligation for free information. Fees are charged only for contracted services. So send for your FREE "Inventor's Kit." It has important Marketing Information, a special "Invention Record Form" and a Directory of 1001 Corporations Seeking New Products.

RAYMOND LEE ORGANIZATION
230 Park Avenue North, New York, NY 10017

At no cost or obligation, please rush my FREE "Inventor's Kit No. A-112"

Name _____
Address _____
City _____ State _____ Zip _____
Phone No _____ Area Code _____

FREE PAMPHLET: "Tips on Marketing Your Invention", from an experienced fee-based invention service company. Write: United States Inventors Service Company, Dept. T, 1435 G Street NW, Washington DC 20005.

INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING at home all makes including transistor. Experimental kit—trouble-shooting. Accredited NHSC, Free Booklet. NILES BRYANT SCHOOL, 3631 Stockton, Dept. A, Sacramento, Calif. 95820.

SCORE high on F.C.C. Exams... Over 300 questions and answers. Covers 3rd, 2nd, 1st and even Radar. Third and Second Test, \$14.50; First Class Test, \$15.00. All tests, \$26.50. R.E.I., Inc., Box 806, Sarasota, Fla. 33577.

UNIVERSITY DEGREES BY MAIL! Bachelors, Masters, Ph.D.'s. Free revealing details. Counseling, Box 317-PE10, Tustin, California 92680.

SELF-STUDY CB RADIO REPAIR COURSE, THERE'S MONEY TO BE MADE REPAIRING CB RADIOS. This easy-to-learn course can prepare you for a career in electronics enabling you to earn as much as \$16.00 an hour in your spare time. For more information write: CB RADIO REPAIR COURSE, Dept. PE107, 531 N. Ann Arbor, Oklahoma City, Okla. 73127.

LEARN WHILE ASLEEP! HYPNOTIZE! Astonishing details, strange catalog free! Autosuggestion, Box 24-ZD, Olympia, Washington 98507.

GRANTHAM'S FCC LICENSE STUDY GUIDE — 377 pages, 1465 questions with answers/discussions — covering third, second, first radiotelephone examinations. \$13.45 postpaid. GSE, P.O. Box 25992, Los Angeles, California 90025.

INTENSIVE 5 week course for Broadcast Engineers. FCC First Class license. Student rooms at the school. Radio Engineering Inc., 61 N. Pineapple Ave., Sarasota, FL 33577 and 2402 Tidewater Trail, Fredericksburg, VA 22401.

HIGHLY EFFECTIVE Degree Program in Electronics Engineering. Advance rapidly! Our 31st Year. Free literature. Cook's Institute, Box 20345, Jackson, Miss. 39209.

1977 TESTS-ANSWERS for FCC First Class License. Plus "Self-Study Ability Test." Proven! \$9.95. Moneyback Guarantee. "FREE" BROCHURE. Command, Box 26348-P, San Francisco 94126.

OCTOBER 1977

GET your Commercial FCC License. New Exams by author of successful published workbooks of FCC Practice Tests. 500 Questions Second Class, \$11.95; 200 First Class, \$7.95; 100 Radar, \$4.95; Postpaid. Save, all three \$19.95. Complete mathematical solutions. Free counselling service. Victor Veley, P.O. Box 14, La Verne, Calif. 91750.

MICROCOMPUTERS—Learn microcomputer and micro-processing software and hardware fundamentals for hobby or career expansion. Send \$5.95 per book to: Computer Concepts, P.O. Box 641, Dept. 23A, Hackensack, N.J. 07602.

COMPUTER PROGRAMMING (BASIC and FORTRAN), Mathematics, Electronics, FCC license. Free information: Intermountain Technical Institute, Box 258, Jerome, Idaho 83338.

MUSICAL INSTRUMENTS

UP TO 60% DISCOUNT. Name brand instruments catalog. Freeport Music, 114 G. Mahan St., W. Babylon, N.Y. 11704.

BUSINESS OPPORTUNITIES

I MADE \$40,000.00 Year by Mailorder! Helped others make money! Free Proof. Torrey, Box 318-NN, Ypsilanti, Michigan 48197.

FREE CATALOGS. Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

MAILORDER MILLIONAIRE helps beginners make \$500 weekly. Free report reveals secret plan! Executive (1K10), 333 North Michigan, Chicago 60601.

GET RICH with: Secret Law that smashes debts and brings you \$500 to \$5 Million cash. Free report! Credit 4K10, 333 North Michigan, Chicago 60601.

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Postcard brings facts about this unusual opportunity. Write today! Barta-AL, Box 248, Walnut Creek, CA 94597.

NEW LUXURY Car Without Cost. Free Details! Codex-ZZ, Box 6073, Toledo, Ohio 43614.

MECHANICALLY INCLINED individuals desiring ownership of Small Electronics Manufacturing Business — without investment. Write: Marks, 92-K9 Brighton 11th, Brooklyn, New York 11235.

\$500 PER DAY POSSIBLE. New C.B. related business. Send 25 cents. P.A. Schubert Company, P.O. Box 187, Howell, Mich. 48843.

\$500.00 WEEKLY! IMMEDIATE Home income stuffing envelopes. FREE Supplies! Guaranteed! Send 25 cents, Stamp. ALCO, B19110-PE0, Las Vegas, NV 89119.

CONSULTING BUSINESS: How to start, operate, promote. \$1,000 weekly. Get rich giving advice! Free Details... write: Hamilton, Dept. PE-10, Box 88043, Indianapolis, IN 46208.

STUFF ENVELOPES, \$250 per 1,000. Free Supplies, send stamped, self-addressed envelope: Midwest Data Systems, P.O. Box 3684, Peoria, IL 61614.

EARN \$1,000 MONTHLY

Work one hour daily in the privacy of your home and in your spare time. "GUARANTEED," "FREE DETAILS" write: UNICORN, ZE 7350 NUGGET COURT, COLORADO SPRINGS, COLO. 80911.

HOME ENTERTAINMENT FILMS

SHOP EARLY FOR CHRISTMAS! Order Columbia, Universal & Sportlite Super 8 sound & silent action films. "Wheels Keep Rolling" 1978 Indy 500 film. Super 8 color 200' reel only \$18.95 ea plus 75 cents shipping. Make selections from Columbia catalog 85 cents; Universal 8 catalog 75 cents; Sportlite forms 35 cents. SPORTLITE Elect-10, 20 N. Wacker Dr., Chicago, IL 60606.

REAL ESTATE

BIG...FREE...FALL CATALOG! Over 2,500 top values coast to coast! UNITED FARM AGENCY, 612-EP, West 47th, Kansas City, MO 64112.

EMPLOYMENT OPPORTUNITIES

ELECTRONICS/AVIONICS EMPLOYMENT OPPORTUNITIES. Report on jobs now open. Details FREE. Aviation Employment Information Service, Box 240E, Northport, New York 11768.

OVERSEAS JOBS! All Occupations! Complete Details. Where and How to Apply. Latest Company lists. Resume Tips. \$2.00. Information Services, P.O. Box 3345P, Cocoa, Florida 32922.

DO-IT-YOURSELF

MODULAR TELEPHONES now available. Sets and components, compatible with Western Electric concept. Catalog 50 cents. Box 1147W, San Diego, California 92112.

TAPE-SLIDE SYNCHRONIZER, lap-dissolve, multiprojector audiovisual plans \$8.50. Free Catalog. Millers, 1896 Maywood, South Euclid, OH 44121.

MAKE PROFESSIONAL QUALITY PC boards with silk-screen techniques. Complete information, \$4.95 postpaid. TerraTronic Research, Box 513SP, Quincy, Ill. 62301.

REPAIRS AND SERVICES

SERVICEMEN — Cleaners, Lubricants, Adhesives for all electronic repairs — Write for FREE catalog. Projector-Recorder Belt Corp., Box 176, Whitewater, WI 53190. (414) 473-2151.

HIGH FIDELITY

DIAMOND NEEDLES and Stereo Cartridges at Discount prices for Shure, Pickering, Stanton, Empire, Grado and ADC. Send for free catalog. LYLE CARTRIDGES, Dept. P, Box 69, Kensington Station, Brooklyn, New York 11218.

RUBBER STAMPS

RUBBER STAMPS, BUSINESS CARDS. Many new products. Catalog, Jackson's, Dept. K, Brownsville Rd., Mt. Vernon, Ill. 62864.

BOOKS AND MAGAZINES

FREE book prophet Elijah coming before Christ. Wonderful bible evidence. Megiddo Mission, Dept. 64, 481 Thurston Rd., Rochester, N.Y. 14619.

POPULAR ELECTRONICS INDEXES For 1976 now available. Prepared in cooperation with the Editors of "P/E," this index contains hundreds of references to product tests, construction projects, circuit tips and theory and is an essential companion to your magazine collection. 1976 Edition, \$1.50 per copy. All editions from 1972 onward still available at the same price. Add \$.25 per order for postage and handling, \$.50 per copy, foreign orders. INDEX, Box 2228, Falls Church, Va. 22042.

TECHNICAL MANUALS — Ameco, Arri, Cowan, Gilfer, Rider, RCA Radio Callbook, Sams, Tab, T.I. Postage 35 cents bk, ppd. Five. Madison Electronics, 1508 McKinney, Houston, Texas 77002.

HYPNOTISM

SLEEP learning. Hypnotic method. 92% effective. Details free. ASR Foundation, Box 23429EG, Fort Lauderdale, Florida 33307.

FREE Hypnotism. Self-Hypnosis. Sleep Learning Catalog! Drawer H400, Ruidoso, New Mexico 88345.

AMAZING self-hypnosis record releases fantastic mental power. Instant results! Free trial. Write: Forum (AA10), 333 North Michigan, Chicago 60601.

MISCELLANEOUS


CORVAIR PARTS—catalog of 3,000 Corvair parts — \$2.25. Clark's Corvair Parts, Shelburne, Mass. 01370. (413) 625-9092.

DELICIOUS! Chicken Vegetable Soup recipe \$1.50 and SASE. RMSSR ZD, P.O. Box 34052, Phoenix, Arizona 85067.

HOW TO CHOOSE A PROJECTION TV SCREEN (AND WHY TO CHOOSE OURS)

The screen you select for your projection TV shouldn't be just an afterthought. It can be one of the most critical components in your system.

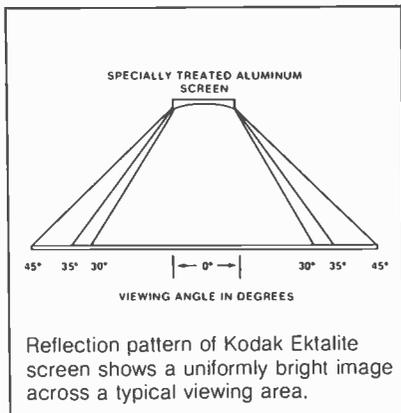Since most lenses gather less than 10% of the light from the



picture tube, what your audience sees (or doesn't see) depends largely on the efficiency of the screen.

The two most important criteria are: How bright is the reflected image in the actual viewing area? And how well is ambient light deflected?


The Kodak Ektalite screen. Brighter, better image for your audience.

The Ektalite screen combines a specially treated aluminum foil surface and a curved shape. These two features work together to "focus" a bright image into a viewing area roughly 60 degrees wide by 30 degrees high.

The level of reflectivity is 10 times that of a conventional matte screen. And because ambient light originating outside the viewing area is rejected, the Ektalite screen can be used in normal room light.

Blacker blacks mean brighter colors.

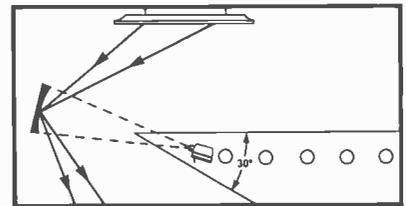Images on an Ektalite screen appear richer, more exciting than on conventional screens. That's because the screen is dark except for the light projected onto it. This background "blackness" brings out color saturation and contrast.



The Ektalite screen deflects ambient light away from the line of vision of the audience, so screen image is bright and clear even with room lights on.

Images are crisp and bright—not washed out by stray light. You get more impact from your picture.

Send the coupon for full details on the Kodak Ektalite screen, plus a list of AV dealers.



Eastman Kodak Company
Dept. A0030
Rochester, N.Y. 14650

Please send complete technical details on the Kodak Ektalite screen, plus a list of AV dealers.

Name _____


Title _____

Organization _____

Address _____

City _____

State _____ Zip _____

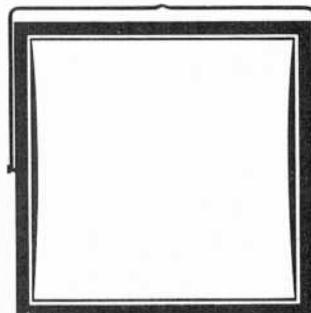

Kodak Ektalite projection screen

ATTENTION DEALERS:

Announcing

Jim-pak[®]

electronic components

One-Stop Component Center

★ Over 200 quality items including integrated circuits, resistors, diodes, transistors, capacitors, connectors, switches, sockets, LEDs and Data Books covering all JIM-PAK[®] items.

- ★ Immediate delivery on all orders
- ★ Store display racks available
- ★ Stock rotation and return policy
- ★ Direct mail program available from list of active electronic buyers in dealers' area.
- ★ National advertising campaign in leading electronics magazines to include list of qualifying dealers
- ★ Nationally known manufacturers' products at prices every dealer can afford
- ★ Guaranteed products
- ★ Standard industry part numbers



A component line of proven sellers developed for the independent dealer. Ideal for computer shops, school stores, electronic dealers, hobby shops, or any location where there is a potential market for electronic sales.

A product line which supplies most of your needs from one distributor with a reputation for fast and efficient service. Attractive and compact display racks make initial installation of the JIM-PAK[®] line easy.

Your customers deserve the best. Now you can profitably retail name brand components at competitive prices. Be the first in your area to announce and sell the JIM-PAK[®] line. Write or call today.




FOR MORE INFORMATION AND PRICING SCHEDULE CONTACT:

, a division of James Electronics, 1021 Howard Avenue, San Carlos, California 94070, (415) 592-8097

CIRCLE NO 28 ON FREE INFORMATION CARD

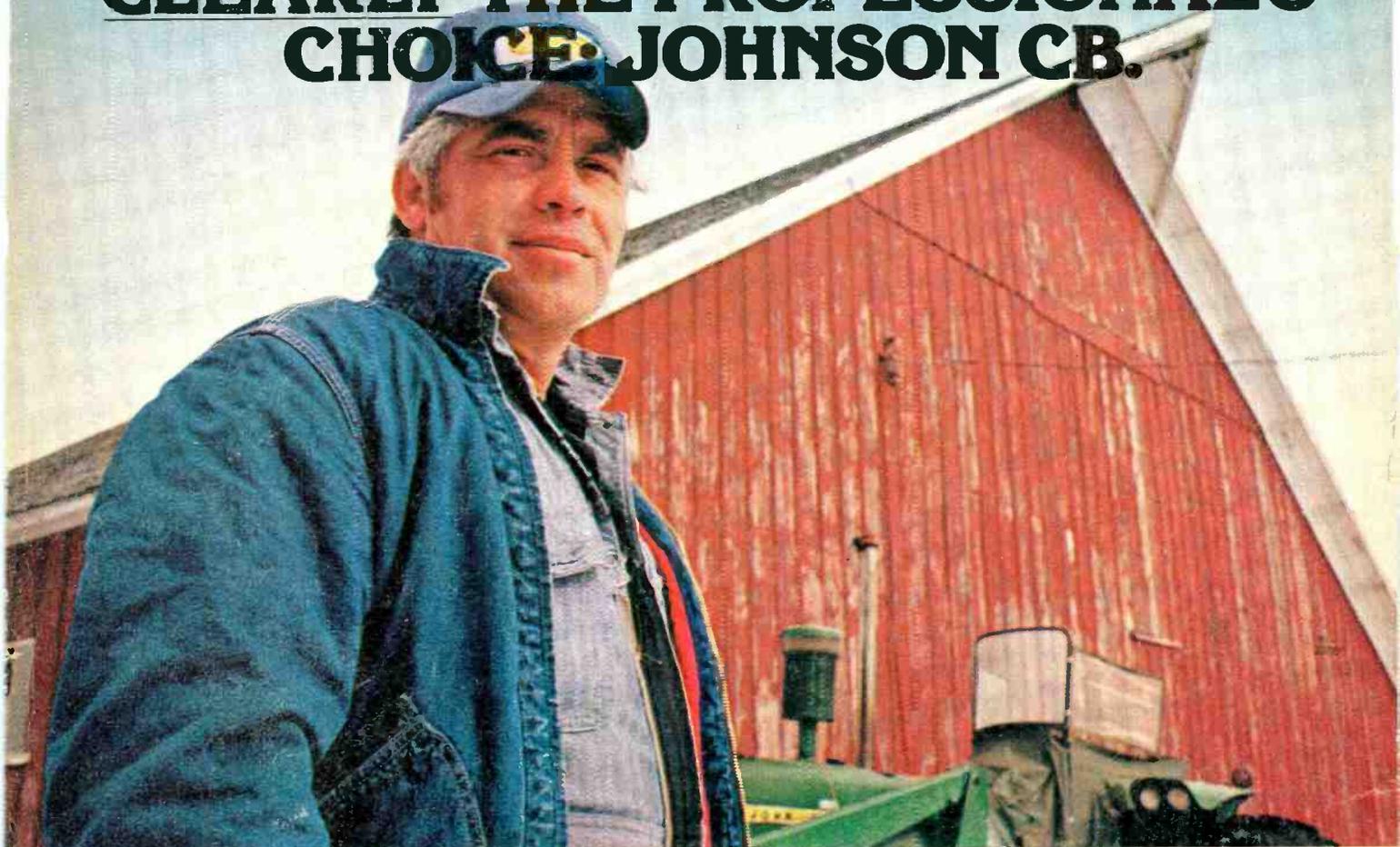CLEARLY THE PROFESSIONAL'S CHOICE. JOHNSON CB.



Two to one over the next leading brand. That's how American farmers rate Johnson CB.

CB radio is becoming increasingly important on American farms to help save time, save fuel and to increase efficiency and productivity.

Performance and reliability mean a lot to these professionals.

The CB radio farmers use? Johnson... In a recent survey, Johnson was named more than twice as often as the next leading brand when farmers were asked what make of CB radio they owned.*

And for 1977, we've got a whole new line of 40-channel CBs for farmers, for you and for everybody who's serious about quality. CBs with more features and more value per dollar than ever before.

Exclusive features like our

X300D single chip frequency synthesis circuitry for greater accuracy and reliability.

And our exclusive Tapered Automatic Noise Limiter that adjusts itself to changing noise conditions. Or the brightest idea in S/Rf meters yet—Johnson's Power-Bar LED meter that can be read accurately at a glance from any angle. Johnson's electronic speech compression gives maximum transmit range and Johnson's voice-tailored audio circuitry delivers quieter, better reception.

Of course, you still get Johnson's solid, made-in-America quality and reliability. Plus the best warranty/service protection in CB—one-year on parts and labor with more than 1,000 Authorized Johnson CB Service Centers nationwide.

Johnson CB. Clearly the professional's choice.

A copy of the Farmer Survey is available upon request.



JOHNSON

PERSONAL COMMUNICATIONS DIVISION
E. F. JOHNSON COMPANY, CLEAR LAKE, IOWA 50428
In Canada: A. C. Simmonds & Sons, Ltd.

CIRCLE NO. 33 ON FREE INFORMATION CARD

