Wireless World

JUNE 1954 TWO SHILLINGS


RADIO, TELEVISION AND ELECTRONICS

WIRELESS WORLD

RANGE OF BICC T/V DOWNLEADS								
TYPE OF CABLE	LIST No.	NOMINAL IMPEDANCE ohms	SIZE OF INNER CONDUCTOR inch	NOMINAL OVERALL DIAMETER	NOMINAL ATTENUATION at 50 Mc/s db/100 ft.			
	STANDA	RD CABLES	FOR SERVICE	AREAS				
Coaxial	T.3008	55	7/.0076	.159	5.1			
	T.3158	- 75	1/.022	.202	3.1			
1	T.3159	75	7/.0076	.202	3.3			
Unscreened Twin	T.3066	80	1/.936	.100 x .160	3.0			
Screened Twin	T.3121	75	ī/.029	.228 5.				
1.1.1								
LOW-ATTENUATION CABLES FOR FRINGE AREAS								
Coaxial Solid	T.2134	55	1/.048	.264	2.0			
Coaxial Semi- airspaced Screened Twin	T.3116	75	I/.048	.290	1.55			
(filled)	T.3135	75	I/.048	.297	2.7			

AVAILABLE IN STANDARD LENGTHS ON 100 yd. REELS

there is a

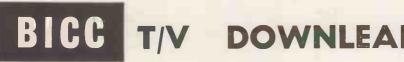

for every installation

The table above lists the comprehensive range of **BICC** Television Downleads.

Further information is given in our current Publication No. 244 which is available on request.

BRITISH INSULATED CALLENDER'S CABLES LIMITED 21, Bloomsbury Street, London, W.C.1

JUNE, 1954



Wipeless World RADIO, TELEVISION

AND ELECTRONICS

44th YEAR OF PUBLICATION

Managing Editor : HUGH S. POCOCK, M.I.E.E. Editor : H. F. SMITH

JUNE 1954

In This Issue

EDITORIAL COMMENT		255
COLOUR TELEVISION ON 405 LINES		256
WORLD OF WIRELESS		258
FRENCH TELEVISION PROGRESS. By Charles Bovill		261
MAGNETIC RECORDING TAPE. By H. G. M. Spratt		264
BOOKS RECEIVED		267
FURTHER NOTES ON THE MIDGET SENSITIVE T.I	R.F.	
RECEIVER. By J. L. Osbourne		268
RADIO RECEIVER MEASUREMENTS		271
VALVES FOR BANDS III, IV AND V. By D. N. Corfield	5	272
PIEZOELECTRIC CRYSTALS. By S. Kelly		275
LETTERS TO THE EDITOR		281
NEW LICENCE REGULATIONS		283
THE DIODE RECTIFIER IN VALVE VOLTMETERS-1.	By	
M. G. Scroggie		284
FRENCH COMPONENTS SHOW, 1954. By E. Aisberg	• • •	287
CAVITY RESONATORS. By " Cathode Ray "		290
SHORT-WAVE CONDITIONS		294
PHYSICAL SOCIETY'S EXHIBITION		295
TEST AND MEASURING GEAR	• •	299
PLOTTING AIRCRAFT POSITIONS		303
RANDOM RADIATIONS. By " Diallist "		
UNBIASED. By "Free Grid "		306

 PUBLISHED MONTHLY (last Monday of preceding month)
 by
 ILIFFE & SONS LTD., Dorset House. Stamford

 Street, London, S.E.1.
 Telephone : Waterloo 3333 (60 lines).
 Telegrams : "Ethaworld, Sedist, London." Annual

 Subscription : Home and Overseas, £1 7s. 0d. U.S.A. \$4.50.
 Canada \$4.00.
 BRANCH OFFICES: Birmingham : King Edward

 House, New Street, 2.
 Coventry : 8-10
 Corporation Street.
 Glasgow : 26B
 Renfield Street, C.2.
 Manchester : 260
 Deansgate, 3.

D



VALVES, TUBES & CIRCUITS

18. VALVES FOR A.C. MAINS-OPERATED F.M./A.M. RECEIVERS

Following the decision to adopt frequency modulation for the British V.H.F. sound broadcasts in Band II (87.5 to 100 Mc/s), attention will be focussed on the design and construction of receivers which, whilst designed for F.M. reception, can also operate on the existing A.M. wavebands. The accompanying table shows how six recently developed Mullard valves may be arranged in a receiver for F.M./A.M. operation with an A.C. mains supply. Each of these valves has a B9A (noval) base and a heater voltage of 6.3 V. By the use of suitable switching arrangements it is possible for some of the valves to perform different functions during F.M. and A.M. reception.

	FUNCTION				
VALVE TYPE	F.M. OPERATION	A.M. OPERATION			
ECC85 Triode I Triode 2	R.F. amplifier Additive mixer	_			
ECH8I Heptode Triode	lst I.F. amplifier —	Mixer Local oscillator			
EF85	2nd I.F. amplifier	I.F. amplifier			
Diode I EABC80 Diodes 2 & 3 Triode	Ratio detector A.F. amplifier	Detector A.F. amplifier			
EL84	Power amplifier	Power amplifier			
EZ80	Rectifier	Rectifier			

ECC85 Double Trlode. Consisting of two identical triodes with separate cathodes, the ECC85 is designed for use in the "front-end" stage of an F.M. receiver at V.H.F. One section is used as a self-oscillating additive mixer and this is preceded by the other section which functions as a low-noise R.F. amplifier. The presence of the R.F. amplifier ensures that oscillator radiation from the aerial is low. With the ECC85, which has been designed with extensive screening between the two sections, the radiation is reduced to an acceptable amount, being less than with earlier double triodes. The use of a triode as R.F. amplifier has the added advantage of a lower noise level combined with higher slope than would be obtained with multi-grid valves.

ECH81 Triode Heptode. For A.M. reception the ECH81 can be used in the conventional type of triode-heptode frequency changer input circuit. The two sections have entirely separate electrode structures thus enabling the heptode section to provide the first stage of I.F. amplification with F.M. operation.

EF85 Variable-mu High-slope Pentode. This valve can be used as an I.F. amplifier for both F.M. and A.M. reception since it combines the high slope required for amplification of the F.M. signals with the variable-mu characteristics

desirable for A.M. operation in conjunction with the ECH81 as frequency changer.

EABC80 Triple Dlode Triode. One of the three diodes in the EABC80 has a separate cathode, the remaining two diodes and the triode sharing the other cathode. With this construction it is possible to use this valve in a ratio detector circuit in which two diodes with separate cathode are required. In addition these two diodes have been designed with low internal impedances (approx. 200 Ω) whose ratio never exceeds 1.5. The third diode is used in A.M. reception as a conventional detector and generator of A.G.C. voltages. The triode section of this valve is suitable for use as an A.F. amplifier, its characteristics being similar to the triode section of the Mullard EBC41.

EL84 Output Pentode. This output pentode, which is already familiar to amplifier designers, has a maximum anode dissipation of 12W. It has been specially designed to provide **the** low distortion required for high-fidelity applications such as V.H.F. sound broadcasting using F.M.

EZ80 Full-wave Rectifier. The EZ80, an indirectly-heated full wave rectifier, can supply a maximum output current of 90 mA. It is therefore suitable for use in a combined F.M./A.M. receiver using the range of valves listed above.

Reprints of this advertisement, together with additional data may be obtained free of charge from the address below.

MULLARD LTD., Technical Service Department, Century House, Shaftesbury Avenue, W.C.2



JUNE 1954

New Licences

E have long thought the broadcast sound and vision receiving licences issued by the Post Office to be queer documents. Nearly 10 years ago, we protested that some of the provisions of the sound licence were unduly restrictive. As a result a few changes were made, but fewer than we would have liked. There still remain clauses that must be a source of minor annoyance to the very few people who trouble to read the licences, and, at the same time, have a dislike of unwarranted bureaucratic "bossiness."

For example, on what grounds does the Postmaster-General forbid a direct connection between mains and aerial? A deplorable practice, admittedly, but surely a matter for the P.M.G.'s colleague the Minister of Health, who may have the expense of treating transgressors for shock under the National Health Service. Perhaps, however, this clause is intended rather as a recommendation than a veto; the warning that the licence does not confer authority to infringe copyright is rather more forthright but surely equally irrelevant. A gun licence does not warn the holder against using the weapon for, say, felonious wounding.

Several of the apparently irrelevant clauses of the broadcast licences are perpetuated in the large crop of new radio licences recently issued by the Post-master-General which are summarized elsewhere in this issue. No doubt these relatively harmless things are done in drafting by over-cautious officials whose main object is to protect their department from possible litigation. There are also several apparent anomalies, particularly in the matter of charges, between one class of licence and another. Why, for instance, should a single ambulance vehicle, equipped with radio-telephony for expediting its journeys of mercy, pay $\pounds 3$ a year, while a whole police communication network, with an unlimited number of stations, pays only $\pounds 2$?

The charge for one new type of licence seems altogether excessive, and will, we hope, be revised. This is the Hotels licence, for which it is apparently proposed to charge, for sound broadcast reception, a fee of £1, plus £1 a year for each room installed. For television the fee is £3 plus £3. We should imagine that only the luxury hotel could afford to pay these charges.

Shared Television Masts

SO far as competitive television is concerned, there is only one point on which the political parties are agreed: this is that the aerials of the Independent Television Authority, if it comes into existence, should be carried on the masts of the B.B.C.'s present stations. What the B.B.C. itself thinks of this proposal, incidentally, is not stated.

At first sight the idea seems technically to have everything in its favour. The existing B.B.C. main stations were planned to give the most economical coverage of the densely populated areas, and it is doubtful if better sites could be chosen. For the viewer there is a distinct advantage in having both the B.B.C. and the I.T.A. transmissions radiated from the same point. This would allow combination receiving aerials to be used, pointed in the same direction. With separate transmitter sites, most viewers would have to erect more clumsy, unsightly and costly aerials. Where neighbours share a chimney stack, an impossible situation might arise.

All the B.B.C. "standard" stations have Band II slot aerials, for future use in sound broadcasting, occupying the top 100ft of the mast. It should be technically possible to interlace a high-gain Band III television aerial with the slot system, but, if this proved unexpectedly difficult, the portion of the mast immediately below the slotted section might be used without excessive loss of range.

On the masts of the five lower-power B.B.C. stations to be erected shortly provision has been made for Band III aerials, and there seems no *technical* reason why they should not be used by the I.T.A. If enough Band III channels could be freed for both B.B.C. and I.T.A. programmes, the two services could be "diplexed" to a common aerial.

VOL. 60 No. 6

Colour Television on 405 Lines

Demonstration of Compatible Systems for British Standards

HEN the Television Advisory Committee issued their first report in 1953 they suggested that a compatible colour television system for Britain could be achieved by an adaptation of the American N.T.S.C. system,* with the colour signal transmitted outside the normal video band, either in an adjacent clear space or in part of any already-occupied adjacent channel. This method, of course, requires more bandwidth than the normal N.T.S.C. system, where the colour signal is transmitted within the same band as the monochrome signal. It has the great advantage, however, that the colour signal cannot interfere with the monochrome signal and produce a pattern of crawling white dots on the screens of black-and-white receivers. In this respect it is more compatible than the normal N.T.S.C. system-although the T.A.C.'s interpretation of compatibility suggests that the colour signal should be kept within the same band as the monochrome signal. The possible application of this "adjacent channel" system to British television has already been discussed in Wireless World.+

The idea has now been tried out on an experimental

* Wireless World, Nov. 1953, p. 524 † Wireless World, Dec. 1953, p. 599

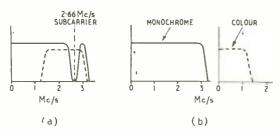


Fig. 1. Frequency characteristics of (a) N.T.S.C.-type signal adapted to British standards and (b) "adjacent channel" signal. The dip in the monochrome characteristic at (a) represents filtering to remove colour-signal interference.

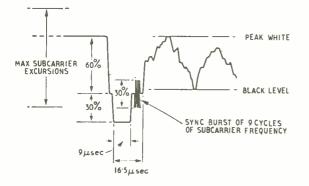


Fig. 2. Showing how the standard 405-iine waveform is modified to carry the extra colour information in the N.T.S.C.-type system using a sub-carrier.

basis by Marconi's, and recently in London they gave a demonstration of it on a 405-line closed-circuit television system. At the same time a demonstration was given of a straightforward adaptation of the normal N.T.S.C. system to British standards, and it should be mentioned here that Marconi's were really presenting the two systems for comparison purposes : they were not advocating either one or the other. Comparisons could be made between the resultant pictures as they appeared on colour monitors and on ordinary black-and-white commercial receivers. It was also possible to see the effects of different bandwidths in the channels conveying the colour information. The subjects televised were live scenes, both indoor and outdoor, a colour film and some still colour transparencies. On the same evening as the demonstration, L. C. Jesty, of Marconi's, discussed some of the technical points in a lecture to the Institution of Electronics.

The frequency characteristic of the "adjacent channel" type of colour transmission is shown in Fig. 1(b) alongside that of N.T.S.C.-type signal at (a). In both cases the brightness information is transmitted in the full 3-Mc/s bandwidth and provides the ordinary black-and-white picture for existing receivers. The remaining information, hue and saturation, appears at the transmitting end in the form of two colourdifference signals, which are modulated on to two components of a carrier frequency displaced 90 deg in phase. In the wide-band system (b) this carrier is transmitted outside of the monochrome signal, whereas in the N.T.S.C.-type system (a) it takes the form of a sub-carrier (actually 2.6578125 Mc/s) on the main signal, so that the colour information is transmitted within the monochrome 3-Mc/s band. Fig. 2 shows how the standard 405-line waveform is adapted to the N.T.S.C. type of signal. It will be noted that the peak-white/sync-pulse ratio has been reduced from 70/30 to 60/30 to accommodate (partially) the positive excursions of the colour sub-carrier. In addition, the back porch of the sync pulse carries a short burst of sub-carrier frequency which is used for synchronizing the homodyne colour-signal detectors in the receiver.

It was clear from the demonstration that the adjacent-channel system (b) gave better colour pictures than the N.T.S.C. type of system, and on the screens of the ordinary black-and-white receivers there was no sign of an interference pattern. Another point in its favour, mentioned by Mr. Jesty in his lecture, was that it would make for simpler and less expensive receivers than those required for the N.T.S.C. system. For possible colour transmissions in Bands IV and V the extra bandwidth required would not present any difficulties (the T.A.C. having already proposed that channel widths of 7.5 Mc/s should be made available to stations). On Bands I and III, however, it would be necessary, as Mr. Jesty pointed out, to make the colour signal of one station overlap the monochrome signal of the station in the

adjacent channel.** The cross-talk between them would probably be troublesome in fringe areas, but it could possibly be overcome by the use of directional aerials.

At the demonstration comparisons could also be made between two possible methods of presenting the colour pictures, namely the R.C.A. tri-colour cathoderay tube⁺⁺ and a triple-tube projection system using optical combination of primary-colour images. Most observers agreed that the tri-colour tube gave the better pictures, both in colour rendering and definition. This was in spite of the fact (mentioned by Mr. Jesty) that in the R.C.A. tube the pattern of maskholes and dots is liable to cause an interference pattern when interacting with our 405 scanning lines. Moreover, it seems that R.C.A., in order to avoid this beat effect with their 525-line structure, have made the pattern of holes and dots a good deal coarser than would otherwise be desirable, and as a result the definition of the tube is limited to about 250 lines.

The live scenes in the demonstration were televised by a new type of camera which uses only two pick-up tubes as compared with the three tubes in the R.C.A. colour camera. This represents an important step towards the ultimate aim of a single-tube camera. The principle of operation takes advantage of the fact that the eye is not able to see colour in fine detail, and in this way the camera is well adapted to the transmission systems (Fig. 1), which both make use of the same peculiarity. One pick-up tube produces a normal-definition monochrome picture of 3-Mc/s bandwidth while the other is arranged to give two

** Wireless World, Nov. 1953, p. 509.

tt Wireless World, May 1954, p. 242.

low-definition colour signals, actually the red and blue primary-colour components. These are obtained by means of a filter consisting of alternate red and blue stripes arranged at right angles to the scanning lines. The green component is not required because it is not transmitted separately in the Fig. 1 systems but derived at the receiving end by subtracting the red and blue signals from the monochrome signal (which, of course, contains all three colour components).

This arrangement is obviously more economical than the three-tube type of camera, which produces red, green and blue colour-component signals of normal definition and combines them to form the monochrome signal, using only the red and blue outputs to provide the information for the transmitted colour signal (which does not need the full definition in any case). It also has advantages over the singletube type of camera, which uses a very fine-pitch colour grid on the pick-up tube with red, green and blue stripes at right angles to the scanning lines. With this the pitch of the colour grid has to be about three times the definition of the equivalent monochrome picture, so that red, green and blue colour-component signals can be obtained for each individual picture element. By contrast, the two-colour grid in the Marconi camera is much coarser and gives exactly half the definition of the equivalent monochrome picture (1.5 Mc/s) since this is all that is required for colour information in the transmission system. Another advantage of the two-tube arrangement is that because the two-colour image is of low definition it does not have to be so accurately registered with the green image (contained in the monochrome picture) as in the three-tube camera, where all three images are of normal definition.

Monochrome Television Camera


AT another recent demonstration by Marconi's a new camera for monochrome television, the Marconi Mark III, was shown in operation on a closed circuit. It can be used with either the 3-in or the new 4½-in English Electric image orthicon,* and in the demonstration the latter was employed.

As shown in the photograph, the camera has a fourlens turret, the lens in the lower left corner being the operative one. A control of light intensity is provided by means of discs in the turret, one of which carries a number of fixed filters and the other of which provides a continuous control of light transmission. Partly because of the placing of the tube and its coils to one side of the apparatus, and partly because of the use of electronic temperature control of certain windings, it has been possible to dispense with a blower for cooling.

The viewfinder is of the electronic type and is in a separate unit pivoted to the top of the camera. It is possible, therefore, to tilt the camera to any angle and yet keep the viewfinder in a position convenient to the operator.

The camera is designed for the 405, 525 and 625-line systems and with the $4\frac{1}{2}$ -in tube is claimed to give an output signal/noise ratio of better than 40 db. The sensitivity is such that for the best picture an incidental illumination of 10—20 ft candles is needed with an f/5:6 aperture. The power consumption is 1.5 kVA * Wireless World. May 1954, p. 225 and the camera weighs 140 lb and measures only $17\frac{1}{4}$ in. high by $15\frac{1}{4}$ in. wide by $26\frac{1}{2}$ in. deep.

A new flying-spot film scanner was also demonstrated and is suitable for 50- or 60-c/s frame frequencies. Scanning is effected with the film stationary and the film is pulled down during the frame flyback period of some 1 msec. It is the ingenious mechanical arrangement which permits this extremely rapid pull down that constitutes the main new feature of the scanner. The present model is for 16-mm film and for standard 2-in. by 2-in. miniature slides.

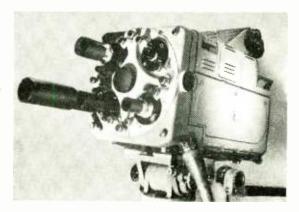

WORLD OF WIRELESS

European Television Exchange • Earl's Court Plans • Increased Radio Exports • Cable & Wireless Jubilee

International Television

A FURTHER STAGE in the organization of the series of eighteen relays of television programmes between eight European countries for June and July was reached in Brussels early in May.

At the invitation of the European Broadcasting Union, which is co-ordinating the relays, the engineers and programme officials of the various broadcasting authorities met the technicians of the telecommunications administrations who will be responsible for the provision of cable links. The temporary radio links and the standards conversion centres will be the responsibility of the broadcasting authorities.

The telecommunications administrations have to provide a complicated network of international telephone circuits for: (1) programme sounds and commentaries in different languages; (2) operational instructions between administrations; and (3) connecting the national control points with the international co-ordination centre being set up at Lille.

Show News

THE DEMAND for space at the National Radio Show to be held at Earl's Court, London, from August 25th to September 4th, has been greater than at any time since the war, with the result that it may be necessary to reduce the amount of space devoted to combined electronic demonstration stands. All three Services will be participating this year and the scope of the Technical Training Display—introduced two years ago—will be enlarged. Incidentally, the Radio Industry Council has issued a booklet on careers in radio and electronics which is available on request.

With seven different sources of television programmes available for piping to the stands, receivers will be able to be demonstrated outside the normal B.B.C. transmitting hours. In addition a signal will also be available for demonstrating Band-III receivers and convertors.



Increased Exports

RADIO EXPORTS set up a new record in March with a total value of just over $\pounds 2,800,000$. Direct exports of communications equipment, broadcast transmitters, radar and other navigational aids and electronic equipment for industry accounted for $\pounds 1.3M$. This figure does not include equipment installed in exported ships and aircraft.

The March figure brought the total for the first quarter of the year to £6.9M.

C. & W. Jubilee

"THE cable engineers and the wireless engineers of the past have been replaced by a new generation of telecommunication engineers, conversant with the strong points of each method," writes Maj. Gen. L. B. Nicholls, chairman of Cable & Wireless, Ltd., in a booklet entitled "World-Wide Communication" issued to mark the company's silver jubilee. Brief explanations are given in the 40-page booklet of the methods employed to send messages and illustrations over the company's 114 W/T circuits, 85 R/T circuits, 18 radio phototelegraphy circuits and 150,000 miles of submarine cable.

In the section dealing with development and production work carried on at Radio House, reference is made to the development of the double current cable code (DCCC). This system enables two separate channels of communication to be sent over a single radio path. The signals of the two tape transmitters are fed alternately into a common sending unit and converted to DCCC. It can also be used as an automatic repetition system in bad operating conditions.

Patent Office Library

AN EXTENSION to the Patent Office Library in Chancery Lane, London, W.C.2, recently opened to the public, provides immediate access to over 3,500 scientific and technical periodicals published since

1920. Hitherto, much of this material has been available only on request. Another important addition to the library is the provision of a section for bibliographies and extracts.

The library remains open to the public until 9 p.m. on Mondays to Fridays and until 5 p.m. on Saturdays.

OPERATIONAL TRAINING. To provide radar training for Merchant Navy navigation officers under operational conditions the Sir John Cass College, London, has put into commission this 112-ft. motor yacht. It has classroom accommodation for 20 students and is equipped with Marconi and Decca radar, Decca navigators, Kelvin-Hughes echo-sounders and Marconi d.f. and radio-telephone gear. The radar observer courses in "Sir John Cass" last a fortnight.

Radio Expedites Goods Collection

AN interesting experiment is being conducted in Leicester by British Road Services with the object of improving the collection of goods from traders' premises. Three parcels vans are equipped with v.h.f. radio telephones and messages and instructions reaching the depot from traders requiring urgent collection can be passed on to the radio-equipped van nearest the premises concerned. This obviates the delay in waiting for a van to become available or of sending one specially from the depot.

Vans are equipped with 3-wait Pye sets and the traffic control station, which is located on a tall building and remotely controlled, has a 15-watt set. Amplitude modulation is used.

PERSONALITIES

The new post of chief engineer of the Communications Division of Marconi's W.T. Co., has been accepted by C. Gillam, who has been with the company since 1930. In 1942, he took over responsibility for aerial designs and became chief of the Aerial Design and Systems Planning Group on its formation in 1948, in which capacity he was responsible for the design of aerials and associated equipment for communications, broadcasting and television. His contributions to Wireless World include articles on the Wrotham aerial system.



N. C. STAMFORD.

C. GILLAM.

N. C. Stamford, M.Sc., M.I.E.E., recently appointed education officer of the Institution of Electrical Engineers in succession to W. H. Taylor (see below), was lecturer in electrical engineering in the University of Manchester from 1933 to 1944. In that year he was appointed principal of Marconi College, with additional responsibility for education and training in Marconi's W.T. Company. He subsequently became deputy education and training officer to the British Electricity Authority.

W. H. Taylor, B.Sc., A.M.I.E.E., recently appointed controller of Education and Personnel Services to the General Electric Company, was education officer of the Institution of Electrical Engineers for six years from 1947.

Dr. Alfred N. Goldsmith, a co-founder and director of the Institute of Radio Engineers, has relinquished the editorship of the *Proceedings of the I.R.E.*, which he has held since 1913. In recognition of his services he has been appointed Editor Emeritus and given the Founder's award. He is succeeded by John R. Pierce.

Richard Arbib, managing director of Multicore Solders, is on a two-months' tour of the U.S.A. and has visited the Chicago Radio Parts Show (May 17th-20th). The British Industries Corporation, distributors for a number of U.K. manufacturers, including Multicore, had a stand at the Chicago show. **Col. J. Reading,** M.B.E., B.Sc.(Eng.), M.I.E.E., an assistant engineer-in-chief, Post Office, has been appointed chairman of the council of the Institution of Post Office Electrical Engineers and of the board of editors of the institution's journal. He was for many years secretary of the institution. Col. Reading joined the equipment branch of the Engineering Department of the Post Office in 1925 and returned to the Post Office in 1946 after war service. He was for some time chief signals officer at the War Office.

E. D. Hart, M.A., A.Inst.P., A.M.I.E.E., who was for many years with Marconi Instruments, and, since 1952, has been head of the Technical Department of Mullard's equipment division, has been appointed deputy director of the Scientific Instrument Manufacturers' Association. He is chairman of the Joint Advisory Committee on Radio Communication and Radar Measuring Instruments set up by R.C.E.E.A., R.E.C.M.F. and S.I.M.A. The new secretary of S.I.M.A., following Mr. Peacock's resignation (see below), is Miss G. E. Moss, B.A., formerly clerk to the council.

A. G. Peacock, B.Sc., A.Inst.P., has resigned the secretaryship of the Scientific Instrument Manufacturers' Association and has joined the board of Mervyn Instruments, manufacturers of scientific and industrial electronic equipment, of St. John's, Woking, Surrey. He is perhaps best known as the honorary exhibition secretary of the Physical Society.

P. A. Thorogood, G4KD, has accepted the invitation of the Radio Society of Great Britain to organize the eighth Amateur Radio Exhibition which is to be held at the Royal Hotel, Woburn Place, London, W.C.1, from November 24th to 27th. Mr. Thorogood, who has organized the Electrical Engineers' (A.S.E.E.) Exhibitions, is chairman of the London u.h.f. group of the R.S.G.B.

C. E. Hay has been appointed by Communication Systems, Ltd., to fill the newly-established post of technical director. He has been transferred from the parent organization, Automatic Telephone and Electric Company, which he joined in 1945 from the Ministry of Aircraft Production.

G. W. Cussans, flying radio officer with the British Overseas Airways Corporation, has been elected chairman of the Radio Officers' Union for 1954. He was a sea-going operator with Marconi Marine before joining Imperial Airways (predecessor of B.O.A.C.) in 1936. From 1945 to 1948 he was senior instructor at Hythe, Southampton.

OUR AUTHORS

D. N. Corfield, whose article on valves for Bands III. IV and V appears in this issue, spent a short period in the research laboratories of Ericsson Telephones before going to Standard Telephones and Cables in 1927, where he was concerned with carrier telephones and repeater equipment. He was for four years chief engineer of the subsidiary company Kolster-Brandes and since the war has been in charge of the Brimar Valve Application Department. Mr. Corfield is a member of the committee responsible for building the Television Society's u.h.f. 405-line transmitter installed at Norwood. He has been active as an amateur transmitter, G5CD, since 1923.

Charles B. Bovill, who reviews in this issue the development of the French 819-line television system, has been working in France for some time on the Decca Navigator chain of stations. He has been with Decca since 1946. His radio career began in 1933 when he joined the Gramophone Company on the development of broadcast receivers. In 1936 he went to the Air Ministry Aeronautical Inspection Directorate Radio Department and two years later joined Marconi's Aircraft Division acting as liaison engineer between the company and Coastal and Bomber Commands of the R.A.F. In 1942 he was commissioned in the R.A.F.V.R. and was officer in charge of the Air Operational Research Group of the Inter-Services Research Bureau.

H. G. M. Spratt, contributor of the article in this issue on magnetic recording tape, was, until recently, manager of the Magnetic Tapes Division of the Minnesota Mining and Manufacturing Company. Prior to that he was for a short time assistant chief engineer at Marconi Instruments and during the war was engaged on radio and radar in the Ministry of Supply. For seven years before the war Mr. Spratt worked on the development of high-definition television at E.M.I. and Philco. He started his career as a heavy engineer designing motors and generators.

OBITUARY

J. E. Nickless, M.I.E.E. (G2KT), who was for fifty years with Bullers, Ltd., and was the company's technical adviser on radio components (he retired in 1948), died at the age of 75 on May 2nd. He was well known in amateur circles and was a vice-president of the Southend and District Radio Society.

IN BRIEF

Broadcast Receiving Licences current in Great Britain and Northern Ireland at the end of March totalled 13,436,793, including 3,248,892 for television and 226,667 for car radio. The month's increases were 75,868 for television, 7,631 for sound only and 3,158 for sets fitted in cars.

Physical Society Show.—Both exhibitors and visitors to the Physical Society's annual exhibition will welcome the proposal to hold next year's exhibition in a larger hall. In spite of the co-operation of the governors of Imperial College, the growing interest in the show has made the space available at the college inadequate. It is expected that the 1955 exhibition will be held in the Royal Horticultural Hall, London, S.W.1, towards the end of April.

1954 Amateur Show.—It has been decided by the Radio Society of Great Britain to hold the eighth Amateur Radio Exhibition at the Royal Hotel, Woburn Place, London, W.C.1, from November 24th to 27th. The emphasis will be on "transistors and emergency equipment for portable and mobile use."

Electrical "Noise."—A five-day summer school on the theory of electrical conduction and noise will be held at the Centre for Continued Studies, Primrose Hill, Selly Oak, Birmingham, 29, from September 27th to October 1st. Particulars of the course, for which the fee is £5 (excluding meals and accommodation), can be obtained from the Director of Extra-Mural Studies, The University, Edmund Street, Birmingham, 3.

Electronics in Industry.—Some typical applications of clectronics to mechanical handling equipment will be shown and, in some cases, demonstrated by a few of the 200 exhibitors at the Mechanical Handling Exhibition, which opens at Olympia on June 9th for eleven days. Among the organizations known to be featuring electronic control gear are:—The British Electrical Development Association, B.T.-H., English Electric and Goring Kerr. A preview of the exhibition will be given in the June issue of *Mechanical Handling* which is organizing the show.

Home Service Coverage has been further improved by the installation of two permanent 2-kW transmitters at Scarborough, Yorks (1151 kc/s), and Ramsgate, Kent (1484 kc/s). They replace temporary transmitters which have been in use for some time. Wireless Dinner Club.—At the annual general meeting and dinner of the British Wireless Dinner Club, which has a membership of 500, Maj. Gen. C. H. H. Vulliamy, C.B., D.S.O., was elected president in succession to A. V-M. C. W. Nutting, C.B.E., D.S.C. The new vicepresident is H. Bishop, C.B.E., director of technical services, B.B.C.

Ten-Year Index.—The annual indexes to the four parts of the *Proceedings of the Institution of Electrical Engineers* for the years 1942-1951 have been collated and published as a collective index by the Institution. In addition to indexing every author, speakers in discussions and every key word in the titles of papers, the ten-year index includes a subject index in which titles of papers are collected under forty broad headings. The 500-page index costs 25s.

INDUSTRIAL NEWS

Transmitters for three television stations (both vision and sound), with associated aerial systems, have been ordered from **Marconi's** by the Danish broadcasting authority. They are to be installed at Copenhagen, Odense and Aarhus. The 625-line vision transmitters are to be amplitude-modulated while f.m. will be used for sound.

Cable Ship Radio.—The new cable ship Recorder (3,300 tons) for Cable & Wireless, Ltd., which was recently launched at Newcastle-upon-Tyne, will be equipped with Kelvin-Hughes radar and echo-sounders and Marconi radio-communication and sound amplifying gear.

B.B.C. and British Movietonews used Leevers-Rich magnetic recording gear when covering the Royal Australasian Tour. The recorders used by Movietonews are fitted with a synchronizing device, which, by means of a pulse recorded on the tape during the filming, ensures that when the tape is transcribed to the film perfect synchronism with the picture will be maintained.

"Navigator," the demonstration motor yacht of the Decca Company, is on a two-months' cruise of North European ports. She is equipped with the three types of radar (45, 12 and 159B) and the latest Decca Navigator (Mark V), which is capable of receiving the transmissions from nine chains working on different frequencies. Some 3,200 radar installations for 780 shipowners plus installations in vessels of the Royal Navy and 25 Commonwealth and foreign navies, have been undertaken by Decca. Navigator installations now total over 2,200.

South African Enquiry.—W. L. Procter (Pty.), Ltd., of 63, Strand Street, Cape Town, distributors of highfidelity radio and audio equipment and components would like to receive catalogues from British manufacturers. Their London representatives are: William Dunn & Company, Ltd., 12-15, Finsbury Circus, London, E.C.2.

Clare Instrument Company, of Rickmansworth, Herts, which was recently formed by J. de Gruchy, has opened a London office at 39, Victoria Street, S.W.1 (Tel.: Abbey 1816). A multirange instrument incorporating the principles of protection described by Mr. de Gruchy in our September, 1953 issue, will be produced by the company.

The Engineering Division of International Aeradio, Ltd., has moved from Bovingdon Airport to new premises adjoining the I.A.L. Printing and Publishing Division at Hayes Road, Southall, Middlesex (Tel.: Southall 2411).

Aerialite, Ltd., has opened a sixth depot—at 19, Blythswood Street, Glasgow, C.2. (Tel.: Central 2299.)

Radio-communication equipment and navigational aids are to be installed by Marconi Marine in the six vessels being built for the fleet of the Sugar Line, Ltd. Marconi equipment is also to be installed in the Union-Castle Line's new 7,450-ton motorship *Tintagel Castle* and the 9,000-ton motor tanker *Regent Royal* of the Regent Petroleum Tankship Company.

French Television Progress

Plans for Extending the Service

By CHARLES BOVILL. A.M.I.E.E., M.Brit.L.R.E.



OME three years ago it was unusual to see a television aerial in France, although there were regular broadcasts from stations in Paris and Lille. To-day, however, aerials are to be seen on the rooftops of very many houses, both in the towns and in the country, and even the smallest radio shops display television sets for sale.

The sudden increase in the popularity of this form of entertainment is generally considered to be largely due to the success of the Coronation relay, which was seen by millions of French people, very many of whom had never seen or been previously interested in television. Another factor which has stimulated interest is the very good quality of the 819-line system, which is now the established French standard. French people have appreciated the fact that this is a very high definition system which cannot be superseded for some years to come, and they feel that a receiver can be invested in without danger of it becoming out of date. Moreover, the close spacing of the lines enables very pleasing pictures to be obtained from large-screen tubes.

When the 819-line system was first proposed it was looked upon as a dangerous step to take and technicians were apprehensive on account of the many problems which its use incurred. One of the main difficulties anticipated was serious phase distortion in the system due to the wide bandwidth which the high-definition system employs. This can occur in many parts of the chain between the studios and the transmitter aerial. It is therefore greatly to the credit of the engineers concerned, both in the Radiodiffusion Television Française and in the French radio industry, that the difficulties have been largely overcome by the use of ingenious phasing networks, negative feedback arrangements and other techniques, many of which have their origin in radar engineering. In the latest transmitters being built in France, correction is applied at the final modulator stage of the transmitter, an M-derived filter being used for the purpose.

Probably the most critical part of a wide-band television system is in the coaxial cable from the studio to the transmitter. In the case of the Paris station this is relatively long and undoubtedly some

The 819-line test card used by La Radiodiffusion Television Française.

phase distortion occurs in it. French television experts state that the best way of judging the amount of phase distortion which occurs in the coaxial, and also the best way of seeing how good the 819-line system can be, is to view from signals transmitted from the Lille station. At this station, a Lille studio broadcast, which involves negligible coaxial cable transmission, can be compared with a relayed programme from Paris which must pass through the long coaxial cable from the studio to the transmitter. This comparative test indicates that if the coaxial cable technique can be improved there is very little wrong with the 819-line system.

Frequency Sharing Troubles

An unexpected problem was met last winter as a result of anomalous propagation conditions which caused interference to reception on the 185.25-Mc/s frequency shared by the Paris and Lille transmitters. This was overcome by using the offsetting technique which detunes the two transmitters by half the line frequency, here about 10 kc/s. The technique was originally developed in the U.S.A. and is now in general use for overcoming the difficulties of operating television stations on common frequencies. To understand the principle of the system, consider first the situation that occurs with perfectly synchronized transmitters. Under these conditions, when there is zero frequency difference between the carriers, there will appear at many reception points a second picture which will resemble the well-known "ghost image." The appearance of the unwanted picture must clearly depend upon the relative phase of the two signals at the receiving aerial, Thus, even with perfect synchronization of carrier frequencies, there will be many localities where reception must be unsatisfactory.

Under practical conditions it is almost impossible to achieve perfect frequency synchronization as there must be some wandering of the frequencies of the two carriers. At the receiver detector this frequency

WIRELESS WORLD, JUNE 1954



Pair of 30-cm relay aerials with electromagnetic lenses, built by Cie Generale de Telegraphie Sans Fil.

Television relay station in the Paris-Strasbourg chain at Dabo la Hoube in the Jura, constructed by Cie Generale de Telegraphue Sans Fil.



wandering is translated into a heterodyne effect which appears on the screen of the receiver as a series of horizontal bars moving up and down. This effect takes place under conditions of a much greater ratio of wanted-to-unwanted signal and at ranges from the unwanted signal transmitter which are far in excess of those where the form of ghost image is seen. It is therefore an effect which can be most objectionable when even a very small interfering signal is present, such as occurs with abnormal propagation conditions. Furthermore, it cannot be eliminated by such simple expedients as orientation of the receiving aerial.


The problem of the "venetian blind effect," as it is so aptly called, led to the development of the offset system in the following way. Under conditions of a small frequency difference between two carriers there are only a few horizontal bars and the cycles of the beat between the two carriers appear as positively and negatively interfering pictures. As the difference between the carrier frequencies is increased the beat interference pattern becomes one of thin lines which is very much less annoying to the viewer. At the same time the odd and even lines have interfering images of opposite polarity which are cancelled out by the integrating effect of the eye at normal viewing distance. The critical offset fre-quency will be half the line frequency (10 kc/s with the 819-line system) to achieve the best all-round result. In order that the offset system can function correctly, it is of course necessary to maintain highly stable frequency control at the transmitters, which are working on what is virtually a common wavelength. Practical tests have indicated that a total frequency excursion of up to 2 kc/s, inclusive of both transmitters, is permissible without objectionable interference effects at the receiver. In the case of the Paris and Lille transmitters this means that a frequency stability to within one part of 200,000 is required.

Eiffel Tower Installation

The value of the famous Eiffel Tower to radio has always been considerable from the time that Ducretet sent the first message from its summit in 1898. The massive aerials which for so many years hung from its top gallery to anchor points on the Champ de Mars, and which were used for time signals, have now been removed, and the Eiffel Tower is almost exclusively used for television work, for which it is an ideal transmission site. The 1,000ft elevation of the aerials is unique and enables the signals radiated to have an unobstructed path over a very large area. Not only does it allow the outside broadcast vans to work from considerable distances away, but it also enables relays to be installed which feed the subsidiary stations at Lille and at Strasbourg.

The Paris-Lille relay has been in operation for some time now, but the one to Strasbourg is more recent. It begins with a 3-cm link to Meudon, where the first of ten relay stations is located. From here the remainder of the links operate on a wavelength of 30 cm. The total length of the relay to Strasbourg is about 280 miles.

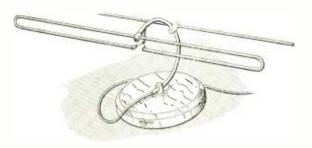At present the Eiffel Tower transmitter radiates 12 kW and the equipment is housed in the top of the tower. A new transmitter is now being installed which will enable 150 kW to be radiated, and this will be housed at the base of the tower. The output of this transmitter and also that of the sound transmitter will be connected to a "diplexer," and thence through



Simple indoor television aerial with folded dipole and adjustable director on a marble base.

Typical television receiving aerial for the 819-line system made by Radio Industrie.

a single balanced feeder, over 1,000ft long, to a turnstile aerial on top of the mast, which will radiate both vision and sound signals. The total loss in the feeder will be of the order of 30 per cent. The existing transmitter is modulated at the final stage, but the high-power equipment will be modulated at low level. When the new transmitter is installed the old one will be removed from the top of the Tower and set up as a standby at the base.


These changes to the station will doubtless be welcomed by the engineers who operate the equipment, as throughout the winter they have to mount the last 570ft of the tower on foot to the transmitter room, since the hydraulic lifts, installed many years ago, become unserviceable in cold weather.

Following upon the success of the present highdefinition transmitters, further expansion is being carried out, and in the near future new stations will be put into service at Lyon and at Marseilles, and a 200-kW station is being planned for Alsace. In the meantime the aerial mast at the Strasbourg station is being doubled in height in order to increase the field strength in the fringe areas.

The expansion of French television is intended to be in two stages. In the first stage more small relays will be built to serve thickly populated districts, such stations being satellites to the main stations. It is intended to have "branch lines" off the main relay chain from Paris to Strasbourg which will feed relays at Nancy, Reims and Amiens. The main station at Lyon will have a satellite to cover the lower part of the Rhône Valley, and the Marseilles station will have satellites at Toulon and at Nice to cover the south-east coast of France, where the population is relatively dense.

The ultimate plan, which was agreed upon in principle at the international conference at Stockholm in 1952, is for almost complete coverage of France. Owing to the topography of the country, which includes two major mountainous regions, there will be a requirement for a total of 45 stations. The implementation of this plan must depend largely upon funds granted by the Government and from the revenue from licences. At present the French television licence costs 4,350 francs, which is the equivalent of slightly more than £4 6s.

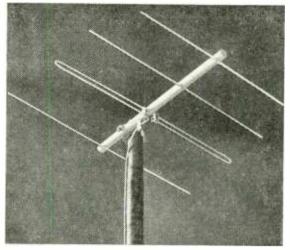The French television authorities are fully aware of the geographical importance of France for interna-



tional television relays, and their plans are centred round Strasbourg as the hub of European television relays. In the plan proposed, transmissions from Germany, Switzerland and Italy would enter France at Strasbourg and from there be relayed on to Paris and London. A radio link from Strasbourg to Paris is already being built, and the "inward" relay stations will occupy the same sites as the "outward" relay stations from Paris to Strasbourg.

In eastern France there are many localities where several programmes can be picked up, including the local programme. As there is a difference between the French standard and the European standard, as used in Germany and Switzerland, special receivers are needed-not only for the difference between the 819- and 625-line transmissions and their attendant variation in black-level percentage, but also the sound section of the receiver must be capable of receiving a.m. or f.m. signals. One manufacturer is marketing a receiver of this type aptly named the "Strasbourg," since in this town the Baden Baden transmitter can provide adequate signal strength. On the other hand, the first privately owned television station in Europe, at Saarbrücken, is using the French 819line standard.

The station to be built for Monte Carlo, which will also be privately owned, will naturally use the French standard, and will probably be providing a regular programme for the Riviera by the end of the year. Both the Monte Carlo and Saarbrücken stations will transmit on frequencies in the 200-Mc/s band.

Indoor Receiving Aerials

Reception of the high-definition programmes has not presented many difficulties, and the normal folded dipole with a reflector and one or two directors is the most popular type in use. This aerial provides the 10-Mc/s bandwidth required and it is coupled to the receiver by a 72-ohm unbalanced coaxial cable. Very many receivers now operate from indoor aerials in the Paris region, and such aerials are becoming increasingly popular since on the 1¹₂-metre wavelength a dipole aerial is of small enough dimensions to be made up as an attractive ornament. For the fringe areas these aerials are supplied with a self-contained pre-amplifier which gives 20 db gain. Interference from motor cars is markedly less on the 185Mc/s transmissions than on the 46-Mc/s transmission, which puts out the programme on the old 441line standard in Paris.

Although France was criticized very strongly by other countries in Europe for adopting the 819-line standard and breaking away from the so-called European standard of 625 lines, recent events and rebroadcasts, such as the epoch-making Coronation relay, have shown that definition conversion can be carried out very satisfactorily and without noticeable detriment to picture quality. Once such techniques are perfected the international exchange of programmes becomes possible, and the question of standardization becomes of secondary importance, since, by the very nature of the wavelengths used for television, international reception must always depend upon local rebroadcasts, except in isolated cases, for which "multi-standard" receivers of the type already described are available. However, this raises the delicate matter of the necessity for standardization for television systems, which is better left alone, not only by the French.

Let it suffice to conclude with a word of admiration for General Leschi, the Technical Director La Radiodiffusion Television Française for having the courage to adopt and to try the high-definition system, and for the French radio industry for supporting it by technical development and making it a success.

Magnetic Recording Tape

Measurement of Coercivity and Remanence

By H. G. M. SPRATT, B.Sc., M.I.E.E.

N a recent paper¹ on magnetic-tape recording it was clearly shown that, despite the use of h.f. bias, which subjects the tape to several magnetization cycles as it passes the recording head, a truly symmetrical hysteresis loop is seldom, if ever, reached before the tape has left the field. At the same time confirmation was provided of the fact, well known in practice, that the optimum bias current lies well below the saturation level. A valid measurement of coercivity or remanence, however, implies the use of a hysteresis loop which is both symmetrical and extends up to complete saturation in both directions of magnetization. Indeed, quite apart from the standard definitions of these quantities, measurements made under any other conditions would be difficult to repeat and useless for comparison purposes. It might therefore be assumed that such measurements were not only irrelevant but actually misleading when attempting to assess tape quality. Experience shows, however, that knowledge of these quantities is of considerable value in predicting performance, while the curves from which they are obtained may yield additional pointers to behaviour.

In what follows it is proposed to describe the most convenient method of measuring coercivity and remanence and to indicate the additional information to be derived from the curves. Before doing so, however, the practical importance of these two quantities will be briefly discussed.

In the sphere of magnetic recording the term "coercivity" is undoubtedly the better known of the two. This is because it is common practice for manufacturers to describe their tapes as of low, medium


or high coercivity, an excellent idea, marred unfortunately by some confusion as to what constitutes medium and what high. Low-coercivity tapes, rather less popular now than in the past, have values extending up to 150 oersteds and are characterized by low optimum bias currents, easy erasure and relatively poor frequency response. High-coercivity tapes, with coercivity values extending from about 320 oersteds upwards, have exactly the opposite characteristics and are in little demand except for special purposes. Medium-coercivity tapes have coercivities ranging from 220 to 320 oersteds and combine most of the virtues of the other two types without their drawbacks. In practical usage other variables such as mechanical defects and differences in the performance characteristics of recording equipments can easily mask the slight but definite difference resulting from a 10 per cent change in coercivity, e.g., from 230 to 255 oersteds. Nevertheless, an accuracy of measurement within this percentage is essential for comparison purposes.

Remanence values have far less significance for the user than those of coercivity. This is slightly illogical since he is certainly interested in sensitivity and undistorted output capacity, quantities which are dependent upon remanence. Actually knowledge of the remanent flux is more useful still, since total flux, not flux density, determines sensitivity and coating thickness does vary from tape to tape. The bulk of tapes have remanence values lying within the range 400 and 900 gauss.

The necessity for a symmetrical hysteresis loop when measuring coercivity or remanence rules out completely the use of a static or point-to-point plotted B-H curve and demands a dynamic test obtained by applying a steady alternating magnetizing force to

San Brank Providence

[&]quot;An Investigation into the Mechanism of Magnetic-Tape Recording." P. E. Axon, *7.1.E.E.* Vol. 99, Pt. III, pp. 109-126 (May, 1952)

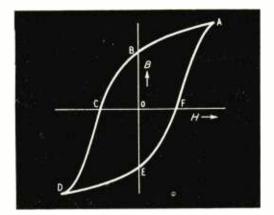

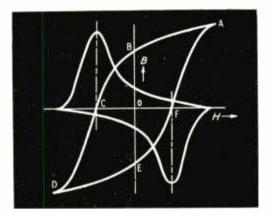


Fig. 1. Typical hysteresis loop under steady state a.c. conditions and (right) Fig. 2. Hysteresis curve together with the time differential curve of flux density (dB, dt).

the tape specimen. The resulting hysteresis loop will then be of the form shown in Fig 1 where the significant values are the magnetizing force OC or OF (the coercivity) and the flux density, OB or OE (the remanence). Obviously in a dynamic test these quantities can be determined only by reading them off a presentation of the loop on a cathode-ray oscilloscope.

To provide such a presentation we must clearly have available a voltage proportional to H for applying to the X-plates and one proportional to B for the Y-plates. As will appear later the first is easily obtained, the second not so easily. There is, however, no difficulty in providing a voltage proportional to dB/dt, the time differential of B, and one recognized procedure, which will be followed here, for obtaining a voltage proportional to B is to take the dB/dt value and integrate it. The integral is, however, less accurate than the differential from which it was obtained as will appear later. Apart from that, the coercivity value can be read off the differential curve —if it is shown—equally well and, moreover, this


curve will reveal variations and abnormalities completely hidden in the integrated curve.

In Fig $\overline{2}$ are shown both the integrated curve, i.e., the hysteresis loop again, and the differential curve. The pronounced peaks appearing in the latter obviously correspond to the points of greatest slope in the hysteresis Visual inspection shows, loop. however, that these points of greatest slope are the points where the loop cuts the H axis, i.e., the points giving the value of coercivity. Experience shows that the greatest slope always coincides with this point for a homogeneous ferromagnetic material and is entirely unaffected by increasing the maximum value of H once that value has been raised to the saturating point.

The design of equipment for obtaining both differential and integrated curves will now be

WIRELESS WORLD, JUNE 1954

considered. If we have an air-cooled solenoid whose length is large and whose winding depth is small compared with its diameter and feed it from an a.c. source, say the 50 c/s mains, the instantaneous flux density in the neighbourhood of the centre will be uniform and proportional to the magnetizing current. A small search coil placed in this region with its axis parallel to that of the solenoid will accordingly have an output voltage which is proportional to the rate of change of this flux density and hence to that of the magnetizing current. If now we place a sample length of magnetic tape inside the search coil, the output voltage will increase as a result of the magnetization of the tape. This voltage value is of little use to us as it stands since we require, not the total voltage, but the increase only. To extract this difference a second identical search coil is placed near, but not too near, the first and connected in series opposition to it. In the absence of the tape the combined output of the two coils will be zero. This balance will, however, be upset by the insertion of the tape, the resulting voltage being that due solely

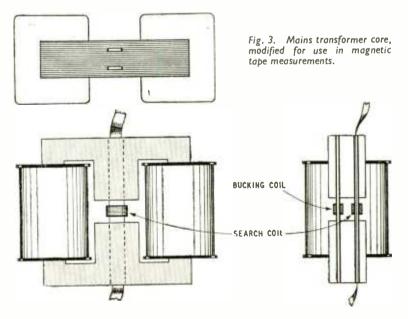


to the induction in the tape. Theoretically, therefore, in order to present the differential curve on a cathode-ray tube, all that is needed is to apply this voltage to the Y-plate amplifier while a voltage proportional to the magnetizing current, obtained from the voltage drop across a resistance in series with the magnetizing winding, is applied to the X-plate amplifier.


Practical Precautions

In practice it is extremely difficult to design an air-cored solenoid to provide continuously the neces-sary alternating H of 1,000 oersteds maximum without overheating, but the use of an iron core with a large air gap will solve this problem. A core corresponding to the larger size of radio-receiver mains transformer is quite suitable provided the centre limb is cut away sufficiently to give the necessary gap and some of the inner laminations clipped back to form an aperture down which the tape can be threaded as indicated in Fig. 3. A tube of nonmagnetic material of correct cross-section to accommodate three or four samples of standard $\frac{1}{4}$ in-wide tape is introduced into this aperture and the search coil, located in the air gap, surrounds it. The compensating or bucking coil is also placed in the gap but separated slightly from the first. If the closest possible symmetry is desired, two identical apertures can be provided, equidistant from the centre line of the core, one for the tube and search coil, the other for the bucking coil. The magnetizing winding is wound on the two outside limbs of the core.

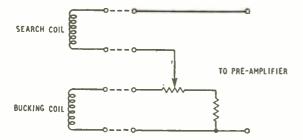The search coils should be as small as possible to ensure intimate linkage with the tape flux and uniform flux density across the coil. As, however, they must be wound with several hundreds of turns to provide





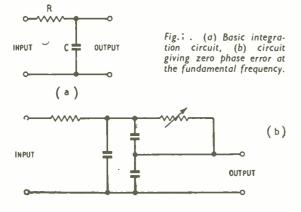

adequate sensitivity—and probably even then require the help of a pre-amplifier—a wire gauge of 48 to 50 is essential. The leads from the coils must be closely twisted together to prevent stray pick-up and taken to a terminal panel some few inches away from the core.

It is too much to hope that, even if initial balance between the coils is achieved by adjustment of turns, this balance will be maintained permanently. Accordingly, the leads from the two coils should be taken separately to the pre-amplifier, where a small adjusting potentiometer is provided as shown in Fig. 4. Adjustment for balance is made by raising the magnetizing current from zero to maximum with no tape in the unit and full gain in the Y-plate amplifier. Under these conditions there should be no vertical deflection of the trace. Actually, this is likely to prove a council of perfection, even with the help of the potentiometer, owing to slight deviations from 180 degrees of phase between the coils. Final balance will be achieved either by adjustment of coil position or earthing point or the insertion of a piece of lamination into the gap near the compensating coil.

As implied above, provision must be made for full control of the value of the magnetizing current, and this is best effected by driving the magnetizing coils from a Variac transformer. In order to permit earthing of these coils, an isolating transformer should also be included.

The oscilloscope and its amplifiers should be checked for phase error, which will almost inevitably exist to some extent in the low-frequency range employed. A satisfactory test is to apply a 50 c/s voltage to the X-plates and at the same time a small fraction of the same voltage, derived from a resistance potentiometer, to the Y-plate amplifier. The appearance of a closed loop on the screen indicates phase shift in the amplifier and this must be reduced as far as possible by such means as increasing the values of bypass and coupling capacitors. The same procedure should then be carried out on the X-plate amplifier. As regards the type of oscilloscope, a double-beam tube is recommended because of the advantages to be gained by using the second trace as a marker.

Integrating Networks

As already explained, the hysteresis loop is obtained from the differential curve by integration and accordingly all that would appear necessary would be the insertion of an integrating network somewhere between the junction of the search coils and the Y-plates. In fact, care is needed in the choice of the network and as some loss of grain will certainly be involved, an additional stage of amplification will be required. The basic integrating network is the well-known RC combination shown in Fig. 5(a) but if it is used, the value of C will have to be made so large relative to R in order to avoid undue phase error that the insertion loss will exceed 40 db. This network, too, has the particular drawback of introducing a greater phase error for the fundamental frequency than for the harmonics, whereas the reverse is the lesser evil. The rather more elaborate network of Fig. 5(b) can be designed to give zero error at the fundamental frequency and only 0.3 degree at the 3rd harmonic for an attenuation not exceeding 25 db, and is therefore much more suitable for our purpose. Obviously the most convenient place for the integra-(Continued on page 267)

tor and the additional stage of amplification is in the pre-amplifier, where arrangements can easily be made to switch both in and out as required.

It now remains to discuss briefly the two curves which should, of course, be similar to those shown in Fig. 2. Provided H_{max} is sufficiently high to take the tape up into saturation, both remanence, OB or OE, and coercivity, OC or OF, can be read directly off the hysteresis loop. The coercivity can also be determined, and somewhat more accurately, from the differential curve by measuring the distance between the peaks and the B-axis. Provided all mains pick-up has been removed from the trace and the centring is frequently checked, no difficulty should be experienced in reading to an accuracy within 5 per cent.

As suggested right at the beginning, the values of coercivity and remanence do not strictly apply to the conditions under which tape is normally used : nevertheless they prove in practice extremely useful for comparison purposes. In much the same way the height of the peaks in the differential curve is worth noting. It represents the maximum value of the slope of the hysteresis loop and would accordingly be a direct measure of sensitivity if the operating curve extended to saturation as this does. Even so, in comparison tests a high peak can infallibly be associated with a high sensitivity. It might also be expected that the degree of flatness of the top of the peak would indicate the undistorted output capacity of the tape. Unfortunately, on the normal cathode-ray tube the peaks are never sufficiently wide to show any sensible flatness on the top.

Perhaps the most striking feature of the differential curve is its sensitiveness to inhomogeneity of the magnetic material in the coating. If this coating contains two magnetic materials of different coercivities, it is very unlikely that the hysteresis loop will betray the fact. On the other hand it is equally unlikely that the differential curve will not. The presence of more than

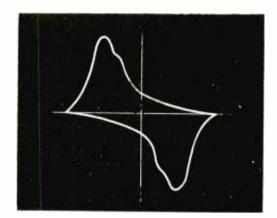


Fig. 6. Distortion of the differential curve due to inhomogeneity of the magnetic material.

one component will be revealed by either asymmetry of the peak or even possibly a subsidiary peak as shown in Fig. 6.

It is doubtful whether all useful information extractable from the curves has been covered in this article. That must be left to the user's experience and own particular interests. It only remains to point out that, the more elusive the detail sought, the greater the care needed in balancing the coils and eliminating the last traces of phase error and mains pick-up when the apparatus is finally set up.

REFERENCES

"A 60-cycle Hysteresis Loop Tracer for Small Samples of Low-Permeability Material," D. E. Wiegand and W. W. Hansen. Trans. A.I.E.E., Vol. 66, pp. 119-31 (1947).

"The Measurement of the Magnetic Properties of Fine Wire," P. T. Hobson, E. S. Chatt and W. P. Osmond. *Elect. Engng.*, Vol. 19, pp. 383-8 (Dec., 1947).

BOOKS RECEIVED

A Textbook of Radar, by the Staff of the Radiophysics Laboratory, C.S.I.R.O., Australia. Second edition, edited by E. G. Bowen, Ph.D., M.Sc. Broad survey of fundamental principles and their practical realization. Chapters are devoted to the applications of radar in navigation and surveying, and to meteorology and the physical sciences. Pp. 617+XIII; Figs. 352. Price 45s. Cambridge University Press, 200, Euston Road, London, N.W.1.

L'Ionosphère, by G. de Maximy. Treatise on the principles of forecasting frequencies for optimum propagation in telecommunications. Pp. 54; Figs. 23. Price 750 Fr. Editions Chiron, 40, rue de Seine, Paris, 6.

Automatic Voltage Regulators and Stabilizers, by G. N. Patchett, Ph.D., B.Sc., A.M.I.E.E., A.M.Brit.I.R.E. Wide survey of electro-mechanical and electronic methods of regulation, including a bibliography of more than 600 references. Pp. 335; Figs. 196. Price 50s. Sir Isaac Pitman and Sons, Parker Street, London, W.C.2. Television Engineers Pocket Book. Edited by E.

Television Engineers Pocket Book. Edited by E. Molloy and J. P. Hawker. A compendium of data for dealers and servicemen, including chapters on current practice in television receiver design and fault diagnosis. Pp. 228, Figs. 104, and numerous tables. Price 10s 6d. George Newnes, Tower House, Southampton Street, London, W.C.2.

Introduction to Colour TV, by M. Kaufman and H. Thomas. Description of N.T.S.C. (American) colour

television system and analysis of typical receiver circuits. Pp. 140; Figs. 74 Price \$2.10. John F. Rider, Publisher, 480, Canal Street, New York, 13.

Highlights of Colour Television, by John R. Locke, Jr. Introduction to principles of colour television as exemplified by the American National Television System Committee's recommendations. Pp. 44; Figs. 29. Price 99 cents. John F. Rider, Publisher, 480, Canal Street, New York, 13.

TV Manufacturers Receiver Trouble Cures. Edited by Milton S. Snitzer. Volume 5 of a series dealing with American commercial receivers. Pp. 109; Figs. 47. Price \$1.80. John F. Rider, Publisher, 480, Canal Street, New York, 13.

Specialized Home and Portable Radio Manual. Volume 8. Service data covering R.C.A. receivers issued between June, 1951, and December, 1953. Pp. 96 with numerous illustrations. Price \$1.65. John F. Rider, Publisher, 480, Canal Street, New York, 13.

Thyratron Inverter A Correction

In the circuit of Fig. 7, p. 240, May issue, the top end of the 3-12, 1-W resistor in the switching circuit should go to the moving arm of the switch, and not to the "on" contact.

WIRELESS WORLD, JUNE 1954

Further Notes on the Midget

Details of Chassis Layout and Circuit Additions for Long-wave Reception

B y J. L. **OSBOURNE**


HIS article gives constructional details of the receiver, theoretical aspects of which were described last month. Details are also given of a method of adding a long-wave band to the receiver, such a band being necessary because there are large areas of this country in which best reception of the Light Programme is provided by the B.B.C. long-wave transmitter on 200 kc s. The photographs illustrating this article show the cabinet and method of chassis construction adopted by the author for the single and two-band versions and the full circuit diagram of the two-band receiver is given in Fig. 1.

It was originally intended to use a long-wave bandpass filter employing two LC circuits coupled as on medium waves, but such an arrangement has a number of disadvantages. For example, it is necessary to have a tapping point on the second long-wave inductor to feed the crystal, and a change over switch is necessary to select the medium- or long-wave tapping point as desired. One would be extremely fortunate to obtain a commercial inductor with a suitably positioned tapping point and in general hand-wound coils would be used. Moreover, to give a pass band of approximately 10 kc s at 200 kc s, a coupling coefficient of the order of 1/30 is necessary and, if the long-wave inductors have a value of 2.2 mH, the coupling transformer requires primary and secondary in-ductances of approximately 70μ H. Though not impossible, it is difficult to wind by hand two inductors of this value on a small former although, of course, it would be fairly simple to do so using a dust-iron core

of the type used for medium-wave tuning inductors. If the long-wave coils have Q values of 100 (a typical practical value) a coupling coefficient of 1/30 is more than three times critical coupling and the frequency response has pronounced "rabbit's-ears." To avoid this, the coils can be damped by parallel resistors, but this reduces the gain. Thus, as pointed out in last month's issue, the addition of the long-wave band is by no means as straightforward as might be imagined.

It was considered unnecessary to go to the lengths detailed in the previous paragraph to obtain reception on a band containing so few signals, and a simple circuit was therefore sought which would permit the use of untapped commercial coils and would not require a coupling transformer. After some experimenting, the method finally adopted is that shown in Fig. 2. The long-wave coils L_5 and L_6 are simply coupled by a small capacitor C20 between their " hot " ends; although this circuit has the appearance of a bandpass filter it would be flattery to call it so.

The inductor L_6 is very heavily damped by the detector which is effectively in parallel with it. This damping is more serious than on medium waves because, for a given Q, a long-wave coil has approximately five times the dynamic resistance of a mediumwave coil. In fact the effective Q of L_6 is probably less than 1/6th of its nominal value because of detector damping. On the other hand L_3 is relatively undamped, having only the anode a.c. resistance of VI (1 $M\Omega$) across it. When two coils of markedly different O values are coupled, the resulting response

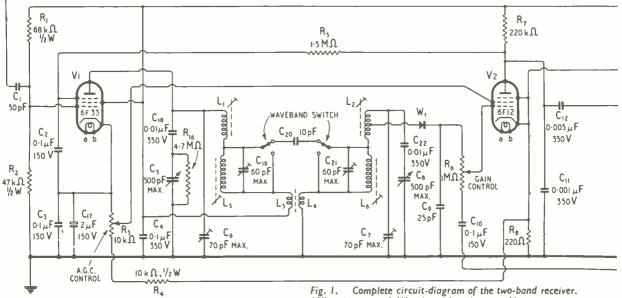

Complete circuit-diagram of the two-band receiver. (All resistors are $\frac{1}{4}$ -W unless otherwise stated.)

Sensitive T.R.F. Receiver


bears little resemblance to the wanted flat-topped curve. The capacitor C_{20} is in effect a matching component and is used in much the same way as the coupling capacitor in the "Modern Crystal Set" described by B. R. Bettridge in the September, 1951 issue of *Wireless World*.

The optimum value for C_{g0} was found by experiment to be approximately 10 pF. With this value the sensitivity of the receiver on long waves is of the same order as on medium waves and in the London area it was found possible to receive three signals including the Light Programme at good entertainment level.

The method of waveband selection can be followed from Fig. 1; the long-wave coils L_5 and L_6 are connected in series with the medium-wave coils L_1 and L_2 respectively. In one position of the 2-pole 2-way switch L_5 and L_6 are short-circuited to give medium-wave reception; in the other position the switch connects the coupling capacitor C_{20} between the "hot" ends of L_5 and L_6 . The coupling transformer L_3L_1 is in circuit on both wavebands, but it has negligible effect on the long-wave performance because the mutual inductance between the windings (of the order of 1 μ H) is so small compared with the inductance of L_5 and L_6 (approximately 2 mH).

A minor modification found necessary in the longwave receiver is the addition of a 0.001- μ F capacitor C_{23} from V3 anode to earth. This is necessary to prevent instability at high settings of the volume control, the r.f. filtering being less effective than on medium waves. The trouble is due to the proximity of the anode lead of V3 to the tuning inductors and can be cured alternatively by screening the lead.

In the original circuit the fixed vanes of one section of the tuning capacitor are at h.t. potential and, with the close vane spacing used in modern components, it was found that sparking tended to occur between

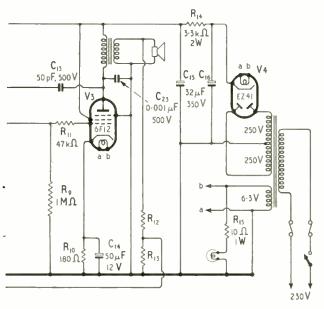





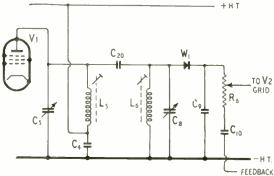


Fig. 2. Essential features of long-wave tuning arrangements.

fixed and moving vanes at certain settings of the tuning capacitor, particularly when it was briskly rotated. This is avoided in the circuit of Fig. 1 by the inclusion of a 0.01- μ F capacitor C₁₈, the fixed vanes being earthed by the 4.7-M Ω resistor R₁₆, which is too high to give appreciable damping of the tuned circuit. To prevent misalignment a similar com-ponent C_{22} is connected in series with the detector section of the tuning capacitor. These additional series capacitors cause approximately 5 per cent. reduction in the maximum capacitance of the tuning capacitors and increase the lowest frequency receivable on medium waves to approximately 580 kc/s. If the full frequency coverage is required, it can be obtained by increasing the number of turns on L_1 and L_2 to 60. Alternatively, curtailment of the band can be avoided by using larger capacitors (say $0.1-\mu F$) for C₁₈ and C₂₂ but the smaller capacitors were used by the author to conserve space.

A tendency has been noted in a receiver constructed to the circuit shown last month to oscillate at a very low frequency when tuned to a very strong signal and with a high volume control setting. The receiver does not always exhibit this behaviour and, when present, it occurs only on the strongest signals, disappearing on slight mistuning and on reducing the output volume. This has been traced to the variations in h.t. voltage which occur at high volume settings (the maximum undistorted output of the receiver is less than 1 watt). These variations affect the gain of earlier stages and set up steady oscillation. This

269


effect can be eliminated by connecting a small electrolytic capacitor (C_{17}) from V1 cathode to earth. Any capacitance greater than 2 μ F is adequate and the voltage rating need not exceed 150 volts.

The dial lamp is a 6.3-volt 0.3-amp. type operated from the l.t. winding of the mains transformer via a $10-\Omega$, 1-W resistor R₁₅ which drops the voltage available at the lamp to approximately 4. This reduces the brightness of the bulb, but the tuning scale is still adequately illuminated. The series resistor was included to give the bulb a long life; the author has used this technique for some time and has some bulbs which are still giving satisfactory illumination after more than five years' operation.


The accompanying photographs illustrate the method of construction used by the author for the single- and

two-band models, the additional components required for long-wave reception being indicated in dotted lines. The receiver is housed in a cabinet measuring $5in \times 5\frac{3}{4}in \times 11\frac{1}{2}in$ (outside measurements). The chassis measures $3\frac{1}{2}in \times 15\frac{5}{4}in \times 10\frac{1}{2}in$, the front-toback measurement being 1 inch smaller than the corresponding internal measurement of the cabinet, to leave room for the loudspeaker and the tuning drum drive. The chassis is spaced from the front of the cabinet by a folded piece of aluminium which supports the tuning capacitor, the tuning scale and the indicator lamp.

To keep hum at a low level, the three valves are grouped at one end of the chassis and the mains transformer is mounted at the other, the intervening space on the top of the chassis being occupied by the rectifier, smoothing capacitors, output transformer and tuning capacitor. Under the chassis, almost all the components associated with V1, V2 and V3 are mounted on the valve-holder tags or on two 5-way tag strips mounted on either side of the line of valves. The $50-\mu F$ cathode decoupling capacitor C_{11} is, however, rather bulky and is secured to the tags of a 7-way tag strip underneath the mains transformer.

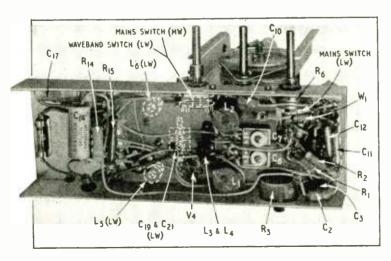

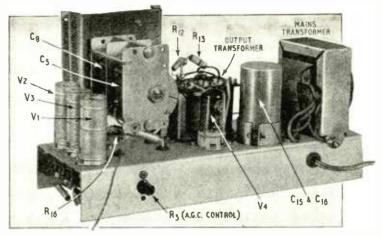Underside of chassis showing modifications and positions of additional components for long-wave reception.



Principal components mounted above the chassis.

This tag strip also serves to terminate the l.t. winding and to support the resistor R_{15} . All the inductors and trimmers are located in the centre of the chassis near to the waveband switch. To facilitate alignment these are all adjustable from underneath the chassis. The a.g.c. control is mounted on the rear flange of the chassis and, when the chassis is in position in the cabinet, the adjusting screw projects through a hole in the back of the cabinet. A.g.c. can therefore be adjusted without removing the back from the cabinet. Once set, however, the a.g.c. control needs very little attention. The author's receiver has been in use for several months and during that time there has been no need to touch this control.

In the single-band model the three knobs control the volume, tuning and a rotary mains on-off switch, but in the two-band model the on-off switch is combined with the volume control and the third knob controls the miniature Yaxley-type waveband switch. This is a 3-pole, 2-way type of which two poles are used. The additional coils and trimmers required for longwave reception are accommodated under the chassis near the waveband switch as shown in dotted lines. Fairly smill components are necessary to fit into the

space available and the trimmers are a pair of miniature compression-type capacitors of 60-pF maximum capacitance mounted on a steel strip attached to the chassis by stand-off pillars. The long-wave coils are Osmor Type QA6.

Long-wave alignment should be carried out after the receiver has been aligned for medium-wave reception as described in last month's issue. Long-wave alignment should then be carried out in the following way. Adjust C_p and C_{21} for maximum output with a modulated input at 350 kc s and the tuning capacitor set to maximum capacitance, and adjust L_3 and L_6 , for maximum output with a modulated input at 150 kc/s. Finally repeat the initial adjustment at 350 kc/s.

The quality of reproduction of this receiver is extremely good and, in fact, the excellent response to frequencies above 5 kc/s is an embarrassment during medium-wave listening after

dark, each heterodyne whistle being reproduced with uncomfortable clarity. Constructors with an interest in experimenting might care to try the effect of increasing the value of C_{13} to reduce the high-note response; it might even be anadvantage to use a 300 or 500pF variable capacitor to act as a variable tone control.

Radio Receiver Measurements

International Recommendations on Methods of Testing Sound-broadcasting Receivers

PUBLICATION 69* of the International Electrotechnical Commission, like others in its series, expresses "as nearly as possible, an international consensus of opinion" on its subject, and the national committees represented on the I.E.C. are pledged to bring their own countries' rules into harmony with the recommendations "in so far as national conditions will permit."

Comparing the scope of this document with the British Standard Glossary of the same subject, recently reviewed[†], one observes that it includes a number of characteristics omitted from BS.2065-notably hum, square-wave tests, stability of tuning, automatic frequency correction, acoustic feedback and radiationand in the single matter of frequency response characteristics it even specifies conditions for acoustical measurement; in spite of this, the treatment is on the whole simpler. It owes a great deal to the American I.R.E. "Standards on Radio Receivers," a number of clauses being almost word for word. But there are some rather surprising differences; for example, the standard dummy aerial, which, although based on the form that has long been familiar, shows some changes in component values. This, however, is only the beginning of the section on dummy aerials, which are dealt with much more thoroughly than usual. Not only is provision included in the type shown here for correcting the output resistance of one signal generator, and for two-signal tests with 1:1 and 10:1 ratios, but additional units are specified for simulating indoor aerials over two ranges of frequency, car aerials, and pick-up by mains. Procedure for frame-aerial receivers is laid down in detail.

The standard 30 per cent modulation at 400 c/s is retained, and so is the 50 mW standard output, but 5 mW and 500 mW are allowed as alternatives to meet special conditions.

The method of hum measurement provides data from which behaviour on supply mains of different waveforms can be predicted: along with pure d.c. or sinusoidal a.c. is applied 2 per cent audio frequency varied over the whole of the a.f. range, and a curve is drawn of hum output against this frequency; mainsfrequency harmonics in the output are also noted, and tests are repeated with different levels of unmodulated carrier wave present, to show modulation hum.

In contrast to the considerable amount of detail on these and other subjects, the methods of measuring harmonic distortion (total and individual) are dismissed in five lines, with no diagram. It might be expected that this brief treatment would provide room only for broad principles, so it is surprising to read that "During the measurement the loudspeaker has to be in its normal position."


* "Recommended Methods of Measurement on Receivers for Amplitude-Modulation Broadcast Transmissions" (First Edition). Central Office of the I.E.C., Geneva, Switzerland. 1954. Price: S.Fr.10. † BS.2065:1954. See Wireless World, April 1954, p. 188.

WIRELESS WORLD, JUNE 1954

The two common methods of intermodulation measurement are indicated, along with a note that disagreement among the principal workers in this field precludes rigid standards at the present time.

It is a pity that the wording of this international technical document should sometimes be so slipshod. For example, in Clause 21.3: "In the case of a loud-speaker for which the magnetic field is produced by a D.C. current, only the current in the speech coil should be considered for hum measurements." One might ask, what if the loudspeaker has not got a case? And, seeing that "D.C." presumably stands for "direct current," what is the significance of "D.C. current"? Wherever the words "the case of " occur (which they do frequently) the sense would be improved by striking them out. But these details apart, what exactly does this particular instruction mean? The French version fails to supply a clue, for this sentence is omitted from it! Unfortunately, badly expressed and ambiguous instructions are by no means rare.

Nevertheless, this publication does bring together a series of measurements well calculated to determine the practical capabilities of receivers within the terms of reference, with due regard (except, possibly, in the acoustic measurements) for what is reasonably practicable in equipment; and it is to be hoped that it will help to eliminate unnecessary differences in the basis of reckoning receiver performance. The fact that we have had to wait until now for an international recommendation on a.m. broadcast sound receivers emphasizes the need, as regards f.m. and vision receivers, for early and close collaboration between workers in all countries, so that differences can be eliminated before they have become too firmly rooted. M. G. S.

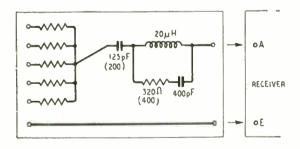

The I.E.C. standard artificial outdoor aerial for 0.15-26.1 Mc s differs from the American I.R.E. specification by two component values (I.R.E. values shown in brackets) and by the addition of five resistors for matching to one or two signal generators. Their values are such as always to bring the total generator output resistance to 80 Ω_{λ} , regardless of whether one or two generators are in use.

Valves for Bands III, IV and V

Half Way Between Ordinary Electrode Structures and Disc-Seal Techniques

By D. N. CORFIELD* D.L.C., A.M.LE.E

RECEIVING valves for Bands III, IV and V generally differ from those used in lower frequency bands because it is essential for the r.f., mixer and i.f. stages to give more gain in order to achieve a similar signal-to-noise ratio. Television receivers for Band I generally have an i.f. not exceeding 20 Mc/s, a pentode mixer and a single pentode r.f. stage, and a signal-tonoise ratio between 6 and 8 db is achieved in good designs. This figure may not be obtained, however, on all channels in Band I unless a modern type of r.f. pentode is used. Earlier types of r.f. pentode such as the 8D3, 6F12, Z77 and EF91 developed during the war have a single cathode connection, with the result that their input impedance is about 8.9 k!? at 45 Mc/s but only 3.8 k? at 67 Mc/s. This value is below the critical damping necessary for the bandwidth required, so the gain is lower and the noise worse for Channel V than for Channel I.

Modern r.f. pentodes such as the 6BW7, 6BX6 and EF80 have two separate connections from the actual cathode to the circuit, one being used for the input circuit and the other for the output circuit. This avoids


* Standard Telephones and Cables.

a common cathode impedance in both circuits (inductance of the single lead) which normally couples them together and has the effect of lowering the impedance of the input circuit. As a result of this technique the input impedance of the 6BW7, for example, is 18 k_{2}^{12} at 45 Mc/s and 6.5 k¹² at 67 Mc/s. These figures are twice as high as those of the earlier types.

Current television receivers designed for use on both Bands I and III use a higher i.f., usually around 34-35 Mc/s, and the improved input impedance of modern r.f. pentodes is desirable here also. This is because it is not a good thing for the circuit damping (necessary for bandwidth requirements), to be provided wholly by the valve, since replacing a valve could change appreciably the i.f. response characteristics.

These points are mentioned because the use of multiple connections is a feature of valves designed for the higher frequencies, although such connections are not necessarily always to the cathode.

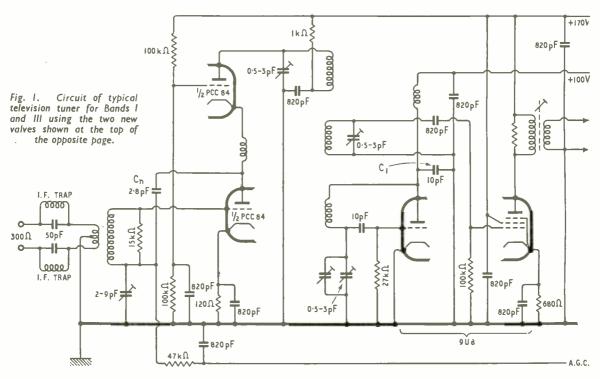The front end of receivers for Bands I and III usually takes the form of a multiple-position tuner comprising an r.f. stage and a mixer/oscillator, the tuned circuits being switched by ganged switches and



WIRELESS WORLD, JUNE 1954

rotated on a turret. In order to conserve space and obtain improved performance new mixers have been designed, and these are generally triode pentodes. Typical examples are the 6U8/ECF82 and ECF80 with their a.c./d.c. versions 9U8/PCF82 and PCF80. These valves have much higher triode and pentode slopes than the types of triode pentode with which we are familiar. The 6U8, for example, has a triode slope of 8.5 mA/V and a pentode slope of 5.2 mA/V. The high triode slope ensures ready oscillation and the high pentode slope good conversion conductance as a mixer. Apart from the heater the two units are quite separate and this tends to reduce the possibility of oscillator radiation via the mixer portion.

The r.f. stage for such tuners does not use an r.f. pentode but a double triode in a "cascode" circuit. Triodes will always give lower noise than pentodes because of what is known as partition noise. The cathode current of a pentode comprises two portions, the anode current and the screen current, and both contribute to the noise but only the anode current to the useful signal. A pentode has, as a first approximation, three times the noise it would have if used connected as a triode. There are, of course, some snags in using triodes as r.f. amplifiers and they normally need to be neutralized in order to achieve stability. The cascode system is a trick which creates a stable circuit from two triodes.

Fig. 1 shows a typical tuner circuit for Bands I and III. The lower triode of the first valve is used with an earthed cathode and the upper one with an earthed grid. The lower section has a fairly high input impedance but gives little gain except for the step up in the input transformer because it is working into the cathode impedance of the other section, which is very low. This upper section gives quite a good gain and the overall result is a gain from the aerial input to the mixer grid of about ten times (23 db). There is often a small coil between the anode of the first triode and the cathode of the second one, and this is for peaking the frequency characteristic of the circuit above 200 Mc/s to improve the gain. A small neutralizing capacitor is connected from the anode of the first section to the series-tuned grid circuit; this is not primarily for the purpose of obtaining stability but for improving the signal-to-noise ratio. Valves suitable for this circuit are the PCC84/7AN7, 6BQ7A, 6BK7A and 6BZ7; these give a noise ratio of about 7 db.


The mixer circuit is conventional except that a negative temperature-coefficient capacitor C_1 is required across the oscillator tuned circuit, otherwise the frequency drift is excessive. The maximum drift on Band III allowable in this country is rather less than in the U.S.A. and on the Continent because we use a.m. sound as against interchannel f.m. A proposed B.R.E.M.A. figure is 50 kc/s maximum.

Conventional British multi-channel tuners use very tiny coils for the circuits; some, in fact, are just straps across adjacent switch contacts. Their Q is, therefore, poor and so is the L/C ratio, the C being mainly valve capacitance and strays. As a result the frequency stability is not very good.


Oscillator Drift Problem


One possible approach to the oscillator drift problem is exemplified in a Band III to Band I convertor designed by the author. The oscillator uses a trough tuned line, electron-coupled oscillator fashion. The triode grid is tapped two-thirds of the way up the line

WIRELESS WORLD, JUNE 1954

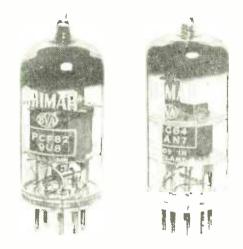

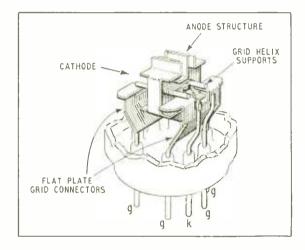New valves for Band III television tuners. On the left the 9U8 PCF82 triode-pentode frequency changer and on the right the PCC84 7AN7 double-triode cascode r.f. amplifier.



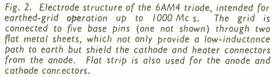

and the cathode one-third of the way up, the heater lead being taken back inside the line. The two tuning capacitors, one variable (bandspread) and one fixed (bandset), are across the hot end of the line and the mixer is coupled to the oscillator cathode. Such a tuned circuit has a drift of 20 kc/s from cold and a drift of 100 c/s per volt for h.t. variations. Lines of this type need not be of any particular shape or size and can be bent, and if they are not required to be continuously tuned the capacitors can be switched in discrete steps. The author has used this type of tuned circuit for years in a receiver covering both the 2-metre amateur band and the 90-Mc/s f.m. band, and in fact it is not difficult to arrange this form of circuit to cover a frequency range of 3 to 1.

Valves for Bands IV and V require higher slopes and lower noise factors than for Band III. This can only be achieved by closer electrode spacings and multiple connections to the essential electrodes. An example of such a valve is the 6AM4 which is an earthed-grid r.f. amplifier or mixer for use. up to 1,000 Mc/s. Since the common electrode is the grid this uses five separate grid connections. In order to reduce the lead inductance the structure is mounted horizontally right down on the glass base (see Fig. 2). The slope of the valve is 9.8 mA/V.

Table I gives some idea of the increased difficulties of manufacture resulting from attempting to obtain similar performance at higher and higher frequencies. A quite modern type, the 12AT7, is given for comparison purposes. The 6AM4 has a grid-cathode clearance of only one-thousandth of an inch and the grid is wound with 14-thou' wire with a gap of two thous between turns. The reduction of grid-cathode spacing is necessary in order to maintain the required value of mutual conductance, and the grid-anode spacing has to be similarly reduced to keep the amplification factor in proportion. More turns per inch and thinner wire on the grid helix are an outcome of the generally smaller electrode structure. The valve will give a noise factor of about 6 db as an r.f. amplifier in Band IV and about 9 db as a mixer, and Fig. 3 at the bottom of the page shows a circuit including both these applications.

The corresponding oscillator valve is the 6AF4, which has a slope of 6.6 mA/V. It has two grid connections and three anode connections, as it is normally used with the cathode choked and the grid or anode earthed. More expensive valves, because of their construction, are the disc-seal types also known as lighthouse, planar, pencil or rocket valves. The grid, anode and, in the case of tetrodes, screen grid are brought out to discs or rings which can be clamped into the circuit and thereby provide a continuous and therefore infinite number of connections. These give even better performances than normal valves but in their present form are unlikely to be used in Bands IV and V for domestic television.

Crystal Mixture

A type of mixer commonly used for these bands is the crystal mixer, the most popular being the silicon type although germanium ones are also available. These mixers are somewhat critical of heterodyne voltage and give a conversion loss of about 6 db. A convertor can be made for Band IV with a noise factor of about 7 db if considerable care is taken. This figure can only be achieved if the first stage of the i.f. amplifier has very low noise, and this is usually obtained by using a cascode or neutralized triode for the first i.f. stage. It is also essential that the heterodyne voltage is free from noise and spurious frequen-

INPUT

125N

Fig. 3. The 6AM4 triode used as an r.f. amplifier and as a mixer in a Band IV receiving circuit (70 cm). The oscillator (not shown) is coupled inductively to the silverstrip line. cies. Since the noise output from the crystal is proportional to the crystal current generated by the applied heterodyne voltage, the presence of anything other than the frequency required $(\pm a \text{ few cycles}$ ideally) merely increases the noise without improving the signal. This is one effect responsible for poor noise figures in crystal mixers, particularly when the oscillator is operating at harmonic frequency or is generated by a lower frequency crystal, but it can be reduced by the insertion of a sharp filter or high-Q break between the heterodyne source and the mixer.

On all high frequency bands care must be exercised in the coupling between stages, particularly that between the aerial feeders and the first stage, and it should be remembered that the coupling that gives the maximum gain rarely gives the best signal-to-noise ratio. The lowest noise is usually obtained when the coupling is tighter than that required for normal gain.


Mention was made earlier of the importance of a low-noise r.f. stage to reduce the effect of mixer noise, and here it is worth noting the effect on noise factor of adding r.f. stages in front of a receiver in Band IV. With a noise factor about 6 db in the receiver, the addition of a disc-seal pre-amplifier of 20 db gain reduces this to 3 db while a further pre-amplifier brings it down to 2 db.

This article is based on a lecture recently given by the author to the Television Society.

 TABLE I.—CRITICAL DIMENSIONS IN U.H.F. AND

 V.H.F. TRIODES

grid- cathode clearance	grid- anode clearance	grid turns per in.	grid wire size
0.003in	0.015in	156	0.002in
0.00275in	0.013in	147	0.0015in
0.002in	0.017in	200	0.001in
0.001in	0.008in	295	0.00125in
	cathode clearance 0.003in 0.00275in 0.002in	cathode clearanceanode clearance0.003in0.015in0.00275in0.013in0.002in0.017in	cathode clearanceanode clearanceturns per in.0.003in0.015in1560.00275in0.013in1470.002in0.017in200

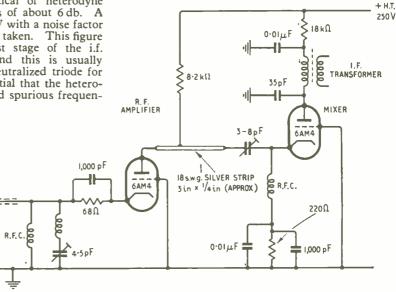

Piezoelectric Crystals

Survey of Physical Properties and Their Practical Exploitation

By S. KELLY*

BEFORE 1939 only two types of piczoelectric material were generally available; these were quartz and Rochelle sait. Quartz plates were used principally as resonators and oscillators, and Rochelle salt was the activating unit in crystal gramophone pickups, Since the end of the war an increasing number of piezoelectric materials have been made available, usually accompanied by cryptic initials which often mean less than nothing to the practising radio engineer unacquainted with chemical jargon; and he should not be blamed for misconceptions, especially when the various claims for different types of crystals appear to be mutually contradictory. Most of these new crystals have been developed with specific engineering applications in view and can be divided into two major classes: (a) as resonators, (b) as electromechanical transducers.

The underlying physical principle of these two types of crystal is identical, and the differences are of degree and application rather than fundamental. It is the purpose of this article to try to sort the sheep from the goats and at the same time establish some form of pedigree of the crystals used as electromechanical transducers, in particular those which are used in the manufacture of gramophone pickups.

Crystal Materials.—Quartz is still the major source of plates for precise control of frequency. It is interesting to note that bimorph† construction, at present extensively used on electromechanical crystal devices, was first introduced by the Curie brothers in their classic investigation of the piczoelectricity of quartz about 1880.¹

Tourmaline is at present of little more than academic interest, although it has been used as a sub-standard for pressure calibration of microphones.

Ethylene diamine tartrate (E.D.T.) and dipotassium tartrate (D.K.T.) are used

* Cosmocord, Ltd. \dagger A bimorph is essentially a mechanical transformer, consisting of two slabs of crystal material cemented together, with electrodes connected so that one element expands (for a bender type of crystal) or shears (for a torsional type) in one direction, while the other element contracts or shears in the opposite direction. The amplification of movement is (L/T)2 where L is the length and T the thickness of the bimorph.

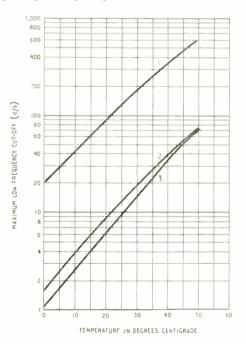


Fig. 1. Variation in low-frequency cut-off due to change of conductance with temperature in three grades of ammonium dihydrogen phosphate.

as resonators in crystal filters for carrier telephone systems. Their stability is sufficient for this application, and it is possible that they may replace quarts.

tion, and it is possible that they may replace quarts.⁴ Lithium sulphate (L.H.) is used principally as a volume expander in high-frequency (ultrasonic) applications, but is largely being supplanted by ammonium dihydrogen phosphate (A.D.P.). Apart from A.D.P., none of the foregoing crystals finds any commercial use as transducers in gramophone pickups or microphones.

There are, therefore, only three general types of crystal available for use in commercial transducers. These are : —

(a) Sodium potassium tartrate (Rochelle salt),

(b) Ammonium dihydrogen phosphate (A.D.P.),


(c) Polycrystalline barium titanate (Ceramics).

There is a fundamental difference between the first two crystals and the third in that the former are single crystals grown from a solution, whereas the latter is an aggregate of micro-crystals sintered to shape. By virtue of the asymmetry of the basic crystal structure a voltage will be generated across two electrodes of a correctly oriented slab when a force is applied to it (usually but not always perpendicular to the faces which are furnished with electrodes). In the case of barium titanate ceramics in which the crystals are

completely randomly oriented, the charges on the individual micro - crystals will cancel. By subjecting the fired and "electroded" slab to a high potential gradient the domains of favourably oriented microcrystals grow at the expense of the others, and ultimately approximately 7 to 10 per cent of the domains are aligned in the correct direction.

A.D.P.-Ammonium dihydrogen phosphate was developed at the beginning of the war to meet the need for high-power under-water transducers. It has a higher voltage sensitivity ("g" co-efficient, discussed later) than Rochelle salt, but a very low dielectric constant, with the result that most A.D.P. crystal units are designed to work into a 5-M Ω load. This high value of load resistance can be reduced to a value of $1 M\Omega$ and still maintain a satisfactory low-frequency

WIRELESS WORLD, JUNE 1954

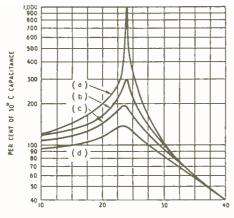

TEMPERATURE IN DEGREES CENTIGRADE

Fig. 2. Change of capacitance in Rochelle salt element with temperature. (a) X-cut plate, no restraint; (b) torque bimorph, no restraint; (c) bimorph mounted in pickup; (d) bimorph set in casting resin.

response by shunting the pickup with a condenser of about four times the crystal capacitance; but the voltage sensitivity of the pickup will also be reduced by the same factor (\times 4). The capacitance is quite stable with temperature and pickups have successfully withstood the test of immersion in boiling water for half an hour with no apparent deterioration in performance.

There is, however, a snag! At frequencies below resonance, the crystal transducer behaves as a generator in series with a capacitance terminated with a resistance. In the case of Rochelle salt and barium titanate the conductance, G, is sufficiently small for it to be neglected, but in the case of A.D.P. the value is relatively high and variable, being a function of the purity of the crystal and the temperature. It is usual to express this conductance in terms of the low-frequency cut-off rather than an absolute value, and the cut-off frequency is that at which $G = \omega C$. This is the familiar -3 db point on RC-coupled amplifiers.

The graph, Fig. 1, shows the variation of low-frequency cut-off (-3 db point) with temperature for three different grades of A.D.P. These curves are taken under open circuit conditions and because of this disability and the low dielectric constant, A.D.P. is not often used as a transducer in pickups.

Rochelle Salt .- This compound has the highest electro-mechanical coupling coefficient of any commercially available piezoelectric material. It has a reasonably high dielectric constant, a low density and a fairly low Young's modulus, all of which combine, as we shall see later, to make a highly efficient widefrequency-range bimorph. The capacitance versus temperature anomaly which occurs at the Curie point of 23.8 deg C can be a nuisance for some applications, but is not very important for gramophone pickups. Fig. 2 shows the variation of capacitance with temperature for Rochelle salt under four conditions; curve (a) is for a single shear plate, as cut from the virgin crystal, with no restraint, (b) is for a torsional type bimorph, again with no restraint, and curve (c) is the same crystal fitted into a gramophone pickup with correctly applied viscous damping and restraining members, and curve (d) is with the crystal firmly clamped. In the latter case the crystal was cast in a block of cold-set-

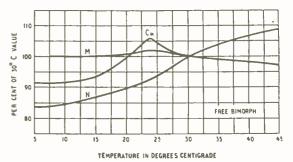


Fig. 3. Variation with temperature of effective mass (M), compliance (Cm) and the equivalent mechanical-electrical transformation ratio (N) in a free bimorph of Rochelle salt.

ting Araldite "D" of approximately 1 inch cube. The above graph shows that the effect of the capacitance anomaly is strictly a function of the conditions under which the crystal is used.

Fig. 3 shows the variation of the other constants with temperature; M is the effective mass, C_m compliance, and N the transducer ratio, all referred to 30 deg C. Except at very low frequencies the load impedance is considerably greater than the crystal impedance. The average value of the crystal used in present-day gramophone pickups is 1,500 ρ F at 80 deg F (27.5 deg C) and this corresponds to a capacitive reactance of about 1 M Ω at 100 c/s. The crystal capacitance will be greater than nominal between 55 deg F (14 deg C) and 80 deg F, and the variation of low-frequency performance will be within 3 db over this temperature range.

Humidity does not present any serious problem with present-day commercially available pickups, although a limiting temperature of 45 deg C is imposed from practical considerations. At a temperature greater than 55 deg C the Rochelle salt will disintegrate in its own water of crystallization. The life of a crystal at 45 deg C can be considered infinite. At 55 deg C it is of the order of 18 months, at 60 deg C it is about 14 days and at 65 deg C it is about 30 minutes. The above figures were taken with normal production crystals fitted into hermetically sealed production type pickups. The ultimate life of a Rochelle salt pickup under normal used conditions is determined by the care and control exercised in the initial fabrication of the crystal to the point when it is hermetically sealed. If the crystal is not hermetically sealed, the life is only a few hours under humidity conditions of 95 to 99 per cent relative humidity and if the crystal contains any excess moisture at the time of sealing, its life will be reduced. Normally, in the crystal fabrication shops, temperature and humidity are controlled at $21 \pm 1 \text{ deg C}$, $45 \pm 2 \text{ per cent r.h.}$ Under these conditions plain unprotected crystals can be stored indefinitely. Fig. 4 shows the relation between temperature and humidity for onset of dehydration, and beginning of solution, these being determined by (1) the point at which dehydration can be observed after 168 hours subjected to the conditions shown in the graph, and (2) in which the insulation resistance drops below 10,000 M Ω under the conditions specified. These curves are for unprotected, uncoated crystals.

Barium Titanate.—All the foregoing crystals (including quartz) can be grown from solution under carefully controlled conditions at temperatures between 25 deg C and 400 deg C, according to the type of crystal.³ The melting point of barium titanate is of the order of 1,500 deg C, and to the present date it has not been possible to grow pure barium titanate monocrystals larger than 1 or 2 mm side in commercial quantities. Barium titanate elements are, there-fore, produced by a sintering process in which the carefully prepared primary materials (usually barium carbonate and titanium dioxide), together with various admixtures, are either slip-cast as in traditional pottery manufacture or mixed with a binder such as Bentonite and pressed to form on a tableting machine. The "green" slab is then fired in a sintering furnace at a controlled temperature which results in the material becoming a homogeneous solid mass. The consistency of the barium titanate at the sintering temperature is little stiffer than jam, and unless care is taken considerable distortion usually takes place especially if elements are of large area, unsupported, or of thin cross-section: the shrinkage is large and where precise dimensions of the finished product are required the fired slabs must be ground to size. (Part of the secret of successful manufacture of barium titanate is in obtaining the correct temperature for the correct length of time, the rest being careful chemical control, applied force and classic learning.) The resultant slab is an aggregate of micro-crystals of barium titanate randomly oriented. Whilst each individual crystal is piezoelectric they mutually cancel and the material behaves as a dielectric of high permittivity, but if the plate is subjected to a high unidirectional potential gradient for a period and this potential is then removed, the material will appear to be piezoelectric, and the magnitude of this phenomenon will be a function of the polarizing potential gradient and time.

Fig. 5 shows the variation of coupling coefficient versus polarizing potential gradient for pure barium titanate when applied for about 1 hour at room temperature, the polarizing voltage may be reduced to about half of this value if applied at just above the Curie temperature (about 120 deg C) and allowed to cool to lower than 50 deg C with the potential still applied: but it is usual to apply the maximum field consistent with the elements not breaking down during the polarizing process.

Above the Curie temperature (120 deg C) the crystal has a cubic form, the eight corners of the cube being barium atoms (each barium atom is shared between eight adjacent cells). One oxygen atom occupies the centre of each of the six sides, and since each is shared with the adjacent cell there are three oxygen atoms. The titanium atom is in the centre of the cell and is relatively free to move within it. It will normally be in a "potential well" adjacent to one or other of the oxygen atoms, but if the thermal energy is sufficient it may jump from the neutral position of one oxygen atom to any of the other five in a completely random manner. At temperatures below 120 deg C, the titanium atom will move permanently towards one of the oxygen atoms, the cell will assume tetragonal form (actually the length will increase by about 1 per cent in the direction of the titanium atom movement). If the titanium atoms in sufficient adjacent cells are locked in the same direction a domain will be formed and will be ferro-electric. The crystals (and therefore the domains) are randomly oriented in the sintered aggregate and no residual polarization will occur, application of a unidirectional bias will result in more and more domains aligning themselves in the direction of the electrical field as it is increased. At maximum field strength (just below the breakdown point) about 10 per cent of the domains are aligned in the direction of the field, and the plate has expanded by about 6 parts in 10,000 in that direction. On removal of the polarizing field it will be found that the majority of the domains remain aligned in the preferred direction.

Application of alternating potential to the plate will cause it to alternatively expand and contract, the absolute value of this mechanical variation being proportional to the applied voltage. The mechanical movement is probably caused by the growth and contraction in the preferred direction of the aligned domains at the expense of their neighbours, rather than any reversal in the domains themselves. The mechanical strain is quite considerable and can be well in excess of the elastic strength of the material. It is interesting to note that crystals firmly cemented (with a thermo-setting resin) to a heavy metal support and then polarized inevitably shatter when the polarizing field exceeds about 20-25 volts per 0.001in.

Various additions are made to the pure barium titanium oxide to improve its properties. The addition of strontium will reduce the Curie point, whilst the addition of lead will increase it. One particular artifice is to add zirconium, which increases the lowtemperature transition point to a limit of approximately 45 deg C and which will give an enhanced "g" coefficient. This can be very important to gramophone pickup manufacturers, because it will result in a

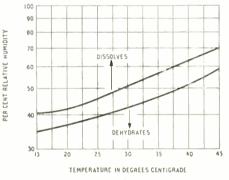


Fig. 4. Temperature and humidity in relation to the onset of dehydration and solution in Rochelle salt.

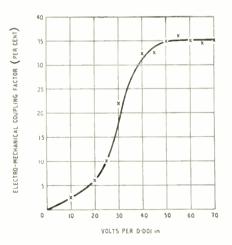


Fig. 5. Relation between potential gradient of polarization and electro-mechanical coupling factor in barium titanate.

WIRELESS WORLD, JUNE 1954

sensitivity gain of approximately 3 db at temperatures below 45 deg C, but if the crystal is subjected to temperatures above this limit the coupling will revert to the lower value.

As stated before, the asymmetry of barium titanate disappears above the upper Curie point (about 120 deg C) and if a pre-polarized barium titanate aggregate is subjected to temperatures above about 80 deg C it will tend to lose its polarization. It has been found that minor quantities of impurities adversely affect the life of barium titanate, in some cases reducing the sensitivity by 50 per cent in a matter of weeks or months; the effect is quite unpredictable and to eliminate it requires most careful chemical control. The addition of lead or calcium has the effect of "locking" the domains so that the stability of the crystal is considerably improved, especially when used as a driver. The manufacturers will usually guarantee the sensitivity of the element to deteriorate by not more than 10 per cent over a period of one year.

The maximum coupling coefficient figures for pure barium titanate of 0.35 measured under laboratory conditions are not realized in practice, a value of about 0.2 being usual. This is due to two causes: (a) an admixture of lead or calcium, and (b) either by reversed polarizing or subjecting the crystal to elevated temperature for a short while, in order to stabilize the element. Fig. 6 shows the temperature dependence of barium titanate. The anomaly at about +5 deg C shows up as a hysteresis loop of the dielectric constant, dissipation factor and voltage output ("g" coefficient). It will be seen from the middle curve that if the unit is polarized at a temperature lower than the discontinuity (Y) and the temperature is increased, the "g" coefficient will decrease to some value, and then if the temperature is reduced below the discontinuity point the lower value of "g" will be obtained (Z). The the addition of zirconium will increase the temperature of discontinuity to a maximum of approximately 45 deg C, whilst the addition of lead will reduce it to about -20 deg C. Calcium will reduce the discontinuity temperature to still lower values.

Unlike Rochelle salt and A.D.P., ceramic bimorphs at present available are in bender form only. The coupling coefficient (and hence the conversion efficiency) is much lower than Rochelle salt and A.D.P. but barium titanate has the advantages of a higher working temperature than Rochelle salt, a high permittivity (about five times that of Rochelle salt and 100 times A.D.P.) resulting in a lower electrical impedance than other crystals for a given size of plate, and a stable capacitance temperature performance together with improved humidity resistance characteristic. It is not by itself completely proof against humidity, in that the insulation resistance of the bimorph will be reduced under conditions of high humidity due to absorption of water vapour, although the crystal can easily be dried out.

Crystal Coefficients.—Crystals are anisotropic, that is the various electrical and mechanical properties are different in different directions of the crystal and are not constant in all directions as are those of isotropic materials. Of the 32 known crystal classes, 20 will show piezoelectric effects (which are due to lack of symmetry of the crystal), and depending on the crystal asymmetry they may have from 3-21 elastic constants. 0-18 piezoelectric constants, and 1-6 dielectric constants.1 Crystallographers refer these constants to the X, Y, and Z rectangular axes, and where crystals are cut at oblique axes (for instance, zero temperature coefficient cuts of quartz, etc.) transformation equations have been evolved by means of which the new constants can be calculated in terms of the standard constants."

TABLE 1 Comparative Table of Electromechanical Materials

Crystal and Mode	$\frac{\text{Strain out}}{\text{Field in}} d$	Dielectric Constant' «	Field_out Stress in g	Elastic Modulus Y	Coupling Coefficient $k = \sqrt{d.g.Y}$	Specific Gravity	Frequency Constant ¹ $\sqrt{Y} 4\rho$	Maximum operating temp. °C.
Rochelle salt (30°C.) X-cut expander Y-cut expander A.D.P. Expander and thickness Lithium sulphate Thickness D.K.T. Expander D.K.T. E.D.T. XY-cut expander Thickness Murmaline Thickness Multipliers- M.K.S. C.g.S,	165 27 24 2.3 16.0 11.0 11.3 1.93 190 78 10 ^{-1*} m, V 10 ^{-1*} cm, V	200 9.2 15.3 4.5 10.3 6.5 8.2 6.6 1700 1700	0.093 0.33 0.177 0.058 0.175 0.192 0.156 0.033 0.0125 0.0052 V.m Newton V.cm. 10 ⁻³ dyne	31.0 10.0 19.3 80 46 25 26 160 110 110 110 10 [*] Newton m [*] 10 ^{1*} dyne cm [*]	0.69 0.30 0.29 0.10 0.36 0.23 0.22 0.10 0.56 0.22	1.77 1.77 1.80 2.65 2.06 1.99 1.53 3.1 5.7 5.7	2100 1180 1630 2700 2360 1770 2050 3600 2250 c s. m. <u>kc s. cm</u> 10	45 120 550 75 110 100 1000 100

Relative to vacuum.

⁴ The density ρ should be given in kg m³ in the M.K.S. system and is obtained by multiplying the specific gravity by 1000. The frequency constant is then obtained in c,s. m = kc s. mm.

Note: Expander units are used for making bimorphs.

The various constants have now been more or less standardized and are shown on Table 1, which lists the major piezoelectric crystals currently available for commercial use. This table relates only to expander modes, expansion and compression of crystal elements taking place either parallel or at right angles to the applied electric fields, and covers only the more useful expander modes of these crystals.

The dielectric, piezoelectric and elastic constants are interrelated and are given below; in order to prevent misunderstanding of the terms "stress" and "strain," the following definition is used in this article:—

When a solid body is in equilibrium under a given system of externally impressed forces, its state of deformation is called a "strain," while the forces, which necessarily occur in equal and opposite pairs, give rise to a "stress."

"d" Coefficient, Column 1.-This expresses the strain obtained for an applied electric field strength and practically is the ratio of expansion of the plate for the voltage applied. The direction of the expansion (i.e., a contraction is a negative expansion) is directly dependent on the sign of the applied field. It is usually in a direction perpendicular to the applied field although in special cuts such as the "L" cut in Rochelle salt it can be parallel to it. This condition holds whether the applied voltage is direct or alternating. The instantaneous increase in length of the crystal will be directly proportional to the instantaneous applied voltage. In the case of ferro-electric crystals such as Rochelle salt at temperatures between the Curie points of -18 degC and +23.8 deg C, and barium titanate, it is not strictly true because of the phenomenon of ferroelectric hysteresis, but for a practical application, especially at low field strengths, this can be neglected.

Permittivity (Dielectric Constant) κ , Column 2 is the dielectric constant referred to a vacuum, and is independent of the intensity of the electric fields normally encountered, except in the case of Rochelle salt between the Curie points of $-18 \deg C$ and +23.8deg C where the material is ferro-electric and is voltage sensitive. The Rochelle salt values given are for weak fields and are applicable where the crystal is used as a voltage generator such as a gramophone pickup or microphone.

"g' " Coefficient, Column 3. This coefficient represents the open circuit voltage per unit applied force. If a unit step function of force is applied the instantaneous voltage developed will be proportional to this force, but this voltage will then decrease in an exponential manner, with time, dependent on the leakage resistance across the terminals and the capacity of the crystal (see Fig. 7). As a matter of interest, under conditions of very low humidity and extreme care being taken with the insulation and mounting of the crystal, Rochelle salt bimorphs have still shown 60 per cent of their peak voltage several minutes after the step function has been applied. When an alternating force is applied, the instantaneous open circuit voltage is proportional to the instantaneous applied force. This is one of the most important coefficients in the design of transducers, because it specifies the maximum available voltage under known working conditions.

In the case of a gramophone pickup the maximum available force is of the order of a 5×10^{-2} Newtons and for a microphone is usually about 10^{-3} Newtons (a Newton is 10^{5} dynes). This constant thus gives a direct comparison of the voltage sensitivity of the


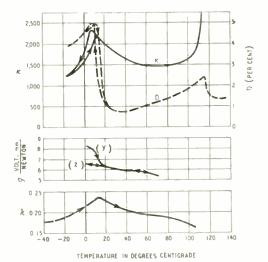


Fig. 6. Temperature dependence in barium titanate of dielectric constant (κ), dissipation factor(D), voltage output coefficient (g) and electro-mechanical coupling coefficient (k).

Fig. 7. The voltage developed by a step function of force will decay due to the finite resistance of the crystal.

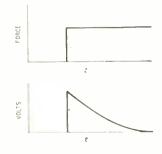

various materials, always assuming, of course, that the plates of the various materials being compared are identical in size.

Young's Modulus, Column 4. This is for the particular crystal cut stated. It is an important coefficient because it will decide the low-frequency impedance of the final crystal unit, in general a low value of Y is preferred.

Coupling Coefficient k, Column 5. By definition, a transducer is a converter of one form of energy to another and in the case of crystals the two forms of energy are electrical and mechanical. The electrical constants of the crystal will therefore be a function of the mechanical loading applied to it and vice versa. For example, if the crystal is firmly clamped so that it cannot possibly move and the dielectric constant of the crystal is measured, one obtains the minimum electrical capacitance of the crystal. If the tightness of the clamp is reduced some additional energy will be stored in mechanical form and the measured dielectric constant will have increased. Ultimately, where the crystal is completely free to move, the maximum quantity of mechanical energy will be stored and this is commonly called the free dielectric constant. The ratio of the clamped and free dielectric constants is determined by the coupling coefficient k; it is defined as the square root of the ratio of total energy stored in mechanical form to the total electrical energy absorbed by the crystal. The following equation gives the rela-

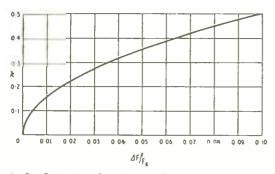


Fig. 8. Derivation of coupling coefficient from the relationship of the resonant frequencies of the freely suspended crystal.

tions where the values d, κ and Y are as defined above : ---

$$k = \sqrt{\frac{\frac{d}{\kappa}}{4\pi Y}}$$

An alternative way of obtaining the coupling coefficient is : ---

$$k = \sqrt{d.g.}\overline{Y}$$

The simplest method of measuring this parameter is by measuring the resonant and anti-resonant frequencies of the crystal; and the relation between the coupling coefficient and these frequencies with an accuracy sufficient for practical purposes is : -

$$k = 1.58 \sqrt{\frac{\Delta F}{F_{B}}}$$

where F is the resonant frequency and ΔF is the difference between the resonant and anti-resonant

frequencies. The graph of Fig. 8 plots this equation. Several precautions must be taken during the measurements. The crystal must be freely suspended, preferably at its nodal point and the source impedance of the electrical generator must be extremely high and preferably resistive in order that electrical loading effects be reduced to negligible proportions.

When comparing the "goodness" of two different crystal materials, this coefficient is usually the first to be considered. In the case of barium titanate, the final efficiency of the product is controlled to a large extent by the manufacturing processes rather than an inherent quality of the crystal, as in classic crystals such as Rochelle salt or quartz, and the coupling coefficient is the parameter often used for quality control of the various production processes.

Columns 6 and 7 show the density and the frequency constants, whilst Column 8 is the maximum operating temperature. The frequency constant relates the resonant frequency and length of the freely suspended crystal when in longitudinal vibration.

As before stated, the table relates to single plate units, but for pickup engineering applications the mechanical impedence of these plates is too great; the bimorph construction is usually used in order to achieve reasonably low working mechanical impedances.

(To be concluded)

References ¹ "Oeuvres de Pierre Curie." Gautier-Villars (Paris) (1908), pp. 200-205. ² "Piezoelectric Crystals and their Application to Ultra-

sonics." W. P. Mason (van Nostrand), pp. 165-189. ³ "Crystal Growth." H. E. Buckley (Chapman and

Hall), pp. 43-71. ⁴ "Piezoelectricity." W. G. Cady (McGraw Hill), pp.

17-21. ⁵ "Piezoelectric Crystals and their Application to Ultrasonics." W. P. Mason (van Nostrand), pp. 443-461. ⁶ "The M.K.S. System of Units." T. McGreevy

SMALL-CRAFT RADIO

The converted 60-ft lifeboat " Aries," which, with a crew of four, is making a double crossing of the Atlantic, has been fitted with Admiralty - type communication equipment. Sub. Lt. E. Skelton, R.N.V.W.R. (G3JOQ), is shown in this Wireless World photograph at the controls of the 15-W m.f. (330-550 kc/s) section of the Type 619 transmitter. The 40watt h.f. section (1.5-16 Mc,s) is on the right and in the centre is the receiver, Type CAT, which covers 60 kc/s to 32 Mc/s in eight steps. The power pack is under the desk. The installation was carried out by Rees Mace who also fitted a Pye PTC117 a.m. radio-telephone transmitter-receiver operating on 121.5 Mc/s in the wheelhouse for communication with aircraft.



WIRELESS WORLD, JUNE 1954

LETTERS EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

Relaxation Oscillators

IT is pointed out to me by W. T. Cocking that I was in error in saying that a certain dynatron charac-teristic had d.c. negative resistance.* He reminds me that d.c. resistance can only be negative when the ratio of applied direct voltage to direct current is negative, as it can be in those dynatrons whose anode current is negative over a certain range of anode voltage (but not in the example I showed). Over this range of negative current, the a.c. resistance is first negative and then positive, and if the valve is operated in the positive-a.c. negative-d.c. region it delivers d.c. power to the load and anode-voltage source.

I entirely agree that this is the only strictly correct interpretation of "d.c. negative resistance," and it seems that I myself was caught in one of the meshes of the trap I have so often warned others about-the anomalous terms with which our craft is littered. As a sop to common usage (or perhaps through sheer forgetfulness!) I wrote "d.c." when I ought to have stuck to my principles and made it "z.f." Appeasement is a rotten policy!

The distinction I was trying to show between the dynatron and most other negative-resistance devices (transitron, back-coupled valves, etc.) is analogous to that between "d.c. amplifiers" and "a.c. amplifiers." "A.c. amplifiers" have reactive couplings which prevent them from holding indefinitely a changed steady output current or voltage caused by a similar but smaller change at the Transitrons and back-coupled valves likewise input. have reactive couplings that prevent a positive increase in steady potential from causing a steady negative in-crease in current. The negative resistance of a dynatron, on the other hand, is analogous to the amplification of a "d.c. amplifier." In the same way that my expression "d.c. negative resistance" was wrong, so is everybody's "d.c. amplifier." Apart from the fact that most so-called d.c. amplifiers are not current amplifiers at all, the ratio of steady output current (or voltage) to input is, in general, not equal to the amplification.

Even if no one was actually misled by my common but wrong use of "d.c.," I ought to have called the peculiar dynatron characteristic "z.f. a.c. negative resistance "—to signify a.c. negative resistance at fre-quency indefinitely close to zero. I hope that would satisfy even the rigorous mathematicians!

E. F. Good raises an objection to the last paragraph of the same article, in which I included sinusoidal RC oscillators in the relaxation category. While sharing with him and apparently other readers a feeling that this is not quite right, I am unrepentant. First, because in this matter I was following B. van der Pol, whom one would hesitate to contradict on the subject of relaxation oscillators; and, secondly, because if one denies that RC sinusoidal oscillators are relaxation oscillators one is faced with the awkward obligation of specifying precisely when they turn into relaxation oscillators as the negative feedback is progressively increased.

"CATHODE RAY."

* "Relaxation Oscillators," Wireless World. April, 1954, p. 195.

Marine V.II.F. Telephony

WITH reference to your Editorial in the February issue of Wireless World, may I call your attention to a letter written by me to the Editor of Wireless Engineer and published in October, 1940, on the use of double modulation on v.h.f. transmissions?

I suggest that it should be fairly simple to provide for

marine v.h.f. transmitters to be modulated either in the f.m. or a.m. mode as required, and many receivers are now available which can be switched to receive either f.m. or a.m. as required.


It is interesting to note that this double-modulation method of providing stereophonic or binaural broadcast-ing is now being used in the U.S.A., as reported in Electronics, February, 1954, issue.

I am rather surprised that the B.B.C. has not made use of this method to permit either binaural transmission from the Wrotham station or to enable receivers capable of receiving on a.m. only to sample the advantage of v.h.f. broadcasting. Port Moresby, Papua.

W. C. GEE.

Williamson Tone Compensating Unit

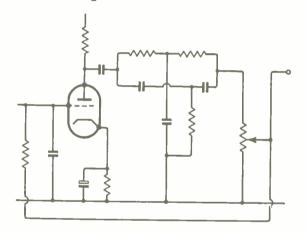JOHN J. CLARK suggests (April issue, p. 177) that the slope can be varied by adjusting the loop gain, but as C. Robinson points out (May issue, p. 224), the suggested modification will affect the overall gain of the



amplifier. One way to overcome this defect is to take the output from the potentiometer tap, so that the proportion of the output fed back to the input remains constant, whilst the gain within the loop varies. constant, whilst the gain within the loop varies. This gives a constant overall gain for most settings of the potentiometer, but varies the rate at which the gain falls off near the "cut-off point."

Whitton, Middx. G. A. ASKEW

Undecoupled?

WHY should L. Bainbridge-Bell (May issue) pick on "decoupling to" for his criticism? There are hundreds of other equally offensive (to the grammarian) terms in the electronics world, let alone in others. He also infers that "decoupling to cathode" is somehow worse (grammatically) than "decoupling to earth." Indeed, if we have an h.t. supply of zero a.c. impedance, we

could profitably decouple a screen-grid h.t. supply to h.t.! The difference between "couple" and "decouple" is simply one of purpose. A coupling capacitor (sic; no steam engines in my equipment!) does not remove a.c. fluctuations from an anode, whereas a decoupling capacitor would (since we always make our measure-ments with respect to earth). Does Mr. Bainbridge-Bell's "grid leak" allow the inside of his valve to spill all over the chassis? What memorandum about gramophones does a "gramophone record" contain? Would a "four-stroke" make a cat purr?

On another topic, with regard to "Cathode Ray's" helpful suggestions concerning baby alarms; why trouble the poor baby-sitter all the time. For most of the infant's needs, a "tele-film," shown on a screen near the cot, to be triggered by the baby-cry-analyser, of the infant's mother making suitable area and the infant's mother making suitable goo-goo noises is all that is needed. Only for very urgent needs would the babysitter's viewing be disturbed at all.

KEITH A. M. HARDISTY. Cambridge.

Plug-and-Socketry

MAY an overseas reader express an unavoidably_delayed opinion on the article by C. Lister in your February issue? Party No. I seems to have the better system of names. The fact that the pins of some chassis or panel mounting plugs are recessed out of harm's way does not turn such plugs into sockets. The pins of others are not recessed and the mating cord socket remains wholly outside the panel when contact is made. Surely Mr. Lister has forgotten that household necessity, the "long cord," which comes out when an appliance is to be used at some distance from the nearest wall socket. In this case Party No. 2 would have a plug fitting into a plug. If Mr. Lister dislikes "*n*-pin plug" he could always say "*n*-contact plug," but one feels that objection to the former on the grounds of redundancy is rather like being horrified at every split infinitive.

Mr. Lister has my warm approval, however, in ventilat-ing this matter. Though only an occasional buyer, I am often irritated at the inadequate or misleading descriptions of their wares given by some of your advertisers. One employs the term "motor" in two senses, (a) motor only, and (b) motor plus turntable, in the same advertisement. Again, if a meter or fuse-holder is not panel mounting, should it be allowed to hang freely from the chassis at the ends of its leads? "Surface mounting" or "flush mounting" gets rid of that uncertainty which is the real gravamen of my reproach. There is no way of knowing how many actual or potential customers in this country are affected but, doubless, few would notice the redundancies were it not for the three weeks' wait and half-crown that it costs to find out by air mail what the advertiser really means. Manufacturers' catalogues are not always helpful even when they are available. Dunedin, New Zealand. S. G. EM

S. G. EMSLIE.

Television Convertors

THE Band III convertor described by G. H. Russell in your May issue offers an attractive solution to the conversion problem, but it seems doubtful if such a simple device could give an adequate performance in most areas. No amount of filtering in the convertor could cut out direct pick-up of a strong Band I signal by a sensitive receiver tuned to it, unless the receiver were very well screened. Few commercial sets are, and patterns due to beating between carriers would be inevitable.

Furthermore, with two local oscillators running, one in the convertor and one in the set, an almost infinite number of beats can be found to exist between their harmonics, sufficiently close to the carrier in Band III, Band I or the i.f., to cause patterning.

Oscillator stability is a big problem in Band III fre-quency changers, and if the two oscillator drift errors add, which is not unlikely, very poor tuning stability would result. A far less hazardous conversion would be to change

the Band III signal straight down to the receiver i.f. and to link-couple it into the first i.f. transformer of the i.f. strip, switching from Band I to Band III simply by switching the h.t. from one "front end" to the other. Some adjustment of the tuning of this transformer would be necessary to restore the i.f. curve to its original shape, but this should not prove difficult.

Salford, Lancs. R. WARD.

Die Castings

I WAS very interested to read your account of the B.S.I. Certification Scheme for zinc alloy die castings which appeared in the April issue. This scheme should encourage the wider use of high-quality die castings in industries such as your own.

Your comparison between zinc alloy die castings and cast iron may, however, give your readers a wrong impression, since the tables published in BS1004 give figures for the tensile strength of zinc alloy die cast test pieces ranging from 16 to 20 tons per square inch. These figures compare more than favourably with the average tensile strengths of ordinary iron castings, which range

from 10 to 12 tons per square inch. The value of zinc alloy die castings lies not only in the high strength of the material, but in the intricate shapes which can be mass-produced with high dimensional accuracy. The new Licence Scheme will no doubt encourage many manufacturers in the telecommunications industry to make further use of certified zinc alloy die RONALD W. BAILEY, castings.

Zinc Alloy Die Casters Association.

" Cascode "

Oxford.

THE recently developed series-connected twin-triode r.f. amplifier which, with the advent of Band III frequencies has a particular application in television receivers, is repeatedly referred to, in and out of the literature, as a cascode circuit. This confuses with the original cascode circuit by Wallman, which used parallelconnected triodes to h.t.

The new circuit affords a distinct advantage to the original by the extended grid base obtained by series connection, minimizing cross-modulation of the vision and accompanying sound signals. Also the original cascode employed a frequency-selective neutralizing circuit, whereas the grounded cathode triode of the series-connected amplifier generally includes a neutralizing capacitive bridge, with balance independent of frequency.

These differences would indicate the need for a more positive identification of the new circuit. "Extended Base Cascode" would identify one merit, but does not embrace the second.

The American 6BQ7 when used similarly is identified as a "Driven Grounded Grid R.F. Amplifier" which is to be commended more than the loosely used cascode identity.

Colwyn Bay.

S. L. FIFE.

Transistor Applications

THE exploitation of any new device is nowhere more rapid than in the U.S.A., and the transistor is no excep-tion. According to the April, 1954 *Electronics* a tran-sistor pre-amplifier is now embodied in a hand-type moving-coil microphone, its use lifting the output to about the level of that of a carbon type. It is said that the background noise is considerably reduced.

A carrier telephone system which employs some 300 transistors has been installed in a rural area. It covers 26 miles or so of country, includes three terminal units and, several repeater amplifiers, and the use of transistors is said to reduce the size of these equipments to 1/10th and the power requirements to 1/20th of that of valve equipment.

WIRELESS WORLD, JUNE 1954



New Licence Regulations

Amending Transmitting and Receiving Licences

NDER the 1949 Wireless Telegraphy Act, and its extensions covering the Channel Islands and the Isle of Man, the Postmaster-General is empowered to make such regulations as are necessary to licence transmitting and receiving stations. No such regulations regarding fees had been made until April 5th when two Statutory Instruments* covering broadcast receiving licences and sundry transmitting licences were laid before Parliament. They are scheduled to come into operation on June 1st. Co-incident with the introduction of these new fees the P.M.G. has revised some of the regulations covering the issue of licences.

So far as broadcast receiving licences are concerned the main changes are in the fees payable. As has already been announced in Parliament, television receiving licences are to cost £3 per annum. In the past an hotel has been licensed as a single household, irrespective of the number of rooms equipped for radio reception, but the new regulations provide for licences for hotels at £1 (sound) and £3 (sound and vision) for each room equipped.

On the transmitting licence side there have been many changes. In general the technical requirements are more stringent except that for amateurs there has been an easing of restrictions. There have been a number of changes in the charges for transmitting licences—both increases and decreases—which, incidentally, are based on the estimated administrative costs for the various classes of licence. It is the intention of the P.M.G. to issue the new licences on the first renewal after the introduction of the new regulations and charges on June 1st.

Mobile Radio

To ensure that these new Statutory Instruments are fully discussed in the House of Commons, Capt. L. P. S. Orr, M.P., who is chairman of the Mobile Radio Users' Association, has announced that he is putting down a Prayer for their annulment. The question of the legality of the original charge for mobile radio licences is, as already reported,[†] being contested by one user who has served a writ on the Post Office. It is also claimed that some of the regulations laid down in the licences are contrary to the provisions of the Wireless Telegraphy Act.

Now for the details of the new transmitting licences. Brief descriptions are given in S.I. 1954/439 of seventeen different types of licence, but this is not a complete list, for there are in addition a number of special licences; in fact there are some cases where there is only one licence in existence. In other cases, such as that for the radio control of industrial equipment and telemetering, new licence regulations are in course of preparation.

On perusing the provisions of the new "private

WIRELESS WORLD, JUNE 1954

mobile radio licence," which will supersede the business radio licence, the technical requirements appear to be more stringent. On investigation, however, it will be found that the technical limitations laid down, which were not included in the old licence, are, in fact, a reiteration of the P.M.G.'s specification issued to manufacturers for the type-approval of their equipment. The licence charges have been reduced from £5 to £3 per transmitter and a composite licence for all the stations in a network will be issued. It is something of an anomaly that whereas ambulance services come under the "private mobile radio" category and will pay the £3 fee, there is a separate "police and fire service" licence for which the fee is £2 p.a. for each fixed station, irrespective of the number of mobile transmitters used.

Amateur Sound and Vision

Instead of the previous arrangement whereby charges for amateur sound transmitting licences varied according to the power of the station (10 W, \pounds 1; 25 W, 30s; over 25 W, \pounds 2 p.a.) the new regulations provide for a uniform fee of \pounds 2 p.a. The initial charge of 10s or \pounds 1 according to the radiated power will no longer be made. Operators may not at present use portable equipment or operate from an alternative address without first applying to the Post Office and the charges for "P" or "A" operation have been 10s each. Under the new regulations operation from a temporary alternative address or location is covered by the main licence. Provided the periods of "P" or "A" operation do not exceed four consecutive weeks the Post Office will not need to be notified.

A "sound mobile licence" which is supplementary to the main amateur transmitting licence will in future be available for $\pounds 1$ and this will permit the licensee to operate in a vehicle or vessel. Amateur equipment, whether mobile or fixed, may not be used at sea or within any estuary, dock or harbour.

The P.M.G. is introducing the award of a certificate (Amateur Radio Certificate) which will be granted to those who pass the City and Guilds Radio Amateur Examination and a 12-w.p.m. morse test. Holders will be permitted to operate a transmitter under the supervision of a licensed operator without themselves holding a licence.

A licence to operate an amateur television station will in future cost $\pounds 2$ instead of $\pounds 3$, and as at present, it limits transmission to visual images. An operator may send his call in morse but to radiate sound he will also need an amateur sound licence.

A licence for the radio control of models is provided for in the new regulations. This costs $\pounds 1$ for five years. The operator will not have to pass a test.

There will in future be a "training establishment licence" (£2 for five years) which will permit the establishment of a transmitting and receiving station for "wireless telegraphy" which, within the meaning of the Wireless Telegraphy Act, covers radar.

^{*} S.I. 1954/438 "The Wireless Telegraphy (Broadcast Licence Charges) Regulations" (4d) and S.I. 1954/439 "The Wireless Telegraphy (General Licence Charges) Regulations" (6d), H.M.S.O. † Wireless World, March, 1954, p. 124.

The Diode Rectifier in Valve Voltmeters By M. G. SCROGGIE, B.Sc., M.I.E.E.

Limitations of Use Imposed by Specified Maximum Error

HE majority of valve voltmeters for alternating voltages use a diode rectifier followed by what may be called a current amplifier or direct-voltage valve voltmeter. A previous article1 reviewed the whole design of this rectifier circuit, including methods for dealing with its non-linearity, which of course is of chief importance at low voltages. The present article is confined to causes of error other than non-linearity, and has especially in view (though not exclusively) use at frequencies lower than r.f. At such frequencies one reasonably expects a fairly high standard of accuracy to be attainable. On the other hand, the sources of voltage being measured are unlikely to be low-loss tuned circuits, and, as was emphasized previously, when a non-resonant source is being measured the error due to diode loading is appreciable with much less source resistance than is often supposed, especially when one is accustomed to using the instrument across r.f. tuned circuits. For 1 per cent error, say, a diode voltmeter with a load resistance of $1 \text{ M}\Omega$ is actually worse than an ordinary 1,000-ohmsper-volt metal-rectifier meter on a 50-V or higher range!

With an ordinary voltmeter, the source-resistance error can be calculated from the voltmeter resistance. In one way of looking at the matter, this resistance and the resistance of the source of voltage form a potential divider as in Fig. 1, and the voltage actually read (assuming the meter otherwise free from error)

 $\frac{R_m}{R_m + R_s} \frac{E}{E}$ instead of E. An error of x per cent

is caused by R, when it is x per cent of $R_m + R_s$, or (assuming x is reasonably small) very nearly x per cent of R_m . If R_m were 50,000 Ω , for example, and the maximum source-resistance error tolerated were 1 per cent, the maximum source resistance that need not be corrected for would be just over 500 Ω .

An alternative viewpoint that shows the same result is to suppose that the voltage to be measured is due to a constant current I flowing through the source resistance. It is therefore equal to IR_s . When the meter is connected, the resistance through which I passes is R_s and R_m in parallel, i.e. $R_m R_s ((R_m + R_s))$. The ratio of voltage read to voltage before the meter

 R_{m} as before. was connected is therefore $R_m = R_s$ as before. If one seeks to apply this calculation to a diode voltmeter the question at once arises, where is R_m? And if the voltage being measured is across a tuned circuit there may also be doubt about R₃. One thing that must not be done is to work on the assumption that R_m is the load resistance of the diode, i.e. the resistance across which the rectified voltage is developed -R in Fig. 2. In general one cannot regard the

Wireless World, March 1952, pp. 89-94.

rectifier as equivalent to an ordinary resistance, for during the greater part of each cycle of the input voltage the diode is non-conducting so that the rectifier as a whole is an open circuit and imposes little or no load on the voltage source, while during the remainder of the cycle it is conducting and passing a relatively heavy current into the capacitor C. Notwithstanding this, however, it is found that in the special case of the source of voltage being a resonant circuit the damping effect of connecting the rectifier across it is equivalent to that of an ordinary resistance. The reason is that the flywheel effect of the stored energy in the resonant circuit maintains its pure voltage waveform in spite of the great variability of the load across it.

Effective Input Resistance

It is sometimes stated that the value of this equivalent resistance, which we shall call R,-the effective input resistance of the rectifier, or the resistance which, if substituted for the rectifier, would draw from the voltage source the same amount of energy during each cycle-is half the diode load resistance (R). But it is not always made clear at the same time that this is not even approximately true if the input voltage is small or the source-resistance error is large, and that it applies only to the series-diode circuit, Fig. 2(a). \mathbf{R}_i varies with input voltage, because at very small inputs a diode is far from being a perfect rectifier. Throughout this article, however, we shall assume that the input is sufficient (say at least several volts) for the performance of actual diodes to be not greatly different from that of an ideal diode having infinite resistance when the anode is negative with respect to the cathode and either zero or a constant small resistance when it is positive. If for the moment we also assume that the Fig. 2(a) circuit is used, with no source resistance, then V_r , the rectified output across R, is equal to the peak value of the sinusoidal input voltage. Since the forward resistance of the diode is assumed zero and its backward resistance is infinite, R is the only power-dissipating element in the circuit, the power being V_r^2 R. This must be equal to the input power, which by definition of R_i is E_{rms}^2/R_i . Since the peak value, $E_{max} = \sqrt{2} E_{rms} = V_r$, $E_{rms}^2 = V_r^2$, so $R_r = R_2$. In practice this theoretical value is a reasonably good approximation when the input voltage is at least a few volts and there is no series resistance other than a low-resistance diodein other words, conditions are such that V_r is not more than one or two per cent less than E_{max} .

In Fig. 2(a), R is shut off from E by the non-conducting series diode for almost the whole of every cycle, but in the shunt-diode circuit, Fig. 2(b), a.c. is driven through R by E all the time (the impedance of

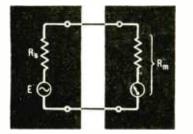


Fig. 1. Diagram representing a source of voltage as an e.m.f. E in series with internal resistance R., being measured by a voltmeter with resistance R....

C being assumed negligible), so R_i in this case is equivalent to R'2 in parallel with R; i.e., R 3.

To prevent the alternating voltage across R in the shunt circuit from being passed on, some kind of simple filter is usually employed, perhaps the com-monest being as in Fig. 2(c) or (d). If the impedances of C1 and C2 are negligible in comparison with the resistances, it can easily be found in the same wayby reckoning the d.c. and a.c. resistances in parallelthat in Fig. 2(c) $R_i = \frac{R_1 R_2}{R_1 + 3R_2}$, and in Fig. 2(d) it is

 $(R_1 + R_2)R_2$. In both circuits it is assumed that there

is no current path between the output terminals other than those shown. To make the output in Fig. 2(d) equal to the r.m.s. value of sinusoidal E, $(R_1 + R_2)$ must be about equal to $\sqrt{2} R_1$, in which case $R_i = R_1/3.83 = R_2/1.59 - (R_1 + R_2)/5.42$. And if in (c) $R_1 = R_2$, $R_i - R_1 = R_2/4 - (R_1 + R_2)/2$. All these, of course, are subject to the assumptions made; with large input voltages the actual R_i tends towards these figures, but around bottom-bend level the whole matter becomes far more complicated. In general, R_i is greater (loss smaller) at small input voltages in the series circuit (a), and less in the shunt circuit, than large-voltage values. At high frequencies the additional losses in the capacitances may be serious and would have to be taken into account in any accurate evaluation of

R_i. The importance of R_i is that when it comes across a resonant circuit it reduces that circuit's dynamic resistance (which we shall call R₂). The voltage developed across the circuit by a given e.m.f. or current is proportional to the dynamic resistance. So the ratio of voltage with the rectifier connected to the voltage without the rectifier is $R_{i}R_{r}$ ($R_{i} + R_{r}$) to R_{i} ,

Fig. 2. The four types of diode rectifier considered. (a) is the series-diode type, (b) the simple shunt-diode, and (c) and (d) are shunt-diode circuits with two varieties of simple filter for removing the a.v. component from the output.


WIRELESS WORLD, JUNE 1954

or $R_{1}(R)$ R_r) to one. In other words, the calculation is exactly the same as for an ordinary meter, Fig. 1, R, now taking the place of R_m, and R_r the place of R.. For example, if a series-diode voltmeter with a load resistance R of $3M\Omega$ were used to measure the voltage across a resonant circuit with a dynamic resistance of $80 \text{ k}\Omega$, R₁ would be 1,500 k Ω , so the factor by which the voltage was reduced by the meter would be approximately 1500 1580 - 0.95; i.e., 5 per cent error. The desirability of making R_i large is especially great in the valve voltmeter used to indicate Q in the

usual type of Q meter measurement, for this damping error directly affects the readings and is not cancelled out as in the reactance-variation method.

Peak Clipping

So much for measurements on resonant circuits. From now on we shall assume that the source of voltage can be represented, as in Fig. 1, by an e.m.f. E in series with a resistance-the source resistance R_s. Such a source has no stored energy to meet the relatively heavy demand at the positive peak of each cycle, when the diode is conducting; consequently the positive peaks-which are what the diode voltmeter measures-are clipped short and the readings are low. If R_s and the forward resistance of the diode (r_n) were nil, C or C, in all the circuits in Fig. 2 would charge up to the full peak value, E_{max} . To do this, the portion of each cycle during which the diode conducted would have to be infinitesimally small and the current infinitely great, so even a very small value of $\mathbf{R}_s = r_a$ is sufficient to modify the situation considerably. If we restrict the error due to it to, say, 1 per cent, so that V_r is only 1 per cent less than E_{max} , the period of diode conduction cannot extend far each side of the positive peak; and since during this brief period C has to take in enough charge to feed R for the whole cycle, the charging current is bound to be relatively heavy. To restrict the voltage dropped in R, by this heavy current to 1 per cent of E_{max}, it is

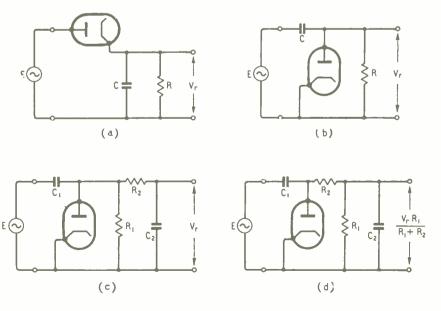

285

obvious that R_s must be very small compared with R, which carries a far smaller current.

In the article previously referred to there was a curve, due to D. A. Bell², showing how the "efficiency of rectification," V_r/E_{max} , varies with R_s/R . Although one could see from this curve that an efficiency of 99 per cent (i.e., error 1 per cent) necessitated R, being a very small fraction of R, the scale was such that it was very difficult to see even roughly how small. One object of the present article will be to remedy this by showing the upper part of the curve on a larger scale. Another object is to take account of the value of C on the small errors. But the main object is to extend the information, hitherto available only for the series-diode circuit, to the shunt circuit and the variants shown in Fig. 2. While a very large amount of information has been published on the series circuit, the shunt circuit seems to have been almost Admittedly the series circuit performs ignored. better in nearly every respect, but for use in measuring instruments it is not generally so convenient as the shunt circuit. Even data about Fig. 2(b) do not really meet the need, because in order to keep the following amplifier from being overloaded by a.c. the circuits used in practice are more likely to be (c) or (d), and what then is the load resistance?

(To be Concluded)

² Wireless Engineer, Oct. 1941, pp. 395-404. Actually a similar calculation had been presented, slightly differently, by F. M. Colebrook eleven years earlier (Wireless Engineer, Nov. 1930, pp. 595-603).



Aerial scanner of R.C.A. lightweight search radar being installed in plastic nose radome of Boeing 80-ton "Stratofreighter." Now a standard fitting in these aircraft, it can be used to locate storm fronts, as a collision warning device and as a navigational aid, by showing up prominent land features. Two display indicators are fitted, one shared by pilot and co-pilot and the other for the navigator, who also controls the equipment's various functions.

News from the Clubs

Birmingham.—June meetings of the Slade Radio Society include a talk on "Receiver Design" by G. Nicholson (11th) and another on "Servicing Car Radio" by W. E. Lewis (25th). The second of the season's events for the Harcourt Trophy will be a midnight d.f. test on the 12th/13th. The society meets at the Church House, High Street, Erdington, on alternate Fridays at 7.45. Sec.t C. N. Smart, 110, Woolmore Road, Erdington, Birmingham, 23.

Brighton and District Radio Club continues to meet each Tuesday at 7.30 at the Eagle Inn, Gloucester Road, Brighton. The club transmitter (G3EVE) is on the air on 80 and 160 metres (phone and c.w.) on some Tuesdays. A quantity of components has been acquired and it is proposed to start an "assisted constructional scheme" to help young members in building their equipment. Sec.: T. J. Huggett, 15, Waverley Crescent, Brighton, Sussex.

Hastings.—The Hastings and District Amateur Radio Club will again be exhibiting at the Hobbies and Crafts Exhibition in the New Pavilion, Falaise Road, Hastings, during the town's Carnival Week (July 3rd-10th). The club station, G6HH/A, will be manned during the exhibition from 10.00 to 22.00 each day except Sunday, July 4th, and will operate in the 80-metre band. Amateurs are invited to arrange schedules. Sec.: W. E. Thompson, 8, Coventry Road, St. Leonards-on-Sea, Sussex.

QRP.—The QRP Society is organizing a campaign to encourage the use of low power by all stations participating in local nets. The society considers that there is no justification for stations to use 150 watts when 5W will adequately cover the neighbourhood. The society would like to hear from clubs interested in QRP with a view to organizing contests and trials. Sec.: J. Whitehead, 92, Rydens Avenue, Walton-on-Thames, Surrey.

Commercial Literature

Measuring Instruments, including signal generators, valvevoltmeters, Q-meters, frequency meters, bridges and microwave test equipment, described in a 1954 catalogue of 200 pages, handsomely bound and illustrated, from Marconi Instruments, Longacres, St. Albans, Herts. A functional diagram accompanies the description of each instrument.

Power Resistors, wire-wound, with values from 10 to $30,000 \ \Omega$ and power ratings from 10 to 40 watts. Leaflet from R.M. Electric, Team Valley, Gateshead 11, Co. Durham.

Lead-through Capacitors, Hi-k miniature ceramic types, for Band III and IV television tuners. Also Hi-k ceramic disc capacitors for decoupling in television receivers. Two technical bulletins from The Telegraph Condenser Company, North Acton, London, W.3.

Slotted Angle Strips in steel for Meccano-type construction of racks, frames, etc. Leafle's from Dexion, Triumph House, 189, Regent Street, London, W.1.

Voltage Stabilizer with output voltage continuously variable between 200 and 240 volts and maintained to within 0.25%. Input voltage variation possible is $-17\frac{1}{2}$ % to $+6\frac{1}{2}$ %. Leaflet from Servomex Controls, Crowborough Hill, Jarvis Brook, Sussex.

Miniature Soldering Irons of the pencil type made by Oryx. One model, for 6-volt operation, gives a high bit temperature of almost 400°C; another, already supplied for 6-, 12- and 24-volt working, is now available for 50 volts. Leaflet from Anglo-Netherland Technical Exchange, 3, Tower Hill, London, E.C.3.

Encapsulation of small units in suitable potting resins: a service offered by Lion Switchgear and described in a leaflet from their Works at Hanworth Trading Estate, Hampton Road, Feltham, Middx.

Components and Accessories; an information folder for insertion in their catalogue from Webb's Radio, 14, Soho Street, London, W.1.

High-Fidelity Audio Amplifier of 12 watts output, substantially flat from 2 c/s to 160 kc/s, with negative feedback of 26 db and distortion of less than 0.1_{0}° . Also a pre-amplifier and remote control unit for use with it. Specifications on a leaflet from Pye, St. Andrews Road, Cambridge.

WIRELESS WORLD, JUNE 1954

French Components Show, 1954

Preponderance of Electronic and Television Equipment

By E. AISBERG*

DINCE the world's first components exhibition was staged in Paris in 1934, the area covered by the "Salon de la Pièce Détachée" has grown from 600 to 6,000 sq. metres. Like its British counterpart, the R.E.C.M.F. show, the French Salon confines itself to components, accessories and measuring instruments produced by the home industry.


Three main tendencies were in evidence this year. First and foremost, equipment for professional and industrial use took pride of place. What was at one time essentially a radio show has become an exhibition of general electronics. No doubt the heavy demands imposed on the French industry by the armed Services are responsible for this tendency, and, as a result, technical considerations are becoming of greater importance than purely commercial ones. Now that supplies are plentiful, choice is determined largely by quality, but of course price is important in components for broadcast receivers, both sound and vision. Lastly there is a trend, more and more in evidence, towards the production of many new television components.

Sound Broadcast Equipment.—Since March 28th the Paris f.m. station, which had previously been conducting low-power experimental transmission, has been regularly at work on 96.1 Mc/s with a power output of 20 kW. The coming of f.m. has been responsible for some novelties amongst components. Several coil manufacturers have produced special assemblies for the 90-Mc/s frequency band, as well as wide-band i.f. transformers and windings for discriminator circuits.

* Editor, Toute la Radio.



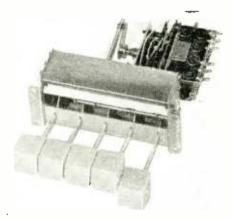"Rabbit's-ear" dual loudspeaker with one operative and one passive unit. (Elipson).




Device to enable a rotary switch to be push-button operated (S.T.A.R.E.).

Loudspeakers designed to handle a wide range of audio frequencies were well in evidence. Besides the usual electro-dynamic types several manufacturers have introduced dual units with concentrically mounted electro-static or piezo-electric units capable of reproducing audio frequencies up to 15,000 c/s. The coming of f.m. was not the sole cause of the development of such loudspeakers; they are required also for the reproduction of high-quality microgroove records. If the manufacturers of television receivers would only take the trouble to give proper attention to the a.f. portions of their sets, viewers could take full advantage of the wide-band sound transmissions which accompany the pictures. Most French televisors, alas, are provided with rather rudimentary a.f. amplifiers and small loudspeakers and so are incapable of reproducing more than a narrow band of audio frequencies.

Before we leave loudspeakers another interesting novelty must be mentioned. This is an instrument with a focusing baffle shaped like a rabbit's ear. In addition to a normal, energized reproducer there is a second one, exactly similar but mounted horizontally. The latter receives no audio input; actually, its speech coil is short-circuited. The purpose of the "parasitic" speaker is to absorb the resonance peaks of the other to some extent. Since it is precisely similar to the energized one, it has the same resonances and the currents in its speech coil serve to damp the movement of the cone.

Television Equipment.—The new television components show, on the one hand, a tendency to simplify manufacturing processes with a view to price reductions, and on the other a desire to enable the user


WIRELESS WORLD, JUNE 1954

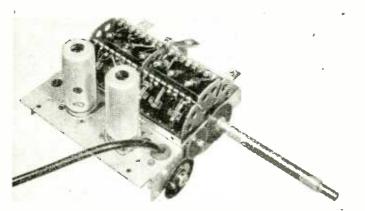

to receive several stations, possibly with different standards of definition.

Printed-circuit technique has now for the first time been used in the manufacture of television receivers. The French term *circuits appliqués* is perhaps more accurate. Two manufacturers showed assemblies made by cementing a plate of copper, 0.03 mm to 0.05 mm thick, to an insulating backing and removing unwanted metal by chemical methods.

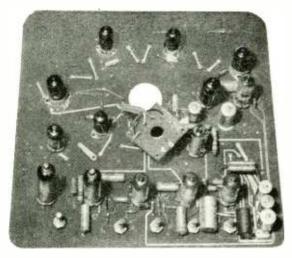A complete TV receiver chassis constructed in this way may contain no more than a few dozen soldered joints, as against the thousand or so called for by ordinary wiring methods. Deflector coil assemblies are also made by the applied circuit method. Much



Front and back views of printed circuit panel for a television receiver. (Visseaux).




Dual moving-coil and piezo-e'ectric loudspeaker. (Musicalpha) and (left) Six-channel television tuner. (Vidéon).

use also is made of the new magnetic materials for TV purposes.

Cathode-ray tubes shown had screen diameters ranging from 36 to 66 cm, anything less than 36 cm being of no account. Tubes with 43-cm screens are already in mass production and the large-scale manufacture of 54-cm tubes will soon be under way. Wide-angled tubes with deflection up to 90 deg are becoming common.

Two types of "rotactor" (rotary switching coil units) enabling reception to take place on any one of several channels were exhibited. They are equipped with readily interchangeable coils.

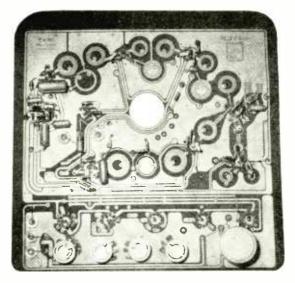Several standards of definition have to be taken





Printed circuit amplifier panel for a magnetic recorder. (Aréna).

WIRELESS WORLD, JUNE 1954

288



Servicing oscilloscope with 3-in. c.r. tube. (Centrad).

into account in France. In addition to the 819-line transmissions on the official French standard, 441-line transmissions will continue until 1958. Again there are many viewers in the regions near the eastern frontier who receive the German 625-line transmissions. One thus finds television measuring instruments, pattern generators and the like, designed to deal with this multiplicity of scanning systems.

Measuring Instruments.—Amongst these there is a large variety of new instruments designed to meet widely different needs. There are galvanometers so completely water-tight that they can be used submerged in several metres of water. More and more instruments are seen with scales of up to 270 deg. With the higher and higher sensitivity that is being achieved a microammeter with a full-scale deflection for a current of 1 μ A comes as no surprise.

One ingenious means of improving the oscilloscope must be mentioned. It consists of a fluorescent scale engraved on a sheet of Perspex, which is placed in front of the screen. The screen is illuminated from the side and the brilliance can be varied at will.

Electronic Equipment.—In France, as elsewhere, the semiconductors are beginning to figure prominently in the field of electronics, germanium and silicon diodes being in common use. Several firms showed transistors, though these are not as yet generally available.

An ingenious device is a d.c. "transformer" which enables direct voltages to be increased or decreased at will. The appliance contains a 2-

position switch. In one position the switch connects a bank of capacitors in series; in the other it connects them in parallel. The capacitors may thus be charged in parallel and discharged in series and the voltage increased. It can be decreased by charging in series and discharging in parallel. The principle is an old one; but this practical application is new and the device is completely reliable.

To sum up, the Salon must have made a very satisfactory impression on any technical visitor. Quality, reliability and ingeniousness were its outstanding characteristics, all of which serve to exemplify the liveness and virility of the industry.

HONG KONG HARBOUR RADIO

A V.H.F. radio-telephone system has been installed at Hong Kong to provide direct communication between ships in the harbour and subscribers on the Hong Kong telephone exchange. In addition to providing this facility the new system affords direct communications between moored ships and greatly assists loading and unloading operations.

The ship-to-shore radio link is provided by a portable batteryoperated f.m. transmitter-receiver, which is taken on board from the pilot's cutter as soon as the ship enters the harbour and set up in some suitable position.


To facilitate operation the network is divided into several groups, each group being allotted two wavelengths, one for transmit and one for receive, and all groups work through a permanent land station linked by

One of the G.E.C. mobile radio-telephones being taken aboard the pilot's cutter for transference to a ship entering the harbour. On the extreme right is shown a ground-plane aerial set up aboard ship in Hong Kong harbour for ship-to-shore communications. cables to the main telephone exchange.

Ship stations operate from a 12-volt battery and the equipment for each comprises a calling decoder, portable aerial mast, transmitter, receiver, desk controller and all

necessary cabling; the gear can be set up on board and working in a matter of minutes.

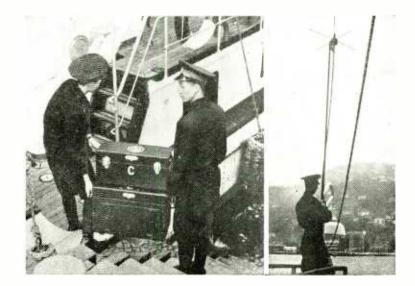All the equipment was made by the General Electric Company of England and the service is operated by Cable and Wireless.



Cavity Resonators

Empty Boxes Instead of Coils and Capacitors

By "CATHODE RAY"

N microwave equipment, the parts that correspond to wiring at lower frequencies are commonly referred to as "plumbing," from the obvious resemblance of waveguides and associated metalwork to the pipes with which builders in this country decorate the outsides of houses. The precision of manufacture and installation has to be a good deal higher than in domestic plumbing, however. After having been accustomed to making electrical connections from A to B by means of almost any old piece of wire, the constructor's graduation to microwaves comes rather painfully. Whether the same can be said of the theory side is perhaps a more open question. Anybody who has been brought up to think exclusively in currents and circuits probably finds it very difficult to imagine how electricity can be sent along a pipe. If, however, he had begun with microwaves, which would have meant thinking in fields from the start, the idea of currents travelling along wires might have appeared strange and difficult. Supposing I had a very limited time in which to do my best for someone who knew nothing at all about electricity, I think I might choose waveguides rather than wires. Even though speaking tubes are no longer standard equipment in the really modern home or office, so that an actual demonstration might be difficult to arrange, it is easy to imagine how they work. And if one can visualize sound waves going along pipes, why not electromagnetic waves? Communication by wire is a much more surprising phenomenon

Acoustic Resonant Cavities

It is the same with resonant cavities. We radio people are so used to our tuned circuits being made up of coils and capacitors that we are baffled when asked to accept an empty copper box as a tuned circuit. But if we could start again with no electrical knowledge at all, surely it would be the coil and capacitor that would be baffling, rather than the cavity? After all, everyone is accustomed to acoustical resonant cavities. Even the washer-up can hardly have failed to notice that while a bottle is being filled with water the sound, produced by the resonant cavity formed by the unfilled portion of the bottle being shock-excited by the impact of the water, rises in pitch as the cavity becomes smaller. And I suppose we have all played tunes by acoustically shock-exciting our mouths-another form of resonant cavity-by tapping our teeth with a pencil or blowing air between our lips and simultaneously varying the size of the cavity. By slightly modifying the blowing technique we can obtain much clearer notes, caused by continuous oscillation in the cavity, commonly referred to as whistling. To whistle a low note we have to make the mouth

cavity larger than for a high note. If anyone asks about dental cavities, the answer is that in a well-kept mouth they should always be small enough for their resonant frequency to be above audibility.

Another example of acoustic resonant cavity, introduced to most of us at an extremely tender age—probably on first visiting the seaside—is a shell held to the ear, which, like an electrical tuned circuit, selectively amplifies the frequencies to which it resonates, causing otherwise barely audible sea noises to roar forth impressively. And when listening to speech or music, one can, by making a cavity with the hands close to the ear, distort the sounds in just the same way as a tooresonant audio amplifier or loudspeaker.

The classical example, which so far I have not been privileged to witness, is the famous tenor lifting his empty glass after dinner and shattering it with one strong sustained note sung at its resonant frequency. But in this country such behaviour, even by famous tenors, is probably considered bad form, and one would have to go abroad to stand any chance at all. However, with so many less spectacular but perhaps more instructive demonstrations right at hand, there is really no need.

Now of course the fact that enclosed or nearly enclosed spaces have acoustical resonance does not prove that they also have electromagnetic resonance, nor does it explain how such electromagnetic resonance (if any) takes place. But we do know that there is a very close analogy between the generation, transmission, propagation and reception of sound waves, and of electromagnetic waves, so at least our examples of acoustic resonant cavities should lead us to expect something corresponding in electromagnetics; and by tracing the analogy between sound and electromagnetic waves we ought to be able to get some idea of how electromagnetic cavities resonate. To make this approach it is necessary to have a fairly comprehensive mathematical knowledge of sound waves, and their differences as well as resemblances to electromagnetic waves. Anybody who has such knowledge will probably be able to follow this line for himself without the doubtful benefit of my assistance. The rest of us will be content with the general picture.

Another approach is from what we know about transmission lines, resonant stubs and waveguides. Anyone who has grasped the theory of these three items can go on to resonant cavities on the basis that cavities are to waveguides as resonant stubs are to transmission lines. One learns that long lines, made up of uniformly distributed inductance and capacitance, transmit electromagnetic waves, and that certain comparatively short lengths, either short-circuited or open-ended, resonate, and are equivalent to tuned circuits (but in general are much better, in terms of Q. Similarly, a pipe or waveguide, provided its diameter is large enough in relation to the frequency, transmits electromagnetic waves; and a certain length of waveguide (such as a half wavelength) acts as a high-Q resonator. A closed length of waveguide is one possible form of cavity. And, just as waveguides have different "modes" of wave transmission, so cavity resonators have different modes of oscillation. Cavities, then, are best considered as an extension of the study of waveguides, especially as regards the question of modes.

The shapes of cavities are by no means only the same as commonly used types of waveguide. One possible, and in fact highly efficient but not usually convenient, shape is spherical. A very usual one, again not related to waveguide shape, is the toroid or American doughnut; for example, in klystrons, where it is termed the rhumbatron.

Still another approach, short-circuiting the study of waveguides, is by way of ordinary inductance-capacit-ance or LC-tuned circuits. The rhumbatron just mentioned is sometimes introduced as a development of a tuned circuit consisting of a single-turn coil and a single pair of capacitor plates, as in Fig. 1(a). By putting together a sufficient number of turns in parallel around a circle, as at (b), one forms a rhumbatron. Although this view may be better than nothing if a knowledge of waveguides and wave propagation is lacking, it doesn't get us very far. And it may be misleading in that the inductance and capacitance are not really separate, even in this shape, and obviously are not if the shape is a sphere, cube or cylinder. It is therefore hopeless to try to analyse a resonant cavity, as one can an ordinary tuned circuit, by measuring L its inductance; C, its capacitance; and r, the resistance which, if connected in series with L, would account for all the losses (Fig. 2). On the other hand, it is quite easy to find a cavity's resonant frequency. Actually, it has many resonant frequencies, but "the" resonant frequency, if not more particularly specified, is taken as the lowest. And it is fairly easy, by means of the frequency-variation method, to measure the Q



(a)

Above: Fig. 1. One way of looking at the toroidal-shaped resonant cavity (b) used in klystrons is as an extension of a single-turn coil and a single - pair - of - plates capacitor (a). In fact however the inductance and capacitance are not completely separate, even in this shape.

Right : Fig. 2. However a resonator is made up. it can be represented by this equivalent circuit. The values L, C and r usually depend on frequency and on what are reckoned as the terminals of the resonator.

WIRELESS WORLD, JUNE 1954

of a cavity. The one remaining item needed to specify its performance as a resonator is its impedance, measured at resonance, when it is equivalent to a high resistance—the "dynamic resistance." This is more difficult, but can be done if the points between which the resistance is reckoned are indicated.

These three things, usually written as f_{0} , Q and R_d respectively, together with the terminal points of R_d, are sufficient to specify any kind of tuned circuit, whether its inductance and capacitance are distributed or lumped. If lumped, then L, C and r can easily be found from f_{0} , Q and R_d, because

 $f_0 \simeq \frac{1}{2\pi\sqrt{LC}}$ (when Q is not small) $Q = \frac{2\pi f L}{r}$ and $R_d = \frac{L}{Cr}$

If they are distributed, as in a stub or cavity resonator, the values of L, C and r found from these equations are the component values of the equivalent lumped tuned circuit.

Why we use Cavities

Just in case anyone may not be quite clear why people should bother with cavities instead of the good old coil and capacitor (or, alternatively, bother with a coil and capacitor when it seems that an empty screening can is sufficient) let us dispose of that point before going any farther.

The advantage of the coil and capacitor is that their construction enables a comparatively large amount of inductance and capacitance to be got into a small space. Thereby it is practicable to tune to Droitwich (200 kc/s) in even a "ladies' handbag" portable set. Theoretically it is possible to tune to Droitwich with a resonant cavity, but its dimensions would have to be of the order of half a mile, which would create some practical difficulties, notably in the matter of manual tuning control. Even at the London television frequency (45 Mc/s) a cavity-tuned receiver would resemble a battery of Lancashire boilers. The conventional tuned circuit meanwhile is still entirely convenient at this frequency. But at the much-discussed Band III frequencies (around 200 Mc/s) one is beginning to feel a shortage of turns when trying to arrange step-up or step-down ratios. And if we had to go to Bands IV or V, in the upper hundreds of megacycles, this difficulty would become so acute that a semi-distributed construction such as the "butterfly" circuit would probably be adopted. An alternative is the stub or short resonant line, already mentioned, but this is not particularly compact by presentday standards: at 600 Mc/s a quarter-wave stub is $12\frac{1}{2}$ cm long—say 5in. A cavity is still less convenient, because it has to be wide and deep as well as long. It comes into its own in the thousands of megacycles, where lumped tuned circuits are right out of it, and stubs in turn are beginning to be difficult because their short-circuiting ends, which are supposed to be almost negligibly small compared with the length, no longer are.

The higher the frequency, the greater the tendency to radiate. Although radiation from a coil can be prevented from going far enough to cause trouble, by shutting it up in a metal can, it is not thereby prevented from being a loss to the coil. Apart from the difficulty of getting few enough turns at very high frequencies, therefore, the coil is out of it because of excessive radiation losses. For the same reason tuning stubs always take the coaxial form, in which the outer conductor completely screens the inner*; not the parallel-wire type, which radiates. When the frequency is so high that the length of a coaxial stub is so short that its outer diameter cannot be incomparably smaller still and at the same time give adequate clearance between low-resistance conductors, then one might as well drop the inner conductor and make it a cavity, for the dimensions will not be unreasonably large.

And so we are left with an empty metal box. It acts as its own screening can, so the radiation loss is practically nil. The only dielectric concerned is the air inside, so the dielectric loss also is practically nil. (If we were really fussy we could pump the air out; sometimes this has to be done anyway, if the resonator is part of a valve.) The only conductor concerned is the metal of the box, which is nearly always copper; and since the currents flow only on the inner skin† the inner surface of high-class cavities is polished and silverplated. All these things having been properly attended to, the losses are extremely small, and the Q values are fantastic by conventional tuned-circuit standards-30,000 and more is not unusual. Of course, a cavity is not usually made just for the sake of being set into oscillation; it is expected to work for its living, and the load to which it is coupled pulls down the overall Q. But for best results it ought not to be pulled down too much; in this respect the cavity is like any other tuned circuit.

Although Q is often expressed (as we have already done) as the ratio of inductive (or capacitive) reactance to equivalent series resistance, this is just a special case of the general definition, which takes the form of the ratio of energy stored to energy lost. The energy stored in a cavity resonator is stored in the electric and magnetic fields inside, so other things being equal is proportional to the volume. The energy lost is lost in the inner surface, so other things being equal is proportional to the area of that surface. One would expect, then, that the highest Q would be obtained in the shape that has the largest ratio of volume to surface area; which is the sphere. In practice the cylinder is little if any behind the sphere, and is obviously easier to make.

Field Patterns

In such a very introductory look at cavities I really don't think we had better delve deeply into the business of modes; it can all be found in the books on microwaves, which are full of diagrams looking like latitude and longitude lines on hemispherical maps of the world. The full lines are electric lines of force, and the dotted lines are magnetic lines of force, and all of them are as imaginary as lines of latitude and longitude. They just show the directions and roughly the relative intensities of the fields at chosen instants during the cycle of oscillation. In a conventional tuned circuit the electric and magnetic departments are kept almost completely separate, in the capacitor and coil respectively, but in a cavity they share the same space. The analogous fact in an organ pipe or other acoustic resonant cavity is that the air inside vibrates to and fro (velocity wave) and is alternately compressed and ex-

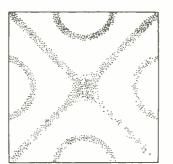


Fig. 3. One example of Chladni's figures, in which the pattern into which powder sprinkled on a plate forms itself when the plate is set into vibration shows the mode of vibration. The dark or powdery parts are the nodes, where there is no vibration.

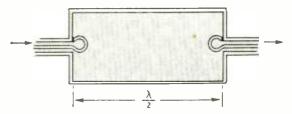


Fig. 4. Rectangular resonant cavity with input and output coupling loops.

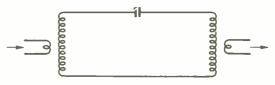


Fig. 5. Circuit equivalent to Fig. 4.

panded (pressure wave). And just as an acoustic cavity resonates at one series of frequencies from end to end, and another from side to side, the electromagnetic cavity resonates at various series of frequencies depending on the mode. In both acoustic and electromagnetic kinds of cavity, a standing-wave pattern is set up at resonance, and the mode is the particular pattern. Hence all the pretty diagrams. Anyone who has studied loudspeakers knows that the cone can vibrate in a large number of different modes, at different frequencies. The modes of vibration of a flat plate can be shown visually by sprinkling it with fine powder, which is thrown off the vibrating parts on to the stationary parts, forming what are called Chladni's figures (Fig 3).

In a two-conductor line, whether parallel-wire or coaxial, both electric and magnetic lines of force are transverse; that is to say, at right angles to the direction of travel. The electric lines stretch between the two conductors and the magnetic lines encircle them. But in a waveguide, where there is no second conductor, one lot of lines is partly along the pipe. The British custom is to divide all modes into two main classes, according to which lot of lines this is. In America they are classified according to which lot it Thus modes which have electric lines going isn't. along the guide are in the British system called \breve{E} modes. In America they are called TM (transverse magnetic). Actually both lots of lines are transverse, but only the magnetic lines are exclusively so. The other class of modes is called H (for magnetic field) or TE (transverse electric). Individual modes in each class are distinguished by little numbers, e.g. Ho1,

^{* &}quot;Some Coaxial Problems," Wireless World, Dec., 1953, p. 571. † "Skin Effect," Wireless World, Nov., 1953, p. 537.


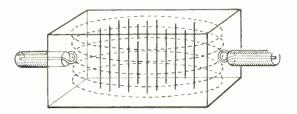


Fig. 6. The dotted loops are magnetic lines of force and the verticals within them are electric lines of force characteristic of the lowest-frequency mode of oscillation set up as in Fig. 4.

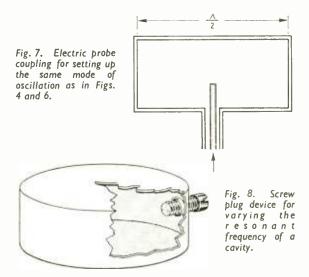

according to the number of half-waves in the field pattern across the main dimensions. This is where I refer you to the books for details.

Important Modes

Resonant cavities, unlike waveguides, do not have a continuous wave movement in one direction; there is a standing wave pattern, and these patterns or modes are classified in the same way as for waveguides, except that one more number is needed-to indicate how many half-cycles there are of standing wave. Although there are innumerable possible modes, it is only the very few of lowest "order" (and therefore frequency) that are used; the others are merely a nuisance. A good deal of the design of a cavity resonator is a matter of discouraging unwanted modes, so as to make sure that at any one time it oscillates with one intended pattern at one intended frequency. Here again there is the acoustical analogy. If you, like me, have a member of the family who is learning to play a wind instrument, you will know what I mean. Such instruments, it seems, require skill to ensure that the column of air therein does not vibrate in some undesired mode, instead of or in addition to what is wanted.

In both musical and electromagnetic instruments, a good deal depends on how the driving or exciting unit is coupled to the resonator. In microwave plumbing, one can place a probe (which is like a tiny rod aerial) in the direction along which the electric lines of force are wanted, or a loop in such a position as to encircle magnetic lines where they

are wanted. Fig. 4 shows a rectangular cavity magnetically coupled to a source via a coaxial line at one end and to a load at the other, making a system equivalent (at the resonant frequency) to the circuit in Fig. 5. The input loop in Fig. 4 starts an electromagnetic wave with the magnetic lines going through the loop, and therefore at right-angles to the paper. The corresponding electric lines are from top to bottom. When the wave reaches the far end it is (except for energy taken out by the coupling there) reflected. The magnetic field is reflected without change of phase so the round trip is a whole wavelength and the reflected energy arrives back in phase with what is just being delivered by the loop. Most of it is reflected again; and so forth, until the build-up in the cavity is very large. Since some of the magnetic field at the outlet end passes through the loop there, it generates an e.m.f. and so starts a wave along the outlet line. The field pattern in the resonator is represented conventionally as in Fig. 6; the mode is H_{011} or TE_{011} . If the cavity were twice as long, or the frequency twice as high, it would be H_{012} , because there would be two half-wavelengths from end to end.

Because the electric lines are vertical, an alternative way of establishing resonance of the same mode is shown in Fig. 7. The total distance from the probe to the end walls and back is only half a wavelength, but the electric field is reversed in phase on reflection, so the reflected wave again arrives in phase. No load is shown here, so presumably the cavity is very sharply resonant indeed, and the input impedance would go through very violent changes of magnitude and phase if the frequency were varied through f_0 .

There are two other methods of exciting cavities: through a slot, or little open window between the source and the cavity; and by shooting electrons through the cavity. This last method is very important, as we shall see.

An aspect of the subject yet to be mentioned is tuning. Obviously one way of tuning a cavity is to vary its length. One can think of a cylinder in a petrol engine as a resonator tuned rapidly to and fro over a wide range of frequency. We would be well advised to do no more than think about it, because as a practical arrangement it would not be very efficient. Steel piston rings, though no doubt excellent as a gas and oil tight joint, would not be conspicuously satisfactory for microwaves. However, suitable cylinder and piston combinations are in fact used as resonators for wide ranges of tuning. More often quite a small range is sufficient, and then a popular method is a screw plug (Fig. 8). The acoustic analogy might lead one to suppose that screwing the plug in, by reducing the volume of the cavity, would raise the resonant frequency. It might do so, but on the other hand it might lower it; all depending on whether it occupied space formerly dominated by electric or magnetic field. If electric field, then the result would be the same as if part of the space between capacitor plates were filled with metal-the capacitance would be increased and frequency lowered. Screwing a plug into the haunt of magnetic field, on the other hand, is like copper-slug tuning in coils-the inductance is reduced and frequency raised.

Applications

The uses of cavities? Obviously, for general tuning purposes. But there are one or two rather interesting special uses. Cavities can hardly be mentioned at all without bringing to mind the cavity magnetron,

WIRELESS WORLD, JUNE 1954

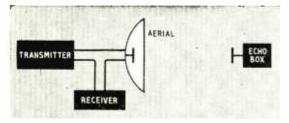


Fig. 9. Echo box method of checking the frequency and overall efficiency of a radar set.

which might quite well be called the valve that won the war. I gave some account of this last year,* along with the klystron,† which also incorporates one or more resonant cavities. In both of these the cavities are thrown into resonance by controlled electrons flying past or through them.

Another use is as a wavemeter. For rough tuning over a wide range there is the piston type, and for fine tuning the plug or plunger controlled by a micrometer movement. The enormously high Q enables the resonant frequency to be very precisely indicated. But, in contrast to the conventional absorption wavemeter, one must beware of responses at unwanted modes.

The high Q comes in very useful for testing radar The higher the Q the longer the oscillations sets. in the resonator take to die out after the power has been cut off. With a Q of the order of 30,000, they go on for quite a long time-at least several microseconds. That may not strike one as being an unendurably long time, but a wavelength of 3 cm means 10,000 cycles per microsecond. Briefly, the procedure is to set up a cavity resonator with a little dipole receiving aerial at a fixed distance from the radar aerial (Fig. 9). Each pulse from the radar, if it is working on the correct frequency (the frequency to which the cavity or "echo box" is tuned) sets the box into oscillation. At the end of the pulse the oscillations die away exponentially and are picked up by the radar receiver. Since each microsecond delay between pulse and received signal appears as a range of 164 yards on the receiver, the time taken for the oscillations to die away to the just-detectable level is known, and of course the longer this is the better the radar set as a whole, for it increases with transmitter power, receiver sensitivity, and efficiency of feeders, aerial, etc.

Speed of E.M. Waves

My last example of the use of a cavity resonator is a very special one. Some years ago, Dr. Essen of the National Physical Laboratory used a resonant cylinder about 7in long to measure the speed of electromagnetic waves in a vacuum with great accuracy. The dimensions of this cylindrical cavity were made correct within one hundred-thousandth of an inch, and the result of the measurement was given as 299,792.5 \pm 3 km/s. Since there is no reason to believe that the speed of electromagnetic waves at the frequency of the measurement (10,000 Mc/s) is any different from those at 500,000,000 Mc/s, this is accepted also as a measurement of the speed of light. Certainly it agrees well with accurate direct measurements of the speed of light. The speed is so enormous that the early methods necessitated a distance of many miles. Now seven inches is enough.

Transistor Stagnation

DEVELOPMENT of transistors is being held up by the unwillingness of possible users to co-operate with the manufacturers, according to B. R. Bettridge in a recent lecture to the Brit. I.R.E. Engineers were tending to sit down and wait for the super-device they felt was just around the corner, he said, instead of getting down to experimental work with existing transistors and making demands for specific improvements. Consequently the manufacturers were not very sure in which directions to guide their development work and the awaited improvements were slow in coming. The whole situation was a vicious circle which could only be broken by the users thoroughly exploring the potentialities of the transistor and pointing out the best lines of development.


Mr. Bettridge spoke about the use of other materials besides germanium for transistors, but said there were difficulties in manufacturing them in the form of single crystals.

Short-wave Conditions

Predictions for June

THE full-line curves given here indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during June.

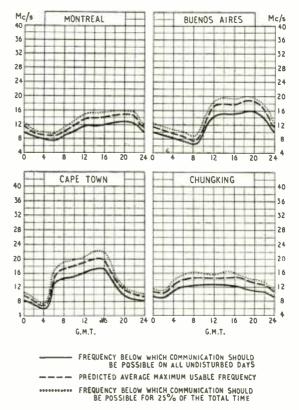Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.



^{* &}quot;Valves for Microwaves," Wireless World, Sept., 1953, p. 417. † "More Valves for Microwaves," Wireless World, Oct., 1954, p. 479.

Physical Society's Exhibition

Electronic Techniques in Research and Measurement

This report is followed by surveys of recently introduced valves and allied devices; also of test and measuring gear. These surveys cover exhibits at both the Physical Society's and R.E.C.M.F. shows. Some products appeared at both, so no distinction is made in the surveys between the two exhibitions.

RESEARCH

THE transistor has stimulated research into semi-conducting materials and the possibilities of finding substitutes for or perhaps even better substances than germanium for this and other applications of solid-state electronics. Germanium belongs to Group IV of the periodic table of the elements with a chemical valency of 4, and on theoretical grounds it has been predicted that intermetallic compounds of elements from the groups above and below with valencies of 5 and 3, which solidify in a zinc-blende structure similar to germanium should exhibit comparable electrical properties.

electrical properties. One of the principal difficulties in making electrically significant compounds is the maintenance of exact molecular proportions during the alloying process. The Services Electronics Research Laboratory showed examples of miniature vacuum furnaces and methods of controlling the reaction, and also a series of representative specimen compounds.

Provisional constants for some of these compounds are as follows:--

	Energy gap (eV)	Melting point °C	Electron mobility cm'sec per V'cm
Aluminium a n t i - monide Gallium arsenide Gallium antimonide Indium phosphide Indium arsenide Indium antimonide	1.65 1.2 0.71 1.2 0.48 0.18	1,060 1,280 725 1,050 950 525	100 3,500 700 14,000 50,000
Germanium	0.72	960	3,600

It will be seen that gallium arsenide has properties similar to germanium and may be expected to be less sensitive to temperature since the energy (gap) required to free an electron-hole pair from the crystal valency bond is greater.

The exceptionally high electron mobility and the low energy gap of indium antimonide suggest that it should be very useful as a thermoelectric generating material, and better than germanium as a material for measuring flux density by means of the Hall effect.* A demonstration

WIRELESS WORLD, JUNE 1954

was given with a small specimen of this material embedded in potting resin, which gave full-scale deflection on a Pye "Microvolter" when rotated in the earth's magnetic field.

An exhaustive study of the dielectric properties of ceramics formed by various proportions of the oxides of magnesium, silicon and aluminium has been made by the Research Laboratory of B.T.H. In the most favourable proportions the losses (tan δ) are as low as 0.0001-0.0005 at 3,000 Mc/s; the dielectric constant is about 6. Conducting glasses made with vanadium oxide and other admixtures and having resistivities at room temperature of the order of 10' were also shown by B.T.H.

A sensitive method of measuring frequency fluctuations is embodied in the "periodmeter"⁺ which was shown by H.M. Underwater Detection Establishment. Time intervals between zero transits of the wave under examination are displayed on an arbitrary time base as successive vertical deflections, and the shape of the envelope gives useful information on the nature and components of any frequency irregularity. The resolution is 1 c/s in 10 kc/s and one oscillogram showed that the equipment is capable of giving accurate information on magnetic tape speed, well below the generally accepted limits for fluctuation in recorders. It has also been applied to the measurement of the mean frequency of noise in a narrow band, and to the detection of pulse signals in noise.

Apparatus for the measurement of very weak sounds (of the order of 7 phons) was demonstrated by G.E.C. Research Laboratories. It has been designed primarily for the investigation of hum produced by fluorescent lighting chokes. A soundproof double box, lead-lined, is used to contain the choke under test and a sensitive microphone, and a special pre-amplifier in which the anode current of the first valve is only 60 μ A has been developed to reduce the electrical noise level. This amplifier is in tubular form so that it can be used for general measurement with minimum disturbance of the sound field.

The National Coal Board are investigating a method developed in the Physics Department of King's College, Newcastle, of detecting the presence of air in fire-damp drained from pit workings by measuring' the velocity of sound through the gas by a pulse technique. The position of the pulse on a c.r. tube display is arranged to indicate all mixtures on a horizontal trace and an alarm relay is operated when the air content lies between 50 and 100 per cent. A commercial gas analyser working on the same principle is made by Sir Howard Grubb, Parsons and Company.

An unusual application of electro-acoustics methods is to be found in the "apidictor" shown by the research department of Wayne Kerr Laboratories. A microphone and switched selective amplifier are used to monitor the sounds made by bees in a hive and to give information on the health of the queen and the imminence of swarming without disturbing the life of the colony.

Other research items noted in passing were a d.c. mercury pump (A.E.R.E.) in which transverse current and a magnetic field at right angles force the liquid upwards in accordance with the classical "left-hand rule"; and an e.h.t. supply unit (A.S.R.E.) in which the valve heaters are energized by capacitive feed from the anodes through miniature r.f. transformers which can be suspended in the wiring in multiplier circuits

† Wireless Engineer, Nov., 1953, p. 274.

^{*} See Wireless World, Nov, 1950, p. 415.

NON-INDUSTRIAL ELECTRONICS

THE counting and sizing of microscopic particles, such as blood corpuscles and dust, is a job which plainly calls for electronic techniques. The most popular method seems to be to place the particles on the slide of an ordinary microscope and scan them with a flying-spot cathode ray tube "looking" down through the eyepiece; a photocell on the other side of the slide then transforms the light modulated by the particles into pulses, and these are passed to an electronic counter during the period of one frame. Instruments working on this principle were shown by Mullard and University College, London. To avoid the possibility of a large particle being counted several times as a result of being on more than one scanning line, both instruments use a double scanning spot with an extra photocell. When the first of the two spots encounters the particle a pulse is counted in the normal way, but when, on the next scanning sweep, both spots encounter the particle the pulse from the second photocell is used to cancel the output of the first one, and so on. Size analysis of particles is accomplished in the University College instrument by a pulse-width discriminator which only accepts photocell pulses of certain durations, and in the Mullard instrument by increasing the separation of the two spots so that the second "inhibiting" spot only comes into action with particles of a certain size.

Another type of particle which can only be counted by electronic means is that produced by radioactive materials, and in this field the scintillation counter is becoming increasingly popular because of its great sensitivity-up to 80 times that of a Geiger-Muller counter. Burndept were showing an interesting example which was fitted with a lead collimator round the detecting crystal to give directional properties. With this the counting rate falls to one half of its peak value when the counter

is moved as little as 5½ degrees from the source of radiation. For the actual process of counting, as distinct from detecting, Ericsson Telephones were demonstrating a versatile equipment based on their well-known Dekatron tube. This is designed on the "add-on" unit principle so that any number of decades, each incorporating a Dekatron, can be plugged together to count up to whatever figure the user requires.

A new method of displaying the electrical activity of the heart which is now becoming increasingly popular is the vectorcardiogram. This gives a two-dimensional picture by presenting on one diagram recordings made simultaneously across two planes of the heart. In the vectorcardiograph shown by the Cambridge Instrument Company the amplified signal from one set of electrodes is connected to the Y plates of a c.r. tube and the signal from the other electrodes to the X plates, the result on the screen being a complicated loop somewhat akin to a Lissajous figure. This trace gives the properties of magnitude, sense and direction of the heart voltage, while the time scale is provided by a recording camera. Ordinary electrocardiograms can also be displayed.

Another interesting Lissajous-type display on a cathode ray tube was given by a number and letter generator shown by the Admiralty Signal and Radar Establishment. This presented the face of a clock, with moving hands giving the actual time and with the letters A S R E in the middle. The basic generator waveform was an ordinary sine wave produced by an RC oscillator. From this four secondary sine waves were derived, each dis-placed 90° in phase, and from these in turn came eight sets of half sine waves (positive and negative) and four sets of sine waves of twice the original frequency, making 16 waveforms altogether With these it was claimed that all figures and all the letters of the alphabet could be produced.

(Right) Ericsson counter with "addon ' decades.

(Below) Vectorcardiograph with recording camera by Cambridge Instru-



(Right) Mullard flying-spot particle counter.


WIRELESS WORLD, JUNE 1954

INDUSTRIAL ELECTRONICS

THE precision tachometer for measuring rotational speeds of aircraft engines, made by Plessey, is essentially an electronic counting device using Dekatron cold cathode tubes to give four decades. Electrical pulses from the engine shaft are registered on the counter tubes for a period of precisely 1 second, the marker pulses for which are derived from 4-kc/s quartz oscillator through two scale-of-two counting circuits followed by three Deka-trons. The display on the four counting Dekatrons is held for 0.7 sec for reading and then automatically set to zero for the next count. Alternatively the display can be held indefinitely until reset by push-button. The instrument is said to have an accuracy of 0.025 per cent.

In the Labgear (Cambridge) electronic tachometer (D4105) speeds up to 150,000 r.p.m. can be measured Normally the time datum is derived from 50-c/s mains, but terminals are also provided for an external 1-kc/s oscillator. Timing intervals of 0.1, 1 and 10 sec, and 1, 2, 10 and 20 minutes can be used, and the instrument is basically a combination of the D4102 automatic timer and D4104 Dekatron basic counter.

For the measurement of displacements, bridge methods involving change of capacitance or inductance are general. Wayne Kerr demonstrated applications of a 3-terminal a.c. capacitance bridge in mechanical engineering prob-(continuous sheet micrometer) which makes use of a differential transformer with movable core, actuated by a spring-loaded roller. The bridge is balanced by the standard Fielden pointer servo mechanism and can be supplied as a simple indicator, as an error indicator or as a recorder. Salford Electrical Instruments demonstrated a differential electromagnetic transducer designed for operation from a.c. mains, which could be used for remote

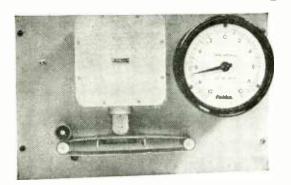

(Above) Fielden continuous sheet micrometer.

position control or for the measurement of displacement

A self-contained industrial servo unit (Type R1219) shown by Ediswan, is mounted on a standard 19-in panel and contains a feedback push-pull amplifier, with provision for internal or external reference voltages, adjustto the centre-tapped field winding of a Type FA2 Ever-shed and Vignoles d.c. servo motor. The unit which provides a standing torque of 22 oz-in can be used to drive a variable-ratio transformer in voltage or current stabil-izers, for process control or in machine tool pattern follower systems. It was shown connected to a model giving constant tension in a wire, irrespective of winding speed or direction.

Ultrasonic techniques are finding increasing applications in industry, and Mullard were showing, in addition to their high-powered ultrasonic drill, examples of work cleaned with the aid of high-frequency vibration. By generated with standard Mullard equipment, it was demonstrated that improved results could be obtained in less time. For removing the surface film from optical lenses a magnetostriction transducer working at 25 kc/s is satisfactory, while for intricate engine parts, ball races, etc., a quartz crystal using frequencies of the order of 1 Mc/s is most effective in dislodging dirt from confined spaces.

SEMI-CONDUCTORS AND VALVES


MOST manufacturers are now prepared for the coming of Band III television with new valves for the front end of receivers or tuner units. All assume the same type of circuit-cascode signal-frequency amplifier plus frequency changer, as described in our April issue-and all the valves are very similar to each other. For the double-triode cascode stage there are the Mullard PCC84, the Osram B319, the Brimar 7AN7/PCC84 and the Ediswan 30L1, all designed to operate at 90 V h.t. (each section) and with mutual conductances of about 6 mA/V. For the triode pentode frequency changer there are the Mullard PCF80, the Osram LZ319, the Brimar 9U8/PCF82 and the Ediswan 30C1. All eight valves have 0.3-A heaters for connecting in series heater chains.

Another sign of the times was the appearance of several Another sign of the times was the appearance of several ranges, or partial ranges, of valves for a.m./f.m. receivers. Amongst these were a number of multiple valves intended to serve several purposes. With the Brimar 6U8 triode pentode, Osram B309 double triode and Mullard ECC85 double triode, for example, one half would be an r.f. amplifier and the other a self-oscillating mixer. With the Brimar 6T8 and Mullard EABC80, both




Portable precision (Left) tachometer (Plessey).
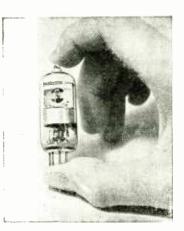
> (Right) G.E.C. tunable magnetron showing form of cavities.



triple-diode triodes, two of the diodes would be used in an f.m. ratio detector, the third as an a.m. detector and the triode section as an a.f. amplifier.

The design of low-power tunable magnetrons of the conventional type for operation at frequencies of the order of 10,000 Mc/s becomes difficult because of mechanical complications. G.E.C. were showing that a simple type of magnetron can be devised to give adequate output for most low-power applications by the use of electron interaction with space harmonics of the resonator field. The valve (type VX3238) has a simple form of anode with two resonant cavities, mounted within a glass bulb through which it radiates directly into an output waveguide. It operates with the same voltage and magnetic field as a magnetron with ten to fourteen cavities of the usual type. By adjusting an external cavity coupled to the valve a tuning range of at least 400 Mc/s can be achieved with a single control and with a power of not less than 100 mW. Pulse operation is possible and a peak power of the order of 1W may be obtained at a peak current of about 50 mA. G.E.C. also had another low-power tunable magnetron

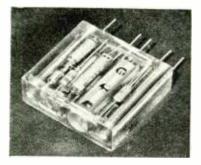

Example of Wayne Kerr "potted" circuit element with provision for dissipating heat from encapsulated valve.


(type VX3809) with an interdigital anode structure. It operates at an anode voltage of 700-800V and gives an output power of 4-8 watts over a tuning range of 8.8-11.6 cm.

Cooling transmitting valves by water vapour instead of forced air or circulating water is claimed to give greater heat dissipation for a given size of valve. Ediswan were showing two of their "Vapotron" valves with special anode structures rather like copper pineapples for this type of operation. The valve is arranged to bring water to boiling point and advantage is taken of the loss of heat in evaporation. The water is self-circulating and no pumps are required.

In cathode ray tubes the most interesting exhibit was a 21-inch rectangular tube, type MW33-21, made by Mullard and intended for export receivers. It has a tetrode gun with an extra electrode at cathode potential for giving uniformity of focus over the whole screen. 20th Century Electronics were showing new versions of their singlebeam oscilloscope tubes with the novel feature of squarc screens.

It goes without saying that the transistor field is expanding rapidly, and junction types were on view for the first time. Among these were the Mullard OC70 and OC71—high stability types with large current gains, hermetically sealed in glass and intended for use in hearing aids. They replace the OC10, OC11 and OC12 (also on show) which came out some time ago. Among point transistors, one of the latest types was the GET2, made by G.E.C. This is similar to the well-known GET1, but works at a lower voltage and has a higher current gain-3.8 as compared with 2.5. In addition the "knee" of the $I_c - V_c$ characteristic is much sharper than in the GET1. This firm were also showing experimental p-n-p and n-p-n junction transistors in oscillator and amplifier circuits, one oscillator being powered from two dissimilar metal electrodes immersed in tap water! An experimental point type with electrode spacing of only one thousandth of an inch was capable of operating at frequencies as high as 40 Mc/s.

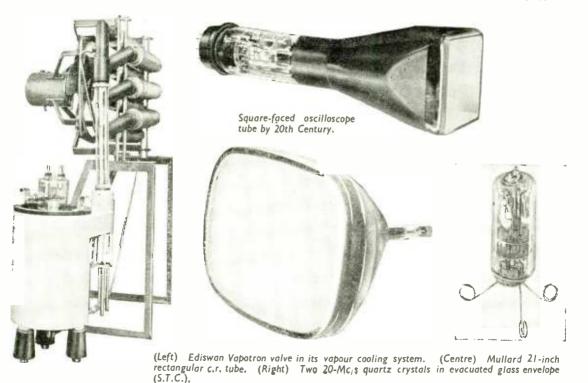Turning to more prosaic semi-conductor devices, Brimar were showing a new metal rectifier, type RM5,



WIRELESS WORLD, JUNE 1954

intended for receiver h.t. supplies. With an input voltage of 250 volts r.m.s. it will give a maximum d.c. output current of 300 mA. It measures $1\frac{1}{8}$ in square by 6 in long. For e.h.t. applications Westinghouse had some small tubular rectifiers, types 39E and 39K, with wire ends and diameters of $\frac{4}{32}$ in. Individual elements are rated at 85 V maximum peak inverse and 100 μ A mean d.c. output current. This firm were also showing hermetically sealed versions of their 36EHT and 16HT rectifiers.

Among the quartz crystals on show were some interesting overtone crystals by S.T.C. for operation at frequencies up to 200 Mc/s. They have a frequency tolerance of ± 0.005 per cent and an equivalent series resistance of 1 ohm per Mc/s. One example was a crystal working on a 9th overtone at 180 Mc/s.

One of the many problems associated with "potting" circuit elements is the dissipation of heat generated by encapsulated valves. The method adopted by Wayne Kerr is to enclose the valve (sub-miniature types are generally used) in a perforated metal tube with the closed end flush with, or very slightly proud of, the face of one side of the moulding. The assembly is then mounted so that this face makes contact with the metal chassis, or with a metal bracket of sufficient size, to carry away the heat from the tube.

Among the many activities of Wayne Kerr is investigating the qualities and characteristics of the various resins used in this potting, or encapsulating, process. This year they staged a demonstration showing, by means of polarized light, the strains and stresses set up in certain mouldings on solidification and it was shown also how such stresses can be avoided by using suitable mixtures.

Makers*: Brimar (V, C, G); Ediswan (V, C); English Electric (V, C); Ferranti (V, C); Mullard (V, C, G, T); Osram (V, C, G, T); Pye (Q); Salford (Q, R); S.T.C. (Q, R, G, T); Westinghouse (R, G).

*Abbreviations: V, valves; C, cathode-ray tubes; G, germanium diodes; T, transistors; R, metal rectifiers; Q, quartz crystals.

TEST AND MEASURING GEAR

Apparatus Shown at the R.E.C.M.F. and Physical Society's Exhibitions

AMONG the very few new meters to be seen at either show was the "Duo Meter" (British Physical Laboratories) which, as its name suggests, incorporates two meter movements, each with its own range switch, so that voltage and current (d.c. or a.c.) can be measured simultaneously. The same firm also showed single meters with very clear-reading 270° scales. The sensitivity of the Pye "Scalamp" galvanometers has now been doubled, as a result of suspension improvements. Another wellknown range of instruments, the Evershed "Megger," has been extended by a mains-driven model with a test voltage of 10 kV. It has two scales: 0-1,000 M Ω and 60-200,000 M Ω .

New valve voltmeters continue to be produced. The Solartron 20 c/s-20 kc/s phase-sensitive voltmeter brought out last year has been supplemented by a model for 0.5 c/s-l kc/s, which is easier to use, because the four-phase output from the OS103 oscillator obviates the necessity for frequency-sensitive phasing adjustments on the voltmeter. Elaborate use of negative feedback in the Solartron VF252 voltmeter enables +1% accuracy to be claimed over a range of 10 c/s to 100 kc/s, while exceptional sensitivity readings can be made down to 20 "V. Instruments in this class are necessarily large and mainsdriven; in complete contrast is the Furzehill V210 crystal diode valve voltmeter, which, although provided with six d.c. ranges (1-300 full-scale) and all these except the 300-V range for a.c., are completely self-contained, including batteries, in the very small case shown here. A flashing neon tube indicates when the unit is on, and also by its frequency gives a guide to the condition of the batteries. The Cintel signal-level meter comprises an amplifier, meter, and calibrated attenuator; its frequency range is 20 c/s-100 kc/s, and lowest range 0-1 mV. An instrument shown by Joyce, Loebl comprises a sub-standard a.c. voltmeter preceded by a highly-stabilized amplifier, enabling nearly the full accuracy of the meter to be retained, with the addition of very high input impedance. Although not a precision instrument, the Langham Thompson cathode-follower unit also operates as a high-to-low impedance matcher, and is notable for its extremely small size, in spite of containing its own battery power. The principle of the well-known heterodyne type of

The principle of the well-known heterodyne type of wave analyser for a.f. has been adopted by Airmec in an instrument covering the wide r.f. range of 30 kc/s-30 Mc/s. To avoid second-channel difficulties the i.f. is 0 ± 3 kc/s. This instrument, type 853, is suitable for measurements of field-strength, interference, insertion gain and loss, frequency, etc. There are few new oscilloscopes, though a number of improved models. Mark II of the Mullard wide-band oscilloscope is an engineered version of the model previously shown, having a flexible and comprehensive triggered time base of constant sweep length, and calibrated delay circuits. It is particularly suitable for the analysis of high-speed complex waveforms. The Furzehill oscilloscopes, notable for some years for their directcoupled amplifiers, are now obtainable with single-stroke time base, and one of them (type 0.100) has calibrated time and voltage. There is also an entirely new and relatively small general-purpose model (0.120) at a moderate price.

The construction of decade resistance boxes has changed little for a good many years, but now a notable departure by Tinsley is the substitution of printed units in place of the groups of conventional wire-wound resistors. Compactness, stability and low reactance are combined with higher power dissipation. Another new decade resistance technique has been developed by Pye: a box giving very precise and stable small increments of resistance. If steps of 0.0001Ω were provided in the conventional manner they would be subject to large uncertainty owing to switch contacts. In the Pye box low-resistance steps are brought in by shunting a fixed resistance with relatively large values of resistance, sufficient to swamp the switch resistance very effectively. Total range in the specimen shown is 50-61.111 Ω ; the 50 Ω residual resistance can be tolerated in bridge and other measurements for accurate low resistance, because they would risk to more precise standards through overloading, Furzchill have introduced a workmanlike highdissipation five-decade $\pm 1-\%$ resistance box (R600) totalling over $1 M\Omega$ in steps of 10Ω . A precise decade of capacitance is costly, but where

A precise decade of capacitance is costly, but where $\pm 1\%$ is good enough the box now produced by Servomex gives $0.001-0.999 \ \mu$ F inexpensively, using three 3-pole wafer switches and groups of capacitors in 1:2:2:5 ratio. The principle of the Sullivan capacitor introduced some years ago, in which the range of a 100-pF variable air capacitor is multiplied tenfold by a decade unit also with air dielectric, has now been extended in a model having the same total capacitance made up of a 10-pF variable (giving more precise readings) and two decade units. This capacitor is incorporated in a new Schering bridge covering 0.1 pF-100 μ F with $\pm 0.01\%$ precision. British Physical Laboratories also showed a Schering bridge using a tuned visual null indicator. The trend towards transformer ratio arms continues. Langham




Furzehill V210 portable valve voltmeter.



Miniaturized cathode follower unit made by Langham Thompson.



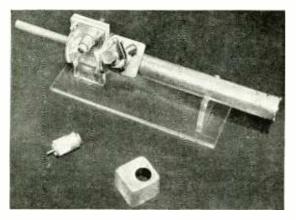Standing-wave indicator for 3-cm band made by Elliott.



Piston attenuator made by Advance Components.

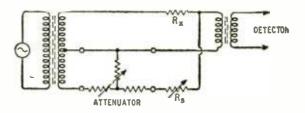


Fig. 1. In transformer-ratio bridges for v.h.f., the range of values of the standard resistance $R_{\rm s}$, and of the ratio, is limited. In an exhibit by Wayne-Kerr this limitation was shown to be overcome by an attenuator inserted as shown.

Thompson have a capacitance bridge on this principle, reading up to 250 pF in three ranges; and Wayne-Kerr (who use it exclusively in their bridges) have two new self-contained mains-driven models with "magic-eye" balance indicator; the B321 for inductance and resistance, with a discrimination of $0.00001 \,\mu$ H at $10 \, \text{kc/s}$ (max. $10 \, \text{mH}$), and the B221 for capacitance and conductance, with a discrimination of $0.0001 \,\mu$ H at $10 \, \text{kc/s}$ (max. $100 \,\mu$ F). An interesting feature of both these bridges is that the readings come up in figures at a window, as in a cyclometer, and the unit symbol and the position of the decimal point is controlled by the range switch! Errors in reading are thereby excluded. An experimental v.h.f. bridge technique demonstrated by Wayne-Kerr is shown schematically in Fig. 1. Where values of standard resistance or transformer ratio would in the ordinary way be impractically high, an attenuator is used instead. A modification of the Marconi Instruments universal bridge is now available under the type number TF868/1, having the alternative frequency of $10 \, \text{kc/s}$ to give greater discrimination when measuring low values of reactance. Finally in this section, two Hay bridges for measuring incremental inductance of iron-cored components: the Furzehill B800 covering 50 mH-500 H in four ranges at frequencies of 25-2,000 c/s; the other by Cintel, 10 mH-1,000 H in seven ranges, at 50 c/s. Both provide for Q measurement from 3 upwards, and convenient application of desired amounts of a.c. and d.c.


Adjustable stabilized power supplies are indispensable laboratory equipment, and there is now a much wider choice of units, especially for a.c. and for relatively heavy currents. The Solartron range of valve-stabilized d.c. power units has been extended by compact and inexpen-sive chassis models for incorporating in experimental equipment; they also provide unstabilized l.t. a.c. Although h.t. accumulators have been virtually banished, it has been difficult to find a substitute for the large l.t. accumulators, but a unit is now offered by Servomex providing up to 7 A at 1-30 V, stabilized within 25 mV. It is a servo-controlled motor-regulated equipment. Two l.t. power outputs, each up to 20 A 14 V, a.c. or d.c. or both, but unstabilized, are provided from a Joyce, Loebl unit. Of the new a.c. mains stabilizers, the Cintel employs a motor-operated Variac, and full load at 230 V is 15 A. The Sorensen type of stabilizer is supplied by Langham Thompson with maximum outputs from 0.25-15 kVA and uses the saturable-reactor principle. The difficulty of making saturated transformer regulation satisfactory against variations in frequency and load power factor without reducing the high-speed correction of voltage variations is solved in a novel manner by Philips: the quick-acting transformer is used straightforwardly for voltage stabilization, and is compensated for frequency and power-factor variations by a separate electronic chain which (since these variations are much slower) is not restricted in design by the need for fast response.

The Elliott power frequency generator, a production form of a prototype shown a year or two ago, is a link between stabilized a.c. power units and signal generators. (Continued on page 301) It provides two outputs of 70 VA at 0-750 V, 0-5 A, and 40-2,500 c/s. Output stability is better than $\pm 0.02\%$, and frequency better than $\pm 0.005\%$; and the relative phase can be adjusted from 0° to 360°. The basis is an RC oscillator, amplified, and stabilized by negative feedback.


Arranged in ascending order of frequency, new signal sources begin with the Solartron OS103 decade oscillator, at 0.1 c/s, or even (to order) 0.01 c/s. The top frequency in both models is 11.1 kc/s. A special feature is the fourphase output, intended primarily for use with the phasediscriminating voltmeter already mentioned. Associated Electronic Engineers have two RC a.f. oscillators : one to provide 4 watts output over the usual 20 c/s-20 kc/s in three ranges; and the other with slightly less output but exceptionally pure waveform-a total harmonic content of 0.06% is claimed. Airmec showed two r.f. signal generators to Government specification for use under arduous field conditions in any climate, and provided with both a.m. and f.m.: type 871 covering 85 kc/s-32 Mc/s and type 872 20-80 Mc/s. Also, mainly for use with a r.f. wave analyser to be mentioned later, a calibrating oscillator, type 858, 30 kc/s-30 Mc/s, for providing accurately known fixed outputs at 10 mV, 100 mV and 500 mV, with less precise interpolation. The Wayne-Kerr v.f. oscillator, 10 kc/s-10 Mc/s, is now provided (as type S341) with a 50-c/s square-wave output. Increasing interest in the v.h.f. and u.h.f. bands has brought forth a number of new oscillators. Particularly suitable for television ser-vicing in bands I and III is the Advance Ql, covering

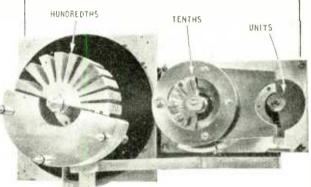7.5-250 Mc/s, with such facilities as sine and square-wave modulation, and output variable 1 mV-100 mV, at a very reasonable price. The well-known D1 10-300 Mc/s signal generator is now modified as D1/D with direct-reading voltage and frequency scales. Its inductive continuously variable 20-db attenuator, as well as the familiar resistive step attenuator, is now separately available. The 300-1,000 Mc/s L1 signal generator shown last year is now in production, and its piston attenuator is separately available. It works in the H₁₁ mode, is provided with a screen to exclude E modes, and a crystal diode for monitoring the output, and its attenuation range is 126 db. The Standard Telephones QD2, a high-performance signal generator covering the range 96-160 Mc/s, also employs a piston attenuator, calibrated in decibels and millivolts or microvolts from 0.5 V-100 mV to an accuracy of ± 1 db. Particular attention has been paid to linear modulation up to 90 per cent depth at frequencies 30 c/s-10 kc/s. The extensive "Windsor" range of Taylor testgear will shortly include a synchronized TV pattern generator having a carrier range of 40-240 Mc/s and output approximately $50 \,\mu$ V-10 mV, available for either 405-line or 525-line standards.

A considerable amount of new microwave apparatus was shown this year, including X-band (3 cm) waveguide test benches by Decca, Elliott, Ferranti, Marconi Instru-ments, and Metrovick. The Ferranti outfit is a break-away from the usual assembly of pipes, the guides being milled out of the two heles of the two the test of the two heles of the two heles. milled out of the two halves of a light-alloy block. Another of its notable features is a three-klystron input, to facilitate measurements at several spot frequencies without readjustment. The attenuator elements in most microwave equipment are thin nichrome films deposited on rhomboidal glass slips, giving a wide frequency range and little reflection. For use with the Elliott X-band torque-vane wattmeter shown last year there is now an artificial load with ceramic element and a quarter-wavelength slider for the elimination of standing-wave errors. A different approach to the standing-wave problem is shown in the Wayne-Kerr instrument, which contains two vanes on the same suspension, separated by quarter of a wavelength, as shown in Fig. 2. The same firm also demonstrated an X and S band Q meter, incorporating a new klystron oscillator unit obtainable separately. The Q meter oscilloscopically compares the decay of oscillations in a resonant cavity with the known rate of a capacitor discharge, and an accuracy better than ±1%, is claimed.




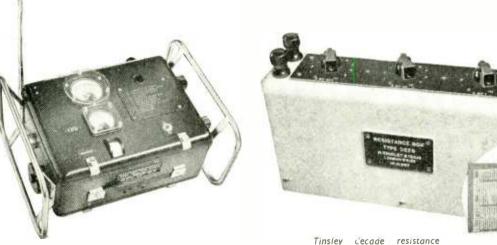
Sullivan decade air-dielectric capacitor; the capacitor marked "units" is 10 pF and continuously variable.




Transmitter and receiver performance tester made by Wayne-Kerr.

WIRELESS WORLD, JUNE 1954

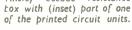

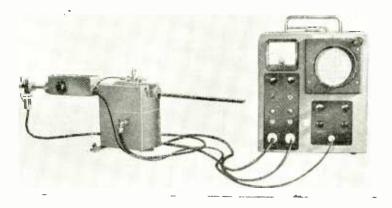

Reverting to Elliott X-band equipment, other wellengineered items are a precision wavemeter of the piston type with a resetting accuracy of 0.0003 in, with clockgauge method of position indication within 0.01 mm. Equipment for the 0.9 cm band was also shown. The trend towards cleaner exteriors and the use of clock gauges for position indication was also exemplified on the Metrovick stand. Standing-wave-ratio measuring gear by Marconi Instruments incorporated a mechanically reciprocated receiver probe and a c.r. display. Barr & Stroud, besides a nichrome/glass attenuator, showed an automatic X-band aerial diagram plotter, recording in cartesion form on Teledeltos paper. The previously shown E'co plotter is now "tidied up," and an interesting feature of the demonstration was the "free-space" cabinet for the aerial, lined with aquadag-coated slats—analogous to the acoustic rooms used for testing loudspeakers.

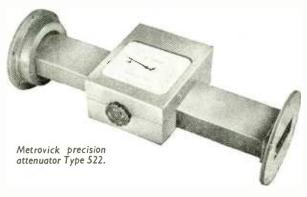

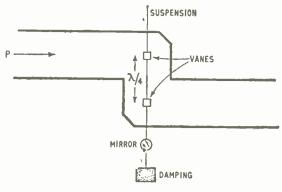


Fig. 2. Suspended-vane Wayne-Kerr waveguide wattmeter; two vanes are used to minimize standing-wave errors.

Marconi Instruments automatic standingwave indicator.

The remaining instruments fall outside the foregoing categories. The Marconi Instruments TF982 mobile v.h.f. test set, for example, includes almost everything: r.f. oscillator, a.m. modulator, a.f. oscillator, i.f. check with four crystals, r.f. power meter, a.f. power meter, multi-range test set, and attenuator terminating unit. Another new exhibit by the same firm was the TF1054 radio-noise and fieldstrength measuring equipment for the range 0.15-2.4 Mc/s. The TF1055 is the same except for frequency range 2.4-30 Mc/s. They will be used to test compliance with the new legal requirements for the suppression of inter-

ference, and consist of two receivers with loop and rod acrials; gain is standardized by a noise diode. Similar models are being produced to extend the frequency range up to 600 Mc/s. The Wayne-Kerr Test Set X740A is a Service instrument for the comprehensive testing of v.h.f. transmitter-receivers by non-technical personnel. Although weighing only 161b, it includes a.f. and r.f. signal generators, v.h.f. wattmeter and a.f. output meter, and the results of measurements are indicated as "Pass" or "Reject." Tests include transmitter power output, noise, and modulation depth, and receiver sensitivity and noise. Development of the accurate Solartron feedback voltmeter already mentioned necessitated precise calibration, and the instrument for doing this was shown, as model AT203, since it is of general utility for use with amplifiers, valve voltmeters, etc. It takes a 10-V signal at 0-300 kc/s, provides a meter check of correct level, and subdivides it down to $10 \,\mu$ V. A new Cintel frequency monitor has been produced, similar in technique to other models by this firm, but with a frequency range extended to 20 Mc/s. Frequencies over 10 Mc/s are divided by 10 for measurement. The oscilloscopic spectrometer by Salford Instruments contains 38 filters which analyse an incoming signal and present the relative outputs as vertical lines on the c.r.t. screen. The range is 10 c/s-100 kc/s. C.r.t. presentation of families of valve curves has been adapted by Mullard for transistors, and is obviously a great labour saver. A frequency-standardizing equipment by British Physical Laboratorics uses the B.B.C. broadcast transmission on 200 kc/s to control a chain of multi-vibrators and a clock; accuracy about 1 in 10⁶. The same firm showed a frequency discriminator for giving direct reading of the difference between two frequencies. A possible application is the reading of weather conditions from radio sondes. Servomex demonstrated a great improvement on the usual rather crude method of testing stickiness of meter movements. The equipment consists in effect of a 3-speed slow time base. An important feature is protection against external surges, etc., that would otherwise cause misleading irregularities in the movement of the pointers.

Interference Suppression

BRIEF reference is made to the work on the design of inexpensive radio-interference suppression chokes with ferromagnetic cores, undertaken by the British Electrical and Allied Industries Research Association during the past year, in the 33rd annual report of the E.R.A. A comprehensive survey, however, of this work has been prepared under the title "The Properties and Design of Iron-Ored Suppression Chokes," by J. Miedzinski, B.Sc., and will eventually be available from the E.R.A., Thorncroft Manor, Dorking Road, Leatherhead, Surrey, Further reports on the properties of the core materials are being prepared.

Reference is also made in the annual report to the work undertaken on the measurement of radio interference from high-voltage transmission lines and a survey covering this investigation is in course of preparation.

WIRELESS WORLD, JUNE 1954

Plotting Aircraft Positions

AN aircraft plotting system in which the radio bearings from a number of direction-finding stations are passed automatically to a traffic control centre and there displayed on a map of the service area has been developed by Standard Telephones and Cables. It is intended to operate primarily in conjunction with a network of S.T.C. cathode-ray v.h.f. direction finders Type PV1B, but it is possible to adapt it for use with certain other types of v.h.f. direction-finding equipments. It enables the position of an aircraft to be determined by radio bearings taken on v.h.f. telephone messages and the time taken to fix its position is less than that normally required for the aircraft to establish its identity. The actual position can be passed back on completion of the identifying or other message.

The principal equipment required at the position-finding centre is a display cabinet fitted with a ground-glass screen on which is engraved a map of the service area showing the usual topographical features and any other

special data required. The screen can be either 40 in or 60 in square. Mounted at the back of the cabinet is an assembly of projection cathoderay tubes, each corresponding as closely as possible to the position danide d.f. stations comprising the network. These projector units are similar to those used in projection television receivers, but have deflector coils designed to give very high angular accuracy. They project a rotatable trace on to the map as shown in the illustration. The point of intersection of three such traces, as in normal radio d.f. practice, gives the position of the aircraft.

Signals for operating the display are sent automatically by the d.f. stations as soon as a bearing is determined, and there is no delay beyond that needed for the bearing and with the PV1B equipment it is almost instantaneous. The signals can be sent over any ordinary communication channel, line or radio, so that the position-finding centre can be located at any convenient site inside or outside the service area of any of the d.f. stations.

The d.f. stations need not necessarily be devoted exclusively to this aircraft position-finding system and in the case of the PV1B equipment the addition of a telemeter sending attachment enables it simultaneously to perform local services at aerodromes



Display screen of the S.T.C. aircraft position-finding system showing bearings automatically relayed from three d.f. stations.

WIRELESS WORLD, JUNE 1954



In TRIX Sound Equipment, versatility is allied to quality. Quality of design, of workmanship and materials, outstanding quality of performance. TRIX continues to lead the way in the development of sound reproduction. Our range of standard units is the widest available, for we place at your disposal the complete service in sound.

> RE48. duty Model A heavy reflex type weather - proof horn speaker with exceptional ce. Very suitable

range and performance. Ve for all public address work.





This outstanding 30 watt high fidelity amplifier provides all the features needed to cover the large majority of Sound installations. It is designed for A.C. operation and can also be used on batteries with a 6 volt adaptor unit. Inputs for 2 Microphones, and one Gramophone pickup, with individual mixing controls. Separate controls for Bass and Treble boost. The amplifier is a 4 stage, high-gain type suitable for use with ribbon microphones, without additional pre-amplification. Special anti-microphonic features incorporated. High and low

features incorporated. High and low impedance inputs.

Push-pull output circuit with inverse feed-back. High and low impedance tappings, including 100 volt line matching





Telegrams and Cables: TRIXADIO, WESDO, LONDON

RANDOM RADIATIONS

By "DIALLIST"

Any Old Tubes?

SOME TIME AGO a wireless dealer told me of an episode which had been puzzling him quite a bit. A small van arrived at his shop one day. From it descended a couple of " spiv " types, who asked if he'd any discarded television c.r. tubes, offering to pay good money for any that passed a "little test." Not liking the look of the men and realizing that they were up to no good, he chased them out. But what could their particular ramp be? What on earth could they do with cast-off c.r. tubes? The answer, as he had just discovered when I saw him a day or two before writing this, was tied up with the fact that none that he might have offered would have passed that "little test." He is a skilled man, who looks after his customers well, reactivating (where possible) tubes whose emission is down and giving a new lease of life to any suffering from cathode-to-heater short-circuit by fitting an isolating transformer. Any tube that he discards is a genuine dud. The aforesaid test would have led to the purchase of any tube if it suffered from nothing beyond the defects mentioned. Not all dealers are as scrupulous or as skilled as he is and anyway the isolating transformer can't be used where the mains supply is d.c. These things had made it well worth the while of his unsavoury visitors to equip themselves with a small motor van and to make dealing in discarded cathode-ray tubes a whole-time job.

Service !

How do they make their profit? My dealer had found the answer to that question when spending the Easter holiday with an entirely nontechnical relative of his in another town. The relative, who owns a 15inch television receiver, had been roped in to subscribe to a ridiculously low-priced all-in maintenance scheme operated by newcomers to the neighbourhood. He was de-lighted with it: "Other firms wouldn't insure my set because it is nearly two years old. But they did; and when the tube passed out last week they fitted a new one without a murmur." My dealer asked whether the present tube carried a

guarantee: "They say that they keep that, as they're maintaining the set. He asked whether the dark patch in the middle of the screen was there when the set was returned with its replacement tube: "Oh, yes; they tell me that these tubes always have it when new, but that it soon wears off." Whipping off the back of the set the dealer found, as he'd come by now to expect, that the "new" c.r. tube had been provided with an isolating transformer for its heater. I'm not saying that this is what is done with all the c.r.t. throw-outs that are bought; there may be perfectly legitimate uses that I am not aware of for some of them. But this incident certainly provides food for thought.

Those D-d Dots

FOR SOME TIME now I've been suffering from an annoying form of television interference: innumerable white dots peppered in random fashion all over the screen. At first sight one might think that an unsuppressed motor-car engine had been left running rather fast some little way from the house. But that isn't the answer, for it's always there: Saturdays, Sundays, every day; and

at all hours, even the small ones. Having found that all my neighbours were experiencing the same thing, I made a report to the Post Office and two of their engineers arrived to investigate. Well, I hardly need say that the interference was far less intense than I'd ever known it in many weeks, and as we watched the screen it became feebler and feebler. When they made a tour round the neighbourhood they couldn't get so much as a smell of it, even with their most sensitive apparatus. Shortly after they'd gone it was back again as bad as ever. One can't help wondering whether the person responsible for the interference spotted the Post Office van and took action accordingly.

A Grim Business

RECEIVING a present from a friend on the Continent can be no light matter in the queer times in which we live. Early in April I heard that a pair of valves of a new type were on their way to me. Time passed. Then came a letter from the Customs folk, asking me to complete section so-and-so of the enclosed form. This was almost as big as one's daily newspaper, but my

ASSOCIATED "WIRELESS WORLD" PUBLIC	ATIC	ONS
TECHNICAL BOOKS	Net Price	By Post
RADIO DESIGNER'S HANDBOOK, F. Langford-Smith, B.Sc., B.E., M.I.R.E., A.M.I.E.E., A.M.I.E. 4th Edition	42,-	43,6
INTRODUCTION TO VALVES, R. W. Hallows, M.A. (Cantab.), M.I.E.E., and H. K. Milward, B.Sc. (Lond.), A.M.I.E.E.	8,6	8,10
FELEVISION ENGINEERING: Principles and Practice. VOLUME ONE: Fundamentals, Camera Tubes, Television Optics, Electron Optics. A B.B.C. Engineering Training Manual. S. W. Amos, B.Sc. (Hons.), A.M.I.E.E., and D. C. Birkinshaw, M.B.E., M.A., M.I.E.E., in collaboration with J. L. Bliss, A.M.I.E.E.	30'-	30 '8
WIRELESS WORLD TELEVISION RECEIVER MODEL II: Complete constructional details with notes on modernizing the original design	3.6	3'9
RADIO INTERFERENCE SUPPRESSION as Applied to Radio and Television Reception. G. L. Stephens, A.M.I.E.E.	10'6	10,11
SOUND RECORDING AND REPRODUCTION. A B.B.C. Engineering Training Manual. J. W. Godfrey and S. W. Amos, B.Sc. (Hons.), A.M.LE.E	30'- 30 -	30 8 30 7
FOUNDATIONS OF WIRELESS. M. G. Scroggie, B.Sc., M.I.E.E. 5th Edition	12,6	13/-
TELEVISION RECEIVING EQUIPMENT. W. T. Cocking, M.I.E.E. 3rd Edition A complete list of books is available on application	18'-	18'8
Obtainable from all leading booksellers or from		
ILIFFE & SONS LTD., Dorset House. Stamford Street, Lo	ndon,	S.E.1.

section consisted of only about half a dozen questions. There was a footnote to the effect that the questionee should reply "Not Known" to any to which he didn't know the answers. As I did not know the weight, the value and so on, this didn't take long. Having signed and dated the document, I returned it with a letter assuring Her Majesty's Officers that I had no intention of selling these articles and that they were purely for my own use for experimental purposes. When the package eventually turned up I found that it bore a label, attached by the sender, on which were the answers to all the questions to which I'd had to reply "Not Known!"

Here's Hoping

BY THE TIME that you read this the international exchange of television programmes will probably have had some trial runs. I hope sincerely that the whole thing will be a real success for it's an excellent idea. I trust that the fears expressed to me when the whole thing was very much in the embryo stage by one of those concerned in trying to organize it will prove completely baseless. "How's the eight-nation hook-up coming along?" I asked. "The gods send it isn't an eight-nation muck-up," was his gloomy reply!

Try It : It Works!

ISN'T IT about time that the powers that be stopped kidding themselves (and trying to kid others) that the policy of persuading people to fit suppressors to motor vehicles is ever going to be successful? From checks that I've made on vehicles passing my own house I'd say that somewhere about 80 per cent of the cars, vans and lorries over a year old continue to radiate interference as freely as ever. If the authorities won't bring pressure to bear, there's one way in which owners of television receivers can. Comparatively few tradesmen seem to have "suppressed" their lorries and delivery vans. When the arrival of your groceries, fish or coal results in a snowstorm on the television screen, or in unpleasant noises from the loudspeaker of the short-wave receiver, a 'phone call to the owner of the offending vehicle to the effect that, if he doesn't mend his ways and spend the necessary couple of shillings on having a suppressor fitted, you'll find another supplier, usually produces rapid and satisfactory results.

BULGIN TEST-PRODS

for Experimenters, Laboratory Workers, Servicemen

New Streamlined moulded body, designed for easy manipulation and safety. Fully insulated, approx. 6in. long. Metal parts highly Nickelplated.

Fused models normally supplied 60 mA., unless otherwise requested. For 500V. use, 250V. normal maximum. Ideal for use by Experimenters, Servicemen, and Laboratory workers.



MANUFACTURERS OF RADIO AND ELECTRONIC COMPONENTS

A. F. BULGIN & CO. LTD., BYE-PASS RD., BARKING, ESSEX

Telephone: RIPpleway 3474 (5 lines)

proof and safe.

UNBIASED |

$R = V^2 + 3W$

THE cryptic title to this item, "lifted" direct from the pages of *Amateur Photographer*, lends support to the doubts I cast last month on the somewhat dogmatic statement of an A.M.I.E.E. that repeatedly switching on and off an electric lamp —and by legitimate inference a thermionic valve—does nothing to shorten the life of the filament.



Forcibly impressed

If the writer in A.P. and the official publication of a well-known lamp and valve manufacturer, which he quotes, be correct (and who should know better than a manufacturer of these devices?) the switching process *does* shorten filament life owing to the heavy initial surge of current through the cold filament. The writer does not say why this heavy initial surge of current shortens its life but surely it can be for no other reason than that it causes a very large and sudden expansion of this delicate thread of wire.

The lamp and valve manufacturer's publication suggests the use of a series resistor-which can be shorted out after a few seconds-to combat this. It also gives the formula at the head of this note for calculating the value of the resistor; R being the required resistance in ohms, V the voltage applied to the lamp and W the lamp wattage. It is useless for those opposed to my views to say that this initial surge is serious only in the case of over-run photographic floodlights, for projector lamps are also mentioned and these are not over-run devices. The A.P. expert further states that the argument applies to all filament lamps."

I admit, however, that it does

306

By FREE GRID

apply in lesser degree to ordinary domestic lamps owing to their lower running temperature and in even less degree to valves with their comlow-temperature dullparatively emitter filaments, but it does apply a bit. Could anything meet the case more aptly than the schoolboy's translation of the well-known Latin tag "Magna est veritas et prevalebit, namely, "Great is truth and it shall prevail a bit?" I myself recollect so translating this tag in my youth and the enormity of my error was so forcibly impressed on me that its recollection still prevails more than a bit. In this case the truth I spoke about filament life prevailed-at any rate a little bit.

Clinical Radiometry

IT IS astonishing what little use we make of the vast resources of electronics to lessen the labour of man by relieving him of irksome repetitive tasks that could be better done by a machine.

A glaring instance of this came to my notice recently when I happened to be in a hospital ward where several patients were recovering from the immediate effects of an operation which, as after all operations, meant that a nurse was kept trotting round every half-hour to take each patient's pulse and recording it on a chart.

Apart from the fact that it disturbed the patient to be seized by the wrist and manhandled—or should it be womanhandled?—just when he had fallen into a doze it was obvious that, in this particular men's ward at any rate, entirely false readings were being obtained. As the nurse was an exceptionally attractive-looking girl her approach every half-hour accentuated the patient's heart action and in some cases caused it to miss a beat.

This sort of thing causes cardiac strain at a time when it can least be tolerated and the pulse readings are not, of course, a true reflection of the patient's post-operative condition. I pointed this out to the house



physician, who at once grasped my point, and the pretty nurse, and replaced her by a more homely looking specimen of her profession with medically satisfactory results.

All these undesirable effects could be avoided and the nurse released for other duties if use were made of the radio-sonde principle whereby changes in the many meteorological "variables" are continually transmitted,

In these days of miniaturization it should not be difficult to construct a micro-wave transmitter not much bigger than a wrist watch. Each transmitter in a ward would work on a slightly different frequency and would radiate a few yards to the ward-sister's office where heartbeats could be read at once and at any or every moment from a battery of small c.r. tubes, one for each patient; any glaring irregularities could be made to cause a red light to flash in order to attract attention. If necessary, film recordings could be made.

By various modifications temperatures and other variables could be similarly transmitted. Maybe the sub-miniature wrist transmitters could be made simpler if they merely had to feed induction signals to a copper band around the ward; a technique about which I wrote last month.

Does It Matter?

HALF-TRUTHS are notoriously dangerous, far more so, in fact, than honest straightforward lies and it is for this reason that I am sorry to see the radio correspondents of certain newspapers telling their readers that television stations have not the coverage of ordinary sound broadcasting stations because TV waves, unlike ordinary radio waves, can only travel in straight lines.

This is such a glib and simple explanation that it is swallowed without question by the lay mind and if you try to challenge it the layman who has accepted it is apt to be rather resentful at any attempt to rob him of it; he usually asks somewhat truculently what is your explanation of the undeniable facts of the case that the reliable range of TV stations is not much more than an optical one. You usually find yourself launched on a full-scale

lecture on wave propagation which is far beyond your hearer's understanding and so he soon loses patience and dismisses you as a charlatan.

Perhaps after all it is better to let the public stew in the technical heresies which it loves. Does it matter, for instance, that most people believe that George Stephenson invented the steam locomotive or that Watt invented electric lamps and fires?

WIRELESS WORLD, JUNE 1954

The PERFECT TEST TEAM



The illustration depicts a set of modern " AVO " testgear being used to measure the " Q " of the secondary winding of the second I.F. transformer on a chassis of unknown characteristics-just one of many tests which can be performed by this combination of instruments.

A signal of predetermined frequency from the "AVO" Wide Range Signal Generator is being fed into the Electronic Test Unit, where it is amplified and fed to the secondary winding of the transformer. The Electronic Testmeter is connected across the tuned circuit under test and from the readings obtained and the controls of the Electronic Test Unit, the "Q" of the circuit can be determined.

The three instruments, shown as a team, cover a very wide field in measurement and form between them a complete set of laboratory testgear, ruggedly constructed to withstand hard usage.



ELECTRONIC TESTMETER A 56-range instrument combining the solution of an eleicate galvanometer with the robustness ease of hand, ing of an basically of a highly stable of the solution of the ELECTRONIC TESTMETER Resistance: 2 onn to 10 Megonmi Operates on 100-130v. and 200-260v. 50-60 c.s. A.C. mains

Sole Proprietors and Manufacturers :---



ELECTRONIC TEST UNIT For measuring small values of A.C. Voltage, inductance, capacity angle "Q⁶ at adjustance, capacity angle "AVO" instruments, it can be used "AVO" suitable Signal Generatori "Why Voltmetter combination. Valve Voltmetter combination. As a Wide Range Amplifier, it is Valve Voltmeter combination. As a wide Range Amplifier, it is capable of an amplification factor of 40 ± 2 - 3db between 30cls and 20Mcls 40±2-3db between 30c/s and 20Mc/s As a Capacity Meter, it covers measurements at radio frequency from 5P to 900pF in two distinctly ealibrated ranges. calibrated ranges. As an measurements from 5µH, to SomH, in six ranges. SomH, in six ranges. As a "Q, Meter, it indicates R.F. As and condenset losses at frequen-cies up to 20 Mc/s cies up to 20 Mc/s Operates on 100-130y, and 200. calibrated ranges. cies up to 20 Mcls Operates on 100-130v. and 200-260v. 50-60 cls. A.C. mains.



TTI. A

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD. WINDER HOUSE · DOUGLAS STREET · LONDON Telephone: VICtoria 3404/9 S.W.1

The best which present techniques can devise ...


Like its predecessor, the QUAD II embodies outstanding features anticipating trends in both amplifier and associated equipment design. The importance of these features will be apparent to all who have followed the growth of high quality reproduction in recent years.

The criterion, as always, is that the reproduced sound shall be the closest approach to the original—that the enjoyment and appreciation of music may be unimpeded. This is reflected throughout the electrical and mechanical design. It is reflected, too, in the straightforward and logical system of control, achieved without the sacrifice of a single refinement or adjustment capable of contributing to the final objective. The QUAD II for convenience of installation, is constructed in two units—the main amplifier and the control unit. Each is complementary to the other, offering in complete form the best which present techniques can devise.



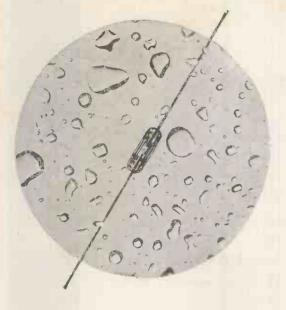ACOUSTICAL MANUFACTURING CO. LTD., HUNTINGDON, ENGLAND







All glass POINT CONTACT

GERMANIUM DIODE

ABRIDGED DATA

Forward Current:

at	+0.25V	••••	,	Auj001 <
at	+1.0V	••••		>8mA

Reverse Current at 25°C :

at	-1.5V	 	< 20µA
at	- 10V	 	< 200µA
at	- 20V	 	< 800µA
at	- 30V	 	<1.25mA

Operating Ambient Temperature: - 50 to +75°C.

R.F. Characteristics: the OA73 is suitable for operation as a wideband R.F. detector.

Fusion sealed

Penetration of water vapour is undoubtedly one of the major factors which affect the stability and reliability of germanium diodes. Partial and complete sealing techniques, while keeping the inside of diodes moisture-free, have in the past often introduced other undesirable fillings.

The Mullard aim has been not only to safeguard diodes from the ill-effects of water vapour, but also to reduce the number of different materials used in construction and so minimise the risk of contamination. The ultimate point in the evolution of this type of construction is marked by the OA73, the first of a Mullard range of *all-glass* diodes.

In this latest form of construction the glass envelope is melted onto the lead-in wires, so forming properly made fusion joints similar to those employed with great success in the many millions of radio valves which are made each year. These joints are entirely sealed and there is no possibility of performance being jeopardised by the entry of moisture or any other substance.

The OA73 has been specially designed for industrial and telecommunications use. It has been tested to the full tropical specifications for the CV442 and is an approved type.



MULLARD LIMITED, COMMUNICATIONS & INDUSTRIAL VALVE DEPT. CENTURY HOUSE, SHAFTESBURY AVE., LONDON, W.C.2

3



Hearing is believing ...

The human ear is capable of hearing approximately one per cent harmonic distortion. Yet even in equipment where this distortion has been reduced to a lower level, the difference between "live" and reproduced sound can still be detected.

The development by Goodmans engineers of the elusive quality of "PRESENCE" is therefore significant for the High Fidelity enthusiast. "PRESENCE" goes beyond the response curve. It implies more than the wide range of response in perfect balance for which Goodmans speakers are noted.

The additional quality of "PRESENCE" offers the nearest possible approach to listening to the actual recording session of the music of your choice.

For the enjoyment of High Fidelity reproduction in its truest form, every link in the chain of reproduction, from pickup to speaker, must be equal to its function. Make an opportunity to listen to a Goodmans speaker. You will find that it is more than equal to its task. For what may be the first time for you, you will hear the music of your choice as it should be played—as it was recorded with all its depth and richness of feeling.

> We will be pleased to supply free dimensioned drawings of specially designed standard or corner reflex cabinets. Numbers of cabinets have been sold reputedly to our design but which do not conform to our specification. Before purchase, it is therefore advisable to check carefully that the specification has in fact been carried out.

AXIOM 22 MK. II £14.14.0 (Tax	free) AXIOM	102	£9.18.2	(Inc. Tax)
AXIOM 150 MK. 11 £10.5.6 (Tax	free) AXIOM	101	£6.12.1	(Inc Tax)



AXIOM WORKS. WEMBLEY, MIDDX. 'Phone: WEM 1200 Cables: "Goodaxiom" Wembley, England



A.F. TRANSFORMERS AND CERAMIC ROTARY SWITCHES

The "Hyperloy" series of A.F. Transformers and Chokes of over a 100 Specifications is now available in hermetically-sealed containers capable of withstanding the most rigorous climatic conditions. Also available in similar gas-tight containers is a range of Bi-limboid transformers having hum-cancelling windings for use in situations demanding the lowest hum-levels without recourse to expensive mumetal screening.

The high-quality ceramic rotary switch is designed

for use in low-power transmitters, instruments or for similar circuit selection functions. The insulating material is "Frequentite", and silver-alloy contacts ensure very low contact resistance and trouble-free service over a long life.

A "Wearite" Switch Chest is available for laboratories and research organisations and contains all necessary component parts to permit of the assembly of switches to meet particular requirements.

WRIGHT & WEAIRE LTD 131 SLOANE STREET · LONDON · S.W.I · Telephone: SLOANE 2214/5

Now... the ultimate in Amplifier Performance


Based on the World-famous Williamson circuit and utilising the latest Partridge ultra-linear C-core output transformer, the RD SENIOR represents the ultimate in modern high fidelity amplifiers. Used in conjunction with a Control Unit embodying every possible refinement, it combines faultless reproduction, flexibility of control and absolute reliability to provide a performance to satisfy the most exacting requirements.

- ** RD SENIOR "
 * Ultra-linear C-core output transformer
 * Power Output : 15/20 watts. Peak: 25. watts.
 * Frequency Response: ±.1 DB 20-20,000 cps.
 * Distortion : .08% for 15 watts. .3% for 20 watts.
 * Intermodulation Distortion : .35%-15 watts.
 * N.F.B.: 20 DB (10-50,000 cps.)
 * Partridge Transformers throughout.
 * RD SENIOR " MAIN AMPLIFIER
 * 278
 - 5 - 10 - 10 0B -15 -15 -20 -20 -25 -25 -30 -35 - 35 -40 10 20 100 200 500 JK 2.6 510 10 K 20 K 50 K 100 10 HI-PASS C.P.S. LOW-PASS

FILTER CHARACTERISTICS

- * 2-position High Pass Filter.
- ★ 3-position Low Pass Filter.
- ★ 6 Playback characteristics.
- ★ 2 Radio Inputs.
- ★ Microphone Input.
- Very high input sensitivity, average on LP 8 m/V.
- ★ Input and Output Jacks on front panel.
- * Illuminated translucent control panel.
- * Negligible hum and noise.
- Close tolerance high stability components throughout.
- Wide range switched Bass and Treble controls.
- ★ All Filter and Tone controls operate on all inputs and are all completely independent of one another.

"RD SENIOR" CONTROL UNIT

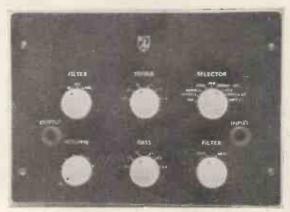

6 '

£28

£15

"the ideal unit for domestic use at reasonable cost"

The following is an extract from one of the many unsolicited letters of appreciation we receive concerning our amplifiers, In this case from a customer in Calgary, Alberta, shortly after he had taken delivery of a BABY de-luxe Mk. II amplifier and JUNIOR Mk. II pre-amplifier.

"Regarding the amplifier, I should like to compliment you on its excellence of construction. In addition, the performance with my speaker assembly is superb and streets ahead of anything in its field that my friends or I have heard locally. Managing this with so simple a design is, in my opinion, a remarkable achievement. The degree of control available in the pre-amplifier, also, appears to be just right with what limited experience I have had to date. In my opinion, the pair fulfils all requirements as the ideal unit for domestic use at reasonable cost, giving faithful musical reproduction without the freak effects I have heard with some amplifiers."

(The original letter may be inspected at our premises)

BRIEF SPECIFICATION

Power Output : 8/10 watts. Frequency Response : \pm .25 DB. 30-20,000 cps. Distortion : .2 per cent for 8 watts. NFB : 20 DB (30-20,000 cps.) Hum and Noise : -85 DB below 8 watts. Input Sensitivity : 40/60 m/V (P.U.) Variable Low Pass Filter : 7.5 kcs.-4 kcs. Six position switched BASS and TREBLE Controls. Four Playback Characteristics. Two Radio Inputs. Spare Power : 300 V. 40 m/A. 6.3 V. 2 A.



First introduced just over a year ago this amplifier has gained an enviable reputation both in this country and abroad and has fully justified our original claim of being the World's finest medium priced amplifier. Besides the many hundreds supplied throughout this country, the amplifier is already in use in over 20 overseas countries. The design of both amplifier and pre-amplifier remains unchanged and they are offered as the ideal basis on which to develop a home high fidelity system at moderate cost. For a further improvement in versatility the pre-amplifier may be directly replaced by the new RD SENIOR Control Unit to provide a performance which at £29 is quite unsurpassed by anything at present on the market.

RD BABY de-luxe Mk. II Amplifier,

with RD JUNIOR Mk. II pre-amplifier



RD BABY de-luxe Mk. II amplifier, with



RD SENIOR Control Unit

Detailed technical leaflets describing the above units and those on the opposite page will gladly be forwarded post free on request. Response curves and Illustrations are included.

Main London Agents : B. K. Partners Ltd., City Sale & Exchange Ltd., The Gramophone Exchange Ltd., H. C. Harridge, Mall Order Supply Co., and Webbs Radio. Also available from leading dealers in the Provinces, or, if In any difficulty, please apply direct.

Sole Agents in : AUSTRALIA, BRIT. N. BORNEO, COLOMBIA, HONG KONG, ITALY, JAMAICA, SOUTH AFRICA. Trade and Export enguiries invited.

ROGERS **D**EVELOPMENTS **C**O

MANUFACTURERS OF PRECISION BUILT SOUND EQUIPMENT "RODEVCO HOUSE," 116, BLACKHEATH ROAD, GREENWICH, LONDON, S.E.10.

Telephone: TIDeway 1723.

Telegrams : RODEVCO, GREEN, LONDON.

WIRELESS WORLD

JUNE, 1954

Industry is Solving Valve Testing Problems

WITH THE MULLATO HIGH SPEED VALVE TESTER

Industries which deal extensively with radio and other electronic equipment are finding the Mullard High Speed Electronic Valve Tester ideal for routine checks. This instrument provides the quickest method of checking large quantities of valves, and can be operated if necessary by nontechnical personnel after only a few minutes' instruction.

Write for full details and a copy of the folder "High Speed Testing in Industry" to Department E.V.D. at the address below.



MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, W.C.2

MVM266A

£1 DEPOSIT will secure for you the FINEST in

	Description	CRED Cash Price		£1 8 M	De- osit fthly. st. of	HI Depo		1	CHASE 12 fthly. Inst.	18
	GW18 Williamson Amplifier GW18C Williamson Amplifier (with	£33	5	0	90/-	£11	1	8	42/5	28/6
	cover) GW12 Williamson Amplifier	£36 £27	0 10	0	96/6 74/	£12 £9	0 3		44/4 35/-	30/- 24/-
	GW12C Williamson Amplifier (with cover) MA5 Amplifier MA5C Amplifier (with cover) F/TC Tone Control F/U/TC Tone Control PFA Tone Control	£10	0 10 10 10 14 18	0 0 0 0 0	78/- 36/- 38/- 28/6 38/6 50/-	£4 £4 £3	13 10 16 10 14 6	8	37/- 18/4 19/6 15/- 20/- 24/6	25/6 12/6 13/4 10/4 13/8 16/8
	LOWTHER DT41 Tuner Unit AM/FM Tuner Unit A15F Amplifier Master Control Unit	£37 £22 £45 £20	6 0 0 0	3 0 0 0	100/- 58/6 122/- 53/-	£12 £7 £15 £6	2 6 0 13	8	48/3 28/- 58/4 25/9	18/11
	LEAK RC/PA/U Pre Amplifier Varislope Pre Amplifier Steel Cutting Filter TL/12 Amplifier TL/10 Amplifier & Pre Amp. VS Tuner Unit	£9 £12 £5 £28 £28 £35	9 12 10 7 7 0	0 0 0 0 0	26/- 34/- 16/- 76/- 76/- 94/-	£3 £4 £1 £9 £9 £11	3 4 16 9 9 13	08	14/ 17/4 9/3 36/2 36/2 46/6	9/6 11/9 6/5 24/6 24/6 31/6
	QUAD Mk. II Amplifier & Pre Amp	£42	0	0	114/-	£14	0	0	53/4	36/-
And and a second s	ROGERS Senior Control Unit Mk. II Baby De Luxe Ampl. Mk. II Junior Pre Amplifier Mk. II Minor Amplifier RD Minor Baffle RD Junior Corner Horn Junior Tuner Unit	£28 £15 £14 £9 £12 £8 £18 £18 £25	0 0 0 17 15 17 6	0 0 0 6 0 6 1	75/- 39/6 37/6 25/- 34/6 24/6 50/- 66/6	£9 £5 £4 £3 £4 £2 £6 £8	6 0 13 0 5 18 6 9	8 0 4 0 10 4 0 0	20/- 19/- 13/4	23/7 13/6 12/10 9/- 12/- 8/9 16/8 21/6

HIGH FIDELITY EQUIPMENT

Use our PERSONAL CREDIT PLAN to buy all your requirements. An innovation is an arrangement whereby, after sending us £1 initial deposit, you can purchase any of the following equipment over 9 months. Your purchase becomes your own property immediately and you make only 8 further equal monthly payments as shown. You may also buy on extended hire purchase terms over EIGHTEEN months. Please add carriage and packing to your deposit. If you do not see any of your needs here please send us your inquiry.

> For Loudspeakers suitable for use with the above, see our announcement elsewhere in this issue.



WE ARE SOLE AGENTS FOR ROGERS HIGH FIDELITY EQUIPMENT IN THIS AREA

E.&G. MAIL ORDER SUPPLY CO.

The RADIO CENTRE 33 Tottenham Court Road, London, W.I.

Telephone : MUSeum 6667

JUNE, 1954

K K A N

T-R CELLS

For incorporation in military and marine radar equipment, a comprehensive range of 3 cm. and 10 cm. T-R. Cells is available.

TTR. 31 A tunable high Q T.R. Cell for use with $\frac{2}{5}$ in. diameter circular waveguide.

Frequency Range : 9,100-9,900 Mc/s. Band Width : 5 Mc/s.

Handling Power : 50 kW. peak.

Band Width :

Write for :-

SERIES COMPONENTS

- T. R. CELLS

TTR. 31 MR Tunable medium Q T.R. Cells for use with standard and American waveguide (TTR.31MR) or §in. diameter TTR. 31 MC circular waveguide (TTR.31MC). Frequency Range : 9,100-9,900 Mc/s.

25 Mc/s.

Handling Power: 50 kW. peak. details of these and other T.R. Cells from our range

Full details of these and other T.R. Cells from our range will be supplied on request.

'PENTLAND' SERIES RESIN CAST COMPONENTS

LIST ES/V/I LIST ES/T/6

The Ferranti "Pentland" series of components includes Power Transformers and Chokes, Signal and Pulse Transformers and Delay Networks.

These units are cast in a solid block of synthetic resin which replaces the oil-filled container previously considered essential for high quality components and below are listed some of the notable advantages conferred by this technique :

Extreme robustness combined with minimum weight and volume.

Complete hermetic sealing.

Fire risk greatly reduced.

Reliable operation through a wide range of ambient temperatures and climatic conditions.

"Pentland" series components are designed to customers' specification and full details will be supplied on request.



FERRANTI LTD FERRY ROAD EDINBURGH 5

0

DE

*

100 MR 100 100 MR 200 100 MR

WALKIEPHONE

2002 5002 5002

3000 3000 AUG

JUNE, 1954

PORTABLE RADIO-TELEPHONE FOR CIVIL ENGINEERING COMMUNICATIONS

> For purposes of routine inspection and maintenance the Pye V.H.F. Walkiephone makes a valuable but inexpensive addition to any V.H.F. scheme. Unimpeded by this lightweight equipment one man becomes a constant source of information and, when required, a centre of control. In places both unexpected and inaccessible the Pye "Walkiephone" ensures the smooth control of emergency operations. Robust, reliable, and economical in use, the complete equipment weighs only $10\frac{1}{2}$ lbs. with batteries.



ENGLAND

Pye (New Zealand) Ltd., P.O. Box 2839, Auckland, C.I, New Zealand.

Pye Canada, Ltd., Ajax, Ontario, Canada. Pye-Electronic Pty., Ltd., 65 Park Street, Abbotsford, Melbourne, Victoria, Australia. Pye Ireland, Ltd., Manor Works, Dundrum, Dublin, Eire.

.

Pye Radio & Television (Pty.) Ltd. P.O. Box 10648, Johannesburg, South Africa.

PYE LIMITED .

CAMBRIDGE

E3

WORLD-WIDE DEMAND FOR STENTORIAN HIGH FIDELITY UNITS

Phenomenal success of new line

Never production, have we created a world-wide demand in a matter of months. It sounds incredible, but that is just what has happened with our High Fidelity range. Since they were first introduced last Autumn, we have received orders for these units from

U.S.A. · CANADA AUSTRALIA · SOUTH AFRICA PORTUGAL · BELGIUM · SWEDEN MEXICO · VENEZUELA COLOMBIA

and even from behind the Iron Curtain!

In this country, their success has been phenomenal: more than 1,400 users have taken the trouble to write us — a most impressive tribute. The amazing quality of reproduction at remarkably low cost is made possible only by the Whiteley patented Cambric Cone, and by our specialisation and complete control of manufacture from raw material to finished product.

Write for dimensional drawings of suitable cabinets and leaflet giving full technical details, or ask your dealer to demonstrate. Alternatively, these speakers may be heard at our London Office, 109 Kingsway, W.C.2, any Saturday between 9 and 12 noon.

WHITELEY ELECTRICAL RADIO CO. LTD MANSFIELD ' NOTTS

Stentorian HIGH FIDELITY UNITS

WITH THE PATENTED CAMBRIC CONE

MODEL H.F.610. 6" Steel unit, incorporating 10,000 gauss magnet. Handling capacity. 3 watts. Frequency response, 60 c.p.s.-12,000 c.p.s. Bass resonance, 70 c.p.s. Price <u>£2,10.6</u> (Tax Paid)

MODEL H.F.810. 8" Steel unit, incorporating 10,000 gauss magnet. Handling capacity, 5 watts. Frequency response, 50 c.p.s.-12,000 c.p.s. Bass resonance, 65 c.p.s. Price £3.0.6 (Tax Paid)

MODEL H.F.912. 9" Die-cast unit, incorporating 12,000 gauss magnet. Handling capacity, 7 watts. Frequency response, 40 c.p.s.-13,000 c.p.s. Bass resonance, 45 c.p.s. Price £3.7.0 (Tax Paid)


MODEL H.F.1012. 10" Die-cast unit, incorporating 12,000 gauss magnet. Handling capacity, 10 watts. Frequency response, 30 c.p.s.-14,000 c.p.s. Bass resonance, 35 c.p.s.

Price £3.13.6 (Tax Paid)

Transformer available if required All models available either 3 or 15 ohms.



Prov. Pat. 10037/53

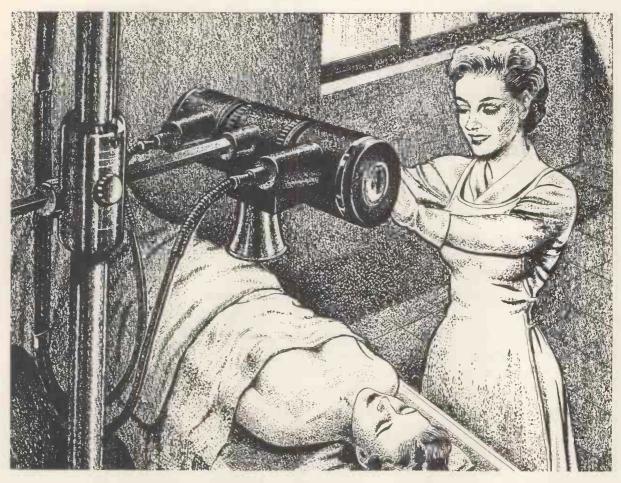

Correct Diagnosis depends upon CONSTANT VOLTAGE

Medical science to-day relies to an increasing degree on electronic instruments for the diagnosis of disease. The accuracy of the results obtained is of vital importance and is dependent on the reliability of the electricity supply available. ADVANCE Constant Voltage Transformers provide the means for regulating the inevitable fluctuating mains voltages which both shorten the life and impair the efficiency of such equipment. They are used in many hospitals and medical laboratories for this very purpose. A wide range of models is available with ratings from 4 watts to 6 kilowatts. All these models provide a stabilized output voltage to within ± 1 per cent for mains variations of up to ± 15 per cent.

Full details given in folder W/15 gladly sent on request.



ADVANCE COMPONENTS LTD., MARLOWE RD., WALTHAMSTOW, LONDON, E.17 GD

Phone : LARkswood 4366

Recondition

Certainly-

if it's an 'English Electric' T901A

all Munun

Every home constructor will appreciate 'English Electric's 'unique C.R. Tube Reconditioning Service. It means that when your C.R.T. ceases to work, you can, if it's an 'English Electric' metal tube in physically sound condition, take it to your dealer and exchange it for a good-as-new and guaranteed one—for f_{12} . A nice little saving of f_{10} for you.

Write to 'English Electric' for a complete specification of the T901A the finest tube that any constructor can buy, and you have started saving money right away.

*The tube specified by the designers of the 'Tele-King', 'Magnaview' and 'Super-Visor' circuits and 'Viewmaster' conversion circuit.

* ENGLISH ELECTRIC'T901A THE BRITISH MADE LONG-LIFE RECONDITIONABLE TUBE

If you have any difficulty in obtaining supplies write to:

The ENGLISH ELECTRIC Company Limited, Television Department, Queens House, Kingsway, London, W.C.2

a C.R.T. Z

WIRELESS WORLD

JUNE, 1954

1 kW Channelised Transmitter

THE GFT.560 is a 1kW channelised transmitter with

a frequency range of 1.5—30 Mc/s. It consists of three basic cabinets—r.f. unit, modulator unit, and power supply unit—combinations of which can be used to provide multi-frequency working as well as a number of different types of emission. The wave change facilities of the transmitter are both rapid and reliable—a valuable asset when the operating frequency is changed many times each day.

The GFT.560 is fully tropicalised, and its unit construction facilitates future expansion of the initial installation, should the need arise.

For use in conjunction with the GFT.560 there are ancillary units that enable the transmitter to be remotely controlled over a two wire telephone circuit : operational adjustments are dialled to the transmitter.

The versatility and reliability of this new Mullard transmitter make it particularly suitable for h.f. en-route, ground-to-air services and pointto-point communication networks. A team of Mullard communication engineers is available to advise on the use of the GFT.560 in such applications. They will also assist in planning complete communication systems, if required.

ABRIDGED DATA

Frequency Range 1.5 — 30 Mc/s Frequency Stability To Atlantic City, 1947, standards Power Output 1 kW Types of Emission c.w., m.c.w., telephony, frequency shift, single and independent sideband. (A1, A2, A3, F1, A3a and A3b) Output Impedance 600 ohms balanced twin feeder Power Supply 400Y, 50-60 c/s, 3-phase



SPECIALISED ELECTRONIC EQUIPMENT

MULLARD LTD . EQUIPMENT DIVISION . CENTURY HOUSE . SHAFTESBURY AVENUE . WC2

(MI434)

1

1

TAR COM NUM

1

Constant of

١

P

١

ij.

1

MANUFACTURERS OF EQUIPMENT, and DEVELOPMENT GROUPS are invited to send today for this NEW complete catalogue of Ediswan Clix Radio, Television and Electronic Components. Just write "Components Catalogue please" on your business letterhead and we will send you a copy.

EDISWAN

RADIO COMPONENTS

THE EDISON SWAN ELECTRIC COMPANY LIMITED, Member of the A.E.I. Group of Companies155 Charing Cross Road, London, W.C.2 and Branches. Telephone: Gerrard 8660. Telegrams: Ediswan, Westcent, London.C.R.12Radio Components Sales Office: 21 Bruton Street, London, W.1Telephone: Mayfair 5543

WIRELESS WORLD

JUNE, 1954

... more than you BARGAIN FOR!



16

DON'T be caught on the horns of a dilemma ! Be-aware of the power, quality and performance that Osmor "Q" range Coilpacks provide. Miniature in size, moderate in cost they have everything that only the highest degree of long practised technical skill can ensure—extra selectivity, super sensitivity, adaptability. Size only l² x 3½ x 2¼, with variable iron-dust cores and Polystyrene formers. Builtain trimmers. Tropicalised. Prealigned, receiver-tested and guaranteed. Only 5 connections to make. All types for Mains and Battery superheets, and T.R.F. receivers. Ideal for the reliable construction of new sets, also today for particulars !

today for particulars !

SEPARATE COILS: A full range is available for all popular wavebands and purposes. Fully descriptive leaflet and connection data available. Just note these "5 Star Features." ★ Only lin. high. ★ Packed in damp-proof containers. * Variable iron-dust cores. * Fitted tags for easy 4/ connection. 🛨 Low loss Polystyrene formers. each



A Spotlight on another of the Colls in the Osmor "O" Range. M.W. TRF REACTION COIL

TYPE Q R 11 **4**'o 3-winding coil for

use in an aerial or HF use in an aerial of HF stage with variable cores. (Matches with coil QAII or QHFII at 4/- each if required). For L.W. similar coils QRI2 (4/9) QAI2 and QHFI2 (4/- each) are available available.

TWO for the Price of ONE

The NEW OSMOR **CHASSIS CUTTER**

An inexpensive but invaluable tool of entirely An inexpensive but invaluable tool of entirely new design. Cuts two hole sizes with any one reversible punch and die; and can be operated with a spanner or tommy-bar, Blanks easily removed. For use on steel up to 18 s.w.g. Brass and Dural up to 16 s.w.g. Aluminium and Copper up to 14 s.w.g







Lines-you're on the right lines!



A U T O M A T I C F R E Q U E N C Y MONITOR (1 Mc/s)

Designed for the measurement of any frequency in the range 10 c/s

to 1 Mc/s with a basic accuracy of \pm 0.005% \pm 0.1, 1.0, or 10 c/s.

Higher accuracies available if required. The unknown frequency is determined by counting the number of cycles that pass through a 'gate'

open for a selectable time interval of 0.1, 1.0, or 10 seconds. The

result is presented on six panel mounted meters each scaled 0 to 9 and is in decimal notation. Full information available on request.

GINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

WORSLEY BRIDGE ROAD · LONDON · SE26

Telephone HiTher Green 4600

SALES AND SERVICING AGENTS

00000

F. C. Robinson & Partners Ltd., 287 Deansgate, Manchester, 3 Hawnt & Co. Ltd., 59 Moor St. Birmingham, 4 Atkins, Robertson & Whiteford Ltd., 100 Torrisdale Street, Glasgow, S.2

Approved to ENTIRELY NEW Inter-Service Standards

A miniature range of Hunts Electrolytics approved to Inter-Service standards RCS 134 Issue 3 and RCL 134 Addendum Issue 2. Temperature range:

 -30° C to $+70^{\circ}$ C max. Please write for leaflet giving details of complete range.

		_				
	TYP	E L31/1.	PATTERN	CE4.	CLASS HI	_
Сар µF	Peak Working Volts at 70°C.	Max. R.M.S. Current at 50/c/s (mA)	L.	inches) D.	List Number	Inter-Service Cat. Number
50	25	70		5	JB 53AKZ	Z145512
100	25	100	134	5050	JB 54KZ	Z145514
1000	25	600	3		JB 57KZ	Z145520
25	50	60	$\begin{vmatrix} \frac{1}{4} \\ \frac{3}{4} \end{vmatrix}$	5	JB102BKZ	Z145508
50	50	100	$\left \frac{3}{4}\right $	5050	JB103KZ	Z145513
500	50	450	3		JB106AKZ	Z145519
8	150	60	14	5	BI53BKZ	Z145502
16	150	90		<u>ମ</u> ାପ୍ତ ମ୍ବାପ ମାସ ମାସ	JBI 54KZ	Z145505
32	150	160	13	34	JB181KZ	Z145509
8	350	75	13	5	JB403KZ	Z145503
16	350	120	13	34	JB405KZ	Z145506
32	350	225	2		JB407AKZ	Z145510
4	450	50	$\frac{3}{4}$	5 8 3 4	JB552KZ	Z145501
8	450	100		34	JB553BKZ	Z145504
16	450	175	2	1	JB554AKZ	Z145507
32	450	275	3	1	JB555AKZ	Z145511
		PE L32/1.	PATTERN		CLASS HI	P.
3000	25	1100	41/2		KB 62KZ	Z145557
1500	50	1000	412	1 3	KBIIIKZ	Z145555
60	350	350	2	13	KB430KZ	Z145552
100	350	450	3	13	KB4IIKZ	Z145554
32	450	275	3	1	KB555BKZ	Z145551
60	450	450	3	13	KB581KZ	Z145553
1	ТҮР	E L32/3.	PATTERN	CE6.	CLASS HI	
32+32	350	200	2	13	KB4I7KZ	Z145601
60+100	3 50	400	41/2	13	KB420KZ	Z145603
60+250	3 50	400	4 <u>1</u>	34	KB422KZ	Z145605
100+200	350	550	$4\frac{1}{2}$	13	KB423KZ	Z145606
32+32	450	300	3		KB564AKZ	Z145602
60 + 100	450	550	41	13	KB565KZ	Z145604



TROL

All units are insulated by a Suflex sleeve and dimensions must be increased by $\frac{1}{6}$ " on the length and $\frac{1}{16}$ " on the diameter to allow for this sleeve.


CAPACITORS

REGISTERED TRADE MARK

A. H. HUNT (Capacitors) LIMITED WANDSWORTH LONDON S.W. 18 Tel: BATtersea 1083-7 Est. 1901 And in Canada • HUNT CAPACITORS (Canada) Ltd., AJAX, ONTARIO

8

Illustration Actual Size

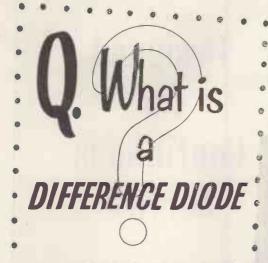

The XC14 Difference Diode is the latest sub-miniature cold cathode diode developed by Hivac especially for use in the telecommunications and computer fields A DIFFERENCE DIODE IS A COLD CATHODE DIODE CHARACTERISED BY A LARGE DIFFERENCE BE-TWEEN THE STRIKING AND MAINTAINING VOLTAGES.

tions and computer fields. The striking and maintaining voltages are controlled between limits giving a minimum difference of 70V, which makes the XC14 ideal for storing, counting, gating and similar functions in electronic circuits.

Phone : HARrow 2655



Characteristics of the XC14 DIFFERENCE DIODÉ

Strike Voltage.....145-170V. Maintaining Voltage at 0.5mA......75V maximum. Maximum continuous current rating.....0.75mA.



Cables : Hivac, Harrow.

Designed for Continuous Service

ATE/TMC Transmission equipment is designed to offer an operating administration the maximum facility in the performance of maintenance routines. Jack-in panel frames fitted with quickly detachable functional units ensure the most rapid form of servicing yet devised. You are invited to apply for a copy of "Unit Construction Practice" which describes the technique employed.

AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

Radio and Transmission Division, Strowger House, Arundel Street, London, W.C.2. Telephone: TEMple Bar 9262. Cablegrams: Strowgerex London. Manufacturers:—AUTOMATIC TELEPHONE & ELECTRIC CO. LTD., Liverpool and London. TÉLEPHONE MANU-FACTURING CO. LTD., St. Mary Cray, Kent.



A NEW-PRINCIPLE A-C AUTOMATIC VOLTAGE STABILISER

We can supply from stock all types of American tubes, condensers, valves, potentiometers, etc. We have now had released to us by a Government Department the design of our "A.C. Mains Regulator, Automatic, Step, Mark II", and are therefore manufacturing this unit for general sale. It ideally fills the need for a cheap, small and light Stabiliser. Although it measures only $8\frac{1}{2}$ in. x $4\frac{1}{2}$ in. x 5 in., weighs as little as 11 lbs., and costs only $\pounds 24$ net, it has a performance fully equal to any similarly rated Automatic Stabiliser of the resonated, saturated core type, without any of the disadvantages.

ASR-1150 has a pure output waveform, is unaffected by changes in mains frequency, and works equally well from no-load to full load, which is 1150 VA. It has a stabilised output at 230V unless otherwise ordered.

Many other Automatic Voltage Stabilisers are now manufactured by us, and all are available for immediate delivery. In some cases the constancy of output is as high as 0.15%. Models are available from 200 VA to 30 kVA, single phase. 3-Phase Stabilisers are also available. Prices are *extremely* competitive.

The NEW "ASR-1150" costs only £24 net

Complete information is obtainable from: **GLAUDE LYONS LTD.,** STABILISER DIVISION, QUEEN'S HOUSE, 180-182 TOTTENHAM COURT ROAD, LONDON, W.1 (Telephone MUSeum 3025-6 Ext. 13)

MEMO: If you are interested in infinitely-variable Transformers, do not forget the almost indispensable "VARIAC" (Reg'd. Trademark). Models are available from 170VA to 21kVA. Our Catalogue V-549 (3rd Edition) tells the whole story, and will gladly be mailed free and post free, on request.



RCA is first choice for television equipments

RCA TELEVISION in the Philippines and Thailand has quickly followed the first TV installation in Asia in 1953. The first transmitter in Japan has now expanded to three ... all completely RCA-equipped.

So the tremendous educational and cultural capacities of television are being introduced 'round the world . . . the most powerful means ever conceived for public enlightenment and international understanding.

Abroad, as in the U.S.A., RCA provides everything for television . . . from camera to antenna, from mobile remote units such as pictured here to complete studio and transmitter equipments. RCA also makes available the services of distributors and companies long versed in the electronic needs of their countries.

You can look with confidence to RCA for this complete co-ordinated service . . . manufacturing, installation facilities, instruction, servicing . . . *everything* that goes to make RCA TV such a dependable instrument of education and enjoyment throughout the world.

Your RCA distributor or company will gladly tell you about RCA TV; or write to RCA International Division.




RCA produces complete TV studio equipments, from microphones to monitoring consoles. This scene shows a broadcast from the RCA-equipped station DZAQ-TV, Manila.

World Leader in Radio First in Recorded Music First in Television



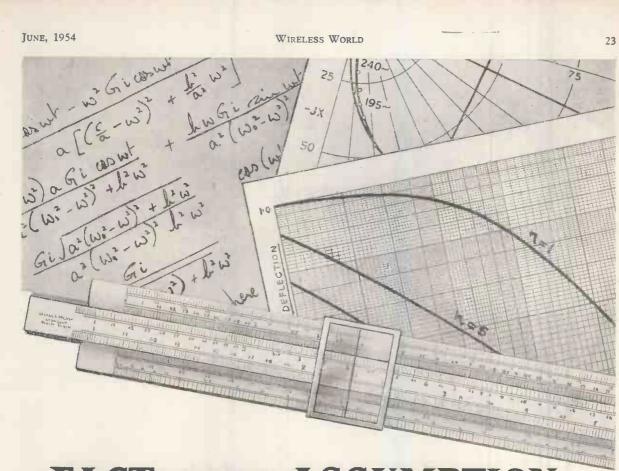"Marca Registrada" **RADIO CORPORATION of AMERICA** RCA BUILDING 30 ROCKEFELLER PLAZA, NEW YORK, N.Y., U.S.A.



FACT versus ASSUMPTION


Vibration effects can be assessed by assumption, estimation and long calculation. Prototypes can be built on those assumptions, but with many anxious moments awaiting operational test results—results moments nullify months of patient effort. It is much simpler, and certainly more economical, to conduct preliminary tests in the laboratory by creating vibrations under controlled conditions—and so obtain the facts. That is the precise function of Goodmans Vibration Generators. They provide vibratory sinusoidal forces at controlled frequency and amplitude, by which specific vibratory conditions over a wide frequency range can be accurately simulated to assess their effects on materials, structures and components.

Applications include FATIGUE TESTING, ELEC-TRICAL COMPONENT TESTING, VALVE MIC-ROPHONY TESTING, TORSIONAL VIBRATION TESTING, FLEXURE TESTING OF METALS AND PLASTICS, ETC., AND MECHANICAL STRUCTURE TESTING.



VIBRATION GENERATORS

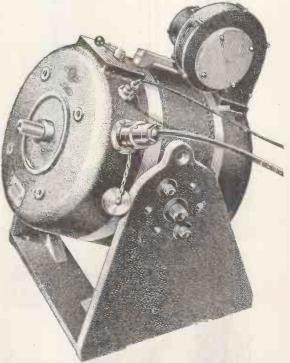GOODMANS INDUSTRIES LIMITED. Axiom Works, Wembley, Middx. Tel: WEMbley 1200 (8 lines)



The range includes models from the 8/600 illustrated. developing a force of \pm 300lb. to the midget model with a force of \pm 2lb.

No Second Chance . . . ?

When there's a special recording to be done ... when there's no chance of a second take, or repeats will send costs soaring — that's when you need the M.S.S. White Label Master Disk.

Out of every hundred recording disks made at M.S.S. most are graded as excellent for direct play-back, but only about <u>three</u> meet our stringent demands for master recordings. That will give you an idea what we mean by perfection! And that is why so many of the World's recording and broadcasting companies rely upon M.S.S. Disks. There is a range of M.S.S. Disks to suit all types of recording work. May we send you further information?

MSS direct recording disks




M.S.S. RECORDING COMPANY LTD, POYLE CLOSE, COLNBROOK, BUCKS, ENGLAND. COLNBROOK 284.



Second Way, Exhibition Grounds, Wembley, Middlesex. Telephone : Wembley 1212

· Some alored

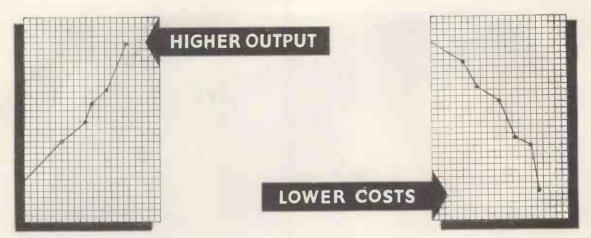

See the latest equipment for speeding production at Britain's fourth **MECHANICAL HANDLING** EXHIBITION & CONVENTION

OLYMPIA · LONDON · 9-19 JUNE 1954

MECHANICAL HANDLING is so important that no industry can function properly without it ; unnecessary work is eliminated, bottlenecks are overcome, and production is increased many-fold. Britain's Mechanical Handling Exhibition and Convention—held every second year—is the biggest of its kind in the world. Nowhere else can you see such a comprehensive range of equipment, or hear experts in so many industries discuss the latest machines and methods.

This year's Exhibition will demonstrate the enormous strides made in handling techniques during the last two years, and bring to the Convention platform Britain's leading mechanical handling engineers who will point the way to higher output at lower cost. Plan your visit today! Post the coupon for details.

The world's largest display of

Conveyors, clevators, hoists, stackers, cranes, mechanical loaders and shovels, fork lift trucks, industrial trucks, coal handling plants, overhead runways, aerial ropeways, grain handling plant, wagon tipplers, pneumatic installations and ancillary equipment.

Many working exhibits

So vast is this exhibition that ample floor space is provided for much of the equipment to be demonstrated under working conditions.

Special Facilities:

Full information service; free consulting bureau; overseas visitors' reception and lounge; industrial cinema; post office, etc.

Organized by 'MECHANICAL HANDLING'-the journal of industrial mechanization



To: 'Mechanical Handling,' Dorset House, Stamford Street, London, S.E.I. Please send me the 1954 Exhibition Brochure with details of Convention, free season ticket, etc. NAME________ADDRESS _______

AD

Potted with 'Araldite'

For potting and sealing electrical components, 'Araldite' is without equal. In addition to its remarkable electrical and mechanical qualities, 'Araldite' offers outstanding adhesion to metals, whilst shrinkage on setting is exceptionally low. 'Araldite' is resistant to high temperatures, humidity and corrosive agents and satisfies the Services specification for the sealing and potting of electrical equipment. This new epoxy resin is being extensively used for potting and sealing components for radio, electronics and electrical engineering. Our illustration shows an inductance and mica dielectric capacitor network for shaping a transmitted radar pulse. Potting in 'Araldite' *Photo by courtery of Telegraph Condenser Company Ltd.*

reduction in size and weight.

13 kV. PK. PFN 55 Ω 0'5μSEC. 2000 PRF.

T.C.C

These are the new Epoxies! "Araldite" (regd.) epoxy resins are obtainable in the following forms:—

Hot and cold setting adhesives for metals and most other materials in common use.

• Casting Resins for the electrical, mechanical and chemical engineering industries.

 Surface Coating Resins for the paint industry and for the protection of metal surfaces.

Full details will be sent gladly on request.

'Araldite'

epoxy casting resins

Aero Research Limited

A Ciba Company, DUXFORD, CAMBRIDGE. Telephone: Sawston 187

\$ 264-65

28

REAL HIGH FIDELITY at modest cost.

• Manufacturer-to-Consumer policy saves you one-third cost ! !

We are now specialising in the supply of units for making up high-fidelity Radio and Record-reproducing Equipments for use in the Home, small Halls, Schools and Gramophone Societies and single items for replacing in existing equip-ments and radiograms.

Our Chief Engineer, who is operating a Technical



No. 1 "SYMPHONY" AMPLIFIER is a 3-channel S-watt Gram/Radio Amplifier with asconishingly flexible tone control. You can lift the treble, the bass, or-and here is the unique feature--the middle frequencles to suit your own ear characteristics and the record or radio programme being heard. It is thus possible to arrange the frequency-response of the amplifier to a curve equal and opposite to the resultant curve of the other items in the chain so that what finally registers in the brain is as per original. This flexibility of control is far more impor-tant than mere nominal linear response of the amplifier Scratch-Cut is also fitted and special negative-feedback circuit employed. The Amplifier can accommodate a wide variety of records from old 78's to new L.P.'s. Input is for all types of pick-up of 0.2v. output or more and there is full provision (and power) for Radio Tuner. It is available to match 2/3 or 15 ohms speakers. Price: 10 gns. (carriage 5/-). Fitted in Portable Steel Cabinet, 35/- extra.



No. 2" SYMPHONY " AMPLIFIER as No. I but with No. 2" STMPHONT "AMPLIFIER as No. 1 but with IC-watt Push-Pull triode output and triodes throughout. Woden mains and output transformers and choke. Full provision and power for Tuner. Output tapped 3, 7.5 and IS ohms. Competes with the most expensive ampli-fiers on the market yet costs only IS gns. (carriage 5/-). Fitted in portable Steel Cabinet 2 gns. extra.



SYMPHONY " AMPLIFIERS with REMOTE CONTROL. Both the above model Amplifiers are avail-able with all controls on a separate Control Panel with up to 4 feet flexible cable which simply plugs into the ampli-fier. Enables the Amplifier proper to be sat in the bottom of a cabinet whilst the controls are mounted conveniently higher up. Extra cost 2 gns.

" STUDIO SYMPHONY " AMPLIFIERS, Models I and 2, new models specially designed to get the maximum out of the revolutionary new Collaro Studio pick-ups and heads type "P." Specification as per our Standard out of the revolutionary new Collaro Studio pick-ups and heads type "P." Specification as per our Standard Symphony models but with high-gain, low-noise, built-in Pre-amplifier stage with separate switched correctors for Std. and L.P. Third position on switch provides input matching for Acos and similar output pick-ups. These remarkable new models thus provide all the facilities and matching of our Standard Symphony Amplifiers PLUS the specialised Collaro matchings. See March issue of "The Gramophone" for review of these Instruments. Price: No. 1, £12/7/6; No. 2, 17 gns. Carriage 5/- Guidance Service, is available daily, including Saturdays, from 10 a.m. to 6 p.m., or will deal with enquirles by return of post. Our new illus-trated Catalogue and Supplement will be a great boon to those desiring high quality equipment for modest expenditure. Send two 24d. stamps for your copy now. It may well save you pounds.

GARRARD 3-SPEED GRAM UNIT MODEL "TA," fitted with the latest High-Fidelity Acos HGP35 Pick-up Heads (one for Std. and one for L.P.). Price El2/15-, post and pack. 2/6. Heads only, 43/- each, post 1/-.

MODEL "TB," as above, but with two separate Decca XMS Heads, £13/17/6, post and pack. 2/6. Or with two separate Decca Crystal Heads £12/5/-. Or with Garrard Head for fibres (78) and Decca Crystal for L.P., £12/5/-. COLLARO latest model A.C.3/544 3-SPEED GRAM UNIT, with new "STUDIO" Pick-up type "O" or "P," £10/6/1, post 2/6.

COLLARO latest model 3RC531 AUTOCHANGER COLLARO latest model 3RC531 AUTOCHANGER We are pleased to say that after most careful and rigorous, trial, we can highly recommend these latest improved Auto-Changers by Collaro. The standard of engineering is of the highest and in addition to being very easy and quick and fool-proof in operation, they are fitted with the revolutionary high-fidelity plug-in "STUDIO" Pick-up heads of which the Type "O" is matched to radio sets and medium-gain amplifiers and the Type "P" is designed for high-gain amplifiers. The Type "P" is exactly matched to our new model Studio Symphony Amplifiers. The price complete with either type pick-up head is £15(3)-. The 3RC522 as above, but mixes 10-inch and 12-inch records, costs £17/10/-. Carriage 5/-. Delivery from stock. Illustrated Leaflet 2¹/₂d.

COLLARO "STUDIO" PICK-UP (Arm and Head) type "O" or "P," 74/8, post 2/-.

NEW TYPE ACOS PICK-UPS. Arm with one HGP39 head (Standard or L.P.), £3/8/9, or with both heads, £5/11/-. Post 1/6. Heads separately, 42/3d. each. Immediate delivery

TAPE RECORDING EQUIPMENT. We recommend TAPE RECORDING EQUIPMENT. We recommend and have in stock for immediate delivery the latest TRU-VOX TAPE DECK at 22 gns., a suitable high-fidelity Tape/Gramophone/Microphone/Radio Amplifier to match at 16 gns., and a Portable Cabinet to house these and speaker at 95/-. Also a new Complete Recorder in-corporating above Deck and Amplifier with actual space for fitting Radio Tuner. Price 49¹/₂ gns. Leaflets 7¹/₂d.




WE OLD CODGERS have fallen in love at last—with a wizard Tape Recorder and 'struth it is the new GRU NDIG 700L. There is no doubt in our mind that this is the finest Tape Recorder under £100 on the market today, and we recommend it to all those desiring to acquire a real high.fdairx Recorder for both real high-fidelity Recorder for both speech and music. Price 80 gns., complete, or £28 down and 5 gns., per month for 12 months. Call for a Demonstration or send $2\frac{1}{2}d$. for Leaflet.

GOODMANS CORNER CABINETS (left) for the AXIOM ISO Mark 2 manufactured by us to measurements. Height, 46in. Price: complete kit in plain board with felt, 8 gns. Price ready built, 10 gns. Finished in figured walnut, 16 gns. Other veneers to order. Carriage extra according to area. "(SYMPHONY" BASS REFLEX CABINET KITS. 30in high constituted followed with the heavy inter a pon-

"SYMPHONY" BASS REFLEX CABINET KITS. 30in. high, consist of fully-cut gin. thick, heavy, inert, non-resonant patent acoustic board, deflector plate, feit, all screws, etc., and full instructions. 8in. speaker model, 85/-; 10in. speaker model, 97/6; 12in. speaker model, 45/7/6. The design is the final result of extensive research in our own laboratory and is your safeguard of optimum acoustic results. Carriage 7/6. Ready built, 10/6 extra.

HIRE PURCHASE FACILITIES NOW AVAILABLE on orders of £15 or over. Send one-third deposit with order, balance over 6 or 12 monthly instalments. State which required.

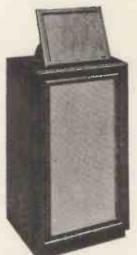NORTHERN RADIO SERVICES II & 16 KINGS COLLEGE RD., ADELAIDE RD., LONDON, N.W.3. Phone: PRImrose 8314 Tubes: Swiss Cottage and Chalk Farm. Buses: 2, 13, 31, 113, 187,




REGD. DESIGN

"SYMPHONY" BASS REFLEX CABINETS, fully finished in figured walnut, oak or mahogany to above Regis-tered Design and to match our Console Amplifier Cabinet, cabilize the burnis of subto enabling the housing of a whole enabling the nousing of a whole equipment in a two-plece suite, cost: [2in. speaker model, £11/101-; 10in., £11; Bin., £10/10/., Carriage according to area. The I0in. model is ideal for the WB HF fol2 (see "The Gramophone" review March). March).



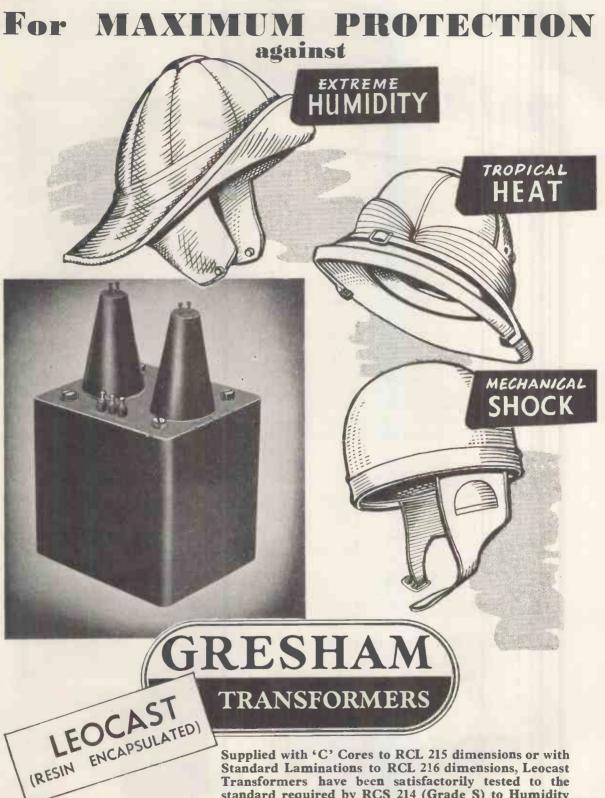CONSOLE AMPLIFIER CONSOLE APPLITER CABINETS (above), 33in, high, lift-up lid with piano hinge, take Gram Unit or Auto-changer, Amplifier, Pre-ampli-fier, and Radio Feeder Unit, finished medium walnut veneer. De Luxe version, 10 gns., carriage according to area. Bass Reflex Cabinets to match available as above.



Standard Laminations to RCL 216 dimensions, Leocast Transformers have been satisfactorily tested to the standard required by RCS 214 (Grade S) to Humidity Class H.1. The dielectric qualities of the resins used make Leocast Transformers particularly suitable for high-voltage applications.

GRESHAM TRANSFORMERS LTD., TWICKENHAM ROAD, HANWORTH, MIDDX. FELtham 2271-4

29

HARACTERISTIC CURVES

APLODE

ANODE CURRENT IN AMPS

AVERAGE

If your field of design covers R.F. Heating it is highly probable that there is a place in your specification for the Ediswan E.S. 833.

DATA for the Designers File

The ES.833 is a high mu triode particularly suitable for use as an R.F. Power Amplifier, Oscillator or Class B modulator.

The anode and grid connections are brought out at the top and are taken through metal to glass seals to heavy current terminals. As a result of this construction the valve is exceptionally efficient at higher radio frequencies and may be operated under class "C' CW conditions at a maximum input of 2kW at frequencies up to 30Mcs. At reduced input rating it is possible to operate the valve as high as 75Mcs.


RATING

Filament Voltage (volts)	Vf	10.0
Filament Current (amps)	If	10.0
Maximum Anode Voltage (volts)	V _{a (max)}	3,0 00
Maximum Anode Dissipation (watts)	W _{a (max)}	300
Amplification Factor	μ	35
Maximum Operating Frequency at full rating		*30 Mc/s

* At higher frequencies the maximum permissible anode voltages and inputs must be reduced.

'Radyne' Pre-Heating Equipment incorporates the E.S. 833

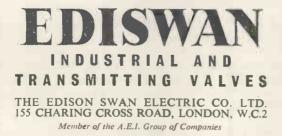This small dielectric oven will fully plasticise 6 ozs. of plastic material in one minute. The output of the equipment is approximately 600W. at a frequency of approximately 37 m/cs.



phone.

THE NEW with ALL Tape Recorder the ALL-R

SUITCASE TAPE RECORDER SPECIFICATION * Tape speed 7 in. per second. * Miniature Mullard valves. * Twin track heads. * Three specially designed recording motors provide fast forward run and 50 sec. rewind without unlacing tape. * INDEPENDENT forward run and 50 sec. rewind without unlacing tape. ★ INDEPENDENT BASS AND TREBLE CONTROLS for recording and playback. ★ Negligible wow and flutter. ★ Overall negative feedback. ★ 1,200ft. tape will provide ONE hour playing time. ★ Amplifier may be used independently for high quality record reproduction. ★ High flux speaker. ★ Provision for external speaker. ★ Romette Desk Micro-phone.

Because . . .

its unique lightweight custom-built chassis embraces the latest techniques of recorder construction.

its compact lightweight design features a detachable lid, giving complete access to the controls.

it is the smallest lightweight portable fully automatic tape recorder using 7in. Spools.

. . . and it costs only

HIRE PURCHASE £15/15/- deposit. 12 monthly instalments of 60/-, or 18 monthly instalments of 42/-. 12 monthly CREDIT TERMS. Send only £6 to secure with 8 further monthly payments of £6. Carr. and pkg. 15/-.

See them at the Radio Centre

E. & G. MAIL ORDER SUPPLY COMPANY 33 Tottenham Court Road, London, W.I Telephone : MUSeum 6667

COMPLETE WITH MICROPHONE AND TAPE

GNS.

Designed and manufactured by Tape Recorders (Electronics) Tape Ltd.

We stock and recommend these HIGH GRADE LOUDSPEAKERS. They are available under our PERSONAL CREDIT scheme as shown :---

	CASH	OREDIT SALE 9 payments	H.P. TERMS	
	PRICE	Send first payment with order	Deposit	12 monthly payments
WHARFEDALE W15CS Super I2CSAL W12CS W12CS W12CS W10CS (B) Golden 10 Bronze 10 Super 8CSAL Super 5 Super 5	$\begin{array}{c} \pounds 17 & 10 & 0 \\ \pounds 15 & 10 & 0 \\ \pounds 17 & 10 & 0 \\ \pounds 9 & 15 & 0 \\ \pounds 9 & 5 & 0 \\ \pounds 12 & 6 & 6 \\ \pounds 7 & 13 & 3 \\ \pounds 4 & 12 & 8 \\ \pounds 6 & 13 & 3 \\ \pounds 6 & 6 & 7 \\ \pounds 3 & 3 & 11 \\ \pounds 6 & 13 & 3 \\ \pounds 2 & 0 & 0 \end{array}$	42/10 39/4 42/10 26/2 24/8 31/10 21/8 14/6 19/5 18/9 11/5 19/5 8/6	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	22/- 20/7 22/- 14/2 13/4 16/11 11/10 8/2 10/9 10/1 6/6 10/9 5/-
W.B. 12in. Concentric Duplex (less transformer) Do., (with transformer)	£22 11 0 £23 16 0	57/11 60/-	£7 10 4 £7 19 0	29/6 30/9
10in. Concentric Duplex (less transformer) Do., (with transformer) Tweeter Unit HF610 High Fidelity HF810 High Fidelity HF912 High Fidelity HF912 High Fidelity HF1012 High Fidelity	£9 7 6 £10 15 6 £3 15 6 £2 10 6 £3 0 6 £3 7 0 £3 13 6	24/11 28/- 12/- 9/- 10/- 11/- 12/-	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	13/9 15/4 7/6 6/- 6/6 6/11 7/3
GOODMANS Axiom 22 Axiom 101 Axiom 102 Axiom 150	£14 14 0 £6 12 1 £9 18 0 £10 5 6	37/6 19/2 26/5 27/-	£5 4 0 £2 4 0 £3 6 0 £3 8 6	19/2 10/7 14/4 14/9



THE BURGOYNE CUSTOM BUILT 8 VALVE Superhet

Radiogram Chassis SPECIFICATION KAOIOGRAM GRASSIS * Extra large fully illuminated coloured tuning scale 113/in. * 64/in. * Wavebands 16-50; 1900-550; 1,000-2,000 metres. * Bass and treble controls for cut and lift. * Magic eye tuning indicator. * Precision flywheel tuning. * Chassis size 12/in. * 7/in. * Over-all height 9/in. Chassis size 12/in. * 8 Mazda valves 6C9, 6F15, 6L1, 6LD20. UU7, 6MI and (2)6P25. * Speech coil impedance 3 or 15 ohms. * Extension speaker sockets. * Specifically designed for perfect reproduction of the LONG PLAYING record. * Brilliant reproduction on radio. * TWO YEARS' GUARANTEE. SPECIFICATION

24 GNS 200-250v. A.C. 50 c/s ONLY

HIRE PURCHASE Deposit 154/- with 12 monthly payments of 29/-. CREDIT SALE TERMS No Deposit, 9 monthly payments of 59/- the first payment being sent with your order. Carr. and Packing 7/6 extra

31

JUNE, 1954

A New Portable Wave Analyser THE WAYNE KERR MODEL A.321

An audio frequency analyser of the heterodyne type to measure the relative levels of the components of a complex waveform down to -75 db below fundamental.

It is light, compact and simple to operate and can be supplied either in a transportable case or for standard 19 rack mounting.

Specification

FREQUENCY COVERAGE: 50-20,000 c/s in two ranges

FREQUENCY STABILITY: Better than $\pm 1\%$

INPUT LEVEL:

FREQUENCY RESPONSE: ACCURACY OF HARMONIC MEASUREMENTS:

INPUT IMPEDANCE: SELECTIVITY:

HUM LEVEL: POWER SUPPLY: POWER CONSUMPTION: DIMENSIONS: WEIGHT:

Between -20 and +20 db relative to ImV into 600 ohms adjusted by a 5 step attenuator and fine control of 0-10 db Flat to within ± 1 db over the whole working range. **LEVEL STABILITY:** ± 1 db if mains supply voltage remains within $\pm 5\%$ Harmonics below fundamental to $-55 \text{ db} \pm 5\%$ to $-75 \text{ db} \pm 10\%$ or $\pm 1 \text{ db}$ whichever is the greater. 100,000 ohm unbalanced (greater than 25,000 ohm. balanced, can be supplied to order) Constant over the frequency range. 2 stage crystal filter, mid band frequency 100 Kc/s. Flat top $(\pm 1 \text{ db})$ pass band extending over 10 c/s ± 1 c/s. -55 db 110/115 and 200/250 volts 40/60 c/s

> Approx. 60 watts In case 20" × 9" × 81 31 lbs. approx.



THE WAYNE KERR LABORATORIES LIMITED . NEW MALDEN . SURREY . MALDEN 2202

WIRELESS WORLD



THE PF91 amplifier, with its PF91A remote control unit, is the culmination of many years of research into the problem of Hi Fi reproduction. Its performance will astound the ordinary listener and critical engineer alike. Record players, tape recorders, microphones or radio tuners can be used with the PF91-a versatile and practical unit for those who demand perfect sound reproduction in the home, the school, the broadcasting studio or the social club.

POWER AMPLIFIER PF91.


26 db negative feedback and an output from 2 c.p.s. to 160,000 c.p.s. (over 16 octaves).

A combination of negative and positive feedback raises the damping factor of the amplifier to infinity thereby ensuring full control of loudpeaker speech coil movement.

The accurate reproduction of sounds rich in harmonics sets a new standard in the enjoyment of modern recordings.

The output transformer is a specially designed component to meet the exacting specification of the amplifier.

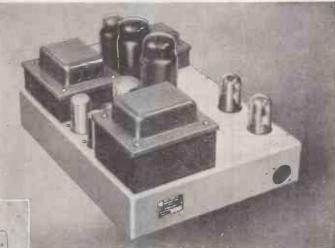The Power Amplifier is capable of handling peak power pulses in excess of the maximum rating without noticeable distortion.





REMOTE CONTROL UNIT PF9IA.

This unit enables remote control of the amplifier up to a distance of 20 ft. (6m).

Cathode follower output from the Remote Control unit reduces cable losses when the Power Amplifier is remotely controlled.

Four switched inputs and the choice of three equalisation networks for L.P., N.A.B. and 78 recording characteristics.

Continuously variable lift and cut controls for bass and treble with clearly marked level positions.

Incorporates a treble filter control, giving three sharp cut-off frequencies and an unrestricted response position.

The Pre-Amplifier incorporated ensures sufficient gain on all inputs for the full loading of the Power Amplifier.

E

в

JUNE, 1954



The performance of only as good as

Multiway Plugs and Sockets for quick action and positive contact


These reliable Plugs and Sockets, proved in service, provide a quick positive connection for up to 28 terminations. They need lower insertion pressure per contact than any comparable product, and when fully mated a dust and damp proof seal is provided between Plug and Socket. Considerable latitude in matching can be allowed when they are used in rack mounting applications.

These components are in regular use by :-- The English Electric Co. Ltd., Messrs. Marconi's Wireless Telegraph Co.Ltd. and Messrs. Standard Telephones& Cables Ltd.

WIRELESS WORLD

any equipment is its terminals



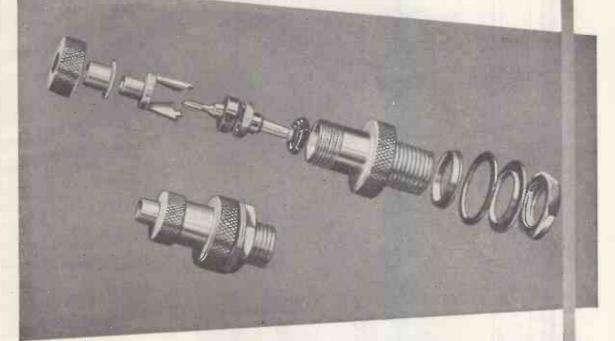

These versatile Miniature connectors provide perfect coupling between co-axial cables and instruments, and are extensively used in Television, Radar, and Communications equipment. They are 100% pressure and flash tested before despatch. The full range consists of a variety of Cable and Panel Mounting units of either plug or socket type, and a recent addition is an elbow connector for applications where it is desired to keep the face of the panel clear. Suitable for use with co-axial cable Uniradio 32 and 43. Miniature hermetically sealed Co-axial Plugs and Sockets to RCS.322

POWER CONTROLS LIMITED

EXNING ROAD, NEWMARKET. TELEPHONE NEWMARKET 3181 .

JUNE, 1954



SIGNAL GENERATOR

Band 3 for TV.

Are your laboratories suitably equipped to investigate the many problems relating to the design of receivers to handle commercial television on Band 3? One of the essential pieces of test gear is an AM/FM Signal Generator, such as GM.2889.

Features :---

- Frequency range 5-225 Mc/s in one band.
- 2 Marker oscillator 15-30 Mc/s.

RANSFORMER CO. LTD

- 3 A.M. Modulation int. 400 c/s ext. 0-10 Mc/s.
- 4 F.M. Modulation sweep 0-15 Mc/s.
- 5 Output impedance 75 and 300 ohms.

INDUSTRIAL X-RAY EQUIPMENT · ELECTRONIC APPARATUS LAMPS AND LIGHTING EQUIPMENT · ARC AND RESISTANCE WELDING PLANT AND ELECTRODES · MAGNETIC FILTERS BATTERY CHARGERS AND RECTIFIERS · H.F. HEATING GENERATORS • RADIO AND TELEVISION RECEIVERS





(PI 410 REV.)

INDUSTRIAL ELECTRONICS

This Woden Transformer is typical of many supplied for Industrial Electronics and is for incorporation in a large R.F. Heater made by a well known manufacturer. Transformers in this field are individually and specially constructed to suit design of heater. Price is an important factor and all Woden Transformers are built at the lowest cost, consistent with first-class workmanship and materials, to guarantee the utmost reliability in service.

WODEN TRANSFORMER CO. LTD.

MOXLEY RD., BILSTON, STAFFS. Telephone: Bitston 41959

sm/W. 2097 a.

DUBILIER HIGH STABILITY RESISTORS

Some outstanding features :

- 1. Dubilier High Stability Resistors have a low temperature coefficient of resistance not exceeding minus 0.03% for values up to $100K\Omega$ and not exceeding minus 0.04%per °C for values above 100 K to 1 mΩ.
- 2. The voltage coefficient is low and does not exceed 0.002% per volt applied. The noise level is very low and is less than 0.5 μ V per volt applied and in most instances is less than 75% of this value.
- 3. The resistors have excellent high frequency characteristics with low capacitance of the order of 0.5 pF and with an excellent inductance to resistance ratio.
- 4. The long term stability is excellent in both working and idling conditions and is of the order of 1%. The resistors are of particularly robust construction and suitable for use under the most stringent conditions.

Catalogue HSR 753 giving details of the full range of Dubilier High Stability Resistors will be sent to you upon request.

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, LONDON, W.3 'Phone : Acorn 2241 (5 lines) 'Grams : Hivoltcon, Wesphone. London Cables : Hivoltcon, London. Marconi International Code

مددب



Tannoy talking points ...

Transient Response

Transient response is an indication of the ability of a pick-up, amplifier or loudspeaker to follow accurately extremely rapid changes of state. The loudspeaker must not reproduce self generated sounds after the electrical input has ceased. Amplifiers must not mutilate wave forms, and gramophone pick-ups must be capable of following record grooves without wear on the record. All of these devices must possess adequate damping of an electrical and/or mechanical nature and have a basic frequency response extending well outside the normal audio range. All resonances must be suppressed and it is not sufficient to place them outside the audio range in the hope of maintaining the extreme limits of frequency response. Details of this nature are the subject of constant research by Tannoy development engineers - Practitioners in Sound. The Tannoy Dual Concentric Loudspeaker is one result of patient work by Tannoy Research Engineers. Its level frequency response from 20-20,000 c.p.s., excellent spacial distribution, and lower intermodulation products than many so-called high fidelity amplifiers, has earned for it an outstanding reputation throughout the World. Full technical details and suggestions for Enclosure designs may be obtained from



PRODUCTS LIMITED



Sound Practitioners


and the second

WEST NORWOOD, LONDON, S.E.27

TEL: GIPSY HILL II31

JUNE, 1954

Tor the LABORATORY and PRODUCTION LINE

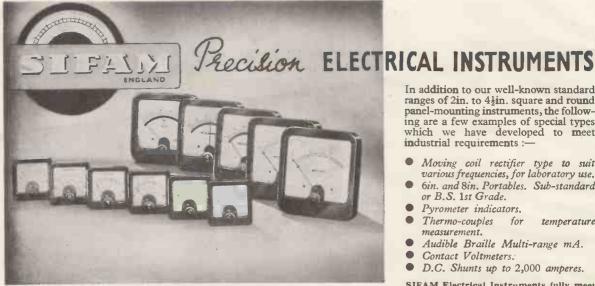

Write for illustrated catalogue detailing the wide SIFAM range. In addition to our well-known standard ranges of 2in. to 41 in. square and round panel-mounting instruments, the following are a few examples of special types which we have developed to meet industrial requirements :-

- Moving coil rectifier type to suit various frequencies, for laboratory use.
- 6in. and 8in. Portables. Sub-standard or B.S. 1st Grade.
- Pyrometer indicators.
- Thermo-couples for temperature measurement.
- Audible Braille Multi-range mA.
- Contact Voltmeters:
- D.C. Shunts up to 2,000 amperes,

SIFAM Electrical Instruments fully meet the high standards of accuracy and re-liability demanded by modern industrial techniques, production control, laboratory testing, etc.

SIFAM ELECTRICAL INSTRUMENT CO. LTD. Leigh Court, Torquay. Telephone : TORQUAY 4547-8



High quality material and dimensional precision are attributes of Bullers diepressed products. Prompt delivery at competitive prices.



for general insulation

We specialise in the manufacture of - PORCELAIN

REFRACTORIES for high-temperature insulation

FREQUELEX for high-frequency insulation PERMALEX & TEMPLEX for capacitors BLIC


ED


LLERS LIMI Porcelain Works: Sales Office: MILTON, 6, LAURENCE POUNTNEY HILL, TIPTON. STOKE-ON-TRENT LONDON, E.C.4 Stoke-on-Trent 5164 MANsion House 9971

Iron Works: STAFFORDSHIRE Tipton 1691

Standard

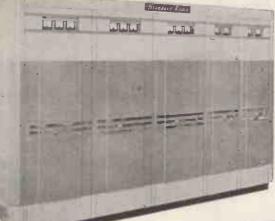in **G** Continents The D.S. Radio POINT-TO-POINT TRANSMOTTER



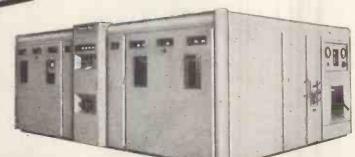

on Christmas Day, 1953.

owerful 40 kilowatt D.S.13's were used to transmit Her Majesty the

Queen's Speech direct from Auckland, New Zealand, to the United Kingdom

More than 180 of these transmitters are in use throughout the World

* Available for early delivery

D.S. series of transmitters $\star \star \star$				
*D.S.10	3/5 kW	kW Double Sideband		
*D.S.12		Independent or Single Sideband 🛣		
		Independent or Single Sideband 🛣		

Write for Radio leaflets : Type **D.S.10** No. 179/14 Type **D.S.12** No: 129/14 Type **D.S.13** No. 130/14





Standard Telephones and Cables Limited

Registered Office ; Connaught House, 63-Aldwych, London, W.C.2. RADIO DIVISION · OAKLEIGH ROAD · NEW SOUTHGATE . LONDON. N.I.I

С

JUNE, 1954





actual size

- Completely enclosed in high-grade phenolic mouldings, keeping resistance elements dust-free.
- Solder tags are heavily silver-plated and designed to withstand soldering heat and , bending without loss of rigidity.
- Spindles are fully insulated and provided with integral control knobs for finger or screwdriver adjustment.
- Tapped for 2-hole 6BA fixing on ³/₄" centres.

These Egen potentiometers are based on long experience of the needs of television and electronic equipment manufacturers.

EGEN ELECTRIC LTD

CHARFLEET INDUSTRIAL ESTATE - CANVEY ISLAND - ESSEX 'Phone: CANVEY 691 and 692



RADIO JACK



Extend the application of, and get greater enjoyment from, your Tape Recorder with the TRUVOX "Radio Jack"... designed to give you direct reception from either of two local stations (at the flick of a switch) or to make recordings, for future playback, of any of the programmes radiated by the selected stations. Housed in a cast case, jewel goldhammered finish : extremely simple to use and attractive in appearance. The "Radio Jack" can be used also with any amplifier having a high impedance microphone input jack. Connection to your instrument is simplicity itself... just plug it in by means of the BSS standard two-pole telephone jack which is an integral part of the design of this unique unit. It is only a $\frac{1}{4}$ in.

PRICE £2.18.6

(PLUS 21/5d. PURCHASE TAX)

Send now for full details to

TRUVOX LIMITED

Sales Office : 15 Lyon Road, Harrow, Middlesex. Telephone : Harrow 9282 Technical & Service Depts : 328 The Broadway, Station Road, Harrow. Telephone : Harrow 4455

Announcing the NEW **TEST OSCILLATOR No. 2 Type 872**

Frequency Range: 20-40 Mc/s.

40-80 Mc/s.

Output Level: $I\mu V$ to 100 mV from a source impedance of 75 ohms, $0.1\mu V$ to 10 mV from a source impedance of 7.5 ohms.


Attenuators: Step attenuators giving a complete coverage of the output signal levels in 2 db steps are provided.

Amplitude Modulation: Internal modulation of 30% at 1000 c/s. Frequency Modulation: Deviations continuously controllable from 0 to 40 kc/s at 1 kc/s.

Power Supplies: The instrument will operate from either a 12 volt D.C. supply or from 100-130 and 200-250 volts, 50 c/s mains.

THE TEST OSCILLATOR NO. 2 TYPE 872 has been developed and manufactured for the Ministry of Supply by Airmec in conjunction with the Signals Research and Development Establishment. It is a transportable, hermetically-sealed signal generator of very small size and extreme robustness, designed for use under field conditions in any climate, but it is equally suitable for employment in the laboratory or workshop.

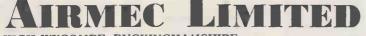Full details of this or any other Airmec instrument will be forwarded gladly upon request.



HIGH WYCOMBE, BUCKINGHAMSHIRE. Cables : Airmec, High Wycombe.

Tel. : High Wycombe 2060.



JUNE, 1954

If the bap Fits

No doubt about it — it's bound to be a perfect fit if it's a McMurdo CT8/P Cavity Cap! It's specially designed to fit the new television cathode ray tubes with cavity caps without soldering or loading. Here's how: we mould an A.H.T. connecting cable into a polythene shroud which acts like a suction cap and seals off the CRT cap. No soldering or loading is necessary so the possibility of a corona discharge around the tube connection is nicely avoided.

THE ·Mc MURDO · INSTRUMENT · CO · LTD

Victoria Works, Ashtead, Surrey • Telephone: ASHTEAD 3401

Here's quick, safe anchorage!

U.I.C. "Cactus" and "Porcupine" Tags and the almost limitless variety of Stand-Off Insulators will solve all your anchorage problems quickly, easily and efficiently.

These latest aids to neat and economical wiring and component assembly are tough, fireproof, and constructed entirely without solder. Only low-loss ceramics and electro-plated brass are used in the manufacture of these best of all anchorages.

Unique design

nsulation perfection

Gompetitive prices



Write for Catalogue Section 3a

UNITED INSULATOR COMPANY LIMITED OAKCROFT ROAD, TOLWORTH, SURBITON, SURREY Telephone : Elmbridge 5241-2-3-4

SPECIALISTS IN ELECTRO TECHNICAL CERAMICS & COMPONENTS - SPECIALISTS IN ELECTRO TECHNICAL CERAMICS & COMPONENTS

Introducing

THE FIRST OF THE "ELAC" RANGE OF ELLIPTICAL LOUDSPEAKERS

This new addition to the wide range of ELAC loudspeakers is particularly recommended for use with Television Receivers. The speaker gives a fuller bass response and a considerably clearer top response. The Magnet System is completely shrouded, which reduces stray magnetic field to the absolute minimum. Available in Flux Densities 6,500 and 9,500 gauss.

Prices: 4 x 7G (Type No. 47/90), 19/10 inc. P.T. 4 x 7D (Type No. 47/91), 25/1 inc. P.T.

ELECTRO ACOUSTIC INDUSTRIES LTD. STAMFORD WORKS, BROAD LANE, TOTTENHAM, N.15



JUNE, 1954




FOR ANY OF YOUR STANDARD OR SPECIAL APPLICATIONS

A few of the very low capacitance types are:

Type No.	Capacit. µµ F/ft.	Impedance.ohms	0.D.
C.44	4.I	252	1.03″
C.4	4.6	229	1.03"
C.33	4.8	220	0.64″
C.3	5.4	197	0.64"
C.22	5.5	184	0.44″
C.2	6.3	171	0.44″
C.11	6.3	173	0.36″
C.1	7.3	150	0.36″



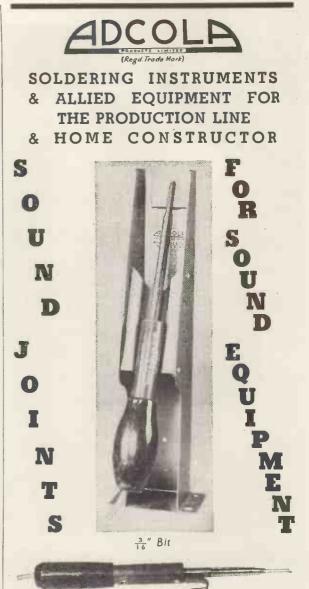

1" Bit Instrument Model

SUPPLIED IN ALL VOLT RANGES STANDARD VOLTAGES STOCKED 6/7, 12/13, 22/24, 50/55, 100/110, 200/20, 230/50

"ADCOLA" PVC & POLYTHENE E L E C T R I C A L C A B L E STRIPPERS ALSO AVAILABLE IN ALL VOLT RANGES. WRITE FOR CATALOGUES

A DCOLA PRODUCTS LTD. Sales Offices & Works: CRANMER COURT, CLAPHAM HIGH ST., LONDON, S.W.4. MACaulay 4272 Marconi



Pulse Generator TF 675E

The Pulse Generator that incorporates an r.f. output modulator

A compact, convenient pulse source for general laboratory use, giving positive or negative pulses, variable between 0.15 µsec and 40 µsec duration, accompanied or preceded by a synchronising pulse of either polarity, at recurrence frequencies between 50 c/s and 50 kc/s, free running or triggered. For r.f. work it incorporates a series modulator providing for the pulse modulation of any r.f. signal source.

T

1.25 µsec pulse from TF 675E displayed on a highspeed oscilloscope (M.I. type TF 942)

MARCONI INSTRUMENTS

SIGNAL GENERATORS · VALVE VOLTMETERS · Q METERS · FREQUENCY STANDARDS BRIDGES · WAVEMETERS · WAVE ANALYSERS · BEAT FREQUENCY OSCILLATORS MARCONI INSTRUMENTS LIMITED · ST. ALBANS · HERTS · Telephone: St. Albans 6161/7 Midland Office: 19 The Parade, Leamington Spa Northern Office: 30 Albion Street, Kingston-upon-Hull Export Office: Marconi House, Strand, W.C.2.

SHORTAGE OF RADIO and T/V ENGINEERS

There is an assured well-paid future for those trained and willing to train in electronics, radar and radio. Modern industrial techniques demand more and more highly trained personnel and the gap between demand and supply is still widening.

This is your opportunity — write for our free brochures giving full details of courses to:

DEPT. 16J. 10 PEMBRIDGE SOUARE, LONDON, W.2.

Telephone: Bayswater 5131/2. The College associated with a world-wide electronics industry. 1413

OF LONDON

NSTITUTES

3 YEAR COURSE

in Telecommunication Engineering (including opportunity for six months' practical attachment) Next course commences on 30th. August, 1954.

4 YEAR COURSE

in Electronic Engineering (including one year's Development Laboratories attachment) Next course commences on 5th. October, 1954.

Associated with **'H.M.V.'** MARCONIPHONE COLUMBIA etc.

FOR TOOL POWER

THE POWER TOOLS THAT

1" 'TOOL POWER' GENERAL PURPOSE DRILL

This is it ! Bridges' newest drill—the only drill in the world with twice the power and 4 times the life of any other drill in its class ! Faster penetration, easier handling, bags of guts—this drill has everything ! And like all 'Tool Power' tools, it's built to last a lifetime.



N. BRIDGES & CO. LTD., BRIDGES PLACE, PARSONS GREEN LANE, LONDON, S.W.6. (RENOWN 1177/8)

output.

balance.

2 speeds—ł track.

Illustrated

Catalogue 6d. post free.

H.P. TERMS

AVAILABLE ON

PURCHASES

OVER £10.

25

HICH

HOLBORN, LONDON,

TEL HOLBORN 6231

GARRARD



W.C.1

H.F.810-8in. steel unit; 10,000 gauss; 5 watts; 50-12,000 cps., 60/6.

H.F.610-6in. steel unit; 10,000 gauss; 3 watts; 60-12,000 cps., 50/6.

DUROFIX the only adhesive with all these qualities

LPLU


A clean, free-flowing liquid, Durofix is the perfect adhesive for such work as securing coil windings and terminations, binding laminations, locking trimmer condensers and cores, fixing diaphragms to movingcoils of speakers, knot fixing on Nylon, and for fixing felt to wood or

DUROFIX SPECIFICATION Tensile Strength Approx. 10,000 lb/sq.in. Resistivity (50% Relative Humidity) 1010 ohms/cm. cube. Dielectric Strength 600/1200 volts/mil. Thermal Conductivity (3.1 to 5.1) x 10+6 cu/sec/sq.cm/°C/cm Temperature Stability Satisfactory from minus 40°C to plus 120° C Water Resistance Yery good up to boiling point. metal. Durofix more than meets the most exacting requirements of radio and T.V. manufacture, and is ideal for servicing and home construction. Used by Famous Radio & T.V. Manufacturers Durofix is a Rawlplug product—famous throughout the world for finest quality and complete dependability. For further Technical Information and Prices write toINSULATING HEATPROOF WATERPROOF WATERPROOF NON-CORROSIVE 5 MINUTE DRYING STICKS almost any material OUTSTANDING ADHESIVE STRENGTH

world wide demand

AMBASSADOR

Viscount Series

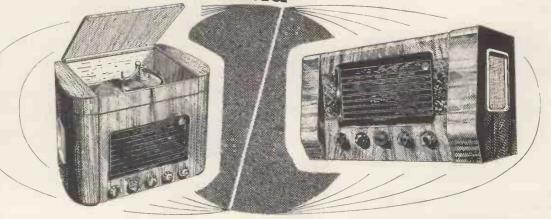

The

Full details on request :


world wide reception

THE RAWLPLUG CO. LTD., CROMWELL RD., LONDON, SW7 FRObisber 8111 (10 lines) Grams: Rawlplug Southkens London

Such it is for the AMBASSADOR VISCOUNT Series. Reports reach the factory daily as to the excellence of their performance in all parts of the world. Nine Valves (Viscount 2). Eight Wavebands (all coil ranges). Push-Pull Output. Low Signal to Noise Ratio. Shortly in production—a 5 valve version of the VISCOUNT for those who desire a lower priced receiver but the same H.F. performance. Watch out for the VISCOUNT 3.

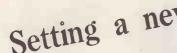AMBASSADOR RADIO AND TELEVISION, PRINCESS WORKS, BRIGHOUSE, ENGLAND





CALIBRATING UNIT AT203

Range: DC---300 Kc/s

Voltage Output : 10 volts-10 microvolts

Accuracy: $\pm 0.5\%$




FEEDBACK VOLTMETER **VF252**

Range: 10c/s-100 Kc/s

Sensitivity: 1.5 mV-150 volts f.s.d.

Accuracy: $\pm 1\%$

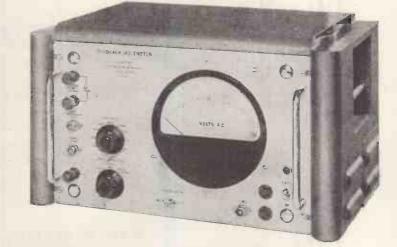



Write for full details of these two new instruments. to :---

SOLARTRON LABORATORY INSTRUMENTS LIMITED

Solartron Works, Queens Road, Thames Ditton, Surrey.

Telephone : Emberbrook 5611 PBX



Special Amplifiers, Transformers, Chokes and Laboratory Apparatus. A full range of Microphones and Loudspeakers available. For superb reproduction of gramophone records use the Monarch or Regent and A 1254C. Obtain details from your local retailer or wholesaler. In case of difficulty and all overseas enquiries, write to "Dept. AB" at the address below.

N. MIERS & CO. LTD., 115 Gower Street, London, W.C.1

Telephone: EUSton 7515.

Cables: MIERSCO.



WIRELESS WORLD

-RELAYS-

53

A compact design for close stacking

SERIES 595 D.C. OPERATED

For further details of our range please write.

TELEPHONE : NEWMARKET 3181-2-3

TELEGRAMS : MAGNETIC NEWMARKET

This extremely compact relay has its connections to both contacts and coil brought conveniently to one end, and is designed without projections to facilitate close stacking where banks of Relays are in use. The contact current handling capacity is exceptionally high in relation to the overall dimensions of the Relay. Good armature design has reduced the effects of shock, vibration and acceleration, and the spring type hinge eliminates backlash friction and risks of

MAGNETIC DEVICES LTD

displacement.

MDA

NEW IMPRESSION NOW READY



 $8\frac{3}{4}'' \times 5\frac{1}{2}''$ **1,522 pages** 42s. net. By post 43s. 6d.

This book must not be distributed to Australia, New Zealand or the Americas. Edited by F. Langford-Smith, B.Sc., B.E. Senior Member I.R.E. (U.S.A.), A.M.I.E. (Aust.)

Radio Designer's Handbook

The first impression of this greatly enlarged fourth edition sold out within a few weeks of publication and a second impression has been produced to meet the enormous demand.

Radio Designer's Handbook is a comprehensive reference book, the work of 10 authors and 23 collaborating engineers, containing a vast amount of data in a readily accessible form. The book is intended especially for those interested in the design and application of radio receivers or audio amplifiers. Television, radio transmission and industrial electronics have been excluded in order to limit the work to a reasonable size.

Published for "WIRELESS WORLD"

From booksellers or from : Iliffe & Sons Ltd., Dorset House, Stamford Street, London, S.E.1











radio ceramics

for

STEATITE & PORCELAIN PRODUCTS LTD.



Stourport-on-Severn, Worcestershire. Tel: Stourport III. Telegrams: Steatain, Stourport




HUDSON RADIO-TELEPHONES

MODELS

AM/250/M 5 watt Mobile 60 to 100 Mc/s AM/250/M MK2 as above but with P.A. AM/150/M 5 watt Mobile 100 to 185 Mc/s AM/250/F 6 watt Fixed Station 60 to 100 Mc/s AM/150/F 5 watt Fixed Station 100 to 185 Mc/s HED 102 Walkie-Talkie 60 to 132 Mc/s FM 101 10 watt FM Fixed Station 60 to 185 Mc/s FM 102 10 watt FM Mobile Station 60 to 185 Mc/s

Supplied to the G.P.O. and the Home Office

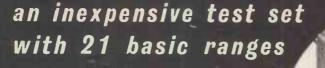HUDSON ELECTRONIC DEVICES LTD. APPACH ROAD, LONDON, S.W.2 Tel.: TULSE HILL 4861



The Pullin Series 100 Multi-Range Test Set is an Inexpensive piece of equipment invaluable to radio and electronic engineers. It is a compact, portable instrument with a total of 21 basic self contained ranges which provide adequate facilities for the measurement of A.C. voltage, D.C. voltage and current, and resistance. All voltage measurements are at 10,000 Ohms per volt.

instrumentation by

LABORATORY INSTRUMENTS DYNAMOMETER TESTING SETS INDUSTRIAL SWITCHBOARD INSTRUMENTS PORTABLE TESTING SETS

SERIES 100 MULTI-RANGE TEST SETS

MEASURING INSTRUMENTS (PULLIN) LTD., ELECTRIN WORKS, WINCHESTER STREET, ACTON, LONDON, W.3 - PHONE: ACORN 4651-4995

RETAIL

COMPLETE

CAR AERIAL

THE AUTOX

Fitted quickly in any position on any car entirely from the outside!

The "AUTEX" is the last word in car aerial design and combines an attractive appearance with high efficiency. Above all its unique construction enables fitting to be carried out without the necessity of getting under the car wings, scuttle and dashboard, etc. By means of a split washer device the "AUTEX" is fixed from OUTSIDE the car—on a flat or curved surface and at any angle from horizontal to vertical. No assembling is necessary—the aerial is wired complete for immediate installation.

Model TCA/462/36. With mounting assembly of sturdy die-cast metal; three section telescopic rod (extended 60in., closed 24in.) of high-grade brass. All exposed parts heavily chromium plated and with fully weatherproofed connec-


ANTIFERENCE

IMITE

tions. Complete with 36in. low-loss co-axial polythene insulated P.V.C. covered cable, fitted with standard co-axial plug.

LIST PRICE 37'6

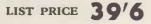Model TCA/462/60 as above but with 60in. cable.



Special packing glands ensure a smooth telescopic rod action and entirely prevent any rattle. In efficiency the "AUTEX" is up to the very highest standard in common with all ANTIFERENCE Radio and Television aerials.

> Sales Division: Bicester Road, Aylesbury, Bucks. Telephone: Aylesbury 1467/8



CLOSED 24 ins (61·O cm.) EXTENDED 62 ins. (157·5 cm.)

95

ONE

HOLE

FIXING

entirely from the

outside

FULLY

SCREENED

Memo <u>TELMAG</u> are the <u>specialists</u> in grain oriented Steel Transformer cores, Toroids, C Cores and special applications ... Must contact them without delay!

Please write for technical literature, available upon request.

We maintain a specialised advisory service and are always



G126

pleased to co-operate on any specific problem. **TELCON-MAGNETIC CORES LIMITED** CHAPELHALL INDUSTRIAL ESTATE, CHAPELHALL, LANARKSHIRE, Tel.: AIRDRIE 2283

THE NEW TK9 Single-Speed TAPE RECORDER

For Successful

TELMAG ADVISORY SERVICE

A masterpiece of compactness and engineering. Unique features include: Precision Place Indicator, Automatic Track Switch, Universal Magic Eye, etc., etc. Recording time 14 hours. Tape speed 34 inches per second. Sound Frequency Range 50-9,000 c/s. PRICE 65 GNS.

PRICE 65 GNS. less microphone, Grundig "Golden Voice"" moving coil microphone (GDM.5) 6 gns. Grundig "Silver Voice" crystal microphone (GXM.1) 4¹ gns.

THE FAMOUS 700L Two-Speed TAPE RECORDER

Sound Recording

LAPE RECORDER Used by leading musicians throughout the world. Two hours , effect speech recording or one hour high-fidelity music recording. Unlque Grundig condenser microphone as sensitive as the human ear. Tape speed 74 inches and 34 inches per second. Sound Frequency Ranges: 50-10,000 c/s at 74 in. per second, and 50-6,000 c/s at 33 in. per second. PRICE 20 Cols

PRICE 80 GNS.

including condenser microphone

HIRE PURCHASE TERMS AVAILABLE Most Radio and Photographic Dealers stock Grundig. Ask for a demonstration, or write for illustrated Folders to : Dept. W.W., Grundig (Gt. Brituin) Ltd., Kidbrooke Park Road, London. S.E.3.

GRUNDIG



Dithtorthon Bithenell



Faithful reproduction starts with the microphone. A tone control, with its top-cut and bass-boost, can compensate, but can never add fidelity. It cannot correct distortions, whether of speech or music. A distorted sibilant must remain distorted, a muffled piano must remain muffled. The microphone alone receives the sound and must pass it on without coloration, false emphasis or attenuation. And that indeed is the characteristic of the Goodmans Z33. For it has an inherently flat response, and is unusually free from " peaking." Moreover, its high sensitivity ensures that nothing of the original sound is lost. The brief specification tells its own story.

SOME BRIEF DETAILS

OUTPUT IMPEDANCE Standard Mode. 20 ohms FREQUENCY RESPONSE 50-10,000 c/s +5 db. DIMENSIONS O max. diameter 3in. Overall length 33in., WEIGHT (including loft. screened cable) 14 ozs., with transformer 16 ozs. FINISH Polychromatic Old Gold, front cover and base anodised, Dyed Gold. Or Grey crackle and chromium. Incorporating recessed "ON/OFF" switch.

THE PRICE

With built-in matching transformer providing 200 ohms, 600 ohms or Hi-Z impedances 30/- extra



odmans masters of quality reproduction

GOODMANS INDUSTRIES LIMITED, AXIOM WORKS, WEMBLEY, MIDDX.

Telephone: Wembley 1200 (8 lines)

You can count on these for a reliable performance

STAND-OFF INSULA-TORS. Working voltage 1,500/5,000. Very high insulating resistance. Ceramic non-tracking. Silicone treated to repel moisture (ideal for tropics). Tag or spill end. We have a full range to cover most needs.

60

S.L.8 SPIN WHEEL DRIVE. A precision slide rule drive complete with 3 band glass scale. The spin wheel drive glves perfect control through ratio 24:1. Fitted with constant velocity coupling, eliminating strain on condenser and providing mechanical and electrical isolation from vibration and noise.

M.G. GANG CON-DENSER. Available as 1, 2 or 3 gang, 490 p.F. nominal capacity, matched and standardised to close limits. Cadmium plated and standardised to close limits. Cadmium plated steel frame. Aluminium Vanes. Low loss non-hygroscopic insulation. Length excluding spindle: 1 gang—1 Jin. to 3 gang -3§in. Price 1 gang, 9/3, 2 gang, 14/-, 3 gang, 18/3

Write for full details of the complete range of precisionbuilt components for Radio and Television industry.

JACKSON BROS. (London) LTD., KINGSWAY : WADDON · SURREY Telephone : CROydon 2754-5. Telegrams : WALFILCO, SOUPHONE, LONDON.

TWO HOURS RECORDING on standard 1200 ft. spool TO THE TRADE: and TEN WATTS OUTPUT Ask for details of

With standard 1200ft. spools, the SIMON Portable Tape Recorder affords two hours recording and brilliant playback-at 10 watts output if required. Twin tracks, two speeds. Frequency response is wide: 50-12,000 c/s at 7½in./sec. and 50-7,000 c/s at 3%in./sec. Bass and treble are independently variable.

Designed for the discriminating user, the SIMON Portable opens up new fields of activity in tape recording.

SIZE LOUDSPEAKER ... POWER SUPPLY INPUT CHANNELS

18 in. x 15 in. x 10 in. ... 61 in. built-in monitor 200/250v. 50 Cycles A.C. ... High Impedance for microphone; low or high impedance for radio **POWER CONSUMPTION** 100 watts approx.



ortable TAPE RECORDER

Ask for

"THE GENTLE ART OF TAPESMANSHIP" and Information Sheet TI/6

SIMON SOUND SERVICE LTD. (Dept, W) 48-50 GEORGE ST., LONDON, W.1. Phone: WELbeck 2371 (5 lines)

- * Separate capstans
- ★ Three motor drive
- * Drop-in loading

★ Monomaster "Finger- ★ Fast rewind and wind-tip" Control

★ Provision for Remote Control and indepen-dent use of amplifier for P.A., etc.

SIMON for Sound Recording at a Sensible Price

special Dealer facilities and Information Sheet T1/6

Loud-speaker Manufacturers to the radio industry since 1930



We don't make

... every kind, size and shape of loud-speaker that radio and television designers may need. By concentrating on two basic types and a range of sizes between 5" and 12" in diameter, including elliptical models, we can cover most normal requirements and give set-makers the benefits of productuniformity and competitive price which result only from large and economic production runs.

We do invite Chief Engineers and Purchasing Officers to send for our technical data sheets, which summarise the distinctive features of R. & A. Reproducers and transformers. An indication of the size and sensitivity required will enable us to send the appropriate sheets.

REPRODUCERS AND AMPLIFIERS LIMITED WOLVERHAMPTON ENGLAND

Telephone : Wolverhampton 22241 (5 lines) Telegrams : Audio, Wolverhampton

MAINTAINING A REPUTATION

Deflector Coils type DC300/C. As specified for the "Teleking," "Supervisor" and "Magnaview."

Conversion circuits for 14in. and 17in. C.R. Tubes available. Send 9d. and S.A.E. Every day we read the words: "I am ordering Allen Components because they are so highly recommended by my friends."

We are proud of our reputation. Since we pioneered Wide Angle scanning some years ago we naturally carried on our policy of producing components designed to the highest specification and engineered to the closest tolerance. In these days of shortages and lowered standards such a policy is not easy to carry out and it has necessitated unrelaxed attention to detail in all our departments. The result of this care is apparent in all our products, in which good workmanship is combined with high reliability.

May we suggest you ask your friends

From all Leading Stockists.



COMPONENTS LIMITED

FIDELITY

AMPLIFIER

AMPLIFIER

Output : 10-12 watts. Distortion : Less than .1% total harmonic at

Crown Works, Lower Richmond Rd., Richmond, Surrey Telephone: Prospect 9013 Send 9d. and S.A.E. for Circuit Diagram

THE NEW

Cirmstrong A·10 HIGH

Specialists in High Quality Reproduction for over 20 years

Cuestiony A.10.

CONTROL UNIT


Controls: 1. Input (a) Radio 50-150 Millivolts. (b) Gram. (low impedance) 15-100 m.v. (c) Gram. (high impedance) 70-150 m.v. (d) Microphone 10-100 m.v. 2. Equaliser (a) 78⁴ (b) 78⁴. (c) L.P. (d) American NARTB 3. Filter (a) Roll-off 5 kcs. (grad). (b) 7 kcs. (c) 9 kcs. (d) 9 kcs. (steep). (e) Level response. 4. Treble lift or cut of 15 db. 5. Bass lift or cut of 15 db. 6. Volume control combined with on/off switch. Valve: Mullard ECC83 double triode. Power supply for radio unit 300 v. 20 ma., 6.3 v. 1.5 a. Finished: Hammered bronze with engraved Florentine bronze panel.

SEE PAGE 141 FOR OUR RADIO AND T.V. MODELS. WRITE TO US FOR DESCRIPTIVE LITERATURE.

★ DEMONSTRATIONS at your local High Fidelity specialists or at our showrooms in Holloway 9 a.m. to 6 p.m. weekdays (Sats. until 5 p.m.) also Special High Fidelity Demonstrations on Thursday evening 8 p.m. 8 watts. Frequency response: 10-100,000cps., within 1 db 15-30,000cps. Hum level: Better than 80 db down. Damping factor: 40. Feed-back: 3 loops, main overall loop being 26 db obtained by means of a tertiary winding on the output transformer. Input required: 250 milliwatts for 10 watts output. Valves used: Mullard low noise pentode EF86, ECC82, double triode, 2 EL37, triode-tetrode connected, GZ32 indirectly heated rectifier. Components: All fully tropicalised. Mains transformer by WODEN, PARTRIDGE output transformer, TCC condensers, Morganite controls and resistors. Mains input: Model A10, 200-250 v. A.C. 50 cycles, Model A10E, 100-110 v. A.C. 40-60 cycles. Finished: Hammered bronze.


★ THE A.10 INC TERS, and no	ng prices of High ORPORATES AL additional filter	L Fidelity I L NECESS units are	ARY FIL- required.
PRICE : AMPLIFIER	£19·15·0	ONTROL UNI	r £9.15.0

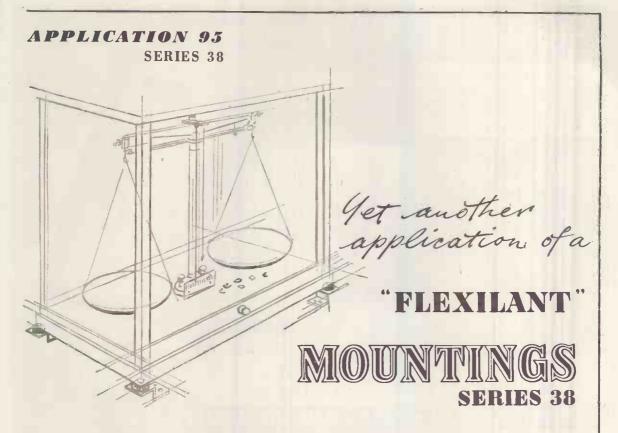ARMSTRONG WIRELESS & TELEVISION CO.. LTD., WARLTERS ROAD, HOLLOWAY, LONDON N.7. Tel.: NOR 3213/4



IN this instance the Series 38 "Flexilant" Mounting protects a delicate instrument from vibration and shock. Other applications are manifold — from aircraft to power-station instrument panels: from ship's instruments to the protection of pyrometers in a steel works.

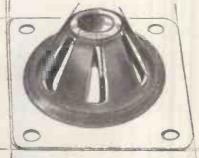We produce a range of components that absorb vibration; eliminate noise; suppress shock. Our new catalogue lists all these for you.



RUBBER BONDERS LIMITED

IN ASSOCIATION WITH EMPIRE RUBBER COMPANY (Proprietors : H.G. MILES LTD.)


DUNSTABLE · · · BEDFORDSHIRE

TELEPHONE: DUNSTABLE \$33-\$36 (4 LINES) TELEGRAMS: SPANOIT. DUNSTABLE

JUNE, 1954



Valves and Electronics ...

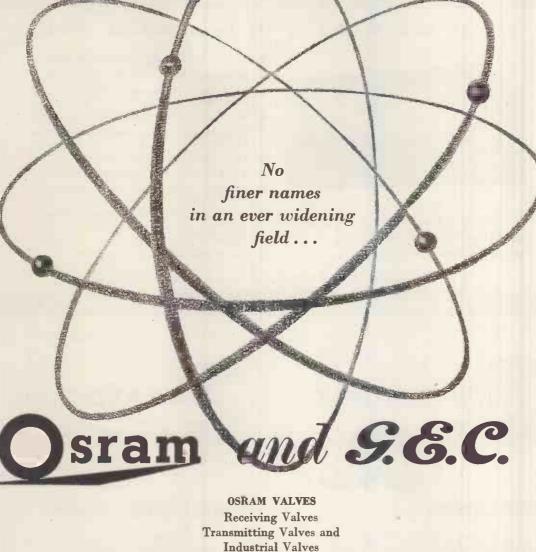

G.E.C. ELECTRONIC DEVICES Transistors Silicon Diodes Germanium Diodes Cathode Ray Tubes Miniature Neon Indicators Voltage Stabiliser Tubes Geiger Müller Tubes Photoelectric Cells Barretters

THE GENERAL ELECTRIC COMPANY LIMITED, MAGNET HOUSE, KINGSWAY, LONDON, W.C.2





STRATTON & CO. LTD., ALVECHURCH ROAD, BIRMINGHAM, 31



Mullard

Ferroxcube

being extruded into rods for H.F. cores.

MAGNETIC MATERIALS research and manufacturing facilities have established

Extensive

Mullard as the leading producers of magnetic materials. They were the first, for example, to introduce Ferroxcube, the world's most efficient magnetic ferrite; 'Ticonal' anisotropic permanent magnets, renowned for their high stability and high energy output; and Magnadur, an entirely new type of permanent magnet with the insulating properties of a ceramic. The wealth of experience gained from these developments is

available to all users of magnetic materials through the Mullard advisory service. An enquiry to the address below will put a team of specialised engineers at your disposal.





* TICONAL' PERMANENT MAGNETS . MAGNADUR (Formerly Ferroxdure) PERMANENT MAGNETS . FERROXCUBE MAGNETIC CORE MATERIAL

MULLARD LTD., CUMPONENT DIVISION, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2.

ER RADIO CO. B. H. MORRIS & CO. (RADIO) LTD. EST. 40 YRS.

(Dept W.W.) 207 EDGWARE RD., LONDON, W.2.

Tel.: AMBassador 4033 & PADdington 3271

MAY BE BUILT FOR £31 · 19 ·

including all valves. (plus cost of CRT)

The NEW PREMIER TELEVISOR

Brief Technica! Details are as follows: 20 valves (plus tube) Superhet Receiver, tunable from 40-68 Mc/s without coil or core changing. Wide Angle scanning Flyback EHT giving 14 kV, Duomag Focaliser, permanent magnet focussing with simple picture centring adjustments, suitable for any 17 in. or 14 in. wide angle Tube, may also be used with a 12 in. Tube with very minor modifications. modifications.

VISION CIRCUIT Common RF Amplifier single valve frequency changer, two IF stages, Video Detector and Noise Limiter followed by special type of Video Output Valve. ALL COLLS PRE-TUNED ASSURING ACCURATE ALIGNMENT AND EXCELLENT BAND-WIDTH.

SOUND CIRCUIT Coupling from anode of frequency changer, two IF stages, Double Diode Triode detector and first LF Amplifier, Diode Noise Limiter and Beam type Output Valve, feeding a 10in. Speaker. ALL COLS PRE-TUNED.

TIME BASES 2 valve sync. Separator, giving very firm lock and excellent interlace.

LINE TIME BASE Blocking Oscillator using a pentode driving a high efficiency output stage comprising Ferroxcube Cored Output Transformer with Booster Diode.

FRAME TIME, BASE Blocking Oscillator driving a Beam Output Valve coupled through a Transformer to the high efficiency FERROX-CUBE Cored Scanning Coils.

POWER PACK Double wound Mains Transformer supplying all L.T. and H.T. using two full-wave Rectifiers.

THE COMPLETE TELEVISOR IS SAFE TO HANDLE, BEING COMPLETELY ISOLATED FROM THE MAINS BY A DOUBLE WOUND MAINS TRANSFORMER. ALL PRESET CONTROLS CAN BE ADJUSTED FROM THE FRONT, MAKING SETTING UP VERY SIMPLE.

The Televisor may be constructed in 5 easy stages: (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point, wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced.

Console Cabinets in figured walnut can be supplied for the above receiver at a cost of £13/10/-, plus 21/- packing and carriage, as previously advertised.

Instruction book 3/6 Post Free.

The PREMIER DE Luxe PORTABLE MAGNETIC TAPE RECORDER KIT

Including ALL parts, Valves, Portable Cabinet, 8in.Loudspeaker, Tape-Table, Reel of 'Scotch Boy' Tape and Rewind Spool, and Microphone. PRICE £37.4.0

THE 7-VALVE AMPLIFIER IS SPECIALLY DESIGNED FOR HIGH QUALITY REPRODUCTION

Brief specification: VALVE LINE-UP: EF37A First Stage, 6SL7 Second Stage and Tone Control; 6V6 Output 6X5 Rectifier; VT501 Blas and Erase Oscillator; 7193 Record Level Amplifier; 6US Magic Eye Record Level Indicator. OUTPUT: 4 Watts. FREQUENCY RANGE: 50 c.p.s. to 9,000 c.p.s. CONTROLS: Volume; Record/ Playback Switch; Treble Boost; Bass Boost—on/off. MICROPHONE : Crystal-specially designed for Premier by famous manufacturer.

SEPARATE UNITS CAN BE SUPPLIED AS LISTED BELOW

	140 mg	VILD DELOTT
AMPLIFIER KIT (including 8in, Speaker) £1		
AMPLIFIER (already built, wired and tested) £1	4 15	O plus 7/6 pkg./carr.
	7 10	O plus 7/6 pkg./carr.
	E4 19	6 plus 5/- pkg./carr-
MICROPHONE£	2 19	6 plus 1/- pkg./carr.
REEL OF NEW M.C2-III "SCOTCH BOY " TAPE		
(1,200It.)£	21 15	0.plus I/- pkg./care

This is credited if a complete kit of the Tape Recorder is ordered.

> Supplied completely assembled 39 GNS. Plus I gn. Pkg. & Carr.



TERMS OF BUSINESS: Cash with order or C.O.D. over £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated

and Cream.

WIRELESS WORLD

69



JUNE, 1954



BROOKES Crystals



mean DEPENDABLE frequency control

 Illustrated above are Left: Type G2 Crystal Unit Frequency 50 kc/s.
 Right: Type G1 Crystal Unit Frequency 100 kc/s.

ALL Brookes Crystals are made to exacting standards and close tolerances. They are available with a variety of bases and in a wide range of frequencies. There is a Brookes Crystal to suit your purpose let us have your enquiry now.



Brookes Crystals Ltd. Suppliers to Ministry of Supply, Home Office, B.B. C., etc. EARLSWOD STREET, LONDON S.E.10 Telephone : GREenwich 1828 Grams: Xtals, Green, London, Cables: Xtals, London



DIRECT READING. ZERO CURRENT DRAIN.

THREE SECONDS PERIOD.

LAMP OPERATES FROM MAINS OR 4 VOLT BATTERY. BRIGHT SPOT-AND-HAIRLINE

AND-HAIRLINE INDICATOR.

SCALAMP ELECTROSTATIC VOLTMETER

This instrument introduces a completely new conception of electrostatic voltmeter. It is compact,

portable and robust, and does not require critical levelling or special mounting. The movement has a taut suspension, is critically damped, and readings can be taken with rapidity and ease. Three models are available:

Cat. No. W.W. 11308 I - 5 kV A.C. D.C. Cat. No. W.W. 11309 3 - 10 kV A.C. D.C. Cat. No. W.W. 11310 5 - 18 kV D.C. and 5 - 12 kV A.C. R.M.S.

Please write for illustrated leaflet.

3



W. G. PYE & CO. LTD. GRANTA WORKS, CAMBRIDGE

70

WIRELESS WORLD

NEW ARCOLECTRIC SIGNAL LAMPS

For Low Voltage or Mains

Illustrated are a few signal lamps taken from our wide range. The insulation of every Arcolectric signal lamp will resist a flash test of 1.500 volts A.C.

The S.L.90 illustrated here is a typical Arcolectric low voltage signal lampholder. It is designed to accept popular M.E.S. bulbs. The bulb is accessible from front or rear of panel. The domed plastic lens surrounded by a polished chrome bezel gives a most attractive panel appearance. This holder can be fixed in a single ³" hole.

The mains voltage signal lamp S.L.88/N is supplied complete with an M.E.S. neon tube and a suitable series resistance.

Write for Catalogue No. 128

TEHESILTO





S.L.90

S.L.86

RCOLECTRI



SL 82 CENTRAL AVENUE, WEST MOLESEY, SURREY ' TELEPHONE: MOLESEY 4336 (3 LINES)

MAGNETIC

tensile strength.

(0.000039 inch).

6

Gives the highest possible signal-to-noise ratio—excelling in high-frequency response.

Has a superlative dimensional stability-negligible stretch, and the highest possible

Discourages static collection during fast forward, and fast re-wind operations.

The Kraft Paper base has been selected

reasons why those concerned

PRICE

with recorded sound choose

RECORDING

Does not curl-lies flat on the transducer head, giving better frequency response, and smooth tracking.

Has the lowest possible surface friction-reducing wear on transducer heads, and guide pillars.

Has the best possible dispersion of oxide particles, free from coagulation, and flocculation ensuring low noise level.

correctly heat-dried to preclude locking " and sticking, layer-to-layer, " blocking under storage conditions.

The Lacquer is formulated to attain the maximum adhesion to the base material.

Suitable for Single or Double Track Recording. Length 1,200ft. on 7in. Diameter Spool-Frequency response 50 C.P.S. to 10 on 7in. Diameter Spool-Frequency response 50 C kc/s. at 7.5 in. per sec. Breaking strain exceeds 4lb.

AGNETIC COATI l G 38 GROSVENOR GARDENS LONDON SWI Telephone : SLOANE 9129 WORKS & LABORATORY: 25 DASHWOOD TRADING ESTATE LARCH ROAD . LONDON . SWI2 BALHAM 5579

The pigment is dispersed and milled, with the highest degree of control, ensuring a uniform dispersion c oxide particles within the binder. XIX thus of the

The spools were designed to incorporate the "universal" hub, perfect balance, and negligible rotation noise. 12 the

TAPE

"FERROVOICE" products are subject continuous development by to technical staff.

The control of the second sec





JUNE, 1954





Only the Monarch Autochanger has all these features. Its record performance, fidelity reproduction and absolute reliability are acclaimed by music lovers and record enthusiasts everywhere—it's the first choice of the experts.

WORLD'S FINEST AND MOST WANTED AUTOCHANGER

Birmingham Sound Reproducers Limited, Claremont Works, Old Hill, Staffs.

BRITISH MADE BRIMAR VALVES

more reliable than EVER!

Brimar's long experience in the manufacture of special-quality TRUSTWORTHY valves is now being reflected throughout the entire Brimar range.

Improved production methods, new and better assembly jigs, tighter control on the composition of materials, and the closer supervision of vital processes have resulted in valves with more uniform characteristics, greater mechanical strength and a higher standard of reliability as shown in the 12AT7. The 12AT7 is a very reliable frequency changer and is widely used in modern TV receivers, VHF and UHF communications equipment. It is also frequently employed in industrial equipment, computors, navigational aids and test equipment.

BRIMAR BRIME

Use the BRIMAR 12AT7 with improved performance at NO EXTRA COST

now is the time

BRIMAR	MULLARD	MARCONI OSRAM	COSSOR EMITRON
12AT7	ECC81	B152 & B309	I2AT7

to BRIMARIZE, Standard Telephones and Cables Limited FOOTSCRAY SIDCUP KENT FOOtscray 3333

75

"I have just had one of the thrills of my life" "I am happy to award five stars (which, I suppose, is the spirituous equivalent of an 'Oscar'), to the Cosmocord HGP 39 pick-up, the Goodmans Audiom 60 loudspeaker and the WB Pressure Tweeter and Crossover."

... wrote P. WILSON in the "Gramophone".

Now Mr. Wilson is not only a well known technical expert, but he is old enough to have become blasé, and yet here he is, admitting to a new experience—to a realism of record reproduction that has taken him aback. The record that prompted his comments was Decca's version of the Beethoven Fifth. The HGP 39 pick-up (that small but vital link) was one of the acos Hi-g series.

Reproduction like this *is* thrilling, and Cosmocord's big contribution to it costs so little. Only £1.12.0 (plus 10/3 P.T.) for the HGP 39. Amazing —ask Mr. Wilson!



CRYSTAL PICK-UPS

COSMOCORD LIMITED · ENFIELD · MIDDLESEX

ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.

GD




. . always well ahead

WIRELESS WORLD

"BELLING - LEE" NOTES

Choice of an Aerial

How often the choice of a television aerial is considered unworthy of much thought. Fifty to a hundred but "any old aerial will do." In a paper by C. B. B. Wood, Research Department, Engineering Division, B.B.C., and published in the Journal of the Television Society for October-December 1953, Mr. Wood says: "It is an unfortunate feature of television in its present state that very few decibels in signal-to-noise ratio separate the very best pictures and those that are unacceptable, and the addition of only three decibels of noise in reproduction can easily turn a moderate original Mr. Wood was writing about Telerecording, but a decibel is always a decibel, and when we say that a certain aerial is better by three decibels, that is important. Those who spend their days and evenings endeavouring to receive a good picture in areas of weak signal know all this, or they just would not get a picture, and that is why so many "Belling-Lee" aerials are seen in out-of-the-way places. Only too many viewers receive a picture too easily, they do

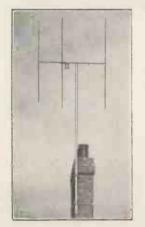

"Belling-Lee" " Junior Multirod," 3-element array.

not realise how much better their picture would be if they fitted an outside aerial by "Belling-Lee." Approximately 50 per cent of all television aerials sold are made by "Belling-Lee."

We are fully aware that most of the people with "Belling-Lee" aerials on their roofs do not know

AT LAST! A REALLY COMPACT FLEX-LEAD SUPPRESSOR

そうそうそうそうそうそうそうそう



for use with appliances using up to 2 amp.(2-core)

EFFECTIVE AT T.V. FREQUENCIES ONLY

However efficient flex lead suppressors may be when fitted to household appliances and small electrical tools, up to now they have been regarded as a necessary

evil, due mainly to their bulk. Not so with the new "Belling-Lee" flex lead suppressor L.1314. This is contained in a compactly moulded case of robust design, only $2\frac{3}{4}$ in. $\times \frac{3}{4}$ in. $\times \frac{3}{4}$ in., specifically designed to be fitted within 6in. of the offending component of an appliance.

Not for use with heavy duty appliances, such as smoothing irons.



bow lucky they are to be receiving such a good picture. They put their trust in their radio dealer who did not let them down. The radio dealer knows that mechanically as well as electrically "Belling-Lee" aerials are as trouble-free as experience and care can make them.

ANovelValveExtractor and Pin Straightener

This novel valve extractor is suitable for B7G, B8A and B9A valves and enables their removal from equipment made up of closely packed components. The extractor is moulded in rubber, and the handle incorporates a pin straightener for B7G and B9A types.

This is accurately moulded in a hard

phenolic material, and will obviate the damage to valves and/or sockets, caused through trying to force insertion with distorted pins.




Value extractor and pin straightener.

Advertisement of BELLING & LEE LTD. Great Cambridge Rd., Enfield, Middx. Written 24th April, 1954.

77

JUNE, 1954

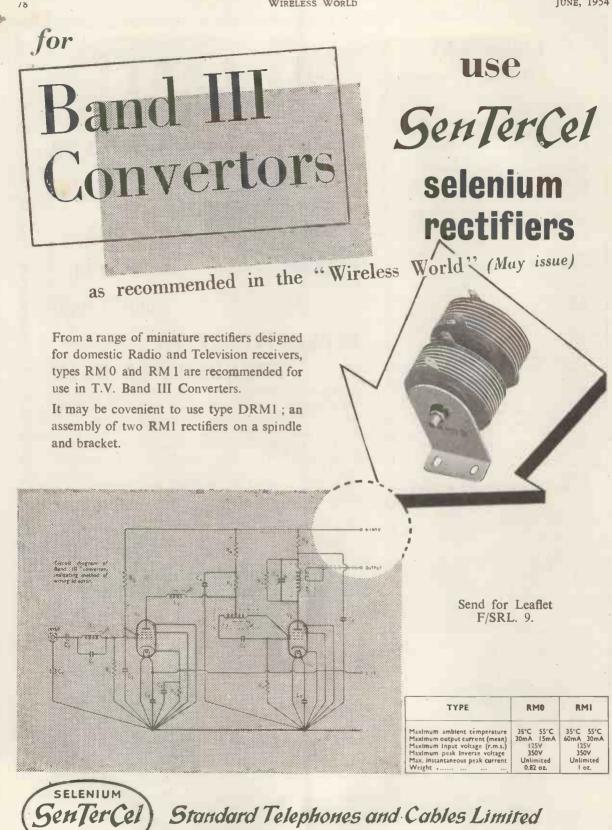


(Registered Office: Connaught House, Aldwych, W.C.2) RECTIFIER DIVISION: Warwick Road, Boreham Wood, Hertfordshire. Telephone : Elstree 2401 Telegrams : Sentercel, Borehamwood

MARCONI HR 21 Independent Sideband HF Receiver for point-to-point services

This receiver is designed for independent sideband reception of telephony and covers the frequency range 3-27.5 Mc/s. It provides : selection of one of 6 crystal controlled spot frequencies or continuous tuning over the whole range, motor driven automatic frequency correction, reducing errors of up to 3 Kc/s to substantially zero mistune. Reconditioned or local carrier may be used for demodulation, full metering and monitoring facilities.

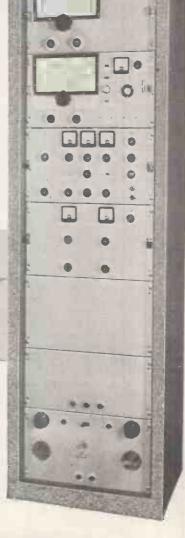Particular attention has been given to ease of servicing and all units are easily withdrawn.



MARCONI

COMPLETE COMMUNICATION SYSTEMS Surveyed, planned, installed, maintained

MARCONI'S WIRELESS TELEGRAPH COMPANY LIMITED . CHELMSFORD . ESSEX

LOUDSPEAKERS-Why an Elliptical Cone?

A standard "His Master's Voice" $13\frac{1}{2}$ " Elliptical Loudspeaker

It is generally agreed that the weakest link in a reproducer chain is the loudspeaker. For example, in the very important matter of frequency response, a response variation of ± 1 db over the useful audio frequency range is fairly easily obtained from an amplifier, but the corresponding deviation for the best loudspeakers is of the order of \pm 5db. Even these loudspeaker variations are only true on the axis of the loudspeaker and off this axis much wider variations are obtained. This relatively poor performance of loudspeakers as compared with other components does not only apply to frequency response, and a similar comparison exists for transient response, distortion etc. Therefore any approach to high fidelity must be based on a first-class loudspeaker, and without it any improvements which may be obtained from amplifiers will be of little avail.

Many of the imperfections of

loudspeakers, particularly as regards frequency and transient response, arise from the fact that in the high frequencies the loudspeaker cone does not act as a simple piston but " breaks up " into its own resonances, which give rise to response changes with frequency and " hangover " effects or poor transient response.

Rigid

chassis

for stability

centering.

of speech coil

Aluminium

centre cone.

These resonances may give either increased or decreased sound output at any particular frequency. An increase in output arises when all the resonating parts of the cone are in phase, that is, they all move forwards and backwards together, and a decrease in output arises when different parts of the cone are vibrating out of phase, that is, when one part of the cone moves forwards while another moves backwards, so that the output from the two parts cancels. These effects can obviously be reduced if the cone is not of a symmetrical conical form, so that although localised break-up cannot be avoided, resonant break-up of the whole cone will not occur, and variations in response and "hangover" effects will be reduced.

The elliptical loudspeaker offers a solution to many of the loudspeaker designer's problems since the lesser Speech coil dustproofed. Wide angle diffusion of high frequencies due to elliptical cone shape.

Felt pad ensures efficient sealing to baffle.


C

degree of symmetry as compared with a circular cone renders the "break up" effects less marked. In addition, for a given frequency response the elliptical cone gives an improved spread of the high frequencies so that the response shows less variation off the loudspeaker axis.

Cone " break up " effects may be further reduced by not making the cone material homogenous throughout, so that the symmetry of the cone is further reduced. This may be done by making the centre of the cone of a material with different elastic properties from the outside, for example the centre of the cone may be made of aluminium and the outside of paper. This arrangement gives a remarkably smooth and wide range response and perhaps gives the best possible reproduction obtainable from cone type loudspeakers. This type of loudspeaker has been embodied in "His Master's Voice" radios and radiogramophones for the past 20 years, and while it is true there has been a trend in the past year or two towards the elliptical loudspeaker technique, the use of the elliptical cone with two different materials for its construction remains an important "His Master's Voice " feature.



VORTEXION

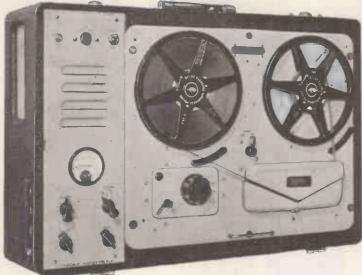

The amplifier, speaker and case, with detachable lid.

measures $8\frac{1}{4}$ in. x $22\frac{1}{2}$ in. x $15\frac{3}{4}$ in. and weighs 30 lb.

PRICE, complete with WEARITE TAPE

TAPE RECORDER

* The noise level is extremely low and audibly the hum level and Johnson noise of the amplifier and deck are approximately equal. Only 25% of this small amount of hum is given by the amplifier alone.

★ Extremely low distortion and back-ground noise, with a frequency response of 50 c/s.—10 Kc/s., plus or minus 1.5 db. A meter is fitted for the measurement of signal level and bias level.

* Sufficient power is available for recording on disc, either direct or from the tape, without additional amplifiers.

A heavy mu-metal shielded microphone transformer is built in for 15-30 ohms balanced and screened line, and requires only 7 micro-volts approximately to fully load.

The .5 megohm input is fully loaded by 8 millivolts and is suitable for crystal P.U.s, microphone or radio inputs.

 \star A power plug is provided for a radio feeder unit, etc. Variable bass and treble controls are fitted for control of the play back signal.

 \star The power output is 3.5 watts heavily damped by negative feedback and an oval internal speaker is built in for monitoring purposes.

+ Facilitles are provided for using the amplifier alone and using power output or headphones while recording or to drive additional amplifiers.

★ The unit may be left running on record or play back even with 1,750 ft. reels with the lid closed.

POWER SUPPLY UNIT to work from 12 volt Battery with an output of 230 v., 120 watts, 50 cycles within 1%. Suppressed for use with Tape Recorder. PRICE £18 0 0.

FOUR CHANNEL ELECTRONIC MIXER

is almost essential for the professional or semiprofessional where a number of different items have to be mixed on one tape recording.


It is recommended by a number of tape recorder manufacturers for this purpose. Any normal input impedance can be supplied to order, balanced or unbalanced, the standard being 15-30 ohms balanced.

The normal output is 0.5 volt on 20,000 ohms or less, but 600 ohms is available as an alternative.

The steel stove enamelled case is polished and fitted with an engraved white panel suitable for making

temporary pencil notes. An internal screened power pack and selenium rectifier feed the five low noise non-microphonic valves.

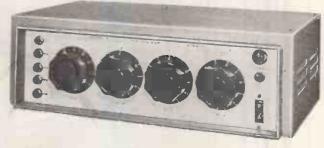Used in many hundreds of large public address installations and recording studios throughout the world.




PRICE £36 15 0.

Manufactured by

VORTEXION LIMITED. 257-263, The Broadway, Wimbledon, London, S.W.19 Telephones: LIBerty 2814 and 6242-3 Telegrams: "Vortexion, Wimble, London."

81

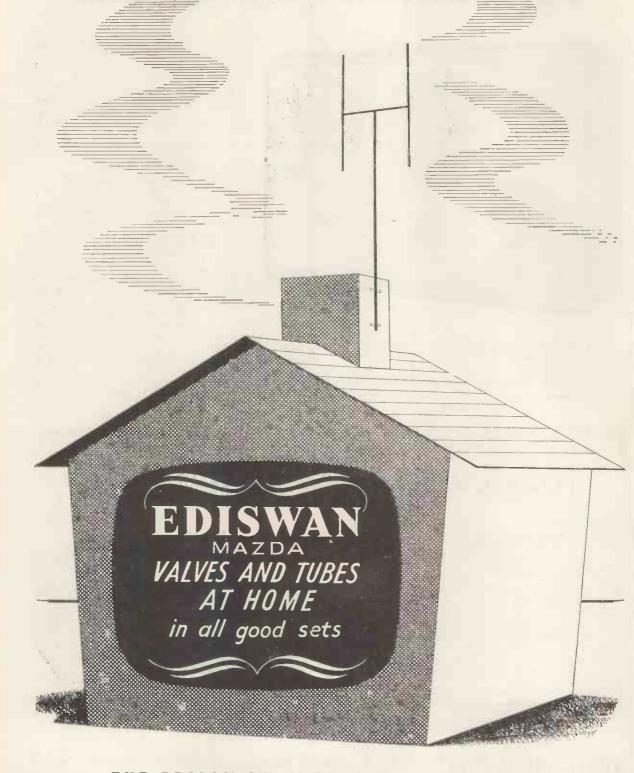

THE EDISON SWAN ELECTRIC COMPANY LIMITED 155 Charing Cross Road, London, W.C.2, and branches Member of the A.E.I. Group of Companies

83

NEW EXPERIMENTAL OUTFITS

EWI INSTITUTES

EXPERIMENTAL OUTFIT

PRACTICAL WAY


Specially prepared sets of radio parts with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business—these Practical Courses are intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM £1 A MONTH

With these outfits, which you receive upon enrolment, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to complete Radio and Television Receiver Testing and Servicing.




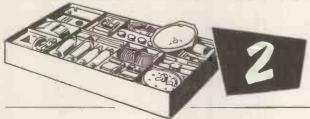RADIO Outfit No. 1.—For carrying out basic practical work in Radio and Electronics, from first principles and leading to the design and building of simple Receivers.



RADIO Outfit No. 2.—With this equipment, you are instructed in the design construction, testing and servicing of a complete modern Superhet Radio Receiver.

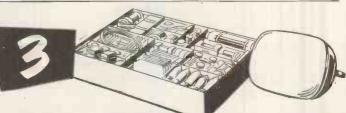TELEVISION Outfit No. 3. ---With this equipment you are instructed in the design, construction, servicing and testing of a modern high-quality Television Receiver.



OTHER COURSES WITH EQUIPMENT INCLUDE: MECHANICS · ELECTRICITY CHEMISTRY · PHOTOGRAPHY CARPENTRY ALSO DRAUGHTSMANSHIP · COMMERCIAL ART AMATEUR S.W. RADIO · LANGUAGES · ETC. POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses : I am Interested in Radio I 📋 , Radio 2 🗋 , Television 🗋 .
Other subjects
To: E.M.I. INSTITUTES, Dept. 127x, 43, Grove Park Road, Chiswick, London, W.4.
NAME
ADDRESS
6/54

E.M.I. INSTITUTES The only Postal College which is part of a world-wide Industrial Organisation

The new Mk. III Camera with 4¹/₂" or 3" image orthicon tube...

The use of the new Marconi camera BD 687 with $4\frac{1}{2}$ " or 3" image orthicon tube and the employment of better circuit techniques in the camera channels have reduced to a negligible degree such faults as black halos, edge effects and electronic ghosts; whilst resolution, grey scale and signal-to-noise ratios are greatly improved. Ingenious design has led to simplicity of control and provided for fully remotely controlled applications.

Besides the camera the channels BD 808/809 comprise a Camera Control and Preview Monitor, Regulated Power Supply Unit and Focus Supply Unit.

MARCONI

Complete Broadcasting and Television Systems

Marconi equipment has been installed in every one of the BBC Television transmitter stations and in the USA, South America, Canada, Italy and Thailand.

MARCONI'S WIRELESS TELEGRAPH CO. LTD., CHELMSFORD, ESSEX

COSSOR presents ...

Cł.

The new Cossor Double Beam Oscillograph MODEL 1052

Two similar amplifier channels with an approximate gain of 2000 and an upper frequency response of 3 megacycles are features of this new Cossor Double Beam general purpose oscillograph. The repetitive or triggered time base has a sweep duration from 200 milliseconds to 5 microseconds.

The instrument will operate from power supplies of any of the various frequencies and voltages encountered in the Armed Services or from standard civil supply mains. The top and side panels are quickly detachable to allow inspection and a removable plate at the rear of the instrument allows access to tube plates, anode and modulator.

and Voltage Calibrator

MODEL 1433

Primarily designed to be used with the new Cossor oscillograph the Cossor Voltage Calibrator model 1433 provides an accurate means of calibration of input voltages to the plates or amplifiers of any oscillograph. Calibrating voltages are read directly from a wide scale meter without any computation being necessary. Measurements can be made to an accuracy of \pm 5% and the instrument can be used in any application where a source of accurately-known voltage is required.

Write for illustrated leaflets about both of these instruments A. C. COSSOR LTD., INSTRUMENT DIVISION, DEPT. 1, HIGHBURY GROVE, LONDON, N.5 Telegrams: Cossor, Norphone, London. Cables: Cossor, London.

COSSOR ELECTRONIC INSTRUMENTS

Telephone : CANonbury 1234 (33 lines)

CI.53

85

JUNE, 1954



SOUND SALES LTD., WEST STREET, FARNHAM, SURREY. Farnham 6461-2-3

to Britain an entirely NEW

Introducing AMPLIFIER & PRE-AMPLIFIER

GNS. COMPLETE A price made possible only by world wide sales.



TL/10 POWER AMPLIFIER

This 10 watt amplifier maintains, in every respect, the world renowned Leak reputation for precision engineering, fine appearance and fastidious wiring.

SPECIFICATION

Circuitry

A triple loop feedback circuit based on the famous TL/12. The output transformer is the same size as in the TL/12.

Maximum power output: 10 watts.

Frequency Response: ±1 db 20 c/s to 20,000 c/s.

Harmonic Distortion: 0.1%, 1,000 c/s, 7.5 watts cutput.

Feedback Magnitude: 26 db, main loop.

Damping Factor: 25.

Hum : --- 80 db referred to 10 watts.

Loudspeaker Impedances: 16 ohms, 8 ohms, and 4 ohms.

H. J. LEAK & CO. LTD., BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3 'Phone: SHEbherds Bush 1173/4

"POINT-ONE" PRE-AMPLIFIER

LEAR

The handsome gold escutcheon plate contributes to the elegant appearance, and blends with all woods.

-1 47 ...

+ Pickup The pre-amplifier will operate from any pickup generally available in the world. A continuously variable input attenuator at the rear of the pre-amplifier permits the instantaneous use of crystal, movingfron and moving-coil pickups.

* Radio The radio input sockets at the rear permit the connection of any tuner unit. An input attenuator is fitted. H.T. and filament supplies are available from the pre-amplifier.

+ Distortion Of the order of 0.1% ★ Write for leaflet W ★

Hum Negligible, due to the use of recently developed valves and special techniques. * Input selector Radio, tape, records ; any and all records

can be accurately equalised.

Treble Continuously variable, +9 db to -15 db at 10,000 c/s.

★ Bass Continuously variable, +12 db to -13

Continuously variable, +12 db to -13 db at 40 c/s. Volume Control and switch The switch controls the power supply to the TL/10 power amplifier. Tape Recording Jacks An exclusive feature. Readily accessible jacks are provided on the front panel for

instantaneous use with Tape Recorders which have built-in (low level) amplifiers.

Telegrams : Sinusoidal, Ealux, London

Cables : Sinusoidal, London


"STROLLER THE EXCITING NEW BATTERY PORTABLE WHICH CONVERTS TO A PICNIC RECORD PLAYER

* Sensitive 4-valve superhet.

- * Attractive 2-tone case and three colour scale.
- * 7 inch elliptical speaker.
- **★** Full A.V.C. and fixed tone correction.
- * Space for Mains Unit.

+ Factory-built look.

The Elpreq "Stroller" is an all-dry battery operated superhet, using frame aerial and 1.5 volt valves Type 1R5, 1T4, 1S5 and 3S4. It is particularly selective and gives powerful results on long and medium waves. Battery con-sumption, however, is quite low. The cabinet is ultra-modern and finished crocodile and/or lizard skin in two shades. The control-board is similarly fin-ished, and with the three-coloured dial, gives the whole a factory-built aspect.

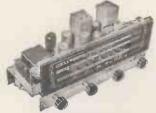

THE "WINDSOR" 5

TABLE RADIO CABINET

Due to a special purchase, we are able to offer this very fine cabinet, size approx. $15\frac{1}{2} \times 14 \times 6\frac{1}{2}$ in.—walnut veneered and satin finished. 37/6, carriage and packing 3/6. Note. This cabinet is the correct one for the chassis above with 6 in. speaker.

A

FEW

This cabinet is offered below cost-it is suitable for a televisor using tube sizes varying from 12in. to 17in., its overall dimensions being 3ft. 5in. high, 1ft. 4in. deep, 1ft. 10in. wide. It is complete with plywood back and "Bowler Hat." Originally made for a very expensive televisor and really good quality. Unrepeatable. Offered at $\pounds 71/5/-$ or $\pounds 2/8/4$ dep., carriage, packing, etc., 12/6. Note: These are cut for 12in. tubes, but the holes for the controls are not drilled.

for the controls are not drilled.

Full constructional details Full constructional details of this superheat and of the Picnic Player unit which, by the undoing of four screws, slips into the cabinet in place of the radio, will be found in our booklet "The Stroller," price 2/6 (returnable if parts purchased). of

purchased). Cost of portable cabinet and all parts for Stroller, including valves, speaker; but not bat-teries, is £8/17/6 (H.P. deposit £2/19/2), carriage 5/-. Cabinet available separately, price 37/6, plus 3/6 postage.

This is a 5-valve A.C. superhet covering the usual long, med-ium and short wavebands. It has a particularly fine clear dial with an extra long pointer travel. The latest type loctal valves are used and the chassis is complete and ready to operate. Chassis the chassis is complete and ready to operate. Chassis size 15in. \times 6in. \times 6in. Price £9/19/6 complete with 8in. speaker. Carriage and insurance 10/-. H.P. terms £3/7/- deposit.



REMAIN

BEETHOVEN 5-VALVE SUPERHET

M. and S.)-large dial, slow motion drive, dust cored colis, etc., £8/17/6, carr. 7/6.



Fine walnut veneered and polished cabinet to take the Beethoven 5-valve Superhet with 64 in 100 speaker, thus making a really excellent table model -worth 818-820. Frice 49(8, carr. and packing, 5f-extra. If bought with the Beethoven chasis, the hire purchase deposit 23/15/8, carr. 10/-.

WELDING Totally enclosed and fitted High, Low and off Switch. Inter-mittent output 4 volts 1,000 amp. Ideal all welding or as power unit for spot welder. Price £4/10/-, Price **£4/10/** carriage an packing 7/6.

WELDING TRANSFORMER



7-WAVE BAND ASSEMBLY


7-wave coil pack for up to 11 mtrs. with R.F. stage, three-gang tuning condenser, slow motion drive, I.F. transformers and numerous other parts, make a really fine receiver. Price 26, plus 10/- post and insurance. Note: The above are new, but removed from chassis

EX-GOVT. BATTERY SET ONLY 30/-



Medium waveband battery superhet, made originally for canteens, etc. In cabinet, less valves, solled needs servicing, few only to clear. Price 30/- each, plus 5/- carriage.

MINIATURE PORTABLE T.V.

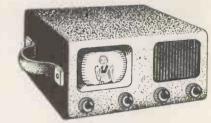

You can probably think of many other reasons when you may need a midget televisor, but it will certainly be useful when :--

(a) Someone is ill, or confined to another room. (b) Your blg T.V. fails.

(c) You want to alter or adjust your big T.V.

The Elpreq Miniature Televisor uses standard conventional circuitry, employ-ing a total of 13 valves and 2 crystal diodes. The cathode ray tube used is a 24in. Service type V.C.R. 139A, which has a standard equivalent and will there-fore always be obtainable. The layout is extremely clean, straightforward, and professional. The wiring, whilst, naturally being alittle more intricate due to minia-turisation, is nevertheless completely accessible, and very good results have been obtained.



The total cost, if you have to buy every part, would come to £16.617, but you may have many of the components already in stock as only standard conventional components are used. A carrying case, similar to the artist's illustration above, will be available shortly. Its size will be approximately 9jin. \times 8in. \times 6in. (internally).

(d) The commercial programmes start.

(e) Servicing an aerial installation.

Full construction data, layouts, diagrams templates, etc., running into some 50 sheets, is available, price 5/~ post free.

COIL PACK 19/6

Manufactured by quite a famous company, this 3-wave Goll Pack incorporates a gram position and Long, Medium and Short wave band, designed for 465 kc/s LP, Brand new and fully guaranteed. Complete with alreadit, only 16/6, limited quantity, so act quickly.



88

٣

F

Γ

-

10

H

2 1

如 置

By

U . 1111 Z

89

1

Ó

CLEARANCE BARGAINS TRULY PORTABLE 4-inch NAVIGATIONAL COMPASS 4/6 wooden carrying case, but In postage 1/6. less fluid. Damaged, but repairable **Record Player** ELECTRICAL To be truly port-K.W. METER 7/6 By Ferranti. Complete works, less the case. able, a record player must be indepenpostage 2/-Slightly damaged, but dent of the mains. repairable, and contains very useful spares. Owing to the cost and weight of dry PORTABLE CABINET batteries, however, Rexine covered. Perfect, with back and handle. 12/6 Ready to take chassis. postage 2/6. Room for batteries or power pack. Size 12in. x 101in. ×71in. DEAF AID 3/6 CASE postage 6d. Polished Bakelite, with pocket clip.

BUTTON

MICROPHONE

Extremely small, carbon granule type. Quantity price 15/- doz.

NOVELTY RADIO

Complete tunable M/L Radio with room for 3in.

speaker in base. Needs only

valves, speaker and batteries.

1/6 postage 6d.

29/6 postage 2/6.

3/6 postage 1/-

2/6 postage 9d

JOINTER In Bakelite case with carbon contacts and trigger action. HAND SPRAY

Made

6/ postage 9d

0

152-153 FLEET STREET, E.C.4. Phone: CENTRAL 2833. Half-day Saturday.

GUN AUTO CHANGE RECORD

Suitable all liquids or powder. Ideal for finishing models, etc.

42-46 WINDMILL HILL, RUISLIP, MIDDX. Phone: RUISLIP 5780. Half-day, Wednesday.

Personal shoppers to any one of these addresses.

Introducing the CLEVELAND SPRINGBAT



it is not advisable to use an electric motor. Fortunately, at the picnic and other functions, when the player is most needed, there are plenty of willing hands to wind. Therefore a spring motor is no objection.



The Cleveland Portable Picnic Player combines the true and full response of electronic recording with the convenience of a modern spring-wound motor. All nicely put together in a handsome carrying case. Price complete ready to work (less batteries) £13/13/-, or £4/11/- deposit, carriage free. Batteries 10/7 the two.

BATTERY AMPLIFIER-

We call this the "Ready." It is a 2-valve amplifier and uses a most efficient circuit, ensuring maximum volume and quality for minimum battery consumption. Midget construction throughout. Size approximately $2 \times 2\frac{1}{2} \times 6in$. Complete, ready to work with O.P. transformer, but less speaker, price 47/6.

THREE OUTSTANDING BARGAINS

CONSORT CABINET In two-tone, highly polished walnut veneer, with contrasting inlaid bands. Lift-up lid and storage compartments. Uncut motor board. Size 2ft foin. wide, 2ft. 5¹/₂in. high, lft. 2in. deep. Clearance to motor board is 6in. Price £9/18/6 plus 15/- carriage and insurance. Or H.P. £3/6/2 deposit. ALL-WAVE RADIO CHASSIS

5-valve superhet for A.C. only. Coloured Edge-lit dial, usual refine-ments, good output on long, medium Price £9/19/6, plus 7/6 carriage and insurance. Or H.P. £3/6/6 deposit.

PLAYER Three-speed with famous Studio pickup for all records. Price £11/ and packing. Or H.P. terms £3/16/8 deposit. Price £11/10/- plus 10/- carr.



29 STROUD GREEN ROAD, FINSBURY PARK. Phone: ARCHWAY 1049. Half-day Thursday.

CLOCK CASE from hard wood, veneered and polished. Un-drilled so suit any clock or other movement. WIRE

JUNE, 1954



No, we do not recommend this method! We offer, instead, SAVAGE 'VLF' and 'LRF' Amplifiers, giving

A SOURCE OF POWER

where it is required for vibration and fatigue testing of structures, components, engineering products, engines, special metals, etc. In this direction, the applications of this equipment are countless, as they are, also, as a variable frequency power source for transformers, meters, motors and electrical component design.

This equipment is inexpensive to purchase, simple and economical to use; gives complete and accurate control at all times.

Ask us TO-DAY for full details, without obligation. Or let us know your problem in this field and we will gladly help you.

W. BRYAN SAVAGE LTD. WESTMORELAND RD., LONDON, N.W.9 TELEPHONE: COLINDALE 7131 Leading organisations now using this equipment include: Bristol Aeroplane Co.; The Brush Electrical Engineering Co., Ltd.; English Electric Co., Ltd.; Ferranti Ltd.; G.E.C.; Handley Page Ltd.; The Imperial College of Science; Siemens Bros. & Co., Ltd.; S.T.C.; Vickers-Armstrongs; R.A.F., Farnborough etc.



LOW RADIC

OUTPUTS 100 watts 'VLF'

3 c/s to 6 c/s

1000 watts · VLF ' 6 c/s to 2000 c/s

MARK II STAR 50 c/s to 10 Kc/s

'LRF' 5Kc/s to 100Kc/s

AMPLIFIERS

To Gladden the Heart of your Development Engineer.

THE QUICK AND ACCURATE PRODUCTION OF PROTOTYPE LAMINATIONS

FREQUENC

We supply prototypes for all new designs in the shortest possible time that size, type, and circumstances permit, in cases of emergency generally within a period of 7-28 days—Nickel Iron Alloy Laminations approximately 40 days. All metals and specifications in most cases immediately available, including High, Medium and Low Silicon Iron, and also in Nickel Iron Alloys. All Nickel Iron Alloy Lamination heat treatment is guaranteed. Send us a sample or sketch of your requirements, together with the specification, which will receive immediate attention.

ELECTRONIC

Telephone : Slough 25171

LIMITED

Telegrams : Lamination, Slough

LAMINATIONS

OXFORD AVENUE, SLOUGH, BUCKINGHAMSHIRE



Both models supplied complete with the renowned RONETTE FC7 Filter Cell Insert Microphone and 1,200 feet of SCOTCH BOY MC2-III Tape



the superb ***ARISTOCRAT''** incorporating the famous TRUVOX Mk. III Tape Deck and the EAP 3 Amplifier

Smart, contemporarystyled cabinet. "Magic Eye" monitoring. Completely portable. Amplifier can be **GNS** used independently for reproduction from gram or radio unit. 7in. x 4in. elliptical speaker. Negative feedback. Miniature BVA valves. Size: $20\frac{3}{4}$ in. x $13\frac{3}{4}$ in. x 9in. Weight: 32 lbs.



the "ELIZABETHAN" now more compact than ever !


Electronic braking. "Magic Eye" plus

headphone monitoring. Miniature BVA valves. 3 watts output. Size:

15% in. x 13% in. x 8% in. Weight: 34 lbs.

GNS

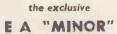2 speed, twin-track recording. Mixing of 2 inputs. Simple push-button control.



This specially designed, 2 waveband, crystal feeder unit enables the "Elizabethan" or "Aristocrat" to operate as a full-size radio! Optional extra at £3-15-0 including tax. the EAP 3 TAPE RECORDER AMPLIFIER recommended and approved by TRUVOX for their Mk. III Tape Deck

Frequency range: 75 c/s—10 kc/s. 3 watts output on playback. Separate high and low gain inputs with mixer control. "Magic Eye" record level indicator. Variable tone control. Amplifier can be used for high-fidelity reproduction from gram or radio feeder unit. Separate power pack, supplying instantaneous braking voltage. Price £15 (carriage extra).

Model EAP2, at the same price, with similar specification, is available for use with the MOTEK and LANE Tape Units.



92

WIRELESS WORLD




- SIGNAL TRACER A.C.
- 5-WATT QUALITY AMPLIFIER A.C. with NFB. 10-WATT P-P QUALITY AMP., A.C. with NFB.
- SIGNAL GENERATOR, A.C. etc., etc.
 - NO TEST GEAR REQUIRED !

Apart from construction details and large blueprint circuits, *Roding's "Home Constructors Handbook" contains complete parts lists and technical descriptions of these outfits, also set building hints, servicing hints and tips, facts and formulae, resistance colour code, symbols, data, etc. AND our current catalogue. Printed on glossy art paper and profusely illustrated throughout, this publication is now acknowledged to be at the top of its class I Over 70,000 copies sold ! Ready-punched chassis and all parts always in stock. Easy-as-ABC construction sheets available. Be wise and DON'T DELAY-SEND FOR YOUR COPY TO-DAY ! Also obtainable from W. H. Smith & Son, Modern Book Co., etc. **RODING LABORATORIES**

(Dept. WW5). BOURNEMOUTH AIRPORT, CHRISTCHURCH.

SWITCHMANSHIP!

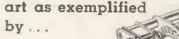A term in current vogue describing the switch-maker's



WINKIF

PRECISION **MULTI-WAY SWITCHES**

The range of Winkler Precision Multi-way Switches fulfils the requirements of the instrument designer for a high grade component consistent with the quality demanded of present-day instruments and electronic equipment.

Now available with up to 30 contacts per wafer, 1 to 16 banks, 1 to 3 pole $\frac{1}{2}$ amp., 80 V.A. per contact Write also for details of WINKLER KEY SWITCHES.

G. A. STANLEY PALMER A. R. Ae. S. Maxwell House, Arundel Street, LONDON, W.C.2.

Phone : TEMple Bar 1610

The Wolf Type 51 trigger-feed soldergun is designed for faster, cheaper and easier soldering and is ideal for rapid work on small connections and repair jobs. The solder is fed automatically with a finger-trigger action and two reels of solder are supplied-one 15 feet acidcored and one 15 feet of resin-cored.

DESIGNED FOR

economical

SOLDER

Only Wolf offer all these profitable advantages : ---

- Perfect balance
- Rapid constant heat Low current consumption
- Localised heat
- Easy grip handle
- 5 feet tough rubber 3-core cable

Electric




FIVE OTHER MODELS

TO CHOOSE FROM

all leading tool merchants and factors

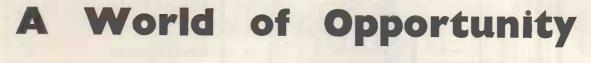WOLF ELECTRIC TOOLS LTD PIONEER WORKS . HANGER LANE . LONDON . W.5 Branches : Birmingham, Manchester, Leeds, Glasgow. Tel : Perivale 5631-4



FOR MEN OF EXPERIENCE, ABILITY AND ENTHUSIASM



We are looking for the right men for our Design and Development Laboratory teams. Our immediate need is for electronic engineers, and if you feel that you have the necessary qualifications please write, in confidence, to Dept C.P.S., Marconi House, Strand, London, W.C.2. Alternatively call personally at Marconi House between 9.30 and 12 any Saturday morning in June for an informal talk.

MARCONI INSTRUMENTS

Binks .

WIRELESS WORLD

REGD. TRADE MAR

JUNE, 1954

MAGNETIC AMPLIFIER CIRCUITS Doctor William A. Geyger

Magnetics Division, U.S. Naval Ordnance Lab'try White Oak, Maryland

Saturable-core reactor devices have been developed into extremely valuable arrangements. Whereas they were originally used to control theatre lighting loads, modulate high-frequency currents in radio transmitters, and to measure large direct currents, they are now applied, for example, as magnetic servo amplifiers, magnetometers, and special components of electronic devices. In fifty years, a great deal of information on these devices and magnetic amplifiers has been accumulated in the form of patents, scientific papers, and technical reports, but in widely scattered sources and several languages and methods of treatment. This book is an up-to-date and systematic treatment of the subject, using uniform terminology and graphic symbols. The whole approach is suitable for easy understanding and for comparison with various circuits.

300 pages 9 × 6 inches 42s 6d

Available from your usual Bookseller

McGraw-Hill Publishing Company Ltd

McGraw - Hill House London EC4



cheaper

for

Plastic Plug Socket



This new Ever Ready Battery, combining a 90 volt high tension unit and a 1.5v low tension section, has been designed for use with the latest Ever Ready low consumption valves, type DK96, DF96, DAF96 and DL96, which use only half the filament current (25mA) of the older series valves (50mA).

ERRE

32

A balanced service life of 300 hours is obtained when the high tension current is 10.5 mA at 90 volts and the low tension current 125 mA at 1.4 volts; the respective cut-off voltages being 40v and 1.0v on load.

The maximum battery dimensions are $7\frac{13}{16}$ " $\times 3\frac{7}{8}$ " $\times 4$ " and the weight is 5 lbs. 10 oz. **Price 16/-.**

BATTERY PLUG

The new Ever Ready plastic 4 pin battery plug has been specially designed to ensure correct and easy battery connections. Plugs are fitted with four staggered metal pins, also four coloured wires 18" in length. List **Price** 2|- complete. Suitable for use with BSS. 1766-1951.



EVER READY DRY BATTERIES FOR RADIOS TORCHES · HEARING AIDS · CYCLE LAMPS



dependent electrical quantities. Send for prices and full specification. BRITISH PHYSIC RADLETT, HERTS. M. R. Supplies Ltd., 68 New Oxford Street, W.C.1

<u>ᲐᲦᲛᲑᲦᲑᲑᲦᲐᲦ</u> Დ Მ Მ ᲓᲛ ᲛᲓᲦ ᲛᲢᲦ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢ<mark>Დ</mark> ᲐᲦᲛᲑᲓᲔᲑᲑᲓ Მ Დ Მ Მ ᲓᲛ ᲛᲓᲦ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ ᲛᲢᲓ Მ Ა Ნ

WIRELESS WORLD



TAPE RECO

HEA Wearite. Br MICROPHON All types a TAP

Ferrograph

Vortexion Grundig 700L

Grundig Tk.9 M.S.S. PMR.3

Reflectograph

Soundmaster (Kit)

Kenton (Truvox Deck)

Reflectograph

E.A. Products for Truvox Reslo Ribbon Microphone Reslo Moving Coil Microphone

Lustraphone LX.55

Scotch Boy, B.A.S.F., Agfa, Gevaert, E SOUNDMASTER PA -send for WEARITE

Oscillator colls, etc., from stock.

AMPLIFIERS AND

Vortexion

C.J.R.

G.B. E.M.I.

Lane

Truvox

Lane Kit

Acos 22.1 crystal

			ine outright purchase
APE RECORDERS	Cash Price	Deposit	heavy item, but that is no
	£ s. d. 79 10 0	£ s. d. 27 0 0	not straight away have the
••••••••••••••••••••••••••••••••••••••	84 0 0	28 0 0 28 0 0	
••••••	84 0 0 68 5 0	28 0 0 22 15 0	by Classic H.P. Here are a
		33 0 0 43 10 0	deposits in relation to the f
	87 0 0	29 0 0	
• • • • • • • • • • • • • • • • • • • •	84 0 0 150 0 0	28 0 0 50 0 0	
	60 0 0	20 0 0	MOTORS AND PICKU
	47 5 0 63 0 0	16 5 0 21 0 0	Thorens 3-speed
			Collaro with pickup
TAPE DECKS	35 0 0	12 0 0	Thorens 3-speed Collaro with pickup Jason Motor, 3-speed Decca GU4 3-speed, with 2 Decca pic (mounted in walnut case) Collaro 3/54 with pickup Monarch Autochangers Garrard R.C.80
	41 0 0	14 0 0	Collaro 3/534 with pickup
· · · · · · · · · · · · · · · · · · ·	23 2 0 39 10 0	8 2 0 13 10 0	Garrard R.C.80 Garrard R.C.90 (as available)
	17 10 0	600	Diamond stylus pickups
· · · · · · · · · · · · · · · · · · ·	17170 2200	512 4 768	Leak 78
RS AND MISCEL			331 Lowther 78 331
KS AND MISCEL		768	Diamond stylus nickun heads
	29 10 0	910 0	Decca STD L.P. ''H'
••••••	13 0 0 15 0 0	5130 500	Connoisseur Std. or L.P.
	16 16 0	5 16 0	RADIO FEEDER
	900	500	Chapman F/M Chapman 8.5
one	600		Chapman 8.6 BS. Lowther R.E.S.
	5 5 0	-	Lowther D. T.4 Lowther D. T.5
	5156 2100		
			Leak Armstrong F.C.38 Armstrong RF.41
MOTORS All types available.			AMPLIFIERS-WITH CO
			GoodsellWilliamson
HEADS /earite. Bradmatic,	010		Leak TL.10 QUAD Mark II Pye F. 9J/F.F.19A Rogers Baby de luxe Bogers Ming
featice. Draomatic,	ett.		Rogers Baby de luxe Rogers Minor
ROPHONE STA	NDS		Rogers Minor Lowther L.E.S. Rogers Senior amplifier and control unit
All types available.			Goodsell CR.500 Armstrong A.10
TAPES			LOUDSPEAK
a, Gevaert, Emitape, Fo	errograph, etc.		Kilmahorn-Vitevor
ASTER PARTS IN			Corner Ribbon-Acoustical Corner-Lowther Tannoy 12/n. in Cabinet
-send for special lis	it.		Wharfedale Super 12CSAL Voight Corner Horn (S/H.)
WEARITE PARTS	;		
stock.			Goodmans Axiom 150
_			Tannoy 12in. Duo Concentric
			Wharfedale W12CS Wharfedale Golden 10CSB
and varied range	e of annow	the ord	LOUDSPEAKER
the largest in			For Goodmans 60 or 150-Corner Bass F

The outright purchase of equipment can be a reason why you should e best of gear available a few examples showing full cash purchase price.

HIGHERIDRITTY

and **COMPONENTS**

		the Second
MOTORS AND PICKUPS	Cash Price	Deposit
Thorens 3-speed	£ s. d. 32 0 0 23 8 11	£ 1. d. 10 13 4
Thorens 3-speed	23 8 11 18 18 0	7 18 11
Decca GU.4 3-speed mounted in walnut case).	18 18 0 12 12 0	6 6 0 4 4 0
(mounted in walnut case)	12 10 0	4 4 0
Monarch Autochangers	10 6 1 18 10 0 19 6 7	3 12 9 5 10 0 6 6 7 7 9 8
Garrard R.C.80	19 6 7 22 8 11	6 6 7 7 9 8
Diamond stylus pickups		1.1.1
Leak 78	17 10 0 17 10 0 21 19 9	5168 5168 7199 7199
Low ther 78	21 19 9 21 1 9 9	7 19 9 7 19 9
Diamond stylus pickup heads Decca STD	5 19 1	2 19 1
L.P	6 18 9	2 6 3
"H" Connoisseur Std. or L.P.	6189 795	
RADIO FEEDER UNI		
Chapman F/M	15 0 0	500766
Chanman 8.5	01 6 6	1413 4
Chapman B.6 BS. Lowther R.E.S. Lowther D.T.4	44 0 0 23 15 9 37 17 10 44 0 0	8 15 9
Lowther D.1.5 J	44 0 0	8 15 9 13 17 10 14 13 8 7 6 8 11 19 0
Leak	22 0 0 34 19 0	11 19 0
Armstrong F.C.38	34 19 0 23 13 0 31 19 8	8 0 0 11 13 4
AMPLIFIERS-WITH CONTR		
GoodsellWilliamson	45 12 0 28 17 0	15 4 0 9 9 0
OUAD Mark II	28 17 0 42 0 0 42 0 0	9 9 0 14 0 0
Pye P.F.91/P.F.19A Rogers Baby de luxe Rogers Minor Lowther L.E.S.	23 0 0	7 13 4
Lowther L.E.S.	11 10 0 23 15 9	8 15 9
Goodsell CR.500	43 0 0 30 10 0	15 4 0 9 9 0 14 0 0 7 13 4 3 16 8 8 15 9 14 6 8 10 3 4 9 16 8
Armstrong A.10	29 10 0	916 8
LOUDSPEAKERS		
Klipschorn-Vitavox Corner Ribbon-Acoustical	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	50 0 0 32 10 0
Corner-Lowther	95 0 0 96 0 0 30 16 0	32 10 0 10 4 0
Wharfedale Super 12CSAL Voight Corner Horn (S/H.)	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	$\begin{array}{cccccccccccccccccccccccccccccccccccc$
Goodmans Axiom 150		2 15 0
Tannoy 121n. Duo Concentric Wharfedale U15CS	27 10 0 17 10 0	3159934 5168
Wharfedale W12CS	9150	$ \begin{array}{r} 3159\\ 934\\ 5168\\ 350\\ 300 \end{array} $
Wharfedale Golden 10C8B	8 6 7	300
LOUDSPEAKER CABI		
For Goodmans 60 or 150-Corner Bass Reflex, Walnut	1910 0	610 0
For Goodmans 150 or 22-Corner Bass Reflex, walnut	25 0 0	8 6 8
For Wharfedale Super. 12CSAL Corner Bass		
Reflex, walnut For Wharfedale Super 12CS/AL-Bass Reflex	21 0 0	
Cabinet	18 0 0	600
a film and the second sec	-	-

GO)


LTD)

Hnd our vast and varie equipment, possibly the largest in the country, is backed by the famous Classic pre-sales test scheme, whereby every piece of apparatus is thoroughly tested before despatch and guaranteed by our own highly skilled technicians, thus enabling us to give a firm guarantee.

GLASSIC ELECTRICAL

352-364 LOWER ADDISCOMBE ROAD · CROYDON · SURREY TEL · ADDISCOMBE 6061-2

JUNE, 1954

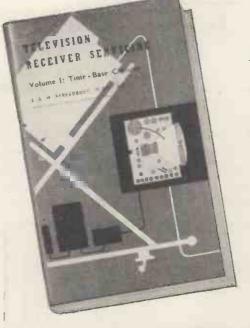


Filling a long-felt need

A valuable, practical book for television- service engineers

Although written specially for the radio servicing engineer who wishes to embark on TV servicing, this book will be invaluable to everyone interested in TV receiver fault-finding. It is written for the practical man in terms he understands, and is fully illustrated by many clear diagrams. It is strongly recommended to prospective candidates for the R.T.E.B.—City & Guilds TV Servicing Certificate Examinations and will be of particular help in the Practical Test.

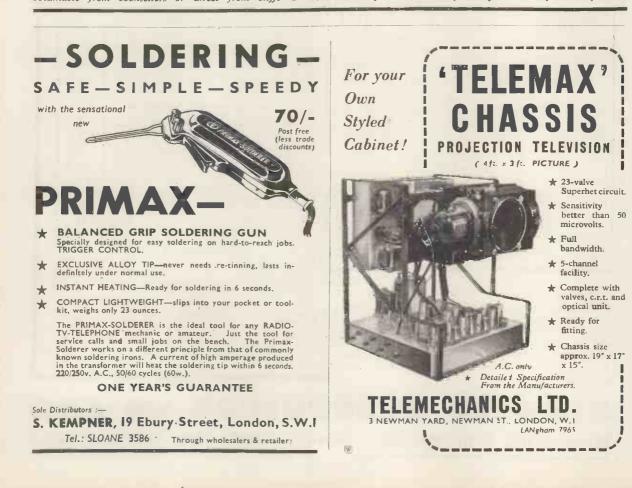TELEVISION RECEIVER SERVICING 21s net By Post 21s 8d Published for "Wireless & Electrical Trader" obtainable from booksellers or direct from Iliffe & Sons Limited, Dorset House, Stamford Street, London, S.E.I





98

WIRELESS WORLD

JUNE, 1954





HARTLEY-TURNER Sound Equipment

Following our recent announcement and introduction to our products, we feel justly proud in presenting the 20 watt Hi-Fidelity Amplifier. Used in conjunction with any suitable high quality speaker, "Hi-Fi" is achieved within the real meaning of the term.



HARTLEY-TURNER 20 WATT AMPLIFIER

Brief specification: Push-pull tetrode output with valve voltage stabiliser for constant screen volts under all conditions. Negative feedback, giving 20 watts into a 4 ohm load. Output impedances, 4 ohms and 15 ohms. A.C. mains operated at 110-115 and 200-250 v. Additional power supply sockets for preamplifier, 6.3 v. 1A, 300 v. 5 mA (stabilised) and for radio tuner unit 6.3 v. 2 A., 300 v. 25 mA. All component parts are of the best quality, the transformers and chokes being our own manufacture to rigid design specifications.

PRICE: £33-0-0 Complete with Valves

Why not send for our illustrated descriptive literature sent free and post free on request? This includes full details of our Long Playing Record Supply Service.



Telephone: RIVerside 7387





WHETHER the need is for a single unit or a supply running into thousands... if it's a Selenium Rectifier that must fulfil critical requirements and maintain its characteristics over long periods... the answer is to be found with Electrix.

• Electrix Rectifiers are characterised by their cool running and consistent longlife conformity to stated specification.

• Manufacturers, Traders and Electronic Engineers, send us your specific requirements.

• Your needs may possibly be met from "standard" types, or

• "To specification" models can be quickly prepared.

• Quotations by return ... and deliveries a matter of days only.

We welcome export enquiries.

Here are some typical "standard" full-wave types

	Cacil
Output 12/15 Volts D.C. I Ampere. List Price	9/-
Output 12/15 Volts D.C. 2.5 Ampere. "	13/6
Output 12/15 Volts D.C. 4 Ampere. "	22/6
Output 12/15 Volts D.C. 6 Ampere. "	35/-
T I C	

Trade Supplied

• Heavy duty rectifiers with say 230/250 volts A.C. input and 220 volts D.C. output a speciality.

• We use only freshly manufactured selenium plates and components, no ex-W.D. materials whatsoever.

HOUSEHOLD ELECTRIX LTD 47-49 HIGH ST., KINGSTON-ON-THAMES Telephone: KINgston 4585

for all Good Instruments

COPPER OXIDE RECTIFIERS A range of rectifiers designed to suit all types of instrument movements.

> The performance data and details of the types available are given in our publication No. C.O.R. 5305/2.

Please apply to the following address :--

RICAL SALFORD 3 WORKS STHEFT ELECTRIC CO. LTD. OF THE GENERAL ENGLAND Subsidiary of



This beautiful and stirring film. The CINEMASCOPE RECORD of the ROYAL TOUR was a production problem to test both technicians and equipment. No delays, errors or retakes were permissible on any of the vital sequences of the rigid schedule. Like the technicians using it, the LEEVERS-RICH SYNCRO-PULSE RECORDER was "on top of the job" throughout this 30,000 miles location.

Technical details and prices from :---LEEVERS-RICH EQUIPMENT LTD. 37 Wardour Street, London, W.I. GERrard 4502



PANORAMIC WAVEFORM ANALYSER

FOR THE ANALYSIS OF VIBRATION, NOISE, DISTORTION AND OTHER COMPLEX WAVEFORMS THE ANALYSER SHOWN HERE IS UNIQUE.

It provides a continuous presentation of the A.F. spectrum simultaneously showing frequencies and amplitudes of the individual components. Frequency components differing from each other by only 10 c.p.s may be distinguished and harmonics, etc. as low as 0.1% of the fundamental shown. Permanent records may be obtained by photographing the display.

FOR FULL TECHNICAL DETAILS OF THIS AND OTHER INSTRUMENTS, PLEASE COMMUNICATE WITH . .

INDUSTRIAL ELECTRONICS DERBY ROAD, EAST SHEEN, LONDON. S.W.14

Telephone : PROspect 8211/2



MODEL 1950/2 A.F. PANORAMIC WAVE ANALYSER



DENCO (CLACTON) LTD. 357/9, Old Road, Clacton-on-Sea, Essex.

JUNE, 1954

K 6



Introducing a new model to our range which has been designed to fulfil the requirements of compactness of design, ease of operation, high standard of performance and attractive appearance.

★ A.C. Mains 200/250 volts.


★ Steel Frame size 14³/₄ x 10⁴/₄ finlshed high gloss cream.

+ 3 motor drive.

★ Low " wow " level.

★ "Drop-in " tape loading.

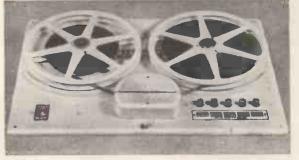- ★ Half track, high impedance record and erase heads, frequency response 50 c/s-10,000 c/s.
- + Push button control,
- ★ Electrical braking system (self contained power pack).
- ★ 2 speeds electrically switched $(7\frac{1}{2}^{"} \text{ and } 4\frac{1}{2}^{"} \text{ per second})$. Giving 1 and $1\frac{3}{4}$ hours respectively.
- * Rewind and fast forward functions without handling tape.



THE NEW UNIT List Price 19 GNS.

> K.5. Single Speed version of K.6 unit available. 110/120 volts. List Price 181 gns.

SEE AND HEAR IT AT YOUR LOCAL DEALER

MODERN TECHNIQUES

138-144 PETHERTON ROAD, LONDON, N.5

Telephone: Canonbury 5896

-M. R. SUPPLIES Ltd.-(Established 1935)

(Established 1935) Immediate despatch of the following first-class material, mostly brand new, fully and fairly described. Prices nett. BIGEOAMMETERS. Very fine offer, limited to about 400 meters only. Deflection 0/50 microamps, first-grade microammeters, 1st, gr. microil, same price. BILLIAMMETERS. Very fine offer how hence that new, 52(6 des. 1/6). Also a few new 24in. first panel 0/50 microammeters, 1st, gr. microil, same price. MILLIAMMETERS. 9(1) millisang, 2in. square model (these are calibrated in knots but(s., deflection is 1 mA.), new, 16/6 (des. 1/-). SELENIUM RECIFIERS (3.F.C.). Exceptional offer of brand new high duty ratings, in very limited supply. Single ut as: 15 voits 75 amps, 30 voits, 30 amps, do voits 15 amps, any one £7/17/16 (des. 7/6). Also to units, 120 voits 12 amps, the pair £11/17/6 (des. 7/6). Also 7 voits 4 amps, 35/-112/15 voits 8 amps, 29/8 (des. either 2/-). We can supply many other rectifier requirements— all new goods.

all new goods. $\forall ARIAG \ TRANSFORMERS, input continuously variable 200/240 v. Output 220 v.$ (or other voltages in same ratio). Loading 1.65 kva. Brand new, in steel oil tankapprox. 10in. × 5in. × 5in. ±55/13/6 (des. 5/-). When these are sold we haal offerslightly used same model at slight reduction in price. Also in stock all models of $Philips Variable Transformers, prices from <math>\pm 7/5/$ - (260 va.) to $\pm 19/17/6$ (2080 v.a), Database contest.

Statisty used same model at sight reduction in price. Also in stock all models of pullips Variable Transformers, prices from £7/5/- (260 v.a.) to £19/17/6 (2080 v.a), to £10/17/6 (2080 v.a), to £11/10/- (2080

makers. 5 mA copper oxide, 8/6.

We guarantee full satisfaction with every item purchased from us.

M. R. SUPPLIES, LTD., 68 New Oxford St., London, W.C.1. Telephone : MUSeum 2958



NEW! The Manning-Carr Miniature **Polarised Relay**

DATA—A Sensitivity of 25 milli-watts and capable of handling mains voltage on the contacts with alternating currents up to 0.25 amps. Being polarised it has the advantage that the Armature contact can be biased to lock in either direction by suitable adjustment of the contact screws, which provides

a useful facility where pulse operation is required. Speed of operation is also high and the Relay will follow A.C. frequency of 50 c.p.s. Resistance up to 8,000 ohms, which is acceptable for Anode circuits. Alternatives to specification if required. Sole Concessionaires.

POST OFFICE TYPES 3,000 AND 600 RELAYS

to specification. Tropicalising, impregnating and Services jungle finish if required. Delivery 3-4 weeks. Manufacturers to H.M. Govt. Depts. and leading contractors.



MAINS TRANSFORMERS

	FULLY INTERLEAVED	•	ELECTRO
1	SCREENED AND IMPREGNATED. ALL GUARANT ALL PRIMARIES ARE 200/250 v. Half Shrouded.	EED.	
	HSM63 (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps.,	16/3	Any Qua
	5 v. at 2 amps HS63. Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at	16/6	LOOK AT
į	2 amps. HS40. Windings as above. 4 v. at 4 amps., 4 v. at 2 amps	16/6	
	Output HS2, 250-0-250 v. 80 m/a.	19/-	for equipme
	HS2. 250-0-250 v. 80 m/a. HS3. 350-0-350 v. 80 m/a., 19/ HS30. 300-0-300 v. 80 m/a. HS2X, 250-0-250 v. 100 m/a., 21/ HS75. 275-0-275 v. 100	19/-	Receiver, R54/
1	HS30X. 300-0-300 v. 100 m/a., 21/ HS3X. 350-0-350 v.	21/-	Transmitter, Scanner, RC94
	100 m/a.	21/-	Test Set, TSI3
I	Fully Shrouded FSM63 (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps.	•	Frequency Me
l	5 v. 2 amps.	16/9	Frequency Me
	FS2. 250-0-250 v. 80 m/a. FS30. 300-0-300 v. 80 m/a., 21/ FS3. 350-0-350 v. 80 m/a	21/	Receiver, BC3
	FS2X. 250-0-250 v. 100 m/a., 23/ FS75. 275-0-275 v. 100 m/a.	23/	Receiver, R89/
	FS30X. 300-0-300 v. 100 m/a., 23/ FS3X. 350-0-350 v. 100 m/a.	23/-	Control Box, Klystron, 723A
	All the above have 6.3 4-0 v. at 4 amps., 5-4-0 v. at 2 amps. FS43. Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v.		Riystron, 7257
I	4 amps., C.T. 5 v, 3 amps. Fully shrouded	47/6	We pay similar
I	4 amps., C. T. 5 v. 3 amps. Fully shrouded F35 X. Output 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps.,	67/6	RECEIVERS.
I	4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded	65/-	AR88D, R65/AI
	3 amps., 5 v. 3 amps. Fully shrouled FS43X. Output 425-0-425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v.	44/-	RI9/TRCI, RI5
I	6 amps., 5 v. 3 amps., e101 shrouded HS6. Output 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v.	63/6	ARTI3, TDE.
ļ	3 amps. For receiver R1355. Half shrouded	26/6	TRANSCEIVE
I	-3 amps, Half shrouded F36. Output 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v.	27/9	522, TCS, BC80
	3 amps. Fully shrouded	29/6	INDICATORS
	2 amps., C.T. 5 v. 3 amps. Fully shrouded	29/9	CPN2, BCII5I, TEST SETS.
	3 amps. Fully shrouded	28/6	"TS" and IEIS
	PRI/I. Output 230 v. at 30 m/a., 6.3 v. at 1.5/2 amps FSI50. 350-0-350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps	21/- 31/6	MODULATO
I	FS150X. Output 350-0-350 v. at 150 m/a, 6.3 v. at 2 amps. C.T. 6.3 v. at 2 amps., C.T. 5 v. at 3 amps. Fully shrouded The above have inputs of 200/250 v.	31/6	CM3.
	OUTPUT TRANSFORMERS		SYNCHRON
	MIDGET OP. 5,000Ω to 3Ω	3/9	RA62, RA88, R
	8,000Ω to 3Ω MOPI. Ratios, 26, 46, 56, 66, 90, 120-150 m/a. max. current, C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel,	3/9	DM28, PU16.
I	C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel, and clamped, each	5/6	TUNINGUN
Į	and clamped, each	17/9 25/9	TN54, TU57, TU
ļ	Chokes for Williamson's Amplifier, 30 H. at 20 m/a	16/6	JB91, JB95, JB9
ł	10 H. at 150 m/a.	32/-	ANTENNA
Į	All 200/250 v. Input.	•	AS27, AT4, AN
۱	F3. 6.3 v. @ 3 amps. F4. 4 v. @ 2 amps. 7/6. F6. 6.3 v. @ 2 amps.	9/6 7/6	MOUNTING
ļ	F3. 6.3 v. @ 3 amps. F4. 4 v. @ 2 amps. 7/6. F6. 6.3 v. @ 2 amps. F6X. 6.3 v. @ 0.3 amps., 5/6. F12X. 12 v. @ 1 amp. FU6. 0-2-4-5-6.3 v. @ 2 amps., 10/ F12. 12.6 v. tapped 6.3 v.	8/-	And almost
ļ	@ 3 amps. F24, 24 v, tapped 12 v, @ 3 amps.	16/6 23/6	unit even if
l	F29. 0-2-4-5-6.3 v. @ 4 amps., 18/9. FU12. 0-4-6.3 v. @ 3 amps. F1124 0-12-24 v @ Lamp	17/6	Phone us im
	F5. 6.3 v. @ 10 amps. or 5 v. @ 10 amps., or 12.6 v. @ 5 amps., or 10 v. @ 5 amps.	34/-	Deal with th
İ	F6/4. Four windings at 6.3 v. tapped 5 v. @ 5 amps. each, giving by suitable series and parallel connections up to 6.3 v. @		established fo
I	20 amps	51/6	which is by fa
l	Quotations, etc.—stamped addressed envelope, please		Ham Equipm
l	C.W.O. (add 1/6 in £ for carriage).		AITHA
ĺ	Export enquiries invited.		
6			JERSEY HO
	H. ASHWORTH (Dept. W.)	N),	MAN
	676, Gt. Horton Road, Bradford 7, Yo	rks.	Telephor
ĺ			

WE PAY TOP PRICES FOR ۲ AMERICAN SURPLUS ELECTRONIC EQUIPMENT Any Quantity or Condition LOOK AT THESE EXAMPLES for equipment in good condition 8 Receiver, R54/APR4 complete ... £200 Transmitter, ET4336 £110 Scanner, RC94 £100 Test Set, TSI3 £100 0 Frequency Meter, TSI75/U £80 Frequency Meter, BC221 £26 Receiver, BC348R £25 Receiver, R89/ARN5 £25 Control Box, 23270..... £5 £3 Klystron, 723A/B We pay similar remarkable prices for:-٠ RECEIVERS. RIII/APR5, R5/ARN7, AR88D, R65/APN9, BC1033, R15/APN3, R19/TRCI, R15/CPN2, BC348. TRANSMITTERS. CPN2, TII/APN3, ARTI3, TDE. TRANSCEIVERS. ARCI, ARC3, SCR-522, TCS, BC800, RTI/APN2. . IDI7/APN3, ID18/ INDICATORS. CPN2, BC1151, BC1152, I-81A, I-82A. TEST SETS. Any unit with prefix "TS" and IE19, BC638, I-208. MODULATORS. BC1091, BC1142, CM3. SYNCHRONISER. BCI148. POWER UNITS. RA34, RA42, RA59, RA62, RA88, RA90, MG149, PE98, PE158, 0 DM28, PU16. TUNING UNITS. TNI7, TNI8, TNI9, TN54, TU57, TU58, TU59. CONTROL GEAR. BC1150, BC1145, JB91, JB95, JB98, JB102, C45-ARCI. ANTENNA GEAR. BC223A, RC94, 0 Ô AS27, AT4, AN104. MOUNTINGS. FT237, FT247A, FT154. And almost every American made unit even if not mentioned above. Phone us immediately, transfer charge. . . Deal with the firm that has been established for twenty-five years and which is by far the largest buyer of Ham Equipment. ALTHAM RADIO CO. JERSEY HOUSE, JERSEY ST. MANCHESTER 4

Telephone : Central 7834/5/6

103

JUNE, 1954

TELCONNECTORS

co-axial plugs and sockets

These connectors enable identical cables to be joined together, or flexible cables to be joined to their lead-sheathed counterparts. They are fully waterproofed and suitable for use up to 3,000 Mc/s. The flange may be fitted to either half for passing cables through panels.

Illustrated is the 53/29M Plug and 53S/29M socket, for use with PT29M cable; also the 53C panel-mounting socket for terminating cable runs and the 53S protective cap

for excluding dust and moisture.

All types are readily available in various sizes and combinations. Write for publication T/1.



THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD Works - - Telcon Works, Greenwich, S.E.10 Tel : GREenwich 3291 Branch Office - 43 Fountain Street, Manchester 2 Tel : Central 0758

TELC

ASK ARTHURS FIRST

★ NEW VALVES
Send your enquiries for all Radio and Electrical goods, especially those in short supply.
We have probably the largest variety of valves in the country. Let us know your requirements.
AVO METERS IN STOCK
Avo Model 7
Avo Model 7
£19 10 0
Avo Model 8
£23 10 0
Signal Generator, Mains and Battery
Models
£30 0 0
Electronic Test Meter
£40 0 0
Valve Characteristics Meter

Also full range TAYLOR METERS. List on request.

VALVE MANUALS Mullard 5 Osram 5 Brimar No. 5 2	Leak TL/10 Amplifier and "Point One "Preampli- fier complete
Mazda, Part 2 2 0 Mullard Valve	corder £68 5 0
Multard value Replacement Guide	Grundig Microphone £6 6 0 Recording Tapes : All makes in stock. Terms C.O.D. or Cash with order. Goods offered subject to being unsold and to price alteration.
Cart DROPS: ARTH	HUR GRAY. LTD.

GRAY HOUSE, 150-152 CHARING CROSS ROAD, LONDON, W.C.2 TEMple Bar 5833/4 and 4765. Cables : TELEGRAY, LONDON

TYPES 3000 and 600 HIGH SPEED and A.C. to 400 VOLTS TROPICALISING-IMPREGNATING UNISELECTOR SWITCHES From 3 to 8 Bank-Al. Resistances **KEY SWITCHES** Several types in stock GOVERNMENT CONTRACTORS PEEDY DELIVERIES DAVIS JACK (RELAYS) 36 PERCY STREET . LONDON . W.I MUSEUM 7960 LANGHAM 4821

cables

MAGNETIC RELAYS

Built to

Specification



This photograph shows a method of assembling zirconium tubes in a zirconium plate backed with a steel plate to form a condenser tube plate. The five zirconium tubes are expanded into zirconium bushes which are then screwed into the steel backing plate and welded on to the zirconium plate.

SOUNDMASTER

MUREX LTD (Powder Metallurgy Division) RAINHAM, ESSEX. Rainham Essex 3322 London Sales Office : CENTRAL HOUSE, UPPER WOBURN PLACE, W.C.I. EUSton 8265



BAIRD TELEVISION . LANCELOT ROAD . WEMBLEY . MIDDX

JUNE, 1954



RADIO EXPORT

TUBES ONLY

1,000 types of Receiving and Transmitting Radio Tubes available ex stock.

HALL ELECTRIC LTD Haltron House, 49-55Lisson Grove, London, N.W.1. Tel.: Ambassador 1041 (5 lines) Cables : Hallectric, London

Other Components by : T.C.C., BELLING-LEE, WELWYN, OSRAM, COSSOR, ERIE.

Come and Hear it! THE WORLD-FAMOUS WILLIAMSON AMPLIFIER

WITH PARTRIDGE TRANSFORMERS & CHOKES

By common consent the finest ever!

ASSOCIATED EQUIPMENT

ASSOCIATED EQUIPPIENT			
Connoisseur 3-speed Motor			11
Collaro 3-speed Transcription Motor	£13	9	6
Collaro AC3/534 with Studio " O " or " P " Pick-up	£10	6	0
Garrard "T" 3-speed Motor with fixed Crystal T.O.H.	£10	12	8
Garrard "T.A." 3-speed Motor choice of MPM2 Heads	£10	16	0
Garrard L.R.S.I. Centre Spindles for 45 records	٤I	3	3
Connoisseur Pick-up with 2 heads	£9	5	6
Decca Pick-up with 2 XMS Heads	£6	9	5
Acos GP20/Hi-G with 2 heads		10	7
Speakers : Goodmans Axiom 150	€10	5	6
			ŏ
Goodmans Axiom 22. Mk II		0	6
		7	0
W.B.HF912 9in. Unit 3 ohm		13	6
W.B.HF1012 10in. Unit 3/15 ohm		13	3
Wharfedale Super 5CS/AL		13	3
Wharfedale Super 8CS/AL			3
Wharfedale Golden 10in			7
Wharfedale Golden/CSB	£8	6	
Wharfedale W12/CS	£9	15	0
Wharfedale Super 12/CS/AL	£17	10	0
Wharfedale Separators Type "B" 1000 c/s, 7-16 ohm	£3	2	6
Wharfedale Separators Type "D" 1000 c/s. 2-6 ohm	€4	2	6
Wharfedale Separators Type "F" 3000 c/s. 7-16 ohm	£2	8	6
Wharfedale MGI Equaliser	£2	17	6
Wharfedale 3-way & section Crossover	£8	10	0

P.A.I. PRE-AMP CASH PRICE £8.18.6 or DEPOSIT £2.19.6 11 PAYMENTS 11.10

TELE-RADIO (1943) LTD. 189 EDGWARE ROAD, LONDON, W.2. Phone: PAD 4455/6 SHOP HOURS: MON.-SAT, 9 a.m. to 6 p.m.

WIRED AND TESTED CASH PRICE £26,15.6

LIPAYMENTS £1.15.8 KIT FORM CASH PRICE £22.1.0

11 PAYMENTS £1.9.5

£8.18.6

£7.7.0

OF

or DEPOSIT

JUNE, 1954

Several more good reasons why our circle of friends keeps enlarging Air Cooled, Compound Filled and Oil Immersed Transformers for every requirement A.I.D. Authority Ref. No.: 6489/53

WILLESDEN TRANSFORMER CO., LTD.,

2a FRITHVILLE GARDENS, SHEPHERDS BUSH, LONDON, W.12.

Telephone : SHEpherds Bush 5819



We invite your enquiries for the Type A1/1 automatic machine, as illustrated. Also for the Type H/1 hand coil winder and Type AW/1 Armature Winding Head.



73 UXBRIDGE ROAD, EALING, LONDON, W.5 Ealing 8322



cordially invite you to visit our Regent Street showroom to hear

the NEW

Also demonstrated

are the latest versions of quality equipment by ACOUSTICAL, GOODSELL, LEAK and ROGERS as well as the NEW HIGH FIDELITY AMPLI-FIER by ARMSTRONG.

THESE EQUIPMENTS CAN BE HEARD WITH A WIDE RANGE OF HIGH QUALITY LOUD-SPEAKER SYSTEMS AND ASSOCIATED EQUIPMENT.

B. K. PARTNERS

229 Regent St., London, W.I. (Entrance Hanover St.) 'Phone REG 1051 & 7363



unit)

CR.500 (complete with multi-stage high gain control

£30.10.0

ultra linear version with an even wider range control unit

£36.10.0 + H.P. TERMS AVAILABLE

This and other high fidelity equipment is demonstrated at our showrooms Daily 10.30 a.m.—5.30 p.m. Saturdays 10.30 a.m.—12.30 p.m.

LTD.

For the accurate distribution of high frequency sounds to ensure maximum fidelity over a wide area there is no satisfactory alternative to the multi-cellular horn and pressure unit. The Vitavox range includes two series of horns with lower cut-off frequencies of 550 and 220 c.p.s. respectively, available in a number of cell combinations to suit particular installations. Two types of pressure unit are supplied, one for general purpose applications and the other for installations calling for the highest possible quality of reproduction. Full details will be supplied on request.

VITAVOX multicell horns and pressure units

VITAVOX LIMITED, Westmoreland Road, London, N.W.9. Telephone : COLindale 8671

The NEW V.200 is now in production!

This exceptionally sensitive Wide-Band, Stabilised A.C. Valve Voltmeter/Amplifier is essential in every well-equipped electronic laboratory and is a pleasure to use.

V.200-Abbreviated Specification. Input Impedance up to 10 meg-100 microvolts to 1000 volts 10 cycles to 10 megacycles Accuracy to 6 M.c/s = \pm 5% protection, LINEAR 65dB of the actual reading.

ohms and 10 p.F.

No ZERO instability-Overload Amplifier.

Delivery: 1-2 months Price Ex Works £112.10.0

FOR

Valve Voltmeters, Oscilloscopes, Frequency Sources, Stabilised A.C. and D.C. Power Supplies, Attenuators,

WRITE TO

hill Laboratories 1

SHENLEY ROAD BOREHAM WOOD HERTS. Cables: FURZLAB, LONDON.


Tel: ELStree 3940.

Jurzehill .



PORTABLE RECORDERS In rexine covered case, fitted with model 5B tape desk, type D.2. C.J.R. amplifier with monitoring. Provision for external loudspeaker.

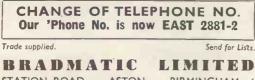speaker. PRICE: £117 (without microphone) High-fidelity sound heads. Type 5RP (Record/play), £3/5/-. Type 6RP (super fidelity), £3/15/-. Type 5E (Erase), £3/5/-. Mumetal Screening cans, 8/6. Amplifiers, microphones. All types and sizes of magnetic tane.



STATION ROAD . ASTON . BIRMINGHAM 6 Grams : Bradmatic, Birmingham

VIEWMASTER"

AS SHOWN

Beautifully designed and finished in Walnut, Oak, Mahogany and Teak, to customers' requirements

Standard "VIEWMASTER " model as shown £13.0.0 Carriage and Packing 15/- extra

Fitted with shelf for easy mounting. These are NOT mass produced and dimensions can be altered to suit personal requirements. Individual and Trade Enquiries to



LONGEST SCALE - SMALLEST SPACE



This compact, robust D.C. Milliameter is flush mounting and is ideal for use in restricted space.

> SCALE LENGTH : 9" RANGE FROM 0-500 μA

The meter with the dead beat movement

The meter measures only 5" across and the depth behind the panel is only 2" yet it retains a scale length of 9". It is available with spade or knife-edge pointer and special scales can be supplied to customers' specification if required. Send for prices and full details. BRITISH PHYSICALRD ABORATORIES Radlett, Herts Tel : Radlett 5674/5/6 LONDON STOCKIST: M. R. SUPPLIES LTD., 68 NEW OXFORD STREET, LONDON, W.C.I am BP.19 Connoisseur with DIAMOND STYLUS! The SUPER LIGHTWEIGHT PICK-UP can now be supplied to orderwith an armature system fitted with diamond stylus. with an armature system fitted with guamond stylus. Price complete with one head (either Standard 78 r.p.m., or Microgrove, 33¹/₃ and 45 r.p.m.) fitted with diamond stylus £7.12.9d. plus Purchase Tax £2.9.0d. Each additional head £5.12.9d. plus Purchase Tax £1.16.2d. Replacement armature system fitted with diamond stylus £3.13.0d. plus Purchase Tax £1.3.5d. 3 HEAD PICK-UP Existing model with sapphire system still available. **3 SPEED MOTOR** New price: Retail Price .. £17 15 '0 Purchase tax... 5 13 11 Total price .. £23 8 11 3 SPEED MOTOR A. R. SUGDEN & (ENGINEERS) LTD. CU. Tel : HALIFAX 69159 Facsimile in Sound WELL GREEN LANE, BRIGHOUSE, YORKSHIRE Telegrams : " Connoiseur, Brighouse" OVERSEAS AGENTS: S. Africa: W. L. Procter (Pty.) Ltd., 63 Strand Street, Cape Town. Australia: J. H. Magrath & Co. Pty. Ltd. 208 Little Lonsdale Street, Melbourne. Canada: The Astral Electric Co. Ltd., 44 Danforth Road, Toronto 13, Ontario. New Zealand: Turnbull & Jones Ltd., Head Office, 12/14 Courtenay Place, Wellington. Hong Kong: The Radio People Ltd., 31 Nathan Road, Hong Kong. Malaya: (Main Dis-tributors) Eastland Trading Co., 1 Prince Street, Singapore.

JUNE, 1954



Evolution

WHARFEDALE WIO/CSB IO" LOUDSPEAKER

First introduced in 1938, this 10in. speaker has been improved in stages and now embodies the following details of good design :

Flux density 14,000 lines. Total flux 74,000 lines. Rigid, open, die-cast chassis.

Cone with bakelised apex and special radial corrugations.

Centring device in bakelised fabric.


Aluminium dome.

Cloth suspension, which involves hand-assembly by experts who have attained a world-wide reputation.

Bass resonance now 45 c/s.

Any speaker maker could produce a loudspeaker including some or all of these specifications. Only WHARFEDALE can produce one which sounds like the W10/CSB.

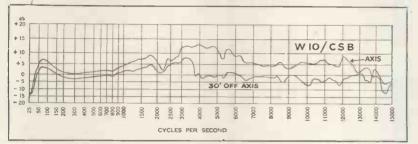After the Super 12/CS/AL—which costs £17 10s. 0d. the W10/CSB is the best single speaker in the Wharfedale range. At £9. 5s. 0d. plus £3. 1s. 6d. P.T. the performance is outstandingly good; some idea of the frequency range if given by the response curve.





32-page catalogue free on request

Whartedale Wireless Works Ltd., BRADFORD ROAD · IDLE · BRADFORD · YORKS Telephone: Idle 1235/6 Grams: Whartdel, Idle, Bradford

The J.E. Tape-Recorder


LIGHT IN WEIGHT - SMALL IN SIZE - LONG RECORDING TIME IT CAN BE USED BOTH VERTICALLY AND HORIZONTALLY

In spite of its exceptionally light weight and convenient shape which makes it truly portable, this recorder is of robust construction and it is fully guaranteed for 12 months. Single switch operates both the mechanism and the amplifier. This feature combined with automatic "Servo" type brakes makes its operation foolproof, and accidental Tape-spilling or tearing a virtual impossibility.

PRICE

39 GNS.

70

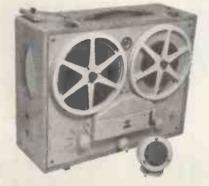

Immediate Delivery We welcome callers at our showroom

I DI DI DOMINI KIDANI (DAS

BREWER STREET, LONDON, W.1.

Tel.: GER. 3376.

Size: $15\frac{3}{8} \times 12 \times 71n$. with Ild. Weight: 25lb. Two speeds by simple switching ($1\frac{1}{2}$ and 3 hrs. Recording Time). Fast Rewind and Forward Speeds. 4.5 Watts output of excellent quality. Provision for monitoring and extension Speaker. Negligible hum, wow and flutter. Exceptionally sensitive, high-class Microphone. Beautifully finished cabinet covered with washable Rexine.

> IN KIT FORM 33 GNS.

> > Open all day

Saturday

CO.

F	OR F	URTHER
1	NFOR	MATION
	please	e send
sta	mped	addressed
	enve	lope.



Valuable Wireless World books

Radio Data Charts

43 Abacs for Receiver, Design Calculations 5th Edition. By R. T. Beatty, M.A., B.E., D.SC., revised by J. McG. Sowerby, B.A., A.M.I.E.E. The problems encountered in radio and electronics are so diverse and numerous that it would hardly be feasible to have an abac for every one. This collection is therefore intended to cover only the most frequently recurring problems, the answers to which provide most of the data needed for the design of radio receivers. In this new edition the reactance charts have been redrawn and the two charts previously included for resistance calculations have now been combined in a single chart.

11in. deep x 81in. 91 pp. 7s. 6d. net. By post 8s.

Television Receiver Model II

Complete constructional details with notes on modernizing the original design. Collected articles reprinted from "Wireless World," describing a complete receiver, using a superheterodyne circuit, which provides a modern standard of performance and is suitable for home construction.

101in. x 71in. 40 pp. 3s. 6d. net. By post 3s. 9d.

Television Receiving Equipment

By W. T. Cocking, M.I.E.E. 3rd Edition. Explains the fundamental principles involved and then describes each stage of the normal television receiver. The text includes notes on special circuits and gives practical details of receiver design. Other chapters are devoted to faults and their remedies, servicing of modern sets and the problems of obtaining selectivity. Mathematical data of particular value to the designer have been collated and appear in appendices. 18s. net. By post 18s. 8d.

F.M. Feeder Unit

S. W. Amos, B.SC. (HONS.), A.M.I.E.E. and G. G. Johnstone, B.SC. (HONS.) A reprint of articles from "Wireless World" describing a simple and inexpensive three-valve adaptor designed to cover the v.h.f. broadcast band 87.5-100 Mc/s, and in particular to receive the B.B.C. frequency-modulated transmissions on 91.4 Mc/s from Wrotham. The unit can be used in conjunction with an audio amplifier or a normal receiver. 104in. x 74in. 16 pp. 2s. 0d. net. By post 2s. 2d.

Obtainable from booksellers or direct from : ILIFFE & SONS LIMITED, DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1






RM POWER RESISTORS

Coated with a non-hygroscopic and fireproof silicone bonded compound. Internal connections made by special method of welding, giving long-term stability under all conditions.

Standard range is shown but we shall be pleased to advise on special types to suit particular requirements.

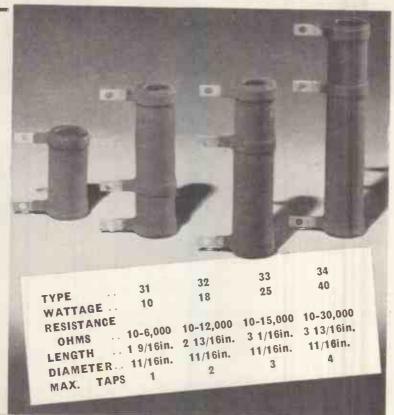R. M. ELECTRIC LTD. TEAM VALLEY, GATESHEAD, II







"UNITELEX PRIMA" PORTABLE TAPE RECORDER: We are appointed stockists for this recorder. Features include ultra modern cabinet design, giving exceptional lightness and portability without sacrifice of quality. Pushbutton control on mechanical side, twin-track heads, dual-speed (7½ in. and 3½ in. per sec.), giving up to two hours playing on one reel of tape; latest type miniature valves used; genuine 10 kcs. response; separate bass and treble controls; magic eye recording level indicator; provision for use as straight playback amplifier from record players or changers; 4-watts output to internal 10in. elliptical high-flux speakers, with provision for feeding two extenal speakers or amplifiers. Price, complete with filter cell microphone housed in recorder, and with 1,200(f. reel of high coercivity tape, 57 guineas. H.P. terms 19 gns. deposit, 12 monthly payments of £3/13/2. Send 2½ d. stamp for illustrated brochure.

GARLAND AMPLIFIER ACII. Self-contained general-purpose amplifier, providing 3.5-watts output. All power supplies derived from mains transformer, ensuring isolated chassis. Standard valves throughout. Volume and Tone Controls incorporated. Negative feedback loop. Price £6/12/6 plus 5/- carriage, etc. Weight 10lb.

tal/12/o plus 5/- carriage, etc. vreight 1010. TRUYOX TAPE DECK MARK III. Incorporating high impedance mu-metal twintrack heads. Two-speed capstan, for tape speeds of 74 and 34 inches per second. Three-heavyduty motors allowing for fast forward and rewind facilities without tape handling. All controls, operated by electrically and mechanically interlocked push buttons. Price £23/2/-. Send S.A.E. for full particulars. Plus 10/- carriage, etc. Delivery from stock. Send 24d, stamp for details of this and of suitable amplifier.

ARTICLE	Ca Pri			De	po	slt		6 onti me	hly ents		12 ont	
Goodmans Axiom 101. 8in. L/Spkr	£6 I	2	I.	£2	4	F		15	9		8	1
Garland Amplifier ACLIA	£6	2	6	£2	4	2		15	9		8	11
Wharfedale Golden CBS. 10in. speaker	£8	6	7	£2	15	7	1	19	11		10	2
Goodmans Audiom 60 Speaker	£8 I	2	6	£2	17	6	٤I	0	8		10	7
B.S.R. 3-speed single player. GU4	£9	5	0	£3	1	8	٤I	2	2		н	4
Connoisseur Pick Up, 2 heads	£9	5	6.	£3	1	10	٤I	2	2		Π.	4
Leak Pre-Amplifier	£9	9	0	£3	3	0	£1	2	7		ii.	7
Wharfedale Wl2/cs. 12in.	£9 1	5	0	£3	5	0	£I	3	4		ii.	n I
Goodmans Axiom 150, Mk. II	£10	5	6	£3	8	6	£I	4	7		12	7
Stella 3-speed Single Player	£10 1	0	0	63	10	0		_			12	10
Leak "Varislope" Pre-Amplifier	£12	2	0	€4	4	0	EL	10	2		15	6
Collaro Auto-changer. 3RC/531	£15	3	10	€5	1	4		_			18	8
B.S.R. "Monarch" 3-speed Auto-change	£16 1	0	3		10	1	11	19	6	£I	0	3
Lane Tape Desk, Mk. IV	617 1		0	€5		8		Ϋ́ι	10	εI	ĭ	5
Collaro auto-changer. 3RC/532		0	0	€5		8		<u> </u>		EI	1	4
Connoisseur 3-speed unit		-		ET		4				εI	8	8
Truvox Tape Deck, Mk. III		2	0	£7	14	0	10	15	2	£1	8	3
Leak "Point One " Amplifier		÷,	0		9	0		7	9		-	-
Q.U.A.D. Amplifier with pre-amplifier		0		1	-	4				£I	14	8
Unitelex "Prima" Tape Recorder.	2.35	U	0	£II	13	4	24	3	8	£2	2	9
(Described above).	£59 I	7	0	£19	19	0	€7	3	0	£3	13	2
ALL GOODS NEW AND UNUSED (except where otherwise stated).												

LAND BROS, LTD. CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8.

 9 a.m. -- 6 p.m. Inurs: 9 a.m. -- 1 p.m. Fri. 9 a.m. -- 7 p.m.
 5 OBELISK PARADE, LEWISHAM, S.E.13. TEL.: LEE GREEN 4038

TEL .: TIDE WAY 4412/3

JUNE, 1954



WIRELESS WORLD



37/6

POST 1/-.

The High Quality Portable "ELIZABETHAN" Tape Recorder 2 SP. Recording medium stundard in plastic coated tape. Tape speeds, 7 in. and 5 in. Persecond. Running time, 60 or 90 minutes. Rewind, 60 seconds. Frequency range, 40 cp.s.-10 Ko.at 7 in presecond. Loudspeaker, 81n. Moving Coll. Output, 3 watts. Maine suppir, 200-250 A.C., 50 c.p.s. Maine consumption, 60 watts. Dimensions, tape. Fully guaranteed. The High Quality Portable to a second se

75/- Post 2/-.

than a brush and twice as fast.

Tax

Free

JUNE, 1954







Copy of assembly instructions and components price list available for 1/3.

JUNE, 1954



WIRFLESS WORLD



An Additional Charge of 10/- is made in each case to cover Carriage and Insurance

• Complete with High Fidelity Crystal "TURNOVER" Head which incor-porates a separate stylus for L.P. and Standard Records.

• Will play 7 inch, 10 inch and 12 inch Records. Brand New and Complete with mounting instructions.

Tel.: CENTRAL 5812-3-4

When submitting orders, please include post and packing

EET. E.C.4

The GOLLARO MODEL 3/514 3-Speed Non-Auto Change Unit

109 & 115, FLEET S

.

• ote or assembled CHASBIS LTD. long × Sin. × Sin. Noil Aperture Sin. × 44 n. THE ASSEMBLY MANUAL IS AVAILABLE FOR 2/-, This gives very detailed practical drawings and layouts and lacludes a component price list. THE COMPLETE RECEIVER CAN BE BUILT FOR £10/7/6 with the OCTAL VALVE LINE UP or for £12/7/6 with Minia-ture Valves.

Replacement RADIO-RADIOGRAM CHASSIS


....

• MODEL AW3-5. A 5-Valve Superhe¹ Receiver covering the standard 3 wave-bands, 16-50, 190-550, 900-2,000 metres. PRICE COMPLETELY ASSEMBLED AND READY FOR USE **£10'10'-**

H.P. Terms £3/10/- Deposit and 10 Months at 15/9. This receiver is for operation on A.C. Mains 200-250 volts. It contains the latest MULLARD VALVE LINE UP, being ECH42 (Freq. Ch.), EF41 (I.F.), EBC41 (Det. 1st Audio), EL41 (Output) and EZ41 (Bect.). It incorporates Negative Feedback and delayed A.V.C., the four controls being (1) Tuning, (2) Wavechange and Gram. Switch, (3) TONE, (4) VOLUME-OFF. It provides really good reproduction on both Gram. and Radio and gives an exceptionally good range of station selection. Overall size 134in. x 7in. high x 6in. deep. Dialaperture 10in. x 44in.





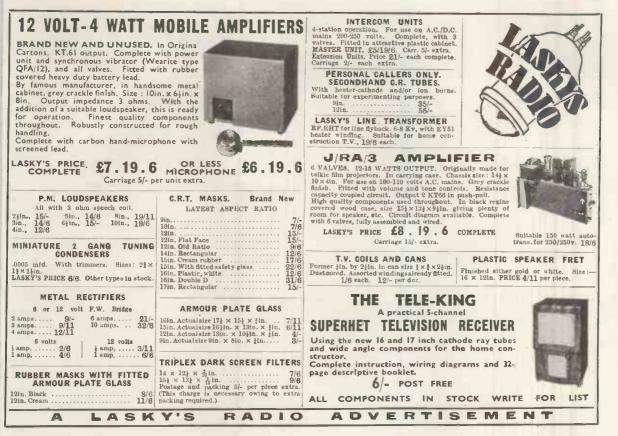



PLEASE NOTE. Carriage and Postal charges refer to the U.K. only. Overseas freight, etc., extra

POWER UNIT TYPE 3 for A.C. mians 50 c/s. **POWER UNIT TYPE 3** for A.C. finants 30 (3). Useful 19in, rack mtg. Power supply: input 200/250 v. A.C.; outputs 200 v. 40 m/a., 6.3 v. 3 a., 4 v. 1.5 a. Complete and fully smoothed, with valve rectifier and meters 0/300 v., 0/150 a. Enclosed chassis, dim. 19 x 7 x 11in. ASK FOR 79/6 acth 79/6 each PAID X/E752 ALSO AVAILABLE P.U. TYPE 3, as above, but less valves and meters. ASK FOR X/E752A. 29/6 each S/- EXTRA
 X/E/52A.
 4-3/9
 each
 5/- EXTRA

 METAL (MINE) DETECTOR No. 5A

 Amplifier Unit with Search Coil Assembly

 ZA22158.

 An A.F. amplifier, employing 3/ARP12's (VP23)

 valve mounted, with battery space in metal case

 I x I x 4½in., plus small metal box fitted with

 controls, which can be fitted to search coil, with

 slight modification (details supplied) and used

 for finding buried metal.

 are 6 "S" type 1½ volt cells, and a 60/90 volts

 H.T. battery (not supplied).

 ASK FOR

 DOLE
 H.T. batte ASK FOR X/E768. CARRIAGE 39/6 each PAID

SPARES KIT FOR AMPLIFIER OF EX-R.N. LOUD HAILER Containing 8 valves, 4/NR77 (EL35), 2/NR73 (ECC31), 2/VR56 (EF36), plus condensers, resis-tors, etc. Electrolytic condenser doubtful due to long storage. In wood box 16 x 124 x 34in, which would make a useful tool or spares box. ASK FOR X/E892 30/- each PACKING 2/6 DINGHY TELESCOPIC MAST

Aluminium telescopes from 14jin, to 7jft. Seven sections, base dia. jin. Wgt. 4 oz. ASK FOR A/G POST 6d. 4/6 each EXTRA X/H489

AERIAL ROD
 ISin. lengths, cooper plates steel tube, ferruled to interlock an aerial of desired length.
 interlock an aerial of desired length.

 dia.
 Ask for X/H709, in. dia.
 Ask for X/H710.

 EITHER
 4/6 lengths
 EXTRA
 RADAR REFLECTOR AERIAL MX/137/A Spider web mesh aerial in original moisture proot carton, with assembly instructions. ASK FOR POST 9d. 4/11 each X/E175 EXTRA MORSE PRACTICE BOARD ONLY Comprises key, buzzer and 'phone terminals on board 6½ x 6½ x ½in., with battery clamps. ASK FOR 5/6 POST 9d 5/6 each X/EIX EXTRA MAINS TRANSFORMER $\begin{array}{c} \label{eq:constraint} \text{MAINS TRANSFORMER} \\ \text{Primary 0.230-250 volts A.C. 50 cycles, Secondary } \\ \text{6.3 volt. 5 amps, 0-210 volts 14mA., 0-460 volts } \\ \text{200 mA. Size 5<math>\frac{1}{2}$ x 5 x 4 $\frac{1}{2}$, or 5 x 4 $\frac{1}{2}$ x 4. ASK FOR ASK FOR POST 1/6 each EXTRA 13/6 each
 CHOKE.
 Ad
 Patt.
 1800, 20H.
 300 m/a.

 Test volts 3,000.
 Wgt.
 141b.
 Dimensions 6½ x
 4½ x 4½in.

 ASK FOR
 E/
 POST 1/6
 1/2
 1/2
 15/- each EXTRA X/H45 HELIOGRAPH. 5 INCHES MK. 5 New condition, comprises I duplex mirror, I signalling mirror, sight and mounting, with signalling attachments and spare mirrors, in pigskin case, with carrying strap. ASK FOR X/H828A 35/- each PAID Order direct from :---

The second

STILL AVAILABLE as detailed previously RIISS RECEIVER UNIT. Reconditioned and tested, used, good condition. In transit case. ASK FOR **62106** CARRIAGE £8.19.6 each X/H916 PAID Also RII55, as above, but loose stored. ASK FOR **\$5.19.6** each 7/6 EXTRA Circuit and data 2/3 THI54B TRANSMITTER UNIT, in transit case **39/6** each 7/6 EXTRA Circuit and data 2/3. ASK FOR X/ESA BC-456 SPEECH MODULATOR UNIT Part of SCR-274-N "Command Equipment" U.S.A., with valves, less dynamotor. In original carton ASK FOR X/E42A POST 27/6 each PAID Also BC-456, as above, but loose stored. ASK FOR X/E42 17/6 each P/ POST PAID Circuit 1/3.
 TRANSMITTER
 TUNING

 stored.
 stored.

 TU7B.
 Range 4,500-6,200 kc/s. ASK FOR X/H29.

 TU8B.
 Range 6,200-7,700 kc/s. ASK FOR X/H470.

 TU9B.
 Range 7,000-10,000 kc/s. ASK FOR X/H470.

 EITHER
 10/- each

 2/- EACH
 TRANSMITTER TUNING UNITS, loose ROTARY CONVERTER TYPE 195 Input 24 volts D.C. Output 230 volts A.C. 100 watts, ASK FOR CARRIAGE £5.19.6 each CARRIAGE X/H914 I.F.F. RECEIVER R3109, ref. 10DB/506. ASK FOR X/H961A 19/6 each PAID SUPPLY UNIT RECTIFIER FOR No. 43 TRANSMITTER Ex. Cdn. army in original wood case. ASK FOR X/H26 **\$25.0.0** ord Phone : South 2706/9. 2, BRIDGE STREET, GLASGOW . C.S SUPPLY CO. LTD. CLYDESDALE

JUNE, 1954

SELENIUM RECTIFIERS L.T. Types H.T. Types H.W. 2/6 v. ½ a.h.w. 1/9 FW. Bridge Types 90 v. 20 mA	R.S.C. TRAP FULLY GUARANTEED, INTER MAINS TRANSFORMERS Primaries 200-230-250 v. 50 c/s.	FILAMENT TRANSFORMERS Primaries 200-250 v, 50 c/s,
6/12 v. 6 a 19/9 CO-AXIAL CABLE. 75 ohms ‡in., 7d. yard.	FULLY SHROUDED UPRIGHT MOUNTING 250-0-250 v. 80 mA., 6.3 v. 2 a., 5 v. 2 a., 16/9 Midget type 2½-3-3in	$\begin{array}{cccccccccccccccccccccccccccccccccccc$
RHEOSTATS (VARIABLE RESISTORS) 2 ohm. 6 amps., 5/9; 0.4 ohms. 25 a., 8/9; 150 ohms. 1.5 amps., 14/9. All complete with control knob.	350-0-350 v. 70 mA., 6.3 v. 2 a., 5 v. 2 a	1.5 a. 17/6 CHARGER TRANSFORMERS All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. 1.5 a., 12/9; 0-9-15 v.
SILVER MIGA CONDENSERS. 5, 10, 15, 20, 25, 30, 35, 50, 100, 120, 150, 180, 200, 330, 300, 400, 470, 500, 1,000 pfd. (.001µF), .002 mfd. (2,000 pfd.). All at 5d. each; 3/9 dozen one type.	300-0-300 v. 100 mA., 6.3 v4 v. 4 a. c.t., 0-4-5 v. 3 a	22/9; 0-9-15-30 v. 3 a., 23/9. ELIMINATOR TRANSFORMERS Primaries 200-250 v. 50 c/s. 120 v. 40 mA 7/11
DIAL BULBS, M.E.S, 8 v. 0.15 a., 6/9 doz. 6.5 v. 0.15 a., 6/9 doz.	350-0 350 v. 150 mÅ., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a. 33/9 350-0.350 v. 160 mÅ., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a. 45/9	120 v. 40 mA. 5-0-5 v. 1 a 14/9
$\begin{array}{c c c c c c c c c c c c c c c c c c c $	350-0-350 v. 250 mA, 6.3 v. 6 a, 4 v. 8 a, 0-2-6 v. 2 a, 4 v. 3 a, for Electronic Eng. Televisor 67/6 425-0-425 v. 200 mA, 6.3 v. 4 v. 4 a, c.t., 6.3-4 v. 4 a, c.t., 6.3-4 v. 4 a, c.t., 0-4.5 v. 3 a, suitable Williamson Amplifier, etc. 67/6 425-0-425 v. 250 mA, 6.3 v. 6 a, 6.3 v. 6 a, 5 v. 3 a. 63/6 5 v. 70 mA, 6.3 v. 2 a, 5 v. 6 a, 5 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a. 12/11 250-0-250 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a. 14/11 350-0-350 v. 80 mA, 6.3 v. 2 a, 5 v. 2 a. 16/9 350-0-350 v. 80 mA, 6.3 v. 2 a, 5 v. 2 a. 16/9	$\begin{array}{c} \textbf{OUTPUT TRANSFORMERS} \\ \textbf{Midget Battery Pentode 66: 1 for 354, etc. 3/6} \\ \textbf{Small Pentode } 5,000\Omega \ to 3\Omega \ 4/9 \\ \textbf{Standard Pentode } 6,000\Omega \ to 3\Omega \ 4/9 \\ \textbf{Standard Pentode } 6,000\Omega \ to 3\Omega \ 4/9 \\ \textbf{Standard Pentode } 0,0000 \ ohms \ to 3 \ ohms \\ \textbf{Multi-ratio 40 mA. 30: 1, 45: 1, 60: 1, } \\ 90: 1, \ Class B Push-Pull \ 5/6 \\ Push-Pull 8 \ Watts 6V6 \ to 3 \ ohms \ 8/9 \\ Push-Pull 10-12 \ Watts \ to match 6V6 \ to \\ 3-5-8 \ or 15\Omega \ 15/9 \\ Push-Pull 20 \ Watts \ high-quality sectionally \\ wound, \ 6L6, \ KT66, \ etc., \ to 3 \ or 15\Omega \ 47/9 \\ \end{array}$
$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	SMOOTHING CHOKES 250 mA., 7-10 H. 200 ohms Shrouded 16/9 250 mA., 3 H. 50 ohms 11/9 100 mA., 5 H. 350 ohms 7/6 80 mA., 10 H. 350 ohms 5/6
MISCELLANEOUS EX-GOVT. ITEMS Slydelock Fuses, 15 amp., 1/9. Bulgin octal type moulded Bakelite, 5-pin or 7-pin Plugs and Sockets, 1/11 pair. Earphones (Single), low resistance, 1/3.	E.H.T. TRANSFORMERS. 2,500 v. 5 mA., 2-0-2 v., 1.1 a., 2-0-2 v. 1.1 a., for vCR97, VCR517 or ACR2X 36/6 5,000 v. 5 mA. 2 v. 2 a. 39/6 39/6	60 mA., 10 H. 400 ohms 4/11 50 mA., 40 H. 1,000 ohms Potted 10/9 MICROPHONE TRANSFORMERS 100 : 1
all values less switch, 2/9; with S.P., switch, 3/9. WIRE WOUND POTS: 30 ohms, 500 ohms, 1,000 ohms, 5K, 20K, 50K (med- ium length spindles), 2/9. 220 ohms, 2K, 10K, 20K, 50K Preset type, 1/9 ea. AMMETERS. Moving coil. G.E.C. 0-5 amps., 2in. scale, 11/9.	Size approximately 12in. x 64in. x 5in. Bakelite	All 230 v. 50 c/s input. 250-0-250 v. 40 mA., 6.3 v. 2 a., 5 v 2 a
EX-GOVT. E.H.T. SMOOTHING CONDENSERS 0.02 mid. 5,000 v. Bakelite Tubulars 1/6 0.2 mid. 5,000 v. Bakelite Tubulars 1/6 1.25 mid. 4,000 v. Blocks 4/9 2.5 mid. 3,500 v. Cans 3/3 1 mid. 9,000 v. Blocks 9/6 (common negative isolated) 9.76 9.76 1.5 mid. 4,000 v. blocks 5/9 EX-GOVT. ACCUMULATORS with non-spill vents. or 3 in wood carrying case 9-7-5in., 14/9, plus 2/6 Carr. EX-GOVT. BLOCK PAPER CONDENSERS 4mid. 500 v 2/9 10 mid. 1500, v.	type available in Brown or Cream. Price of Cabinets, 17/8 ca., carr. 2/6. Suitable fully punched T.R.F. 3-valve and rectifier chassis. yitable fully punched T.R.F. 3-valve and rectifier chassis. Year and rect. Jial Scales, 2 colour, 2 waveband, station named, glass named, glass. 1/6 Dial Scales, 3 colour, 3 waveband, station named, glass 1/9 Suitable coloured Metal Backplates 1/3 Pointers, Double ended 47.R.F. Coils, 2 wavebands with circuit. 6/9 Drum Drives, complete 2/6	1220 v. 350 mA. 29/9 EX-GOVT. \$MOOTHING CHOKES 250 mA. 10 H. 50 ohms. 14/9 250 mA. 10 H. 50 ohms. 14/9 14/9 250 mA. 10 H. 50 ohms. 14/9 150 mA. 10 H. 50 ohms. 14/9 150 mA. 10 H. 100 ohms. 10/11 100 mA. 10 H. 100 ohms. Tropicalised 6/9 100 mA. 5 H. 100 ohms. Tropicalised 3/11 90/100 mA. 10 H. 100 ohms. Potted 8/9 50 mA. 5 H. 100 ohms. Potted 8/9
4 mfd, 1500 v. 4/9 11-7 mfd, 500 v. 8/9 4 mfd, 400 v. plus 2 mfd, 250 v., 1/11. EX-GOVT. TRANSMITTER-RECEIVER TYPE TR9D, complete with all valves, only 47/9, plus carr. 5/	THE SKY CHIEF T.R.F. RECEIVER A design of a 4-stage, 3 valve 200-250 v. A.C. Mains receiver with sclenium rectifier. For inclusion in any of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage	EX-GOVT. T.V. TYPE TRANSFORMERS. All 230 v. 50 c/s input. 1100-0-1100 v. 250 mA. 25/- 25/- 2800 v. 30 mA. 22/9 22/9 22/9 400 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 06 a., 4 v. 3 a., 5 v. 2 a. 22/9
EX-GOVT. AUTO TRANSFORMERS 50 c/s. Double Wound 10-0-200-220-240 v to 10-0-270-200-310 v. 200 watts	followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point to point wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of \$4/16/- including cabinet. P.M. SPEAKERS. All 2-3 ohms. 3½in. Goodmans	$\begin{array}{c} \textbf{CHASSIS} \\ 18 \ {\rm s.w.g. undrilled alu-16 \ {\rm s.w.g. aluminium, reminium amplifier type ceiver type.} \\ (4-sided) \\ 12in. \times 9in. \times 2\frac{1}{2}in6/11 \ 12in. \times 8in. \times 2\frac{1}{2}in5/3 \\ 14in. \times 10in. \times 3in7/11 \ 20in. \times 8in. \times 2\frac{1}{2}in8/11 \\ 16in. \times 10in. \times 3in8/3 \end{array}$
M.E. SPEAKERS. All 2-3 ohms, 61/in. Rola- field 700 ohms, 11/9. 10in R.A. field 600 ohms,	F.M. SPEAKENS, All 2-3 ohms. 3410. Goodmans (Ex New Units), 10/9 5in. Goodmans, 15/6. 64jin. Goodmans, 16/9. 8in. Plessey, 15/9. 8in. R.A. Heavy duty, 18/9. 10in. Rola, 27/9. 10in. Plessey, 18/6. 10in. Rola with Trans 29/6. 12in. Truvox, 49/9.	$\begin{array}{llllllllllllllllllllllllllllllllllll$

R.S.C. 25 WATT "PUSH PULL" AMPLIFIER

Now firmly established and proving extremely popular, our AII Quality Amplifier we consider to be the best value in amplifiers offered to-day. The volume of its high fidelity reproduction is completely controllable, from the sound of a quiet intimate conversation to the full glorious volume of a great orchestra. Its sensitivity is so high that in areas of fair signal strength it can be operated straight from a crystal receiver. Entirely suitable for standard or long playing records in small homes or in large auditoriums. For electronic organ or guitar or for garden parties or dance bands.

The kit is complete to the last detail, and includes easy to follow point-to-point wiring diagrams.

Twin volume controls with twin input sockets allow SIMUL-TANEOUS INPUTS for BOTH MICROPHONE and GRAM, or TAPE and RADIO. SEPARATE BASS and TREBLE CONTROLS giving both LIFT and CUT. FOUR NEGATIVE FEEDBACK LOOPS with 15 db in the main loop from output transformer to voltage amplifier. Frequency response \pm 3 db 50-20,000 c.p.s. Hum and distortion LESS THAN 0.5 per cent. measured at 10 watts. This is comparable with some of the highest priced amplifiers. Six B.V.A. valves, Marconi-Osram KT series output valves. A.C. only, 200-230-250 v. 50 c/s. input. 420 v. H.T. LINE. Paper reservoir condenser. Compact chassis. Matched components. OVERALL SIZE $12 \times 10 \times 9in$. approx. Output impedances for 3 and 15 ohms speakers.

W.B. "STENTORIAN" High fidelity P.M. Speaker, HF1012, 10 watts. 15 ohm (or 3 ohm) speech coil. Where a really good quality speaker at a low price is required we highly recommend this unit with an amazing performance. \$3/13/6.

CONNOISSEUR HIGH FIDELITY LIGHTWEIGHT MAGNETIC PICK-UP, COMPLETE WITH MATCH-ING TRANSFORMER. A fortunate purchase enables us to offer limited supplies. Brand New Boxed and Perfect at a fraction of normal price. Buy Now at only 26/6.



COLLARO 3-SPEED AUTOMATIC RECORD CHANGERS (brand new), type RC3521, complete with 2 plug-in Crystal P.U. heads for long playing or standard records 7, 10 or 12 in. Not intermixed. Mains input 200-250 v. Limited number available at only £9/19/8, plus carr. 5/~.

COLLARO TAPE DESK MOTORS. Shaded pole type. Clockwise or anti-clockwise. Mains input 110-200-250 v., 31/6.

R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu-lator at 2 amps., 25/8. To charge 6 v. or 12 v. battery at 2 a., 31/6. To charge 6 v. or 12 v. battery at 4 a. 49/8 To charge 6 v. or 12 v. battery at 4 a., 49/8. ABOVE KITS CONSIST OF BLACK CRACKLE LO UVRED STEEL CONFER, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDENS AND CIRCUIT. Any type assembled and tested for 6/9 extra.

ror mams input 200-250 v. 50 c/s. Complete kit of parts including point-to-point wiring diagrams and instructions. Amplifier can be used with any type of feeder unit or pick-up. Output is for 2-3 ohm speaker. (We can supply a very suitable 10in, unit by Rola at 27/9.) The amplifier can be supplied ready for use for 25/- extra. Full descriptive leaflet 7d.

R.S.C. MASTER INTERCOMM. UNIT, with pro-vision for up to 4 "Listen—Talk Back Units" individually switched. A high gain amplifier enables speech and other sounds emanating from enables speech and other sounds emanating from the rooms containing remote control units to be heard at the master control. The unit is in kit form and point-to-point wiring diagrams are supplied. A walnut veneered wood or Brown Bakelte cabinet is included. Mains Input is 200-250 v. 50 c/s. H.T. line 300 v. CHASSIS IS NOT "ALIVE." Ideal also for use as "Baby Alarm." Sound ampli-facation 4 watts Price only \$5/19/6. "Listen— Talk Back Unit" can be supplied at 30/- each. Full descriptive leaflet 10d. The Master Unit can be supplied assembled and tested for 30/- extra.

tested for 30/- extra



mA. fully smoothed, from normal. 200-250 v. 50 c/s. mains. For 4-valve superhet receivers. Price with circuit, 35/9. Or ready for use, 42/6. Size of unit 51-4-11 in

BATTERY SET CONVERTER KITS. All parts for barrier set converting any type of battery receiver to all mains. A.C. 200-250 v. 50 c/s. Kit will supply fully smoothed H.T. of 120 v. 90 v. or 60 v. at up to 40 mA., and fully smoothed L.T. of 2 v. at 0.4 a. to 1 a. Price complete with circuit and instructions only 48/9. Supplied ready for use for 7/9 extra.





Available in kit form at **9 gns.** Plus the amazingly low price of **9 gns.** carriage 5/-Or ready for use 50/- extra.

R.S.C. 10-watt "Push-Pull" **HIGH-FIDELITY AMPLIFIER A3**



Complete with integral pre-amp. Tone control stage (as AII amplifier), using negative feedback, giving humproof individual bass and treble lift and cut tone control. Six Negative Feedback Loops. Completely negligible hum and distortion. Frequency response ± 3 db. 30-20,000 c.p.s. Two independently controlled inputs. Six B.V.A. valves. A.C. mains 200-230-250 v. input only. Outputs for 3 or 15 ohm speakers. Kit of parts complete in every detail, \$7/19/6, plus 5/- carriage, or ready for use, 45/-extra. Descriptive leaflet 1/-.

extra. Descriptive leaflet 1/-. FOUR STAGE RADIO FEEDER UNIT. Design of a HIGH FIDELITY. L. and M. wave T.R.F. Unit with self-contained heater supply and thorough H.T. decoupling. Only 250-400 v. 15-20 mA. H.T. required from main amplifier. Three valves and Low Distortion Germanium Diode Detector. Flat topped response char-acteristic. Loaded H.F. coils. Two variable Mu controlled H.F stages, 3 gang condenser tuning Cathode follower output stage Switch position for Gram. and Gram, input and output sockets Performance comparable with the best in Feeder Units. For A.C. mains 200-230-250 v. operation. Size 11.6-74 in. Illustration, full set of easy-to-follow wiring diagrams and instructions and in-dividually priced parts list 2/8. This unit can be built for only £3/15/-, including Dial and Drive Knobs and every item required.


R.S.C. TONE CONTROL-PRE-AMP. UNIT. A complete set of parts for the construction of a very efficient but simple pre-amplifier and tone control unit. For use with any amplifier and pick-up. Fil. supply self-contained. Size 71-5-53 in. approx. Descriptive leaflet 9d. Price. inc. wiring diagrams, 37/6. Ready for use, 15/- extra.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT with case, Mains input 200-250 v. Output 120 v 40 mA. and 2 v. j a. Price with circuit 29/6. Or in working order, 37/6.





JUNE, 1954

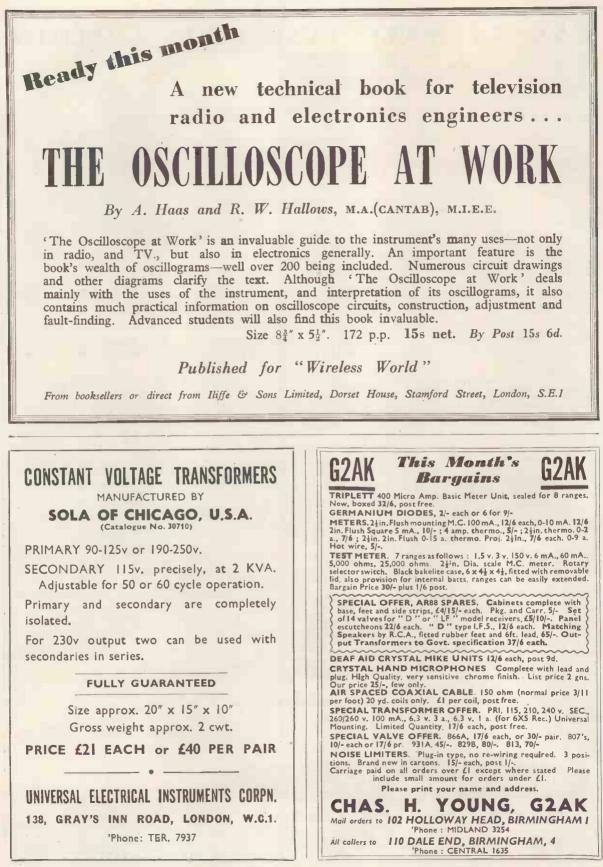



WIRELESS WORLD

For Quality Bargains Always -Best Buy at Britain's

ANOTHER SUPER SNIP!

E.M.I. OUTPUT METER

Just arrived this month a very useful output meter. The instrument itself has a basic movement of I mA and incorporates a full-wave instrument rectifier. There are two ranges 0-500 milliwatts and 0-5 watts and also a decibel scale. The input impedance is 5,000 ohms. These are all BRAND NEW AND UNUSED in sealed Individual Manufacturers cartons, complete with instructions and are offered at about a third of list price. Only 35/- each plus 1/6 post.



E.M.I. OUTPUT METER

VALVE VOLTMETER NO. 2. This well known laboratory instrument operates direct from A.C. mains 200/250 volts 50 cps, and is housed in a grey metal case size ISin. x 7in. x 9in, high and incorporates a 34in. moving coil 200 microamp movement. There are 5 ranges : 0-15, 0-5, 0-15, 0-50, and 0-150 volts A.C. and D.C. measurements may be made up to 300 volts. The input impedance and accuracy are of a very high order. A removable probe is provided for measurements at high frequency. THESE INSTRU-MENTS ARE BRAND NEW, COMPLETE WITH ALL VALVES IN ORIGINAL TRANSIT CASES AND ARE TESTED PRIOR TO DESPATCH. PRICE 415 plus 7/6 carriage. For fuller details and illustration see previous issue. Note: The "x10 multiplier" is still available and is supplied at no extra charge. charge.


GRAYSHAW RESISTANCE CAPACITY BRIDGES. We have pleasure in announcing that we have been appointed London stocklsts for these fine instruments, We can thoroughly recommend these as being superlative value comparing well with far more expensive equipment.

Superative value comparing well with a more expensive equipment. BATTERY SUPERHET. This 4 value receiver 1s contained in a next wooden case size $10\frac{1}{2}$ in. x $7\frac{1}{2}$ in. with built in 5in, speaker. Frequency coverage 1.4 to 4 Mc/s (75 to 215 metres) very useful for trawler bands etc. Supplied ready working with self-contained battery and all values . . . just connect aerial and earth and switch on. Price 79/6 plus 5/6 carriage.

COMMUNICATIONS RECEIVERS. We have a limited quantity of Hallicrafter receivers in stock including the famous SX28 for callers only. The well-known RI155 receivers are still available including Model "N" and those requiring details for the full range of receivers and power packs should send S.A.E. or send 1/3 for Circuit and full details.

should send S.A.E. or send 1/3 for circuit and full details. **TYPE 12 TRANSMITTER.** Mains operated transmitter covering 1.2 to 17.5 Mc/s in four bands crystal or V.F.O. Size 24in. x 12 \pm 1n. x 17 \pm in, weight 134 Ibs. Complete with all valves, ready for operation. In first class con-dition and tested before despatch, with circuit and instructions ONLY £16/16/- plus 14/- carr. We have a few other types of transmitters at bargain prices for callers only.

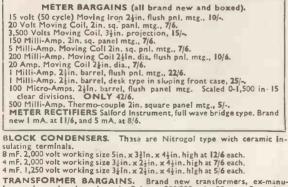UNIVERSAL AVO METERS, MODEL 40. Once more we are able to offer a further supply of these—very little used, thoroughly checked and tested. First class multi-range test meter for ONLY £9/19/6.



TRANSFORMER BARGAINS. Brand new transformers, ex-manu-facturer's surplus, drop through. Primary 200/250 volt, 50 cps. Secondary 310-0-310 v. 70 mA., 6.3, 3 amps 4 v. 2 amps-can be used with 4 volt or 6.3 volt rectifier. Only 9/6 blus 1/6 post. A similar type transformer 325-0-325 100 mA. 6.3 4 amps etg. can be supplied to callers only at 14/6. Filament transformers standard tapped primary-two types, Type "A" 12 volts 1 j amps. 6.3 volts 1 j amps. Type "B" 12 volts 1 j amps., 4 volts 1 j amps. Either type 7/6 cach.



I KW TELEGRAPH TRANSMITTERS. Two HF 300's output. Operation 3.5 mc. to 16 mc.

BC610 TRANSMITTERS with speech amplifier, aerial tuning unit, etc. Brand new.

RCA TRANSMITTERS. Type ET-4336. Complete with original speech amplifier, crystal multiplier and VFO units. Unused and re-conditioned. Can be supplied with very large quantity of spares.

RCA TRANSMITTERS. Type ET-4332 modified by R.A.F. for use on crystal or master oscillator. Complete with speech amplifier.

MAGENTO IN LINE U.C. TELEPHONE SWITCH-BOARDS (complete)

SCR510's, complete with Power Pack and telescopic aerial.

SCR536 (BC611) in excellent condition.

A.R.88D's, A.R. 88LF's, A.R.77's, S27's, HRO, R.109 and others


METAL RECTIFIERS, Type IB, D.C. output 10 amps at 22v-input 220/250v., 50 c/s.

All above items in excellent working condition. Working demonstration upon request.

SPARES A large selection available for SCR399 (BC610), ET4336, SCR610, EE8 Telephones, and Teleprinters type 7B.

TX VALVES 805, 807, 813, 861, 866A, 100TH, 250TH, and many others.

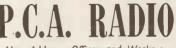Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken.



New Address, Offices and Works :

BEAVOR LANE, HAMMERSMITH, LONDON, W.6 Telephone : RIV 8006

of **KINGST** OOPS



The only "walk-around" radio shop in Surrey

A large and varied stock of Radio Valves, Components, Receivers, Transmitters, Test Equipment, etc.,

> always available at competitive prices. PAY US A VISIT!

PROOPS BROS. LTD. 39, Cambridge Road, Kingston-on-Thames, Surrey Tel. : KINgston 4614 CLOSED-I O'CLOCK WEDNESDAY. OPEN-ALL DAY SATURDAY Correspondence to : 117, Charlotte Street, London, W.I.



The unit is for operation on A.C. mains 200/250 volts

only. Supplied complete £21 · ECD - CD

and ready for immediate use.

plus 17/6 packing, carriage and insurance.

THE UNITS CAN BE SUPPLIED SEPARATELY AS FOLLOWS .-

Cabinet and Gram plus 15/- fracking, and insurance.	together carriage	£16 .	0.	0	
---	----------------------	-------	----	---	--

A LIMITED QUANTITY ONLY OF THESE UNITS IS AVAILABLE.

MAINS NOISE SUPPRESSOR KIT

Consisting of 2 specially designed chokes and 3 condensers. Can be Extremely effective, cuts out all mains noise. assembled in existing receiver or separately as desired. Complete with circuit diagram, 4/3, plus 1/- P.C.



4-watt Amplifier plus 3/6 £5.10.0 packing, carriage and ins. **25** 6in. Elac Speaker plus 1/6 packing, carriage and insurance. 17/6

ELECTROLYTIC CONDENSERS


BRAND NEW

8 mfd. 500 volt. Aluminium Can. Height 2½in.×1§in. dia. Price 1/2 each, 12/- per doz., 140/- per gross. Height S VALVE SUPERHET CHASSIS



Fitted with valve holders, serial, earth and gram. socket. full vision 3 waveband dial and drive assembly, 2-gang tuning condenser. Chassis dimensions: 13jin. long, 5jin. wide, 2jin. deep.

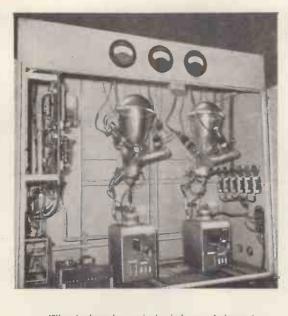: 9/4 Plus 1/6 Pkg., Carr. & Ins. AS A SPECIAL OFFER WE CAN SUPPLY BOTH THE ABOVE, IF PURCHASED TOGETHER, FOR £5.5.0 Plus 7/6 Carr. & Ins.



Where loads, such as toxic chemicals or explosives, call for precision handling, or where the point of life is masked from the operator, radio-controlled equipment is frequently used. Above is a varionic grid controlled rectifier cubicle and electric supply to the motors, driving conveyors at Messrs. Tate and Lyle's new bulk sugar handling plant, Plaistow Wharf Refinery.

POST THIS FORM TODAY

FOR EVERY INDUSTRY large-scale or small

Production executives find MECHANICAL HANDLING an invaluable source of information on the use of mechanical systems. Articles and illustrations show in detail how industrial plants, and comparatively small industries, have used various applications of the latest mechanical handling methods to step up production and reduce human fatigue.

MECHANICAL HANDLING is the only British journal devoted entirely to the subject of mechanical aids to productivity. It caters for every type of industry, describing methods which may well be applied to your business, resulting in an increase of output—without adding to working costs.

Read MECHANICAL HANDLING every month and be fully informed. Post this coupon to obtain the current issue.

то Ψ.Ψ.5.
DORSET HOUSE · STAMFORD STREET · LONDON S.E.I
Please enter my name as a subscriber for the next 12 issues. I enclose remittance value £1 15s. (U.S.A. \$5.50, Canada \$5.00.) Remittances from overseas should be made by money order or bank draft in sterling on London out of a registered account.
Name
Address
Date



MCELROY-ADAMS MFG. GROUP LTD.

Sole concessionaires U.K. for Hallicrafter Communication Equipment

46, GREYHOUND ROAD, LONDON, W.6 Cables : Hallicraft, London Phone : Fulham 1138/9 HAVE YOU A TYPE 18, 21 OR 22 TRANS./RECEIVER ? if so buy these brand-new and boxed ARP12 Valves at 4 for £1, or 5/6 each-while they lat.
TYPE 6C OSCILLOSCOPE UNIT with VCR 138/ECR35 3; inch tube. Valves—2-EF50, 2-EB34. Conversion circuit to standard scope suppled. Price 58/6.
LABORATORY TEST EQUIPMENT. For aligning and checking trans./Receivers. covering 150 to 234 Mc/s. comprising : Type BC906. Frequency Dip Grid Meter. 145-235 Mc/s.
Type BC906. Frequency Dip Grid Meter. 145-235 Mc/s.
Type BC906. Radio Receiver. 150-234 Mc/s.
Type BC906. Radio Receiver. 150-234 Mc/s.
Type BC906. Strequency Dip Grid Meter. 145-235 Mc/s.
Type BC906. Strequency Dip Grid Meter. 150-234 Mc/s.
Type BC906. Frequency Dip Grid Meter. 160.
Malves. Also checks Aerial Resonance.
VA and F.M. bands. Also checks Aerial Resonance.
VALVES. Lists supplied.
CYLOON S CHANNEL PRE-TUNER. Gives 26 D.B. gain.
Fit one of these to your T.V. for better pictures. 1.F. Output 9.5-14 Mc/s, 15.5-22 Mc/s. With valves. EF80, ECC81, 52/6. Less valves, 15/-.
NEW D100 MICRO-AMP. METERS. Al into. Round flush mounting. Made by Ernest Turners. (3/12/6.
MAINS TRANSFORMERS. Input 200/240 v. Output 350-0-350 of 250-0-250 volt 80 mA., and 4 and 6.3 v. 4 a. and 4 and 5 v. 2 a.
Price 21/6. Input 200/240 v. Output tapped 3, 4, 5, 6, 8, 9, 10, 12, 5, 18, 20, 24, 30 volts, 2 amp., 21/6. Output 17-11-5 volts 5 amp., 21/6, 0 utput 17-11-5 volts 1 amp., 16/6. 6.3 v. 2 a., 8/-. All with one year's guarance.
MEW SELENIUM RECTIFIERS. F.W. 12/6 volt 3... All with one year's guarance.
MC MICROPHONES with matched Trans., 15/6.
TEIS TRANSMITTER SECTION. New and co

Phone : PARK 6026

WIRELESS WORLD



THE R.C. "RAMPLER "ALL-DRY PORTABLE A postcard will bring fully descrip-tive illustrated leafiet, including itemised price list, on our latest winner! Up to the time of going to press, all details had not been finalised, but are now ready! Full constructional data for the assembly of a professional 4-valve superhet "all-dry" Medium and Long Wave Portable. Housed in an attractive cream and grey attache case-type cabinet, measuring Sin, x/in, x6jin. deep, and built around a 5in. P.M. speaker. This set really has every. thing. Duilt-in frame aerial in the lid, high quality, extremely sensitive membly during cabinet, are avail-membly of free. All required com-ponents, including cabinet, are avail-mented ater, and build your receiver in time for your holiday 11

in time for your holiday 11
EX-WD. CATEDDE RAY TUBES. Guarancedfullpettere, VCR97 at 40,-YCR917 at 35,-C We also bave VCR97 with slight cut-off, very suitable for oscilloscope, desting purposes, etc., at 16/6 only. All these tubes are brand new in original packing, and tested before despatch. Please add 2/6 packing and carriage for any of the above tubes.
R.F. UNITS. All new condition and complete. Case slice 9/11, X/91, X/

F.S.D. 50 microamp 250 microam 500 500 mA. mA. mA. mA.

10 mA

10 mA. 15 mA

20 mA. 50 mA.

50 mA. 150 mA. 200 mA. 500 mA. 500 mA. 0.5 amp. 1 amp. 3 amp. 5 amp.

6 amp. 20 amp. 50-0-50 amp 10 volt 15 volt 15-0-15 volt

150 volt 300 vol

R.P. Sq. - Flu

RF20, not new, not in perfector. Variable JS/-, Type 27-04+55 M(s), 45/-, Variable Tuning. We have a limited supply of RF27 new condition and complete, but tuning dial damaged. Frice 30/- each only. ALL these units Post Free 1!

LATEST PLESSEY 3-SPEED AUTO-CHANGER. We have just purchased a very limited quantity only of these small A.O. Mixer changers. Require only fin. above and 2jin. below motor board. Complete with turnover crystal head, 29/19/6 only, tax paid.



ANOTHER BARGAIN IN RECOBD CHANCERS. The very latest type 3-speed mixer changer (as illustrated) in cream of borwn, with turnover crystal head. Motor board measuresonly 12in x 10in. Requires only 3in. above board, and 3in. below. Absolutely brand new in sealed cartons at £10/10/- each, tax paid, plus 5/- packing and carriage.

X10/10/- each, tax paid, pins 5/- packing and carriage. MANUFACTURERS' SURFLUS. Few only, iron-cored, 7 wave-band (2 medium, 5 short waves), comprising it coils, trimmers, wave-change switch, etc., etc., complete with copy of manufacturers' orginal circuit, 50/- only, tax paid. Com-pletely assembled. GHT PIOLUP. Com-DECCA, LUCAING HOMET PIOLUP. Com-DECCA. DURING HOMET PIOLUP. Com-duction of the complexity of the piolup. Com-duction of the complexity of the piolup. Com-pleters and the piolup. Com-duction of the piolup. Com-duction of the piolup. Com-ton of the piolup. Complexity of the piolup. Complexity of the piolup. Com-ton of the piolup. Com-duction of th

plete with standard crystalinsert, 32/6 only ! Spare inserts for either Standard or L.P. at

SINGLE PLAYING UNIT, by very famous SINGLE PLAYING UNIT, by very famous Decox X.M.S. plugan C. and D. heads for L.F. and Skandard. 29/9/6 only! G.E.C. RECORDING TAPE. 1,200ft., on metal spool, st bargain price of 17/6 per

spool

METERS

.S.D.	Size	Туре	Fitting Price
roamp	D.C. 21n.	M.C.	R.P
icroamp	D.C. 21in.	M.C.	F.R
	D.C. 2in.	M.O.	R.P 13/6
	D.C. 2in.	M.C.	F.R
	D.C. 2in.	M.C.	F. Sq
	D.C. 2in.	M.C.	F. Sq. (scale calib. 1.5 kV.) 15/-
	D.C. 21in.	M.C.	F.R
	D.C. 24in.	M.C.	Desk Type
	D.C. 2in.	M.C.	F. Sq
	D.C. 24in.	M.C.	R.P
	D.C. 25in.	M.C.	F.R. 10/-
	D.C. 2in.	M.C.	F.R. 7/6
L. \.	D.C. 2in.	M.C.	F.B. 7/8
1.	D.C. 2in.	M.C.	F. Sq
ι. .Α.	D.C. 2in.	M.C.	F. Sq
A.		M.C.	R.P. 10/-
	D.C. 21in. D.C. 2in.	M.C.	
LA.			
LA.	D.C. 21in.	M.C.	F.R
np.	R.F. 2in.	Thermo	
).	R.F. 21in.	Thermo	R.P 10/-
).	R.F. 21n.	Thermo	F. Sq
) _*	D.C. 2in.	M.C.	F. Sq 13/6
) .	R.F. 21in.	Thermo	F.R
p.	D.C. 2in.		R.P. (with shunt) 10/6
i0 amp.	D.C. 2in.	M.C.	F. 8q
lt"	D.C. 2in.	M.C.	R.P
1t	A.C. 21in.	M.C.	F.R 10/-
5 volt	D.C. 21in.	M.C.	F.R 17/6
oit	D.C. 2in.	M.C.	F.R 15/-
ol	D.C. 2in.	M.C.	F. Sq 8/6
- Round	d projection.		Thermo = Thermo-couple.
- Flush			M.C Moving Coli,
= Flush			M.I Moving Ion.

- Moving ion. 31.1.

THE "SUPERIOR " FOUR KIT. Our new form THE "SUPERIOR" FOUR KIT. Our new four-valve receiver. A.C. mains. 500/250 v. Mains. 500/250 v. Mains. 100/250 v. Mains. 100/200 v. Mains.

Complete Instruction booklet with practical and theoretical diagrams is provided. Book-iet available at 1/6, post free. Our price for complete kit, £63/9/8111 Please add 2/6 packing and carriage. If preferred, we can supply Cabinet Assembly only, com-prising Cabinet and back, drilled chassis and bracket, dial,

TAPE RECORDER CABINETS. We can be seen a service of cabinet hands one by perchastic take Trucos or Wearlie Tapo perchastic take trucos or the set of the second or set of the target perchastic take the target perchastic table to the target table target table to the target table target table to the target table target table to take the Elipico AC/64 ML target to the target to take the target to the target to take target to take the target to take target to take the target to take


ply all re-components in the second second second second second right down to the last nut and boil. Valve line-up: 6K7, 6J7 and 6V6. Chassis ready drilled-Cabinet size 12in. Iong by 6in. Bakelite, or wooden, wainut finish cabinet. Complete instruction booklet with practical and theoretical diagrams. Each component brand new and tested prior to packing. Our price 25/10. complete-harmonic thraid new and tested prior to packing. Our price 25/10. complete-harmonic thraid new and tested prior to packing. Our price 25/10. complete-harmonic thraid new and tested prior to packing. Our price 25/10. complete-harmonic thrait and theoretical distribution thrate and tested prior to packing. Our price 25/10. complete harmonic thrate and tested prior to packing. Our price 26/10. complete harmonic to booklet is the most comprehensive available for this type of receiver-Booklet available at 1/6 post receiver-Booklet available at 1/6 post receiver-Booklet available at 1/6 post receiver-Booklet and carriage for com-plete kit. 24 VOLC Output 200/250 v. A.C. 100 watts. Completeip smoothed, incorporates Sodium Lamp transformer. Brand new, 92/6. LIGHTWEIGHT CRYSTAL HEADFHOMES. Brand new, by Rothermel. List price 70-. Our price 25/-11 Limited supply. HEADFHOMES. Brand new, ex-Govt., by 8. G. Brown. Type CHR. Iow resistance, 716 per pair. Type CHR high resistance, 716 per pair. Type CHR high resistance, 716 per pair. HEADFHOMES can also supply very secial brand new American ex-Govt. light weight high resistance phones by Trimm at 15- per pair.

12/6 per pair. We can also supply very special brand new American ex-Govt. light-yeight high resistance phones by Trimm at 15/9. per pair.
 TESTMETER-EX-ARMY. Direct readings to the second secon




Please add postage under £1. C.O.D. or Cash with order. C.O.D. charge extra—Open 9 a.m.-6 p.m., Monday to Friday. Sorry but we close at 1.0 p.m. on Saturday.

wavechange switch, dial, inter, drum pulleys, drive spindle, drive spring and knobs, at 45/-, plus 2/6 packing nd carriage. N.B.—Our Kits are even supplied with sufficient solder for the jobl

RADIO TRADERS LTD.

23 WAR	DOUR ST	. LOND	ON, W.	. (Coventry S	treet end)
	GERrard 397	· · · · · · · · · · · · · · · · · · ·		Grams: "Ra	
		CAPACIT	ORS IN	MOULDED	TUBES.
.001, .02, .0	3, .05, 2,500 v. 1 02, 5,000 v. D.C metal, one hol			• • • • • • • • • • • • • • • • • • • •	2/6
.1, 1,000 v.	metal, one hol	e fixing	NSERS		Per doz.
2 Mfd. 150	v. Tubular Pap	er (aluminius	n tubes), 1/	6 each	15/- 18/-
16 Mfd., 35	v. Electrolytic, 0 v., Electrolytic 0 v., Electrolyt	ic, 2/- each	•••••		21/
24 Mfd., 35 32 Mfd. 45	0 v., Electrolyt 0 v. Electrolytic	c, 2 3 each c, 2/6 each			24/- 27/-
8 x 16 Mfd	., 350 v., 1/6 ea	ch	0 4 1/6 070	-h	15/-
32 Mfd. Me	etal Cans Electr	olytic, 350 v.	, 1/6 each		15/-
32 x 8 Mfd 64 Mfd, Me	. Metal Cans El etal Can Electro	ectrolytic, 27 olytic, 350 v.,	2/6 each	ch	18/-
Condenser	00 v., Electrolytic 0, Electrolytic , 350 v., 1/6 ea: Metal Cans Electro Metal Cans Electro clips for above 0v, Metal Cans, v., 1/- each v. Tubular Pap v. Tubular Pap vular Miniature,	L/- each 25	Mfd 50 y	Tubular Cardbo	3/-
50 Mfd. 12	v., I/- each	. 1/~ Cacit, 2.0			10/6
12 Mid. 50	v. Tubular Pap	er (aluminiu) er (aluminiu)	m tubes), I/ m tubes), I/	- each	10/6
.00005 Tub	ular Miniature,	4/- per doz.	.02, 500 v.	, 4/- per doz., . 4/- per doz.	001, 350 v.
MIDGET	v, Tubular Pap pular Miniature, 205, 350 v., 4 MICA CONE ted Moulded Mi ted Silver Mica ted Carbon Res N RESISTORS	ENSERS:	0001, .0002,	.0003, .0004, .	0005 4/-
200 Assor	ted Silver Mica	s. Popular \	r values		£2 10 0
200 Assort	ed Carbon Res	istors: 1, 1 a	nd watt. ($: \frac{1}{2}$ watt. $3/2$	Good selection	£ 10 0 2 watt 6/-:
					- · ·
HIGH S	TABILITY RE 1% 2% 1/- 9d. 1/3 1/- 1/9 1/3 2 watt	SISTORS:		ALL CINC	4
4 watt	I/- 9d.	6d.each	COMPO	ONENTS IN	
watt watt	1/9 1/3	I/- each	PYE PLU	JGS AND	
8-40 MEG	2 watt	2/6 each	SOCKE	ETS	1/6 pair
10 wat	ND VITREO t, 2/6 ; 15 w CONTROLS.	vatt, 3/-;	20/30 wat	t, 3/6 each.	
W/W V/	CONTROLS. er values, 2-3 w	COLVERN	IOK Isolat	F. 5K PRESET	2/
500 ohn	ROLS WITH	K, 50K, with	spindle	DNICE	3/ 2/6
V/CONT	ROLS: Less	Switch, Pres	et and Spi	indle. MOST	
TWIN	IDGET GAN	IGS0005.	with trimm	ers. PERSPEX	I/9 .,
COVER					5/6 ., 15/- doz.
PUSH B	UTTON KN	OBS	s, no each		3/- ,,
TAG STF 7-way 4	UTTON KN RIPS: 3-way, 2/ - doz.; 28-way ED PILOT L	- doz; 4-way	2/6 doz.; 5	-way, 3/- doz.;	
ASSORT	ED PILOT L. in. Most valu	AMP HOL	DERS		4/: 2/:
POINTE	RKNORS	mall black y	vith line +1	n hole	7/6
Large, #	In hole. 7/6: w	ith spring cl	: Small, ‡i ip. ‡in. hole	in. hole, 6 /-;	4/6
CLIX W	in. hole, 7/6; w ANDER PLU TRIMMER T	GS, Type MR	2. Red, bl	lack, blue	2/
BELLING	TRIMMER T S & LEE. P/M E COILS: Typ	FUSE HOLE	ERS, Type	L356	2/6 each
VALVE	HOLDERS: M	louided. B9	A, 7/6; B7	G, 6/-; EF50,	12/- doz.
6/-; EN for B9A	HOLDERS: M IGLISH OCT , B7G, 6/- doz.; 3 & LEE. PI	AL, 3/- per PAXOLIN	doz. SCF 	ZDA 4-pin UX	3/
BELLING	S & LEE. PL	LUGS AND	SOCKET	TS. Ex-Govt.	1/6 pair
BULGIN	5 & LEE. PL 0 NEW 5-pin, C 1. P73, Plug a 2/6; P200, Plu /-; Dolly Switc ndard Switches FFICE LAMP overs for same OKES, 300 w.,	ind Socket,	2/9 each;	P74, Plug and	No ball
Socket, S.255, 2	2/6; P200, Plu /-: Doily Switc	ig and Socke hes, S.267, 2	-; Dolly S	witches, S.259,	
1/6; Sta	ndard Switches	ACKS No	Dn-off		1/6 each 9/= doz
Lamp C	overs for same		······		9/- doz. 3/- ,,
OUTPU	overs for same OKES, 300 w., T TRANSFO	RMERS.	lulti Ratio,	5/-; Pentode	
or Powe	21"				4/- 10/6 doz.
DRUM	DRIVES, 41in.		10 Fulles, 1	#J	I/- each
ARCOLE	CREEN CAN DRIVES, 4½in. TORS. WX6 CTRIC (White LAMP HOL	ney Lamps), I	Red, green,	clear, 1/6 each	9/- doz. 15/- "
					18/
AIR SPA	Iders, 1/9 each CE TRIMME PF, 20PF, 25PF, PLUG AND	RS. Preset	and spind	le types, 5PL,	15/- "
JONES	PLUG AND	SOCKETS.	4-pin, 2/	6; 6-pin, 3/-;	1.3/i= ,,
8-pin, 3 NUTS.	/6; 10-pin, 4/- 8BA, 3 - ; 6BA TAGS, 1/6 gro	; 12-pin . 2/6 : 4BA.	3/- : 2BA	••••••	6/- pair 4/-gross
SOLDER	TAGS, 1/6 gro RS, 2, 4 and 6B	SS. SHAKE	PROOFW	ASHERS	2/
SHAKEP	ROOF SOLD	ER TAGS,	4BA and 6B	A, 2/-; 2BA	2/3 ,,
PAXOLI	N SHEET, 36	in. x 41 in. x	16 in		2/- each
UNON WI	TH ORDER OF			LL ORDERS	
	REDUCED	PRICES	FOR GRO	OSS LOTS	
Trade (Counter op				Fridays.
-		Callers W			ORT
WH	OLESALE, 1	NQUIRIES			OKI
	E	- QUINES	TRATIC		

VALUE FOR MONEY OFFERS

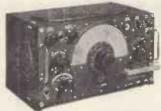

AIR MINISTRY COMMU-NICATION RECEIVER RIISSA. First class condition. Frequency ranges-18.5-7.5 Mc/s, 7.5-3 Mc/s. 1.500-600 kc/s. 500-200 kc/s, 200-75 kc/s. Complete with 9 valves and Magic Eye. Guaranteed absolutely perfect. Price £7/19/6, plus 10/- for packing and carriage.

1155 POWER PACK AND OUTPUT STAGE complete with U50 and KT61 Valves (not surplus), Black crackle case 12 x 8 x 5in., built-in 5in. pm Speaker and phone jack. 200-250 v. A.C. All connections terminate in Jones plug which enables instant operation of receiver without any modifi-cations whatever. Matches in appearance with receiver. Made to "Wireless World" specifications. Built entirely from top grade new components, *£7*/10*j*- plus 3/6 carriage.



G.E.C. VHF RECEIVERS complete with 10 valves. Ex-Govt. Used but guaranteed excellent condition. Valves ZA2's, 954's or EFS0's in HF and 1st Det, stages. Det. 19 in local oscillator, KTW63's in three IF stages, D63 Det. and AVC, LF H63, Output KT63, Noise suppressor D63, Power requirements 6 v. 3 a, 270 v. 80 mA, as used by various British Police forces. 78.5-82 Mc/s, Oscillator Crystal controlled (No crystal Included). Grey enamel steel case with Ild 10 x 8 x 7in. Weight 221bs. Note the amazingly low price, 29/6 plus 5/- carr.

PROMPT DELIVERY AND SATISFACTION GUARANTEED

H.P. RADIO SERVICES LTD. Britain's Leading Radio Mail Order House, 55 COUNTY ROAD, WALTON, LIVERPOOL. 4 Established 1935

Tel. : Aintree 1445

SPECIAL OFFER-"AVO" MINORS, Universal AC/DC. Reconditioned and in perfect order, £5/15/-. "AVO" MINORS, D.C. "E" Type, also reconditioned and AVO MINORS, D.C. TEM Jype, also reconditioned and perfect order £3/5.-ADVANCE SIGNAL GENERATOR. Type E.I. £21. FURZEHILL OSCILLOSCOPE. Type H.L. £28. MEGGER SAFETY OHMMETERS. Perfect. £4/10J-. H.R.O. SENIOR RECEIVERS, as new. Coverage is 7 bands from 30 Mc/s. D.S.T. 100 RECEIVERS, as new. Coverage is 7 bands from 30 Me/s. to 50 Kc/s., £26/10/- each. HAMMERLUND BC779B. Mint condition, rack mtg., £39 HALLICRAFTERS SX28, S27, S41, S38, etc. Perfect cond. AR88LF, AR88D, CR100, from stock. R1155 RECEIVERS, new. A.C. /D.C. MOTORS, suitable for sewing machines, 47/6 each. A.C. /D.C. 12 v-15 v. MOTORS, long spindle for models, 15/- each. 20 WATT P.A. RACK MOUNTING AMPLIFIERS, complete with power pack, 200/250 v. A.C., less valves, £6/10/-. Valves-2 type PX25, I MH4 and I MU14, £2/15/- per set. NEW M/C MICROPHONES, hand type, with 12 yds. heavy duty screened cable, £3/15/- each. B.C.221 FREQUENCY METER, from stock. Many items of American equipment available. B.C.221 FREQUENCY METER, from stock. Many items of American equipment available. TEST EQUIPMENT. We hold a comprehensive stock. Multi-range meters at 1,000 and 20,000 o.p.v., valve testers, signal genes. UNISELECTORS. 4-bank, double wiper, 241- each. 10,000 Ω POTENTIOMETERS, large size, by Colvern, enclosed 8/6 each. 100k, 15w, 9/6 each. MAINS TRANSFORMER. 350-0-350 v. Ellison at 120 mA., 6-24 ES-CTEV. MAINS TRANSFORMER. 350-0-350 v. Ellison at 120 mA., 6.3 v. 5 a., C.T. 5 v. 3 a., 37/6. Full range of all types of Ellison products EVERSHED BRIDGE MEGGERS, 250 v. Special price, £17/10/-EVEN STED BILDE FIELGERS, 230 V. Special price, £17/10/-each, 1,000 V. Meggers in stock. COSSOR DOUBLE BEAM OSCILLOSCOPE, perfect, £33. EDDYSTONE 640 RECEIVER. Perfect, at £22. 6 VOLT (3 at 2 v.) BOXED ACCUMULATORS, 18/-, 1 μ F330 v. METAL CASED TUBULARS, U.S.A., at 4/6 doz. (minimum 2 doz.). H.R.O. COILS. .46-.96 Mc/s., etc., at £2/5/- per coil. LARGE STOCKS OF MOTORS. A.C./D.C. and A.C., 1/16, 1/12, 1, 1 h.p. Vour post enquires welcomed. S.A.E. for reply, please. Orders. C.W.O. or Pro-forma Invoice, no C.O.D. Prices quoted do not Include carriage and packing. All types of equipment purchased. Top prices paid. SERVICE SPARES RADIO 4, LISLE STREET, LONDON, W.C.2

Telephone : GERrord 1734.

MAINS TRANSFORMERS Primary, 200-250 v. P. & P. 2/-. 300-0-300 100 mA., 6 wolt 3 amp., 5 wolt 2 amp., 22/6. Drop thro' 350-0-350 v. 70 2.5 amp., 5 v. 2 amp., 14/6. 70 mA., 6 v. Drop thro' 250-0-250 v. 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6. 280-0-280, drop through, 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6. 250-0-250 80 mA., 6 v. 4 amp., 14/-. Pri. 230 v. Sec. 200-0-200 35 mA., 6 v. 1 amp., 8/6. Drop thro' 280-0-280, 200 mA., 6 v. 5 amps., 5 v. 3 amps., 27/6. Drop thro' 270-0-270 80 mA., 6 v. 3 amp., 4 v. 1.5 amp., 13/8.

Drop thro' 270-0-270 60 mA., 6 v. 3 amp., 11/6.

Auto Trans. Input 200/250. H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 11 amp., 5 v. 3 amp., 25/-. P. & P. 3/-.

Heater Transformer. Pri. 230-250 v. 6 v. 11 amp., 6/- ; 2 v. 21 amps., 5/-

9in. T.V. Gabinsi, front in contrasting walnut veneers, size 164in. long, 114in. high, by 124in. wide. Complete with two pieces expanded aluminium in gold, 12×91n. and 5in. speaker baffle, 15/-, post paid.

P.M. SPEAKERS (closed field) :

	WICD JESS
	trans. trans.
21in	- 15/6
3}in	- 13/6
51n	16/6 12/6
641n	16/6 12/6
8in	18/6 15/-
10in	- 19/6
Truvoz BX11. 12in. P.M.	
coil, 45/ P. & P. 3/6.	

61in. M.E. Speaker, 1,000 ohm field, 15/-.

R. & A. T.Y. Energised 61 in. Speaker, field coll 175 ohms. Requires a mini-num 150 mA. to energise, maximum current 250 mA., 8/6. P. & P. 2/6.

Extension Speaker Cabinet, in contrasting walnut veneer, size 15×10 jin. Will take 61 or 8in. speaker, 17/6.

Completely built All-dry Mains Unit by famous manufacturer, 200/250 v. Metalcasesize 8 × 5 × 31n., Incorporating Westinghouse metal rectifiers, 3 500 mfd., 16 × 24 mfd., mains trans., 3 smoothing chokes, output 90 v. 10 mA. 1.4 v., 0.25 amp., 38/6. P. & P. 2/6

Volume Controls. Long spindle less switch, 50K, 500K, 1 meg., 2/6 each. P. & P. 3d. each.

Volume Controls. Long spindle and switch, $\frac{1}{2}$, $\frac{1}{2}$, 1 and 2 meg., $\frac{1}{2}$, each; 10K and 50K, $\frac{3}{2}$ /6 each. $\frac{1}{2}$ and 1 meg., long spindle double pole switch, minia-ture, $\frac{5}{2}$. P. & P. 3d. each.

Trimmers, 5-40 pf., 5d. ; 10-110, 10-250, 10-450 pf., 10d.

Twin-gaug .0005 Tuning Condenser, 5/-. With trimmers, 7/6.

Line Cord, 2-way 0.3 amp., 60 ohms, per foot, 1/3 per yard.

Twin-Gaug .0005 with feet, size 31×3×18in., 6/6.

3-gang .0005, with feet size 4% × 3×1%in., 7/6.

T.V. Coils, moulded former, iron-cored, wound for re-winding purposes only. All-can 1%×1%in., 1/- each, 2 iron-cores all-can 2%× iin., 1/6 each.

Used Metal Rectifier. 250 v., 150 mA.,

Metal Rectifier. 250 v., 250 mA., 12/6. Metal Rectifier. 230 v., 45 mA., 6/-.

PERSONAL SHOPPERS ONLY. 9in. Enlarger 17/6; 12in. 27/6.

Germanium Crystal Diode, 1/6, post natd.

Television Masks. White Rubber 9in. with glass, 7/6. Cream Rubber, 12in., with armour-plate glass, 15/-.

T.V. Width Controls, 3/6.

T.V. Sub Assembly, all-chassis, 124n.x 34in., with frame osc., line osc., 12 mfd. 275 wkg., Metrosil, 8 condensers, 4 resistors and tag panel, 15/-.

Amplifier Case, black rexine covered, teather carrying handle, chrome plated corners, rubber feet, feit lined, detach-able IId. External dimensions $13\frac{1}{2} \times 13\frac{1}{2} \times 9\frac{1}{2}$ in., £1. P. & P. 2/6.



DECLARATION IS APPLICABLE.

23 HIGH STREET (Uxbridge Road) Telephone : ACOrn 5901. ACTON, W.3

Hours of Bussiness :

Saturday 9-5 p.m. Wednesday 9-1 p.m. Other days 9-4.30 p.m.

Used 12in. C.R. Tube, aluminised, E.H.T. maximum 10 Kv., heaters 2-volt, with heater cathode short, guaranteed for 3 months. Complete with rubber mask, Elac P.M. focus unit, scan coils, low line, low frame and frame o.p. trans. £5/10/-, P. & P. 7/6.

HIGH-IMPEDANCE PLASTIC RECORDING TAPE, by famous manufacturer. 600ft. on aluminium spool, 8/-. 1.200ft. on aluminium spool, 17/6, post paid.




M. & L. Superhet Coils with circuit, 6/6; iron-cored 465 I,F.s. 7/6; min.gang, 5/6; volume control with switch, 4/-; wave-change switch, 5/6; heater trans., 7/6; 4 v/h, 1/6; 4 obsolete ex-Govt.valves, metal rectifier and Xtal diode with circuit, 14/6; 25 × 25 mid., 1/-; 16×16 mid., 33; condenser kit (17), 7/6; resistor kit (14), 3/6.

FULLY SHROUDED MAINS TRANSFORMER, input 110/250, sec. 350-0-350 175 mills., 6.3 v. 7 amp., 5 v. 3 amp., 35/-, P. & P. 3/-.

FULLY SHROUDED CHOKE, 15 Henry 180 mills., 15/-. P. & P. 2/-. FULLY SHROUDED CHOKE, 5 Henry 120 mills., 8/6. P. & P. 2/-.

USED C.R. TUBES. . Heater cathode short, 9in., 45/-; 12in., 75/-. Ion burn, 9in., 35/-; 12in., 55/-. P. & P. on each 7/8.

COMPLETELY BUILT SIGNAL GENERATOR

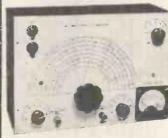


Coverage 120 Kc/s.-320 Kc/s., 300 Kc/s.-900 Kc/s., 900 Kc/s.-2.75 Mc/s., 2.75 Mc/s.-8.5 Mc/s., 8.5 Mc/s.-25 Mc/s., 17 Mc/s.-50 Mc/s., 25.5 Mc/s.-75 Mc/s. Metal case 10 x 63 x 42 in. Size of scale $6\frac{1}{2}$ in. x $3\frac{1}{4}$ in., 2 valves and rectifier. A.C. mains 230/250 v. Internal modulation

400 c.p.s. to a depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel, f4/19/6. Or 34/- deposit and 3 monthly payments of 25/-. P. & P. 4/- extra.

CONSTRUCTOR'S PARCEL No. 1 comprising charsis 123×28×20n., car plated 8 gauge. vh., LF. piste. 2 supporting brackets, i wareband colles, new wave-length station names. Size of scale 114×41n., drive spindle drum. 2 pulleys, pointer, 2 bulb holders, 5 paxolin international octai valve holders, 4 knobs and pair of 465 LFs, 16(6.

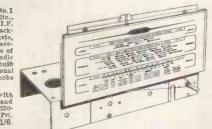As ABOVE, but complete with 16+16 mid. 350 wkg. and semi-shrouded drop thro? 250-0-250 60 mA., 6 v. 3 amp. Pri. 200-250, and twin-gang, 31/6. P. & P. 3/-.



CONSTRUCTOR'S PARCEL. As No. 1, plus 16×10 mid. 350 wkg., semi-shrouded drop-thro. 250-020 60 mA., 6.3 v. 3 a., 5 v. 2 a., twin gang, and 6 L.M.S. superhot colls complete with trimmers and tracking condensers with circuit. $\gtrsim 25/5$, plus 3/6 post and pkg.

B.I. MAINS TRANSFORMERS, chassis mounting, feet and voltage panel Primaries 200/250.

350-0-350 75 mA. 6.3 v. 3 a. tap 4 v. 6.3 v. 1 a., 13/6.

350-0-350 70 mA. 4 v. 5 a., 4 v. 2.5 a. C.T., 18/6. P. & P. on the above C.T., 18/6. P. transformers, 2/-

500-0-500 125 mA. 6.3 v. C.T. 4 a., 6.3 v. C.T. 2 a., 5 v. C.T. 2 a., 27/6. 500-0-500 125 mA. 4 v. C.T. 4 a C.T. 4 a., 4 v. C.T. 2.5 a., 27/6. 4 a., 4 v.

500-0-500 250 mA. 4 v. C.T. 5 a. 4 v. C.T. 5 a., 4 v. C.T. 4 a., 39/6.

P. & P. on the above transformers, 3/-. Line and E.H.T. transformer SVA, using ferrocart core complete with built-fn line and width control. Mounted on small all-chassis. Overall size $4\times \times 18_{10}$, EV51 rec. winding, 27/6. Scan Colls, low line low impedance frame, complete with frame trans-former, to match above, 27/6. P. & P. 2/-.

alve Holders, moulded octal l	Mazda
nd loctal, 7d. each. Paxolln,	octai
fazda and loctal, 4d. each. Mc	nided
37G, B8A and B9A, 7d. each.	B7G
houlded with screening can, 1/6	each
2 mfd., 350 wkg	01-
6×24, 250 wkg.	Al-
mfd., 200 wkg	1/3
0 mfd., 450 wkg	3/6
6 × 8 mfd., 500 wkg.	4/6
6×16 mfd., 500 wkg.	5/9
0 × 10 mmu., 400 wkg.	3/9
2 × 32 mfd., 350 wkg	4/-
2×32 mfd., 350 wkg., and	
25 mfd., 25 wkg.	6/6
0 mfd., 25 wkg.	11d.
50 mfd., 12 v. wkg	1/-
6 mfd., 500 wkg., wire ends	3/3
mfd., 500 v. wkg., wire ends	2/6
mfd., 350 v. wkg., tag ends	1/6
0 mfd., 25 v. wkg., wire ends.	1/9
00 mfd., 350 wkg.	4/-
00+200 mfd., 350 wkg	9/6
6+16 mfd., 350 wkg	3/3
0 mfd., 180 wkg	1/9
5 mfd., 220 wkg	1/6
mfd., 150 wkg.	1/6
0+100 mfd., 280 wkg.	7/6
0 mfd., 12 wkg. 2+32 mfd., min., 275 wkg.	11d.
2+32 mfd., min., 275 wkg.	41-
0 mfd., 50 wkg.	1/9
liniature wire ends moulded,	
100 pf., 500 pf., and .001 ea.	7d.

2

21885111568653

м

Combined 12in. mask and escutcheon In lightly tinted Persper. New aspect, edged in brown. Fits on (ront of cabinet, 17/6.

Frame Oscillator Blocking Trans., 4/6. Tube Mounting Bracket, size 9½ × 4§in. 12in. tube clamps, 2/-.

Smoothing Choke, 2 henry 150 mA 3/6; 250 mA., 10 henry, 10/6 5 henry 250 mA., 60 ohms, 8/6.

P.M. Focus Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15/-.

P.M. Focus Unit for Mazda, 12in., with vernier adjustment, 17/6.

Wide Angle P.M. Focus Units, Vernier adj., state tube, 25/~.

Energised Focus Coil, low resistance mounting bracket, 17/6. Ion Traps for Mullard or English Electric tubes, 5/-, post paid.

465 KG. I.F.s, size 23×18in. Q.110 removed from American equipment, 5/- per pair. Standard 465 KG. iron-cored I.F.s, 4×11×12in., per pr. 7/8. Wearite standard iron-cored 455 KG. I.F.s, 33×18×18in., per pr. 046 9/6

Iron-cored 465 Kc. Whistle Filter, 2/6. OUTPUT TRANSFORMERS. Standard type 5,000 ohms imp., 4/9; 4/21 with extra feed-back windings, 4/3. Minia-ture 4/2-1, 3/3. Multi-milo 3,000, 7,000 and 14,000, 5/6. 10-watk push-pull, 6/6 matching, 7/*. 90-1 3 ohm speech coil, 6/6.

PUSH-BACK CONNECTING WIRE. Doz. yds., 1/6, post paid.

STANDARD WAVE-CHANGE STANDARD WAVE-CHANGE SWITCHES, 4-pole 3-way, 1/9; 5-pole 3-way, 1/9; 3-pole 3-way, 1/9; 9-pole 3-way, 3/6; Ministuretype, long spindle 3-pole 4-way, 4-pole 3-way and 4-pole 2-way, 2/6 each. P. & P. 3d,

465 KC. MIDGET I.F.s. Q.120 size lin.long, lin. wide, kin. deep by very iamons manufacturer. Pre-aligned adjustable iron-dust cores, per pair, 12/6.

Mains Droppers. 0.3 amp., 460 ohms, tapped 280 and 410, 1/6; 0.2 amp.. /17 ohms, tapped at 100 ohms, vitreous, 1/6; 0.3 amps., 950 ohms, tapped 700 and 825, 2/6; 0.2 amp., 1,000 ohms, vitreous, tapped, 2/6; Vitreons, 0.3 amp. 700, tapped 580, 640, 600, 3/6. P. & P. on each 33.



WIRELESS WORLD



VALVE TESTER TYPE 4. 200-230 v. A.C. Input. Ex-Govt. in good condition with descriptive book containing circuit diagram of instru-VALVE TESTER TYPE 4. 200-230 v. A.C. Input. Ex-Govt. in good condition with descriptive book containing circuit diagram of instrument and how to test valves from 1.4 v. to 40 v. With valve-holders for Brit., 4, 5, 7 pin and Octal U.S., 5 and 7 pin. 1/Octal, side contact, large Brit., 4 pin 9 pin, Acorn and diode. Housed in substantial wooden case. Price £7/19/6, carriage 10/-.
 WESTON ALL-PURPOSE AC/DC TEST METER MODEL E.665. New and unused, complete with leads and batteries, £8 each, only, p.p. 3/6.
 WESTON BATTERY OSCILLATOR MODEL E.662, TYPE 2. Also new and unused. Coverage, 100 kc/s-26 mc/s. Audio output aprox. 400 c/s. Available at the ridiculously low price of only £5/19/6, p.p. 4/6. (Oscillator complete with instruction booklet.)
 YEON MALTEY UNITS. Heavy Duty P.M. 20 watts. To fit the above horns. Brand new, £4/9/6, carriage 5/-.
 MMPLIFIERS BY SAVAGE & PARSONS. Output 50 watts. With 4-KT66's in parallel push-pull. Standard 200-250 v. mains input. AC. Output Imparale aprose dons line. High Imp., Gram. and microphone input. Bass boost control fitted. This excellent quality amplifier is housed in a strong metal case and is ready for use. Our price £25, carriage 5/-.

carriage £2

carriage £2. VARIABLE VOLTAGE REGULATOR TRANSFORMERS. Input 230 v. A.C. at 21 amps, output 57.5 in 16 equal steps to 230 v. at 21 amps. Ex-Govt. in perfect condition £15, carr. 10/-. ROTARY CONVERTERS. 230 v. D.C. to 230 v. A.C. at 110 watts. Complete with voltaze controlling sliding resistor. £7/10/-, carr. 10/-. ROTARY CONVERTERS. 12 v. D.C. input. 230 v. output at 100 watts. Brach new. £4/17/6, carriage 5/-. Ditto, 24 v., same price. R.I.155 RECEIVERS. Individually tested and despatched in good working order. Cases slightly soiled. £8/19/6, carriage 10/-. HOOVER 1/6TH H.P. MOTORS. 400-440 v. 3 phase. Standard shaft. 1,426 r.p.m. Brand new in original cartons, £3/10/-, carr. 5/-. ELECTRIC LIGHT CHECK METERS. 200-250 v. A.C. at 10 amps. Bakelite case, in very good condition. 15/-, p.p. 2/6. SIEMENS HIGH SPEED RELAYS. Twin 1,000 ohm coils, as new, 15/- each, p.p. 1/-.

SIEMENS HIGH SPEED RELAYS. Twin 1,000 ohm coils, as new, 15/- each, p.p. 1/-, TRANSFORMERS-E.H.T. Prim. 210-230 v. Sec., 2,000-2,100 v.-2,200 v. at 450 mja. £3; carriage 5/-. TRANSFORMERS. Input volts, 0-10, 20, 30, 50, 100, 150, 200 and 240 v. Output 2,000-0-2,000 v. at 450 mja. £5/10/-, carriage 10/-. TRANSFORMERS. Heavy duty, suitable for welding, 230 v. Prim. 50 cycles, L.T. Variable, 114 v. 134 v. 60-70 amps, £3/19/6, carriage 5/-. TRANSFORMERS. 12 v. Car Radio, ex-Philco, 300 v. H.T. 90 m/a. Brand new and unused, only 12/6, p.p. 2/-. TRANSFORMERS. Auto; 110 or 230 v. In or out, for stepping up or down, 750 watts. Switched and fused. By B.T.H. £4/15/-, carriage 5/-.

carriage 5/

CHROMIUM PLATED EXTENDABLE AERIALS. Min. length 12in., Max. length 60in. 8/6, p.p. 9d.

0-1 m/a., 21 in. F/Mounting, new and boxed	21/-, p.p. 1/-
0-1 m/a. 2in. R.F. Round	5/9, p.p. 1/-
0-30 m/a., 2½in. F/Mounting	12/6. p.p. 1/-
0-30 m/a., 2in. Round, new and boxed	7/6, p.p. 1/-
0-200 m/a., 21in. F/Mounting	12/6, p.p. 1/-
0-10 amps., D.C., 31 in. F/Mounting	15/-, p.p. 1/6
G.E.C. 6in. TABLE FANS. 12 v. D.C. Brand new, 32	6, post paid.
6 WAY SCREENED FLEXIBLE COLOUR CODI	ED CABLE.
PVC covered 151- per 12 vds post 116	

P.V.C. covered, 15/- per 12 yds., post 1/6. 813 CERAMIC VALVE HOLDERS. Brand new, 9/6, p.p. 6d. BATTERIES H.T. AND L.T. Heavy dury layer type. 150 v. tapped at 87 v. H.T. L.T. 4¹ v. Perfect condition. Size 9¹/₂in. x 4¹/₂in. x 4¹/₂in. x 4¹/₂in. y 4¹/₂en. y 4

rack. Price quoted against enquiries. PAINTON PLUGS AND SOCKETS (MIN. JONES TYPE).

Brand new. CARLE ENTRY SOCKETS

CABLE ENTRY PLUGS	CABLE ENTRY SOCKETS
2 pin each 2/- 4 pin 2/6	each 8 way
12 pin	18 way
33 pin 15/ PLUGS each	SOCKETS each
12 way	4 way
E.H.T. OSCILLATOR COIL, R.	18 way
	9d. ODEL ELECTRIC SOLDERING 1. Suitable for 200/240 v. 25 watts.
19/8 post free. PHOTO ELECTRIC MULT	PLIER CELLS. TYPE 931A.
	STOCK : YOUR ENQUIRY
	CT INNON WC2

15 LITTLE NEWPORT ST., LONDON, W.C.2 -GERrard 6794/1453.-

UNIVERSAL ELECTRONIC

ANNUAL HOLIDAY

Please note that all correspondence arriving on JUNE 11th to JUNE 26th inclusive will be dealt with, upon our re-opening on June 28th, 1954. London's finest selection of real quality equipment, at reasonable prices.

London's finest selection of real quality equipment, at reasonable prices. Test Equipment AVO model 7, as new, £15. AVO model D, £12. AVO-Minor, £6/10/-AVO Wide range sig. gen., £20, previous model, £9/10/-. AVO Valve tester roller panel, £11. AVO Valve characteristic meter, as new, £45. COSSOR Double Beam Scopes, from £35 Model. WESTERN Industrial test set, 20,000PV, £20. MARCONI type 887 valve volt-meter, £25. MARCONI type TF144G. TR390. TR157. Signal generators. TF340 output meters, Type 887 valve voltmeters. MARCONI Audio Oscillator and other items of Marconi equipment. EVERSHED Bridge Meggers 500 v.-250 v. Evershed Wee Meggers, £14. PHILIPS audio oscillator, £35. SIMMONDS Q meter, £85. Baceivers. Receivers

HALLICRAFTERS SX28 in excellent condition, £50. SX24 550 Kc/s-42 Mc/s, £30. S20R, £28. S20, £25. S38 ACDC 110-250, £25. S29 Batt. mains, £25. RCA AR77/ 550 Kc/s-30 Mc/s, £30. HRO Junior and Senior receivers complete with coils, from, £30. HALLICRAFTERS marine HTI1 transmitters receivers, £50. NATIONAL NC100, £40. HAM-

MARLUND HQ120X, £40. MANUALS for RCA. AR88D-LF National HRO, S20R, CR100, SX28, AR77/ HQ120, B2 TXRX photostats, 27/6 per copy. Audio Equipment

Audio Equipment TAPE recorders. GRUNDIG type 700L as new, £40. BAIRD mark 1, as new, £40. SIMON SOUND mark 2, £40. SOUNDMIRROR portable, £45. MAGNEGRAPH portable, as new, £35. U.S.A. Webcor latest, 53 model, £75. WANTED URGENTLY At your price.

WANTED URGENTLY At your price. Frequency Meters BC221. TS 174/U TS175/U, TS3, TS13, TS35, TS45, RCA AR88D-LF SX28. S27'S S27CA. Spectrum Analysers. Type TS148 TSX-45E. Klystrons type 723/AB. CV129, 2K39, 2K33, 707A, 707B, any U.S.A. or British VHF or microwave gear, receivers, 1359 P58, 1394 erc. 294 etc.

Shop hours; 9.30 to 6. Thursday to I p.m. Phone GERrard 8410 (Day), MEAdway 3145 (Night). OUR ONLY ADDRESS DEPT. W.



WHOLESALE AND EXPORT L. WILKINSON **19, LANSDOWNE ROAD, CROYDON** Telegrams : " WILCO " CROYDON Phone : CRO 0839 RELAYS-P.O. TYPE 3,000 BUILT TO YOUR SPECIFICATION-EARLY DELIVERY QUOTATION BY RETURN-PLEASE STATE RESISTANCE OF COIL REQUIRED AND CONTACT BUILD UP. RACKS. Standard 6ft. P.O. type for 19in. panels, steel channel sides correctly drilled, heavy angle base. VOLTAGE REGULATORS. Input 230 volt A.C. 21 amps., output 57.5 to 228 volts in 16 steps. With current limiting Reactor. £10. VARIAC TRANSFORMERS. Type 80 CO. Input 200/240 v. Output 220 v. 7.5 amps. £6/10/- each. HIGH STABILITY RESISTORS. 1%, 2%, 5% and wire wound vitreous available ex-stock. Best makes, low prices.

191 KENSAL ROAD, LONDON, W.10

LAD. 0666

For other items available see the advert. of our associated company WILCO ELECTRONICS.

PORTABLE RECORDING OR PROJECTOR CASES. Revine covered. (Ready for carrying löin. x 9jin. x 13m.). Internal dimen-sions, 14in. long. 11jin. deep. 5jin. front height, 8jin. rear height. Weight 6jih. Price 13(6 each. Postage and Packing 2/-

RECTAFORMA BATTERY CHARGER. 12 and 6 volts 4 amps. Complete with fuse and meter. Changeoverswitch from 6 to 12 volts. in an attractive grey crackle cabinet, mains lead and output leads and two battery buildog clips, 84/- each, carriage 2/6.

CONDENSERS. STANDARD CAN TYPES. ALL BY WELL-KNOWN MAKERS.

MAKERs. 12×4 mid. 450 v. 2/e ach. 34×6 mid. 350 v. 3/6 each. 32×3 mid. 350 v. 3/6 each. 32×32×8 mid. 350 v. 5/9 each. 32×32 mid. 350 v. 5/9 each. 32×32 mid. 350 v. 5 mid. 25 v. 4/6. 6 a mid. 350 v. 2/- each. 16×16 mid. 350 v. 2/9 each. 32×16 mid. 350 v. 3/9 each.

MIDGET CAN CONDENSERS. 8 mfd. 500 v., 3/6 each. 250 mfd. 12 v., 1/9 each. 8 mfd. 330 v., 1/1 each. 100 mfd. 25 v., 1/9 each. 16×16 mfd. 450 v., 4/6 each.

CLEM TRAVELLING IRONS. Suitable for all voltages 100/250 volts A.C./ D.C. Supplied with flexible lead and bayonet cap adaptor. Ready for use. Price 21/- each, an ideal for use. present.

CARDBOARD COVERED WIRE ENDED CONDENSERS 8 mid. 500 v., 2/3 each; 16 mid. 500 v., 3/6 each; 20 mid. 500 v., 3/6 each; 25 mid. 25 v., 1/9 each. 50 mid. 50 v., 2/3 each. 8×8 mid., 500 v., 4/-. each.

ELECTRON TRANSFORMERS.

Type LV9 Ratio 1/1.25 giving 25% boost on tube heater. Capacity between windings 16 pF. Secondary to frame, 6 pF. Suitable for High Definition

0.P.4. Dual purpose 12-watt output Transformer. Primary tapped for 2.6V6 or 2.6L6 in Push-Pull. Secondary, 3, 8, 15 ohms, 23/8, each,

MOULDED BAKELITE H.V. CONDENSERS

.1 mfd. 1,000 volts, 1/- each. .01 mfd. 4 kV, 1/8 each. .001 mfd. 4 kV, 1/-each. .001 mfd. 6 kV, 3/6 each.

HEADPHONES Type CLR Low resistance 120 Ω,

Type CLE Low resistance Lou, 7/6 pair. Type CHE High resistance 4,000 Q.

7/6 pear. Type CHE High resistence ... 11/- pair. Type DHE, a super job, 13/9 pair. Headphones, by Trimm Radio Mg. Go., Chicago, U.S.A., 1.2000 each earpices light headband complete with lead and Igranic jack plug, with each and Igranic jack plug,

AIRSCREW ANTIGER CONTROLS, 44Ω resistance, suitable for train sets and chargers, 4/9 ea.

TERMINAL BLOCK, 20-way, 1/6 ea.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; £5 add 2/unless otherwise stated. Mini-mum C.O.D. fee and postage 2/3.

MAIL ORDER ONLY

main's TRANSFORMERS 1-may Mounting Type. MT21. attrime to the second s

The start of the maintent winning.
 The start of the start

VOLUME CONTROLS WIREWOUND CONTROLS 5Ω, 200Ω, 2ΚΩ, 5ΚΩ, 10ΚΩ, 10ΚΩ Double, 20ΚΩ, 25ΚΩ, 50ΚΩ, 30ΚΩ. All 2/4 each.

COLVERN CLR901, 1,000 Ω, 1/9 each COLVERN SLIDER TYPE CLR801, $3K\Omega$ and $5K\Omega$ Double Unit, 1/9 each; $20K\Omega$, 20Ω , 1/3 each.

CONTROLS WITH DOUBLE-POLE SWITCH

EX-GOVT. CONTROLS, ALL CAR-BON TRACK

BON TRACK 500Ω, 600Ω, 1,500Ω Double type, 2KΩ, 5KΩ, 10KΩ, 20KΩ, 25KΩ 50KΩ, 200KΩ, 10KΩ, 4 MegΩ 4 MegΩ, 1 MegΩ, 2 MegΩ, 25KΩ Double type, 50KΩ Double type, All 1/2 each.

VOLUME CONTROLS SINGLE-POLE.

VOLUME CONTRACT SALE SWITCH 500 D, Wirewound, 2/10 each. 5K R, 10K R, 100K R, † Meg R, 1 Meg R Log, † Meg R, 1 Meg R 1 Meg R Log, 2 Meg R, All 3/9 each,

STANDARD CONTROLS (LESS SWITCH) 50KQ, 1 MegQ, 1 MegQ. All 2/6

Special Purpose VALVES

CV509	7/6	VU111	3/6
VR54	2/6	9001	6/3
707	8/6	VU39	8/6
V868	41-	VR65.A	
6G6G	6/6	956	3/6
9004	6/3	9003	6/9
VR136	71-	2X2	5/6
VR66	3/9	VR65	3/9
VU120A	3/6	6887	8/-
9002	6/3	1A5GT	
VR53	7/6	220VSG	6/9
VR91	6/-	931A	6/9
807	8/-	2A7	6/-
5Z3	8/6	6A3	6/9
955	4/-	7475	4/9
TT11	6/6	19	6/-
VR116	4/-	26	6/-
VR56	71-	27	ě/-
954	21-	30	6/-
CV71	ĩ/-	36	6/-
VR137	5/-	84	6/-
VR55	7/3	6L5	6/-
68A7	9/-	2A5	
ATP4	6/9	CV287	6/-
,daa x	010	014011.11	01-
YAXLEY SW	TTCH	ES.	

2 bank (1 bank 3P 2-way, 1 bank,

YAXLEY SWITCHES. 2 bank (1) bank 3P 2-way, 1 bank, IP, 3-way) 1/6 ea. 1 bank 2 pole 5 way, 1/6 ea. 1 bank 4 pole 1 way, 1/8 ea. 2 bank 4 pole 3 way, 1/8 ea. 2 bank 4 pole 3 way, 1/8 ea. 1 bank awitche 2 pole 2 way and 2 pole 1 way. 1/8 ea. 1 bank 3 pole 4 way, 1/8 ea. 1 bank 3 pole 4 way, 1/8 ea. 3 bank 3 pole 3 way, 1/8 ea. 3 pole 1 way. 3 bank 3 pole 3 way, 1/8 ea. 1 pole 6 way, 1/8. 2 pole 2 way, 1/8. 2 pole 4 way, 1/8. 3 bank 4 pole 3 way, 1/8. 5 LEEVING. 4 mm. Permanoid

SLEEVING. 4 mm. Permanoid 4d. yd.

CONCORDIA BELL TRANSFORMER, Bakelite case. 8 v. 1 amp., with taps at 3 v. and 5 v., complete with fuses, 7/6 ea.

HYDROMETERS by Exide Canada, complete in wood case, 7/6 ea. BURGEES MICRO SWITCH, inter-rupter type, Ref. 5C/1910, 3/6 ea.

DIAL BULBS. 6.5 v., .15 a. MES, 15 mm. Ball, 6/6 doz.

VINCES CHAMBERS, VICTORIA

ALPHA $\star \star \star$ -

OUR CATALOGUE IS A MUST EVERY CONSTRUCTOR - SEND YOURS TODAY MUST FOR

HAND MICROPHONE by "REGENT," complete with screened lead and plug-Crystal insert, nickel chrome plated head, listed at 2 gns. Our price, 21/- each.

RECEIVER 1132A

Contains EK32; 4 EF39; 6H6; 6J5; 3 SP61; P61 in good condition. Fitted with tuning meter. Slow-motion drive calibrated dial complete with circuit diagram. 49/6 each. Carriage and packing 7/6.

ENGRAVED KNOBS.

Control Knobs, clearly engraved in gold. Size "A" diameter lin.; Size "B" diameter lin. Both in two colours, Walnut or Cream. Inscriptions available: RADIO : "Volume," "Vol./On/Off," "Wavechange," "On/Off," "Tuning," "SML Gram.," "Radiogram.," "Tone." TELEVISION : "Contrast," "Brilliance," "Brilliance On/Off" "Focus," "Brightness."

AMPLIFIER : " Treble," " Bass " (Plus any above).

TAPE RECORDER: Record/Play. Prices: Size"A,"1/6; "B,"1/2. Plain knobs can be supplied in either size, 1/- each and 8d. each respectively.

Goodmans Heavy Duty 15 Ω **12in. SPEAKER** £5 5 0 each.

THE "EKE" QUALITY 3-WATT AMPLIFIER VALVES 6B8G, 6V6GT, 6X5GT, Neg. feedback (voltage and current). Controlled tone and volume. Dual input network for modern crystal or HIFI magnetic. Less than 1% total 2nd and 3rd Harmonic distortion at 3 watts output from 1,000 C.P.S.

1,250 Ω , 9d. ea. 1,250 Ω , 9d. ea. 5,000 Ω , 1/- ea. 2,000 Ω , 1/- ea. 20 WATT CLIP IN TYPE 1,491 Ω. 1/6 ea. 5 WATT WIRE WOUND. 4000 1.0000 8000 HEATER TRANSFORMERS by RELYANCE

SURPLUS GEAR We have small quantifies of equip-ment which has been removed from Ex-Government surplus gear. It would not pay us to advertise these ltems so we offer them in parcels at 10/- each. Each parcel contains Resistors, Condensers, Tags, Vol. Controls, Transformers, etc., etc.

WE CAN SUPPLY COMPONENTS

WE CAN SUPPLY COMPONENTS FOR: "VIEW MASTER" "SOUND MASTER" PRACTICAL T.V. "SIMPLEX," ETC., ETC.

PIC., PAC. JA-METRE SUPERHET 10-Valve 14-metre Superhet. Ideal for T.V. conversion. I.F. 12 MEGS. Band width 4 MEGS. Co-Axial input and output. Mazda valves with 6.3 v. Filaments, 55/- each. Carriage 5/6.

PLEASE QUOTE

"DEPT. W.W."

REALLY LOW HUM LEVEL AND FREQUENCY RESPONSE. AND EVEN Complete in every detail. PRICE 79/6 ea., plus 2/- post.

A super job Carriage 2/6 each.

WIRELESS WORLD



SQUARE,

LEEDS

1.

LOUDSPEAKER UNITS.

LOUDSPEAKER UNITS. 31n. Plesser Bound type for portables, 12/9 each. Elso, 3jin. Square type speaker, 2 to 3Ω , 13/6 ea. Plesser 5in. unit, 13/6 en. Else 4in. unit with 5in. fitting, 13/6

Elac 61 in. unit, 14/6 ea. Lectrona and R. & A., Sin. units Lectrons and E. & A., Sin. units 16/6 ca. 101n. Plessey lightweight, 19/6 ca. 101n. Elac, 22/8. 101n. Goodmans, 29/6. Sin. Lectrons, with output trans-former, 20/-. Truvog NSI, 1, 21n, unit, 49/8. Truvog wafer speaker, 63/1n, 20/-. Plessey Sin. mains energised, 1,5000 field, 21/-6/1n. Unit with 1,5000 field, 17/6. 5/n. Goodmans PM unit, 14/9.

3,000 Ω	300 🖸	200Ω	175 0
15,000 Ω	9.000 0	225 Q	600 Ω
130 Ω	270 Ω	250 0	750 0
	All 1/-	each.	

IDATEX TRANSFORMERS by **RELYANCE** 220 v. Input 2 volt 5 amp., 4/6. 230 v. Input 2 volt 3.0 amp., 7/9. 230 v. Input 4 volt 1.5 amp., 5/-. 230 v. Input 6 volt 2.0 amp., 10/-. 230 v. Input 6 volt 2.0 amp., 10/-. 230 v. Input 6 3 volt 1.5 amp., 6/-. 250 v. Input 6.3 volt 1.5 amp., 6/-. 250 v. Input 6.3 volt 1.5 amp., 6/-. 250 v. Input 12 volt 1.5 amp., 6/-. 250 v. Input 6.3 volt 1.5 amp.,

++++

JUNE, 1954 -

-MIDLAND INSTRUMENT CO.-

MIDLAND INSTRUMENT CO.
Interface Receivers of the second secon

Ettin hell, self-mergisteri, do Battery required, comprete trady for att, her, boxed, 12/6, post 1/2.
PLESEEY A.C. MAINS, SHADED POLE WITTORS, 200/250.v., as used on the 3-speed gram. units, sites 3in. x3in. 181 k36/-. Our price, new, boxed, 12/6, post 1/3.
SELENUUM RECTIFIERS, full-wave bridge, 12 v. 4 amps., A.C input 16 v., new, output 4-8-12-16-20 v. at 4 amps., new, boxed, 12/6, post 1/3.
CRYSTAL SET COLLS, high gain dual range med. and 1.w., complete with circuit for a crystalset, 2/6, post 4.4. Wariable condensers, 0005 mfd. bakelite dielectric, with pointer knob, 3/6, post 4.4.
Ware-change switches, 6d., post 3d. Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
Wave-change switches, 6d., post 3d.
Circ pluge and sockets, 4 sets 2/-, post 3d.
BOSTIK CEMENT, 4-b. tubed, 1/3, post 7d.
THORAT MICEOPHONES, cartons of 2 mikes, 1/6, post 4d.
May other bargains ; send 3d, with SA.E. for current lists.
MiDLAND INSTRUMENTCO., MOORPOOL CIRCLE, BIRMINGHAM, 17

MIDLAND INSTRUMENT CO., MOORPOOL CIRCLE, BIRMINGHAM, 17

Tel. : HAR 138_

A new edition of a valuable textbook

Handbook of Industrial Electroplating

By E. A. Ollard, A.R.C.S., F.R.I.C., F.I.M., and E. B. Smith. 2nd Edition. Facts, figures and formulae for all who design, erect, maintain or operate electrodeposition plant and for laboratory workers who deal with plating solutions. The second edition has been considerably enlarged and includes new sections on water and drainage, purification of solutions, storage and handling of chemicals and plating-shop costing.

 $8\frac{3}{2}$ " \times $5\frac{1}{2}$ ". 365 pages. 122 illustrations. 68 tables.

Now ready 30s. net. By Post 31s. 2d.

Obtainable from booksellers or from

Dorset House, Stamford Street, London, S.E.1 *************

TELETRON SUPER INDUCTOR COILS **CONVERT YOUR RADIO** RADIO COVENTRY INTO A RADIOGRAM 0 WITH MINIATURE 189. DUNSTABLE ROAD, LUTON DUST CORES WITH OUR ELECTRIC Tel: Luton 2677 Type HAX. RF. Transformer, Triple wound for Xtal diedee. RECORD PLAYER **COMPONENT SPECIALISTS SINCE 1925** Extensively used as Radi "Head" for Recording an Quality amplifiers. 3/- each. Radio All B.V.A. and Tungsram Valves in Stock. EDDYSTONE JUST PLUG IN. Famous "STUDIOGRAM" Port-Port-EDDÝSTONE COMMUNICATION SETS AND COMPONENTS Short Wave Components Catalogue 1/-, plus 3d. postage. We are preparing an entirely new Components Catalogue 1954, which will be interesting and helpful, ready shortly. Price 1/-. Our No. 1 and No. 2 Circuits, 5 Valve Superhet and 4 Watt Amplifier, 1/-, plus postage. Special quotations on kits of parts or large orders. 113 able gramophone record player. No winding. Connect leads to radio Free from overlap SENT FOR DUAL WAVE TRF. COILS 18/6 DEP. Type T&F.A/HF. and T&F.A/D. Tuned anode with reaction. Ac.Pri. Windings with rising characteristic. Pre-aligned. 7/- pair. 8/Het. Range for 5. M. and L.W. 6/- pair. HT's filter, etc. Stamp for data. TELETRON utilise allthe features you expect from a good BF. Coil. pickup circuit and play records through Radio. Adjust by volume control. Plays 10 and 12 inch records at three adjustable speeds, complete with two sapphire needles, which are almost a permanency. Size 13×12 needles, which are almost a permanency. Bize 13×12 ×6. Balance 20/- monthly. A/C only, all voltage model. Cash 211/18/6, carr. 3/6. LISTS. TERMS. Headquarter and General Supplies Ltd. (Dept. W1W) 196/200 Goldharbour Lase, Longhboro June. London, S.E.5 Open all Sat. 1 p.m. Wed. THE TELETRON CO. 266, Nightingale Road, London, N.9. Trade enquiries to sole distributor: 59, Kendal Avenue, N.18. SAM MOZER

AMPLIFIERS

MODEL FC/1. A 31 wait Amplifier. Valves employed EF91, 6V6/G and 5Z4 Con-trols; volume, on/off and tone. Output transformer to a 3 or 15 ohm L/8. Input via to-axial lead. Size of chassis: 9in.long \times 5in.wide \times 5in.high. Price £5, plus 3/6 arr, pkg, and ins.

MODEL FC/2. A push-pull Amplifier. Valves (2) EF91; (2) 6V6/G; (1) 6SN7 and (1) 574. Optrols; volume on/off, treble and bass. Output transformer matched to 3 or 15 ohm. L/S. Input yia co-askillead. Size of chassis: 12in. long x 6in. wide x 5in. high. Price £7/5/- plus 5/- carr., pkg. and ins. THE RECORD REPRODUCER. Valves employed, 6V6, 6X4/5 and SP61. Con-trols; volume, on/off, treble and bass. Output transformer to 3 ohm. L/S. Price E2/1916, bus2/d carr., pkg. and lns.


11 GUNNERBURY LANE, ACTON, W.3. Telephone : ACOrn 5027

ableto supply tape recording/playback amplifiers, both in kit and ready-bullt form, also all your requirements for tape desks, tape, spools, microphones (hand and stand) Cablinets (Console, Table and Portable) and record storage containers.

TRADE ONLY SUPPLIED

V.E.S. WHOLESALE SERVICES LTD.

MODEL FC/1.

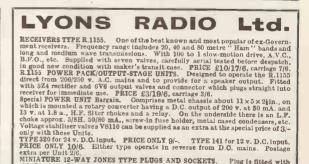

extra per Unit 2/0. MINIATURE 12: WAY JONES TYPE PLUGS AND SOCKETS. Plug is fitted with side brackets, 1 in. centres, and is approx. 1 in. × in. Socket is cased for cable fixing, and its size is approx. 1 in. × 1 in. × in. PRICE 3/- per pair, post 9d.

3 GOLDHAWK ROAD, (Dept. M.W.) SHEPHERD'S BUSH, LONDON, W.12 Telephone : Shepherd's Bush 1729



Edm. 7707

COMMUNICATIONS RECEIVER R1155. The famous ex-Bomber Command Receiver known the world over to be supreme in its class. Covers 5 wave ranges 18.5-7.5 Mc/s, 7.5-3.0 Mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s, and is easily and simply adapted for normal mains use, full details being supplied. Aerial tested before despatch. These are IN EXCELLENT CONDITION IN MAKER'S ORIGINAL TRANSIT CASES, ONLY £9/19/6. A few of the RII55N model can also be supplied. This is the latest version which covers the Trawler Bands, and in addition is fitted with ultra slow motion tuning. Used, but tested working before despatch. ONLY £17/19/6. A factory made Power Pack, Output Stage and Speaker, contained in a black crackled cabinet to match the receiver, can be supplied at ONLY £5/10/-. Operates receiver immediately. DEDUCT 10/- IF PURCHASING RECEIVER AND POWER PACK TOGETHER. Bomber Command Receiver known the world over to be supreme

PACK TOGETHER.

Please add carriage costs of 10/6 for receiver, and 3/- for power pack METERS

F.S.D.	SIZE AND TYPE	PRICE
l milliamp	D.C. 21 in. Flush square	. 15/-
1	D.C. 21 in. Flush circular	. 22/6
	D.C. 21/in, Desk type	
5	D.C. 2in. Flush square	
100	D.C. 21 in. Flush circular	
150	D.C. 2in. Flush square	
500	D.C. 24in. Flush circular	
500	thermo 2in. Flush square	. 5/-
500	thermo 2in. Proj. circular	5/-
20 amps	D.C. 2in. Proj. circular	. 7/6
40 amps	D.C. 2in. Proj. circular	. 7/6
	D.C. Car type moving iron	
15 volts	A.C. 2+in. Flush, circ., mov. iron	
	leand New in Maker's Cartons	

100 MICROAMPS METERS. 24in. circular flush mounting. Widely calibrated scale of 15 divisions marked "yards" which can be rewritten to suit requirements. These movements are almost unobtainable to-day and being BRAND NEW IN MAKER'S CARTONS are a snip at ONLY 42/6.

POWER UNIT TYPE 3. Made for use with the R.1132A, this is a standard rack mounting job to match the receiver, and is for 200/250 v. 50-cycle mains with outputs of 250 v. D.C. 100 mA., and 6.3 v. 4 amp. Fitted with H.T. current meter and voltmeter this is a first-class unit, and can be used for a varlety of receivers. Used, but tested working before despatch. ONLY 90/- (carriage, etc., 5/-). Connecting Cable with Jones Plugs for receiver and power unit 10/c. etc., 5/-). Conne power unit, 10/-.

TRI196 TRANSMITTER SECTION. In perfect condition, less valves. ONLY 12/6 (postage, etc., 2/6).

AVO MODEL 40 UNIVERSAL TEST METERS. Com-pletely self-contained, and provides 40 ranges of A.C./D.C. current, voltage, and resistance. Have had some use but every instrument has been thoroughly checked and tested and is GUARANTEED IN PERFECT WORKING ORDER. ONLY £9/19/6.

OSMOR H.O. COIL PACK. The 3 wave superhet pack recommended for the TRI196 Receiver conversion. ONLY 48/~ 1196 conversion data supplied with coil pack, or separately I/-. 500 KCS. CRYSTALS. Standard 2-pin mounting. equipment and perfect. ONLY 15/- (postage, etc., 1/-). Ex. new

VACUUM PUMPS. For Handymen and Model Makers. Ex-R.A.F. Type B3-Mk. III, made by Romec. BRAND NEW IN MAKER'S CARTONS, ONLY 22/6 (post 2/-).

TRANSFORMERS, FILAMENT. 6.3 v. 2 a., 7/6 ; 6.3 v. 3 a., 10/6 (postage 1/-).

TRANSFORMERS, EHT. Upright mounting. EHT for VCR97 Tube 2,500 v. 5 mA. 2 v. -0-2 v. 1.1 a., 2 v.-0-2 v.

2 a., 37/6. EHT 5,500 v. 5 mA., 2 v. 1 a., 72/6. EHT 7,000 v. 5 mA., 2 v. 1 a., 82/6. EHT 7,000 v. 5 mA., 4 v. 1 a., 82/6. Please add 2/- per transformer postage.

ROTARY POWER UNIT TYPE 104. Input 12 v., Output 230 v. 60 mA., and 6.3 v. 2.5 a., Fully filtered and smoothed, and noise suppressed. Ideal for car radio, etc. ONLY 15/- (postage etc.,2/6). AMERICAN 12 v. DYNAMOTORS. Output 255 v. 60 mA. ONLY 22/6

METAL RECTIFIERS. Selenium full wave bridge 6 or 12 volts; I amp., 7/6; 2 amp., 11/3; 3 amp., 12/6; 4 amp., 15/-.

Cash with order please, and print name and address clearly. Amounts given for carriage refer to inland only.

CORPORATION **U.E.I.** Radio Corner, 138, Gray's Inn Road, London, W.C.I.

Phone : TERMINUS 7937.

(Open until I p.m. Saturdays. We are 2 mln. from High Holborn (Chancery Lane Station) and 5 min. by bus from King's Cross.)



Sprague Condensers. .1 mfd., .01 mfd., .02 mfd., .05 mfd., .005 mfd., Wire Ends, 9d. esch. Burgess Microswitches, universal type change over, size 2in. x ≹in. x

in., 2/6 each. Desk Type 0-1 M/a Moving Coil Meters. 2½in. scale reading, 25/-each, brand new. 0-15 volt A.C. meters 2½in. scale reading, brand new, 9/6 each

Nitrogol Condensers. 4 mfd. 4,000 volt working, size 9in. x 5in. x 34in., brand new, 22/6 each. Paper Mansbridge condensers, 4 mfd. 2,000 volt working. Size : 5in. x 5in. x 24in., 7/6 each. A.C. Mains Transformers. 230 volt 50 cycle Input. Output 1,500

volts 300 Main, Size 74 in. x 6in. x 6in, 69 each. American Rotary Transformers. 12 volts D.C. input. Output 255 volt at 65 M/a. Size 44 in. x 24 in. For Car Radio Operation. Also suitable for running Electric Shavers from your car supply, 22/6 each. Brand new.

Muirhead Switches. Precision built. 8 pole 2 way. Key switch

Muirhead Switches. Precision built. B pole 2 way. Key switch action, brand new, boxed, heavy contacts, 46 each. Ceramic Transmitter Switches. With extra heavy duty silver-plated contacts, 3 bank single pole 6 way, spacing between contacts lin. spacing between wafers 1 jun, and 5 in., 9/6 each. Mains Isolation Transformers for industrial purposes. 230 volt A.C. 50 cycles input. Output 230 volt 50 cycles 1,000 watts, supplied complete in heavy duty metal case, size 13 in. x 10 jin. x 8 in. Price f6/10/. £6/10/-

E6/10/-. Smoothing Chokes. Heavy duty. 20 Henry 300 M/a., 2,000 volts insulation test. Admiralty rating will pass 500 M/a., 17/6 each. Mains Transformers. 230 volt Primary, Secondary 500 x 500 at 170 M/a., 4 volt 4 amp. C.T. W.D. rating insulation test 3,000 volts. Ample space for additional 6.3 winding if required, 22/6. H.R.O. 6 volt Vibrator Power Packs. Output 165 volt 80 M/a. 6.3 volt at 3 amps., 6 x 5 rectifier. Choke condensers smoothed, complete in self-contained crackle cabinet size 7in. x 7 jin. x 6in., battery leads with croc. clips supplied. Brand new, 29/6. Ceramic Switches. Standard spacing, 4 pole 3 way 3 bank. Special price 6/6 each. Brand new and boxed.

Smoothing Chokes. Ex-W.D. 15 Henry at 275 M/a. Ministry rating, resistance 125 ohms, 10/6 each. Meter Switches. Standard Yarley Wafer Type, 8 bank, single pole 9 way, 11 way or 12 way. Size 2‡in, diameter, switch length 5‡in, plus spindle, 2‡in, Price 7/6 each. Microamp Meters. 0-100 Microamps, 2‡in, Flush Panel Mounting scaled 0-1,500 yards, Brand new and boxed, 42/6 each. Rotary Convertors. 24 volt D.C. input. Output 230 volt A.C. mains 50 cycles at 100 watts, 92/6 each, ditto 12 volt input, 102/6. Size 2in, x in, 3/6 pair. Chokes. Heavy Duty Ex-W.D. 20 Henry 120 M/a., size 3in, x 4in, x 2‡in, 10/6 each. Power Packs, Type S441, B, Input voltage 200/250, 50 cycles A.C. Outputs 300 volts 200 mA, L.T. 12 Volt 3 Amp, also separate 12 volt 1 amp, supply operating built in Londex overload relay, with 5U4G valve. Supplied in grey mottled cabinet size 13±in, x 7±in, x 6±in, 624 each.

Soft vare, supplied in grey noticed came is an isjan x r₂m, x Multi Way Switch Boxes, ex bomb release, fitted with 16 toggle switches, ideal for model control, brand new and boxed, 9/6 each. Swinging Chokes. Parmeko. 150 M/a. 4.2/20 Henry, size 3in. x 3in. x 34in. 7:6 each.

Ex Am, Switch Boxes. Moulded Bakelite. Totally enclosed. 3 Way 1/9 each, 5 Way 3/6 each. F24 Camera Control Boxes. Type 35 No. 20, Brand new, 27/6

each.

each. A.C. Mains Transformers, Ex-Admiralty, input voltage 100/250 A.C. at 50 cycles, Outputs 670 x 670 volt at 200 M/a., 6.3 volt 4 amp., 5 volt 3 amp. 49/6 each. P.O. Automatic Telephone Circuit Diallers, Type I, 25 bank, Type 2, 50 bank, 12/6 each. These precision built units have hundreds of potential uses each one being fitted with clockwork control motor. 2 Volt Accumulators, Brand New. Capacity 3 Amp. Hours, size 4 Jir, x 14in, 34 each.

A voit Accumulators, brand New, Capacity 3 Amp. Hours, size 4jir. x 1 jin. x 1 jin. 3 6 each. R.1155 2 Speed Slow Motion Motor Drives. "A" type with double knots, 4/- each. Amplifier Cabinets. Ex-Well Known Manufacturer, sloping desk type, well constructed with ventilated cover, chassis drilled for 5, No holders, size 13in. x 9in. x 7in. Sprayed attractive yellow. 15/6 each.

each. R.1155 Receivers, used models, aerial tested, and in perfect working order, complete with valves. £7/19% each. A.C. Voltmeters. BSI Grade, reading 0-300 volts at 50 cycles, 3½in. flush panel mounting, supplied complete with leads and case. 39/6

each.


Uniselector Switches. 4 Bank double wiper 32/6 each ; ditto 8 Bank 45/- each.

Bank 49/- each. Handsets. Standard P.O. telephone type 12/6 each. Ceramic Switches. 3 pole 4 way 4 bank, standard size wafer, 10/6

each. Please print your name and address clearly, also include postage or carriage on all items.

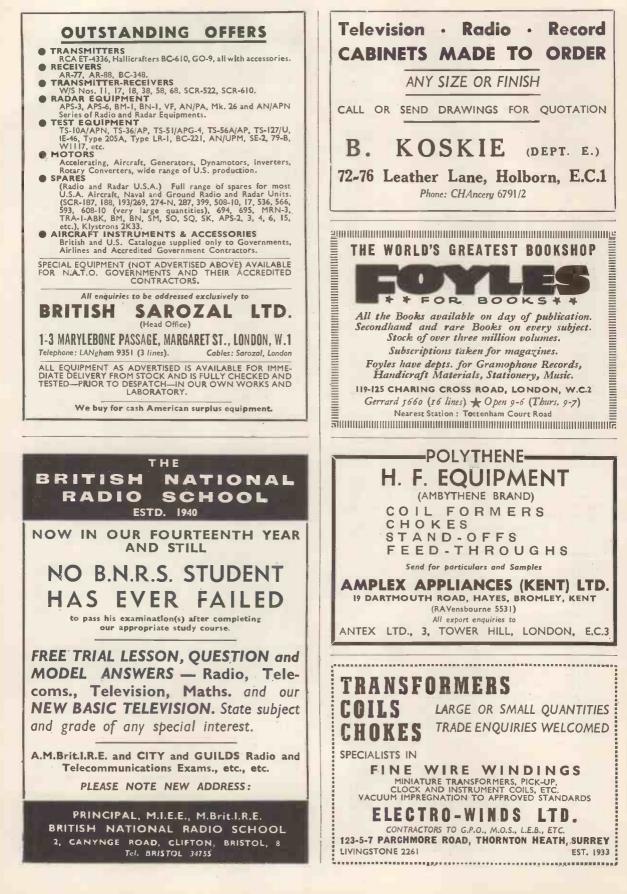Hours of Business : 9 a.m.-6 p.m., excluding Thursday I p.m. Open all day Saturday





Wireless World Classified Advertisements

Rate 7/- for 2 lines or less and 3/6 for every additional line or part thereof, average lines 6 words. Box Number: 2 words plus 1/- (Address replier: Box 0000 c/6 wWireless World" Dorset House, Stamford St., London, S.E.1.) Trade diacount details available on application. Press Day: July 1954 issue, Monday, May 31st. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus Readers are warned that Government surplus components and valves which may be offered for sale through our columns carry no manu-facturers' guarantee : Many of these items will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot under-take to deal with now complaints regarding any take to deal with any complaints regarding any such items purchased.

NEW RECEIVERS AND AMPLIFIERS 12 watt high quality amplifiers, bass and treble boost; £12/15; Iists.-Broadcast & Acoustic Equipment Co., Ltd., Tombiand, Norwich.

MIDGET sensitive T.R.F. receiver ("Wireless World." April 1954), special coils. etc., available (Dept, WW).-Osmor Radio Products, Ltd., 418, Brighton Rd., South Croydon, Surrey, Cro. 5148-9.

MULTIAMSON amplifiers built to author's specification; £29/10; capacity available for wiring and constructional work; write for quotation.—A. J. J., 50, Camrose Ave., Edg-ware, Middx.

A LL types of audio equipment designed and built to order, tone compensation units. Williamsons, ultra-linear, pre-amps, electronic mixers, and all amplifiers up to 1kw. Extended payments available above £20.-Bernard J. Brown, 33. Goldhawk Rd., London, W.12. [0024 Brown, 33, Goldhawk Rd., London, W.12, (0024 C.J.R. ELECTRICIAL & ELECTRICINO DE-VELOPMENT, Ltd., Bickford Rd., Witton, Birmingham, 6 (Eas. 0435), the Midlands specialist manufacturers of high fidelity sound reproduction equipment for the world-famous Williamson amplifier and associated accessories, including tone control stages, loudspeaker crossover units, distortionless contrast ex-penders and radio feeders; send for details and prices. [015]

G.E.C. BRT400B receiver; £90.-Box 4638.

[2793] HRO Rx's and coils in stock, also AR88, BC349R, CR100, etc.—Requirements please to R. T. & I. Service, 250, Grove Green Rd., London, E.11. Ley. 4986. R.F. Units, types 26 @ 37/6, 25 @ 17/6, 24 @ 12/6, brand new in original cartons. -E,W.S. Co., 69. Church Rd., Moseley, Bir-mingham. 2877

LOVELY walnut console cabinet, 41in tall ZoinX18in, with 9-valve feeder unit and Goodman Audiom 150 12in speaker, Willamson amplifier.—Ormerod, 10, Arnside Rd., South-port, Lancs. [284]

 amplifier.—Orinors.
 L2044

 port, Lancs.
 RECEIVERS. AMPLIFIERS—SURPLUS AND

 SECONDHAND WANTED
 receiver

 CHALLICRAFTER communication receiver
 receiver

 Model S.27 in any condition.—Box 5034.
 [2862]


[2862 LOUDSPEAKERS-SURPLUS AND SECONDAAND 3 G.E.O. 42in horn speakers with pressure units and line transformers in very good ondition; £5 each, or offers.-Box 5149, [2893 6 VITAVOX cass "B" Type units; 6 46in Monoplanor Horns Car/Mtg., perfect. £50. Broster, Whitburn Street, Bridgnorth. [2853 ENERGIZED loudspeaker units, 6v d.c. Voigt, Hartley Turner, E.M.I. 230v a.c. Magnavox B:T.H.; cheap; offers.-Box 4886. [2828 ENERGIZED AND

B.T.H.; cneap; offers.—Box 4886. [2828 TEST EQUIPMENT—SURPLUS AND SECONDAND SIGNAL generator, as new, Taylor; would exchange for Avo No. 7 universal, similar condition.—76. The Triangle, Malmesbury, Wilts. Tel. 3208. [2838

Wilts. Tel. 3208. SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your engulries are invited.—Requirements to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986 [0056]

METERS WANTED WE urgently require meters of all types, any quantity large or small; prompt cash or offer by return. ANDERS Electronics, Ltd., 91, Hampstead Rd.. London, N.W.1. Euston 1639. [2778

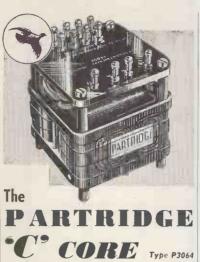New DYNAMOS, MOTORS, ETC. BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C. any mains voltage; also larger types special transformers, chokes, test gear, in-terior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. [0112



p.p. TRANSFORMER

for use in equipment reproducing

Full Audio Frequency Range

with lowest Distortion

- "C" TYPE CORE, grain orientated strip wound.
- POWER RATING : 20 watts for less than 1% distortion.
- LEAKAGE INDUCTANCE : less than 8 mH.
- SELF CAPACITY: 500 pF per half primary.

Size: $2\frac{1}{8}$ in. $\times 2\frac{1}{8}$ in. $\times 3\frac{1}{8}$ in. high. Weight: 21 lbs.

Full advantage is taken in the PARTRIDGE Type P3064 Out-put Transformer of the properties of grain orientated strip wound cores, and performance figures are impressive for such compact dimensions and weight.

Its characteristics permit con-siderable negative feedback being taken from the secondary to a point three or four stages back.

DATA SHEET NO. 5 free on request



NEW DYNAMOS. MOTORS. ETC. ATTERNATORS 230/L/50. 400VA. self-energing is a special television midel same price; voltage regular 30, extra. A.F. No. 2A 1.2hp peid same price; voltage regular 30, extra. A.F. No. 2A 1.2hp peid same price; voltage regular 30, extra. A.F. No. 2A 1.2hp peid same price; voltage regular 30, extra. A.F. No. 2A 1.2hp peid same price; voltage regular 30, extra. A.F. No. 2A 1.2hp peid same price; voltage regular 30, extra. A.F. No. 2A 1.2hp peid same price; voltage regular 30, extra. A.F. No. 2A 1.2hp peid same price; voltage regular 30, extra 10, extr 10, extr 10, extra 10, extr 10, extra 10, extra 10, e

VUTOR: Tel. 253. [0039] DYNAMOS, MOTORS, ETC.-SURPLUS AND CONVERTERS, TOTATY 1007 d.c. to 2307 a.c. 40007, E.D.C. 367 d.c. to 40007 d.c. 125ma, vibrator 507 d.c. to 2407 d.c. 20007; cheap; ofters.-Box 4887

offers.—Box 4887 [2252] RCTARY Converters, guaranteed, 80-3000 watts, 200/230 volts D.C. in/ 230 volts A.C. out; £8-£35.—H. J. Mugdan, Ltd., 23, Brook Mews North, W.2. Pad. 2967 [2270] NEW GRAMOPHONE AND SOUND EQUIPMENT FERROGRAPH magnetic tape recorder, 76gns.

FERCOGRAPH magnetic transformer of the second secon


SOUND DISCS (SUPPLIES), I.td., 178. Bispam Rd., Southport, Lancs. Tel. 88155
 Bytam Rd., Southport, Lancs. Tel. 88155
 Bytam Rd., Southport, Lancs. Tel. 88155
 Bytan Rd., Southport, Southpark,


140



out transformer. "RENEWBAT." Battery desulphator and conditioner 1/9, post 3d. Car size 3/-, post 4d.

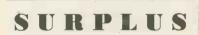CHAMPION PRODUCTS 43 Uplands Way, LONDON, N.21. Phone LAB 4457



- TRYLON LATTICE LADDER TOWERS 50ft. high triangular section, 12in. wide Highest quality, with all hardware. New, in Highest quality, wi original cases. £40.
- TRIPLE DIVERSITY RECEIVERS. 1.5 to 30 Mc/s. Built-in loudspeaker and power supply. Fully metered. Precision H.F., L.F. and B.F. Oscillators. Variable gain and selectivity. Band pass and tone facilities. Full details and photo available.
- 100 WATT BROADCASTING TRANS MITTERS. Made by Woden. Self-contained in 4ft. 6ln, cabinet. Input 190/250 v. A.C. Output 250 watts Triode H.T. 2,200 v. Fully valved, £22/10/-.
- RACKS. 5ft. 6in. high (A), channel iron sides, drilled and tapped shock base de Luxe $\pounds 3/10^{\prime}$. (B) as A only 3ft. 6in. high, 40/-, (C) 5ft. 6in. high, angle iron sides, plain base. RACKS.
- LARGE VALVES. 4212 (250 watts), GU-50, VT-26C, DET-12, VU-29, 830B.
- R.C.A. HIGH POWER LOUD SPEAKERS. 25 watts. Finest quality waterproof construc-tion with output transformer. Can be heard a mile away. £14.
- TRANSMITTING COMPONENTS. Transformers, chokes, condensers, large variety up to 20,000 volts.
- INSULATORS Large quantities of over 50 different types.

WANTED. Technical Manuals or Data of any American or British Service equipment.

Many other items too numerous to mention-Send your requirements. Lists available All packing and shipping facilities.



NEW CRAMOPHONE AND SOUND <u>CUIPMENT</u> CINE-VOX disc recording equipments, type C73 for high-equality recordings from exist-ing microphone equipment; price from 28gns; also available as a complete channel inclusive of mic., amplifier and playback equipment, at Yogns; type C7, for highest quality professional requirements—recorder mechanism at 48gns, or complete channel at 110gns; demonstrations arranged in London. FLEASE write for details to K.T.S., Ltd., 60. Aylward Rd., London, S.W.20 (Liberty 2426). Callers by, appointment only. DISC recording; Presto K.3 portable, com-plets, 255; Presto K.10 portable, complete, as price, 255; Presto K.2 portable, complete, as price, 255; Presto K.1 portable, complete, and with spires, valves, etc.; k110 the 2; DISC recording; Presto K.2 portable, complete, as price, 255; Presto K.1 portable, complete, and with spires, valves, etc.; k100 the 2; DISC recording; Diresto, K.1 portable, complete, as price and with spires, valves, etc.; k100 the 2; DISC more than the disc recorder, model 2300H, H complete microphone, disc, etc., perfect ondition; offers,—1801, London Rd., Leigh-on-sea, Essex. TRANSMITING EQUIPMENT DISC PERSIZE THE CLE DURANT

Constituting in the second sec

Mariborough Yard, Archway, N.15. 10. [0187 NEW COMPONENTS CRYSTAL microphone inserts (Cosmocord Microphone inserts) (Cosmocord free.-Radio-Aid, Ltd. (Retail Dept.), 29. Market St. Walford. 2003 FLUORESCENT fittings. Special reduced price offer, 41 40w white stoved batten complete with ballast starter and tube, ready to plug in, 210/240y a.c. 39/6; these are neat compact fittings suitable for home and work-shop.-Malden Transformer Supplies, Malden Riy. Station, New Malden, Surrey. Mal. 2653 10036

Dug m, 210/240V a.c. 39/6; these are near compact fittings suitable for home and workshop.—Malden Transformer Supplies, Malden Rly. Station, New Malden, Surrey. Mal. 2655.
 COMPONENTS—SURPLUS AND
 ADIO CLEARANCE, Lid., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9183.
 ELECTROLYTICS, capacity voltage, size, type of mounting, price post paid; 400, 69, 11×31, 11, 250, 4256, 69, 11×21, 11, 22, 42, 420, 2759, 11, 22, 210, 42, 410, 42, 500, 1500, 167, 11×3, 110, 226; 20-40, 250, 126, 20, 2759, 11×2, 210, 250, 126, 20, 2759, 11×2, 210, 250, 126, 20, 2759, 11×2, 210, 250, 126, 20, 2759, 11×2, 210, 250, 126, 20, 2759, 11×2, 210, 250, 126, 20, 2759, 11×2, 210, 250, 126, 20, 2759, 11×2, 21, 2500, 11×3, 22, 450/5259, 11×3, 22, clip, 3/9; 20, 4500, 11×3, 22, clip, 2/9; 20, 4500, 11×2, 20, 150, 11×3, 22, clip, 3/9; 20, 4500, 11×3, 22, clip, 2/9; 20, 4500, 11×4, 24, clip, 2/1; 250, 12v, 11×32, 20, 150, 11×4, 20, 110, 20, 129, 11×52, 124, 24, 16, 350/4259, 11×4, 22, clip, 2/9; 20, 120, 11×4, 20, 119, 2/9; 20, 120, 11×4, 20, clip, 2/1; 250, 12v, 11×4, 22, clip, 2/2; 20, 12v, 11×2, 20,

Main's trans., 250-0-250v, 80ma, 6.3v, 2.5A. 6.3v, 0.6A, Pri. 0-210-230-250v, 12/- post paid. Main's trans., Pri. 200/250v, 12/- post paid. (Main's trans., Pri. 200/250v, sec., 305-0-350v, 80mA, 800v 5mA, 6.3v 4.2A 6.9v 0.4A, 2v 2A. (*) 1.1A, 5v 2.3A; these trans. have been taken from ex-Govt. equip.; some may have tag panels broken, but guaranteed O.K.; 13/- post paid ideal for scopes. RADIO CLEARANCE. Ltd.. 27. Tottenham Court Rd. London, W1. Tel. Museum 9188, 10015 Daid. MAINS



Solons save time, reduce costs, Solon soldering is always clean, reliable and simple. Five models, in voltage range 100-250; each with 6 feet Henley flexible. 65 watt; oval tapered or round pencil bits. 125 watt; oval tapered or round pencil bits. 240 watts; oval tapered bit.

Write for Folder Y.10



-THE MODERN BOOK CO.-BRITAIN'S LARGEST STOCKISTS **OF BRITISH and AMERICAN TECHNICAL BOOKS**

Electronic Organs by R. L. Eby. 40s. 0d,.

- Electronic Organs by R. L. Eby. 40s. 0d. Postage 9d. Television Engineers' Pocket Book edited by E. Molloy and J. P. Hawker. 10s. 6d. Postage 6d. The Radlo Amateur's Handbook : 1954, by "A.R.R.L." 30s. 0d. Postage 1s. TV Fault Finding : Data Book No. 5. 5s. 0d. Postage 3d. Handbook for Wireless Operators by the G.P.O. 3s. 0d. Postage 3d. Television Receiver Servicing : Vol. 1— Time Base Circuits by E. A. W. Spreadbury. 21s. 0d. Postage 9d.
- Time Base Circuits by E. A. W. Spreadbury. 21s. 0d. Postage 9d.
 Basic Mathematics for Radio Students by F. M. Colebrook. 10s. 6d. Postage 4d. Radio Control for Model Ships, Boats and Aircraft by F. C. Judd. 8s. 6d.
- Postage 4d.
- International Radio Tube Encyclopaedia by B. B. Babini. 42s. 0d. Postage Is. Radio Engineering by F. E. Terman. 50s. 0d.
- Postage Is. Electronic Gadgets for the Constructor by E. N. Bradley. 3s. 6d. Postage 3d. Radio Valve Data compiled by "Wireless World." 3s. 6d. Postage 3d. Electronics by A. T. Starr. 32s. 6d. Postage

Electrical Engineers' Reference Book edited by E. Molloy, 70s. 0d. Postage Is. Radio Designer's Handbook by F. Langford-Smith. 42s. 0d. Postage Is.



Phone: PADdington 4185. Open all day Saturday.



The keener and more discerning your ear, the more important it is that you should insist on hearing a Duode.

Compare Duode detail, Duode transients, the clear, clean Duode extreme top; hear the hard, true Duode bass, then listen for the missing items—no resonances, no harshness, no boom. In these positive and negative virtues lie the secrets of Duode power to give supreme, lasting pleasure.

For the owner of discriminating ears a Duode is the soundest possible long-term investment

If your dealer really knows anything about good sound he will know Duode. If you cannot obtain satisfaction, write to'us.

BARKER SOUND REPRODUCERS 3 Newman Yard, London, W.1




Get this FREE Book!

ENGINEERING **OPPORTUNITIES'** reveals how you can become technically qualified at home for a highly paid key-appointment in the vast Radio and Television Industry. In 144 pages of intensely interesting matter, it includes full details of our up-to-出 the-minute home study courses in all branches of TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency and General Wireless Courses. We definitely Guarantee

"NO PASS-NO FEE"

ENGINEERING OPPORTUNITIES

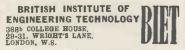If you're earning less than £15 a week this enlightening book is for you. Write for your copy today. It will be sent FREE and without obligation.



COMPONENTS-SURPLUS AND SECONDHAND SUPREME RADIO, 7465, Romford Rd., Manor Park, London, E.12, Tel, 111, 1260. Est. RADIO and television component bargains at the right price. EARTF rods, copper tube type, 18in long, our price 1/8 ea. STEEL chassis, ready punched. for superhet layout, 14in X6in X3in, amazing bargain at 2/6 ea.

STZE: Sin X4U/n X7in, weight 13/2/0, 25/- each plus 2/- carriage.
 Waltron'S Wilfer Wilfer Strokes 48, Stafford St., Wolverhampton. [OOID
 BENTLEY, Ltd., 38, Chalcot Rd., N.W.I.
 Condensers, 200vdc working, 0.5mid. 61, electrolytics, all all cass. 16X45X6mid 960v. 3/6, 6X45X6mid 960v. 3/7.
 Condensers, Condensers, 1/6, volume conrols, 50K, less switch, 1/6, not set.
 Soto ohm, 3/-; X-Govt, new semi-midget multi-ratio output transformer, 2/-; 550 ohm wire wound pre-set potentiometers. 1/6; volume conrols, 50K, less switch, 1/6, not set.
 Condensers, 600, 0005mid 4/- doz, 0.1mid 350v mica mould 6/- doz; ex-unit bargains: relay actuating gear train and contacts, 2/6; component assembly consisting of 5 condensers, 6 resistors and transformer, 2-2/-; ditto, but iron cored coli in enclosed former, easily rewound, transformer, several condensers, resistors and choke, 2/-; new wire would viterous resistors. 10%, 40, 70, 75, 90, 130, 150, 270, 500, 680, 900, 18K, 4/RK, 5KK, 6.9K, 7.5K, 15K, 20K, 35K, 43K, 4/RK, 5KK, 6.9K, 7.5K, 15K, 20K, 35K, 44K, 4/RK, 5KK, 10K, any size 2/-; wire holders, English 5-pin, moulded, 54, 21K, 22K, 55K, 44K, 4/RK, 54K, 69K, 7.5K, 15K, 20K, 35K, 44K, 4/RK, 54K, 69K, 7.5K, 15K, 20K, 35K, 900, 14K, 10K, any size 2/-; wire holders, English 5-pin, moulded, 54, 21K, 21K, 22K, 35K, 44K, 4/R, 54K, 987, 64, 75K, 15K, 20K, 35K, 900, 250, 156, 157, 7, V01110, 3/-; 200, 100, 400, 500, 250, 150, 170, 100, 400, 500, 250, 176, 100, 577, 7, 100, 400, 500, 250, 150

vide; s.a.e. for live no. WANTED, EXCHANCE, ETC. WantED, Wilcox Gay V.F.O. units in new or modified condition. McELROY-ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., London, W.6. Tel. Fulham [0194





Specialists in the manufacture of the HIGHEST OUALITY CHASSIS

> Model FC.38

RADIOGRAM

CHASSIS We have a comprehensive range of superb Chassis ranging from 8 valve superheterodyne to a 15 valve Band-spread receiver. The three most popular models, universally acclaimed are :--FC.38-8 valve-all-wave-Price £23/13/-

(inc. tax). RF.41-10

(mc. tax). RF.41-10 valve—all-wave—Price '£31/19/8 (inc. tax). EXP 125/A — 14 valve — all-wave — Price £48/19/5 (inc. tax).

RADIOGRAMS As introduced in March our "Special" Radio-cabineted receiver incorporates the magnificent FC.38 Chassis, the very latest 3 speed inter-mixing Record Changer and a High Flux 10in. P.M. Loudspeaker.



" Special " Radiogram Price 79 Gns.

(inc. tax).

TELEVISION

The TV.5 Range is available in many forms and incorporates all the most up-to-date improvements such as 5-chan-nel selector switching and aluminised flat faced tube and tinted filter.

★ PROVISION IS NOW MADE FOR A 13-CHANNEL ADAPTOR, WHICH WILL BE AVAILABLE AT A NOMINAL CHARGE WHEN REQUIRED.

The TV.5 Range really gives the BLACK AND WHITE PICTURE. the TRUE

- TV.5 14in. Chassis, £54/-/3 (inc. P.T.). TV.5 14in. Table Model, £61/19/- (inc. P.T.). TV.5 14in. Console, £72/9/- (inc, P.T.). TV.5 17in. Chassis, £64/15/11 (inc. P.T.). TV.5 17in. Console, £82/19/- (inc. P.T.).

*

SEE PAGE 62 FOR DETAILS OF OUR NEW AMPLIFIER

Our Showroom at the address shown below is open daily from 9 a.m. to 6 p.m. (Satur-days 5 p.m.) and we are always delighted to demonstrate any of our Models or supply any information regarding them. If unable to visit us please send for the specifications you may require you may require.





AMPLIFIERS A.C./D.C. 110-250. Output 4 Watts.

2UL41 in push-pull, UCH42 phase splitter and Ist amplifier, UAF42 mike stage. Size 9 x 4 x 4in. Ideal for Rec. Players, Baby Alarms, Tape Rec. and unlimited other uses. 90/-, pp. 3/-. Output Transformers to match, 16/6.



E.H.T. TRANS-FORMERS

5-6 Kv. with U22 Rect. 37/6, pp. 2/6.

TRANSFORMERS (tropicalised), 300-0-300, 200/250 v., 80 mA., 6.3 v. at 3 amp., 4 v. at 2 amp. 13/6, pp. 1/6

METAL RECTIFIERS. 280 v. 80 mA. H/W. 6/6, pp. 6d.

Hundreds of Bargains in TV & Radio Components. Send for list.

Jackson's Radio Supplies 163, Edgware Road, London, W.2



Tel. GUL 6077/8 Cab. "Shemanskee, London"

THE MAGNEGRAPH **RECORDING CO. LTD.** I, Hanway Place, London, W.I.

SPECIALISTS ONLY IN MAGNETIC RECORDING EQUIPMENT.

Send stamped addressed envelope for details of :-

- + HIRES
- * SALES
- REPAIRS *
- * DEVELOPMENT
- DESIGN \star
- * ACCESSORIES
- Telephone: Langham 2156

WANTED, EXCHANGE, ETC.

TS47AP, TS174, TS175/U, TS148 or TSX-4SE; analyser; BC221 freq. meters, TS69, and any U.S.A. test gear; Klysrons type 723/AB, 2K53 ZK39 ZK41; receiver, APR4 and units TN16 17-18-19; RCA AR88D, S27 and SX28s and S27CA; microwave equipment; highest offers given by return.-Ger. 8410. Universal Elec-tronics 27. Lisle St., Leicester Square, Lon-don, W.C.2.

WANTED, receivers A.P.R.4, also T.N. 16, 17, 18, 19, etc., and any radio test gear. LESLIE DIXON & Co., 214, Queenstown Rd, Battersea, S.W.8. Macaulay 2159. [0176

WANTED, R.C.A. transmitters, all types or any R.C.A. components, including chassis and metal work. Greyhound Rd., London, W.6. Tel. Fulham 1138/9. [0196]

WANTED. Tuning units. TN17, TN18, TN19, for R54/APR4: £50 each offered. Box

[0261 4963. WANTED, service sheet for receiver R103A. —Write E. W. Bonson, 70, Kensington Ave., Manor Park. E.12. [2887]

Ave., Manor Park, E.12. WANTED. G.E.C. Wobbulator; good price paid.—Reynoids, 48. Melford Rd., London, [2809]

WANTED. TCS/6 or TCS/12 transmitters in mint condition; also control boxes for in

MCELROY-ADAMS MFG. GROUP, Ltd. Greyhound Rd., London, W.6. Tel. Fu 1138/9. 46 Fulham [0195

WANTED. HRO colls, Rxs, etc., A.R.885. B53485, S275, etc.—Details to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley, 4966. [0163]

WANTED, set manufacturers' or ex-Govern-ment radio equipment, large or small quan-tities of valves, electrolytics, speakers, meters, also components. LOWE BROS., 5, Fitzroy St., London, W.1. Tel. Museum 4388. [2703

URGENTLY waited, manuals or instruction books, data, etc., on American or British army, Navy or Alr Force radio and electrical equipment.-Harris, 93, Wardour St., W.I. Tel. Gerrard 2504.

Works, Beavor Lane. Hammersmith, W.6. Riv. [0080]

ALTHAM RADIO Co. pay highest prices in Althe trade for all American equipment, in-Jersey House, Jersey St., Manchester, 4. Tel. [0228] Central 7364-5-6.

Central 7834-5-6. WANTED, R.C.A. speech amplifiers, type MI-11220, J or K, and aerial tuning units BC 935a.-Offers, stating quantity and price. to P.C.A. hadio, Office and Works, Beavor Lane. Hammersmith, W.6. Tel. Riv. 8006.

WANTED, good quality communication rxs... prices paid, established since 1937—willer's Radio, 538, Newport Court 1 min. from Leices-ter Sq. Tube. Tel. Ger. 4636. Call, write or send. Hours of business 10-6 p.m. Open all day Saturday.

WANTED, signal generators types 30, 31, 51, 53, 54, 56 and 101; also any American test eculoment with prefix TS or BC; American re-celvers types AR88, APR4 or similar.—Send price and details to Hatfield Instruments, Ltd., 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing (0037

0779/9857. [0037] WILL buy ART/13.747A or T47 type trans-mitter: R5/ARN7 radio compass receiver; BC348 receiver; ARO3 radio complete; R/7 receiver; BC312 and BC342 receivers; APN9 Loran transceiver; R39B Glidepath; 788C alti-meter receiver; IE52C scope; RA20 power units; T17 microphones; TS67 test sets.—Write H. J. Burke Co., 49, Washington Avenue, Little Ferry, N.J. [2843

VALVES 500 valves, type DET12 (VT62), for sale, 11/- each.—Pype Haves Radio, 606, Kingsbury Rd., Birmingham, 24. [2766] VALVES WANTED

VALVES WANTED A LL types valves wanted; state price and quantity available.—Box 4441. [2710 A LL types of valves required for cash; state quantity and condition.—Bentley, Ltd., 38, Chalcot Rd., N.W.1. Primrose 9090. [2715 60/_ paid for 783A/BS, 457-8135, also re-quantity.—Write/tel. Pype Hayes Radio, 606. Kingsbury Rd. Birmingham. 24. Erdington 4942. [2456]

CONTACT LENSES MODERN CONTACT LENS CENTRE, 7(J.1), Booklet sent. [021] CABINETS

L EWIS RADIO have the best selection and finest finish.—See page 151. [0224 WALNUT radiogram cabinets; details. Cabinetware, Ia. Heyes St., Blackburn. W Cabinetware, 1a. Heyes St., Black Str., WALNUT radiogram and television cabinets, soundly constructed; starmp for details.-R. Shaw 69. Fairlop Rd., Leytonstone, E.11. [2462] Most types of coil winding undertaken. Very quick deliveries, small or large quantities. Transformers, Chokes, Solenoids, Relay Coils, etc., wound on your own bobbins or formers for your own assembly. Impregnating (varnish) on all work done if required. Best quality material used. Single prototypes made to high standards, regulation and cool running, etc.

FOR CATHODE RAY TUBE FAILURES. Special low capacity secondary winding for Heater/Cathode shorts to restore picture after this fault has occurred. All Primaries tapped, framed and tag panelled. 200/250, 2 v. at 2 a., 4 v. at 2 a., 6 3 v. at 2 a., 10.8 v. at 0.3 a., at 29/6 each. (Discount to trade)

EMISSION REJUVENATORS. 200/250 tapped output tapped in steps. 2 v. to $2\frac{1}{2}$ v. to $2\frac{3}{2}$ v. at 2 a., at $3\frac{3}{6}$ deach. Output 200/250 tapped in steps 6.3 v. to 7 v. to 8 v. up to $9\frac{1}{2}$ v. at 2 a., at 37/6 each. (Discount to trade) Both space wound for Heater/Cathode shorts

also

T.V. HEATER TRANSFORMERS. 200/250 6.3 v. at 7 a., 0-2-6.3 v. at 2 a., at 19/6 net.

T.V. AUTO TRANSFORMERS. 0-190-210-230-240 at 6.3 v. at 7 a., 0-2-6.3 v. at 2 a., at 27/6 net.

T.V. FRAME TRANSFORMER. 60 H. magnetic deflection, suitable for most home constructed sets at 15/6 net.

ULLY SHROUDED, 200/250 input, 350/0/350 v. at 150 mA., 6.3 v. 5 a., 5 v. 3 a., FULLY 49/6 nett.

NORTHERN TRANSFORMER CO. 215 BARKEREND ROAD BRADFORD, YORKS



ANNOUNCEMENT

DENCO (CLACTON) LIMITED

In order to avoid confusion between the well-known trademark "DELCO" and our own trademark "DENCO" and as "DELCO" was registered as a trademark before "DENCO", we have agreed to withdraw our "DEN-CO" trademarks from the Register and revert to our former trademark "MAXI O". In future all of our products will be manufactured, advertised and sold under the registered trademark "MAXI O".

DENCO(CLACTON)LIMITED

357/359 OLD RD., CLACTON-ON-SEA, ESSEX



SHORT SPECIFICATION

S Ω to 5 Meg. Ω 10 pF. to 25 μ F. Inductors can be matched, or compared with external

C. L.

standards standards. Scale Accuracy: From $\pm 2\%$ at X1 to $\pm 5\%$ at X10. Finith: Smart gray leatheretic covered case, perpex secutcheon outlined with burnished aluminium. Asingle as piecels used as a separate audio source.

PRICE £5.5.0 complete, carriage free. Guaranteed for I year Please write for full specification.

Our terms are cash with order or C.O.D. Complete satis-faction or money refunded. Write to :-

SWAN ELECTRONICS. 43, BOURNEMOUTH ROAD, PECKHAM, LONDON, S.E.15 Telephone : NEW Cross 7136.

CABINETS made to order. Send details for quotations. BASS Reflex Cabinets, finished in period or contemporary styles; see display advertisement, page No. 155. CABINETS for Goodmans and Send details

Speakers speakers YOU can see your cabinet being made in our cabinet making shop. Open till 5.30 Saturdays. A. DAVIES & Co. (Cabinet Makers), 3, Park-hill Place, of Parkhill Rd., Hampstead, N.W.3. Gulliver 5775.

MAINS transformers rewound, new trans-tormers to any specification. MOTOR rewinds and complete overhauls; first-class workmanship; fully guaranteed. F.M. ELECTRIC Co., Ltd., Potters Bildgs., Warser Gate, Nottingham. Est. 1917. Tel. 47698.

47898 [0113 -Model

LOUDSPEAKERS repaired promptly.-Dudspeaker Service, Bullingdon Rd., [2837

SERVICE sheets for hire or sale, over 2,000 models, radio and television; s.a.e. en-guiries.-W. Gilbert, 24. Frithville Gardens, London, W.12.

Lonoon, W.12. 12874 TRANSFORMER rewind service, mains, E.H.T. transformers and chokes, prompt delivery, range of replacement types ex stock or manufactured to your specification, METROPOLITAN RADIO SERVICE Co., 75, Kilburn Lane, London, W.10. Ladbroke 2296.

Co., 2296. [0200

Kilburn Lane, Loudon, (0200 MAINS transformers, E.H.T. line outputs, chokes and field colls, etc., promptly and efficiently rewound or manufactured to any specification; 12 months' guarantee. LADBROKE REWIND SERVICE Ltd., 820a, Harrow Rd., Kensai Rise, N.W.10, Lad. (0222, 024)

nard W.12

Brown, 33, Goldhawk Rd., London, W.12.
 2024 transformer; rewind, mains outputs and i.f.s. etc.; all types of new trans., etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth. [2526]
 A professional sound recordists and members of the Association of Professional Recording Studies, we are particularly well qualified to give advice and service on all aspects of sound recording. Circuits designed, repairs and modifications carried out qualified to give advice and service to trade and amateur; design, manufacture and repair of electronic equipment a speciality. Circuits end anamateurit esign, manufacture and repair of electronic equipment carried out by specialists: See also below:—Autochangers, 48-hour service; leaning and adusting at fixed price of 45-plus carriage; also all repairs carried out; trade enquirias invited; callers by appointment of 190, way appointment of the adving and adving and repairs carried out; trade equipment a speciality. Lore of 45-plus carriage; also all repairs carried out; trade ond any specialists: equal attention given to small or large orders. See also below:—Autochangers, 48-hour service; for the sound. Sog (21100)
 AMATURE rewinding service to the trade, avacuums, drills, srinders, bool drivers.

ARMATURE rewinding service to the trade, vacuums, drills, grinders, hood dryers, dental motors vacuum cleaner armatures re-placed from stock. 24 hours service; every job guaranteed; we also specialise in complete over-nauls and rebuilds of vacuum cleaners; all vacuum cleaner parts, hoses, bearings, fans, brushes, for any make in stock.-Regam Elec-tric 95. Park Lane. Leeds. 1. [0028

FOR Sale.—Goodwill, equipment and stock of Gui de Buire. Ltd., specialists in sound recording.—Address enquiries to Receiver for Debentureholders, 121. Queen Victoria St.. London, E.C.4.

London, E.C.4. [287] BUSINESS OPPORTUNITIES OLD-ESTABLISHED firm of exporters in the electronic field, invite manufacturers seek-ing overseas sales to communicate Box 0239. A DVERTISER desires contact suitable sales-organizing direct sales of radios, radiograms and tape-recorders to consumers; partnership basis; all other arrangements completed; please give full details of sales experience.—Box 4689. [2805




After considerable research into the many problems of V.H.F. Frequency Modulation reception, we are pleased to announce that our Tuner Type FM81 is available to experimenters and enthusiasts.

The excellent reproduction with absence of background noise provides an amazing degree of realism when used with Wide amazing Range reproduction equipment.

The FM81 uses the latest valves and techniques; Tuned R.F. stage; Frequency Changer; 2 I.F. stages; Ratio Discrimin-ator; A.V.C.

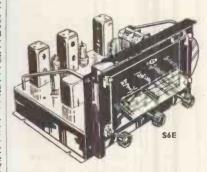Tunable between 87.5 Mc/s.-100 Mc/s., the FM81 will receive the B.B.C. Frequency Modulated V.H.F. transmissions approximately 50/60 miles radius from WROTHAM Please send for leaflet.



- SGBS 9 Band (6 Electrical band spread) with K.F. F.C. 2 I.F. Delayed Amplified A.V.C. Variable Selectivity. Fly Wheel Tuning, Tropicalised. Suitable for use with any High Quality Amplifier. £44. Tax paid.
- A new model similar to the well-known S6BS but only 3 Wave Bands ; 16m-50m, 195m-550m, 800m-2,000m. £30. Tax paid. **S6**
- As S6 but 4 Wave Bands ; 12.5m-37m, 35m-100m, 90m-250m, 190m-550m. £30. S6E Tax paid.
- 3 Wave Bands, 16m-2,000m, R.F. pre-Amplifier, variable selectivity I.F. Delayed amplifier A.V.C. very low distortion. £211/6/8. Tax paid. **S**5
- S5E As S5 but 12.5m-550m. £21/6/8. Tax paid.
 - The Standard high-quality Feeder Unit Specification as S5 but without R.F. Specification as S5 but amplifier. £16. Tax paid.

A modified version of all models is available for use with Leak, Acoustical and other High Quality Amplifiers.

C. T. CHAPMAN (Reproducers) LTD. RILEY WKS., RILEY ST., CHELSEA, S.W.IO FLAxman 4577/8

Export Enguiries Invited



FINANCIAL & PARTNERSHIP RADIO, Television and Public Address. Addressed to progressive Television and Fadio engineers. One half of the shares of a Limited Company in old established business for sale, including valuable stock in trade, and all assets; no liabilities; Lancashire coast town; balance of shares held by working electronic negineer of high standard; an assured [288 Work WANTED Assembly work WANTED Assembly, wiring of all types of electronic R.A.E., 377, High Rd., London, N.2. 10219 A paproved contractors for machining. work, and toroidal winding, speciality. distrene work, and toroidal winding, speciality. distrene work, and toroidal winding, speciality. distrene work, and toroidal winding, for short-assem-bly runs and protypes, Collwinding Services, 2667/8930. [2868

ELECTRONIC sub-contracts and prototypes; modern miniature technique, exp. govern-ment work, skilled labour only.—Astra Radio and Television, Electra House Haslemere, Surrey. Tel Haslemere 1134 [2835]

Surrey. Tel Haslemere 1134 [2253] MISCELLANEOUS COLL winding machines; from £15.—Hawkins. 170, Witton Rd., Birmingham, 6. [2879] METALWORK, all types cablaets. chassis, racks, etc., to your own specifications; capacity available for small milling and capstan work up to lin bar. PHILPOTT'S METAL WORKS, Ltd. (G4B1), Chapman St., Loughborough. [0208]

PHILPÓTT'S METAL WORKS, Ltd. (G4B1), Chapman St., Loughborough. [0208
YOUR own tape recording transferred to disc.-Write, call or 'phone Queensway, Yrivate Recording Studios, 123, Queensway, W.2 Tal Bay, 492. Studio recordings, tape recording service. [2507
'W. 1944 April/Dec. volumes 1945 to 'ISS2 (Feb. 1945 missing) best offer; Haynes R10 E.H.T. unit 70/-; Haynes S112 Scanning unit (imperfect) 20/-; Elac R25 Mk II focus unit 25/-.-Box 5051. [2869
PLYWOOD-Hardboards, Send s.a.e. for free price lists and samples, including 'yain ma-hogany ply 10d so ft, sheets 721mx36in: hard-board all sizes, from 6d sg ft; free delivery (100 miles).-N. Gerver, 2-10. Mare St., Lon-don. E. Amherst 5806. [0027
FNGRAVING amateurs and trade could take the future by yetting in touch with A.G. En-graving. 19a. Winmill Rd., London, S.W.18. Bat. 5793. Brass, bronze, erinoid, Perspex dials: one knob or repetition equally entertained. [034

one knob or repetition equally entertained. 10034 10034 10034 10034 10034 10034 10034 10035 f0034

A.R.M.C.M. [0121 BRITISE SOUND RECORDING ASSOCIA-TION Details of membership, open to the professional sound recording high quality reproduction and other branches of audio engineering, together with details of the Lon-don lecture programme and the Manchester, Portsmouth and Cardiff Centres, may be ob-tained from the Hon. Membership Secretary, H. J. Houlgate, A.M.I.E.E., 12, Strongbow Rd,, Eltham, S.E.9. [0031

[0031 SITUATIONS VACANT The engagement of persons answering these advertisements must be made through the local office of the Ministry of Labour and National Service, etc., if the applicant is a man aged 18-64 or a woman aged 18-59 inclusive, unless he or she or the employer is excepted from the provisions of The Notification of Vacancies Order 1952.

UNIVERSITY OF SOUTHAMPTON.

A TECHNICIAN with an interest in the development of electrical instruments is re-quired in the Department of Mechanical Engineering. The selected candidate will be expected to apply his knowledge to the prob-lems of measurement which occur in general engineering research. Technical education to Higher National Certificate or equivalent standard is required.—Applications in writing giving full details of education. qualifications and experience. together with the names of two persons to whom reference may be made, to the Secretary and Registrar. The University, Southampton, before June 15. [2866] ELECTRONIC engineer required immediately from development work on deaf alds.— Thomas Thirzk, 41, Lodge Rd., Crydon, Surrey. Thornton Heath 2165. [2524]



METERS. New, boxed. M.C. 2jin. Fl. rd., 130 v. (1 m/a.F.S.D., Bec., 15/6; 10 m/a., 20 m/a., 100 m/a. 200 m/a., 300 m/a., M.I. 15 v. 20 a. Proj. T.C. 1 a. M.C. 30a. Alit & J. each. 2 in. B. d. C. 5 m/a., 100 m/a. T.C. 3 a. at 7/- each. 2 in. B. d. Proj. M.O. 30 m/a. 7/- 6 in. M.I., Proj. Metal case, 30/- 24in. Fl. rd. met. 6 m/a. TC (500µa.F.S.D.) 17/6. 34in. 3,500 v. M.C. Proj. 10/- 21n. sq. fl. 20 v. M.C. 8/6. 60in. proj. met. 250 v. 500 cycles M.L. 17/6. R1155. slow motion drives, 7/6; B.F.O. Box, 4/-: 1.F. Pilter, 2/6. T.V. Pre-amps., with 1/VR136, 71-: with 2 VR51, 17/6. Trans. Input 110/240 v. Outputs 500-0350 10 m/a. 6.3 v. 4 a., 4 v. 2 a., new 16/6. Metal Rectifers. HW 270 v. 80 m/a., 6/-; 460 v. 500 m/a. 600 v. 30 m/a., 6/6; HW CT 2 v. ta., 1/8. BC610 Tank Coins, 5/-. POTENTIOMETERS 31n. dla., 20k. 10 w., 3/-. CONDERES 15 kV vereranio, 4 each 500 pF and 750 pF, in sealed case, 5/-. DYNAMOTORS, solide cases, 5/-.

20 k. 10 w., 31-. CONDENSERS 15 kVw ceramic, 1 each 500 pF and 750 pF, in sealed case, 51-.
 DYNAMOROBS, solide casea, D.C. (approx. 250 v. 80 m/a., at6 v.), 8/6. 24 v. to 250 v. 100 m/a. (twice), 17/8. RELAT 12 v. actuating toothed bakelite wheel, 2/6. Rai707A. 160/200 mc/s. 14 vires. Brand new, 75/- (carr. 7/6). WAVEMETES, new, 3/VH22, 3/VH33, 1/635, 140/250 mc/s. (less mater), 30/- 230 v. input, power pack for this 22/6.
 I.F.T.s. new, canned 7 mc/s. (R1355) or 10/13 mc/s., 1/6. R. UNITS type 24, 15/-; 22 17/6; 236 25/-; 27 45/-; (26 and 27 with broken dials, 35/-). Universal 4/6 cR100 Fower Facks (R0 tary) 6 v. D. C. 200 v. 80 m/a.smoothed, auppressed, 15/6 (carr. 5/6). NOISE LEP 9H 100 m/a. 7/6; 5H 200 m/a. 4/8; 50H 20 m/a. 4/6 (CR108), new, with valves. 4/VB55, 1.6V85, 1/0/172, 30/- (carr. 5/-).
 BELLS, underdome 60 v. A. C. 3/6; G. P. O. 50 v. A. C. Magneto Hingers, 5/6. ALADDIN FORMERS, 1, 4 or 11.- carr. 5/-2.
 BELLS, unth slug, 40. val. 2. 0. val. C. Magneto Hingers, 5/6. ALADDIN FORMERS, 1, 400 (NT00), 2.2, 3, 6.3, 10.12, 15.20, 22, 27, 33.9, 47. 100 @ 64. (5/- doz.), 1000 FH HS 92. DRIVES, epi-cul. 1/-. ELOWERS A. C. 400/2000 cg/cle all 0. v. 5/6, D. C. 28 v. shunt, 7/6. HEADPHONE CORDS, with plays. A. BAIVES, and enquiries, S.A.E. please 1

List and enquiries, S.A.E. please ! Terms : Cash with order. Postage extra Immediate delivery.

Callers and Post W. A. BENSON (WW), 308 Bathbone Rd., Liverpool 13, STO 1604 Liverpool, 1 ROY 1130





MAJOR

10 VALVE RADIOGRAM CHASSIS £32/8/4

Fidelia

HAND BUILT QUALITY UNITS

Cool quality sound reproduction is just as easy to get as mediocre results if you go about it the right way. Naturally we believe our equipment is one of the main requirements, but then a lot of our customers believe so also. Certainly used with suitable speakers and granophone pick-ups it gives reproduction not exceeded by speakeding much more money. Technical details willingly sent on request.

ALL MODELS have triode output stages. Variable Selectivity, Separate Bass and Treble Controls. Calhode follower detector, 20-20,000 cucks and in a sector, 20-20,000

MFTFRS

FOR WORKSHOP AND LABORATORY

Electrical test instruments re-paired and calibrated, all types

and makes, animeters, volt-meters, ohmmeters, DC/AC multirange meters, etc., meters converted and rescaled to speci-fication. Quick service for

industry

THE ELECTRICAL INSTRUMENT

REPAIR SERVICE

329 Kilburn Lane, London, W.9, Tel 1 AD 4168

secure

electronic apparatus, instrument cabinets

and so on we have a steady ebb and flow of

spare skilled sub-assembly capacity. It would perhaps be worth your while to

INSTRUMENTATION DIVISION of COSTAIN-JOHN BROWN LIMITED

enquire about it.

BOXES OF

We cannot guess how

pressed you may be to

assemblies. In making our own requirements of electrical control panels,

first-class

Tricks/

sub-

ELECTRO TIC

-DEVELOPMENTS-

2 AMHURST BOAD, TELSCOMBE CLIFFS, Nr. Brighton, SUSSEX Tel : Peacehaven 3156



DIELECTRIC TRIMMER AIR Protected by Acetate Case Capacities from 4 to 70pF in voltages of 500 and 1,000 D.C. Width 16.5 mm. Length 22 mm. Acetate Insulation dust cover optional. over 10,000 megohms. Power factor less than ,001.

Type approved Cat. A. No. 464.



NEW G.E.C., S.T.C. AND "WESTA-LITE" SELENIUM RECTIFIERS. Largest L.T. range in Great Britaln. Latest Current Products. NOT Surplus.

CURRENT PRICE LIST

DEDUCT 15% FROM S.T. & C. PRICES. S.T. & C. E.H.T. K3/15, 4/5 ; K3/45, 8/2 ; K3/50, 8/8 ; K3/100, 14/8. BRIDGE CONNECTED FULL WAVE.

wised price, same both types. 17 v. 12 a., 102/-; 20 a., 118/-; 30 a., 164/-; 50 a., $\pounds 12/15/-; 33 v. 6 a., 91/-; 10 a., 104/-; 12 a.,$ 168/-; 20 a., 188/-; 54 v. 6 a., 120/-; 10 a.,142/-; 72 v. 6 a., 154/-; 10 a., 178/-; 100 v. 6 a., $<math>\pounds 11: 10 a., \pounds 12/15/-; all post 1/10.$

ETT; 10 a., E12(17)*, an post //10. "WESTALITE" (BRIDGE), 12-15 v. D.C., 1.2 a., 15/10; 2.5 a., 27/8; 5 a., 31/9; 10 a., 54/6; 20 a., 99/6; 30 a., 144/10; 50 a., 257/*; 24 v. 1.2 a., 15/10; 2.5 a., 27/8; 5 a., 51/*; 10 a., 92/7; 20 a., 176/2; 36 v. 1.2 a., 27/8; 2.5 a., 51/*; 5 a., 69/10; 10 a., 130/9; E.H.T. RECTS., 14D, 134, 22/*; 36 E.H.T.60, 31/10 all post extra 31/10, all post extra.



SITUATIONS VACANT RADIO technician required as

RADIO technician required as SIGNALS Assistant Inspector of Police by Nyasaland Government for one tour of 2-3 years with prospect of permanency; salary, etc., 651 rising to £1,103 a year, commencing salary according to experience outfit allowance £50, uniform allowance £10 a year, free passages, liberal leave on full salary; candidates must be between 21 and 30 years of age, of good education and physique, not below 5ff 7in in height, normal vision without glasses; they must have a sound knowledge of H.F. & V.H.F. fixed and mobile simplex and duplex radio telephone systems and low power petrol/electric chargers and alternators; knowledge of morse and ability to instruct trainees in radio sub-jects desirable. WRITE to the Crown Agents, 4. Millbank. London S.W.I. State age, name in block letters, full qualifications and experience and quote _MI/36023/WF.

A ERONAUTICAL Radio Engineers.

A shown in the field radio Engineers. MARCONN'S WIRELESS TELEGRAPH Co... Ltd., are continuely expanding their already when activities in the field of aeronautical radio-thet, field and alse sharp for the one of the of arborne and ground communications and radio and radar navigational aids for both ciril and military purposes.—Any engineer who is in-terested in this field should apply in confidence, giving details of his experience, etc., and quoting reference S.A.44, to The Manager, Aeronautical Division, Marconi's Wireless Tele-graph Co., Ltd., Dept. C.P.S., 336-7, Strand. W.C.2. ICXPERIENCED Microwaye Engineers

XPERIENCED Microwave Engineers

ARE invited to apply to Decca Radar, Ltd., to join the Company in its extensive work in a wide field of microwave link and radar development; the Company offers excellent star-ting salaries and first-rate opportunities for men to exploit their initiative and to rise rapidly to responsible posts; graduates without indus-trial experience who are prepared to under-take intensive training are also invited to apply for junior posts; applicants must be of British nationality.—Apply, Ref. RLA/13, Decca Radar, Ltd., Research Laborator, 2, Toworth Rise, Surbiton, Surrey. [2509 DE HAVILLAND PROPELLERS, LIMITED.

DE HAVILLAND PROPELLERS, LIMITED. REQUIRE an Engineer to act as a representa-tive in Australia in connection with guided weapon trals. THE post is largely administrative but a good practical engineering background with special experience in the electronic field required; several years work in industry essential; men with experience on radar in the R.A.F. or R.N. during 1930-1945 and have since been working in industry on projects incorporating electronic equipment are particularly welcomed to apply: applicants must have personality and organis-ing ability and lie in the age group 28-35; they must be prepared to stay in Australia for several years with periodic visits in the U.K. WRITE or 'phone: The Fersonnel Manager (Technical Employment), De Havilland Pro-pellers, Ltd., Hatfield, Herts. [2855] E. K. ColE, Ltd. (Malmesbury Division): THE Malmesbury Division of E. K. Cole, Ltd.

E. K. COLE, Ltd. (Malmesbury Division): THE Malmesbury Division of E. K. Cole, Ltd., is engaged in the development and production of radar and communication equipment asso-ciated with high priority defence projects. Vacancies exist in the Development Depart-ment for project engineers, engineers and assistant engineers with training and experi-ence in the following fields:-PULSE dricuits. PULSE dricuits. PULSE dricuits. PULSE modulators. strobe systems, Video amplifiers, time base generators, etc. MICROWAVE technique. Aerial design for radar scanners and wave-guide components for high power T/R units H.F. and V.H.F. Communication. Airborne and ground receivers, transmitters and aerial systems. High frequency power transformers for air-borne equipment. MECHANICAL engineering. Light mechanisms and structures for radar scanners. APPLICANTS should have had technical train-

Light michanisms and structures for rada-scanners. APPLICANT'S should have had technical train-ing to Degree or Higher National Certificate experience is necessary. Commencing salaries will be dependent on qualifications and ex-perience, and will compare favourably with scales prevailing in the radio industry. Hous-ing accommodation may be available in the near future for successful married applicants. A superannuation scheme is in operation, to gether with canteen and full welfare facilities. Applicants should apply in the first instance for a technical staff application form \$> Per-sonnel Manager, E. K. Cole, Ltd., Manesbury. Wits.

Wilts. 2732 M. L. VIATION Co. Ltd., White Waltham, I. Madenhead, Berks. VACANCIES for experienced AIRCRAFT electrical draughtsman for a wide range of high priority experimental and de-velopment work; salary recording to experience APPLY stating see, experience 2nd salary re-quired to The Chief Draughtsman. [2519] E LECTRONIC Test Engineers and Calibrators: Staff appointment and generous bonus Scheme. - Apply to Dawe Instruments, Har-equin Avenue, Great West Road, Brentford. [2831



"I hope," said one of our customers, after giving us a more lavish amount of praise than usual, "that this letter will not induce you to lower your standards on the grounds that your trans-formers are too good and last too long."

A swelled head is not one of our afflictions, and the compliments have precisely the opposite effect.



Nursteed Road, Devizes, Wilts.

Tel.: Devizes 536

1526 8 3 10 200

146

SAMSON'S

SURPLUS STORES

SPECIAL OFFER OF HEAVY DUTY TRANSFORMERS BRAND NEW U.S.A. SOLA CONSTANT VOLTAGE TRANSFORMERS. Prim. 95-250 v. Sec. 115 v. 17.4 a., 50-60 cy. Approx. weight 200 lb. Callers only. £21

DOUBLE WOUND TRANSFORMERS by Jefferson, U.S.A. Prim. 200-260 v., 50 cy. Sec. 115 v. 8.7 a. £5/19/6, carr. 7/6.

AMERICAN HEAVY DUTY L.T. TRANSFORMERS. Prim. 115 v. Sec. 17 v., 15 a., and 2.2 v. 18 a. 35/-, carr. 4/-.

ADMIRALTY TYPE. Prim. 180-230 v. Sec. 4.2 + 4.2 v., 10 a. 25/-, carr. 2/6.

BRITISH LT. TRANSFORMERS. Prim. 200-240 v. Sec. 6.3 v. 15 a. 23/6, carr. 2/-. Prim. 200-240 v. Sec. tapped 5, 74, 10 v. 5 a. 22/6, carr. 2/-. Prim. 200-240 v. Sec. tapped 9 v. 15 v., 4 a. 23/6, carr. 1/-R.A.F. TIELD TELEPHONES. Hand Generator type complete with hand set, or breast and head phones, 45/- each. Carr. $\delta/$ -. State which type required.

ARMY FIELD TELEPHONES. D5 Buzzer Type with hand set and single head phone. 52/6, carr. 5/-

169/171 Edgware Road London, W.2. Tel.: PAD 7851 125 Tottenham Court Road, W.I. Tel.: EUS 4982

All orders and enquiries to our Edgware Road branch, please. This is open all day Saturday

THE

DESIGN and **DEVELOPMENT** of specialised equipment for Research and Industry.

DUN (electronics) & CO., 17 Victoria Gardens, London, W.11. Park 6636



Specialists can supply from stock, and maintain:-

Grundig Emicorda Prima Truvox Editor Baird Impresario, etc., etc.

Free demonstration and advice

DIXON'S ELECTRONIC SALES & SERVICE 229 OXFORD RD., MANCHESTER 13 Telephone : ARD 4269





WIRELESS WORLD

SITUATIONS VACANT FERGUSON RADIO CORP., Ltd., have vacan-

SITUATIONS VALANT FERGUSON RADIO CORP., Ltd., have vacan-cles for;-SENIOR Engineers with initiative and sound technical background for work on a wide range of projects in the field of electronics, including Television, Radio, Communications and Test Equipment Permanent posts for men able to carry responsibility in rapidly expanding departments offering a exceptional promotion and long-term prospects. JUNIOR Engineers of ability for work on Development projects offering a wide experi-ence in the fields of Television, Radio, Com-munications and Test Equipment, with excellent prospects for advancement. VAOANCIES exist in Laboratories situated both at Enfield and Spennymoor Co. Durham. These Laboratories are well enuipped and working eing assistance company's femion and proportie cases. Applications is made and giving full particulars as to age, qualifications and experience, etc. Ltd., Gt. Cambridge Rd., Enfield. Midlesex. Northern Montarger, Ferguson Radio Corp. Ltd., Gt. Cambridge Rd., Enfield. Midlesex. Northern PolyTECHNIC. Holloway. N London, N.7.

Ltd., Gt. Cambridge tur, Eunited v. (2747 N. Condon, M.7. THE Governing Body invite applications for appointment as from September next as full-time Grade "B" teacher of telecommunica-tions engineering for the erroll Technological Gertificate of the Granut and Chulds of London Institute In the Granut Chulds of London Institute of taken and television engineering in is desirable: salary on scale \$490X£25X with the Burnham Award. FORM of application, together with full par-ticulars, will be forwarded on receipt of a stamped addressed foolscap envelope. R. H. CORRELL, AS.A.A., Clerk. [2802 A. ASSISTANT Station Superintendents

with the Burnnam Award.
FORM of application, together with full particulars, will be forwarded on receipt of a stamped addressed foolscap envelope.
R. H. CURRELL, A.S.A.A. Clerk. [2802]
A. ASSISTANT Tactaion Superintendents (M2C/30482/WF) required by the Nigerian Broadcasting Service for two tours of 15 to 18 months each in the first instance. Salary, etc., according to experience in scale £807, rising to experience in operation and maintenance of radio equipment. They should have had experience at a broadcasting studio or transmitting centre, or at a wireless transmitting and receiving station.
(B) CANIDIATES should have some administrative ability and have had wide theoretical and practical experience of low-requency amplifiers and radio equipment. WRITE to the Crown Agents 4. Millbark London, S.W.I. State age, name in block letters, full qualifications required are: [a) sound to which application is made. [2836]
PAIDCATIONS are invited for the following radic design and development of electromechanical and electronic equipment for singer in design and development of electrical concerning. (b) Institution and experience in light electrical experience in light electrical electronic devices for alteratic Essential qualifications required are: [a) sound technical background in light development of electrical engineering. (b) Institute Ester Y.E.
A MAN to act as Schot calcratic Essential qualifications are (c) and practical experience or allow request and with the ability to adapt himself to this of agood practical lays with border as schot alto a sincer ratio or electronic engineering. (c) ability to with engineerine condition of the electrical, electronic conditering

radar experience. THESE positions are permanent and progressive and attractive salaries are offered for able and experienced men. ASSISTANCE with housing for some of the posts may be given, and a staff pension scheme

posts may be given, and a staff pension scheme is in operation. APPLICATIONS to Dept. C.P.S., 336-7, Strand. W.C.2, quoting reference 456V. RADIO engineer, licensed, required by Morton Air Services, Ltd., Croydon Airport, —Apply in person or writing. [2734]





BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

JUNE, 1954

WIRELESS WORLD

SITUATIONS VACANT BUSH RADIO. Ltd., require for their development laboratories at Chiswick, W.4: 1. DEVELOPMENT engineers with at least 5 years' practical experience of domestic radio, television or communications circuit develop-ment; should be familiar with mechanical lay-out for production. 2. ASSISTANT development engineers with 2 years' practical experience of radio or television development and sound knowledge of measure-ment rechnique. 3. TECKNICAL assistants. Should have some practical experience and a real interest in radio and television. Preferably with technical know-iedge to Inter B.S. standard. FOR Grades 1 and 2 it is desirable that appli-cants hold a degree or its equivalent qualifica-tion in engineering. ALL the above positions are progressive and offer excellent prospects to men with ideas and the initiative to carry them out. WRITE, giving full details of career to date and salary expected to: The Chief Engineer. Sush Radio, Ltd., Power Rd., Chiswick, W.4. [2806]

DEPUTY Chief Mechanical Inspector required

DEPUTY Chief Mechanicai Inspector required by MARCONI'S WIRELESS TELEGRAPH Co... Ltd., Chelmsford; this is a responsible appoint-ment; applicants must have served an Engin-ering Apprenticeship and possess a degree in Mechanical Engineering or its equivalent; light engineering factory experience with sheet metal work, welding, machine shop practice, tools and jigs, finishing processes, etc., is essential, together with ability to organize a Mechanical Inspection Department; the appointme cyllent is permas.-Plase rite giving full details of predications and experience and quoting ref. 911G to Dept. C.P.S., Marconi House, 356/7, Strand, W.C2.

MURPHY RADIO. Ltd., have vacacies in qualified engineers to design and develop the following:-I. V.H.F. and U.H.F. communications equip-

ment. Airborne and ground radar equipment. Computing devices and servo systems. Nucleonic equipment and measuring instru-3.

ments. The salary range is £600-£1,100 per annum, depending upon experience. Further posts are available to engineers of H.N.C. standard or equivalent having less experience, the salary range being £450 to £650 per annum. These vacancies are at Welwyn Garden City, but one or two vacancies of a similar nature are avail-able at the Ruislip works.—Applications, giving age, full details of bualifications, experience and salary required, should be forwarded to Personnel Department (E.D.L.), Murphy Radio, Ltd., Welwyn Garden City, Herts. [2686 ELECTRONIO Engineers are invited to apply for the following positions with The English Electric Co. Ltd., Luton, for work on Guided Missiles. (a) SENIOR Electronic Engineer for field trials

Missiles. (a) SENIOR Electronic Engineer for field trials of a V.H.F. radio link, with previous experience of H.F. communication equipment. Applicants must be prepared to accept responsibility for equipment trials at locations in the United Kingdom other than Luton. Housing assistance may be given

Kingdom other than Luton. Housing assistance may be given. (b) SENIOR Radar Engineers for work on radar equipment covering a broad field. A good theoretical knowledge and sound practical experience of radar systems is essential. Assistance with housing may be given. (c) SENIOR Light Current Engineers, Physicists or Mathematicians, with an engineer bias for design and development work on a range of simulators and analogue computing devices, Responsibilities will include the design and supervision of construction of complete com-putors.

supervision of construction of construction putors. (d) SENIOR Microwave Engineer for investiga-tion of new methods of construction for miniaturisation and weight reduction, design and engineering to the production stage. Degree standard and experience essential. The successful applicant may be appointed in charge of a group. Assistance with housing may be given.

Successful approaches the set of a group. Assistance with housing may be group. Assistance with housing may be develop equipment and new technique of ground terring. Applicants should be of degree or HNC, standard with design experience. Apply it to circuit development work. One vacancy exists in a group working on the application of transistors. Assistance with housing may be given. (g) SENIOR Electronics and the ability to application of transistors. Assistance with housing may be given. (g) SENIOR Electronic brain dealty of a work on radio and radar systems design. Applicants should have a good academic background and an inventive turn of mind, with extensive

Showing the second seco

GALPIN'S

147

ELECTRICAL STORES

408 HIGH STREET, LEWISHAM, S.E.I3. Tel.: Lee Green 0309. Nr. Lewisham Hospital.

TERMS : CASH WITH ORDER. NO C.O.D.

All goods sent on 7 days' approval against cash.

EARLY CLOSING DAY THURSDAY

CONVERTORS, 400 watts output, 24 volts D.C. input, 50 volts 50 cycles I phase output. Com-plete with step-up transformer from 50 volts to 230 volts at 400 watts. £12/10/e each C/F. Ditto 200 watts. £9/10/- each C/F, fully guaranteed

ROTARY CONVERTORS. 230 volts D.C. input, 230 volts A.C. output. 50 cycles I phase at 250 watts. £15 each C/F. 230 volts D.C.

HEAVY DUTY CHARGERS. 200/250 volts A.C. Input 36 volts at 36 amps. Output D.C. £25, C/F.

LARGE STUD TYPE DIMMER RESIS-TANCES or 200/250 volts at 400 watts, 32/6 each.

EX-RADAR MAINS TRANSFORMERS. In-put 230 volts. Output 4 or 5 Kilo-volts at 30 min., also 3 L.T. windings 4 v. 2 a., 6.3 v. 2 a., 2 v. 2 a., these transformers are capable of a larger output than stated and are immersed in oil. £3/15/- each, carriage 5/-.

DIMMER RESISTANCES. Large type 2,000 watts rating. 45/- each, carriage 5/-

METAL RECTIFIERS, suitable for 6/12/24 volts at 10 amps. charging with the correct trans-former, complete. 97/6 each.

12/24 VOLT RECTIFIERS, at 4 amps., with suitable Mains Transformer, 200/230 volts input. 55/- each.

MAINS TRANSFORMERS (NEW), input 200/250 volts in steps of 10 volts, output 350/0/350 volts, 180 m/amps., 4 volts 4 amps., 5 volts 3 amps., 6.3 volts 4 amps., 45/- each, post 1/6; another 350/0/350 volts 180 m/amps., 6.3 volts 8 amps., 0/4/5 volts 4 amps., 45/- each, post 1/6; another 500/0/500 volts 150 amps., 4 volts 4 amps. C.T., 6.3 volts 4 amps., C.T., 5 volts 3 amps., 47/6 each, post 1/6; another 425/0/425 volts 160 m/amps., 6.3 volts 4 amps., C.T., twice 5 volts 3 amps., 47/6 each, post 1/6.

MAINS TRANSFORMERS (NEW), suitable for spot welding, input 200/250 volts, in steps of 10 volts, output suitably tapped for a combination of either 2/4/6/8/10 or 12 volts 50/70 amps. 95/each, carr. 7/6.

MAINS TRANSFORMERS, 200/250 volts input, output a combination of 6, 12, 18, 24, 30 and 36 volts at 6 amps. 45/- each, post 1/6.

MAINS TRANSFORMERS, 200-250 volts input, output 400/0/400 volts, 280 m/amps., 6.3 v. 8 a., 2 v. 3 a., 5 v. 3 a., 4 v. 2 a., 4 v. 2 a., the last two heaters insulated at 8,000 volts, 85/- each; another 200/230 volts input, output tapped 0, 9, 18 volts at 4 amps., 25/- each, post 1/-.

MAINS TRANSFORMERS (NEW), 200/250 volts input in steps of 10 volts, output 0, 6, 12, 24 volts 6 amps., 42/6 each, post 1/6. Another as above but 10-12 amps., 55/- each, post 1/6, another as above but 25/30 amps., 75/- each, carriage 3/6; another, input as above, output 0/18/30/36 volts 6 amps., 47/6 each, post 1/6.

Ex-U.S.A. ROTARY CONVERTORS, 12 volts D.C. input, outputs 500 volts 50 mA., 275 v. 100 mA. Complete with smoothing. 22/6 each, carriage 2/6. As new.

Ex-NAVAL ROTARY CONVERTORS, 110 v. D.C. input, 230 volts A.C. 50 cy., 1 ph. 250 watts output. Weight approx. 100 lb. £12/10/-, clforward.

Ex-W.D. U.S.A. HAND GENERATORS, less winding handle, output 425 volts at 110 mA., at 6.3 v., $2\frac{1}{2}$ amps., complete with smoothing, 30/- each, carriage 2/6.

ELECTRIC LIGHT CHECK METERS, useful for sub-letting, garages, etc., all for 200/250 volts A.C. mains, 5 amp. load, 19/- each ; 10 amps., 22/6 : 20 amps., 27/- ; 25 amps., 32/6.

METERS. Moving coil, 0 to 14 amps., 18/6 each. Ditto, Moving Iron, suitable for A.C. 0 to 30 amps., 25/- each. Another moving coil, 100 to 250 amps., D.C. 35/- each, all 4in. scale.

1,000 WATT AUTO WOUND VOLTAGE CHANGER TRANSFORMER tapped 0/110/ 200/230/250 volts. £5/15/- each, cargiage 4/6.

FULLY GUARANTEED Model B3, Long, Med., Short (5 Valves) B3 Plus Push Pull Stage £12.12.0 £15.15.0 (6 Valves) B3 Double Feature P/Pull £18, 18, 0 & RF Stage (7 Valves) Model B6 SixWavebands £15.15.0 Med, L, 4 Short(Bd-Spread) B6 Plus Push Pull Stage

DIRECT FROM THE MANUFACTURER

Dulci Radio/Radiogram Chassis

A/C 100-120 & 200-250 VOLTS. All chassis II jin x 7 in, x 8 jin, high, Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4, Flywheel tuning. Negative feedback over entire

type valves 68E0, object feedback over entry Flywheel tuning. Negative feedback over entry Flywheel tuning. Engraved knobs. 3 Tone position

£23 .

THE DULCI CO. LTD. 9/ VILLIERS ROAD, LONDON, N.W.2 Telephone : Willesden 7778 4 CIRCUIT SUPPLEMENT Re-introductions of our popular Supacircuits • "Ajax " 5 valve All-wave AC Superhet • "Supa 30 " Feeder Unit • "Supa 40 " Feeder Unit · Feeder Unit Power Pack and Amplifier All the above, together with Parts lists, descriptions, etc., included. with each copy of our profusely illustrated "THE HOME CONSTRUCTOR " PRICE 2/6 ONLY

which also contains a number of other circuits (Crystal, TRF, Superhet, Ampli-fler, etc.), lots of servicing, constructional notes, resistance colour code, technical information, helpful hints, etc., and

FULL

layout, wiring and constructional details for building a variety of superhets. Catalogue of our quality products included

Obtainable from all W. H. Smith's Book. stalls and stationers everywhere. (ask for "Supacoils Home Constructor and Supplement")

Or direct from :

SUPACOILS, 21 Markhouse Road, (Return of post Mail Order), Walthamstow, London, E.17. (Nr. James St. Riwy. Stn., Buses 685, 687)



the Manufacturers.



WIRELESS WORLD

SITUATIONS VACANT NAPIER & SON, Ltd., Luton Airport, have the following vacancies in the Instrumen-tation Department:— 1. TECHNICAL Assistant with practical elec-tronics background in field of instrumentation familiarity with C.R.O. technique desirable. Higher National Certificate standard or equiva-lent essential. Ref. 1295. 2. LABORATORY Assistant (e)ectronics). Higher National Certificate standard desirable. Ref. 1297. 3. LABORATORY Assistant

Higher National Certificate standard desirable.
Ref. 1297
J. LABORATORY Assistant (instruments).
Higher National Certificate standard desirable.
practical background in instrumentation particularly with pyrometry experience.
Ref. 1298.
THESE posts offer vide variety of work on instrumentation for dight testing of aircraft and aircraft engines.—Apply, with full particulars of qualifications.
TELECTRONIC engineers required by The General Electric Co., Ltd., Brown's Lane, Allesley. Coventry, in their development laboratories, for work on the following items:—

(a) DESIGN of R.F. modulators.
(b) INVESTIGATION into valve parameters.
(c) DESIGN of valve test apparatus associated with (b) above.

TRIALS team in connection with guided

(e) DEVELOPMENT of pulse circuitry tech-

(d) TRIALS team in connection with guided weapons.
(e) DEVELOPMENT of pulse clrouitry techniques for guided weapons.
(f) SERVO-MECHANISMS.
(g) MICROWAVE development.
(h) TEST equipment.
(i) GENERAL radar circuit development.
(j) POWER units including electronic stabilizers and rectifier systems.
(k) Magnetic amplifiers.
APPLICANTS, preferably with a degree or an equivalent qualification, should have had at least two years' experience in the development and engineering of Service equipment as well as experience in one of the above.-Reply. Stating age, qualifications and experience. to The Personnel Manager, Ref. R.G. [2714]
FERRANTI, Ltd., Manchester, have staff development work on an important radio telecontrol project at their new laboratories at Wythenshawe, South Manchester.
(i) ENGINEERS for research and development work in the following fields:
RADAR. radio and electronic circuits, microwaves, vacuum and/or high voltage techniques, servo control and hydraulic systems and electronechanical devices and testing equipment associated with the above.
QUALIFICATIONS include a degree in Physics or Electrical Engineering or Mechanical Science, or equivalent qualifications, and at least two years' previous experience. Salary according to qualifications and experience the range foo-£1,000 per annum.
PLEASE quote reference WE.
(2) TECHNICAL assistants for experimental work in the fields isted in (1) above.
QUALIFICATIONS required; a degree or Higher National Certificate in Electronical conditions. Salary in the frange of 2400-£600, according to age and experience.
APPLICATION forms from Mr. R. J. Hebbert, Staff Manager, Ferranti, Ltd., Hollinwood,

benefits. APPLICATION forms from Mr. R. J. Hebbert, Staff Manager, Ferranti, Ltd., Hollinwood, Staf

Lancs. PLEASE quote appropriate reference. [2664

bridge.

Bridge: [2689]
SERVICE Engineers required for installations and trials of aeronautical and marine navigational equipment. Applicants must be of good appearance, prepared to travel in U.K. and have the following qualifications:---(a) AERONAUTICAL: under 35 years of age with electrical and radio theory to C. & G. Radio III standard.
(b) MARINE: AC & DC electrical theory to approximately O.N.C. standard. Knowledge of electronics or radar preferable.
GOOD conditions: expense and travelling allow-ances; pension scheme. Apply with full details including salary, quoting no. 1477 to Personnel Maranger, Sperty Gyroscope Co., Ltd., Great West Road, Brentford, Middlesex [2847]

West Road, Brentford, Middlesex [2847] FIRST-CLASS openings for young men with service or amateur radio experience, on work which introduces them to television tech-nique.-Apply in writing to Personnel Manager, Pye, Ltd., St. Andrew's Rd., Cambridge. [2690 R ADIO and television engineers wanted, for Merseyside district. Good job for good men. Staff rate, payment for overtime, Sick Pay and Pension Scheme after qualifying period.


Pay' and Pension Scheme alter quanty are period. APPLICANTS should give full details of age. training qualifications and experience. If re-quired for interview expenses will be paid.— Apply Box 4305 [2699] LeCTRONICS Technician required for work on 15 mflion Volt Linear Accelerator. Experience in pulse technique desirable; salary according to experience in scale £450 to £550. plus London Weighting. Write enclosing two copies of references within 7 days, Cierk to the Governors, St. Barthlomew's Hospital, Lon-don, E.C.I. marking the envelope "Electron-ics." [2848]



CABL	ES	A	ND	FL	EXES
CHEAPE	R IN	ODI) LE	NGTI	I COILS
No coil und					
			and g		
(100 yd. Coi	ls can b	esuppl			
TWIN FLAT	1/044	3/029			Do. 7/044 W/E
RUBBER	39/-		59/-		156/- 198/-
PLASTIC Single V.I.R.		49/-21/-		99/- 34/-	155/- 196/-
Single Plastic		22/-	_	38/-	66/
CIRCITI A D	main 1	1100 0	100 40	100	3 Core
CIRCULAR		14/36 2		/36	23/36 40/36
RUBBER			81/- 7		75/- 100/-
Padd / Braider			54/- 7		63/- 89/-

FLEX, Plastic T.T. or flat, 13/9. Maroon 24/- (in 10/20 yd.

PLEX, Flasse 1.1.9, may all colls 20/-3. 100 yd. Colls Transparent Plastic, T.T. or flat, 15/-; 100 yd. Colls Marcon T.T. D. V., 27/6. Leasthan 100 yd. lot of any-thing supplied justadd 5%. 7/044 and heavier supplied nas little as one yard at a time. Send for lists, every type ever made is arguinable. Add part carriage to small orders please. British Distributing (W.W.), 591 Green Lanes, London, N.8. MOU. 0055/6.

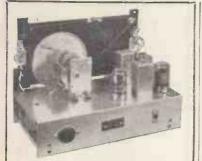

SUPERHET TUNER UNIT S/H3. Three wavebands, 16-50, 200-500, 800-2000 metres, flywheel tuning, coloured edgelit station flywheel tuning, coloured edgent station named dial, complete with valves, 757, 787, 6H6GT, escutcheon, plugs and leads, designed to operate with all types of High Fidelity equipment and tape recorders, £10/10/-.

T.R.F. TUNER UNIT R/F2. A med. wave Turer Unit, employing a Variable Mu H.F. Pentode, coupled to an infinite impedance detector, with a cathode follower, exception-ally sensitive, the ultimate in design for distortionless output for High Fidelity equipment. Station named, edgelit, glass dial, chassis size 8½in.x4in.x2in.,valves,6K7GT,6SL7GT, complete with leads and plugs, £6/15/-. chassis

A.C. AMPLIFIER. A 3 valve amplifier for A.C. mains, 200/250 volts, employing negative feedback tone control, giving an output of four watts, with input network for all P.U. types. Complete less 5/- carriage/insurance. Complete less speaker, £6/10/-, plus

"DULCI" RADIO/RADIOGRAM CHASSIS, full range of these outstanding chassis available, illustrated details from-

O. GREENLICK LTD. 14, Hillside Rd., Tottenham, London, N.15 Tel. : STA. 2991.

SOUTHERN RADIO'S WIRELESS BARGAINS

TELESONIC 4-valve Battery Portable. Complete with Hivac Valves. In Metal Carrying Case, Simply converted to Personal Portable, £2 including Conversion Sheet.

TRANSMITTER-RECEIVERS. Type "18" Mark III. COMPRISING SUPER-HET RECEIVER and TRANSMITTER. TWO UNITS CON-TAINED IN METAL CARRYING CASE. Com-

TAINED IN PICAL CARATING CASE. Complete. 8-valves. BARGAIN CLEARANCE OF REMAINING STOCK, £4/10/-. RECEIVERS TYPE * 109" 8-VALVES WITH VIBRATOR PACK FOR 6-volts. BUILT-IN SPEAKER. 1.8 to 8.5 Mcs. Contained In Metal Case. Perfect. 100 ONLY, £5. Bargain Clear-

SPEAKER. 1.8 to 8.5 Mcs. Contained In Metal Case. Perfect. 100 ONLY, 45. Bargain Clear-ance of Remaining Stock. BOMBSIGHT COMPUTERS. Ex-R.A.F. New. Contains Gyro, Motors, Rev. Counters, Gear Wheels, etc., etc. Ideal for Model Makers, etc., 43/5/-, plus IO/- carriage. CRYSTAL MONITORS. Type 2. New in Transit Case. Less Crystals, 8/6 each. LUFBRA HOLE CUTTERS. ADJUSTABLE aro 34 ins. For Meral. Wood Plastic, etc. 4/6.

LUFBRA HOLE CUTTERS. ADJUSTABLE 2 to 34 ins. For Metal, Wood, Plastic, etc., 6/6. RESISTANCES. 100 Assorted. Useful Values. Wire end, 12/6 per 100. CONDENSERS. 100 Assorted. Mica. Metal Tub, etc., 15/- per 100. PLASTIC CASES. 14 in. by 102 in. Trans-parent. Ideal for Maps, Photos, Display etc., 5/6. STAR IDENTIFIERS. Type 1 A-N. Covers both Hemispheres. In Case, 5/6. CONTACTOR TIME SWITCHES. Complete in Sound Proof Case. 21 moulses per sec. Thermo-

in Sound Proof Case. 21mpulses per sec. Thermo-static Control, 11/6. REMOTE CONTACTORS for use with above,

7/6. MORSE TAPPERS. Standard Type ex-Govt., 3/6. Heavy Duty Type "D," 8/6. COMPLETE MORSE PRACTICE SET with BUZZER, 6/9. DIMMER CONTROLS. Bakelite. Wire Wound. New, 1/3 each. MAGNETIC RELAY SWITCH. Bakelite.

5c/723, 2/6 each. METERS. 12 Instruments may need adjustment

or cases broken, 35/- for 12.

Full List OF RADIO BOOKS 24d. SOUTHERN RADIO SUPPLY LTD

II Little Newport Street, London, W.C.2. Gerrard 6653.

SITUATIONS VACANT FERRANTI, Ltd., Edinburgh, have vacancies for Electronic Engineers in their Test Equipment Laboratory for the following dutles: 1) DESIGN of precision test equipment for radar and specialized valves. (2) TESTING of prototype products. APPLICANTS should preferably have some radar experience and be of degree or equivalent standard, though experienced applicants with lower qualifications will be considered. Good prospects in an expanding organization. Staff Pension Scheme — Apply, quoting "EE/TEL," and giving full details of training, qualifica-tions and experience, to the Personnel Officer. Fernanti, Ltd.. Ferry Rd.. Edinburgh, 5. IL ECEMENCI

ELECTRICAL Test Room Assistant required for adjusting and calibrating various types of multi-range test sets, able to read and work to circuit diagrams. WRITE. E.I.R.S., 329, Kilburn Lane, W.9

R ADIO and television engineer required, fully experienced all makes, for benchwork; good salary and opportunities; references.—Sayer, 5. Heath Rd., Petersfield, Hants. [2840 TELEVISION makes for a series.]

TELEVISION radio service engineer required. fully experienced all makes, able to drive, good wages, permanent position.—Jones, Ltd., High St., Cobham, Surrey, Tel. Cobham 176.

SERVICE engineer (TV and radio) wanted for out-of-the-ordinary job; some ability as a draughtsman would be an advantage.—Box 4506. [2752

ADIO service mechanics required by Smiths (Radiomobile, Ltd., for many parts of the country.--Write details of experience and quali-fleations to Personnel Officer, Goodwood Works, North Circular Rd., London, N.W.2.

North Circular Rd., London, N.W.2. [0342] A Notth Circular Rd. [0342] A Nothology (1014)
DRAUGETSMAN aged 22-25 years required for mechanical and electronic work. Must be neat and accurate and capable of making production drawings from original sketches and

ideas. EXCELLENT working conditions, bus services to Kingston, London, Guildford, pass the pre-

to Kingston, London, Guildford, pass the pre-mises. CANTEEN, pension scheme, sports and social club, with recreational facilities. APPLICANTS must be of British nationality. Pull details of experience and salary required should be addressed to:— THE Joint Secretary, Cottage Laboratories. Ltd., Portsmouth Rd., Cobham, Surrey. [2814 VACANCIES exist for junior engineers and laboratory assistants on work connected with expending programme involving radar and associated devices. Qualifications required are as follows:—

as follows.— JUNIOR Engineers.—Should be of Graduate standard with preferably some Services or laboratory experience of radar. LABORATORY Assistants.—Should be of matri-culation standard in mathematics and physics and familiar with the use of normal test equipment; a student member would be suit-able.


SALARIES according to are and experience. Applications should be made in writing in the first instance to the Chief Development Engin-er, Decca Radar, Lid., 9, Davis Rd., Tolworth, Surbiton, Surrey. SENIOR and Junior Electronic Engineers re-quired for audio and acoustic projects. Applicants should give full details of qualifica-tions and experience by letter to-Personnel Manager, Pye, Ltd., St. Andrew's Rd., Cam-pridge.

bridge. [2812] TEST Room Supervisor required by electronic and radar firm of international repute for appointment which will provide an outstanding opportunity to the successful applicant in an entirely new production group located in the South Coast area. ESSENTIAL qualifications are:— (a) GOOD technical background. (b) EXPERIENCE of the testing requirements associated with the production of microwave radar, servo and pulse equipment. (c) ABILITY to organise and control staff. SUPERANNUATION scheme exists and housing assistance may be given. Write fullest details of education, experience and age to—Box 4907. [2832]

DRAUGHTSMEN, Junior or Senior, required for light mechanical engineering in con-nection with electronics. Experience in this branch not essential. Apply in writing to-R. Y. Pickering & Co., Ltd., Wishaw, Lanark-bire **[2813**

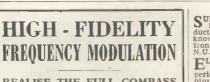shire. [2813] EXPERIENCED radio testers and inspectors required for production of communication and radio apparatus, also instrument makers, wirers and assemblers, for factory test appara-tus.—Apply Personnel Manager, E. K. Cole, Ltd., Ekco Works, Malmesbury, Wilts. [0238]





REALISE THE FULL COMPASS OF YOUR EQUIPMENT.

OUR "WW" DESIGN FM AM VHF RECEIVER is available for EX-STOCK DELIVERY FIELD-PROVEN RELIABILITY AND SENSITIVITY.

Chassis with power supply	£15.0.0				
Less P/S	£11.17.6				
Complete kits	£7.5.0				
Leaflet 1/0.					

Ring ARC 5078 for a demonstration. Trade enquiries invited. BEL SOUND PRODUCTS CO., Marlborough Yard, Archway, London, N.19.



TRANSFORMERS & COILS SPECIFICATION ТО MANUFACTURED OR REWOUND Filter Coils ± 1% a Speciality.

JOHN FACTOR LTD. 9-11 EAST STREET, TORQUAY, DEVON 'Phone : Torquay 2162

MALVYN ENGINEERING WORKS Precision Engineers

Manufacturers of: Chassis, Small Pressings, Machined Components, Wiring and Mechanical Assemblies to specification.

Single and Production Quantities. Enquiries Invited. 100 PARK ROAD, WARE, HERTS.

-Telephone: Ware 465-

PLESSEY GRAM. MOTORS. Shaded pole, 200/250 PLESNEY GRAM. MOTORS, Shaded pole, 200/200 AC. 12(6, post.)... INDICATOR UNIT 184, Contains VCR.97, VCR.139, 4 EF.50, 3 VR.54, 3 VR.55, 6 VK.92, and 4 Mains metal Rectifiers, Resistors, Fots., Condensers, etc. EcotARY TRANSPORMERS. 20 watt, H.T. 480 v... L.T. 1) volts. Suit small car radios, etc. 15/- each, post 2/-. MOTOR GENERATOR. Type M. Ref. 10k/1859, Input 11 volt, output 200 v. 50 m.a., another 13 v. In same output, D.C. Suitable Car Radlos. 10/-, in post 2/-TERMINAL BLOCKS. Type 5c/430. 2-way. A/6 dozen, 5c/431 2-way larger type, 7/6 dozen, 5c/432 3-way, 7/6 dozen. Type 5c/868 5-way, 9/- dozen. post S. way, 7/6 dozen. Type berges owney, 6/1
 Did any type.
 UNIVERSAL COUPLERS. Two elzes, 21n. long takes 3/16in.rod, smallertype takes jin.rod. Useful driving at angle. 1/9 each. 13/4 dozen, add postage.
 HYDROGEN GENERATORS. Contain Lithium Hydrade, for inflating Met. ballons. 3/8 each, post 1/.
 TOGGLE SWITCHES. Type 5d/531 Single Pole.
 C. New Y/6 dozen, post 9d. 72/2. gross, post free. Send 6d. for new list.
 C. NOBTHALL
 16, HOLLY ROAD, QUINTON, BIRMINGHAM, 32. Phone WOO. \$166.

SUB-EDITOR for technical books; should have experience of book or magazine pro-duction as well as technical and scientific knowledge (particularly electricity and elec-tronics); applicants must be members of the N.U.J.-BOX 4505. [2753


ELECTRONIC Engineering Company hav pertence of test gear; rate up to 4/6 per hour plus bonus, for a 44hr week; accommodatio for single men; canteen facilities.—Apply Per sonnel Officer, Airmec Ltd., High Wycombe. have

sonnel Officer, Alrmec Ltd., High Wyom 2009 ELECTRONIC test engineer required for pro-totype testing to specification; ability to work with minimum supervision and assistance on all types of test gear essential. Apply The Wayne Kerr Engineering Co., Ltd., Tolworth Close, Surbiton, Surrey. [Z796 TELEVISION engineers required for demon-stration installation unit (T.V. transmis-sion equipment); must be willing to travel overseas.-Apply bletter in first instance to: Engineer-in-Charge. Demonstration and In-stallation Section, Pye, Ltd., Cambridge. [2761] FOGINEER required to undertake the develop-E MGINER required to undertake the develop-ment of transformers and iron-cored com-ponents; a degree, or equivalent, and some experience of this type of work are desirable. -Apply in writing to Advance Components, Ltd., Back Rd., Shernhall St., London, E.17.

expertence of this type of work are desirable. —Apply in writing to Advance Components. Itd., Back R.C., Shernhall St., London, E.T. — PRAUGHTSMEN required; electronic instru-ment or radio experience; salary according to qualifications; Saturday interview if needed; opportunity to broaden experience, with reput-able firm; near city centre and all amenities. —Apply Marconi Instruments, Itd., Longacres. ELECTRONIC Engineer (about 30 years) re-guired by Scientific Instruments. Good prospects for keen man. Camden Town district. Five-day week, superannuation, good welfare and salary required to Box 5084. [2876 Matter Science and all amenities. —ADIO.—A gentleman to take charge of the to assist in simple development an advantage; South Croydon district.—Box 428, c/o George Murray (Advtg.), Itd., Brettenham House. Lancaster Place, W.C.2. [2894] —RANFORMER Designer required for de-velopment projects involving audio-fre-quency power transformers, Julis and Frances. ADIO and radar testers; first-class men-reduced for work on V.H.F. communica-ind atar' equipment by Midland manufac-tres.—Men with wide experience of fault finding anny of the fields mentioned should write, siving full details, to Box 4508. [275 ENFIENCED Lault-finders wanted by Midland and radar' equipment by Midland manufac-ting and radar testers; first-class men-reduced for work on V.H.F. communica-tion gear and Government contracts for radio and radar' equipment by Midland manufac-ting manufacturers of radio equipment; permanent posts located in the Midlands are offered to men with experience of fault finding in any of the fields mentioned should write, siving full details, to Box 4508. [2755 ENIOR Mechanical Designers and Draughts-ment required for Radio and Traughts-ment ment for Apply in writing, siving full details of age: experience and caleresion personnel Department. Apply in writing, siving full details of age: experience and caleresion personnel Department. Apply in writing, giv

Weiwyn Garden City, quoting "Design Depart-ment." **PARTRIDGE TRANSFORMERS**, Ltd., have vacancy for a senior transformer designer, applicants must have considerable experience in the design and development of all types of audio and power transformers, interesting and permanent position.-Written applications to Managing Director, Partridge Transformers, Ltd., Tolworth. Surrey. **ELECTRONIC** engineers experienced in design, construction and operation of elec-tronic equipment, required to work on the measurement of vibration of engines, etc.; some measurement of vibration of engines, etc.; some fortificate; salary 2400-2700.-Appipt Labour Manager (A), Rolls-Royce, Ltd., Derby. [2797] **L.B.M. UNITED**, KINGDOM has a vacancey for Manager (A), Rolls-Royce, Ltd., Derby, [2767] I.B.M. UNITED KINGDOM has a vacancy for a graduate physicist or electrical engineer in its London Patent Department; applicants must have a good knowledge of electronics, preferably with development or research experi-ence; a knowledge of electronic computers is desirable; previous patent experience is not essential. THIS post offers excellent prospect of advance-ment to a young graduate inferested in elec-tronic computer work or wishing to enter the £550 to £800 depending upon qualifications and experience.

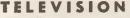4550 to f2600 depending upon qualifications and experience. The second secon



"Fringe " and "Long distance viewers is vastly improved with the SPENCER-WEST type AC/3 Pre-Ampli-fier. The specification includes a first stage neutralised triode cathode coupled stage neutralised triode cannote coupled to a grounded grid triode. The optimum arrangement for best "noise factor." Self-contained power supply unit com-plete with correctly adjusted interference filter. Price complete, 10 gns. from your dealer or direct. Leaflets, etc., on request.

RECEIVER CONVERSION TO

The type AC/4 Converter units for perfect simple conversion. Price complete wIth 5 valves and self-contained power unit, etc. 15 gns. Available for Brighton booster on London receivers (type AC/4KL) and all other conversions. Leaflets on request.

SPENCER-WEST QUAY WORKS, GT. YARMOUTH Phone : Gt. Yarmouth 3009.



SYNCHRONOUS CLOCK UNITS. Self-starting, 200-230 v. A.O., 50 cycle, fitted Sangano motors consumption 24 watks, size 24in. dam., 21m. decp, geared 1 rev. 60 mins. friction reset. Ideal movements for electric clocks. Frice 22/6 cuch, post paid.

SPECIAL OFFER-100 wstł Auto Transformer, A.C. 230/50 volt input, 110 volt output, 12/6 each. P. & P. 2/-, Vibrator Power-Pack 12 volt D.C. input, 210 volt 70 m/a., smooth D.G. output. Ideal for car radio, 21/- each. P. & F. 2/-.

Please Print Name & Address when ordering. Cash with order. Money Back Guarantee.

C.O.D. and 'Phone Orders Accepted.

UNIVERSAL TRADERS (W.W.) 44, LONDON RD., TWICKENHAM, MIDDLESEX POPesgrove 6040.

SITUATIONS VACANT DESIGN & Development Engineers for work vibration testing. Experience of vibration phenomena desirable. Electrical and mechani-cal engineers of H.N.C. standard required. State age, experience, salary. Goodmans Indus-tries, Ltd., Axiom Works, Wembley, Middlesex.

tries, Ltd., Axiom Works, Wembley, Middlesex, ENGINEER, experience of mechanical design of subminiature electronic equipment. Applicants should be familiar with layout and wiring to interservice standards, design and manufacture of mechanical parts and prepara-tion of working drawings. Degree not essen-tial, preference given to persons with good practical experience. (Ref. 86.) EXPERIENCED Wiremen for work on experi-mental subminiature electronic equipment. Applicants should be used to working direct from circuit diagrams and be familiar with workshop practice. Ability to prepare draw-ings an advantage. (Ref. 87.) PLEASE write in detail, quoting reference number of position sought, to: The Personnel Manager (Technical Employment). De Havil-land Propellers, Ltd., Manor Rd., Hatfield, Herts.

Manager (Technical Employment), E. (2892) and Propellers, Ltd., Manor Rd., Haffield, Herts. (2892) SCIENTIFIC Instrument Makers in North London have a few vacancies for skilled laboratory assistants and wiremen for the development and production of high quality electrical and electronic apparatus. Flye-day week, canteen, good welfare facilities.—Please apply, stating age, experience and salary re-quired to Box 5083. (2875) TECHNICAL Correspondent for leading. valve conversant with modern valve and electronic technique; C. & G. Radio standard; age 20-30; work involves technical liaison between Fac-tories/Sales Department/Publicity Department/ customers; salary depends on qualifications and experience; pension scheme.—Box 5151. [2901] PAPER capacitor development engineer re-nerce, ability to originate protypes and assess their market potentialities.—Reply, in con-fidence, stating age, qualifications. Stating age, qualifications. 2005 Required by a large protypes and assess their market potentialities.—Reply, in con-fidence, stating age, qualifications. Stimmary of experience and salary required, to Box 5110. (2885)

experience and salary required, to Box 5110. [2885] ReQUIRED in Buckinghamshire. experienced assistant (male) for mintenance of elec-trical (including electronic and photo-electronic) iaboratory equipment; skilled R.A.F. tradesman considered; salary £8 to £11. according to age and qualifications; good working conditions. Reply, giving age, particulars of education and experience, to Box 4507. [2754] LECTRONIC engineer required to supervise testing of prototype electronic equipment; an ablity to quickly diagnose faults, and a wide experience of modern test equipment are essen-tial qualifications; this is a staff position offering good prospects to the right applicant. —Apply The Wayne Kerr Engineering Co., Ltd., Toworth Close, Surbicon, Surrey, 12790 MALE trainee, age 25-35, requiring the sound electronic electronic, equipment and installa-tions in operating theatres, salary according to age and experience.—Apply in writing to the Secretary, The London Hospital, White-chapet, E.I. ASUSTANT (Scientific).—The Civil Service

TENGTNEERING and physical sciences.
CHEMISTRY, blo-chemistry and metal-lurgy.
CHEMISTRY, blo-chemistry and metal-lurgy.
BIOLOGICAL Sciences.
CHU GENERAL (including geology, meteor-ology, general work ranging over two or more groups (1) to (HI) and highly skilled work in aboratory crafts such as glass-blowing).
SALARY according to age up to 25: £250 at 18 to £380 (men) or £340 (women) at 25, to £520 (men) or £435 (women); somewhat less in provinces. Opportunities for promotion.
FURTHER particulars and application forms from Civil Service Commission. Scient Miller and the science of the science



MONEY BACK

GUARANTEE

4/6

CWO OR COD

SIDELIGHTS. 1/9. Infra-red glass. Easily changed for clear or red. Ideal tail lamps. New, ex-W.D. Post 9d.

AMPLIFIERS. Push-pull. 77/6. 7 watts output. A.C. or Universal. 4 valves and 1 rec. Post 2/6.

AMPLIFIERS. 57/6. 4 watts output. 3 valves. A.C. or A.C./D.C. Post 2/6.

RECTIFIERS. 8/9. T.V. type. Salvage, guaranteed. 250 volt at 200 m/A. Also 180 volt at 40 m/A 3/9, and New, 300 volt at 200 m/A 12/9. Post 1/- each.

TELESCOPIC MASTS. Ex-W.D., but unused. Extend to 7ft. 6in. Base diameter §in., tip §in. Closed length 15in. Ideal aerial. GIFT PRICE 5/9. Post 1/3.

CRYSTALS. Germanium. Brand new, made by B.T.H. Give first-class results. SPECIAL OFFER 1/9, post 6d.

TRANSFORMERS. Microphone trans., 2/9, ex-W.D., fully shielded. Post I/-. Pick-up trans., 2/9, E.M.I. type, fully shielded case. Post I/-

EXTENSION SPEAKER CABINETS. 9/9 Polished, for 8in. speaker. Post 2/6.

EXTENSION SPEAKERS. Brand new 641n.p.m. speaker (low impedance). Mounted on polished and veneered baffle scand, gold fret. 5ft. lead ready connected. ONLY 19/9. Post 1/9.

RADIOGRAM CHASSIS. End-drive. £6/17/6. Salvage, reconditioned, 3 wave-band, 5 valve superhet (latest midgets), ext. speaker and pick-up sockets, Post 3/6.

MIDGET T.R.F. RADIOS. 4 valve, L. & M. wave-bands. Walnut plastic or white cabinet. Complete. £6/9/6, plus 3/6 P. & P.

P.M. SPEAKERS. 12in. Truvox 47/6, 10in. 25/9, 8in. 18/6, 6½in. 14/9, 5in. 13/9, all 3 ohms. Best makes. P. & P. 1/9.

MOTORS. 12-24 volt, with flexible shaft. 18 ct. gold brushes. 17/6. Post 2/6,

MINIATURE M/C 'PHONE SPEAKERS, Ideal personal extension speaker, or quality microphone. REDUCED to 2/9. Post 3/-.

DUAL SEATS, DUNLOPILLO, FOR MOTORCYCLES. New Bargains. Not MOTORCYCLES. New Bargains. Not covered. 37/6. Carr. 2/6d.

SEND STAMP FOR 1954 CATALOGUE

LEWIS RADIO CO.

invite you to send 1/- for our 1954 Catalogue of ALL types of :-

> CABINETS AUTO-CHANGERS RADIO AND T/V CHASSIS AND LOUDSPEAKERS

CABINETS

made to individual specification.

TAPE RECORDERS

Send for full details of the "ELIZABETHAN" Portable 2-speed Tape Recorder at 48 gns. All "Sound-' parts stocked—send for list. master'

TELEVISION

All "Viewmaster " and " Tele-King " parts-stocked. Send for our lists.

AMPLIFIERS

Full details available of our $4\frac{1}{2}$ and 5 watt domestic amplifiers.

Dept. 654; 120, Green Lanes, Palmers Green, London, N.13 Tel : BOWes Park 6064

OFFERS SPECIAL

ELECTRO MAGNETIC COUNTERS. Post Office type counding up to 9,999 operating from 14 yolts D.C. Coll resistance 3 ohms, overall size 44 x 14 x 14, perfectcondition, 12/6 each, post 1/. ALKLUM LONG LIFE BATTERIES, 12 yolt Input 65 A.H. Price complete, uncharged, 210. Carr. 10/.-YENTAXIA EXTRACTION FANS. 230 y. Bakelite cased, silent running, 90/.-, post 2/. ELOWER MOTORS, Dual voltage 12/24 y., recom-mended for car cooling or heating, 5/.-, post 2/. TELEPHONES. For intercommunication between 2 or more positions, these "call and reply" wall sets are a complete unit with bell, mike, and receiver in neat wood case and only need a length of twin bell wire between them. Brand new, suitable for office or home, 25 per pair.

where between energy and the state of the st

Net 5 inch authority on the biowers. Ex-R.A.F. VACUUM PUMPS or Rotary vane blowers. Ex-R.A.F. Brand new. 7 cu. ft. per min., 10 lbs. per sq. inch at 1,200 r.p.m. 22/6. Post 2/-. R.F. UNITS TYPE 26. 50-655 M/c.A. Variable tuning, complete with valves. A fortunate purchase enables us to offer these units at the special low price of 35/-, rotation.

poet 2/6. EECEIVER R.1355. Specified for "Inexpensive Television." In original packing. With all valves, 38/6, carriage 7/6. AMPLIFIERS. A high-fidelity unit with separate Bass and Treble-controls, constant impedance attenuator for sotting volume level. In metai case with handles, 16 watt output, for 200/250 v. A.C. Mains operation. Intended for use with the Gaumont British Projector. Idealfor P.A. work, dances, etc. Less valves. 51/21/0. Or complete with all valves, £15/12/6. Carr.10/.

SI2101-. Of complete with all valves, F10110/-. SPEAKDS. P.A. Goodmans P.M. 121n. 15 ohms. SPEAKDS. P.A. Goodmans P.M. 121n. 15 ohms. Type T.s. A high-classspeaker at a low price. Ideal for GENTER El132A. 100/124 Mo/s. with 200/250 v. A.C. Power Pack and all valves, &&/15/s.- carr. 104-. ROTARY CONVERTERS. Input 24 volts D.C., output 200 volts A.C., 50 eveles. 100 watt 92/6 each. Also available with 12 voltinput, 102/6, carr. 5/-. MOVING GOL METER with 1 M/A movement, 241n. flush, rectifier type, scaled 0/100 volts A.C. Resistance 100 k. ohms. A very useful basic meter, 30/-. Ful lists available.



KEECO

TEL: GRA 6677

621 ROMFORD ROAD , LONDON . E.12

.

152

WOOLWICH POLYTECHNIC COLEGE OF ENGINEERING AND SCIENCE WITH TRACHERS RECOGNISED BY UNIVERSITY OF LONDON PRINCIPAL: J. 8. Tait, Ph.D., B.Se., A.R.T.O. M.LE.E., A.M.I.Mech.E. Students read for Internal Degrees and are affiliated to the University of London Union and Athletic Union. B.Se. ENGINEERING Civil, Mech-anical, Electrical, Telecommunications. B.Sc. Special CHEMISTRY B.Sc. Special MATHEMATICS B.Sc. Special PHYSICS B.Sc. GENERAL All the above are Three Year Courses. A WOOLWICH POLYTECHNIC

B.Sc. GENERAL All the above are Three Year Courses. A Preliminary One Year Course is available for those not possessing G.C.E. in suitable subjects and levels, making a Four Year Course for the Degree. FIRST MEDICAL EXAMINATION One Year Course

PROFESSIONAL COURSES Higher National Diplomas One Year Course in

Engineering Associateship of Royal Institute of

Associateship of Royal Institute of Chemistry Three Year Courses for students who have attained a suitable standard. Fees: £28 per Academic Year (No Fee if under 18 years of age) plus £2 Union Fee, Advice and Information on Scholarshipe, Deferment Entrance Standard, etc., available on request to Prinelpal, Woolwich Polytechnie, S.E.18. (Woolwich 2856)

TELEVISION ENGINEER

Important and progressive Group of Television and Radio Relay Companies invite applications from fully competent and experienced men for the position of Television Engineer. State age, qualifica-tions experience and salary required to :. CITY RELAY SERVICES, LTD., 24 NEW CHAPEL STREET, MILL HILL, BLACKBURN.

WORLEY TRANSFORMERS QUALITY P.P.O./P. TRANS, 20w., super Silcor lams Section low leakage windings, prim. ind. 75H. leakage ind. 075H. Sec. 3 and 15 ohms Prim. to Indiv. requirements. Barondei and term... wt. 5] bs. 5. ard. Divisit. 100 ard. 100 m.h. 1266 Det Her, Isolation Trans., 25% sec. boost volt. 2 v., 1066 : 6.3 v., 106. MAINS TRANS. 0-200/250 v. tapped prim. 3500-0-350 v. 30 m.h. 8 v. 2 a., 6.3 v. 4 a., etc., 1070 21/- 6.3 v. 14 a. Ht. Trans., 7/6. Quotations for specials and rewinds. Part P. & P. J-2. PAWSONS RD. W. CROYDON THO 1565. 2. PAWSONS RD. W. CROYDON, THO 1665

NORWOOD TECHNICAL COLLEGE

NORWOOD TECHNICAL COLLEGE Training in Rado, Radar, Television and Electronics. Day and Evening Classes in preparation for Grad.Brit. I.R.E. City and Guild's Examina-tions, P.M.G. Certificates, R.T.E. B. Radio and Television Servicing Cortificates. Also special courses in Radar, Television, Electronics (Instrumentation).

London Fees for Full-time day Classes: FREE if under 18 years. £23 per year if 18 years or over, Further particulars from Secretary, Norwood Technical College. West Norwood, London, S.E.27. (432).

THE NORTHERN POLYTECHNIC HOLLOWAY ROAD, LONDON, N.7 Principal: T. J. DRAKELEY, C.B.E., D.Sc., Ph.D., F.R.I.C., F.I.R.I. Department of Telecommunications Engineering FURTHER EDUCATION. The senior

courses are intended for students who desire to qualify for technical positions in radio, radar and television work. They are planned to include three years full-time study after to include three years' full-time study after which the student may remain for individual research. Full preparation is given for the Graduateship Examination of the Britl.R.E., and for the Full Technological Certificate of the City and Guilds of London Institute in Telecommunications Engineering. Evening classes covering the above, and radio and television servicing are also held. Prospectus free on application to the Secretary.

WIRELESS WORLD

SITUATIONS VACANT WINELESS WORLD Standard, for television and radio coll factory, 44-hour 5-day week, salary in accord-ance with experience. -Apply to Miss K. S. Cowan, Personnel Officer, Mitcham Works, Ltd., Winchelsea Rd., Harlesden, N.W.10. [Oloo WiREMAN for modern research laboratory, capable of working to verbal instruction and able to do original layouts; City and Guilds or National Certificate an advantage, at least 3 years' experience imperative. -(Ref. 71) Write in detail, quoting reference No. of position sought to: The Personnel Dept. (Technical Employment), De Haviliand Pro-pellers, Ltd., Hatfield, Herts. Izalf JUNIOR electrical engineer required for the electrical testing section of development laboratory of cable makers in the Manchester district; the work involves electrical measure-ments appropriate to the light current field; work on special problems in connection with Television Receivers. Some knowledge of theory is expected, and practical experience with re-relvers is desirable. Applicants should not he isable for National Service. Apply stating full particulars, to the Personnel Dept. [Betrical full marticulars, to the Personnel Dept. [Betrical sesting MALL manufacturers in audio and electronics and practical experience with re-relvers is desirable. Applicants should not be inable for National Service. Apply stating full particulars, to the Personnel Dept. [Betric & Malli manufacturers in audio and electronics and practical experience; duties may cover wide field, and further the hert experience with relevers is desirable. Applicants should not be inable for National Service. Apply stating full particulars, to the Personnel Dept. [Betric & Malli manufacturers in audio and electronics and practical experience; duties may cover wide field, and applicant fier trial period; correspine Malli manufacturers in undio and electronics and practical experience; duties may cover wide field, and applicant fier trial period; correspine Mandi unior enginee

and experience, the median end of the solution
nection with interviews will be paid.—Box d742. [2815] RAUGHTSMEN: vacancies will be available shortly in West London area for senior and intermediate draughtsmen with good experience in radio or telecommunications equipment: interesting work associated with tooling test gear. and quantity production of latest design airborne transmitter and receiver equipments: posts provide scope for initiative and extending experience in this field.—Reply in confidence. stating age, technical training experience and present salary. Box 4500 THE GENERAL ELECTRIC Co., Ltd., have vacancies at Stamore for Electronic and Electrical Engineers for work menority approximation of the previous experience in dard and/or with previous experience in dard and/or with previous experience in development work. The work is interesting and there are openings in each of the following redstring.

SERVO-MECHANISMS and magnetic ampli-

Aers. MICROWAVE circuits. 3. PULSE circuits. 4. GENERAL radar circuits and C.R.T. radar for presentation. 5. PREPARATION of G.W. equipment for

presentation. 5. PREPARATION of G.W. equipment for trials. APPLICATIONS should be made in writing. stating age. qualifications and experience. and should indicate the specific interest of the applicant. All positions are permanent in idea: working surroundings, and there are excellent welfare and social facilities. Please reply to the Personnel Manager (Ref. WW/MW.2). Brown's Lane Division. The G.E.C. Stanmore Laboratories. The Grove. Stanmore Common. Stanmore. Middlesex. ELECTRONIC engineer required by Birming-ham company handling wide range of industrial and laboratory instrument; applicants (are in 0) must have inst-class education and derive in 0 industrial processes; commencing sala. y £750-£1,000 according to age and ex-perience; pension scheme.—Box 5027. (2860)



RG/250. 10 valve chassis with contrast ex-pansion, variable selectivity, £35. RG/160. 7 valve chassis, bass and treble controls,

RG/160. 7 valve chassis, bass and treble controls, push-pull output, £20. RG/127. 6 valve all-wave chassis with push-pull output. £17/5/-. TU/100/6. All-wave tuning unit for use with amplifiers. 6.3 heaters. £13/10/-. TU/100/4. For 4 v. heater supply. £14. AC/DC models are available.

Full details gladly sent on request.

16 Mare Street, London, E.8. Amh 4400



Contractors to The Ministry of Supply Repairs by akilled craitsmen of all makes and types of Voltmaters, Anmeters, Miltranameters, Multrange Test meters. Electrical Thermometers, Recording Instruments, etc. Quick deliveries-for speedy estimate send dejective instruments by registered post to :---



MAINS TRANSFORMERS. Input 200/ 240 v. Output 350-0-350, or 250-0-250 v. both with 6.3 v. and 5 v. tappings. 21/-, postage 9d. OUTPUT TRANSFORMERS. Standard

Size. 6/9 each, post 6d. HALFWAVEMETAL RECTIFIERS. 125 v. 60 mA. 4/3, 100-mA. 4/9; 125 mA. 5/6; 230 v. 250 mA. 16/6, post 6d. METAL RECTIFIERS. 12 v. 3 A, 10/-,

METAL RECTIFIERS. 12 v. 3 A, 10/-, 12 v. 2 a, 9/-, post 9d. .0005 TW/N GANG TUNING CON-DENSERS, 6/6 each. Ditto midgets, 7/6 each, post 9d. SPEAKERS. All brand new, permanent magnet. 3µin., 16/6, Sin., 16/9; 6µin., 15/9; 8in., 21/6. Postage 1/-. SPEAKER CABINETS. Polished wood, matil grillur 6in. 16/64 Bin 19/6 port 1/4

metal grilles, 6in., 16/6; 8in., 19/6, post 1/-. AMPLIFIERS. 3 valve A.C. Mains complete, brand new, £4/10/-, post 2/-. SHORTWAVE RECEIVERS.

SHORTWAVE RECEIVERS. R.103A for use on 100/110 and 230/50 volt A.C. and 12 volt battery. Comprising 6 valves and built-in vibrator pack covering 1.7 Mc/s to 7.5 Mc/s. Brand new in perfect working order, £9/15/-each. each. EARPHONES 60 ohm C.L.R., 5/- per pair.

4,000 ohm, 17/6 per pair, post 9d. Government Surplus. 2 VALVE AMPLI-FIERS. Type A.1134A, with valves. Not guaranteed. Working. IS/- each, post 2/-SOLDER. IIb. reels 40/60, S/- reel, post

50 MFD. MOTOR CAPACITORS. Brand new, 10/6 each, post 9d. BRAND NEW AND BOXED METERS.

BRAND NEW AND BOXED METERS. 0/2 Hot wire ammeters, 2in-square, 5/6 each. 0/6 Thermo-Couple ammeters, 21:n. 10/-. 0/30 mA M.C. D.C. 21:n. flush, 9/- each. 0/15 volt A.C. M.I. 21:n. flush, 12/6 each. 0/200 mA D.C.M.C. 21:n. flush, 9/- each. 0/300 mA D.C.M.C. 21:n. flush, 9/- each. 0/1 mA M.C.D.C.21:n. Square flush, 12/6 each. 0/1 Thermo-Coupled Ammeters 21:n. pro-ierting R = 6/e each.

amp, 7/6 each, post 9d. APE DECK CABINETS.

Finished in TAPE grey, blue, size 1441n. x 16in. x 11in. deep, £3/7/6 each, carr. 2/-. Please state alternative colour

SMALL WOODEN CARRYING CASES. 12in. x Bin. x 5in. deep, fitted leather handle and lid clasp, 7/6 each, post 1/6. ELECTRIC BOWL FIRES. Brand new. Cast Base, highly polished aluminium bowl. 750 or 600 watt at 200/50 volts A.C. and D.C.,

33/- each, carr. paid. Obtainable from :-

J. & S. KAYE SUPPLIES (Dept W.W.)

(Late Universal Engineering Co.)

11, St. Anns Road, Harrow, Middx. Tel: HAR, 1432

Shop hours : 9 to 6 Mon. to Sat. Half-day Wed

WEBB'S SERVICE DEPARTMENT for complete renovation of complex

communications receivers of any make

Test report issued showing sensitivity, selectivity, signal/noise

equal to, or better than, makers'

WEBB'S RADIO,

14, SOHO STREET, LONDON, W.1

original figures.

WIRELESS WORLD

 BURLESS WORLD

 STUTION YOAR

 By Structure of a serial systema in the series of the seri

tion and technical experience and outside broadcast equipment. WRITE to the Crown Agents, 4, Millbank, Lon-don, S.W.I. State age, name in block letters, full qualifications and experience and quote reference number shown against the post for which application is made. [289] ELECTRONIC engineer to work within our trials division at Edinburgh; the nature of the work involves conducting trials and evalu-sting the performance of fire control; naviza-tional and landing systems under development: applicants should possess a physics degree or considerable recent practical experience in this field: good opportunity in expanding depart-ment; staff pension scheme. Apply, quoting Ref. EF/TID and giving full details of quali-fications and experience, to the Personnel Officer, Ferrant, Ltd., Ferry Rd., Edinburgh, 5 CIMIESTEV OF SUPPLY requires Assistant

ment Exchange quoting offer to: [2896 [1590. [2896] ELECTRONIC engineers to work within our trais division at Edinburgh; the nature of the work involves conducting trials and evaluat-ing the performance of fire control; navigational and landing systems under development; appli-cants should possess a physics degree or con-siderable recent practical experience in this field; good opportunity in expanding depart-ment, staff pensiou scheme.—Apply, quoting Ref. EE/TID and giving full details of quali-fications and experience, to the Personnel Officer, Ferranti, Ltd., Ferry Rd., Edinburgh, 5.

Drucer, Ferranu, Ltd., Ferry Kd., Edinburgh, S. DRAUGHTSMEN are required for permanent posts in the field of Radar Engineering. Excellent opportunities for advancement, Salaries beyond A.E.S.D. rates to suitable applicants. Staff pension scheme and canteen facilities. 5-day week. British Nationality essential. Posts to be filed in the following grades: Senior Section Leader. Checker Draughtsman and Senior Design Draughtsman, intermed ate Draughtsman. Circuit Draughts-man, Installation Draughtsman. — Apply, quoting Ref. RLA/21, Chief Draughtsman, Decca Radar, Ltd., Research Laboratory. 2. Tolworth Rise, Surbiton. furrey. [2656]



SITUATIONS VACANT ELECTRONIC INSTRUMENTS, Ltd. of Rich-mond, Surrey, has vacancy for Chief In-spector. Applicantis must have sound, practical experience in testing mechanical and electronic apparatus, together with administrative ability. A key post in expanding firm, Applica-tion in first instance by letter giving full details of experience and salary. [2667] ABORATORY engineer required for design or object and development of H.F. testing equipment for coaxia and telephone cables; engineering or physics degree essential and approximately two years' experience desirable; 25-26 years of age; £460-£600 according to qualifications and experience, to Personnel Manager, Standard Telephones & Cables, Ltd., North Wolwich, E.16. [259] THE BRITISH TABULATING MACHINE Co. T. Ltd., require an electronic draughtsman for their Research Labtoratory at Suprement

experience, to Personnel Manager, Standard Telephones & Cables, Ltd., North Wolwich, E.G. 2025 THE BRITISH TABULATING MACHINE Co., The Ltd., require an electronic draughtsman for their Research Laboratory at Stevenage. Here their Research Laboratory at Stevenage. 2017 ECCA RADAR, Ltd., Invite applications Defore negineers and technicians with ex-perience of installation or maintenance of radar, for field duties with the Companys Heavy Installations Division on the installation of high-power radar equipments; the appoint-ments will be permanent and pensionable: applications giving details of experience and stating salary required should be addressed to the Personnel Officer, Decca Radar, Ltd., Shan-non Corner, New Malden, Surrey, quoting refer-ence HD.3 [2736 Brintheir Laboratories at Shepherdis Bush for Engineers or Physicists to work on sound re-cording and reproducing equipment, including stereophonic systems; applicatis should have good qualifications, prefirably an honours degree, or give evidence of exceptional ability and inderst in electronics and sound re-sonic flowedge of radio and radar and ex-perisonnel Manager, British Acoustic Films. Ltd. Woodger Rd. W.Z. [2007] Roby Meteorological Office. Qualifications:-Basic knowledge of radio and radar and ex-perisone in maintenance/operation of radar equipment including oscilloscopes, Successful applicants serve in United Kingdom and over-seas. Commencing London salary £445 st age 25 or over rising annually to £540 sub (Dept. S.E.17

chal salary 220 to 250 by the period prospects. Apply to Borough Employment Exchange (Dept. W.W.4). 236, Walworth Rd., Lordon S.E.17. [297] TrANSISTORS.—The British Tabulating Machine Co., Ltd., Icknield Way, Letche worth, Herts, has a vacancy for a grauno-ment work on the use of the prospects. and switching in digital computing, radar, the ransistor circuit techniques or of pulse circuits as used in digital computing, radar, experience and training, should be sent to Personnel Officer. [288] Et the development of small motors and other the design of small electromagnetic compo-ing in collaboration with or wald computing, the design of small electromagnetic devices the commencing salary will be of the order of the commencing salary will be of the order of the commencing salary will be of the order of the commencing salary will be of the order of the commencing salary will be of the order of the commencing salary will be of the order of the commencing salary will be of the order of the sales of excited studies in the field of oromunications and severience.—Application for these first of excites the opportunity of the ad-production plais and the main object of the commencing salary will be of the order of excites and theoretical studies in the field of formunications and general electronics; guali-first or second-class honours degree with ossibilities of establishment through the first or second-class through the field of formunications and general electronics; gual-first or second-class through the first or promotion to higher-grade posts on staff of Scientific Advise to Air Ministry. Applica-tion forms, quoting Al09/54A, from M.L.N.S. Technica and Scientific Arguiter to air ministry. Applica-tion forms, quoting Al09/54A, from M.L.N.S. Technica and Scientific

CAPACITOR Engineeri AACANT

STUATIONS VACANT STUATIONS VACANT C operation of the production stage a limited range of special duty capacitors; the secellart scope for an enthusiastic and indus-trious man, aged 25 to 30 years, salary in accor-dance with qualifications and experience; our staff are aware of this vacancy, and applications; the secellart scope for an enthusiastic and indus-trious man, aged 25 to 30 years, salary in accor-dance with qualifications and experience; our staff are aware of this vacancy, and applications; the company's business, which covers a secellart scope for ageners, second and the required; vacancies arise from an expan-sion of the company's business, which covers ad some industrial experience; for the junior vacancies the minimum technical qualification required is the City & Guilds Certificate in triecommunications; applications will be compared in strictest confidence; near city centre and all amenities; Saturday interview if re-compared in strictest confidence; near city centre and all amenities; Saturday interview if re-tred all amenities; Saturday interview if re-tred to build up and conford an entilely new roup working on advanced valve applications; his is an opportunity for a near of initiative sound working the engaged on initiative techniques in the electronic field, particularly which application to radio and television and sound working the abound of the organical experi-mental work and an ability fo guide the work sound working the abound regultient field, particularly techniques in the detert offer, A.A.C. (2020) DVNG development engineers are used the required to assist in the development of pre-rison detertonic and ability of guide the work required to assist in the development of pre-rison detertonic and ability for guide the work required to assist in the development of pre-rison detertonic and ability of guide the work required to assist in the development of pre-required to assist in the development of pre-rison detertonic and abili

Chief Engineer, Messrs. Furzehill Laboratories, Ltd., Shenley Rd., Boreham Wood, Herts. 0030
 MURALTY-Royal Naval Scientific Ser-interprimental Officers and Assist-ant Experimental Officers equired in Experi-mental Establishments in London, Portsmouth, Weymouth areas, Gloucestershire and Scotland the majority of posts, are failed the engineer interprimental efficiency of the engineer of the interprimental engineer of the following vacancies in their expanding development laboratories and design department: (a) development engineers, with experi-ence in one or several of the following fields of engineer for work on centimeers, which experi-ence in one or several of the following fields of engineer for work on centimeertic waveguide and aerial systems; (c) engineer to take charge of model and assembly shop laid out for small qualifications, to The Secretary, Messre. Barr & Stroud, Ltd., Annelsaland Glasgow, W. 3274

& Stroud, Ltd., Anniesland, Glasgow, W. . [2758] THE WAR OFFICE requires for No. 35 Base Workshop R.E.M.E., Old Dalby, Leicester-shire: one Mechanical Engineering Officer (Main Grade) to control Workshop repairing radar and associated equipment; knowledge and experi-ence of modern electronic and allied engineering progress and process methods and technique of management essential, also ability to organize large repair programmes and production; in-clusive salary range £1,000-£1,320 (London). Applicants must be British of British parentage and Corporate Members of the Institution of Electrical Engineers or have passed or be exempt from Sections A and B of their membership examination; starting salary fixed according to age, qualingtion and and subject to satisfac-tory service; post femporary but long term pos-sibilities.-Application forms from M.L.N.S.. Technical and Scientific Register (K), 26, King St., London, S.W.1, quoting D258/54A. [2894]

RADIO & TELEVISION COMPONENTS WE OPERATE A PROMPT & EFFICIENT MAIL ORDER SERVICE. "VIEW MASTER" &"TELE-KING" specialists Easy terms available, JAMES H. MARTIN & CO.,

FINSTHWAITE, NEWBY BRIDGE. ULVERSTON, LANCS,

EITUATIONS VACANT B.E.O. requires Senior Lecturer in General Section of Engineering Training Depart-ment, Evesham. Candidates should possess de-gree or equivalent in Electrical engineering or physics. Previous experience in teaching and industry an advantage. Dutles concern presen-tation of fundamental principles of sound and vision broadcasting to technical and non-tech-nical staff and successful candidate will super-vise four lecturers and generally develop work of Section. Starting salary 2990 (may be higher for exceptional qualifications) rising by 5 annual increments to £1.320 max. Apply E.O. B.E.C. London, W.I., quoting ref. E.914, within 7 days. [2864 SITUATIONS WANTED

E.914, within 7 days, 2864 SITUATIONS WANTED Relating mirs, energetic experienced execu-tive, technical.—Box 4688. 2803 R ADIO and television service engineer, 35, qualified, experienced, own car, desires change; N.W. London.—Box 5091. [2878 TECHNICAL TRAINING CITY & GUILDS (Electrical, etc.) on "No For full details of modern courses in all panches of Electrical Technology, send for our 144-page handbook—free and post free, B.I.E.T. (Dept. 388A), 29, Wright's Lane, London, W.8. [UITION

COVENTRY TECHNICAL COLLEGE.

COVENTRY TECHNICAL COLLEGE. SESSION 1954-55. ELECTRONIC Engineering. APPLICATIONS invited for entry to 3-year full-time course commencing September, 1954, from those requiring comprehensive training to advanced level in Electronic Engineering, qualifying for technical posts in radio, tele-communications, television and industrial electronics. Sylabus will cover requirements of C. & G., Brit.I.R.E., and I.E.E. examinations. Entry age 16 or over. Application forms and further information from Principal, Technical College, The Buits, Coventry. I2866 NoTHING succeeds like success! What we have done a thousand times we can do again for you-see the B.N.R.S. advt., page 138. [0172 WirelESS operating; attendance and postal courses.—Stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7. DIM

SEE the world as a radio officer, short train-ing, low fees, scholarships, boarding/day students; stamp for prospectus.-Wireless Col-lege, Colwyn Bay. [0018

SEE the world as a radio officer, short train-ling, low fees, scholarships, boarding/day students; stamp for prospectus.-Wireless Col-lege, Coluster and Back (Eng.); prospectus fee-trachnical College, Hull. Learning College, Hull. Coll. Teleonomunications, Radar Main-tenance Cert, and B.Sc. (Eng.); prospectus fee -Technical College, Hull. Learning College, Hull. Learning College, Hull. Learning College, Hull. Coll. Teleonomunications, Radar Main-tenance Cert, and B.Sc. (Eng.); prospectus fee M. Institutes, Dept. WW47, 43, Grove Park Rd., London, W.4. T/V Guilds, R.T.E.B. Cert, etc., on "no pass-noise" terms. Over 95% successes, De-tainshook-free.-B.L.E.T. (Dept. 367, 101 Garding, etc., on "no-pass-noise", for M. M.I.Mech.E., A.M.Brits.I.R.E., City and Guilds, etc., on "no-pass-noise", for Hulds, etc., on "no-pass-noise", for Hulds, etc., on "no-pass-noise" terms: over 95% successes; for details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook-free-B.L.E.T. (Dept. 387B). 29, Wrisht's Lane-London, W.8. Colle W to youths 16 upwards after qualification iucrative positions as Radio Officers.-Apply British School of Telegraphy, 179, Clapham Rd, 8.W.9 (Est. 1906). Recognised by Ministry of Education. Moderate fees. Modern equipment. Also postal courses in theory of Wireless Tele-sraphy for P.M.G. Certs and Amateur Trans-mitting Licence. Joinst collage in every passe of radio and television engineering, specialing in the practical Radio Engineers have available home study courses in every passe of radio and television engineering. Specialing in the practical Radio for gapter-ties in the wetail trade; enrolments limited, fees may be orbained Jostus Conse In every phases of radio and television and all pranches of electronics; courses for the hobby enthusiast or for those alming at the A.M.Brit.I.R.E., City and Guilds Te

VV offers.--113, Manor Fain, Les 12822 S.E.13. BOCKLETS "How to Use Ex-Govt. Lenses and Prisms," Nos. 1 and 2, price 2/6 each; ex-Govt. optical lists free for s.a.e.--H. English, Rayleigh Rd., flutton, Brentwood, Esser. [018] I.P.R.E. technical publications, 5,500 Align-ment Peaks for Superheterodynes, 5/9, post free; data for constructing TV aerial Strength meter, 7/6; sample copy "The Practical Radio Engineer, "quarterly publication of the Institute 2/-; membership and examination data, 1/-.-Sec., I.P.R.E., 20, Fairfield Rd., London, N.B. [0089]

WIRELESS WORLD





	Use this Form for your Sales and Wants To "Wireless World" Classified Advertisements Dept., Dorset House, Stamford Street, London, S.E.I. PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW • RATE: 7/- for TWO LINES, 3/6 every Additional Line. Average six words per line. • Cheques, etc., payable to lliffe & Sons Ltd., crossed & Co. • PRESS DAY, MAY 31st FOR JULY
	Please write in BLOCK LETTERS with ball pen or pencil.
NAME	ADDRESS



WIRELESS WORLD

156

Printed in Great Britain for the Pablishers, Liffs & SONS LTD., Dorset House, Stamford St., London, S.E. L. & CONNWALL PRESS LTD., Paris Garden, London, S.E. L. Wirrless World can be blackained abroad from the following: AUSTALLIA AND NEW ZRALAND; Gordon & Gordon & Gordon, Ltd., LKDIA: A. H. Wheeler & Co. CANADA: The VMm. Duwson Subscription service Ltd.; Gordon & Gorde, Ltd. Soura Arrita: New Agency, Ltd., William Dawson & Sons (S.A.), Ltd., UNITED STATES; The International News Roy.

JUNE, 1954

FOCUS ON LEADERSHIP

MINIATURE LEAD-THROUGH & STAND-OFF

ACTUAL SIZE

THESE new additions to our range of Hi-k Ceramic Condensers have been designed for Television Receivers incorporating Band 3 and Band 4 tuners. Their outstanding features are : extremely small series inductance, efficient decoupling, and small physical size. The Stand-off Types are particularly suitable for cathode and screen decoupling.

Construction

The tubular bodies are a specially selected material of the barium-titanate group of ceramics with a dielectric constant of 3,000. The four constructions at present available provide two for lead-through purposes and two for stand-off purposes. The former have an 18 gauge tinned copper wire running through the body and protruding each end, whilst the latter have a looped termination at one end.

Method of installation

Lead-through Type CC160S is intended for soldering direct into a tuner plate, the hole in the plate being 'burst' rather than punched. A solder ring is employed for soldering the condenser into the plate, thus forming a fillet which gives a sound electrical and mechanical joint.

Lead-through Type CC161S has a flange around the centre of the body so that it may be mounted on a tuner plate having a punched hole of 0.166" diameter (Drill No. 19).

Stand-off Type CC162S has a mounting flange at the base of the body enabling the condenser to be soldered to any part of a flat chassis.

Stand-off Type CC163S has a mounting flange approximately half way up the body, and requires a punched hole in the chassis of 0.166" diameter (Drill No. 19).

In both of these Stand-off Condensers the end of the 'hot' electrode furthest from the connecting loop is spaced approximately 2.5 mm. away from the ' earthy' outside end.

Capacity: 1,000 pF. Working Voltage: 350v. D.C. Insulation Resistance: Greater than 5,000 megohms at 500v. D.C. Capacity Tolerance: -20% to +80%.



Wireless World **NEW edition of Modern Solder:**

MATONERINS

now available FREE

CONSTITUTION OF ALLOYS OF ERSIN MULTICORE SOLDER

PROPERTIES OF SOLDERS

TELEVISION AND RADIO TRANSMITTERS AND RECEIVER

Pages from "MODERN SOLDERS".

SOLDERS

Ersin Multicore is the only solder in the world supplied ' containing 3 or 5 cores of Ersin Flux, a high-grade rosin which has been subjected to a complex chemical process to increase its fluxing action without impairing in any way the well-known noncorrosive properties of the original rosin.

The core construction ensures flux continuity which, with the correct soldering technique, avoids dry or H.R. joints. There are no wasted lengths of solder without flux.

Unless otherwise specified, Ersin Multicore Solder is supplied as standard to manufacturers in 6 alloys, 9 gauges and 2 flux percentages on nominal 7 lb. reels. Approved by A.I.D., G.P.O., A.R.B., D.T.D.599, R.C.S.1,000 and all U.S.A. Federal specifications. Widely used by U.S.A. manufacturers where it is specially imported from England.

MULTICORE

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS

A completely revised edition "Modern Solders" has been prepar to meet the demands of Laborate Engineers and Technicians. Inform tion on melting points, standard gaug constitution of alloys and use of solo has been brought up to date.

IUNE, 1

The latest Multicore products-5 Co Solder, Solder Rings, Tape Sold Automatic Soldering Head and oth -are described with their specific us "Modern Solders" is fully illustrated a contains many useful graphs and tabl

Available only to manufacturers a laboratories using solder. Please app on your official paper for a copy of t useful reference book. Other interest users of solder are invited to write complimentary copies of "Hints Soldering" and "Multicore Sold Technical Summary".

For Service Engineers and Electronic Enthusiasts SIZE I CARTONS 5/- RETAIL

Cat. Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. Length per carton
C16014	60/40	14	21 feet
C16018	60/40	18	56 ,,
C14013	40/60	13	19 ,,
C14016	40/60	16	38 ,

7 lb. reel and size 1 carton illustrated. Bulk prices for 7 lb, reels on request

LTD.

(BOXMOOR 3636)

ERSIN Multico's SOLDER